


25<sup>TH</sup> EDITION v 1948

# The radio amateur's handbook

THE STANDARD MANUAL OF AMATEUR  
RADIO COMMUNICATION



\$2.00

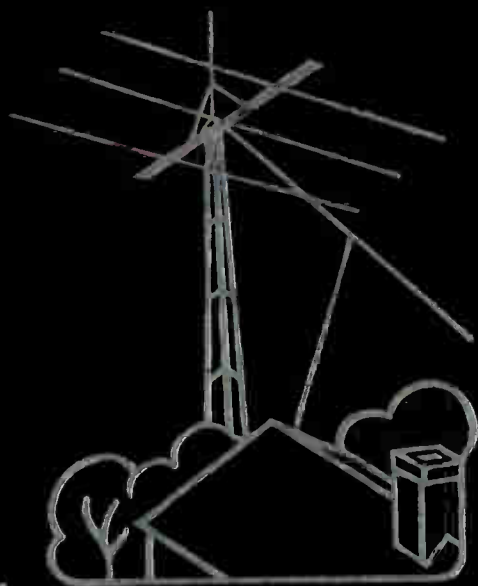

---

PUBLISHED BY THE AMERICAN RADIO RELAY LEAGUE

---





























---

**THE  
RADIO  
AMATEUR'S  
HANDBOOK**

---
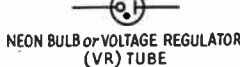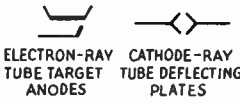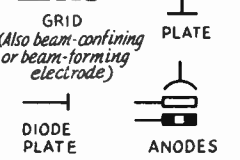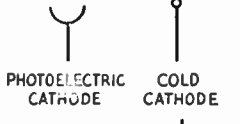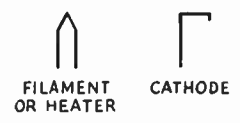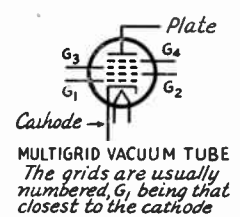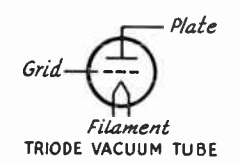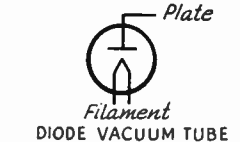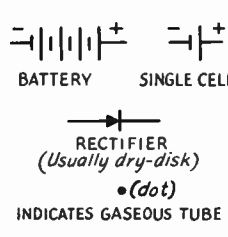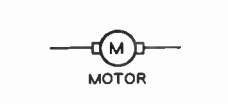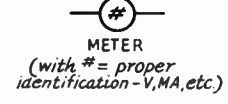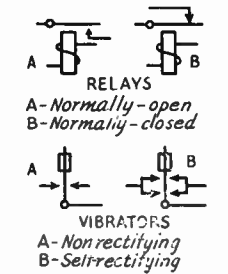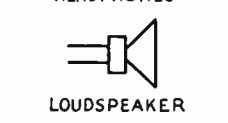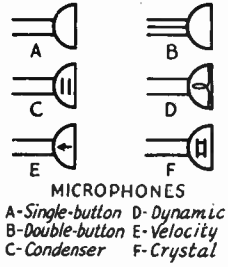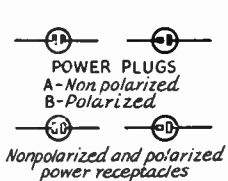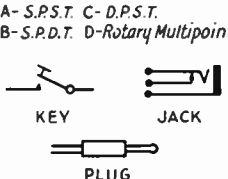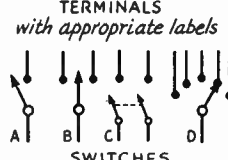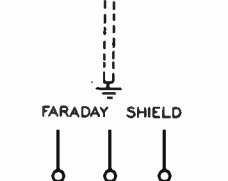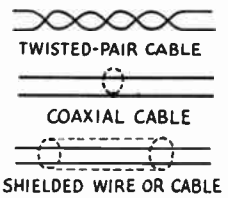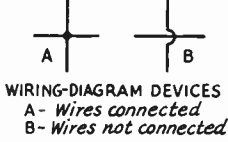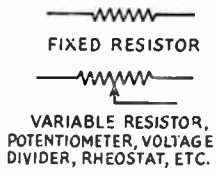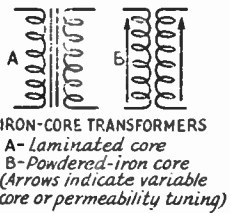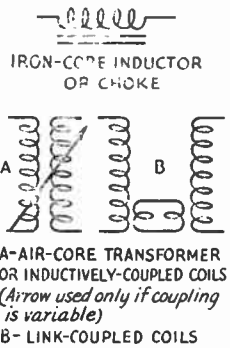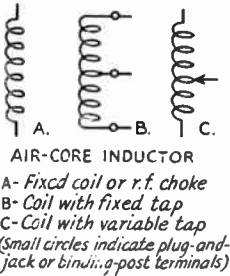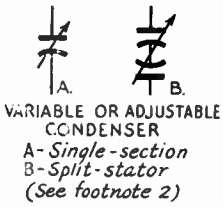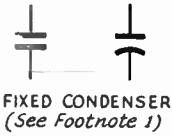
# SCHEMATIC SYMBOLS USED IN CIRCUIT DIAGRAMS



<sup>1</sup> Where it is necessary or desirable to identify the electrodes, the curved element represents the outside electrode (marked "outside foil," "ground," etc.) in fixed paper- and ceramic-dielectric condensers, and the negative electrode in electrolytic condensers.

<sup>2</sup> In the modern symbol, the curved line indicates the moving element (rotor plates) in variable and adjustable air- or mica-dielectric condensers.

In the case of switches, jacks, relays, etc., only the basic combinations are shown. Any combination of these symbols may be assembled as required, following the elementary forms shown.

TWENTY-FIFTH EDITION

1948

# THE RADIO AMATEUR'S HANDBOOK

*by the*

HEADQUARTERS STAFF OF THE  
AMERICAN RADIO RELAY LEAGUE



*Published by*

THE AMERICAN RADIO RELAY LEAGUE, INC.  
West Hartford, Connecticut, U. S. A.

**COPYRIGHT 1948 BY**

**THE AMERICAN RADIO RELAY LEAGUE, INC.**

*Copyright secured under the Pan-American Convention*

**This work is Publication No. 6 of The Radio Amateur's Library, published by the League. All rights reserved. No part of this work may be reproduced in any form except by written permission of the publisher. All rights of translation are reserved. Printed in U. S. A.**

*Twenty-Fifth Edition*

**December, 1947, 100,000 copies**

**(Of the previous twenty-four editions, 1,748,250 copies were published.)**

**THE RUMFORD PRESS  
CONCORD, NEW HAMPSHIRE, U. S. A.**

# Foreword

In twenty-two years of continuous publication *The Radio Amateur's Handbook* has become as much of an institution as amateur radio itself. Produced by the amateur's own organization, the American Radio Relay League, and written with the needs of the practical amateur constantly in mind, it has earned universal acceptance not only by amateurs but by all segments of the technical radio world, from students to engineers, servicemen to operators. This wide dependence on the *Handbook* is founded on its practical utility, its treatment of radio communication problems in terms of how-to-do-it rather than by abstract discussion and abstruse formulas.

But there is another factor as well: dealing with a fast-moving and progressive science, sweeping and virtually continuous modification has been a feature of the *Handbook* — always with the objective of presenting the soundest and best aspects of current practice rather than the merely new and novel. Its annual rewriting is a major task of the headquarters group of the League, participated in by skilled and experienced amateurs well acquainted with the practical problems in the art.

In contrast to most publications of a comparable nature, the *Handbook* is printed in the format of the League's monthly magazine, *QST*. This, together with extensive and usefully-appropriate catalog advertising by manufacturers producing equipment for the radio amateur, makes it possible to distribute for a very modest charge a work which in volume of subject matter and profusion of illustration surpasses most available radio texts selling for several times its price.

This twenty-fifth edition of the *Handbook* is featured by the complete rewriting of most of the material. The textbook style that made the book so useful for training purposes during the war years has been replaced by a simpler and more understandable discussion of those basic facts that an amateur should know to get the most out of designing and using his apparatus. Owners of previous editions will recognize immediately that the over-all plan of the book has been changed — achieving, we believe, the object of segregating the material so that it can be most conveniently used. A great deal of new equipment has been constructed especially for this edition. As always, the object has been to show the best of current technique through equipment designs proved by thorough testing. As the art grows, the problem of presenting a representative selection of gear grows with it — a state of affairs that is reflected in an increase of well over a hundred pages in this edition. New chapters on ultrahigh frequencies, station assembly, and the elimination of interference to broadcasting have been added to round out the treatment of all phases of amateur radio. The material on operating has likewise been greatly expanded. Altogether, this revision is the most comprehensive of recent years.

The *Handbook* has long been considered an indispensable part of the amateur's equipment. We earnestly hope that the present edition will succeed in bringing as much assistance and inspiration to amateurs and would-be amateurs as have its predecessors.

KENNETH B. WARNER  
*Managing Secretary, A.R.R.L.*

WEST HARTFORD, CONN.  
December, 1947





# Table of Contents

---

Frontispiece . . . . .	2
The Amateur's Code . . . . .	8
Chapter I . . . . . Amateur Radio . . . . .	9
Chapter II . . . . . Electrical Laws and Circuits . . . . .	17
Chapter III . . . . . Vacuum-Tube Principles . . . . .	59
Chapter IV . . . . . High-Frequency Communication . . . . .	78
Chapter V . . . . . High-Frequency Receivers . . . . .	85
Chapter VI . . . . . High-Frequency Transmitters . . . . .	140
Chapter VII . . . . . Power Supplies . . . . .	232
Chapter VIII . . . . . Keying and Break-In . . . . .	262
Chapter IX . . . . . Radiotelephony . . . . .	273
Chapter X . . . . . Antennas and Transmission Lines . . . . .	327
Chapter XI . . . . . About V.H.F. . . . .	389
Chapter XII . . . . . V.H.F. Receivers . . . . .	394
Chapter XIII . . . . . V.H.F. Transmitters . . . . .	418
Chapter XIV . . . . . V.H.F. Antennas . . . . .	444
Chapter XV . . . . . U.H.F. and Microwaves . . . . .	454
Chapter XVI . . . . . Measuring Equipment . . . . .	471
Chapter XVII . . . . . Assembling a Station . . . . .	495
Chapter XVIII . . . . . The Amateur's Workshop . . . . .	502
Chapter XIX . . . . . Eliminating Broadcast Interference . . . . .	509
Chapter XX . . . . . Operating a Station . . . . .	516
Chapter XXI . . . . . Message Handling . . . . .	523
Chapter XXII . . . . . Emergency Operation . . . . .	531
Chapter XXIII . . . . . League Operating Organization . . . . .	541
Chapter XXIV . . . . . Miscellaneous Data . . . . .	548
Chapter XXV . . . . . Vacuum-Tube Data . . . . .	562
Index . . . . .	609

---

# THE AMATEUR'S — CODE —

---

**ONE** *The Amateur is Gentlemanly . . .* He never knowingly uses the air for his own amusement in such a way as to lessen the pleasure of others. He abides by the pledges given by the ARRL in his behalf to the public and the Government.

**TWO** *The Amateur is Loyal . . .* He owes his amateur radio to the American Radio Relay League, and he offers it his unswerving loyalty.

**THREE** *The Amateur is Progressive . . .* He keeps his station abreast of science. It is built well and efficiently. His operating practice is clean and regular.

**FOUR** *The Amateur is Friendly . . .* Slow and patient sending when requested, friendly advice and counsel to the beginner, kindly assistance and coöperation for the broadcast listener; these are marks of the amateur spirit.

**FIVE** *The Amateur is Balanced . . .* Radio is his hobby. He never allows it to interfere with any of the duties he owes to his home, his job, his school, or his community.

**SIX** *The Amateur is Patriotic . . .* His knowledge and his station are always ready for the service of his country and his community.

# Amateur Radio

Amateur radio is a scientific hobby, a means of gaining personal skill in the fascinating art of electronics and an opportunity to communicate with fellow citizens by private short-wave radio. Scattered over the globe are more than 100,000 amateur radio operators who perform a service defined in international law as one of "self training, intercommunication and technical investigations carried on by . . . duly authorized persons interested in radio technique solely with a personal aim and without pecuniary interest."

From a humble beginning at the turn of the century, amateur radio has grown to become an established institution. Today the American followers of amateur radio number 80,000, a group of trained communicators from whose ranks will come the professional communications specialists and executives of tomorrow — just as many of today's radio leaders were first attracted to radio by their early interest in amateur radio communication. A powerful and prosperous organization now provides a bond between amateurs and protects their interests; an internationally-respected magazine is published solely for their benefit. The Army and Navy seek the cooperation of the amateur in developing communications reserves. Amateur radio supports a manufacturing industry which, by the very demands of amateurs for the latest and best equipment, is always up-to-date in its designs and production techniques — in itself a national asset. Amateurs have won the gratitude of the nation for their heroic performances in times of natural disaster. Through their organization, amateurs have cooperative working agreements with such agencies as the United Nations and the Red Cross. Amateur radio is, indeed, a magnificently useful institution.

Although as old as the art of radio itself, amateur radio did not always enjoy such prestige. Its first enthusiasts were private citizens of an experimental turn of mind whose imaginations went wild when Marconi first proved that messages actually could be sent by wireless. They set about learning enough about the new scientific marvel to build home-made stations. By 1912 there were numerous Government and commercial stations, and hundreds of amateurs; regulation was needed, so laws, licenses and wavelength specifications for the various services appeared. There was then no amateur organization nor spokesman.

The official viewpoint toward amateurs was something like this:

"Amateurs? . . . Oh, yes. . . . Well, stick 'em on 200 meters and below; they'll never get out of their backyards with that."

But as the years rolled on, amateurs found out how, and DX (distance) jumped from local to 500-mile and even occasional 1,000-mile two-way contacts. Because all long-distance messages had to be relayed, relaying developed into a fine art — an ability that was to prove invaluable when the Government suddenly called hundreds of skilled amateurs into war service in 1917. Meanwhile U. S. amateurs began to wonder if there were amateurs in other countries across the seas and if, some day, we might not span the Atlantic on 200 meters.

Most important of all, this period witnessed the birth of the American Radio Relay League, the amateur radio organization whose name was to be virtually synonymous with subsequent amateur progress and short-wave development. Conceived and formed by the famous inventor, the late Hiram Percy Maxim, ARRL was formally launched in early 1914. It had just begun to exert its full force in amateur activities when the United States declared war in 1917, and by that act sounded the knell for amateur radio for the next two and a half years. There were then over 6000 amateurs. Over 4000 of them served in the armed forces during that war.

Today, few amateurs realize that World



**HIRAM PERCY MAXIM**  
President ARRL, 1914-1936

War I not only marked the close of the first phase of amateur development but came very near marking its end for all time. The fate of amateur radio was in the balance in the days immediately following the signing of the Armistice. The Government, having had a taste of supreme authority over communications in wartime, was more than half inclined to keep it. The war had not been ended a month before Congress was considering legislation that would have made it impossible for the amateur radio of old ever to be resumed. ARRL's President Maxim rushed to Washington, pleaded, argued, and the bill was defeated. But there was still no amateur radio; the war ban continued. Repeated representations to Washington met only with silence. The League's offices had been closed for a year and a half, its records stored away. Most of the former amateurs had gone into service; many of them would never come back. Would those returning be interested in such things as amateur radio? Mr. Maxim, determined to find out, called a meeting of the old Board of Directors. The situation was discouraging: amateur radio still banned by law, former members scattered, no organization, no membership, no funds. But those few determined men financed the publication of a notice to all the former amateurs that could be located, hired Kenneth B. Warner as the League's first paid secretary, floated a bond issue among old League members to obtain money for immediate running expenses, bought the magazine *QST* to be the League's official organ, started activities, and dunned officialdom until the wartime ban was lifted and amateur radio resumed again, on October 1, 1919. There was a headlong rush by amateurs to get back on the air. Gangway for King Spark! Manufacturers were hard put to supply radio apparatus fast enough. Each night saw additional dozens of stations crashing out over the air. Interference? It was bedlam!

But it was an era of progress. Wartime needs had stimulated technical development. Vacuum tubes were being used both for receiving and transmitting. Amateurs immediately adapted the new gear to 200-meter work. Ranges promptly increased and it became possible to bridge the continent with but one intermediate relay.

### ● TRANSATLANTICS

As DX became 1000, then 1500 and then 2000 miles, amateurs began to dream of trans-Atlantic work. Could they get across? In December, 1921, ARRL sent abroad an expert amateur, Paul F. Godley, 2ZE, with the best receiving equipment available. Tests were run, and *thirty* American stations were heard in Europe. In 1922 another trans-Atlantic test was carried out and 315 American calls were logged by European amateurs and one French and two British stations were heard on this side.

Everything now was centered on one objective: two-way amateur communication across the Atlantic! It must be possible — but somehow it couldn't quite be done. More power? Many already were using the legal maximum. Better receivers? They had superheterodynes. Another wavelength? What about those undisturbed wavelengths *below* 200 meters? The engineering world thought they were worthless — but they had said that about 200 meters. So, in 1922, tests between Hartford and Boston were made on 130 meters with encouraging results. Early in 1923, ARRL-sponsored tests on wavelengths down to 90 meters were successful. Reports indicated that *as the wavelength dropped the results were better*. A growing excitement began to spread through amateur ranks.

Finally, in November, 1923, after some months of careful preparation, two-way amateur trans-Atlantic communication was accomplished, when Schnell, 1MO, and Reinartz, 1XAM (now W9UZ and W3RB, respectively) worked, for several hours with Dely, 8AB, in France, with all three stations on 110 meters! Additional stations dropped down to 100 meters and found that they, too, could easily work two-way across the Atlantic. The exodus from the 200-meter region had started. The "short-wave" era had begun!

By 1924 dozens of commercial companies had rushed stations into the 100-meter region. Chaos threatened, until the first of a series of national and international radio conferences partitioned off various bands of frequencies for the different services. Although thought still centered around 100 meters, League officials at the first of these frequency-determining conferences, in 1924, wisely obtained amateur bands not only at 80 meters but at 40, 20, 10 and even 5 meters.

Eighty meters proved so successful that "forty" was given a try, and QSOs with Australia, New Zealand and South Africa soon became commonplace. Then how about 20 meters? This new band revealed entirely unexpected possibilities when 1XAM worked 6TS on the West Coast, direct, at high noon. The dream of amateur radio — daylight DX! — was finally true.

From then until "Pearl Harbor," when U. S. amateurs were again closed down "for the duration," amateur radio thrilled with a series of unparalleled accomplishments. Countries all over the world came on the air, and the world total of amateurs passed the 100,000 mark. . . . ARRL representatives deliberated with the representatives of twenty-two other nations in Paris in 1925 where, on April 17th, the International Amateur Radio Union was formed — a federation of national amateur radio societies. . . . The League began issuing certificates to those who could prove they had worked all six continents. More than six thousand amateurs have been awarded WAC certificates.

## AMATEUR RADIO

### ● PUBLIC SERVICE

Amateur radio is a grand and glorious hobby but this fact alone would hardly merit such wholehearted support as is given it by our Government at international conferences. There are other reasons. One of these is a thorough appreciation by the Army and Navy of the value of the amateur as a source of skilled radio personnel in time of war. Another asset is best described as "public service."

About 4000 amateurs had contributed their skill and ability in '17-'18. After the war it was only natural that cordial relations should prevail between the Army and Navy and the amateur. These relations strengthened in the next few years and, in gradual steps, grew into co-operative activities which resulted, in 1925, in the establishment of the Naval Communications Reserve and the Army-Amateur Radio System (now the Military Amateur Radio System). In World War II thousands of amateurs in the Naval Reserve were called to active duty, where they served with distinction, while many other thousands served in the Army, Air Forces, Coast Guard and Marine Corps. Altogether, more than 25,000 radio amateurs served in the armed forces of the United States. Other thousands were engaged in vital civilian electronic research, development and manufacturing. They also organized and manned the War Emergency Radio Service, the communications section of OCID.

The "public-service" record of the amateur is a brilliant tribute to his work. These activities can be roughly divided into two classes, expeditions and emergencies. Amateur co-operation with expeditions began in 1923 when a League member, Don Mix, ITS, of Bristol, Conn. (now assistant technical editor of *QST*), accompanied MacMillan to the Arctic on the schooner *Bowdoin* with an amateur station. Amateurs in Canada and the U.S. provided the home contacts. The success of this venture was such that other explorers followed suit. During subsequent years a total of perhaps two hundred voyages and expeditions were assisted by amateur radio, and for many years no expedition has taken the field without such plans.

Since 1913 amateur radio has been the principal, and in many cases the only, means of outside communication in several hundred storm, flood and earthquake emergencies in this country. The 1936 eastern states flood, the 1937 Ohio River Valley flood, the Southern California flood and Long Island-New England hurricane disaster in 1938, and the Florida-Gulf Coast hurricanes of 1947 called for the amateur's greatest emergency effort. In these disasters and many others — tornadoes, sleet storms, forest fires, blizzards — amateurs played a major rôle in the relief work and earned wide commendation for their resourcefulness in effecting communication where all other means had failed. During 1938 ARRL inaugurated a new emergency-preparedness

program, registering personnel and equipment in its Emergency Corps and putting into effect a comprehensive program of coöperation with the Red Cross, and in 1947 a National Emergency Coördinator was appointed to full-time duty at League headquarters.

### ● TECHNICAL DEVELOPMENTS

Throughout these many years the amateur was careful not to slight experimental development in the enthusiasm incident to international DX. The experimenter was constantly at work on ever-higher frequencies, devising improved apparatus, and learning how to cram several stations where previously there was room for only one! In particular, the amateur pressed on to the development of the very high frequencies and his experience with five meters is especially representative of his initiative and resourcefulness and his ability to make the most of what is at hand. In 1924, first amateur experiments in the vicinity of 56 Mc. indicated that band to be practically worthless for DX. Nonetheless, great "short-haul" activity eventually came about in the band and new gear was developed to meet its special problems. Beginning in 1934 a series of investigations by the brilliant experimenter, Ross Hull (later *QST*'s editor), developed the theory of v.h.f. wave-bending in the lower atmosphere and led amateurs to the attainment of better distances; while occasional manifestations of ionospheric propagation, with still greater distances, gave the band uniquely-erratic performance. By Pearl Harbor thousands of amateurs were spending much of their time on this and the next higher band, many having worked hundreds of stations at distances up to several thousand miles. Transcontinental 6-meter DX is now a commonplace occurrence; even the oceans have been bridged! It is a tribute to these indefatigable amateurs that today's concept of v.h.f. propagation was developed largely through amateur research.

The amateur is constantly in the forefront of technical progress. His incessant curiosity, his eagerness to try anything new, are two reasons. Another is that ever-growing amateur radio continually overcrowds its frequency assignments, spurring amateurs to the development and adoption of new techniques to permit the



A corner of the ARRL laboratory.

accommodation of more stations. For examples, amateurs turned from spark to c.w., designed more selective receivers, adopted crystal control and pure d.c. power supplies. From the ARRL's own laboratory in 1932 came James Lamb's "single-signal" super-heterodyne — the world's most advanced high-frequency radiotelegraph receiver — and, in 1936, the "noise-silencer" circuit. Amateurs are now turning to speech "clippers" to reduce bandwidths of 'phone transmissions and investigating "single-sideband suppressed-carrier" systems which promise to halve the spectrum space required by a voice-modulated signal.

During the recent war, thousands of skilled amateurs contributed their knowledge to the development of secret radio devices, both in Government and private laboratories. Equally as important, the prewar technical progress by amateurs provided the keystone for the development of modern military communications equipment. Perhaps more important today than individual contributions to the art is the mass cooperation of the amateur body in Government projects such as propagation studies; each participating amateur station is in reality a separate field laboratory from which reports are made for correlation and analysis.

Emergency relief, expedition contact, experimental work and countless instances of other forms of public service — rendered, as they always have been and always will be, without hope or expectation of material reward — made amateur radio an integral part of our peacetime national life. The importance of amateur participation in the armed forces and in other aspects of national defense have emphasized more strongly than ever that amateur radio is vital to our national existence.

### ● THE AMERICAN RADIO RELAY LEAGUE

The ARRL is today not only the spokesman for amateur radio in this country but it is the largest amateur organization in the world. It is strictly of, by and for amateurs, is noncommercial and has no stockholders. The members of the League are the owners of the ARRL and *QST*.

The League is organized to represent the amateur in legislative matters. It is pledged to promote interest in two-way amateur communication and experimentation. It is interested in the relaying of messages by amateur radio. It is concerned with the advancement of the radio art. It stands for the maintenance of fraternalism and a high standard of conduct.

One of the League's principal purposes is to keep amateur activities so well conducted that the amateur will continue to justify his existence. Amateur radio offers its followers countless pleasures and unending satisfaction. It also calls for the shouldering of responsi-



The operating room at W1AW.

bilities — the maintenance of high standards, a cooperative loyalty to the traditions of amateur radio, a dedication to its ideals and principles, so that the institution of amateur radio may continue to operate "in the public interest, convenience and necessity."

The operating territory of ARRL is divided into fifteen U. S. and five Canadian divisions. The affairs of the League are managed by a Board of Directors. One director is elected every two years by the membership of each U. S. division, and a Canadian General Manager is elected every two years by the Canadian membership. These directors then choose the president and vice-president, who are also members of the Board. The managing secretary, treasurer and communications manager are appointed by the Board. The directors, as representatives of the amateurs in their divisions, meet annually to examine current amateur problems and formulate ARRL policies thereon.

ARRL owns and publishes the monthly magazine, *QST*. Acting as a bulletin of the League's organized activities, *QST* also serves as a medium for the exchange of ideas and fosters amateur spirit. Its technical articles are renowned. It has grown to be the "amateur's bible," as well as one of the foremost radio magazines in the world. Membership dues include a subscription to *QST*.

ARRL maintains a model headquarters amateur station, known as the Hiram Percy Maxim Memorial Station, in Newington, Conn. Its call is W1AW, the call held by Mr. Maxim until his death and later transferred to the League station by a special FCC action. Separate transmitters of maximum legal power on each amateur band have permitted the station to be heard regularly all over the world. More important, W1AW transmits on regular schedules bulletins of general interest to amateurs, conducts code practice as a training feature, and engages in two-way work on all popular bands with as many amateurs as time permits.

At the headquarters of the League in West Hartford, Conn., is a well-equipped laboratory to assist staff members in preparation of technical material for *QST* and the *Radio Amateur's Handbook*. Among its other activities the League maintains a Communica-

tions Department concerned with the operating activities of League members. A large field organization is headed by a Section Communications Manager in each of the country's seventy-one sections. There are appointments for qualified members as Official Relay Station or Official 'Phone Station for traffic handling; as Official Observer for monitoring frequencies and the quality of signals; as Route Manager and 'Phone Activities Manager for the establishment of trunk lines and networks; as Emergency Coördinator for the promotion of amateur preparedness to cope with natural disasters; and as Official Experimental Station for those pioneering the frequencies above 50 Mc. Mimeographed bulletins keep appointees informed of the latest developments. Special activities and contests promote operating skill. A special section is reserved each month in *QST* for amateur news from every section of the country.

## ● AMATEUR LICENSING IN THE UNITED STATES

The Communications Act lodges in the Federal Communications Commission authority to classify and license radio stations and to prescribe regulations for their operation. Pursuant to the law, FCC has issued detailed regulations for the amateur service.

A radio amateur is a duly authorized person interested in radio technique solely with a personal aim and without pecuniary interest. Amateur operator licenses are given to U. S. citizens who pass an examination on operation and apparatus and on the provisions of law and regulations affecting amateurs, and who demonstrate ability to send and receive code at 13 words per minute. Station licenses are granted only to licensed operators and permit communication between such stations for amateur purposes, i.e., for personal noncommercial aims flowing from an interest in radio technique. An amateur station may not be used for material compensation of any sort nor for broadcasting. Narrow bands of frequencies are allocated exclusively for use by amateur stations. Transmissions may be on any frequency within the assigned bands. All the frequencies may be used for c.w. telegraphy and some are available for radiotelephony by any amateur, while others are reserved for radiotelephone use by persons having at least a year's experience and who pass the examination for a Class A license. The input to the final stage of amateur stations is limited to 1000 watts and on frequencies below 60 Mc. must be adequately-filtered direct current. Emissions must be free from spurious radiations. The licensee must provide for measurement of the transmitter frequency and establish a procedure for checking it regularly. A complete log of station operation must be maintained, with specified data. The station license also authorizes the holder to operate portable and mobile stations on

certain frequencies, subject to further regulations. An amateur station may be operated only by an amateur operator licensee, but any licensed amateur operator may operate any amateur station. All radio licensees are subject to penalties for violation of regulations.

Amateur licenses are issued entirely free of charge. They can be issued only to citizens but that is the only limitation, and they are given without regard to age or physical condition to anyone who successfully completes the examination. When you are able to copy 13 words per minute, have studied basic transmitter theory and are familiar with the law and amateur regulations, you are ready to give serious thought to securing the Government amateur licenses which are issued you, after examination at a local district office or examining points in most of our larger cities, through FCC at Washington. A complete up-to-the-minute discussion of license requirements, and a study guide for those preparing for the examination, are to be found in an ARRL publication, *The Radio Amateur's License Manual*, available from the American Radio Relay League, West Hartford 7, Conn., for 25¢, postpaid.

## ● LEARNING THE CODE

In starting to learn the code, you should consider it simply another means of conveying information. The spoken word is one method,

A	<u>didah</u>	N	<u>dahdit</u>
B	<u>dahdididit</u>	O	<u>dahdahdah</u>
C	<u>dahdidahdit</u>	P	<u>didahdahdit</u>
D	<u>dahdidit</u>	Q	<u>dahdahdidah</u>
E	<u>dit</u>	R	<u>didahdit</u>
F	<u>dididahdit</u>	S	<u>didit</u>
G	<u>dahdahdit</u>	T	<u>dah</u>
H	<u>didididit</u>	U	<u>dididah</u>
I	<u>didit</u>	V	<u>didididah</u>
J	<u>didahdahdah</u>	W	<u>didahdah</u>
K	<u>dahdidah</u>	X	<u>dahdididah</u>
L	<u>didahdidit</u>	Y	<u>dahdidahdah</u>
M	<u>dahdah</u>	Z	<u>dahdahdidit</u>
1	<u>didahdahdahdah</u>	6	<u>dahdidididit</u>
2	<u>dididahdahdah</u>	7	<u>dahdahdididit</u>
3	<u>dididididahdah</u>	8	<u>dahdahdahdidit</u>
4	<u>dididididah</u>	9	<u>dahdahdahdahdit</u>
5	<u>dididididit</u>	0	<u>dahdahdahdahdah</u>

Period: didahdidahdidah. Comma: dahdahdididahdah. Question mark: dididahdahdidit. Error: dididididididit. Double dash: dahdididahdah. Wait: didahdididit. End of message: didahdidahdit. Invitation to transmit: dahdidah. End of work: didididahdidah. Fraction bar: dahdididahdit.

Fig. 1-1 — The Continental (International Morse) code.

the printed page another, and typewriting and shorthand are additional examples. Learning the code is as easy — or as difficult — as learning to type.

The important thing in beginning to study code is to think of it as a language of *sound*, never as combinations of dots and dashes. It is easy to “speak” code equivalents by using “dit” and “dah,” so that A would be “didah” (the “t” is dropped in such combinations). The sound “di” should be staccato; a code character such as “5” should sound like a machine-gun burst: didididit! Stress each “dah” equally; they are underlined or italicized in this text because they should be slightly accented and drawn out.

Take a few characters at a time. Learn them thoroughly in *didah* language before going on to new ones. If someone who is familiar with code can be found to “send” to you, either by whistling or by means of a buzzer or code oscillator, enlist his cooperation. Learn the code by *listening* to it. Don’t think about speed to start; the first requirement is to learn the characters to the point where you can recognize each of them without hesitation. Concentrate on any difficult letters.

### ● ACQUIRING SPEED BY BUZZER PRACTICE

Regular practice periods will develop code proficiency. Two people can learn the code together, sending to each other by means of a buzzer-and-key outfit. An advantage of this system is that it develops sending ability, too, for the person doing the receiving will be quick to criticize uneven or indistinct sending. If possible get an experienced operator for the first few sessions to learn how well-sent characters should sound.

Either the buzzer set shown in Figs. 1-2 and 1-3 or the audio oscillator described will give satisfactory results as a practice set. The battery-operated audio oscillator in Figs. 1-4 and 1-5 is easy to construct and is effective. If nothing is heard in the headphones when the

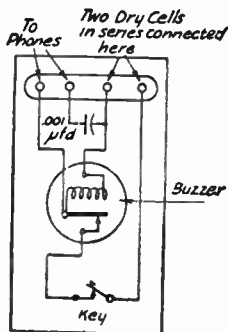


Fig. 1-2 — The headphones are connected across the coils of the buzzer, with a condenser in series. If the value shown gives an excessively loud signal, it may be reduced to 470  $\mu\text{fd}$ . or 220  $\mu\text{fd}$ .

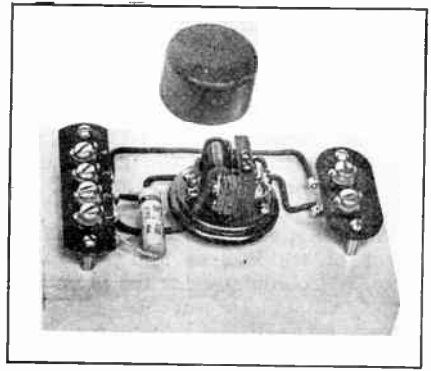


Fig. 1-3 — The cover of the buzzer unit has been removed in this view of the buzzer code-practice set.

key is depressed, reverse the leads going to either transformer winding (do not reverse both windings).

With a practice set ready, send single letters at first. When each character can be read quickly follow this by slow sending of complete words and sentences. Have the material sent at a rate slightly faster than you can copy easily; this speeds up your mind. Write down each letter you recognize. Do *not* try to write down the dots and dashes; write down letters. Don’t stop to compare the sounds of different letters, or think too long about a letter or word that has been missed. Go right on to the next one, or each “miss” will cause you to lose several characters. If you exercise a little patience you will soon be getting every character. When you can receive 13 words a minute (65 letters a minute), have the sender transmit code groups rather than English text. This will prevent you from recognizing a word “on the way” and filling it in before you’ve really listened to the letters themselves.

After you have acquired reasonable proficiency, concentrate on the less common characters, as well as the numerals and punctuation. These prove the downfall of many applicants taking the code examination.

### ● LEARNING BY LISTENING

WIAW conducts practice transmissions nightly, Monday through Friday, at speeds from 9 to 35 w.p.m. Such practice tapes start at 10 p.m. EST (EDST in summer). In addition, the Official Bulletins, also sent from WIAW, give added practice at 15 and 25 w.p.m. See the Operating News section announcements of the WIAW operating schedule, and Code Proficiency Program notes, in the latest copy of *QST*. Practice until you can mail in what you have copied over the air on WIAW’s monthly “qualifying run” to get a 15-word-per-minute Code Proficiency Certificate or a sticker for advanced speeds. As soon as you can, listen on a real communications receiver (with beat oscillator) and have the fun of learning by listening.



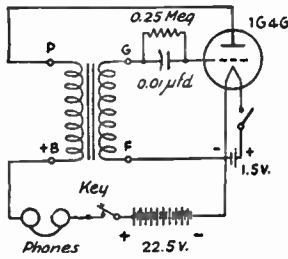


Fig. 1-4 — Wiring diagram of a simple vacuum-tube audio-frequency oscillator for use as a code-practice set

## ● USING A KEY

The correct way to grasp the key is important. The knob of the key should be about eighteen inches from the edge of the operating table and about on a line with the operator's right shoulder, allowing room for the elbow to rest on the table. A table about thirty inches in height is best. The spring tension of the key varies with different operators. A fairly heavy spring at the start is desirable. The back adjustment of the key should be changed until there is a vertical movement of about one-sixteenth inch at the knob. After an operator has mastered the use of the hand-key the tension should be changed and can be reduced to the minimum spring tension that will cause the key to open immediately when the pressure is released. More spring tension than necessary causes the expenditure of unnecessary energy. The contacts should be spaced by the rear screw on the key only and not by allowing play in the side screws, which are provided merely for aligning the contact points. These side screws should be screwed up to a setting which prevents appreciable side play, but not adjusted so tightly that binding is caused. The gap between the contacts should always be at least a thirty-second of an inch, since too-finely spaced contacts will cultivate a nervous style of sending which is highly undesirable. On the other hand, too-wide spacing (much over one-sixteenth inch), may result in unduly heavy or "muddy" sending.

Do not hold the key tightly. Let the hand rest lightly on the key. The thumb should be against the left side of the knob. The first and

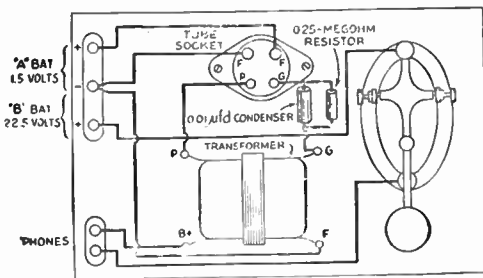


Fig. 1-5 — Layout of the audio-oscillator code-practice set. All parts may be mounted on a wooden baseboard, approximately 5 × 7 inches in size.

second fingers should be bent a little. They should hold the middle and right sides of the knob, respectively. The fingers are partly on top and partly over the side of the knob. The other two fingers should be free of the key. Fig. 1-6 shows the correct way to hold a key.

A wrist motion should be used in sending. The whole arm should not be used. One should not send "nervously" but with a steady flexing of the wrist. The grasp on the key should be firm, but not tight, or jerky sending will result. None of the muscles should be tense but they should all be under control. The arm should rest lightly on the operating table with the wrist held above the table. An up-and-down motion without any sideway action is best. The fingers should never leave the key knob.

Good sending may seem easier than receiving, but don't be deceived. A beginner should not attempt to send fast. Keep your transmitting speed down to your receiving speed, and bend your efforts to sending well. Do not try to speed things up too soon. A slow, even rate of

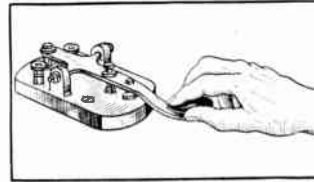


Fig. 1-6 — This sketch illustrates the correct position of the hand and fingers for good sending with a telegraph key.

sending is the mark of a good operator. Speed will come with time alone. Leave special types of keys alone until you have mastered the knack of handling the standard key. Because radio transmissions are seldom free from interference, a "heavier" style of sending is best to develop for radio work. A rugged, heavy key will help in developing this characteristic.

To become expert in transmitting good code, after you have thoroughly learned each letter and numeral and can both send and copy letters without hesitation, your best practice is to listen to commercial automatic-tape stations. Perfectly-sent code can be accomplished only by a machine, and you want to get fixed in your mind, indelibly, the correct formation of each and every code character and in particular the associated spaces. One of the best methods for deriving this association is to find a commercial or other tape station sending at about your maximum receiving speed. Notice the formation of each letter, the spaces left between letters and words, and the proportion in length of dits to dahs. Listen to the transmissions as you would at a musical concert, concentrating on assimilating every detail. The spaces between words may seem exaggerated, simply because you have probably been running yours together. A score of other details where the auto-

matic transmission is different than yours will very likely show up in the same text. From all this you will learn where your own faults lie and be able to correct them.

● THE AMATEUR BANDS

Amateurs are assigned bands of frequencies at approximate octave intervals throughout the spectrum. Like assignments to all services, they are subject to modification to fit the changing picture of world communications needs.

Below is a summary of the U. S. amateur bands on which operation is permitted as of our press date. Figures are megacycles. A0 means an unmodulated carrier, A1 means c.w. telegraphy, A2 is m.c.w., A3 is AM 'phone, A4 is facsimile, A5 is television; NBFM designates narrow-band frequency- or phase-modulated radiotelephony; and FM means frequency modulation, 'phone (including NBFM) or telegraphy.

The future of the prewar amateur band at 1.75 Mc. has not been finally determined, it depending principally on the disposition of the navigational service now operating there. The 1947 International Radio Conference has resulted in certain changes in present bands expected to become effective late in 1949. They are: a reduction in the 20-meter band to make it thenceforth 14,000-14,350 kc.; a new band 21,000-21,450 kc.; and a shift in the 11-meter band to make it 26,960-27,230 kc. Additional changes, probably effective earlier than 1949,

3.500-4.000	—	A1
3.850-4.000	—	A3, Class A only
3.850-3.900	—	NBFM, Class A only
7.000-7.300	—	A1
14.000-14.400	—	A1
14.200-14.300	—	A3, Class A only
14.200-14.250	—	NBFM, Class A only
27.160-27.430	—	A0, A1, A2, A3, A4, FM
28.000-29.700	—	A1
28.500-29.700	—	A3
28.500-29.000	—	NBFM
29.000-29.700	—	FM
50.0-54.0	—	A1, A2, A3, A4
51.0-52.5	—	NBFM
52.5-54.0	—	FM
144	-148	— A0, A1, A2, A3, A4, FM
235	-240	— A0, A1, A2, A3, A4, FM
420*	-450*	— A0, A1, A2, A3, A4, A5, FM
1,215	-1,295	} A0, A1, A2, A3, A4, A5, FM, Pulse
2,300	-2,450	
3,300	-3,500	
5,650	-5,925	
10,000	-10,500	
21,000	-22,000	
All above 30,000		

\* Peak antenna power must not exceed 50 watts.

will shift the 1 1/4-meter band to its permanent location 220-225 Mc., and expand the 1215-Mc. band so that its top limit will be 1300 Mc. Because of the possibility of such changes, and because the portion of each band available for 'phone operation is customarily varied from time to time in accordance with changes in amateur operational habits, in such respects each amateur should keep himself currently informed by consulting *QST* or writing ARRL for latest information.

# Electrical Laws and Circuits

Everyone knows that radio is electrical in nature, and it is taken for granted that to know anything about the operation of radio equipment you have first to know something about electricity and electrical circuits. The amount of electrical knowledge you need in an amateur radio depends on how far you delve into the technicalities of the various types of transmitters, receivers and measuring equipment that amateurs use. If you're just getting started you do not need very much, but as you progress you will find that you will acquire, more or less unconsciously, a great deal of basic information. That is, you will if you

make a conscientious effort to understand and analyze the things that you observe in using radio gear.

The purpose of this chapter is to provide the answers to many questions about circuits that will come up in the course of building and operating an amateur station. It is intended as a *practical* reference section rather than a course in "theory." You can study it consecutively if you wish, of course. However, it should be even more valuable to you in showing how everyday problems can be solved when the occasion to solve them arises.

## Fundamentals

### ● ELECTRIC AND MAGNETIC FIELDS

At the bottom of everything in electricity and radio is a **field**. Although a field is not too easy to visualize, we need to have some appreciation of what it is if electrical effects are to be understood. When something occurs at one point in space because something else happened at another point, with no visible means by which the "cause" can be related to the "effect," we say the two events are connected by a "field." It does not matter whether or not the field is "real" — that is, whether it is something physical although, like air, invisible. The important point is that the distant effects are *predictable*, and it is convenient to attribute them to properties of a field. The fields with which we are concerned are the **electric** and **magnetic**, and the combination of the two called the **electromagnetic field**.

A field has two important properties, *intensity* (*magnitude*) and *direction*. That is, the field exerts a *force* on an object immersed in it; intensity measures the amount of force exerted while direction tells the direction in which the object on which the force is exerted will tend to move. An electrically-charged object in an electric field will be acted on by a force that will tend to move it in a direction determined by the direction of the field. Similarly, a magnet in a magnetic field will be subject to a force. Everyone has seen demonstrations of

magnetic fields with pocket magnets, so intensity and direction are not hard to grasp.

A "static" field is one that is fixed in space. Such a field can be set up by a stationary electric charge (**electrostatic field**) or by a stationary magnet (**magnetostatic field**). But if either an electric or magnetic field is moving in space or changing in intensity, the motion or change sets up the other kind of field. That is, a changing electric field sets up a magnetic field, and a changing magnetic field generates an electric field. This interrelationship between magnetic and electric fields makes possible such things as the electromagnet and the electric motor. It also makes possible the **electromagnetic waves** by which radio communication is carried on, for such waves are simply traveling fields in which the energy is alternately handed back and forth between the electric and magnetic fields.

### *Lines of Force*

We need, obviously, some way to compare the intensity and direction of different fields. This is done by picturing the field as made up of **lines of force**, or **flux lines**. These are purely imaginary threads that show, by the direction in which they lie, the direction the object on which the force is exerted will move. The *number* of lines in a chosen cross section of the field is a measure of the *intensity* of the force. The number of lines per square inch, or per square centimeter, is called the **flux density**.

## ● ELECTRICITY AND THE ELECTRIC CURRENT

Electrical effects are caused by extremely small particles of electricity called **electrons**. Everything physical is built up of atoms, particles so small that they cannot be seen even through the most powerful microscope. But the atom in turn consists of still smaller particles — several different kinds of them. One type of particle is the electron. An ordinary atom consists of a central core, called the **nucleus**, around which one or more electrons circulate somewhat as the earth and other planets circulate around the sun. Both the nucleus and the electrons are electrical, but the kind of electricity associated with the nucleus is called **positive** and that associated with the electrons is called **negative**.

The important fact about these two “opposite” kinds of electricity is that they are strongly attracted to each other. Also, there is a strong force of repulsion between two charges (a collection of electrified particles is called a **charge**) of the *same* kind. The positive nucleus and the negative electrons are attracted to each other, but two electrons will be repelled from each other and so will two nuclei. The fact that an atom contains both positive and negative charges makes it tend to stay together as a unit; in a normal atom the positive charge on the nucleus is exactly balanced by the total of the negative charges on the electrons. It is possible, though, for an atom to lose one of its electrons; when that happens the atom has a little less negative charge than it should — or, to put it another way, it has a net positive charge. Such an atom is said to be **ionized**, and in this case the atom is a **positive ion**. If an atom picks up an extra electron, as it sometimes does, it has a net negative charge and is called a **negative ion**. A positive ion will attract any stray electron in the vicinity, including the extra one that may be attached to a nearby negative ion. In this way it is conveniently possible for electrons to travel from atom to atom, and when such movement occurs on a measurable scale (millions or billions of electrons moving) we have a detectable **electric current**.

### Conductors and Insulators

The movement of electrons can take place in a solid, a liquid, or a gas. In liquids and gases, positive and negative ions, as well, are free to move when attracted electrically, but in solids only the electrons move. However, movement of electrons or ions is not possible in all substances. Atoms of some materials, notably metals and acids, will give up an electron readily, but atoms of other materials will not part with any of their electrons even when the electric force is extremely strong. Materials in which electrons or ions can be moved with relative ease are called **conductors**, while those that refuse to permit such movement are

called **nonconductors** or **insulators**. The following listing shows how some common materials divide between the conductor and insulator classifications:

<i>Conductors</i>	<i>Insulators</i>
Metals	Dry Air
Carbon	Wood
Acids	Porcelain
	Textiles
	Glass
	Rubber
	Resins

### Electromotive Force

The electric force (called **electromotive force**, and abbreviated **e.m.f.**) that causes current flow may be developed in several ways. The action of certain chemical solutions on dissimilar metals sets up an e.m.f.; such a combination is called a **cell**, and a group of cells forms an **electric battery**. The amount of current that such cells can carry is limited, and in the course of current flow one of the metals is eaten away. The amount of electrical energy that can be taken from a battery consequently is rather small. Where a large amount of energy is needed it is usually furnished by an **electric generator**, which develops its e.m.f. by a combination of magnetic and mechanical means. Large generators in power houses supply the energy that is distributed to homes and factories.

In picturing current flow it is natural to think of a single, constant force causing the electrons to move. When this is so, the elec-

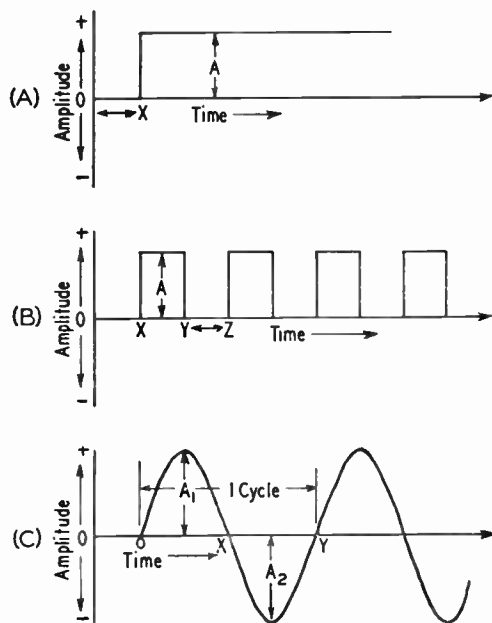


Fig. 2-1—Three types of current flow. A — direct current; B — intermittent direct current; C — alternating current.

trons always move in the same direction through a path or circuit made up of conductors connected together in a continuous chain. Such a current is called a **direct current**, abbreviated **d.c.** It is the type of current furnished by batteries and by certain types of generators. However, it is also possible — and desirable as well — to have an e.m.f. that periodically reverses. With this kind of e.m.f. the current flows first in one direction through the circuit and then in the other. Such an e.m.f. is called an **alternating e.m.f.**, and the current is called an **alternating current** (abbreviated **a.c.**). The reversals (**alternations**) may occur at any rate from a few per second up to several billion per second. Two reversals make a **cycle**; in one cycle the force acts first in one direction, then in the other, and then returns to the first direction. The number of cycles in one second is called the **frequency** of the alternating current.

### Direct and Alternating Currents

The difference between direct current and alternating current is shown in Fig. 2-1. In these graphs the horizontal axis measures time, increasing toward the right away from the vertical axis. The vertical axis represents the amplitude or size of the current, increasing in either the up or down direction away from the horizontal axis. If the graph is *above* the horizontal axis the current is flowing in one direction through the circuit (indicated by the + sign) and if it is *below* the horizontal axis the current is flowing in the reverse direction through the circuit (indicated by the - sign). Fig. 2-1A shows that, if we close the circuit — that is, make the path for the current complete — at the time indicated by *X*, the current instantly takes the amplitude indicated by the height *A*. After that, the current continues at the same amplitude as time goes on. This is an ordinary *direct* current.

In Fig. 2-1B, the current starts flowing with the amplitude *A* at time *X*, continues at that amplitude until time *Y* and then instantly ceases. After an interval *YZ* the current again begins to flow and the same sort of start-and-stop performance is repeated. This is an *intermittent* direct current. We could get it by alternately closing and opening a switch in the circuit. It is a *direct* current because the *direction* of current flow does not change; the graph is always on the + side of the horizontal axis.

In Fig. 2-1C the current starts at zero, increases in amplitude as time goes on until it reaches the amplitude  $A_1$  while flowing in the + direction, then decreases until it drops to zero amplitude once more. At that time (*X*) the *direction* of the current flow reverses; this is indicated by the fact that the next part of the graph is below the axis. As time goes on the amplitude increases, with the current now flowing in the - direction, until it reaches amplitude  $A_2$ . Then the amplitude decreases until finally it drops to zero (*Y*) and the direc-

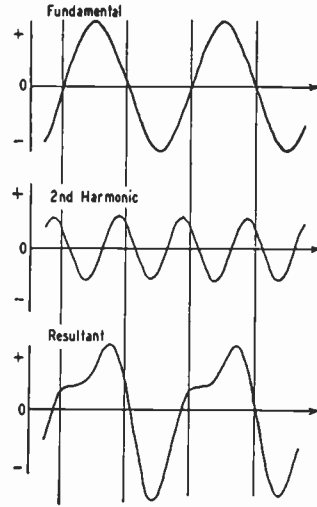


Fig. 2-2 — A complex waveform. A fundamental (top) and second harmonic (center) added together, point by point at each instant, result in the waveform shown at the bottom. When the two components have the same polarity at a selected instant, the resultant is the simple sum of the two. When they have opposite polarities, the resultant is the *difference*: if the negative-polarity component is larger, the resultant is negative at that instant.

tion reverses once more. This is an *alternating* current.

### Waveforms

The graph of the alternating current is what is known as a **sine wave**. Sine-wave alternating current is the simplest — but not the only — kind. Notice that the variations in amplitude are quite regular and that the “negative” half-cycle or alternation is exactly like the “positive” half-cycle except for the reversal of direction. The variations in many a.c. waves are not so smooth, nor is one half-cycle necessarily just like the preceding one in shape. However, these more complex waves actually can be shown to be the sum of two or more sine waves of frequencies that are exact **integral** (whole-number) multiples of some lower frequency. The lowest frequency is called the **fundamental** frequency, and the higher frequencies (2 times, 3 times the fundamental frequency, and so on) are called **harmonics**.

Fig. 2-2 shows how a fundamental and a second harmonic (twice the fundamental) might add to form a complex wave. A little thought will show that simply by changing the relative amplitudes of the two waves, as well as the times at which they pass through zero amplitude, an infinite number of waveshapes can be constructed from just a fundamental and second harmonic. Waves that are still more complex can be constructed if more than two harmonics are used.

### Electrical Units

The unit of electromotive force is called the **volt**. An ordinary flashlight cell generates an

e.m.f. of about 1.5 volts. The e.m.f. commonly supplied for domestic lighting and power is 115 volts, usually a.c. having a frequency of 60 cycles per second. The voltages used in radio receiving and transmitting circuits range from a few volts (usually a.c.) for filament heating to as high as a few thousand d.c. volts for the operation of power tubes.

The flow of electric current is measured in **amperes**. One ampere is equivalent to the movement of many billions of electrons past a point in the circuit in one second. Currents in the neighborhood of an ampere are required for heating the filaments of small power tubes. The *direct* currents used in amateur radio equipment usually are not so large, and it is customary to measure such currents in **milliamperes**. One milliampere is equal to one one-thousandth of an ampere, or 1000 milliamperes equals one ampere.

In assigning a value to an alternating current or voltage, it is necessary to take into account the difference between direct and alternating currents. A "d.c. ampere" is a measure of a *steady* current, but the "a.c. ampere" must measure a current that is continually varying in amplitude and periodically reversing direction. To put the two on the same basis, an a.c. ampere is defined as the amount of current that will cause the same heating effect (see later section) as one ampere of steady direct current. For a sine-wave alternating current, this **effective** (or **r.m.s.**) value is equal to the *maximum* amplitude of the current ( $A_1$  or  $A_2$  in Fig. 2-1C) multiplied by 0.707. The **instantaneous** value of an alternating current is the value that the current measures at any selected instant in the cycle.

If all the instantaneous values in a sine-wave alternating current are averaged over a *half-cycle*, the resulting figure is the **average** value of the alternating current. It is equal to 0.636 times the maximum amplitude. The average value is useful in connection with rectifier systems, as described in a later chapter.

These definitions of units apply to a.c. voltage as well as to current.

## ● FREQUENCY AND WAVELENGTH

### *Frequency Spectrum*

The electrical energy supplied for household use usually has a frequency of 60 cycles per second. Frequencies ranging from about 15 to 15,000 cycles per second are called **audio** frequencies, because the vibrations of air particles that our ears recognize as sounds occur at the same rate. Audio frequencies (abbreviated a.f.) are used to actuate loudspeakers and thus create sound waves.

Frequencies above about 15,000 cycles are called **radio** frequencies (r.f.) because they are

useful in radio transmission. Frequencies all the way up to and beyond 10,000,000,000 cycles have been used for radio purposes. At radio frequencies the numbers become so large that it becomes convenient to use a larger unit than the cycle. Two such units in everyday use are the **kilocycle**, which is equal to 1000 cycles and is abbreviated **kc.**, and the **megacycle**, which is equal to 1,000,000 cycles or 1,000 kilocycles and is abbreviated **Mc**. The accompanying table shows how to convert frequencies expressed in one unit into frequencies in another unit.

The various radio frequencies are divided off into classifications for ready identification. These classifications, listed below, constitute the **frequency spectrum** so far as it extends for radio purposes at the present time.

Frequency	Classification	Abbreviation
10 to 30 kc.	Very-low frequencies	v.l.f.
30 to 300 kc.	Low frequencies	l.f.
300 to 3000 kc.	Medium frequencies	m.f.
3 to 30 Mc.	High frequencies	h.f.
30 to 300 Mc.	Very-high frequencies	v.h.f.
300 to 3000 Mc.	Ultrahigh frequencies	u.h.f.
3000 to 30,000 Mc.	Superhigh frequencies	s.h.f.

### *Wavelength*

We said earlier that radio waves are traveling fields of electric and magnetic force. These fields travel at great speed — so great that, so far as we can observe, "cause" and "effect" are simultaneous. Nevertheless, it does take a definite amount of time for the effect of a field set up at one point to be felt at a point some distance away.

Radio waves travel at the same speed as light — 300,000,000 meters or about 186,000 miles a second. They are always set up by a radio-frequency current flowing in a circuit, because the rapidly-changing current sets up a magnetic field that changes in the same way, and the varying magnetic field in turn sets up a varying electric field. And whenever this happens, the two fields move outward at the speed of light.

Suppose our r.f. current has a frequency of 3,000,000 cycles per second. The fields, then, will go through complete reversals (one cycle) in  $1/3,000,000$  second. In that same period of time the fields — that is, the wave — will move 300,000,000/3,000,000 meters, or 100 meters. (The meter is the unit of length commonly used in all sciences. We could use miles, feet, or inches, though, if those units were more convenient.) By the time the wave has moved that distance the next cycle has begun and a new wave has started out. The first wave, in other words, covers a distance of 100 meters before the beginning of the next, and so on. This distance is the "length" of the wave, or **wavelength**.

The longer the time of one cycle — that is, the lower the frequency — the greater the distance occupied by each wave and hence the longer the wavelength. The relationship be-

tween wavelength and frequency is shown by the formula

$$\lambda = \frac{300,000}{f}$$

where  $\lambda$  = Wavelength in meters  
 $f$  = Frequency in kilocycles

or 
$$\lambda = \frac{300}{f}$$

where  $\lambda$  = Wavelength in meters  
 $f$  = Frequency in megacycles

Example: The wavelength corresponding to a frequency of 3659 kilocycles is

$$\lambda = \frac{300,000}{3650} = 82.2 \text{ meters}$$

Most of our dealings are with frequency, if for no other reason than that it can be measured much more accurately than wavelength. However, we cannot ignore wavelength; it enters into the calculation of the size of "linear" circuits such as antennas.

## Resistance

The ease with which we can force an electric current through a conductor varies with the material, shape and dimensions of the conductor. Given two conductors of the same size and shape, but of different materials, the amount of current that will flow when a given e.m.f. is applied to the conductor will be found to vary with what is called the **resistance** of the material. The lower the resistance, the greater the current for a given value of e.m.f.

Resistance is measured in **ohms**. A circuit has a resistance of one ohm when an applied e.m.f. of one volt causes a current of one ampere to flow. The **resistivity** of a material is the resistance, in ohms, of a cube of the material measuring one centimeter on each edge. One of the best conductors is copper, which is why this metal is so widely used in electrical circuits. It is frequently convenient, in making resistance calculations, to compare the resistance of the material under consideration with that of a copper conductor of the same size and shape; Table 2-1 gives the ratio of the resistivity of the material to that of copper.

The longer the path through which the current flows the higher the resistance of that conductor. For direct current and low-frequency alternating currents (up to a few thousand cycles per second) the resistance is *inversely* proportional to the cross-sectional area of the path the current must travel; that is, given two conductors of the same material and having the same length, but differing in cross-sectional area, the one with the larger area will have the lower resistance.

### Resistance of Wires

It is readily possible to combine all these statements about resistance in a single formula that would enable us to calculate the resistance of conductors of any size, shape and material. However, in most practical cases the problem will be to determine the resistance of a round wire of given diameter and length — or its opposite: finding a suitable size and length of wire to supply a desired amount of resistance. Such problems can be easily solved with the help of the information in the copper-wire table in Chapter Twenty-Four. This table gives the resistance, in ohms per thousand feet, of each standard wire size.

Example: Suppose a resistance of 3.5 ohms is needed and some No. 28 wire is on hand. The wire table in Chapter 24 shows that No. 28 has a resistance of 66.17 ohms per thousand feet. Since the desired resistance is 3.5 ohms, the length of wire required will be

$$\frac{3.5}{66.17} \times 1000 = 52.89 \text{ feet.}$$

Or, suppose that the resistance of the wire in the circuit must not exceed 0.05 ohm and that the length of wire required for making the connections totals 14 feet. Then

$$\frac{14}{1000} \times R = 0.05 \text{ ohm}$$

where  $R$  is the maximum allowable resistance in ohms per thousand feet. Rearranging the formula gives

$$R = \frac{0.05 \times 1000}{14} = 3.57 \text{ ohms/1000 ft.}$$

Reference to the wire table shows that No. 15 is the smallest size having a resistance less than this value.

When the wire is not copper, the resistance values given in the wire table in Chapter Twenty-Four should be multiplied by the ratios given in Table 2-1 to obtain the resistance.

Example: If the wire in the first example were iron instead of copper the length required for 3.5 ohms would be

$$\frac{3.5}{66.17 \times 5.65} \times 1000 = 9.35 \text{ feet.}$$

### Temperature Effects

The resistance of a conductor changes with its temperature. Although it is seldom necessary to consider temperature in making the

**TABLE 2-1**  
**Relative Resistivity of Metals**

Material	Resistivity Compared to Copper
Aluminum (pure) . . . . .	1.70
Brass . . . . .	3.57
Cadmium . . . . .	5.26
Chromium . . . . .	1.82
Copper (hard-drawn) . . . . .	1.12
Copper (annealed) . . . . .	1.00
Iron (pure) . . . . .	5.65
Lead . . . . .	14.3
Nickel . . . . .	6.25 to 8.33
Phosphor Bronze . . . . .	2.78
Silver . . . . .	0.94
Tin . . . . .	7.70
Zinc . . . . .	3.54


resistance calculations required in amateur work, it is well to know that the resistance of practically all metallic conductors increases with increasing temperature. Carbon, however, acts in the opposite way; its resistance *decreases* when its temperature rises. The temperature effect is important when it is necessary to maintain a constant resistance under all conditions. Special materials that have little or no change in resistance over a wide temperature range are used in that case.

### Resistors

Resistance has important uses in electrical and radio circuits. A "package" of resistance made up into a single unit is called a **resistor**. Resistors having the same resistance value may be considerably different in size and construction. The flow of current through resistance causes the conductor to become heated; the higher the resistance and the larger the current, the greater the amount of heat developed. Consequently, high-resistance resistors intended for carrying large currents must be physically large so the heat can be radiated quickly to the surrounding air. If the resistor does not get rid of its heat quickly it might reach a temperature that would cause it to melt or burn. Types of resistors used in radio circuits are shown in the photograph.
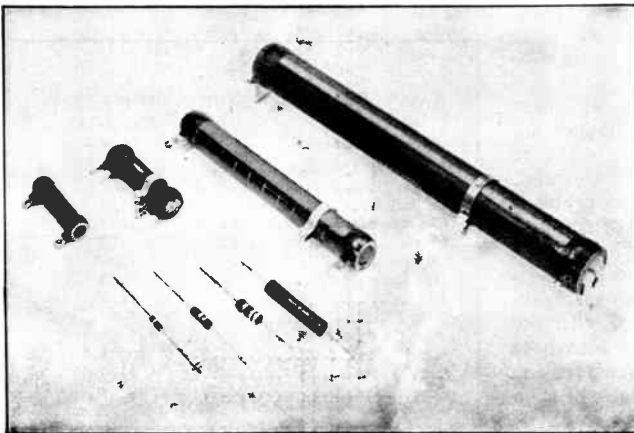
### Conductance

The reciprocal of resistance (that is,  $1/R$ ) is called **conductance**. It is usually represented by the symbol  $G$ , and the higher its value the greater the conductivity of the circuit. A circuit having large conductance has low resistance, and vice versa. In radio work the term is used chiefly in connection with vacuum-tube characteristics. The unit of conductance is the **mho**. A resistance of one ohm has a conductance of one mho, a resistance of 1000 ohms has a conductance of 0.001 mho, and so on. A unit frequently used in connection with vacuum tubes is the **micromho**, or one-millionth of a mho. It is the conductance of a resistance of one megohm.



Types of resistors used in radio equipment. Those in the foreground with wire leads are carbon types, ranging in size from  $\frac{1}{2}$  watt at the left to 2 watts at the right. The larger resistors use resistance wire wound on ceramic tubes; sizes shown range from 5 watts to 100 watts. Three are the adjustable type, using a sliding contact on an exposed section of the resistance winding.

Fig. 2-3 — A simple circuit consisting of a battery and resistor.



### OHM'S LAW

The simplest form of electric circuit is a battery with a resistance connected to its terminals, as shown by the symbols in Fig. 2-3. A complete circuit must have an unbroken path so current can flow out of the battery, through the apparatus connected to it, and back into the battery. The circuit is **broken**, or **open**, if a connection is removed at any point. A **switch** is a device for making and breaking connections and thereby closing or opening the circuit, either allowing current to flow or preventing it from flowing.

The values of current, voltage and resistance in a circuit are by no means independent of each other. The relationship between them is known as **Ohm's Law**. It can be stated as follows: The current flowing in a circuit is directly proportional to the applied e.m.f. and inversely proportional to the resistance. Expressed as an equation, it is

$$I \text{ (amperes)} = \frac{E \text{ (volts)}}{R \text{ (ohms)}}$$

The equation above gives the value of current when the voltage and resistance are known. It may be transposed so that any of the three quantities may be found when the other two are known:

$$E = IR$$

(that is, the voltage acting is equal to the current in amperes multiplied by the resistance in ohms) and

$$R = \frac{E}{I}$$

(or, the resistance of the circuit is equal to the applied voltage divided by the current).

All three forms of the equation are used almost constantly in radio work. It must be



remembered that the quantities are in *volts*, *ohms* and *amperes*; other units cannot be used in the equations without first being converted. For example, if the current is in milliamperes it must be changed to the equivalent fraction of an ampere before the value can be substituted in the equations.

Table 2-II shows how to convert between the various units in common use. The prefixes attached to the basic-unit name indicate the nature of the unit. These prefixes are:

- micro — one-millionth (abbreviated  $\mu$ )
- milli — one-thousandth (abbreviated *m*)
- kilo — one thousand (abbreviated *k*)
- mega — one million (abbreviated *M*)

For example, one microvolt is one-millionth of a volt, and one megohm is 1,000,000 ohms. There are therefore 1,000,000 microvolts in one volt, and 0.000001 megohm in one ohm.

The following examples illustrate the use of Ohm's Law:

The current flowing in a resistance of 20,000 ohms is 150 milliamperes. What is the voltage? Since the voltage is to be found, the equation to use is  $E = IR$ . The current must first be converted from milliamperes to amperes, and reference to the table shows that to do so it is necessary to divide by 1000. Therefore,

$$E = \frac{150}{1000} \times 20,000 = 3000 \text{ volts}$$

When a voltage of 150 is applied to a circuit the current is measured at 2.5 amperes. What is the resistance of the circuit? In this case  $R$  is the unknown, so

$$R = \frac{E}{I} = \frac{150}{2.5} = 60 \text{ ohms}$$

No conversion was necessary because the voltage and current were given in volts and amperes.

How much current will flow if 250 volts is applied to a 5000-ohm resistor? Since  $I$  is unknown,

$$I = \frac{E}{R} = \frac{250}{5000} = 0.05 \text{ ampere}$$

Milliampere units would be more convenient for the current, and  $0.05 \text{ amp.} \times 1000 = 50 \text{ milliamperes}$ .

**SERIES AND PARALLEL RESISTANCES**

Very few actual electric circuits are as simple as the illustration in the preceding section. Commonly, resistances are found connected in a variety of ways. The two fundamental methods of connecting resistances are shown in Fig. 2-4. In the upper drawing, the current flows from the source of e.m.f. (in the direction shown by the arrow, let us say) down through the first resistance,  $R_1$ , then through the second,  $R_2$ , and then back to the source. These resistors are connected in **series**. The current everywhere in the circuit has the same value.

In the lower drawing the current flows to the common connection point at the top of the two resistors and then divides, one part of it flowing through  $R_1$  and the other through  $R_2$ . At the lower connection point these two currents again combine; the total is the same as the current that flowed into the upper common connection. In this case the two resistors are connected in **parallel**.

To change from	To	Divide by	Multiply by
Units	Micro-units Milli-units Kilo-units Mega-units	1000 1,000,000	1,000,000 1000
Micro-units	Milli-units Units	1000 1,000,000	
Milli-units	Micro-units Units	1000	1000
Kilo-units	Units Mega-units	1000	1000
Mega-units	Units Milli-units		1,000,000 1000

**Resistors in Series**

When a circuit has a number of resistances connected in series, the total resistance of the circuit is the sum of the individual resistances. If these are numbered  $R_1, R_2, R_3$ , etc., then

$$R \text{ (total)} = R_1 + R_2 + R_3 + R_4 + \dots$$

where the dots indicate that as many resistors as necessary may be added.

Example: Suppose that three resistors are connected to a source of e.m.f. as shown in Fig. 2-5. The e.m.f. is 250 volts,  $R_1$  is 5000 ohms,  $R_2$  is 20,000 ohms, and  $R_3$  is 8000 ohms. The total resistance is then

$$R = R_1 + R_2 + R_3 = 5000 + 20,000 + 8000 = 33,000 \text{ ohms}$$

The current flowing in the circuit is then

$$I = \frac{E}{R} = \frac{250}{33,000} = 0.00757 \text{ amp.} = 7.57 \text{ ma.}$$

(We need not carry calculations beyond three significant figures, and often two will suffice because the accuracy of measurements is seldom better than a few per cent.)

**Voltage Drop**

Ohm's Law applies to *any part* of a circuit as well as to the whole circuit. Although the current is the same in all three of the resistances in the example, the total voltage divides

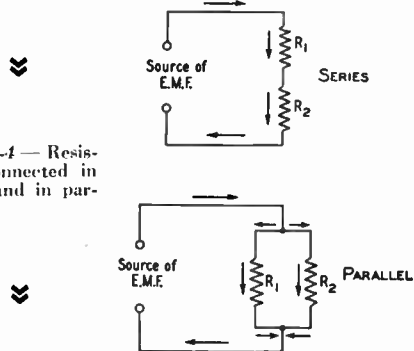


Fig. 2-4—Resistors connected in series and in parallel.

among them. The voltage appearing across each resistor can be found from Ohm's Law.

Example: If the voltage across  $R_1$  (Fig. 2-5) is called  $E_1$ , that across  $R_2$  is called  $E_2$ , and that across  $R_3$  is called  $E_3$ , then

$$\begin{aligned} E_1 &= IR_1 = 0.00757 \times 5000 = 37.9 \text{ volts} \\ E_2 &= IR_2 = 0.00757 \times 20,000 = 151.4 \text{ volts} \\ E_3 &= IR_3 = 0.00757 \times 8000 = 60.6 \text{ volts} \end{aligned}$$

The total voltage must equal the sum of the individual voltage drops:

$$E = E_1 + E_2 + E_3 = 37.9 + 151.4 + 60.6 = 249.9 \text{ volts}$$

The answer would have been more nearly exact if the current had been calculated to more decimal places, but as explained above a very high order of accuracy is not necessary.

In a simple series circuit like that in Fig. 2-5, the voltage drop across each resistance can be calculated very simply, if only the drop and not the current is wanted. The drop across each resistor is proportional to the ratio of the individual resistance to the total resistance. Thus

$$\begin{aligned} E_1 &= \frac{R_1}{R_1 + R_2 + R_3} \times 250 \\ &= \frac{5000}{5000 + 20,000 + 8000} = \frac{5000}{33,000} \times 250 \\ &= 37.8 \text{ volts} \end{aligned}$$

$$E_2 = \frac{20,000}{33,000} \times 250 = 151.5 \text{ volts}$$

$$E_3 = \frac{8000}{33,000} \times 250 = 60.5 \text{ volts}$$

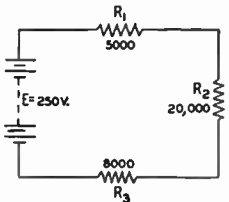


Fig. 2-5 — An example of resistors in series. The solution of the circuit is worked out in the text.

In problems such as this considerable time and trouble can be saved, when the current is small enough to be expressed in milliamperes, if the resistance is expressed in kilohms rather than ohms. When resistance in kilohms is substituted directly in Ohm's Law the current will be in milliamperes if the e.m.f. is in volts.

Example: Since 5000 ohms = 5 kilohms, 20,000 ohms = 20 kilohms, and 8000 ohms = 8 kilohms, the equations above become

$$I = \frac{E}{R} = \frac{250}{33} = 7.57 \text{ ma.}$$

$$\begin{aligned} E_1 &= IR_1 = 7.57 \times 5 = 37.9 \text{ volts} \\ E_2 &= IR_2 = 7.57 \times 20 = 151.4 \text{ volts} \\ E_3 &= IR_3 = 7.57 \times 8 = 60.6 \text{ volts} \end{aligned}$$

**Resistors in Parallel**

In a circuit with resistances in parallel, the total resistance is less than that of the lowest value of resistance present. This is because the total current is always greater than the current in any individual resistor. The formula for finding the total resistance of resistances in parallel is

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots}$$

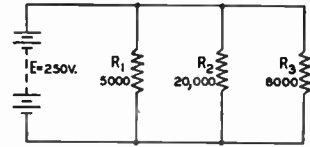


Fig. 2-6 — An example of resistors in parallel. The solution is worked out in the text.

where the dots again indicate that any number of resistors can be combined by the same method. For only two resistances in parallel (a very common case) the formula is

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

Example: If a 500-ohm resistor is paralleled with one of 1200 ohms, the total resistance is

$$R = \frac{R_1 R_2}{R_1 + R_2} = \frac{500 \times 1200}{500 + 1200} = \frac{600,000}{1700} = 353 \text{ ohms}$$

It is probably easier to solve practical problems by a different method than the "reciprocal of reciprocals" formula. Suppose the three resistors of the previous example are connected in parallel as shown in Fig. 2-6. The same e.m.f., 250 volts, is applied to all three of the resistors. The current in each can be found from Ohm's Law as shown below,  $I_1$  being the current through  $R_1$ ,  $I_2$  the current through  $R_2$  and  $I_3$  the current through  $R_3$ .

For convenience, the resistance will be expressed in kilohms so the current will be in milliamperes.

$$I_1 = \frac{E}{R_1} = \frac{250}{5} = 50 \text{ ma.}$$

$$I_2 = \frac{E}{R_2} = \frac{250}{20} = 12.5 \text{ ma.}$$

$$I_3 = \frac{E}{R_3} = \frac{250}{8} = 31.25 \text{ ma.}$$

The total current is

$$I = I_1 + I_2 + I_3 = 50 + 12.5 + 31.25 = 93.75 \text{ ma.}$$

The total resistance of the circuit is therefore

$$R = \frac{E}{I} = \frac{250}{93.75} = 2.66 \text{ kilohms (= 2660 ohms)}$$

**Resistors in Series-Parallel**

An actual circuit may have resistances both in parallel and in series. To illustrate, we use the same three resistances again, but now connected as in Fig. 2-7. The method of solving such a circuit is as follows: Consider  $R_2$  and  $R_3$  in parallel as though they formed a single resistor. Find their equivalent resistance. Then this resistance in series with  $R_1$  forms a simple

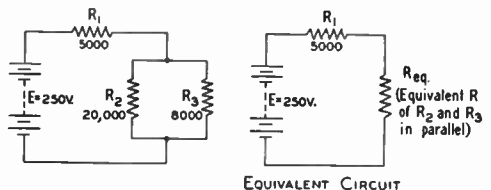


Fig. 2-7 — An example of resistors in series-parallel. The solution is worked out in the text.

series circuit, as shown at the right in Fig. 2-7.

Example: The first step is to find the equivalent resistance of  $R_2$  and  $R_3$ . From the formula for two resistances in parallel,

$$R_{eq.} = \frac{R_2 R_3}{R_2 + R_3} = \frac{20 \times 8}{20 + 8} = \frac{160}{28} = 5.71 \text{ kilohms}$$

The total resistance in the circuit is then

$$R = R_1 + R_{eq.} = 5 + 5.71 \text{ kilohms} = 10.71 \text{ kilohms}$$

The current is

$$I = \frac{E}{R} = \frac{250}{10.71} = 23.4 \text{ ma.}$$

The voltage drops across  $R_1$  and  $R_{eq.}$  are

$$E_1 = IR_1 = 23.4 \times 5 = 117 \text{ volts}$$

$$E_2 = IR_{eq.} = 23.4 \times 5.71 = 133 \text{ volts}$$

with sufficient accuracy. These total 250 volts, thus checking the calculations so far, because the sum of the voltage drops must equal the total voltage. Since  $E_2$  appears across both  $R_2$  and  $R_3$ ,

$$I_2 = \frac{E_2}{R_2} = \frac{133}{20} = 6.75 \text{ ma.}$$

$$I_3 = \frac{E_2}{R_3} = \frac{133}{8} = 16.6 \text{ ma.}$$

where  $I_2$  = Current through  $R_2$   
 $I_3$  = Current through  $R_3$

The total is 23.35 ma., which checks sufficiently close with 23.4 ma., the current through the whole circuit.

There is a general rule for handling such complex circuits: Reduce the various resistances in parallel or series in *parts* of the circuit to *equivalent* resistances that then can be handled as *single* resistances in a simpler circuit. Eventually this process will lead to a simple series or parallel circuit from which the current and voltage drops can be calculated. Once these are known, Ohm's Law can be applied to each part of the circuit to determine currents and voltage drops in individual resistances.

## POWER AND ENERGY

Power — the rate of doing work — is equal to voltage multiplied by current. The unit of electrical power, called the *watt*, is equal to one volt multiplied by one ampere. The equation for power therefore is

$$P = EI$$

where  $P$  = Power in watts

$E$  = E.m.f. in volts

$I$  = Current in amperes

Common fractional and multiple units for power are the *milliwatt*, one one-thousandth of a watt, and the *kilowatt*, or one thousand watts.

Example: The plate voltage on a transmitting vacuum tube is 2000 volts and the plate current is 350 milliamperes. (The current must be changed to amperes before substitution in the formula, and so is 0.35 amp.) Then

$$P = EI = 2000 \times 0.35 = 700 \text{ watts}$$

By substituting the Ohm's Law equivalents for  $E$  and  $I$ , the following formulas are obtained for power:

$$P = \frac{E^2}{R}$$

$$P = I^2 R$$

These formulas are useful in power calculations when the resistance and either the current or voltage (but not both) are known.

Example: How much power will be used up in a 4000-ohm resistor if the voltage applied to it is 200 volts? From the equation

$$P = \frac{E^2}{R} = \frac{(200)^2}{4000} = \frac{40,000}{4000} = 10 \text{ watts}$$

Or, suppose a current of 20 milliamperes flows through a 300-ohm resistor. Then

$$P = I^2 R = (0.02)^2 \times 300 = 0.0004 \times 300 = 0.12 \text{ watt}$$

Note that the current was changed from milliamperes to amperes before substitution in the formula.

Electrical power in a resistance is turned into heat. The greater the power the more rapidly the heat is generated. We said earlier that if a resistor is to handle considerable power it must be large in size and must be constructed in such a way that the heat will be carried off rapidly by the surrounding air. This prevents the temperature of the resistor from rising to a dangerous point. Resistors for radio work are made in many sizes, the smallest being rated to "dissipate" (or carry safely) about  $\frac{1}{4}$  watt. The largest resistors used in amateur equipment will dissipate about 100 watts.

However, electrical power is not always turned into heat. The power used in running a motor, for example, is converted to mechanical motion. The power supplied to a radio transmitter is largely converted into radio waves. Power applied to a loudspeaker is changed into sound waves. Nevertheless, every electrical device has some resistance, so a part of the power supplied to it is dissipated in that resistance and hence appears as heat even though the major part of the power may be converted to another form.

## Efficiency

In devices such as motors and vacuum tubes, the object is to obtain power in some other form than heat. Therefore power used in heating is considered to be a loss, because it is not the *useful* power. The *efficiency* of a device is the *useful* power output (in its converted form) divided by the power input to the device. In a vacuum-tube transmitter, for example, the object is to convert power from a d.c. source into a.c. power at some radio frequency. The ratio of the r.f. power output to the d.c. input is the efficiency of the tube. That is,

$$Eff. = \frac{P_o}{P_i}$$

where  $Eff.$  = Efficiency (as a decimal)

$P_o$  = Power output (watts)

$P_i$  = Power input (watts)

Example: If the d.c. input to the tube is 100 watts and the r.f. power output is 60 watts, the efficiency is

$$Eff. = \frac{P_o}{P_i} = \frac{60}{100} = 0.6$$

Efficiency is usually expressed as a percentage; that is, it tells what per cent of the input power will be available as useful output. The efficiency in the above example is 60 per cent.

If a resistor is used purely for generating heat — as in an electric heater or cooker — its efficiency is practically 100 per cent, because all of the power input is converted into the desired form of power output. However, generating heat is usually not the desired end when resistors are used in radio equipment. The power losses in them are tolerated because very often a resistor performs a function that could not be conveniently or economically performed by any other device.

### Energy

In residences, the power company's bill is for electric energy, not for power. What you pay for is the *work* that electricity does for you, not the *rate* at which that work is done.

## Capacitance and Condensers

Suppose two flat metal plates are placed close to each other (but not touching) as shown in Fig. 2-8. Normally, the plates will be electrically "neutral"; that is, the number of electrons in each plate will just balance the number of atomic nuclei and there will be no electric charge.

Now suppose that the plates are connected to a battery through a switch, as shown. At the instant the switch is closed, electrons will be attracted from the upper plate to the positive terminal of the battery, and the same number will be repelled into the lower plate from the negative battery terminal. This electron movement will continue until enough electrons move into one plate and out of the other to make the e.m.f. between them the same as the e.m.f. of the battery. (That this must be so should be fairly obvious. The plates are conductors, and when they are connected to the battery, the battery voltage must appear between them.)

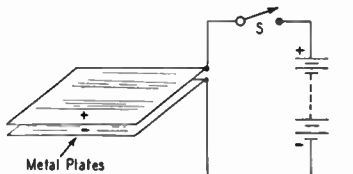


Fig. 2-8 — A simple condenser.

If the switch is opened after the plates have been charged, the top plate is left with a deficiency of electrons and the bottom plate with an excess. In other words, the plates remain charged despite the fact that the battery no longer is connected. They remain charged because with the switch open there is nowhere for the electrons to go. However, if a wire is touched between the two plates (short-circuiting them) the excess electrons on the bottom plate will flow through the wire to the upper plate, thus restoring electrical neutrality to both plates. The plates have then been discharged.

Electrical work is equal to power multiplied by time; the common unit is the **watt-hour**, which means that a power of one watt has been used for one hour. That is,

$$W = PT$$

where  $W$  = Energy in watt-hours

$P$  = Power in watts

$T$  = Time in hours

Other energy units are the **kilowatt-hour** and the **watt-second**. These units should be self-explanatory.

Energy units are seldom used in amateur practice, but it is obvious that a small amount of power used for a long time can eventually result in a "power" bill that is just as large as though a large amount of power had been used for a very short time.

The two plates constitute an electrical condenser, and from the discussion above it should be clear that a condenser possesses the property of storing electricity. It should also be clear that during the time the electrons are moving — that is, while the condenser is being charged or discharged — a *current* is flowing in the circuit even though the circuit is "broken" by the gap between the condenser plates. However, the current flows *only* during the time of charge and discharge, and this time is usually very short. There can be no *continuous* flow of direct current through a condenser.

The charge or quantity of electricity that can be placed on a condenser when a given voltage is applied depends on its **capacitance** or **capacity**. The larger the plate area and the smaller the spacing between the plates the

TABLE 2-III  
Dielectric Constants and Breakdown Voltages

Material	Dielectric Constant	Puncture Voltage*
Air	1.0	19.8-22.8
Alsimag A196	5.7	240
Bakelite (paper-base)	3.8-5.5	650-750
Bakelite (mica-filled)	5-6	475-600
Celluloid	4-16	
Cellulose acetate	6-8	300-1000
Fiber	5-7.5	150-180
Formica	4.6-4.9	450
Glass (window)	7.6-8	200-250
Glass (photographic)	7.5	
Glass (Pyrex)	4.2-4.9	335
Lucite	2.5-3	480-500
Mica	2.5-8	
Mica (clear India)	6.4-7.5	600-1500
Mycalex	7.4	250
Paper	2.0-2.6	1250
Polyethylene	2.3-2.4	1000
Polystyrene	2.4-2.9	500-2500
Porcelain	6.2-7.5	40-100
Rubber (hard)	2-3.5	450
Steatite (low-loss)	4.4	150-315
Wood (dry oak)	2.5-6.8	

\* In volts per mil (0.001 inch).



Fig. 2-9 — A multiple-plate condenser. Alternate plates are connected together.

greater the capacitance. The capacitance also depends upon the kind of insulating material between the plates; it is smallest with air insulation, but substitution of other insulating materials for air may increase the capacitance of a condenser many times. The ratio of the capacitance of a condenser with some material other than air between the plates, to the capacitance of the same condenser with air insulation, is called the **specific inductive capacity** or **dielectric constant** of that particular insulating material. The material itself is called a **dielectric**. The dielectric constants of a number of materials commonly used as dielectrics in condensers are given in Table 2-III. If a sheet of photographic glass is substituted for air between the plates of a condenser, for example, the capacitance of the condenser will be increased 7.5 times.

### Units

The fundamental unit of capacitance is the **farad**, but this unit is much too large for practical work. Capacitance is usually measured in **microfarads** (abbreviated  $\mu\text{fd.}$ ) or **micromicrofarads** ( $\mu\mu\text{fd.}$ ). The microfarad is one-millionth of a farad, and the micromicrofarad is one-millionth of a microfarad. Condensers nearly always have more than two plates, the alternate plates being connected together to form two sets as shown in Fig. 2-9. This makes it possible to attain a fairly large capacitance in a small space as compared to a two-plate condenser, since several plates of smaller individual area can be stacked to form the equivalent of a single large plate of the same total area. Also, all plates, except the two on the ends, are

exposed to plates of the other group on *both sides*, and so are twice as effective in increasing the capacitance.

The formula for calculating the capacitance of a condenser is:

$$C = 0.224 \frac{KA}{d} (n - 1)$$

where  $C$  = Capacitance in  $\mu\mu\text{fd.}$

$K$  = Dielectric constant of material between plates

$A$  = Area of one side of *one* plate in square inches

$d$  = Separation of plate surfaces in inches

$n$  = Number of plates

If the plates in one group do not have the same area as the plates in the other, use the area of the *smaller* plates.

Example: A "variable" condenser has 7 semicircular plates on its rotor, the diameter of the semicircle being 2 inches. The stator has 6 rectangular plates, with a semicircular cut-out to clear the rotor shaft, but otherwise large enough to face the entire area of a rotor plate. The diameter of the cut-out is  $\frac{1}{2}$  inch. The distance between the adjacent surfaces of rotor and stator plates is  $\frac{1}{8}$  inch. The dielectric is air. What is the capacitance of the condenser with the plates fully meshed?


In this case, the "effective" area is the area of the rotor plate minus the area of the cut-out in the stator plate. The area of either semicircle is  $\pi r^2/2$ , where  $r$  is the radius. The area of the rotor plate is  $\pi/2$ , or 1.57 square inches (the radius is 1 inch). The area of the cut-out is  $\pi(\frac{1}{4})^2/2 = \pi/32 = 0.10$  square inch, approximately. The "effective" area is therefore  $1.57 - 0.10 = 1.47$  square inches. The capacitance is therefore

$$C = 0.224 \frac{KA}{d} (n - 1) = 0.224 \frac{1 \times 1.47}{0.125} (13 - 1) \\ = 0.224 \times 11.76 \times 12 = 31.6 \mu\mu\text{fd.}$$

(The answer is only approximate, because of the difficulty of accurate measurement, plus a "fringing" effect at the edges of the plates that makes the actual capacitance a little higher.)

The usefulness of a condenser in electrical circuits lies in the fact that it can be charged

Fixed and variable condensers. The bottom row includes, left to right, a high-voltage mica fixed condenser, a tubular electrolytic, tubular paper, two sizes of "postage-stamp" micas, a small ceramic type (temperature compensating), an adjustable condenser with ceramic insulation (for neutralizing in transmitters), a "button" ceramic condenser, and an adjustable "padding" condenser. Four sizes of variable condensers are shown in the second row. The two-plate condenser with the micrometer adjustment is used in transmitters. The condenser enclosed in the metal case is a high-voltage paper type used in power-supply filters.

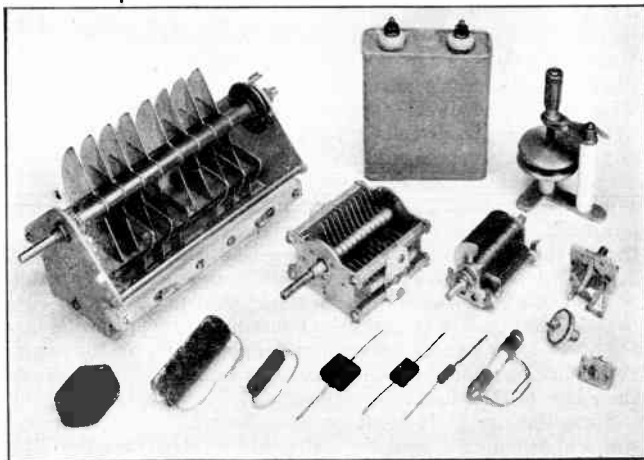

with electricity at one time and then discharged at a later time. In other words, it is capable of storing electrical energy that can be released later when it is needed; it is an "electrical reservoir."

**Condensers in Radio**

The types of condensers used in radio work differ considerably in physical size, construction, and capacitance. Some representative types are shown in the photograph. In "variable" condensers (almost always constructed with air for the dielectric) one set of plates is made movable with respect to the other set so that the capacitance can be varied. "Fixed" condensers — that is, having fixed capacitance — also can be made with metal plates and with air as the dielectric, but usually are constructed from plates of metal foil with a thin solid or liquid dielectric sandwiched in between, so that a relatively large capacitance can be secured in a small unit. The solid dielectrics commonly used are mica and paper. An example of a liquid dielectric is mineral oil, but it is seldom used by itself in present-day condensers. The "electrolytic" condenser uses aluminum-foil plates with a semiliquid conducting chemical compound between them; the actual dielectric is a very thin film of insulating material that "forms" on one set of plates through electrochemical action when a d.c. voltage is applied to the condenser. The capacitance obtained with a given plate area in an electrolytic condenser is very large, compared with condensers having other dielectrics, because the film is so extremely thin — much less than any thickness that is practicable with a solid dielectric.

**Voltage Breakdown**


When a high voltage is applied to the plates of a condenser, a considerable force is exerted on the electrons and nuclei of the dielectric. Because the dielectric is an insulator the electrons do not become detached from atoms the way they do in conductors. However, if the force is great enough the dielectric will "break down"; usually it will puncture and may char (if it is solid) and permit current to flow. The **breakdown voltage** depends upon the kind and thickness of the dielectric, as shown in the table. It is not directly proportional to the thickness; that is, doubling the thickness does not quite double the breakdown voltage. If the dielectric is air or any other gas, breakdown is evidenced by a spark or arc between the plates, but if the voltage is removed the arc ceases and the condenser is ready for use again. Breakdown will occur at a lower voltage between pointed or sharp-edged surfaces than between rounded and polished surfaces; consequently, the breakdown voltage between metal plates of given spacing in air can be increased by buffing the edges of the plates.

Since the dielectric must be thick to withstand high voltages, and since the thicker the


dielectric the smaller the capacitance for a given plate area, a high-voltage condenser must have more plate area than a low-voltage condenser of the same capacitance. High-voltage high-capacitance condensers are physically large. The breakdown voltage of paper-dielectric condensers can be increased by saturating the paper with a special insulating oil and by immersing the condenser in oil. Electrolytic condensers can stand 400 to 500 volts before the dielectric film breaks down.

● **CONDENSERS IN SERIES AND PARALLEL**

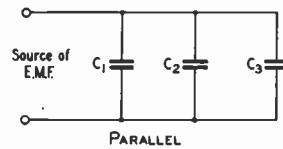The terms "parallel" and "series" when used with reference to condensers have the same circuit meaning as with resistances. When



PARALLEL

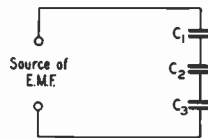

SERIES

Fig. 2-10 — Condensers in series and parallel.

a number of condensers are connected in parallel, as in Fig. 2-10, the total capacitance of the group is equal to the sum of the individual capacitances, so

$$C \text{ (total)} = C_1 + C_2 + C_3 + C_4 + \dots$$

However, if two or more condensers are connected in series, as in the second drawing, the total capacitance is less than that of the smallest condenser in the group. The rule for finding the capacitance of a number of series-connected condensers is the same as that for finding the resistance of a number of parallel-connected resistors. That is,

$$C \text{ (total)} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \dots}$$

and, for only two condensers in series,

$$C \text{ (total)} = \frac{C_1 C_2}{C_1 + C_2}$$

The same units must be used throughout; that is, all capacitances must be expressed in either  $\mu\text{fd.}$  or  $\mu\mu\text{fd.}$ ; you cannot use both units in the same equation.

Condensers are connected in parallel to obtain a larger total capacitance than is available in one unit. The largest voltage that can be applied safely to a group of condensers in parallel

is the voltage that can be applied safely to the condenser having the *lowest* voltage rating.

When condensers are connected in series, the applied voltage is divided up among the various condensers; the situation is much the same as when resistors are in series and there is a voltage drop across each. However, the voltage that appears across each condenser of a group connected in series is in *inverse* proportion to its capacitance, as compared with the capacitance of the whole group.

Example: Three condensers having capacitances of 1, 2 and 4  $\mu\text{fd.}$ , respectively, are connected in series as shown in Fig. 2-11. The total capacitance is

$$C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} = \frac{1}{\frac{1}{1} + \frac{1}{2} + \frac{1}{4}} = \frac{1}{\frac{7}{4}} = \frac{4}{7} \\ = 0.571 \mu\text{fd.}$$

The voltage across each condenser is proportional to the *total* capacitance divided by the capacitance of the condenser in question, so the voltage across  $C_1$  is

$$E_1 = \frac{0.571}{1} \times 2000 = 1142 \text{ volts}$$

Similarly, the voltages across  $C_2$  and  $C_3$  are

$$E_2 = \frac{0.571}{2} \times 2000 = 571 \text{ volts}$$

$$E_3 = \frac{0.571}{4} \times 2000 = 286 \text{ volts}$$

totaling approximately 2000 volts, the applied voltage.

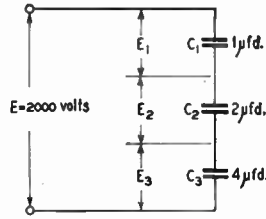


Fig. 2-11 — An example of condensers connected in series. The solution to this arrangement is worked out in the text.

Condensers are frequently connected in series to enable the group to withstand a larger voltage (at the expense of decreased total capacitance) than any individual condenser is rated to stand. One very common application of this arrangement is in the filter circuits of high-voltage power supplies. However, as shown by the previous example, the applied voltage does not divide equally among the condensers (except when all the capacitances are the same) so care must be taken to see that the voltage rating of no condenser in the group is exceeded. It does no good, for example, to connect a condenser in series with another if the capacitance of the second is many times as great as the first; nearly all of the voltage still will appear across the condenser having the smaller capacitance.

## Inductance

It is possible to show that the flow of current through a conductor is accompanied by magnetic effects; a compass needle brought near the conductor, for example, will be deflected from its normal north-south position. The stronger the current, the more pronounced is the magnetic effect. The current, in other words, sets up a magnetic field.

If a wire conductor is formed into a coil, the same current will set up a stronger magnetic field than it will if the wire is straight. Also, if the wire is wound around an iron or steel "core" the field will be still stronger. The relationship between the strength of the field and the intensity of the current causing it is expressed by the **inductance** of the conductor or coil. If the same current flows through two coils, for example, and it is found that the magnetic field set up by one coil is twice as strong as that set up by the other, the first coil has twice as much inductance as the second. Inductance is a property of the conductor or coil and is determined by its shape and dimensions. The unit of inductance (corresponding to the ohm for resistance and the farad for capacitance) is the **henry**.

If the current through a conductor or coil is made to vary in intensity, it is found that an e.m.f. will appear across the terminals of the conductor or coil. This e.m.f. is entirely separate from the e.m.f. that is causing the current

to flow. The strength of this "induced" e.m.f. becomes greater, the greater the intensity of the magnetic field and the more rapidly the current (and hence the field) is made to vary. Since the intensity of the magnetic field depends upon the inductance, the induced voltage (for a given current intensity and rate of variation) is proportional to the inductance of the conductor or coil.

The fact that an e.m.f. is "induced" accounts for the name "inductance" — or "self-inductance" as it is sometimes called. The induced e.m.f. tends to send a current through the circuit in the *opposite* direction to the current that flows because of the external e.m.f. so long as the latter current is *increasing*. However, if the current caused by the applied e.m.f. *decreases*, the induced e.m.f. tends to send current through the circuit in the *same* direction as the current from the applied e.m.f. The effect of inductance, therefore, is to oppose any *change* in the current flowing in the circuit, regardless of the nature of the change. It accomplishes this by storing energy in its magnetic field when the current in the circuit is being increased, and by releasing the stored energy when the current is being decreased. The effect is the same as the mechanical inertia that prevents an automobile from instantly coming up to speed when the accelerator pedal is pressed, and that prevents it from coming to

an instant stop when the brakes are applied.

The values of inductance used in radio equipment vary over a wide range. Inductance of several henrys is required in power-supply circuits (see chapter on Power Supply) and to obtain such values of inductance it is necessary to use coils of many turns wound on iron cores. In radio-frequency circuits, the inductance values used will be measured in **millihenrys** (a millihenry is one one-thousandth of a henry) at low frequencies, and in **microhenrys** (one one-millionth of a henry) at medium frequencies and higher. Although coils for radio frequencies may be wound on special iron cores (ordinary iron is not suitable) most r.f. coils made and used by amateurs are the "air-core" type; that is, wound on an insulating form consisting of nonmagnetic material.

**Inductance Formula**

The inductance of air-core coils may be calculated from the formula

$$L (\mu h.) = \frac{0.2 a^2 n^2}{3a + 9b + 10c}$$

- where  $L$  = Inductance in microhenrys
- $a$  = Average diameter of coil in inches
- $b$  = Length of winding in inches
- $c$  = Radial depth of winding in inches
- $n$  = Number of turns

The notation is explained in Fig. 2-12. The quantity  $c$  may be neglected if the coil only has one layer of wire.

Example: Assume a coil having 35 turns of No. 30 d.s.c. wire on a form 1.5 inches in diameter. Consulting the wire table (Chapter 24), 35 turns of No. 30 d.s.c. will occupy 0.5 inch. Therefore,  $a = 1.5$ ,  $b = 0.5$ ,  $n = 35$ , and

$$L = \frac{0.2 \times (1.5)^2 \times (35)^2}{(3 \times 1.5) + (9 \times 0.5)} = 61.25 \mu h.$$

To calculate the number of turns of a single-layer coil for a required value of inductance:

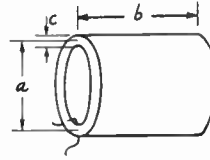


Fig. 2-12 — Coil dimensions used in the inductance formula.

$$N = \sqrt{\frac{3a + 9b}{0.2a^2} \times L}$$

Example: Suppose an inductance of 10 microhenrys is required. The form on which the coil is to be wound has a diameter of one inch and is long enough to accommodate a coil length of 1 1/4 inches. Then  $a = 1$ ,  $b = 1.25$ , and  $L = 10$ . Substituting,


$$N = \sqrt{\frac{(3 \times 1) + (9 \times 1.25)}{0.2 \times 1^2} \times 10}$$

$$= \sqrt{\frac{14.25}{0.2} \times 10} = \sqrt{712.5}$$

$$= 26.6 \text{ turns.}$$

A 27-turn coil would be close enough to the required value of inductance, in practical work. Since the coil will be 1.25 inches long, the number of turns per inch will be  $27/1.25 = 21.6$ . Consulting the wire table, we find that No. 18 enameled wire (or any smaller size) can be used. We obtain the proper inductance by winding the required number of turns on the form and then adjusting the spacing between the turns to make a uniformly-spaced coil 1.25 inches long.

Every conductor has inductance, even though the conductor is not formed into a coil. The inductance of a short length of straight wire is small — but it may not be negligible, because if the current through it changes its intensity rapidly enough the induced voltage may be appreciable. This will be the case in even a few inches of wire when an alternating current having a frequency of the order of 100 Mc. is flowing. However, at much lower frequencies the inductance of the same wire could be left out of any calculations because the induced voltage would be negligibly small.

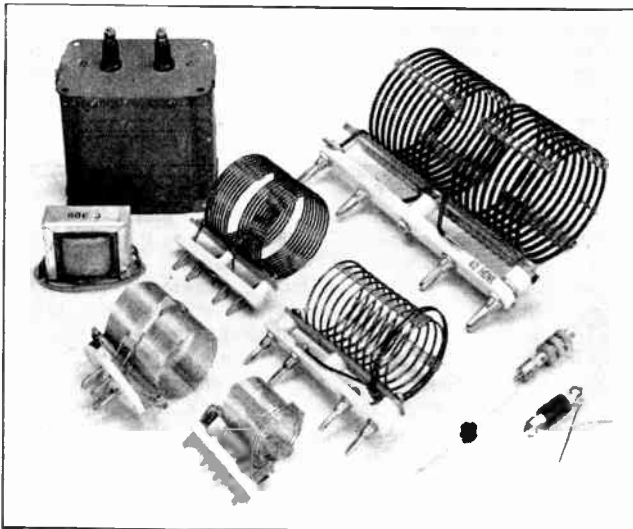

Inductance coils for power and radio frequencies. The two iron-core coils at the upper left are "chokes" for power-supply filters. The three "pic"-wound coils at the lower right are used as chokes in radio-frequency circuits. The other coils are for r.f. tuned circuits ranging in power from 25 watts to a kilowatt.



## ● IRON-CORE COILS

We mentioned earlier that the inductance of a coil wound on an iron core is much greater than the inductance of the same coil wound on a nonmagnetic core. As a crude analogy, iron has a much lower "resistance" to the magnetic force than nonferrous materials, just as metals have much lower resistance to the flow of electric current than nonmetallic substances.

### Permeability

For example, suppose that the coil in Fig. 2-13 is wound on an iron core having a cross-sectional area of 2 square inches. When a certain current is sent through the coil it is found that there are 80,000 lines of force in the core. Since the area is 2 square inches, the flux density is 40,000 lines per square inch. Now suppose that the iron core is removed and the same current is maintained in the coil, and that the flux density without the iron core is found to be 50 lines per square inch. The ratio of the flux density with the given core material to the flux density (with the same coil and same current) with an air core is called the **permeability** of the material. In this case the permeability of the iron is  $40,000/50 = 800$ . The inductance of the coil is increased 800 times by inserting the iron core, therefore.

The permeability of a magnetic material is not constant, unfortunately, but varies with the flux density. At low flux densities (or with an air core) increasing the current through the coil will cause a proportionate increase in flux. For example, if there are 2000 lines per square inch at a given current, doubling the current will increase the flux density to 4000 lines per square inch. But this cannot be carried on indefinitely; at some value of flux density, depending upon the kind of iron, it will be found that doubling the current only increases the flux density by, say, 10 per cent. At very high flux densities, increasing the current may cause no appreciable change in the flux at all. When this is so, the iron is said to be **saturated**. "Saturation" causes a rapid decrease in permeability, because it decreases the ratio of flux lines to those obtainable with the same current and an air core. Obviously, the inductance of an iron-core coil is highly dependent upon the current flowing in the coil. In an air-core coil, the inductance is independent of current because air does not "saturate."

In amateur work, iron-core coils such as the one sketched in Fig. 2-13 are used chiefly in power-supply equipment. They usually have direct current flowing through the winding, and the variation in inductance with current is usually undesirable. It may be overcome by keeping the flux density below the saturation point of the iron. This is done by cutting the core so that there is a small "air gap," as indicated by the dashed lines. The magnetic "resistance" introduced by such a gap is so large

— even though the gap is only a small fraction of an inch — compared with that of the iron that the gap, rather than the iron, controls the flux density. This naturally reduces the inductance compared to what it would be without the air gap — but only for *small* currents. It actually results in a *higher* inductance when the current is large; furthermore, the inductance is practically constant regardless of the value of the current. Further information on the construction of such inductance coils will be found in the chapter on Power Supply.

### Eddy Currents and Hysteresis

When alternating current flows through a coil wound on an iron core the magnetic flux in the core goes through variations in intensity and direction that correspond to the variations in the alternating current. Variations in a magnetic field cause an e.m.f. to be induced, as previously explained, and since iron is a conductor a current will flow in the core. Such currents (called **eddy currents**) represent a waste of power because they flow through the resistance of the iron and thus cause heating. Eddy-current losses can be reduced by **laminating** the core; that is, by cutting it into thin strips. These strips or **laminations** must be insulated from each other by painting them with some insulating material such as varnish or shellac.

There is also another type of energy loss in an iron core: the iron tends to resist any change in its magnetic state, so a rapidly-changing current such as a.c. is forced continually to supply energy to the iron to overcome this "inertia." Losses of this sort are called **hysteresis** losses.

Eddy-current and hysteresis losses in iron increase rapidly as the frequency of the alternating current is increased. For this reason, we can use ordinary iron cores only at power and audio frequencies — up to, say, 15,000 cycles. Even so, a very good grade of iron or steel is necessary if the core is to perform well at the higher audio frequencies. Iron cores of this type are completely useless at radio frequencies.

For radio-frequency work, the losses in iron cores can be reduced to a satisfactory figure by grinding the iron into a powder and then mixing it with a "binder" of insulating material in such a way that the individual iron particles are insulated from each other. By this means cores can be made that will function satisfac-

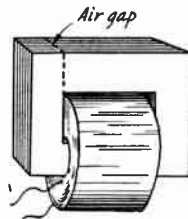


Fig. 2-13 — Typical construction of an iron-core coil. The small air gap prevents magnetic saturation of the iron and increases the inductance at high currents.

torily even through the v.h.f. range — that is, at frequencies up to perhaps 100 Mc. Because a large part of the magnetic path is through a nonmagnetic material, the permeability of the iron is low compared to the values obtained at power-supply frequencies. The core is usually in the form of a “slug” or cylinder which fits inside the insulating form on which the coil is wound. Despite the fact that, with this construction, the major portion of the magnetic path for the flux is in the air surrounding the coil, the slug is quite effective in increasing the coil inductance. By pushing the slug in and out of the coil the inductance can be varied over a considerable range.

● INDUCTANCES IN SERIES AND PARALLEL

When two or more inductance coils (or inductors, as they are frequently called) are connected in series (Fig. 2-14, left) the total inductance is equal to the sum of the individual inductances, *provided the coils are sufficiently separated so that no coil is in the magnetic field of another.* That is,

$$L_{\text{total}} = L_1 + L_2 + L_3 + L_4 + \dots$$

If inductances are connected in parallel (Fig. 2-14, right), the total inductance is

$$L_{\text{total}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4} + \dots}$$

and for two inductances in parallel,

$$L = \frac{L_1 L_2}{L_1 + L_2}$$

Thus the rules for combining inductances in series and parallel are the same as for resistances, *if the coils are far enough apart so that each is unaffected by another's magnetic field.* When this is not so the formulas given above cannot be used.

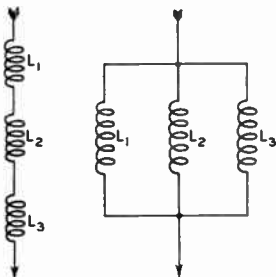


Fig. 2-14 — Inductances in series and parallel.

In calculating the total inductance of a combination of iron-core coils to be used in a d.c. circuit, it must be remembered that the inductance of each coil may change with the amount of current that flows through it. With air-core coils there is no such change.

Although there is frequent occasion to combine resistances or capacitances in series or

parallel in amateur work, there is relatively little necessity for such combinations of inductances — or rather, the cases that do arise in practice seldom require calculations.

● MUTUAL INDUCTANCE

If two coils are arranged with their axes on the same line, as shown in Fig. 2-15, a current sent through Coil 1 will cause a magnetic field which “cuts” Coil 2. Consequently, an e.m.f. will be induced in Coil 2 whenever the field strength is changing. This induced e.m.f. is similar to the e.m.f. of self-induction, but since it appears in the *second* coil because of current flowing in the *first*, it is a “mutual” effect and

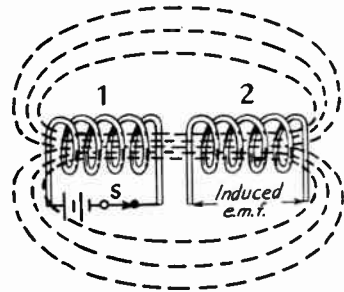


Fig. 2-15 — Mutual inductance. When the switch, S, is closed current flows through coil No. 1, setting up a magnetic field that induces an e.m.f. in the turns of coil No. 2.

results from the **mutual inductance** between the two coils.

Mutual inductance may be large or small, depending upon the self-inductances of the coils and the proportion of the flux set up by one coil that cuts the turns of the other coil. If all the flux set up by one coil cuts all the turns of the other coil the mutual inductance has its maximum possible value. If only a small part of the flux set up by one coil cuts the turns of the other the mutual inductance is relatively small. Two coils having mutual inductance are said to be **coupled**.

The ratio of actual mutual inductance to the maximum possible value that could be obtained with two given coils is called the **coefficient of coupling** between the coils. Coils that have nearly the maximum possible mutual inductance are said to be **closely**, or **tightly**, coupled, but if the mutual inductance is relatively small the coils are said to be **loosely** coupled. The degree of coupling depends upon the physical spacing between the coils and how they are placed with respect to each other. Maximum coupling exists when they have a common axis, as shown in Fig. 2-15, and are as close together as possible. The coupling is least when the coils are far apart or are placed so their axes are at right angles.

The maximum possible coefficient of cou-

pling is 1. This value is closely approached only when the two coils are wound on a closed iron core. The coefficient with air-core coils may run as high as 0.6 or 0.7 if one coil is wound over the other, but will be much less if the two coils are separated.

If two coils having mutual inductance are connected to the same source of current, the magnetic field of one coil can either aid or oppose the field of the other. In the former case

the mutual inductance is said to be "positive"; in the latter case, "negative." Positive mutual inductance means that the total inductance is *greater* than the sum of the two individual inductances. Negative mutual inductance means that the total inductance is *less* than the sum of the two individual inductances. The mutual inductance may be made either positive or negative simply by reversing the connections to *one* of the coils.

## Time Constant

Both inductance and capacitance possess the property of storing energy — inductance stores magnetic energy and capacitance stores electrical energy. In the case of inductance, electrical energy is converted into magnetic energy when the current through the inductance is increasing, and the magnetic energy is converted back into electrical energy (and thereby restored to the circuit) when the current is decreasing. It is this alternate storing and releasing of energy that makes inductance oppose a change in the current through it. The self-induced e.m.f. is the means by which energy is put into and taken out of the magnetic field.

In the case of capacitance, energy is stored in the condenser (actually in the electric field between the plates) whenever the voltage applied to the condenser is increasing, and restored to the circuit when the applied voltage is decreasing. That is, current flows *into* the condenser in the first case, and *out* of the condenser in the second.

### Capacitance and Resistance

In Fig. 2-16A a battery having an e.m.f.,  $E$ , a switch,  $S$ , a resistor,  $R$ , and condenser,  $C$ , are connected in series. Suppose for the moment that  $R$  has zero resistance — in other words, is short-circuited — and also that there is no other resistance in the circuit. If  $S$  is now closed, condenser  $C$  will charge *instantly* to the battery voltage; that is, the electrons that constitute the charge redistribute themselves in a time interval so small that it can be considered to be zero. As soon as the condenser is fully charged the current flow stops completely. But since the condenser became fully charged in zero time, the current during the instantaneous charge must have been very large; mathemati-

cally, it would be *infinitely* large if the time actually was zero — this regardless of the actual number of electrons that moved. At the instant of closing the switch, therefore, the condenser can be considered to have a "resistance" of zero, a resistance that becomes an open circuit the instant the charge is complete.

If a finite value of resistance,  $R$ , is put into the circuit the condenser no longer can be charged instantaneously. If the condenser is initially uncharged, it will have zero "resistance" at the instant  $S$  is closed, but now the amount of current that can flow is limited by  $R$ . The infinitely-large current required to charge the condenser in zero time cannot flow through  $R$ , because even with  $C$  considered as a short-circuit the current in the circuit as a whole will be determined by Ohm's Law. If the battery e.m.f. is 100 volts, for example, and  $R$  is 10 ohms, the maximum current that can flow with  $C$  short-circuited is 10 amperes. Even this much current can flow *only* at the very instant the switch is closed. As soon as *any* current flows, condenser  $C$  begins to acquire a charge, which means that the voltage across the condenser plates rises. Since the upper plate (in Fig. 2-16A) will be positive and the lower negative, the voltage on the condenser tends to send a current through the circuit in the opposite direction to the current from the battery. The voltage on the condenser, in other words, opposes the battery voltage. Immediately after the switch is closed, therefore, the current drops below its initial Ohm's Law value, and as the condenser continues to acquire charge and its potential rises, the current becomes smaller and smaller.

The length of time required to complete the charging process depends upon the capacitance of the condenser and the resistance in the circuit. More time is taken if either of these quantities is made larger. Theoretically, the charging process is never really finished, but practically the current eventually drops to a value that is smaller than anything that can be measured. The time constant of such a circuit is the length of time, in seconds, required for the voltage across the condenser to reach 63 per cent of the applied e.m.f. (this figure is chosen for mathematical reasons). The voltage

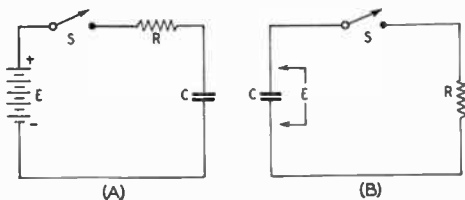


Fig. 2-16 — Schematics illustrating the time constant of an RC circuit.

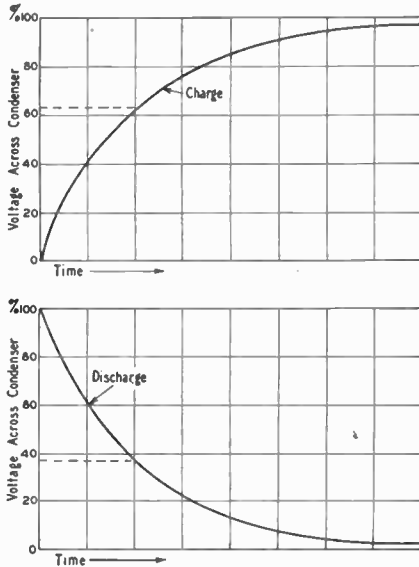


Fig. 2-17 — How the voltage across a condenser rises, with time, when a condenser is charged through a resistor. The lower curve shows the way in which the voltage decreases across the condenser terminals on discharging through the same resistor.

across the condenser rises logarithmically, as shown by Fig. 2-17.

The formula for time constant is

$$T = CR$$

where  $T$  = Time constant in seconds  
 $C$  = Capacitance in farads  
 $R$  = Resistance in ohms

If  $C$  is in microfarads and  $R$  in megohms, the time constant also is in seconds. The latter units usually are more convenient.

Example: The time constant of a 2- $\mu$ fd. condenser and a 250,000-ohm resistor is

$$T = CR = 2 \times 0.25 = 0.5 \text{ second}$$

If the applied e.m.f. is 1000 volts, the voltage across the condenser plates will be 630 volts at the end of  $\frac{1}{2}$  second.

If a charged condenser is *discharged* through a resistor, as indicated in Fig. 2-16B, the same time constant applies. If there were no resistance, the condenser would discharge *instantly* when  $S$  was closed, and for *instantaneous* discharge the current would have to be infinitely large. However, if  $R$  is present the current cannot exceed the value given by Ohm's Law, where  $E$  is the voltage to which the condenser is charged and  $R$  is the resistance. Since  $R$  limits the current flow, the condenser voltage cannot instantly go to zero, but it will decrease just as rapidly as the condenser can rid itself of its charge through  $R$ . When the condenser is discharging through a resistance, the time constant (calculated in the same way as above) is the time (in seconds) that it takes for the condenser to *lose* 63 per cent of its

voltage; that is, for the voltage to drop to 37 per cent of its initial value.

Example: If the condenser of the example above is charged to 1000 volts, it will discharge to 370 volts in  $\frac{1}{2}$  second through the 250,000-ohm resistor.

### Inductance and Resistance

A comparable situation exists when resistance and inductance are in series. In Fig. 2-18, first consider  $L$  to have no resistance (which would be impossible, since the conductor of which it is composed always has resistance) and also assume that  $R$  is zero. Then closing  $S$  would tend to send a current through the circuit. However, the instantaneous transition from no current to a finite value, however small, represents a very rapid *change* in current, and a back e.m.f. is developed by the self-inductance of  $L$  that is practically equal and opposite to the applied e.m.f. The result is that the initial current is very small. However, the back e.m.f. depends upon the *change* in current and would cease to offer opposition if the current did not *continue* to increase. With no resistance in the circuit (which would lead to an infinitely-large current, by Ohm's Law) the current would increase forever, always increasing just fast enough to keep the e.m.f. of self-induction equal to the applied e.m.f. Since such a circuit never would "settle down," the time constant of an inductive circuit without resistance is infinitely long.

When resistance is in series, Ohm's Law sets a limit to the value that the current can reach. In such a circuit the current is small at first, just as in our hypothetical case without resistance. But as the current increases the voltage drop across  $R$  becomes larger. The back e.m.f. generated in  $L$  has only to equal the *difference* between  $E$  and the drop across  $R$ , because that difference is the voltage actually applied to  $L$ . This difference becomes smaller as the current approaches the final Ohm's Law value. Theoretically, the back e.m.f. never quite disappears (that is, the current never quite reaches the Ohm's Law value) but practically it becomes unmeasurable after a time. The difference between the actual current and the Ohm's Law value also becomes undetectable. The time required for this to occur is greater the larger the value of  $L$ , and is shorter the larger  $R$  is made. The time constant of an inductive circuit is the time in seconds required for the current to reach 63 per cent of its final value. The formula is,

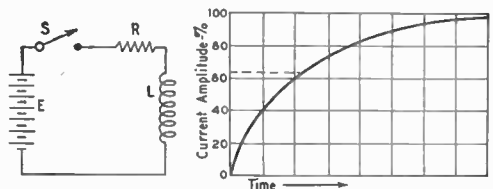


Fig. 2-18 — Time constant of an LR circuit.

$$T = \frac{L}{R}$$

where  $T$  = Time constant in seconds  
 $L$  = Inductance in henrys  
 $R$  = Resistance in ohms

The resistance of the wire in a coil acts as though it were in series with the inductance.

Example: A coil having an inductance of 20 henrys and a resistance of 100 ohms has a time constant of

$$T = \frac{L}{R} = \frac{20}{100} = 0.2 \text{ second}$$

if there is no other resistance in the circuit. If a d.c. e.m.f. of 10 volts is applied to such a coil, the final current, by Ohm's Law, is

$$I = \frac{E}{R} = \frac{10}{100} = 0.1 \text{ amp. or } 100 \text{ ma.}$$

The current would rise from zero to 63 milliamperes in 0.2 second after closing the switch.

An inductor cannot be discharged in the same way as a condenser, because the magnetic field disappears as soon as current flow ceases. Opening  $S$  does not leave the inductor "charged." The energy stored in the magnetic field instantly returns to the circuit when  $S$  is opened. The rapid disappearance of the

field causes a very large voltage to be induced in the coil — ordinarily many times larger than the voltage applied, because the induced voltage is proportional to the *speed* with which the field changes. The common result of opening the switch in a circuit such as the one shown is that a spark or arc forms at the switch contacts at the instant of opening. If the inductance is large and the current in the circuit is high, a great deal of energy is released in a very short period of time. It is not at all unusual for the switch contacts to burn or melt under such circumstances.

"Filter" circuits used in power-supply equipment represent an excellent example of the application of the  $CR$  or  $L/R$  time constant to practical work, although calculations of the type illustrated above are seldom necessary with such circuits. An understanding of the principles also is necessary in numerous special devices that are coming into widespread use in amateur stations, such as electronic keys, shaping of keying characteristics by vacuum tubes, and timing devices and control circuits. The time constants of circuits are also important in such applications as automatic gain control and noise limiters.

## Alternating Currents

### ● PHASE

You cannot really understand alternating currents until you have a clear picture of **phase**. Essentially it means "time," or the *time interval* between the instant when one thing occurs and the instant when a second related thing takes place. As a homely example, when a baseball pitcher throws the ball to the catcher there is a definite interval, represented by the time of flight of the ball, between the act of throwing and the act of catching. The throwing and catching are therefore "out of phase" because they do not occur at exactly the same time.

Time differences are measured in seconds, minutes, hours, and so on. In the baseball example the ball might be in the air two seconds, in which case it could be said that the throwing and catching were out of phase by two seconds. However, simply saying that two events are out of phase does not tell us which one occurred first. To give this information, the later event is said to lag the first in phase, while the one that occurs first is said to lead. Thus, throwing the ball "leads" the catch by two seconds, or the catch "lags" the throw by two seconds.

In a.c. circuits the current amplitude changes continuously, so the concept of phase or time obviously has utility whenever it becomes necessary to specify the value of the current at a particular instant. Phase can be measured

in the ordinary time units, such as the second, but there is a more convenient method: since each a.c. cycle occupies exactly the same amount of time as every other cycle of the same frequency, we can use the cycle itself as the time unit. When this is done it does not matter whether one cycle lasts for a sixtieth of a second or for a millionth of a second so long as *all the cycles are the same*. In other words, using the cycle as the time unit makes the specification or measurement of phase independent of the frequency of the current, so long as only one frequency is under consideration at a time. If there are two or more frequencies, the measurement of phase has to be modified just as the measurements of two lengths must be reconciled if one is given in feet and the other in meters.

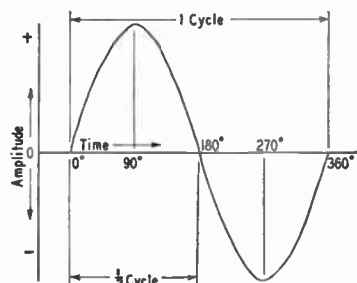


Fig. 2-19 — An a.c. cycle is divided off into 360 degrees that are used as a measure of time or phase.

The time interval or "phase difference" under consideration usually will be less than one cycle. Phase difference could be measured in decimal parts of a cycle, but for many reasons it is more convenient to divide the cycle into 360 parts or degrees. A phase degree is therefore  $1/360$  of a cycle. (The reason for this choice of unit is this: In a sine-wave alternating current, the value of the current at any instant is proportional to the sine of the angle that corresponds to the number of degrees — that is, length of time — from the time the cycle began. There is of course no actual "angle" associated with an alternating current.) Fig. 2-19 should help make this method of measurement clear.

### Measuring Phase

In a steady alternating current each cycle is exactly like the preceding one. To compare the phase of two currents of the same frequency, we measure between corresponding parts of cycles of the two currents. This is shown in Fig. 2-20. The current labeled *A* leads the one marked *B* by 45 degrees, since *A*'s cycles begin 45 degrees sooner in time. (It is equally correct to say that *B* lags *A* by 45 degrees.) The amplitudes of the individual currents do not affect their relative phases — current *B* is shown as having smaller amplitude than *A*. Regardless of the amplitudes, the lagging current always would begin its cycle (the start of the cycle is considered to be the point at which it is passing through zero and starting to increase in the positive direction) the same number of degrees after the current that leads begins its cycle.

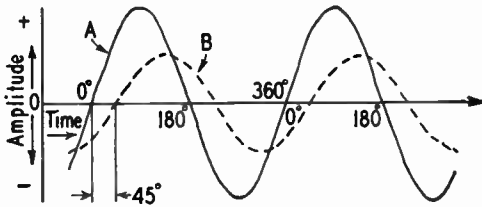


Fig. 2-20 — When two waves of the same frequency start their cycles at slightly different times, the time difference or phase difference is measured in degrees. In this drawing wave *B* starts 45 degrees (one-eighth cycle) later than wave *A*, and so lags 45 degrees behind *A*.

Two important special cases are shown in Fig. 2-21. In the upper drawing *B* lags 90 degrees behind *A*; that is, its cycle begins just one-quarter cycle later than that of *A*. When one wave is passing through zero, the other is just at its maximum point. Note that (using *A* as a reference) in the first quarter cycle *A* is positive and *B* is negative; in the second quarter cycle both *A* and *B* are positive, but one is decreasing while the other is increasing; in the third quarter cycle *A* is negative while *B* is positive; and in the last quarter cycle both are negative.

In the lower drawing *A* and *B* are 180 degrees out of phase. In this case it does not matter which one we consider to lead or lag. *B* is always positive while *A* is negative, and vice versa. The two waves are thus *completely* out of phase.

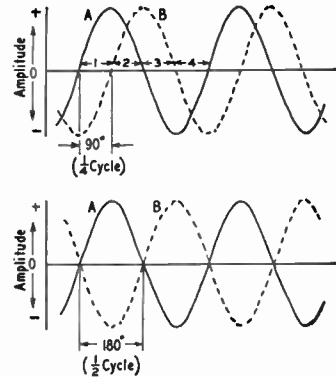


Fig. 2-21 — Two important special cases of phase difference. In the upper drawing, the phase difference between *A* and *B* is 90 degrees; in the lower drawing the phase difference is 180 degrees.

The waves shown in Figs. 2-20 and 2-21 could represent current, voltage, or both. *A* and *B* might be two currents in separate circuits, or *A* might represent voltage while *B* represented current in the same circuit. If *A* and *B* represent two currents in the *same* circuit (or two voltages in the same circuit) the *actual* current (or voltage) would take a *single* value at any instant. This value would equal the sum of the two at that instant. (We must take into account the fact that the sum of positive and negative values is actually equal to the *difference* between them.) The resultant current (or voltage) also is a sine wave, because adding any number of sine waves of the same frequency always results in a sine wave also of the same frequency.

## ● REACTANCE

The discussion of capacitance and inductance earlier in this chapter was confined to cases where only d.c. voltages were applied. To understand what happens in a condenser or inductance when an *a.c.* voltage is applied, it is necessary to become acquainted with a fundamental *definition* of electric current (as contrasted to the physical *description* of current given earlier). By definition, the amplitude of an electric current is the *rate* at which electric charge is moved past a point in a circuit. If a large quantity of charge moves past the observing point in a given time, the current is large; if the quantity is small in the same amount of time, the current is small.

### Alternating Current in Condensers

The quantity of charge that can be placed on a condenser of given capacitance is propor-

tional to the voltage applied to the condenser. As we explained earlier, the condenser becomes charged *instantly* if there is no resistance in the circuit. Suppose a sine-wave a.c. voltage is applied to a condenser in a circuit containing no resistance, as indicated in Fig. 2-22. For convenience, the first half-cycle of the applied voltage is divided into eight equal time intervals. In the period *OA*, the voltage increases from zero to 38 volts; at the end of this period the condenser is charged to that voltage. In the next interval the voltage increases to 71 volts; that is, 33 volts additional. In this second interval a *smaller* quantity of charge has been added than in the first interval, because the voltage rise during the second interval was smaller. Consequently the average current during the second interval is smaller than during the first. In the third interval, *BC*, the voltage rises from 71 to 92 volts, an increase of 21 volts. This is less than the voltage increase during the second interval, so the quantity of electricity added to the charge during the third interval is less than the quantity added during the second. In other words, the average current during the third interval is still smaller. In the fourth interval, *CD*, the voltage increases only 8 volts; the charge added is smaller than in any preceding interval and therefore the current also is smaller. By dividing the first quarter cycle into a very large number of intervals it could be shown that the current charging the condenser has the shape of a sine wave, just as the applied voltage does. But the current is largest at the beginning of the cycle and becomes zero at the maximum value of the voltage (the condenser cannot be charged to a higher voltage than the maximum applied, so no further current can flow) so there is a phase difference of 90 degrees between the voltage and current. During the first quarter cycle of the applied voltage the current is flowing in the normal way through the circuit, since the condenser is being charged. Hence the current is positive during this first quarter cycle, as indicated by the dashed line in Fig. 2-22.

In the second quarter cycle — that is, in the time from *D* to *H*, the voltage applied to the

condenser decreases. During this time the condenser *loses* the charge it acquired during the first quarter cycle. Applying the same reasoning, it is plain that the current is small from *D* to *E* and continues to increase during each succeeding interval. However, the current is flowing *against* the applied voltage because the condenser is *discharging into the circuit*. Hence the current is *negative* during this quarter cycle.

The third and fourth quarter cycles repeat the events of the first and second, respectively, with this difference — the polarity of the applied voltage has reversed, and the current changes to correspond. In other words, *an alternating current flows through a condenser when an a.c. voltage is applied to it*. As shown by Fig. 2-22, the current starts its cycle 90 degrees before the voltage, so the current in a condenser *leads the applied voltage by 90 degrees*.

### Capacitive Reactance

Remembering the definition of current as given at the beginning of this section, as well as the mechanism of current flow described above, it should be plain that the more rapid the voltage rise the larger the current, because a rapid change in voltage means a rapid transfer of charge into or out of the condenser. The rapidity with which the voltage changes depends upon two things: (1) the amplitude of the voltage (the greater the maximum value, the faster the voltage must rise from zero to reach that maximum in the time of one-quarter cycle if the frequency is fixed); (2) the frequency (the higher the frequency, the more rapidly the voltage goes through its changes in a given time if the maximum amplitude is fixed). Also, the amplitude of the current depends upon the capacitance of the condenser, because the larger the capacitance the greater the amount of charge transferred during a given change in voltage.

The fact that the current flowing through a condenser is directly proportional to the applied a.c. voltage is extremely important. It is exactly what Ohm's Law says about the flow of direct current in a resistive circuit, and so leads us to the conclusion that Ohm's Law may be applied to an alternating-current circuit containing a condenser. Of course, a condenser does not offer "resistance" to the flow of alternating current, because the condenser does not consume power as a resistor does. It merely stores energy in one part of the cycle and returns it to the circuit in the next part. Furthermore, the larger the capacitance the larger the current; this is just the opposite of what we expect with resistance. And finally, the "opposition" offered by a condenser to alternating current depends on the *frequency* of that current. But with a given capacitance and a given frequency, the condenser follows Ohm's Law on a.c.

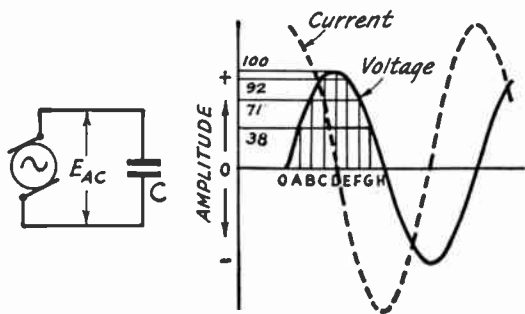


Fig. 2-22 — Voltage and current phase relationships when an alternating voltage is applied to a condenser.

Since the opposition effect of a condenser is not resistance, it is called by another name, **reactance**. But because reactance holds back current flow in a similar fashion to resistance, the unit of reactance also is the ohm. The reactance of a condenser is

$$X_c = \frac{1}{2\pi fC}$$

where  $X_c$  = Condenser reactance in ohms  
 $f$  = Frequency in cycles per second  
 $C$  = Capacitance in farads  
 $\pi = 3.14$

The fundamental units (cycles per second, farads) are too large for practical use in radio circuits. However, if the capacitance is in microfarads and the frequency is in megacycles, the reactance will come out in ohms in the formula.

Example: The reactance of a condenser of 470  $\mu\text{fd.}$  (0.00047  $\mu\text{fd.}$ ) at a frequency of 7150 kc. (7.15 Mc.) is

$$X = \frac{1}{2\pi fC} = \frac{1}{6.28 \times 7.15 \times 0.00047} = 47.4 \text{ ohms}$$

**Inductive Reactance**

In the case of an alternating voltage applied to a circuit containing only inductance, with no resistance, it must be remembered that in such a resistanceless circuit the current always changes just rapidly enough to induce a back e.m.f. that equals and opposes the applied voltage. In Fig. 2-23, the cycle is again divided off into equal intervals. Assuming that the current has a maximum value of 1 ampere, the instantaneous current at the end of each interval will be as shown. The value of the *induced* voltage is proportional to the *rate at which the current changes*. It is therefore greatest in the intervals *OA* and *GH* and least in the intervals *CD* and *DE*. The induced voltage actually is a sine wave (if the current is a sine wave) as shown by the dashed curve. The *applied* voltage, because it is always equal to and opposed by the induced voltage, is equal to and 180 degrees out of phase with the induced

voltage, as shown by the second dashed curve. The result, therefore, is that the current flowing in an inductance is 90 degrees out of phase with the applied voltage, and lags behind the applied voltage. This is just the opposite of the condenser case.

Just enough current will flow in an inductance to induce an e.m.f. that just equals the applied e.m.f. Since the value of the induced e.m.f. is proportional to the rate at which the current changes, and this rate of change is in turn proportional to the frequency of the current, it should be clear that a small current changing rapidly (that is, at a high frequency) can generate a large back e.m.f. in a given inductance just as well as a large current changing slowly (low frequency). Consequently, the current that flows through a given inductance will decrease as the frequency is raised, if the applied e.m.f. is held constant. However, with both frequency and inductance fixed, the current will be larger when the applied voltage is increased, because the necessary rate of change in the current to induce the required back e.m.f. can only be obtained by having a greater total current flow under such circumstances. Again, when the applied voltage and frequency are fixed, the value of current required is less, as the inductance is made larger, because the induced e.m.f. also is proportional to inductance.

Just as in the capacitance case, the key point here is that — with the frequency and inductance fixed — an increase in the applied a.c. voltage causes a proportionate increase in the current. This is Ohm's Law again — and, again, the opposition effect is similar to, but not identical to, resistance. It is called **inductive reactance** and, like capacitive reactance, is measured in ohms. There is no energy loss in inductive reactance; the energy is stored in the magnetic field in one quarter cycle and then returned to the circuit in the next.

The formula for inductive reactance is

$$X_L = 2\pi fL$$

where  $X_L$  = Inductive reactance in ohms  
 $f$  = Frequency in cycles per second

$L$  = Inductance in henrys

$\pi = 3.14$

Example: The reactance of a coil having an inductance of 8 henrys, at a frequency of 120 cycles, is

$$X_L = 2\pi fL = 6.28 \times 120 \times 8 = 6029 \text{ ohms}$$

In radio-frequency circuits the inductance values usually are small and the frequencies are large. If the inductance is expressed in millihenrys and the frequency in kilocycles, the conversion factors for the two units cancel, and the formula for reactance may be used without first converting to fundamental units. Similarly, no conversion is necessary if the inductance is in microhenrys and the frequency is in megacycles.

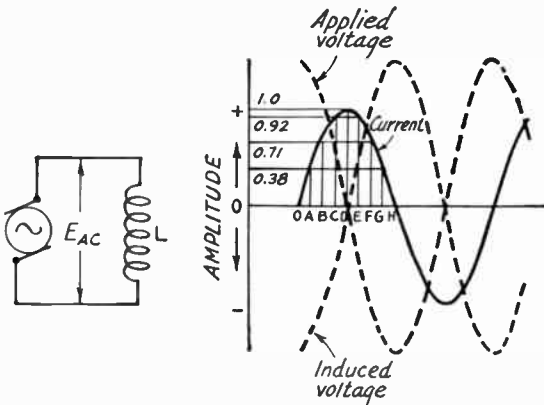


Fig. 2-23 — Phase relationships between voltage and current when an alternating voltage is applied to an inductance.



Example: The reactance of a 15-microhenry coil at a frequency of 14 Mc. is

$$X_L = 2\pi fL = 6.28 \times 14 \times 15 = 1319 \text{ ohms}$$

### Ohm's Law for Reactance

Ohm's Law for an a.c. circuit containing *only* reactance is

$$I = \frac{E}{X}$$

$$E = IX$$

$$X = \frac{E}{I}$$

where  $E$  = E.m.f. in volts

$I$  = Current in amperes

$X$  = Reactance in ohms

The reactance may be either inductive or capacitive.

Example: If a current of 2 amperes is flowing through the condenser of the previous example (reactance = 47.4 ohms) at 7150 kc., the voltage drop across the condenser is

$$E = IX = 2 \times 47.4 = 94.8 \text{ volts}$$

If 400 volts at 120 cycles is applied to the 8-henry inductance of the previous example, the current through the coil will be

$$I = \frac{E}{X} = \frac{400}{6029} = 0.0663 \text{ amp. (66.3 ma.)}$$

These examples show that there is nothing complicated about using Ohm's Law for a reactive a.c. circuit. The question naturally arises, though, as to what to do when the circuit consists of an inductance in series with a capacitance. In such a case the same current flows through both reactances. However, the voltage across the coil *leads* the current by 90 degrees, and the voltage across the condenser *lags* behind the current by 90 degrees. The coil and condenser voltages therefore are 180 degrees out of phase.

A simple circuit of this type is shown in Fig. 2-24. The same figure also shows the current (heavy line) and the voltage drops across the inductance ( $E_L$ ) and capacitance ( $E_C$ ). It is assumed that  $X_L$  is larger than  $X_C$  and so has a larger voltage drop. Since the two voltages are completely out of phase the *total* voltage ( $E_{AC}$ ) is equal to the *difference* between them. This is shown in the drawing as  $E_L - E_C$ . Notice that, because  $E_L$  is larger than  $E_C$ , the resultant voltage is exactly in phase with  $E_L$ . In other words, the circuit as a whole simply acts *as though it were an inductance* — an inductance of smaller value than the actual inductance present, since the effect of the actual inductive reactance is reduced by the capacitive reactance in series with it. If  $X_C$  is larger than  $X_L$ , the arrangement will behave like a capacitance — again of smaller reactance than the actual capacitive reactance present in the circuit.

The "equivalent" or total reactance of any circuit containing inductive and capacitive reactances in series is equal to  $X_L - X_C$ . If

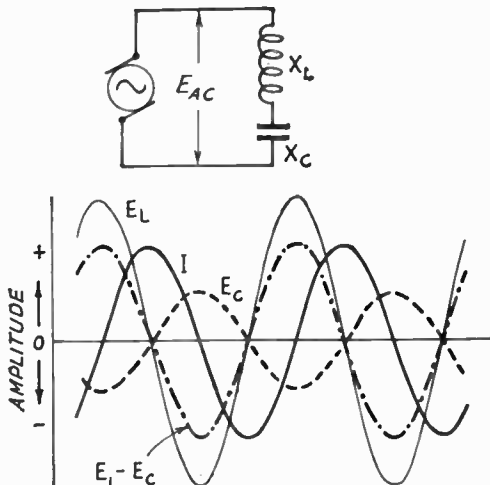


Fig. 2-24 — Current and voltages in a circuit having inductive and capacitive reactances in series.

there are several coils and condensers in series, we simply add up all the inductive reactances, then add up all the capacitive reactances, and then subtract the latter from the former. It is customary to call inductive reactance "positive" and capacitive reactance "negative." If the equivalent or net reactance is positive, the voltage leads the current by 90 degrees; if the net reactance is negative, the voltage lags the current by 90 degrees.

### Reactive Power

A curious feature of the drawing in Fig. 2-24 is that the voltage drop across the coil is larger than the voltage applied to the circuit. At first glance this might seem to be an impossible condition. But it is not; the reason is that neither the coil nor condenser *consumes* power. Actually, when energy is being stored in the coil's magnetic field, energy is being returned to the circuit from the condenser's electric field, and vice versa. This stored energy is responsible for the fact that the voltages across reactances in series can be larger than the voltage applied to them.

It will be recalled that in a resistance the flow of current causes heating and a power loss equal to  $I^2R$ . The power in a reactance is equal to  $I^2X$ , but is not a "loss"; it is simply power that is transferred back and forth between the field and the circuit but not used up in heating anything. In the quarter cycle when the current and voltage in a reactance both have the same polarity, energy is stored in the field; in the quarter cycle when the current and voltage have *opposite* polarity the energy is returned to the circuit. To distinguish this "nondissipated" power from the power which is actually consumed, the unit of reactive power is called the volt-ampere instead of the watt. Reactive power is sometimes called "wattless" power.

● IMPEDANCE

Although resistance, inductive reactance and capacitive reactance all are measured in ohms, the fact that they all are measured by the same unit does not indicate that they can be combined indiscriminately. Reactance does not absorb energy; resistance does. Voltage and current are in phase in resistance, but differ in phase by a quarter cycle in reactance. Furthermore, in inductive reactance the voltage leads the current, while in capacitive reactance the current leads the voltage. All these things must be taken into account when reactance and resistance are combined together in a circuit.

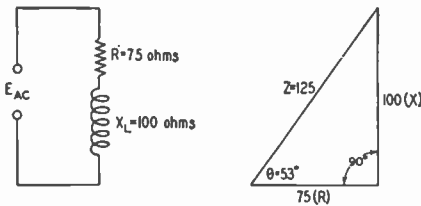


Fig. 2-25 — Resistance and inductive reactance connected in series.

In the simple circuit shown in Fig. 2-25, for example, it is not possible simply to add the resistance and reactance together to obtain a quantity that will indicate the opposition offered by the combination to the flow of current. Inasmuch as both resistance and reactance are present, the total effect can obviously be neither wholly one nor the other. In circuits containing both reactance and resistance the opposition effect is called **impedance**. The unit of impedance is also the ohm.

If the inductance in Fig. 2-25 were short-circuited, only the resistance would remain and the circuit would simply have a resistance of 75 ohms. In such a case the current and voltage would be in phase. On the other hand, if the resistance were short-circuited the circuit simply would have a reactance of 100 ohms, and the current would lag behind the voltage by one-quarter cycle or 90 degrees. When both are in the circuit, it would be expected that the impedance would be greater than either the resistance or reactance. It might also be expected that the current would be neither in phase with the voltage nor lagging 90 degrees behind it, but would be somewhere between the complete in-phase and the 90-degree phase conditions. Both things are true. The larger the reactance compared with the resistance, the more nearly the phase angle approaches 90 degrees; the larger the resistance compared to the reactance, the more nearly the current approaches the condition of being in phase with the voltage.

It can be shown that resistance and reactance can be combined in the same way that a right-angled triangle is constructed, if the re-

sistance is laid off to proper scale as the base of the triangle and the reactance is laid off as the altitude to the same scale. This is also indicated in Fig. 2-25. When this is done the hypotenuse of the triangle represents the impedance of the circuit, to the same scale, and the angle between  $Z$  and  $R$  (usually called  $\theta$  and so indicated in the drawing) is equal to the phase angle between the applied e.m.f. and the current. It is unnecessary, of course, actually to draw such a triangle when impedance is to be calculated; by geometry,

$$Z = \sqrt{R^2 + X^2}$$

In the case shown in the drawing,

$$Z = \sqrt{(75)^2 + (100)^2} = \sqrt{15,625} = 125 \text{ ohms.}$$

The phase angle can be found from simple trigonometry. Its tangent is equal to  $X/R$ ; in this case  $X/R = 100/75 = 1.33$ . From trigonometric tables it can be determined that the angle having a tangent equal to 1.33 is approximately 53 degrees. Fortunately, in ordinary amateur work it is seldom necessary to give much consideration to the phase angle because in most practical cases the angle will either be nearly zero (current and voltage in phase) or close to 90 degrees (current and voltage approximately a quarter cycle out of phase).

A circuit containing resistance and capacitance in series (Fig. 2-26) can be treated in the same way. That is, the impedance is

$$Z = \sqrt{R^2 + X^2}$$

and the phase angle again is the angle whose tangent is equal to  $X/R$ . It must be remembered, however, that in this case the current *leads* the applied e.m.f., while in the resistance-inductance case it *lags* behind the voltage.

In neither case is the impedance of the circuit equal to the simple arithmetical sum of the resistance and reactance. With  $R = 75$  ohms and  $X_L = 100$  ohms, simple addition would give 175 ohms while the actual impedance is 125 ohms. However, if either  $X$  or  $R$  is very small compared to the other (say, 1/10 or less) the impedance is very nearly equal to the larger of the two quantities. For example, if  $R = 1$  ohm and  $X = 10$  ohms,

$$Z = \sqrt{R^2 + X^2} = \sqrt{(1)^2 + (10)^2} = \sqrt{101} = 10.05 \text{ ohms.}$$

Hence if either  $X$  or  $R$  is at least 10 times as large as the other, the error in assuming that the impedance is equal to the larger of the two will not exceed  $\frac{1}{2}$  of 1 per cent, which is

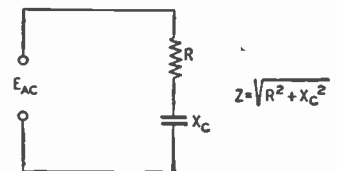


Fig. 2-26 — Resistance and capacitive reactance in series.

usually negligible. This fact is frequently useful.

In working with impedance, remember that one of its components is reactance and that the reactance of a given coil or condenser changes with the applied frequency. Therefore, impedance also changes with frequency. The change in impedance as the frequency is changed may be very slow if the resistance is considerably larger than the reactance. However, if the impedance is mostly reactance a change in frequency will cause the impedance to change practically as rapidly as the reactance itself changes.

### Ohm's Law for Impedance

Since impedance is made up of resistance and reactance, Ohm's Law can be applied to circuits containing impedance just as readily as to circuits having resistance or reactance only. The formulas are

$$I = \frac{E}{Z}$$

$$E = IZ$$

$$Z = \frac{E}{I}$$

where  $E$  = E.m.f. in volts

$I$  = Current in amperes

$Z$  = Impedance in ohms

Example: Assume that the e.m.f. applied to the circuit of Fig. 2-25 is 250 volts. Then

$$I = \frac{E}{Z} = \frac{250}{125} = 2 \text{ amperes.}$$

The same current is flowing in both  $R$  and  $X_L$ , and Ohm's Law as applied to either of these quantities says that the voltage drop across  $R$  should equal  $IR$  and the voltage drop across  $X_L$  should equal  $IX_L$ . Substituting,

$$E_R = IR = 2 \times 75 = 150 \text{ volts}$$

$$E_{X_L} = IX_L = 2 \times 100 = 200 \text{ volts}$$

The arithmetical sum of these voltages is greater than the applied voltage. However, the *actual*

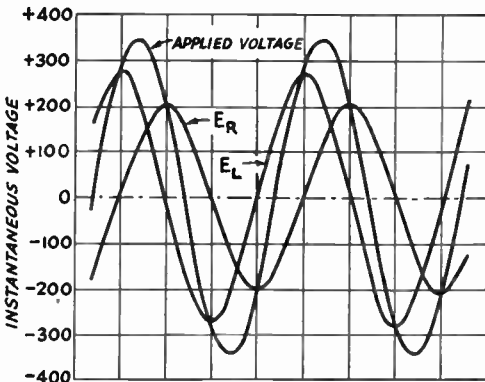


Fig. 2-27 — Voltage drops around the circuit of Fig. 2-25. Because of the phase relationships, the applied voltage is less than the arithmetical sum of the drops across the resistor and inductor.

sum of the two when the phase relationship is taken into account is equal to 250 volts r.m.s., as shown by Fig. 2-27, where the instantaneous values are added throughout the cycle. Whenever resistance and reactance are in series, the individual voltage drops always add up, arithmetically, to more than the applied voltage. There is nothing fictitious about these voltage drops; they can be measured readily by suitable instruments. It is simply an illustration of the importance of phase in a.c. circuits.

A more complex series circuit, containing resistance, inductive reactance and capacitive reactance, is shown in Fig. 2-28. In this case it is necessary to take into account the fact that the phase angles between current and voltage differ in all three elements. Since it is a series circuit, the current is the same throughout. Considering first just the inductance and

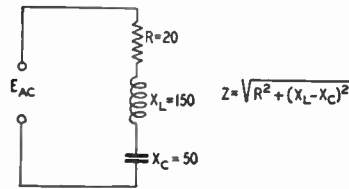


Fig. 2-28 — Resistance, inductive reactance, and capacitive reactance in series.

capacitance and neglecting the resistance, the phase relationships are the same as in Fig. 2-24. The net reactance in Fig. 2-28 is

$$X_L - X_C = 150 - 50 = 100 \text{ ohms (inductive)}$$

Since the series reactances can be lumped into one equivalent reactance, it is easy to find the impedance of the circuit by the rules previously given. The impedance of a circuit containing resistance, inductance and capacitance in series is

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Example: In the circuit of Fig. 2-28, the impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(20)^2 + (150 - 50)^2} = \sqrt{(20)^2 + (100)^2}$$

$$= \sqrt{10,400} = 102 \text{ ohms}$$

The phase angle can be found from  $X/R$ , where  $X = X_L - X_C$ .

### Parallel Circuits

Suppose that a resistor, condenser and coil are connected in parallel as shown in Fig. 2-29 and an a.c. voltage is applied to the combination. In any one branch, the current will be unchanged if one or both of the other two branches is disconnected, so long as the applied voltage remains unchanged. For example,  $I_L$ , the current through the inductance, will not change if both  $R$  and  $C$  are removed (although the total current,  $I$ , will change). Thus the current in each branch can be calculated quite simply by the Ohm's Law

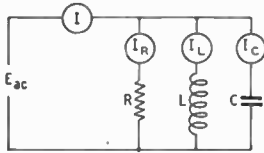


Fig. 2-29 — Resistance, inductance and capacitance in parallel. Instruments connected as shown will read the total current,  $I$ , and the individual currents in the three branches of the circuit.

formulas given in the preceding sections, if the voltage and reactance or resistance are known. The total current,  $I$ , is the sum of the currents through all three branches — not the arithmetical sum, but the sum when phase is taken into account.

The currents through the various branches will be as shown in Fig. 2-30, assuming for purposes of illustration that  $X_L$  is smaller than  $X_C$  and that  $X_C$  is smaller than  $R$ , thus making  $I_L$  larger than  $I_C$ , and  $I_C$  larger than  $I_R$ . The current through  $C$  leads the voltage by 90 degrees and the current through  $L$  lags the voltage by 90 degrees, so these two currents are 180 degrees out of phase. As shown at E, the total reactive current is the difference between  $I_C$  and  $I_L$ . This resultant current lags the voltage by 90 degrees, because  $I_L$  is larger than  $I_C$ . When the reactive current is added to  $I_R$ , the total current,  $I$ , is as shown at F. It can be seen that  $I$  lags the applied voltage by an angle smaller than 90 degrees and that the total current, while less than the simple sum (neglecting phase) of the three branch currents, is larger than the current through  $R$  alone.

The impedance looking into the parallel circuit from the source of voltage is equal to the applied voltage divided by the total or "line" current,  $I$ . In the case illustrated,  $I$  is greater than  $I_R$ , so the impedance of the circuit is less than the resistance of  $R$ . How much less depends upon the net reactive current flowing through  $L$  and  $C$  in parallel. If  $X_L$  and  $X_C$  are very nearly equal the net reactive current will be quite small because it is equal to the difference between two nearly equal currents. In such a case the impedance of the circuit will be almost the same as the resistance of  $R$  alone. On the other hand, if  $X_L$  and  $X_C$  are quite different the net reactive current can be relatively large and the total current also will be appreciably larger than  $I_R$ . In such a case the circuit impedance will be lower than the resistance of  $R$  alone.

The calculation of the impedance of parallel circuits is somewhat complicated. Fortunately, calculations are not necessary in most amateur work except in a special — and simple — case treated in a later section of this chapter.

### Power Factor

In the circuit of Fig. 2-25 an applied e.m.f. of 250 volts results in a current of 2 amperes.

If the circuit were purely resistive (containing no reactance) this would mean a power dissipation of  $250 \times 2 = 500$  watts. However, the circuit actually consists of resistance and reactance, and only the resistance consumes power. The power in the resistance is

$$P = I^2 R = (2)^2 \times 75 = 300 \text{ watts}$$

This is the actual power consumed by the circuit as compared to the apparent power input of 500 watts. The ratio of the power consumed to the apparent power is called the power factor of the circuit, and in the case used as an example would be  $300/500 = 0.6$ . Power factor is frequently expressed as a percentage; in this case, the power factor would be 60 per cent.

"Real" or dissipated power is measured in watts; apparent power, to distinguish it from real power, is measured in volt-amperes (just like the "wattless" power in a reactance). It is simply the product of volts and amperes and has no direct relationship to the power actually used up or dissipated unless the power factor of the circuit is known. The power factor of a purely resistive circuit is 100 per cent or 1, while the power factor of a pure reactance is zero. In this illustration, the reactive power is

$$VA \text{ (volt-amperes)} = I^2 X = (2)^2 \times 100 = 400 \text{ volt-amperes.}$$

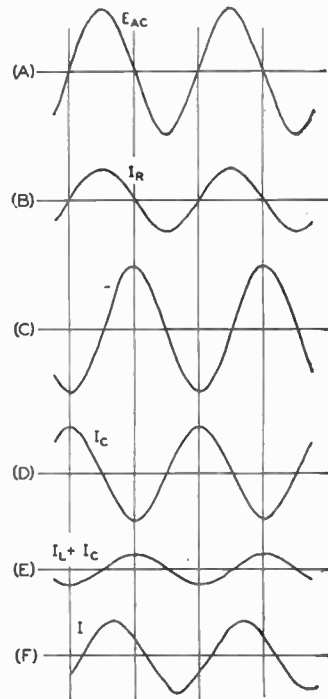


Fig. 2-30 — Phase relationships between branch currents and applied voltage for the circuit of Fig. 2-29. The total current through  $L$  and  $C$  in parallel ( $I_L + I_C$ ) and the total current in the entire circuit ( $I$ ) also are shown.

### Complex Waves

It was pointed out early in this chapter that a complex wave (a "nonsinusoidal" wave) can be resolved into a fundamental frequency and a series of harmonic frequencies. When such a complex voltage wave is applied to a circuit containing reactance, the current through the circuit will not have the same waveshape as the applied voltage. This is because the reactance of a coil and condenser depend upon the applied frequency. For the second-harmonic component of a complex wave, the reactance of the coil is twice and the reactance of the condenser one-half their values at the fundamental frequency; for the third harmonic the coil reactance is three times and the condenser reactance one-third, and so on.

Just what happens to the current waveshape depends upon the values of resistance and

reactance involved and how the circuit is arranged. In a simple circuit with resistance and inductive reactance in series, the amplitudes of the harmonics will be reduced because the inductive reactance increases in proportion to frequency. When a condenser and resistance are in series, on the other hand, the harmonics are likely to be accentuated because the condenser reactance becomes lower as the frequency is raised. When both inductive and capacitive reactance are present the shape of the current wave can be altered in a variety of ways, depending upon the circuit and the "constants," or values of  $L$ ,  $C$  and  $R$ , selected.

This property of nonuniform behavior with respect to fundamental and harmonics is an extremely useful one. It is the basis of "filtering," or the suppression of undesired frequencies in favor of a single desired frequency or group of such frequencies.

## Transformers

It has been shown in the preceding sections that, when an alternating voltage is applied to an inductance, an e.m.f. is induced by the varying magnetic field accompanying the flow of alternating current. If a second coil is brought into the same field, a similar e.m.f. likewise will be induced in this coil. This induced e.m.f. may be used to force a current through a wire, resistance or other electrical device connected to the terminals of the second coil.

Two coils operating in this way are said to be coupled, and the pair of coils constitutes a transformer. The coil connected to the source of energy is called the primary coil, and the other is called the secondary coil.

### Types of Transformers

The usefulness of the transformer lies in the fact that electrical energy can be transferred from one circuit to another without direct connection, and in the process can be readily changed from one voltage level to another. Thus, if a device to be operated requires, for example, 115 volts and only a 440-volt source is available, a transformer can be used to change the source voltage to that required. The transformer, of course, can be used only on a.c., since no voltage will be induced in the secondary if the magnetic field is not changing. If d.c. is applied to the primary of a transformer, a voltage will be induced in the secondary only at the instant of closing or opening the primary circuit, since it is only at these times that the field is changing.

As shown in Fig. 2-31, the primary and secondary coils of a transformer may be wound on a core of magnetic material. This increases the inductance of the coils so that a relatively small number of turns may be used to induce

a given value of voltage with a small current. A closed core (one having a continuous magnetic path) such as that shown in Fig. 2-31 also tends to insure that practically all of the field set up by the current in the primary coil will cut the turns of the secondary coil. However, the core introduces a power loss because of hysteresis and eddy currents so this type of construction is practicable only at power and audio frequencies. The discussion in this section is confined to transformers operating at such frequencies.

### Voltage and Turns Ratio

For a given varying magnetic field, the voltage induced in a coil in the field will be proportional to the number of turns on the coil. If the two coils of a transformer are in the same field (which is the case when both are wound on the same closed core) it follows that the induced voltages will be proportional to the number of turns on each coil. In the case of the primary, or coil connected to the source of power, the induced voltage is practi-

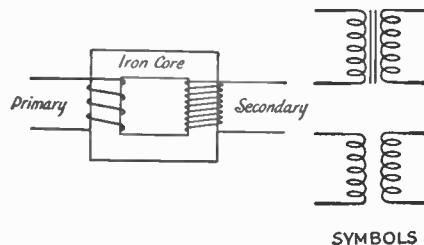


Fig. 2-31 — The transformer. Power is transferred from the primary coil to the secondary by means of the magnetic field. The upper symbol at right indicates an iron-core transformer, the lower one an air-core transformer.

cally equal to, and opposes, the applied voltage. Hence, for all practical purposes,

$$E_s = \frac{n_s}{n_p} E_p$$

where  $E_s$  = Secondary voltage

$E_p$  = Primary voltage

$n_s$  = Number of turns on secondary

$n_p$  = Number of turns on primary.

The ratio  $n_s/n_p$  is called the turns ratio of the transformer.

Example: A transformer has a primary of 400 turns and a secondary of 2800 turns, and 115 volts is applied to the primary. The secondary voltage will be

$$E_s = \frac{n_s}{n_p} E_p = \frac{2800}{400} \times 115 = 7 \times 115 = 805 \text{ volts}$$

Also, if 805 volts is applied to the 2800-turn winding (which then becomes the primary) the output voltage from the 400-turn winding will be 115 volts.

Either winding of a transformer can be used as the primary, providing the winding has enough turns to induce a voltage equal to the applied voltage without requiring an excessive current flow.

#### Effect of Secondary Current

The current that flows in the primary when no current is taken from the secondary is called the magnetizing current of the transformer. In any properly-designed transformer the primary inductance will be so large that the magnetizing current will be quite small. The power consumed by the transformer when the secondary is "open" — that is, not delivering power — is only the amount necessary to supply the losses in the iron core and in the resistance of the wire of which the primary is wound.

When current is drawn from the secondary winding, the secondary current sets up a magnetic field of its own in the core. The field from the secondary current always reduces the strength of the original field. But if the induced voltage in the primary is to equal the applied voltage, the original field *must* be maintained. Consequently, the primary current must change in such a way that the effect of the field set up by the secondary current is completely canceled. This is accomplished when the primary draws additional current that sets up a field exactly equal to the field set up by the secondary current, but which opposes the secondary field. The additional primary current is thus 180 degrees out of phase with the secondary current.

In practical calculations on transformers it is convenient to neglect the magnetizing current and to assume that the primary current is caused entirely by the secondary load. This is justifiable because the magnetizing current should be very small in comparison with the load current when the latter is near the rated value.

If the magnetic fields set up by the primary and secondary currents are to be equal, the primary current multiplied by the primary

turns must equal the secondary current multiplied by the secondary turns. From this it follows that the primary current will be equal to the secondary current multiplied by the turns ratio, secondary to primary, or

$$I_p = \frac{n_s}{n_p} I_s$$

where  $I_p$  = Primary current

$I_s$  = Secondary current

$n_p$  = Number of turns on primary

$n_s$  = Number of turns on secondary

Example: Suppose that the secondary of the transformer in the previous example is delivering a current of 0.2 ampere to a load. Then the primary current will be

$$I_p = \frac{n_s}{n_p} I_s = \frac{2800}{400} \times 0.2 = 7 \times 0.2 = 1.4 \text{ amp.}$$

Although the secondary voltage is higher than the primary voltage, the secondary current is lower than the primary current, and by the same ratio.

#### Power Relationships; Efficiency

A transformer cannot create power; it can only transfer and transform it. Hence, the power taken from the secondary cannot exceed that taken by the primary from the source of applied e.m.f. There is always some power loss in the resistance of the coils and in the iron core, so in all practical cases the power taken from the source will exceed that taken from the secondary. Thus,

$$P_o = nP_i$$

where  $P_o$  = Power output from secondary

$P_i$  = Power input to primary

$n$  = Efficiency factor

The efficiency,  $n$ , always is less than 1. It is usually expressed as a percentage; if  $n$  is 0.65, for instance, the efficiency is 65 per cent.

Example: A transformer has an efficiency of 85% at its full-load output of 150 watts. The power input to the primary at full secondary load will be

$$P_i = \frac{P_o}{n} = \frac{150}{0.85} = 176.5 \text{ watts}$$

The efficiency of a transformer is usually — by design — highest at the normal power output for which it is rated. The efficiency decreases with either lower or higher outputs. On the other hand, the losses in the transformer are relatively small at low output but increase as more power is taken. The amount of power that the transformer can handle is determined

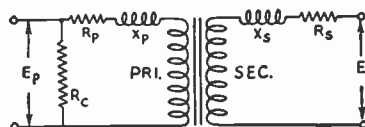


Fig. 2-32 — The equivalent circuit of a transformer includes the effects of leakage inductance and resistance of both primary and secondary windings. The resistance  $R_c$  is an equivalent resistance representing the constant core losses. Since these are comparatively small, their effect may be neglected in many approximate calculations.

by its own losses, because these heat the wire and core and raise the operating temperature. There is a limit to the temperature rise that can be tolerated, because too-high temperature either will melt the wire or break down the insulation between turns. A transformer always can be operated at reduced output even though the efficiency is low, because the actual loss also will be low under such conditions.

The full-load efficiency of small power transformers such as are used in radio receivers and transmitters usually lies between about 60 per cent and 90 per cent, depending upon the size and design.

### Leakage Reactance

In a practical transformer not all of the magnetic flux is common to both windings, although in well-designed transformers the amount of flux that "cuts" one coil and not the other is only a small percentage of the total flux. This leakage flux acts in the same way as flux about any coil that is not coupled to another coil; that is, it causes an e.m.f. of self-induction. Consequently, there are small amounts of leakage inductance associated with both windings of the transformer, but not common to them. Leakage inductance acts in exactly the same way as an equivalent amount of ordinary inductance inserted in series with the circuit. It has, therefore, a certain reactance, depending upon the amount of leakage inductance and the frequency. This reactance is called leakage reactance.

In the primary, the current flowing through the leakage reactance causes a voltage drop. This voltage drop increases with increasing primary current, hence it increases as more current is drawn from the secondary. The induced voltage consequently decreases, because the applied voltage has been reduced by the voltage drop in the primary leakage reactance. The secondary induced voltage also decreases proportionately.

When current flows in the secondary circuit the secondary leakage reactance causes an additional voltage drop that further reduces the voltage available from the secondary terminals. Thus, the greater the secondary current, the smaller the secondary terminal voltage becomes. The resistances of the primary and secondary windings of the transformer also cause voltage drops when current is flowing; although these voltage drops are not in phase with those caused by leakage reactance, together they result in a lower secondary voltage under load than is indicated by the turns ratio of the transformer.

At power frequencies (60 cycles) the voltage at the secondary, with a reasonably well-designed transformer, should not drop more than about 10 per cent from open-circuit conditions to full load. The drop in voltage may be considerably more than this in a transformer operating at audio frequencies because the

leakage reactance increases directly with the frequency.

### Impedance Ratio

In an ideal transformer — one without losses or leakage reactance — the following relationship is true:

$$Z_p = Z_s N^2$$

where  $Z_p$  = Impedance of primary as viewed from source of power

$Z_s$  = Impedance of load connected to secondary

$N$  = Turns ratio, primary to secondary

That is, a load of any given impedance connected to the secondary of the transformer will be changed to a different value "looking into" the primary from the source of power. The amount of impedance transformation is proportional to the square of the primary-to-secondary turns ratio.

Example: A transformer has a primary-to-secondary turns ratio of 0.6 (primary has 6/10 as many turns as the secondary) and a load of 3000 ohms is connected to the secondary. The impedance looking into the primary then will be

$$Z_p = Z_s N^2 = 3000 \times (0.6)^2 = 3000 \times 0.36 = 1080 \text{ ohms}$$

By choosing the proper turns ratio, the impedance of a fixed load can be transformed to any desired value, within practical limits. The transformed or "reflected" impedance has the same phase angle as the actual load impedance; if the load is a pure resistance the load presented by the primary to the source of power also will be a pure resistance.

The above relationship is sufficiently accurate in practice to give quite adequate results, even though it is based on an "ideal" transformer. Aside from the normal design requirements of reasonably low internal losses and low leakage reactance, the only other requirement to be met is that the primary have enough inductance to operate with low magnetizing current at the voltage applied to the primary. Despite a common — but mistaken — impression, a transformer operating with

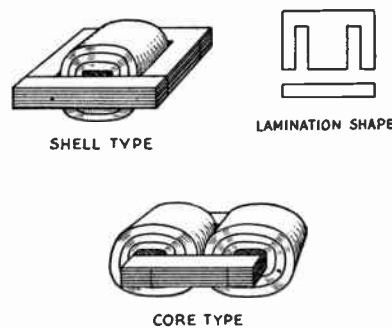


Fig. 2-33 — Two common types of transformer construction. Core pieces are interleaved to provide a continuous magnetic path with as low reluctance as possible.

a load does not "have" an impedance; the primary impedance — as it looks to the source of power — is determined by the load connected to the secondary and by the turns ratio. If the characteristics of the transformer have an appreciable effect on the impedance presented to the power source, the transformer is either poorly designed or is not suited to the voltage applied to it. Most transformers will operate quite well at voltages from slightly above to well below the design figure.

### Impedance Matching

Many devices require a specific value of load resistance (or impedance) for optimum operation. The resistance of the actual load that is to dissipate the power may differ widely from this value; so the transformer is frequently called upon to transform the actual load into one of the desired value. This is called **impedance matching**. From the preceding,

$$N = \sqrt{\frac{Z_s}{Z_p}}$$

where  $N$  = Required turns ratio, secondary to primary

$Z_s$  = Impedance of load connected to secondary

$Z_p$  = Impedance required

Example: A vacuum-tube a.f. amplifier requires a load of 5000 ohms for optimum performance, and is to be connected to a loud-speaker having an impedance of 10 ohms. The turns ratio, secondary to primary, required in the coupling transformer is

$$N = \sqrt{\frac{Z_s}{Z_p}} = \sqrt{\frac{10}{5000}} = \sqrt{\frac{1}{500}} = \frac{1}{22.4}$$

The primary therefore must have 22.4 times as many turns as the secondary.

Impedance matching means, in general, adjusting the load impedance — by means of a transformer or otherwise — to a desired value. However, there is also another meaning. It is possible to show that any source of power will have its *maximum possible* output when the impedance of the load is equal to the internal impedance of the source. The impedance of the source is said to be "matched" under this condition. However, the efficiency is only 50 per cent in such a case; just as much power is used up in the source as is delivered to the load. Because of the poor efficiency, this type of impedance matching is limited to cases where only a small amount of power is available. Getting the most power output may be more important than efficiency in such a case.

### Transformer Construction

Transformers usually are designed so that the magnetic path around the core is as short as possible. A short magnetic path means that the transformer will operate with fewer turns, for a given applied voltage, than if the path were long. It also helps to reduce flux leakage and therefore minimizes leakage reactance. The number of turns required also is affected by the

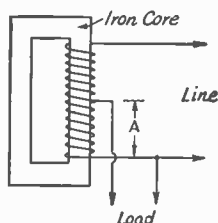


Fig. 2-34 — The autotransformer is based on the transformer principle, but uses only one winding. The line and load currents in the common winding ( $A$ ) flow in opposite directions, so that the resultant current is the difference between them. The voltage across  $A$  is proportional to the turns ratio.

cross-sectional area of the core. Transformer design data will be found in Chapter Seven.

Two core shapes are in common use, as shown in Fig. 2-33. In the shell type both windings are placed on the inner leg, while in the core type the primary and secondary windings may be placed on separate legs, if desired. This is sometimes done when it is necessary to minimize capacity effects between the primary and secondary, or when one of the windings must operate at very high voltage.

Core material for small transformers is usually silicon steel, called "transformer iron." The core is built up of laminations, insulated from each other (by a thin coating of shellac, for example) to prevent the flow of eddy currents. The laminations are overlapped at the ends to make the magnetic path as continuous as possible and thus reduce flux leakage.

The number of turns required on the primary for a given applied e.m.f. is determined by the type of core material used, the maximum permissible flux density, and the frequency. As a rough indication, windings of small power transformers frequently have about two turns per volt on a core of 1-square-inch cross section and have a magnetic path 10 or 12 inches in length. A longer path or smaller cross section requires more turns per volt, and vice versa.

In most transformers the coils are wound in layers, with a thin sheet of paper insulation between each layer. Thicker insulation is used between coils and between coils and core.

### Autotransformers

The transformer principle can be utilized with only one winding instead of two, as shown in Fig. 2-34; the principles just discussed apply equally well. A one-winding transformer is called an autotransformer. The section of the winding common to both the line and load circuits carries less current than the remainder of the coil, because the line and load currents are out of phase as explained previously. Hence the common section of the winding may be wound with comparatively small wire.

This advantage of the autotransformer is of practical value only when the primary (line) and secondary (load) voltages are not very different. On the other hand, it is frequently undesirable to have a direct connection between the primary and secondary circuits. For these reasons the autotransformer is used chiefly for boosting or reducing power-line voltage by relatively small amounts.



## Radio-Frequency Circuits

## ● RESONANCE

Fig. 2-35 shows a resistor, condenser and coil connected in series with a source of alternating current. Assume that the frequency can be varied over a wide range and that, at any frequency, the voltage of the source always has the same value.

At some *low* frequency the condenser reactance will be much larger than the resistance of  $R$ , and the inductive reactance will be small compared with either the reactance of  $C$  or the

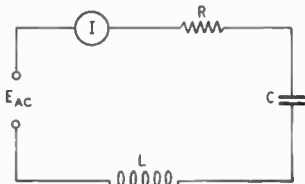


Fig. 2-35 — A series circuit containing  $L$ ,  $C$  and  $R$  is "resonant" at the applied frequency when the reactance of  $C$  is equal to the reactance of  $L$ .

resistance of  $R$ . (The resistance,  $R$ , is assumed to be the same at all frequencies.) On the other hand, at some very *high* frequency the reactance of  $C$  will be very small and the reactance of  $L$  will be very large. In the *low*-frequency case the amount of current that can flow will be determined practically entirely by the reactance of  $C$ ; since  $X_C$  is large at the low frequency, the current will be small. In the *high*-frequency case the amount of current that can flow will be determined almost wholly by the reactance of  $L$ ;  $X_L$  is large at the high frequency so the current is again small.

Now condenser reactance *decreases* as the frequency is raised, but inductive reactance *increases* with frequency. At *some* frequency, therefore, the reactances of  $C$  and  $L$  will be equal. At that frequency the voltage drop across the coil equals the voltage drop across the condenser, and since the two drops are 180 degrees out of phase they cancel each other completely. At that frequency the amount of current flow is determined wholly by the resistance,  $R$ . Also, at that frequency the current has its largest possible value (remember that we assumed the source voltage to be constant regardless of frequency). A series circuit in which the inductive and capacitive reactances are equal is said to be **resonant**; or, to be "in resonance" or "in tune" at the frequency for which the reactances are equal.

Resonance is not peculiar to radio-frequency circuits alone. It can occur at any a.c. frequency, including power-line frequencies. However, resonant circuits are used principally at radio frequencies; in fact, at those frequencies the circuits used almost always are resonant.

## Resonant Frequency

The frequency at which a series circuit is resonant is that for which  $X_L = X_C$ . Substituting the formulas for inductive and capacitive reactance gives

$$f = \frac{1}{2\pi\sqrt{LC}}$$

where  $f$  = Frequency in cycles per second

$L$  = Inductance in henrys

$C$  = Capacitance in farads

$\pi$  = 3.14

These units are inconveniently large for radio-frequency circuits. A formula using more appropriate units is

$$f = \frac{10^6}{2\pi\sqrt{LC}}$$

where  $f$  = Frequency in kilocycles (kc.)

$L$  = Inductance in microhenrys ( $\mu$ h.)

$C$  = Capacitance in micromicrofarads

( $\mu\mu$ fd.)

$\pi$  = 3.14

Example: The resonant frequency of a series circuit containing a 5- $\mu$ h. coil and a 35- $\mu\mu$ fd. condenser is

$$\begin{aligned} f &= \frac{10^6}{2\pi\sqrt{LC}} = \frac{10^6}{6.28 \times \sqrt{5 \times 35}} \\ &= \frac{10^6}{6.28 \times 13.2} = \frac{10^6}{83} = 12,050 \text{ kc.} \end{aligned}$$

The formula for resonant frequency is not affected by the resistance in the circuit.

## Resonance Curves

If a plot is drawn of the current flowing in the circuit of Fig. 2-35 as the frequency is varied (the applied voltage being constant) it would look like one of the curves in Fig. 2-36. At frequencies very much higher than the resonant frequency the current is limited by the inductive reactance; the condenser and resistor have only a negligible part. At frequencies very much lower than resonance the condenser limits the current, the resistor and inductance playing very little part. Exactly at resonance the current is limited only by the resistance; the smaller the resistance the larger the resonant current. The shape of the **resonance curve** at frequencies *near* resonance is determined by the ratio of reactance to resistance at the particular frequency considered. If the reactance of either the coil or condenser is of the same order of magnitude as the resistance, the current decreases rather slowly as the frequency is moved in either direction away from resonance. Such a curve is said to be **broad**. On the other hand, if the reactance is considerably larger than the resistance the current decreases rapidly as the

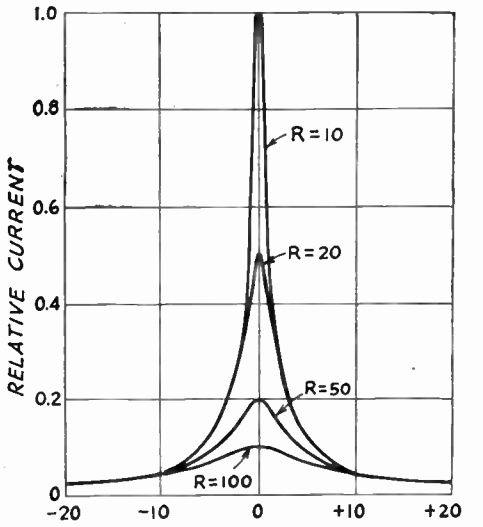


Fig. 2-36 — Current in a series-resonant circuit with various values of series resistance. The values are arbitrary and would not apply to all circuits, but represent a typical case. It is assumed that the reactances (at the resonant frequency) are 1000 ohms (minimum  $Q = 10$ ). Note that at frequencies at least plus or minus ten per cent away from the resonant frequency the current is substantially unaffected by the resistance in the circuit.

frequency moves away from resonance and the circuit is said to be sharp. Curves of differing sharpness are shown in Fig. 2-36. A sharp circuit will respond a great deal more readily to the resonant frequency than to frequencies quite close to resonance; a broad circuit will respond almost equally well to a group or band of frequencies centering around the resonant frequency.

Both types of resonance curves are useful. A sharp circuit gives good selectivity — the ability to select one desired frequency and discriminate against others. A broad circuit is used when the apparatus must give about the same response over a band of frequencies rather than to a single frequency alone.

**Q**

Most diagrams of resonant circuits show only inductance and capacitance; no resistance is indicated. Nevertheless, resistance is always present. At frequencies up to perhaps 30 Mc. this resistance is mostly in the wire of the coil. Above this frequency energy loss in the condenser (principally in the solid dielectric which must be used to form an insulating support for the condenser plates) becomes appreciable. This energy loss is equivalent to resistance. When maximum sharpness or selectivity is needed the object of design is to reduce the inherent resistance to the lowest possible value.

We mentioned above that the sharpness of the resonance curve is determined by the ratio of reactance to resistance. The value of the

reactance of either the coil or condenser at the resonant frequency, divided by the resistance in the circuit, is called the  $Q$  (quality factor) of the circuit, or

$$Q = \frac{X}{R}$$

where  $Q$  = Quality factor  
 $X$  = Reactance of either coil or condenser, in ohms  
 $R$  = Resistance in ohms

Example: The coil and condenser in a series circuit each have a reactance of 350 ohms at the resonant frequency. The resistance is 5 ohms. Then the  $Q$  is

$$Q = \frac{X}{R} = \frac{350}{5} = 70$$

Since the same current flows in  $R$  that flows in  $X$ , the  $Q$  of the circuit also is the ratio of the reactive power to the "real" power, or power dissipated in the resistance. The term "volt-ampere-to-watt" ratio or, when the power is large, "kva.-to-kw. ratio," therefore is sometimes used instead of " $Q$ ." To put it another way, the  $Q$  of the circuit is the ratio of the energy stored (in either the magnetic or electric field) to the energy dissipated as heat in the resistance.

The effect of  $Q$  on the sharpness of resonance of a circuit is shown by the curves of Fig. 2-37. In these curves the frequency change is shown in percentage above and below the resonant frequency.  $Q$ s of 10, 20, 50 and 100 are shown; these values cover much of the range commonly used in radio work.

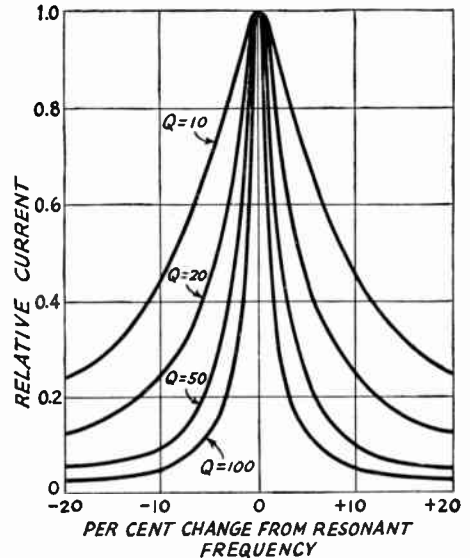


Fig. 2-37 — Current in series-resonant circuits having different  $Q$ s. In this graph the current at resonance is assumed to be the same in all cases. The lower the  $Q$ , the more slowly the current decreases as the applied frequency is moved away from resonance.

## Voltage Rise

When a voltage of the resonant frequency is inserted in series in a resonant circuit, the voltage that appears across either the coil or condenser is considerably higher than the applied voltage. The current in the circuit is limited only by the actual resistance of the coil-condenser combination in the circuit and may have a relatively high value; however, the same current flows through the high reactances of the coil and condenser and causes large voltage drops. (As explained above, the reactances are of opposite types and hence the voltages are opposite in phase, so the net voltage around the circuit is only that which is applied.) The ratio of the reactive voltage to the applied voltage is equal to the ratio of reactance to resistance. This ratio is the  $Q$  of the circuit. Therefore, the voltage across either the coil or condenser is equal to  $Q$  times the voltage inserted in series with the circuit.

Example: The inductive reactance of a circuit is 200 ohms, the capacitive reactance is 200 ohms, the resistance 5 ohms, and the applied voltage is 50. The two reactances cancel and there will be but 5 ohms of pure resistance to limit the current flow. Thus the current will be  $50/5$ , or 10 amperes. The voltage developed across either the coil or the condenser will be equal to its reactance times the current, or  $200 \times 10 = 2000$  volts. An alternate method: The  $Q$  of the circuit is  $X/R = 200/5 = 40$ . The reactive voltage is equal to  $Q$  times the applied voltage, or  $40 \times 50 = 2000$  volts.

## Parallel Resonance

When a variable-frequency source of constant voltage is applied to a parallel circuit of the type shown in Fig. 2-38 there is a resonance effect similar to that in a series circuit. However, in this case the current (measured at the point indicated) is *smallest* at the frequency for which the coil and condenser reactances are equal. At that frequency the current through  $L$  is exactly canceled by the out-of-phase current through  $C$ , as explained in an earlier section, so that only the current taken by  $R$  flows in the line. At frequencies *below* resonance the current through  $L$  is larger than that through  $C$ , because the reactance of  $L$  is

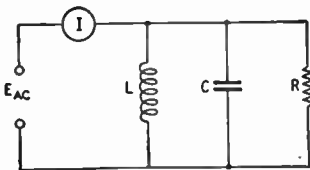


Fig. 2-38 — Circuit illustrating parallel resonance.

smaller and that of  $C$  higher at low frequencies; there is only partial cancellation of the two reactive currents and the line current therefore is larger than the current taken by  $R$  alone. At frequencies *above* resonance the situation is reversed and more current flows through  $C$  than through  $L$ , so the line current again increases. The current at resonance, being deter-

mined wholly by  $R$ , will be small if  $R$  is large and large if  $R$  is small.

The resistance  $R$  shown in Fig. 2-38 seldom is an actual physical resistor. In most cases it will be an "equivalent" resistance that corresponds to the effect of an actual energy loss in the circuit. This energy loss can be inherent in the coil or condenser, or may represent en-

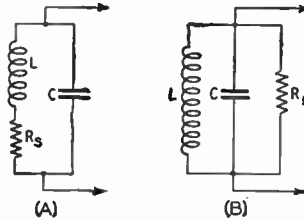


Fig. 2-39 — Series and parallel equivalents when the two circuits are resonant. The series resistor,  $R_s$ , in A can be replaced by an equivalent parallel resistor,  $R_p$ , in B, and vice versa.

ergy transferred to a load by means of the resonant circuit. (For example, the resonant circuit may be used for transferring power from a vacuum-tube amplifier to an antenna system.)

Parallel and series resonant circuits are quite alike in some respects. For instance, the circuits given at A and B in Fig. 2-39 will behave identically, when an external voltage is applied, if (1)  $L$  and  $C$  are the same in both cases; and (2)  $R_p$  multiplied by  $R_s$  equals the square of the reactance (at resonance) of either  $L$  or  $C$ . When these conditions are met the two circuits will have the same  $Q$ s. (These statements are approximate, but are quite accurate if the  $Q$  is 10 or more.) Now the circuit at A is a *series* circuit if it is viewed from the "inside" — that is, going around the loop formed by  $L$ ,  $C$  and  $R$  — so its  $Q$  can be found from the ratio of  $X$  to  $R_s$ .

What this means is that a circuit like that of Fig. 2-39A has an equivalent parallel impedance (at resonance) equal to  $R_p$ , the relationship between  $R_s$  and  $R_p$  being as explained above. Although  $R_p$  is not an actual resistor, to the source of voltage the parallel-resonant circuit "looks like" a pure resistance of that value. It is "pure" resistance because the coil and condenser currents are 180 degrees out of phase and are equal; thus there is no reactive current. At the resonant frequency, then, the parallel impedance of a resonant circuit is

$$Z_r = QX$$

where  $Z_r$  = Resistive impedance at resonance  
 $Q$  = Quality factor  
 $X$  = Reactance (in ohms) of either the coil or condenser

Example: The parallel impedance of a circuit having a  $Q$  of 50 and having inductive and capacitive reactances of 300 ohms will be

$$Z_r = QX = 50 \times 300 = 15,000 \text{ ohms.}$$

At frequencies off resonance the impedance is no longer purely resistive because the coil and condenser currents are not equal. The off-resonant impedance therefore is complex, and

is lower than the resonant impedance for the reasons previously outlined.

The higher the  $Q$  of the circuit, the higher the parallel impedance. Curves showing the variation of impedance (with frequency) of a parallel circuit have just the same shape as the curves showing the variation of current with frequency in a series circuit. Fig. 2-40 is a set of such curves.

### Q of Loaded Circuits

In many applications of resonant circuits the only power lost is that dissipated in the resistance of the circuit itself. At frequencies below 30 Mc. most of this resistance is in the coil. Within limits, increasing the number of turns on the coil increases the reactance faster than it raises the resistance, so coils for circuits in which the  $Q$  must be high are made with relatively large inductance for the frequency under consideration.

However, when the circuit delivers energy to a load (as in the case of the resonant circuits used in transmitters) the energy consumed in the circuit itself is usually negligible compared with that consumed by the load. The equivalent of such a circuit is shown in Fig. 2-41A, where the parallel resistor represents the load to which power is delivered. If the power dissipated in the load is at least ten times as great as the power lost in the coil and condenser, the parallel impedance of the resonant circuit itself will be so high compared with the resistance of the load that for all practical purposes the impedance of the combined circuit is equal to the load resistance. Under these conditions the  $Q$  of a parallel-

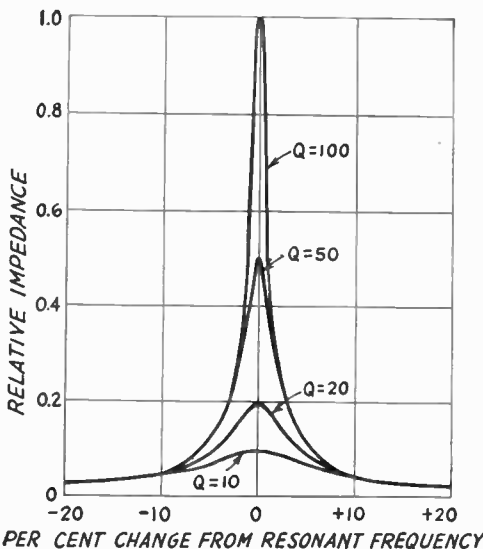


Fig. 2-40 — Relative impedance of parallel-resonant circuits with different  $Q$ s. These curves are similar to those in Fig. 2-37 for current in a series-resonant circuit. The effect of  $Q$  on impedance is most marked near the resonant frequency.

resonant circuit loaded by a resistive impedance is

$$Q = \frac{Z}{X}$$

where  $Q$  = Quality factor

$Z$  = Parallel load resistance (ohms)

$X$  = Reactance (ohms) of either the coil or condenser

Example: A resistive load of 3000 ohms is connected across a resonant circuit in which the inductive and capacitive reactances are each 250 ohms. The circuit  $Q$  is then

$$Q = \frac{Z}{X} = \frac{3000}{250} = 12$$

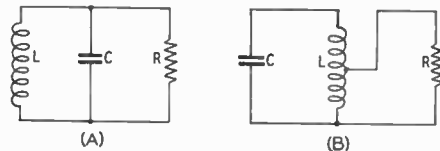


Fig. 2-41 — The equivalent circuit of a resonant circuit delivering power to a load. The resistor  $R$  represents the load resistance. At B the load is tapped across part of  $L$ , which by transformer action is equivalent to using a higher load resistance across the whole circuit.

The effective  $Q$  of a circuit loaded by a parallel resistance becomes higher when the reactances of the coil and condenser are decreased. A circuit loaded with a relatively low resistance (a few thousand ohms) must have low-reactance elements (large capacitance and small inductance) to have reasonably high  $Q$ .

The effect of a given load resistance on the  $Q$  of a circuit can be changed by connecting the load across only part of the circuit. A common method is to tap the load across part of the coil, as shown in Fig. 2-41B. The smaller the portion of the coil across which the load is tapped, the less the loading on the circuit; in other words, tapping the load "down" is equivalent to connecting a higher value of load resistance across the whole circuit. This is similar in principle to impedance transformation with an iron-core transformer. In high-frequency resonant circuits the impedance ratio does not vary exactly as the square of the turns ratio, because all the magnetic flux lines do not cut every turn of the coil. A desired reflected impedance usually must be obtained by experimental adjustment.

### L/C Ratio

The formula for resonant frequency of a circuit shows that the same frequency always will be obtained so long as the product of  $L$  and  $C$  is constant. Within this limitation, it is evident that  $L$  can be large and  $C$  small,  $L$  small and  $C$  large, etc. The relation between the two for a fixed frequency is called the  $L/C$  ratio. A high- $C$  circuit is one which has more capacity than "normal" for the frequency; a low- $C$  circuit one which has less than normal capacity. These terms depend to a

considerable extent upon the particular application considered, and have no exact numerical meaning.

### LC Constants

As pointed out in the preceding paragraph, the product of inductance and capacity is constant for any given frequency. It is frequently convenient to use the numerical value of the *LC* constant when a number of calculations have to be made involving different *L/C* ratios for the same frequency. The constant for any frequency is given by the following equation:

$$LC = \frac{25,330}{f^2}$$

where *L* = Inductance in microhenrys ( $\mu\text{h.}$ )

*C* = Capacitance in micromicrofarads ( $\mu\mu\text{fd.}$ )

*f* = Frequency in megacycles.

Example: Find the inductance required to resonate at 3650 kc. (3.65 Mc.) with capacitances of 25, 50, 100, and 500  $\mu\mu\text{fd.}$  The *LC* constant is

$$LC = \frac{25,330}{(3.65)^2} = \frac{25,330}{13.35} = 1900$$

$$\text{With } 25 \mu\mu\text{fd. } L = 1900/C = 1900/25 = 76 \mu\text{h.}$$

$$50 \mu\mu\text{fd. } L = 1900/C = 1900/50 = 38 \mu\text{h.}$$

$$100 \mu\mu\text{fd. } L = 1900/C = 1900/100 = 19 \mu\text{h.}$$

$$500 \mu\mu\text{fd. } L = 1900/C = 1900/500 = 3.8 \mu\text{h.}$$

## COUPLED CIRCUITS

### Energy Transfer and Loading

Two circuits are coupled when energy can be transferred from one to the other. The circuit delivering power is called the **primary circuit**; the one receiving power is called the **secondary circuit**. The power may be practically all dissipated in the secondary circuit itself (this is usually the case in receiver circuits) or the secondary may simply act as a medium through which the power is transferred to a load resistance where it does work. In the latter case, the coupled circuits may act as a radio-frequency impedance-matching device. The matching can be accomplished by adjusting the loading on the secondary and by varying the amount of coupling between the primary and secondary.

A general understanding of coupling methods is essential in amateur work, but there is seldom, if ever, need for *calculation* of the performance of coupled circuits. Very few radio amateurs have the equipment necessary for measuring the quantities that enter into such calculations. In actual practice, the adjustment of a coupled circuit is a cut-and-try process. Satisfactory results readily can be obtained if the principles are understood.

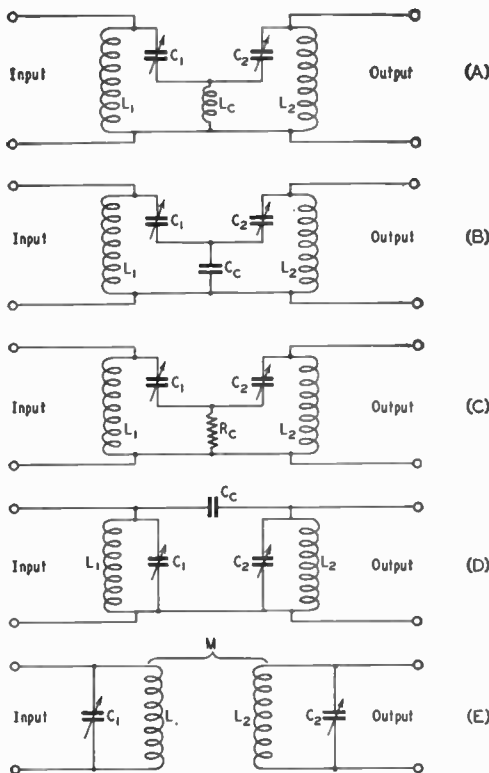


Fig. 2-42 — Basic methods of circuit coupling.

### Coupling by a Common Circuit Element

One method of coupling between two resonant circuits is through a circuit element common to both. The three variations of this type of coupling shown at A, B and C of Fig. 2-42, utilize a common inductance, capacitance and resistance, respectively. Current circulating in one *LC* branch flows through the common element (*L<sub>c</sub>*, *C<sub>c</sub>*, or *R<sub>c</sub>*) and the voltage developed across this element causes current to flow in the other *LC* branch.

If both circuits are resonant to the same frequency, as is usually the case, the value of impedance — reactance or resistance — required for maximum energy transfer is generally quite small compared to the other reactances in the circuits. The common-circuit-element method of coupling is used only occasionally in amateur apparatus.

### Capacitive Coupling

In the circuit at D the coupling increases as the capacitance of *C<sub>c</sub>*, the "coupling condenser," is made greater (reactance of *C<sub>c</sub>* is decreased). When two resonant circuits are coupled by this means, the capacitance required for maximum energy transfer is quite small if the *Q* of the secondary circuit is at all high. For example, if the parallel impedance of the secondary circuit is 100,000 ohms, a

reactance of 10,000 ohms or so in the condenser will give ample coupling. The corresponding capacitance required is only a few micromicrofarads at high frequencies.

### Inductive Coupling

Fig. 2-42E shows inductive coupling, or coupling by means of the magnetic field. A circuit of this type resembles the iron-core transformer, but because only a small percentage of the magnetic flux lines set up by one coil cut the turns of the other coil, the simple relationships between turns ratio, voltage ratio and impedance ratio in the iron-core transformer do not hold.

Three common types of inductively-coupled circuits are shown in Fig. 2-43. In the first two, only one circuit actually is resonant. The circuit at A is frequently used in receivers for coupling between amplifier tubes when the tuning of the circuit must be varied to respond to signals of different frequencies. Circuit B is used principally in transmitters, for coupling a radio-frequency amplifier to a resistive load. Circuit C is used for fixed-frequency amplification in receivers. The same circuit also is used in transmitters for transferring power to a load that has both reactance and resistance.

In circuits A and B the coupling between the primary and secondary coils usually is "tight" — that is, the coefficient of coupling between the coils is large. With tight coupling either circuit operates much as though the device to which the untuned coil is connected were simply tapped across a corresponding number of turns on the tuned-circuit coil. Any resistance in the circuit to which the untuned coil is connected is coupled into the tuned circuit in proportion to the mutual inductance. This "coupled" resistance increases the effective series resistance of the tuned circuit, thereby lowering its  $Q$  and selectivity. If the circuit to which the untuned coil is connected has reactance, a certain amount of reactance will be "coupled in" to the tuned circuit. The coupled reactance makes it necessary to readjust the tuning whenever the coupling is changed, because coupled reactance tunes the circuit just as the actual coil and condenser reactance does.

These circuits may be used for impedance matching by adjusting the mutual inductance between the coils. This can be done by varying the coupling, changing the number of turns in the untuned coil, or both. The parallel impedance of the tuned circuit is affected by the coupled-in resistance in the same way as it would be by a corresponding increase in the actual series resistance. The larger the value of coupled-in resistance the lower the parallel impedance. By proper choice of the number of turns on the untuned coil, and by adjustment of the coupling, the parallel impedance of the tuned circuit may be adjusted to the value required for the proper operation of the device to which it is connected.

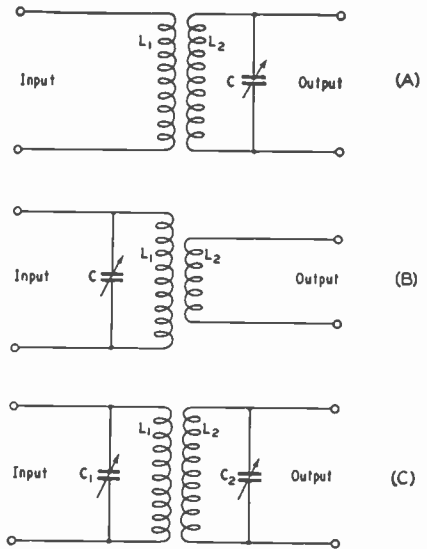


Fig. 2-43 — Types of inductively-coupled circuits. In A and B, one circuit is tuned, the other untuned. C shows the method of coupling between two tuned circuits.

### Coupled Resonant Circuits

When the primary and secondary circuits are both tuned, as in Fig. 2-43C, the resonance effects in both circuits make the operation somewhat more complicated than in the simpler circuits just considered. Imagine first that the two circuits are not coupled and that each is independently tuned to the resonant frequency. The impedance of each will be purely resistive. If the two are then coupled, the secondary will couple resistance into the primary, causing its parallel impedance to decrease. As the coupling is made greater (without changing the tuning of either circuit) the coupled resistance becomes larger and the parallel impedance of the primary continues to decrease. Also, as the coupling is made tighter the amount of power transferred from the primary to the secondary will increase — but only up to a certain point. The power transfer becomes maximum at a "critical" value of coupling, but then decreases if the coupling is tightened beyond the critical point. At critical coupling, the resistance coupled into the primary circuit is equal to the resistance of the primary itself. This represents the matched-impedance condition and gives maximum power transfer.

Critical coupling is a function of the  $Q$ s of the two circuits taken independently. A higher coefficient of coupling is required to reach critical coupling when the  $Q$ s are low; if the  $Q$ s are high, as in receiving applications, a coupling coefficient of a few per cent may give critical coupling.

With loaded circuits it is not impossible for the  $Q$  to reach such low values that critical coupling cannot be obtained even with the highest practicable coefficient of coupling (coils

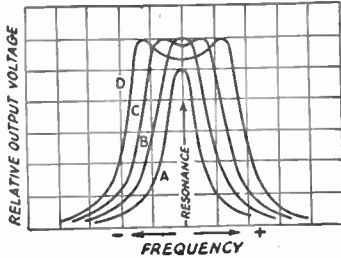


Fig. 2-44 — Showing the effect on the output voltage from the secondary circuit of changing the coefficient of coupling between two resonant circuits independently tuned to the same frequency. The voltage applied to the primary is held constant in amplitude while the frequency is varied, and the output voltage is measured across the secondary.

as physically close as possible). In such case the only way to secure sufficient coupling is to increase the  $Q$  of one or both of the coupled circuits. This can be done either by decreasing the  $L/C$  ratio or by tapping the load down on the secondary coil. If the load resistance is known beforehand, the circuits may be designed for a  $Q$  in the vicinity of 10 or so with assurance that sufficient coupling will be available; if unknown, the proper  $Q$ s can be determined by experiment.

**Selectivity**

In A and B, Fig. 2-43, only one circuit is tuned and the selectivity curve will be that of a single resonant circuit having the appropriate  $Q$ . As stated, the effective  $Q$  depends upon the resistance connected to the untuned coil.

In Fig. 2-43C, the selectivity is the same as that of a single tuned circuit having a  $Q$  equal to the product of the  $Q$ s of the individual circuits — if the coupling is below critical and both circuits are tuned to resonance. The  $Q$ s of the individual circuits are affected by the degree of coupling, because each couples resistance into the other; the tighter the coupling, the lower the individual  $Q$ s and therefore the lower the over-all selectivity.

If both circuits are independently tuned to resonance, the over-all selectivity will vary about as shown in Fig. 2-44 as the coupling is varied. At loose coupling, A, the output voltage (across the secondary circuit) is small and the selectivity is high. As the coupling is increased the secondary voltage also increases until critical coupling, B, is reached. At this point the output voltage at the resonant frequency is maximum but the selectivity is lower than with looser coupling. At still tighter coupling, C, the output voltage at the resonant frequency decreases, but as the frequency is varied either side of resonance it is found that there are two "humps" to the curve, one on either side of resonance. With very tight coupling, D, there is a further decrease in the output voltage at resonance and the "humps" are farther away from the resonant frequency. Resonance curves such as those at C and D

are called flat-topped because the output voltage does not change much over an appreciable band of frequencies.

Note that the off-resonance humps have the same maximum value as the resonant output voltage at critical coupling. These humps are caused by the fact that at frequencies off resonance the secondary circuit is reactive and couples reactance as well as resistance into the primary. The coupled resistance decreases off resonance and the humps represent a new condition of impedance matching — at a frequency to which the primary is detuned by the coupled-in reactance from the secondary.

When the two circuits are tuned to slightly different frequencies a double-humped resonance curve results even though the coupling is below critical. This is to be expected, because each circuit will respond best to the frequency to which it is tuned. Tuning of this type is called stagger tuning, and often is used when substantially uniform response over a wide band of frequencies is desired.

**Link Coupling**

A modification of inductive coupling, called link coupling, is shown in Fig. 2-45. This gives the effect of inductive coupling between two coils that have no mutual inductance; the link is simply a means for providing the mutual inductance. The total mutual inductance between two coils coupled by a link cannot be made as great as if the coils themselves were coupled. This is because the coefficient of coupling between air-core coils is considerably less than 1, and since there are two coupling points the over-all coupling coefficient is less than for any pair of coils. In practice this need not be disadvantageous because the power transfer can be made great enough by making the tuned circuits sufficiently high- $Q$ . Link coupling is convenient when ordinary inductive coupling would be impracticable for constructional reasons. It finds wide use in transmitters, for example.

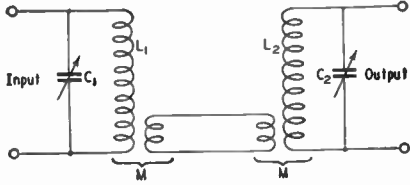


Fig. 2-45 — Link coupling. The mutual inductances at both ends of the link are equivalent to mutual inductance between the tuned circuits, and serve the same purpose.

The link coils usually have a small number of turns compared with the resonant-circuit coils. The number of turns is not greatly important, because the coefficient of coupling is relatively independent of the number of turns on either coil; it is more important that both link coils should have about the same number of turns. The length of the link between the

coils is not critical if it is very small compared with the wavelength; if the length becomes an appreciable fraction of a wavelength the link operates more as a transmission line than as a means for providing mutual inductance. In such case it should be treated by the methods described in Chapter Ten.

### Piezoelectric Crystals

A number of crystalline substances found in nature have the ability to transform mechanical strain into an electrical charge, and vice versa. This property is known as piezoelectricity. A small plate or bar cut in the proper way from a quartz crystal, for example, and placed between two conducting electrodes, will be mechanically strained when the electrodes are connected to a source of voltage. Conversely, if the crystal is squeezed between two electrodes a voltage will develop between the electrodes.

Piezoelectric crystals can be used to transform mechanical energy into electrical energy, and vice versa. They are used, for example, in microphones and phonograph pick-ups, where mechanical vibrations are transformed into alternating voltages of corresponding frequency. They are also used in headsets and loudspeakers, transforming electrical energy into mechanical vibration. Crystal plates for these purposes are cut from large crystals of Rochelle salts.

Crystalline plates also are mechanical vibrators that have natural frequencies of vibration ranging from a few thousand cycles to several megacycles per second. The vibration frequency depends on the kind of crystal, the way the plate is cut from the natural crystal, and on the dimensions of the plate. Such a crystal is, in fact, the mechanical counterpart of an electrical tuned circuit; its resonant frequency is the natural frequency of the mechanical vibration. Because of the piezoelectric effect, the crystal plate can be coupled to an electrical circuit and made to substitute for

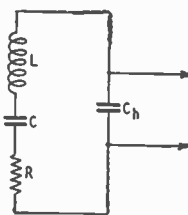


Fig. 2-46 — Equivalent circuit of a crystal resonator.  $L$ ,  $C$  and  $R$  are the electrical equivalents of mechanical properties of the crystal;  $C_h$  is the capacitance of the electrodes with the crystal plate between them.

a coil-and-condenser resonant circuit. The thing that makes crystals valuable as "resonators" is the fact that they have extremely high  $Q$ , ranging from 5 to 10 times the  $Q$ s obtainable with  $LC$  resonant circuits.

Analogies can be drawn between various mechanical properties of the crystal and the electrical characteristics of a tuned circuit. This leads to an "equivalent circuit" for the crystal. The electrical coupling to the crystal is through the electrodes between which it is sandwiched; these electrodes form, with the crystal as the dielectric, a small condenser like any other condenser constructed of two plates with a dielectric between. The crystal itself is an equivalent to a series-resonant circuit, and together with the capacitance of the electrodes forms the equivalent circuit shown in Fig. 2-46. The equivalent inductance of the crystal is extremely large and the series capacitance,  $C$ , is correspondingly low; this is the reason for the high  $Q$  of a crystal. The electrode capacitance,  $C_h$ , is so very large compared with the series capacitance of the crystal that it has only a very small effect on the resonant frequency. It will be realized, also, that because  $C_h$  is so large compared with  $C$  the electrical coupling to the crystal is quite loose.

Crystal plates for use as resonators in radio-frequency circuits are almost always cut from quartz crystals, because quartz is by far the most suitable material for this purpose. Quartz crystals are used as resonators in receivers, to give highly-selective reception, and as frequency-controlling elements in transmitters.

## Practical Circuit Details

### COMBINED A.C. AND D.C.

Most radio circuits are built around vacuum tubes, and it is the nature of these tubes to require direct current (usually at a fairly high voltage) for their operation. They convert the direct current into an alternating current (and sometimes the reverse) at frequencies varying from ones well down in the audio range to well up in the superhigh range. The conversion process almost invariably requires that the direct and alternating currents meet somewhere in the circuit.

In this meeting, the a.c. and d.c. are actually combined into a single current that "pulsates" (at the a.c. frequency) about an average value equal to the direct current. This is shown in Fig. 2-47. It is easier, though, to think of them

separately and to consider that the alternating current is superimposed on the direct current. Thus we look upon the actual current as having two components, one d.c. and the other a.c.

If the alternating current is a sine wave, its positive and negative alternations have the same maximum amplitude. When the wave is superimposed on a direct current the latter is alternately increased and decreased by the same amount. There is thus no average change in the direct current. If a d.c. instrument is being used to read the current, the reading will be exactly the same whether or not the sine-wave a.c. is superimposed.

However, there is actually more power in such a combination current than there is in the direct current alone. This is because power



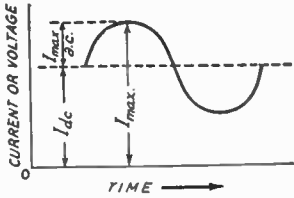


Fig. 2-47 — Pulsating current, composed of an alternating current or voltage superimposed on a steady direct current or voltage.

varies as the *square* of the instantaneous value of the current, so more power is added to the circuit on the half-cycle of the a.c. wave that *increases* the instantaneous current than is subtracted on the half-cycle that *decreases* it. If the peak value of the alternating current is just equal to the direct current, the average power in the circuit is 1.5 times the power in the direct current alone.

In many circuits, also, we may have two alternating currents of different frequencies; for example, an audio frequency and a radio frequency may be combined in the same circuit. The two in turn may be combined with a direct current. In some cases, too, two r.f. currents of widely-different frequencies may be combined in the same circuit.

**Series and Parallel Feed**

Fig. 2-48 shows in simplified form how d.c. and a.c. may be combined in a vacuum-tube circuit. (The tube is shown only in bare outline; so far as the d.c. is concerned, it can be looked upon as a resistance of rather high value. On the other hand, the tube may be looked upon as the *generator* of the a.c. The mechanism of tube operation is described in the next chapter.) In this case, we have assumed that the a.c. is at radio frequency, as suggested by the coil-and-condenser tuned circuit. We also assume that r.f. current can easily flow through the d.c. supply; that is, the impedance of the supply at radio frequencies is so small as to be negligible.

In the circuit at the left, the tube, tuned circuit, and d.c. supply all are connected in series. The direct current flows through the r.f. tuned circuit to get to the tube; the r.f. current generated by the tube flows through the d.c. supply to get to the tuned circuit. This is **series feed**. It works because the impedance of the d.c. supply at radio frequencies is so low that it does not affect the flow of r.f. current, and because the d.c. resistance of the coil is so low that it does not affect the flow of direct current.

In the circuit at the right the direct current does not flow through the r.f. tuned circuit, but instead goes to the tube through a second coil, *RFC* (radio-frequency choke). Direct current cannot flow through *L* because a **blocking condenser**, *C*, is placed in the circuit to prevent it. (Without *C*, the d.c. supply would be short-circuited by the low resistance of *L*.) On the other hand, the r.f. current generated by the tube can easily flow through *C* to the tuned circuit because the capacitance

of *C* is intentionally chosen to have low reactance (compared with the impedance of the tuned circuit) at the radio frequency. The r.f. current cannot flow through the d.c. supply because the inductance of *RFC* is intentionally made so large that it has a very high reactance at the radio frequency. The resistance of *RFC*, however, is too low to have an appreciable effect on the flow of direct current. The two currents are thus in *parallel*, hence the name **parallel feed**.

Both types of feed are in use. They may be used for both a.f. and r.f. circuits. In parallel feed there is no d.c. voltage on the a.c. circuit (the blocking condenser prevents that); this is a desirable feature from the viewpoint of safety to the operator, because the voltages applied to tubes — particularly transmitting tubes — are dangerous to human beings. On the other hand, it is somewhat difficult to make an r.f. choke work well over a wide range of frequencies. Series feed is usually preferred, therefore, because it is relatively easy to keep the impedance between the a.c. circuit and the tube low.

**By-Passing**

In the series-feed circuit just discussed, it was assumed that the d.c. supply had very low impedance at radio frequencies. This is not likely to be true in a practical power supply — if for no other reason than that the normal physical separation between the supply and the r.f. circuit would make it necessary to use rather long connecting wires or leads. At radio frequencies, even a few feet of wire can have fairly large reactance — too large to be considered a really “low-impedance” connection.

To get around this, an actual circuit would be provided with a **by-pass condenser**, as shown in Fig. 2-49. Condenser *C* is chosen to have low reactance at the operating frequency, and is installed right in the circuit where it can be wired to the other parts with quite short connecting wires. (The condenser will be an open circuit for the d.c. voltage across which it is connected, of course.) Since condenser *C* offers a low-impedance path, the r.f. current will tend to flow through it rather than through the d.c. supply; thus the current is confined to a known path rather than one of dubious impedance through the power supply.

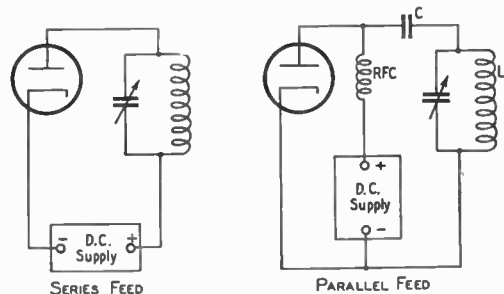


Fig. 2-48 — Illustrating series and parallel feed.

To be effective, a by-pass should have very low impedance compared to the impedance of the circuit element around which it is supposed to shunt the current. The reactance of the condenser should not be more than one-tenth of the impedance of the by-passed part of the circuit. Very often the latter impedance is not known, in which case it is desirable to use the largest capacitance in the by-pass that circumstances permit. To make doubly sure that r.f. current will not flow through a non-r.f. circuit such as a power supply, an r.f. choke may be connected in the lead to the latter, as shown in Fig. 2-49. The choke, having high reactance, will prevent the r.f. from going where it is not wanted and thereby ensure that it goes where it is wanted — i.e., through the by-pass condenser.

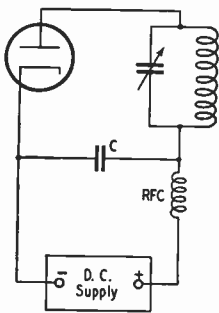


Fig. 2-49 — Typical use of a by-pass condenser in a series-feed circuit.

The use of a by-pass condenser is not confined only to circuits where r.f. is to be kept out of a d.c. source. The same type of by-passing is used when audio frequencies are present in addition to r.f. Because the reactance of a condenser changes with frequency, it is readily possible to choose a capacitance that will represent a very low reactance at radio frequencies but that will have such high reactance at audio frequencies that it is practically an open circuit. A capacitance of 0.001  $\mu$ f. is practically a short-circuit for r.f., for example, but is almost an open circuit at audio frequencies. (The actual value of capacitance that is usable will be modified by the impedances concerned.)

By-pass condensers also are used in audio-frequency circuits, to carry the audio frequencies around a d.c. supply. In this case a capacitance of several microfarads is needed if the reactance is to be low enough at the lower audio frequencies.

#### Distributed Capacitance and Inductance

In the discussions earlier in this chapter it was assumed that a condenser has only capacitance and that a coil has only inductance. Unfortunately, this is not strictly true. There is always a certain amount of inductance in a conductor of any length, and since a condenser is made up of conductors it is bound to have a little inductance in addition to its intended capacitance. Also, there is always capacitance

between two conductors or between parts of the same conductor, and so we find that there is appreciable capacitance between the turns of an inductance coil.

This distributed inductance in a condenser and the distributed capacitance in a coil have important practical effects. Actually, every condenser is a tuned circuit, resonant at the frequency where its capacitance and distributed inductance have the same reactance. The same thing is true of a coil and its distributed capacitance. At frequencies well below these "natural" resonances, the condenser will act like a normal capacitance and the coil will act like a normal inductance. Near the natural resonant points, the coil and condenser act like self-tuned circuits. Above resonance, the condenser acts like an inductance and the coil acts like a condenser. If we want our circuit components to behave properly, they must always be used at frequencies well on the low side of their natural resonances.

Because of these effects, there is a limit to the amount of capacitance that can be used at a given frequency. There is a similar limit to the inductance that can be used. At audio frequencies, capacitances measured in microfarads and inductances measured in henrys are practicable. At low and medium radio frequencies, inductances of a few millihenrys and capacitances of a few thousand micromicrofarads are the largest practicable. At high radio frequencies, usable inductance values drop to a few microhenrys and capacitances to a few hundred micromicrofarads.

Distributed capacitance and inductance are important not only in r.f. tuned circuits, but in by-passing and choking as well. It will be appreciated that a by-pass condenser that actually acts like an inductance, or an r.f. choke that acts like a condenser, cannot work as it is intended they should. That is why you will find, in the circuits described later in this *Handbook*, by-pass condenser capacitances and r.f.-choke inductances that may look rather small — considering that, theoretically, a larger condenser or larger coil should be even more effective at its job.

#### Grounds.

Throughout this book you will find frequent references to ground and ground potential. When a connection is said to be "grounded" it does not mean that it actually goes to earth (although in many cases such earth connections are used). What it means, more often, is that an actual earth connection *could* be made to that point in the circuit without disturbing the operation of the circuit in any way. The term also is used to indicate a "common" point in the circuit where power supplies and metallic supports (such as a metal chassis) are electrically tied together. It is customary, for example, to "ground" the negative terminal of a d.c. power supply, and to "ground" the filament or heater power supplies for vacuum

tubes. Since the cathode of a vacuum tube is a junction point for grid and plate voltage supplies, it is a natural point to "ground." Also, since the various circuits connected to the tube elements have at least one point connected to cathode, these points also are "returned to ground."

"Ground" is therefore a common reference point in the circuit. In circuit diagrams, it is customary (for the sake of making the diagrams easier to read) to show such common connections by the ground symbol rather than by showing a large number of wires all connected together.

"Ground potential" means that there is no "difference of potential" — that is, no voltage — between the circuit point and the earth. A direct earth connection at such a point would cause no disturbance to the operation of the circuit.

### Single-Ended and Balanced Circuits

With reference to ground, a circuit may be either single-ended (unbalanced) or balanced. In a single-ended circuit, one *side* of the circuit is connected to ground. In a balanced circuit, the *electrical midpoint* of the circuit is connected to ground, so that the circuit has two ends each at the same voltage "above" ground. A balanced circuit also is called a "symmetrical" circuit.

Typical single-ended and balanced circuits are shown in Fig. 2-50. R.f. circuits are shown in the upper line, while iron-core transformers (such as are used in power-supply and audio circuits) are shown in the lower line. The r.f. circuits may be balanced either by connecting the center of the coil to ground or by using a "balanced" or "split-stator" condenser — that is, one having two identical sets of stator and rotor plates with the rotor plates on the same shaft — and connecting the condenser rotor to ground. In the iron-core transformer, one or both windings may be tapped at the center of the winding to provide the ground connection.

In the single-ended circuit, only one side of the circuit is "hot" — that is, has a voltage that differs from ground potential. In the balanced circuit, both ends are "hot" and the grounded center point is "cold" — that is, at ground potential. The applications of both types of circuits are discussed in later chapters.

### Nonlinear Circuits; Beats

The circuits that have been discussed in this chapter are, essentially, ones obeying Ohm's Law. That is, an increase or decrease of the applied voltage causes an exactly proportional increase or decrease in current. (This neglects relatively minor effects such as the temperature rise and consequent change in resistance of conductors with increasing current, etc.) However, many devices (such as vacuum tubes under some conditions of operation) do not obey any such straightforward rules. There may be no current flow at

all with an applied voltage of one polarity, but the current may be large if the polarity of the voltage is reversed. Also, the current may increase with increasing voltage up to a certain point and then stay at a fixed value no matter how much more the voltage is raised. Such devices, and the circuits in which they are used, are called **non-linear**.

One important result of nonlinearity is the behavior of the circuit when two or more alternating currents of different frequencies are flowing in it. In a normal circuit, the two frequencies will have no particular effect on each other. However, if two (or more) alternating currents of different frequencies are present in a nonlinear circuit, additional currents having frequencies equal to the sum, and difference, of the original frequencies will be set up. These sum and difference frequencies are called the **beat frequencies**. For example, if frequencies of 2000 and 3000 kc. are present in a normal circuit only those two frequencies exist, but if they are passed through a nonlinear circuit there will be present in the output not only the two original frequencies of 2000 and 3000 kc. but also currents of 1000 (3000 - 2000) and 5000 (3000 + 2000) kc. Suitable circuits can be used to select the desired beat frequency.

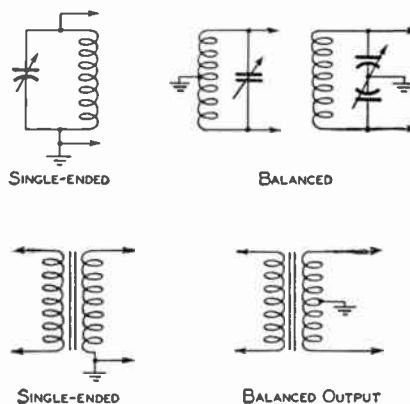


Fig. 2-50 — Single-ended and balanced circuits.

Beat frequencies are generated, and used to advantage, in very many radio circuits. For example, all of our modern reception methods are based on the use of beat frequencies.

### Shielding

Two circuits that are physically near each other usually will be coupled to each other in some degree even though no coupling is intended. The metallic parts of the two circuits form a small capacitance through which energy can be transferred by means of the electric field. Also, the magnetic field about the coil or wiring of one circuit can couple that circuit to a second through the latter's coil and wiring. In many cases these unwanted couplings must be

prevented if the circuits are to work properly.

Capacitive coupling may readily be prevented by enclosing one or both of the circuits in grounded low-resistance metallic containers, called shields. The electric field from the circuit components does not penetrate the shield, because the lines of force are short-circuited by the metal. A metallic plate, called a baffle shield, inserted between two components also may suffice to prevent electrostatic coupling between them. Very little of the field tends to bend around such a shield if it is large enough to make the components invisible to each other.

Similar metallic shielding is used at radio frequencies to prevent magnetic coupling. In this case the magnetic field induces a current in the shield; this current in turn sets up its own magnetic field opposing the original field. The amount of current induced is proportional to the frequency and also to the conductivity of the shield; therefore the shielding effect increases with frequency and with the conductivity and thickness of the shielding material.

A closed shield is required for good magnetic shielding; in some cases separate shields, one about each coil, may be required. The baffle shield is rather ineffective for magnetic shielding, although it will give partial shielding if placed at right angles to the axes of, as well as

between, the two coils to be shielded from each other.

Shielding a coil reduces its inductance, because part of its field is canceled. Also, there is always a small amount of resistance in the shield, and there is therefore an energy loss. This loss raises the effective resistance of the coil. The decrease in inductance and increase in resistance lower the  $Q$  of the coil. The reduction in inductance and  $Q$  will be small if the shield is sufficiently far away from the coil; the spacing between the sides of the coil and the shield should be at least half the coil diameter, and the spacing at the ends of the coil should at least equal the coil diameter. The higher the conductivity of the shield material, the less the effect on the inductance and  $Q$ . Copper is the best material, but aluminum is quite satisfactory.

At low (audio) frequencies this type of magnetic shielding does not work, because the current induced in the shield is too small. For good shielding at audio frequencies it is necessary to enclose the coil in a container of high-permeability iron or steel. This provides a much better path for the magnetic flux than air — so much so that most of the stray flux stays in the iron in preference to spreading out in the space around the coil. In this case the shield can be quite close to the coil without harming its performance.

# Vacuum-Tube Principles

Present-day methods of radio communication rely heavily on the vacuum tube. The tube is used to generate radio-frequency power, to amplify it in transmitters, to amplify and detect weak radio signals picked up from distant stations, to magnify the human voice, to change alternating current into direct current for power supplies — in fact, to do innumerable things that, without it, could not be done. An understanding of vacuum-tube principles is just as necessary to the radio amateur as an understanding of the circuit principles discussed in Chapter Two.

In this chapter we shall confine ourselves to the *fundamentals* of vacuum-tube operation. The special circuits and special types of tubes

that find application in amateur radio will be taken up in later chapters.

The operation of vacuum tubes can be predicted mathematically, just as the operation of circuits can be predicted from mathematical formulas. It happens, though, that the amateur rarely has need to perform any calculations in connection with vacuum tubes, other than simple ones having to do with the power supplies for the tube elements. These are straightforward applications of Ohm's Law. Tube manufacturers invariably supply sets of data that give optimum operating conditions for their tubes, and thus save any need for calculation. What you need, to get the most out of your tubes, is mostly a picture of how they work.

## Diodes and Rectification

### ● CURRENT IN A VACUUM

The outstanding difference between the vacuum tube and most other electrical devices is that the electric current does not flow through a conductor but through empty space — a vacuum. This is only possible when "free" electrons — that is, electrons that are not attached to atoms — are somehow introduced into the vacuum. It will be recalled from Chapter Two that electrons are particles of negative electricity. Free electrons in an evacuated space therefore can be attracted to a positively-charged object within the same space, or can be repelled by a negatively-charged object. The movement of the electrons under the attraction or repulsion of such charged objects constitutes the current in the vacuum.

The most practical way to introduce a sufficiently-large number of electrons into the evacuated space is by **thermionic emission**.

#### *Thermionic Emission*

If a thin wire or filament is heated to incandescence in a vacuum, electrons near the surface are given enough energy of motion to fly off into the surrounding space. The higher the temperature, the greater the number of electrons emitted. A more general name for the filament is **cathode**.

If the cathode is the only thing in the vacuum, most of the emitted electrons stay in its immediate vicinity, forming a "cloud" about the cathode. The reason for this is that

the electrons in the space, being negative electricity, form a negative charge (**space charge**) in the region of the cathode. The negatively-charged space repels those electrons nearest the cathode, tending to make them fall back on it.

Now suppose a second conductor is introduced into the vacuum, but not connected to anything else inside the tube. If this second conductor is given a positive charge with respect to the cathode, electrons in the space will be attracted to the positively-charged conductor. The conductor can be given the requisite charge by connecting a source of e.m.f. between it and the cathode, as indicated in Fig. 3-1. The electrons emitted by the cathode and attracted to the positively-



charged conductor then constitute an electric current, with the circuit completed through the source of e.m.f. In Fig. 3-1 this e.m.f. is supplied by a battery ("B" battery); a second battery ("A" battery) is also indicated for heating the cathode or filament to the proper operating temperature.

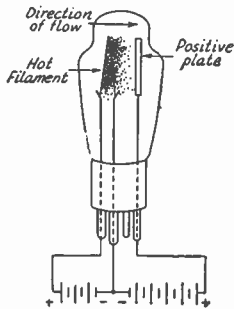


Fig. 3-1 — Conduction by thermionic emission in a vacuum tube. One battery is used to heat the filament to a temperature that will cause it to emit electrons. The other battery makes the plate positive with respect to the filament, thereby causing the emitted electrons to be attracted to the plate. Electrons captured by the plate flow back through the battery to the filament.

The positively-charged conductor is usually a metal plate or cylinder (surrounding the cathode) and is called an **anode** or **plate**. Like the other working parts of a tube, it is a tube element or electrode. The tube shown in Fig. 3-1 is a two-element or two-electrode tube, one element being the cathode or filament and the other the anode or plate.

Since electrons are *negative* electricity, they will be attracted to the plate *only* when the plate is positive with respect to the cathode. If the plate is given a negative charge, the electrons will be repelled back to the cathode and no current will flow in the vacuum. The vacuum tube therefore can conduct *only in one direction*.

### Cathodes

Before electron emission can occur, the cathode must be heated to a high temperature. The only satisfactory way to heat it is by electricity. However, it is not essential that the heating current flow through the actual metal that does the emitting. The filament or heater can be electrically separate from the emitting cathode, and very many tubes are built that way. Such a cathode is called *indirectly heated*, while an emitting filament is called *directly heated*. Fig. 3-2 shows both types in the forms in which they are commonly used.

Obviously, the cathode should emit as many electrons as possible with the least possible heating power. A plain metal cathode is quite inefficient in this respect. Much greater electron emission can be obtained at relatively low tem-

peratures, by using special cathode materials. One of these is **thoriated tungsten**, or tungsten in which thorium is dissolved. Still greater efficiency is achieved in the **oxide-coated cathode**, a cathode in which rare-earth oxides form a coating over a metal base.

Although the oxide-coated cathode has much the highest efficiency, it can be used successfully only in tubes that operate at rather low plate voltages. Its use is therefore confined to receiving-type tubes and to the smaller varieties of transmitting tubes. The thoriated filament, on the other hand, will operate well in high-voltage tubes and is therefore found in most of the transmitting types used by amateurs.

### Plate Current

The number of electrons attracted to the plate depends upon the strength of the positive charge on the plate — that is, on the amount of voltage between the cathode and plate. The electron current — called the **plate current** — increases as the plate voltage is increased (although the relationship is not the simple proportionality of Ohm's Law). Actually, this statement is true only up to a certain point; if the plate voltage is made high enough, *all* the electrons emitted by the cathode would be attracted to the plate. Obviously, when this occurs, a further increase in plate voltage cannot cause an increase in plate current.

Fig. 3-3 shows a typical plot of plate current with increasing plate voltage for a two-element tube or diode. A curve of this type can be obtained with the circuit shown, if the plate voltage can be increased in small steps and a current reading taken (by means of the current-indicating instrument — a "milliammeter") at each voltage. The plate current is zero with no plate voltage and the curve rises almost in a straight line until a "saturation point" is reached. This is where the positive

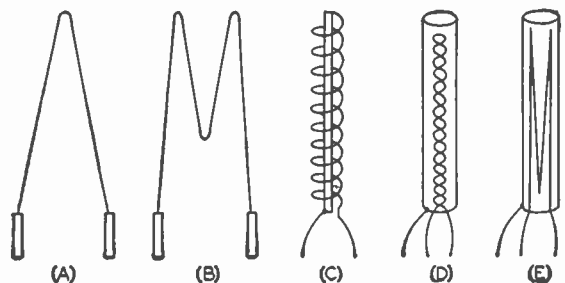


Fig. 3-2 — Types of cathode construction. Directly-heated cathodes or filaments are shown at A, B, and C. The inverted V filament is used in small receiving tubes, the M in both receiving and transmitting tubes. The spiral filament is a transmitting-tube type. The indirectly-heated cathodes at D and E show two types of heater construction, one a twisted loop and the other bunched heater wires. Both types tend to cancel the magnetic fields set up by the current through the heater.

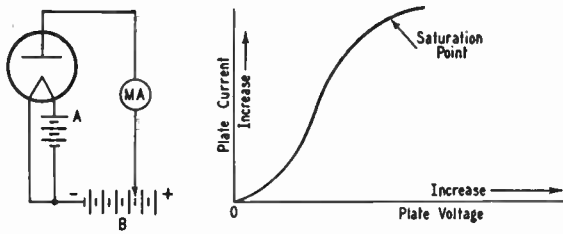


Fig. 3-3 — The diode, or two-element tube, and a typical curve showing how the plate current depends upon the voltage applied to the plate.

charge on the plate has completely overcome the space charge and practically all the electrons are going to the plate. At any higher voltages the plate current stays at the same value.

The curve of Fig. 3-3 does not show actual values of plate voltage and plate current, since these will vary with the type of tube. The shape of the curve, however, is typical of all diodes.

The plate voltage multiplied by the plate current is the *power input* to the tube. In a circuit like that of Fig. 3-3 this power is all used in heating the plate. If the power input is large, the plate temperature may rise to a very high value (the plate may become red or even white hot). The heat developed in the plate is radiated to the bulb of the tube, and in turn radiated by the bulb to the surrounding air.

is, during the half-cycle when the upper end of the transformer winding is positive. During the negative half-cycle there is simply a gap in the current flow. This rectified alternating current therefore is an *intermittent* direct current. (The "humps" in the output current may be smoothed out by a "filter.") A filter uses inductance and capacitance to store up energy during the time that current flows through the diode, energy that is then released to the circuit during the period when the diode is non-conducting. Filters of this type are discussed in later chapters.)

The load resistor, *R*, represents the actual circuit in which the rectified alternating current does work. All tubes work into a load of one type or another; in this respect a tube is much like a generator or transformer. A circuit that did not provide a load for the tube would be like a short-circuit across a transformer; no useful purpose would be accomplished and the only result would be the generation of heat in the transformer. So it is with vacuum tubes;

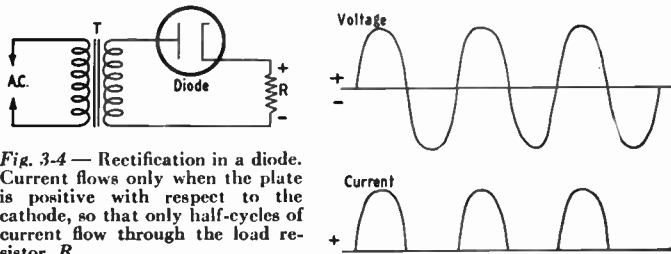


Fig. 3-4 — Rectification in a diode. Current flows only when the plate is positive with respect to the cathode, so that only half-cycles of current flow through the load resistor, *R*.

## ● RECTIFICATION

Since current can flow through a tube in only one direction, a diode can be used to change alternating current into direct current. It does this by permitting current to flow when the plate is positive with respect to the cathode, but by shutting off current flow when the plate is negative.

Fig. 3-4 shows a representative circuit. Alternating voltage from the secondary of the transformer, *T*, is applied to the diode tube in series with a load resistor, *R*. The voltage varies as is usual with a.c., but current flows through the tube and *R* only when the plate is positive with respect to the cathode — that

they must *deliver* power to a load in order to serve a useful purpose. Also, to be *efficient* most of the power must do useful work in the load and not be used in heating the plate of the tube. This means that most of the voltage should appear as a drop across the load rather than as a drop between the plate and cathode of the diode. That is, the "resistance" of the tube should be small compared to the resistance of the load.

Notice that, with the diode connected as shown in Fig. 3-4, the polarity of the voltage drop across the load is such that the end of the load nearest the cathode is positive. If the connections to the diode elements are reversed, the direction of rectified current flow also will be reversed through the load.

## Vacuum-Tube Amplifiers

### ● TRIODES

#### Grid Control

It was shown in Fig. 3-3 that, within the normal operating range of a tube, the plate current will increase when the plate voltage

is increased. The reason why all the electrons are not drawn to the plate when a *small* positive voltage is placed on it is that the space charge (which is negative) counteracts the effect of the positive charge on the plate. The higher the positive plate voltage, the more

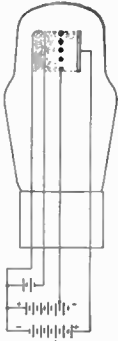


Fig. 3-5 — Construction of an elementary triode vacuum tube, showing the filament, grid (with an end view of the grid wires) and plate. The relative density of the space charge is indicated roughly by the dot density.

effectively the space charge is overcome.

If a third element — called the **control grid**, or simply **grid** — is inserted between the cathode and plate as in Fig. 3-5, it can be used to control the effect of the space charge. If the grid is given a positive voltage with respect to the cathode, the positive charge will tend to neutralize the negative space charge. The result is that, at any selected plate voltage, more electrons will flow to the plate than if the grid were not present. On the other hand, if the grid is made negative with respect to the cathode the negative charge on the grid will *add* to the space charge. This will *reduce* the number of electrons that can reach the plate at any selected plate voltage.

The grid is inserted in the tube to control the space charge and not to attract electrons to itself, so it is made in the form of a wire mesh or spiral. Electrons then can go through the open spaces in the grid and to the plate.

#### Characteristic Curves

For any particular tube, the effect of the grid voltage on the plate current can be shown by a set of **characteristic curves**. A typical set of curves is shown in Fig. 3-6, together with the circuit that is used for getting them. With several fixed values of plate voltage (in these curves, the plate voltage is increased in 50-volt steps, starting at 100 volts) the grid voltage is varied in small steps and a plate-current reading taken at each value of grid voltage. The curves show the result. In Fig. 3-6, the grid voltage is varied between zero and 25 volts negative with respect to the cathode. It can be seen that, for each value of plate voltage, there is a value of negative grid voltage that will reduce the plate current to zero; that is, there is a value of negative grid voltage that will cut off the plate current.

The curves could be extended by making the grid voltage positive as well as negative. The practical effect would be to lengthen each of the curves upward along the same line. However, in some types of operation the grid is

always kept negative with respect to the cathode, and the particular tube used as an illustration happens to be one that normally would be used that way. Whenever the grid is negative, it repels electrons and therefore none of them reaches it; in other words, no current flows in the grid circuit. When the grid is positive, it attracts electrons and a current (**grid current**) flows, just as current flows to the positive plate. Whenever there is grid current there is an accompanying power loss in the grid circuit, but so long as the grid is negative there is no current and therefore no power is used.

It is obvious that the grid can act as a valve to control the flow of plate current. Actually, the grid has a much greater effect on plate current flow than does the plate voltage. A *small* change in grid voltage is just as effective in bringing about a given change in plate current as is a *large* change in plate voltage.

The fact that a small voltage acting on the grid is equivalent to a large voltage acting on the plate indicates the possibility of **amplification** with the triode tube; that is, the generation of a large voltage by a small one, or the generation of a relatively large amount of power from a small amount. The many uses of the electronic tube nearly all are based upon this amplifying feature. The amplified power or voltage output from the tube is not obtained from the tube itself, but from the source of e.m.f. connected between its plate and cathode. The tube simply *controls* the power from this source, changing it to the desired form.

To utilize the controlled power, a load must be connected in the plate or "output" circuit, just as in the diode case. The load may be either a resistance or an impedance. The term "impedance" is frequently used even when the load is purely resistive.

#### Tube Characteristics

The physical construction of a triode determines the relative effectiveness of the grid and plate in controlling the plate current. If a very small change in the grid voltage has just as much effect on the plate current as a very large change in plate voltage, the tube is said

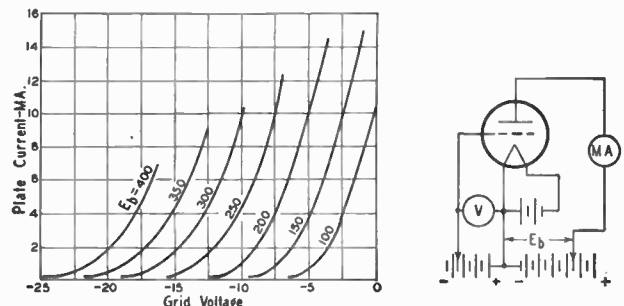


Fig 3-6 — Grid-voltage-vs.-plate-current curves at various fixed values of plate voltage ( $E_b$ ) for a typical small triode. Characteristic curves of this type can be taken by varying the battery voltages in the circuit at the right.



to have a high amplification factor. Amplification factor is commonly designated by the Greek letter  $\mu$ . An amplification factor of 20, for example, means this: if the grid voltage is changed by 1 volt, the effect on the plate current will be the same as when the plate voltage is changed by 20 volts. The amplification factors of triode tubes range from 3 to something of the order of 100. A high- $\mu$  tube is one with an amplification factor of perhaps 30 or more; medium- $\mu$  tubes have amplification factors in the approximate range 8 to 30, and low- $\mu$  tubes in the range below 7 or 8.

It would be natural to think that a tube that has a large  $\mu$  would be the best amplifier, but such is not necessarily the case. If the  $\mu$  is high it is difficult for the plate to attract large numbers of electrons. Quite a large change in the plate voltage must be made to effect a given change in plate current. This means that the resistance of the plate-cathode path — that is, the plate resistance — of the tube is high. Since this resistance acts in series with the load, the amount of current that can be made to flow through the load is relatively small. On the other hand, the plate resistance of a low- $\mu$  tube is relatively low. Whether or not a high- $\mu$  tube is better than one with a low  $\mu$  depends on the operation we want the tube to perform.

The best all-around indication of the effectiveness of the tube as an amplifier is its **transconductance** — also called **mutual conductance**. This characteristic takes account of both amplification factor and plate resistance, and therefore is a sort of figure of merit for the tube. Actually, transconductance is the change in plate current divided by the change in grid voltage that causes the plate-current change (the plate voltage being fixed at a desired value). Since current divided by voltage is equal to conductance, transconductance is measured in the unit of conductance, the mho. Practical values of transconductance are very small, so the micromho (one-millionth of a mho) is the commonly-used unit. Different types of tubes have transconductances ranging from a few hundred to several thousand. The higher the transconductance the greater the possible amplification.

● AMPLIFICATION

To understand amplification, it is first necessary to become acquainted with a type of graph called the **dynamic characteristic**. Such a graph, together with the circuit used for obtaining it, is shown in Fig. 3-7. The curves are taken with the plate-supply voltage fixed at the desired operating value. The difference between this circuit and the one shown in Fig. 3-6 is that there is a load resistance connected in series with the plate of the tube in Fig. 3-7, while there is none in Fig. 3-6. Fig.

3-7 thus shows how the plate current will vary, with different grid voltages, when the plate current is made to flow through a load and thus do useful work.

The several curves in Fig. 3-7 are for various values of load resistance. The effect of the amount of load resistance is worth noting. When the resistance is small (as in the case of the 5000-ohm load) the plate current changes rather rapidly with a given change in grid voltage. If the load resistance is high (as in the 100,000-ohm curve), the change in plate current for the same grid-voltage change is relatively small, so the curve tends to be straighter.

Going now to Fig. 3-8, we have the same type of curve, but with the circuit arranged so that a source of alternating voltage (signal) is inserted between the grid and the grid battery ("C" battery). The voltage of the grid battery is fixed at -5 volts, and from the curve

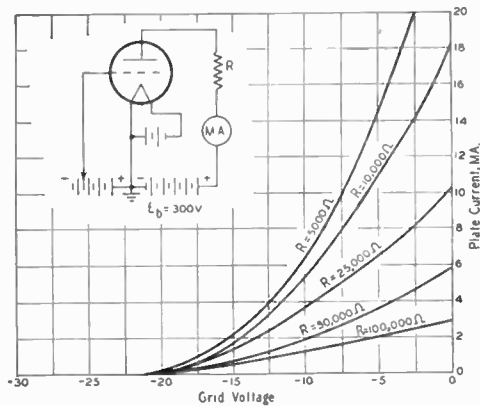


Fig. 3-7 — Dynamic characteristics of a small triode with various load resistances from 5000 to 100,000 ohms.

it is seen that the plate current at this grid voltage is 2 milliamperes. This current flows when the load resistance is 50,000 ohms, as indicated in the circuit diagram. If there is no a.e. signal in the grid circuit, the voltage drop in the load resistor is  $50,000 \times 0.002 = 100$  volts, leaving 200 volts between the plate and cathode.

Now when a sine-wave signal having a peak value of 2 volts is applied in series with the bias voltage in the grid circuit, the instantaneous voltage at the grid will swing to -3 volts at the instant the signal reaches its positive peak, and to -7 volts at the instant the signal reaches its negative peak. The maximum plate current will occur at the instant the grid voltage is -3 volts. As shown by the graph, it will have a value of 2.65 milliamperes. The minimum plate current occurs at the instant the grid voltage is -7 volts, and has a value of 1.35 ma. At intermediate values of grid voltage, intermediate plate-current values will occur.

The instantaneous voltage between the plate and cathode of the tube also is shown on the

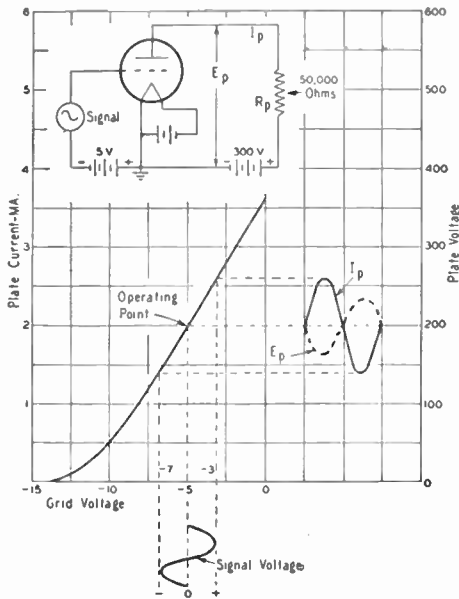


Fig. 3-8 — Amplifier operation. When the plate current varies in response to the signal applied to the grid, a varying voltage drop appears across the load,  $R_p$ , as shown by the dashed curve,  $E_p$ .  $I_p$  is the plate current.

graph. When the plate current is maximum, the instantaneous voltage drop in  $R_p$  is  $50,000 \times 0.00265 = 132.5$  volts; when the plate current is minimum the instantaneous voltage drop in  $R_p$  is  $50,000 \times 0.00135 = 67.5$  volts. The actual voltage between plate and cathode is the difference between the plate-supply potential, 300 volts, and the voltage drop in the load resistance. The plate-to-cathode voltage is therefore 167.5 volts at maximum plate current and 232.5 volts at minimum plate current.

This varying plate voltage is an a.c. voltage superimposed on the steady plate-cathode potential of 200 volts (as previously determined for no-signal conditions). The peak value of this a.c. output voltage is the difference between either the maximum or minimum plate-cathode voltage and the no-signal value of 200 volts. In the illustration this difference is  $232.5 - 200$  or  $200 - 167.5$ ; that is, 32.5 volts in either case. Since the grid signal voltage has a peak value of 2 volts, the voltage-amplification ratio of the amplifier is  $32.5/2$  or 16.25. That is, approximately 16 times as much voltage is obtained from the plate circuit as is applied to the grid circuit.

One feature of the alternating component of plate voltage is worth special note. As shown by the drawings in Fig. 3-8, the positive swing in the grid signal voltage is accompanied by a downward swing in the voltage ( $E_p$ ) between the plate and cathode of the tube. Also, when the alternating grid voltage swings in the negative direction, the plate-to-cathode voltage swings to a higher value. In other words, the

alternating component of the plate voltage swings in the negative direction (with reference to the no-signal value of plate-cathode voltage) when the grid swings in the positive direction, and vice versa. This means that the alternating component of plate voltage (that is, the amplified signal) is 180 degrees out of phase with the signal voltage on the grid.

### Bias

The fixed negative grid voltage (called grid bias) in Fig. 3-8 serves a very useful purpose. In the first place, one of the things we want to do in the type of amplification shown in this drawing is to obtain, from the plate circuit, an alternating voltage that has the same waveshape as the signal voltage applied to the grid. To do so, we must choose an operating point on the straight part of the curve; not only that, the curve must be straight in both directions from the operating point at least far enough to accommodate the maximum value of the signal applied to the grid. If the grid signal swings the plate current back and forth, over a part of the curve that is not straight, as in Fig. 3-9, the shape of the a.c. wave in the plate circuit will not be the same as the shape of the grid-signal wave. In such a case the output waveshape will be distorted.

The second reason for using negative grid bias is this: The grid will not attract electrons — that is, there will be no grid current — if the grid is always negative with respect to the cathode. When the grid has a negative bias, any signal whose peak positive voltage does not exceed the fixed negative voltage on the grid cannot cause grid current to flow. With no current flow there is no power consumption, so the tube will amplify without taking any power from the signal source. However, if the positive

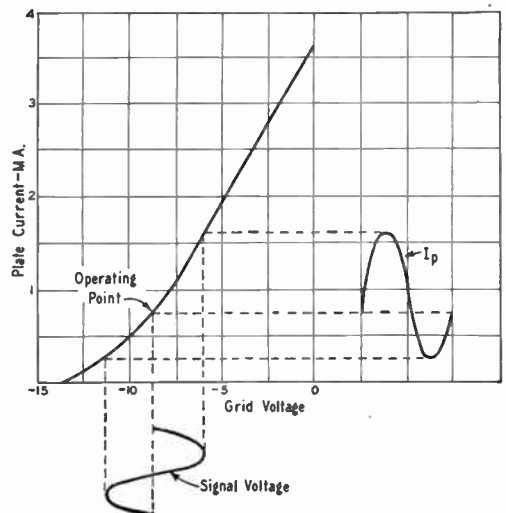


Fig. 3-9 — Harmonic distortion resulting from choice of an operating point on the curved part of the tube characteristic. The lower half-cycle of plate current does not have the same shape as the upper half-cycle.

peak of the signal does exceed the negative bias, current will flow in the grid circuit during the time the grid is positive. While it is perfectly possible to operate the tube in the "positive-grid region," in many cases we do not want the grid to consume power.

Distortion of the output waveshape that results from working over a part of the curve that is not straight (that is, a **nonlinear** part of the curve) has the effect of transforming a sine-wave grid signal into a more complex waveform. As explained in Chapter Two, a complex wave can be resolved into a fundamental and a series of harmonics. In other words, distortion from nonlinearity causes the generation of harmonic frequencies — frequencies that are not present in the signal applied to the grid. Harmonic distortion is undesirable in most amplifiers, although there are occasions when harmonics are deliberately generated and used. This is particularly so in certain types of r.f. transmitting circuits.


### Amplifier Output Circuits

The thing that is wanted from the output circuit of a vacuum-tube amplifier is the *alternating* component of plate current or plate voltage. The d.c. voltage on the plate of the tube is essential, of course, for the tube's operation. However, it almost invariably would cause difficulties if it were applied, along with the a.c. output voltage, to the load. The output circuits of vacuum tubes are therefore arranged so that the a.c. is transferred to the load but the d.c. is not.


Three types of coupling are in common use at audio frequencies. These are **resistance coupling**, **impedance coupling**, and **transformer coupling**. They are shown in Fig. 3-10. In all three cases the output is shown coupled to the grid circuit of a subsequent amplifier tube, but the same types of circuits can be used to couple to other devices than tubes.

In the resistance-coupled circuit, the a.c. voltage developed across the plate resistor  $R_p$  (that is, between the plate and cathode of the tube) is applied to a second resistor,  $R_g$ , through a coupling condenser,  $C_c$ . The condenser "blocks off" the voltage on the plate of the first tube and prevents it from being applied to the grid of tube  $B$ . The latter tube should have negative grid bias, of course, and this is supplied by the battery shown. No current flows in the grid circuit of tube  $B$  and there is therefore no d.c. voltage drop in  $R_g$ ; in other words, the full voltage of the bias battery is applied to the grid of tube  $B$ .


The grid resistor,  $R_g$ , usually has a rather high value (0.5 to 2 megohms). The reactance of the coupling condenser,  $C_c$ , must be low enough compared to the resistance of  $R_g$  so that the a.c. voltage drop in  $C_c$  is negligible at the lowest frequency to be amplified. If  $R_g$  is at least 0.5 megohm, a 0.1- $\mu$ fd. condenser will be amply large for the usual range of audio frequencies.

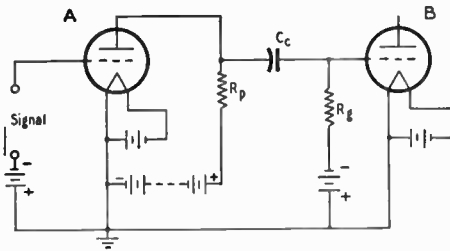

RESISTANCE COUPLING

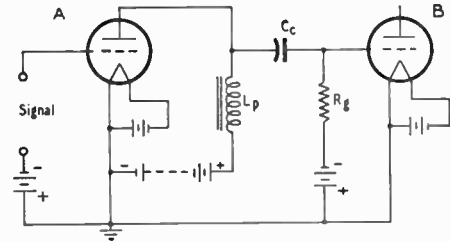

IMPEDANCE COUPLING

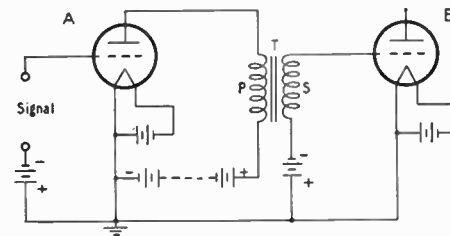

TRANSFORMER COUPLING

Fig. 3-10 — Three basic forms of coupling between vacuum-tube amplifiers.

So far as the alternating component of plate voltage is concerned, it will be realized that if the voltage drop in  $C_c$  is negligible then  $R_p$  and  $R_g$  are effectively in parallel (although they are quite separate so far as d.c. is concerned). The resultant parallel resistance of the two is therefore the actual load resistance for the tube. That is why  $R_g$  is made as high in resistance as possible; then it will have the least effect on the load represented by  $R_p$ .

The impedance-coupled circuit differs from that using resistance coupling only in the substitution of a high-inductance coil (usually several hundred henrys) for the plate resistor. The advantage of using an inductance rather than a resistor is that its impedance is high for alternating currents, but its resistance is relatively low for d.c. (A resistor, of course, has the same resistance for d.c. that it does for a.c.). It thus permits us to obtain a high value of load impedance for a.c., but without an excessive d.c. voltage drop that would use up a good deal of the voltage from the plate supply.

The transformer-coupled amplifier uses a transformer with its primary connected in the

plate circuit of the tube and its secondary connected to the load (in the circuit shown, a following amplifier). There is no direct connection between the two windings, so the plate voltage on tube *A* is isolated from the grid of tube *B*. The transformer-coupled amplifier has the same advantage as the impedance-coupled circuit with respect to loss of voltage from the plate supply. There is an additional advantage as well: if the secondary has more turns than the primary, the output voltage will be "stepped up" in proportion to the turns ratio.

All three circuits have good points. Resistance coupling is simple, inexpensive, and will give the same amount of amplification — or voltage gain — over a wide range of frequencies; it will give substantially the same amplification at any frequency in the audio range, for example. Impedance coupling will give somewhat more gain, with the same tube and same plate-supply voltage, than resistance coupling. However, it is not quite so good over a wide frequency range; it tends to "peak," or give maximum gain, over a comparatively narrow band of frequencies. With a good transformer the gain of a transformer-coupled amplifier can be kept fairly constant over the audio-frequency range. On the other hand, transformer coupling is best suited to triodes having amplification factors of about 10 or less, for the reason that the primary inductance of a practicable transformer cannot be made large enough to work well with a tube having high plate resistance.

#### Voltage and Power Amplifiers

In the preceding discussion of amplifiers we have talked chiefly about voltage gain. That is only part of the picture. The end result of any amplification is that the amplified signal does some *work*. As a familiar example, an audio-frequency amplifier usually drives a loudspeaker that in turn produces sound waves. The greater the amount of a.f. *power* supplied to the 'speaker, the louder the sound it will produce.

In some amplifiers, therefore, *power* output rather than voltage is the primary consideration. A tube is operated somewhat differently when we want the greatest possible power than it is when we want the largest possible voltage. It is chiefly a matter of the resistance of the load. It was mentioned in Chapter Two that any source of power will deliver the largest possible output when the resistance of the load is equal to the internal resistance of the source. In the case of a vacuum tube, the "source" resistance is the plate resistance of the tube. Therefore if we want the utmost power from the tube the load resistance should be equal to the plate resistance of the tube. Actually, however, this is not the best operating condition because the use of such a relatively low value of load resistance generally results in more distortion than we want.

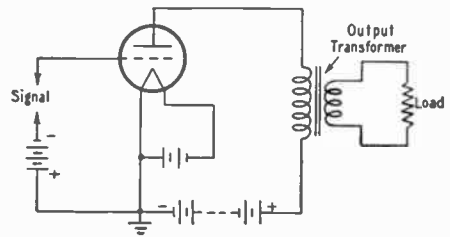


Fig. 3-11 — An elementary power-amplifier circuit in which the power-consuming load is coupled to the plate circuit through an impedance-matching transformer.

For this reason the load resistance for a power amplifier usually is two or three times the plate resistance; this represents a good compromise between distortion and power output.

Fig. 3-11 shows an elementary power-amplifier circuit. It is simply a transformer-coupled amplifier with the load connected to the secondary. Although the load is shown as a resistor, it actually would be some device, such as a loudspeaker, that employs the power usefully. The resistance of the actual load is rarely the right value for "matching" the load resistance that the tube wants for optimum power output. Therefore the transformer turns ratio is chosen to reflect the proper value of resistance into the primary. The turns ratio may be either step-up or step-down, depending on whether the actual load resistance is higher or lower than the load the tube wants.

About the only time that voltage rather than power is wanted is when a tube is working into a following amplifier, as in the circuits given in Fig. 3-10. Even then, this is only so when the grid of the second tube always operates in the negative-voltage region. If the signal applied to its grid is large enough to overcome the bias and make grid current flow, power is consumed and special methods are required for transferring maximum power rather than maximum voltage. There are, nevertheless, many useful applications for tube circuits intended to deliver maximum voltage rather than maximum power. The chief difference is that the load resistance is made as high as possible for a voltage amplifier. This means that of the total voltage generated (part of which is lost in the plate resistance of the tube), the major portion will appear across the load resistance if the latter is large compared to the tube resistance. The amount of power that can be obtained under these conditions is small, but the voltage output is large.

Resistance- and impedance-coupled amplifiers are primarily voltage amplifiers, because neither type is capable of transferring power efficiently. For efficient power transfer the transformer is a practical necessity.

The best triodes for power amplification are those having low and medium values of amplification factor. High- $\mu$  tubes make the best

voltage amplifiers, but have relatively little power output. These statements are true principally for amplifiers operating without grid current, which is the only type we have considered so far. Other types of operation are taken up in later chapters. A tube operated in the fashion we have described is called a Class A amplifier.

The **power-amplification ratio** of an amplifier is the ratio of the power output obtained from the plate circuit to the power required from the a.c. signal in the grid circuit. There is no power lost in the grid circuit of a Class A amplifier that is operating without grid current, so such an amplifier has an infinitely large power-amplification ratio. Another term used in connection with power amplifiers is **power sensitivity**. It means the ratio of the power output to the grid signal voltage that causes it. A tube with high power sensitivity is one that will give a large power output with a relatively small signal voltage on its grid.

### Parallel and Push-Pull

When it is necessary to obtain more power output than one tube is capable of giving, two or more tubes may be connected in **parallel**. In this case the similar elements in all tubes are connected together. This method is shown in Fig. 3-12 for a transformer-coupled amplifier. The power output is in proportion to the number of tubes used; the grid signal or "exciting" voltage required, however, is the same as for one tube.

If the amplifier operates in such a way as to consume power in the grid circuit, the grid power required also is in proportion to the number of tubes used.

An increase in power output also can be secured by connecting two tubes in **push-pull**. In this case the grids and plates of the two tubes are connected to opposite ends of a balanced circuit as shown in Fig. 3-12. At any

instant the ends of the secondary winding of the input transformer,  $T_1$ , will be at opposite polarity with respect to the cathode connection, so the grid of one tube is swung positive at the same instant that the grid of the other is swung negative. Hence, in any push-pull-connected amplifier the voltages and currents of one tube are out of phase with those of the other tube.

In push-pull operation the even-harmonic (second, fourth, etc.) distortion is balanced out in the plate circuit. This means that for the same power output the distortion will be less than with parallel operation.

The exciting voltage measured between the two grids must be twice that required for one tube. If the grids consume power, the driving power for the push-pull amplifier is twice that taken by either tube alone.

### Cascade Amplifiers

It is of course thoroughly possible to take the output of one amplifier and apply it as a signal on the grid of a second amplifier, then take the second amplifier's output and apply it to a third, and so on. Each amplifier is called a stage, and a number of amplifier stages used to successively increase the amplitude of the signal are said to be in **cascade**.

The number of amplifiers that can be connected in cascade is not unlimited. If the overall amplification becomes too great, there is danger that some of the output voltage will get back into one of the early stages. This "feedback," discussed in the next section, may make the amplifier unstable and prevent it from functioning as it should.

## ● FEED-BACK

As we have shown, there is more energy in the plate circuit of an amplifier than there is in the grid circuit. It is easily possible to take a part of the plate-circuit energy and insert it into the grid circuit. When this is done the amplifier is said to have **feedback**.

There are two types of feedback. If the voltage that is inserted in the grid circuit is 180 degrees out of phase with the signal voltage acting on the grid, the feedback is called **negative**, or **degenerative**. On the other hand, if the voltage is fed back *in phase* with the grid signal, the feedback is called **positive**, or **regenerative**. With negative feedback the voltage that is fed back *opposes* the signal voltage; this decreases the amplitude of the voltage acting between the grid and cathode. With a smaller signal voltage, of course, the output also is smaller. The effect of negative feedback, then, is to *reduce* the amount of amplification.

### Negative Feed-Back

The circuit shown at A in Fig. 3-13 gives degenerative feedback. Resistor  $R_c$  is in series with the regular plate resistor,  $R_p$ , and

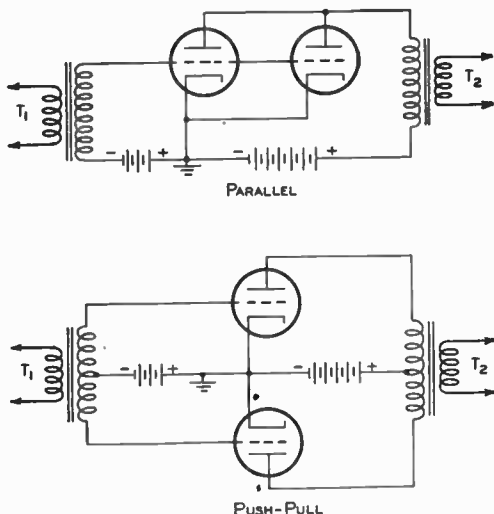


Fig. 3-12 — Parallel and push-pull a.f. amplifier circuits.

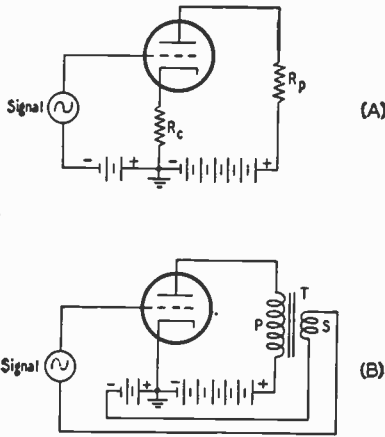


Fig. 3-13—Circuits for producing feed-back. In A, part of the a.c. plate voltage appears across the cathode resistor,  $R_c$ , and is therefore also applied between grid and cathode. The feed-back is negative in this case. In B, the voltage that is generated in the secondary of the transformer is inserted in series in the grid circuit. Feed-back may be either positive or negative, depending upon the transformer connections.

thus is a part of the load for the tube. Therefore, part of the output voltage will appear across  $R_c$ . However,  $R_c$  also is connected in series with the *grid* circuit, and so the output voltage that appears across  $R_c$  is in series with the signal voltage. In this circuit, the output voltage across  $R_c$  opposes the signal voltage and the actual a.c. voltage between the grid and cathode therefore is equal to the *difference* between the two voltages.

While it would be natural to assume that there could be no point in reducing the amplification by negative feed-back, it does have uses. The greater the amount of negative feed-back (when properly applied) the more independent the amplification becomes of tube characteristics and circuit conditions. This means that the frequency-response characteristic of the amplifier becomes *flat*—that is, amplification tends to be the same at all frequencies within the range for which the amplifier is designed. Also, any distortion generated in the plate circuit of the tube tends to “buck itself out” when some of the output voltage is fed back to the grid. Amplifiers with negative feed-back are therefore comparatively free of harmonic distortion. These advantages, secured at the expense of voltage amplification, are worth while if the amplifier otherwise has enough gain for its intended use.

The circuit shown at B in Fig. 3-13 can be used to give either negative or positive feed-back. In this case the secondary of a transformer is connected back into the grid circuit to insert a desired amount of feed-back voltage. Reversing the terminals of either the primary or secondary of the transformer (but not both windings simultaneously) will reverse the phase of the voltage fed back. Thus either type of feed-back is available.

### Positive Feed-Back

Positive feed-back *increases* the amplification because the fed-back voltage adds to the original signal voltage and the resulting larger voltage on the grid causes a larger output voltage. It has the opposite characteristics to negative feed-back; the amplification tends to be greatest at one frequency (depending upon the particular circuit arrangement) and harmonic distortion is increased. If the energy fed back becomes large enough, a self-sustaining oscillation will be set up at one frequency; in this case *all* the signal voltage on the grid is supplied from the plate circuit; no external signal is needed. It is not even necessary to have an external signal to *start* the oscillation; any small irregularity in the plate current—and there are always some such irregularities—will be amplified and thus give the oscillation an opportunity to build up. Oscillations obviously would be undesirable in an audio-frequency amplifier, and for that reason (as well as the others mentioned above) positive feed-back is never used in a.f. amplifiers. Positive feed-back finds its use in “oscillators” at both audio and radio frequencies, as described in a subsequent section.

The two circuits shown in Fig. 3-13 are only two of many that can be used to provide feed-back. Despite differences in appearance, such circuits are alike in this fundamental—energy is fed back from the output circuit to the grid circuit in the proper phase to give the type of feed-back that is wanted.

### ● INTERELECTRODE CAPACITANCES

Each pair of elements in a tube actually forms a small “condenser,” with each element acting as a condenser “plate.” There are three such capacitances in a triode—that between the grid and cathode, that between the grid and plate, and that between the plate and cathode. The capacitances are very small—only a few micromicrofarads at most—but they frequently have a very pronounced effect on the operation of an amplifier circuit.

#### Input Capacitance

It was explained previously that the a.c. grid voltage and a.c. plate voltage of an amplifier are 180 degrees out of phase, using the cathode of the tube as a reference point. However, these two voltages are *in phase* if we go around the circuit from plate to grid as shown in Fig. 3-14. This means that their sum is acting between the grid and plate; that is, across the grid-plate capacitance of the tube. When an a.c. voltage is applied to a condenser, a current flows through the condenser. As viewed from the source of the signal on the grid, this current is flowing because of the signal voltage.

The larger the current, the lower the effective reactance in the grid circuit. The larger the grid-plate capacitance the larger the current;

also, the greater the voltage amplification the larger the current, because this puts more voltage across the grid-plate condenser. The result is that the source of signal "sees" a capacitive reactance that is much smaller than the actual reactance of the capacitance between the grid and cathode.

Since a small reactance is equivalent to a large capacitance, the input capacitance of an amplifier may be many times its actual grid-cathode capacitance. In practice, the input capacitance of a triode may be as much as a few hundred micromicrofarads, particularly if the triode has a large amplification factor. Such a capacitance is not negligible, even at audio frequencies, when it is placed in parallel with a resistor of 50,000 ohms or more.

### Tube Capacitance at R.F.

At radio frequencies the reactances of the interelectrode capacitances drop to such low values that they must always be taken into account in circuit design. A resistance-coupled amplifier cannot be used at r.f., for example, because the reactances of the interelectrode "condensers" are so low that they, and not the resistors, would be the actual load. Furthermore, they are so low that they practically short-circuit the input and output circuits and thus the tube is unable to amplify. We get around this at radio frequencies by using *tuned* circuits for the grid and plate, and making the tube capacitances part of the tuning capacitances. In this way the circuits can have the high impedances necessary for satisfactory amplification.

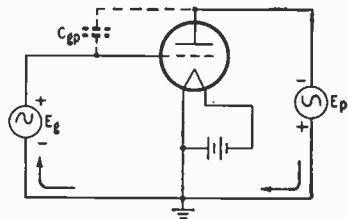


Fig. 3-14 — The a.c. voltage appearing between the grid and plate of the amplifier is the sum of the signal voltage and the output voltage, as shown by this simplified circuit. Instantaneous polarities are indicated.

The grid-plate capacitance is important at radio frequencies because it is, in effect, a coupling condenser between the grid and plate circuits. Since its reactance is relatively low at r.f., it offers a path over which energy can be fed back from the plate to the grid. In practically every case the feed-back is in the right phase and of sufficient amplitude to cause oscillation, so the amplifier becomes useless. Special circuits can be used to prevent feed-back but they are, in general, not too satisfactory when used in radio receivers. (They are, however, widely used in transmitters.) A better solution to this problem is found in the use of the screen-grid tube.

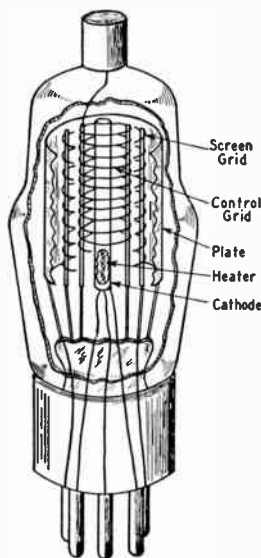


Fig. 3-15 — Representative arrangement of elements in a screen-grid tube, with front part of plate and screen grid cut away. In this drawing the control-grid connection is made through a cap on the top of the tube, thus eliminating the capacitance that would exist between the plate-and grid-lead wires if both passed through the base. Some modern tubes that have both leads going through the base use special shielding and construction to eliminate interlead capacitance.

## ● SCREEN-GRID TUBES

The grid-plate capacitance can be eliminated — or at least reduced to a negligible value — by inserting a second grid between the control grid and the plate, as indicated in Fig. 3-15. The second grid, called the **screen grid**, acts as a shield between the control grid and plate. It is made in the form of a grid or coarse screen so that electrons can pass through it; a solid shield would entirely prevent the flow of plate current. The screen grid is usually grounded through a by-pass condenser that has low reactance at the radio frequency being amplified.

Because of the shielding action of the screen grid, the plate voltage cannot control the flow of plate current as it does in a triode. In order to get electrons to the plate, it is necessary to apply a positive voltage (with respect to the cathode) to the screen. The screen then attracts electrons much as does the plate in a triode tube. In traveling toward the screen the electrons acquire such velocity that most of them shoot between the screen wires and go on to the plate. A certain proportion do strike the screen, however, with the result that some current also flows to the screen-grid circuit of the tube.

A tube having a cathode, control grid, screen grid and plate (four elements) is called a **tetrode**.

### Pentodes

When an electron traveling at appreciable velocity through a tube strikes the plate it dislodges other electrons which "splash" from the plate into the interelement space. This is called **secondary emission**. In a triode the negative grid repels the secondary electrons back into the plate and they cause no disturbance. In

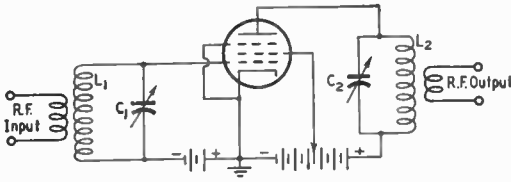


Fig. 3-16 — Simplified pentode r.f.-amplifier circuit.  $L_1C_1$  and  $L_2C_2$  are tuned to the same frequency.

the screen-grid tube, however, the positively-charged screen *attracts* the secondary electrons, causing a reverse current to flow between screen and plate.

To overcome the effects of secondary emission, a third grid, called the **suppressor grid**, may be inserted between the screen and plate. This grid, which usually is connected directly to the cathode, repels the relatively low-velocity secondary electrons. They are driven back to the plate without appreciably obstructing the regular plate-current flow. A five-element tube of this type is called a **pentode**.

Although the screen grid in either the tetrode or pentode greatly reduces the influence of the plate upon plate-current flow, the control grid still can control the plate current in essentially the same way that it does in a triode. Consequently, the grid-plate transconductance (or mutual conductance) of a tetrode or pentode will be of the same order of value as in a triode of corresponding structure. On the other hand, since the plate voltage has very little effect on the plate-current flow, both the amplification factor and plate resistance of a pentode or tetrode are very high. In small receiving pentodes the amplification factor is of the order of 1000 or higher, while the plate resistance may be from 0.5 to 1 or more megohms. Because of the high plate resistance, the actual voltage amplification possible with a pentode is very much less than the large amplification factor might indicate. A voltage gain in the vicinity of 50 to 200 is typical of a pentode stage.

#### Pentode R.F. Amplifier

Fig. 3-16 shows a simplified form of r.f. amplifier circuit, using a pentode tube. Radio-frequency energy in the small coil coupled to  $L_1$  is built up in voltage in the tuned circuit,  $L_1C_1$ , when  $L_1C_1$  is tuned to resonance with the frequency of the incoming signal. The voltage that appears across  $L_1C_1$  is applied to the grid and cathode of the tube and is amplified by the tube. A second resonant circuit,  $L_2C_2$ , is the load for the plate of the tube, its parallel impedance being high because it is tuned to resonance with the frequency applied to the grid. R.f. output can be taken from the coil coupled to  $L_2$ . The screen-grid voltage is obtained from a tap on the plate battery; most tubes are designed for operation with the

screen voltage considerably lower than the plate voltage. In this circuit the batteries are assumed to have low impedance for the r.f. current; in a practical circuit, by-pass condensers would be used to make sure that the impedances of the return paths actually are low enough to be negligible.

In addition to their applications as radio-frequency amplifiers, pentode or tetrode screen-grid tubes also can be constructed for audio-frequency power amplification. In tubes designed for this purpose the shielding effect of the screen grid is not so important; the chief function of the screen is to serve as an accelerator of the electrons, so that large values of plate current can be drawn at relatively low plate voltages. Such tubes have quite high power sensitivity compared to triodes of the same power output. Harmonic distortion is somewhat greater with pentodes and tetrodes than with triodes, however.

#### Variable- $\mu$ Tubes

The mutual conductance of a vacuum tube decreases with increasing negative grid bias, assuming that the other electrode voltages are held constant. Since the mutual conductance controls the amount of amplification, it is possible to adjust the gain of the amplifier by adjusting the grid bias. This method of gain control is universally used in radio-frequency amplifiers designed for receivers. Some means of controlling the r.f. gain is essential in a receiver having a number of amplifiers, because of the wide range in the strengths of the incoming signals.

The ordinary type of tube has what is known as a **sharp cut-off characteristic**. The mutual conductance decreases at a uniform rate as the

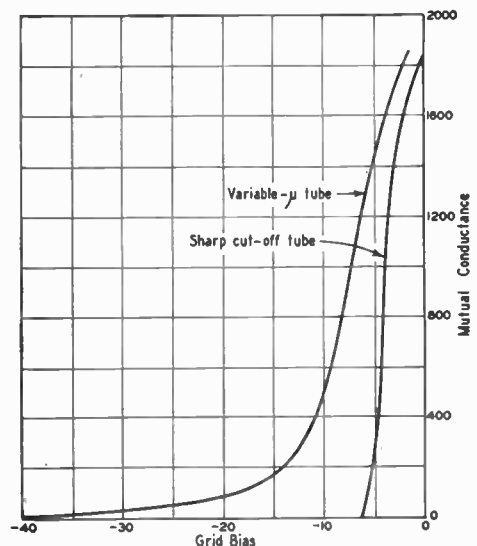


Fig. 3-17 — Curves showing the relationship between mutual conductance and negative grid bias for two small receiving pentodes, one a sharp cut-off type and the other a variable- $\mu$  type.



negative bias is increased, as shown in Fig. 3-17. The amount of signal voltage that such a tube can handle without causing distortion is quite limited, and not sufficient to take care of very strong signals. To overcome this, some tubes are made with a variable- $\mu$  characteristic (that is, the amplification factor changes with the grid bias), resulting in the type of curve shown in Fig. 3-17. It is evident that the variable- $\mu$  tube can handle a much larger signal than the sharp cut-off type before the signal swings either beyond the zero grid-bias point or the plate-current cut-off point.

## OTHER TYPES OF AMPLIFIERS

In the amplifier circuits so far discussed, the signal has been applied between the grid and cathode and the amplified output has been taken from the plate-to-cathode circuit. That is, the *cathode* has been the common point, or meeting point, for the input and output circuits. However, since there are three elements (the screen and suppressor in a pentode ordinarily do not enter *directly* into the amplifying action) it is possible to use any one of the three as the common point. This leads to two different kinds of amplifiers, commonly called the grounded-grid amplifier (or grid-separation circuit) and the cathode follower.


These two circuits are shown in simplified form in Fig. 3-18. In both circuits the resistor  $R$  represents the load into which the amplifier works; the actual load may be resistance-capacitance-coupled, transformer-coupled, may be a tuned circuit if the amplifier operates at radio frequencies, and so on. Also, in both circuits the batteries that supply grid bias and plate power are assumed to have such negligible impedance that they do not enter into the operation of the circuits.

### Grounded-Grid Amplifier

In the grounded-grid amplifier the input signal is applied between the cathode and grid, and the output is taken between the plate and grid. The grid is thus the common element. The plate current (including the a.c. component) has to flow through the signal source to reach the cathode. Since this source always has appreciable impedance, the alternating plate current causes a voltage drop that acts between the grid and cathode. Because of the phase relationship between the signal and output voltages, the circuit is degenerative. Also, since the source of signal is in series with the load through the plate-to-cathode resistance of the tube, some of the power in the load is supplied by the signal source. The result of these two things is that the signal source is called upon to furnish a considerable amount of power.

The grounded-grid amplifier finds its chief application at v.h.f. and u.h.f., where the more conventional amplifier circuit fails to work properly. With a triode tube designed for

Fig. 3-18 — In the upper circuit, the grid is the junction point between the input and output circuits. In the lower drawing, the plate is the junction. In either case the output is developed in the load resistor,  $R$ , and may be coupled to a following amplifier by the usual methods.

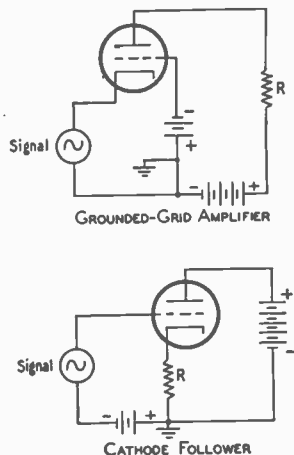

this type of operation, an r.f. amplifier can be built that is free from the type of feed-back that causes oscillation. This requires that the grid act as a shield between the cathode and plate, reducing the plate-cathode capacitance to a very low value.

### Cathode Follower

The cathode follower uses the plate of the tube as the common element. The input signal is applied between the grid and plate (assuming negligible impedance in the batteries) and the output is taken from between cathode and plate. This circuit, like the grounded-grid amplifier, is degenerative. In fact, *all* of the output voltage is fed back into the input circuit to buck the applied signal. The input signal therefore has to be larger than the output voltage; in other words, the cathode follower not only gives no voltage gain but actually results in a *loss* in voltage. (It can still give just as much *power* gain as ever, though.)

The cathode follower has two advantages: It has a very high input impedance (impedance between grid and ground—in the customary cathode-follower circuit the plate is at ground for signal voltage); and its output impedance is very low. (The large amount of negative feed-back has the effect of greatly reducing the plate resistance of the tube.) These two characteristics are valuable in an amplifier that must work over a very wide range of frequencies. Also, the high input impedance and low output impedance can be used to obtain an impedance step-down over wide ranges of frequencies that could not possibly be covered by a transformer. The cathode follower is useful both at audio and radio frequencies.

## CATHODE CIRCUITS AND GRID BIAS

Most of the equipment used by amateurs is powered by the a.c. line. This includes the filaments or heaters of vacuum tubes. Although supplies for the plate (and sometimes the grid) are usually rectified and filtered to

give "pure" d.c. — that is, direct current that is constant and without a superimposed a.c. component — the relatively large currents required by filaments and heaters make a d.c. supply impracticable.

### Filament Hum

Alternating current is just as good as direct current from the heating standpoint, but some of the a.c. voltage is likely to get on the grid and cause a low-pitched "a.c. hum" to be superimposed on the output. The voltage can get on the grid either by a direct circuit connection, through the electric field about the heater, or through the magnetic field set up by the current.

Hum troubles are worst with directly-heated cathodes or filaments, because with such cathodes there has to be a direct connection between the source of heating power and the rest of the circuit. The hum can be minimized by either of the connections shown in Fig. 3-19. In both cases the grid and plate-return circuits are connected to the electrical midpoint (center-tap) of the filament supply. Thus, so far as the grid and plate are concerned, the voltage and current on one side of the filament are balanced by an equal and opposite voltage and current on the other side. This balances out the hum. The balance is never quite perfect, however, so filament-type tubes are never completely hum-free. For this reason directly-heated filaments are used chiefly in transmitting power tubes, where the amount of hum introduced is quite small in comparison to the power-output level.

With indirectly-heated cathodes the source of heating power does not introduce hum by a direct connection. The chief problem with such tubes is the magnetic field set up by the heater. Occasionally, also, there is leakage between the heater and cathode; leakage that allows a small a.c. voltage to get to the grid. Both these things are principally a matter of tube design. However, it is found in practice that, if hum appears, grounding one side of the heater supply will help to reduce it. Sometimes better results are obtained if the heater supply is center-tapped and the center-tap grounded, as in Fig. 3-19.

### Cathode Bias

In the simplified amplifier circuits discussed in this chapter, grid bias has been supplied by a battery. However, it is seldom obtained that way in an actual piece of equipment that operates from the power line. **Cathode bias** is the type commonly used.

The cathode-bias method uses a resistor connected in series with the cathode, as shown at *R* in Fig. 3-20. The direction of plate-current

flow is such that the end of the resistor nearest the cathode is positive. The voltage drop across *R* therefore places a *negative* voltage on the grid. This negative bias is obtained from the steady d.c. plate current.

If the alternating component of plate current flows through *R* when the tube is amplifying, the voltage drop caused by the a.c. will be degenerative (note the similarity between this circuit and that of Fig. 3-13A). To prevent this the resistor is by-passed by a condenser, *C*, that has very low reactance compared to the resistance of *R*. The capacitance required at *C* depends upon the value of *R* and the frequency being amplified. Depending on the type of tube and the particular kind of operation, *R* may be between about 250 and 3000 ohms. For good by-passing at the low audio frequencies, *C* should be 10 to 50 micro-

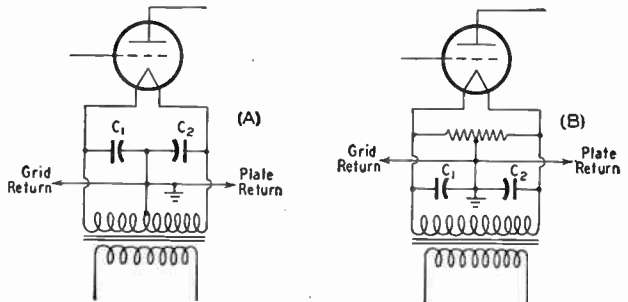


Fig. 3-19 — Filament center-tapping methods for use with directly-heated tubes.

farads (electrolytic condensers are used for this purpose). At radio frequencies, capacitances of about 100  $\mu\text{fd.}$  to 0.1  $\mu\text{fd.}$  are used; the small values are sufficient at very high frequencies and the largest at low and medium frequencies. In the range 3 to 30 megacycles a capacitance of 0.01  $\mu\text{fd.}$  is satisfactory.

The value of cathode resistor can easily be calculated from the known operating conditions of the tube. The proper grid bias and plate current always are specified by the manufacturer. Knowing these, the required resistance can be found by applying Ohm's Law.

Example: It is found from tube tables that the tube to be used should have a negative grid bias of 8 volts and that at this bias the plate current will be 12 milliamperes (0.012 amp.). The required cathode resistance is then

$$R = \frac{E}{I} = \frac{8}{0.012} = 667 \text{ ohms.}$$

The nearest standard value, 680 ohms, would be close enough. The power used in the resistor is

$$P = EI = 8 \times 0.012 = 0.096 \text{ watt.}$$

A  $\frac{1}{4}$ -watt or  $\frac{1}{2}$ -watt resistor would have ample rating.

The current that flows through *R* is the *total* cathode current. In an ordinary triode amplifier this is the same as the plate current, but in a screen-grid tube the cathode current is the sum of the plate and screen currents.

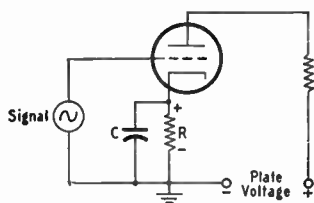


Fig. 3-20 — Cathode biasing. *R* is the cathode resistor and *C* is the cathode by-pass condenser.

Hence these two currents must be added when calculating the value of cathode resistor required for a screen-grid tube.

Example: A receiving pentode requires 3 volts negative bias. At this bias and the recommended plate and screen voltages, its plate current is 9 ma. and its screen current is 2 ma. The cathode current is therefore 11 ma. (0.011 amp.). The required resistance is

$$R = \frac{E}{I} = \frac{3}{0.011} = 272 \text{ ohms.}$$

A 270-ohm resistor would be satisfactory. The power in the resistor is

$$P = EI = 3 \times 0.011 = 0.033 \text{ watt.}$$

The cathode resistor method of biasing is convenient because it avoids the use of batteries or other source of fixed voltage. However, that is not its only advantage: it is also self-regulating, because if the tube characteristics vary slightly from the published values (as they do in practice) the bias will increase if the plate current is slightly high, or decrease if it is slightly low. This tends to hold the plate current at the proper value. For the same reason, the value of the cathode resistance is not highly critical. Cathode bias also avoids any tendency toward unwanted feed-back that might occur when a single fixed-bias source is used to furnish bias for several amplifiers. Even a very small a.c. voltage drop in the impedance of a bias source can cause oscillation (if the feedback is positive) or loss of gain (if the feedback is negative) when the voltage is applied to the first stage of amplification in an amplifier having several stages, simply because the gain in a multistage amplifier is likely to be very large.

The calculation of the bias resistor in a resistance-coupled amplifier is not as easy as the examples above. This is because the actual voltages that should be used on the plate and grid are not ordinarily known. The difficulty is that the voltage drop in the plate resistor causes the actual voltage at the plate of the tube to be considerably less than the plate-supply voltage, and the lower plate voltage requires a different value of bias than that given in the published operating conditions for the tube. The proper voltages can be found by a cut-and-try process from the tube characteristic curves. However, representative data for the tubes commonly used as resistance-coupled amplifiers are given in Chapter Nine, including cathode-resistor values.

## Screen Supply

In practical circuits using tetrodes and pentodes the voltage for the screen frequently is taken from the plate supply through a resistor. A typical circuit for an r.f. amplifier is shown in Fig. 3-21. Resistor *R* is the screen dropping resistor, and *C* is the screen by-pass condenser. In flowing through *R*, the screen current causes a voltage drop in *R* that reduces the plate-supply voltage to the proper value for the screen. When the plate-supply voltage and the screen current are known, the value of *R* can be calculated from Ohm's Law.

Example: An r.f. receiving pentode has a rated screen current of 2 milliamperes (0.002 amp.) at normal operating conditions. The rated screen voltage is 100 volts, and the plate supply gives 250 volts. To put 100 volts on the screen, the drop across *R* must be equal to the difference between the plate-supply voltage and the screen voltage; that is,  $250 - 100 = 150$  volts. Then

$$R = \frac{E}{I} = \frac{150}{0.002} = 75,000 \text{ ohms.}$$

The power to be dissipated in the resistor is

$$P = EI = 150 \times 0.002 = 0.3 \text{ watt.}$$

A  $\frac{1}{2}$ - or 1-watt resistor would be satisfactory.

The reactance of the screen by-pass condenser, *C*, should be low compared with the screen-to-cathode impedance. For radio-frequency applications a capacitance of 0.01  $\mu\text{fd}$ . is amply large.

In some circuits the screen voltage is obtained from a voltage divider connected across the plate supply. The design of voltage dividers is discussed in Chapter Seven.

## SPECIAL TUBE TYPES

### Beam Tubes

"Beam tetrodes" are tetrode tubes constructed in such a way that the power sensitivity is very high. Beam tubes are useful as both radio-frequency and audio-frequency power amplifiers, and are available in output ratings from a few watts up to several hundred watts. The grids in a beam tube are so constructed and aligned as to form the electrons traveling to the plate into concentrated beams. This makes it possible to draw large plate currents at relatively low plate voltages, and also

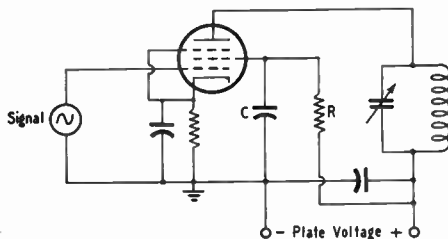


Fig. 3-21 — Screen-voltage supply for a pentode tube through a dropping resistor, *R*. The screen by-pass condenser, *C*, must have low enough reactance to bring the screen to ground potential for the frequency or frequencies being amplified.

reduces the number of electrons that are captured by the screen. Additional design features overcome the effects of secondary emission, so that a suppressor grid is not needed.

Beam tubes are used with the same circuits, and operated in the same way, as conventional tetrodes and pentodes.

#### Multipurpose Tubes

A number of "combination" tubes are available to perform more than one function, particularly in receiver circuits. For the most part these are simply multiunit tubes made up of individual tube-element structures, combined in a single bulb for compactness and economy.

Among the simplest multipurpose types are full-wave rectifiers, combining two diodes in one envelope, and twin triodes, consisting of two triodes in one bulb. More complex types include duplex-diode triodes (two diodes and a triode in one structure), duplex-diode pentodes, converters and mixers (for superheterodyne receivers), combination power tubes and rectifiers, and so on. In many cases the nature of the tubes so combined can be identified by the name given the composite structure.

#### Mercury-Vapor Rectifiers

For a given value of plate current, the power lost in a diode rectifier will be reduced if it is possible to decrease the voltage drop from plate to cathode. A small amount of mercury in the tube will vaporize when the cathode is

heated and, further, will ionize when plate voltage is applied. The positive ions neutralize the space charge and reduce the plate-cathode voltage drop to a practically constant value of about 15 volts, regardless of the value of plate current.

Since this voltage drop is smaller than can be attained with purely thermionic conduction, there is less power loss in a mercury-vapor rectifier than in a vacuum rectifier. Also, the voltage drop in the tube is constant despite variations in load current. Mercury-vapor tubes are widely used in rectifiers built to deliver large power outputs.

#### Grid-Control Rectifiers

If a grid is inserted in a mercury-vapor rectifier it is found that, with sufficient negative grid bias, it is possible to prevent plate current from flowing. However, this is true *only if the bias is present before plate voltage is applied*. If the bias is lowered to the point where plate current can flow, the mercury vapor will ionize and the grid will lose control of plate current, because the space charge disappears when ionization occurs. The grid can assume control again only after the plate voltage is reduced below the ionizing voltage.

The same phenomenon also occurs in triodes filled with other gases that ionize at low pressure. Grid-control rectifiers or thyratrons find considerable application in "electronic switching."

## Oscillators

It was mentioned earlier in this chapter that if there is enough positive feed-back in an amplifier circuit, self-sustaining oscillations will be set up. When an amplifier is arranged so that this condition exists it is called an oscillator.

Oscillations normally take place at only one frequency, and a desired frequency of oscillation can be obtained by using a resonant circuit tuned to that frequency. The proper phase for positive feed-back can be obtained quite easily from a single tuned circuit. For example, in Fig. 3-22A the circuit  $LC$  is tuned to the desired frequency of oscillation. The coil  $L$  is tapped and the cathode of the tube is connected to the tap. The grid and plate are connected to opposite ends of the tuned circuit. There will be a voltage drop across the tuned circuit, a voltage drop that increases progressively along the turns of the coil when viewed from one end. At an instant when the upper end of  $L$  is positive, for instance, the lower end is negative. However, the tap on the coil is at an intermediate voltage and so is negative with respect to the upper end of  $L$ , and positive with respect to the lower end. Or, viewed from the tap, the upper end of  $L$  is positive and the lower end is negative. There-

fore the grid and plate ends of the coil are opposite in polarity, or opposite in phase. This is the right phase relationship for positive feed-back.

The amount of feed-back depends on the position of the tap. If the tap is too close to either end of the coil the circuit will not oscillate. If the tap is too near the grid end the voltage drop is too small to give enough feed-back, and if it is too near the plate end the impedance between the cathode and plate is too small to permit good amplification. Maximum feed-back usually is obtained when the tap is somewhere near the center of the coil.

It will be observed that the circuit of Fig. 3-22A is parallel fed,  $C_b$  being the blocking condenser. The value of  $C_b$  is not critical so long as its reactance is low at the operating frequency.

Condenser  $C_g$  is the grid condenser. It and  $R_g$  (the grid leak) are used for the purpose of obtaining grid bias for the tube. In this (and practically all) oscillator circuits the tube generates its own bias. When the grid end of the tuned circuit is positive with respect to the cathode, the grid attracts electrons from the cathode. These electrons cannot flow through  $L$  back to the cathode because  $C_g$  "blocks"

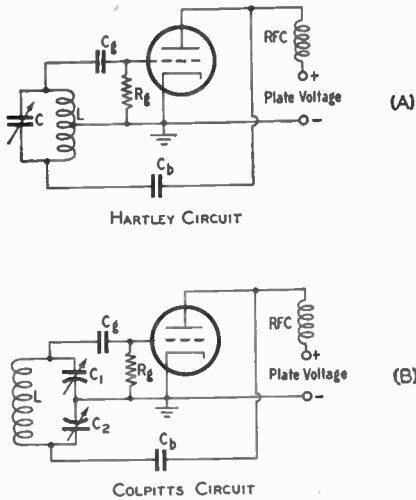


Fig. 3-22 — Basic oscillator circuits. Feed-back voltage is obtained by tapping the grid and cathode across a portion of the tuned circuit. In the Hartley circuit the tap is on the coil, but in the Colpitts circuit the voltage is obtained from the drop across a condenser.

direct current. They therefore have to flow or "leak" through  $R_g$  to cathode, and in doing so cause a voltage drop in  $R_g$  that places a negative bias on the grid. The amount of bias so developed is equal to the grid current multiplied by the resistance of  $R_g$  (Ohm's Law). The value of grid-leak resistance required depends upon the kind of tube used and the purpose for which the oscillator is intended. Values range all the way from a few thousand to several hundred thousand ohms. The capacitance of  $C_g$  should be large enough to have low reactance at the operating frequency.

The circuit shown at B in Fig. 3-22 uses the voltage drops across two condensers in series in the tuned circuit to supply the feed-back. Other than this, the operation is the same as just described. The feed-back can be varied by varying the ratio of the reactances of  $C_1$  and  $C_2$  (that is, by varying the ratio of their capacitances). To maintain the same oscillation frequency the total capacitance across  $L$  must be constant; this means that every time  $C_1$ , for example, is adjusted to change the feed-back,  $C_2$  must be adjusted in the opposite sense to return the total capacitance and thereby the frequency to the original value.

Another type of oscillator, called the **tuned-plate tuned-grid** circuit, is shown in Fig. 3-23. Resonant circuits tuned approximately to the same frequency are connected between grid and cathode and between plate and cathode. The two coils,  $L_1$  and  $L_2$ , are not magnetically-coupled. The feed-back is through the grid-plate capacitance of the tube, and will be in the right phase to be positive when the plate circuit,  $C_2L_2$ , is tuned to a slightly higher frequency than the grid circuit,  $L_1C_1$ . The amount of feed-back can be adjusted by vary-

ing the tuning of either circuit. The frequency of oscillation is determined by the tuned circuit that has the higher  $Q$ . The grid leak and grid condenser have the same functions as in the other circuits. In this case it is convenient to use series feed for the plate circuit, so  $C_b$  is a by-pass condenser to guide the r.f. current around the plate supply.

Practically all feed-back oscillator circuits (and there is an endless variety of them) are variations of these general types. They differ in details and appearance, and some use two or more tubes to accomplish the purpose. However, the basic feature of all of them is that there is positive feed-back in the proper amplitude to sustain oscillation.

### Oscillator Operating Characteristics

As a general rule, oscillators are *power-generating* devices. There are exceptions: in some cases the oscillator is used primarily to generate a *voltage* that is then applied to an amplifier that does not require power in its grid circuit. This type of oscillator is used principally in certain types of measuring equipment; the oscillators used in transmitters and receivers usually are called upon to deliver some power.

When an oscillator is delivering power to a load, the adjustment for proper feed-back will depend on how heavily the oscillator is loaded. If the feed-back is not large enough — that is, if the grid excitation is too small — a slight change in load may tend to throw the circuit into and out of oscillation. On the other hand, too much feed-back will make the grid current excessively high, with the result that the power loss in the grid circuit is larger than necessary. The oscillator itself supplies this grid power, so excessive feed-back lowers the over-all efficiency because whatever power is used in the grid circuit is not available as useful output.

One of the most important considerations in oscillator design is frequency stability. Almost invariably we want the generated frequency to be as constant as possible. The principal factors that cause a change in frequency are (1) temperature, (2) plate voltage, (3) loading, (4) mechanical variations of circuit elements. Temperature changes will cause vacuum-tube elements to expand or contract slightly, thus causing variations in the interelectrode capacitances. Since these are unavoidably part of the tuned circuit, the frequency will change correspondingly. Temperature changes in the

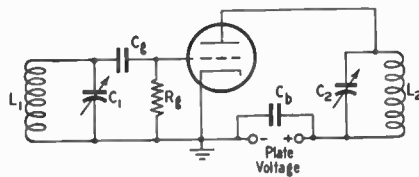


Fig. 3-23 — The tuned-plate tuned-grid oscillator.

coil or condenser will alter their inductance or capacitance slightly, again causing a shift in the resonant frequency. These effects are relatively slow in operation, and the frequency change caused by them is called drift.

Load variations act in much the same way as plate-voltage variations. A temperature change in the load may also result in drift.

Plate-voltage variations will cause a corresponding shift in frequency; this type of frequency shift is called dynamic instability. Dynamic instability can be reduced by using a tuned circuit of high effective  $Q$ . Since the tube and load represent a relatively low resistance in parallel with the circuit, this means that a low  $L/C$  ratio ("high- $C$ ") must be used and that the circuit should be lightly loaded. Dynamic stability also can be improved by using a high value of grid leak; this increases the grid bias and raises the effective resistance of the tube as seen by the tank circuit. Using relatively high plate voltage and low plate current also helps.

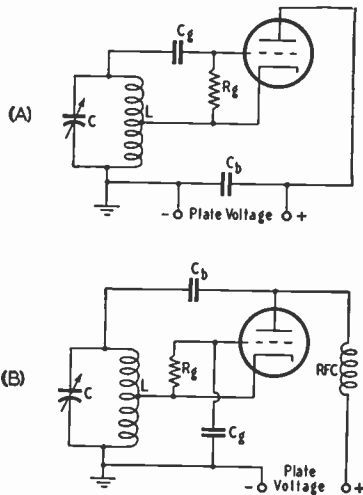


Fig. 3-24 — Showing how the r.f. ground on a typical oscillator circuit (Hartley) may be placed on either the plate (A) or grid (B) instead of the more conventional method of grounding the cathode. Provided the proper provisions are made for supplying cathode and plate voltages, the circuit operation is unchanged by shifting the r.f. ground to any desired point.

Mechanical variations, usually caused by vibration, cause changes in inductance and/or capacitance that in turn cause the frequency to "wobble" in step with the vibration.

Methods of minimizing frequency variations in oscillators are taken up in detail in later chapters.

#### Ground Point

In the oscillator circuits shown in Figs. 3-22 and 3-23 the cathode is connected to ground. It is not actually essential that the radio-frequency circuit should be grounded at the cathode; in fact, there are many times when

an r.f. ground on some other point in the circuit is desirable. The r.f. ground can be placed at any point so long as proper provisions are made for feeding the supply voltages to the tube elements.

Fig. 3-24 shows the Hartley circuit with (A) the plate end of the circuit grounded, and (B) the grid end. In A, no r.f. choke is needed in the plate circuit because the plate already is at ground potential and there is no r.f. to choke off. All that is necessary is a by-pass condenser,  $C_b$ , across the plate supply. Direct current flows to the cathode through the lower part of the tuned-circuit coil,  $L$ .

The grounded-grid circuit at B is essentially the same as the circuit in Fig. 3-22A except that the ground point and negative plate-voltage connection have been placed at the grid end of the tuned circuit.

One advantage of either type of circuit (the one in Fig. 3-24A is widely used) is that the frame of the tuning condenser can be grounded. With a grounded-cathode oscillator, both ends of the tuned circuit are "hot"; that is, there is an r.f. voltage to ground from both ends of the circuit. When the ordinary type of tuning condenser is used in such a circuit there is a slight change in capacitance when the hand is brought near the tuning shaft for adjustment of capacitance. This "hand capacitance" or "body capacitance" is annoying because the oscillator frequency changes when the hand is brought near the tuning control. It is overcome by grounding (for r.f.) the condenser shaft and by using a condenser that has a frame with metal end plates.

Tubes having indirectly-heated cathodes are more easily adaptable to circuits grounded at other points than the cathode than are tubes having directly-heated filaments. With the latter tubes special precautions have to be taken to prevent the filament from being bypassed to ground by the capacitance of the filament-heating transformer.

### ● NEGATIVE-RESISTANCE OSCILLATORS

If a tuned circuit could be built without resistance, a small amount of energy introduced into the circuit would start an oscillation that would continue indefinitely. It would do so because, in a circuit having no power losses, the power never diminishes and therefore is always available to keep the oscillation going. Of course, such a circuit cannot be built.

However, it was explained in Chapter Two that a resonant circuit has a definite value of parallel impedance at resonance, and that that impedance is a pure resistance. If we could connect across the circuit a value of "negative" resistance equal to the parallel resistance of the circuit, the negative resistance would cancel the "positive" (real) resistance of the circuit and we would have a circuit that is, in effect, without resistance.

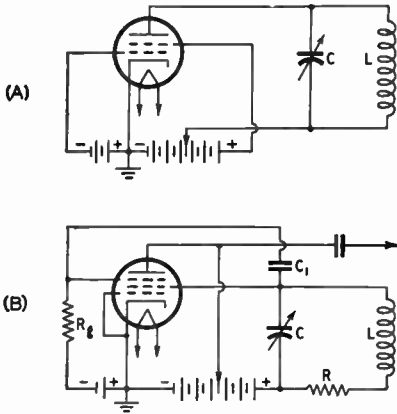


Fig. 3-25 — Negative-resistance oscillator circuits. A, dynatron; B, transitron.

A negative resistance is one having the opposite characteristics to real or positive resistance. In a negative resistance the current *increases* when the voltage is decreased, and vice versa. Also, a negative resistance does not consume power; it generates it. Under certain conditions a vacuum tube can be made to operate like a negative resistance, and thus can be connected to a tuned circuit to set up oscillations. Two circuits for doing this are shown in Fig. 3-25.

The circuit at A is called the **dynatron** oscillator. It functions because of the secondary emission from the plate that occurs in certain types of screen-grid tetrodes. It makes use of the fact that, at certain values of screen voltage, the plate current of a screen-grid tetrode decreases when the plate voltage is increased. This gives a negative plate-resistance characteristic.

In Fig. 3-25B, negative resistance is produced by virtue of the fact that, if the suppressor grid of a pentode is given negative bias, electrons that normally would pass through the suppressor to the plate are turned back to the screen, thus increasing the screen current and reversing normal tube action. The negative resistance produced between the screen and suppressor grids is sufficiently low so that ordinary tuned circuits will oscillate readily up to 15 Mc. or so. This circuit is known as the **transitron**.

For most amateur applications, negative-resistance oscillators do not have enough advantages to bring them into wide use. Feedback oscillators are generally more adaptable to wide frequency ranges, can generate more power, and are more readily adjusted to meet varying conditions. The transitron oscillator is used occasionally in measuring equipment.

# High-Frequency Communication

Much of the appeal of amateur communication on the high frequencies lies in the fact that the results are not always predictable. Transmission conditions on the same frequency vary with the year and even with the time of day. Although these variations usually follow certain established cycles, many peculiar effects can be observed from time to time. Every radio amateur should have some understanding of the known facts about radio-wave propagation so that he will stand some chance of interpreting the unusual conditions when they occur. The observant amateur is in an excellent position to make worth-while contributions to the science, provided he has

sufficient background to understand his results. The serious amateur can, for example, cooperate with the National Bureau of Standards in its NBS-ARRL 28-Mc. Observing Project, about which more is said at the end of this chapter. Or he may develop a new theory of propagation for the very-high frequencies or the microwave region, as did the late Ross Hull. By making extensive observations of 56-Mc. conditions over a long-distance path and correlating the results with various weather conditions, Mr. Hull was able to establish the now-accepted theory of "tropospheric bending."

## What To Expect on the Various Amateur Bands

The 3.5-Mc., or "80-meter," band is a more useful band during the night than during the daylight hours. In the daytime, one can seldom hear signals from a distance of greater than 100 miles or so, but during the darkness hours distances up to several thousand miles are not unusual, and transoceanic contacts are regularly made during the winter months. During the summer, the static level is high in some parts of the world, and the sharp crashes of static often make reception difficult. The 3.5-Mc. band supports the majority of the traffic nets throughout the country, and it is also a great gathering place for "rag-chewers." Low power and simple antennas can be used here with good results.

The 7-Mc., or "40-meter," band has many of the same characteristics as 3.5, except that the distances that can be covered during the day and night hours are increased. During daylight, distances up to a thousand miles can be covered under good conditions, and during the dawn and dusk periods in winter it is possible to work stations as far as the other side of the world, the signals following the darkness path. The winter months are somewhat better than the summer ones. Rag-chewing, traffic handling and DX (working foreign countries) are popular activities on the band, in the order named. Here again antennas are not too im-

portant, although results will be improved in proportion to the effectiveness of the antenna system. In general, summer static is much less of a problem than on 80 meters, although it can be serious in the semitropical zones.

The 14-Mc., or "20-meter," band is probably the best one for long-distance work. During portions of the sunspot cycle it is open to some part of the world during practically all of the 24 hours, while at other times it is generally useful only during daylight hours and the dawn and dusk periods. DX activity is paramount, with rag-chewing next. Being less consistent, day by day, traffic handling is not too general, although many long-distance schedules are kept on the band. Effective antennas are more necessary than on the lower frequencies, but many amateurs enjoy excellent results with simple antennas and low power. Automobile ignition and other types of man-made interference begin to be a problem on this band.

The 28-Mc. band is generally considered to be a DX band during the daylight hours and a local rag-chewer's band during the hours of darkness. However, during parts of the sunspot cycle, the band is "open" into the late evening hours for DX communication. The band is even less consistent than 14 Mc., but this very fact is what makes it so fascinating



for its many followers. It is not unusual for a foreign station to appear suddenly with a loud signal when only U.S. stations, or none at all, are being heard. High-performance antennas are almost a necessity for best results, but its small dimensions make the rotary beam a

popular choice for the band. These antennas can be turned to direct the radiation in the desired direction, and they are used to provide useful gain on reception as well. A good antenna is far more important on this band than high power.

## Characteristics of Radio Waves

Radio waves differ from other forms of electromagnetic radiation (such as light and heat) in the manner in which they are generated and detected and in their wavelength. The wavelength spectrum of radio waves is greater than either heat or light, and ranges from approximately 30,000 meters to a small fraction of a centimeter. This corresponds to a frequency range of about 10 kc. to 1,000,000 Mc. They travel at the same velocity as light waves (about 186,000 miles per second in free space) and can be reflected, refracted and diffracted the way light and heat waves can.

The passage of radio energy through space is explained by a concept of traveling electrostatic and electromagnetic waves. The energy is evenly divided between the two types of fields, and the lines of force of these fields are at right angles to each other, in a plane perpendicular to the direction of travel. A simple representation of this is shown in Fig. 4-1.

### Polarization

The polarization of a radio wave is taken as the direction of the lines of force in the electrostatic field. If the plane of this field is perpendicular to the earth, the wave is said to be vertically polarized; if it is parallel to the earth, the wave is horizontally polarized. The longer waves, when traveling along the ground, usually maintain their polarization in the same plane as was generated at the antenna. The polarization of shorter waves may be altered during travel, however, and sometimes will vary quite rapidly.

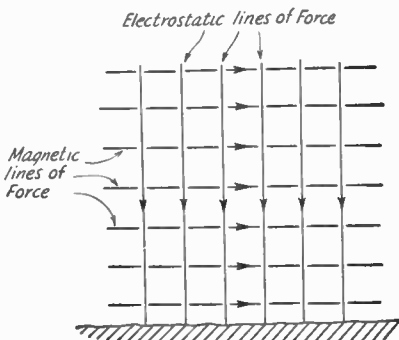


Fig. 4-1 — Representation of electrostatic and electromagnetic lines of force in a radio wave. Arrows indicate instantaneous directions of the fields for a wave traveling toward the reader. Reversing the direction of one set of lines would reverse the direction of travel.

### Reflection

Radio waves may be reflected from any sharply-defined discontinuity of suitable characteristics and dimensions encountered in the medium in which they are traveling. Any conductor (or any insulator having a dielectric constant differing from that of the medium) offers such a discontinuity if its dimensions are at least comparable to the wavelength. The surface of the earth and the boundaries between ionospheric layers are examples of such discontinuities. Objects as small as an airplane, a tree or even a man's body will readily reflect the shorter waves.

### Refraction

As in the case of light, a radio wave is bent when it moves obliquely into any medium having a refractive index different from that of the medium it leaves. Since the velocity of propagation differs in the two mediums, that part of the wave front that enters first travels faster if the new medium has a higher velocity of propagation. This tends to swing the wave front around, or "refract" it, in such a manner that the wave is directed in a new direction. If the wave front is one that is traveling obliquely away from the earth, and it encounters a medium with a higher velocity of propagation, the wave will be directed back toward the earth. If the new medium has a lower velocity of propagation, the opposite effect takes place, and the wave is directed away from the earth. Refraction may take place either in the ionosphere (ionized upper atmosphere) or the troposphere (lower atmosphere), or both.

### Diffraction

When a wave grazes the edge of an object in passing, it tends to be bent around that edge. This effect, called diffraction, results in a diversion of part of the energy of those waves which normally follow a straight or line-of-sight path, so that they may be received at some distance below the summit of an obstruction, or around its edges.

### Types of Waves

According to the altitude of the paths along which they are propagated, radio waves may be classified as ionospheric waves, tropospheric waves or ground waves.

The ionospheric wave (sometimes called the sky wave), is that part of the total radiation

that is directed toward the ionosphere. Depending upon variable conditions in that region, as well as upon transmitting wavelength, the ionospheric wave may or may not be returned to earth by the effects of refraction and reflection.

The tropospheric wave is that part of the total radiation that undergoes refraction and reflection in regions of abrupt change of dielectric constant in the troposphere, such as the boundaries between air masses of differing temperature and moisture content.

The ground wave is that part of the total radiation that is directly affected by the presence of the earth and its surface features. The

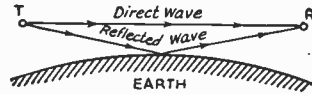


Fig. 4-2—Showing how both direct and reflected waves may be received simultaneously in v.h.f. transmission.

ground wave has two components. One is the **surface wave**, which is an earth-guided wave, and the other is the **space wave** (not to be confused with the ionospheric or sky wave). The space wave is itself the resultant of two components — the direct wave and the ground-reflected wave, as shown in Fig. 4-2.

## Ionospheric Propagation

Communication between distant points by means of radio waves of frequencies ranging between 3 and 30 Mc. depends principally upon the ionospheric wave. Upon leaving the transmitting antenna, this wave travels upward from the earth's surface at such an angle that it would continue out into space were its path not bent sufficiently to bring it back to earth. The medium that causes such bending is the **ionosphere**, a region in the upper atmosphere, above a height of about 60 miles, where free ions and electrons exist in sufficient quantity to cause a change in the refractive index. This condition is believed to be the effect of ultraviolet radiation from the sun. The ionosphere is not a single region but is composed of a series of layers of varying densities of ionization occurring at different heights. Each layer consists of a central region of relatively dense ionization that tapers off in intensity both above and below.

### Refraction, Absorption and Reflection

For a given density of ionization, the degree of refraction becomes less as the wavelength becomes shorter (as the frequency increases). The bending, therefore, is less at high than at low frequencies, and if the frequency is raised to a sufficiently high value, a point is finally reached where the refractive bending becomes too slight to bring the wave back to earth, even though it may enter the ionized layer along a path that makes a very small angle with the boundary of the ionosphere.

The greater the density of ionization, the greater the bending at any given frequency. Thus, with an increase in ionization, the minimum wavelength that can be bent sufficiently for long-distance communication is lessened and the **maximum usable frequency** is increased.

The wave necessarily loses some of its energy in traveling through the ionosphere, this absorption loss increasing with wavelength and also with ionization density. Unusually high ionization, especially in the lower strata of the ionosphere, may cause complete absorption of the wave energy.

In addition to refraction, reflection may take place at the lower boundary of an ionized layer if it is sharply defined; i.e., if there is an appreciable change in ionization within a relatively short interval of travel. For waves approaching the layer at or near the perpendicular, the change in ionization must take place within a difference in height comparable to a wavelength; hence, ionospheric reflection is more apt to occur at longer wavelengths (lower frequencies).

### Critical Frequency

When the frequency is sufficiently low, a wave sent vertically upward to the ionosphere will be bent sharply enough to cause it to return to the transmitting point. The highest frequency at which such reflection can occur, for a given state of the ionosphere, is called the **critical frequency**. Although the critical frequency may serve as an index of transmission conditions, it is not the highest useful frequency, since other waves of a higher frequency that enter the ionosphere at angles smaller than 90 degrees (less than vertical) will be bent sufficiently to return to earth. The maximum usable frequency, for waves leaving the earth at very small angles to the horizontal, is in the vicinity of three times the critical frequency.

Besides being directly observable by special equipment, the critical frequency is of more practical interest than the ionization density because it includes the effects of absorption as well as refraction.

### Virtual Height

Although an ionospheric layer is a region of considerable depth it is convenient to assign to it a definite height, called the **virtual height**. This is the height from which a simple reflection would give the same effect as the gradual refraction that actually takes place, as illustrated in Fig. 4-3. The wave traveling upward is bent back over a path having an appreciable radius of turning, and a measurable interval of time is consumed in the turning process. The

virtual height is the height of a triangle formed as shown, having equal sides of a total length proportional to the time taken for the wave to travel from  $T$  to  $R$ .

### Normal Structure of the Ionosphere

The lowest normally useful layer is called the  $E$  layer. The average height of the region of maximum ionization is about 70 miles. The ionization density is greatest around local noon; the layer is only weakly ionized at night, when it is not exposed to the sun's radiation. The air at this height is sufficiently dense so that free ions and electrons very quickly meet and recombine.

In the daytime there is a still lower ionized region, the  $D$  layer. The  $D$ -layer intensity is proportional to the height of the sun and is greatest at noon. Low-frequency waves (80 meters) are almost completely absorbed by this layer while it exists, and only the high-angle radiation is reflected by the  $E$  layer. (Lower-angle radiation travels farther through the  $D$  layer and is absorbed.)

The second principal layer is the  $F$  layer, which has a height of about 175 miles at night. At this altitude the air is so thin that recombination of ions and electrons takes place very slowly, inasmuch as particles can travel relatively great distances before meeting. The ionization decreases after sundown, reaching a minimum just before sunrise. In the daytime the  $F$  layer splits into two parts, the  $F_1$  and  $F_2$  layers, with average virtual heights of, respectively, 140 miles and 200 miles. These layers are most highly ionized at about local noon, and merge again at sunset into the  $F$  layer.

### Cyclic Variations in the Ionosphere

Since ionization depends upon ultraviolet radiation, conditions in the ionosphere vary with changes in the sun's radiation. In addition to the daily variation, seasonal changes result in higher critical frequencies in the  $E$  layer in summer, averaging about 4 Mc. as against a winter average of 3 Mc. The  $F$  layer shows little variation, the critical frequency being of the order of 4 to 5 Mc. in the evening. The  $F_1$  layer, which has a critical frequency near 5 Mc. in summer, usually disappears entirely in winter. The critical frequencies for the  $F_2$  are highest in winter (11 to 12 Mc.) and lowest in

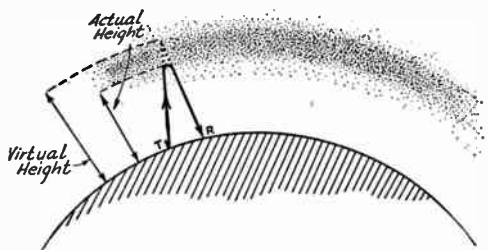


Fig. 4-3 — Bending in the ionosphere, and the echo or reflection method of determining virtual height.

summer (around 7 Mc.). The virtual height of the  $F_2$  layer, which is about 185 miles in winter, averages 250 miles in summer.

Seasonal transition periods occur in spring and fall, when ionospheric conditions are found highly variable.

There are at least two other regular cycles in ionization. One such cyclic period covers 28 days, which corresponds with the period of the sun's rotation. For a short time in each 28-day cycle, transmission conditions reach a peak. Usually this peak is followed by a fairly rapid drop to a lower level, and then a slow building-up to the next peak. The 28-day cycle is particularly evident in the 14- and 28-Mc. amateur bands.

The longest cycle yet observed covers about 11 years, corresponding to a similar cycle of sunspot activity. The effect of this cycle is to shift upward or downward the values of the critical frequencies for  $F$ - and  $F_2$ -layer transmission. The critical frequencies are highest during sunspot maxima and lowest during sunspot minima. It is during the period of minimum sunspot activity when long-distance transmissions occur on the lower frequencies. At such times the 28-Mc. band is seldom useful for long-distance work, while the 14-Mc. band performs well in the daytime but is not ordinarily useful at night. The most recent sunspot maximum is considered to have occurred in 1938.

### Magnetic Storms and Other Disturbances

Unusual disturbances in the earth's magnetic field (magnetic storms) usually are accompanied by disturbances in the ionosphere, when the layers apparently break up and expand. There is usually also an increase in absorption during such a period. Radio transmission is poor and there is a drop in critical frequencies so that lower frequencies must be used for communication. A magnetic storm may last for several days.

Unusually high ionization in the region of the atmosphere below the normal ionosphere may increase absorption to such an extent that sky-wave transmission becomes impossible on high frequencies. The length of such a disturbance may be several hours, with a gradual falling off of transmission conditions at the beginning and an equally gradual building up at the end of the period. Fade-outs, similar to the above in effect, are caused by sudden disturbances on the sun. They are characterized by very rapid ionization, with sky-wave transmission disappearing almost instantly, occur only in daylight, and do not last as long as the first type of absorption.

Magnetic storms frequently are accompanied by unusual auroral displays, creating an ionized "curtain" in the polar regions which can act as a reflector of radio waves. Auroral reflection is occasionally observed at frequencies as high as 54 Mc. It is characterized on 28 Mc. by a flutter on all signals which makes voice work

difficult but not impossible. Directive antennas must be pointed toward the north and not in the direction of the station being worked.

#### Sporadic-E Layer Ionization

Occasionally scattered patches of clouds of relatively dense ionization appear at heights approximately the same as that of the *E* layer. The effect is to raise the critical frequency to a value perhaps twice that which is returned from any of the regular layers by normal refraction. Distances of about 500 to 1250 miles may be covered at 50 Mc. if the ionized cloud is situated midway between transmitter and receiver, or is of any very considerable extent. This effect, while infrequently observed in winter, is prevalent during the late spring and early summer, with no apparent correlation of the condition with the time of day.

The presence of sporadic-*E* refraction on the 14- and 28-Mc. bands is indicated by an abnormally short distance between the transmitter and the point where the wave first is returned to earth as when, for example, 14-Mc. signals from a transmitter only 100 miles distant may arrive with an intensity usually associated with distances of this order on 7 and 3.5 Mc.

#### Scatter

Scatter signals are heard on any band, but are more easily recognizable on the higher frequencies because of the extended skip zone. They are signals reflected from large discontinuities at a distance, such as sharp concentrations of ionization in any of the normal layers, sporadic-*E* clouds or (rarely) large land objects. They result in one's hearing signals within the normal skip zone. Scatter signals are never very loud, and have a slight flutter characteristic. A further indication of scatter reflection is that, when beam antennas are used to indicate the direction of arrival of the wave, the ray path is not necessarily the direct route but can even be at right angles or in the opposite direction.

#### Meteor Trails

Another phenomenon generally encountered in the 28-Mc. band, but also observed in the 14- and 50-Mc. bands, is one characterized by sudden bursts of intensity of a signal. These bursts last less than a second, generally, and are caused by reinforced reflection from the ionized trail of a meteor. The meteor, entering the earth's atmosphere at high velocity, heats by friction against the atmosphere and leaves a trail of ionized atmosphere. It takes a finite time for the ionized molecules to recombine, and during this time a small ionized cloud exists. If it is in the ray path of a signal, it may serve to reinforce the signal and cause the

burst in intensity. When the meteor is moving in a direction somewhat parallel to the ray path, it can induce a rising or falling "whistle" on the signal, for a second or so. The effects of bursts and whistles can be observed at any time during the day or night, if there is any marked meteor activity, and during rare "meteor showers" the ionized clouds can serve in almost the same manner that sporadic-*E* does to make long-distance work possible on 50 Mc.

#### Wave Angle

The smaller the angle at which a wave leaves the earth, the less will be the bending required in the ionosphere to bring it back and, in general, the greater the distance between the point where it leaves the earth and that at which it returns. This is shown in Fig. 4-4. The vertical angle which the wave makes with a tangent to the earth is called the wave angle or angle of radiation.

#### Skip Distance

Since greater bending is required to return the wave to earth when the wave angle is high, at the higher frequencies the refraction frequently is not enough to give the required bending unless the wave angle is smaller than a certain angle called the *critical angle*. This is illustrated in Fig. 4-4, where waves at angles of *A* or less give useful signals while waves sent at

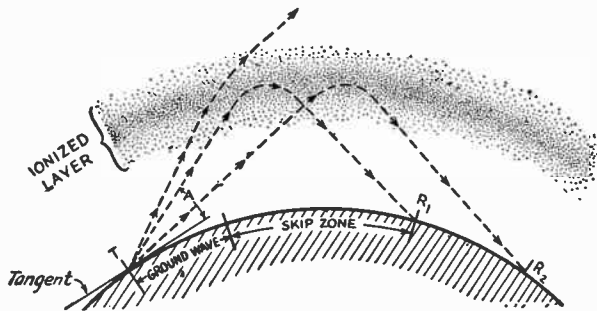


Fig. 4-4 — Refraction of sky waves, showing the critical wave angle and the skip zone. Waves leaving the transmitter at angles above the critical (greater than *A*) are not bent enough to be returned to earth. As the angle is increased, the waves return to earth at increasingly greater distances.

higher angles penetrate the layer and are not returned. The distance between *T* and *R*<sub>1</sub> is, therefore, the shortest possible distance over which communication by normal ionospheric refraction can be accomplished.

The area between the end of the useful ground wave and the beginning of ionospheric-wave reception is called the skip zone. The extent of skip zone depends upon the frequency and the state of the ionosphere, and is greater the higher the transmitting frequency and the lower the critical frequency. Skip distance depends also upon the height of the layer in which the refraction takes place, the higher layers giving longer skip distances for

the same wave angle. Wave angles at the transmitting and receiving points are usually, although not always, approximately the same for any given wave path.

It is readily possible for the ionospheric wave to pass through the *E* layer and be refracted back to earth from the *F*, *F*<sub>1</sub> or *F*<sub>2</sub> layers. This is because the critical frequencies are higher in the latter layers, so that a signal too high in frequency to be returned by the *E* layer can still come back from one of the others, depending upon the time of day and the existing conditions. Depending upon the wave angle and the frequency, it is sometimes possible to carry on communication via either the *E* or *F*<sub>1</sub>-*F*<sub>2</sub> layers on the same frequency.

#### **Multihop Transmission**

On returning to the earth the wave can be reflected upward and travel again to the ionosphere. There it may once more be refracted, and again bent back to earth. This process may be repeated several times. Multihop propagation of this nature is necessary for transmission over great distances because of the limited heights of the layers and the curvature of the earth, since at the lowest useful wave angles (of the order of a few degrees, waves at lower angles generally being absorbed rapidly at high frequencies by being in contact with the earth) the maximum one-hop distance is about 1250 miles for refraction from the *E* layer and around 2500 miles for the *F*<sub>2</sub> layer. However, ground losses absorb some of the energy from the wave on each reflection (the amount of the loss varying with the type of ground and being least for reflection from sea water). Thus, when the distance permits, it is better to have one hop rather than several, since the multiple reflections introduce losses that are higher than those caused by the ionosphere alone.

#### **Fading**

Two or more parts of the wave may follow slightly different paths in traveling to the receiving point, in which case the difference in path lengths will cause a phase difference to exist between the wave components at the receiving antenna. The field strength therefore may have any value between the numerical sum of the components (when they are all in phase) and zero (when there are only two components and they are exactly out of phase). Since the paths change from time to time, this causes a variation in signal strength called **fading**. Fading can also result from the combination of single-hop and multihop waves, or the combination of a ground wave with an ionospheric or tropospheric wave. Such a condition gives rise to an area of severe fading near the limiting distance of the ground wave, better reception being obtained at both shorter and longer distances where one component or the other is considerably stronger. Fading may be rapid or slow, the former type usually resulting

from rapidly-changing conditions in the ionosphere, the latter occurring when transmission conditions are relatively stable.

It frequently happens that transmission conditions are different for waves of slightly different frequencies, so that in the case of voice-modulated transmission, involving sidebands differing slightly from the carrier in frequency, the carrier and various sideband components may not be propagated in the same relative amplitudes and phases they had at the transmitter. This effect, known as **selective fading**, causes severe distortion of the signal.

#### **Tropospheric Propagation**

Changes in refractive index of air masses in the lower atmosphere often permit work over greater-than-normal distances on 28 Mc. and higher frequencies. The effect can be observed on 28 Mc., but it is generally more marked on 50 and 144 Mc. The subject is treated in detail in Chapter Eleven.

### ● OPTIMUM WAVE ANGLES

One of the requirements in high-frequency radio transmission is to send a wave to the ionosphere in such a way that it will have the best chance of being returned to earth. This is chiefly a matter of the angle at which the wave enters the layer, although in some cases polarization may be of importance. The desirable conditions change considerably with variations in frequency.

The desirable conditions for waves of different frequencies can be summarized as follows, in terms of the various amateur bands:

#### **3.5 Mc.**

Waves at all angles of radiation usually will be reflected, so that no energy is lost by high-angle radiation. However, the lower-angle waves will, in general, give the greatest distances. Polarization on this band is not of great importance.

#### **7 Mc.**

Under most conditions, angles of radiation up to about 45 degrees will be returned to earth; during the sunspot maximum still higher angles are useful. It is best to concentrate the radiation below 45 degrees. Polarization is not important, except that losses probably will be higher with vertical polarization.

#### **14 Mc.**

For long-distance transmission, most of the energy should be concentrated at angles below about 20 degrees. Higher angles are useful for comparatively short distances (300-400 miles), although 30 degrees is about the maximum useful angle. Aside from the probable higher losses with vertical polarization, the polarization may be of any type.

**28 Mc.**

Angles of 10 degrees or less are most useful. As in the case of 14 Mc., polarization is not important.

● **PREDICTION CHARTS**

The National Bureau of Standards offers prediction charts three months in advance, for use in predicting and studying long-distance communication on the usable frequencies above 3.5 Mc. By means of these charts, it is possible to predict with considerable accuracy the maximum usable frequency that will hold over any path on the earth during a monthly period. The particular great-circle path is drawn by the operator on a piece of transparent paper, and the prediction charts include maps that make this a simple matter. Control points are then marked on this great-circle route at distances of 2000 kilometers from each station. By moving the transparent paper over the prediction chart and observing where the control points fall, the maximum usable frequency can be obtained for any hour of the 24. The charts are based on ionosphere soundings made at a number of stations throughout the world, coupled with considerable statistical data. The charts are conservative enough to enable the amateur to anticipate and plan his best operating times, particularly on the 14-

and 28-Mc. bands. Amateurs who work on 50 Mc. and are interested in the occasional  $F_2$  "openings" in this band watch the charts with great interest. They can be obtained from the Superintendent of Documents, U. S. Government Printing Office, Washington 25, D. C., for 15 cents a copy or \$1.50 per year on subscription. They are called "CRPL-D Basic Radio Propagation Predictions."

● **N.B.S.-A.R.R.L. 28-MC. OBSERVING PROJECT**

Any amateur with 28-Mc. receiving and transmitting equipment can apply to the National Bureau of Standards and ask to take part in the 28-Mc. Observing Project. This service provides valuable information for the NBS in their propagation work, and only requires that the amateur make regular monthly reports on a minimum number of schedules or receiving observations. Complete report forms are furnished by the Bureau, together with a simplified 28-Mc. prediction chart that shows what the Bureau has predicted for each particular month. The program is not confined to amateurs in the United States, and stations throughout the world are taking an active part. Address your application to Central Radio Propagation Laboratory, National Bureau of Standards, Washington 25, D. C.

# High-Frequency Receivers

A good receiver in the amateur station makes the difference between mediocre contacts and solid QSOs, and its importance cannot be emphasized too much. In the v.h.f. bands that are not too crowded, sensitivity (the ability to bring in weak signals) is the most important factor in a receiver. In the more crowded amateur bands, good sensitivity must be combined with selectivity (the ability to distinguish between signals separated by only a small frequency difference) for best results and general ease of reception. Using only a simple receiver, old and experienced operators can copy signals that would be missed entirely by newer amateurs, but their success is because of their experience and not the receiving equipment. On the other hand, a less-experienced operator can use modern techniques to obtain the same degree of success, provided he understands the operation of his more advanced type of receiver and how to get the most out of it.

A number of signals may be picked up by the receiving antenna, and the receiver must be able to separate them and allow the operator to copy the one he wants. This ability is called "selectivity." To receive weak signals, the receiver must furnish enough amplification to amplify the minute signal power delivered by the antenna up to a useful amount of power that will operate a loudspeaker or set of headphones. Before the amplified signal can operate the 'speaker or 'phones, however, it must be converted to audio-frequency power by the process of detection. The sequence of amplification is not too important — some of the amplification can take place (and usually does) before detection, and some can be used after detection.

There are two major differences between receivers for 'phone reception and for c.w. reception. A 'phone signal has sidebands that

make the signal take up about 6 or 8 kc. in the band, and the audio quality of the received signal is impaired if the passband of the receiver is less than this amount. On the other hand, a c.w. signal occupies only a few hundred cycles at the most, and consequently the passband of a c.w. receiver can be small. In either case, if the passband of the receiver is more than is necessary, signals adjacent to the desired one can be heard, and the selectivity of the receiver is said to be poor. The other difference is that the detection process delivers directly the audio frequencies present as modulation on a 'phone signal, but there is no modulation on a c.w. signal and additional technique is required to make the signal audible. It is necessary to introduce a second radio frequency, differing from the signal frequency by a suitable audio frequency, into the detector circuit to produce an audible beat. The frequency difference, and hence the beat-note, is generally of the order of 500 to 1000 cycles, since these tones are within the range of optimum response of both the ear and the headset. If the source of the second radio frequency is a separate oscillator, the system is known as heterodyne reception; if the detector itself is made to oscillate and produce the second frequency, it is known as an autodyne detector. Modern superheterodyne receivers (described later) generally use a separate oscillator to generate the beat-note. Summing up the two differences, 'phone receivers can't use as much selectivity as c.w. receivers, and c.w. receivers require some kind of beating oscillator to give an audible signal. Broadcast receivers can receive only 'phone signals because no beat oscillator is included. On the other hand, communications receivers include beat oscillators and often some means for varying the selectivity.

## Receiver Characteristics

### *Sensitivity*

Confusion exists among some radio men when talking about the "sensitivity" of a receiver. In commercial circles it is defined as

the strength of the signal (in microvolts) at the input of the receiver that is required to produce a specified audio power output at the 'speaker or headphones. This is a perfectly-satisfactory definition for broadcast and com-

munications receivers operating below about 20 Mc., where general atmospheric and man-made electrical noises normally mask any noise generated by the receiver itself.

Another commercial definition of sensitivity measures the merit of a receiver by defining the sensitivity as the signal at the input of the receiver required to give an audio output some stated amount (generally 10 db.) above the noise output of the receiver. This is a much more useful sensitivity measure for the amateur, since it indicates how well a weak signal will be reproduced and is not merely a measure of the over-all gain, or amplification, of the receiver. However, it is still not an absolute method for comparing two receivers, because the passband width of the receiver plays a large part in the result.

The random motion of the molecules in the antenna and receiver circuits generates small voltages called **thermal-agitation noise** voltages. The frequency of this noise is random and the noise exists across the entire radio spectrum. Its amplitude increases with the temperature of the circuits. Only the noise in the antenna and first stage of a receiver is normally significant, since the noise developed in later stages is masked by the amplified noise from the first stage. Since the only noise that is amplified is that which falls within the passband of the receiver, the noise appearing in the output of a receiver is less when the passband is reduced (the effect of the "tone control" of a broadcast receiver). Similar noise is generated by the current flow within the first tube itself; this effect can be combined with the thermal noise and called **receiver noise**. Since the passband of two receivers plays an important part in the sensitivity measured on a signal-to-noise basis as described in the preceding paragraph, such a sensitivity measurement puts more emphasis on passband width than on the all-important "front-end" design of the receiver.

The limit of a receiver's ability to detect weak signals is the thermal noise generated in the input circuit. Even if a perfect noise-free tube were developed and used throughout the receiver, the limit to reception would be the thermal noise. (Atmospheric-and-man-made noise is a *practical* limit below 20 Mc., but we are looking for a measure of comparison of receivers.) The degree to which a receiver approaches this ideal is called the **noise figure** of the receiver, and it is expressed as the ratio of noise power at the input of the receiver required to increase the noise output of the receiver 3 db. Since the noise power passed by the receiver is dependent on the passband (which is the same for the receiver noise and the noise introduced to the receiver), the figure is one that shows how far the receiver departs from the ideal. The ratio is generally expressed in db., and runs around 6 to 12 db. for a good receiver, although figures of 3 to 4 db. have been obtained with special techniques. Com-

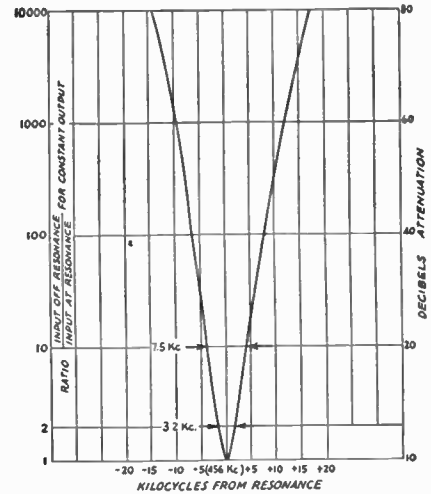


Fig. 5-1 — Typical selectivity curve of a modern superheterodyne receiver. Relative response is plotted against deviations above and below the resonance frequency. The scale at the left is in terms of voltage ratios, the corresponding decibel steps are shown at the right.

parisons of noise figures can be made by the amateur with simple equipment, as described in Chapter Sixteen.

### Selectivity

Selectivity is the ability of a receiver to discriminate against signals of frequencies differing from that of the desired signal. The over-all selectivity will depend upon the selectivity of the individual tuned circuits and the number of such circuits.

The selectivity of a receiver is shown graphically by drawing a curve that gives the ratio of signal strength required at various frequencies off resonance to the signal strength at resonance, to give constant output. A resonance curve of this type (taken on a typical communications-type superheterodyne receiver) is shown in Fig. 5-1. The **bandwidth** is the width of the resonance curve (in cycles or kilocycles) of a receiver at a specified ratio; in Fig. 5-1, the bandwidths are indicated for ratios of response of 2 and 10 ("2 times down" and "10 times down").

A receiver is more selective if the bandwidth (or passband) is less, but the bandwidth must be sufficient to pass the signal and its sidebands if faithful reproduction of the signal is desired. In the crowded amateur bands, it is generally advisable to sacrifice fidelity for selectivity, since the added selectivity reduces adjacent-channel interference and also the noise passed by the receiver. If the selectivity curve has steep sides, it is said to have good **skirt selectivity**, and this feature is very useful in listening to a weak signal that is adjacent to a strong one. Good skirt selectivity can only be obtained by using a large number of tuned circuits.



## Stability

The stability of a receiver is its ability to give constant output, over a period of time, from a signal of constant strength and frequency, and also its ability to remain tuned to a signal under varying conditions of gain-control setting, temperature, supply-voltage changes and mechanical shock and distortion. In other words, it means the ability "to stay put" on a given signal. The term "unstable" is also applied to a receiver that breaks into oscillation or a regenerative condition with some settings of its controls that are not specifically intended to control such a condition. This type of instability is sometimes encountered in high-gain amplifiers.

## Fidelity

Fidelity is the relative ability of the receiver to reproduce in its output the modulation (keying, voice, etc.) carried by the incoming signal. For exact reproduction the bandwidth must be great enough to accommodate the carrier and all of the sidebands before detection, and all of the frequency components of the modulation after detection. For perfect fidelity, the relative amplitudes of the various components must not be changed by passing through the receiver. However, fidelity plays a very minor rôle in amateur communication, where the important requirement is to transmit intelligence and not "high-fidelity" signals.

## Detection and Detectors

Detection is the process of recovering the modulation from a signal. Any device that is "nonlinear" (i.e., whose output is not *exactly* proportional to its input) will act as a detector. It can be used as a detector if an impedance for the desired modulation frequency is connected in the output circuit, so that the detector output can develop across this impedance.

Detector sensitivity is the ratio of desired detector output to the input. Detector linearity is a measure of the ability of the detector to reproduce the exact form of the modulation on the incoming signal. The resistance or impedance of the detector is the resistance or impedance it presents to the circuits it is connected to. The input resistance is important in receiver design, since if it is relatively low it means that the detector will consume power, and this power must be furnished by the preceding stage. The signal-handling capability means the ability of the detector to accept signals of a specified amplitude without overloading or distortion.

### Diode Detectors

The simplest detector is the diode rectifier. A galena, silicon or germanium crystal is an imperfect form of diode (a small current can pass in the reverse direction), and the principle of detection in a crystal is similar to that in a vacuum-tube diode.

Circuits for both half-wave and full-wave diodes are given in Fig. 5-2. The simplified half-wave circuit at 5-2A includes the r.f. tuned circuit,  $L_2C_1$ , a coupling coil,  $L_1$ , from which the r.f. energy is fed to  $L_2C_1$ , and the diode,  $D$ , with its load resistance,  $R_1$ , and bypass condenser,  $C_2$ . The flow of rectified r.f. current causes a d.c. voltage to develop across the terminals of  $R_1$ , and this voltage varies with the modulation on the signal. The - and + signs show the polarity of the voltage. The variation in amplitude of the r.f. signal with

modulation causes corresponding variations in the value of the d.c. voltage across  $R_1$ . The

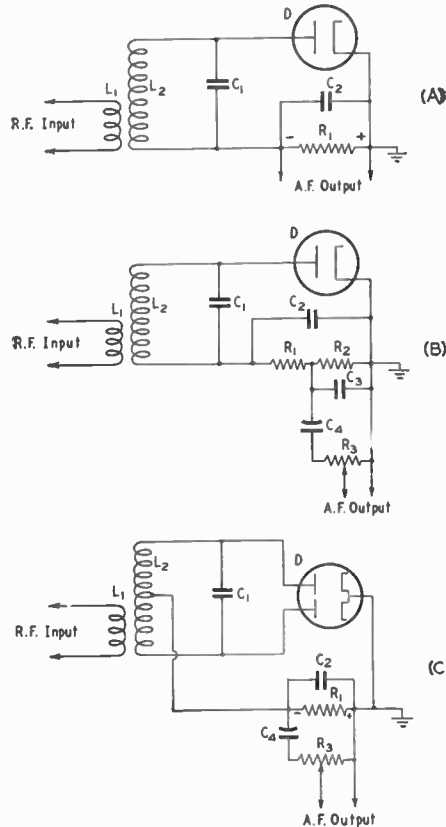


Fig. 5-2 — Simplified and practical diode detector circuits. A, the elementary half-wave diode detector; B, a practical circuit, with r.f. filtering and audio output coupling; C, full-wave diode detector, with output coupling indicated. The circuit,  $L_2C_1$  is tuned to the signal frequency; typical values for  $C_2$  and  $R_1$  in A and C are 250  $\mu$ fd. and 250,000 ohms, respectively; in B,  $C_2$  and  $C_3$  are 100  $\mu$ fd. each;  $R_1$ , 50,000 ohms; and  $R_2$ , 250,000 ohms.  $C_4$  is 0.1  $\mu$ fd. and  $R_3$  may be 0.5 to 1 megohm.

load resistor,  $R_1$ , usually has a rather high value of resistance, so that a fairly large voltage will develop from a small rectified-current flow.

The progress of the signal through the detector or rectifier is shown in Fig. 5-3. A typical modulated signal as it exists in the tuned circuit is shown at A. When this signal is applied to the rectifier tube, current will flow only during the part of the r.f. cycle when the plate is positive with respect to the cathode, so that the output of the rectifier consists of half-cycles of r.f. still modulated as in the original signal. These current pulses flow in the load circuit comprised of  $R_1$  and  $C_2$ , the resistance of  $R_1$  and the capacity of  $C_2$  being so proportioned that  $C_2$  charges to the peak value of the rectified voltage on each pulse and retains enough charge between pulses so that the voltage across  $R_1$  is smoothed out, as shown in C.  $C_2$  thus acts as a filter for the radio-frequency component of the output of the rectifier, leaving a d.c. component that varies in the same way as the modulation on the original signal. When this varying d.c. voltage is applied to a following amplifier through a coupling condenser ( $C_4$  in Fig. 5-2B), only the variations in voltage are transferred, so that the final output signal is a.c., as shown in D.

In the circuit at 5-2B,  $R_1$  and  $C_2$  have been divided for the purpose of providing a more effective filter for r.f. It is important to prevent the appearance of any r.f. voltage in the output of the detector, because it may cause overloading of a succeeding amplifier tube. The audio-frequency variations can be transferred to another circuit through a coupling condenser,  $C_4$  in Fig. 5-2B, to a load resistor,  $R_3$ , which usually is a "potentiometer" so that the volume can be adjusted to a desired level.

Coupling to the potentiometer (gain control) through a condenser also avoids any flow of d.c. through the gain control. The flow of

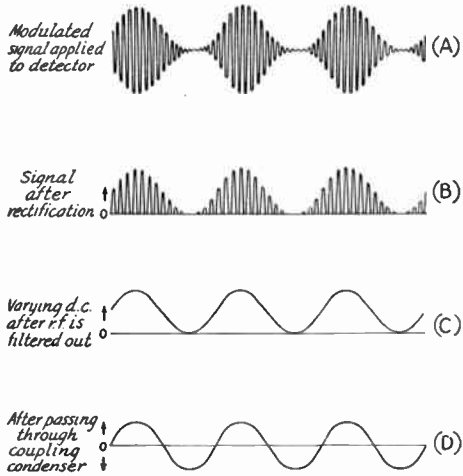


Fig. 5-3 — Diagrams showing the detection process.

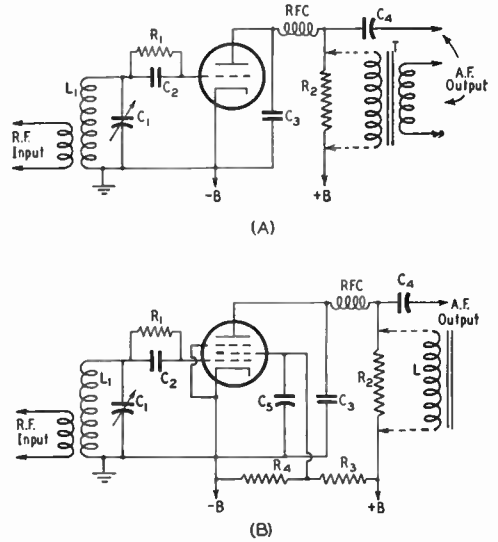


Fig. 5-4 — Grid-leak detector circuits, A, triode; B, pentode. A tetrode may be used in the circuit of B by neglecting the suppressor-grid connection. Transformer coupling may be substituted for resistance coupling in A, or a high-inductance choke may replace the plate resistor in B.  $L_1C_1$  is a circuit tuned to the signal frequency. The grid leak,  $R_1$ , may be connected directly from grid to cathode instead of across the grid condenser as shown. The operation with either connection will be the same. Representative values for components are:

Component	Circuit A	Circuit B
$C_2$	100 to 250 $\mu\text{fd.}$	100 to 250 $\mu\text{fd.}$
$C_3$	0.001 to 0.002 $\mu\text{fd.}$	250 to 500 $\mu\text{fd.}$
$C_4$	0.1 $\mu\text{fd.}$	0.1 $\mu\text{fd.}$
$C_5$		0.5 $\mu\text{fd.}$ or larger.
$R_1$	1 to 2 megohms.	1 to 5 megohms.
$R_2$	50,000 ohms.	100,000 to 250,000 ohms.
$R_3$		50,000 ohms.
$R_4$		20,000 ohms.
L		500-henry choke.
RFC	2.5 mh.	2.5 mh.
T	Audio transformer.	

The plate voltage in A should be about 50 volts for best sensitivity. In B, the screen voltage should be about 30 volts and the plate voltage from 100 to 250.

d.c. through a high-resistance gain control often tends to make the control noisy (scratchy) after a short while.

The full-wave diode circuit at 5-2C differs in operation from the half-wave circuit only in that both halves of the r.f. cycle are utilized. The full-wave circuit has the advantage that very little r.f. voltage appears across the load resistor,  $R_1$ , because the midpoint of  $L_2$  is at the same potential as the cathode, or "ground" for r.f., and r.f. filtering is easier than in the half-wave circuit.

The reactance of  $C_2$  must be small compared to the resistance of  $R_1$  at the radio frequency being rectified, but at audio frequencies must be relatively large compared to  $R_1$ . This condition is satisfied by the values shown. If the capacity of  $C_2$  is too large, response at the higher audio frequencies will be lowered.

Compared with other detectors, the sensitiv-

ity of the diode is low. Since the diode consumes power, the  $Q$  of the tuned circuit is reduced, bringing about a reduction in selectivity. The linearity is good, however, and the signal-handling capability is high.

### Grid-Leak Detectors

The grid-leak detector is a combination diode rectifier and audio-frequency amplifier. In the circuits of Fig. 5-4, the grid corresponds to the diode plate and the rectifying action is exactly the same as just described. The d.c. voltage from rectified-current flow through the grid leak,  $R_1$ , biases the grid negatively with respect to cathode, and the audio-frequency variations in voltage across  $R_1$  are amplified through the tube just as in a normal a.f. amplifier. In the plate circuit,  $R_2$  is the plate load resistance,  $C_3$  is a by-pass condenser and  $RFC$  an r.f. choke to eliminate r.f. in the output circuit.  $C_4$  is the output coupling condenser. With a triode, the load resistor,  $R_2$ , may be replaced by an audio transformer,  $T$ , in which case  $C_4$  is not used.

Since audio amplification is added to rectification, the grid-leak detector has considerably greater sensitivity than the diode. The sensitivity can be further increased by using a screen-grid tube instead of a triode, as at 5-4B. The operation is equivalent to that of the triode circuit. The screen by-pass condenser,  $C_5$ , should have low reactance for both radio and audio frequencies.  $R_3$  and  $R_4$  constitute a voltage divider on the plate supply to furnish the proper d.c. voltage to the screen. In both circuits,  $C_2$  must have low r.f. reactance and high a.f. reactance compared to the resistance of  $R_1$ ; the same applies to  $C_3$  with respect to  $R_2$ . The reactance of  $RFC$  will be high for r.f. and low for audio frequencies.

Because of the high plate resistance of the screen-grid tube, transformer coupling from the plate circuit of a screen-grid detector is not satisfactory. An impedance ( $L$  in Fig. 5-4B) can be used in place of a resistor, with a gain in sensitivity because a high value of load impedance can be developed with little loss of plate voltage as compared to the voltage drop through a resistor. The coupling coil,  $L$ , for a screen-grid detector should have an inductance of the order of 300 to 500 henrys.

The sensitivity of the grid-leak detector is higher than that of any other type. Like the diode, it "loads" the tuned circuit and reduces its selectivity. The linearity is rather poor, and the signal-handling capability is limited. The signal-handling capability can be improved by reducing  $R_1$  to 0.1 megohm, but the sensitivity will be decreased.

### Plate Detectors

The plate detector is arranged so that rectification of the r.f. signal takes place in the plate circuit of the tube, as contrasted to the grid rectification just described. Sufficient negative

bias is applied to the grid to bring the plate current nearly to the cut-off point, so that the application of a signal to the grid circuit causes an increase in average plate current. The average plate current follows the changes in signal amplitude in a fashion similar to the rectified current in a diode detector.

Circuits for triodes and pentodes are given in Fig. 5-5.  $C_3$  is the plate by-pass condenser, and, with  $RFC$ , prevents r.f. from appearing in the output.  $R_1$  is the cathode resistor which provides the operating grid bias, and  $C_2$  is a by-pass for both radio and audio frequencies across  $R_1$ .  $R_2$  is the plate load resistance across which a voltage appears as a result of the rectifying action described above.  $C_4$  is the output coupling condenser. In the pentode circuit at B,  $R_3$  and  $R_4$  form a voltage divider to supply the proper potential (about 30 volts) to the screen, and  $C_5$  is a by-pass condenser between screen and cathode.  $C_5$  must have low reactance for both radio and audio frequencies.

In general, transformer coupling from the plate circuit of a plate detector is not satisfactory, because the plate impedance even of a triode is very high when the bias is set near the plate-current cut-off point. Impedance coupling may be used in place of the resistance

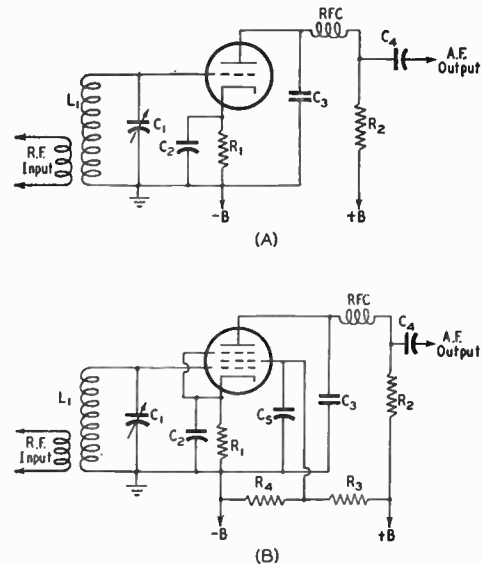


Fig. 5-5 — Circuits for plate detection. A, triode; B, pentode. The input circuit,  $L_1C_1$ , is tuned to the signal frequency. Typical values for the other components are:

Component	Circuit A	Circuit B
$C_2$	0.5 $\mu$ fd. or larger.	0.5 $\mu$ fd. or larger.
$C_3$	0.001 to 0.002 $\mu$ fd.	250 to 500 $\mu$ fd.
$C_4$	0.1 $\mu$ fd.	0.1 $\mu$ fd.
$C_5$		0.5 $\mu$ fd. or larger.
$R_1$	25,000 to 150,000 ohms.	10,000 to 20,000 ohms.
$R_2$	50,000 to 100,000 ohms.	100,000 to 250,000 ohms.
$R_3$		50,000 ohms.
$R_4$		20,000 ohms.
RFC	2.5 mh.	2.5 mh.

Plate voltages from 100 to 250 volts may be used. Effective screen voltage in B should be about 30 volts.

coupling shown in Fig. 5-5. The same order of inductance is required as with the pentode grid-leak detector described previously.

The plate detector is more sensitive than the diode since there is some amplifying action in the tube, but less so than the grid-leak detector. It will handle considerably larger signals than the grid-leak detector, but is not quite so tolerant in this respect as the diode. Linearity, with the self-biased circuits shown, is good. Up to the overload point the detector takes no power from the tuned circuit, and so does not affect its  $Q$  and selectivity.

#### Infinite-Impedance Detector

The circuit of Fig. 5-6 combines the high signal-handling capabilities of the diode detector with low distortion (good linearity), and, like the plate detector, does not load the tuned circuit it connects to. The circuit resembles that of the plate detector, except that the load resistance,  $R_1$ , is connected between cathode and ground and thus is common to both grid and plate circuits, giving negative feed-back for the audio frequencies. The cathode resistor is by-passed for r.f. ( $C_2$ ) but not for audio, while the plate circuit is by-passed to ground for both audio and radio frequencies.  $R_2$  forms, with  $C_3$ , an  $RC$  filter to isolate the plate from the "B" supply at a.f. An r.f. filter, consisting of a series r.f. choke and a shunt condenser, can be connected between the cathode and  $C_4$  to eliminate any r.f. that might otherwise appear in the output.

The plate current is very low at no signal, increasing with signal as in the case of the plate detector. The voltage drop across  $R_1$  similarly increases with signal, because of the increased plate current. Because of this and the fact that the initial drop across  $R_1$  is large, the grid cannot be driven positive with respect to the cathode by the signal, hence no grid current can be drawn.

### ● REGENERATIVE DETECTORS

By providing controllable r.f. feed-back or regeneration in a triode or pentode detector circuit, the incoming signal can be amplified many times, thereby greatly increasing the sensitivity of the detector. Regeneration also increases the effective  $Q$  of the circuit and increases the selectivity because the maximum regenerative amplification takes place only at the frequency to which the circuit is tuned. The grid-leak type of detector is most suitable for the purpose. Except for the regenerative connection, the circuit values are identical with those previously described for this type of detector, and the same considerations apply. The amount of regeneration must be controllable, because maximum regenerative amplification is secured at the critical point where the circuit is just about to oscillate, and the critical point in turn depends upon circuit conditions, which may vary with the

frequency to which the detector is tuned. In the oscillating condition, a regenerative detector can be detuned slightly from an incoming c.w. signal to give *autodyne* reception.

Fig. 5-7 shows the circuits of regenerative detectors of various types. The circuit of A is for a triode tube, with a variable by-pass condenser,  $C_3$ , in the plate circuit to control regeneration. When the capacity is small the tube does not regenerate, but as it increases toward maximum its reactance becomes smaller until a critical value is reached where there is sufficient feed-back to cause oscillation. If  $L_2$  and  $L_3$  are wound end-to-end in the same direction, the plate connection is to the outside of the plate or "tickler" coil,  $L_3$ , when the grid connection is to the outside of  $L_2$ .

The circuit of 5-7B is for a pentode tube, regeneration being controlled by adjustment of the screen-grid voltage. The tickler,  $L_3$ , is in the plate circuit. The portion of the control resistor between the rotating contact and ground is by-passed by a large condenser (0.5  $\mu$ fd. or more) to filter out scratching noise when the arm is rotated. The feed-back is adjusted by varying the number of turns on  $L_3$  or the coupling between  $L_2$  and  $L_3$ , until the tube just goes into oscillation at a screen potential of approximately 30 volts.

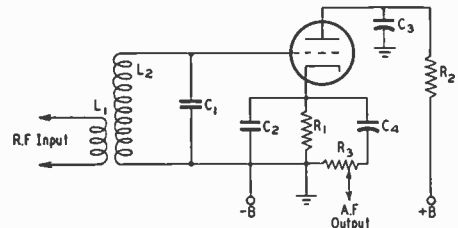


Fig. 5-6 — The infinite-impedance detector. The input circuit,  $L_2C_1$ , is tuned to the signal frequency. Typical values for the other components are:

$C_2$  — 250  $\mu$ fd.       $R_1$  — 0.15 megohm.  
 $C_3$  — 0.5  $\mu$ fd.       $R_2$  — 25,000 ohms.  
 $C_4$  — 0.1  $\mu$ fd.       $R_3$  — 0.25-megohm volume control.

A tube having a medium amplification factor (about 20) should be used. Plate voltage should be 250 volts.

Circuit C is identical with B in principle of operation, except that the oscillating circuit is of the Hartley type. Since the screen and plate are in parallel for r.f. in this circuit, only a small amount of "tickler" — that is, relatively few turns between the cathode tap and ground — is required for oscillation.

#### Smooth Regeneration Control

The ideal regeneration control would permit the detector to go into and out of oscillation smoothly, would have no effect on the frequency of oscillation, and would give the same value of regeneration regardless of frequency and the loading on the circuit. In practice, the effects of loading, particularly the loading that occurs when the detector circuit is coupled to an antenna, are difficult to overcome. Like-

wise, the regeneration is usually affected by the frequency to which the grid circuit is tuned.

In all circuits it is best to wind the tickler at the ground or cathode end of the grid coil, and to use as few turns on the tickler as will allow the detector to oscillate easily over the whole tuning range at the plate (and screen, if a pentode) voltage that gives maximum sensitivity. Should the tube break into oscillation suddenly as the regeneration control is advanced, making a click, the operation often can be made smoother by changing the grid-leak resistance to a higher or lower value. The wrong grid leak plus too-high plate and screen voltage are the most frequent causes of lack of smoothness in going into oscillation.

### Antenna Coupling

If the detector is coupled to an antenna, slight changes in the antenna constants (as when the wire swings in a breeze) affect the frequency of the oscillations generated, and thereby the beat frequency when c.w. signals are being received. The tighter the antenna coupling is made, the greater will be the feedback required or the higher will be the voltage necessary to make the detector oscillate. The antenna coupling should be the maximum that will allow the detector to go into oscillation smoothly with the correct voltages on the tube. If capacity coupling to the grid end of the coil is used, only a very small amount of capacity will be needed to couple to the antenna. Increasing the capacity increases the coupling.

At frequencies where the antenna system is resonant the absorption of energy from the oscillating detector circuit will be greater, with the consequence that more regeneration is needed. In extreme cases it may not be possible to make the detector oscillate with normal voltages, causing so-called "dead spots." The remedy for this is to loosen the antenna coupling to the point that permits normal oscillation and smooth regeneration control.

### Body Capacity

A regenerative detector occasionally shows a tendency to change frequency slightly as the hand is moved near the dial. This condition (body capacity) can be caused by poor design of the receiver, or by the antenna if the detector is coupled directly to it. If body capacity is present when the antenna is disconnected, it can be eliminated by better shielding, and sometimes by r.f. filtering of the 'phone leads. Body capacity that is present only when the antenna is connected is caused by resonance effects in the antenna, which tend to raise the whole detector circuit above ground potential. A good, short ground connection should be made to the receiver and the length of the antenna varied electrically (by adding a small coil or variable condenser in the antenna lead) until the effect is minimized. Loosening the coupling to the antenna circuit also will help.

### Hum

Hum at the power-supply frequency may be present in a regenerative detector, especially when it is used in an oscillating condition for c.w. reception, even though the plate supply itself is free from ripple. The hum may result from the use of a.c. on the tube heater, but effects of this type normally are troublesome

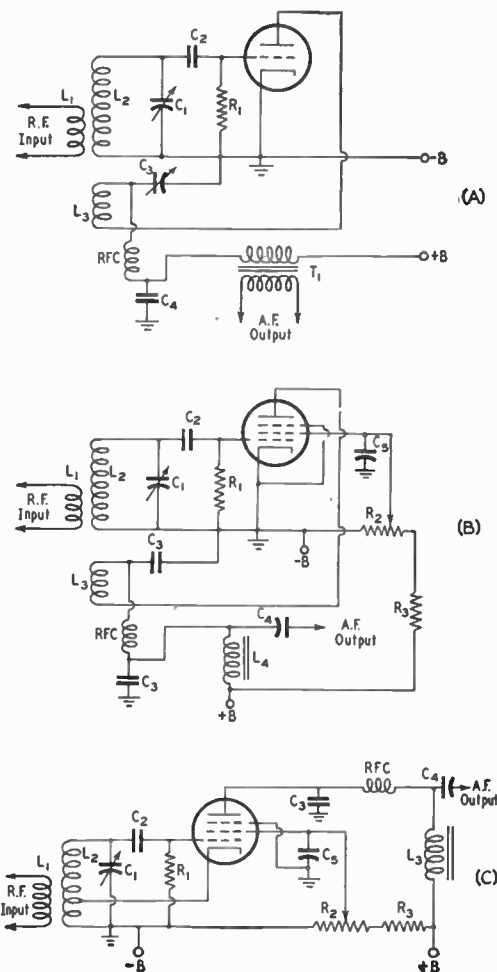


Fig. 5-7 — Triode and pentode regenerative detector circuits. The input circuit,  $L_2C_1$ , is tuned to the signal frequency. The grid condenser,  $C_2$ , should have a value of about 100  $\mu\text{fd.}$  in all circuits; the grid leak,  $R_1$ , may range in value from 1 to 5 megohms. The tickler coil,  $L_3$ , ordinarily will have from 10 to 25 per cent of the number of turns on  $L_2$ ; in C, the cathode tap is about 10 per cent of the number of turns on  $L_2$  above ground. Regeneration-control condenser  $C_3$  in A should have a maximum capacity of 100  $\mu\text{fd.}$  or more; by-pass condensers  $C_3$  in B and C are likewise 100  $\mu\text{fd.}$   $C_5$  is ordinarily 1  $\mu\text{fd.}$  or more;  $R_2$ , a 50,000-ohm potentiometer;  $R_3$ , 50,000 to 100,000 ohms.  $L_4$  in B ( $L_3$  in C) is a 500-henry inductance,  $C_4$  is 0.1  $\mu\text{fd.}$  in both circuits.  $T_1$  in A is a conventional audio transformer for coupling from the plate of a tube to a following grid. RFC is 2.5 mh. In A, the plate voltage should be about 50 volts for best sensitivity. Pentode circuits require about 30 volts on the screen; plate potential may be 100 to 250 volts.

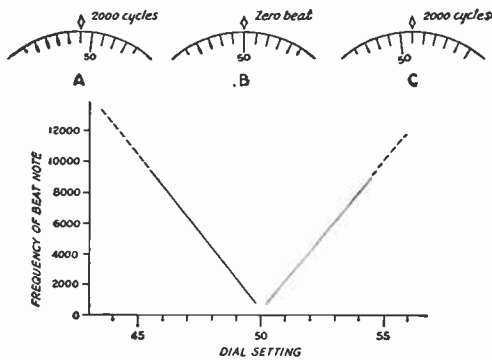


Fig. 5-8 — As the tuning dial of a receiver is turned past a c.w. signal, the beat-note varies from a high tone down through “zero beat” (no audible frequency difference) and back up to a high tone, as shown at A, B and C. The curve is a graphical representation of the action. The beat exists past 8000 or 10,000 cycles but usually is not heard because of the limitations of the audio system.

only when the circuit of Fig. 5-7C is used, and then only at 14 Mc. and higher frequencies. Connecting one side of the heater supply to ground, or grounding the center-tap of the heater-transformer winding, is good practice to reduce hum, and the heater wiring should be kept as far as possible from the r.f. circuits.

House wiring, if of the “open” type, will have a rather extensive electrostatic field which may cause hum if the detector tube, grid lead, and grid condenser and leak are not electrostatically shielded. This type of hum is easily recognizable because of its rather high pitch (a result of harmonics in the power-supply system).

Antenna resonance effects frequently cause a hum of the same nature as that just described which is most intense at the various resonance points, and hence varies with tuning. For this reason it is called **tunable hum**. It is prone to occur with a rectified-a.c. plate supply, when the receiver is put “above ground” by the antenna, as described in a preceding paragraph. The effect is associated with the non-linearity of the rectifier tube in the plate supply. Elimination of antenna resonance effects as described and by-passing the rectifier plates to cathode (using by-pass condensers of the order of 0.001  $\mu$ fd.) usually will cure it.

### Tuning

For c.w. reception, the regeneration control is advanced until the detector breaks into a “hiss,” which indicates that the detector is

oscillating. Further advancing the regeneration control after the detector starts oscillating will result in a slight decrease in the strength of the hiss, indicating that the sensitivity of the detector is decreasing.

The proper adjustment of the regeneration control for best reception of c.w. signals is where the detector just starts to oscillate, when it will be found that c.w. signals can be tuned in and will give a tone with each signal depending on the setting of the tuning control. As the receiver is tuned through a signal the tone first will be heard as a very high pitch, then will go down through “zero beat” (the region where the frequencies of the incoming signal and the oscillating detector are so nearly alike that the difference or beat is less than the lowest audible tone) and rise again on the other side, finally disappearing at a very high pitch. This behavior is shown in Fig. 5-8. It will be found that a low-pitched beat-note cannot be obtained from a strong signal because the detector “pulls in” or “blocks”; that is, the signal tends to control the detector in such a way that the latter oscillates at the signal frequency, despite the fact that the circuit may not be tuned exactly to resonance. This phenomenon, commonly observed when an oscillator is coupled to a source of a.c. voltage of approximately the frequency at which the oscillator is operating, is called “locking-in”; the more stable of the two frequencies assumes control over the other. “Blocking” usually can be corrected by advancing the regeneration control until the beat-note occurs again. If the regenerative detector is preceded by an r.f. amplifier stage, the blocking can be eliminated by reducing the gain of the r.f. stage. If the detector is coupled to an antenna, the blocking condition can be satisfactorily eliminated by advancing the regeneration control or loosening the antenna coupling.

The point just after the detector starts oscillating is the most sensitive condition for c.w. reception. Further advancing the regeneration control makes the receiver less prone to blocking by strong signals, but also less capable of receiving weak signals.

If the detector is in the oscillating condition and a ‘phone signal is tuned in, a steady audible beat-note will result. While it is possible to listen to ‘phone if the receiver can be tuned to exact zero beat, it is more satisfactory to reduce the regeneration to the point just before the receiver goes into oscillation. This is also the most sensitive operating point.

## Audio-Frequency Amplifiers

The ordinary detector does not produce very much audio-frequency power output — usually not enough to give satisfactory sound volume, even in headphone reception. Consequently, audio-frequency amplifiers are used after the detector to increase the power level.

One amplifier usually is sufficient for headphones, but two stages generally are used where the receiver is to operate a loudspeaker. A few milliwatts of a.f. power are sufficient for headphones, but a loudspeaker requires a watt or more for good room volume.

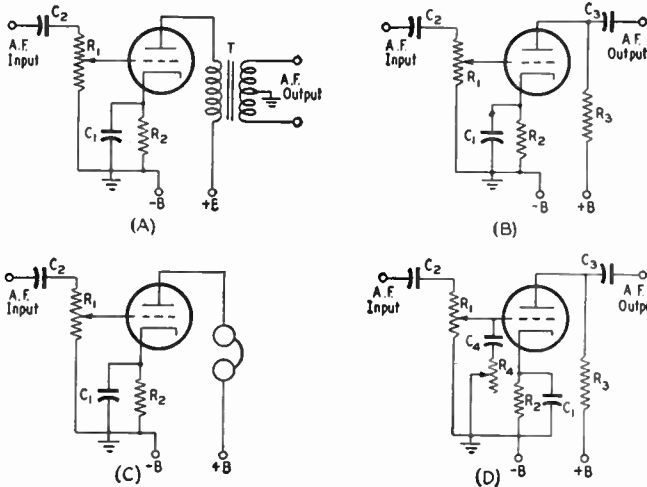


Fig. 5-9 — Audio-amplifier circuits used for voltage amplification and to provide power for headphone output. The tubes are operated as Class A amplifiers. A simple tone-control circuit ( $R_4C_4$ ) is shown in D.

### Headset and Voltage Amplifiers

The circuits shown in Fig. 5-9 are typical of those used for voltage amplification and for providing sufficient power for operation of headphones. Triodes usually are preferred to pentodes because they are better suited to working into an audio transformer or headset, the input impedances of which are of the order of 20,000 ohms.

In these circuits,  $R_2$  is the cathode bias resistor and  $C_1$  the cathode by-pass condenser. The grid resistor,  $R_1$ , gives volume-control action. Its value ordinarily is from 0.25 to 1 megohm.  $C_2$  is the input coupling condenser, already discussed under detectors; it is, in fact, identical to  $C_4$  in Figs. 5-4 and 5-5, if the amplifier is coupled to a detector. In 5-9D,  $C_4$  and  $R_4$  are a simple "tone-control" circuit. As  $R_4$  is made smaller,  $C_4$  by-passes more of the high audio frequencies.  $R_4$  should be large compared to the reactance of  $C_4$  at the highest audio frequency.

In all receivers using tubes with indirectly-heated cathodes, the negative grid bias of audio amplifiers usually is secured from the voltage drop in a cathode resistor. The cathode resistor must be by-passed by a condenser having low reactance at the lowest audio frequency to be amplified, compared to the resistance of the cathode resistor (10 per cent or less). In battery-operated receivers, which use filament-type tubes, a separate grid-bias battery generally is used.

### Power Amplifiers

A popular type of power amplifier is the single tetrode, operated Class A or AB; the circuit diagram is given in Fig. 5-10A. The grid resistor,  $R_1$ , may be a potentiometer for volume control, as shown at  $R_1$  in Fig. 5-9. The output transformer,  $T$ , should have a turns ratio suitable for the loudspeaker used; many of the

small loudspeakers now available are furnished complete with output transformer.

When greater volume is needed, a pair of tetrodes or pentodes may be connected in push-pull, as shown in Fig. 5-10B. Transformer coupling to the voltage-amplifier stage is the simplest method of obtaining push-pull input for the amplifier grids. The interstage transformer,  $T_1$ , has a center-tapped secondary

with a secondary-to-primary turns ratio of about 2 to 1. An output transformer,  $T_2$ , with a center-tapped primary must be used. No bypass condenser is needed across the cathode resistor,  $R$ , in Class A operation since the a.f. current does not flow through the resistor as it does in single-tube circuits.

### Headphones and Loudspeakers

Two types of headphones are in general use, the magnetic and crystal types. They are shown in cross-section in Fig. 5-11. In the magnetic type the signal is applied to a coil or pair of coils having a great many turns of fine wire wound on a permanent magnet. (Headphones having one coil are known as the "single-pole" type, while those having two coils, as shown in Fig. 5-11, are called "double-

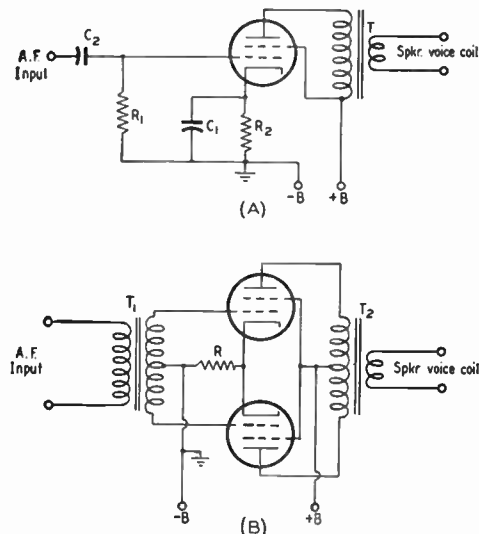


Fig. 5-10 — Power-output audio-amplifier circuits. Either Class A or AB amplification may be used.

pole.") A thin circular diaphragm of iron is placed close to the open ends of the magnet. It is tightly clamped by the earpiece assembly around its circumference, and the center is drawn toward the permanent magnet under some tension. When an alternating current flows through the windings the field set up by the current alternately aids and opposes the steady field of the permanent magnet, so that

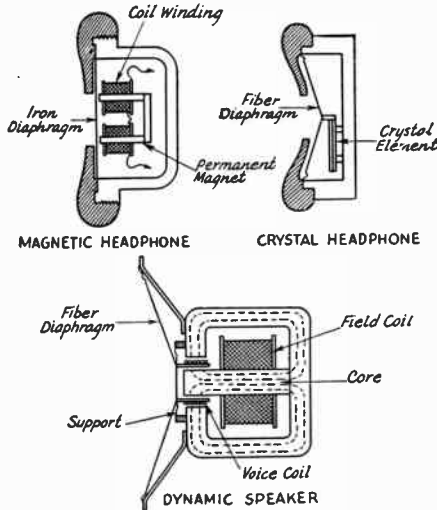


Fig. 5-11 — Headphone and loudspeaker construction.

the diaphragm alternately is drawn nearer to and allowed to spring farther away from the magnet. Its motion sets the air into corresponding vibration. Although the d.c. resistance of the coils may be of the order of 2000 ohms, the a.c. impedance of a magnetic-type headset will be of the order of 20,000 ohms at 1000 cycles.

In the crystal headphone, two piezoelectric crystals made of Rochelle salts are cemented together in such a way that the pair tend to be bent in one direction when a voltage of a certain polarity is applied and to bend in the other direction when the polarity is reversed. The crystal unit is rigidly mounted to the earpiece, with the free end coupled to a diaphragm. When an alternating voltage is applied, the alternate bending as the polarity of the applied voltage reverses makes the diaphragm vibrate back and forth. The impedance is several times that of the magnetic type.

Magnetic-type headsets tend to give maximum response at frequencies of the order of 500 to 1000 cycles, with a considerable reduction of response at frequencies both above and below this region. The crystal type has a "flatter" frequency-response curve, and is particularly good at reproducing the higher audio frequencies. The peaked response curve of the magnetic type is advantageous in code reception, since it tends to reduce interference from signals having beat tones lying outside the region of maximum response, while the crystal type is better for the reception of voice and music. Magnetic headsets can be used in circuits in which d.c. is flowing, such as the plate circuit of a vacuum tube, provided the current is not too large to be carried safely by the wire in the coils; the limit is a few milliamperes. Crystal headsets must be used only on a.c. (since a steady d.c. voltage will damage the crystal unit), and consequently must be coupled to the tube through a device, such as a condenser, that isolates the d.c. voltage but permits the passage of an alternating current.

The most common type of loudspeaker is the dynamic type, shown in cross-section in Fig. 5-11. The signal is applied to a small coil (the voice coil) which is free to move in the gap between the ends of a magnet. The magnet is made in the form of a cylindrical coil, slightly smaller than the form on which the voice coil is wound, with the magnetic circuit completed through a pole piece which fits around the outside of the voice coil, leaving just enough clearance for free movement of the coil. The path of the flux through the magnet is as shown by the dotted lines in the figure. The voice coil is supported so that it is free to move along its axis but not in other directions, and is fastened to a fiber or paper conical diaphragm. When current is sent through the coil it moves in a direction determined by the polarity of the current, and thus moves back and forth when an alternating voltage is applied. The motion is transmitted by the diaphragm to the air, setting up sound waves.

The type of 'speaker shown in Fig. 5-11 obtains its fixed magnetic field by electromagnetic means, direct current being sent through the field coil for this purpose. Other types use permanent magnets to replace the electromagnet, and hence do not require a source of d.c. power. The voice coils of dynamic 'speakers have few turns and therefore low impedance, values of 3 to 15 ohms being representative.

## Tuning and Band-Changing Methods

### Band-Changing

The resonant circuits that are tuned to the frequency of the incoming signal constitute a special problem in the design of amateur receivers, since the amateur frequency assignments consist of groups or bands of frequencies

at widely-spaced intervals. The same *LC* combination cannot be used for, say, 14 Mc. to 3.5 Mc., because of the impracticable maximum-minimum capacity ratio required, and also because the tuning would be excessively critical with such a large frequency range. It is necessary, therefore, to provide a means for



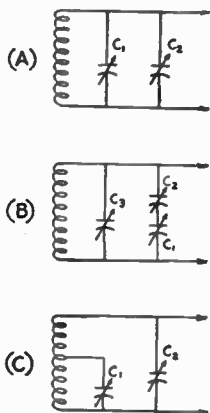


Fig. 5-12—Essentials of the three basic band-spread tuning systems.

changing the circuit constants for various frequency bands. As a matter of convenience the same tuning condenser usually is retained, but new coils are inserted in the circuit for each band.

One method of changing inductances is to use a switch having an appropriate number of contacts, which connects the desired coil and disconnects the others. Another is to use coils wound on forms with contacts (usually pins) which can be plugged in and removed from a socket.

### Bandspreading

The tuning range of a given coil and variable condenser will depend upon the inductance of the coil and the change in tuning capacity. For ease of tuning, it is desirable to adjust the tuning range so that practically the whole dial scale is occupied by the band in use. This is called **bandspreading**. Because of the varying widths of the bands, special tuning methods must be devised to give the correct maximum-minimum capacity ratio on each band. Several of these methods are shown in Fig. 5-12.

In A, a small **bandspread condenser**,  $C_1$  (15- to 25- $\mu\text{fd.}$  maximum capacity), is used in parallel with a condenser,  $C_2$ , which is usually large enough (100 to 140  $\mu\text{fd.}$ ) to cover a 2-to-1 frequency range. The setting of  $C_2$  will determine the minimum capacity of the circuit, and the maximum capacity for bandspread tuning will be the maximum capacity of  $C_1$  plus the setting of  $C_2$ . The inductance of the coil can be adjusted so that the maximum-minimum ratio will give adequate bandspread. In practicable circuits it is almost impossible, because of the nonharmonic relation of the various bands, to get full bandspread on all bands with the same pair of condensers, especially when the coils are wound to give continuous frequency coverage on  $C_2$ , which is variously called the **band-setting** or **main-tuning condenser**.  $C_2$  must be reset each time the band is changed.

The method shown at B makes use of condensers in series. The tuning condenser,  $C_1$ , may have a maximum capacity of 100  $\mu\text{fd.}$  or more. The minimum capacity is determined principally by the setting of  $C_3$ , which usually has low capacity, and the maximum capacity by the setting of  $C_2$ , which is of the order of 25 to 50  $\mu\text{fd.}$  This method is capable of close adjustment to practically any desired degree of bandspread. Either  $C_2$  and  $C_3$  must be adjusted for each band or separate preadjusted condensers must be switched in.

The circuit at C also gives complete spread on each band.  $C_1$ , the bandspread condenser, may have any convenient value of capacity; 50  $\mu\text{fd.}$  is satisfactory.  $C_2$  may be used for continuous frequency coverage ("general coverage") and as a band-setting condenser. The effective maximum-minimum capacity ratio depends upon the capacity of  $C_2$  and the point at which  $C_1$  is tapped on the coil. The nearer the tap to the bottom of the coil, the greater the bandspread, and vice versa. For a given coil and tap, the bandspread will be greater if  $C_2$  is set at larger capacity.  $C_2$  may be mounted in the plug-in coil form and preset, if desired. This requires a separate condenser for each band, but eliminates the necessity for resetting  $C_2$  each time the band is changed.

### Ganged Tuning

The tuning condensers of the several r.f. circuits may be coupled together mechanically and operated by a single control. However, this operating convenience involves more complicated construction, both electrically and mechanically. It becomes necessary to make the various circuits track — that is, tune to the same frequency at each setting of the tuning control.

True tracking can be obtained only when the inductance, tuning condensers, and circuit inductances and minimum and maximum capacities are identical in all "ganged" stages. A small **trimmer** or **padding condenser** may be connected across the coil, so that variations in minimum capacity can be compensated. The fundamental circuit is shown in Fig. 5-13, where  $C_1$  is the trimmer and  $C_2$  the tuning condenser. The use of the trimmer necessarily

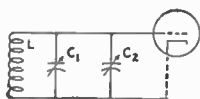


Fig. 5-13—Showing the use of a trimmer condenser, to set the minimum circuit capacity in order to obtain true tracking for gang-tuning.

increases the minimum circuit capacity, but it is a necessity for satisfactory tracking. Midget condensers having maximum capacities of 15 to 30  $\mu\text{fd.}$  are commonly used.

The same methods are applied to bandspread circuits that must be tracked. The circuits are identical with those of Fig. 5-12. If both general-coverage and bandspread tuning are to be available, an additional trimmer condenser must be connected across the coil in each circuit shown. If only amateur-band tuning is desired, however, then  $C_3$  in Fig. 5-12B, and  $C_2$  in Fig. 5-12C, serve as trimmers.

The coil inductance can be adjusted by starting with a larger number of turns than necessary and removing a turn or fraction of a turn at a time until the circuits track satisfactorily. An alternative method, provided the inductance is reasonably close to the correct value initially, is to make the coil so that the last turn is variable with respect to the whole

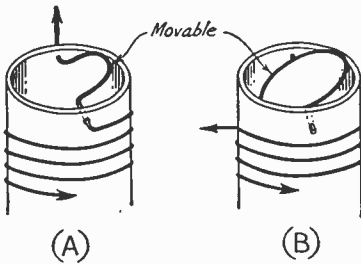


Fig. 5-14 — Methods of adjusting the inductance for gauging. The half-turn in A can be moved so that its magnetic field either aids or opposes the field of the coil. The shorted loop in B is not connected to the coil, but operates by induction. It will have no effect on the coil inductance when the axis of the loop is perpendicular to the axis of the coil, and will give maximum reduction of the coil inductance when rotated 90°. The loop can be a solid disk of metal and give exactly the same effect.

coil, or to use a single short-circuited turn the position of which can be varied with respect to the coil. The application of these methods is shown in Fig. 5-14.

Still another method for trimming the inductance is to use an adjustable brass (or copper) or powdered-iron core. The brass core acts like a single shorted turn, and the inductance of the coil is decreased as the brass core, or "slug," is moved into the coil. The powdered-iron core has the opposite effect, and *increases* the inductance as it is moved into the coil. The *Q* of the coil is not affected materially by the use of the brass slug, provided the brass slug has a clean surface or is silverplated. The use of the powdered-iron core will actually raise the *Q* of a coil, provided the iron core is of a type suitable for the frequency in use. Good powdered-iron cores can be obtained for use up to about 50 Mc.

## The Superheterodyne

For many years (up to about 1932) practically the only type of receiver to be found in amateur stations consisted of a regenerative detector and one or more stages of audio amplification. Receivers of this type can be made quite sensitive but they are lacking in stability and selectivity, particularly on the higher frequencies. Strong signals block them easily and, in our present crowded bands, they are seldom used except in emergencies. They have been replaced by superheterodyne receivers, generally called "superhets."

### The Superheterodyne Principle

In a superheterodyne receiver, the frequency of the incoming signal is changed to a new radio frequency, the intermediate frequency (abbreviated "i.f."), then amplified, and finally detected. The frequency is changed by means of the heterodyne process, the output of a tunable oscillator (the high-frequency, or local, oscillator) being combined with the incoming signal in a mixer or converter stage (first detector) to produce a beat frequency equal to the intermediate frequency. The audio-frequency signal is obtained at the second detector. C.w. signals are made audible by autodyne or heterodyne reception at the second detector.

As a numerical example, assume that an intermediate frequency of 455 kc. is chosen and that the incoming signal is on 7000 kc. Then the high-frequency oscillator frequency may be set to 7455 kc., in order that the beat frequency (7455 minus 7000) will be 455 kc. The high-frequency oscillator could also be set to 6545 kc. and give the same difference frequency. To produce an audible c.w. signal at the second detector of, say, 1000 cycles, the autodyning or heterodyning oscillator would be set to either 454 or 456 kc.

The frequency-conversion process permits r.f. amplification at a relatively low frequency, the i.f. High selectivity and gain can be obtained at this frequency, and this selectivity and gain are constant. The separate oscillators can be designed for stability and, since the h.f. oscillator is working at a frequency considerably removed from the signal frequency, its stability is practically unaffected by the incoming signal.

### Images

Each h.f. oscillator frequency will cause i.f. response at two signal frequencies, one higher and one lower than the oscillator frequency. If the oscillator is set to 7455 kc. to tune to a 7000-kc. signal, for example, the receiver can respond also to a signal on 7910 kc., which likewise gives a 455-kc. beat. The resultant undesired signal of the two frequencies is called the *image*.

The radio-frequency circuits of the receiver (those used before the frequency is converted to the i.f.) normally are tuned to the desired signal, so that the selectivity of the circuits reduces or eliminates the response to the image signal. The ratio of the receiver voltage output from the desired signal to that from the image is called the *signal-to-image ratio*, or *image ratio*.

The image ratio depends upon the selectivity of the r.f. tuned circuits preceding the mixer tube. Also, the higher the intermediate frequency, the higher the image ratio, since raising the i.f. increases the frequency separation between the signal and the image and places the latter further away from the resonance peak of the signal-frequency input circuits. Most receiver designs represent a compromise between economy (few r.f. stages) and image rejection (large number of r.f. stages).

## Other Spurious Responses

In addition to images, other signals to which the receiver is not ostensibly tuned may be heard. Harmonics of the high-frequency oscillator may beat with signals far removed from the desired frequency to produce output at the intermediate frequency; such spurious responses can be reduced by adequate selectivity before the mixer stage, and by using sufficient shielding to prevent signal pick-up by any means other than the antenna. When a strong signal is received, the harmonics generated by rectification in the second detector may, by stray coupling, be introduced into the r.f. or mixer circuit and converted to the intermediate frequency, to go through the receiver in the same way as an ordinary signal. These "birdies" appear as a heterodyne beat on the desired signal, and are principally bothersome when the frequency of the incoming signal is not greatly different from the intermediate frequency. The cure is proper circuit isolation and shielding.

Harmonics of the beat oscillator also may be converted in similar fashion and amplified through the receiver; these responses can be reduced by shielding the beat oscillator and operating it at low output level.

## The Double Superheterodyne

At high and very-high frequencies it is difficult to secure an adequate image ratio when the intermediate frequency is of the order of 455 kc. To reduce image response the signal frequently is converted first to a rather high (1500, 5000, or even 10,000 kc.) intermediate frequency, and then — sometimes after further amplification — reconverted to a lower i.f. where higher adjacent-channel selectivity can be obtained. Such a receiver is called a **double superheterodyne**.

## FREQUENCY CONVERTERS

The first detector or mixer resembles an ordinary detector. A circuit tuned to the intermediate frequency is placed in the plate circuit of the mixer, to offer a high impedance to the i.f. voltage that is developed. The signal- and oscillator-frequency voltages appearing in the plate circuit are by-passed to ground, since they are not wanted in the output. The i.f. tuned circuit should have low impedance for these frequencies, a condition easily met if they do not approach the intermediate frequency.

The conversion efficiency of the mixer is the ratio of i.f. output voltage from the plate circuit to r.f. signal voltage applied to the grid. High conversion efficiency is desirable. The mixer tube noise also should be low if a good signal-to-noise ratio is wanted, particularly if the mixer is the first tube in the receiver.

The mixer should not require too much r.f. power from the h.f. oscillator, since it may be

difficult to supply the power and yet maintain good oscillator stability. Also, the conversion efficiency should not depend too critically on the oscillator voltage (that is, a small change in oscillator output should not change the gain), since it is difficult to maintain constant output over a wide frequency range.

A change in oscillator frequency caused by tuning of the mixer grid circuit is called **pulling**. If the mixer and oscillator could be completely isolated, mixer tuning would have no effect on the oscillator frequency; but in practice this is a difficult condition to attain. Pulling should be minimized, because the stability of the whole receiver depends critically upon the stability of the h.f. oscillator. Pulling decreases with separation of the signal and h.f.-oscillator frequencies, being less with high intermediate frequencies. Another type of pulling is caused by regulation in the power supply. Strong signals cause the supply voltage to change, and this in turn shifts the oscillator frequency.

## Circuits

If the first detector and high-frequency oscillator are separate tubes, the first detector is called a "mixer." If the two are combined in one envelope (as is often done for reasons of economy or efficiency), the first detector is called a "converter." In either case the function is the same, however.

Typical mixer circuits are shown in Fig. 5-15. The variations are chiefly in the way in which the oscillator voltage is introduced. In 5-15A, a pentode functions as a plate detector; the oscillator voltage is capacity-coupled to the grid of the tube through  $C_2$ . Inductive coupling may be used instead. The conversion gain and input selectivity generally are good, so long as the sum of the two voltages (signal and oscillator) impressed on the mixer grid does not exceed the grid bias. It is desirable to make the oscillator voltage as high as possible without exceeding this limitation. The oscillator power required is negligible. If the signal frequency is only 5 or 10 times the i.f., it may be difficult to develop enough oscillator voltage at the grid (because of the selectivity of the tuned input circuit). However, the circuit is a sensitive one and makes a good mixer, particularly with high- $G_m$  tubes like the 6AC7 and 6AK5. A good triode also works well in the circuit, and

**TABLE 5-1**  
Circuit and Operating Values for Converter Tubes

Tube	Plate Volts	Screen Volts	Cathode Resistor	Screen Resistor	Grid Leak	Grid I
6BE6	250	100	100 <sup>1</sup>	22,000	22,000	0.5 ma.
6K8	250	100	240 <sup>1</sup>	27,000	47,000	0.15-0.2
6SA7	250	100	0 <sup>1</sup> 160 <sup>2</sup>	18,000	22,000	0.5
6SB7Y	250	100	0 <sup>1</sup> 75 <sup>2</sup>	12,000 15,000	22,000	0.35

<sup>1</sup>Self-excited.

<sup>2</sup>Separate excitation.

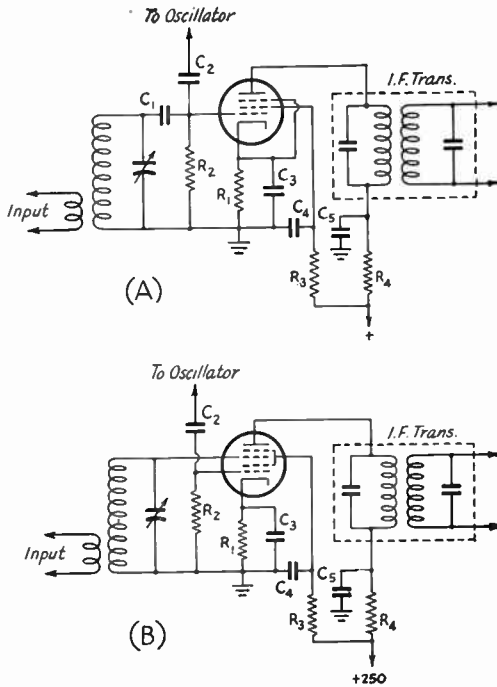


Fig. 5-15—Typical circuits for separately-excited mixers. Grid injection of a pentode mixer is shown at A, and separate excitation of a pentagrid converter is given in B. Typical values for B will be found in Table 5-1—the values below are for the pentode mixer of A.  
 $C_1$  — 10 to 50  $\mu\text{fd}$ .  $R_2$  — 1.0 megohm.  
 $C_2$  — 5 to 10  $\mu\text{fd}$ .  $R_3$  — 0.17 megohm.  
 $C_3, C_4, C_5$  — 0.001  $\mu\text{fd}$ .  $R_4$  — 1500 ohms.  
 $R_1$  — 6800 ohms.  
 Positive supply voltage can be 250 volts with a 6AC7, 150 with a 6AK5.

tubes like the 7F8 (one section), the 6J6 (one section) and the 6J4 work well. When a triode is used, care should be taken to see that the signal frequency is short-circuited in the plate circuit, and this is done by mounting the tuning capacitor of the i.f. transformer directly from plate to cathode.

It is difficult to avoid “pulling” in a triode or pentode mixer, however, and a pentagrid converter tube used as a mixer provides much better isolation. A typical circuit is shown in Fig. 5-15B, and tubes like the 6SA7, 7Q7 or 6BE6 are commonly used. The oscillator voltage is introduced into the electron stream of the tube through an “injection” grid. Measurement of the rectified current flowing in  $R_2$  is used as a check for proper oscillator-voltage amplitude. Tuning of the signal-grid circuit can have little effect on the oscillator frequency because the injection grid is isolated from the signal grid by a screen grid that is at r.f. ground potential. The pentagrid mixer is not quite as sensitive as a triode or pentode mixer, but its splendid isolating characteristics make it a very useful circuit.

Many receivers use pentagrid converters,

and two typical circuits are shown in Fig. 5-16. The circuit shown in Fig. 5-16A, which is suitable for the 6K8, 7D7, 7J7 or 7S7, is for a “triode-hexode” converter. A triode oscillator tube is mounted in the same envelope with a hexode, and the control grid of the oscillator portion is connected internally to an injection grid in the hexode. The isolation between oscillator and converter tube is reasonably good, and very little pulling results, except on signal frequencies that are quite large compared with the i.f.

The pentagrid-converter circuit shown in Fig. 5-16B can be used with a tube like the 6SA7, 7Q7 or 6BE6. Generally the only care necessary is to adjust the feed-back of the oscillator circuit to give the proper oscillator r.f. voltage. This condition is checked by measuring the d.c. current flowing in grid resistor  $R_2$ .

A more stable receiver generally results, particularly at the higher frequencies, when separate tubes are used for the mixer and oscillator. Practically the same number of circuit components is required whether or not a combination tube is used, so that there is little difference to be realized from the cost standpoint.

Typical circuit constants for converter tubes are given in Table 5-I. The grid leak referred to is the oscillator grid leak or injection-grid return,  $R_2$  of Figs. 5-15 and 5-16.

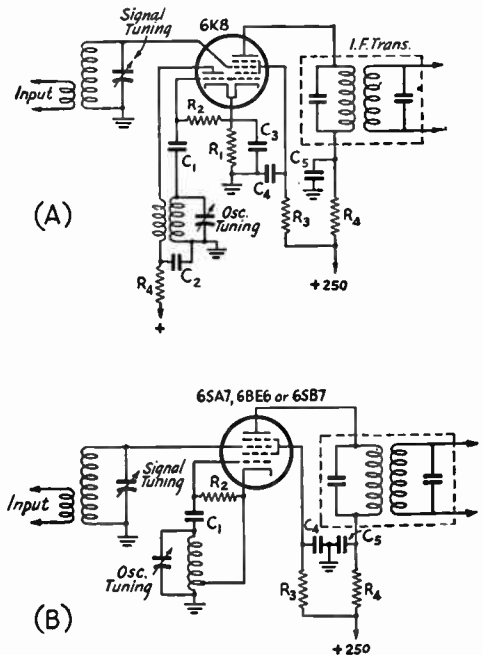


Fig. 5-16—Typical circuits for triode-hexode (A) and pentagrid (B) converters. Values for  $R_1, R_2$  and  $R_3$  can be found in Table 5-1, others are given below.  
 $C_1$  — 47  $\mu\text{fd}$ .  $C_3$  — 0.01  $\mu\text{fd}$ .  
 $C_2, C_4, C_5$  — 0.001  $\mu\text{fd}$ .  $R_4$  — 1000 ohms.

## ● THE HIGH-FREQUENCY OSCILLATOR

Stability of the receiver is dependent chiefly upon the stability of the h.f. oscillator, and particular care should be given this part of the receiver. The frequency of oscillation should be insensitive to changes in voltage, loading, and mechanical shock. Thermal effects (slow change in frequency because of tube or circuit heating) should be minimized. These ends can be attained by the use of high-grade insulating materials and circuit components, suitable electrical design, and careful mechanical construction.

In addition, the oscillator must be capable of furnishing sufficient r.f. voltage and power for the particular mixer circuit chosen, at all frequencies within the range of the receiver, and its harmonic output should be as low as possible to reduce the possibility of spurious response.

It is desirable to make the  $L/C$  ratio in the oscillator tuned circuit low (high- $C$ ), since this results in increased stability. Particular care should be taken to insure that no part of the oscillator circuit can vibrate mechanically. This calls for short leads and "solid" mechanical construction. The chassis and panel materials should be heavy and rigid enough so that pressure on the tuning dial will not cause torsion and a shift in the frequency. Care in mechanical construction of a receiver is repaid many times over by increased frequency stability.

### Circuits

Several oscillator circuits are shown in Fig. 5-17. The point at which output voltage is taken for the mixer is indicated in each case by  $X$  or  $Y$ . Circuits A and B will give about the same results, and require only one coil. However, in these two circuits the cathode is above ground potential for r.f., which often is a cause of hum modulation of the oscillator output at 14 Mc. and higher frequencies when indirectly-heated-cathode tubes with a.c. on the heaters are used. The circuit of Fig. 5-17C reduces hum because the cathode is grounded. It is a simple circuit to adjust, and it is also the best circuit to use with filament-type tubes. With filament-type tubes, the other two circuits would require r.f. chokes to keep the filament above r.f. ground.

Besides the use of a fairly high  $C/L$  ratio in the tuned circuit, it is necessary to adjust the feed-back to obtain optimum results. Too much feed-back will cause the oscillator to "squeg," or operate at several frequencies simultaneously; too little feed-back will cause the output to be low. In the tapped-coil circuits (A, B), the feed-back is increased by moving the tap toward the grid end of the coil; in C, by increasing the number of turns on  $L_2$  or by moving  $L_2$  closer to  $L_1$ .

The oscillator plate voltage should be as low as is consistent with adequate output. Low

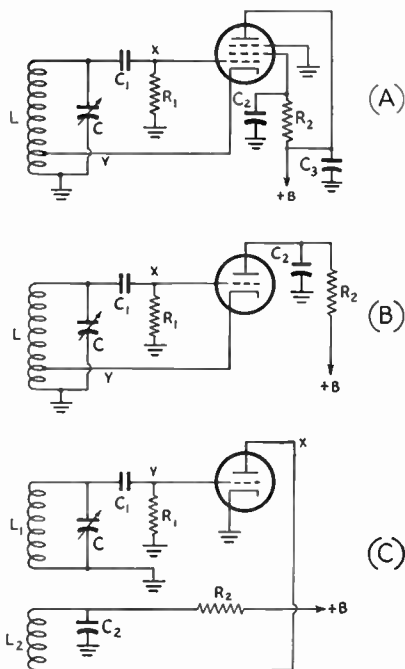


Fig. 5-17 — High-frequency oscillator circuits. A, pentode grounded-plate oscillator; B, triode grounded-plate oscillator; C, triode oscillator with tickler circuit. Coupling to the mixer may be taken from points X and Y. In A and B, coupling from Y will reduce pulling effects, but gives less voltage than from X; this type is best adapted to mixer circuits with small oscillator-voltage requirements. Typical values for components are as follows:

	Circuit A	Circuit B	Circuit C
$C_1$ —	100 $\mu\text{fd.}$	100 $\mu\text{fd.}$	100 $\mu\text{fd.}$
$C_2$ —	0.1 $\mu\text{fd.}$	0.1 $\mu\text{fd.}$	0.1 $\mu\text{fd.}$
$C_3$ —	0.1 $\mu\text{fd.}$		
$R_1$ —	47,000 ohms.	47,000 ohms.	47,000 ohms.
$R_2$ —	47,000 ohms.	10,000 to 25,000 ohms.	10,000 to 25,000 ohms.

The plate-supply voltage should be 250 volts. In circuits B and C,  $R_2$  is used to drop the supply voltage to 100–150 volts; it may be omitted if voltage is obtained from a voltage divider in the power supply.

plate voltage will cause reduced tube heating and thereby reduce frequency drift. The oscillator and mixer circuits should be well isolated, preferably by shielding, since coupling other than by the means intended may result in pulling.

If the h.f.-oscillator frequency is affected by changes in plate voltage, it is good practice to use a voltage-regulated plate supply employing a VR tube except, of course, in receivers operated from batteries. Changes in plate-supply voltage are caused not only by variations in the line voltage but by poor regulation in the power supply. When a.c. is used, the controlled tubes draw less current from the power supply as the signal increases, and this change in power-supply load causes the power-supply voltage to vary if it isn't regulated. The use of Class AB audio amplification may also cause severe changes in the power-supply voltage.

## A Two-Tube Superheterodyne Receiver

By using multipurpose tubes, it is possible to build a superheterodyne receiver using only two tubes. One tube is used as a pentagrid converter, and the other tube (a dual triode) acts as an autodyne detector working at the intermediate frequency, and as a stage of audio amplification.

A receiver of this type is shown in Figs. 5-18 through 5-22. The circuit diagram is given in Fig. 5-19. A 6K8 is used to convert the frequency of the incoming signal to the fixed or intermediate frequency, and the two triode sections of a 6SN7 serve as the regenerative detector and audio amplifier respectively.  $L_1C_1$  is the r.f. circuit, tuned to the signal, and  $L_2$  is the antenna coupling coil.  $C_7$  is a by-pass condenser across the 1.5-volt battery used to bias the signal grid of the 6K8 and the half of the 6SN7 used as an audio amplifier. The high-frequency oscillator tank circuit is  $L_3C_3C_4$ , with  $C_3$  for band-setting and  $C_4$  for bandspread.

The i.f. tuned circuit (or regenerative detector circuit) is  $L_5C_5$ . This must be a high- $C$  circuit if stability better than that of an ordinary regenerative detector is to be secured. The frequency to which it is tuned should be in the vicinity of 1600 kc.  $L_5$  and its tickler coil,  $L_6$ , are wound on a small form, and  $L_5$  is tuned by a fixed mica condenser of the low-drift type. Since these condensers are rated with a capacity tolerance of 5 per cent, it is sufficient to wind  $L_5$  as specified under Fig. 5-19. The resulting resonant frequency will be in the correct region. No manual tuning is necessary, and therefore the frequency of this circuit need not be adjusted.  $C_2$  is the regeneration-control condenser, isolated from the d.e.

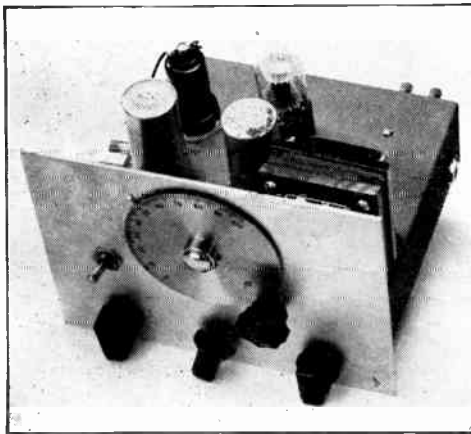


Fig. 5-18 — Panel view of the two-tube superheterodyne receiver. The panel is cut from a sheet of  $\frac{1}{8}$ -inch aluminum. It is 6 inches high and 8 inches wide. The controls along the bottom, from left to right, are mixer tuning, oscillator padder and i.f. regeneration. The "B" switch is to the left of the tuning dial.

supply by the choke, *RFC*. Only enough turns need be used on  $L_6$  to make the detector oscillate readily when  $C_2$  is at half capacity or more.

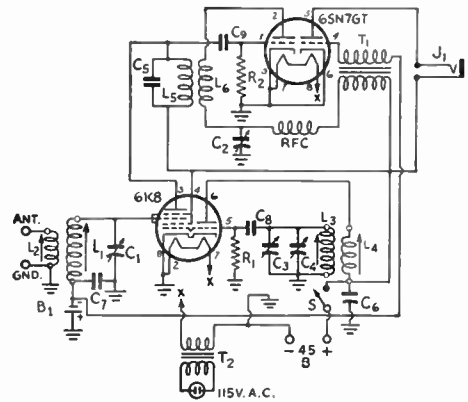


Fig. 5-19 — Circuit diagram of the two-tube superheterodyne receiver.

$C_1$ ,  $C_2$ ,  $C_3$  — 100- $\mu$ fd. variable (Millen 19100).

$C_4$  — 15- $\mu$ fd. variable (Millen 20015).

$C_5$  — 210- $\mu$ fd. silvered mica.

$C_6$  — 0.01- $\mu$ fd. paper.

$C_7$  — 0.0047- $\mu$ fd. mica.

$C_8$ ,  $C_9$  — 100- $\mu$ fd. mica.

$R_1$  — 47,000 ohms,  $\frac{1}{2}$  watt.

$R_2$  — 1 megohm,  $\frac{1}{2}$  watt.

$L_1$ ,  $L_2$ ,  $L_3$ ,  $L_4$  — See coil table.

$L_5$  — 55 turns No. 30 d.s.c., close-wound on  $\frac{3}{4}$ -inch diam. form (National PRF-2); inductance 10  $\mu$ h.

$L_6$  — 18 turns No. 30 d.s.c., close-wound on same form as  $L_5$ ; see Fig. 5-20.

$B_1$  — 1.5-volt bias battery.

$J_1$  — Open-circuit jack.

*RFC* — 2.5-mh. r.f. choke.

$S$  — S.p.s.t. toggle switch.

$T_1$  — Interstage audio transformer (Stancor A-4205).

$T_2$  — 6.3-volt filament transformer.

The second section of the 6SN7 is transformer-coupled to the detector, and battery bias is used. The headphone output is taken from  $J_1$ , in the plate circuit.

Looking at the top of the chassis from in front, the r.f. or input circuit is at the left, with  $C_1$  below the chassis and  $L_1L_2$  just behind it. The 6K8 is directly to the rear of the coil. The h.f.-oscillator padding condenser,  $C_3$ , underneath, the socket for  $L_3L_4$  and the 6SN7 are in line at the center of the chassis. At the right, underneath the audio transformer,  $T_1$ , is the i.f. regeneration-control condenser,  $C_2$ . The bandspread tuning condenser,  $C_4$ , is mounted on the panel with its shaft  $3\frac{7}{8}$  inches from the bottom edge of the panel. The audio transformer should be set back far enough so that there will be sufficient space for the bearing for the vernier knob of the National Type G dial. The "B" switch,  $S$ , is to the left of the dial.

A pair of terminals set in the left-hand edge

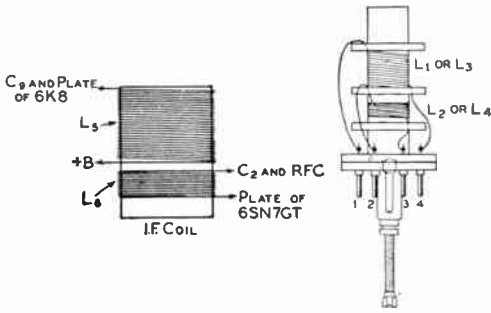


Fig. 5-20—How the coils for the two-tube superheterodyne receiver are wound. In both cases both windings are in the same direction. In the case of the i.f. coil at the left, the top end of the upper winding,  $L_5$ , is connected to  $C_9$  and Pin 3 of the 6K8 socket, the lower end of  $L_5$  is connected to Pin 4 of the 6K8, the upper end of the lower winding,  $L_6$ , is connected to the stator of  $C_2$  and the lower end of  $L_6$  goes to Pin 2 on the 6SN7GT socket.

In the case of the plug-in coils, the coil sockets and plug-in form bases are wired so that the upper end of  $L_3$  connects to the stator of  $C_3$ , the lower end of this winding to the chassis, the upper end of the lower winding,  $L_4$ , to  $C_5$  and the lower end of  $L_4$  goes to Pin 6 on the 6K8 socket. When the coil is plugged into the mixer stage, the upper end of the top winding should go to the stator of  $C_1$ , the lower end to  $C_7$ ; and the biasing battery, the upper end of the lower winding to the chassis and the lower end of the bottom winding to the antenna terminal.

of the chassis provide connections for antenna and ground, while another pair at the rear are for the "B"-battery connections. The antenna and B+ terminals must be insulated from the chassis. A jack in the right-hand side is provided for headphones, and 115 volts a.c. for the heater transformer,  $T_2$ , is plugged in at the rear. The headphone jack is insulated from the chassis by means of fiber washers.  $T_2$  is placed under the chassis near the headphone jack.

Referring to the bottom view of Fig. 5-22, the biasing battery is to the left below  $C_1$ . It is a pen-light flashlight cell soldered between the coil-socket terminal and ground. Immediately below it is the by-pass condenser,  $C_7$ .  $C_6$  is soldered between the socket terminal for  $L_4$

and ground. The r.f. choke is supported at one end by a small fiber lug strip and soldered to  $C_2$  at the other. The i.f. transformer,  $L_5L_6$ , is between the two tube sockets.  $L_5$  is connected between the proper tube-socket terminals and  $C_5$  is soldered across these same terminals.  $C_9$  is fastened directly between the two tube sockets and  $C_8$  between the 6K8 socket and the proper terminal of the socket for  $L_3$ . Clearance holes are drilled in the chassis for wiring to the switch, to the stator terminal of  $C_1$ , and to the grid cap of the 6K8. The rotor terminal of  $C_4$  is grounded to the panel by a lug fastened under one of the mounting pillars. Two holes also are provided for the leads to  $T_1$ .

Coils for the receiver are wound on Millen shielded  $\frac{1}{2}$ -inch diameter forms, Type 74001, which are provided with slug-type inductance trimmers.

The method of winding is indicated in Fig. 5-20; if the connections to the circuit are made as shown, there will be no trouble in obtaining the necessary oscillation. Both coils on each form should be wound in the same direction.

### Adjustment

To test the receiver, first try out the i.f. circuit. Connect the filament and "B" supplies and place both tubes in their sockets. Put a high-frequency coil in the r.f. socket, but do not insert a coil in the oscillator socket. The only test which needs to be made is to see if the detector oscillates properly. Advance  $C_2$  from minimum capacity until the detector goes into oscillation, which will be indicated by a soft hiss. This should occur at around half scale on the condenser. If it does not occur, check the coil ( $L_5L_6$ ) connections and winding direction and, if these seem right, add a few turns to the tickler,  $L_6$ . If the detector oscillates with very low capacity at  $C_2$ , it will be advisable to take a few turns off  $L_6$  until oscillation starts at about midscale.

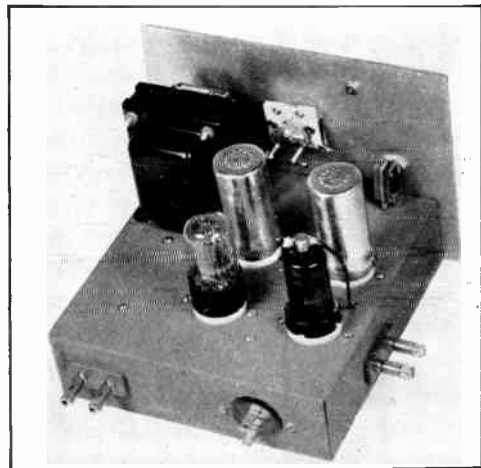


Fig. 5-21—A back-of-panel view of the two-tube superheterodyne receiver. The chassis is 7 × 7 × 2 inches.

### TWO-TUBE SUPERHET COIL DATA

$L_1$ or $L_3$		$L_2$ or $L_4$	
A. 90 turns No. 30 d.s.c., close wound	20 turns No. 30 d.s.c.		
B. 65 turns No. 26 d.s.c., close wound	15 turns No. 26 d.s.c.		
C. 45 turns No. 22 d.s.c., close wound	15 turns No. 26 d.s.c.		
D. 24 turns No. 22 enam.; $1\frac{1}{8}$ in. long	15 turns No. 26 d.s.c.		
E. 20 turns No. 22 enam.; $1\frac{1}{8}$ in. long	15 turns No. 26 d.s.c.		

Frequency Range	Coil at $L_1$ - $L_2$	Coil at $L_3$ - $L_4$
1700 to 3200 kc.	A	B
3000 to 5700 kc.	B	C
5400 to 10,000 kc.	C	D
9500 to 14,500 kc.	E	D

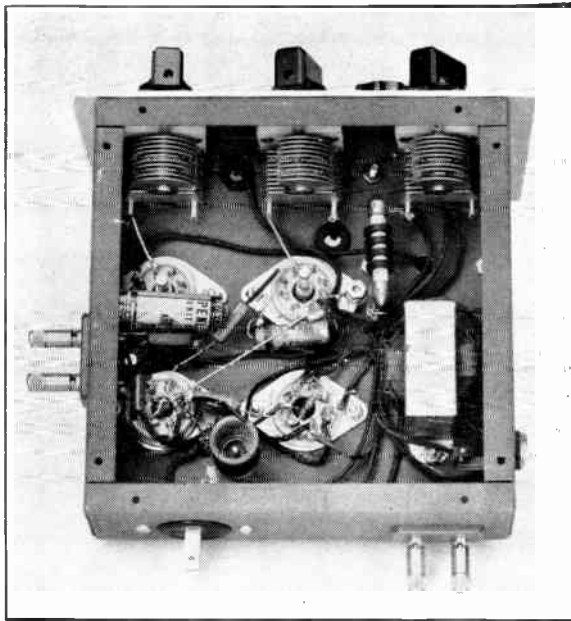


Fig. 5-22 — Bottom view of the two-tube superheterodyne receiver. The i.f. coil is between the two tube sockets near the rear of the chassis. The transformer to the right is the filament transformer.

After the i.f. has been checked, plug in an oscillator coil for a range on which signals are likely to be heard at the time. The 5400-10,000-ke. range is usually a good one. The coils are arranged so that a minimum number is needed, even though two are used at a time. With Coil C in the r.f. socket and D in the oscillator socket, set  $C_1$  at about half scale and turn  $C_3$  slowly around midscale until a signal is heard. Then tune  $C_1$  for maximum volume. Should no signals be heard, the probability is that the oscillator section of the 6K8 converter tube is not working, in which case the same method of testing is used as described above for the i.f. detector — check wiring, direction of windings of coils, and finally, add turns to the tickler,  $L_4$ , if necessary.

The same oscillator coil, D, is used for two frequency ranges. This is possible because the

oscillator frequency is placed on the low-frequency side of the signal on the higher range. This gives somewhat greater stability at the highest frequency range. Some pulling — a change in beat-note as the r.f. tuning is varied by means of  $C_1$  — will be observed on the highest frequency range, but it is not serious in the region of resonance with the incoming signal frequency.

The receiver will respond to signals either 1600 ke. lower or 1600 ke. higher than the oscillator frequency. The unwanted response is discriminated against by the selectivity of the r.f. circuit. On the three lower

frequency ranges, when it is possible to find two tuning spots on  $C_1$  at which incoming noise peaks up, the lower-frequency peak is the right one. The oscillator frequency is 1600 ke. higher than that of the incoming signal on these three ranges and 1600 ke. lower on the fourth range. The inductance of the coils to hit the desired ranges can be adjusted by means of the trimming slug in the coil forms.

The regeneration control may be set to give desired sensitivity and left alone while tuning; only when an exceptionally strong signal is encountered is it necessary to advance it more to keep the detector in oscillation. It should be set just on the edge of oscillation for 'phone reception.

The "B"-battery current is between 4 and 5 ma., so a standard 45-volt block will last hundreds of hours.

## The Intermediate-Frequency Amplifier

While the simple receiver just described is capable of highly-satisfactory results, it does not take full advantage of the superheterodyne principle. One major advantage of the superhet is that high gain and selectivity can be obtained by using a good i.f. amplifier. This can be a one-stage affair in simple receivers, or two or three stages in the more complex sets.

### Choice of Frequency

The selection of an intermediate frequency is a compromise between various conflicting factors. The lower the i.f. the higher the selectivity and gain, but a low i.f. brings the image nearer the desired signal and hence decreases the image ratio. A low i.f. also increases pulling

of the oscillator frequency. On the other hand, a high i.f. is beneficial to both image ratio and pulling, but the selectivity and gain are lowered. The difference in gain is least important.

An i.f. of the order of 455 ke. gives good selectivity and is satisfactory from the standpoint of image ratio and oscillator pulling at frequencies up to 7 Mc. The image ratio is poor at 14 Mc. when the mixer is connected to the antenna, but adequate when there is a tuned r.f. amplifier between antenna and mixer. At 28 Mc. and on the very-high frequencies, the image ratio is very poor unless several r.f. stages are used. Above 14 Mc., pulling is likely to be bad unless very loose coupling can be used between mixer and oscillator.



With an i.f. of about 1600 kc., satisfactory image ratios can be secured on 14, 28 and 50 Mc., and pulling can be reduced to negligible proportions. However, the i.f. selectivity is considerably lower, so that more tuned circuits must be used to increase the selectivity. For frequencies of 28 Mc. and higher, the best solution is to use a double superheterodyne, choosing one high i.f. for image reduction (5 and 10 Mc. are frequently used) and a lower one for gain and selectivity.

In choosing an i.f. it is wise to avoid frequencies on which there is considerable activity by the various radio services, since such signals may be picked up directly on the i.f. wiring. The frequencies mentioned are fairly free of such interference.

### Fidelity; Sideband Cutting

Modulation of a carrier causes the generation of sideband frequencies numerically equal to the carrier frequency plus and minus the highest modulation frequency present. If the receiver is to give a faithful reproduction of modulation that contains, for instance, audio frequencies up to 5000 cycles, it must be capable of amplifying equally all frequencies contained in a band extending from 5000 cycles above to 5000 cycles below the carrier frequency. In a superheterodyne, where all carrier frequencies are changed to the fixed intermediate frequency, this means that the i.f. amplifier should amplify equally well all frequencies within that band. In other words, the amplification must be uniform over a band 10 kc. wide, with the i.f. at its center. The signal-frequency circuits usually do not have enough over-all selectivity to affect materially the "adjacent-channel" selectivity, so that only the i.f.-amplifier selectivity need be considered.

A 10-kc. band is considered sufficient for reasonably-faithful reproduction of music, but much narrower bandwidths can be used for communication work where intelligibility rather than fidelity is the primary objective. If the selectivity is too great to permit uniform amplification over the band of frequencies occupied by the modulated signal, the higher

modulating frequencies are attenuated as compared to the lower frequencies; that is, the upper-frequency sidebands are "cut." While sideband cutting reduces fidelity, it is frequently preferable to sacrifice naturalness of reproduction in favor of greater selectivity.

The selectivity of an i.f. amplifier, and hence the tendency to cut sidebands, increases with the number of amplifier stages and also is greater the lower the intermediate frequency. From the standpoint of communication, sideband cutting is not serious with two-stage amplifiers at frequencies as low as 455 kc.

### Circuits

I.f. amplifiers usually consist of one or two stages. At 455 kc. two stages generally give all the gain usable, and also give suitable selectivity for good-quality 'phone reception.

A typical circuit arrangement is shown in Fig. 5-23. A second stage would simply duplicate the circuit of the first. The i.f. amplifier practically always uses a remote cut-off pentode-type tube operated as a Class A amplifier. For maximum selectivity, double-tuned transformers are used for interstage coupling, although single-tuned circuits or transformers with untuned primaries can be used for coupling, with a consequent loss in selectivity. All other things being equal, the selectivity of an i.f. amplifier is proportional to the number of tuned circuits in it. The use of too many high-Q tuned circuits in an amplifier is not generally feasible, however, because of stability problems.

In Fig. 5-23, the gain of the stage is reduced by introducing a negative voltage to the lead marked "to a.v.c." or a positive voltage to  $R_1$  at the point marked "to manual gain control." In either case, the voltage increases the bias on the tube and reduces the mutual conductance and hence the gain. When two or more stages are used, these voltages are generally obtained from common sources. The decoupling resistor,  $R_3$ , helps to isolate the amplifier from the power supply and thus prevents stray feed-back.  $C_2$  and  $R_4$  are part of the automatic volume-control circuit (described later); if no a.v.c. is used, the lower end of the i.f.-transformer secondary is simply connected to ground.

In a two-stage amplifier the screen grids of both stages may be fed from a common supply, either through a resistor ( $R_2$ ) as shown, the screens being connected in parallel, or from a voltage divider across the plate supply. Separate screen voltage-dropping resistors are preferable for preventing undesired coupling between stages.

Typical values of cathode and screen resistors for common tubes are given in Table 5-II. The 6K7, 6SK7, 6SG7, 6BA6 and 7H7 are recommended for i.f. work.

When two stages are used the high gain will tend to cause instability and oscillation, so that good shielding, by-passing, and careful

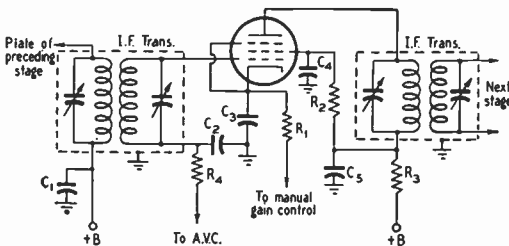


Fig. 5-23 — Typical intermediate-frequency amplifier circuit for a superheterodyne receiver. Representative values for components are as follows:

- $C_1$  — 0.1  $\mu$ fd. at 455 kc.; 0.01  $\mu$ fd. at 1600 kc. and higher.
- $C_2$  — 0.01  $\mu$ fd.
- $C_3, C_4, C_5$  — 0.1  $\mu$ fd. at 455 kc.; 0.01  $\mu$ fd. above 1600 kc.
- $R_1, R_2$  — See Table 5-II.  $R_3$  — 1800 ohms.
- $R_4$  — 0.27 megohm.

**TABLE 5-II**  
**Cathode and Screen-Dropping**  
**Resistors for R.F. or I.F. Amplifiers**

Tube	Plate Volts	Screen Volts	Cathode Resistor	Screen Resistor
6AB7	300		200 ohms	33,000 ohms
6AC7	300		160	62,000
6AK5	180	170	200	27,000
6AU6	250	150	68	33,000
6BA6	250	100	68	33,000
6J7	250	100	1200	270,000
6K7	250	125	240	47,000
6SG7	250	125	68	27,000
6SG7	250	150	200	47,000
6SH7	250	150	68	39,000
6SJ7	250	100	820	180,000
6SK7	250	100	270	56,000
7G7/1232	250	100	270	68,000
7H7	250	150	180	27,000

circuit arrangement to prevent stray coupling, with exposed r.f. leads well separated, are necessary.

**I.F. Transformers**

The tuned circuits of i.f. amplifiers are built up as transformer units consisting of a metal-shield container in which the coils and tuning condensers are mounted. Both air-core and powdered-iron-core universal-wound coils are used, the latter having somewhat higher *Q*s and, hence, greater selectivity and gain per unit. In universal windings the coil is wound in layers with each turn traversing the length of the coil, back and forth, rather than being wound perpendicular to the axis as in ordinary single-layer coils. In a straight multilayer winding, the turns on adjacent layers at the edges of the coil have a rather large potential difference between them as compared to the difference between any two adjacent turns in the same layer; hence a fairly large capacity can exist between layers. Universal winding, with its "criss-crossed" turns, tends to avoid building up such potential differences, and hence reduces distributed-capacity effects.

Variable tuning condensers are of the midget type, air-dielectric condensers being preferable because their capacity is practically unaffected by changes in temperature and humidity. Iron-core transformers may be tuned by varying the inductance (permeability tuning), in which case stability comparable to that of variable air-condenser tuning can be obtained by use of high-stability fixed mica condensers. Such stability is of great importance, since a circuit whose frequency "drifts" with time eventually will be tuned to a different frequency than the other circuits, thereby reducing the gain and selectivity of the amplifier. Typical i.f.-transformer construction is shown in Fig. 5-24.

Besides the type of i.f. transformer shown in Fig. 5-24, special units to give desired selectivity characteristics are available. For higher-than-ordinary adjacent-channel selectivity triple-tuned transformers, with a third tuned circuit inserted between the input and output

windings, are used. The energy is transferred from the input to the output windings via this tertiary winding, thus adding its selectivity to the over-all selectivity of the transformer. Variable-selectivity transformers also can be obtained. These usually are provided with a third (untuned) winding which can be connected to a resistor, thereby loading the tuned circuits and decreasing the *Q* and selectivity to broaden the selectivity curve. The variation in selectivity is brought about by switching the resistor in and out of the circuit. Another method is to vary the coupling between primary and secondary, overcoupling being used to broaden the selectivity curve and undercoupling to sharpen it.

**Selectivity**

The over-all selectivity of the i.f. amplifier will depend on the frequency and the number of stages. The following figures are indicative of the bandwidths to be expected with good-quality transformers in amplifiers so constructed as to keep regeneration at a minimum:

Intermediate Frequency	Bandwidth in Kilocycles		
	2 times down	10 times down	100 times down
One stage, 455 kc. (air core) . . .	8.7	17.8	32.3
One stage, 455 kc. (iron core) . .	4.3	10.3	20.4
Two stages, 455 kc. (iron core) . .	2.9	6.4	10.8
Two stages, 1600 kc. . . . .	11.0	16.6	27.4
Two stages, 5000 kc. . . . .	25.8	46.0	100.0

**Tubes for I.F. Amplifiers**

Variable- $\mu$  (remote cut-off) pentodes are almost invariably used in i.f. amplifier stages, since grid-bias gain control is practically always applied to the i.f. amplifier. Tubes with high plate resistance will have least effect on the selectivity of the amplifier, and those with high mutual conductance will give greatest

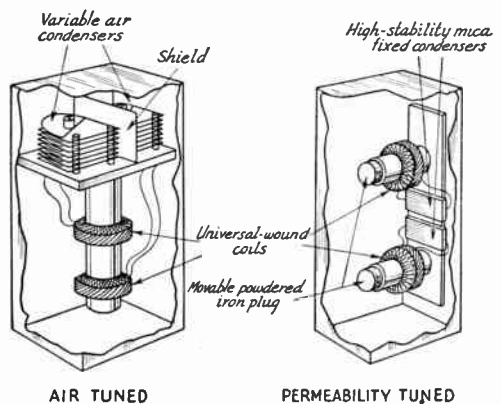


Fig. 5-24 — Representative i.f.-transformer construction. Coils are supported on insulating tubing or (in the air-tuned type) on wax-impregnated wooden dowels. The shield in the air-tuned transformer prevents capacity coupling between the tuning condensers. In the permeability-tuned transformer the cores consist of finely-divided iron particles supported in an insulating binder, formed into cylindrical "plugs." The tuning capacity is fixed, and the inductances of the coils are varied by moving the iron plugs in and out,

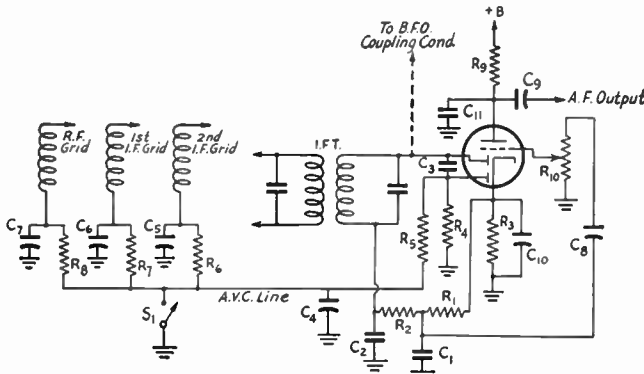


Fig. 5-25 — Automatic volume-control circuit using a dual-diode-triode as a combined a.v.c. rectifier, second detector and first audio-frequency amplifier.

- R<sub>1</sub> — 0.27 megohm.
- R<sub>2</sub> — 50,000 to 250,000 ohms.
- R<sub>3</sub> — 1800 ohms.
- R<sub>4</sub> — 2 to 5 megohms.
- R<sub>5</sub> — 0.5 to 1 megohm.
- R<sub>6</sub>, R<sub>7</sub>, R<sub>8</sub>, R<sub>9</sub> — 0.25 megohm.
- R<sub>10</sub> — 0.5-megohm variable.
- C<sub>1</sub>, C<sub>2</sub>, C<sub>3</sub> — 100  $\mu$ fd.
- C<sub>4</sub> — 0.1  $\mu$ fd.
- C<sub>5</sub>, C<sub>6</sub>, C<sub>7</sub> — 0.01  $\mu$ fd.
- C<sub>8</sub>, C<sub>9</sub> — 0.01 to 0.1  $\mu$ fd.
- C<sub>10</sub> — 5- to 10- $\mu$ fd. electrolytic. C<sub>11</sub> — 270  $\mu$ fd.

gain. The choice of i.f. tubes has practically no effect on the signal-to-noise ratio, since this is determined by the preceding mixer and r.f. amplifier (if the latter is used).

When single-ended tubes are used, care should be taken to keep the plate and grid leads well separated. With these tubes it is advisable to mount the screen by-pass condenser directly on the bottom of the socket, crosswise between the plate and grid pins, to provide additional shielding. The outside foil of the condenser should be connected to ground.

## ● THE SECOND DETECTOR AND BEAT OSCILLATOR

### Detector Circuits

The second detector of a superheterodyne receiver with an i.f. amplifier performs the same function as the detector in the simple receiver, but usually operates at a higher input level because of the relatively great amplification ahead of it. Therefore, the ability to handle large signals without distortion is preferable to high sensitivity. Plate detection is used to some extent, but the diode detector is most popular. It is especially adapted to furnishing automatic gain or volume control. The basic circuits have been described, although in many cases the diode elements are incorporated in a multipurpose tube that contains an amplifier section in addition to the diode.

### The Beat Oscillator

Any standard oscillator circuit may be used for the beat oscillator required for heterodyne

reception. Special beat-oscillator transformers are available, usually consisting of a tapped coil with adjustable tuning; these are most conveniently used with circuits such as those shown at Fig. 5-17A and B, with the output taken from Y. A variable condenser of about 25- $\mu$ fd. capacity may be connected between cathode and ground to provide fine adjustment. The beat oscillator usually is coupled to the second-detector tuned circuit through a fixed capacitor of a few  $\mu$ fd. capacity.

The beat oscillator should be well shielded, to prevent coupling to any part of the circuit except the second detector and

to prevent its harmonics from getting into the front end of the receiver and being amplified with desired signals. To this end, the plate voltage should be as low as is consistent with sufficient audio-frequency output. If the beat-oscillator output is too low, strong signals will not give a proportionately strong audio response.

When an oscillating second detector is used to give the audio beat-note, the detector must be detuned from the i.f. by an amount equal to the frequency of the beat note. The selectivity and signal strength will be reduced, while blocking will be pronounced because of the high signal level at the second detector.

## ● AUTOMATIC VOLUME CONTROL

### Principles

Automatic regulation of the gain of the receiver in inverse proportion to the signal strength is a great advantage, especially in 'phone reception, since it tends to keep the output level of the receiver constant regardless of input-signal strength. It is readily accomplished in superheterodyne receivers by using the average rectified d.c. voltage, developed by the received signal across a resistance in a detector circuit, to vary the bias on the r.f. and i.f. amplifier tubes. Since this voltage is proportional to the average amplitude of the signal, the gain is reduced as the signal strength becomes greater. The control will be more complete as the number of stages to which the a.v.c. bias is applied is increased. Control of at least two stages is advisable.

### Circuits

A typical circuit using a diode-triode type tube as a combined a.v.c. rectifier, detector and first audio amplifier is shown in Fig. 5-25. One plate of the diode section of the tube is used for signal detection and the other for a.v.c. rectification. The a.v.c. diode plate

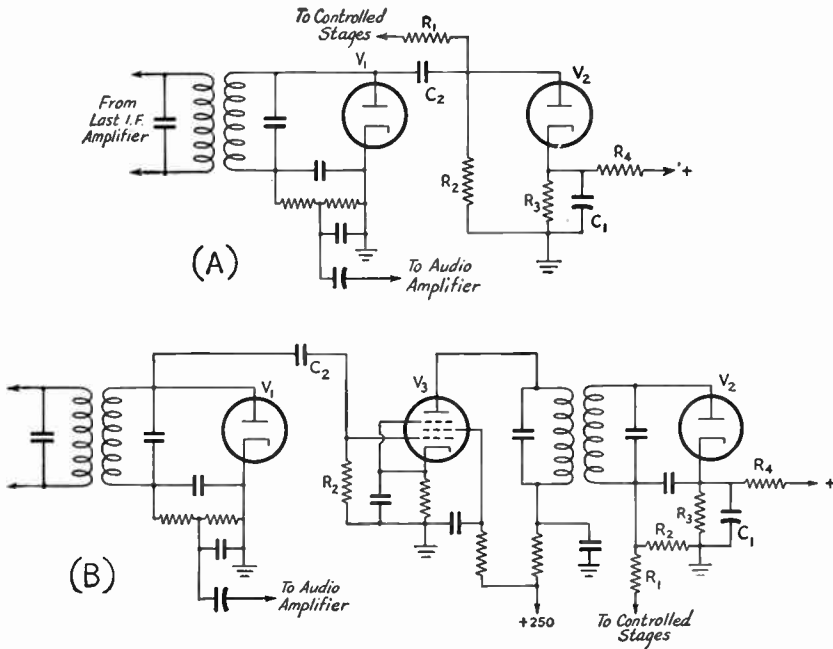


Fig. 5-26 — Delayed a.v.c. is shown at A, and amplified and delayed a.v.c. is shown in B. The circuit at B gives excellent a.v.c. action over a wide range, with no impairment of sensitivity for weak signals. For either circuit, typical values are:  
 $C_1$  — 0.001  $\mu$ fd.  
 $C_2$  — 100  $\mu$ fd.  
 $R_1, R_2$  — 1.0 megohm.  
 $R_3, R_4$  — Voltage divider.

Resistors  $R_3$  and  $R_4$  are carefully proportioned to give the desired delay voltage at the cathode of diode  $V_2$ . Bleeder current of 1 or 2 ma. is ample, and hence the bleeder can be figured on 1000 or 500 ohms per volt. The delay voltage should be in the vicinity of 3 or 4 for a simple receiver and 20 or 30 for a multitube high-gain affair.

is fed from the detector diode through the small coupling condenser,  $C_3$ . A negative bias voltage resulting from the flow of rectified carrier current is developed across  $R_4$ , the diode load resistor. This negative bias is applied to the grids of the controlled stages through the filtering resistors,  $R_5, R_6, R_7$  and  $R_8$ . When  $S_1$  is closed the a.v.c. line is grounded, thereby removing the a.v.c. bias from the amplifier without disturbing the detector circuit.

small signal. This is undesirable, because the full amplification of the receiver then could not be realized on weak signals. In the audio-diode circuit this fixed bias would cause distortion, and must be avoided; hence, the return is made directly to the cathode.

It does not matter which of the two diode plates is selected for audio and which for a.v.c. Frequently the two plates are connected together and used as a combined detector and a.v.c. rectifier. This could be done in Fig. 5-25. The a.v.c. filter and line would connect to the junction of  $R_2$  and  $C_2$ , while  $C_3$  and  $R_4$  would be omitted from the circuit.

**Time Constant**

**Delayed A. V. C.**

The time constant of the resistor-condenser combinations in the a.v.c. circuit is an important part of the system. It must be high enough so that the modulation on the signal is completely filtered from the d.c. output, leaving only an average d.c. component which follows the relatively slow carrier variations with fading. Audio-frequency variations in the a.v.c. voltage applied to the amplifier grids would reduce the percentage of modulation on the incoming signal, and in practice would cause frequency distortion. On the other hand, the time constant must not be too great or the a.v.c. will be unable to follow rapid fading. The capacitance and resistance values indicated in Fig. 5-25 will give a time constant that is satisfactory for high-frequency reception.

In Fig. 5-25 the audio-diode return is made directly to the cathode and the a.v.c. diode return to ground. This places negative bias on the a.v.c. diode equal to the d.c. drop through the cathode resistor (a volt or two) and thus delays the application of a.v.c. voltage to the amplifier grids, since no rectification takes place in the a.v.c. diode circuit until the carrier amplitude is large enough to overcome the bias. Without this delay the a.v.c. would start working even with a very

**C. W.**

A.v.c. can be used for c.w. reception but the circuit is more complicated. The a.v.c. voltage must be derived from a rectifier that

is isolated from the beat-frequency oscillator (otherwise the rectified b.f.o. voltage will reduce the receiver gain even with no signal coming through). This is generally done by using a separate a.v.c. channel connected to an i.f. amplifier stage ahead of the second detector (and b.f.o.). If the i.f. selectivity ahead of the a.v.c. rectifier isn't good, strong adjacent signals will develop a.v.c. voltages that will reduce the receiver gain while listening to weak signals. When clear channels are available, however, c.w. a.v.c. will hold the receiver output constant over a wide range of signal input.

#### *Amplified A.V.C.*

The a.v.c. system shown in Fig. 5-25 will not hold the audio output of the receiver ex-

actly constant, although the variation becomes less as more stages are controlled by the a.v.c. voltage. The variation also becomes less as the delay voltage is increased, although there will of course be variation in output if the signal intensity is below the delay-voltage level at the a.v.c. rectifier. In the circuit of Fig. 5-25, the delay voltage is set by the proper operating bias for the triode portion of the tube. However, a separate diode may be used, as shown in Fig. 5-26A. Since such a system requires a large voltage at the diode, a separate i.f. stage is sometimes used to feed the delayed a.v.c. diode, as in Fig. 5-26B. A system like this, sometimes called an amplified a.v.c. system, gives excellent control once the delay voltage is reached, and yet maintains full receiver sensitivity up to that point.

## Noise Reduction

#### *Types of Noise*

In addition to tube and circuit noise, much of the noise interference experienced in reception of high-frequency signals is caused by domestic electrical equipment and by automobile ignition systems. The interference is of two types in its effects. The first is the "hiss" type, consisting of overlapping pulses similar in nature to the receiver noise. It is largely reduced by high selectivity in the receiver, especially for code reception. The second is the "pistol-shot" or "machine-gun" type, consisting of separated impulses of high amplitude. The "hiss" type of interference usually is caused by commutator sparking in d.c. and series-wound a.c. motors, while the "shot" type results from separated spark discharges (a.c. power leaks, switch and key clicks, ignition sparks, and the like).

#### *Impulse Noise*

Impulse noise, because of the extremely short duration of the pulses as compared to the time between them, must have high pulse amplitude to contain much average energy. Hence, noise of this type strong enough to cause much interference generally has an

instantaneous amplitude much higher than that of the signal being received. The general principle of devices intended to reduce such noise is that of allowing the signal amplitude to pass through the receiver unaffected, but making the receiver inoperative for amplitudes greater than that of the signal. The greater the amplitude of the pulse compared to its time of duration the more successful the noise reduction, since more of the constituent energy can be suppressed.

In passing through selective receiver circuits, the time duration of the impulses is increased, because of the *Q* or flywheel effect of the circuits. Hence, the more selectivity ahead of the noise-reducing device, the more difficult it becomes to secure good noise suppression.

#### *Audio Limiting*

A considerable degree of noise reduction in code reception can be accomplished by amplitude-limiting arrangements applied to the audio output circuit of a receiver. Such limiters also maintain the signal output nearly constant without fading. These output-limiter systems are simple, and adaptable to most receivers. However, they cannot prevent noise peaks from overloading previous circuits.

## A Simple Audio Noise Limiter

The limiter shown in Fig. 5-27 is plugged into the receiver 'phone jack and the headphones are plugged into the limiter, so that no work on the receiver is required. The limiter will also keep the strength of c.w. signals at a constant comfortable level and will do much to relieve the operating fatigue resulting from long hours of listening to crackles, key clicks, blocking signals, and the like.

As can be seen from the wiring diagram in Fig. 5-28, two 1N34 crystal diodes, individually biased by 1½-volt dry cells, are used to

short-circuit any signal coming through the 'phone circuit that has an amplitude greater than about 3 volts, peak-to-peak. Hence if the audio gain of the receiver is adjusted to give a signal of this amplitude — comfortable headphone volume — noise peaks of greater amplitude will be short-circuited and not heard in the headphones. A 6AL5 twin diode can be substituted for the two 1N34 crystals, but a heater supply will be required and it is generally more convenient to build the limiter as shown. No current is drawn from the two cells

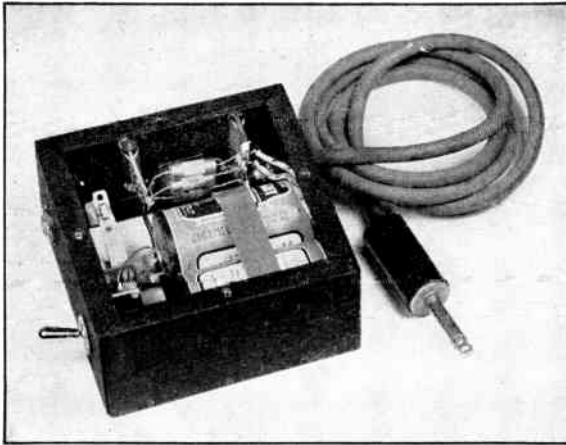


Fig. 5-27 — A crystal-diode noise limiter for use between receiver and headphones. Built in a 4 × 4 × 2-inch box, it contains the limiter crystals, bias cells, headphone jack and on-off switch, and is provided with a cord and plug to connect to the receiver headphone output.

Although primarily intended for c.w. reception, the limiter also is highly effective on 'phone signals when the audio volume level is properly set and the r.f. gain is automatically controlled.

used for bias, and they will last their shelf life.

The limiter can be built in a 4 × 4 × 2-inch cabinet, as shown in Fig. 5-27. By removing the two sides of the cabinet, all of the components can be mounted in the frame. The two dry cells can be taped together and then held in place by heavy leads soldered to them, or special clips can be made of spring brass. The two 1N34 crystal diodes are best mounted on tie-points, and the pigtailed of the diodes should be held in a pair of long-nose pliers while soldering to them, because too much heat from the soldering iron may decrease the effectiveness of the crystal. The pliers conduct away the heat that might otherwise reach the crystal.

● SECOND-DETECTOR NOISE-LIMITER CIRCUITS

The circuit of Fig. 5-29 "chops" noise peaks at the second detector of a superhet receiver by means of a biased diode, which becomes nonconducting above a predetermined signal level. The audio output of the detector must pass through the diode to the grid of the amplifier tube. The diode normally would be nonconducting with the connections shown were it not for the fact that it is given positive bias from a 30-volt source through the adjustable potentiometer,  $R_3$ . Resistors  $R_1$  and  $R_2$  must be fairly large in value to prevent loss of audio signal.

The audio signal from the detector can be considered to modulate the steady diode current, and conduction will take place so long as the diode plate is positive with respect to the

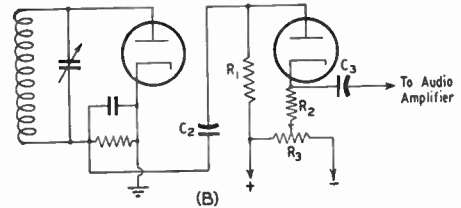
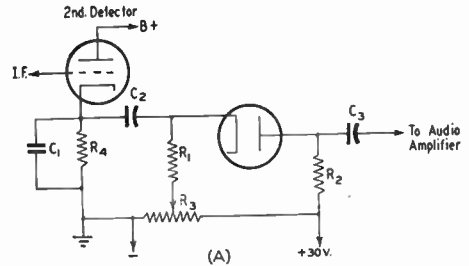


Fig. 5-29 — Series-valve noise-limiter circuits. A, as used with an infinite-impedance detector; B, with a diode detector. Typical values for components are as follows:  
 $R_1$  — 0.27 megohm.  $R_4$  — 20,000 to 50,000 ohms,  
 $R_2$  — 47,000 ohms.  $C_1$  — 270  $\mu$ fd.  
 $R_3$  — 10,000 ohms.  $C_2, C_3$  — 0.1  $\mu$ fd.

All other diode-circuit constants in B are conventional.

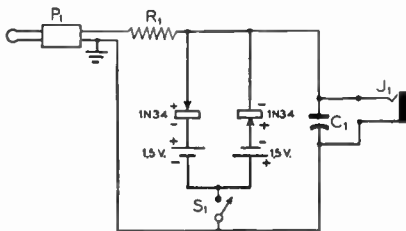


Fig. 5-28 — Practical noise-limiter circuit for headphone reception.

$C_1$  — 0.005  $\mu$ fd.  $J_1$  — Single-circuit jack.  
 $R_1$  — 15,000 ohms,  $\frac{1}{2}$  watt.  $P_1$  — Headphone plug.  
 $S_1$  — S.p.s.t. toggle.

cathode. When the signal is sufficiently large to swing the cathode positive with respect to the plate, however, conduction ceases, and that portion of the signal is cut off from the audio amplifier. The point at which cut-off occurs can be selected by adjustment of  $R_3$ . By setting  $R_3$  so that the signal just passes through the "valve," noise pulses higher in amplitude than the signal will be cut off. The circuit of Fig. 5-29A, using an infinite-impedance detector, gives a positive voltage on rectification. When the rectified voltage is negative, as it is from the usual diode detector,

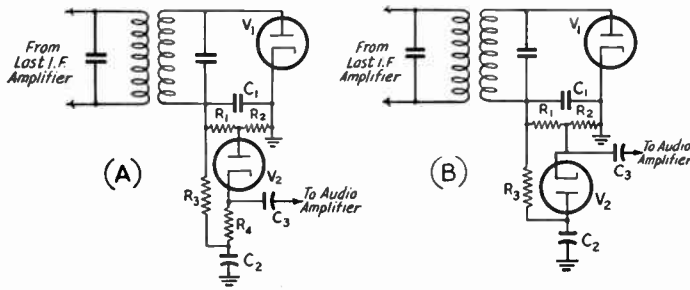


Fig. 5-30 — Self-adjusting series (A) and shunt (B) noise limiters. The functions of  $V_1$  and  $V_2$  can be combined in one tube like the 6H6 or 6AL5, or Type 1N34 crystals can be used.

- $C_1$  — 100  $\mu\text{fd}$ .
- $C_2, C_3$  — 0.05  $\mu\text{fd}$ .
- $R_1$  — 0.27 meg. in A; 47,000 ohms in B.
- $R_2$  — 0.27 meg. in A; 0.15 meg. in B.
- $R_3$  — 1.0 megohm.
- $R_4$  — 0.82 megohm.

the circuit arrangement shown in Fig. 5-29B must be used.

An audio signal of about ten volts is required for good limiting action. When a beat oscillator is used for c.w. reception the b.f.o. voltage should be small, so that incoming noise will not have a strong carrier to beat against and so produce large audio output.

Second-detector noise-limiting circuits that automatically adjust themselves to the receiver carrier level are shown in Fig. 5-30. In either circuit,  $V_1$  is the usual diode second detector,  $R_1R_2$  is the diode load resistor, and  $C_1$  is an r.f. by-pass. A negative voltage proportional to the carrier level is developed across  $C_2$ , and this voltage cannot change rapidly because  $R_3$  and  $C_2$  are both large. In the circuit at A, diode  $V_2$  acts as a conductor for the audio signal up to the point where its anode is negative with respect to the cathode. Noise peaks that exceed the maximum carrier-modulation level will drive the anode negative instantaneously, and during this time the diode does not conduct. The large time constant of  $C_2R_3$  prevents any rapid change of this reference voltage. In the circuit at B, the diode  $V_2$  is inactive until its cathode voltage exceeds its anode voltage. This condition will obtain under noise peaks and, when it does, the diode  $V_2$  short-circuits the signal and no voltage is passed on to the audio amplifier. Practical values for these two circuits will be found in the six- and eight-tube superheterodynes described later in this chapter. Diode rectifiers such as the 6H6 and 6AL5, or the 1N34 germanium crystal diode, can be used for these types of noise limiters. Neither circuit is useful for c.w. reception, but they are both quite effective for 'phone work.

### I.F. Noise Silencer

In the circuit shown in Fig. 5-31, noise pulses are made to decrease the gain of an i.f. stage momentarily and thus silence the receiver for the duration of the pulse. Any noise voltage in excess of the desired signal's maximum i.f. voltage is taken off at the grid of the i.f. amplifier, amplified by the noise-amplifier stage, and rectified by the full-wave diode noise rectifier. The noise circuits are tuned to the i.f. The rectified noise voltage is applied as a pulse of negative bias to the

No. 3 grid of the 6L7 i.f. amplifier, wholly or partially disabling this stage for the duration of the individual noise pulse, depending on the amplitude of the noise voltage. The noise-amplifier/rectifier circuit is biased by means of the "threshold control,"  $R_2$ , so that rectification will not start until the noise voltage exceeds the desired signal amplitude. With automatic volume control the a.v.c. voltage can be applied to the grid of the noise amplifier, to augment this threshold bias. In a typical instance, this system improved the signal-to-noise ratio some 30 db. (power ratio of 1000) with heavy ignition interference, raising the signal-to-noise ratio from -10 db. without the silencer to +20 db. with the silencer.

### ● SIGNAL-STRENGTH AND TUNING INDICATORS

A useful accessory to the receiver is an indicator that will show relative signal strength. Not only is it an aid in giving reports to transmitting stations, but it is helpful also in aligning the receiver circuits, in conjunction with a test oscillator or other steady signal.

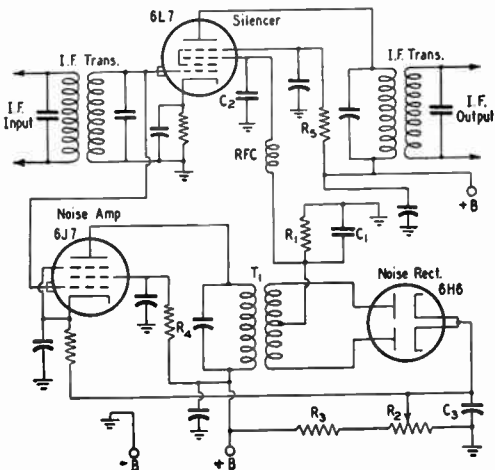


Fig. 5-31 — I.f. noise-silencing circuit. The plate supply should be 250 volts. Typical values for components are:  $C_1$  — 50-250  $\mu\text{fd}$ . (use smallest value possible without r.f. feed-back).

- $C_2$  — 47  $\mu\text{fd}$ .
- $C_3$  — 0.1  $\mu\text{fd}$ .
- $R_1$  — 0.1 megohm.
- $R_2$  — 5000-ohm variable.
- $R_3$  — 22,000 ohms.
- $R_4, R_5$  — 0.1 megohm.
- $T_1$  — Special i.f. transformer for noise rectifier.

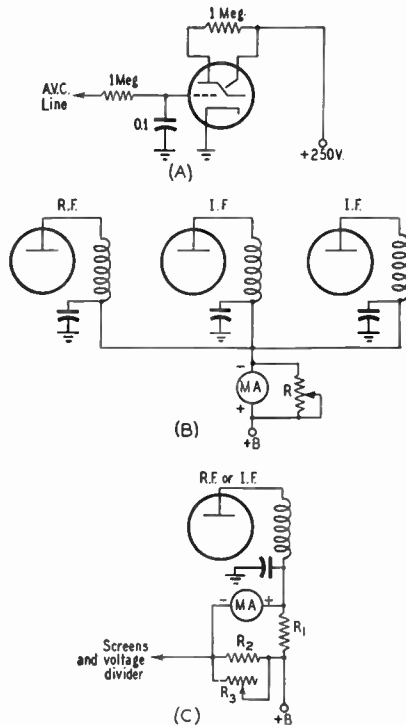


Fig. 5-32—Tuning-indicator or S-meter circuits for superhet receivers. A, electron-ray indicator; B, plate-current meter for tubes on a.v.c.; C, bridge circuit for a.v.c.-controlled tube. In B, resistor  $R$  should have a maximum resistance several times that of the milliammeter. In C, representative values for the components are:  $R_1$ , 270 ohms;  $R_2$ , 330 ohms;  $R_3$ , 1000-ohm variable.

Three types of indicators are shown in Fig. 5-32. That at A uses an electron-ray tube, several types of which are available. The grid of the triode section usually is connected to the a.v.c. line. The particular type of tube used depends upon the voltage available for its

grid; where the a.v.c. voltage is large, a remote cut-off type (6G5, 6N5 or 6AD6G) should be used in preference to the more sensitive sharp cut-off type (6E5).

In B, a milliammeter is connected in series with the d.c. plate lead to one or more r.f. and i.f. tubes, the grids of which are controlled by a.v.c. voltage. Since the plate current of such tubes varies with the strength of the incoming signal, the meter will indicate relative signal intensity and may be calibrated in S-points. The scale range of the meter should be chosen to fit the number of tubes in use; the maximum plate current of the average remote cut-off r.f. pentode is from 7 to 10 milliamperes. The shunt resistor,  $R$ , enables setting the plate current to the full-scale value ("zero adjustment"). With this system the ordinary meter reads downward from full scale with increasing signal strength, which is the reverse of normal pointer movement (clockwise with increasing reading). Special instruments in which the zero-current position of the pointer is on the right-hand side of the scale are used in commercial receivers.

The system at C uses a 0-1 milliammeter in a bridge circuit, arranged so that the meter reading and the signal strength increase together. The current through the branch containing  $R_1$  should be approximately equal to the current through that containing  $R_2$ . In some manufactured receivers this is brought about by draining the screen voltage-divider current and the current to the screens of three r.f. pentodes (r.f. and i.f. stages) through  $R_2$ , the sum of these currents being about equal to the maximum plate current of one a.v.c.-controlled tube. Typical values for this type of circuit are given. The sensitivity can be increased by increasing the resistance of  $R_1$ ,  $R_2$  and  $R_3$ . The initial setting is made with the manual gain control set near maximum, when  $R_3$  should be adjusted to make the meter read zero with no signal.

## A Six-Tube General-Coverage and Bandspread Superheterodyne

A superhet receiver of simple construction, having a wide frequency range for general coverage as well as full bandspread for amateur-band reception, is shown in Figs. 5-33 to 5-38. The circuit uses six tubes and gives continuous coverage from about 2.4 to 47 Mc. An additional range, 0.55 to 1.6 Mc., covers the broadcast band. The receiver is intended for a.c. operation and requires a filament supply delivering 6.3 volts at 1.65 amp., and a "B" supply of 200 to 250 volts at 70 ma.

### The Circuit

The circuit diagram is given in Fig. 5-34. A 6K8 is used as a combined oscillator-mixer followed by a 6SK7 i.f. amplifier. The inter-

mediate frequency is 456 kc. The oscillator is tuned 456 kc. higher than the signal on frequencies up to 27 Mc.; above 27 Mc. the oscillator is 456 kc. lower than the signal. Manual gain control is applied to the i.f. stage, and a.v.c. is applied to both the i.f. and mixer stages. One section of the 6H6 double diode is used as the second detector and the other section as a series-type noise limiter. One half of a 6SL7GT double triode is used as the b.f.o. tube and the other triode is used in the first audio stage. The b.f.o. is capacity-coupled to the detector by soldering one end of an insulated wire to the detector plate and wrapping several turns of the wire around the b.f.o. grid lead. This capacity is designated  $C_{C1}$  in the di-



Fig. 5-33 — A front view of the six-tube receiver. The general-coverage and the band-spread-tuning dials are to the left and right of the panel. The antenna trimmer condenser is centered below the main tuning dials. The i.f. gain control, noise-limiter switch, a.v.c.-b.f.o. switch, b.f.o. pitch control, head-phone jack, stand-by switch, and a.f. gain control are shown from left to right across the bottom of the panel. A suitable power supply for the receiver is mounted in the 'speaker cabinet shown at the right of the receiver.



agram. A small mica by-pass condenser,  $C_{21}$ , connected between the first-audio grid and ground, prevents the b.f.o. signal from leaking into the audio system. This will occur without the by-pass condenser because of the capacity coupling that exists inside the 6SL7GT. The condenser can be connected from grid to ground, as shown, or from plate to ground.

Both headphone and loudspeaker output are available, with the headphone output taken from the plate circuit of the triode audio stage at  $J_1$ , and the loudspeaker output taken from the plate of the 6V6GT audio-amplifier stage. The 'phone jack is wired in a manner that grounds the 6V6 input grid when the 'phones are plugged in.

A VR-105 regulator tube is used to stabilize the voltage applied to the plates of the high-frequency oscillator and b.f.o. tubes, and to the screen grid of the i.f. amplifier. Positive bias for the 6SK7 is obtained from a bleeder network connected to the regulated supply.

### Construction

The parts arrangement is shown in Figs. 5-35 and 5-36 and the components are identified in the captions accompanying the photographs. The chassis on which the parts are mounted measures  $2 \times 7 \times 11$  inches, and the cabinet that houses the finished receiver measures  $8 \times 8\frac{1}{4} \times 14\frac{1}{2}$  inches. A panel measuring  $8 \times 12$  inches is included as part of the cabinet, and the variable condensers are mounted on this panel. The sockets for the 6K8 and the r.f. coils are mounted on 1-inch-long metal pillars. Holes  $1\frac{1}{4}$  inches in diameter are cut in the chassis just below the three sockets and the *below-deck* leads are passed through these holes. Although the No. 12 wire leads between the oscillator band-set condenser may appear to be unduly long, it is of no consequence since the leads are associated with the oscillator circuit rather than the mixer circuit. The dials used with these two condensers (shown in the front view) are

Millen No. 10039. The bandspread condenser is a four-plate (two stator and two rotor) affair made by pulling out plates from the original. Inasmuch as bandspread is obtained by the parallel-condenser-and-coil method (this system allows adequate bandspread to be obtained without the bother of tapping the coils or using series condensers), it is necessary to adjust the  $L/C$  ratio of the oscillator circuit until the desired degree of bandspread is obtained. A four-plate condenser of the type recommended will give full bandspread when used with the coils listed in the coil chart. The 3.5-Mc. band is broken into two sections — 3.5 to 3.8 Mc. and 3.7 to 4.0 Mc. This division, necessary if full bandspread is to be obtained on the higher-frequency bands, offers no operating disadvantage and, as a matter of fact, is a decided advantage because it gives full bandspread to the c.w. and 'phone portions of the 80-meter band.

### COIL TABLE FOR THE SIX-TUBE SUPERHETERODYNE

Range	Turns			
	$L_1$	$L_2$	$L_3$	$L_4$
550-1600 kc. ....	12	150	12	67
2.4 to 6.45 Mc. (80 meters)	12	31	10	29
6.4 to 13.8 Mc. (40 meters)	10	17	7	12
13.8 to 27 Mc. (20 meters)	9	10	7	5
23.5 to 47 Mc. (10-11 meters)	3	3	$3\frac{1}{4}$	$1\frac{1}{2}$

The broadcast-band coils are close-wound with No. 30 d.s.c. on 4-prong forms having a diam. of  $1\frac{1}{2}$  inches and a winding length of  $2\frac{1}{2}$  inches.  $L_1$  is wound on a cardboard tube of  $\frac{3}{4}$ -inch diam., and is mounted inside the form.  $L_2$  has a winding length of  $2\frac{1}{4}$  inches, and  $L_4$  has a length of  $15/16$  inch. Coils for all other bands are wound on 1-inch diam. forms (Millen 45004) with No. 26 d.s.c. wire. The turns of  $L_2$  and  $L_4$ , with exception of  $L_4$  for 10 meters, are spaced to a length of 1 inch;  $L_4$  for 10 meters is close-wound. Antenna and tickler coils,  $L_1$  and  $L_3$ , are close-wound, spaced about  $\frac{1}{16}$  inch from the bottom of the main windings, except for 10 meters. The antenna coil for 10 meters is interwound with  $L_2$ , and the tickler coil is directly adjacent to  $L_4$ .

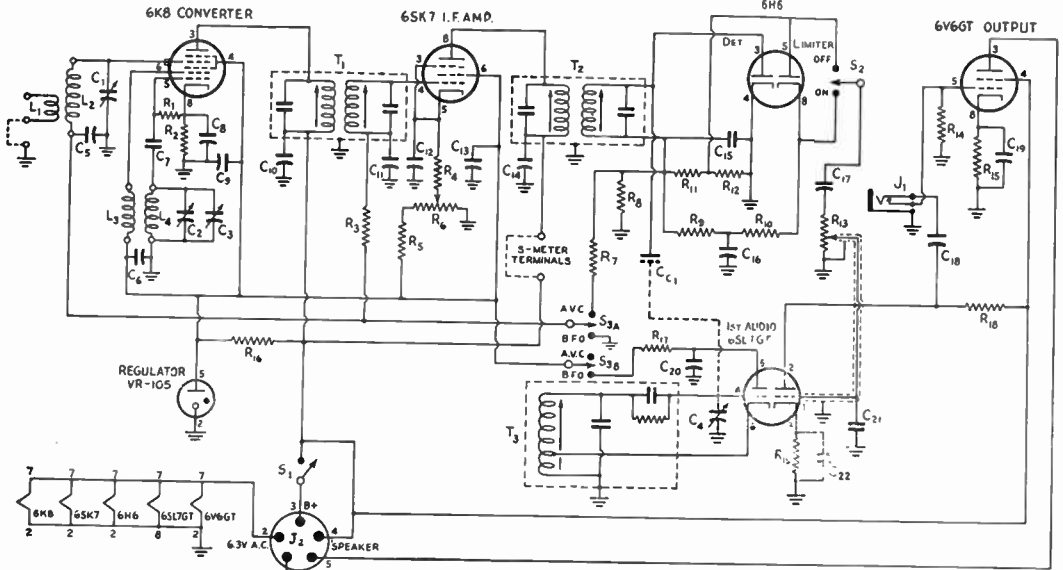


Fig. 5-34 — Circuit diagram of the six-tube receiver.

- C<sub>1</sub>, C<sub>2</sub> — 140- $\mu$ fd. midjet variable (Millen 22140).
- C<sub>3</sub> — 25- $\mu$ fd. midjet variable (Millen 20025).
- C<sub>4</sub> — 35- $\mu$ fd. midjet variable (Millen 20035).
- C<sub>5</sub>, C<sub>6</sub>, C<sub>8</sub>, C<sub>9</sub>, C<sub>10</sub>, C<sub>11</sub>, C<sub>12</sub>, C<sub>13</sub>, C<sub>14</sub>, C<sub>16</sub>, C<sub>18</sub>, C<sub>20</sub> — 0.01- $\mu$ fd. paper, 400 volts.
- C<sub>7</sub>, C<sub>15</sub>, C<sub>21</sub> — 100- $\mu$ fd. mica.
- C<sub>17</sub> — 0.05- $\mu$ fd. paper, 400 volts.
- C<sub>19</sub>, C<sub>22</sub> — 10- $\mu$ fd. 25-volt electrolytic.
- C<sub>21</sub> — See text.
- R<sub>1</sub>, R<sub>5</sub>, R<sub>17</sub> — 47,000 ohms.
- R<sub>2</sub> — 220 ohms.
- R<sub>3</sub>, R<sub>18</sub> — 0.1 megohm.
- R<sub>4</sub> — 180 ohms.
- R<sub>6</sub> — 2000-ohm wire-wound potentiometer.
- R<sub>7</sub>, R<sub>8</sub>, R<sub>9</sub> — 1.0 megohm.
- R<sub>10</sub> — 0.82 megohm.
- R<sub>11</sub>, R<sub>12</sub> — 0.27 megohm.

- R<sub>13</sub> — 1-megohm carbon potentiometer.
  - R<sub>14</sub> — 0.22 megohm.
  - R<sub>15</sub> — 220 ohms, 1 watt.
  - R<sub>16</sub> — 7500 ohms, 10 watts.
  - R<sub>19</sub> — 2200 ohms.
- All resistors  $\frac{1}{2}$  watt unless otherwise noted.
- L<sub>1</sub> through L<sub>4</sub> — See coil table.
  - J<sub>1</sub> — Closed-circuit jack.
  - J<sub>2</sub> — 5-prong chassis-mounting male plug.
  - S<sub>1</sub> — S.p.s.t. toggle switch.
  - S<sub>2</sub> — S.p.d.t. toggle switch.
  - S<sub>3A-B</sub> — D.p.d.t. toggle switch.
  - T<sub>1</sub> — 456-ke. interstage i.f. transformer, permeability-tuned (Millen 64455).
  - T<sub>2</sub> — 456-ke. diode transformer (Millen 64453).
  - T<sub>3</sub> — 456-ke. b.f.o. assembly (Millen 65456).

The mixer section was designed with short leads between the tuning condenser and r.f. coil. The tuning condenser, C<sub>1</sub>, is mounted on the panel well down toward the coil socket. An "L"-shaped metal shield is mounted on the coil socket as shown in Fig. 5-35. The shield is

2½ inches wide, has a 2¼-inch base, and the vertical portion is 3¼ inches high. This shield was inserted between the mixer coil and the diode coupling transformer because of magnetic coupling that occurred between the two circuits when the receiver was operated at the lower frequencies. A 6-inch length of 150-ohm Twin-Lead is used between the antenna input terminals and the antenna winding, L<sub>1</sub>. The by-pass con-


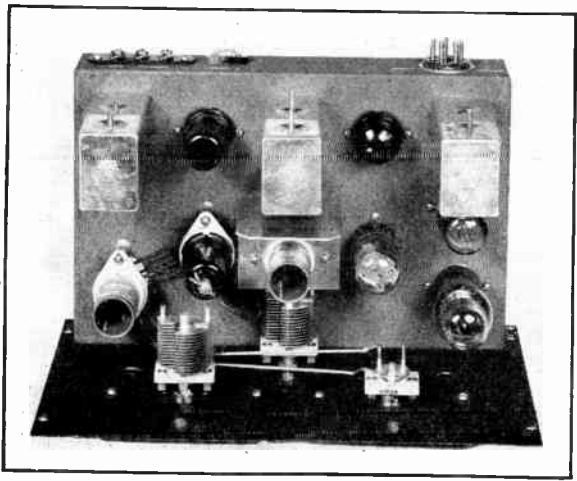


Fig. 5-35 — A top view of the six-tube superheterodyne. Coupling transformers T<sub>1</sub> and T<sub>2</sub>, the i.f. amplifier and double-diode tubes, and the b.f.o. assembly are in line across the rear of the chassis. The mixer and oscillator coils are to the right and left of the 6K8 converter tube. The sockets for the tube and the coils are mounted above the chassis. An aluminum shield is mounted on the mixer-coil socket and provides shielding between this coil and the diode-coupling transformer (see text). The 6SL7GT is to the right of the mixer coil, and the output and regulator tubes are at the right front of the chassis.

*Fig. 5-36* — This bottom view of the six-tube receiver shows how the by-pass and coupling condensers are closely grouped around the tube sockets. The chassis and panel are fastened together by the switches and controls mounted along the front wall of the chassis. The antenna terminals, S-meter tip-jacks, and the power-input connector,  $J_2$ , are at the rear.

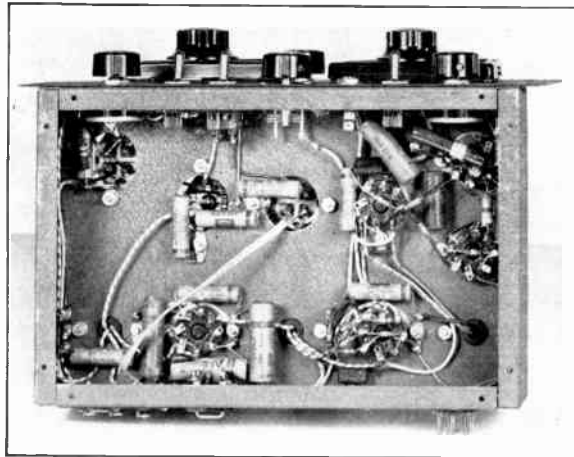

condensers for the r.f. section are mounted below the chassis and are connected with the shortest possible leads.

The wiring of the components associated with the rest of the receiver circuit does not call for any special treatment with the exception of the lead to the grid of the first audio amplifier — this lead is made with shielded wire. The by-pass condensers are kept as close as possible to the tubes and circuit points that they by-pass, and spare socket prongs are used as tie-points wherever possible. Only three independent tie-point strips are required: one is at the top left-hand corner (Fig. 5-36) for the connection between the 6SK7 cathode resistor and the lead to the tube, one at the lower left-hand corner for mounting of the 6SK7 grid-leak resistor, and one to the left of the double diode for mounting of the a.v.c. filter resistor,  $R_7$ . The pin-jacks, shown at the rear of the chassis, are shorted out, or eliminated entirely, if the use of an external S-meter unit is not contemplated.

### Tuning


The first step in putting the receiver into operation is to align the i.f. amplifier. This should preferably be done with the aid of a test oscillator, but if one is not available the circuits may be aligned on hiss or noise. The beat oscillator can also be used to furnish a signal for alignment, by coupling its output temporarily to the grid of the 6K8. A d.c. voltmeter can be used to measure the voltage developed across  $R_{11}R_{12}$  during alignment.

When the i.f. is aligned, the mixer grid and oscillator coils for a band can be plugged in.  $C_3$  should be set near maximum capacity and  $C_2$  tuned from maximum capacity until a signal is heard. The capacity of  $C_2$  should be further reduced until the same signal is heard a second time, this setting being the one that places the oscillator frequency on the high side of the incoming signal. The high-capacity setting of  $C_2$  is used when the receiver is tuned to the 10- or 11-meter bands. The mixer tuning condenser,  $C_1$ , is adjusted for maximum signal strength after the oscillator adjustment has been completed. With  $C_2$  set at the low-frequency end of an amateur band, further tuning should be done with  $C_3$ , and the band should be found to cover about ninety per cent of the dial.  $C_3$  can of course be used for bandspread

tuning outside as well as inside the amateur bands.

The bandspread condenser need not be tuned for coverage of the broadcast band. Of course, it can be used for vernier tuning in the event that critical tuning is required to separate stations operating on nearly the same frequency. Ordinarily,  $C_3$  can be set at minimum capacity while the tuning of stations is done with  $C_2$ .

It is convenient to calibrate the receiver, using the scales provided for the purpose. Calibration points may be taken from incoming signals whose frequencies are known, from a calibrated test oscillator, or from the harmonics of a 100-ke. oscillator, as described in

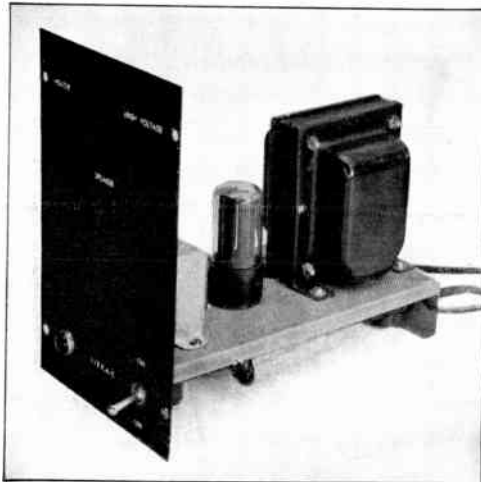

*Fig. 5-37* — A combination speaker and power supply unit for the 6-tube superheterodyne receiver. The power transformer, filter choke and rectifier tube are mounted on an open-ended chassis measuring  $1\frac{1}{2} \times 4 \times 8$  inches. The chassis and panel are fastened together by the toggle switch and the pilot-light assembly. The filter condensers are mounted below the chassis. A five-wire cable, at the rear of the chassis, connects the power supply and the speaker to the receiver. The speaker can be mounted on either the right or left side of the cabinet shown in Fig. 5-33.

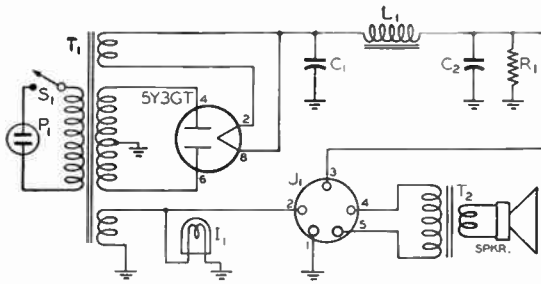


Fig. 5-38 — Power-supply circuit diagram.  
 C<sub>1</sub>, C<sub>2</sub> — 20- $\mu$ fd. 450-volt paper electrolytic.  
 R<sub>1</sub> — 47,000 ohms, 2 watts.  
 L<sub>1</sub> — 8-henry 75-ma. filter choke (Stancor C-1355).  
 I<sub>1</sub> — 6.3-volt pilot-lamp-and-socket assembly.  
 J<sub>1</sub> — 5-prong socket on power cable.  
 P<sub>1</sub> — 115-volt a.c. line plug.  
 S<sub>1</sub> — S.p.s.t. toggle switch.  
 SPKR — Six-inch permanent magnet speaker.  
 T<sub>1</sub> — Power transformer, 350 volts each side of center-tap, 70-ma. rating. Filament windings: 5 v. 3 amp.; 6.3 v. 3 amp. (Stancor P-4078).

Chapter Sixteen. The mixer need not be calibrated, since tuning of the mixer circuit has little effect on the oscillator frequency. However, a mixer calibration can be made to insure that the circuit is tuned to the desired signal rather than to an image.

**Power Supply**

A power supply suitable for the 6-tube receiver is shown in Figs. 5-37 and 5-38. The arrangement of components can be determined from Fig. 5-37. An output transformer and speaker are both mounted in the 7½ × 8 × 8-inch cabinet that houses the power supply. This particular supply need not be used with the receiver if another supply of suitable design is available. It is only necessary that the supply deliver a well-filtered output of 250 volts at 70 ma.

**A Signal-Strength Indicator (S-Meter)**

If your receiver has no built-in S-meter and you would like one for comparing signal strengths (and for help in aligning your receiver), the unit shown in Figs. 5-39 and 5-41 can be used. The wiring diagram, Fig. 5-40, is an adaptation of Fig. 5-32C, and uses a 0-1 milliammeter as the indicator. A variable shunt, R<sub>1</sub>, allows the meter sensitivity to be regulated to suit the particular receiver, and R<sub>4</sub> is for setting the meter to zero with no signal. The meter can be connected in the plate

circuit of any r.f. or i.f. amplifier controlled by the a.v.c.

The construction of the unit is apparent from the photographs and is not at all critical.



Fig. 5-39 — Front view of the signal-strength indicator. The 0-1 milliammeter is mounted in a metal meter case. The zero-adjustment potentiometer, R<sub>4</sub>, is mounted below the top of the cabinet by means of a "U"-shaped bracket; the potentiometer shaft is slotted so that it can be adjusted with a screwdriver. A new face, calibrated in S-units, can be pasted to the 0-1 ma. scale, or a calibration chart can be attached to the cabinet.

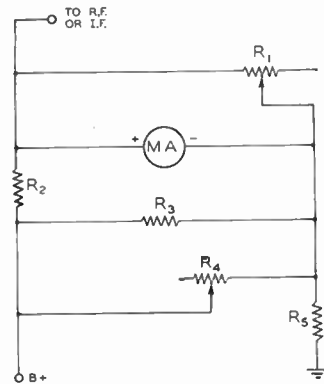


Fig. 5-40 — Wiring diagram of the signal-strength indicator.

- R<sub>1</sub> — 100-ohm wire-wound potentiometer.
- R<sub>2</sub> — 220 ohms, ½ watt.
- R<sub>3</sub> — 680 ohms, ½ watt.
- R<sub>4</sub> — 1000-ohm wire-wound potentiometer.
- R<sub>5</sub> — 4700 ohms, 1 watt.
- MA — 0-1 ma. d.c. meter.

If possible and desirable, the meter and circuit can be built into the receiver instead of being made a separate unit.

**S-Meter Calibration**

It is customary to calibrate in terms of S-units up to about midscale, and then in "decibels above S9" over the upper half of the scale. Although there are no standards, current practice is to use about 6-db. steps in the S-scale, and a 100-microvolt signal for "S9."

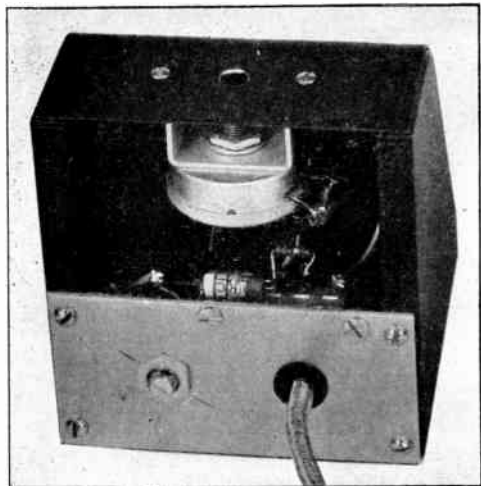


Fig. 5-41 — This rear view of the S-meter shows the meter shunt,  $R_1$ , and a tie-point strip mounted on a metal strip attached to the rear side of the meter cabinet. Resistors  $R_2$ ,  $R_3$  and  $R_5$  are mounted on the tie-point strip. A three-wire cable, running out of the case through a rubber grommet, connects the meter to the receiver.

Such a calibration requires an accurate r.f. signal generator, and relatively few amateurs have access to laboratory equipment of this type. Also, the scale will be accurate only on the radio frequency at which the calibration is made. On different bands — or even in different parts of the same band — the r.f. gain of the receiver will change and the calibration will not hold.

An S-meter is principally useful for making comparisons between signals on or near the same frequency. For this purpose it is entirely satisfactory to choose arbitrarily a signal that seems to you to be about the right strength to represent "S9," adjust the meter sensitivity to give a suitable reading on that signal, and then divide off the scale into equal intervals from zero to 9.

Alternatively, points can be taken by comparing with another receiver that does have a calibrated S-meter. The two receivers may be connected to the same antenna so that simultaneous measurements can be made on incoming signals, provided their antenna input impedances are not widely different. Local signals should be used to avoid fading effects.

## Improving Receiver Selectivity

### ● INTERMEDIATE-FREQUENCY AMPLIFIERS

As mentioned earlier in this chapter, one of the big advantages of the superheterodyne receiver is the improved selectivity that is possible. This selectivity is obtained in the i.f. amplifier, where the lower frequency allows more selectivity per stage than at the higher signal frequency. For 'phone reception, the limit to useful selectivity in the i.f. amplifier is the point where so many of the sidebands are cut that intelligibility is lost, although it is possible to remove completely one full set of sidebands without impairing the quality at all. Maximum receiver selectivity in 'phone reception requires excellent stability in both transmitter and receiver, so that they will both remain "in tune" during the transmission. The limit to useful selectivity in code work is around 50 or 100 cycles for hand-key speeds, but it is difficult to use this much selectivity because it requires remarkable stability in both transmitter and receiver, and to tune in a signal becomes a major problem.

#### Single-Signal Effect

In heterodyne c.w. reception with a superheterodyne receiver, the beat oscillator is set to give a suitable audio-frequency beat-note when the incoming signal is converted to the intermediate frequency. For example, the beat oscillator may be set to 456 kc. (the i.f. being 455 kc.) to give a 1000-cycle beat-note. Now,

if an interfering signal appears at 457 kc., or if the receiver is tuned to heterodyne the incoming signal to 457 kc., it will also be heterodyned by the beat oscillator to produce a 1000-cycle beat. Hence every signal can be tuned in at two places that will give a 1000-cycle beat (or any other low audio frequency). This audio-frequency image effect can be reduced if the i.f. selectivity is such that the incoming signal, when heterodyned to 457 kc., is greatly attenuated.

When this is done, tuning through a given signal will show a strong response at the desired beat-note on one side of zero beat only, instead of the two beat-notes on either side of zero beat characteristic of less-selective reception, hence the name: **single-signal reception**.

The necessary selectivity is difficult to obtain with nonregenerative amplifiers using ordinary tuned circuits unless a very low i.f. or a large number of circuits is used. In practice it is secured either by regenerative amplification or by a crystal filter.

#### Regeneration

Regeneration can be used to give a pronounced single-signal effect, particularly when the i.f. is 455 kc. or lower. The resonance curve of an i.f. stage at critical regeneration (just below the oscillating point) is extremely sharp, a bandwidth of 1 kc. at 10 times down and 5 kc. at 100 times down being obtainable in one stage. The audio-frequency image of a given signal thus can be reduced by a factor of

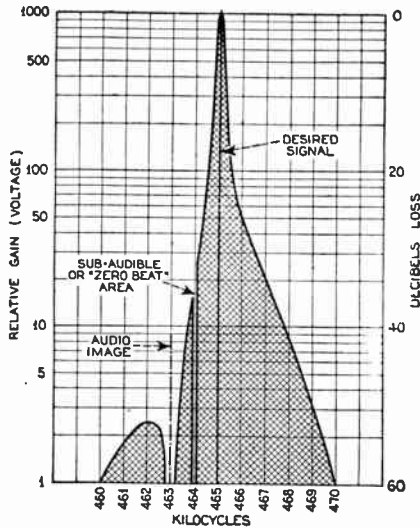


Fig. 5-42 — Graphical representation of single-signal selectivity. The shaded area indicates the over-all bandwidth, or region in which response is obtainable.

nearly 100 for a 1000-cycle beat-note (image 2000 cycles from resonance).

Regeneration is easily introduced into an i.f. amplifier by providing a small amount of capacity coupling between grid and plate. Bringing a short length of wire, connected to the grid, into the vicinity of the plate lead usually will suffice. The feed-back may be controlled by the regular cathode-resistor gain control. When the i.f. is regenerative, it is preferable to operate the tube at reduced gain (high bias) and depend on regeneration to bring up the signal strength. This prevents overloading and increases selectivity.

The higher selectivity with regeneration reduces the over-all response to noise generated in the earlier stages of the receiver, just as does high selectivity produced by other means, and therefore improves the signal-to-noise ratio. The disadvantage is that the regenerative gain varies with signal strength, being less on strong signals, and the receiver selectivity varies accordingly.

### Crystal Filters

The most satisfactory method of obtaining high selectivity is by the use of a piezoelectric quartz crystal as a selective filter in the i.f. amplifier. Compared to a good tuned circuit, the  $Q$  of such a crystal is extremely high. The dimensions of the crystal are made such that it is resonant at the desired intermediate frequency. It is then used as a selective coupler between i.f. stages.

Fig. 5-42 gives a typical crystal-filter resonance curve. For single-signal reception, the audio-frequency image can be reduced by a factor of 1000 or more. Besides practically eliminating the a.f. image, the high selectivity of the crystal filter provides great discrimina-

tion against signals very close to the desired signal in frequency, and, by reducing the bandwidth, reduces the response of the receiver to noise both from sources external to the receiver and in the radio-frequency stages of the receiver itself.

### Crystal-Filter Circuits; Phasing

Several crystal-filter circuits are shown in Fig. 5-43. Those at A and B are practically identical in performance, although differing in details. The crystal is connected in a bridge circuit, with the secondary side of  $T_1$ , the input transformer, balanced to ground either through a pair of condensers,  $C-C$  (A), or by a center-tap on the secondary,  $L_2$  (B). The bridge is completed by the crystal and the phasing condenser,  $C_2$ , which has a maximum capacity somewhat higher than the capacity of the crystal in its holder. When  $C_2$  is set to balance the crystal-holder capacity, the resonance curve of the crystal circuit is practically symmetrical; the crystal acts as a series-resonant circuit of its high  $Q$  and thus allows signals of the desired frequency to be fed through  $C_3$  to  $L_3L_4$ , the output transformer. Without  $C_2$ , the holder capacity (with the crystal acting as a dielectric) would pass signals of undesired frequencies.

The phasing control has an additional function besides neutralization of the crystal-holder capacity. The holder capacity becomes a part of the crystal circuit and causes it to act as a parallel-tuned resonant circuit at a frequency slightly higher than its series-resonant frequency. Signals at the parallel-resonant frequency thus are prevented from reaching the output circuit. The phasing control, by varying the effect of the holder capacity, permits shifting the parallel-resonant frequency over a considerable range, providing adjustable rejection of interfering signals. The effect of rejection is illustrated in Fig. 5-42, where the audio image is reduced, by proper setting of the phasing control, far below the value that would be expected if the resonance curve were symmetrical.

### Variable Selectivity

In circuits such as A and B, Fig 5-43, variable selectivity is obtained by adjustment of the variable input impedance, which is effectively in series with the crystal resonator. This is accomplished by varying  $C_1$  (the selectivity control), which tunes the balanced secondary circuit of  $T_1$ . When the secondary is tuned to i.f. resonance the parallel impedance of the  $L_2C_1$  combination is maximum and is purely resistive. Since the secondary circuit is center-tapped, approximately one-fourth of this resistive impedance is in series with the crystal through  $C_3$  and  $L_4$ . This lowers the  $Q$  of the crystal circuit and makes its over-all selectivity minimum. At the same time, the voltage applied to the crystal circuit is maximum.

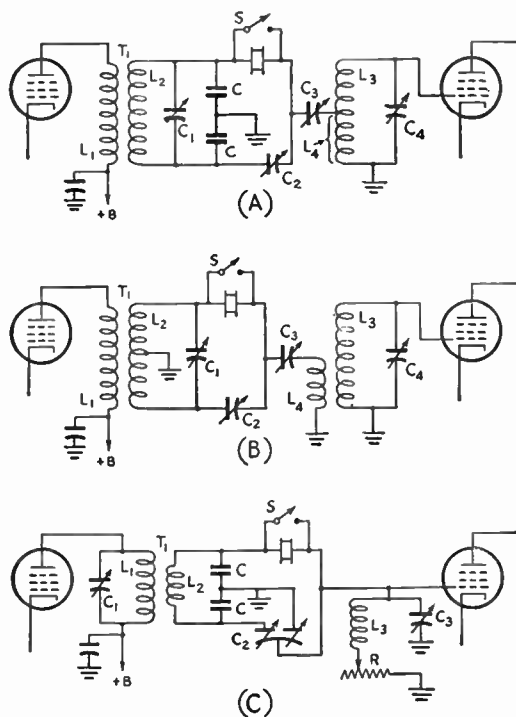


Fig. 5-43 — Crystal-filter circuits of three types. All give variable bandwidth, with C having the greatest range of selectivity. Their operation is discussed in the text. Suitable circuit values are as follows: Circuit A.  $T_1$ , special i.f. input transformer with high-inductance primary,  $L_1$ , closely coupled to tuned secondary,  $L_2$ ;  $C_1$ , 50- $\mu\text{mfd.}$  variable;  $C_2$ , each 100- $\mu\text{mfd.}$  fixed (mica);  $C_3$ , 10- to 15- $\mu\text{mfd.}$  (max.) variable;  $C_4$ , 50- $\mu\text{mfd.}$  trimmer;  $L_3C_3$ , i.f. tuned circuit, with  $L_3$  tapped to match crystal-circuit impedance. In circuit B,  $T_1$  is the same as in circuit A except that the secondary is center-tapped;  $C_1$  is 100- $\mu\text{mfd.}$  variable;  $C_2$ ,  $C_3$  and  $C_4$ , same as for circuit A;  $L_2L_3$  is a transformer with primary,  $L_4$ , corresponding to tap on  $L_3$  in A. In circuit C,  $T_1$  is a special i.f. input transformer with tuned primary and low-impedance secondary;  $C_1$ , each 100- $\mu\text{mfd.}$  fixed (mica);  $C_2$ , opposed stator phasing condenser, approximately 8- $\mu\text{mfd.}$  maximum capacity each side;  $L_3C_3$ , high-Q i.f. tuned circuit;  $R$ , 0 to 3000 ohms (selectivity control).

## RADIO-FREQUENCY AMPLIFIERS

While selectivity to reduce audio-frequency images can be built into the i.f. amplifier, discrimination against radio-frequency images can only be obtained in circuits ahead of the first detector. These tuned circuits and their associated vacuum tubes are called radio-frequency amplifiers. For top performance of a communications receiver on frequencies above 7 Mc., it is mandatory that it have one or two stages of r.f. amplification, for image rejection and improved sensitivity. (The improvement in sensitivity that can be obtained will be discussed later.)

Receivers with an i.f. of 455 kc. can be expected to have some r.f. image response at a signal frequency of 14 Mc. and higher if only one stage of r.f. amplification is used. (Regeneration in the r.f. amplifier will reduce image

response, but regeneration is often a tricky thing to control.) With two stages of r.f. amplification and an i.f. of 455 kc., no images should be apparent at 14 Mc., but they will show up on 28 Mc. and higher. Three stages or more of r.f. amplification, with an i.f. of 455 kc., will reduce the images at 28 Mc., but it really takes four or more stages to do a good job. The better solution at 28 Mc. is to use a "triple-detection" superheterodyne, with one stage of r.f. amplification and a first i.f. of 1600 kc. or higher. A regular receiver with an i.f. of 455 kc. can be converted to a triple-detection superhet by connecting a "converter" (to be described later) ahead of the receiver.

For best selectivity, r.f. amplifiers should use high-Q circuits and tubes with high input and output resistance. Variable- $\mu$  pentodes are practically always used, although triodes (neutralized or otherwise connected so that they won't oscillate) are often used on the higher frequencies because they introduce less noise. Pentodes are better where maximum image rejection is desired, because they have less loading effect on the circuits.

## CROSS-MODULATION

Since a one- or two-stage r.f. amplifier will have a passband measured in hundreds of kc. at 14 Mc. or higher, strong signals will be amplified through the r.f. amplifier even though it is not tuned exactly to them. If these signals are strong enough, their amplified magnitude may be measurable in volts after passing through several r.f. stages. If this undesired signal is strong enough after amplification in the r.f. stages to shift the operating point of a tube (by driving the grid into the positive region), the undesired signal will modulate the desired signal. This effect is called cross-modulation, and is often encountered in receivers with several r.f. stages that are working at high gain. It is readily detectable as a superimposed modulation on the signal being listened to, and often the effect is that a signal can be tuned in at several points. It can be reduced or eliminated by greater selectivity in the antenna and r.f. stages (difficult to obtain), the use of variable- $\mu$  tubes in the r.f. amplifier, reduced gain in the r.f. amplifier, or reduced antenna input to the receiver.

### Gain Control

To avoid cross-modulation and other overload effects in the first detector and r.f. stages, the gain of the r.f. stages is usually made adjustable. This is accomplished by using variable- $\mu$  tubes and varying the d.c. grid bias, either in the grid or cathode circuit. If the gain control is automatic, as in the case of a.v.c., the bias is controlled in the grid circuit. Manual control of r.f. gain is generally done in the cathode circuit. A typical r.f. amplifier

stage with the two types of gain control is shown in Fig. 5-44.

**Tracking**

In a simple receiver with no r.f. stage, it is no inconvenience to adjust the high-frequency oscillator and the mixer circuit independently, because the mixer tuning is broad and requires little attention over an amateur band. However, when r.f. stages are added ahead of the mixer, the selectivity of the r.f. stages and mixer makes it awkward to use a two-control receiver over an entire amateur band, even though the mixer and r.f. stages are ganged and require only one control. Hence most receivers with one or more r.f. stages gang all of the tuning controls to give a single-tuning-control receiver. Obviously there must exist a constant difference in frequency (the i.f.) between the oscillator and the mixer/r.f. circuits, and when this condition is achieved the circuits are said to track.

Tracking methods for covering a wide frequency range, suitable for general-coverage receivers, are shown in Fig. 5-45. The tracking capacity,  $C_5$ , commonly consists of two condensers in parallel, a fixed one of somewhat less capacity than the value needed and a smaller variable in parallel to allow for adjustment to the exact proper value. In practice, the trimmer,  $C_4$ , is first set for the high-frequency end of the tuning range, and then the tracking condenser is set for the low-frequency end. The tracking capacity becomes larger as the

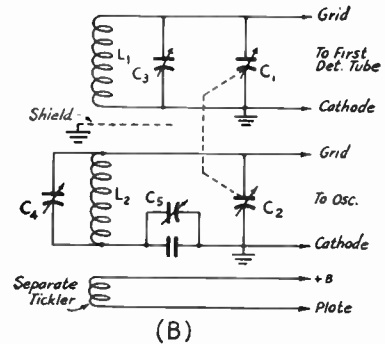
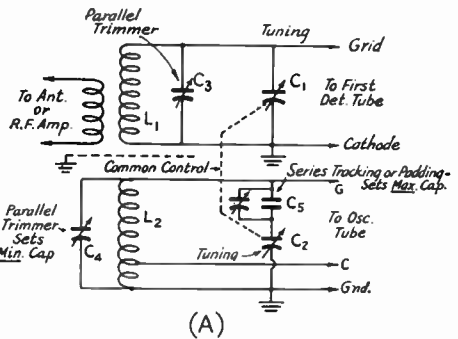


Fig. 5-45 — Converter-circuit tracking methods. Following are approximate circuit values for 450- to 465-kc. i.f.s, with tuning ranges of approximately 2.15-to-1 and  $C_2$  having 140- $\mu$ fd. maximum, and the total minimum capacitance, including  $C_3$  or  $C_4$ , being 30 to 35  $\mu$ fd.

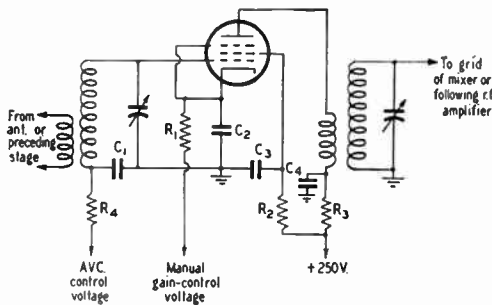


Fig. 5-11 — Typical radio-frequency amplifier circuit for a superheterodyne receiver. Representative values for components are as follows:

- $C_1, C_2, C_3, C_4$  — 0.01  $\mu$ fd. below 15 Mc., 0.001  $\mu$ fd. at 30 Mc.
- $R_1, R_2$  — See Table 5-11.
- $R_3$  — 1800 ohms.
- $R_4$  — 0.22 megohm.

percentage difference between the oscillator and signal frequencies becomes smaller (that is, as the signal frequency becomes higher). Typical circuit values are given in the tables under Fig. 5-45. The coils can be calculated quite closely by using the ARRL Lightning Calculator, but they will have to be trimmed in the circuit for best tracking.

In amateur-band receivers, tracking is simplified by choosing a bandspread circuit that gives practically straight-line-frequency tuning

Tuning Range	$L_1$	$L_2$	$C_5$
1.7-4 Mc.	50 $\mu$ h.	40 $\mu$ h.	0.0013 $\mu$ fd.
3.7-7.5 Mc.	14 $\mu$ h.	12.2 $\mu$ h.	0.0022 $\mu$ fd.
7-15 Mc.	3.5 $\mu$ h.	3 $\mu$ h.	0.0045 $\mu$ fd.
14-30 Mc.	0.8 $\mu$ h.	0.78 $\mu$ h.	None used

Approximate values for 450- to 465-kc. i.f.s with a 2.5-to-1 tuning range,  $C_1$  and  $C_2$  being 350- $\mu$ fd. maximum, minimum including  $C_3$  and  $C_4$  being 40 to 50  $\mu$ fd.

Tuning Range	$L_1$	$L_3$	$C_5$
0.5-1.5 Mc.	240 $\mu$ h.	130 $\mu$ h.	425 $\mu$ fd.
1.5-4 Mc.	32 $\mu$ h.	25 $\mu$ h.	0.00115 $\mu$ fd.
4-10 Mc.	4.5 $\mu$ h.	4 $\mu$ h.	0.0028 $\mu$ fd.
10-25 Mc.	0.8 $\mu$ h.	0.75 $\mu$ h.	None used

(equal frequency change for each dial division), and then adjusting the oscillator and mixer tuned circuits so that both cover the same total number of kilocycles. For example, if the i.f. is 455 kc. and the mixer circuit tunes from 7000 to 7300 kc. between two given points on the dial, then the oscillator must tune from 7455 to 7755 kc. between the same two dial readings. With the bandspread arrangement of Fig. 5-12C, the tuning will be practically straight-line-frequency if the capacity actually in use at  $C_2$  is not too small; the same is true of 5-12A if  $C_1$  is small compared to  $C_2$ .



## An Amateur-Band Eight-Tube Superheterodyne

An advanced type of amateur receiver incorporating one r.f. amplifier stage, variable i.f. selectivity and audio noise limiting is shown in Figs. 5-46, 5-48 and 5-49. As can be seen from the circuit in Fig. 5-47, a 6SG7 pentode is used for the tuned r.f. stage ahead of the 6K8 converter. An antenna compensator,  $C_4$ , controlled from the panel, allows one to trim up the r.f. stage when using different antennas that might modify the tracking. The cathode bias resistor of the r.f. stage is made as low as possible consistent with the tube ratings, to keep the gain and hence the signal-to-noise ratio of the stage high. The oscillator portion of the 6K8 mixer is tuned to the high-frequency side of the signal except on the 28-Mc. band, the usual custom nowadays in communications receivers. The oscillator tuning condenser,  $C_{17}$ , is of higher capacity than the r.f. and mixer tuning condensers, in the interest of better oscillator stability.

The i.f. amplifier is tuned to 455 kc., and the first stage is made regenerative by soldering a short length of wire to the plate terminal of the socket and running it near the grid terminal, as indicated by  $C_{C1}$  in the diagram. Regeneration is controlled by reducing the gain of the tube, and  $R_{12}$ , a variable cathode-bias control, serves this function. The second i.f. stage uses a 6K7, selected because high gain is not necessary at this point.

Manual gain-control voltage is applied to the r.f. and second i.f. stages. It is not applied to the mixer because it might pull the oscillator frequency, and it is not tied in with the first i.f. amplifier because it would interlock with the regeneration control used for controlling the selectivity. However, the a.v.c. voltage is applied to the r.f. and both i.f. stages, with the result that the selectivity of the regenerative


stage decreases with loud signals and gives a measure of automatic selectivity control. Using a negative-voltage power supply for the manual gain control is more expensive than the familiar cathode control, but it allows a wide range of control with less dissipation in the components. The a.v.c. is of the delayed type, the a.v.c. diode being biased about  $1\frac{1}{2}$  volts by the cathode resistor of the diode-triode detector-audio stage.

The second-detector-and-first-audio is the usual diode-triode combination and uses a 6SQ7. A 1N34 crystal diode is used as a noise limiter, and is left in the circuit all of the time. As is common with this type of circuit, it has little or no effect when the b.f.o. is on, but it is of considerable help to 'phone reception on the bands where automobile ignition is a factor. The constructor can satisfy himself on its operation when first building the receiver and working on it out of the case. By leaving one end of the 1N34 floating and touching it to the proper point in the circuit, a marked drop in ignition noise will be noted.

The b.f.o. is capacity-coupled to the detector by soldering one end of an insulated wire to the a.v.c. diode plate and wrapping several turns of the wire around the b.f.o. grid lead. This capacity is designated  $C_{C2}$  in the diagram. The wire was connected to the a.v.c. diode plate lead for wiring convenience — the a.v.c. coupling condenser,  $C_{32}$ , passing the b.f.o. voltage without introducing appreciable attenuation.

Headphone output is obtained from the plate circuit of the 6SQ7 at  $J_1$ , and loudspeaker output is available from the 6F6 audio-amplifier stage. High-impedance or crystal headphones are recommended for maximum headphone output.

Fig. 5-46 — An amateur-band eight-tube receiver. The knobs on the left control audio volume (upper) and b.f.o. pitch, and the two on the right handle r.f. and i.f. gain (upper) and i.f. regeneration. The knob to the left of the large tuning knob is fastened to the MAN.-A.V.C.-B.F.O. switch, and the one on the right is for the antenna trimmer. The toggle switch under the dial throws high negative bias on the r.f. stage during transmission periods.

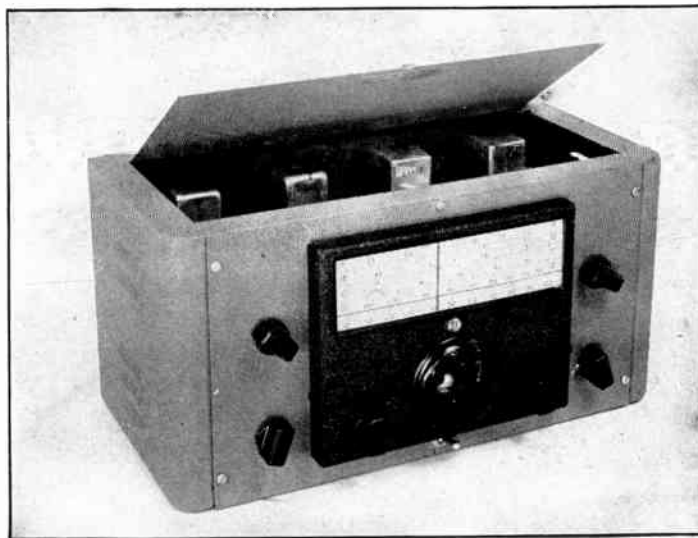

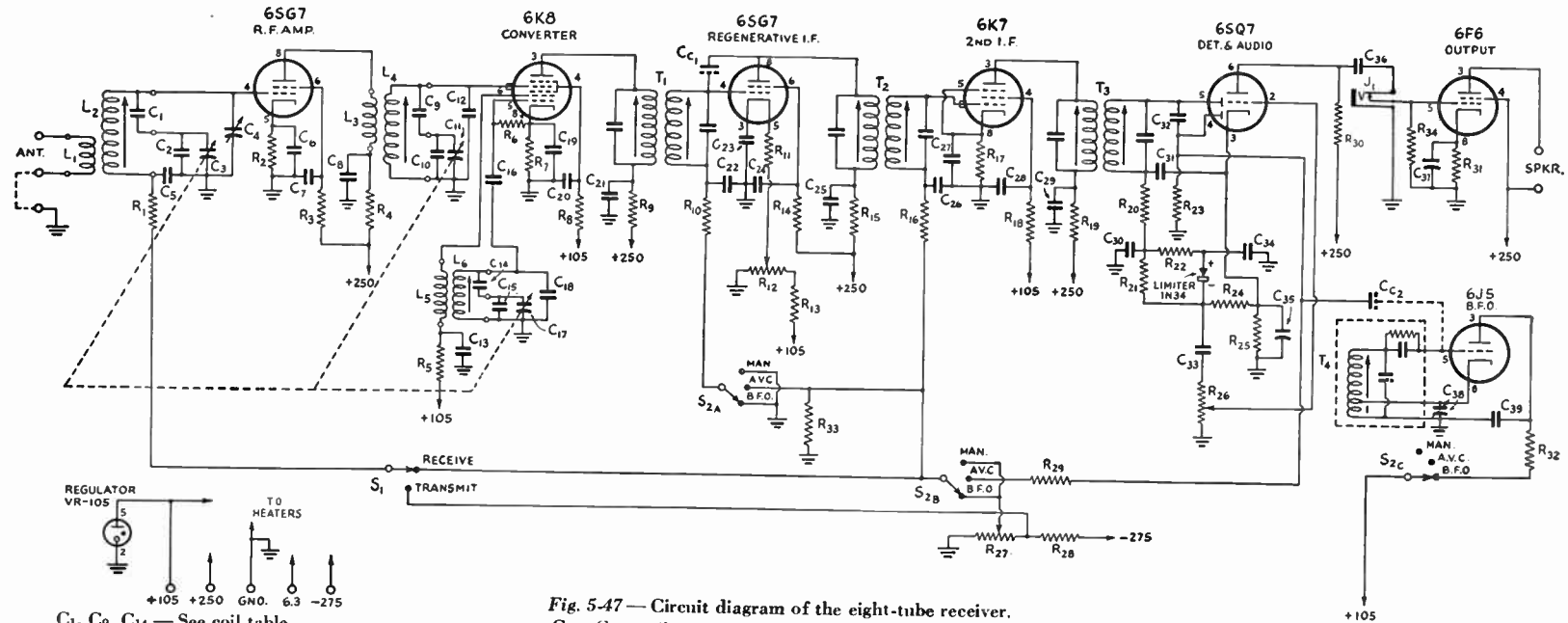


Fig. 5-47—Circuit diagram of the eight-tube receiver.

- C<sub>1</sub>, C<sub>9</sub>, C<sub>14</sub>** — See coil table.  
**C<sub>2</sub>, C<sub>10</sub>, C<sub>12</sub>, C<sub>18</sub>** — 10- $\mu$ fd. ceramic.  
**C<sub>3</sub>, C<sub>11</sub>** — 15- $\mu$ fd. midget variable (National UM-15).  
**C<sub>4</sub>** — 15- $\mu$ fd. midget variable (Hammarlund HF-15).  
**C<sub>5</sub>, C<sub>6</sub>, C<sub>7</sub>, C<sub>8</sub>, C<sub>13</sub>, C<sub>19</sub>, C<sub>20</sub>, C<sub>21</sub>, C<sub>22</sub>, C<sub>23</sub>, C<sub>24</sub>, C<sub>25</sub>, C<sub>26</sub>, C<sub>27</sub>, C<sub>28</sub>, C<sub>29</sub>, C<sub>30</sub>** — 0.01- $\mu$ fd. mica.  
**C<sub>15</sub>** — 37- $\mu$ fd. ceramic (10 and 27 in parallel).  
**C<sub>16</sub>, C<sub>30</sub>, C<sub>32</sub>** — 100- $\mu$ fd. mica.  
**C<sub>17</sub>** — 35- $\mu$ fd. midget variable (National U M-35).  
**C<sub>31</sub>** — 220- $\mu$ fd. mica.  
**C<sub>33</sub>** — 0.05- $\mu$ fd. paper, 200 volts.  
**C<sub>34</sub>** — 0.1- $\mu$ fd. paper, 200 volts.  
**C<sub>35</sub>, C<sub>37</sub>** — 10- $\mu$ fd. 25-volt electrolytic.  
**C<sub>38</sub>** — 0.1- $\mu$ fd. paper, 400 volts.  
**C<sub>38</sub>** — 35- $\mu$ fd. midget variable (Hammarlund HF-35).


- CC<sub>1</sub>, CC<sub>2</sub>** — See text.  
**R<sub>1</sub>, R<sub>10</sub>, R<sub>16</sub>, R<sub>30</sub>** — 0.1 megohm.  
**R<sub>2</sub>** — 68 ohms.  
**R<sub>3</sub>, R<sub>14</sub>** — 33,000 ohms.  
**R<sub>4</sub>, R<sub>5</sub>, R<sub>8</sub>, R<sub>9</sub>, R<sub>15</sub>, R<sub>18</sub>, R<sub>19</sub>** — 470 ohms.  
**R<sub>6</sub>, R<sub>13</sub>, R<sub>20</sub>, R<sub>21</sub>** — 47,000 ohms.  
**R<sub>7</sub>** — 220 ohms.  
**R<sub>11</sub>** — 180 ohms.  
**R<sub>12</sub>** — 2000-ohm wire-wound potentiometer.  
**R<sub>17</sub>** — 330 ohms.  
**R<sub>22</sub>, R<sub>23</sub>, R<sub>29</sub>, R<sub>33</sub>** — 1.0 megohm.  
**R<sub>24</sub>, R<sub>28</sub>** — 0.15 megohm.  
**R<sub>25</sub>** — 2700 ohms.  
**R<sub>26</sub>** — 1.0-megohm carbon potentiometer.  
**R<sub>27</sub>** — 25,000-ohm carbon potentiometer.

- R<sub>31</sub>** — 470 ohms, 1 watt.  
**R<sub>32</sub>** — 27,000 ohms.  
**R<sub>34</sub>** — 0.22 megohm.

- All resistors  $\frac{1}{2}$  watt unless otherwise noted.  
**L<sub>1</sub> through L<sub>6</sub>** — See coil table.  
**J<sub>1</sub>** — Closed-circuit jack.  
**S<sub>1</sub>** — S.p.d.t. toggle switch.  
**S<sub>2A-B-C</sub>** — Three-pole 3-position wafer switch (Centralab 2507).  
**T<sub>1</sub>, T<sub>2</sub>** — 456-kc. interstage i.f. transformer, permeability-tuned (Millen 64456).  
**T<sub>3</sub>** — 456-kc. diode transformer, permeability-tuned (Millen 64454).  
**T<sub>4</sub>** — 456-kc. b.f.o. assembly, permeability-tuned (Millen 65456).

*Fig. 5-48* — This view of the eight-tube receiver chassis shows the mounting of the tuning condensers and the placement of most of the large components. The three shielded plug-in-coil assemblies can be seen to the left of the tuning gang. The 6K8 converter is the tube on the left nearest the panel.

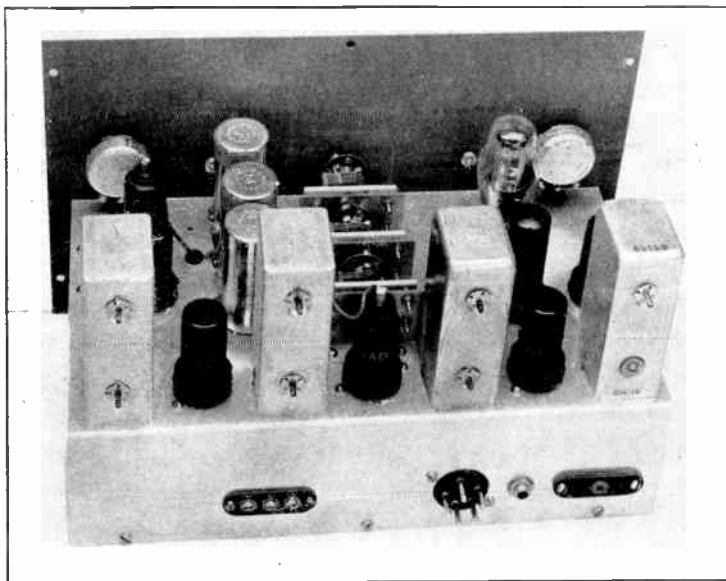The antenna terminal strip, power-supply plug, headphone jack and speaker terminals are mounted on the rear (foreground in this view) of the chassis.



### Construction

The receiver is built on an aluminum chassis mounted in a Par-Metal CA-202 cabinet, and a Millen 10035 dial is used for tuning. The chassis is made of  $\frac{1}{16}$ -inch-thick stock, bent into a "U"-channel, and measures 13 inches wide and  $7\frac{1}{4}$  inches deep on the top. It is  $3\frac{3}{8}$  inches deep at the rear and  $\frac{1}{8}$  inch less at the front. The rear edge is reinforced with a piece of  $\frac{3}{8}$ -inch square dural rod that is tapped for screws through the bottom of the cabinet, further to add to the strength of the structure when finally assembled. The various components that are common to the front lip of the chassis and the panel are used to tie the two together.

The shield panel used to mount the antenna compensator condenser is also made of  $\frac{1}{16}$ -inch aluminum with a  $\frac{3}{16}$ -inch lip on the side for mounting. Part of the lip must be cut away to clear wires and mounting plates on some sockets, so it is advisable to put in the panel after most of the assembly and wiring have been completed. Flexible couplings and bakelite rod couple the condenser to the panel bushing.

The three tuning condensers are mounted on individual brackets of  $\frac{1}{16}$ -inch aluminum. The brackets measure  $2\frac{1}{2}$  inches wide and  $1\frac{9}{16}$  high, with  $\frac{1}{2}$ -inch lips. A cover of thin aluminum — not shown in the photographs — slides over the condenser assembly to dress up the top view a bit. The dust cover is not necessary for satisfactory operation of the receiver.

Ceramic sockets are used for the plug-in coils and for the r.f. amplifier, converter and b.f.o. tubes. Mica condensers were used throughout the receiver for by-passing wherever feasible, because they lend themselves well to compact construction. Paper condensers could be used in the i.f. amplifier but they would crowd things a bit more,

In wiring the receiver, small tie-points were used wherever necessary to support the odd ends of resistors and condensers, and rubber grommets were used wherever wires run through the chassis, with the exception of the tuning-condenser leads. The latter leads, being of No. 14 wire, are self-supporting through the  $\frac{5}{16}$ -inch clearance holes and do not require grommets. The same heavy wire was used for the grid and plate leads of the r.f. stage and the plate lead of the oscillator, to reduce the inductance in these leads. The tuning condensers are grounded back at the coil sockets and not above the chassis as might be the tendency. Screen, cathode and plate by-pass condensers are grounded at a single point for any tube wherever possible, although  $C_2$  is grounded at the r.f.-coil socket,  $C_8$  is grounded at the converter-coil socket, and  $C_{13}$  is returned at the oscillator-coil socket. The plate and B+ leads from  $T_1$  are brought back to the converter socket through shield braid, and  $C_{21}$  is returned to ground at the converter socket.

The b.f.o. pitch condenser,  $C_{38}$ , is insulated from the chassis and panel by fiber washers, and the rotor is connected back to the tube socket by braid that shields the stator lead. This is done to reduce radiation from the b.f.o. which might get in at the front end of the i.f. amplifier.

The coils are wound on Millen 74001 permeability-tuned coil forms, according to the coil table. Series condensers are mounted inside the forms on all bands except the 80-meter range, where no condenser is required and the tuning condenser is jumped directly to the grid end of the coils. In building the coils, the washers are first drilled for the leads and then cemented to the form with Duco or other cement. The bottom washer is cemented close to the terminal pins, leaving just enough room

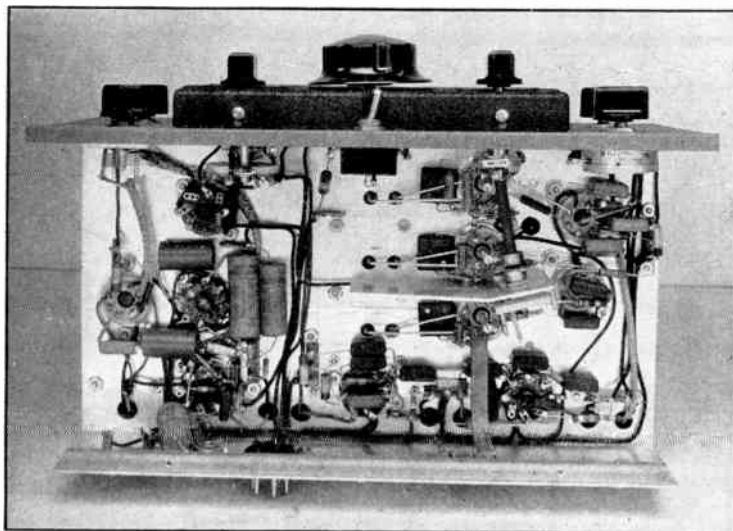


Fig. 5-19 — The mica by-pass condensers used throughout the r.f. and i.f. stages are grouped around the sockets of their respective tubes. Tie-points are used wherever necessary to support small resistors and condensers. The antenna trimmer condenser is mounted on a bracket which also serves as shielding between the mixer- and r.f.-coil sockets, and it is offset to allow access to the trimmer screws on the coil forms. The plate and B+ leads from the first i.f. transformer,  $T_1$ , are run in shielded braid, as are the leads from the h.f.o. pitch-control condenser and the volume control.

to get the soldering iron in to fasten the coil ends and to leave room for the series condenser. The large coils,  $L_2$ ,  $L_4$  and  $L_6$ , were wound first in every case, and then a layer of polystyrene Scotch Tape wrapped over the coil, after which the smaller winding was put on and the ends of the windings soldered in place. Since for maximum range of adjustment it is desirable to allow the powdered-iron slug to be fully withdrawn from the coil, keeping the coils at the base end of the form allows the iron slug to travel out at the other end, under which condition the adjusting screw on the slug projects the least. To secure the wires after winding, drops of cement should be placed on them where they feed through the polystyrene washers.

#### Alignment

If a signal generator is available, it can be used to align the i.f. amplifier on 455 kc. in the usual manner. If one is not available, the coupling at  $C_{C1}$  can be increased to the point where the i.f. stage oscillates readily and the h.f.o. transformer is then tuned until a beat note is heard. The other transformers can then be aligned until the signal is loudest, after which  $C_{C1}$  should be decreased until the i.f. oscillates with the regeneration control,  $R_{12}$ , about 5 degrees from maximum. The trimmers on  $T_1$  then should be tuned to require maximum advancing of the regeneration control for oscillation, with a set value of  $C_{C1}$ . When properly tuned, the oscillation frequency of the i.f. stage and the frequency for maximum gain in the regenerative condition will be the same.

With a set of coils in the front end, set the tuning dial near the high-frequency end and tune in a strong signal or marker with the adjustment screw on the oscillator coil. The converter and r.f. coils can then be peaked, with the antenna compensator set at about half

capacitance. Then tune to the other end of the band and see if you have enough bandsread. If the bandsread is inadequate, it means that  $C_{14}$  is too large, and it should be reduced by using a smaller size of condenser or a combination that gives slightly less capacitance. The tracking of the converter and r.f. coils can be checked by reapeaking the position of the slugs in the coils at the low-frequency end. If the converter- or r.f.-coil tuning slugs have to be advanced farther into the coil (to increase the inductance) it indicates that  $C_9$  or  $C_1$  should be larger. Tracking by the method described is at best a compromise, although to all intents and purposes the loss from some slight misalignment is completely unimportant. Another method would be to tap the tuning condensers on the coil in the familiar bandsreading manner, but this requires considerable time and patience. However, with the series condensers as used in this receiver, the tuning curve is more crowded at the high-frequency end of a range than at the low, and this would be reduced somewhat by the tapped-coil bandsread.


#### COIL DATA FOR THE EIGHT-TUBE SUPERHETERODYNE

Coil	3.5 Mc.	7 Mc.	14 Mc.	28 Mc.
$L_1$	15 t.	9 t.	6 t.	4 t.
$L_2, L_4$	76 t.	33 t.	19 t.	8 t.
$C_1, C_9$	short	27 $\mu$ fd.	15 $\mu$ fd.	20 $\mu$ fd.
$L_3$	25 t.	11 t.	7 t.	4 t.
$L_5$	10 t.	8 t.	4 t.	2 t.
$L_6$	47 t.	32 t.	14 t.	6 t.
$C_{14}$	short	42 $\mu$ fd.	27 $\mu$ fd.	51 $\mu$ fd.

All coils wound on Millen 74001 forms, close-wound. 3.5-Mc. coils wound with No. 30 enam.; 7-Mc. coils wound with No. 30 d.s.e.; 14- and 28-Mc. coils wound with No. 30 d.s.e. on primaries and ticklers and No. 24 enam. on secondaries.  $C_{14}$  for 7-Mc. range made by connecting 27- and 15- $\mu$ fd. condensers in parallel.  $C_1$ ,  $C_9$  and  $C_{14}$ , Erie Ceratronics, mounted in coil form.

Fig. 5-50 — Power-supply wiring diagram.

- C<sub>1</sub>, C<sub>2</sub> — 16- $\mu$ fd. 450-volt electrolytic.
- C<sub>3</sub>, C<sub>4</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- R<sub>1</sub> — 500 ohms, 10 watts, wire-wound.
- R<sub>2</sub> — 5000 ohms, 10 watts, wire-wound.
- R<sub>3</sub> — 0.1 megohm, 1 watt, composition.
- L<sub>1</sub> — 30-henry 110-ma. filter choke (Stancor C-1001).
- T<sub>1</sub> — 350-0-350 volts, 90 ma.; 5 volts at 3 amp., 6.3 volts at 3.5 amp.

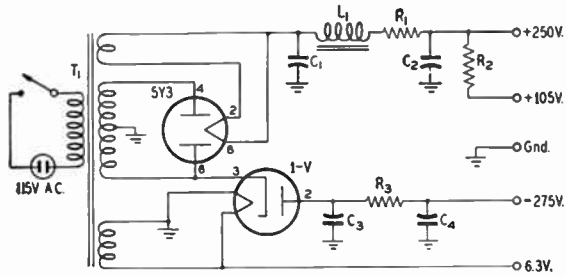

The adjustment of  $L_5$  can be made, if deemed necessary, by lifting the cathode end of  $R_6$  and inserting a 0-1 millimeter. If the tickler coil has the right number of turns, the current will be from 0.15 to 0.2 ma., and it won't change appreciably over the band. Although such a grid-current check is a fine point and not really necessary, it is a simple way to determine that the oscillator portion is working, since the cold ends of  $L_5$  and  $L_6$  are at the same end of the form — the plug end — and this necessitates winding the two coils in opposite directions.

Some trouble may be experienced with oscillation in the r.f. stage at 28 Mc. However, a grounding strap of spring brass, mounted under one of the screws holding the mixer-coil socket to ground the shield when the coil is

plugged in, will normally clear up the trouble. Inadequate coupling to the antenna will also let the r.f. stage oscillate under some tuning conditions, and close coupling is highly recommended for stability in this stage and also for best signal response. A 10-ohm resistor from  $L_2$  to the grid of the 6SG7 will also do the trick.

It will be found that the over-all gain of the receiver is quite high on the lower-frequency bands, requiring that the r.f. gain be cut down to prevent overloading on strong signals. For c.w. reception, the regeneration control is advanced to the point just below oscillation and the b.f.o. is detuned slightly to give the familiar single-signal effect. For 'phone reception,  $S_2$  is switched to "A.V.C." and volume-control adjustments made with the audio control,  $R_{26}$ . If desired, the regeneration control can be advanced until the i.f. is oscillating weakly, and then a heterodyne will be obtained on weak carriers, making them easy to spot. Strong carriers will pull the i.f. out of oscillation because the developed a.v.c. voltage reduces the gain, and hence a simple form of automatic selectivity control is obtained. If it is considered desirable to reduce the i.f. gain when switched to the "A.V.C." position, the regeneration control can be used for this purpose. The "MAN." position permits manual gain-control operation with the b.f.o. off.

The switch  $S_1$  is used for receive-transmit and throws about 40 volts negative on the grid of the first r.f. stage.

### Power Supply

A power supply suitable for the eight-tube receiver is shown in Figs. 5-50 and 5-51. An idea of the parts arrangement can be obtained from Fig. 5-51, although there is nothing critical about this portion of the receiver. If one wants a neat-looking station with no loose power supplies in sight, the power supply can be built into one corner of the loudspeaker cabinet.

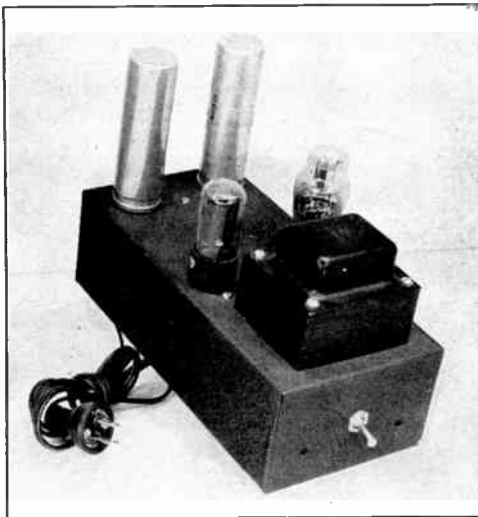


Fig. 5-51 — Power supply for the eight-tube receiver. Two rectifiers are required because a separate supply is incorporated for gain-control purposes. The filter choke and the negative-supply filter condensers are mounted under the chassis. At the rear of the chassis is the socket for the power cable.

## Improving Receiver Sensitivity

Early in this chapter it was pointed out that the sensitivity (signal-to-noise ratio) of a receiver on the higher frequencies above 20 Mc. is dependent upon the bandwidth of the receiver and the noise contributed by the "front

end" of the receiver. Neglecting the fact that the image rejection is poor, a receiver with no r.f. stage is generally satisfactory, from a sensitivity point, in the 3.5- and 7-Mc. bands. However, as the frequency is increased and the

atmospheric noise becomes less, the advantage of a good "front end" becomes apparent. Hence at 14 Mc. and higher it is worth while to use at least one stage of r.f. amplification ahead of the first detector for best sensitivity as well as image rejection. The multigrid converter tubes have very poor noise figures, and even the best pentodes and triodes are three or four times noisier when used as mixers as they are when used as amplifiers.

If the purpose of an r.f. amplifier is to improve the receiver noise figure at 14 Mc. and higher, a high- $G_m$  pentode or triode should be used. Among the pentodes, the best tubes are the 6AC7, 6AK5 and the 6SG7, in the order named. The 6AK5 takes the lead above 30 Mc. The 6J4, 6J6 and 7F8 are the best of the triodes. For best noise figure, the antenna circuit should be coupled a little heavier than optimum. This condition leads to poor selectivity in the antenna circuit, so it is rather futile to try to combine best sensitivity with maximum selectivity in this circuit.

When a receiver is satisfactory in every respect (stability and selectivity) except sensitivity on 14 and/or 28 Mc., the best solution for the amateur is to add a preamplifier, a stage or two of r.f. amplification designed expressly to improve the sensitivity. If image rejection is lacking in the receiver, some selectivity should be built into the preamplifier (it is then called a preselector). If, however, the receiver operation is poor on the higher frequencies but is satisfactory on the lower ones, a "converter" is the best solution.

Some commercial receivers that appear to lack sensitivity on the higher frequencies can be improved simply by tighter coupling to the antenna. Since the receiver manufacturer has no way to predict the type of antenna that will be used, he generally designs the input for some compromise value, usually around 300 or 400 ohms in the high-frequency ranges. If your antenna matches to something far different from this, the receiver effectiveness can be improved by proper matching. This can be accomplished by changing the antenna to the right value (as determined from the receiver instruction book) or by using a simple matching device as described later in this chapter. Overcoupling the input circuit will often im-

prove sensitivity but it will, of course, always reduce the image-rejection contribution of the antenna circuit.

Commercial receivers can also be "hopped up" by substituting a high- $G_m$  tube in the first r.f. stage if one isn't already there. The amateur must be prepared to take the consequences, however, since the stage may oscillate, or not track without some modification. A simpler solution is to add the "hot" r.f. stage ahead of the receiver.

### Regeneration

Regeneration in the r.f. stage of a receiver (where only one stage exists) will often improve the sensitivity because the greater gain it provides serves to mask more completely the first-detector noise, and it also provides a measure of automatic matching to the antenna through tighter coupling. However, accurate ganging becomes a problem, because of the increased selectivity of the regenerative r.f. stage, and the receiver almost invariably becomes a two-handed-tuning device. Regeneration should not be overlooked as an expedient, however, and many amateurs have used it with considerable success. High- $G_m$  tubes are the best as regenerative amplifiers, and the feed-back should not be controlled by changing the operating voltages (which should be the same as for the tube used in a high-gain amplifier) but by changing the loading or the feed-back coupling. This is tricky and another reason why regeneration is not too widely used.

### Gain Control

In a receiver front end designed for best signal-to-noise ratio, it is advantageous in the reception of weak c.w. signals to eliminate the gain control from the first r.f. stage and allow it to run "wide open" all of the time. If the first stage is controlled along with the i.f. (and other r.f. stages, if any), the signal-to-noise ratio of the receiver will suffer. As the gain is reduced, the  $G_m$  of the first tube is reduced, and its noise figure becomes higher. An elaborate receiver might well have separate gain controls for the first r.f. stage and for all i.f. stages.

## A Dual-Triode Preamplifier


The 6J6 preamplifier shown in Figs. 5-52, 5-54 and 5-55 is a simple device that can be used ahead of a receiver on 14 or 28 Mc. to improve the sensitivity. It is designed to be built for one band only and left fixed, although coil dimensions are given for both the 10- and 20-meter bands.

As can be seen from the circuit diagram in Fig. 5-53, the input circuit uses a reactance network,  $C_1C_2$ , to enable the operator to adjust the input of the preamplifier to whatever

impedance his antenna system works into best. Higher impedances require that the ratio of  $C_1$  to  $C_2$  be made larger. Final peaking is done with  $L_1$ , and the only trimming done during actual operation is in the output circuit,  $L_2C_5$ .  $C_5$  is made variable and is the only control easily accessible to the operator. This circuit provides some additional selectivity ahead of the receiver for image rejection, but the input circuit is coupled heavily to the antenna and hence adds no selectivity. The antenna circuit

◆  
**Fig. 5-52** — A one-tube 6J6 preamplifier for boosting receiver sensitivity on 14 or 28 Mc. Note the two holes in front of the antenna posts through which the antenna-coupling condensers are adjusted.

◆

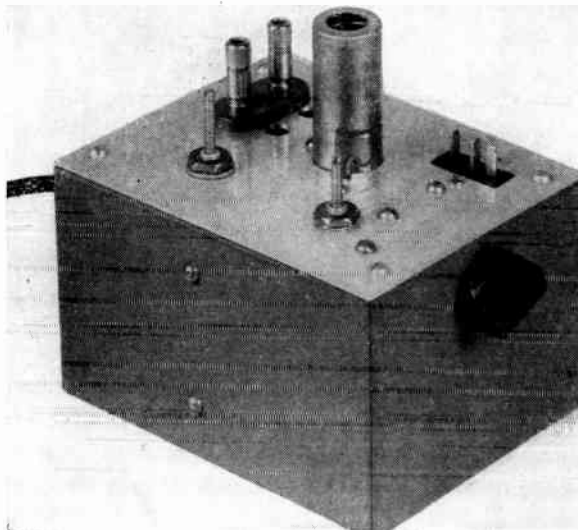

requires no retuning over the bands. With this type of input matching, an antenna with a "flat" line works best, since there are some impedances presented by tuned lines that are difficult to match with this arrangement.


The first half of the 6J6 acts as a cathode-follower stage, and its output signal is developed across  $R_1$ . The second half of the tube acts as a grounded-grid r.f. amplifier and hence requires no neutralization. With the output of the preamplifier connected to a receiver but with the input disconnected from the antenna, it is possible to make the amplifier oscillate, but connecting an antenna and tuning the input properly results in a stable amplifier. A regenerative condition in the amplifier will

require retuning of the input circuit over an amateur band, and is to be avoided.

### Construction

The construction of the unit is a simple matter. With the single exception of the interstage shield, all of the components are mounted on the 4 × 5-inch piece of aluminum used to replace one side of the 3 × 4 × 5-inch box. This makes it easy to work on the unit, since all of the construction work can be done with the chassis removed from the box. The two condensers,  $C_1$  and  $C_2$ , are supported by No. 12 tinned wire soldered to the input terminals (a National FWH assembly) and a lug on a small National GS-10 stand-off insulator. The output tuning condenser,  $C_5$ , is mounted on a small aluminum bracket. All r.f.-circuit grounds are brought to a single lug under one of the 6J6 socket mounting screws. The power leads are brought out through a Jones P-303-AB miniature plug, and the lip of the case must be cut out slightly to clear one bracket of this plug. The output cable, a length of RG-58/U, is secured to a small tie-point which also serves as a tie-point for the ends of  $L_3$ . The outer conductor of the cable is grounded by the tie-point mounting bracket.

The interstage shield is fastened to one side of the case only, and it is juggled into place after the chassis is fastened down. The interstage shield has a notch to clear the r.f.-circuit ground lug, and another notch holds the output cable in place. A small hole is necessary to pass the lead from  $L_1$  to the grid of the tube. This grid lead must be connected after the shield is in place, but it is the only connection that can't be made beforehand. The grounded grid lead, from Pin 6, runs across the socket to the socket center shield, to Pin 3, and to ground.

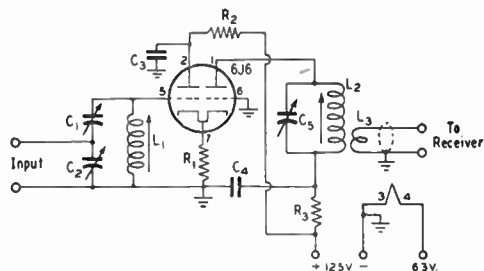

**Fig. 5-53** — Circuit diagram of the 6J6 cathode-coupled preamplifier.

- $C_1, C_2$  — 3- to 30- $\mu$ fd. mica trimmer (National M-SO).
  - $C_3, C_4$  — 0.001- $\mu$ fd. mica, smallest size.
  - $C_5$  — 35- $\mu$ fd. midget variable (Millen 20035).
  - $R_1$  — 470 ohms,  $\frac{1}{2}$ -watt carbon.
  - $R_2, R_3$  — 1500 ohms,  $\frac{1}{2}$ -watt carbon.
  - $L_1$  — 28 Mc.: 17 turns No. 22 d.c.c., close-wound.
  - 14 Mc.: 34 turns No. 30 d.c.c., close-wound.
  - $L_2$  — 28 Mc.: 10 turns No. 18 enam., space-wound to fill form.
  - 14 Mc.: 20 turns No. 22 d.c.c., close-wound.
  - $L_3$  — 3 turns No. 18 flexible hook-up wire close-wound over ground end of  $L_2$ .
- Coils are wound on National NR-50 forms.

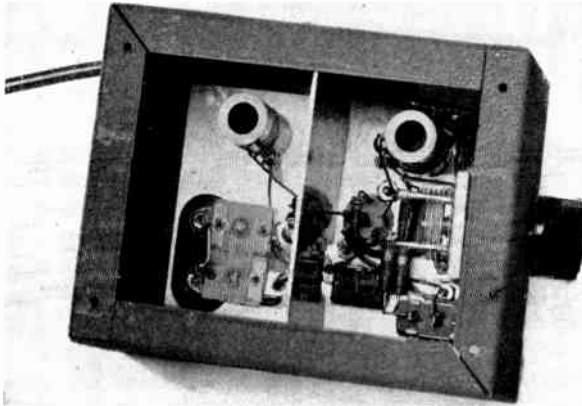


Fig. 5-54 — A view of the underside of the preamplifier shows the shield partition in place.


### Adjustment

The permeability-tuned coils and the adjustable input condensers make adjusting the preamplifier a fairly easy job. Connecting the amplifier to the receiver,  $C_5$  is set at about half scale and the core of  $L_2$  adjusted for resonance, as indicated by a slight increase in noise in the receiver. Then different ratios of  $C_1$  to  $C_2$  are tried, resonating the circuit with the slug in  $L_1$ , until best results are obtained. If  $C_1$  is small compared with  $C_2$ , the loading on the input circuit will be light, and if it is too light the amplifier will oscillate. This is remedied by increasing the capacity of  $C_1$  (or decreasing that of  $C_2$ ) and reresonating  $L_1$ . If the receiving antenna uses a tuned line, some combinations may occur where proper loading cannot be obtained, in which case it may be

necessary to resort to an external tuned circuit link-coupled to the input of the preamplifier. With a reasonably "flat" line, no difficulty should be encountered.

If the input circuit is too lightly loaded by the antenna, the preamplifier may be regenerative. While it will be sensitive in this condition, the regeneration will sharpen the input circuit so much that it will be necessary to retune  $L_1$  several times across the band. Since the best noise figure generally obtains when the antenna coupling is slightly more than "critical coupling," there is no advantage in the regenerative condition except possibly the improved image rejection. The disadvantage of having to retune  $L_1$  is obvious, however.

Fig. 5-55 — The preamplifier chassis removed from the case shows the parts arrangement. All r.f. grounds are made to one common point.

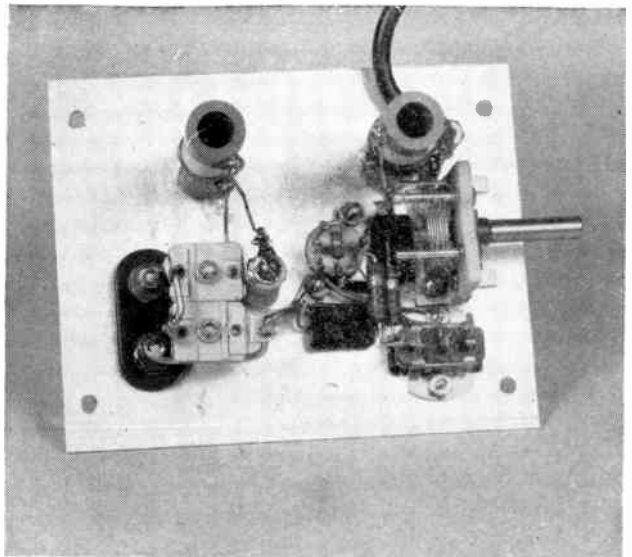

## An Antenna-Coupling Unit for Receiving

It will often be found advantageous on the 14- and 28-Mc. bands to tune (or match) the receiving-antenna feedline to the receiver, in order to get the most out of the antenna. A compact unit for this purpose is shown in Fig. 5-56. The wiring diagram, Fig. 5-57, shows that the unit is a simple pi-section coupler. Through proper selection of condensers and inductances, a match can be obtained over a wide range of values. It can be placed close to the receiver and left connected all

of the time, since it will have little or no effect on the lower frequencies. A short length of 300-ohm Twin-Lead is convenient for connecting the coupler to the receiver.

The antenna coupler is built in a 3 × 4 × 5-inch metal cabinet. All of the components except the two pairs of terminals are mounted on one panel. The condensers are mounted off the panel by the spacers furnished with the condensers, and a clearance hole for the shaft prevents any short-circuit to the panel. The



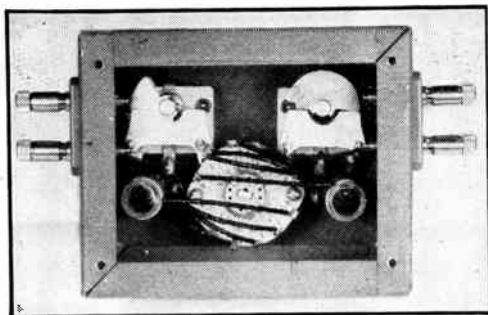


Fig. 5-56 — Rear view of the antenna-coupling unit. The two coils can be seen directly below the two tuning condensers.

coils, wound on National PRD-2 polystyrene forms, are fastened to the panel with brass screws, and the coils should be wound on the forms as far away as possible from the mounting end. If this still leaves the coil ends within  $\frac{1}{2}$  inch of the panel, the forms should be spaced away from the panel by National XP-6 buttons. The switch should be wired so that the switching sequence puts in, in each coil, 0 turns,  $2\frac{1}{2}$  turns,  $6\frac{1}{2}$  turns,  $14\frac{1}{2}$  turns and 30

turns. All of the wiring, with the exception of the input and output terminals, can be done with the panel removed from the box.

The unit is adjusted for maximum signal by switching to different coil positions and adjusting  $C_1$  and  $C_2$ . It will not be necessary to retrim the condensers except when going from one end of a band to the other, and when the unit is not in use, as on 7 and 3.5 Mc., the coils should be switched out of the circuit and the condensers set at minimum.

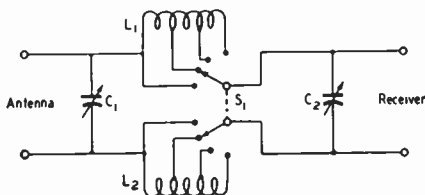


Fig. 5-57 — Circuit diagram of the coupling unit.  
 $C_1, C_2$  — 100- $\mu$ fd. midget variable (Millen 22100).  
 $L_1, L_2$  — 30 turns No. 18 d.c.c. close-wound on  $\frac{1}{2}$ -inch diameter polystyrene form, tapped at  $2\frac{1}{2}$ ,  $6\frac{1}{2}$  and  $14\frac{1}{2}$  turns.  
 $S_1$  — 2-circuit 5-position single-section ceramic wafer switch (Mallory 173C).

## Extending the Tuning Range

As mentioned earlier, when a receiver doesn't cover a particular frequency range, either in fact or in satisfactory performance, a simple solution is to use a converter. A converter is another "front end" for the receiver, and it is made to tune the proper range or to give the necessary performance. It works into the receiver at some frequency between 1.6 and 10 Mc. and thus forms with the receiver a "triple-detection" superhet.

There are several different types of converters in vogue at the present time. The commonest type, since it is the oldest, uses a regular tunable oscillator, mixer, and r.f. stages as desired, and works into the receiver at a fixed frequency. A second type uses broad-banded r.f. stages in the r.f. and mixer stages of the converter, and only the oscillator is tuned. Since the frequency the converter works into is high (7 Mc. or more), little or no trouble with images is experienced, despite the broad-band r.f. stages. A third type of converter uses broad-banded r.f. and output stages and a fixed-frequency oscillator (self- or crystal-controlled). The tuning is done with the receiver the converter is connected to. This is an excellent system if the receiver itself is well shielded and has no external pick-up of its own. Many war-surplus receivers fall in this category. A fourth type of converter uses a fixed oscillator with ganged mixer and r.f. stages, and requires two-handed tuning, for the r.f. stages and for the receiver. The r.f. tuning is not critical, however, unless there are many stages.

The broad-banded r.f. stages have the advantage that they can be built with short leads, since no tuning capacitors are required and the unit can be tuned initially by trimming the inductances. They are a little more prone to cross-modulation than the gang-tuned r.f. stages, however, because of the lack of selectivity. The fourth type of converter, although the most difficult to build, is probably the most satisfactory, particularly if a crystal-controlled high-frequency oscillator is used. It not only has the advantage of the best selectivity and protection against images and cross-modulation, but the crystal gives it a stability unobtainable with self-controlled oscillators. Amateurs who specialize in operation on 28 and 50 Mc. often develop good converters for use ahead of conventional communications receivers, and the extra trouble often pays off in outstanding performance for the station.

While converters can extend the operating range of an existing receiver, their greatest advantage probably lies in the opportunity they give for getting the best performance on any one band. By selecting the best tubes and techniques for any particular band, the amateur is assured of top receiver performance. With separate converters for each of several bands, changes can be made in any one without disabling or impairing the receiver performance on another band. The use of converters ahead of the low-frequency receiver is rapidly becoming standard practice on the bands above 14 Mc.

## A One-Tube Converter for 10 and 11 Meters

The 10- and 11-meter converter shown in Figs. 5-58 and 5-60 is a simple unit that can be built in a few hours, for a cost of less than ten dollars. The converter uses a fixed-frequency oscillator and tunable input and output circuits. The fixed oscillator frequency is selected to take advantage of the calibration and band-spread offered by the communications receiver into which the converter works. Because of the light current consumption — 10 to 12 ma. — it is usually possible to operate the converter from the receiver power supply.

The circuit diagram, Fig. 5-59, shows that a Type 6BE6 miniature pentagrid-converter tube is used. The tuning range of the oscillator allows the oscillator to be set 4 to 6 Mc. below the frequency of the signal (input) circuit, and the receiver into which the converter works must be able to cover the range 4–6 Mc.

A Hartley circuit is used in the oscillator portion of the 6BE6. Coil  $L_3$  is connected in parallel with condensers  $C_2$  and  $C_4$ , and the frequency of the oscillator is determined by the values of these three components. The frequency of the oscillator must remain fixed after the converter has once been adjusted, and, as a result, stability is an important requirement. This condition is obtained by using a high- $C$  tank circuit, with the 100- $\mu\text{fd}$ . condenser,  $C_4$ , providing the major portion of the capacity. The variable condenser,  $C_2$ , is used as a vernier control for selection of a spot-frequency within the oscillator-frequency range. Feed-back control for the oscillator is obtained by moving the 6BE6 cathode tap on

$L_3$ . Bias voltage for the oscillator is developed across resistor  $R_1$ , and  $C_6$  is the grid-blocking condenser. Condenser  $C_6$  keeps the screen grid at ground r.f. potential, and the dropping resistor,  $R_2$ , reduces the receiver supply voltage to 100 volts — the value recommended for the 6BE6 screen grid. The exact value for this resistor cannot be suggested at this time because the receiver supply voltage must be known before the resistance can be calculated. However, the resistor will carry about 7 ma., and it will probably have a resistance somewhere between 10,000 and 22,000 ohms.

The input circuit consists of coils  $L_1$  and  $L_2$  and condenser  $C_1$ . The antenna coil,  $L_1$ , is center-tapped to allow changing from the doublet to a single-wire type of antenna without the necessity for grounding one of the input terminals.

The output circuit uses a parallel tank circuit,  $C_3L_4$ , an output link,  $L_5$ , and a decoupling network formed by condenser  $C_7$  and resistor  $R_3$ .

Antenna change-over and stand-by switching is done with the selector switch,  $S_{A-B-C-D}$ . When set at one of the two positions, sections  $A$  and  $B$  will connect the antenna to the converter input coil while section  $C$  will connect the output link,  $L_5$ , to the output jack,  $J_1$ . At the same time, section  $D$  will complete the high-voltage connection between the input jack,  $J_2$ , and the plate and screen circuits. When the selector switch is thrown to the second position the antenna will be connected to the receiver and plate and screen voltage will be removed from the 6BE6. This action of disconnecting the antenna and high voltage during transmission periods prevents converter-tube overload and damage to the input coils that might be caused by the strong transmitter signal. A toggle switch,  $S_2$ , is used as the heater on-off control.

### Construction

A utility box, measuring  $3 \times 4 \times 5$  inches, serves as the chassis and cabinet for the converter. The variable condensers, switches, pilot-light assembly and jacks should be mounted on the front and rear walls as shown in Fig. 5-60. The condensers are mounted in line on the front wall, with the shafts centered exactly 1 inch down from the top of the box. The pilot-light assembly and switches are mounted below the condensers and, in each case, are centered  $11/16$  inch above the bottom edge of the case.

The tube socket is mounted on the top cover of the utility box and is located  $1\frac{3}{8}$  inches from the front edge. Holes to pass the coil-form mounting screws are drilled on either side of the tube socket; these holes are  $\frac{7}{8}$  inch in from the

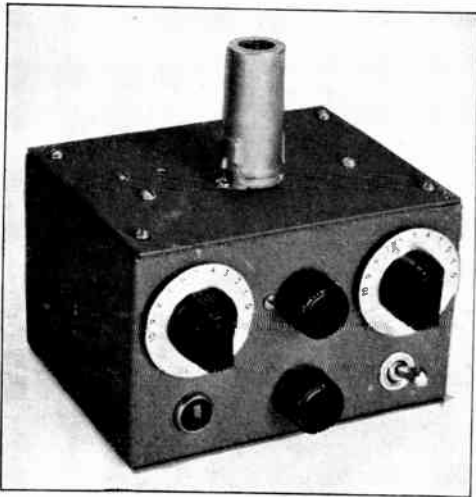


Fig. 5-58 — A front view of the ten-meter converter. The components and controls on the front wall of the case, from left to right, are as follows: top row, r.f. tuning control, oscillator tuning knob, and i.f. circuit control; bottom row, dial-light assembly, antenna change-over switch, and filament switch.

ends of the cover. A tie-point strip is mounted to the rear and right of the tube socket.

Wiring of the unit will be greatly simplified if the wiring is divided into two jobs. The first half includes the wiring associated with the parts mounted on the case walls. This includes the jumper connections on the selector switch and the connections between this switch and the input and output jacks and terminals. Amphenol 300-ohm Twin-Lead is used between the antenna terminals and switch sections *A* and *B* but ordinary hook-up wire, twisted to form a low-impedance line, can be used. The lead from the switch to the output jack should be placed up against the rolled-over edge of the box, to obtain as much shielding as possible. The pilot light and toggle switch can be wired at this time, and a 6-inch lead should be left hanging from the switch side of the pilot light so that the tube filament circuit can be completed when the unit is assembled. The plate by-pass condenser, *C*<sub>7</sub>, can be connected between the rotor terminals of the i.f. and oscillator condensers, and the decoupling resistor, *R*<sub>3</sub>, can be mounted between *C*<sub>3</sub> and section *D* of the selector switch.

The input and output coils should now be wound on the forms suggested in the parts list. Holes, separated by the recommended distance, are drilled straight through the forms, and the ends of the windings are pulled through these holes and cemented in place. The antenna coil is wound directly below the grounded end of the grid coil, *L*<sub>2</sub>, and the output link is wound over the cold end of *L*<sub>4</sub>. It will not be possible to pass the top end of the output link, *L*<sub>5</sub>, through a hole because *L*<sub>4</sub> is directly below this winding and, as a result, the free end of the link should be held in place with Scotch Tape or cement until the coil is mounted and wired. The oscillator coil, *L*<sub>3</sub>, can be wound on a dowel or tube of 5/8-inch diameter; the coil will expand to a 3/4-inch diameter when it has been slipped off the form.

The tube socket, tie-point strip and coils are now mounted in place on the box cover. Soldering lugs are placed under each of the tube-socket mounting nuts. The oscillator coil is soldered between one of the lugs and one of the tie-point terminals. Condenser *C*<sub>4</sub> is connected across the ends of *L*<sub>3</sub>, and the grid resistor, grid-blocking condenser and screen by-pass are wired into the circuit. If the receiver supply voltage is known at this time it is possible to calculate the correct value for the screen-dropping resistor, and the resistor can be mounted on the tie-point strip. The resistor value is obtained from the equation

$$R \text{ (ohms)} = \frac{\text{supply voltage} - 100}{0.0073}$$

Example: Supply voltage 250; the resistor value is  $\frac{250 - 100}{0.0073} = 20,500$  ohms. Anything within 10% of this figure would be satisfactory.


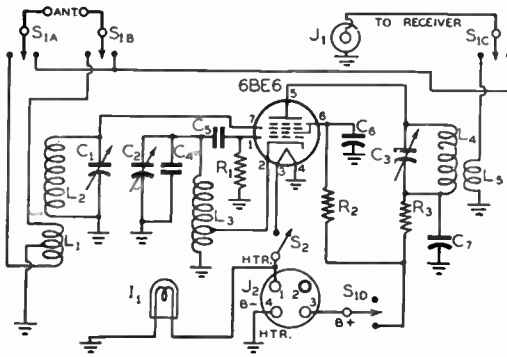


Fig. 5-59 — Circuit diagram of the low-cost ten-meter converter.

- C*<sub>1</sub>, *C*<sub>2</sub> — 15- $\mu$ fd. variable (Millen 20015).
- C*<sub>3</sub> — 75- $\mu$ fd. variable (Millen 20075).
- C*<sub>4</sub> — 100- $\mu$ fd. silver mica.
- C*<sub>5</sub> — 47- $\mu$ fd. mica.
- C*<sub>6</sub>, *C*<sub>7</sub> — 0.01- $\mu$ fd. paper.
- R*<sub>1</sub> — 22,000 ohms, 1/2 watt.
- R*<sub>2</sub> — Screen resistor; see text.
- R*<sub>3</sub> — 1,000 ohms, 1 watt.
- L*<sub>1</sub> — 5 turns No. 22 d.c.c., 3/16-inch diam., close-wound and center-tapped.
- L*<sub>2</sub> — 13 turns No. 22 d.c.c., 3/16-inch diam., 7/8 inch long.
- L*<sub>3</sub> — 6 turns No. 14 tinned, 3/4-inch diam., 3/4 inch long.  
Cathode tap 1 3/4 inches from cold end.
- L*<sub>4</sub> — 78 turns No. 32 d.c.c., 3/16-inch diam., 1 1/4 inches long.
- L*<sub>5</sub> — 10 turns No. 32 d.c.c., close-wound.
- Coils *L*<sub>1</sub>, *L*<sub>2</sub>, *L*<sub>4</sub> and *L*<sub>5</sub> wound on National Type PRE-3 forms.
- I*<sub>1</sub> — 6.3-volt pilot-lamp-and-socket assembly.
- J*<sub>1</sub> — Panel-mounting female socket (Jones S-101).
- J*<sub>2</sub> — Panel-mounting male socket (Amphenol 86-CP4).
- S*<sub>1A-B-C-D</sub> — 4-pole double-throw selector switch (Mal-lory 3212J).
- S*<sub>2</sub> — S.p.s.t. toggle switch.

An 8-inch lead should be connected to the high-voltage end of the screen-resistor mounting terminal; the free end of this lead will be connected to the selector switch during the final stage of the wiring. The grounded ends of *L*<sub>2</sub> and *L*<sub>5</sub>, and the center-tap of *L*<sub>1</sub>, are connected to the grounded soldering lugs, and 2-inch tinned wire leads are connected to the following points: one to each soldering lug and one each to Pins 5 and 7 of the tube socket. A connection is now made between the cathode prong of the tube socket and the tap on coil *L*<sub>3</sub>, and a connection is made between the screen dropping-resistor, *R*<sub>2</sub>, and the screen-grid pin (No. 6) of the socket.

The top cover is now attached to the case and the wiring completed. Few connections remain to be made and, in each case, wires are already provided and soldered in place at one end. After the wiring has been completed it should be given a final check before the testing is started, paying special attention to the heater and plate circuits. Extreme care must be taken while soldering leads that terminate at the ends of *L*<sub>1</sub>, *L*<sub>2</sub>, *L*<sub>4</sub> and *L*<sub>5</sub>. These coils are wound on polystyrene forms which melt and lose shape if subjected to intense heat for any length of time.

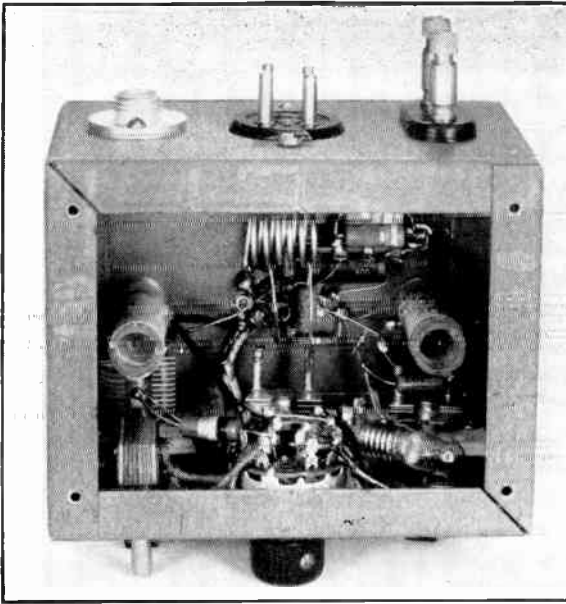

*Fig. 5-60* — An inside view of the ten-meter converter. The r.f. and i.f. coils are at the right and left ends of the box, respectively. The oscillator coil may be seen to the rear of the tube socket. This view also shows the arrangement of the components mounted on the front wall of the case and the location of the input and output connectors which are mounted on the rear wall. The plate bypass condenser is in a vertical position between the oscillator and the i.f. tuning condensers.

### Testing

Adjustment of the converter is convenient if a test oscillator is available, but it is not necessary. Power for the unit can be obtained from the receiver with which the converter is to be used, or from a separate power supply. The converter requires 6.3 volts at 0.45 ampere for the heater and pilot lamp, and 200 to 250 volts d.c. at 10 to 12 ma. for the plate and screen.

After the power supply has been connected, it is advisable to check the screen and plate voltages with a voltmeter. It may be necessary to change the screen-dropping resistor,  $R_2$ , if the voltage at Pin 6 isn't between 90 and 110.

A coaxial or shielded cable should be connected from the converter output jack to the receiver input terminals. The cable must be shielded to avoid the pick-up of unwanted signals. If your transmitter uses VFO, set it to 28 Mc. and your receiver to 4 Mc. If you don't have VFO but use crystal control, set the receiver to your crystal frequency minus 24 Mc. If, for example, your crystal gives a harmonic

at 28,650 kc., set the receiver to 4650 kc. The converter oscillator condenser,  $C_2$ , should now be adjusted until the VFO or crystal harmonic can be heard. If the harmonic can't be heard, run a wire from the antenna posts of the converter close to the transmitter oscillator. If the signal from the transmitter oscillator is too loud, reduce the length of the wire or remove it entirely. When the signal is reasonably weak in the converter, the input and output tuning

capacitors,  $C_1$  and  $C_3$ , can be tuned to make sure that the coils don't need trimming to bring the tuning ranges within the bands.

Once the converter has been carefully set up on a known frequency within the 10- or 11-meter bands,  $C_2$  is left fixed and the tuning is done with the receiver. The frequency of the incoming signal can be read directly from the receiver, by adding 24 to the receiver frequency in Mc. For example, a 28-Mc. signal will tune at 4 Mc., and a 29.250-Mc. signal will fall at 5.250 Mc. When tuning the 11-meter band, the setting of  $C_2$  is changed so that a signal frequency of 27 Mc. corresponds to 4.0 Mc. on the receiver.

The converter, when properly aligned and working into an average receiver, gives a signal-to-noise ratio of 10 to 1 with an input signal of about 10 microvolts. In operation,  $C_1$  and  $C_3$  need not be touched over a tuning range of about 150 or 200 kc. on the receiver. Therefore, these controls should be touched up at intervals if the entire 10-meter band is being combed.

## A Bandpass Converter for 14, 28, and 50 Mc.

The converter shown in Figs. 5-62, 5-63, 5-64 and 5-65 will give reception in the 14-, 28- and 50-Mc. bands with any receiver capable of tuning to 7.3 Mc. To simplify construction, the r.f. stages are fixed-tuned and only the local oscillator is tuned when running across a band. The bandwidth of the r.f. stages is sufficient to accept any signal over an amateur band without noticeable attenuation. The broad-banding is obtained by loading the circuits with resistors to reduce the  $Q$ , using a

minimum of capacity for the same reason, and then "staggering" the circuits; i.e., tuning them to slightly different frequencies so that the resultant passband is broad and nearly flat within the required range. The input circuit, from the antenna, must be broad, and this can only be obtained by heavy coupling to the antenna. This condition coincides with the condition for best signal transfer.

As can be seen from the wiring diagram in Fig. 5-61, the only tuning controls in the r.f.

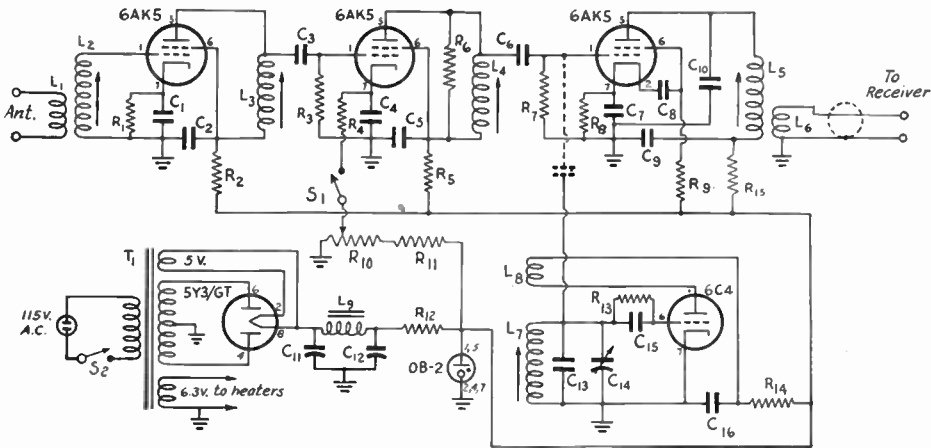


Fig. 5-61 — Circuit diagram of the bandpass converter.

- C<sub>1</sub>, C<sub>2</sub>, C<sub>4</sub>, C<sub>5</sub>, C<sub>7</sub>, C<sub>8</sub>, C<sub>16</sub> — 0.001- $\mu$ fd. postage-stamp mica.
  - C<sub>3</sub>, C<sub>6</sub> — 100- $\mu$ fd. postage-stamp mica.
  - C<sub>9</sub> — 0.01- $\mu$ fd. mica.
  - C<sub>10</sub>, C<sub>15</sub> — 51- $\mu$ fd. ceramic (Eric N150).
  - C<sub>11</sub>, C<sub>12</sub> — 16- $\mu$ fd. 450-volt electrolytic.
  - C<sub>13</sub> — 27- $\mu$ fd. ceramic (Eric N150) across C<sub>14</sub> plus additional capacity mounted in L<sub>7</sub>L<sub>8</sub> form. See coil table.
  - C<sub>14</sub> — 11- $\mu$ fd. midget variable (Hammarlund HF-15 with one stator plate removed).
  - R<sub>1</sub>, R<sub>4</sub> — 180 ohms.
  - R<sub>2</sub>, R<sub>5</sub>, R<sub>13</sub>, R<sub>15</sub> — 270 ohms.
  - R<sub>3</sub>, R<sub>6</sub>, R<sub>8</sub> — 6800 ohms.
  - R<sub>7</sub> — 1.5 megohms.
  - R<sub>0</sub> — 1.0 megohm.
  - R<sub>10</sub> — 2000-ohm potentiometer, wire-wound.
  - R<sub>11</sub> — 10,000 ohms, 2 watts.
  - R<sub>12</sub> — 1250 ohms, 10 watts, wire-wound.
  - R<sub>13</sub> — 51,000 ohms, 1 watt.
- All resistors 1/2 watt unless otherwise specified.
- L<sub>1</sub>-L<sub>8</sub> — See coil table.
  - L<sub>9</sub> — 8-henry 50-ma. filter choke (Stancor C-1279).
  - S<sub>1</sub> — S.p.s.t. rotary switch.
  - S<sub>2</sub> — S.p.s.t. switch, mounted on R<sub>10</sub>.
  - T<sub>1</sub> — 300-0-300 volts, 50-ma. power transformer, with 5- and 6.3-volt windings (UTC R-6).

stages are the powdered-iron slugs of the coils. These are used to resonate the coils with the circuit capacities to the signal frequency. The loading resistors, R<sub>3</sub> and R<sub>6</sub>, are used to broaden the circuits. The plate and screen voltages are the same on each r.f. amplifier tube, to reduce the number of by-pass condensers, and filter resistors are used to prevent over-all feed-back through the common power lead. Another possible source of over-all feed-back is the heater circuit, and in this converter the "hot" heater lead to the input stage was run in shield braid to reduce the possibility of feed-back.

The oscillator is a straight plate-tickler type using a 6C4, and it is coupled to the mixer through a capacity shown as dashed lines in the diagram. Actually the coupling capacitor consists of a short length of wire near the grid of the mixer tube.

The output frequency is 7.3 Mc. approximately, and this is the fre-

quency to which C<sub>10</sub>L<sub>5</sub> is tuned. If a frequency slightly below 7.0 Mc. is used, there is a possibility that the fourth harmonic of the receiver high-frequency oscillator will find its way into the converter when operating in the 28-Mc. band, resulting in a constant signal that has only nuisance value. A low-impedance shielded

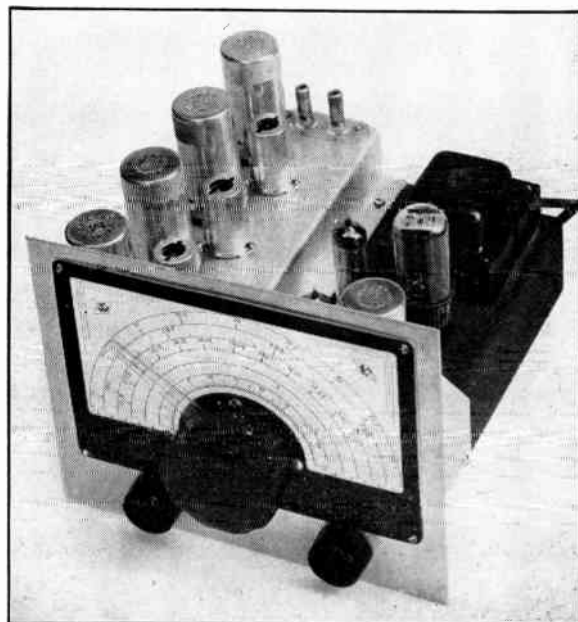


Fig. 5-62 — A 28-Mc. converter that uses fixed-tuned r.f. stages and thus eliminates the ganging problem. The knob at left is for the "send-receive" switch, and the right-hand knob is for gain control.

COIL DATA FOR THE BANDPASS CONVERTER

Coil	14 Mc.	28 Mc.	50 Mc.
<i>L</i> <sub>1</sub>	13 t. No. 26 d.c.c.	8 t. No. 26 d.c.c.	5 t. No. 26 d.c.c.
<i>L</i> <sub>2</sub>	35 t. No. 24 d.c.c.	23 t. No. 24 d.c.c.	8 t. No. 24 d.c.c. spaced wire diam.
<i>L</i> <sub>3</sub> , <i>L</i> <sub>A</sub>	25 t. No. 24 d.c.c.	8½ t. No. 24 d.c.c.	5 t. No. 24 d.c.c. spaced twice wire diam.
<i>L</i> <sub>5</sub>	37 t. No. 26 enam.	Same	Same
<i>L</i> <sub>6</sub>	9 t. No. 26 enam.	Same	Same
<i>L</i> <sub>7</sub>	4 t. No. 24 d.c.c. (spaced to occupy ¼ inch)	7 t. No. 20 enam.	2 t. No. 24 d.c.c. spaced wire diam.
<i>L</i> <sub>8</sub>	3 t. No. 26 d.c.c.	3 t. No. 26 d.c.c.	2 t. No. 24 d.c.c.
<i>C</i> <sub>13</sub>	150 μfd.	27 μfd.	22 μfd.

*L*<sub>1</sub> wound over ground end of *L*<sub>2</sub>, tape insulation. *L*<sub>8</sub> spaced from *L*<sub>7</sub> by washer thickness. All coils close-wound unless otherwise specified. All coils wound on Millen 74001 permeability-tuned forms.


line feeds the 7.3-Mc. output into the communications receiver. The communications receiver furnishes the necessary selectivity.

The cathode bias of the second r.f. amplifier is varied by the gain control, *R*<sub>10</sub>, to avoid blocking by strong signals. The send-receive switch, *S*<sub>1</sub>, is used to turn off the converter during transmission periods. The power switch, *S*<sub>2</sub>, is mounted on the gain control and is used to turn off the power to the converter.

The power supply is regulated, using the miniature equivalent of the VR-105, and the stabilized 105 volts is fed to all stages.
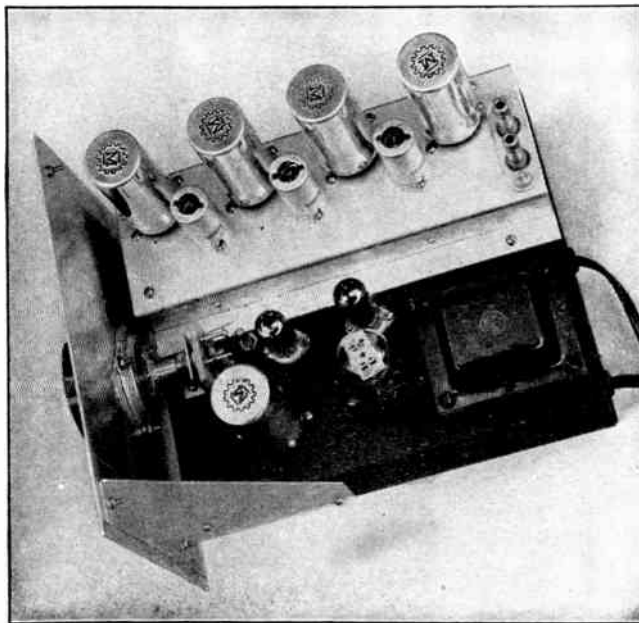
#### Construction

The r.f. stages and mixer are built as a separate unit on a strip of aluminum, to furnish a chassis in which the grounds are more certain than they would be on a black-crackled steel chassis, and it also makes a well-shielded amplifier when mounted on the steel chassis.



The steel chassis is a standard 7 × 11 × 2-inch affair. A panel is used to support the National ACN dial, and to reduce metal work on the steel chassis the panel is supported away from the chassis by an aluminum bracket on one side and by two of the screws that fasten the dial to the panel. Holes in the chassis allow access to the tuning slugs of the r.f. coils.

The tuning condenser is mounted on a small aluminum bracket fastened to the chassis by two screws and to the condenser by the shaft bushing. This results in a rigid mount that contributes considerably to the mechanical stability of the oscillator.


The construction of the aluminum channel is apparent from Fig. 5-64. It is 3 inches wide and 1¼ inches high, and is bolted to the side of the steel chassis and to the top. A small strip of bakelite, supported away from the side by screws and small spacers, is used to support the power-supply end of the filter resistors, *R*<sub>2</sub>, *R*<sub>5</sub> and *R*<sub>15</sub>. The ends are fed through small holes in the bakelite and then wrapped around the strip before being soldered together.

In the heater circuits of the miniature tubes, Pin 4 is grounded to a lug under the nut fastening the socket, and Pin 3 is the "hot" heater lead. In the case of the input 6AK5, the hot heater lead was led back in shield braid, and the braid was grounded at the lug grounding Pin 4, and to lugs at two other points along the way. These latter lugs are under the nuts fastening the sockets for *L*<sub>3</sub> and the output coil, *L*<sub>5</sub>*L*<sub>6</sub>.



Fig. 5-63 — Another view of the converter showing the r.f. sub-chassis. Note the bracket on the tuning condenser, used to avoid back-lash.

Fig 5-64 — The straightforward arrangement of the r.f. components is shown in this view of the subchassis. The straight side is screwed to the side of the chassis.

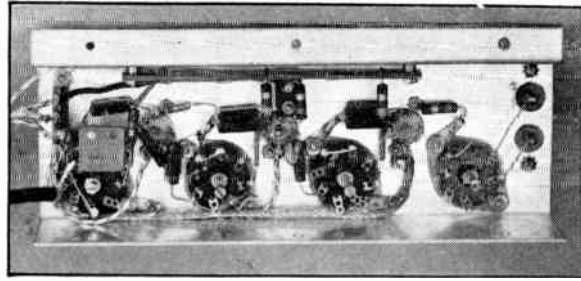

◆

The cathode and screen/plate bypass condensers are grounded to lugs under nuts holding the sockets of their respective plate coils. Since it doesn't matter where the cathode resistors are grounded, they are returned to lugs under the coil sockets ahead of them. Pins 1 and 2 of the coil sockets are grounded to the lugs just mentioned, the No. 3 pins of the coil sockets for  $L_3$ ,  $L_4$  and  $L_5$  go to the plates of their respective tubes, and the No. 4 pins of the same sockets are connected to the screen pins on the tube sockets. The grid condensers,  $C_3$  and  $C_6$ , are tied from Pin 7 on the coil sockets to the grid pins on the tube sockets.

The oscillator and power-supply wiring on the steel chassis is conventional, with the exception of the oscillator coupling condenser. A small National TPB bushing is mounted on the chassis where it will be parallel to the lead on the grid side of  $R_7$ . This bushing is connected to the stator of  $C_{14}$  and the "hot" side of  $L_7$  by a heavy wire, and coupling is obtained by the capacity between this bushing and the grid lead of the mixer stage. The output cable from  $L_6$  is a length of RG-59/U 70-ohm cable. If one of the free points on the OB-2 voltage-regulator tube socket is used as a tie-point for  $C_{12}$  and  $L_9$ , as was done in this case, be sure to clip off the pin on the tube. If this isn't done, a discharge will be obtained inside the tube, since the free pin projects inside the tube envelope and acts as an anode.

The coils for the converter are wound on Millen 74001 tuned plug-in coil forms. The coils are started on the form about  $\frac{1}{8}$  inch above the lower limit of travel of the iron slug. In the case of  $L_3$  and  $L_4$ , one end of the winding is connected to Pin 4 and the other to Pin 7. A jumper is then run from Pin 7 to Pin 3. This jumper has the effect of tapping down the plate on the coil, since the jumper has some reactance at these frequencies. In the case of the oscillator coil, the padding condenser,  $C_{13}$ , is mounted inside the coil, although it could be mounted on the coil socket. The tickler,  $L_8$ , is wound on the form away from the slug end. The mixer output capacitor,  $C_{10}$ , is mounted on the socket. All coils are securely fastened with coil dope, and this is particularly important in the case of the oscillator coil assembly, to insure long-time stability.

#### Alignment

After the wiring has been completed and checked, the oscillator should be checked first. Put a voltmeter across  $R_{14}$  and see if the volt-

age increases slightly when the grid of the oscillator tube is touched. If it does, it shows that the circuit is oscillating, and the coil can be tuned to frequency with the iron slug.

Couple the output of the converter to a communications receiver on 7.3 Mc. and adjust the slug of  $L_5$  for maximum noise in the receiver, with power to the converter and the converter gain control at minimum. Some kind of signal will be needed with which to establish the oscillator frequency accurately, and this signal can be a harmonic from the station transmitter or a test generator. For 28-Mc. alignment, set the signal source at about 28.5 Mc. and the tuning dial at 35 and adjust the slug on the oscillator coil until the signal is heard. Short the input of the receiver with a carbon resistor equal in value to the impedance of the antenna line. Having established the tuning range — and checking it at other points if available — peak  $L_2$ ,  $L_3$  and  $L_4$  on noise. Tuning across the band, the output noise should peak near the center of the range and

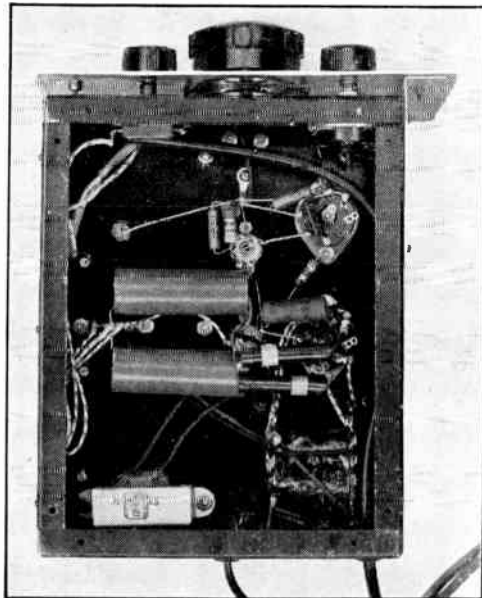


Fig. 5-65 — A view underneath the chassis shows the polystyrene bushing used to couple from the oscillator to the mixer. The panel is mounted away from the chassis to simplify mounting of the dial. The tuning screws of the r.f. coil project through holes in the chassis.

fall off slightly at either end. By increasing the inductance of  $L_4$  — running the slug in — and decreasing the inductance of  $L_3$ , it will be possible to get practically uniform noise output over the entire range. It will be found that  $L_2$  tunes very broadly when loaded by the resistor or the antenna, and its resonance should be checked with this load disconnected, to make certain that the coil can be made to tune through resonance. A sharp increase in the noise will serve as an indication, and it may be found necessary to retard the gain control for this test, to prevent oscillation in the r.f. stages.

If any queer burbles or sudden peaks of noise are encountered, it indicates regeneration in the r.f. stages. If this is encountered, the r.f. stages can be worked on while removed from

the chassis, since there will be enough stray oscillator output to the mixer to receive signals, and the various plate- and heater-supply leads can be investigated with a 0.001- $\mu$ fd. mica condenser until the source of feed-back is found. Poor grounds can also give trouble.

Under normal conditions, the gain of the communications receiver following the converter will have to be reduced considerably, since the gain of the converter runs around 40 db. It will be found to require very little antenna for normal pick-up, but in order to give it every break it should be used with the best antenna available. Some experiment with the input coupling may be necessary if a tuned antenna is used, but this might be only a tuned circuit with a link line running to the converter input.

## Tuning a Receiver

### *C. W. Reception*

For making code signals audible, the beat oscillator should be set to a frequency slightly different from the intermediate frequency. To adjust the beat-oscillator frequency, first tune in a moderately-weak but steady carrier with the beat oscillator turned off. Adjust the receiver tuning for maximum signal strength, as indicated by maximum hiss. Then turn on the beat oscillator and adjust its frequency (leaving the receiver tuning unchanged) to give a suitable beat-note. The beat oscillator need not subsequently be touched, except for occasional checking to make certain the frequency has not drifted from the initial setting. The b.f.o. may be set on either the high- or low-frequency side of zero beat.

The use of a.v.c. is not generally satisfactory in c.w. reception, except in receivers expressly designed for the purpose, because the rectified beat-oscillator voltage in the second detector circuit also operates the a.v.c. circuit. This gives a constant reduction in gain and prevents utilization of the full sensitivity of the receiver. Hence the gain should be manually adjusted to give suitable audio-frequency output.

To avoid overloading in the i.f. circuits, it is usually better to control the i.f. and r.f. gain and keep the audio gain at a fixed value than to use the a.f. gain control as a volume control and leave the r.f. gain fixed at its highest level, except when there are few loud signals on the band and a low noise level.

### *Tuning with the Crystal Filter*

If the receiver is equipped with a crystal filter the tuning instructions in the preceding paragraph still apply, but more care must be used both in the initial adjustment of the beat oscillator and in tuning. The beat oscillator is set as described above, but with the crystal filter in operation and adjusted to its sharpest position, if variable selectivity is available. The

initial adjustment should be made with the phasing control in the intermediate position. After it is completed, the beat oscillator should be left set and the receiver tuned to the other side of zero beat (audio-frequency image) on the same carrier to give a beat-note of the same tone. This beat will be considerably weaker than the first, and may be "phased out" almost completely by careful adjustment of the phasing control. This is the adjustment for normal operation; it will be found that one side of zero beat has practically disappeared, leaving maximum response on the desired side.

An interfering signal having a beat-note differing from that of the a.f. image can be similarly phased out, provided its carrier frequency is not too near the desired carrier.

Depending upon the filter design, maximum selectivity may cause the dots and dashes to lengthen out so that they seem to "run together." It must be emphasized that, to realize the benefits of the crystal filter in reducing interference, it is necessary to do *all* tuning with it in the circuit. Its selectivity is so high that it is often impossible to find the desired station quickly, should the filter be switched in only when interference is present.

### *'Phone Reception*

In reception of 'phone signals, the normal procedure is to set the r.f. and i.f. gain at maximum, switch on the a.v.c., and use the audio gain control for setting the volume. This insures maximum effectiveness of the a.v.c. system in compensating for fading and maintaining constant audio output on either strong or weak signals. On occasion a strong signal close to the frequency of a weaker desired station may take control of the a.v.c., in which case the weaker station will practically disappear because of the reduced gain. In this case better reception may result if the a.v.c. is switched off, using the manual r.f. gain con-



trol to set the gain at a point that prevents "blocking" by the stronger signal.

A crystal filter will do much toward reducing interference in 'phone reception. Although the high selectivity cuts sidebands and thereby reduces the audio output, especially at the higher audio frequencies, it is possible to use quite high selectivity without destroying intelligibility even though the "quality" of the transmission may suffer. As in the case of c.w. reception, it is advisable to do all tuning with the filter in the circuit. Variable-selectivity filters permit a choice of selectivity to suit interference conditions.

An undesired carrier close in frequency to a desired carrier will heterodyne with it to produce a beat-note equal to the frequency difference. Such a heterodyne can be reduced by adjustment of the phasing control in the crystal filter. It cannot be prevented in a "straight" superheterodyne having no crystal filter.

A tone control often will be of help in reducing the effects of high-pitched heterodynes, sideband splatter and noise, by cutting off the higher audio frequencies. This, like sideband cutting with high selectivity, causes some reduction in naturalness.

#### *Spurious Responses*

Spurious responses can be recognized with-

out a great deal of difficulty. Often it is possible to identify an image by the nature of the transmitting station, if the frequency assignments applying to the frequency to which the receiver is tuned are known. However, an image also can be recognized by its behavior with tuning. If the signal causes a heterodyne beat-note with the desired signal and is actually on the same frequency, the beat-note will not change as the receiver is tuned through the signal; but if the interfering signal is an image, the beat will vary in pitch as the receiver is tuned. The beat oscillator in the receiver must be turned off for this test. Using a crystal filter with the beat oscillator on, an image will peak on the side of zero beat opposite that on which the desired signal peaks.

Harmonic response can be recognized by the "tuning rate," or movement of the tuning dial required to give a specified change in beat-note. Signals getting into the i.f. via high-frequency oscillator harmonics tune more rapidly (less dial movement) through a given change in beat-note than do signals received by normal means.

Harmonies of the beat oscillator can be recognized by the tuning rate of the beat-oscillator pitch control. A smaller movement of the control will suffice for a given change in beat-note than is necessary with legitimate signals.

## Building a Receiver

In building a receiver, as in most other pieces of radio gear, following a few basic laws during the construction will more often than not result in a reliable job that won't have a lot of "bugs" which require cleaning out before the receiver will perform properly. The more complex a circuit is, and the more gain it has, the better are the chances for trouble, but a large number of tubes doesn't necessarily indicate that a receiver will be difficult to make work properly.

#### *Feed-Back*

Probably the greatest source of trouble in receivers is from undesirable feed-back. Feed-back giving rise to regeneration and oscillation can occur in any part of the receiver that has gain: the r.f., i.f. and audio amplifiers. It can occur in a single stage or it may appear as an over-all feed-back through several stages that are on the same frequency. To avoid feed-back in a single stage, the output must be isolated from the input in every way possible, with the vacuum tube furnishing the only coupling between the two circuits. For example, an oscillation can be obtained in a r.f. or i.f. stage if there is any undue capacitive or inductive coupling between output and input circuits, if there is too high an impedance between cathode and ground or screen and ground, or if there is any appreciable im-

pedance through which the grid and plate currents can flow in common. This simply means good shielding of coils and condensers in r.f. and i.f. circuits, the use of good by-pass condensers (mica at 14 Mc. and higher, and with short leads), and returning all by-pass condensers (grid, cathode, plate and screen) with short leads to one spot on the chassis. If single-ended tubes are used, the screen or cathode by-pass condenser should be mounted across the socket, to serve as a shield between grid and plate pins. Less care is required as the frequency is lowered, but in high-impedance circuits like those found in high-gain audio amplifiers, it is sometimes necessary to shield grid and plate leads and to be careful not to run them close together. If this precaution is not observed, serious audio feed-back may result.

To avoid over-all feed-back in a multistage amplifier, strict attention must be paid to avoid running any part of the output circuit back near the input circuit without first filtering it carefully. Since the signal-carrying parts of the circuit (the "hot" grid and plate leads) can't be filtered, the best design for any multistage amplifier is a straight line, to keep the output as far away from the input as possible. For example, an r.f. amplifier might run along a chassis in a straight line, run into a mixer where the frequency is changed, and then the i.f. amplifier could be run back parallel to the

r.f. amplifier, provided there was a very large frequency difference between the r.f. and the i.f. amplifiers. However, to avoid any possible coupling, it would be better to run the i.f. amplifier off at right angles to the r.f.-amplifier line, just to be on the safe side. Good shielding is important in preventing over-all oscillation in high-gain-per-stage amplifiers, but it becomes less important when the stage gain drops to a low value. In a high-gain amplifier, the power leads (including the heater circuit) are common to all stages, and they can provide the over-all coupling if they aren't properly filtered. Good by-passing and the use of series isolating resistors will generally eliminate any possibility of coupling through the power leads. R.f. chokes are used in the heater leads where necessary, because the voltage drop through resistors would be too great.

### *Instability*

Receivers that drift rapidly as the tubes warm up and take hours to "settle down" are a nuisance. Thermal drift is a difficult thing to eliminate, but it can be minimized by using ceramic instead of bakelite insulation in the r.f. circuits (particularly the oscillator), a large cabinet compared with the chassis (to provide for good radiation of developed heat), minimizing the number of high-wattage resistors in the receiver itself and putting them in the power supply, and not mounting the oscillator coils and tuning condenser too close to a tube.

Sensitivity to vibration and shock is also a bother, and can be minimized by using good mechanical support for coils and tuning condensers, a heavy chassis, and by not hanging any of the oscillator-circuit components in the air on long leads. Tie-points should be used wherever necessary to avoid long leads on components in the oscillator circuits. Stiff long wires used for wiring components are no good if they can vibrate, and stiff short leads are

excellent because they can't be made to vibrate. Susceptibility to vibration and shock is to be avoided in the oscillators of a receiver and in the first stage of a high-gain audio amplifier.

### *Hum*

A steady a.c. hum in the background of a receiver is a nuisance when listening closely for weak signals. If it appears when no signals are present, it is introduced in the audio circuit and comes from running a grid lead too close to an a.c. heater lead. Shielding or a change in location of the wire will generally eliminate it. It is a good idea to keep all audio grid leads close against the chassis if they are unshielded, to reduce their chances of picking up a.c. hum.

Hum present only on a carrier indicates a.c. modulation of the high-frequency oscillator. It can be avoided by using an oscillator circuit with a grounded cathode, by keeping the grid lead of the oscillator away from the a.c. heater leads, and by making sure that any transformer mounted on the same chassis with the high-frequency oscillator doesn't have loose laminations and a tendency to vibrate.

### *Smooth Tuning*

Smooth tuning is a great convenience to the operator, and can be obtained by taking pains with the mounting of the dial and tuning condensers. They should have good alignment and no back-lash. If the condensers are mounted off the chassis on posts instead of brackets, it is almost impossible to avoid some back-lash unless the posts have extra-wide bases. The condensers should be selected with good wiping contacts to the rotor, since with age the rotor contacts can be a source of erratic tuning. All joints in the oscillator tuning circuit should be carefully soldered, since a loose connection or "rosin joint" can develop trouble that is sometimes hard to locate.

## Servicing Superhet Receivers

### *I.F. Alignment*

A calibrated signal generator or test oscillator is a very useful device for initial alignment of an i.f. amplifier. Some means for measuring the output of the receiver is required. If the receiver has a tuning meter, its indications will serve the purpose. Lacking an S-meter, a high-resistance voltmeter or preferably a vacuum-tube voltmeter can be connected across the second-detector load resistor, if the second detector is a diode. Alternatively, if the signal generator is a modulated type, an a.c. voltmeter can be connected across the primary of the transformer feeding the speaker, or from the plate of the last audio amplifier through a 0.1- $\mu$ f. blocking condenser to the receiver chassis. Lacking an a.c. voltmeter, the audio output can be judged by ear, although this method is not as accurate as the others. If the

tuning meter is used as an indication, the a.v.c. of the receiver should be turned on, but any other indication requires that it be turned off. Lacking a test oscillator, a steady carrier tuned through the input of the receiver (if the job is one of just touching up the i.f. amplifier) will be suitable. However, with no oscillator and tuning an amplifier for the first time, one's only recourse is to try to peak the i.f. transformers on "noise," a difficult task if the transformers are badly off resonance, as they are apt to be. It would be much better to spend a little time and haywire together a simple oscillator for test purposes.

Initial alignment of a new i.f. amplifier is as follows: The test oscillator is set to the correct frequency, and its output is connected to the grid of the last i.f. amplifier tube and to the chassis. The trimmer condensers of the transformer feeding the second detector are then

adjusted for maximum output, as shown by the indicating device being used. The oscillator output lead is then clipped on to the grid of the next-to-the-last i.f. amplifier tube, and the second-from-the-last transformer trimmer adjustments are peaked for maximum output. This process is continued, working back from the second detector, until all of the i.f. transformers have been aligned. It will be necessary to reduce the output of the test oscillator as more of the i.f. amplifier is brought into use, because the increased gain is likely to cause overloading and consequent inaccurate adjustments. It is desirable in all cases to use the minimum oscillator signal that will give useful output readings. The i.f. transformer in the plate circuit of the mixer is aligned with the signal introduced to the grid of the mixer. Since the tuned circuit feeding the mixer grid may have a very low impedance at the i.f., it may be necessary to boost the test generator output or to disconnect the circuit temporarily from the mixer grid.

If the i.f. amplifier has a crystal filter, the filter should first be switched out and the alignment carried out as above, setting the test oscillator as closely as possible to the crystal frequency. When this is completed, the crystal should be switched in and the oscillator frequency varied back and forth over a small range either side of the crystal frequency to find the exact frequency, as indicated by a sharp rise in output. Leaving the test oscillator set on the crystal peak, the i.f. trimmers should be realigned for maximum output. The necessary readjustment should be small. The oscillator frequency should be checked frequently to make sure it has not drifted from the crystal peak.

A modulated signal is not of much value for aligning a crystal-filter i.f. amplifier, since the high selectivity cuts sidebands and the results may be inaccurate if the audio output is used as the tuning indication. Lacking the a.v.c. tuning meter, the transformers may be conveniently aligned by ear, using a weak unmodulated signal adjusted to the crystal peak. Switch on the beat oscillator, adjust to a suitable tone, and align the i.f. transformers for maximum audio output.

An amplifier that is only slightly out of alignment, as a result of normal drift or aging, can be realigned by using any steady signal, such as a local broadcast station, instead of the test oscillator. One's 100-ke. standard makes an excellent signal source for "touching up" an i.f. amplifier. Allow the receiver to warm up thoroughly, tune in the signal, and trim the i.f. for maximum output.

If you bought your receiver instead of making it, be sure to read the instruction book carefully before attempting to realign the receiver. Most instruction books include alignment details, and any little special tricks that are peculiar to that particular type of receiver will also be described.

### R.F. Alignment

The objective in aligning the r.f. circuits of a gang-tuned receiver is to secure adequate tracking over each tuning range. The adjustment may be carried out with a test oscillator of suitable frequency range, with harmonics from your 100-ke. standard or other known oscillator, or even on noise or such signals as may be heard. First set the tuning dial at the high-frequency end of the range in use. Then set the test oscillator to the frequency indicated by the receiver dial. The test-oscillator output may be connected to the antenna terminals of the receiver for this test. Adjust the oscillator trimmer condenser in the receiver to give maximum response on the test-oscillator signal, then reset the receiver dial to the low-frequency end of the range. Set the test-oscillator frequency near the frequency indicated by the receiver dial and carefully tune the test oscillator until its signal is heard in the receiver. If the frequency of the signal as indicated by the test-oscillator calibration is higher than that indicated by the receiver dial, more inductance (or more capacity in the tracking condenser) is needed in the receiver oscillator circuit; if the frequency is lower, less inductance (less tracking capacity) is required in the receiver oscillator. Most commercial receivers provide some means for varying the inductance of the coils or the capacity of the tracking condenser, to permit aligning the receiver tuning with the dial calibration. Set the test oscillator to the frequency indicated by the receiver dial, and then adjust the tracking capacity or inductance of the receiver oscillator coil to obtain maximum response. After making this adjustment, recheck the high-frequency end of the scale as previously described. It may be necessary to go back and forth between the ends of the range several times before the proper combination of inductance and capacity is secured. In many cases, better over-all tracking will result if frequencies near but not actually at the ends of the tuning range are selected, instead of taking the extreme dial settings.

After the oscillator range is properly adjusted, set the receiver and test oscillator to the high-frequency end of the range. Adjust the mixer trimmer condenser for maximum hiss or signal, then the r.f. trimmers. Reset the tuning dial and test oscillator to the low-frequency end of the range, and repeat; if the circuits are properly designed, no change in trimmer settings should be necessary. If it is necessary to increase the trimmer capacity in any circuit, it indicates that more inductance is needed; if less capacity resonates the circuit, less inductance is required.

Tracking seldom is perfect throughout a tuning range, so that a check of alignment at intermediate points in the range may show it to be slightly off. Normally the gain variation from this cause will be small, however, and it

will suffice to bring the circuits into line at both ends of the range. If most reception is in a particular part of the range, such as an amateur band, the circuits may be aligned for maximum performance in that region, even though the ends of the frequency range as a whole may be slightly out of alignment.

#### **Oscillation in R.F. or I.F. Amplifiers**

Oscillation in high-frequency amplifier and mixer circuits may be evidenced by squeals or "birdies" as the tuning is varied, or by complete lack of audible output if the oscillation is strong enough to cause the a.v.c. system to reduce the receiver gain drastically. Oscillation can be caused by poor connections in the common ground circuits. Inadequate or defective by-pass condensers in cathode, plate and screen-grid circuits also can cause such oscillation. A metal tube with an ungrounded shell will cause trouble. Improper screen-grid voltage, resulting from a shorted or too-low screen-grid series resistor, also may be responsible for such instability.

Oscillation in the i.f. circuits is independent of high-frequency tuning, and is indicated by a continuous squeal that appears when the gain is advanced with the c.w. beat oscillator on. It can result from defects in i.f.-amplifier circuits similar to those above. Inadequate cathode by-pass capacitance is a common cause of such oscillation. An additional by-pass condenser of 0.1 to 0.25  $\mu$ f. often will remedy the trouble. Similar treatment can be applied to the screen-grid and plate by-pass filters of i.f. stages.

#### **Instability**

"Birdies" or a mushy hiss occurring with tuning of the high-frequency oscillator may indicate that the oscillator is "squegging" or oscillating simultaneously at high and low

frequencies. This may be caused by a defective tube, too-high oscillator plate or screen-grid voltage, excessive feed-back, or too-high grid-leak resistance.

A varying beat-note in c.w. reception indicates instability in either the h.f. oscillator or beat oscillator, usually the former. The stability of the beat oscillator can be checked by introducing a signal of intermediate frequency (from a test oscillator) into the i.f. amplifier; if the beat-note is unstable, the trouble is in the beat oscillator. Poor connections or defective parts are the likely cause. Instability in the high-frequency oscillator may be the result of poor circuit design, loose connections, defective tubes or circuit components, or poor voltage regulation in the oscillator plate-and/or screen-supply circuits. Mixer pulling of the oscillator circuit also will cause the beat-note to "chirp" on strong c.w. signals because the oscillator load changes slightly.

In 'phone reception with a.v.c., a peculiar type of instability ("motorboating") may appear if the h.f.-oscillator frequency is sensitive to changes in plate voltage. As the a.v.c. voltage rises the electrode currents of the controlled tubes decrease, decreasing the load on the power supply and causing its output voltage to rise. Since this increases the voltage applied to the oscillator, its frequency changes correspondingly, throwing the signal off the peak of the i.f. resonance curve and reducing the a.v.c. voltage, thus tending to restore the original conditions. The process then repeats itself, at a rate determined by the signal strength and the time constant of the power-supply circuits. This effect is most pronounced with high i.f. selectivity, as when a crystal filter is used, and can be cured by making the oscillator relatively insensitive to voltage changes and by regulating the plate-voltage supply.

## **Narrow-Band Frequency- and Phase-Modulation Reception**

The only FM (frequency modulation) and PM (phase modulation) in general use on the frequencies below 30 Mc. is of the "narrow-band" variety, in which the channel width of the signal is no greater than that of an AM signal. Normal wide-band FM (and PM) receiving techniques, which involve the use of limiter and discriminator circuits, are not generally applicable to the reception of narrow-band FM (and PM), and most amateurs use their regular communications receivers with no modification.

#### **FM Reception**

In the reception of FM signals by a normal communications receiver, the a.v.c. is switched off and the incoming signal is not tuned "on the nose," as indicated by maximum reading

of the S-meter, but slightly off to one side or the other. This puts the carrier of the incoming signal on one side or the other of the i.f. selectivity characteristic (see Fig. 5-1). As the frequency of the signal changes back and forth over a small range with modulation, these variations in frequency are translated to variations in amplitude, and the consequent AM is detected in the normal manner. The signal is tuned in (on one side or the other of maximum carrier strength) until the audio quality appears to be best. The audio output from the signal depends on the *slope* of the i.f. characteristic and the amount of *swing* (deviation) of the signal. If the audio is too weak, the transmitting operator should be advised to increase his swing slightly, and if the audio quality is bad ("splashy" and with serious dis-

tortion on volume peaks) he should be advised to reduce his swing. Coöperation between transmitting and receiving operators is a necessity for best audio quality. The transmitting station should always be advised immediately if at any time his bandwidth exceeds that of an AM signal, since this is a violation of the FCC regulations, except in those portions where wide-band FM is permitted.

#### ***PM Reception***

PM signals can be received in the same way that NFM (narrow-band FM) signals are, except that in this case the audio output will appear to be lacking in "lows," because of the differences in the deviation-*vs.*-audio characteristics of the two systems. This can be remedied to a considerable degree by advancing the tone control of the receiver to the point

where more nearly normal speech output is obtained.

NPM signals can also be received on communications receivers by making use of the crystal filter, in which case there is no need for audio compensation. The crystal filter should be set to the sharpest position and the carrier should be tuned in on the crystal peak, *not* set off to one side. The phasing condenser should be set not for exact neutralization but to give a rejection notch at some convenient side frequency such as 1000 cycles off resonance. There is considerable attenuation of the side bands with such tuning, but it is not *selective* attenuation except for the added selectivity of the i.f. amplifier, and it can readily be overcome by using additional audio gain. FM signals received through the crystal filter in this fashion will have a "boomy" characteristic because the lower frequencies are accentuated.

# High-Frequency Transmitters

A transmitter for the low-frequency amateur bands (4 to 30 Mc.) consists essentially of an oscillator and usually, but not always, one or more amplifiers, one of which feeds radio-frequency power to the antenna or transmission line.

The oscillator, fed by a source of d.c. power, such as rectified 60-cycle house current, a d.c.

generator or batteries, serves to generate a relatively small amount of power at a selected radio frequency. The amplifiers perform the function of increasing the r.f. power at that frequency, or a multiple of it, to the level desired before feeding it to the antenna system. In other words, a transmitter is a device that converts d.c. power to power at radio frequencies. Several typical transmitter arrangements are shown in the diagrams of Fig. 6-1. At A, the oscillator feeds directly into the antenna. At B, the output of the oscillator is fed to an amplifier which feeds the antenna. In the arrangements of C, D and E, the oscillator output is fed to a frequency-multiplying amplifier which doubles the frequency before passing the energy along to the next stage. As the diagram indicates, it is often possible to operate more than one transmitter stage from a single power supply.

In a telegraph (c.w.) transmitter, means is provided for breaking the transmitted energy up into the characters of the Continental (International Morse) code. In 'phone transmitters, power at audio voice frequencies is combined with the d.c. input so as to superimpose (modulate) those frequencies on the steady r.f. output (carrier) from a transmitter which otherwise is essentially the same as that most often used for telegraphy.

To minimize interference when a large number of stations must work in one frequency band, the power output of a transmitter must be as stable in frequency and as free from spurious radiations as the state of the art permits. The steady r.f. output must be free from amplitude variations attributable to ripple from the plate power supply or other causes, its frequency should be unaffected by variations in supply voltages or inadvertent changes in circuit constants, and there should be no radiation on other than the intended frequency which might cause interference to other radio services.

The design of any particular transmitter is based primarily upon the power-output level desired and the number of bands to be covered and their frequencies. Added to these are the factors of operating convenience and space restrictions. Portable and mobile equipment require special consideration in design.

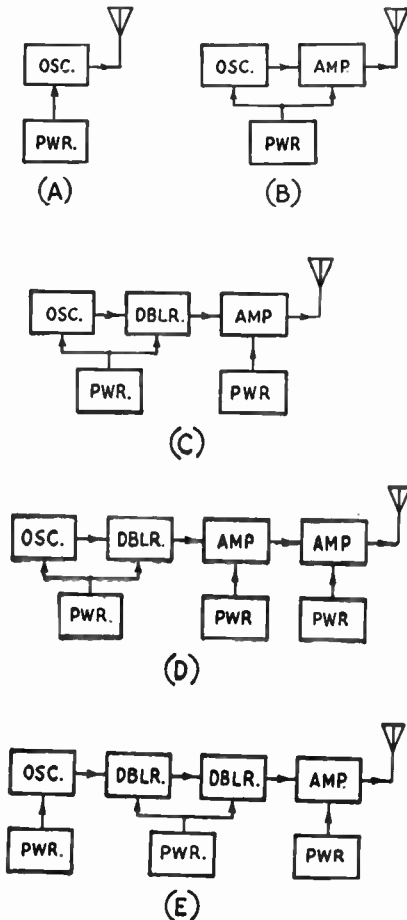


Fig. 6-1 — Block diagrams showing typical combinations of oscillator and amplifiers and power-supply arrangements for transmitters. A wide selection is possible depending upon the number of bands in which operation is desired and the power output.

## Variable-Frequency Oscillators

Two general classes of oscillators are used in amateur transmitters. A crystal-controlled oscillator is a fixed-frequency oscillator. The frequency generated is held within very close limits (a few cycles per megacycle) by a quartz crystal. The frequency is determined almost entirely by the thickness of the crystal. Other constants in the circuit have relatively little effect. The frequency of a self-controlled or variable-frequency oscillator (VFO) is determined principally by the values of inductance and capacitance which make up the oscillator tank circuit.

The disadvantage of the crystal type of oscillator is that a different crystal must be used for each frequency desired in any one amateur band. By making the inductance, capacitance, or both variable in the self-controlled oscillator, it may be operated at any frequency desired at the turn of a dial, in the manner of a receiver. The disadvantage of a VFO is that much care must be exercised in the design and construction if the frequency stability is to approach that of a crystal-controlled oscillator.

Although the trend in recent years has been toward the VFO with its greater flexibility, the crystal oscillator still is widely used by beginners and in certain types of operation because of the ease with which frequency stability and calibration may be maintained.


### ● VFO CIRCUITS

#### *Tickler-Feed-Back Circuit*

Fig. 6-2 shows several types of self-controlled oscillator circuits. In the tickler-feed-back circuit of A, the frequency is determined principally by the values of  $C_1$  and  $L_1$ . Feed-back is provided by the coupling between  $L_1$  and  $L_2$ . It may be adjusted by varying the number of turns in  $L_2$  or by changing the coupling between  $L_1$  and  $L_2$ . When connected as shown, the two coils must be wound in the same direction. If they are wound in opposite directions, the connections to one of the coils must be reversed.

#### *T.G.T.P. Oscillator*

In the tuned-grid tuned-plate (t.g.t.p.) circuit of Fig. 6-2B, the  $L_1C_1$  tank has the higher  $Q$  because of the relatively high value of  $C_1$ . Therefore it forms the principal control over frequency.  $L_3C_2$  is used primarily for adjustment of feed-back, although its effect upon frequency is considerable. Feed-back is through the plate-grid capacitance of the tube.  $L_1$

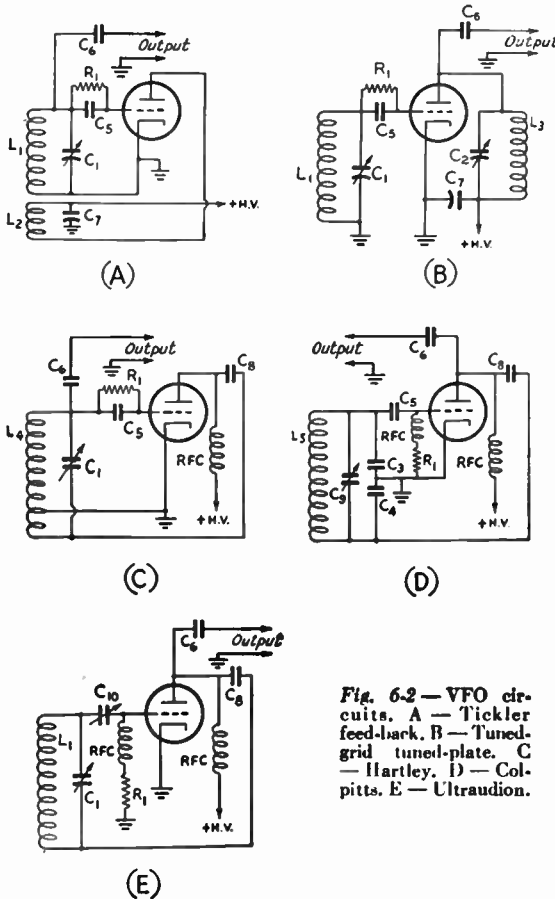

**Fig. 6-2 — VFO circuits. A — Tickler feed-back. B — Tuned-grid tuned-plate. C — Hartley. D — Colpitts. E — Ultraudion.**

- Approximate values are as follows:
- $C_1$  — Tank tuning condenser. For 3.5 Mc. — 500  $\mu\text{fd.}$  or more total, including any fixed capacitance which may be used for handsread purposes.
  - $C_2$  — Plate tank condenser — 100- $\mu\text{fd.}$  variable.
  - $C_3$  — Tank condenser — 0.003- $\mu\text{fd.}$  mica for 3.5 Mc.
  - $C_4$  — Tank condenser — 0.001- $\mu\text{fd.}$  mica for 3.5 Mc.
  - $C_5$  — Grid condenser — 100  $\mu\text{fd.}$  or less, mica.
  - $C_6$  — Output coupling condenser — 100  $\mu\text{fd.}$  or less, mica.
  - $C_7$  — Plate by-pass condenser — 0.01- $\mu\text{fd.}$  paper.
  - $C_8$  — Plate blocking condenser — 0.001- $\mu\text{fd.}$  mica.
  - $C_9$  — Tuning condenser — 250- $\mu\text{fd.}$  variable.
  - $C_{10}$  — Grid condenser — 100  $\mu\text{fd.}$  or less, variable.
  - $R_1$  — Grid leak — 50,000 ohms.
  - $L_1$  — Tank coil — 4.3  $\mu\text{hy.}$  for 3.5 Mc. with 500  $\mu\text{fd.}$
  - $L_2$  — Tickler winding — approximately one-third the number of turns in  $L_1$ , wound over bottom portion of  $L_1$  or adjacent to it.
  - $L_3$  — Plate tank coil — 22  $\mu\text{hy.}$  for 3.5 Mc. with 100- $\mu\text{fd.}$  condenser.
  - $L_4$  — Tank coil — same as  $L_1$ , tapped approximately one-third from plate end.
  - $L_5$  — Tank coil — 3.3  $\mu\text{hy.}$  for 3.5 Mc. with capacitance values given for  $C_3$ ,  $C_4$  and  $C_9$ .
  - RFC — Parallel-feed r.f. choke — 2.5 mh.

and  $L_3$  are not coupled. For positive feedback,  $L_3C_2$  must be tuned to a frequency higher than that of  $L_1C_1$ . Maximum feedback occurs when the two circuits are tuned close (but not exactly) to the same frequency. Power output is taken from the plate tank circuit,  $L_3C_2$ .

### Hartley

The Hartley circuit of Fig. 6-2C is quite similar to the tickler-feed-back circuit of A, except that the tank condenser is connected across both plate and grid portions of a single winding. The frequency is determined principally by the values of  $L_4$  and  $C_1$ . Feed-back may be adjusted by moving the cathode tap which is the r.f. ground point.

### Colpitts

The Colpitts circuit of Fig. 6-2D also is similar, the principal difference being that the voltage division between the grid and plate portions of the circuit is by capacitive means rather than inductive. Frequency is determined chiefly by the values of  $L_5$ , and the resultant of  $C_3$  and  $C_4$  in series and  $C_9$  in parallel. Feed-back may be adjusted by changing the ratio of  $C_3$  to  $C_4$ ,  $C_9$  being used to adjust frequency.

### Ultraudion

A variation of the Colpitts is the ultraudion circuit of Fig. 6-2E. The grid-cathode and plate-cathode capacitances of the tube serve as the capacitive voltage divider. The circuit is tuned to the desired frequency by  $C_1$ . Feed-back may be adjusted within limits by alteration of the value of the grid coupling condenser,  $C_{10}$ . (See "Frequency-Multiplying Oscillators" this chapter for additional VFO circuits.)

### Push-Pull VFO Circuits

Two tubes may be used in push-pull in an oscillator. The two tubes provide an increase in power output over that obtainable from a single tube. Since they are effectively in series across the tuned circuit, their effect on frequency stability is less than that of a single tube. So far as tube effects are concerned, the same order of stability may be obtained with half the total capacitance in the tank circuit required for a single tube.

The Hartley and tickler-feed-back circuits lend themselves most readily to a push-pull arrangement, as shown in Fig. 6-3. In the Hartley of A, excitation may be adjusted by moving the grid taps, keeping them in positions symmetrical in respect to the center-tap. In the tickler-feed-back circuit of B, excitation is adjusted by changing the number of turns in  $L_3$ , keeping the number of turns equal either side of the center-tap.  $L_3$  should be wound over the center portion of  $L_2$ .

Capacitance coupling may be used if a push-

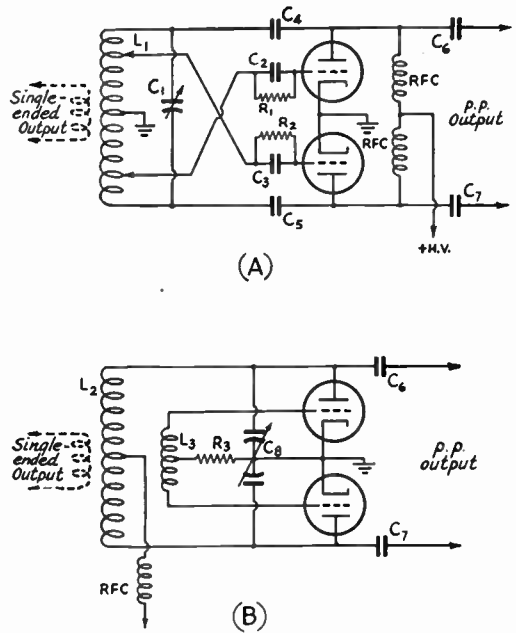


Fig. 6-3—Push-pull VFO circuits. A—Hartley. B—Tickler feed-back.

Approximate values are as follows:

- $C_1$ —Tank condenser—500  $\mu\text{fd}$ . total, including any fixed capacitance used for bandspread purposes, for 3.5 Mc.
- $C_2, C_3$ —Grid condenser—100  $\mu\text{fd}$ . or less, mica.
- $C_4, C_5$ —Plate blocking condenser—0.001- $\mu\text{fd}$ . mica.
- $C_6, C_7$ —Output coupling condenser—100  $\mu\text{fd}$ . or less, mica.
- $C_8$ —Tank condenser—500  $\mu\text{fd}$ . per section, including any fixed capacitance used for bandspread purposes, for 3.5 Mc.
- $R_1, R_2$ —Grid leak—50,000 ohms.
- $R_3$ —Grid leak—25,000 ohms.
- $L_1$ —Tank coil—4.3  $\mu\text{hy}$ ., tapped at center, for 3.5 Mc., and 500  $\mu\text{fd}$ .
- $L_2$ —Tank coil—8.6  $\mu\text{hy}$ ., tapped at center, for 3.5 Mc., and 250  $\mu\text{fd}$ . total across coil.
- $L_3$ —Tickler coil—approximately one-third number of turns in  $L_2$ , tapped at center, wound over center of  $L_2$  or between halves of  $L_2$ .
- RFC—R.f. choke—2.5 mh.

pull oscillator is to feed a push-pull amplifier, but inductive coupling, which assures a better circuit balance, is preferable if the oscillator is to be coupled to a single-tube amplifier. (See "Interstage Coupling" this chapter.)

(See "Frequency-Multiplying Oscillators" this chapter for additional VFO circuits.)

### Factors in VFO Design and Construction

To provide satisfactory performance on the air, considerable care must be exercised in the design and construction of a VFO. Since the frequency depends upon the  $L$  and  $C$  in the circuit, anything which operates to change these values will cause a change in frequency. For stability which will approach that of which a crystal oscillator is capable, the values of inductance and capacitance must be held within extremely small tolerances.

It is not too difficult to provide a satisfactory



coil and condenser for the tank circuit. But the tube must be connected across this circuit and its effect upon frequency is by no means negligible nor easily controlled. The tube has the effect of a capacitance which can be made to hold satisfactorily constant only with great care. It is obvious too that the connection of any reactive load, such as an antenna or the input of an amplifier stage, will change the frequency, since this load must be connected across the frequency-determining circuit, thereby changing the net value of inductance or capacitance as the case may be. An antenna and feeders cannot be held sufficiently rigid to prevent changes in their capacitance. Under practical operating conditions the input circuit of an amplifier may develop changes in the reactance which it presents across the oscillator circuit, especially while it is being tuned or alternately connected and disconnected, which it is in effect if the amplifier is keyed. Isolating amplifiers (see "R.F. Power Amplifiers" this chapter) can be used to reduce these effects.

#### Chirp

Variations in the plate voltage of the oscillator tube cause changes of appreciable magnitude in the effective input capacitance of the tube. If the oscillator can be run continuously during transmission, this effect can be made negligible by the use of a regulated plate-voltage supply. But if the oscillator must be keyed for break-in work, an objectionable shift in frequency with keying (*chirp*) can be avoided only by reducing the time constant of the keying circuit to the point where the change in frequency between zero-voltage and full-voltage conditions takes place so rapidly that the ear cannot detect it. The time constant is reduced by minimizing any capacitance which may appear across the key contacts, including by-pass condensers in the transmitter. Unfortunately, as discussed in Chapter Eight, a certain time lag is required to eliminate clicks. Therefore the measures necessary for the elimination of chirps and clicks are in opposition. A compromise is usually necessary. It is possible that the keying of an amplifier may constitute little improvement over oscillator keying, for reasons previously given, unless sufficient isolation is provided between the oscillator and the keyed stage.

#### Drift

The effects of temperature are characterized by a slow drift or creep in frequency. Part of this change, especially for the first few minutes after power is applied to the oscillator, may be attributable to change in tube-electrode capacitance as the tube heats up. But over a protracted period of time, drift is a result of small changes with temperature in physical dimensions of the coil and condenser in the tank circuit. Good design dictates that these components be isolated as much as possible from the heat developed in the tubes and power-supply

equipment. With care, frequency drift can be brought within satisfactory limits by mounting the tubes external to the enclosure surrounding the tank coil and condensers and the use of zero-temperature mica condensers for all tank capacitance other than that required for tuning purposes, by providing ventilation and by keeping the power input to the oscillator at a minimum — not more than a few watts. Where maximum stability with temperature change is desired, temperature-compensating condensers may be used to form part of the tank-circuit capacitance.

#### Mechanical Considerations

Any mechanical vibration which causes a change in the capacitance across the tank circuit will cause a corresponding change in frequency. This should be minimized by solid construction, secure wiring and by cushioning the mounting of the oscillator unit against shocks. The oscillator should be thoroughly shielded from the strong r.f. fields of the antenna and adjacent high-power amplifier stages which may, through overloading of the oscillator grid, cause roughening of the oscillator signal.

#### VFO Tank Capacitance and Tuning Systems

All of the previously-mentioned effects upon the frequency of an oscillator may be minimized by the use of high capacitance in the tank circuit, thus making uncontrollable capacitance changes a small percentage of the total circuit capacitance. The same effect can be obtained by tapping the tube elements across only a portion of the circuit, as shown in Fig. 6-4, so that the tube capacitance shunts only a part of the tank circuit. A tube of low or medium amplification factor is preferable as an oscillator because changes in loading — tuning of the output circuit of the oscillator or following amplifier stages as well as plate-voltage variations — have less influence upon the effective input capacitance of the tube than with a high- $\mu$  tube.

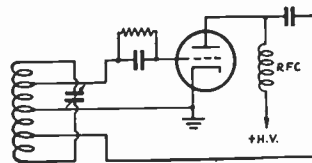


Fig. 6-4 — Oscillator tubes are sometimes connected across only a portion of the tank coil to reduce the effects of the tube on the tuned circuit. In this Hartley circuit, the grid and plate connections are made to taps instead of to the ends of the coil.

Because it is considered easier to maintain percentage stability at lower frequencies, VFOs usually are designed to operate at a frequency not higher than the 3.5-Mc. band, the higher-frequency bands being reached by frequency-multiplier stages which are discussed under

"Frequency-Multiplying Amplifiers." At 3.5 Mc., a tank capacitance of 500 to 1000  $\mu\text{mfd.}$  is considered adequate, with values increased in proportion if the oscillator is designed to operate at lower frequencies.

Any of the bandsread tuning systems used in receivers may be applied to the oscillator circuits which have been under discussion. The parallel-condenser system is used most widely since it lends itself well to the high- $C$  circuits which should be used in VFOs. Plug-in coils for changing oscillator frequency ranges are not recommended because experience has shown that the coil contacts may become the source of frequency instability.

## ● VFO ADJUSTMENT

### Tuning Characteristics

With the exception of the t.g.t.p., all normally-operating VFO circuits will function quite uniformly, over the range of an amateur band at least, as soon as plate voltage is applied. If, through incorrect adjustment of excitation or overloading the circuit does not oscillate, the plate current will be the zero-bias value for the tube at the plate voltage at which it is being operated, falling to a lower value when oscillation takes place. If the oscillator is functioning, touching the grid with the finger will cause a variation in plate current. The value of plate current to be expected with a given tube when oscillating depends upon such factors as plate voltage, grid-leak resistance, excitation adjustment and loading. It should remain essentially constant with reasonable changes in tuning capacitance. With normal excitation adjustment, the plate current should show an increase when the load is connected. Excitation and grid-leak resistance should be adjusted for maximum frequency stability — not maximum output.

With the t.g.t.p. circuit, oscillation takes place only when the plate tank circuit is tuned to a frequency higher than that to which the grid circuit is tuned, and maximum output usually occurs when the two are tuned close (but not exactly) to the same frequency. If the plate tuning condenser has sufficient range to tune the circuit to a frequency lower than that of the grid circuit, oscillation will cease and the plate current will be relatively high, as shown at the left in Fig. 6-5. As the plate circuit is tuned past the point of resonance with the grid circuit in the high-frequency direction, the plate current will drop suddenly (point *A*) indicating the starting of oscillation, then dip rapidly to a minimum (point *C*) where the power output is greatest. As the tuning capacitance is decreased further, the plate current will rise gradually to point *B* where it will jump to a higher value, indicating that oscillation has ceased. For maximum frequency stability, the circuit should be tuned in the region *D-E*.

When the oscillator is loaded, the characteristic is similar (see dashed curve in Fig. 6-5),

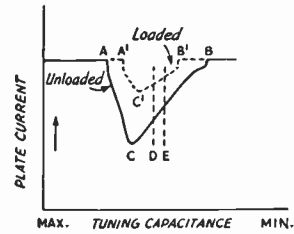


Fig. 6-5 — General tuning characteristic of the t.g.t.p. VFO circuit and triode, tetrode or pentode crystal oscillators. As the capacitance of the plate tank condenser is decreased from maximum, oscillation will start suddenly, the plate current dropping abruptly, as shown at point *A*. As the capacitance is decreased further, the plate current will dip to a minimum, *C*, and then gradually rise to point *B* where an abrupt rise in plate current will indicate that oscillation has ceased. Maximum output will be obtained at point *C*, but the oscillator should be adjusted for operation in the *D-E* region for best frequency stability.

but the minimum plate-current dip is much less pronounced and the range of plate tuning over which the circuit will oscillate becomes less as the loading is increased.

If the oscillator is delivering sufficient power, an r.f. indicator should show maximum r.f. voltage at the grid and plate terminals and decrease to zero voltage at the cathode in all of the circuits shown in Fig. 6-2. The Hartley circuit of Fig. 6-2C, the Colpitts of *D* and the ultraudion circuit of *E* have the disadvantage in construction that the tuning control (tuning-condenser rotor shaft) must be insulated.

### Checking VFO Stability

A VFO should be checked thoroughly before it is placed in regular operation on the air. Since succeeding amplifier stages may affect the signal characteristics, final tests should be made with the complete transmitter in operation. Almost any VFO will show signals of good quality and stability when it is running free and not connected to a load. A well-isolated monitor is a necessity. Perhaps the most convenient, as well as one of the most satisfactory, monitoring arrangements is a well-shielded receiver combined with a crystal oscillator. (See "Crystal Oscillators.") The crystal frequency should lie in the band of the lowest frequency to be checked and in the frequency range where its harmonics will fall in the higher-frequency bands. The receiver b.f.o. is turned off and the VFO signal is tuned to beat with the signal from the crystal oscillator instead. In this way any receiver instability caused by overloading of the input circuits which may result in "pulling" of the h.f. oscillator in the receiver, or by a change in line voltage to the receiver when the transmitter is keyed, will not affect the reliability of the check. Most present-day crystals have a sufficiently-low temperature coefficient to give a satisfactory check on drift as well as on chirp and signal quality if they are not overloaded.

Harmonics of the crystal may be used to

beat with the transmitter signal when monitoring at the higher frequencies. Since any chirp observed at the lower frequencies will be magnified at the higher frequencies, most-accurate checking can be done by monitoring at the higher frequencies.

The distance between the crystal oscillator and receiver should be adjusted to give a good beat between the crystal oscillator and the transmitter signal. When using harmonics of the crystal oscillator, it may be necessary to

attach a piece of wire to the oscillator as an antenna to give sufficient signal in the receiver.

Checks may show that the stability is sufficiently good to permit oscillator keying at the lower frequencies, where break-in operation is of greater value, but that chirp becomes objectionable at the higher frequencies. If further improvement does not seem possible, it would be logical in this case to use oscillator keying at the lower frequencies and amplifier keying at the higher frequencies.

## Crystal Oscillators

### ● SIMPLE CIRCUITS

The simplest crystal-controlled oscillator circuits are shown in Fig. 6-6. Since the crystal is the equivalent of a tuned circuit of fixed frequency, it will be observed that each of the crystal circuits is essentially the equivalent of one of the VFO circuits of Fig. 6-2.

#### Triode, Tetrode and Pentode Oscillators

The triode crystal circuit of Fig. 6-6A is the equivalent of the t.g.t.p. circuit in which the crystal replaces the tuned grid circuit. The pentode circuit of B is the same except for the substitution of a screen-grid tube for the triode. This circuit sometimes is operated with the suppressor by-passed and raised to a positive voltage of about 50 instead of grounded as shown. The same circuit is used for tetrodes, such as the 6V6 and 6L6, the suppressor connection being omitted. Tuning characteristics are similar to those of the t.g.t.p. circuit shown in Fig. 6-5.

#### Pierce Oscillator

The circuit shown in Fig. 6-6C is known as the Pierce circuit. It is the equivalent of the ultraudion variation of the Colpitts. The crystal replaces the single tuned circuit and thus this oscillator requires no tuning adjustment and will work without change in values over a wide range of crystal frequencies. Since excitation otherwise is not adjustable, the condenser  $C_5$  sometimes is required to obtain satisfactory operation. Less power is obtainable from the Pierce circuit than from the others because the crystal is directly in the power-delivering circuit which limits the r.f. voltage that may be developed without danger to the crystal. Triodes also may be used in this circuit. (See "Frequency-Multiplying Oscillators" this chapter for additional crystal-oscillator circuits.)

### ● POWER LIMITATIONS OF CRYSTALS

Although high-power crystal oscillators sometimes are used in cases where utmost simplicity must be the paramount consideration, the oscillator normally should be considered as a frequency-generating device only, with power output of secondary importance.

While crystal-controlled oscillators are much more tolerant than VFOs in respect to temperature changes, the danger of crystal fracture, as well as drift, places a limitation on the amount of power output obtainable. With the

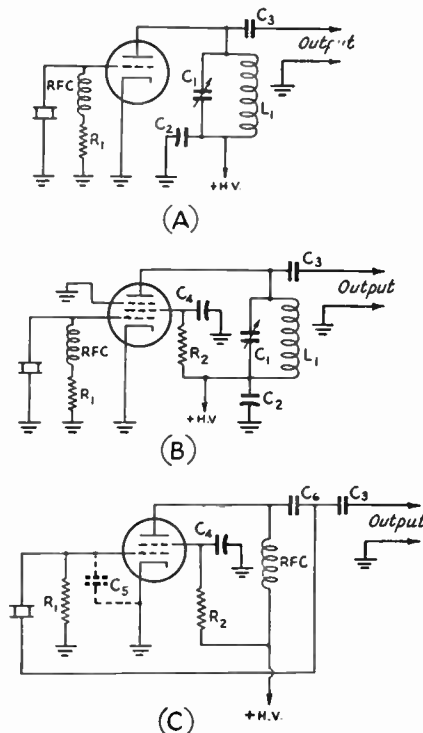


Fig. 6-6 — Simple crystal-oscillator circuits. A — Triode. B — Tetrode or pentode. C — Tetrode Pierce. Other crystal-oscillator circuits are shown in Fig. 6-18.

Approximate values are as follows:

- $C_1$  — Tank condenser — 100- $\mu$ fd. variable.
- $C_2$  — Plate by-pass condenser — 0.01- $\mu$ fd. paper.
- $C_3$  — Output coupling condenser — 100  $\mu$ fd. or less, mica.
- $C_4$  — Screen by-pass condenser — 0.01- $\mu$ fd. paper.
- $C_5$  — Feed-back condenser — 50 to 100  $\mu$ fd.
- $C_6$  — Plate blocking condenser — 0.001- $\mu$ fd. mica.
- $R_1$  — Grid leak — 50,000 ohms.
- $R_2$  — Screen voltage-dropping resistor — 25,000 to 50,000 ohms.
- $L_1$  — Tank coil — 22  $\mu$ hy. for 3.5 Mc.; 7.5  $\mu$ hy. for 7 Mc.
- RFC — Parallel-feed r.f. choke — 2.5 mh.

large prewar-type crystals, triode crystal oscillators may be operated with proper adjustment at plate voltages as high as 200 or 250, but the voltage should be reduced to 150 to 200 for the new-type smaller crystals. Low- or medium- $\mu$  triodes are preferable as oscillators. Beam tetrodes or pentodes, with their high power-sensitivity and reduced grid-plate capacitance, require less voltage across the crystal than a triode for the same amount of output. Therefore the larger-type crystals can be operated with plate voltages of 300 or 400 with power output up to 10 or 15 watts if required. The smaller crystals may take plate voltages up to 300 or 325 before showing marked instability. However, as stated previously, it is always advisable to limit the input to the oscillator and depend upon amplifiers for the desired power.

With the simple crystal-oscillator circuits shown in Fig. 6-6, excitation, and therefore r.f. voltage across the crystal, is greatest when the oscillator is unloaded and it is under this condition that danger to the crystal is greatest.

### ● GRINDING CRYSTALS

Crystal blanks, cut to approximate frequency, are available at very reasonable prices. With proper equipment and a little care, these blanks can be ground to the desired frequency. Complete crystal-grinding equipment includes several components. First necessity is a flat piece of plate glass, about 4 inches square or larger. To hold the crystal flat while grinding a flat "button" (shown in Fig. 6-7), also of plate glass, either round or square and slightly larger than the crystal, is required. Both pieces may be obtained at glass stores. Two grades of abrasive, No. 303 emery for surface grinding and No. 600 Carborundum for edge grinding

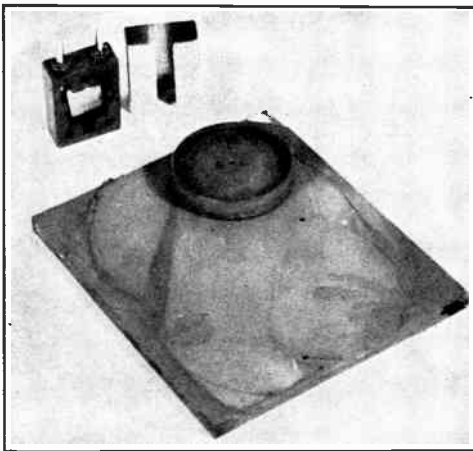


Fig. 6-7—The equipment necessary for grinding a crystal blank to frequency. A piece of plate glass and a "button" of the same material are essential. The "quick-change" adaptation for the crystal holder is a convenience. Not shown, but also convenient, are a small paint brush for spreading abrasive and a toothbrush for scrubbing.

and beveling are obtainable from hardware stores or opticians'-supply houses. A small paint brush is handy for moistening the abrasive and spreading it around the lapping plate. To facilitate frequent checking of frequency during the grinding process, the quick-change holder shown in Fig. 6-8 is desirable. It consists of an FT243 holder with a sliding cover fashioned from sheet metal. Soap, warm water and a toothbrush are used to clean and rinse

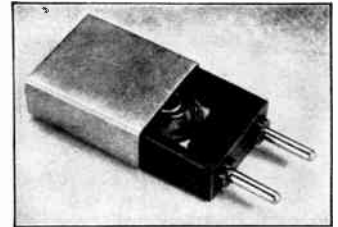


Fig. 6-8—The quick-change crystal holder with sliding cover.

the crystal. Lintless cloth from an optician's or a clean towel can be used for drying.

Present-day electrodes have raised lands on each corner, as shown in Fig. 6-9, and the crystal should lie at least halfway across these lands and should not be larger than the electrode. The electrodes should be cleaned as carefully as the crystal. Before final assembly both crystal and electrodes should be handled carefully by the corners or edges after their last good scrubbing.

### How To Grind

The actual grinding is done as follows: Spread the 303 abrasive over an area about a half inch square on the lapping plate, wet the brush, mix water into the spot and spread the abrasive over the lapping plate. Always keep the abrasive moist. Take the button, put a drop of water at its center, and press the dry crystal blank over the drop of water. There should be just enough water in the drop so that it squeezes out under the edges of the blank, where it is wiped away. Place the button, blank down, on the emery and put the index finger in the center of the button. Use just enough pressure to move the button in a figure-8 pattern. This motion is used because it helps keep the blank flat.


After grinding through ten or fifteen "8s" the blank should be rechecked for frequency and activity. The blank's activity is a term used in crystal making to describe how strongly a crystal will oscillate. This may be indicated by the magnitude of the dip in the plate current, grid current to the next stage, or rectified grid current in the crystal oscillator. (See "Maximum Grid Current" this chapter.) It is nearly impossible to tell how much change in frequency will occur during the grinding of a crystal, because pressure on the button, the amount of abrasive, and the area of the "8" all will vary the frequency. The frequency change probably will be between 200 and 1000 cycles per "8," using a 7-Mc. crystal. The

crystal can be moved along faster as the operator becomes more familiar with the technique, but for the beginner frequent checks of activity are in order so that any drop can be corrected.

To grind a crystal successfully the activity must be good when the crystal is brought to the desired frequency. There are several ways to raise the activity. Assuming that, with careful grinding on a flat plate with a flat button, the two faces of the crystal are parallel, the major cause of low activity will be dirt or moisture on the crystal or electrodes. Before checking activity the crystal should be scrubbed carefully with the toothbrush, using warm water and soap. Wipe the crystal clean and be sure that the electrodes are clean and dry. If the activity is still down the next thing is to bevel all eight edges of the crystal. The beveling can be done with either fine or coarse abrasive, but is usually more effective with the coarse. Beveling, incidentally, will also raise the frequency because of the quartz ground off during the process.

Although beveling will usually improve the activity, another method — and probably the simplest — is to change electrodes. The land heights on the electrodes have a critical effect on activity. If the center of the crystal becomes too high and the lands are so low that the center of the crystal touches the center of the

Fig. 6-9 — The  $\frac{1}{2} \times \frac{1}{2}$ -inch electrodes used in modern crystal holders, showing the lands at the corners between which the crystal is firmly held.

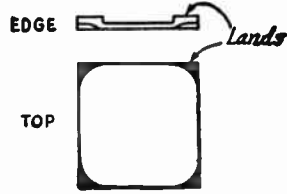

electrodes, the crystal will stop oscillating.

The last step — and the most drastic method of raising activity — is to edge-grind adjacent edges. This grinding is best done with coarse abrasive and should be followed by a slight bevel to remove any chips which may remain. By checking the crystal frequently, a drop in activity can be corrected by the above methods. If the crystal is ground too far and goes completely dead, the frequency may be too high when the crystal is again reactivated.

Most crystals produced in the last five years or so have been brought to the desired frequency by an etching process. This process is not only a convenient means of quantity production, but it also results in a completely clean surface for the crystal, which plays an important part in the activity of the crystal and the maximum power it will handle without overheating. Therefore regrinding may impair the performance of etched crystals, since regrinding destroys the etched surface.

## R.F. Power Amplifiers

### ● SCREEN-GRID AMPLIFIERS

Since the power output from an oscillator is limited for reasons previously stated, r.f. power greater than 10 or 15 watts, if the oscillator is crystal-controlled, or a watt or two if VFO is used, usually is obtained by feeding the output of the oscillator into one or more amplifiers as may be required to raise the power level to that desired before feeding it to the antenna.

Fig. 6-10 shows a fundamental amplifier circuit. The oscillator output is fed into the grid circuit of the amplifier. Power output is taken from the plate circuit. Both grid and plate circuits are tuned to the frequency of the oscillator. It will be noticed, however, that this fundamental circuit is the same as the circuit shown for the tuned-grid tuned-plate oscillator of Fig. 6-2B. Therefore the amplifier circuit itself will function as an oscillator, independently of the oscillator feeding it, unless measures are taken to make this condition impossible.

Feed-back is through the path provided by the grid-plate capacitance of the tube. Therefore an obvious measure is to decrease this capacitance so that the feed-back is not sufficient to support oscillation. This can be done by using a well-screened tube in the amplifier, as shown in Fig. 6-11A, and arranging the ampli-

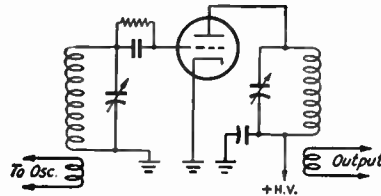


Fig. 6-10 — Fundamental r.f. power-amplifier circuit. Means must be provided to prevent oscillation since the circuit is the same as that for a t.g.t.p. oscillator. See text for discussion.

fier-circuit components, particularly the grid and plate tank coils, so that no other coupling for feed-back from output to input circuits exists. Tubes such as the 6K7, 6AG7, 2E25, 807, 814 and 4-125A and similar types can be used successfully in this way. The less-completely screened tubes, such as the 6F6, 6V6, 6L6 and 813 usually require other means of stabilization.

The equivalent push-pull circuit is shown in Fig. 6-11B. The r.f. chokes are used so that the centers of the coils will not be grounded for r.f. through the power supply, thus setting up two distinct tank circuits, each consisting of half of the coil and one section of the split-stator condenser. The circuits for pentodes are the same with the addition of the grounded suppressor grid.

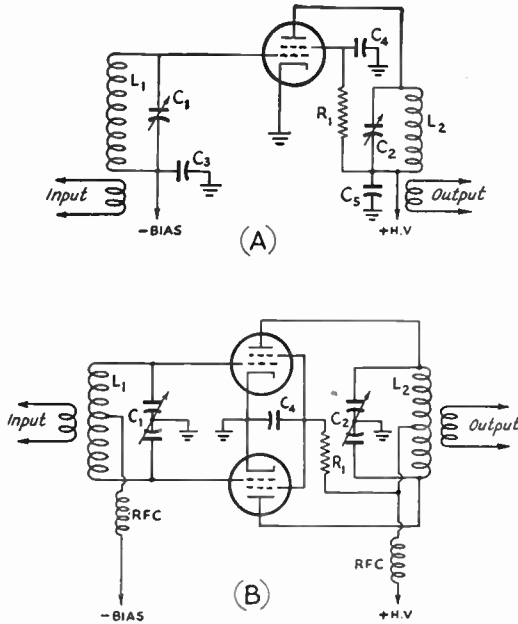


Fig. 6-11 — Screen-grid amplifier circuits. A — Single-tube amplifier. B — Push-pull.

$L_1C_1$  (grid tank) and  $L_2C_2$  (plate tank) are tuned to the frequency being fed to the amplifier.

$C_3$  — Grid by-pass condenser — 0.01- $\mu$ fd. paper.

$C_4$  — Screen by-pass condenser — 0.01- $\mu$ fd. paper.

$C_5$  — Plate by-pass condenser — 0.01- $\mu$ fd. paper.

$R_1$  — Screen voltage-dropping resistor.

RFC — Isolating r.f. chokes — 1 to 2.5 mh.

## ● NEUTRALIZED TRIODE AMPLIFIERS

Another method of preventing feed-back is to neutralize the effect of the grid-plate capacitance by feeding, through a separate path to the grid, a voltage which is equal, but in opposite phase, to the voltage fed back from plate to grid through the plate-grid capacitance of the tube.

The most commonly-used circuits for this purpose are shown in Fig. 6-12. Amplifiers using these systems of neutralization are known as **plate-neutralized amplifiers**. In each case, the midpoint of the plate tank circuit, either coil or condenser, is grounded, so that the voltages at opposite ends of the tank are essentially equal, but 180 degrees out of phase.

The value of voltage fed back to neutralize the amplifier is adjusted to match that fed back through the grid-plate capacitance of the tube by adjusting the capacitance of the neutralizing condenser,  $C_6$ .

### Capacitive Voltage Division

In Fig. 6-12A, the division of voltage across the tank circuit is dependent upon the ratio of the capacitances of the two sections of the tank condenser. Since these capacitances are equal in a split-stator condenser, the voltages at the ends of the tank circuit in respect to the

cathode, which is connected to the center of the tank circuit through ground, are equal. Therefore the neutralizing voltage is the same as the feed-back voltage when the capacitance of the neutralizing condenser is equal to the grid-plate capacitance of the tube.

In this circuit, the output (plate-cathode) capacitance of the tube shunts only one section of the tank condenser. Therefore that half of the tank circuit has a greater total capacitance across it than the other half. Since the added capacitance is fixed in value, this means that the ratio of capacitance across the two sections does not remain constant for all settings of the tank condenser, especially if the tube output capacitance is large. When the tank condenser is at maximum capacitance, the tube capacitance usually is a small percentage of the condenser capacitance and therefore the unbalance between the two sections is at a minimum. However, when the tank condenser is set near minimum capacitance, the tube capacitance may be as large or larger than the condenser capacitance and the unbalance is appreciable. Therefore a fixed adjustment of the neutralizing condenser may not hold neutralization for all settings of the tank condenser. This condition can be corrected by connecting a condenser,  $C_7$ , of capacitance equal to the tube output capacitance across the neutralizing-condenser side of the tank circuit, as shown in Fig. 6-13, to

balance the tube capacitance which appears across the other side. The alternative is to adjust the inductance of the coil so that the circuit tunes to the desired frequency near the maximum-capacitance setting of the tank condenser, where the unbalance is less than near minimum capacitance.

### Inductive Voltage Division

In Fig. 6-12B, the voltage division for neutralization is dependent upon the ratio of inductances in the two sections of the coil. The coil usually is tapped at the center to give equal voltages at the ends of the tank circuit. However, the tap may be placed off center, thus making the voltage at the plate end of the circuit higher or lower than the voltage at the other end of the circuit in respect to cathode. In this case, the capacitance of the neutralizing condenser must be altered to compensate. If the plate end of the coil has more inductance than the other end, the capacitance of the neutralizing condenser must be greater than the grid-plate capacitance of the tube. If the plate end has less inductance than the other end, the neutralizing capacitance must be less than the grid-plate capacitance of the tube.

One disadvantage of the circuit of Fig. 6-12B is that when plug-in coils are used to change the amplifier tuning from one fre-

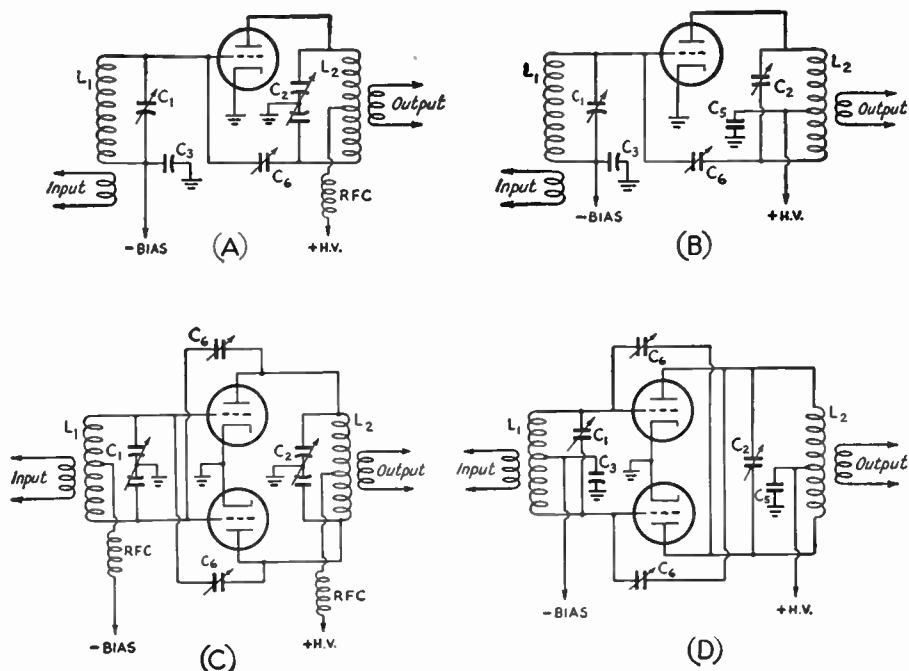


Fig. 6-12 — Neutralized triode-amplifier circuits. A and B — Single-tube amplifier. C and D — Push-pull.  $C_6$  should have approximately the same value as the plate-grid capacitance of the tube when the plate tank circuit is grounded at the center (see text for other conditions). All other values same as corresponding values given under Fig. 6-11.

quency band to another, it may be difficult to tap the coils for each band with sufficient similarity to avoid the necessity for readjustment of the neutralizing condenser each time coils are changed.

### Push-Pull Neutralized Amplifiers

Since a push-pull circuit is a balanced arrangement, it is more easily neutralized and a single adjustment of the neutralizing condenser will hold over a greater tuning range. Circuits with inductive and capacitive voltage division are shown in Fig. 6-12C and D. While the circuit of C usually is considered preferable, inductive voltage division, as shown at D, sometimes is employed to permit the use of single-section tank condensers. In theory the single-section condensers introduce an unbalance in respect to ground, but in practice, the unbalance may not be so serious that the circuit cannot be used successfully, at least at 3.5 and 7 Mc.

### OTHER NEUTRALIZING CIRCUITS

Additional, but less widely-used neutralizing circuits are shown in Fig. 6-14. The circuit of Fig. 6-14A is similar to that of Fig. 6-12A, except that the voltage division takes place in the grid circuit instead of the plate circuit. Any voltage which may be fed back to the grid circuit through the grid-plate capacitance of the tube is divided in the grid tank circuit so that half appears at the grid, while the other half is fed, 180 degrees out of phase, back to

the plate. In another similar version the grid tank coil, instead of the condenser, is used as the voltage divider, the circuit being similar to Fig. 6-12B.

### Link Neutralization

The link neutralizing circuit of Fig. 6-14B sometimes is useful as an expedient to stabilize a screen-grid amplifier which is not sufficiently screened or shielded. It has the advantage that it may be added readily to an already-existing amplifier circuit without the necessity for a major alteration in either grid or tank circuits which would be required to shift the ground point to the center of the tank circuit. The link provides the path for coupling back the neutralizing voltage and proper phasing is dependent upon the polarization of the two link coils. Connections to one of the link coils may be switched to obtain correct polarization.

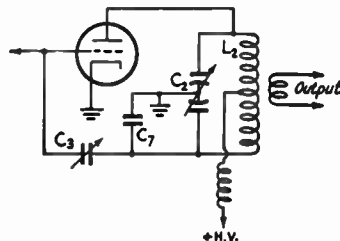


Fig. 6-13 — In this neutralizing circuit,  $C_7$ , which has the same capacitance as the output capacitance of the tube, has been added to compensate for the tube capacitance across the upper half of the circuit.

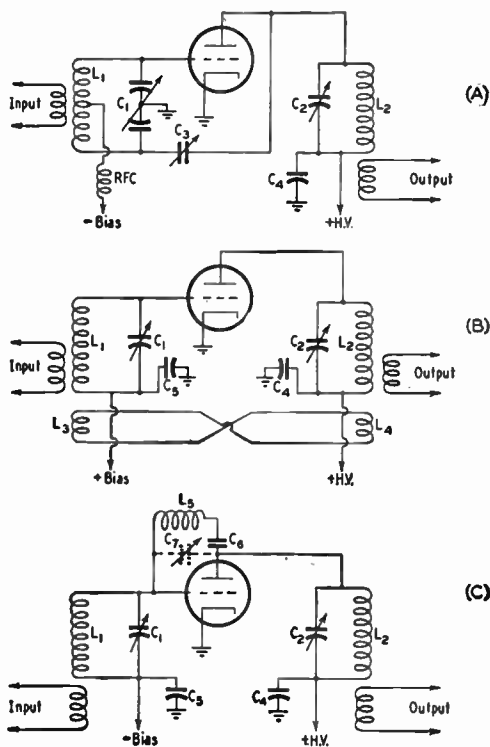


Fig. 6-14 — Additional, but less commonly-used neutralizing circuits. A — Grid neutralizing. B — Link neutralizing. C — Inductive neutralization.

$L_1C_1$ ,  $L_2C_2$  — Tank circuits tuned to operating frequency.

$C_3$  — Neutralizing condenser — approximately same capacitance as grid-plate capacitance of tube.

$C_4$  — Plate by-pass condenser — 0.01- $\mu$ fd. paper.

$C_5$  — Grid by-pass condenser — 0.01- $\mu$ fd. paper.

$C_6$  — Voltage-blocking condenser — 0.001- $\mu$ fd. mica.

$C_7$  — Variable condenser to tune trap circuit to operating frequency with  $L_5$  and grid-plate capacitance of tube.

$L_3$ ,  $L_4$  — Neutralizing links — 2 to 10 turns, depending upon frequency.

$L_5$  — Neutralizing trap coil — to tune to operating frequency with  $C_7$  and grid-plate capacitance of tube.

### Inductive Neutralization

The inductive-neutralization arrangement of Fig. 6-14C consists merely of making the plate-grid capacitance of the tube part of a circuit tuned to the frequency at which the amplifier is designed to operate. Since such a circuit presents a high impedance to the flow of current at the frequency to which it is tuned (wavetrap), it prevents voltage feed-back.

All of the circuits of Fig. 6-14 have disadvantages in amateur practice, particularly in respect to the tuning range over which a single adjustment of neutralization will hold.

## Frequency Multipliers

### ● FREQUENCY-MULTIPLYING AMPLIFIERS

Output at a multiple of the frequency at which it is being driven may be obtained from an amplifier stage if the output circuit is tuned to a harmonic of the exciting frequency instead of the fundamental. Thus when the frequency at the grid of the stage is 3.5 Mc., output at 7 Mc. may be obtained by tuning the plate tank circuit to 7 Mc. The circuit otherwise remains the same although some of the values may change. Since the input and output circuits are not tuned to the same frequency, neutralization is not required, unless the stage is to be operated at the fundamental also.

#### Push-Pull Multiplier

A single-tube amplifier, or an amplifier with tubes in parallel, will deliver output at either even or odd multiples of the frequency at which it is being driven. A push-pull amplifier does not work satisfactorily at even multiples, but very well at odd multiples.

#### Push-Push Multiplier

A two-tube circuit which works well at even harmonics, but not at the fundamental or odd harmonics, is shown in Fig. 6-15. It is known as the push-push circuit. The grids are connected in push-pull while the plates are connected in parallel.

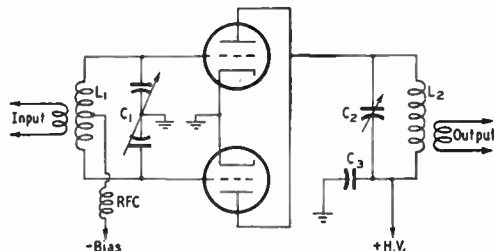


Fig. 6-15 — Circuit of a push-push frequency multiplier for even harmonics. The grid tank circuit,  $L_1C_1$ , is tuned to the frequency of the preceding driving stage, while the plate tank circuit,  $L_2C_2$ , is tuned to an even multiple of that frequency, usually the second harmonic.  $C_3$  is the plate by-pass capacitor, usually a 0.01- $\mu$ fd. paper condenser, while  $RFC$  is a 2.5-mh. r.f. choke.



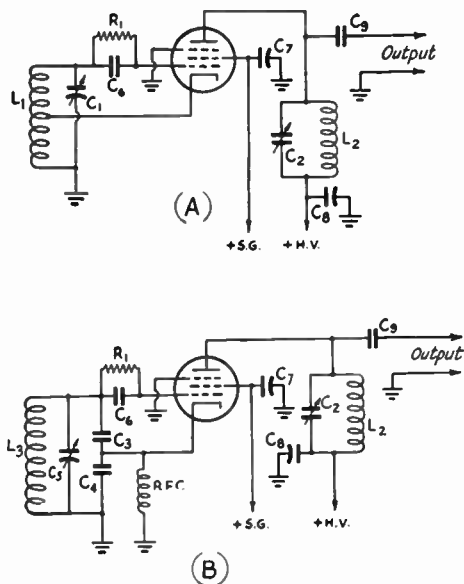


Fig. 6-16 — ECO circuits. A — Hartley. B — Colpitts. Approximate values are as follows:

- C<sub>1</sub> — Oscillator tank condenser — for 3.5 Mc.: 500  $\mu\text{fd.}$  or more total, including any fixed capacitance which may be employed for bandsread purposes.
- C<sub>2</sub> — Output tank condenser — 100- $\mu\text{fd.}$  variable.
- C<sub>3</sub> — Tank condenser — 0.003- $\mu\text{fd.}$  mica for 3.5 Mc.
- C<sub>4</sub> — Tank condenser — 0.001- $\mu\text{fd.}$  mica for 3.5 Mc.
- C<sub>5</sub> — Tuning condenser — 250- $\mu\text{fd.}$  variable for 3.5 Mc.
- C<sub>6</sub> — Grid condenser — 100  $\mu\text{fd.}$  or less, mica.
- C<sub>7</sub> — Screen by-pass condenser — 0.01- $\mu\text{fd.}$  paper.
- C<sub>8</sub> — Plate by-pass condenser — 0.01- $\mu\text{fd.}$  paper.
- C<sub>9</sub> — Output coupling condenser — 100  $\mu\text{fd.}$  or less, mica.
- R<sub>1</sub> — Grid leak — 50,000 ohms.
- L<sub>1</sub> — Oscillator tank coil — 4.3  $\mu\text{hy.}$  tapped approximately one-third from ground end for 3.5 Mc. (with 500  $\mu\text{fd.}$ ).
- L<sub>2</sub> — Output tank coil — 22  $\mu\text{hy.}$  for 3.5 Mc., 7.5  $\mu\text{hy.}$  for 7 Mc.
- L<sub>3</sub> — Oscillator tank coil — 3.3  $\mu\text{hy.}$  for 3.5 Mc. with capacitance values given for C<sub>3</sub>, C<sub>4</sub> and C<sub>5</sub>.
- RFC — Parallel-feed r.f. choke — 2.5 mh.

Multiplications of three and sometimes four or five are used to reach the bands above 28 Mc. from a lower-frequency crystal, but in the majority of lower-frequency transmitters, multiplication in a single stage is limited to a factor of two because of the rapid decline in efficiency as the multiplication factor is increased. Screen-grid tubes make the best frequency multipliers because their high power-sensitivity makes them easier to drive than triodes.

## ● FREQUENCY-MULTIPLYING OSCILLATORS

### Electron-Coupled Oscillators

Several circuits have been devised in which a single screen-grid tube performs the functions of both an oscillator and an amplifier. The ECO circuits of Fig. 6-16 are of this type.

The screen serves as the plate of a triode oscillator, while the power is taken from a separate tuned output-plate tank circuit.

In Fig. 6-16A, the oscillator circuit is a Hartley in which the ground point has been shifted from the cathode to the "plate." Fig. 6-16B shows the Colpitts modified in a similar manner. The choke, RFC, is required to provide a d.c. path to the cathode without grounding it for r.f. Output at a multiple of the oscillator frequency may be obtained by tuning the output-plate tank circuit to the desired harmonic, although this is seldom done beyond the second harmonic.

In both of these circuits, the oscillator frequency is not entirely independent of tuning or loading in the output plate circuit. The reaction is less, however, when the output-plate circuit is tuned to a harmonic or replaced by an untuned circuit, such as an r.f. choke, as shown in Fig. 6-17. The power output obtainable with the latter arrangement is much lower, however.

### Tri-Tet Circuit

Fig. 6-18 shows three crystal-oscillator circuits which operate on principles similar to those of the ECO. Circuits such as these have the additional advantage that they are invariably found to key more reliably than the simple triode or tetrode circuits, and do not incur the considerable loss in efficiency sometimes involved in detuning the plate circuit far to the high-frequency side of resonance for reliable crystal starting under load.

The extent to which the output-plate circuit reacts on the oscillator portion of the circuit, and the output-circuit tuning characteristics, are influenced to a considerable degree by the effectiveness of the screening of the tube selected. Well-screened tubes always are preferable from the standpoints of both isolation and safety to the crystal.

Fig. 6-18A shows the Tri-tet circuit. The oscillator portion is equivalent to that of a triode crystal oscillator, with the screen serving as the "plate" and the ground point being shifted from the cathode to the "plate." Power is taken from a separate output-plate tank circuit. Since the output-plate circuit returns to cathode through the  $L_1C_1$  tank circuit, the plate contributes to the feed-back to a certain

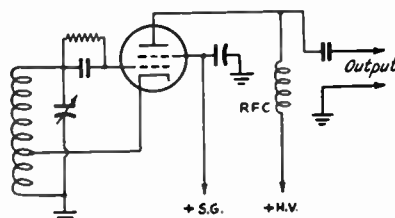


Fig. 6-17 — ECO with an r.f. choke replacing the output tank circuit for the purpose of reducing reaction on the oscillator portion of the circuit.

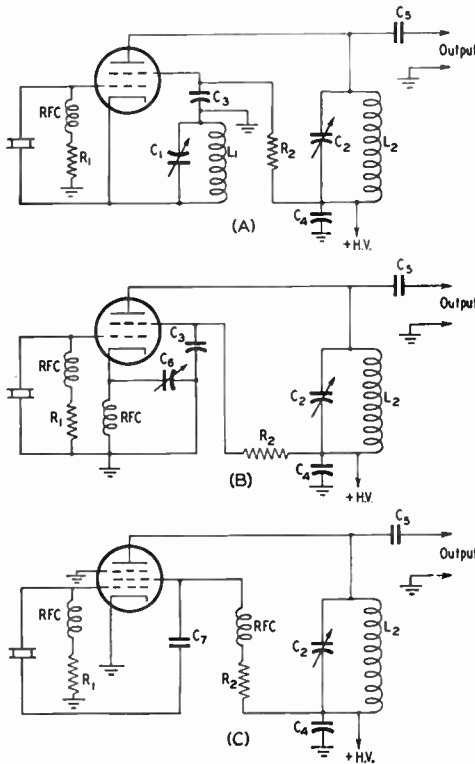


Fig. 6-18 — Crystal-controlled amplifying-oscillator circuits. Approximate values are as follows:

- C<sub>1</sub> — Cathode-tank tuning condenser — 100- $\mu$ fd. variable.
- C<sub>2</sub> — Output-tank tuning condenser — 100- $\mu$ fd. variable.
- C<sub>3</sub> — Screen by-pass condenser ("plate" grounding) — 0.01- $\mu$ fd. paper.
- C<sub>4</sub> — Plate by-pass condenser — 0.01- $\mu$ fd. paper.
- C<sub>5</sub> — Output coupling condenser — 100  $\mu$ fd. or less, mica.
- C<sub>6</sub> — Feed-back-control condenser — 100- $\mu$ fd. variable.
- C<sub>7</sub> — Parallel-feed blocking condenser — 0.001- $\mu$ fd. mica.
- R<sub>1</sub> — Grid leak — 50,000 to 150,000 ohms.
- R<sub>2</sub> — Screen voltage-dropping resistor — 25,000 to 100,000 ohms.
- L<sub>1</sub>C<sub>1</sub> — Tuned to desired harmonic of crystal or well above crystal frequency for fundamental operation (see text).
- L<sub>2</sub>C<sub>2</sub> — Tuned to desired output frequency.
- RFC — Parallel-feed r.f. choke — 2.5 mh.

extent. Therefore,  $L_1C_1$  should always be tuned well to the high-frequency side of the crystal frequency to prevent excessive feedback and consequent unnecessarily-high voltage across the crystal. As with the ECO (Fig. 6-16) and the circuits in Fig. 6-18, harmonic output may be obtained by tuning the output tank circuit,  $L_2C_2$ , to the desired multiple of the crystal frequency. In the Tri-tet circuit best harmonic output will be obtained with  $L_1C_1$  also tuned to the desired harmonic.

When operating the Tri-tet circuit at the crystal frequency,  $L_1C_1$  should be tuned no closer to the crystal frequency than is nec-

essary to make the circuit oscillate without output-plate voltage applied. When the oscillator is to be used to obtain output at the fundamental or at harmonics as desired, the cathode tank circuit,  $L_1C_1$ , may be tuned to the highest multiple of the crystal frequency at which output is required. While the output at the crystal frequency and lower harmonics under this condition is less than the maximum obtainable with optimum cathode-circuit adjustment, it is usually at least as much as is obtainable at the highest harmonic and therefore the power output from the oscillator is approximately the same on all bands.

With well-screened tubes, such as the 6SK7, 2E25 or 802, the output-plate tuning characteristic is like that shown in Fig. 6-19 at the fundamental as well as at the harmonics and the circuit will continue to oscillate regardless of the tuning of the output circuit. However, with poorly-screened tubes, such as the 6V6, 6F6 or 6L6, the circuit will stop oscillating abruptly when the output circuit is tuned to a frequency lower than the crystal frequency, more in the manner of a simple triode or tetrode oscillator. With well-screened tubes, feed-back is at a minimum when the output circuit is unloaded, the excitation increasing as load is increased. This characteristic is opposite to that of the triode or tetrode crystal oscillator.

**Grid-Plate Oscillator**

A less widely-used circuit is the grid-plate crystal-oscillator circuit of Fig. 6-18B. The oscillator portion is similar to the triode Pierce with the screen being used as the "plate," and the ground point shifted to the "plate."  $L_2C_2$  is the output-plate circuit.  $C_6$  adds to the "plate"-cathode capacitance for feed-back-adjustment purposes. As in the Tri-tet circuit, the return for the output-plate circuit to cathode is through  $C_6$  which is common to the grid return, and therefore the isolation between oscillator and output circuits is incomplete and the plate contributes to the feed-back. However, with a well-screened tube the oscillator will continue to function regardless of the tuning of the output circuit. This circuit is used principally for its performance at the crystal fundamental, where it is superior

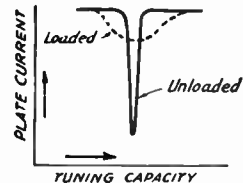


Fig. 6-19 — Plate tuning characteristic for Tri-tet, grid-plate and modified Pierce crystal-oscillator circuits, using well-screened tubes, for loaded (dashed line) and unloaded (solid line) conditions. In this case, the output-plate circuit may be tuned accurately to the minimum plate-current dip for maximum output.

to that of the simple triode or tetrode circuits. Only at odd harmonics is it equal or possibly superior to the Tri-tet circuit.

### Modified Pierce

Another version of the Pierce circuit, adaptable to pentodes, is shown in Fig. 6-18C. The oscillator portion of the circuit is the triode Pierce with the cathode grounded and the

screen serving as the "plate." In this arrangement the output-plate and grid returns are through independent paths and the suppressor provides screening against capacitance coupling. In theory, at least, this circuit provides better isolation between the oscillator and output portions of the circuit than either of the other two. Pentodes, such as the 6SK7, 6AG7 and 802 are suitable for this circuit.

## Interstage Coupling

Of the various systems that have been devised for feeding the output of one stage into the input of another, the inductive-link and capacitive systems are the most widely used in amateur transmitters. The link system is used principally in cases where there must be appreciable physical separation between stages, where balanced and unbalanced circuits are to be coupled, or when minimum circuit capacitance is desired. The capacitive system has the advantages of simplicity, cheapness and compactness, but it does not lend itself so well to the conditions listed above.

### INDUCTIVE SYSTEMS

#### Link Coupling

The link system, examples of which are shown in Fig. 6-20, consists merely of a two-wire low-impedance line with each end terminated in a coil of a few turns coupled tightly to the low-potential point of the output tank coil of the driver and the input tank coil of the driven stage. This low-potential point occurs at the "ground" end of the tank coil in unbalanced circuits (Fig. 6-20A, B and C) and at the center of the tank coil in balanced arrangements (Fig. 6-20B, C and D).

The coupling between the two stages can be adjusted either by changing the number of turns in the link windings or by changing the coupling between the links and the tank coils. This system does not upset the symmetry of a balanced circuit through the introduction of unbalancing capacitances of the single-ended circuit coupled to it.

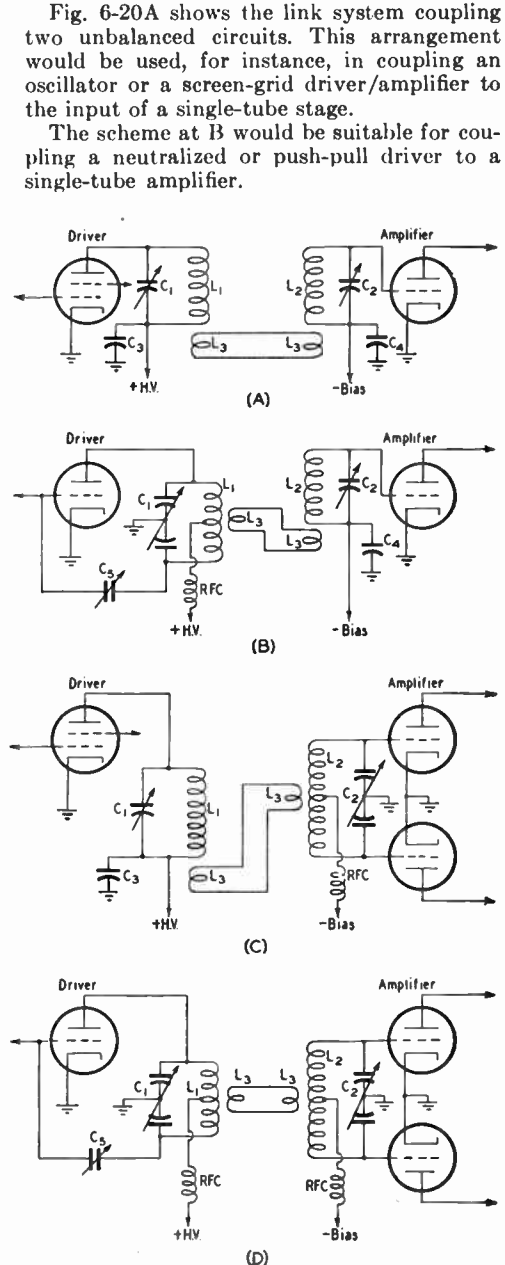


Fig. 6-20 — Link-coupling circuits. A — Unbalanced output to unbalanced input. B — Balanced output to unbalanced input. C — Unbalanced output to balanced input. D — Balanced output to balanced input.

- $C_1$  — Driver-stage plate tank condenser.
- $C_2$  — Driven-stage grid tank condenser.
- $C_3$  — Plate by-pass condenser.
- $C_4$  — Grid by-pass condenser.
- $C_5$  — Neutralizing condenser.
- $L_1$  — Driver output tank coil.
- $L_2$  — Driven-stage input tank coil.
- $L_3$  — Link winding.
- $L_1C_1$  and  $L_2C_2$  are always tuned to the same frequency.
- RFC — R.f. choke.

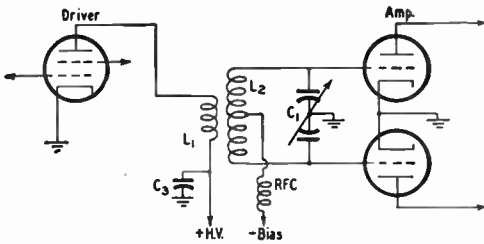


Fig. 6-21 — Inductive coupling from unbalanced output to balanced input.

- C<sub>1</sub> — Driven-stage grid tank condenser.
- C<sub>3</sub> — Plate by-pass condenser.
- L<sub>1</sub> — Self-resonant (approximately) output coil.
- L<sub>2</sub> — Driven-stage grid tank coil.
- L<sub>1</sub> and L<sub>2</sub> should be coupled tightly.
- RFC — R.f. choke.

Fig. 6-20C shows the method applied in coupling the output of an unneutralized driver to a push-pull amplifier, while D is the circuit to be used in coupling a neutralized or push-pull stage to another push-pull input.

**Inductive Coupling**

Another system which is used sometimes in coupling between an unbalanced driver and a

balanced amplifier is shown in Fig. 6-21. The output coil of the driver stage is designed to resonate, with the driver-tube and circuit capacitances, near the desired operating frequency. The amplifier input tank circuit tunes to the operating frequency and serves to a considerable degree also to tune the output circuit of the driver stage, since the two coils are coupled quite tightly. L<sub>1</sub> should be wound centrally over or inside L<sub>2</sub> and the turns of L<sub>1</sub> adjusted experimentally for optimum power transfer.

● **CAPACITIVE COUPLING**

In a capacitive coupling system, the output tank circuit of the driver stage serves also as the input tank circuit of the driven stage. Several arrangements for coupling between balanced and unbalanced output and input circuits, depending upon whether series or parallel power feed is desired, are shown in Fig. 6-22. The coupling usually can be adjusted satisfactorily by changes in the value of the coupling capacitance, but sometimes wide differences in impedances of the two circuits to be coupled make it necessary to tap either the plate of the driver or the grid of the

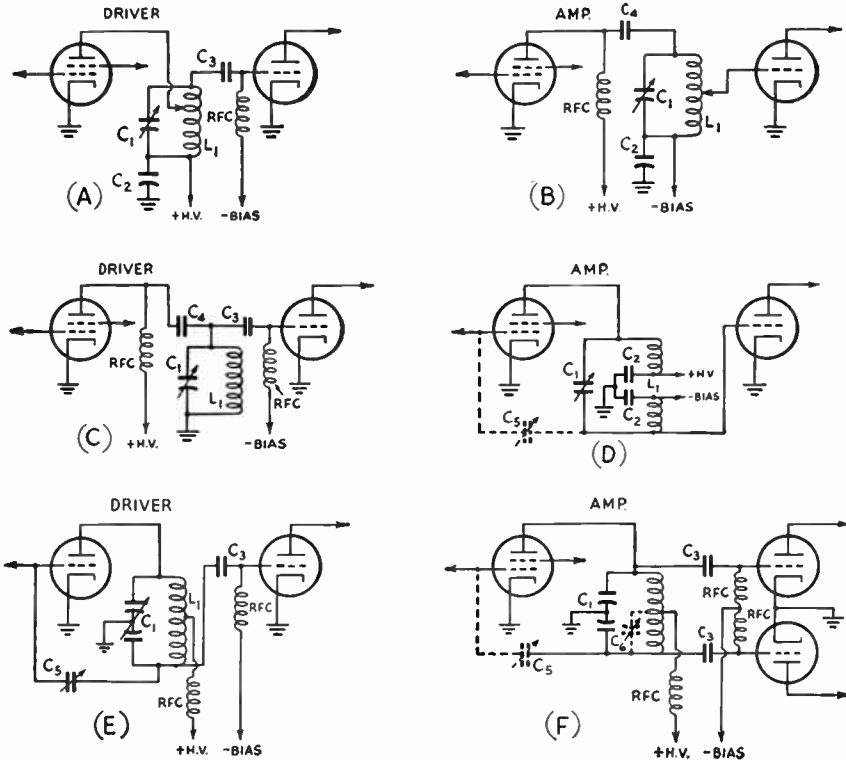


Fig. 6-22 — Examples of capacitive coupling. A — Series plate feed, parallel grid feed. B — Parallel plate feed, series grid feed. C — Parallel feed in both plate and grid. D — Series feed in both plate and grid. E — Balanced feed. F — Single tube to push-pull.

- C<sub>1</sub> — Tank condenser.
- C<sub>2</sub> — By-pass condenser.
- C<sub>3</sub> — Coupling condenser.
- C<sub>4</sub> — Plate blocking condenser.
- C<sub>5</sub> — Neutralizing condenser.
- C<sub>6</sub> — Circuit-balancing condenser.
- L<sub>1</sub> — Tank coil.
- RFC — R.f. choke.

driven tube down on the tank coil, as shown in Fig. 6-22A and B.

With capacitive coupling, the two stages cannot be separated physically any appreciable distance without involving loss in transferred power and the danger of instability because of feed-back which long high-impedance leads may provide. Since both the output capacitance of the driver tube and the input capacitance of the driven tube are lumped across the single tuned circuit, this sometimes makes it difficult, with the high-capacitance of screen-grid tubes, to obtain a tank circuit with a sufficient amount of inductance to provide an efficient circuit for the higher frequencies. Another disadvantage is that it is difficult to preserve circuit balance in coupling from a single-tube stage to a push-pull stage because the circuit tends to become unbalanced by the output capacitance of the driver tube which appears across only one side of the circuit. This does not, however, preclude its use for this purpose, if simplicity in circuit is considered of greater importance, for frequencies below 30 Mc.

The arrangements of Fig. 6-22A and B are most often seen with the plate tap of A and the grid tap of B connected to the top end of the coil, since this connection is satisfactory in the majority of cases. A is used when series driver plate feed is desired; B when series amplifier grid feed is wanted. In the circuit of C, the tank condenser and coil are grounded directly, but parallel power feed is required for both driver plate and amplifier grid.

An arrangement which makes possible series feed to both plate and grid is shown at D.  $L_1$  in D is a single coil, opened at the center for feeding in plate and biasing voltages. Since the by-pass condensers,  $C_2$ , are directly in the tank circuit, they should be of good-grade mica and capable of handling the r.f. current circulating through the tank circuit. Because it provides a "double-ended" output circuit, it may be used in a neutralized amplifier stage simply by the addition of neutralizing condenser  $C_5$ .

The grid of the driven tube and the plate of the driver tube being connected across opposite halves of the tank circuit helps to distribute stray capacitances more evenly, thereby preserving a better circuit balance. A still better balance can be achieved by using a split-stator condenser at  $C_1$  and a single mica condenser at  $C_2$ , grounding the circuit at the split-stator rotor rather than between the two fixed condensers. Excitation may be adjusted, if necessary, by tapping the grid or plate, as may be required, down on the coil. Such a change, however, will necessitate readjust-

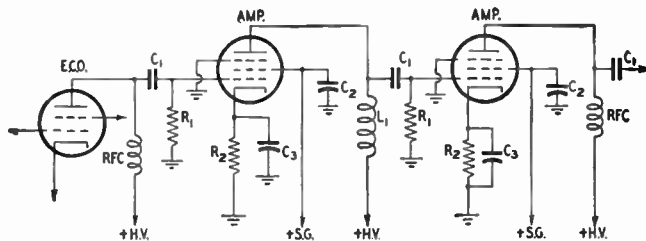


Fig. 6-23 — Diagram showing two isolating-amplifier stages coupled to the output of an ECO.

- |  |   |
|--|---|
| $C_1$ — Coupling condenser — 100 $\mu$ fd. or less, mica.  | $R_1$ — Grid leak — 50,000 to 100,000 ohms.         |
| $C_2$ — Screen by-pass condenser — 0.01- $\mu$ fd. paper.  | $R_2$ — Cathode biasing resistor — 200 to 500 ohms. |
| $C_3$ — Cathode by-pass condenser — 0.01- $\mu$ fd. paper. | $L_1$ — Coupling inductance — see text.             |
|  | RFC — Plate choke — 2.5-mh.                         |

ment of neutralization if the tank is used for neutralizing the driver as suggested.

The circuit of Fig. 6-22E is the preferred arrangement for coupling a neutralized driver to a single-tube amplifier in cases where series feed to the grid of the amplifier is not considered important. F shows the same system feeding a push-pull amplifier. If a more accurate balance is desired, a balancing condenser,  $C_6$ , can be used to compensate for the driver-tube output capacitance across the other half of the circuit.

## ● ISOLATING AMPLIFIERS

In an unneutralized triode amplifier, changes occurring in the plate circuit, such as alterations in plate voltage, plate-tank tuning or loading, will reflect changes in the effective input capacitance of the tube. When the amplifier is connected to a VFO, these variations will change the frequency of the VFO. Neutralization of a triode amplifier or the substitution of a screen-grid tube will reduce these effects, but will not eliminate them entirely, especially in the case of screen-grid tubes whose electrode voltages are not regulated.

Most of the change takes place when the plate tank circuit is tuned near resonance. Therefore one measure which can be taken to improve isolation is the use of a fixed non-resonant circuit instead of the usual tuned tank in the plate circuit.

The diagram of Fig. 6-23 shows two such stages coupled to a VFO. A nonresonant circuit also is substituted in the plate circuit of the ECO. An r.f. choke is used as the non-resonant circuit in the output of the ECO and in the second amplifier.  $L_1$  in the plate circuit of the first amplifier is a winding that is self-resonant with the tube and circuit capacitances at a frequency near but not in the band of frequencies over which the amplifier is intended to operate. This is to prevent forming a low-frequency t.g.t.p. oscillating circuit which occurs when chokes of approximately the same characteristics are used in both input and output circuits of the amplifier tubes. For the

same reason, resistors without chokes are used in the grid circuits.

The power gain of an amplifier of this type is quite small, the purpose being almost entirely that of securing isolation between the VFO and power amplifiers which would react

on the frequency of the oscillator if coupled to it directly. Two amplifier stages of this type usually are necessary before a following amplifier can be tuned or keyed without noticeably affecting the oscillator frequency and stability.

## Amplifier and Multiplier Tank-Circuit Design

### ● *L/C* RATIO

#### Plate Tank Capacitance

Power cannot be readily coupled out of a plate tank circuit if the ratio of inductance to capacitance (*L/C* ratio) is too great. Also, harmonics are more readily generated in a tank circuit in which this ratio is high. On the other hand, a large capacitance and small inductance will cause high currents to circulate in the tank circuit increasing the losses and reducing the

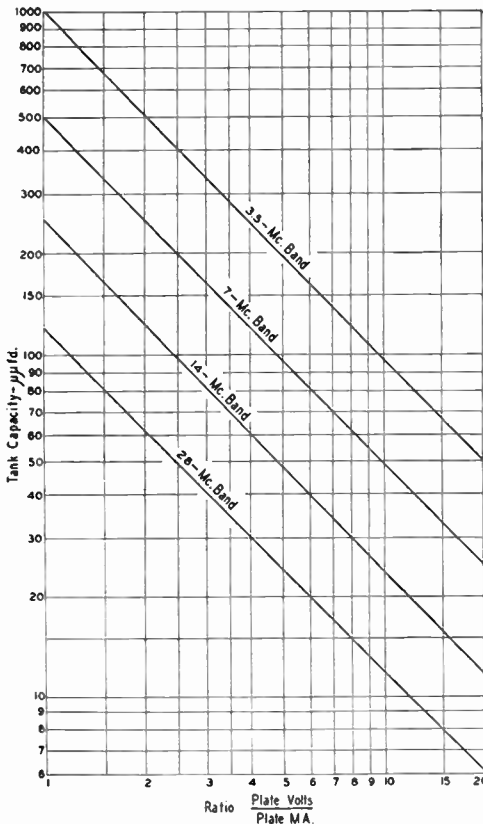


Fig. 6-24 — Chart showing minimum plate tank capacitances recommended with various ratios of plate voltage to plate current, for the four low-frequency amateur bands. In the circuits F, G and H of Fig. 6-25, the values shown by the graph may be divided by four. In circuits C, D, E, I, J and K, the capacitance of each section of the split-stator condenser may be one-half the value shown by the graph. The full graph values should be used for circuits A and B. These values are based on a circuit *Q* of 12.

efficiency of the amplifier. Unless one of these factors is considered to be of greater importance than the other, a compromise value for the *L/C* ratio usually is selected.

With the conditions under which r.f. power amplifiers in amateur transmitters usually are operated, the *L/C* ratio for the same degree of harmonic suppression and coupling varies in inverse proportion to the ratio of d.c. plate voltage to plate current with the amplifier in operation and loaded. The chart of Fig. 6-24 shows recommended values of tank capacitance for a wide range of plate-voltage/plate-current ratios for each of the low-frequency amateur bands. The values given apply to the type of plate tank circuits shown in Fig. 6-25A and B only. Because the tube is connected across only half of the tank in the remainder of the circuits shown in Fig. 6-25, the total capacitance across the tank coil may be reduced to one-quarter that shown by the graph for the same plate-voltage/plate-current ratio. This means that in circuits in which a split-stator condenser is used, the capacitance of each section of the condenser may be half the value shown in the graph, since the two sections are in series across the coil.

The values shown in Fig. 6-24 are the capacitances which should be in actual use when the circuit is tuned to resonance in the selected band — not the maximum rated capacitance of the tank condenser including tube and circuit capacitances. They should be considered minimum values for satisfactory operation. They can be exceeded 50 to 100 per cent without involving an appreciable loss in circuit efficiency.

Approximately the same *L/C* ratio should be used in the plate tank circuit whether the stage is operating as a straight amplifier or multiplying frequency in order to confine the output to the desired multiple as much as possible.

#### Plate Tank Coils

The inductance of manufactured coils usually is based upon the highest plate-voltage/plate-current ratio likely to be used at the maximum power level for which the coils are designed, following the logical conclusion that it is easier to cut off turns than to add them. Therefore in the majority of cases, the capacitance shown by Fig. 6-24 will be greater than that for which the coil is designed and turns

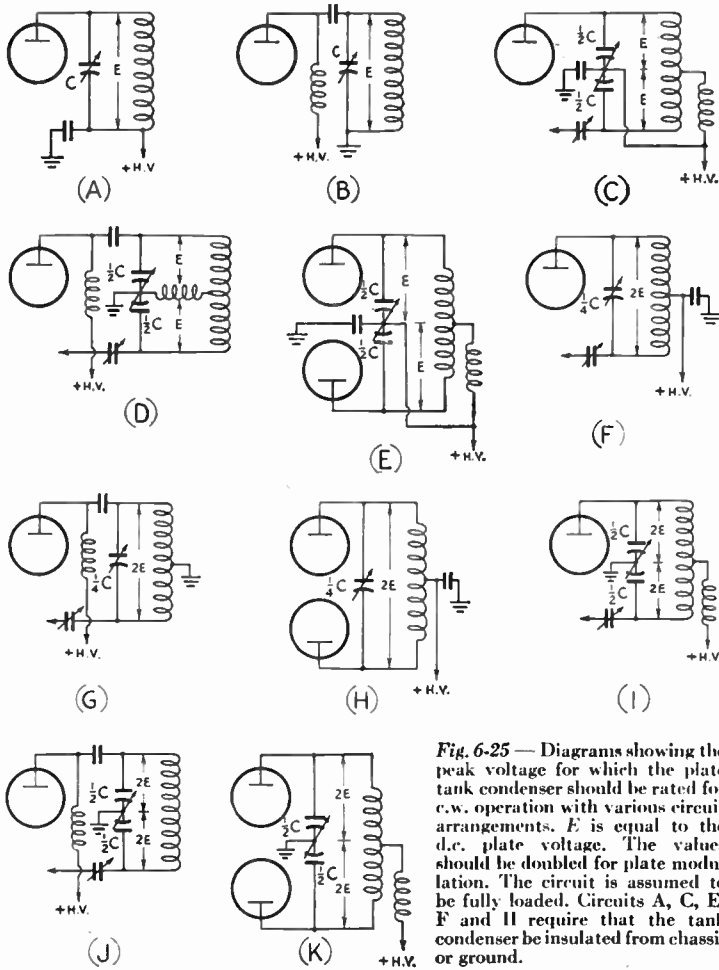


Fig. 6-25 — Diagrams showing the peak voltage for which the plate tank condenser should be rated for c.w. operation with various circuit arrangements.  $E$  is equal to the d.c. plate voltage. The values should be doubled for plate modulation. The circuit is assumed to be fully loaded. Circuits A, C, E, F and H require that the tank condenser be insulated from chassis or ground.

breakdown, the peak r.f. voltage across the tank circuit without modulation may be taken as equal to the d.c. plate voltage. If the d.c. plate voltage also appears across the tank condenser, this must be added to the peak r.f. voltage, making the total peak voltage twice the d.c. plate voltage. If the amplifier is to be plate-modulated, this last value must be doubled to make it four times the d.c. plate voltage, because both d.c. and r.f. voltages double with 100-per-cent plate modulation. At the higher plate voltages, it is desirable to choose a tank circuit in which the d.c. and modulation voltages do not appear across the tank condenser, to permit the use of a smaller condenser with less plate spacing.

Fig. 6-25 shows the peak voltage, in terms of d.c. plate voltage, to be expected across the tank condenser in various circuit arrangements. These peak-voltage values are given assuming that the amplifier is loaded to rated plate current. Without load, the peak r.f. voltage will run much

higher. Since a c.w. transmitter may be operated without load while adjustments are being made, although a modulated amplifier never should be operated without load, it is sometimes considered logical to select a condenser for a c.w. transmitter with a peak-voltage rating equal to that required for a 'phone transmitter of the same power. However, if minimum cost and space are considerations, a condenser with half the spacing required for 'phone operation can be used in a c.w. transmitter for the same carrier output, as indicated under Fig. 6-25, if power is reduced temporarily while tuning up without load.

The plate spacing to be used for a given peak voltage will depend upon the design of the variable condenser, influencing factors being the mechanical construction of the unit, the dielectric used and its placement in respect to intense fields, and the condenser-plate shape and degree of polish. Condenser manufacturers usually rate their products in terms of the peak voltage which can be handled between plates.

### Plate Tank-Condenser Voltage

In selecting a tank condenser with a spacing between plates sufficient to prevent voltage

must be removed to permit the use of the proper value of capacitance. At 28 Mc., and sometimes 14 Mc., the value of capacitance shown by the chart for a high plate-voltage/plate-current ratio will be lower than that attainable in practice with the components available. The design of manufactured coils usually takes this into consideration also and it may be found that values of capacitance greater than those shown in the graph are required to tune these coils to the band.

Manufactured coils are rated according to the plate power input to the tube or tubes when the stage is loaded. Since the circulating tank current is much greater when the amplifier is unloaded, care should be taken to operate the amplifier conservatively when unloaded to prevent damage to the coil from excessive heating.

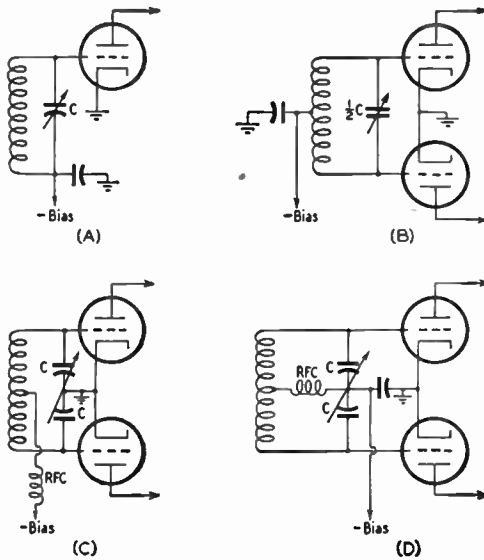


Fig. 6-26 — Diagrams for determining grid tank-condenser capacitance.  $C$  should be a minimum of  $200 \mu\mu\text{fd.}$  for 3.5 Mc.,  $100 \mu\mu\text{fd.}$  for 7 Mc.,  $50 \mu\mu\text{fd.}$  for 14 Mc. and  $25 \mu\mu\text{fd.}$  for 28 Mc.

The tank condenser should have a voltage rating approximately equal to the operating bias voltage plus 20 per cent of the plate voltage for circuit A, twice this value for circuit B and each section of the condenser in circuit D, while the biasing voltage must be added to this latter figure in determining the voltage rating of each section of the condenser in circuit C.

#### Plate-Blocking and By-Pass Condensers

Plate-blocking and by-pass condensers in amplifier stages should have a voltage rating of 25 to 50 per cent above the tube plate-supply voltage if the stage is not modulated or twice this rating if the stage is to be plate-modulated. Paper  $0.01\text{-}\mu\text{fd.}$  condensers are satisfactory for use in exciter stages operating at plate voltages of 500 or less. At higher plate voltages mica condensers having a capacitance of  $0.001$  to  $0.002 \mu\text{fd.}$  with appropriate voltage ratings should be used.

## Amplifier Operating Factors

### ● USING TUBE DATA

Transmitting-tube instruction sheets and data tables specify the limitations on various electrode voltages and currents which should be observed to insure normal tube life. Included also are sets of optimum operating conditions which should be followed as closely as possible to obtain rated output with good efficiency.

#### Filament Voltage

The filament voltage for the indirectly-heated cathode-type tubes found in low-power

### R.F. Chokes

Parallel plate feed provides a considerable measure of protection against serious injury to the operator from accidental contact with high-voltage d.c. in the tank circuit. However, the r.f. choke in this case is called upon to present a high impedance at the operating frequency if serious loss of power in the choke is to be avoided. When a transmitter is designed to operate on all amateur bands from 28 Mc. to 3.5 Mc., loss in r.f. chokes often occurs on one or more of the bands. There is no simple remedy for this difficulty aside from a shift to series plate feed which, of course, nullifies the safety angle. One possible remedy which has not yet been fully developed is the use of different r.f. chokes for each band, the chokes being switched or plugged in along with the tank coil.

### ● GRID TANK CIRCUITS

The value of capacitance to be used in a grid tank circuit when employing link coupling is not critical so long as the  $L/C$  ratio is low enough to permit satisfactory coupling to the driver stage. A capacitance of at least  $200 \mu\mu\text{fd.}$  is recommended for unbalanced grid tank circuits tuned to 3.5 Mc., with the value decreased in proportion as the frequency increases, as given under Fig. 6-26. For unbalanced grid tank circuits, the total condenser capacitance may be cut in half, making the capacitance of each section of a split-stator condenser the same as that of the single condenser used in an unbalanced input grid tank circuit.

Approximate tank-condenser voltage ratings are suggested under Fig. 6-26. Tank coils with a power rating equal to that of the driver plate tank coil should be used in the grid tank circuit.

It is advantageous to operate a link-coupled grid tank circuit of a frequency multiplier with a somewhat higher  $L/C$  ratio than that used for straight amplification from the consideration of driving efficiency, but the ratio cannot be made too great without encountering coupling difficulties.

classifications may vary 10 per cent above or below rating without seriously reducing the life of the tube. But the voltage of the higher-power filament-type tubes should be held closely between the rated voltage as a minimum and 5 per cent above rating as a maximum. Care should be taken to make sure that the plate power drawn from the power line does not cause a drop in filament voltage below the proper value when plate power is applied.

Thoriated-type filaments lose emission when the tube is overloaded appreciably. If the overload has not been too prolonged, emission



sometimes may be restored by operating the filament at rated voltage with all other voltages removed for a period of 10 minutes, or at 20 per cent above rated voltage for a few minutes.

#### Grid Bias

Two values of grid-biasing voltage are of interest in the practical operation of r.f. power amplifiers and frequency multipliers. These are **protective bias** and **operating bias**.

Protective bias must be used with all but "zero-bias"-type tubes to hold the power input to the tube below the rated dissipation value when excitation is removed without removing plate (and screen) voltage. Without excitation, the amplifier delivers no power. Therefore any power input is dissipated in heat which would ruin the tube in a short space of time. This condition exists when the transmitter is keyed ahead of the amplifier, while tuning adjustments are being made, or through failure of a crystal oscillator to function or other accidental failures.

Operating bias is the value of biasing voltage between grid and cathode when the amplifier is being driven and delivering power. The optimum value of biasing voltage for operating under a given set of conditions is listed in tube tables and manuals. Frequency multipliers require a considerably-higher operating bias for most efficient operation.

Protective bias may be any value between that which limits the input to the tube to its rated plate (and screen) dissipation as a minimum, and the operating value as a maximum. It is common practice, however, to set the value at some point between that which is necessary to cut off plate current completely (cut-off value) and the operating value. With fixed plate voltage, the cut-off value for a triode can be determined quite closely by dividing the plate voltage by the amplification factor obtained from the tube data sheet. For screen-grid tubes, the amplification factor of the screen must be used instead. In cases where this is not included in the operating data, the approximate cut-off value may be obtained from an inspection of the plate-current plate-voltage curves which show the plate current for a wide range of plate and biasing voltages.

A factor which must be considered in determining the value of bias which will protect the tube is plate- (and screen-) voltage regulation. If the power-supply regulation is poor, or if the plate or screen is fed from a resistance voltage divider or a voltage-dropping resistor, the electrode voltages will soar as the tube draws less than normal operating current and therefore an increase over the calculated value of cut-off bias will be required to bring the current to zero. This condition is encountered most often in the operation of a screen-grid tube where the screen is not fed from a fixed-voltage source. In such cases, care should be taken to make certain that the proper operat-

ing bias is not exceeded under operating conditions when excitation is applied.

Several different systems for obtaining bias are shown in Fig. 6-27. At A, bias is obtained entirely from the voltage drop across the grid leak,  $R_1$ , caused by the flow of rectified grid current when the amplifier is being driven. This system has the desirable feature that the biasing voltage, being dependent upon the value of grid current, is kept adjusted close to proper operating value automatically over a considerable range of excitation levels. However, when excitation is removed, grid-current flow ceases and the voltage across  $R_1$  falls to zero and there is no bias. Therefore this system provides no protection for the amplifier tube in case excitation fails or is removed.

A battery delivering the required operating bias is used in the arrangement of Fig. 6-27B. Since the biasing voltage still remains when excitation is removed, plate-current flow ceases and the tube is protected. A factor which must be taken into consideration when dry batteries, such as "B" batteries, are used, is the resistance of the batteries. If the internal resistance is high, the resistance will cause an increase, by grid-leak action, in the operating bias above that normally delivered by the batteries. Batteries develop internal resistance with age and should be replaced from time to time. Another factor is that the direction of grid-current flow is such as to reverse the normal direction of current through the battery. This acts to charge the battery. A battery which has been in use for some time, particularly if the grid current under excitation is high, will show a considerably higher-than-rated terminal voltage because of the charging action of the grid current. The terminal voltage of a battery used in transmitter bias service where grid current flows cannot be used as an indication of the condition of the battery. Its internal resistance may be high, even though it shows normal or above-normal terminal voltage. If the grid current in a battery-biased stage falls off after a period of operation and no other reason is obvious, it is probable that the biasing battery should be replaced. The battery life which may be expected in bias service with a given value of grid current will be approximately the same as it would be if that same current were being drawn from the battery.

In Fig. 6-27C, the battery voltage is reduced to the protective value. When excitation is applied, grid-leak action through  $R_2$  supplies the additional biasing voltage necessary to bring the total up to the operating value. This combination of fixed and grid-leak bias is the most popular system, since it combines the safety of protective fixed bias and a measure of automatic adjustment of the operating value through grid-leak action.

In Fig. 6-27D, a power pack is used to supply protective bias. The output of the power pack is connected across the grid resistor which is of the normal grid-leak value for the

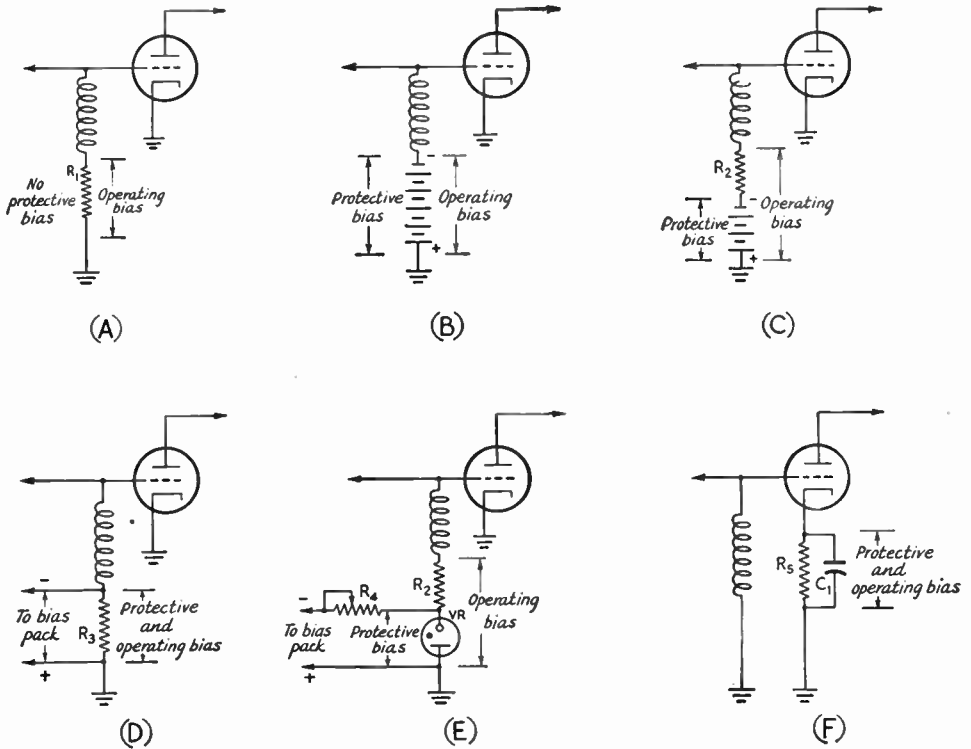


Fig. 6-27 — Various systems for obtaining protective and operating bias for r.f. amplifiers. A — Grid-leak. B — Battery. C — Combination battery and grid leak. D — Grid leak and adjusted-voltage bias pack. E — Combination grid leak and voltage-regulated pack. F — Cathode bias.

tube. The peak voltage output of the transformer used in the power pack must not exceed the operating-bias value. A bleeder resistance cannot be used across the output of the pack, nor can the output voltage be reduced by means of a voltage divider or series dropping resistor without affecting the biasing voltage when excitation is applied.

These restrictions on the use of a power pack can be avoided by the addition of a voltage-regulator tube across the output of the pack, as shown in Fig. 6-27E. The voltage across the regulator tube remains constant with or without grid current flowing. By making the voltage-regulator series resistor,  $R_4$ , of proper value, the output voltage of the pack may be anything within reason above a minimum of approximately twice the voltage rating of the VR tube. These tubes are available for 75, 90, 105 and 150 volts and each tube will handle up to 30 or 40 ma. of grid current. VR tubes may be used in series to obtain regulated voltages above 150, and in parallel for grid currents above 40 ma. It is usual practice to use a VR tube, or combination of VR tubes in series or series-parallel, with the minimum voltage rating which will give plate-current cut-off, and obtain the additional voltage required to bring the total bias up to the operating value by grid-leak action when excitation is applied, as with battery bias in Fig. 6-27C. The use of

VR tubes for this purpose is discussed more fully in Chapter Seven.

A single source of fixed biasing voltage, such as batteries or VR tubes in series, may be used to provide protective bias for more than one amplifier stage, tapping the batteries or connecting to the junction of the tubes in the VR series if lower biasing voltages are required for other stages. In this case, the current flowing through the fixed-bias source is the sum of the individual stages obtaining bias from the source.

In Fig. 6-27F, bias is obtained from the voltage drop across a resistor in the cathode (or filament center-tap) lead. Protective bias is obtained by the voltage drop across  $R_5$  as a result of plate (and screen) current flow. Since plate current must flow to obtain a voltage drop across the resistor, it is obvious that cut-off protective bias cannot be obtained by this system. When excitation is applied, plate (and screen) current increases and the grid current also contributes to the drop across  $R_5$ , thereby increasing the bias to the operating value. Since the voltage between plate and cathode is reduced by the amount of the voltage drop across  $R_5$ , the supply voltage must be the sum of the plate and operating-bias voltages.

The resistance of  $R_5$  should be adjusted to the value which will give the correct operating

bias with rated grid, plate and screen currents flowing with the amplifier loaded to rated input. When excitation is removed, the input to most types of tubes will fall to a value that will prevent damage to the tube, at least for the period of time required to remove plate voltage.

### Calculating Bias-Resistor Values

The calculation of the required grid-leak and cathode biasing-resistor values is not difficult. For simple grid-leak bias, as shown in Fig. 6-27A, the resistance is obtained by dividing the required operating-bias voltage by the rated grid current.

Example: Required operating bias = 100 volts.  
 Rated grid current = 20 ma. = 0.02 amp.  
 Grid-leak resistance =  $\frac{100}{0.02}$  = 5000 ohms.

If a combination of grid-leak and fixed protective bias is used, the amount of protective bias should be subtracted from the required operating-bias voltage before the calculation is made (except in the case of the arrangement of Fig. 6-27D).

Example: Required operating bias = 150 volts.  
 Protective bias from battery or VR tube = 90 volts.  
 150-90 = 60 volts = required bias from grid leak.  
 Rated grid current = 10 ma. = 0.01 amp.  
 Grid-leak resistance =  $\frac{60}{0.01}$  = 6000 ohms.

In the case of a cathode biasing resistor, the rated grid, screen and plate currents under load are added together. The required operating voltage is then divided by this total current to obtain the resistance.

Example: Rated grid current = 15 ma. = 0.015 amp.  
 Rated screen current = 20 ma. = 0.02 amp.  
 Rated plate current = 200 ma. = 0.2 amp.  
 Total rated cathode current = 235 ma. = 0.235 amp.  
 Required operating bias = 150 volts.  
 Cathode resistance =  $\frac{150}{0.235}$  = 638 ohms.

The power rating of the resistor may be determined from Ohm's Law:

$$P = I^2 R$$

Example: In the first example above for grid-leak resistance,  
 $I = 20$  ma. = 0.02 amp.  $I^2 = 0.0004$   
 $R = 5000$  ohms.  
 $P = (0.0004)(5000) = 2$  watts.

Example: In the above example for cathode resistor,  
 $I = 235$  ma. = 0.235 amp.  $I^2 = 0.055$   
 $R = 638$   
 $P = (0.055)(638) = 35.1$  watts.

### Excitation

Excitation, or driving power, is the r.f. power fed to the grid of the amplifier. R.f. power amplifiers in amateur transmitters almost exclusively are operated as Class C amplifiers. A Class C amplifier operates with a relatively high grid-biasing voltage so that plate current flows in pulses over only half or less of the exciting-voltage cycle (operating

angle). It is in this manner that the Class C amplifier operates with high plate efficiency.

For efficient operation a triode amplifier requires a driver capable of delivering 15 to 20 per cent as much power as the rated power output of the amplifier. Screen-grid tubes require much less — usually from 5 to 10 per cent of their rated power output, but the power required by the screen is wasted, since it does not contribute directly to the r.f. power output. Because of their higher power sensitivity, screen-grid tubes require more careful isolation between input and output circuits to prevent self-oscillation.

For the same carrier output, a plate-modulated amplifier requires greater driving power, because the average power input and output increase under modulation. Most tubes, however, have lower ratings for plate-modulated service and therefore the driving power will remain about the same with or without modulation for operation of a given tube at maximum modulated or unmodulated ratings.

To cover tank-circuit and coupling losses, a driver capable of supplying several times the driving power listed in the tube data should be used. A frequency multiplier requires two to three times as much driving power as a straight amplifier, more driving power being required as the multiplying factor increases.

### Power Output

The figure for power output given in the tube data is the r.f. power which the tube can be expected to deliver to the tank circuit under the conditions specified, at the fundamental frequency. Considerably less power usually can be obtained when multiplying frequency. The lower efficiency of frequency multipliers means that the input must be reduced to prevent exceeding the rated dissipation.

### Power Input

Power input for both triodes and screen-grid tubes is the d.c. power input to the plate circuit. It is the product of the d.c. plate voltage and plate current.

Example: Plate voltage = 1250 volts.  
 Plate current = 150 ma. = 0.15 amp.  
 Power input = (1250)(0.15) = 187.5 watts.

### Plate and Screen Dissipation

All of the d.c. power fed to the plate circuit of an amplifier is not converted into r.f. power. Part of it is wasted in heat within the tube. There is a limit to the amount of power that a tube can dissipate in the form of heat without danger of damage to the tube. This is the maximum rated plate dissipation given in tube data. The power dissipated is the difference between the d.c. power input and the r.f. power output.

Since the d.c. power furnished to the screen of a pentode or tetrode does not contribute to the r.f. output, it is entirely dissipated in heat-

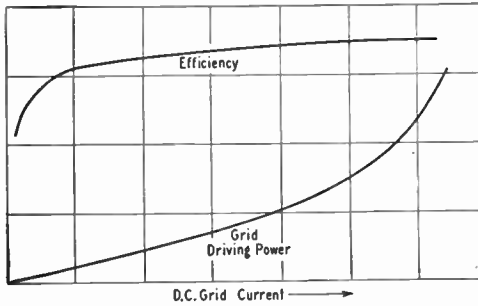


Fig. 6-28 — Curve showing relation between driving power and plate-circuit efficiency of an r.f. power-amplifier stage.

ing the screen, and the maximum-input rating should be carefully observed.

#### Plate Efficiency

The efficiency of an amplifier is the ratio of r.f. power output to the d.c. power input.

$$\begin{aligned} \text{Example: D.c. power input} &= 175 \text{ watts.} \\ \text{R.f. power output} &= 125 \text{ watts.} \\ \text{Dissipation} &= 175 - 125 = 50 \text{ watts.} \\ \text{Efficiency} &= \frac{125}{175} = 0.714 = 71.4 \text{ per cent.} \end{aligned}$$

The plate efficiency at which an r.f. power amplifier can be operated depends chiefly upon the relative driving power delivered to the input circuit. Fig. 6-28 shows that the driving power must be increased considerably out of proportion to the increase in efficiency at the higher efficiencies. An efficiency of 65 to 75 per cent represents a satisfactory balance between power output and driving power. This figure drops to 20 to 50 per cent for frequency multipliers, the efficiency possible decreasing as the order of multiplication increases. When the tube is operated as a straight amplifier, greater driving power than that necessary for reasonable efficiency is not desirable because it results in increased harmonic output.

#### Maximum Plate Current and Voltage

All voltage figures given in tube data, unless otherwise specified, refer to the voltage be-

tween the electrode mentioned and cathode, or filament center-tap. Included are figures for maximum rated plate voltage and plate current. These are the respective maximum values that should be used under any circumstances. Neither should be exceeded to compensate for a lower-than-rated value of the other in attempting to bring the power input up to permissible level. These maximum values should not be used simultaneously unless it is possible to do so without exceeding the rated plate dissipation. In some cases this cannot be done without higher plate efficiencies than are advisable from the consideration of harmonic output.

#### Maximum Grid Current

When a Class C amplifier is properly excited, the grid is driven positive over part of the cycle and rectification takes place as it does in a diode. Rectified grid current flows between grid and cathode within the tube and thence through the external d.c. circuit connecting grid and cathode which must always be provided. This external circuit includes the bias source (grid leak or voltage source) and either the grid r.f. choke with parallel feed, or the tank coil in series-feed arrangements. The flow of rectified current causes heat to be developed at the grid. As with the plate, there is a limit to the heat which the grid can dissipate safely. This limit is expressed in terms of maximum d.c. grid current which should not be exceeded in regular operation of the amplifier. Efficient operation usually can be attained with grid current below the maximum rated value.

#### Interelectrode Capacitances

The value given in tube data for grid-plate capacitance is useful in determining the value of capacitance necessary to neutralize a triode. (See "Neutralized Triode Amplifiers" this chapter.) The input- and output-capacitance values are helpful in arriving at a figure of minimum circuit capacitance, particularly where capacitance coupling is used. (See "Capacitance Coupling" this chapter.)

## Adjustment of R. F. Amplifiers

Sets of typical operating conditions are given in all tube-data sheets and these should be followed closely whenever possible. In amateur service, ICAS (intermittent commercial-amateur service) ratings may be used when this set of ratings is given. When the available plate voltage falls between values given in the data, satisfactory performance may be obtained by using intermediate values for the other voltages and currents listed. Fig. 6-29 shows the connections for a voltmeter and milliammeter to obtain desired readings. While cathode metering often is used for reasons of safety to the operator and meter insulation,

it is frequently difficult to interpret readings that are the resultant of three currents, one of which may be falling while the other two are increasing.

### ● SCREEN-GRID AMPLIFIER ADJUSTMENT

In setting up a screen-grid amplifier for operation, the necessary provisions for bias should be made first. (See "Grid Bias" this chapter.) The driver stage should then be coupled and excitation applied. The output

from the driver should have been checked previously and found to be adequate. When the driver output circuit (and the amplifier grid tank circuit if link coupling is used) is tuned to resonance and properly coupled, a reading of grid current should be obtained. Maximum amplifier grid current should be obtained at the point where the driver plate current dips to minimum.

The value of grid current is influenced by the values of grid-leak resistance and fixed-bias voltage. The grid current will increase with a decrease in grid-leak resistance or fixed biasing voltage. Adequate excitation is indicated only when rated grid current flows when the bias is at the correct operating value with the amplifier loaded.

The coupling to the driver should be adjusted until the grid current is at its maximum rated value or slightly above.

Excitation should then be removed and reduced plate, screen and biasing voltages applied, while a search is made for parasitic oscillations. (See "Parasitic Oscillations" this chapter.) If the screen is fed through a voltage-dropping resistor or voltage divider, plate and screen voltages may be reduced by inserting a 115-volt 50- to 200-watt lamp in series with the primary of the high-voltage transformer, the larger-size lamps being used for higher-power amplifiers. A resistor of 5000 to 10,000 ohms of suitable power rating in series with the high-voltage lead to the amplifier may be used as an alternative, the lower-resistance value being used for higher-power amplifiers.

If the amplifier is entirely stable, no reading of grid current should be obtained at any combination of settings of the input and output tuning condensers without excitation.

The bias may now be increased to its rated value and excitation applied. Readings of screen and plate current should be obtained when excitation is applied. As the plate tank condenser is tuned through its range, the plate current will dip at resonance, while the screen current usually will rise to a peak. The amplifier now may be loaded by coupling it to a following stage, an antenna or a dummy load. As the loading is increased, the plate-current dip at resonance will become less pronounced, indicating that the load is taking power. Each time a change in loading is made, the plate tank circuit should be retuned for the plate-current dip. When the amplifier is partially loaded, the screen and plate voltages may be increased to the full operating value, and the load adjusted to bring the plate current at resonance up to the rated value.

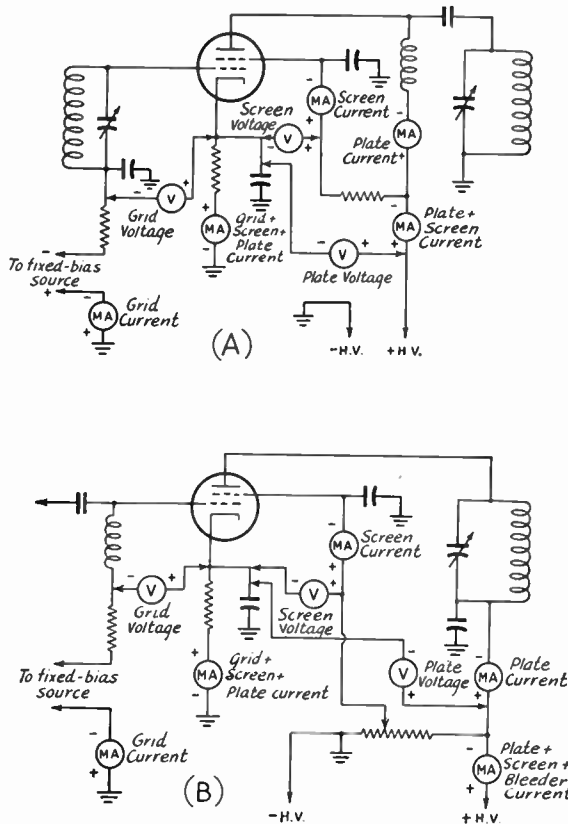


Fig. 6-29 — Diagrams showing placement of voltmeter and milliammeter to obtain desired measurements. A — Series grid feed, parallel plate feed and series screen voltage-dropping resistor. B — Parallel grid feed, series plate feed and screen voltage divider.

With the amplifier operating and fully loaded, the coupling to the exciter should be adjusted to give rated grid current and the biasing voltage checked to make sure that it is the correct operating value. The screen voltage also should be checked at this point if it is being fed through a series resistance or voltage divider.

When operating a screen-grid amplifier more excitation than that required to give maximum output at the operating bias specified should not be used, since overexcitation may increase the screen dissipation unnecessarily. If the screen is fed through a series resistor, overdriving may cause the screen current to increase. This increase in current will cause a greater voltage drop across the series resistor and thus the screen voltage may fall considerably below its correct operating value and the output from the amplifier may suffer accordingly.

When a screen-grid amplifier is operating at rated input and loading, the grid current may be the same, above, or below the value obtained before applying screen and plate voltage, depending upon the screen-voltage adjustment. Screen voltage should never be

applied without first or simultaneously applying plate voltage and load except for short test periods, since without plate voltage and load, the screen input can run to dangerous proportions.

### ● ADJUSTMENT OF TRIODE AMPLIFIERS

Triode amplifiers may be adjusted following the procedure outlined previously for screen-grid tubes (ignoring references to the screen, of course), except that the neutralizing adjustment must be made after the bias and excitation have been initially adjusted. When plate voltage and load are applied to triode amplifiers, the grid current can be expected to fall appreciably below the value obtained without plate voltage or load. Excitation should be sufficient to bring the grid current up to rated value with the amplifier operating and loaded at the rated value of operating bias.

#### *Neutralizing Procedure*

The procedure in neutralizing is essentially the same for all tubes and circuits. The filament of the tube should be lighted and excitation from the preceding stage fed to the grid circuit. There should be no plate voltage on the amplifier.

The grid-circuit milliammeter makes a good neutralizing indicator. If the circuit is not completely neutralized, tuning of the plate tank circuit through resonance will change the tuning of the grid circuit and affect its loading, causing a change in the rectified d.c. grid current. The setting of the neutralizing condenser which leaves the grid current unaffected as the plate tank is tuned through resonance is the correct one. If the circuit is out of neutralization, the grid current will drop perceptibly as the plate tank is tuned through resonance. As the point of neutralization is approached, by adjusting the neutralizing capacitance in small steps the dip in grid current as the plate condenser is swung through resonance will become less and less pronounced, until, at exact neutralization, there will be no dip at all. Further change of the neutralizing capacitance in the same direction will bring the grid-current dip back. The neutralizing condenser should always be adjusted with an insulated screw-driver to avoid hand-capacitance effects.

Adjustment of the neutralizing condenser may affect the tuning of the grid tank or driver plate tank, so both circuits should be retuned each time a change is made in neutralizing capacitance. In neutralizing a push-pull amplifier the neutralizing condensers should be adjusted together, step by step, keeping their capacitances as equal as possible.

With single-ended circuits having split-stator neutralizing, the behavior of the grid meter will depend somewhat upon the type of tube used. If the tube output capacitance is not great enough to upset the balance, the action

of the meter will be the same as in other circuits. With high-capacitance tubes, however, the meter usually will show a gradual rise and fall as the plate tank is tuned through resonance, reaching a maximum right at resonance when the circuit is properly neutralized.

When an amplifier is not neutralized a neon bulb touched to the plate of the amplifier tube or to the plate side of the tuning condenser will glow when the tank circuit is tuned through resonance, providing the driver has sufficient power. The glow will disappear when the amplifier is neutralized. However, touching the neon bulb to such an ungrounded point in the circuit may introduce enough stray capacitance to unbalance the circuit slightly, thus upsetting the neutralizing.

A flashlight bulb connected in series with a single-turn loop of wire  $2\frac{1}{2}$  or 3 inches in diameter, with the loop coupled to the tank coil, also will serve as a neutralizing indicator. Capacitive unbalance can be avoided by coupling the loop to the low-potential part of the tank coil.

If a setting of the neutralizing condenser can be found that gives minimum r.f. current in the plate tank circuit without completely eliminating it, there may be magnetic or capacitance coupling between the input and output circuits external to the tube itself. Short leads in neutralizing circuits are highly desirable, and the input and output inductances should be so placed with respect to each other that magnetic coupling is minimized. Usually this requires that the axes of the coils be at right angles to each other. In some cases it may be necessary to shield the input and output circuits from each other. Magnetic coupling can be detected by disconnecting the plate tank from the remainder of the circuit and testing for r.f. in it (by means of the flashlight lamp and loop) as the tank condenser is tuned through resonance. The driver stage must be operating while this is done, of course.

With single-ended amplifiers there are many stray capacitances left uncompensated for in the neutralizing process. With large tubes having relatively high interelectrode capacitances, these commonly-neglected stray capacitances can prevent perfect neutralization. Symmetrical arrangement of a push-pull stage is about the only way to obtain practically perfect balance throughout the amplifier.

The neutralization of tubes with extremely low grid-plate capacitance, such as the 6L6, is often difficult, since it frequently happens that the wiring itself will introduce sufficient capacitance between the right points to "over-neutralize" the grid-plate capacitance. The use of a neutralizing condenser only aggravates the condition. Inductive or link neutralization has been used successfully with such tubes.

#### *Neutralizing Condenser*

In most cases the neutralizing voltage will be equal to the r.f. voltage between the plate and

grid of the tube, so that for perfect balance the capacitance required in the neutralizing condenser theoretically will be equal to the grid-plate capacitance. If, in the circuits having tapped tank coils, the tap is more than half the total number of turns from the plate end of the coil, the required neutralizing capacitance will increase approximately in proportion to the relative number of turns in the two sections of the coil.

With tubes having grid and plate connections brought out through the bulb, a condenser having at about half scale or less a capacitance equal to the grid-plate capacitance of the tube should be chosen. If the grid and plate leads are brought through a common base the capacitance needed is greater, because the tube socket and its associated wiring add some capacitance to the actual interelement capacitances.

## ● PARASITIC OSCILLATIONS

Parasitic oscillations are oscillations at frequencies other than the operating frequency, which are frequently encountered in the operation of an r.f. power amplifier. Oscillations of this type not only cause the transmission of illegal spurious signals but impair the efficiency of operation. In fact, they can be so severe as to make operation of the stage as an amplifier impossible and may destroy the tube if they are allowed to persist for any appreciable time. Parasitic oscillations may be responsible for erratic tuning characteristics.

Two types are often found to exist either separately or together. The simultaneous use of r.f. chokes in both grid and plate circuits of an amplifier can set up a t.g.t.p. oscillator at low frequencies with the aid of coupling and plate-blocking condensers. A split-stator condenser also can serve to tune the r.f. choke with which it is often associated in either the plate or grid tank circuit. Low-frequency parasitic oscillation sometimes can be detected by listening on a receiver close to the transmitter, when harmonics, usually rough in character, may be heard at regular intervals that are multiples of the fundamental frequency which

may lie anywhere between 1500 kc. and 100 kc. or less. On a calibrated receiver, the fundamental frequency can be determined by observing the spacing between adjacent harmonics. The low-frequency parasitic circuit can be eliminated by using series feed in either grid or plate circuit, thus avoiding the necessity for one of the r.f. chokes. In the case of split-stator tank circuits, the grid r.f. choke can be eliminated if a grid leak is used. When a split-stator plate tank is used with an r.f. choke between the rotor of the condenser and the center-tap of the coil, it will be necessary to use series feed in the grid circuit if the stage is capacitance-coupled to the driver, since the plate radio-frequency choke is essential.

V.h.f. parasitic oscillations usually are the result of a t.g.t.p. circuit set up by connecting leads and capacitances shunting them. When screen-grid tubes are used, they usually can be eliminated by inserting a 50-ohm non-inductive resistor at the screen terminal and a v.h.f. choke at the grid, as shown in Fig. 6-30. With triodes, the choke at the grid terminal usually will kill the parasitic, but sometimes a trap circuit tuned to the frequency of the parasitic is necessary, as shown at C. With the circuit oscillating parasitically, the trap condenser should be adjusted with an insulated screwdriver. When the trap is tuned to the parasitic frequency, oscillation will cease. The frequency range over which the condenser will tune can be altered by spreading or squeezing together the turns of the coil.

Amplifiers can be tested for parasitics by lowering plate (and screen) voltage to about half normal operating value and then reducing the fixed bias, if necessary, until the tube draws 50 per cent or so of normal plate current without excitation. The plate tank condenser should be swung through its range for several different settings of the grid tank condenser or, in the case of capacitance coupling, the plate tank condenser of the driver. If a grid-current reading is obtained, oscillation is taking place. The frequency of the oscillation can be determined by means of an absorption-type frequency meter (see Chapter Sixteen).

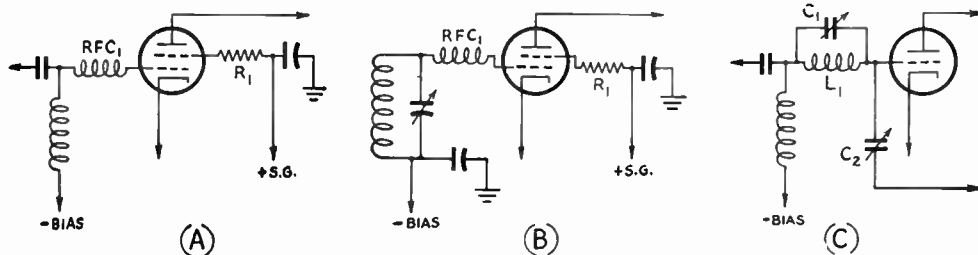


Fig. 6-30 — Methods of suppressing v.h.f. parasitic oscillation in r.f. power amplifiers. A — Parallel grid feed. B — Series grid feed. C — Tuned trap in grid lead. Exact values must be determined experimentally. Approximate values are as follows:

$C_1$  — 30- $\mu$ fd. mica trimmer condenser.

$R_1$  — 50 ohms, 1 watt, noninductive.

$L_1$  — 5 turns No. 14,  $\frac{1}{2}$ -inch diameter,  $\frac{1}{2}$  inch long.

$RFC_1$  — 11 turns No. 20,  $\frac{5}{16}$ -inch diameter,  $\frac{3}{4}$  inch long, wound on 1-watt resistor, 0.1 megohm or more, as a form.

Parasitic oscillation should not be confused with oscillation at or close to the operating frequency caused by insufficient isolation between input and output circuits.

● IMPROPER OPERATION

Inexact neutralization of stray coupling between plate and grid circuits may result in regeneration. This effect is most evident with low excitation, when the amplifier will show a sudden increase in output when the plate tank circuit is tuned slightly to the high-frequency side of resonance. It is accompanied by a pronounced increase in grid current.

Self-oscillation is apt to occur with tubes of high power sensitivity, such as the r.f. pentodes and tetrodes. In event of either regeneration or oscillation, circuit components should be arranged so that those in the plate circuit are well isolated from those of the grid circuit. Plate and grid leads should be made as short as possible and the screen should be by-passed as close to the socket terminal as possible. A cylindrical shield surrounding the lower portion of the tube up to the lower edge of the plate is sometimes required.

“Double resonance,” or two tuning spots on the plate-tank condenser, one giving minimum plate current and the other maximum power output, may occur when the tank-circuit capacitance is too low. A similar effect also occurs at times with screen-grid amplifiers when the screen-voltage regulation is poor, as when the screen is supplied through a dropping resistor. The screen voltage decreases with a decrease in plate current, because the screen current

increases under the same conditions. Thus the minimum plate-current point causes the screen voltage, and hence the power output, to be less than when a slightly higher plate current is drawn.

A phenomenon known as “grid emission” may occur when the amplifier tube is operated at higher than rated power dissipation on either the plate or grid. It is particularly likely to occur with tubes having oxide-coated cathodes, such as the indirectly-heated types. It is caused by the grid reaching a temperature high enough to cause electron emission. The electrons so emitted are attracted to the plate, further increasing the power input and heating, so that grid emission is characterized by gradually-increasing plate current and heat which eventually will ruin the tube if the power is not removed. Grid emission can be prevented by operating the tube within its ratings.

Harmonic Suppression

The most important step in the elimination of harmonic radiation is to use an output tank circuit having a  $Q$  of 12 or more. (See “Tank-Circuit Design” this chapter.) Beyond this it is desirable to avoid any considerable amount of overexcitation of a Class C amplifier, since excitation in excess of that required for normal Class C operation further distorts the plate-current pulse and increases the harmonic content in the output of the amplifier even though the proper tank  $Q$  is used. If the antenna system in use will accept harmonic frequencies they will be radiated when distortion is present, and consequently the antenna coupling system preferably should be selected with harmonic transfer in mind (see Chapter Ten).

Harmonic content can be reduced to some extent by preventing distortion of the r.f. grid-voltage waveshape. This can be done by using a grid tank circuit with high effective  $Q$ . Link coupling between the driver and final amplifier is helpful, since the two tank circuits provide more attenuation than one at the harmonic frequencies. However, the advantages of link coupling in this respect may be nullified unless the  $Q$  of the grid tank is high enough to give good voltage regulation, which minimizes harmonic transfer and thus prevents distortion in the grid circuit.

● CHECKING POWER OUTPUT

As a check on the operation of an amplifier, its power output may be measured by the use of a load of known resistance, coupled to the amplifier output as shown in Fig. 6-31. At A a thermoammeter,  $A$ , and a noninductive (ordinary wire-wound resistors are not satisfactory) resistance,  $R$ , are connected across a coil of a few turns coupled to the amplifier tank coil. The higher the resistance of  $R$ , the greater the number of turns required in the coupling coil. A resistor used in this way is generally called a “dummy antenna.” The loading may

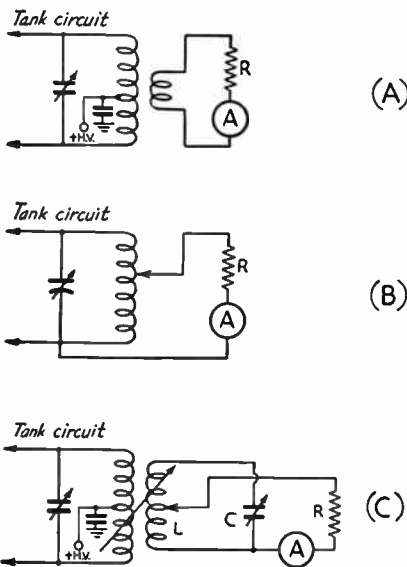


Fig. 6-31 — “Dummy antenna” circuits for checking power output and making adjustments under load without applying power to the actual antenna.



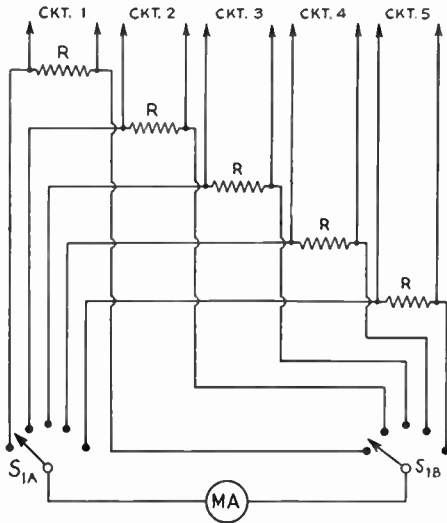


Fig. 6-32 — Method of switching single milliammeter to various circuits with a two-gang switch. The control shaft should be well insulated from the switch contacts, and should be grounded. The resistors, *R*, should have values of resistance ten to twenty times the internal resistance of the meter; 47 ohms will usually be satisfactory. *S*<sub>1</sub> is a 2-section multiposition rotary switch. Its insulation should be ceramic for high voltages, and a suitable insulating coupling should always be used between shaft and control knob.

readily be adjusted by varying the coupling between the two coils, so that the amplifier draws rated plate current when tuned to resonance. The power output is then calculated from Ohm's Law:

$$P \text{ (watts)} = I^2 R$$

where *I* is the current indicated by the thermammeter and *R* is the resistance of the non-inductive resistor. Special resistance units are available for this purpose, ranging from 73 to 600 ohms (simulating antenna and transmission-line impedances) at power ratings up to 100 watts. For higher powers, the units may be connected in series-parallel. The meter scale required for any expected value of power output may also be determined from Ohm's Law:

$$I = \sqrt{\frac{P}{R}}$$

Incandescent light bulbs can be used to re-

place the special resistor and thermoammeter. The lamp should be equipped with a pair of leads, preferably soldered to the terminals on the lamp base. The coupling should be varied until the greatest brilliance is obtained for a given plate input. In using lamps as dummy antennas a size corresponding to the expected power output should be selected, so that the lamp will operate near its normal brilliancy. Then, when the adjustments have been completed, an approximation of the power output can be obtained by comparing the brightness of the lamp with the brightness of one of similar power rating in a 115-volt socket.

The circuit of Fig. 6-31B is for resistors or lamps of relatively high resistance. In using this circuit, care should be taken to avoid accidental contact with the plate tank when the power is on. This danger is avoided by circuit *C*, in which a separate tank circuit, *LC*, tuned to the operating frequency, is coupled to the plate tank circuit. The loading is adjusted by varying the number of turns across which the dummy antenna is connected on *L* and by changing the coupling between the two coils. With push-pull amplifiers, the dummy antenna should be tapped equally on either side of the center of the tank when the circuit of Fig. 6-31B is used.

### Meter Switching


A single milliammeter may be switched to read current in any of several different circuits. The circuit is shown in Fig. 6-32. The resistors, *R*, are connected in the various circuits in place of the milliammeters shown in Fig. 6-29. Since the resistance of *R* is several times the internal resistance of the milliammeter, it will have no practical effect upon the reading of the meter.

When the meter must read currents of widely differing values, a meter with a range sufficiently low to accommodate the lowest values of current to be measured may be selected. In the circuits in which the current will be above the scale of the meter, the resistance of *R* can be adjusted to a lower value which will give the meter reading a multiplying factor. (See Chapter Sixteen.) Care should be taken to observe proper polarity in making the connections between the resistors and the switch.

### Filament and Cathode Connections

In the illustrative diagrams shown up to this point, cathodes have been indicated in all

Fig. 6-33 — Filament connections for transmitting tubes. The by-pass condensers usually are 0.01- $\mu$ fd. paper for frequencies up to 30 Mc. The center-tap resistor may be any low value of 10 to 50 ohms and may be made up of two identical resistors of half value.

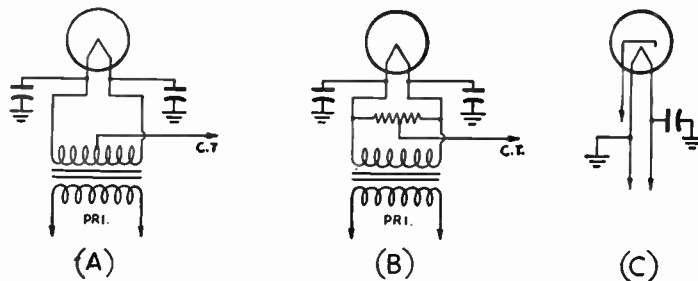

tubes for the sake of facilitating the understanding of the circuits and their operating principles. Actually, only the lower-power transmitting tubes have cathodes of this type. In the larger tubes which have no cathodes as such, the filament itself serves as the cathode and the cathode connections shown are actually made to the center-tap of the filament transformer, as shown in Fig. 6-33A or, if the transformer has no center-tap, to the center of a low resistance connected across the filament, as shown at B. Each side of the filament usually is by-passed as shown.

In the case of cathode-type tubes, the heater

sometimes is grounded directly as shown in Fig. 6-33C; the other side sometimes is by-passed and sometimes is not, as found necessary to minimize hum.

In the descriptions of apparatus to follow, not only the electrical specifications but also the manufacturer's name and type number have been given for many components. This is for the convenience of the builder who may wish to make an exact copy of some piece of equipment. However, it should be understood that a component of different manufacture, provided it has the same electrical specifications, may be substituted in most cases.

## A Simple Single-Tube Transmitter

One of the simplest practical transmitters is shown in the photographs of Figs. 6-34 and 6-36. If the station receiver has a power audio stage which is not required for headphone reception, the tube may be taken from the receiver and used in the transmitter (provided that the tube is a pentode or tetrode as it usually is). A plug inserted in the empty socket in the receiver may be used to obtain power for operating the transmitter.

The circuit is shown in Fig. 6-35. The Tri-tet oscillator circuit is used to permit operation in either the 3.5-Mc. band or the 7-Mc. band with a single 3.5-Mc. crystal. Series plate feed is used and no means of reducing the voltage of the screen below that of the plate is necessary if the supply potential does not exceed 250 to 300 volts.

The cathode circuit is tuned by a fixed mica condenser,  $C_1$ , but if necessary, the tuning of this circuit can be changed by changing the dimensions of the coil,  $L_1$ .

No provision is included for tuning the antenna system, for the sake of maximum sim-

licity. This can be done by selecting the proper feeder length and adjusting the size of the antenna coupling coil,  $L_3$ .

### Construction

To minimize the tools required for the construction of the transmitter the parts are mounted on a simple chassis of wood finished with clear lacquer or shellac. Two  $1\frac{3}{4} \times 9\frac{3}{4}$ -inch strips of  $\frac{1}{2}$ -inch-thick wood are fastened with screws to the two  $4\frac{1}{2} \times 2\frac{1}{2} \times \frac{3}{4}$ -inch end pieces, leaving enough separation between the strips for the Amphenol MIP octal sockets used for the crystal and the socket for the tube. Wood screws can be used to mount the sockets, or they can be bolted to the wood strips with 6-32 machine screws. The key of the tube socket should be mounted toward the front of the transmitter for convenience in wiring the plate circuit to the tuning condenser. Because the tuning condenser does not have a long mounting shank, it is necessary to drill a clearance hole for the shank and then dig away — or counterbore — clearance for the nut. The two Fahnestock clips for the antenna are secured under two of the screws used for fastening the wood strips to the right-hand end piece, and the other two clips used for the key leads are held down by machine screws on the left-hand end piece. The r.f.

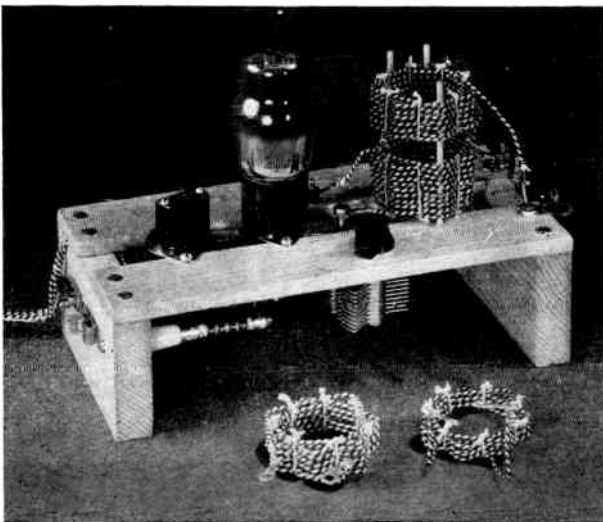


Fig. 6-34 — By using wood for the chassis and simplified construction throughout, this simple oscillator transmitter can be built with very few shop tools. Using a 3.5-Mc. crystal, operation in the 3.5- and 7-Mc. bands is possible by changing the plate and antenna coils. The arrangement is suitable for 6F6, 6V6 or other similar pentodes and tetrodes.

choke is held in place on the left-hand end piece by a machine screw. The four wires used for a power cable are brought out at the rear left under the wood strip — a half-round hole is filed in the end piece to clear the wires.

The plate and antenna coils are held in place on three small sticks set in the top of the chassis — penny suckers are a good source of these sticks. The bottom of the plate coil connects to a brass machine screw soldered to a lug which is sweated to the stator terminal of the tuning condenser, and the screw is built up most of its length by adding nuts or small spacers. The screen end of the coil, the top end of the winding, is fastened to a brass screw that runs through the rear wood strip. The coil ends have lugs soldered to them to facilitate band-changing. The antenna-coil ends similarly fasten to two brass screws supported by short lengths of heavy wire and the wire is sweated to the Fahnestock clips and to the heads of the screws.

### Wiring

The wiring is done with the same wire that is used for the coils, because a single 50-foot roll of No. 18 bell wire, available in any "5 & 10" or hardware store, suffices for the whole rig with some to spare. To insure good electrical connection, the wire is soldered at every connection, which means that the wire is soldered to the heads of the brass machine screws used for the key leads and the screen end of  $L_2$  before the screws are put in place. One key lead, one end of  $R_1$ , the outer foil

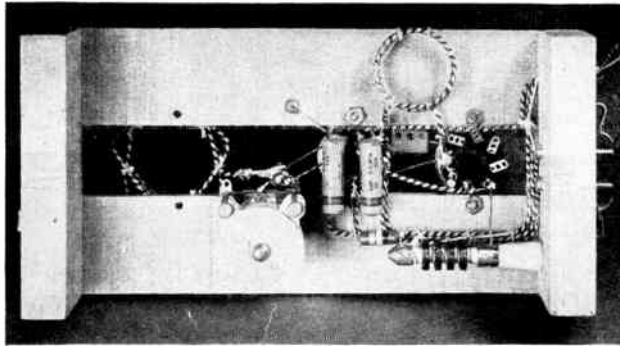


Fig. 6-36 — Bottom view of the simple single-tube transmitter. The cathode coil is between the tube and crystal sockets. The r.f. choke is to the right,  $C_4$  is at left center with the two by-pass condensers,  $C_2$  and  $C_3$ , to the right of it.

connections on  $C_2$  and  $C_3$ , and the lead to Pin 1 of the power plug must be connected to Pin 1 of the tube socket. At the crystal socket, two adjacent pins (e.g., 1 and 8) are bonded together for the grid side of the crystal and the next two pins (e.g., 2 and 3) are bonded together for the cathode side. This permits plugging the crystal into either Pins 8 and 2 or 1 and 3. The connection can be elaborated still further by bonding Pins 4 and 5 with 8 and 1 and tying 6 and 7 to 2 and 3, in which case the crystal can be plugged in any way and it will make the proper connection.

The cathode coil, consisting of 5 turns of No. 18 bell wire, is wound on a 1¼-inch diameter form and then removed and tied with string at a number of places. The cathode coil is mounted by its leads only but, being short, they offer adequate support.

The plate and antenna coils are wound by equally spacing seven nails on a 2-inch diameter circle, driving the nails completely through the board used so that the heads are flush against the board. Small spikes can be used, or nails of the "8-penny" size will be satisfactory if a thin board is used. One end of the wire is secured to a nail and the wire is threaded over alternate nails, so that the coil repeats itself every two turns. When the required number of turns has been made, the end of the wire is wrapped around a nail and the coil tied together with string at the seven cross-over points. Soldering lugs are soldered to the ends of the coil for ease in changing bands.

The four wires coming out the side of the chassis that go to the power plug are twisted together slightly and cabled with string to form a neat cable, and the cable plug,  $P_1$ , is simply the base from an old tube. If the receiver is to be used as a source of power, the base should be one that will fit the power-output tube in the receiver. Break the tube and chew out the glass from inside the base with a pair of pliers, being careful not to break the bakelite of the base. It will help in making connection to the proper pins if a small drill, slightly larger than the diameter of the No. 18 wire, is run through

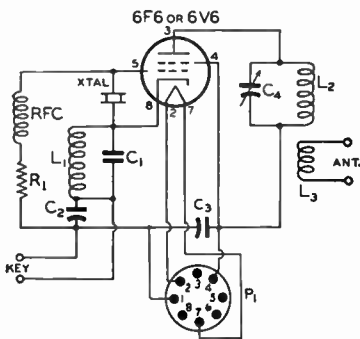



Fig. 6-35 — Wiring diagram of the inexpensive easy-to-build transmitter.

- $C_1$  — 470- $\mu$ fd. mica.
- $C_2, C_3$  — 0.01- $\mu$ fd. 600-volt paper.
- $C_4$  — 140- $\mu$ fd. variable (Hammarlund SM-140 or Bud MC-1876).
- $R_1$  — 0.1-megohm 1-watt composition.
- $L_1$  — 5 turns No. 18 d.c.c., 1¼-inch inside diameter, close-wound.
- $L_2$  — 3.5 Mc.: 19 turns, 7 Mc.: 12 turns.
- $L_3$  — 13 turns and 6 turns. Requires experiment — see text. See text for  $L_2$  and  $L_3$  winding instructions.
- $P_1$  — See text.
- RFC — 2.5-mh. r.f. choke (National R-100L).

the pins before the wires are inserted and soldered in place.
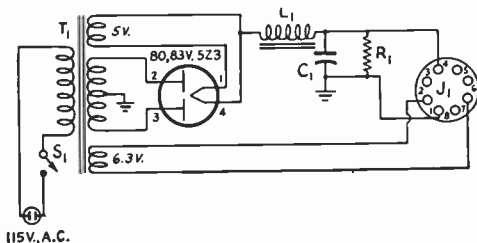
### Tuning

After checking the wiring, plug in a crystal and connect the 7-Mc. coil in place. Place the audio tube from the receiver in the transmitter and plug in the power cable, and connect a key to the clips on the side of the transmitter. If the receiver has push-pull output, it is probably best to remove both power tubes. Set the tuning condenser,  $C_4$ , at about 40 per cent meshed and turn on the power to the receiver. When the tube has had time to warm up — about 30 seconds — close the key and



115V. A.C.

Fig. 6-37 — Circuit diagram of alternative power supply for the simple single-tube transmitter.

$C_1$  — 8- $\mu$ fd. 450-volt electrolytic.

$R_1$  — 25,000 ohms, 10 watts.

$L_1$  — Filter choke — any receiver replacement type, 15 hy. or more, 50 ma. or more.

$J_1$  — 8-prong tube socket.

$S_1$  — S.p.s.t. toggle switch.

$T_1$  — Power transformer — any receiver replacement type, not over 750 volts c.t., 50 ma. or more.

touch a neon bulb to the plate end of  $L_2$ . Or a small 10-watt electric lamp can be connected to the antenna posts with the 6-turn antenna coil in place. If  $C_4$  is set properly, the neon bulb will glow or the lamp will light. If this does not happen, try tuning the plate condenser until signs of output become apparent. The transmitter can then be checked on the 3.5-Mc. band by putting in the proper coils — remembering, however, to turn off the receiver and hold the key closed until the power pack of the receiver has been discharged, to avoid getting a shock when touching the coil terminals. The tuning condenser setting will be about 85 per cent meshed on the lower-frequency band.

It will not be possible in most cases to check the keying on the receiver used to furnish

power to the transmitter, and it is highly advisable to check the keying in a monitor or another receiver. If the keying is chirpy, the cathode coil,  $L_1$ , should be squeezed out of round to reduce its inductance until the keying is better. On the 3.5-Mc. band, best keying will generally be obtained with slightly less capacity at  $C_4$  than the setting for maximum output. In the oscillator shown in the photographs, a slight key click on "break" was reduced almost completely by connecting a 0.1- $\mu$ fd. 600-volt paper condenser directly across the key. Some crystals key better than others.

### Antennas

A 135-foot piece of wire for the antenna can be fed in several ways to give satisfactory results. It can be fed at one end with about 40 feet of open-wire feeders (about 32 feet of Amphenol 300-ohm Twin-Lead) or it can be fed in the center with 100 feet of open-wire feedline (about 80 feet of 300-ohm Twin-Lead). These lengths will enable one to connect the feedline directly to the antenna posts of the transmitter without the necessity for tuning condensers — other lengths may require either series or parallel condensers. Some experiment with the antenna coil may be necessary, but a small flashlight bulb in series with one of the feeders will serve as a good indication of feeder current, and will help in the tune-up process. The lamp need not be shorted during normal operation unless it burns too brightly. A neon bulb will also help in detecting r.f. energy in the transmission line, but it may not always light with this low power.

If room for only a short length of wire is available for the antenna, say 40 or 50 feet, it is best to connect its end to one antenna post and a good ground to the other. Here again some experimentation will be necessary to determine the optimum size of  $L_3$ . The diagram of a suitable alternative power supply is shown in Fig. 6-37.

The power can be increased by substituting a 6L6 for a smaller tube and adding a separate power supply to give 350 volts at 100 ma., but it is not advisable to increase the voltage much above this value without keeping the screen voltage down by the addition of a dropping resistor and another by-pass condenser.

## An Inexpensive Two-Tube Transmitter


Figs. 6-38, 6-40 and 6-41 show the construction of another simple low-power transmitter capable of about twice the output of that from the simple oscillator transmitter. It is shown complete with power supply in Fig. 6-38. The circuit diagram appears in Fig. 6-39. The arrangement consists of a Pierce crystal oscillator and capacitance-coupled to an output stage which may be used either as a straight amplifier at the crystal frequency or as a frequency doubler to deliver output at twice the crystal fre-

quency. This combination has the advantage over a simple oscillator transmitter in that the oscillator is isolated from the effects of tuning and loading. Type 6L6, 6V6 or 6F6 tubes, or their glass equivalents, may be used in either the oscillator or amplifier with only a slight difference in performance at the supplied plate voltage.

By the use of the proper coil at  $L_1$ , output may be obtained at 3.5 or 7 Mc. with a 3.5-Mc. crystal or at 7 or 14 Mc. with a 7-Mc. crystal.

Fig. 6-38 — The complete low-power two-tube transmitter. In the r.f. unit in the foreground, left to right, are the 5-prong socket for the power plug, octal sockets for the crystal, oscillator tube and amplifier tube, and the output tank condensers,  $C_9$  and  $C_{10}$ , with the coil  $L_1$  in between.

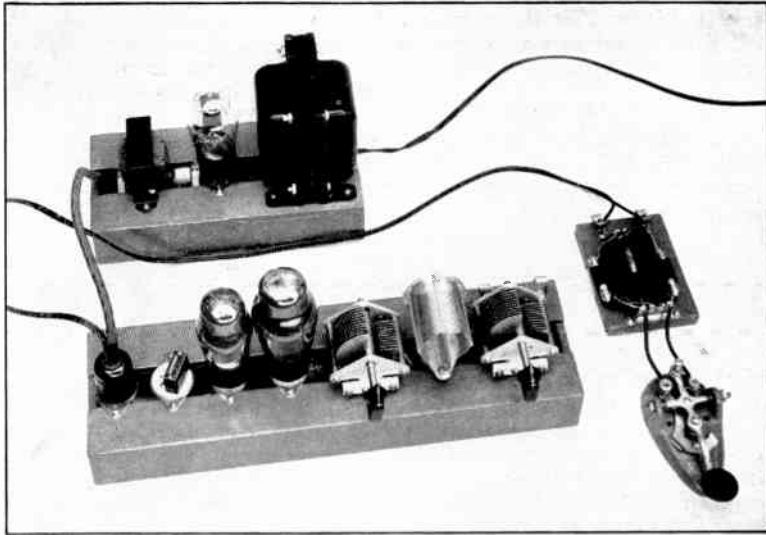On the power-supply chassis at the rear are the filter choke,  $L_2$ , the Type 80 rectifier tube and the power transformer. The filter condensers,  $C_{11}$  and  $C_{12}$ , and the bleeder resistor,  $R_9$ , are underneath. The key-click filter is to the right.



The amplifier input is not tuned so that neutralization is unnecessary.  $C_2$  provides regeneration; its value should not depart appreciably from that specified. The output tank circuit is in the form of a pi-section filter which makes it possible to use the transmitter with a wide variety of antenna systems.

Parallel plate feed is used in the output stage to remove plate voltage from the tuning con-

densers and the coil. Plate voltage is reduced for the oscillator by the series resistor,  $R_8$ , while screen voltage is obtained from the voltage divider made up of  $R_2$  and  $R_3$ . In the amplifier section, the screen voltage is obtained from the second voltage divider consisting of  $R_6$  and  $R_7$ . Grid bias for the oscillator is obtained from the grid leak,  $R_1$ , alone, while a combination of cathode resistor ( $R_5$ ) and grid


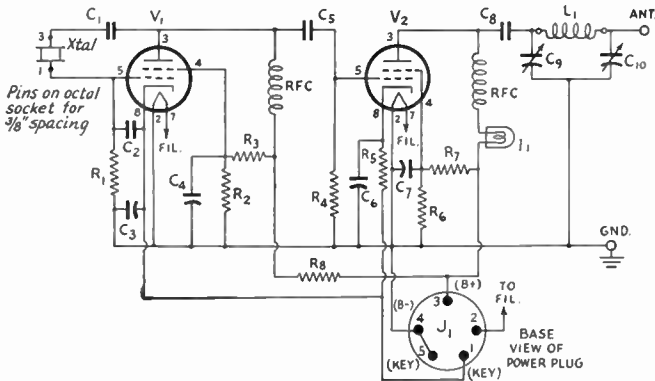


Fig. 6-39 — Circuit diagram of the low-powered two-tube transmitter, power supply and keying filter.

- $C_1, C_8$  — 0.001- $\mu$ fd. mica.
- $C_2, C_5$  — 100- $\mu$ fd. mica.
- $C_3, C_4, C_6, C_7$  — 0.01- $\mu$ fd. paper.
- $C_9, C_{10}$  — 250- $\mu$ fd. variable (National TMS 250).
- $C_{11}, C_{12}$  — 16- $\mu$ fd. 475-volt electrolytic.
- $C_{13}$  — 1- $\mu$ fd. 400-volt paper.
- $C_{14}$  — 0.5- $\mu$ fd. 400-volt paper.
- $R_1, R_3$  — 47,000 ohms, 1 watt.
- $R_2, R_6$  — 0.1 megohm, 1 watt.
- $R_4$  — 22,000 ohms,  $\frac{1}{2}$  watt.
- $R_5, R_{10}$  — 330 ohms, 1 watt.
- $R_7, R_8$  — 15,000 ohms, 2 watts.
- $R_9$  — 20,000 ohms, wire-wound, 10 w.
- $L_1$  — 3.5 Mc.: 32 turns No. 20 d.s.c.,  $1\frac{1}{2}$ -inch diam., close-wound.
- 7 Mc.: 20 turns No. 20 enam.,  $1\frac{1}{2}$ -inch diam.,  $1\frac{1}{2}$  inches long.
- 14 Mc.: 10 turns No. 18 enam.,  $1\frac{1}{2}$ -inch diam., 1 inch long.
- (B & W JEL80, "40" or "20" coils may be substituted.)
- $L_2$  — Filter choke, 10 hy., 130 ma. (Stancor C-2303).
- $I_1$  — 60-ma. dial-lamp assembly.
- $J_1$  — 5-prong chassis-mounting plug.
- $P_1$  — 5-prong female cable plug.
- RFC — 2.5-mh. r.f. choke.
- T — Power transformer: 350 volts each side of center, 100 ma.; 5 v., 3 amp.; 6.3 v., 4.5 amp. (Stancor P-4080).
- $V_1, V_2$  — 6V6, 6L6, 6F6 or glass equivalents.
- $V_3$  — Type 80 rectifier.

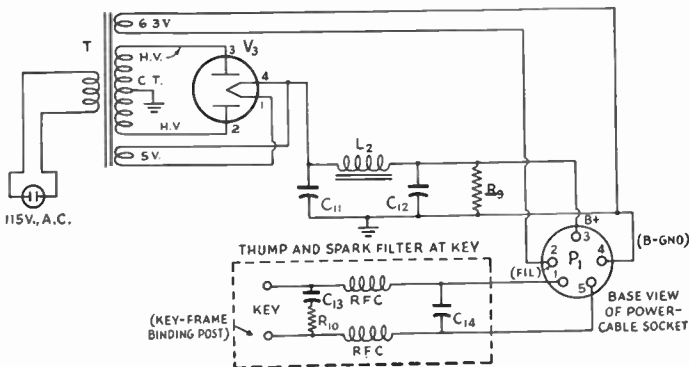

leak ( $R_4$ ) is used for the amplifier. A 60-ma. dial lamp serves as a resonance indicator in tuning up the transmitter.

### Construction

The chassis or frame is made entirely from lattice strip,  $1\frac{1}{2}$  inches wide and  $\frac{1}{4}$  inch thick. The sketch of Fig. 6-41 shows how the strips are fastened together with 1-inch wire brads. The  $1\frac{1}{4}$ -inch spacing between the top strips is appropriate for Millen sockets, but it can be changed to suit sockets of other dimensions, of course.

The completed chassis was given a couple of coats of gray Duco. The sockets are fastened in place by means of small wood screws and are orientated so that most-convenient connections may be made. The power-plug socket has its metal-ring key to the left, the oscillator tube-socket key is to the right, the amplifier tube socket toward the front and the coil socket toward the left.

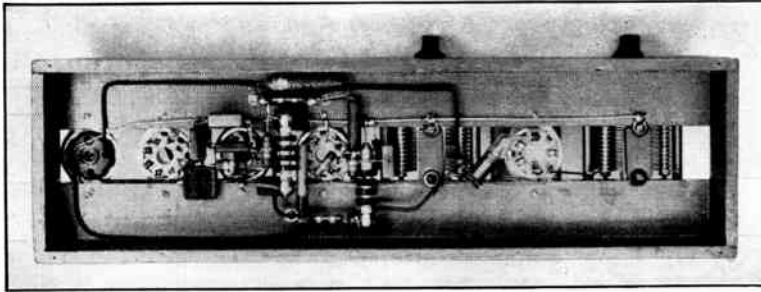


Fig. 6-40 — Bottom view of the 2-tube low-power transmitter. The by-pass condensers, r.f. chokes and resistors are grouped around the tube sockets. The ground wire mentioned in the text runs along the top edge of the lower chassis strip. The indicator lamp,  $I_1$ , is wired in the B+ line just below the amplifier plate r.f. choke. It is placed underneath the chassis where it can be viewed from above through the opening between the chassis strips. The r.f. choke to the right is in the amplifier and the one to the left is in the oscillator circuit.

All wiring is done underneath. The ground wire is a piece of No. 14 bare wire which runs the length of the chassis from the No. 4 prong on the power-supply socket to the rotor of  $C_{10}$ . To this wire all ground connections shown in the diagram are made. Connections to by-pass condensers and r.f. chokes should be as short as possible, the by-pass condensers being connected to the nearest point on the ground wire. A pair of fiber lug strips provides anchorage for resistors and r.f. chokes. "Hot" r.f. leads (those from the plates and control grids of the tubes and the connections between the tuning condensers and the coil) should be short and direct instead of going around right-angle bends. The output terminals are Fahnestock clips fastened to the two sides of  $C_{10}$ .

Homemade coils may be constructed by winding them, according to the dimensions given under Fig. 6-39, on Hammarlund  $1\frac{1}{2}$ -inch diameter 5-prong coil forms. Those shown in the photograph are the B & W JEL series.

Inexpensive components are used in the power supply. The transformer is a broadcast-

receiver replacement type as are the filter components. The chassis is similar to that used for the transmitter, the only difference being in the length —  $9\frac{1}{2}$  inches instead of  $15\frac{1}{2}$  inches. The filter condensers, and the bleeder resistor,  $R_9$ , are placed underneath.

The key-click filter is a separate unit assembled on a small piece of  $\frac{1}{4}$ -inch wood. The connecting leads and the leads to the key should be short if the filter is to be effective. The side of the filter connected to power-plug Pin 5 should be connected to the frame of the key.

### Adjustment

The transmitter should first be tuned up without the antenna connected. It should be remembered that only the second harmonic of crystals between 3500 and 3650 kc. and between 7000 and 7200 kc. are useful in the higher-frequency amateur bands. With a suitable crystal and coil plugged in, the

power supply may be plugged in and the key closed after allowing time for the heaters of the tubes to come up to temperature. The indicator lamp should glow brightly when the key is closed. Setting  $C_{10}$  at about half capacitance,  $C_9$  should be adjusted as  $I_1$  is watched for a dip in illumination. If this dip cannot be found anywhere within the range of

$C_9$ , another setting of  $C_{10}$  should be tried. As soon as the dip has been found, the antenna may be connected, and the tuning process repeated as before. With the antenna connected the dip at resonance will not be so pronounced. In fact, when the amplifier is loaded properly, the dip should be just noticeable — just enough to indicate that the output circuit is tuned to resonance. The proper loading point may be found by adjusting  $C_{10}$  at several fixed settings and rotating  $C_9$  through its range for each setting of  $C_{10}$ . As the proper point is approached, the capacitance of  $C_{10}$  should be adjusted in smaller steps. In most cases the loading will increase as the capacitance setting of  $C_{10}$  is decreased. Near maximum loading, the adjustment is fairly critical. With antennas of certain dimensions, it may be necessary to short-circuit a few turns on  $L_1$  to obtain maximum loading in the 3.5-Mc. band.

While the best antenna within the limits of cost and space should be used, the output circuit provides means of feeding power into a wire of random length; it is not necessary that

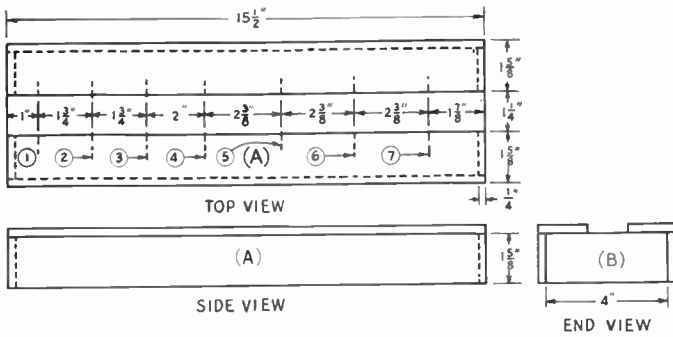


Fig. 6-41 — Sketch showing the important dimensions of the chassis for the simple two-tube transmitter. The center lines are numbered as follows: 1 — power plug, 2 — crystal socket, 3 — oscillator-tube socket, 4 — amplifier-tube socket, 5 — tuning condenser,  $C_2$ , 6 — coil socket, 7 — condenser  $C_{10}$ .

its length be a multiple of a half-wavelength. With the power supply described, an output of about 10 watts should be possible at the crystal fundamental; and 5 or 6 watts when the output stage is used as a frequency doubler. If a milliammeter is connected in series with the key, it should show a reading of about 20 ma. with the amplifier tuned to resonance and un-

loaded at the crystal fundamental, and about 40 ma. when doubling. Loaded, the plate current should run between 70 and 80 ma. With a power-supply voltage of 350, the oscillator plate voltage should be 170, the oscillator screen voltage 90, and the amplifier screen voltage 220, with the amplifier loaded and tuned to resonance.

## A Self-Contained 60-Watt Transmitter for Three Bands

The diagram of Fig. 6-43 shows the circuit of a simple two-stage transmitter. The finished unit, shown in Fig. 6-42, is enclosed in a cabinet, complete with power supply and antenna tuner.

A 6V6GT Tri-tet oscillator drives an 807 output stage directly with simple capacitive coupling. Any one of ten crystals may be selected from the front of the panel by the crystal switch,  $S_1$ . A pair of terminals also is provided at the rear for VFO connection. Bands are changed by means of a system of plug-in coils.

The oscillator circuit operates with either 3.5- or 7-Mc. crystals. In either case, oscillator output may be obtained at the crystal fundamental frequency or its second harmonic. While the output stage may be used as a frequency doubler with fair efficiency, this sort of operation is not recommended unless the unit is to be used as an exciter for a following amplifier.

Parallel plate feed is used in both stages to permit mounting the tuning condensers,  $C_2$  and  $C_3$ , directly on the metal chassis without insulation. The v.h.f. choke  $RF C_2$  and the screen



Fig. 6-42 — A two-stage 60-watt transmitter for three bands. To either side of the milliammeter are the oscillator and amplifier plate-tuning controls. Along the bottom are the crystal switch, the plate-voltage switch, the meter switch, the key jack and the antenna tuning control.

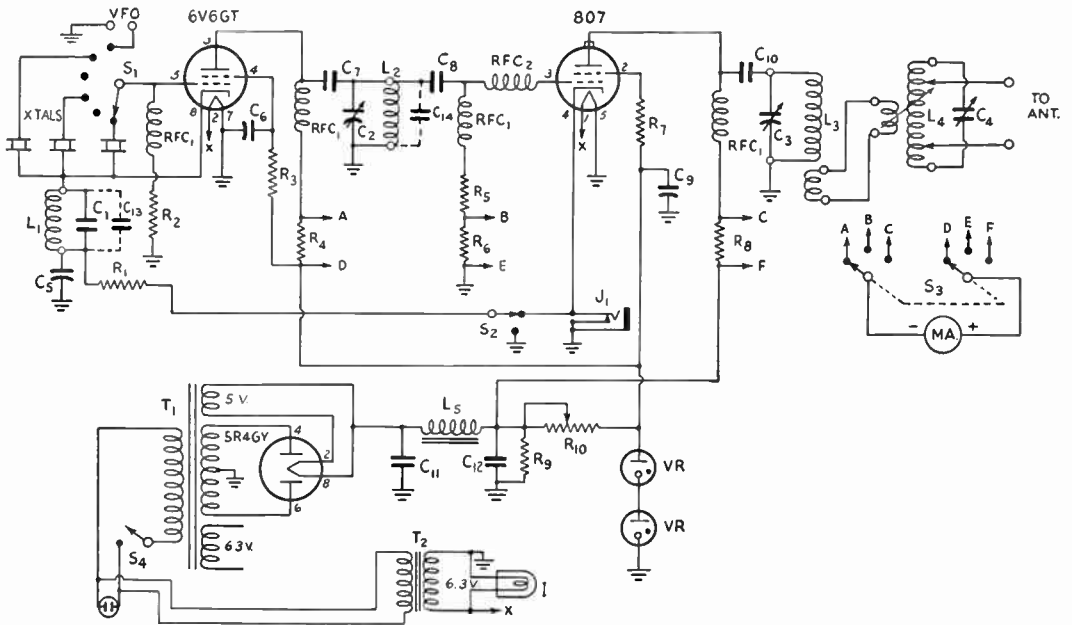


Fig. 6-43 — Circuit diagram of the 3-band 60-watt transmitter.

- C<sub>1</sub>, C<sub>8</sub> — 100- $\mu$ fd. mica.
- C<sub>13</sub> — 100- $\mu$ fd. mica (see text).
- C<sub>2</sub> — 50- $\mu$ fd. variable (National ST-50).
- C<sub>14</sub> — 22- $\mu$ fd. mica (see text).
- C<sub>3</sub>, C<sub>4</sub> — 150- $\mu$ fd. variable (National ST-150).
- C<sub>5</sub>, C<sub>6</sub>, C<sub>9</sub> — 0.01- $\mu$ fd. paper.
- C<sub>7</sub>, C<sub>10</sub> — 0.001- $\mu$ fd. mica.
- C<sub>11</sub>, C<sub>12</sub> — 4- $\mu$ fd. 1000-volt paper.
- R<sub>1</sub> — 220 ohms, 1 watt.
- R<sub>2</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 40,000 ohms, 5 watts.
- R<sub>4</sub> — 100-ma. meter shunt (see text).
- R<sub>5</sub> — 15,000 ohms, 1 watt.
- R<sub>6</sub> — 47 ohms,  $\frac{1}{2}$  watt.
- R<sub>7</sub> — 47 ohms, 1 watt.
- R<sub>8</sub> — 200-ma. meter shunt (see text).
- R<sub>9</sub> — 50,000 ohms, 25 watts.
- R<sub>10</sub> — 10,000 ohms, 25 watts (adjustable).
- L<sub>1</sub> — Oscillator cathode coil:
  - 1A (3.5-Mc. crystals) — 14 turns No. 22 d.c.c., 1-inch diam.,  $\frac{7}{8}$  inch long, 100- $\mu$ fd. mica, C<sub>13</sub> connected in parallel.
  - 1B (7-Mc. crystals) — 10 turns No. 22 d.c.c., 1-inch diam.,  $\frac{7}{8}$  inch long.
- L<sub>2</sub> — Oscillator plate coil:
  - 2A (3.5 Mc.) — 80 turns No. 26 d.c.c.,  $\frac{1}{2}$ -inch diam., close-wound, C<sub>14</sub> connected in parallel.
  - 2B (7 Mc.) — 40 turns No. 24 d.c.c.,  $\frac{1}{2}$ -inch diam., close-wound.
  - 2C — (14 Mc.) 25 turns No. 18 d.c.c.,  $\frac{1}{2}$ -inch diam.,  $1\frac{3}{8}$  inches long.

- L<sub>3</sub> — Amplifier plate coil:
  - 3A (3.5 Mc.) — 24 turns  $1\frac{1}{2}$ -inch diam.,  $1\frac{3}{8}$  inches long (B & W JEL80 with 16 turns removed), 3-turn link.
  - 3B (7 Mc.) — 18 turns  $1\frac{1}{2}$ -inch diam.,  $1\frac{3}{4}$  inches long (B & W JEL40), 2-turn link.
  - 3C (14 Mc.) — 12 turns  $1\frac{1}{2}$ -inch diam., 2 inches long (B & W JEL20), 2-turn link.
- L<sub>4</sub> — Antenna coil:
  - 4A (3.5 Mc.) — 30 turns  $1\frac{3}{4}$ -inch diam., 2 inches long, 3-turn variable link at center (B & W JVL80 with 5 turns removed from each end).
  - 4B (7 Mc.) — 24 turns  $1\frac{3}{4}$ -inch diam.,  $2\frac{3}{8}$  inches long, 3-turn link at center (B & W JVL40).
  - 4C (14 Mc.) — 14 turns  $1\frac{3}{4}$ -inch diam.,  $2\frac{1}{4}$  inches long, 3-turn link at center (B & W JVL20).
- L<sub>5</sub> — 6-henry 175-ma. filter choke.
- I — 6.3-volt signal-lamp assembly.
- J<sub>1</sub> — Closed-circuit jack.
- MA — 0-10 ma. meter.
- RFC<sub>1</sub> — 2.5-mh. r.f. choke.
- RFC<sub>2</sub> — 11 turns No. 20,  $\frac{5}{16}$ -inch diam.,  $\frac{3}{4}$  inch long.
- S<sub>1</sub> — 11-point tap switch, ceramic insulation.
- S<sub>2</sub> — S.p.d.t. toggle.
- S<sub>3</sub> — Double-gang 3-position rotary switch.
- S<sub>4</sub> — S.p.s.t. toggle.
- T<sub>1</sub> — 600 volts each side of center, 200 ma.; 5 volts, 3 amp. (UTC S-11).
- T<sub>2</sub> — 6.3 volts, 3 amp. (UTC S-55).
- VR — Voltage-regulator tubes — VR-150 and VR-105 types in series to give 255 volts.

resistor, R<sub>7</sub>, are necessary to suppress h.f. parasitic oscillations.

The s.p.d.t. toggle switch, S<sub>2</sub>, makes it possible either to key both stages simultaneously for break-in work on the lower frequencies, or the output stage alone at 14-Mc. frequencies where oscillator keying chirp may become noticeable. The unit includes a link-coupled antenna tuner, L<sub>4</sub>C<sub>4</sub>.

The self-contained power supply is built around an inexpensive multiwinding transformer, T<sub>1</sub>. The separate filament transformer, T<sub>2</sub>, makes it possible to cut off the plate voltage

without turning off the heaters of the tubes. A condenser-input filter is used to boost the output voltage to 600 under load. Voltage for the plate of the oscillator and the screen of the 807 is kept from soaring when the key is open by a pair of voltage-regulator tubes. This operating voltage of 255 is dropped to 150 volts for the screen of the 6V6GT by the series resistor, R<sub>3</sub>.

The milliammeter may be switched to read oscillator plate current and 807 grid or plate current by the double-gang switch, S<sub>3</sub>, which connects the meter across the shunting resistors, R<sub>4</sub>, R<sub>6</sub> and R<sub>8</sub>. R<sub>4</sub> and R<sub>8</sub> are adjusted



to multiply the 10-ma. basic meter-scale reading by 10 and 20, making the full-scale reading 100 and 200 ma. respectively when checking plate currents, while the resistance of  $R_6$  is sufficiently high to have negligible effect upon the meter reading when measuring the grid current of the amplifier.

### Construction

Reference should be made to the photographs of Figs. 6-42 through 6-47 for constructional details. The transmitter is built on a  $10 \times 14 \times 3$ -inch chassis which fits a standard  $9 \times 15 \times 10\frac{3}{4}$ -inch cabinet. The r.f. section occupies the front half of the chassis, while the power-supply components are lined up at the rear.

All tube and coil sockets are submounted. The cathode coil,  $L_1$ , requires a 4-prong socket; octals are needed for the 6V6GT, the oscillator plate coil,  $L_2$ , the rectifier and the two VR tubes;  $L_3$  and  $L_4$  require 5-prong sockets.

The oscillator and amplifier groups are separated by a small baffle shield cut from sheet aluminum. It is 4 inches high and 5 inches long and has a cut-out in front for the meter. It is spaced 8 inches in from the right-hand end of the chassis. The line of ten Millen crystal sockets is placed as close to the left-hand edge of the chassis as possible. Each of these requires two clearance holes and a mounting-screw hole between.

Alongside the crystal row are the 6V6GT oscillator tube and its cathode coil,  $L_1$ , followed by the plate coil,  $L_2$ , and the oscillator tuning condenser,  $C_2$ . The latter is mounted directly on the chassis  $4\frac{5}{8}$  inches from the left-hand edge. The oscillator grid and plate chokes are mounted underneath.

On the other side of the baffle shield are the 807 with its plate-circuit choke and blocking condenser,  $C_{10}$ , the output tank condenser and coil,  $C_3$  and  $L_3$ , and the antenna-coupler coil,  $L_4$ . The antenna tuning condenser,  $C_4$ , is mounted under the chassis. The socket for the 807 is spaced as far below the chassis level as possible, without protruding from the bottom, by means of brackets cut from strip metal. The purpose of this is to provide a shield between the input and output sections of the tube. A  $1\frac{7}{8}$ -inch hole is required to clear the tube envelope.  $C_3$  is mounted directly on the chassis with its shaft  $4\frac{5}{8}$  inches from the right-hand end of the chassis to balance the shaft of the oscillator plate-tank condenser.

The antenna tuning condenser,  $C_4$ , must be insulated from the chassis. This is done by means of an aluminum angle bracket and a pair of polystyrene feed-through buttons. The condenser is placed so that its shaft comes  $1\frac{5}{8}$  inches from the end of the chassis to balance the shaft of the crystal switch at the opposite end. The antenna coil is mounted at right angles to  $L_3$ .

The meter switch,  $S_3$ , is mounted at the center between the front edge of the chassis

and the bottom part of the 807. The key jack and power switch,  $S_4$ , are spaced equally to either side of the center of the front edge of the chassis.

The power-supply components are placed as close as possible to the rear edge of the chassis, with the transformer  $T_1$  at the left followed by the rectifier and voltage-regulator tubes, the input condenser,  $C_{11}$ , the filter choke,  $L_5$ , and the output condenser. A large cut-out is required for the transformer terminals and if filter condensers of the type shown are used, holes for the terminals must be provided in addition to the mounting-screw holes. The leads to the filter choke are fed down through a grommet-lined hole next to the choke. The key switch,  $S_2$ , and the antenna terminals are mounted in the rear edge of the chassis where the power cord also enters.

Underneath the chassis, the power wiring was done first, keeping it bunched and close to the chassis wherever possible. The separate filament transformer,  $T_2$ , is fastened to the left-hand end of the chassis. By-pass condensers and r.f. chokes should be placed close to the tube terminals to which they connect. The by-pass condensers should be grounded to the chassis at the nearest available point. The coupling and blocking condensers,  $C_7$ ,  $C_8$  and  $C_{10}$ , should be well spaced from the chassis. The same applies to all r.f. wiring, which should also be kept short and direct between points of connection. The length of leads to resistors is not important. In some cases it may be convenient to use fiber lug strips as anchorages or supports for small resistors and r.f. chokes.

The meter shunts,  $R_4$ ,  $R_6$  and  $R_8$ , are

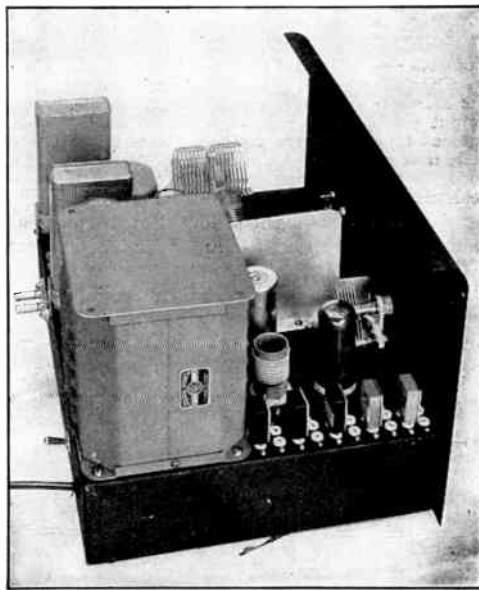


Fig. 6-41 — The oscillator section of the 60-watt transmitter, showing the line of crystal sockets, the cathode coil, the shielded plate coil and the 6V6GT.

mounted directly on the meter switch.  $R_4$  and  $R_8$  are made from No. 30 magnet wire. Approximately 7 feet will be required for  $R_8$  and 14 feet for  $R_4$ . Before the meter is mounted in the panel, it should be connected in series with a 3-volt battery and a variable resistance of about 500 ohms. A resistor with a slider will serve the purpose if no other is available. The resistance should be adjusted until the meter reads full scale. When the shunting wire, cut to a length of two or three feet more than that required is connected across the meter terminals, the reading will drop. The length of the wire should be adjusted, bit by bit, until the reading drops to 1 ma. for  $R_4$  and to  $\frac{1}{2}$  ma. for  $R_8$ . The wire then may be wound on a small form for compactness. A  $\frac{1}{2}$ -watt

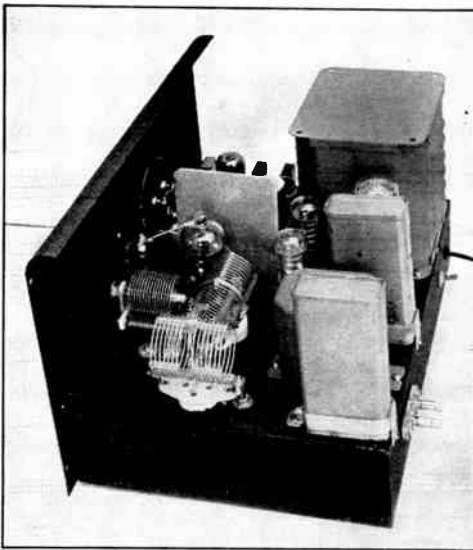


Fig. 6-15 — Looking into the amplifier end of the 60-watt transmitter chassis. The 807 socket is spaced below the chassis to provide shielding between the input and output sections. The coil in the foreground is in the antenna tuner, while the one behind it is the amplifier plate tank coil.

resistor of 100 ohms or more makes a good form and its resistance does not affect the calibration of the shunt to any practical degree.

The link line between the output tank circuit and the antenna tuner, and the connections between the latter and the antenna terminals at the rear, should be made with rigid wire spaced well away from the chassis and surrounding components.

### Coils

The output and antenna tank coils,  $L_3$  and  $L_4$ , are of the B & W JEL and JVL series respectively.

Some of these require pruning, as indicated in Table 6-1 to provide the correct  $L/C$  ratio. The antenna coil,  $L_4$ , requires an extra pair of contacts for the tap leads. Since a center-tap is not required, it may be cut free from the base pin so that this pin may be used

TABLE 6-1  
Coils for 60-Watt Rig

Crystal f.	Output f.	$L_1$	$L_2$	$L_3$	$L_4$
3.5 Mc.	3.5 Mc.	1A	2A	3A	4A
3.5 Mc.	7 Mc.	1A	2B	3B	4B
7 Mc.	7 Mc.	1B	2B	3B	4B
7 Mc.	14 Mc.	1B	2C	3C	4C

for one of the tap contacts. The other tap contact is provided by drilling out the tubular rivet at one of the ends of the coil-supporting base strip and substituting a banana plug as shown in Fig. 6-46. A jack for this plug then is mounted in the chassis close to the coil socket by drilling out a pair of polystyrene button-type feed-through insulators to fit the jack and setting them in the chassis.

The two cathode coils for  $L_1$  are wound on Milten 4-prong 1-inch forms. The one to be used with 3.5-Mc. crystals requires a 100- $\mu$ fd. mica condenser,  $C_{13}$ , connected across it in addition to  $C_1$ . This condenser is mounted inside the form so that it is connected in the circuit along with the coil when the latter is plugged in.

The oscillator plate coils are wound on Milten octal-base shielded plug-in forms. If the forms are of the type with iron-core slugs, these should be removed. The 3.5-Mc. coil requires an extra padding condenser,  $C_{14}$ , of 22  $\mu$ fd. This may be a mica condenser soldered across the winding as shown in the photograph of Fig. 6-46.

### Adjustment

Since the tuning of the cathode tank circuit is fixed, only three circuits, including the antenna circuit, need adjustment. The coil table shows which coils should be plugged in to obtain output depending upon the crystal frequency and the output frequency desired. For initial testing it is well to use a combination giving output in the 3.5- or 7-Mc. band. Before turning on the power supply, a key connected to a plug should be inserted in the key jack and the key switch,  $S_2$ , should be thrown to the amplifier-keying side. This will permit the oscillator to operate alone. When the power plug is inserted, the heaters of the tubes should warm up. The VR tubes should glow as soon as the power switch,  $S_4$ , is


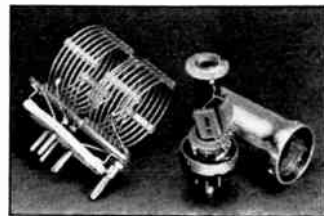


Fig. 6-46 — The antenna coil for the 60-watt transmitter requires the addition of an extra contact which is provided by the banana plug. To the right is the 3.5-Mc. oscillator plate coil with the mica padding condenser connected across the winding.

◆  
 Fig. 6-17 — Bottom view of the 60-watt transmitter, showing the mounting of the 807 socket at the upper center and the location of by-pass condensers, resistors and r.f. chokes. The separate filament transformer is fastened to the left-hand edge of the chassis. The antenna tuning condenser is in the upper right-hand corner, supported on an aluminum angle bracket which is insulated from the chassis by polystyrene buttons.

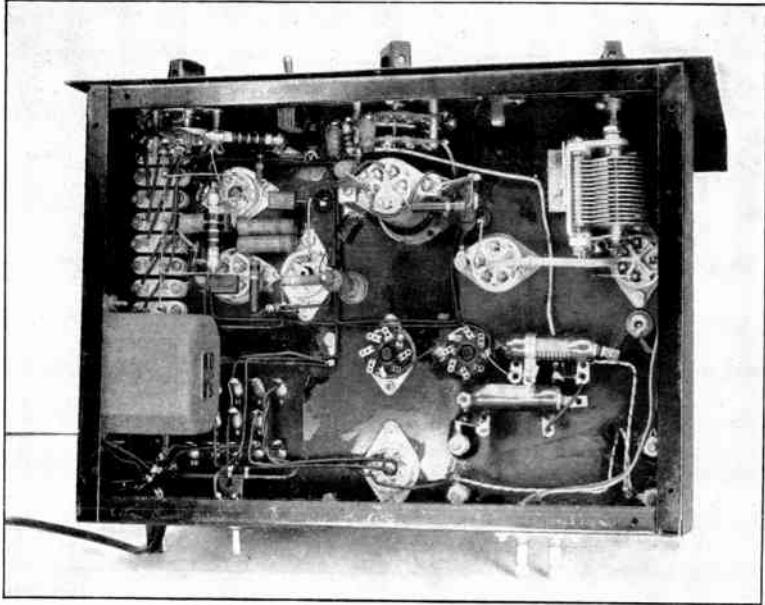

closed. If they do not, the resistance of  $R_{10}$  should be reduced until they do.

With the high voltage applied and the meter switched to the first position for oscillator plate current, the meter should read between 35 and 50 ma. As  $C_2$  is adjusted, a point will be found where the plate current dips to a minimum (between 10 ma. and 30 ma. depending upon the frequency), rising on either side. If  $L_2$  has been made close to specifications, this resonance point should be found with about 60 per cent of maximum capacitance in use at  $C_2$  for 3500 kc., 70 per cent for 7000 kc. and 30 per cent for 14,000 kc. If the plate circuit is tuned to a harmonic of the crystal frequency, the increase in current either side of the minimum should be smooth. However, if the plate circuit is tuned to the crystal frequency, the plate current may jump suddenly to a high value when it is tuned to the high-capacitance side of the minimum plate-current point. This indicates that the circuit has stopped oscillating.  $C_2$  should be set sufficiently to the low-capacitance side of the minimum to insure reliable starting of the oscillator when the power is switched on or when the amplifier is keyed.

When VFO input is used, the cathode tank circuit should be shorted out. Otherwise the adjustment is the same except that the oscillator plate circuit may be tuned for maximum amplifier grid current at the fundamental as well as at the harmonic.

The amplifier should be tuned up first with the antenna coil out of its socket. With the meter switched to the second position where it reads amplifier grid current, a reading of 3 to 9 ma. should be obtained when the key is closed. If no grid-current reading is obtained, it is probable that the oscillator stopped when the key was closed. In this case, the tuning of the

oscillator should be readjusted. In this instance, at least, it has been found that best keying is obtained when the oscillator plate circuit is detuned to the low-capacity side of resonance to a point where the oscillator plate current remains constant with the key open and closed. This refers only to amplifier keying when the oscillator plate circuit is tuned to the crystal fundamental, of course. Readings of 5 to 10 ma. or more should be obtained in all cases. The key should not be held closed for periods longer than necessary to obtain the reading, until the amplifier plate circuit is tuned to resonance.

With the meter switch thrown to the last position, where it reads amplifier plate current, a reading of 100 ma. or more should be obtained. As  $C_3$  is turned through its range the plate current should dip to a minimum of between 10 and 15 ma. With the  $L_3$  coils altered as indicated in the coil table, resonance should occur at approximately 90 per cent for 3500 kc., 30 per cent for 7 Mc. and 15 per cent for 14 Mc.

The antenna should now be connected to the antenna terminals and the antenna coil plugged in. The adjustable link of the antenna coupler should be swung about halfway out and the taps should be placed on the outside turns of  $L_4$ . With the key closed,  $C_4$  should be swung through its range. At some point the amplifier plate current should increase to a maximum, decreasing on either side. Leaving  $C_4$  at the point where maximum plate current is obtained,  $C_3$  should be readjusted for a minimum point which, of course, will be higher than the unloaded minimum obtained before. The adjustments of  $C_3$  and  $C_4$  should be juggled around until a point is reached where any change in  $C_3$  will cause an increase in plate

current, while any adjustment of  $C_4$  will cause a decrease in plate current. If the plate current at this point is less than the maximum rated plate current for the tube, the link coupling should be closed up. If it is greater than 100 ma., the coupling should be reduced. If it is found that the link adjustment is insufficient to bring the plate current to the desired value, the taps should be moved in a turn at a time, keeping them always equidistant from the

ends of the coil. The tap adjustments as well as any change in the position of the link may affect the tuning of the amplifier plate circuit, so it should be retuned to obtain minimum plate current as a final adjustment. This minimum should, of course, be the rated plate current of 100 ma. when the amplifier is fully loaded. The dip in plate current at resonance naturally will be very slight when the amplifier is operating under full load.

## A 150-Watt Transmitter with Plug-In Stages

Figs. 6-48 through 6-55 show a complete 150-watt transmitter with its associated power supply, antenna coupler and control system. In this unit, coverage of all amateur bands from 3.5 to 28 Mc. is accomplished by means of plug-in exciter stages instead of utilizing either bandswitching or plug-in coils. The arrangement permits multiplying frequency from 3.5- and 7-Mc. crystals to the 28-Mc. band, yet provides a ready means of disposing of the unneeded doubler stages when working at low frequencies. This type of construction permits the constructor to build, and operate, a stage at a time, as his finances and time permit. Even the oscillator unit may be used as a low-power transmitter while the doubler and amplifier stages are being built.

The complete tube line-up (for 28-Mc. operation) consists of a 6AG7 crystal oscillator-doubler, doubler stages for the 14- and 28-Mc. bands using 6V6s, and two 807s in parallel as the final amplifier. The oscillator and the two doubler stages are built as separate units, each in a 4 × 4 × 2-inch utility box. These boxes

plug into sockets on the main r.f. chassis. The position into which a given box is plugged depends upon the output frequency desired, as shown in Fig. 6-50. For 3.5- and 7-Mc. operation, the oscillator box is plugged into the position that drives the 807s directly, and the doubler units are not used. For 14-Mc. operation, the oscillator box is moved back one position, and the 14-Mc. doubler stage is plugged into the socket nearest the 807s. For 28-Mc. operation the oscillator and both the 14- and 28-Mc. doublers are used.

Each plug-in stage has a 60-ma. pilot lamp mounted on it as a resonance indicator, and each has terminals brought out from a link to permit coupling to an antenna tuner if low-power operation is desired before the final amplifier is built. Provisions are made for keying the cathode circuit of any stage of the transmitter.

The general construction of the transmitter is shown in Figs. 6-48 and 6-53. Two main chassis are used, one held above the other by angle brackets. The power supply and control

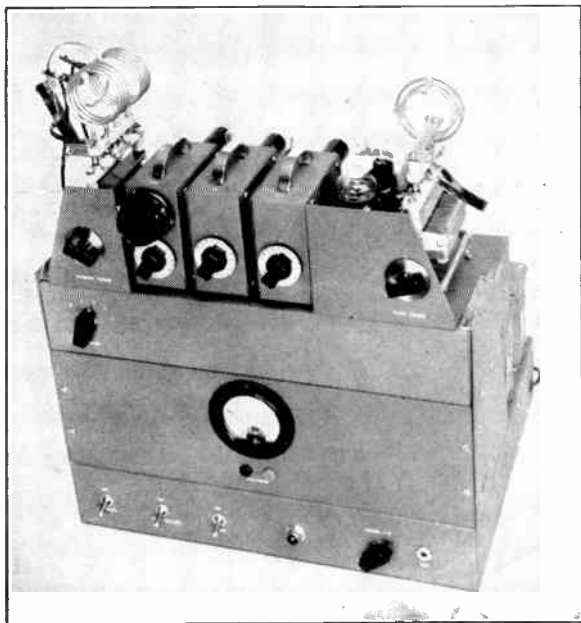


Fig. 6-48 — A compact 150-watt transmitter using plug-in stages. This unit, using 807s in parallel for the final amplifier, is for tabletop use. Three separate plug-in units, shown in the center of the upper chassis, are used for the low-power exciter stages. In this view, the units are in the positions required for 28-Mc output. A built-in antenna tuner is at the upper left, and the tank circuits for the 807s at the right. The meter switch is at the left in the upper chassis and the voltmeter pin jacks below the meter. The toggle switches, from left to right, are  $S_2$ ,  $S_3$  and  $S_1$  in Fig. 6-51. The knob at the right is the 'phone-c.w. switch,  $S_4$ , and the jack is for the key.

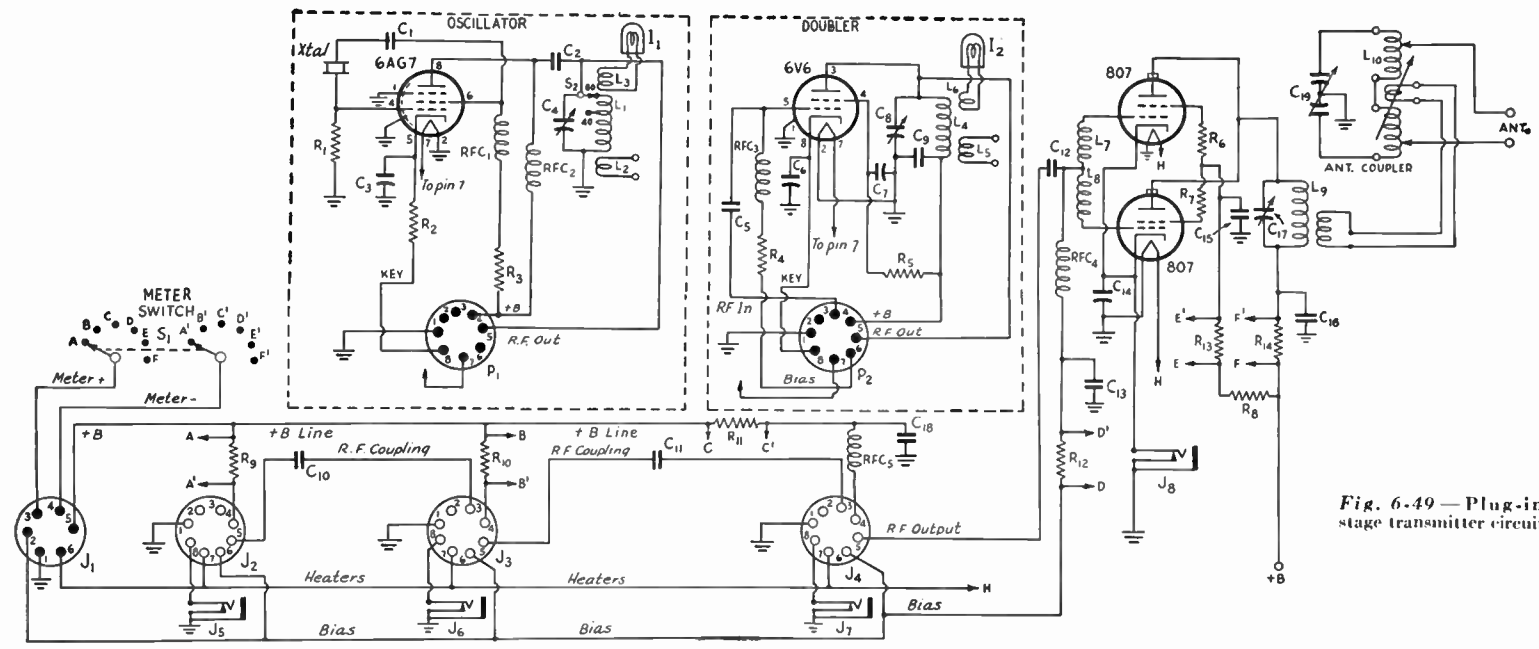


Fig. 6-49 — Plug-in stage transmitter circuit.

- C<sub>1</sub>, C<sub>13</sub> — 0.0015- $\mu$ fd. mica.
- C<sub>2</sub> — 0.001- $\mu$ fd. mica.
- C<sub>3</sub>, C<sub>6</sub>, C<sub>7</sub>, C<sub>14</sub> — 0.01- $\mu$ fd. paper.
- C<sub>4</sub> — 100- $\mu$ fd. receiving-type variable (Millen 19100).
- C<sub>5</sub> — 14 Mc. — 100- $\mu$ fd. mica; 28 Mc. — 22- $\mu$ fd. mica.
- C<sub>8</sub> — 14 Mc. — 50- $\mu$ fd. variable (Millen 19050).
- 28 Mc. — Same with 2 rotor plates removed.
- C<sub>9</sub> — 0.0047- $\mu$ fd. mica.
- C<sub>10</sub>, C<sub>11</sub>, C<sub>12</sub> — 100- $\mu$ fd. mica.
- C<sub>15</sub> — 0.001- $\mu$ fd. 1000-volt mica.
- C<sub>16</sub> — 0.001- $\mu$ fd. 2500-volt mica.
- C<sub>17</sub> — 250- $\mu$ fd. 1500-volt variable (National TMK-250).
- C<sub>18</sub> — 0.0022- $\mu$ fd. mica.
- C<sub>19</sub> — 100- $\mu$ fd. per-section dual transmitting variable, 1500 volts peak (National TMK-100D).

- R<sub>1</sub> — 17,000 ohms, 1/2 watt.
- R<sub>2</sub> — 330 ohms, 1 watt.
- R<sub>3</sub>, R<sub>5</sub> — 22,000 ohms, 1 watt.
- R<sub>4</sub> — 2200 ohms, 1/2 watt.
- R<sub>6</sub>, R<sub>7</sub> — 68 ohms, 1/2 watt.
- R<sub>8</sub> — 30,000 ohms, 20 watts.
- R<sub>9</sub> to R<sub>13</sub> — 100 ohms, 1/2 watt.
- R<sub>14</sub> — Meter shunt, see text.
- L<sub>1</sub> — 27 turns No. 22 d.s.c., tapped 17 turns from ground end, close-wound on 3/4-inch diam. form.
- L<sub>2</sub> — 2 turns No. 20 enam. inside L<sub>1</sub>.
- L<sub>3</sub> — 1 turn at ground end of L<sub>1</sub>.
- L<sub>4</sub> — 14 Mc. — 10 turns No. 22 d.s.c. 1 inch long, 3/4-in. diam. (form National PRF-2).
- 28 Mc. — 4 1/2 turns No. 22 d.s.c. 1 inch long, 3/4-inch diam. (form National PRF-2).
- L<sub>5</sub> — Similar to L<sub>2</sub>.

- L<sub>6</sub> — Similar to L<sub>3</sub>.
- L<sub>7</sub>, L<sub>8</sub> — 18 turns No. 20 d.s.c. close-wound on a 1-watt resistor of any high value.
- L<sub>9</sub> — B & W BEL series. 3.5 Mc. — 40 BEL.; 7 Mc. — 20 BEL.; 14 Mc. — 10 BEL.; 28 Mc. — 10 BEL. with 3 turns removed.
- L<sub>10</sub> — B & W BVL series, no alterations.
- I<sub>1</sub>, I<sub>2</sub> — 60-ma. pilot lamp.
- J<sub>1</sub> — 6-contact male connector (Amphenol 86-CP6).
- J<sub>2</sub>, J<sub>3</sub>, J<sub>4</sub> — Ceramic octal sockets (Millen).
- J<sub>5</sub> to J<sub>8</sub> — Closed-circuit 'phone jack.
- P<sub>1</sub>, P<sub>2</sub> — Low-loss octal plug (Amphenol 86-CP8T).
- RFC<sub>1</sub> to RFC<sub>5</sub> — 2.5-mh. choke (Millen 34102).
- S<sub>1</sub> — 2-section 6-position ceramic rotary switch (Centralab 2511).
- S<sub>2</sub> — Single-pole 2-position ceramic rotary switch (Centralab 2501).

circuits occupy the lower chassis, while all of the r.f. circuits, including the built-in antenna tuner, are in the upper chassis. The entire r.f. unit is removable, permitting the power supply and control circuits to be used with other transmitters of the same chassis size and similar power requirements if desired. All connections between the two chassis are made by a 6-wire cable, a high-voltage lead and a keying lead as shown in Fig. 6-51.

**R.F. Circuits**

In the oscillator, the screen grid of the 6AG7 is used as the anode of a triode Pierce circuit, with electron coupling to an output plate circuit that can be tuned to either the 3.5- or 7-Mc. bands. A tapped coil,  $L_1$  in Fig.

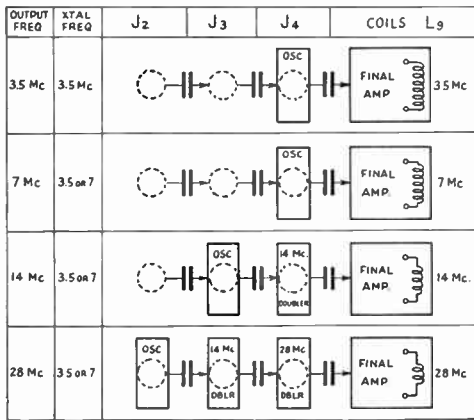


Fig. 6-50— Operating chart for the plug-in-stage transmitter. This chart illustrates the band-changing system used with the various plug-in units used to drive the final amplifier. The columns headed  $J_2$ ,  $J_3$  and  $J_4$  represent the position in Fig. 6-49 a given unit should be plugged in to produce output in a given band. This position is the same for either 3.5- or 7-Mc. crystals. For output at 7-Mc. and higher, the bandswitch in the oscillator unit must be set to the 7-Mc. position.

6-49, and a ceramic bandswitch,  $S_2$ , permit this range to be covered. This type of oscillator lends itself nicely to the needs of this transmitter, since output at 7 Mc. may be obtained with either 3.5- or 7-Mc. crystals with no circuit changes other than switching the plate coil. The output of the oscillator, whether operating at the crystal fundamental or doubling frequency from 3.5 to 7 Mc., is sufficient to drive the 807s with some to spare.

The interstage coupling capacitances are adjusted to give optimum drive regardless of whether the oscillator is feeding the 807 grids or the grid of one of the doubler stages. This is accomplished by a series coupling condenser  $C_5$  inside the doubler boxes in addition to the 100- $\mu$ fd. interstage coupling condensers,  $C_{10}$ ,  $C_{11}$  and  $C_{12}$ . Operating bias for the doublers is obtained from the grid leak,  $R_4$ , in addition to a fixed bias of 90 volts which is applied to all stages to assure plate-current cut-off, in the

doublers, and protection for the 807s if oscillator keying is to be used.

Plug-in coils are used in the plate circuit of the final amplifier. This stage operates as a straight amplifier on all bands. Series feed is used for maximum efficiency. The full plate potential is thus exposed at the tuning condenser and the plate coil, necessitating extreme caution in turning off plate voltage whenever the coils are being changed. Resistors  $R_6$  and  $R_7$  and chokes  $L_7$  and  $L_8$  prevent high-frequency parasitic oscillations. A screen voltage-dropping resistor,  $R_8$ , is used to permit plate-and-screen modulation of the final-amplifier stage.

Coupling to the antenna is accomplished by means of a balanced tank circuit,  $C_{19}$ - $L_{10}$ , link-coupled to the final amplifier. The feedline to the antenna is connected to the antenna coil by adjustable taps to permit almost any line impedance to be matched.

**Power Supply**

In the power-supply circuits, shown in Fig. 6-51, 350 volts at 200 ma. and the regulated fixed bias voltage are obtained from one transformer, while either 750 or 600 volts is obtained from another which has a tapped secondary. A ceramic switch,  $S_4$ , selects the proper taps. In c.w. operation the 807s can be used with 750 volts on their plates, but for 'phone operation, the switch selects taps that reduce this voltage to 600.  $T_3$  supplies the 816 filaments while the other,  $T_4$ , provides filament voltage for the 5U4G, the 6X5 and the r.f. tubes.

The control circuits use three toggle switches,  $S_1$ ,  $S_2$  and  $S_3$ , in a series arrangement so that filament voltage must be turned on first, followed in sequence by the 350- and 750-volt power supplies. Thus, once all tuning-up operations have been concluded,  $S_2$  is used as the transmit/stand-by switch. An a.c. outlet,  $J_1$ , is wired across the primary of the high-voltage transformer so that primary voltage may also be applied to external equipment, such as a modulator supply or an antenna change-over relay, whenever  $S_2$  and  $S_3$  are closed.

A key jack,  $J_2$ , is provided on the power chassis as an operating convenience, eliminating the need for long keying leads running behind the r.f. chassis to the various key jacks. It simply provides an extension from the jacks in the r.f. section.

The meter,  $MA_1$ , is mounted on the power-supply chassis so that it, too, may be used with another transmitter. Pin jacks are provided for the connection of an external voltmeter so that both current and voltage measurements may be made simultaneously. The switch shifts the voltmeter from stage to stage along with the milliammeter.

**R.F.-Chassis Construction**

In Fig. 6-48 the layout of the entire assembly is shown. On the 17  $\times$  7  $\times$  3-inch r.f. chassis,

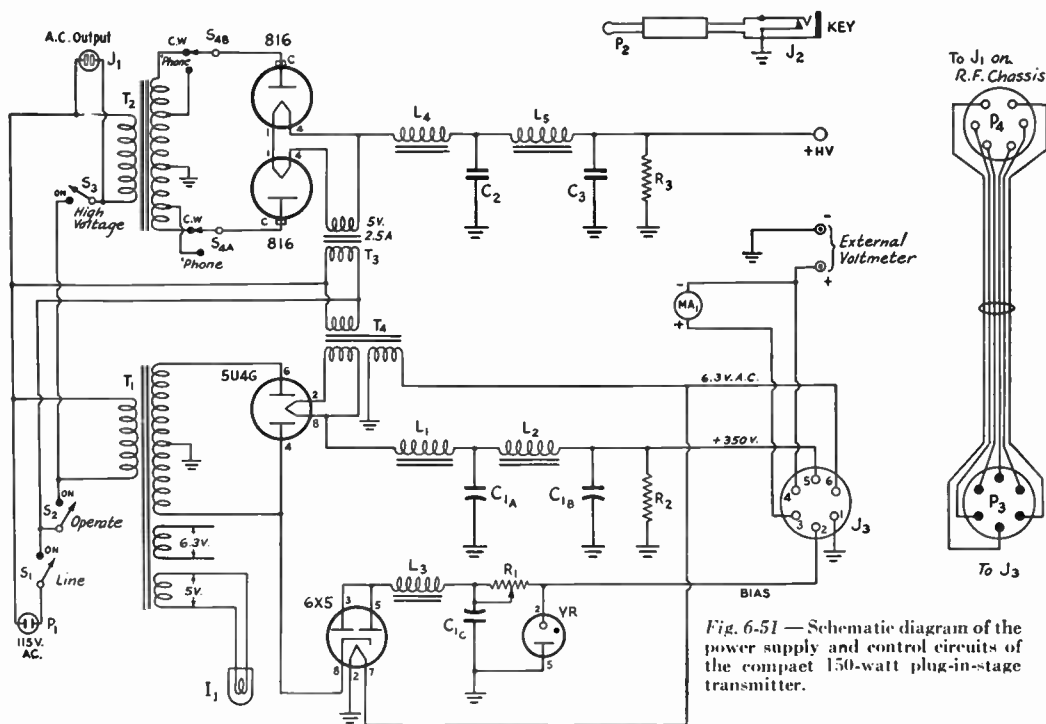


Fig. 6-51 — Schematic diagram of the power supply and control circuits of the compact 150-watt plug-in-stage transmitter.

- C<sub>1</sub> — 3-section 8- $\mu$ fd. 450-volt electrolytic (Mallory RM-265).
- C<sub>2</sub>, C<sub>3</sub> — 4- $\mu$ fd. 1000-volt oil-filled.
- R<sub>1</sub> — 10,000 ohms, 5 watts, adjustable.
- R<sub>2</sub> — 20,000 ohms, 25 watts.
- R<sub>3</sub> — 50,000 ohms, 50 watts.
- L<sub>1</sub> — 5-20-hy. 200-ma. swinging choke, 130 ohms (Thordarson T-19C35).
- L<sub>2</sub> — 12-hy. 200-ma. smoothing choke, 130 ohms (Thordarson T-19C42).
- L<sub>3</sub> — 8-hy. 40-ma. filter choke, 530 ohms (Thordarson T-13C26).
- L<sub>4</sub> — 5-25-hy. 225-ma. swinging choke, 120 ohms (UTC S-32).
- L<sub>5</sub> — 15-hy. 225-ma. smoothing choke, 120 ohms (UTC S-31).
- I<sub>1</sub> — 6.3-volt pilot-lamp assembly.
- J<sub>1</sub> — Female a.c. receptacle (Amphenol 61F1).
- J<sub>2</sub> — Closed-circuit jack.
- J<sub>3</sub> — 6-prong socket (Amphenol 78RS6).

- MA<sub>1</sub> — 0-100-ma. d.c. milliammeter, 3-inch.
- P<sub>1</sub> — Male a.c. line plug.
- P<sub>2</sub> — Phone plug.
- P<sub>3</sub> — Male cable connector, 6-contact (Amphenol 86-PM6).
- P<sub>4</sub> — Female cable connector, 6-contact (Amphenol 78-PF6).
- S<sub>1</sub>, S<sub>2</sub>, S<sub>3</sub> — S.p.s.t. toggle switch.
- S<sub>4</sub> — 2-section 2-position ceramic rotary switch (Mallory 162C).
- T<sub>1</sub> — Replacement-type power transformer, 389-0-389 v. a.c., 200 ma. (Thordarson T-921R21).
- T<sub>2</sub> — Power transformer, 900/750-0-750/900 v. a.c., 200 ma. (UTC S-45).
- T<sub>3</sub> — Filament transformer, 5 volts, 5 amp. (Thordarson T-19F83).
- T<sub>4</sub> — Dual filament transformer, 5 volts, 6 amp., 6.3 volts, 5 amp. (UTC S-67).
- VR — VR-90 voltage-regulator tube.

the antenna coupler is at the left, then the oscillator box, followed in sequence by the two doubler boxes and the final amplifier. The bottom view of the r.f. chassis, Fig. 6-52, shows the location of the ceramic octal sockets for the plug-in stages, the interstage coupling condensers, C<sub>10</sub>, C<sub>11</sub> and C<sub>12</sub>, and the components grouped around the sockets of the 807s. A meter switch, S<sub>1</sub>, appears at the upper left, and the 6-prong chassis plug, J<sub>1</sub>, used to terminate the 6-wire cable that connects the low-voltage supply and the meter circuit to the r.f. chassis is at the lower left. The keying jacks, J<sub>5</sub>, J<sub>6</sub>, J<sub>7</sub> and J<sub>8</sub>, are on the rear side of the r.f. chassis, and the high-voltage terminal is at the lower right.

In placing the ceramic sockets for the plug-in units, care should be taken to line up the terminals in such manner that the plug-in boxes

will be square to the chassis edges when they are in place. A little care and forethought are all that are necessary, bearing in mind that the octal plugs on the bottom of the plug-in boxes must also be aligned with these sockets.

In wiring the r.f. chassis the metering resistors, R<sub>9</sub>, R<sub>10</sub>, R<sub>11</sub>, R<sub>12</sub>, R<sub>13</sub> and R<sub>14</sub>, are mounted on S<sub>1</sub>. R<sub>14</sub>, used to multiply the scale reading of the meter by four when the switch is set to read amplifier plate current, is wound with No. 30 d.s.c. wire on a 1/2-watt resistor of any high value that happens to be handy. Care should be taken to keep lead inductance low in the screen and cathode circuits of the 807 stage. Heavy, short leads are used to tie the paralleled circuit elements together, and both cathode and screen by-pass condensers, C<sub>14</sub> and C<sub>15</sub>, are returned to a common ground point.

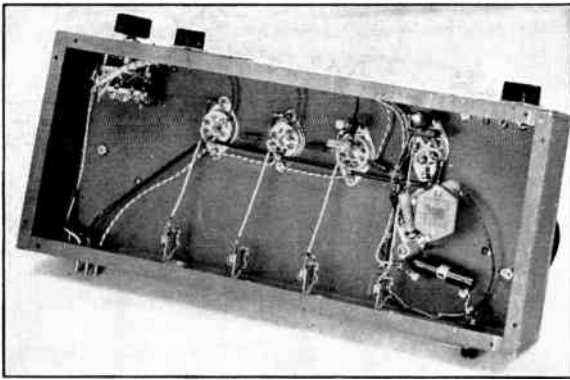


Fig. 6-52 — Bottom view of the r.f. chassis of the plug-in-stage transmitter. The octal sockets for the plug-in units are ranged along the center of the chassis. The components of the 807 stage are at the right. The meter switch is at the upper left, and the power connections and key jacks are on the rear chassis edge.

A  $\frac{3}{8}$ -inch ceramic feed-through bushing brings the high voltage up through the chassis from the plate by-pass condenser and the safety terminal. The plate leads of the 807s are made of flexible shield braid, and run from the tubes to the coil jack-bar. External shielding of the 807s is not required, the shielding afforded by the box-type construction used for the driver stages being sufficient.


The tuning condenser for the 807 plates is raised above the chassis on National GS-10 stand-off insulators to bring the coil mounting, which is bolted to the top of the condenser frame, up to the level of the 807 plate caps. The condenser rotor shaft is fitted with an insulated coupling to insulate it from the steel panel and the control dial. The antenna condenser,  $C_{13}$ , is similarly insulated from both chassis and panel.

Connection from the link winding on the amplifier tank coil to the swinging link of antenna coil,  $L_{10}$ , is made through a length of 300-ohm Twin-Lead, held in place by special stand-off insulators made for this type of line by Amphenol. A bracket-mounted antenna terminal (National FWH) is mounted on the chassis just below the swinging link. Flexible leads made of No. 14 stranded copper wire eased in spaghetti tubing connect this terminal to spring-type clips used to tap the antenna feeders across the required number of turns of the antenna-coupler coil.

Fig. 6-53 — Rear view of the plug-in-stage transmitter. In this view the units are set up for 14-Mc. output. Connections between the two chassis are shown, with the high-voltage lead at the left, the keying lead in the center, and the 6-wire power cable on the right.

### Oscillator and Doubler Units

The arrangement of the parts in the  $4 \times 4 \times 2$ -inch oscillator and doubler boxes is shown in Figs. 6-54 and 6-55 respectively. Only one of the doubler boxes is shown in the photograph as well as in the schematic diagram because the two are identical in appearance and parts placement. A 5-prong ceramic socket is mounted on the front of the oscillator box just above the tuning dial to hold a Dekaxtal multiple-crystal unit. This device provides the additional feature of crystal switching. A standard crystal socket may be substituted if desired, of course. The bandswitch,  $S_2$ , is mounted on the rear of the box, just below the tube socket. The coil form is mounted on the rear bearing bracket of the condenser. The coil itself has three windings, the tapped

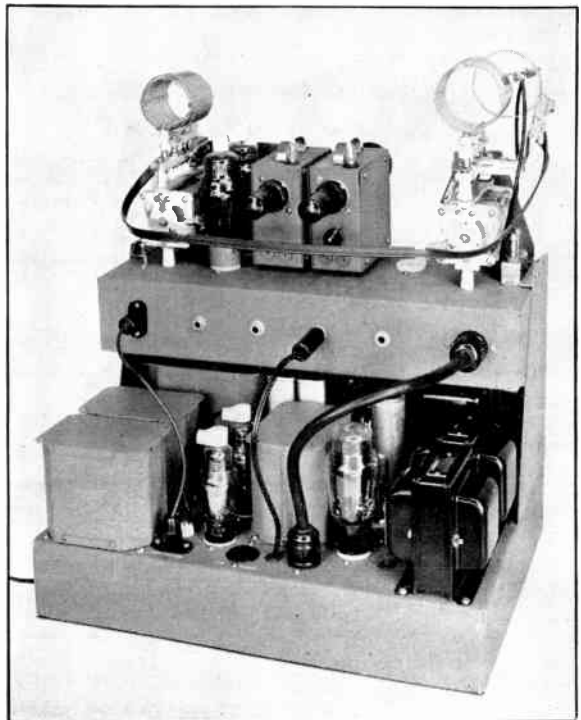



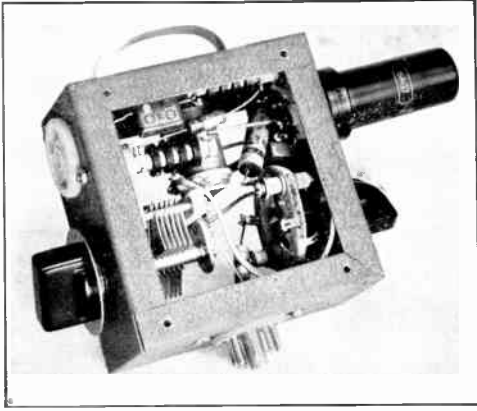


Fig. 6-54 — Interior view of the plug-in oscillator unit used with the compact 150-watt transmitter (side plates removed). The crystal socket is at the upper left, above the plate tuning dial. The plate coil is mounted on the rear bearing bracket of the tuning condenser. The r.f. chokes extend out from the front and rear walls, and the plate-blocking and cathode by-pass condensers are mounted at the tube socket. The bandswitch is mounted on the rear wall of the box, below the tube.

tank coil,  $L_1$ , and two adjustable link windings,  $L_2$  and  $L_3$ , for coupling to the pilot-lamp resonance indicator and to an antenna tuner. The insulated tip jacks used for the antenna-link terminals are at the rear below the switch knob.

Twin-Lead (75-ohm) is used as the link line to the indicator lamp socket and to the tip jacks. The indicator lamp is mounted in a Drake Type 317H socket and is insulated from the box by a grommet which also serves to hold the assembly in place.

The Millen Type 34102 r.f. chokes are mounted from opposite sides of the oscillator box through the holes drilled for mounting the tube socket and the crystal socket. Some care is required in placing these parts to assure clearance between the r.f. chokes and the oscillator coil form.

Construction of the doublers is similar to that of the oscillator, but is simplified by the fact that fewer components are required. The series coupling condenser,  $C_5$ , and the bias resistor,  $R_4$ , are mounted vertically right at the octal plug. The r.f. choke is mounted vertically through one of the holes used to mount the plug.

As indicated below Fig. 6-49, there are minor differences, in addition to the coil specifications, in the circuit values used in the 14- and 28-Mc. doublers.

More than ordinary care should be taken to make clean, firm, soldered connections to the octal plugs used to connect the oscillator and the doublers to the r.f. chassis. These joints are subject to considerable wear and tear, and should be as solid as possible. The pins of the plugs should be scrubbed clean with alcohol after the soldered joint is made to remove all traces of flux or rosin. No. 14

bare tinned wire is used for r.f. leads wherever possible.

#### Building the Power Supply

The arrangement of the parts on the  $17 \times 13 \times 3$ -inch power-supply chassis can be seen in Fig. 6-53. The two power transformers are placed along the front edge of the chassis, each set in about an inch from the side to provide room for the angle brackets used to support the r.f. chassis. The filter chokes are immediately behind their respective transformers. The dual filament transformer used for the 5U4G low-voltage rectifier, the 6X5 bias rectifier, and the tubes in the r.f. chassis are mounted near the center of the chassis, behind the filter condensers, and between the two 816s and the 5U4G. Space for the high-voltage safety terminal, the a.c. power outlet, the keying lead, and the 6-terminal low-voltage output socket is left at the rear of the chassis, keeping the back of the chassis clear so that it may be placed against a wall if the unit is used on the operating desk. The 5-volt transformer for the 816 filaments and the small filter choke used in the bias circuit are mounted beneath the chassis. If a 2.5-volt 5-amp. filament transformer is available, it may be substituted if the 816 filaments are connected in parallel instead of in series as shown in the circuit diagram. The voltage regulator is placed just in front of the 3-section filter condenser. The 6X5 bias rectifier is behind the 5U4G.

Supports made from  $5 \times \frac{1}{2} \times \frac{3}{4}$ -inch blocks of hard wood bolted to the inside of the upright angle brackets carry the weight of the r.f. chassis. Small aluminum angle strips are also bolted to the brackets above the r.f. chassis so that they, with the blocks mentioned above, form a channel into which the r.f. chassis slides like a drawer. This permits

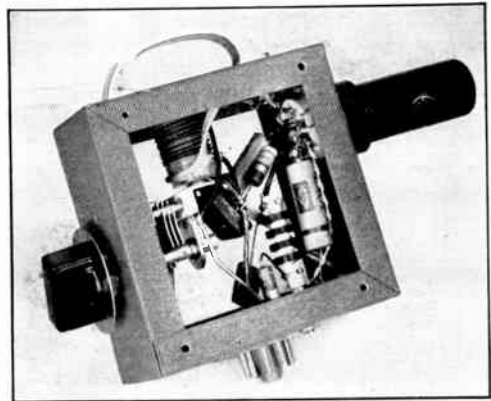


Fig. 6-55 — Interior view of one of the plug-in doubler units used with the compact 150-watt transmitter. The screen and the cathode by-pass condensers run from the tube sockets to ground points. A two-terminal tie-point supports one end of the screen dropping resistor and the plate-blocking condenser. The grid condenser and the bias resistor are mounted vertically through the octal plug. The indicator lamp protrudes from the top.

the r.f. chassis to be removed without unbolting the side brackets, and prevents it from being lifted off the supporting blocks when the plug-in boxes are pulled out of their sockets.

#### Adjustment Procedure

Reference should be made to Fig. 6-50 in setting up the exciter stages to obtain output in the desired band.

The oscillator plate-and-screen current should run between 20 and 30 ma., depending upon whether or not the oscillator is doubling frequency. The dip in current at resonance will be slight when the oscillator is coupled to one of the following stages. The resonance-indicator lamp or the grid current to the final-amplifier stage will be more reliable indicators of maxi-

mum oscillator power output.

The 14-Mc. doubler combined screen-and-plate current also should run between 20 and 30 ma. when loaded, while the reading for the 28-Mc. doubler should run 40 to 50 ma.

With the final amplifier loaded to the rated plate current of 200 ma., the grid current should be adjusted to 8 ma., detuning the oscillator plate-tank circuit if necessary to reduce the grid current to this value. More than adequate drive to the final amplifier increases screen dissipation and actually decreases power output. The doubler circuits should not be detuned because of the danger of exceeding the dissipation rating of the doubler tubes.

The adjustment of antenna tuning and coupling is discussed in Chapter Ten.

## A Three-Stage 250-Watt Transmitter

The three-stage transmitter illustrated in Figs. 6-56 through 6-60 uses a single Hytron 5514 in the output stage. A 6AG7 in a modified Pierce circuit is the crystal oscillator, which can deliver output at the second harmonic as well as the fundamental frequency of the crystal. It drives a pair of 6L6s arranged to operate as either a push-push doubler or a neutralized single-tube amplifier. Capacitance coupling and plug-in coils are used throughout to simplify the circuit and reduce the cost.

#### Circuit Details

Referring to the circuit diagram of Fig. 6-57, a combination of fixed and grid-leak bias is used in all stages to provide tube protection in case of failure of the crystal to function. The full 400 volts of the low-voltage plate supply is used for the plate of the oscillator, but the voltage-dropping resistor,  $R_3$ , reduces this voltage considerably for the screen of the 6AG7. A split-stator condenser,  $C_4$ , is used to provide a balanced input circuit for the push-push stage.  $C_{13}$  is used to compensate for the output capacitance of the 6AG7 which is connected across the other half of the circuit.

Since a push-push stage cannot be used for

straight-through amplification, one of the 6L6s is made inoperative when the stage is not doubling by turning off its filament by means of  $S_1$ . An incidental convenience of this arrangement is that the plate-grid capacitance of the inoperative tube serves as the neutralizing capacitance for the remaining active tube. A split-stator tank condenser,  $C_9$ , is used in the plate circuit of the doubler stage to help in minimizing stray circuit capacitances.

Because both tubes are not always in operation simultaneously, separate screen voltage-dropping resistors,  $R_5$  and  $R_6$ , are used.

Series plate feed is used in the final amplifier and the circuit is so arranged that the d.c. plate voltage appears between both sides of the tank condenser,  $C_{14}$ , and ground, but not between stators and rotors, thus reducing the required condenser-plate spacing. The tank condenser specified has an insulated frame and shaft. Condensers of other types will require good d.c. insulation from both the chassis and the control dial. The output circuit is equipped with links for coupling to the antenna system.

A closed-circuit jack is provided in the cathode circuit in each stage so that any stage may be keyed as desired. These jacks also may

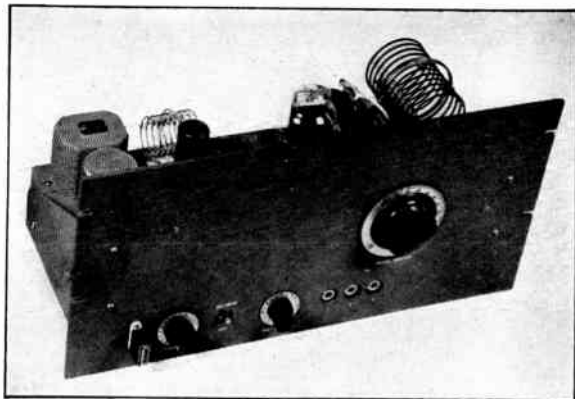


Fig. 6-56 — Front panel view of the 250-watt transmitter. The crystal plugs into a ceramic socket at the lower left. Next in line is the oscillator tuning dial. The toggle switch changes the 6L6 stage from a push-push doubler to a neutralized amplifier. The tuning knob for the 6L6 plate circuit is in the center, followed by the three key jacks. The large dial is connected to the amplifier tuning condenser by an insulated shaft.

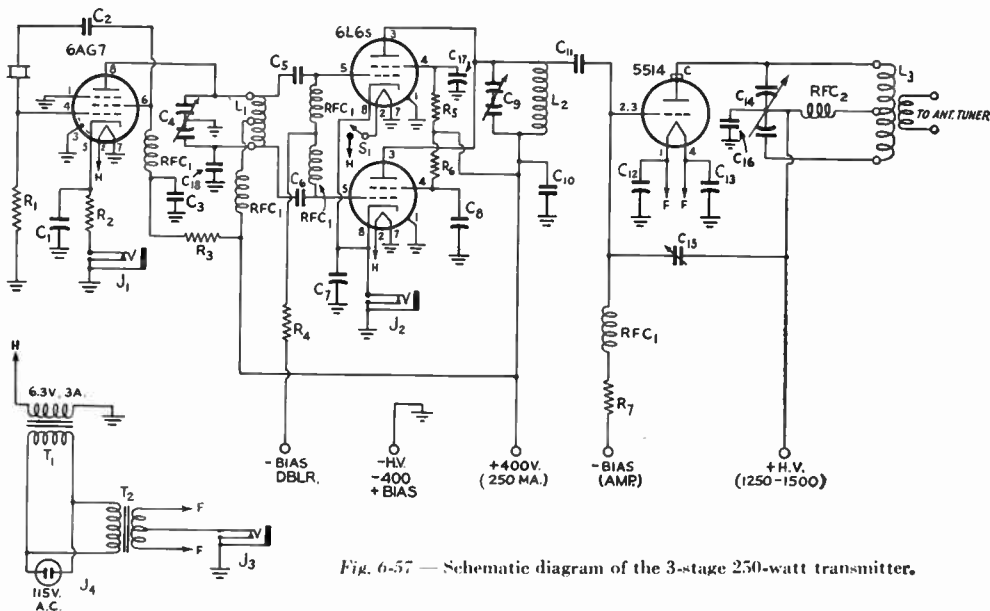


Fig. 6-57 — Schematic diagram of the 3-stage 250-watt transmitter.

- C<sub>1</sub>, C<sub>7</sub>, C<sub>8</sub>, C<sub>12</sub>, C<sub>13</sub>, C<sub>17</sub> — 0.01- $\mu$ fd. paper.
- C<sub>2</sub>, C<sub>3</sub> — 0.0017- $\mu$ fd. mica.
- C<sub>4</sub> — 140- $\mu$ fd. per-section dual variable (Hammarlund HFD-140).
- C<sub>5</sub>, C<sub>6</sub> — 47- $\mu$ fd. mica.
- C<sub>9</sub> — 100- $\mu$ fd. per-section dual variable (Cardwell EU-100-AD).
- C<sub>10</sub> — 0.001- $\mu$ fd. mica.
- C<sub>11</sub> — 47- $\mu$ fd. 1000-volt mica.
- C<sub>14</sub> — 100- $\mu$ fd. per-section transmitting variable (Hammarlund HFD-100-F).
- C<sub>15</sub> — Neutralizing condenser (National ST'N).
- C<sub>16</sub> — 0.001- $\mu$ fd. 5000-volt mica.
- C<sub>18</sub> — 7.5- $\mu$ fd. ceramic (two 15- $\mu$ fd. Erie Ceramicons in series).
- R<sub>1</sub> — 47,000 ohms, 1/2 watt.
- R<sub>2</sub> — 330 ohms, 1/2 watt.
- R<sub>3</sub> — 68,000 ohms, 1 watt.
- R<sub>4</sub> — 4700 ohms, 1 watt.
- R<sub>5</sub>, R<sub>6</sub> — 25,000 ohms, 5 watts.
- R<sub>7</sub> — Bias resistor (see text).
- L<sub>1</sub> — 3.5 and 7 Mc. — 14 turns No. 22 d.s.c., close-wound, 1-inch diam., center-tapped.

- 7 and 14 Mc. — 20 turns No. 22 d.s.c., 1 inch diam., 1 1/8 inches long, center-tapped.
- Above coils wound on Millen Type 45000 forms.
- L<sub>2</sub> — 3.5 Mc. — B & W 80 JCL with 12 turns removed.
- 7 Mc. — B & W 20 JCL.
- 14 Mc. — B & W 10 JCL.
- 28 Mc. — Bud OCL-5.
- (The above coils are supplied with center links. These link windings are unused, but need not be removed.)
- L<sub>3</sub> — B & W TL series.
- 3.5 Mc. — 80 TL; one turn added each side.
- 7 Mc. — 40 TL.
- 14 Mc. — 20 TL.
- 28 Mc. — 10 TL.
- J<sub>1</sub>, J<sub>2</sub>, J<sub>3</sub> — Closed-circuit jack.
- J<sub>4</sub> — 115-v. a.c. male plug.
- RFC<sub>1</sub> — 2.5-mh. 100-ma. r.f. choke.
- RFC<sub>2</sub> — Transmitting r.f. choke (Millen 34140).
- S<sub>1</sub> — S.p.s.t. toggle switch.
- T<sub>1</sub> — Filament transformer, 6.3 volts, 3 amp.
- T<sub>2</sub> — Filament transformer, 7.5 volts, 4 amp. (UTC S-59).

be used for checking cathode currents by means of a meter on a plug.

A 6.3-volt transformer for the tubes in the exciter stages and a 7.5-volt transformer for the 5514 are included on the chassis.

### Construction

The transmitter is built on an 8 x 17 x 3-inch chassis with a standard 10 3/4-inch rack panel. In Fig. 6-58, the exciter stages occupy the right-hand side of the chassis while the output-stage components are grouped to the left. In line, from front to back along the right-hand edge are the 6AG7, a removable shield can which covers L<sub>1</sub>, and the 7.5-volt filament transformer, T<sub>2</sub>. Immediately to the left are the 6L6s and their plate tank coil, L<sub>2</sub>.

The neutralizing condenser for the 5514, C<sub>15</sub>, is mounted on small stand-off insulators in front of the tube. The lead between C<sub>15</sub> and the

grid terminal of the tube passes through a clearance hole in the chassis. The plate tank condenser, C<sub>14</sub>, is elevated on 1/2-inch cone insulators to bring its terminals closer to those of the tank coil at the left. The by-pass condenser, C<sub>16</sub>, is fastened between the rear rotor terminal and the chassis. RFC<sub>2</sub> is to the left of the tank coil.

In the bottom view of Fig. 6-59, the oscillator tank condenser, C<sub>4</sub>, is mounted between the two rows of sockets on metal spacers to bring its shaft level with that of the doubler tank condenser, C<sub>9</sub>, which is mounted on small stand-off insulators to the right. The 6.3-volt filament transformer, T<sub>1</sub>, is fastened to the rear edge of the chassis and the three jacks are set in a row in the opposite front edge.

The circuit diagram of a suitable power supply for operating the 5514 at maximum ratings is shown in Fig. 6-60.

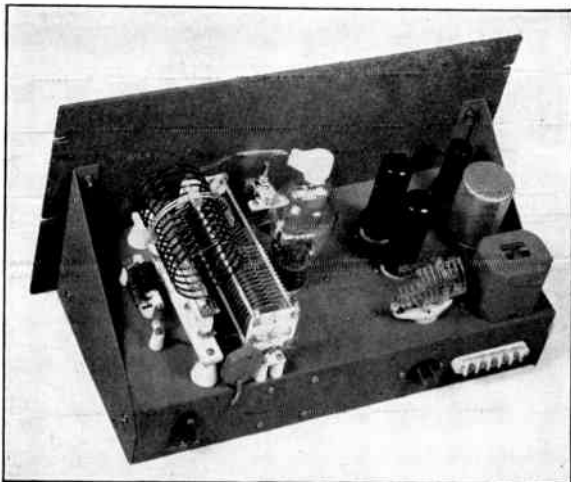


Fig. 6-58 — Chassis layout of the 3-stage 250-watt transmitter. Along the rear edge are the safety terminal for the high-voltage connection, 115-v. a.c. plug for the filament transformers and a terminal strip for bias and low-voltage connections.

### Tuning Characteristics and Circuit Adjustment


The oscillator should function regardless of the tuning of the plate tank circuit. If the plate coils,  $L_1$ , are made closely to the dimensions given, it should be possible to tune to both 3.5 and 7 Mc. with one coil and to 7 and 14 Mc. with the other. The plate-current dip indicating resonance in the output circuit will not be pronounced, so it must be watched for carefully. When the complete transmitter is in operation, the grid current to the final amplifier will be the best indicator of maximum oscillator and buffer-doubler output. With a 400-volt supply, the oscillator screen voltage should be about 180 and the cathode current approximately 18 ma., whether or not the oscillator stage is doubling frequency.

The buffer-doubler should show a cathode current of about 200 ma. with both tubes operating as doublers or 100 ma. with only the single tube in operation as a buffer amplifier. In this stage also, the dip in cathode current at resonance is slight. Grid current to the 6L6s under load should be about 5 ma. per tube. If the difference in grid currents to the two tubes is more than 1 ma., the value of the balancing condenser,  $C_{18}$ , should be changed until balanced grid current is obtained.

With fixed bias applied, a final-amplifier grid current of 100 ma. or more should be obtained before plate voltage is applied to the 5514. Before neutralization, tuning the amplifier plate tank circuit through resonance should cause a wide deflection in grid current. Starting at minimum capacitance, the neutralizing condenser should be adjusted, bit by bit, until the dip in grid current is brought to a barely noticeable minimum or eliminated altogether. Increasing the capacitance of the neutralizing condenser beyond this point should result in an increase in the grid-current dip again. The correct adjustment is the one that produces least change in grid current as the amplifier plate tank circuit is tuned through resonance.

With the amplifier neutralized, plate voltage may be applied and the amplifier coupled to an antenna system and loaded as described in Chapter Ten. For maximum c.w. ratings, the plate voltage should not exceed 1500 volts and the plate current 175 ma., with  $R_7$  500 ohms. Similar ratings with 100-per-cent plate modulation are 1250 volts and 142 ma., with  $R_7$  150 ohms. Under load, the grid current will be less than without load. The excitation should be adjusted to obtain the rated value of 60 ma. under actual operating conditions with load.

Fig. 6-59 — Bottom view of the 3-stage 250-watt transmitter.

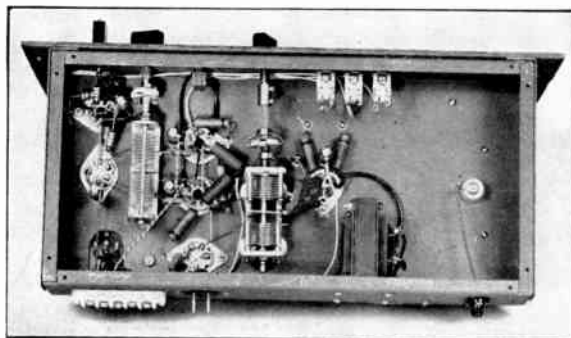

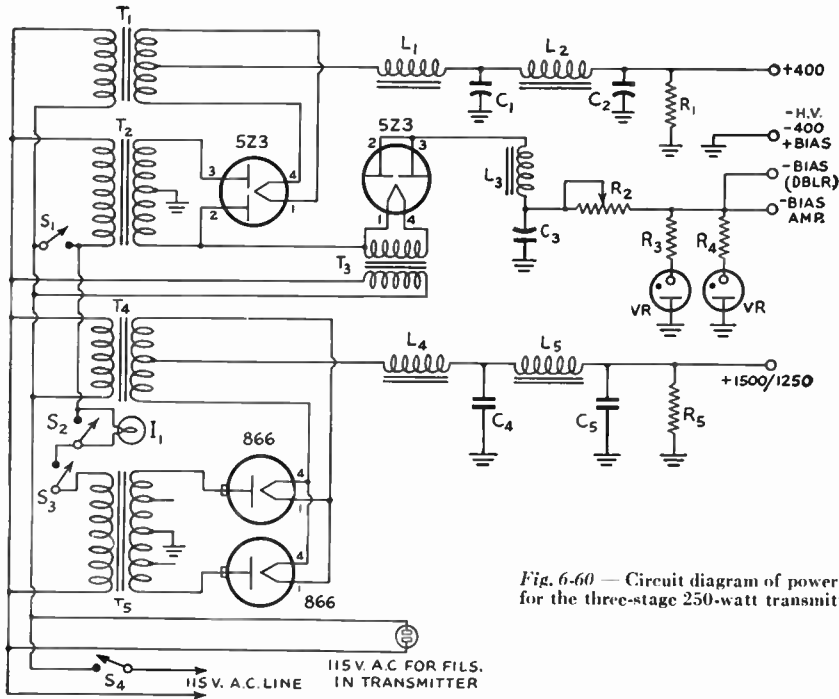


Fig. 6-60 — Circuit diagram of power supply for the three-stage 250-watt transmitter.

- C<sub>1</sub>, C<sub>2</sub>, C<sub>3</sub>— 8- $\mu$ fd. 600-volt-wkg. electrolytic.
- C<sub>4</sub>, C<sub>5</sub>— 4- $\mu$ fd. 2000-volt oil-filled.
- R<sub>1</sub>— 25,000 ohms, 25 watts.
- R<sub>2</sub>— 30,000 ohms, 10 watts, with slider.
- R<sub>3</sub>, R<sub>4</sub>— 47 ohms, 1 watt.
- R<sub>5</sub>— 25,000 ohms, 150 watts.
- L<sub>1</sub>— 5/25-hy. 225-ma. swinging choke.
- L<sub>2</sub>— 20-hy. 225-ma. smoothing choke.
- L<sub>3</sub>— 30-hy. 75-ma. filter choke.
- L<sub>4</sub>— 5/25-hy. 175-ma. swinging choke.
- L<sub>5</sub>— 10-hy. 175-ma. smoothing choke.
- I<sub>1</sub>— 150-watt 115-volt lamp.
- S<sub>1</sub>, S<sub>3</sub>, S<sub>4</sub>— 10-amp. toggle switch.
- S<sub>2</sub>— 5-amp. toggle switch.
- T<sub>1</sub>, T<sub>3</sub>— 5-volt 3-amp. filament transformer.

- T<sub>2</sub>— 100-v. d.c. 225-ma. plate transformer.
  - T<sub>4</sub>— 2.5-volt 10-amp. filament transformer, 10,000-volt insulation.
  - T<sub>5</sub>— 1500/1250-v. d.c. 175-ma.-or-more plate transformer.
  - VR— VR-75 voltage-regulator tube.
- S<sub>4</sub> turns on all filaments in power supply and transmitter and sets up circuit so that S<sub>1</sub> will turn on 400-volt supply. S<sub>1</sub> also sets up the circuit so that S<sub>3</sub> will turn on high-voltage supply. When S<sub>2</sub> is open, the lamp I<sub>1</sub> is inserted in series with the primary of T<sub>5</sub> to reduce voltage during adjustment. In operation of the transmitter, S<sub>1</sub> serves as the stand-by switch. R<sub>2</sub> should be adjusted so that the VR tubes barely ignite with the transmitter not operating.

## A Two-Stage High-Power Transmitter

The photographs of Figs. 6-61, 6-63 and 6-64 show a two-stage transmitter capable of handling a power input of 900 watts on c.w. or 675 watts on 'phone. The circuit diagram is shown in Fig. 6-62. It is a simple arrangement in which a 6L6 Tri-tet crystal oscillator drives an Eimac 4-250A in the output stage, either at the crystal fundamental or at the second harmonic so that the transmitter will cover two bands with a single crystal of proper frequency without doubling in the output stage. Through the use of plug-in coils and a selection of crystals, the transmitter may be used in all bands between 3.5 and 28 Mc. inclusive.

Any one of four crystals may be selected by means of S<sub>1</sub>, although more crystal positions may be added. R<sub>4</sub>, R<sub>5</sub> and R<sub>6</sub> are metering resistors across which the milliammeter is switched to read combined oscillator screen- and-plate current, amplifier grid current or

amplifier cathode current. R<sub>5</sub> has sufficient resistance to have no practical effect upon the meter reading, but the other shunts which are made from copper wire are adjusted to give a meter-scale multiplication of 10, making the full-scale reading 500 ma. The diagram shows both stages keyed simultaneously. If amplifier keying only is desired, R<sub>1</sub> should be connected to ground instead of to the key terminal.

### Construction

The transmitter is built on a 10 × 17 × 3-inch chassis with a 10½-inch standard rack panel. The mechanical arrangement shown in the photographs should be followed as closely as possible, since upon the placement of parts may depend the stability of the amplifier. The oscillator-circuit components are grouped at the left-hand end of the chassis. The Millen crystal sockets are lined up with their centers

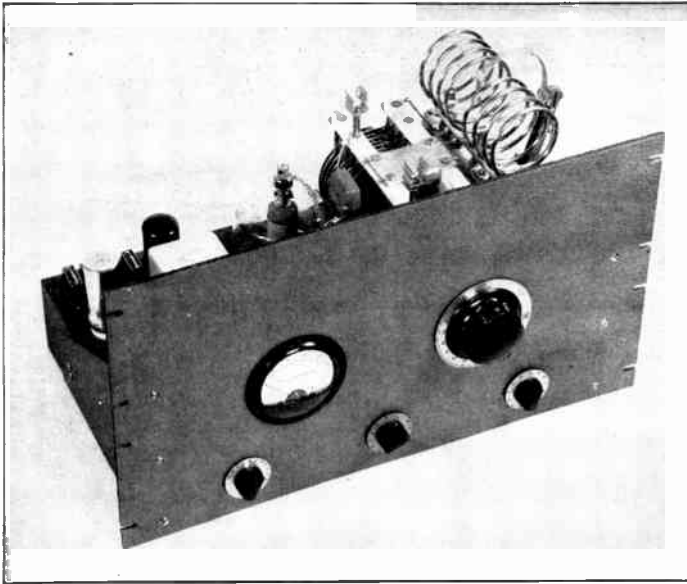


Fig. 6-61 — Front view of the 4-250A transmitter. Along the bottom of the panel, from left to right, are the controls for the oscillator tuning condenser, the crystal switch and the metering switch. The large dial is for the output tank condenser.

1½ inches in from the rear edge of the chassis in the left-hand corner. The sockets for the 6L6 and the plug-in cathode coil, L<sub>1</sub>, are in line with their centers, 3½ inches from the back edge of

the chassis, while the oscillator plate coil is in line with the 6L6, 6 inches from the rear edge of the chassis and 3½ inches from the left-hand end. The crystal switch is placed near the 6L6

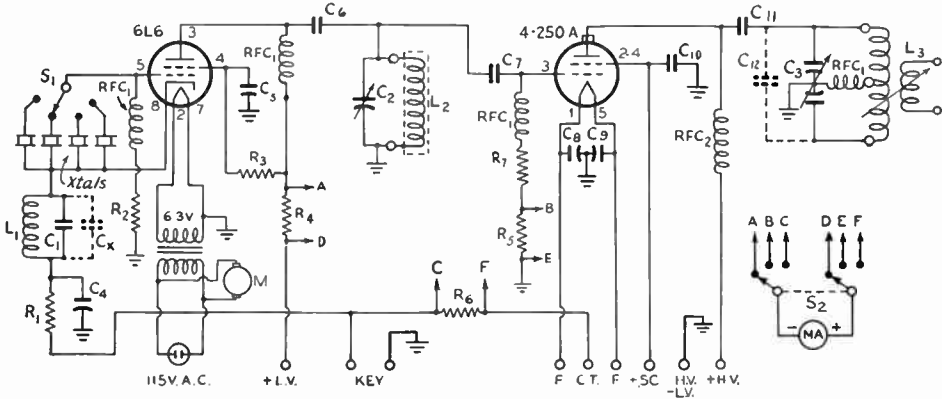


Fig. 6-62 — Circuit diagram of the two-stage high-power transmitter.

- C<sub>1</sub> — 100- $\mu$ fd. mica.
- C<sub>2</sub> — 100- $\mu$ fd. variable (National ST-100).
- C<sub>3</sub> — 50- $\mu$ fd. per-section 0.171-inch-plate-spacing variable (Millen 14050).
- C<sub>4</sub>, C<sub>5</sub>, C<sub>8</sub>, C<sub>9</sub> — 0.01- $\mu$ fd. paper.
- C<sub>6</sub> — 0.0015- $\mu$ fd. mica.
- C<sub>7</sub> — 100- $\mu$ fd. mica, 5000 volts.
- C<sub>10</sub> — 0.001- $\mu$ fd. mica, 5000 volts.
- C<sub>11</sub> — 0.001- $\mu$ fd. mica, 10,000 volts.
- C<sub>12</sub> — Vacuum-type padding capacitor, 25  $\mu$ fd., 16,000 volts (GE G1-122).
- CX — 100- $\mu$ fd. mica (for 3.5-Mc. crystals only).
- R<sub>1</sub> — 220 ohms, 1 watt.
- R<sub>2</sub> — 47,000 ohms, ½ watt.
- R<sub>3</sub> — 5,000 ohms, 10 watts.
- R<sub>4</sub>, R<sub>6</sub> — 58 inches No. 22 copper wire wound on small-diam. form.
- R<sub>5</sub> — 47 ohms, ½ watt.
- R<sub>7</sub> — 5000 ohms, 25 watts.
- L<sub>1</sub> — 3.5-Mc. crystals: 22 turns No. 22 d.s.c., ½-inch diam., close-wound. CX connected across full winding.
- 7-Mc. crystals: 12 turns No. 22 d.s.c., ½-inch diam., close-wound.
- 14-Mc. crystals: 6 turns No. 20 d.s.c., ½-inch diam., ⅝-inch long.
- L<sub>2</sub> — 3.5 Mc.: 40 turns No. 22 d.s.c., 1-inch diam., close-wound.
- 7 Mc.: 20 turns No. 22 d.s.c., 1-inch diam., close-wound.
- 14 Mc.: 9 turns No. 22 d.s.c., 1-inch diam., ¾-inch long.
- 28 Mc.: 5 turns No. 20 enam., ⅝-inch diam., ⅝-inch long (on Millen Type 45500 threaded ceramic form).
- L<sub>3</sub> — B & W TVII-series coils.
- M — Fan motor (Barber-Colman Type d Yab 569 1 with Type Yab 355-2 2½-inch fan; Rockford, Ill.).
- MA — 0-50 milliammeter.
- RFC<sub>1</sub> — 2.5-mh. r.f. choke.
- RFC<sub>2</sub> — Hammarlund CH-500 r.f. choke.
- S<sub>1</sub> — 4-position ceramic tap switch.
- S<sub>2</sub> — Double-gang 3-position switch.



Fig. 6-63—Rear view of the two-stage high-power transmitter, showing the vacuum-type padding condenser in place on top of the tank condenser.


socket and set at an angle with respect to the edges of the chassis. It is controlled by a knob at the center by means of a long  $\frac{1}{4}$ -inch shaft, which runs diagonally across the chassis, and a Millen 39005 all-metal flexible shaft coupling of the "universal-joint" type.

The socket for the 4-250A is centered  $7\frac{3}{4}$  inches from the left-hand end of the chassis and 3 inches from the rear edge. It is spaced  $1\frac{1}{8}$  inches below the chassis on metal pillars so that the base of the tube is shielded from the plate. A spring contact is fastened to the socket so that the metal ring around the base of the tube will be grounded when the tube is inserted in the socket. The 4-250A requires a small amount of forced-air cooling. This is supplied by a small fan, *M*, Fig. 6-62, directed at the base of the tube. A bottom plate should be used on the chassis so that the air will be forced up around the envelope of the tube. The

amplifier plate-tank condenser is placed with its shaft  $5\frac{1}{4}$  inches in from the right-hand edge of the chassis, while the coil-base assembly is elevated on 3-inch cone insulators centered  $2\frac{1}{2}$  inches from the edge. The clips for the padding condenser,  $C_{12}$ , required for the 3.5- and 7-Mc. bands, are mounted on top of the condenser on 1-inch tubular spacers. A pair of long 6-32 mounting screws, passing through the spacers, serve to make the connection between the stators of  $C_3$  and the terminals of  $C_{12}$ . The Hammarlund CH-500 r.f. choke,  $RFC_2$ , is mounted alongside the tank condenser, near the center, with the plate-blocking condenser,  $C_{11}$ , fastened to the top.

Plate voltage is fed from a Millen safety terminal in the rear edge of the chassis to the bottom end of the r.f. choke through a Millen 32101 steatite bushing. The hole for the safety terminal should have a clearance of about  $\frac{1}{16}$

Fig. 6-64—Bottom view showing the arrangement of parts under the chassis. Mounted off the rear edge of the chassis are the oscillator (left) and amplifier (right) grid chokes. The oscillator plate choke is above. The condenser under the crystal-switch control shaft is the coupling condenser,  $C_7$ . The oscillator tuning condenser,  $C_2$ , the 6.3-volt filament transformer and the metering switch are along the front edge of the chassis. The ventilating fan is to the right of the tube socket.

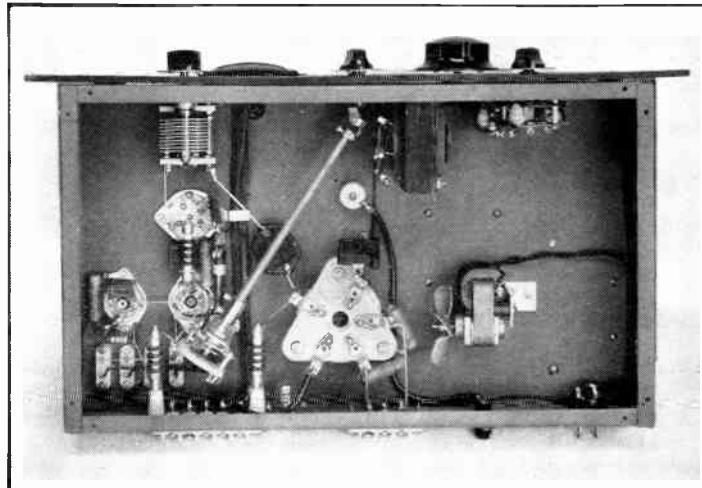

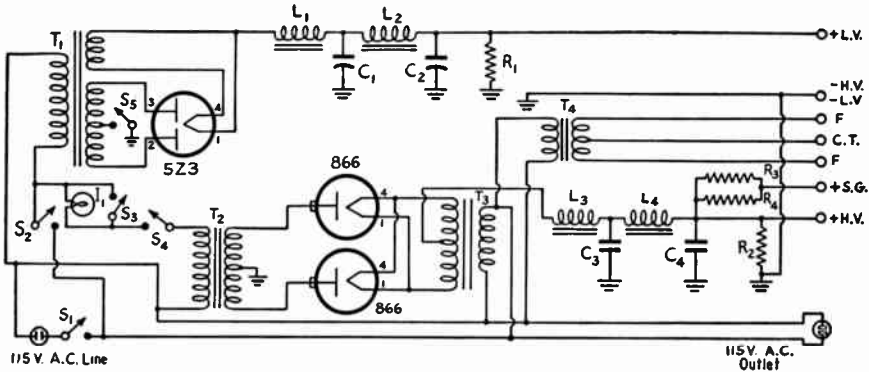


Fig. 6-65 — Diagram of power supply suitable for use with the two-stage high-power transmitter.

- C<sub>1</sub>, C<sub>2</sub> — 8- $\mu$ fd. 600-volt-wkg. electrolytic.
- C<sub>3</sub> — 2- $\mu$ fd. 3000-volt oil-filled.
- C<sub>4</sub> — 4- $\mu$ fd. 3000-volt oil-filled.
- R<sub>1</sub> — 20,000 ohms, 25 watts.
- R<sub>2</sub> — 50,000 ohms, 200 watts.
- R<sub>3</sub>, R<sub>4</sub> — 50,000 ohms, 160 watts.
- L<sub>1</sub>, L<sub>2</sub> — 20-hy. 100-ma. filter choke.
- L<sub>3</sub> — 5/25-hy. 300-ma. swinging choke.
- L<sub>4</sub> — 20-hy. 300-ma. smoothing choke.
- I<sub>1</sub> — 200-watt 115-volt lamp.
- S<sub>1</sub>, S<sub>2</sub>, S<sub>4</sub> — 10-amp. toggle switch.
- S<sub>3</sub> — 5-amp. toggle switch.
- S<sub>5</sub> — Ceramic rotary switch, single section, 2 positions.
- T<sub>1</sub> — Power transformer — 400 v. d.c., 100 ma. or more; 5 v., 3 amp.

- T<sub>2</sub> — Plate transformer — 2500 to 3000 volts d.c., 300 ma. or more.
  - T<sub>3</sub> — 2.5-volt 10-amp. filament transformer, 10,000-volt insulation.
  - T<sub>4</sub> — 5-volt 15-amp. filament transformer.
- S<sub>1</sub> turns on all filaments in power supply except 523; also those in the transmitter and sets up circuit for S<sub>2</sub>. S<sub>2</sub> turns on low-voltage supply and sets up circuit for S<sub>4</sub> which turns on high-voltage supply. Since the oscillator in the transmitter is keyed, it is not necessary to turn off the low-voltage supply for stand-by. S<sub>3</sub> may be used in case it is not desired to turn off the 523 filament while changing bands, etc. When S<sub>3</sub> is open, I<sub>1</sub> is in series with the high-voltage transformer primary to reduce voltage for adjustments.

inch around the part which goes through the chassis, to decrease the danger of a voltage breakdown at this point. The link output terminals are in the right rear corner, insulated from the chassis on a National FWG polystyrene terminal strip.

Underneath, at the amplifier end of the chassis, are the metering switch, S<sub>2</sub>, and the 6.3-volt filament transformer.

On the panel, the milliammeter is placed to balance the amplifier tuning dial, the meter-switch knob to balance that of the oscillator tuning condenser, while the crystal switch is at the center, near the bottom edge. Along the rear edge of the chassis, from right to left, as viewed from the rear, are a terminal strip for making connections to the oscillator supply and to the external screen-voltage dropping resistor, the key jack, filament terminals for the 4-250A including a center-tap connection, a safety terminal for the high-voltage connection, and a male plug for the 115-volt line to the 6.3-volt filament transformer and the fan motor.

The cathode coils, L<sub>1</sub>, are wound on Millen oetal-base shielded forms without tuning slugs. A change in cathode coils is required only with a change in the band in which the crystal lies. The coil for use with 3.5-Mc. crystals requires an additional 100- $\mu$ fd. mica condenser, C<sub>X</sub>, connected across the winding as shown by the dotted lines in Fig. 6-62. This condenser is placed inside the plug-in shield along with the 3.5-Mc. coil. The 100- $\mu$ fd. capacitor, C<sub>1</sub>, which is connected permanently in the circuit,

is sufficient for use with 7- and 14-Mc. crystals. Since larger coils are desirable for the plate circuit of the oscillator, the coils for L<sub>2</sub> are wound on 1-inch diameter forms enclosed in National Type PB-10 plug-in shield cans. The shield should be grounded to the chassis through one of the available pins in the base.

External connections to the unit are indicated in Fig. 6-62. Keying of the oscillator alone is not recommended because of the effects of soaring screen voltage, which makes it impossible to cut off plate and screen currents in this unit without exceeding the normal operating bias. For this reason, it is highly advisable to use an overload relay in the plate-supply circuit of the amplifier, to protect the tube in case the oscillator fails to function. The circuit diagram of a suitable power supply for this transmitter is shown in Fig. 6-65.

**Adjustment**

After the proper coils for the desired band have been plugged in and the crystal switch turned to select the proper crystal, the key may be closed with the low-voltage supply turned on, but with the high-voltage supply turned off. The combined oscillator plate-and-screen current at resonance should be between 35 and 75 ma., depending upon the crystal frequency and whether or not the oscillator is doubling frequency. If the oscillator is operating at the crystal fundamental frequency, oscillation will cease abruptly when the plate tank circuit is tuned to the high-capacitance side of reso-



nance. For reliable operation this circuit should be tuned slightly to the low-capacitance side. When doubling frequency this characteristic disappears so that the plate circuit may be tuned to exact resonance where maximum output should occur.

Tuning the oscillator plate circuit to resonance should result in a grid-current reading when the meter is switched to the second meter-switch position. The reading will vary between 30 and 35 ma. to 50 ma. or more, depending upon the frequency and whether the oscillator is doubling frequency or working "straight through." The potential of the high-voltage supply should be reduced during preliminary adjustments. If no other means of reducing the voltage is available a 200-watt 115-volt lamp may be connected in series with the primary winding of the high-voltage transformer. The plate circuit of the amplifier

should be tuned to resonance first with the antenna link swung out to the minimum-coupling position. The output tank circuit of the amplifier may be coupled through the link coil, either directly to a properly-terminated low-impedance transmission line, or through an antenna tuner to any type of antenna system. With the antenna system connected and the link swung in for maximum coupling, the plate current should increase when the antenna system is tuned through resonance. Every adjustment of the coupling or tuning of the antenna system should always be followed by a readjustment of the tuning of the amplifier tank circuit for resonance. As the loading is increased the plate current at resonance will increase. The loading may be carried up to the point where the plate current (cathode current, minus grid and screen currents) is 300 ma. at 3000 volts.

## An Enclosed 1-Kw. Transmitter

Figs. 6-66, 6-68, 6-69 and 6-71 show different views of an enclosed three-stage transmitter which will handle an input of 1 kw., with c.w. operation on all bands from 3.5 or 7 Mc. to 28 Mc. using either 3.5- or 7-Mc. crystals. Push-pull 813s are used in the final amplifier.


### Circuits

Fig. 6-67 shows the circuit of the exciter. A pair of 807s are used in an arrangement that permits either of the two stages to be used as a Tri-tet oscillator. The second stage may be

operated also as a frequency doubler.

The arrangement shown has a number of advantages. The two 807 stages need not be operated at the same frequency for output on any band, thereby avoiding stabilization difficulties sometimes encountered with tubes of this type when operating as straight amplifiers. It provides for oscillator keying for break-in work at 3.5 and 7 Mc. and amplifier keying for 14 and 28 Mc. where chirp with oscillator keying might become objectionable. Shielding problems are reduced because the first 807

◆  
Fig. 6-66—A three-stage 3.5-30-Mc. kilowatt transmitter using push-pull 813s. Measuring 18 inches wide, 24 inches high, and 16 inches deep, it fits readily on most operating tables. The hinged front panel drops down for coil changing. Interlock switches combined with complete enclosure ensure against accidental contact with any high-voltage circuits when the power is on.  
◆

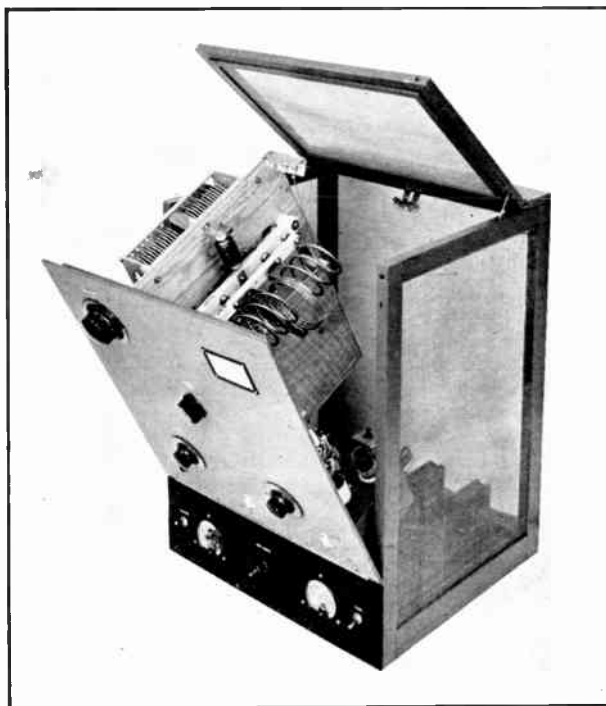

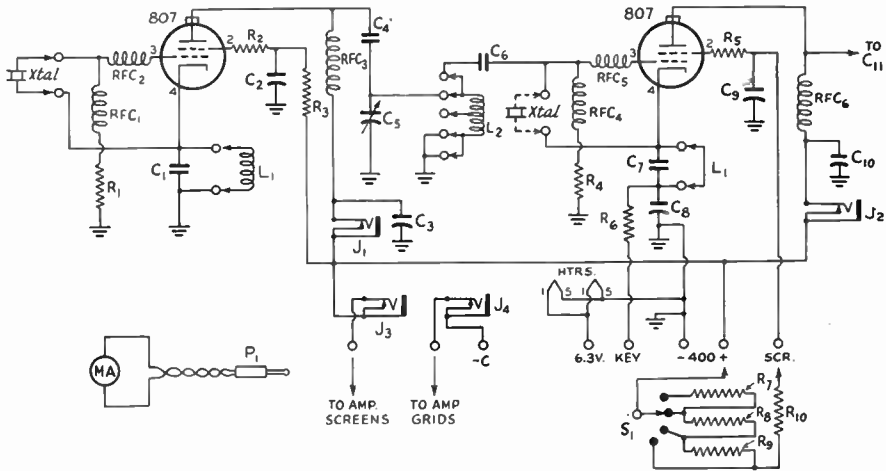


Fig. 6-67 — Circuit diagram of the exciter section of the enclosed 1-kw. transmitter.

$C_1, C_7$  — 150- $\mu$ fd. mica.  
 $C_2, C_3, C_9, C_{10}$  — 0.01- $\mu$ fd. paper, 600 volts.  
 $C_4$  — 470- $\mu$ fd. mica, 1000 volts.  
 $C_5$  — 50- $\mu$ fd. variable (National ST-50).  
 $C_6$  — 100- $\mu$ fd. mica, 1000 volts.  
 $C_8$  — 0.0047- $\mu$ fd. mica.  
 $R_1$  — 0.33 megohm, 1 watt.  
 $R_2, R_5$  — 50 to 100 ohms,  $\frac{1}{2}$ -watt carbon.  
 $R_6$  — 330 ohms, 1 watt.  
 $R_3$  — 25,000 ohms, 10 watts.  
 $R_4, R_7$  — 47,000 ohms, 1 watt.  
 $R_{10}$  — 10,000 ohms, 1 watt.  
 $R_8, R_9$  — 22,000 ohms, 1 watt.  
 $L_1$  — Tri-tet cathode coil; for 3.5-Mc. crystals, 13 turns No. 22 d.s.c., close-wound, diameter 1 inch, shimmed by extra 75- $\mu$ fd. mica condenser inserted inside form. For 7-Mc. crystals: 3 turns

No. 22 d.s.c., close-wound on 1-inch diameter form. (Cathode coils wound on Millen No. 45004 forms.)

$L_2$  — Plate coil; for 3.5 Mc., 36 turns No. 22 d.s.c., close-wound; 7 Mc., 16 turns No. 18 bare, length 2 inches; 14 Mc., 8 turns No. 18 bare, length 2 inches; 28 Mc., 4 turns No. 18 bare, length 1 inch. All coils wound on 1 $\frac{7}{8}$ -inch diameter forms (Millen No. 44001) and tapped at center.

$J_1, J_2, J_3, J_4$  — Closed-circuit jack.

MA — 0–200 d.c. milliammeter.

$P_1$  — Insulated plug.

$RFC_1, RFC_3, RFC_4, RFC_6$  — 2.5-mh. r.f. choke.

$RFC_2, RFC_5$  — Parasitic chokes; 18 turns No. 20 d.e.c. on  $\frac{1}{4}$ -inch diameter form (a high-value 1-watt resistor is suitable as a form).

$S_1$  — 4-position single-pole rotary switch.

never is called upon to operate at the same frequency as either of the two following stages. A single set of coils suffices for both stages of the exciter.

When both 807 stages are in use, the crystal and cathode coils are plugged into the first stage, while a jumper closes the cathode circuit of the second stage. When the second 807 is used as an oscillator, crystal and cathode coil are transferred to the second stage and removal of the coil in the plate circuit of the first stage breaks the connection between the two stages.

Parallel plate and grid feed is used in both exciter stages, while the screens are fed through series voltage-dropping resistors. The value of the resistor for the screen of the second tube may be varied in steps by  $S_1$  and this provides a means of adjusting the excitation to the final amplifier. Jacks are provided for shifting a milliammeter from one circuit to another to obtain readings of plate current in either exciter stage or grid or screen current to the final amplifier.  $RFC_2, RFC_5, R_2$  and  $R_5$  are inserted to prevent v.h.f. parasitic oscillation. The key is in the cathode of the second 807 stage.

The circuit of the push-pull 813 final amplifier is shown in Fig. 6-70. Series feed is used in both grid and plate circuits. Although the 813 is a

screened tube, experience has shown that neutralization is necessary to prevent self-oscillation. A single set of coils suffices for  $L_2$  in both the amplifier section and the exciter section. Variable-link output is provided for coupling to the antenna system.

### Construction

The r.f.-circuit components are assembled on a panel of  $\frac{1}{4}$ -inch crackle-finished tempered Presdwood, 18 inches wide and 19 inches high, backed with copper screening. The panel is hinged at the bottom so that it may be tipped outward, as shown in Fig. 6-66, for changing plug-in coils, etc. Suspended from the back of the panel is a vertical partition of  $\frac{5}{8}$ -inch plywood, 13 $\frac{1}{4}$  inches wide and 18 inches high. This partition also is covered on both sides with copper screening from the bottom edge up to within 6 inches of the top. The lower edge of the partition comes  $\frac{5}{8}$  inch above the lower edge of the panel and is placed 11 $\frac{1}{4}$  inches from the right-hand edge of the panel as viewed from the front. A strip of  $\frac{5}{8}$ -inch plywood 1 $\frac{1}{4}$  inches wide runs across the top of the panel, as shown in Fig. 6-71, and a similar strip  $\frac{5}{8}$  inch wide runs across the bottom of the panel, flush with the lower edge. The bottom strip provides a means of fastening the hinge to the panel.

Thin strips of wood along the vertical edges of the panel serve to hold the copper screening in place, while a metal strip is used to bind the edges of the partition.

The portion of the r.f. circuit shown in Fig. 6-67 is built as a subassembly on a  $5 \times 10 \times 3$ -inch chassis, fastened to the panel in the lower left-hand corner and braced by the partition, as shown in Figs. 6-68 and 6-69. As viewed from the rear, the first 807 is placed near the left-hand edge of the chassis with its cathode-coil socket behind. The tuning condenser,  $C_5$ , is placed between the 807 and the first-stage tank coil, 4 inches from the outside end of the chassis. The socket for the cathode coil for the second 807 is in the rear corner to the right. The socket for the second 807 is set in the right-hand edge of the chassis and a clearance hole for the base of the tube is cut in the partition so that the tube protrudes horizontally as shown in Fig. 6-69. The two crystal sockets are fastened to the front edge of this chassis and protrude through holes cut in the panel.

In the rear edge of the chassis are the four meter jacks and strips bearing the terminals indicated in Fig. 6-67.

The 813s and their input-circuit components are made up as another subassembly on a  $5\frac{1}{2} \times 9\frac{1}{2} \times 1\frac{1}{2}$ -inch chassis which is fastened centrally on the partition with its bottom edge  $3\frac{1}{2}$  inches up from the bottom edge of the partition, as shown in Fig. 6-71. The two tube sockets are submounted as close as possible to the ends of the chassis with their centers  $2\frac{1}{2}$  inches in from the outside edge. Underneath, as shown in Fig. 6-69, the coil socket is centered on the tube sockets and the tank condenser,  $C_{13}$ , is to the left. It is placed so that its dial will balance the dial of  $C_5$  on the panel. The strips which form the neutralizing condensers are mounted on feed-through insulators set in the chassis about  $1\frac{1}{2}$  inches from

the bases of the tubes. A ceramic strip set in the rear edge of the chassis bears the power-supply terminals indicated in Fig. 6-70.

The plate tank condenser for the 813s is fastened to the partition above the screening, the wood serving to insulate the frame and rotors from ground as required. The output tank-coil jack-bar is mounted on short stand-off insulators on the opposite side of the partition, with its center 4 inches below the top edge of the partition.

The link control shaft is coupled to a knob centered on the panel by means of a pair of Millen universal-joint-type shaft couplings. Leads from the link terminals are brought to the upper rear corner of the partition where they connect to a pair of banana plugs which slide into jacks connected to feed-through insulators set in the back of the enclosure. These serve as the output terminals.

Below the main panel is a smaller panel  $5\frac{1}{4}$  inches high which is used for the control switches and meters.

Plenty of room is available within the enclosure to the rear of the panel assembly for filament transformers and the additional terminals, indicated in Fig. 6-72, which serve as junctions between the external and internal power leads. One of the two interlock switches is of the push-button type. This is mounted on an aluminum bracket fastened to the floor

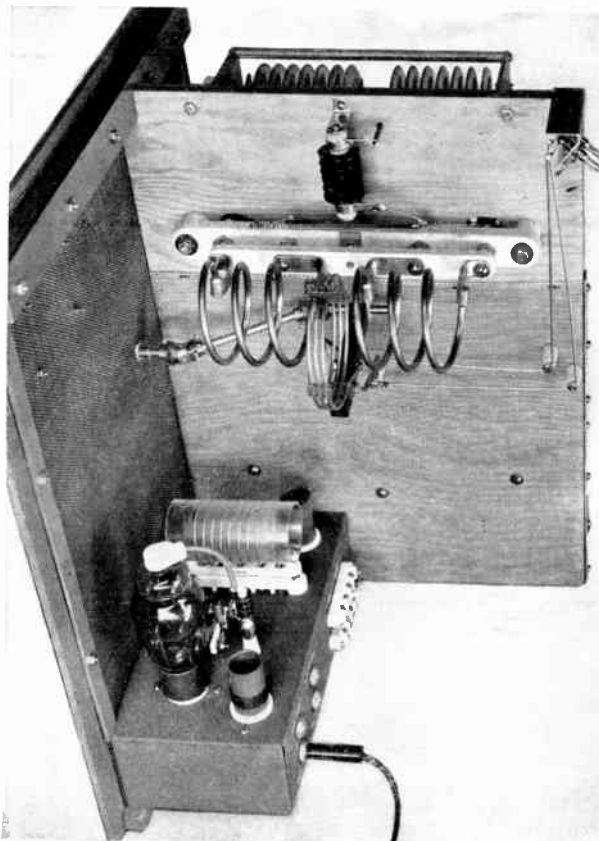


Fig. 6-68 — The exciter unit of the enclosed 1-kw. transmitter is mounted between the vertical partition and the panel, and serves as additional support for both. This view shows the first 807 with its Tri-tet cathode coil in the foreground. The plate tuning condenser is partly concealed by the tube, and to its right is the plate choke. The small bakelite coil form behind the plate coil is the jumper for the second-tube cathode circuit; when the latter tube is used as the oscillator a Tri-tet cathode coil goes in this socket.

The final tank-coil assembly and plate choke are at the top. The banana plugs at the right automatically engage a pair of jacks on the rear of the case when the panel is in position, providing connection to the antenna binding posts.

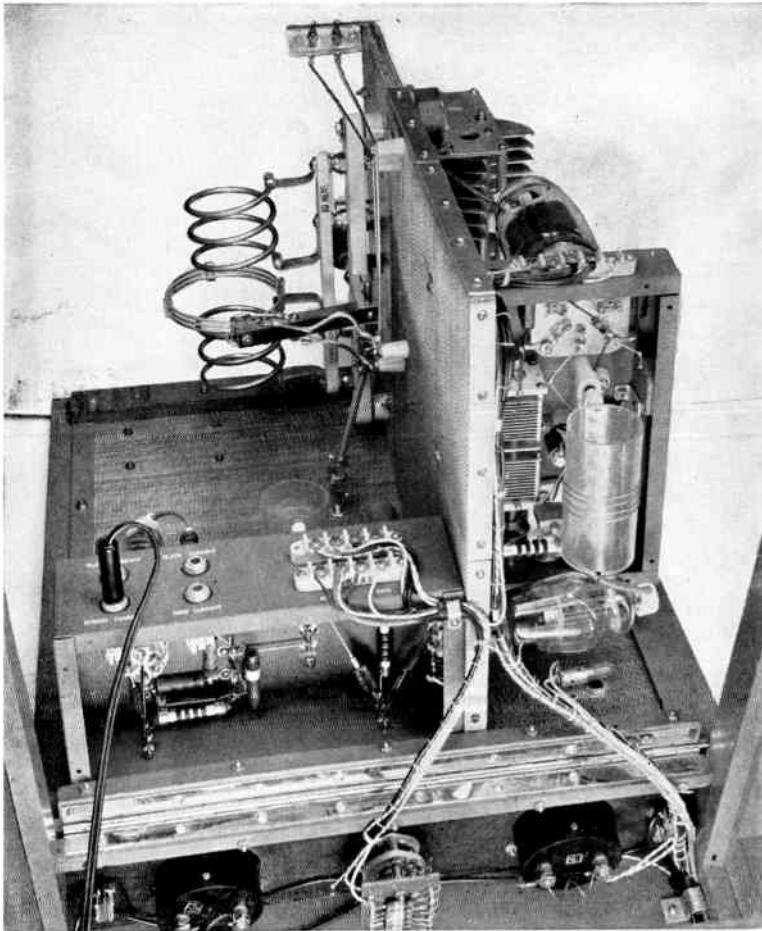


Fig. 6-69 — View from the back of the enclosed 1-kw. transmitter with the front panel dropped down. The second 807 projects through the partition to bring its plate near the tuned circuit that feeds the amplifier grids. The 807 plate choke, visible just below the amplifier grid-tuning condenser, is supported by a feed-through insulator mounted on the end of the exciter chassis. The four metering jacks are accessible only when the case and interlock switches are open, providing for safety.

of the enclosure so that the rear end of the lower edge of the partition closes the switch when the panel is hinged back into place. The circuit is broken as soon as the panel is tipped forward. The second interlock is fastened to the side of the enclosure where it is operated by the top lid.

The frame of the enclosure is made up of  $1\frac{1}{4}$ -inch strips cut from  $\frac{5}{8}$ -inch plywood. It is 18 inches wide,  $24\frac{1}{2}$  inches high and 16 inches deep overall, and has a solid bottom of the same plywood material. The copper screening is tacked over the outside of the panels formed by the framework and the edges of the screening are covered with thin strips of wood. The woodwork is finished off in gray enamel.

#### Power Supply

The diagram of a suitable power supply for operating the 813s at maximum rated input is shown in Fig. 6-73. At current tube prices, however, the 813s are an economical proposition for operation at considerably less than maximum ratings if power-supply considerations make this desirable.

#### Adjustment

Since there is only a maximum of three tuned circuits to adjust, tuning the transmitter for any desired output frequency is a relatively simple job. Undesired harmonic responses, always to be found in a multiband rig, are quite readily identifiable as such, so there is little danger of tuning up on the wrong harmonic if a little care is used in watching the dial readings. For reasons given previously, the design does not provide for operating the first 807 out-

TABLE 6-II

Comb.	Xtal f	Output f	1st 807 Plate	2nd 807 Plate
A	3.5	3.5	—	3.5
B	3.5	7	—	7
C	7	7	—	7
D	3.5	7	3.5	7
E	3.5	14	7	14
F	7	14	7	14
G	3.5	28	14	28
H	7	28	14	28

put at the same frequency as that of the final amplifier and this sort of operation should not be attempted, even if the constructor is willing to make the extra coils, since the simplified construction does not provide the necessary shielding between the input and output circuits of the final amplifier.

The accompanying Table 6-II shows the correct coils to be used in the 807 tank circuits, depending upon the crystal frequency and the desired output frequency. Combinations A, B and C, for 3.5- and 7-Mc. output, permit break-in operation in these two bands, since in each of these cases the keyed stage (the second 807) is operating as the oscillator. In the remainder of the combinations, the keyed stage operates as a frequency multiplier, the first 807 becoming the oscillator, which runs continuously.

Table 6-III gives the approximate dial settings for resonance in the three tank circuits. Variations in wiring or coil dimensions will, of course, alter these readings, but they may be used as a guide. The last column to the right shows the dial setting where undesired crystal-harmonic responses may be expected in the multiplier circuit, the harmonics being identified.

It is advisable initially to choose one of the first three combinations from Table 6-II — one that requires the use of only two stages. With the proper coils and crystal plugged in (be sure to plug the crystal in the right socket!), the low-voltage and bias supplies may be turned on and the key closed. At some point within the range of the 807 tank condenser the plate current should dip to a minimum, rising on either side. If the tank circuit is tuned to the crystal frequency (3.5 Mc. with a 3.5-Mc. crystal or 7 Mc. with a 7-Mc. crystal) the crystal will usually stop oscillating entirely, as indicated by a sudden increase in plate current to a high value when the tank circuit is tuned

Comb.	1st 807	2nd 807	Final Amp.	Undesired Harm., 2nd 807
A	—	75	45	None
B	—	15	25	3rd-90
C	—	15	25	None
D	50	15	25	3rd-90
E	60	20	75	5th-60/6th-85
F	60	20	75	3rd-90
G	70	80	85	6th-20/7th-53
H	70	80	85	3rd-23

to the high-capacitance side of the dip in plate current. The best tuning adjustment under these circumstances is a bit to the low-capacitance side of the dip. When the oscillator tank circuit is tuned to a harmonic of the crystal frequency, the circuit normally will continue to oscillate regardless of the setting of the tank condenser. Tuning is then merely a matter of adjusting the tank circuit to resonance as indicated by the plate-current dip or by maximum final-amplifier grid current. Tuning the tank circuit to resonance should result in a reading of grid current to the final amplifier. The oscillator tank circuit can then be adjusted to a point that will give maximum amplifier grid current consistent with reliable keying. During the adjustment the key should not be held closed longer than is absolutely necessary, since the amplifier screen current will run to a considerably higher-than-normal value without plate voltage and load.

### Neutralizing

The amplifier should be neutralized at this point. At the start the aluminum strips (shown in Fig. 6-71) should be exactly alike — about 1/2 inch by 3 inches, with the centers of the feed-through insulators on which they are mounted 1 1/8 inches from the tube bases. The

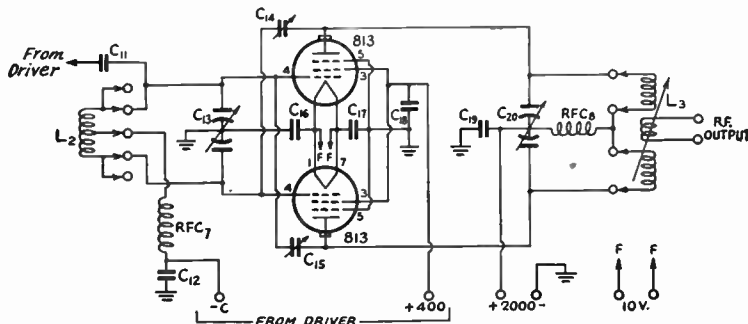


Fig. 6-70 — Circuit of the final amplifier in the enclosed 1-kw. transmitter.

- C<sub>11</sub> — 470- $\mu$ fd. mica, 1000 volts.
- C<sub>12</sub>, C<sub>16</sub>, C<sub>17</sub> — 0.0047- $\mu$ fd. mica.
- C<sub>13</sub> — 100- $\mu$ fd. per-section variable (Cardwell ER-100-AD).
- C<sub>14</sub>, C<sub>15</sub> — Neutralizing condensers; see text.
- C<sub>18</sub> — 0.001- $\mu$ fd. mica, 1000 volts.
- C<sub>19</sub> — 0.001- $\mu$ fd. mica, 5000 volts working.
- C<sub>20</sub> — 100- $\mu$ fd. per-section variable (National TMA-1001A).
- L<sub>2</sub> — Same as L<sub>2</sub> in Fig. 6-67.
- L<sub>3</sub> — Amplifier plate tank coils, Barker & Williamson HDVL series with following modifications:
  - 3.5 Mc.: 9 turns shorted out at each outer end.
  - 7 Mc.: 2 turns shorted out at each outer end.
  - 14 Mc.: 1 turn shorted out at each outer end.
  - 28 Mc.: No modification.
- RFC<sub>7</sub> — 2.5-mh. r.f. choke.
- RFC<sub>8</sub> — 2.5-mh. r.f. choke, 500 ma. (Hammarlund CH-500).

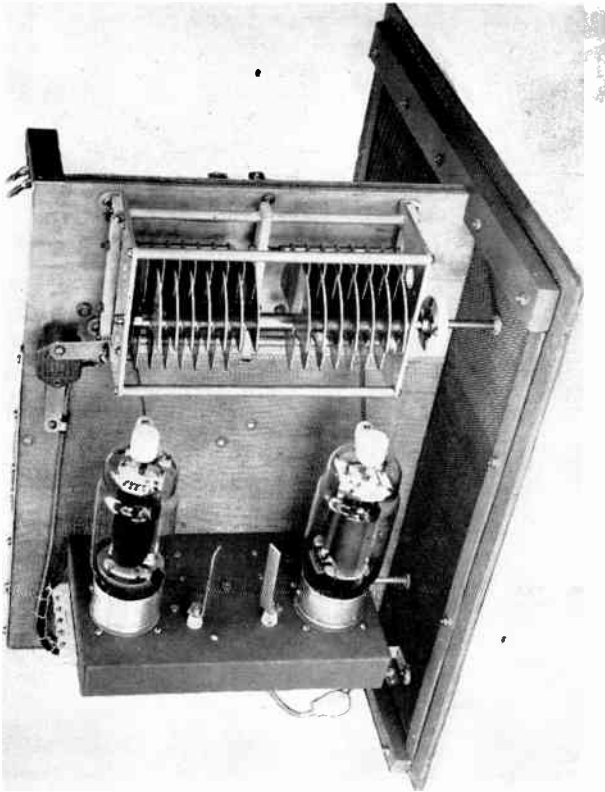


Fig. 6-71 — The amplifier side of the partition in the enclosed 1-kw. transmitter. This view shows the plate tank condenser and the plate by-pass. The aluminum strips between the two 813s, mounted on stand-off insulators, are the neutralizing condensers.


adjustment consists of clipping off the ends of the strips about  $\frac{1}{16}$  inch at a time until the amplifier is neutralized. Any of the usual indicators of neutralization may be employed, the most convenient method being to alter the neutralizing capacitance as described until the grid current remains steady as the plate tank condenser is swung through resonance.

After neutralizing, reduced high voltage may be applied to the amplifier and its plate tank circuit tuned to resonance as indicated by a dip in plate current. The antenna should not be coupled to the output stage until it has been tuned as described, the link being swung as far out as possible during preliminary adjustment.

When the point of resonance has been found, full voltage may be applied and the antenna circuit coupled and tuned in the manner proper for the type of antenna system and antenna tuning arrangement used. Regardless of the system employed, it should be remembered that the last adjustment in coupling and adjusting the antenna to the transmitter is that of tuning the amplifier tank circuit for minimum plate current. This should always be done after every adjustment of antenna coupling or tuning. Otherwise, the amplifier may be operating very inefficiently off resonance and exceeding the dissipation rating of the tubes. Tuning the first 807 as an oscillator is similar

Fig. 6-72 — Schematic of the filament-power and power-terminal wiring of the enclosed 1-kw. transmitter. Two interlocks are included in the control circuit, to turn off the plate power whenever the enclosure is opened.

- I<sub>1</sub> — 6.3-volt pilot-lamp assembly.
- MA — 0-100 milliammeter, shunted to read 1000 ma.
- S<sub>1</sub> — 10-amp. toggle switch.
- S<sub>2</sub> — 15-amp. toggle switch.
- S<sub>3</sub>, S<sub>4</sub> — Interlock switches. See text.
- T<sub>1</sub> — 10-volt 10-ampere filament transformer.
- T<sub>2</sub> — 6.3-volt 3-ampere filament transformer.

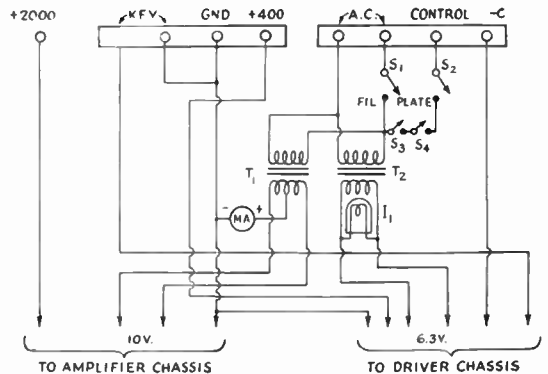

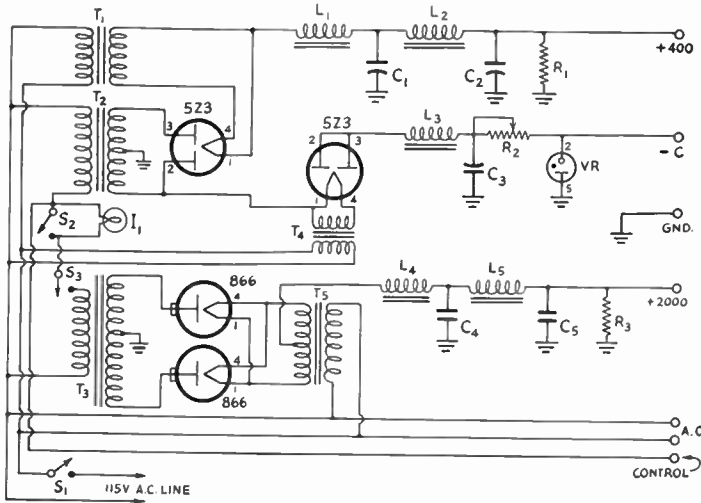


Fig. 6-73 — Circuit diagram of a power supply for the enclosed 1-kw. transmitter.

C<sub>1</sub>, C<sub>2</sub>, C<sub>3</sub> — 8- $\mu$ fd. 600-volt-wkg. electrolytic.  
 C<sub>4</sub> — 2- $\mu$ fd. 2500-volt oil.  
 C<sub>5</sub> — 4- $\mu$ fd. 2500-volt oil.  
 R<sub>1</sub> — 20,000 ohms, 25 watts.  
 R<sub>2</sub> — 50,000 ohms, 25 watts.  
 R<sub>3</sub> — 50,000 ohms, 200 watts.  
 L<sub>1</sub> — 5/25-hy. 300-ma. choke.  
 L<sub>2</sub> — 20-hy. 300-ma. choke.  
 L<sub>3</sub> — 30-hy. 50-ma. choke.  
 L<sub>4</sub> — 5/25-hy. 500-ma. choke.  
 L<sub>5</sub> — 20-hy. 500-ma. choke.  
 I<sub>1</sub> — 150-watt 115-volt lamp.  
 S<sub>1</sub>, S<sub>2</sub> — 10-amp. toggle.  
 S<sub>3</sub> — 5-amp. toggle.  
 T<sub>1</sub>, T<sub>4</sub> — 5-v. 3-a. fil. trans.  
 T<sub>2</sub> — 400 v. d.c., 250-300 ma.  
 T<sub>3</sub> — 2000 v. d.c., 500 ma. or more.  
 T<sub>5</sub> — 2.5 volts, 10-amp., 10,000-volt insulation.  
 VR — Voltage-regulator tube.

to the method outlined for the second tube.

The adjustment of the second tube as a multiplier is simply the selection of the proper coil and tuning to resonance, making certain that it is not tuned to an undesired harmonic.

Table 6-IV shows typical current values which may be expected. They were taken at 100 volts and may vary somewhat because of differences in crystal response and length of leads in the oscillator circuits which may affect feed-back.

The Tri-tet oscillator may be expected to self-oscillate with the crystal removed. With the crystal operating normally, however, no trouble of this sort should be experienced.

At the maximum rated input of just under 1 kw., this transmitter should deliver 600 watts or better on all bands.

**TABLE 6-IV**

Combination	1st 807 at Resonance — Ma.		2nd 807 at Resonance — Ma.		Final Grid — Ma.	
	Key Open	Key Closed	Key Open	Key Closed	No Plate Voltage	Full Load
A	—	—	40-60	40-50	40-50	—
B	—	—	75	40	42	—
C	—	—	65-70	43	46	—
D	46	48	80	38	39	—
E	15	20	64	30	30	—
F	16	100	78	30	32	—
G	40	50	86	18	25	—
H	73	55	81	18	28	—

\* With excitation control at maximum.

## A Simple VFO Crystal Substitute

Figs. 6-74, 6-75 and 6-77 show different views of a VFO unit with sufficient power output to drive the average crystal-oscillator tube. As the circuit diagram of Fig. 6-76 shows, it consists of a 6SK7 ECO followed by a pair of 6F6s as isolating amplifiers. The primary frequency range covered by the oscillator is 3500-4000 kc., but this range may be shifted lower to cover 3395-3800 kc. for multiplying to cover the frequencies in the 10- and 11-meter bands by readjustment of the band-setting condenser, C<sub>2</sub>.

### Construction

The oscillator portion is constructed as a separate unit in a standard 3 × 4 × 5-inch steel box. The tuning condenser, C<sub>1</sub>, and the coil form for L<sub>1</sub> are fastened to the rear wall of the box. C<sub>1</sub> is coupled to the National Type AM dial by a short extension shaft and a flexible coupling. The band-setting air condenser,

C<sub>2</sub>, is mounted against the right side of the box near the lower rear corner where it can be adjusted from the outside with a screwdriver to set the beginning of the tuning range. The tube is mounted externally on top of the box where it will be well ventilated and where its heat will have minimum effect upon the tuned circuit. The coupling lead between the plate of the oscillator tube and the grid of the first 6F6 is made with flexible wire passed through National TPB polystyrene bushings, one in the oscillator compartment and one in the base chassis, the rigid wire which comes with the bushing having first been removed by warming with a soldering iron. The power and keying leads are brought out in a similar manner through holes lined with rubber grommets. The oscillator box is shock-mounted by means of long machine screws at each corner of the bottom plate. The screws pass through grommet-lined holes in the top of the chassis.



*Fig. 6-74*—The complete VFO unit. The oscillator is housed in a separate compartment which is shock-mounted on rubber grommets. The oscillator tube is on top of the compartment. To the rear are the two 6F6 amplifier tubes, the VR tube, the rectifier and the power transformer. In front are the stand-by switch, the power switch, pilot lamp and the two keying jacks. The output terminals are to the right.


The base chassis is  $5 \times 10 \times 3$  inches. The two 6F6s are mounted on either side of the chassis immediately behind the oscillator compartment. Underneath, the filter choke is fastened against the side of the chassis in the left rear near the two filter condensers,  $C_{14}$  and  $C_{15}$ . The two plate r.f. chokes,  $RFC_2$  and  $RFC_3$ , are mounted near their associated tube sockets. On the front edge are the control switches,  $S_1$  for power and  $S_2$  which is the stand-by switch, cutting off plate voltage to all stages. Terminals in parallel with  $S_2$  are mounted in the rear

edge of the chassis to connect to a send-receive relay if this is found desirable. The output terminals are set in the right-hand side.

#### Adjustment

The resistance of  $R_5$  should be adjusted experimentally so that the VR tube is ignited with the key either closed or open. If the glow disappears when the key is closed, the resistance of  $R_5$  should be reduced. With the dial set for maximum capacitance of  $C_1$ ,  $C_2$  should be adjusted with a screwdriver to set the

*Fig. 6-75*—Bottom view of the oscillator compartment. The tuning condenser and the coil are fastened to the rear wall of the box, while the air trimmer is mounted on the lower end in the photograph. The small cone insulator supports the coupling lead to the first amplifier stage.

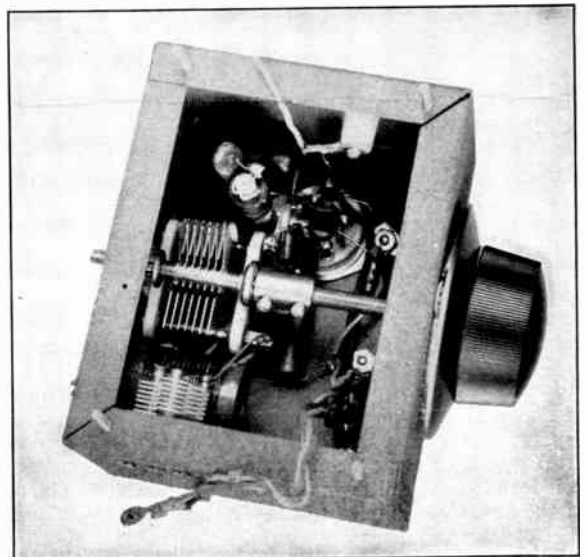



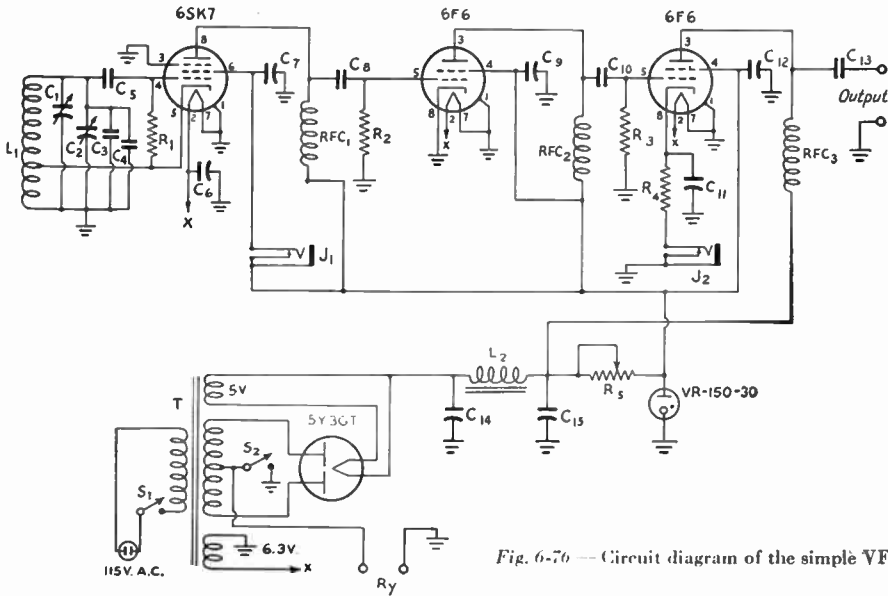


Fig. 6-76 — Circuit diagram of the simple VFO.

- C<sub>1</sub> — 100- $\mu$ fd. variable (Hammarlund MC-100S).
- C<sub>2</sub> — 75- $\mu$ fd. variable (Hammarlund APC75).
- C<sub>3</sub> — 220- $\mu$ fd. zero-temp.-coef. mica.
- C<sub>4</sub> — 68- $\mu$ fd. zero-temp.-coef. mica.
- C<sub>5</sub>, C<sub>8</sub>, C<sub>10</sub>, C<sub>13</sub> — 100- $\mu$ fd. mica.
- C<sub>6</sub>, C<sub>7</sub>, C<sub>9</sub>, C<sub>11</sub>, C<sub>12</sub> — 0.01- $\mu$ fd. paper.
- C<sub>14</sub>, C<sub>15</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- R<sub>1</sub>, R<sub>2</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.
- R<sub>4</sub> — 220 ohms, 1 watt.
- R<sub>5</sub> — 5000 ohms, 25 watts, adjustable.


- L<sub>1</sub> — 17 turns No. 20 enam.,  $1\frac{1}{8}$  inches long, 1-inch diam., tapped 5 turns from ground end.
- L<sub>2</sub> — 30 hy., 50 ma. (Stancor C-1003).
- J<sub>1</sub>, J<sub>2</sub> — Closed-circuit jack.
- RFC<sub>1</sub>, RFC<sub>3</sub> — 2.5-mh. r.f. choke.
- RFC<sub>2</sub> — Millen 17002 ( $\frac{1}{2}$ -inch diam. by  $2\frac{1}{2}$  inches long) polystyrene form wound full with No. 30 d.s.c. wire.
- S<sub>1</sub>, S<sub>2</sub> — S.p.s.t. toggle switch.
- T — 340 volts each side center, 55 ma.; 5 v., 2 a.; 6.3 v.,  $1\frac{1}{2}$  amp.

frequency at 3500 kc. (3395 for 10- and 11-meter operation). C<sub>1</sub> should then cover the range to 4000 kc. (or 3800 kc.).

Coupling to the crystal oscillator in most transmitters is simply a matter of running a wire from the "hot" output terminal (the terminal connected to the plate of the output tube through C<sub>13</sub>) to the grid of the oscillator tube, and the other output terminal to the chassis of the transmitter. In Tri-tet and grid-plate oscillator circuits, the cathode tanks should be short-circuited. In triode or tetrode

crystal-oscillator circuits using parallel plate feed, it may be necessary to shift to series feed to prevent low-frequency parasitic oscillation because of the r.f. chokes in both the input and output circuits. In Pierce circuits, the oscillator tube may be fed as a grounded-grid amplifier by connecting the output terminals of the VFO in series between the cathode and the biasing resistor and by-pass. As an alternative, in this type of circuit, the oscillator tube may be eliminated and the VFO fed to the grid of the next tube.

Fig. 6-77 — Bottom view of the VFO unit showing the filter choke and the various r.f. chokes and by-pass condensers associated with the isolating amplifiers.

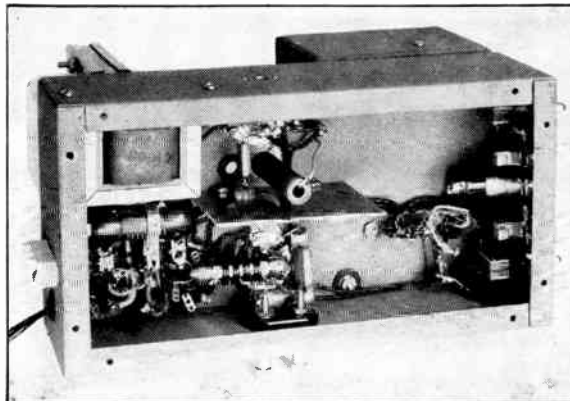

### Keying

Best keying characteristics will be obtained by keying the output stage although a second keying jack,  $J_1$ , is included for use if break-in operation is necessary. Since the key would be at 150 volts above ground, a keying relay or vacuum-tube keyer should be used here to avoid the danger of shock. In keying the oscillator, any key-click-filter lag should be kept at the minimum required for satisfactory click suppression, to avoid chirps. Usually, r.f.

chokes only at the relay terminals will be sufficient. As much lag as is desired can be used when keying the output stage, since keying at this point does not affect the frequency.

The oscillator draws 8 ma. in the plate circuit and 3 ma. in the screen circuit. The plate current of the first amplifier should run about 15 ma. with the oscillator key closed and 32 ma. when excitation is removed. The output-stage currents should be 17 ma. with excitation and 25 ma. without excitation.

## A 100-Watt Output Bandswitching Transmitter or Exciter

The transmitter pictured in Figs. 6-78, 6-80 and 6-81 incorporates bandswitching over all bands from 3.5 to 28 Mc. It consists of a 6V6 Tri-tet oscillator which gives either fundamental or second-harmonic output from a 3.5-Mc. crystal, a 6N7 dual-triode frequency multiplier with its first triode section operating as a doubler from 7 to 14 Mc. and the second section doubling from 14 to 28 Mc., and a final stage with two 807s in parallel. The Tri-tet cathode coil may be cut in or out of the circuit as desired, so that the 6V6 may be used as a straight tetrode crystal oscillator on either 3.5 or 7 Mc. Provision is made for crystal switching, six crystal sockets being included, and a seventh switch position is used for external VFO input. The power output on all bands is in excess of 100 watts when the 807s are operated at ICAS c.w. telegraph ratings.

### Circuit

The circuit diagram of the transmitter is given in Fig. 6-79. The switching circuit is so arranged that the grids of unused 6N7 triode sections are disconnected from the preceding stage and grounded; thus excitation is not ap-

plied to idle doubler tubes. Only one coil is used in the 6V6 stage to cover both 3.5 and 7 Mc.; for 3.5 Mc. an air padding condenser,  $C_2$ , is switched in parallel with the 7-Mc. tank circuit to extend the tuning range to 3.5 Mc.

Capacitance coupling between stages is used throughout. The plates of the first three stages are parallel-fed so that the plate tuning condensers can be mounted directly on the metal chassis. Coupling to the 807 grids is through a tap on each plate coil; this "tapping down" not only provides the proper load for the various driver stages but also helps overcome the effect on the driver tuning ranges of the rather large shunt capacitance resulting from operating the two beam tetrodes in parallel. Series feed is used in the plate circuit of the 807s, the tank condenser being of the type that is insulated from the chassis. Operating bias for the 807s is obtained from a grid-leak resistor, and the screen voltage is obtained through a dropping resistor from the plate supply.

Plate currents of all tubes are read by a 0-100 d.c. milliammeter which can be switched to any plate circuit by means of  $S_4$ . One switch position is provided for checking the final-

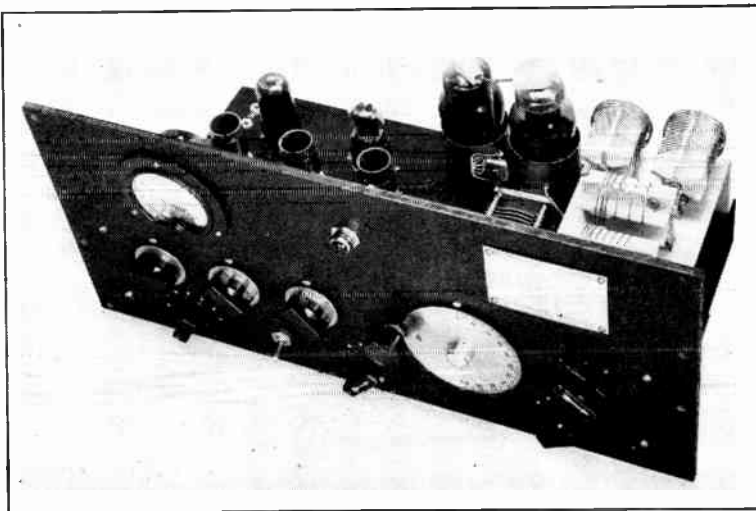


Fig. 6-78 — A 100-watt output transmitter or exciter with bandswitching over four bands. The output stage uses parallel 807s. Crystal switching, with provision for VFO input, and meter switching are incorporated. Tuning control, from left to right, are crystal oscillator-doubler, 14-Mc. doubler, 28-Mc. doubler, and (large dial) final amplifier. The crystal switch is at the lower left corner, driver band-switch in the center, and meter switch at the lower right. The amplifier band-switch is above the meter switch and to the right of the amplifier tuning dial.

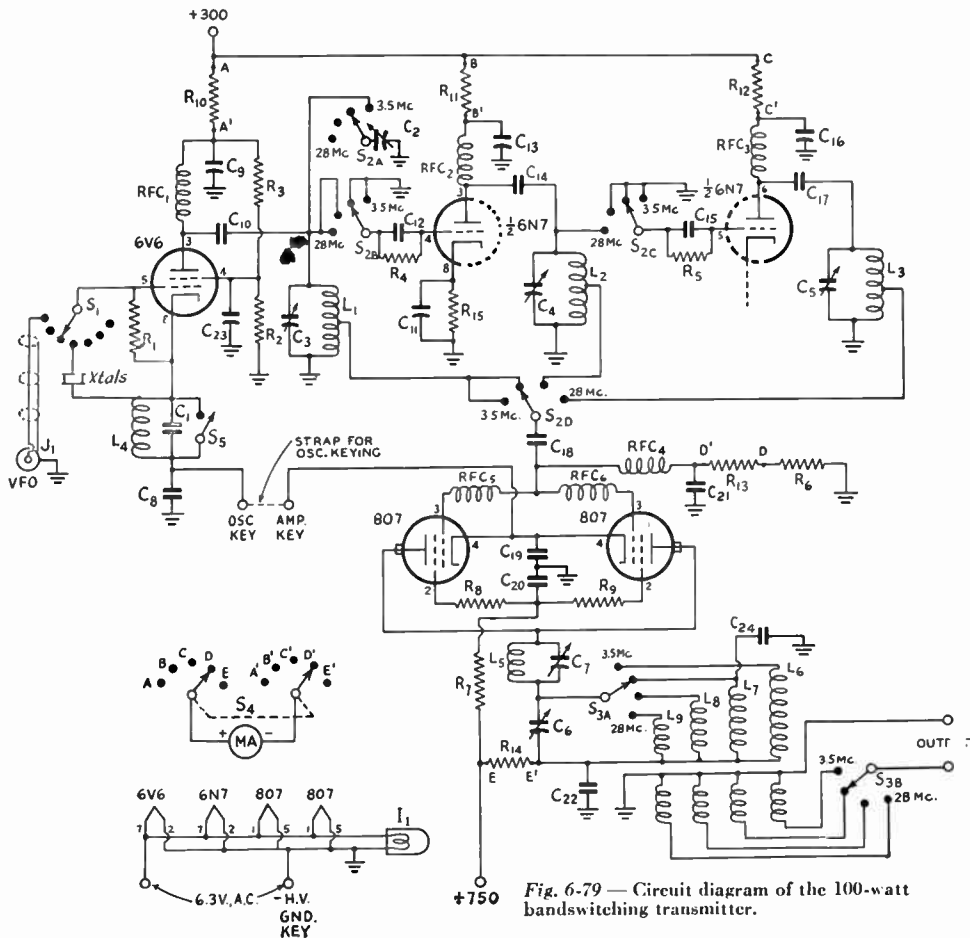


Fig. 6-79 — Circuit diagram of the 100-watt bandswitching transmitter.

- C<sub>1</sub> — 220- $\mu$ fd. mica (mounted inside L<sub>4</sub>).
- C<sub>2</sub> — 140- $\mu$ fd. air padder.
- C<sub>3</sub>, C<sub>4</sub>, C<sub>5</sub> — 100- $\mu$ fd. variable (National ST-100).
- C<sub>6</sub> — 150- $\mu$ fd. variable, 0.05-inch plate spacing (Hammarlund HFB-150-C).
- C<sub>7</sub> — 3-30- $\mu$ fd. ceramic padder.
- C<sub>8</sub>, C<sub>19</sub>, C<sub>21</sub> — 0.0017- $\mu$ fd. mica.
- C<sub>9</sub>, C<sub>11</sub>, C<sub>13</sub>, C<sub>16</sub>, C<sub>23</sub> — 0.01- $\mu$ fd. paper, 600 volts.
- C<sub>10</sub>, C<sub>14</sub>, C<sub>17</sub> — 0.0022- $\mu$ fd. mica, 500 volts.
- C<sub>12</sub>, C<sub>15</sub>, C<sub>18</sub> — 106- $\mu$ fd. mica.
- C<sub>20</sub> — 470- $\mu$ fd. mica, 2500 volts.
- C<sub>22</sub> — 0.0022- $\mu$ fd. mica, 2500 volts.
- C<sub>24</sub> — Sec text.
- R<sub>1</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.
- R<sub>2</sub>, R<sub>3</sub> — 47,000 ohms, 1 watt.
- R<sub>4</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>5</sub> — 22,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>6</sub> — 12,000 ohms, 1 watt.
- R<sub>7</sub> — 25,000 ohms, 10 watts.
- R<sub>8</sub>, R<sub>9</sub> — 68 ohms,  $\frac{1}{2}$  watt.
- R<sub>10</sub>, R<sub>11</sub>, R<sub>12</sub>, R<sub>13</sub>, R<sub>14</sub> — 22 ohms,  $\frac{1}{2}$  watt (R<sub>14</sub> shunted as described below).
- R<sub>15</sub> — 470 ohms, 1 watt.

NOTE: R<sub>14</sub> is shunted by a length of No. 30 wire (about 8 or 10 inches) wound around the resistor, the wire length being adjusted to make the meter read one-fifth normal, increasing the full-scale range to 500 ma.

- L<sub>1</sub> — 21 turns No. 18 on 1-inch form, length 1 inch; tapped 15 turns from ground.
- L<sub>2</sub> — 10 turns No. 18 on 1-inch form, length 1 inch; tapped 7 turns from ground.
- L<sub>3</sub> — 5 turns No. 18 on 1-inch form, length 1 inch; tapped 2 turns from ground.

- L<sub>4</sub> — 13 turns No. 18 on 1-inch form, length 1 inch.
- L<sub>5</sub> — 4 turns No. 18, diam.  $\frac{3}{8}$  inch, length  $\frac{5}{8}$  inch, mounted on C<sub>7</sub>.
- L<sub>6</sub> — 22 turns No. 20, diam.  $1\frac{1}{2}$  inches, length  $1\frac{3}{8}$  inches. Link: 3 turns.
- L<sub>7</sub> — 13 turns No. 16, diam.  $1\frac{1}{2}$  inches, length  $1\frac{3}{8}$  inches. Link: 3 turns.
- L<sub>8</sub> — 7 turns No. 16, diam.  $1\frac{1}{2}$  inches, length  $1\frac{3}{8}$  inches. Link: 3 turns.
- L<sub>9</sub> — 4 turns No. 16, diam.  $1\frac{1}{2}$  inches, length  $1\frac{3}{8}$  inches. Link: 3 turns.

NOTE: L<sub>1</sub>, L<sub>2</sub>, L<sub>3</sub> wound on Millen 15001 forms, L<sub>4</sub> on Millen 15000 form; L<sub>6</sub>, L<sub>7</sub>, L<sub>8</sub>, L<sub>9</sub> are Coto C1680E, C1640E, C1620E and C1610E, respectively, with turns removed to conform to specifications above.

- I<sub>1</sub> — 6.3-volt pilot-lamp assembly.
- J<sub>1</sub> — Coaxial-cable socket (Amphenol).
- MA — 0-100 d.c. milliammeter.
- RFC<sub>1</sub>, RFC<sub>2</sub> — 2.5-mh. r.f. choke (National R-100).
- RFC<sub>3</sub> — 2.5-mh. r.f. choke (National R-100U).
- RFC<sub>4</sub> — 2.5-mh. r.f. choke (Millen 34102).
- RFC<sub>5</sub>, RFC<sub>6</sub> — 18 turns No. 20 d.c.e.,  $\frac{1}{4}$ -inch diam., close-wound on 1-watt resistor (any high value of resistance may be used).

- S<sub>1</sub> — Ceramic wafer switch, 7 positions.
- S<sub>2</sub> — Four-gang 6-position ceramic wafer switch (4 positions used).
- S<sub>3</sub> — Two-gang 4-position ceramic wafer switch (Yaxley 162C).
- S<sub>4</sub> — Two-gang 6-position ceramic wafer switch (3 positions used).
- S<sub>5</sub> — S.p.s.t. toggle switch.

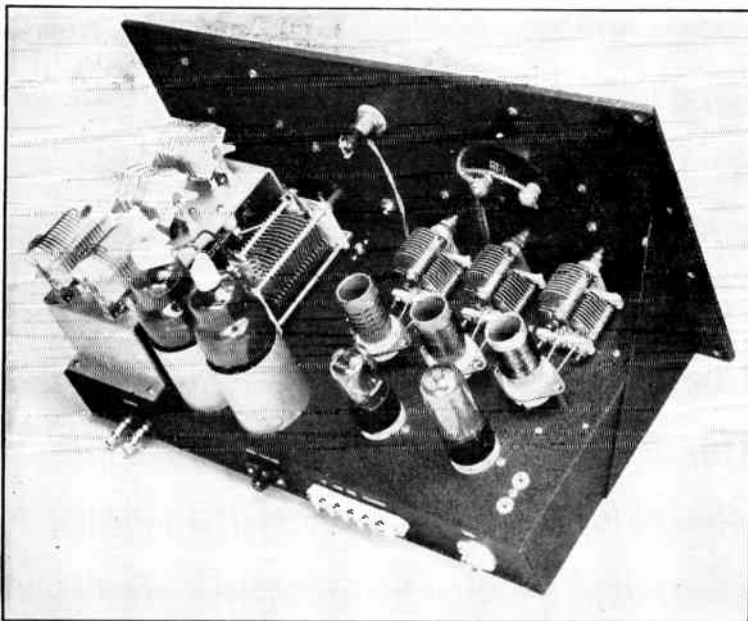


Fig. 6-80 — Top view of the 100-watt band-switching transmitter. The oscillator and doubler coils are of the plug-in type for convenience in mounting and adjustment, but do not need to be changed to cover the frequency range from 3.5 to 30 Mc. The cable terminal on the chassis wall at the right is for VFO input; r.f. output terminals are at the extreme left.

stage grid current. The d.c. cathode returns of both the 6V6 and the 807s are brought out to terminals so that a choice of keying is offered. If the 6V6 cathode lead is grounded, the amplifier alone may be keyed in the cathode circuit; if the two cathode returns are connected together, the oscillator and amplifier may be keyed simultaneously for break-in operation. (The oscillator alone cannot be keyed with the 807 cathodes grounded, because without fixed bias on the latter tubes the plate input would be excessive under key-up conditions.)


To prevent parasitic v.h.f. oscillations, small chokes ( $RFC_5$  and  $RFC_6$ ) are connected in the grid leads to the 807s, and a 68-ohm resistor is connected in each screen lead. These suppressors are mounted as closely as possible to the tube sockets. A parasitic trap,  $L_5C_7$ , is connected in the common plate lead to the 807s. Because of the high power sensitivity of the paralleled 807s and the fact that the

grid-plate capacitance is doubled by the parallel connection, the tubes may oscillate in t.g.t.p. fashion at the operating frequency if the amplifier is run with no load on the plate tank. However, this tendency toward oscillation disappears with a small load (less than one-fourth rated plate current) and the amplifier is perfectly stable under normal loading conditions.

#### Construction

As shown in Fig. 6-80, the amplifier plate coils are mounted on an aluminum bracket supported by the main chassis. The bracket dimensions are  $6\frac{1}{2}$  inches long by 4 inches wide on top, with mounting legs  $2\frac{1}{2}$  inches high. Half-inch lips bent outward from the bottoms of the legs provide means for mounting to the chassis. The amplifier bandswitch,  $S_3$ , is mounted underneath the coil bracket, with the two switch wafers spaced out so they are ap-

Fig. 6-81 — Bottom view of the 100-watt band-switching transmitter. The chassis dimensions are  $8 \times 17 \times 2$  inches and the panel (of crackle-finished Masonite) is  $8\frac{3}{4} \times 19$  inches. Parts layout is described in the text. The 750-volt lead is brought through a Millen safety terminal, and all other power and keying connections go to a ceramic terminal strip at the rear. The connection between the crystal switch and the VFO input socket is through a short length of RG/58U cable.

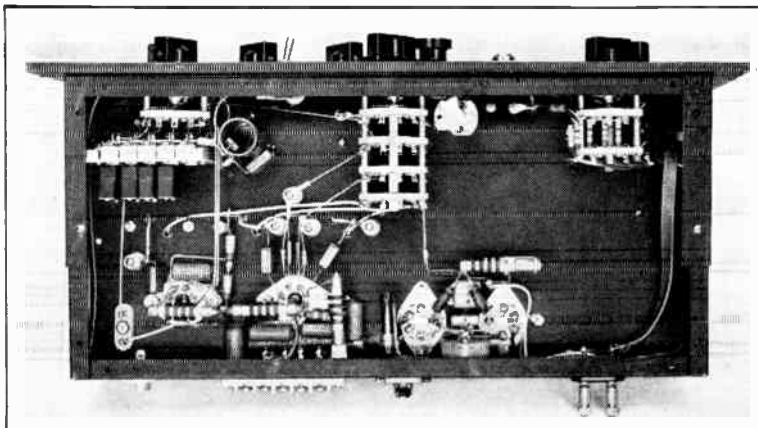

proximately two inches apart. This brings the plate switch section directly under the 28-Mc. tank coil so that the shortest leads can be obtained at the highest frequency. The output link connection runs from the other switch section (at the front) through a length of 300-ohm feeder to terminals on the rear wall of the chassis. Because of the low ratio of plate voltage to plate current, a rather low  $L/C$  ratio must be used in the plate tank circuit to secure a reasonable  $Q$ . The standard coils used are therefore modified to the dimensions given in Fig. 6-79. Other types of manufactured coils (100-watt rating) may be used if desired, provided turns are taken off to bring the 3.5-Mc. band near maximum capacitance on the 150-

28-Mc. doubler, and the rotor of the last section to the grids of the 807s. In this view the right-hand section of the 6N7 is the 14-Mc. doubler. Grid and plate blocking condensers are supported between the tube-socket terminals and small ceramic pillars which serve as tie-points for r.f. wiring. The coil taps to the 807 switch drop through holes in the chassis directly below the proper prongs on the coil sockets. The crystal switch, crystal-holder assembly, oscillator-cathode tuned circuit, and shorting switch,  $S_5$ , are in the upper left-hand corner. The crystal sockets (for the new small crystals) are mounted in a row on a  $1\frac{1}{2} \times 3$ -inch piece of aluminum secured to the chassis by mounting pillars of square alumi-

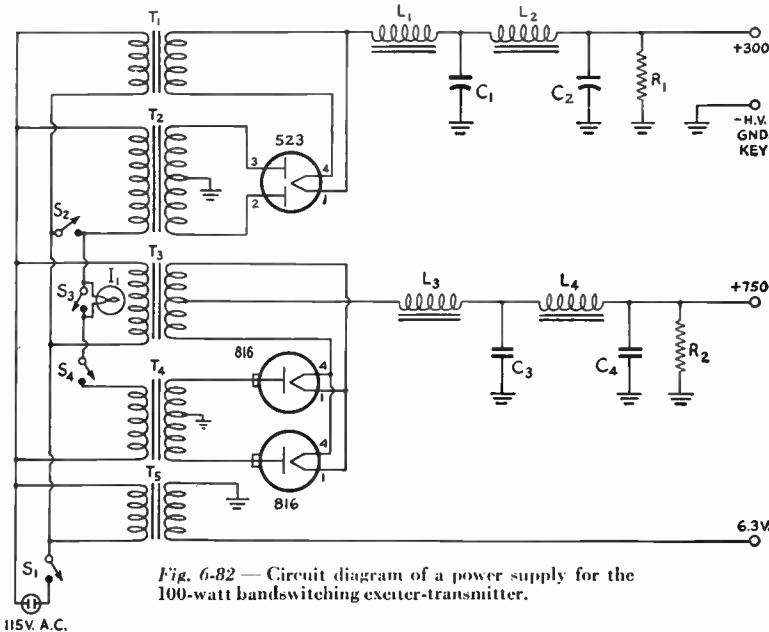


Fig. 6-82 — Circuit diagram of a power supply for the 100-watt bandswitching exciter-transmitter.

- $C_1, C_2$  — 16- $\mu$ fd. 450-volt electrolytic.
- $C_3, C_4$  — 4- $\mu$ fd. 1000-volt oil-filled.
- $R_1$  — 15,000 ohms, 25 watts.
- $R_2$  — 25,000 ohms, 50 watts.
- $L_1, L_2$  — 20-hy. filter choke.
- $L_3$  — 5/25-hy. 250-ma. swinging choke.
- $L_4$  — 20-hy. 250-ma. smoothing choke.
- $I_1$  — 100-watt 115-volt lamp.
- $S_1, S_2$  — 10-amp. toggle switch.
- $S_3, S_4$  — 5-amp. toggle switch.
- $T_1$  — 5-volt 3-amp. filament transformer.
- $T_2$  — Plate transformer, 300 v. d.c., 100 ma. or more.

- $T_3$  — 2.5-volt 1-amp. filament transformer.
- $T_4$  — Plate transformer, 750 v. d.c., 250 ma.
- $T_5$  — 6.3-volt 4-amp. filament transformer.

$S_1$  turns on all filaments in the power supply and transmitter and sets up circuit for  $S_2$ .  $S_2$  turns on low-voltage supply and sets up circuit for  $S_4$  which turns on high-voltage supply. When  $S_3$  is open, high voltage is reduced by  $I_1$  in series with the primary of  $T_4$ . In operating the transmitter, all switches except  $S_2$  are closed.  $S_2$ , then, is the stand-by switch controlling both plate supplies simultaneously.

$\mu$ fd. tank condenser, the 7-Mc. band at 65 to 70 per cent of maximum, and the 14-Mc. band to approximately 30 per cent of maximum. The 28-Mc. band may tune at nearly minimum capacitance, since the minimum circuit capacitance is fairly large.

In the bottom view, Fig. 6-81, the meter switch with its shunting resistors is at the right. The driver bandswitch,  $S_2$ , is in the center; the section nearest the panel is for  $C_2$ , the rotor of the next section goes to the grid of the 14-Mc. doubler, the rotor of the third section to the

num rod. The spare crystal socket on top of the chassis is for old-type crystal holders with  $\frac{3}{4}$ -inch pin spacing. In general, chokes and by-pass condensers are grouped as closely as possible about the tube sockets with which they are associated, to keep r.f. leads short. In the 807 circuit, the screen by-pass condenser,  $C_{20}$ , is mounted vertically from a small metal angle between the two tube sockets, and all grounds for the cathode, screen and grid circuits are brought to a common point between the two sockets.

The condenser,  $C_{24}$ , across only the 7-Mc. 807 tank coil, is actually a  $1 \times 1$ -inch piece of copper with a short tab at one end. The tab is soldered to the plate lead from the coil just under the coil bracket and then bent so that the  $1 \times 1$  portion is parallel to the bracket and separated from it by about  $\frac{1}{8}$  inch. The coil by itself resonated with the stray capacitance at 28 Mc. and absorbed considerable energy when the transmitter was operating on that band; the small capacitance detunes it and prevents such absorption. It may not be needed with other types of coils or different construction.

### Tuning

Preliminary tuning should be done with the plate voltage for the 807s disconnected. Set  $S_2$  and  $S_3$  for 28-Mc. output, set  $S_4$  to read oscillator plate current, and close the key, if oscillator keying is being used. With a 3.5-Mc. crystal, make sure  $S_5$  is open; with a 7-Mc. crystal  $S_5$  should be closed. Rotate  $C_3$  for a small kick in the plate current that indicates resonance at the crystal harmonic, in the case of the Tri-tet, and for the marked dip in plate current that indicates oscillation with the tetrode oscillator. The current should be in the vicinity of 16 to 18 ma. Switch the meter to the 14-Mc. doubler and adjust  $C_4$  to obtain

minimum plate current. This should be about 15 ma. Check the 28-Mc. doubler plate current similarly; it should be between 25 and 30 ma. at resonance. The final-amplifier grid current should be 7 to 8 ma.

Next, connect a 70-ohm dummy antenna or 100-watt lamp to the output terminals, set  $C_6$  near minimum capacitance, and apply plate voltage to the 807s. Adjust  $C_6$  for minimum plate current, which should be about 200 ma. with this load. Readjust the driver circuits for maximum grid current to the 807s.

Tuning procedure for other bands is much the same, except that the amplifier cannot be loaded to full input on the lower frequencies by either the dummy antenna or lamp, with the links furnished with the coils specified. In such cases an antenna should be used to load the transmitter after it has been determined that the various stages are working properly. On 3.5 Mc.,  $C_2$  should be adjusted so that a crystal on 3500 kc. can be made to oscillate with  $C_3$  set near maximum capacitance. Generally,  $C_2$  will be set at approximately full capacity.

The transmitter requires a power supply delivering 60 to 70 ma. at 300 volts for the oscillator and doublers, and one delivering 200 ma. at 750 volts for the 807s. The supply of Fig. 6-82 is suitable.

## A 450-Watt Bandswitching Amplifier

Figs. 6-83, 6-85 and 6-86 show the details of a bandswitching push-pull amplifier for the 3.5-, 7-, 14- and 28-Mc. bands. It is suitable for use with any of the popular 1000- or 1500-volt 100- to 150-ma. triodes. The tubes shown in the photographs are 812s.

As shown in the circuit diagram of Fig. 6-84, all of  $L_1$  in the grid tank circuit and all of  $L_4$  in the plate tank circuit are used for 3.5 Mc. Low-frequency padders,  $C_1$  in the grid circuit and  $C_{10}$  in the plate, are switched across the

coils simultaneously. For 7 Mc., the padding condensers are cut out and  $L_1$  and  $L_4$  are tapped so that only a portion of each coil is in use. At 14 Mc., the coils  $L_2$  and  $L_3$  are used with the padders, while at 28 Mc. the same coils are used without the padders. Links for the two coils in each tank circuit are connected in series.

The components are assembled on a standard 19-inch panel, 10 $\frac{1}{2}$  inches high. The two tubes, the neutralizing condensers and  $L_2$  are

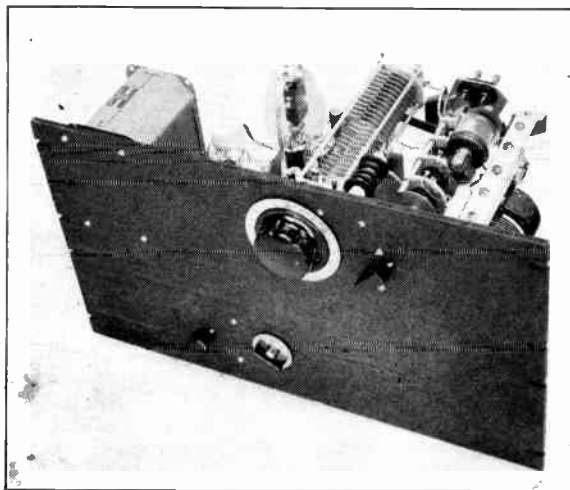


Fig. 6-83 — Top view of the band-switching amplifier. The plate-tank switching assembly is to the right.

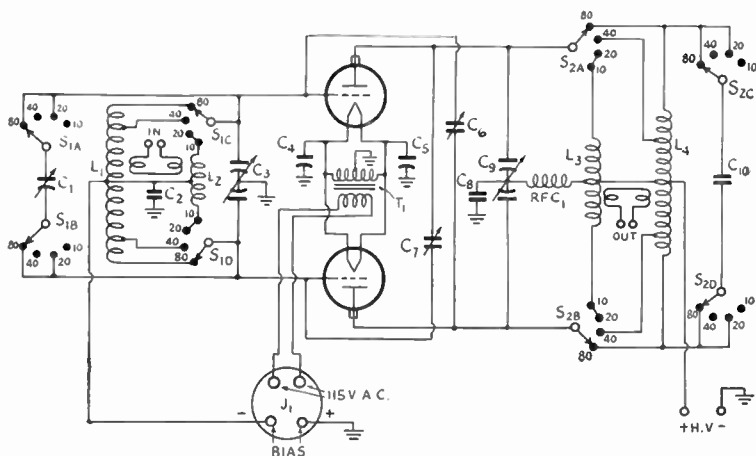


Fig. 6-81 — Circuit diagram of the band-switching push-pull amplifier.

- C<sub>1</sub> — 30- $\mu$ fd. variable, 0.07-inch spacing (Cardwell ZT-30-AS).
- C<sub>2</sub> — 0.001- $\mu$ fd. mica.
- C<sub>3</sub> — 35- $\mu$ fd.-per-section variable (Millen 24935).
- C<sub>4</sub>, C<sub>5</sub> — 0.01- $\mu$ fd. paper.
- C<sub>6</sub>, C<sub>7</sub> — Neutralizing condenser (National NC-800).
- C<sub>8</sub> — 0.001- $\mu$ fd. 5000-volt mica.
- C<sub>9</sub> — 65- $\mu$ fd.-per-section variable (Hammarlund HFBD-65-F).
- C<sub>10</sub> — 50- $\mu$ fd. vacuum capacitor (Type GE GL-1138).

- L<sub>1</sub> — B & W 80BC1, tapped at 12th turn from each end.
- L<sub>2</sub> — 10 turns No. 14 enam., 1 $\frac{1}{4}$ -inch diam., 1 inch long.
- L<sub>3</sub> — B & W 10TCL.
- L<sub>4</sub> — B & W 80TCL reduced to 21 turns, tapped at 3rd turn from each end.
- J<sub>1</sub> — 4-prong socket connector.
- RFC<sub>1</sub> — 1-mh. r.f. choke (National R-154U)
- S<sub>1</sub>, S<sub>2</sub> — 4-gang 4-position ceramic rotary switch (Mal-lory 164-C).
- T<sub>1</sub> — 6.3 volts, 8 amp. (UTC S61).

mounted on top of a 5 × 10 × 3-inch chassis fastened to the panel with its center 7 inches from the left-hand edge and its bottom edge  $\frac{3}{4}$  inch above the lower edge of the panel. The tubes are spaced  $5\frac{1}{4}$  inches, center to center, and their sockets are submounted and centered  $1\frac{3}{4}$  inches from the right-hand edge of the chassis as viewed from the rear. L<sub>2</sub> is wound on a polystyrene form mounted on a National AR coil-plug strip. Its socket is centered between the tubes and  $\frac{5}{8}$  inch from the

edge of the chassis. A 5 $\frac{3}{4}$  × 2-inch cut-out is made in the outside edge of the chassis to clear the grid bandswitch, S<sub>1</sub>. A 1 $\frac{3}{4}$ -inch piece of the cut-out is left and bent inward at right angles to provide a mounting for the switch. The coil for L<sub>1</sub> is removed from its plug strip and transferred to a Millen plug strip which has the required additional contacts for the 7-Mc. taps. The cut-out is notched at the top to provide clearance for the terminals of the coil socket.

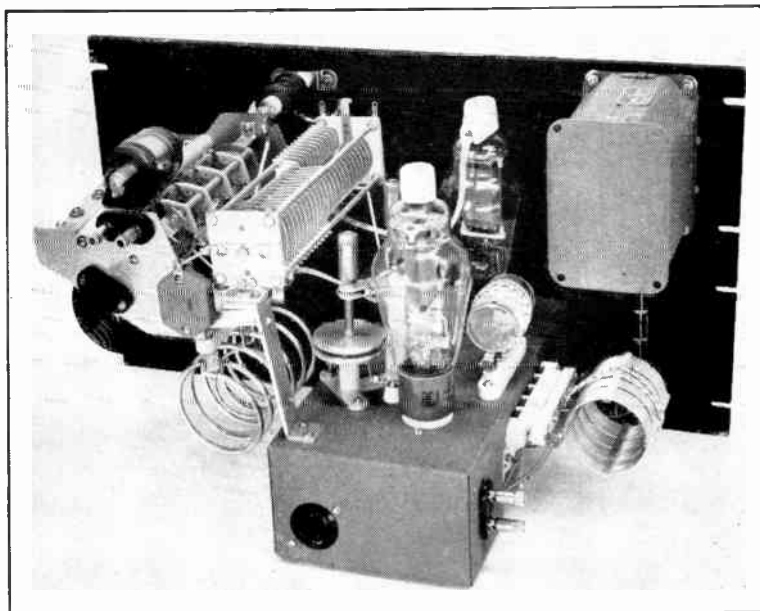


Fig. 6-85 — Rear view of the band-switching amplifier.

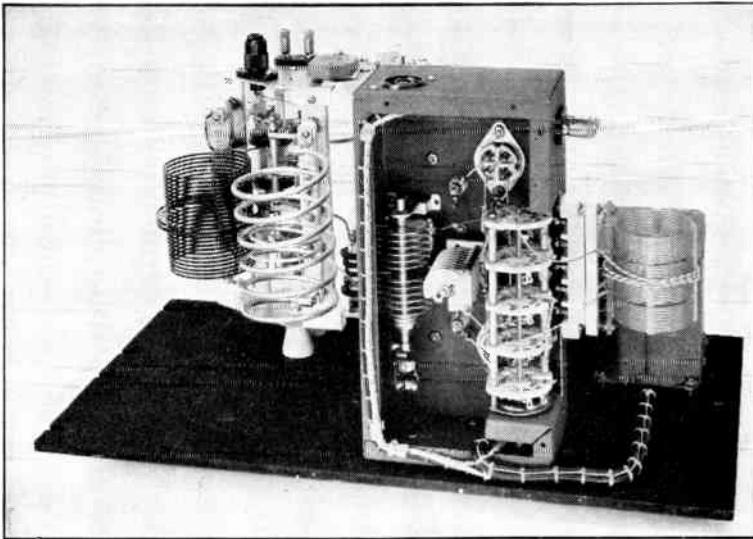


Fig. 6-86 — Bottom view of the band-switching amplifier showing the grid-circuit assembly to the right and the plate-circuit group to the left.

Underneath the chassis,  $C_1$  is mounted vertically on spacers at the center, while the grid tuning condenser,  $C_3$ , is mounted as close to the inside edge as possible. Leads between the lower terminals of the neutralizing condensers and the grid terminals of the tube sockets are fed down through the top of the chassis via small feed-through insulators. Link input terminals are mounted on the outside edge of the chassis, near the rear, while 115-

volt a.c. and biasing connections are made through a cable socket set in the rear edge. The filament transformer is mounted on the upper right-hand corner of the panel, as viewed from the rear of the unit.

The plate tuning condenser,  $C_9$ , is mounted on aluminum-strip brackets fastened to the chassis to bring its shaft  $8\frac{3}{4}$  inches from the right-hand edge of the panel (as viewed from the front) and  $2\frac{1}{2}$  inches from the top. Alumi-

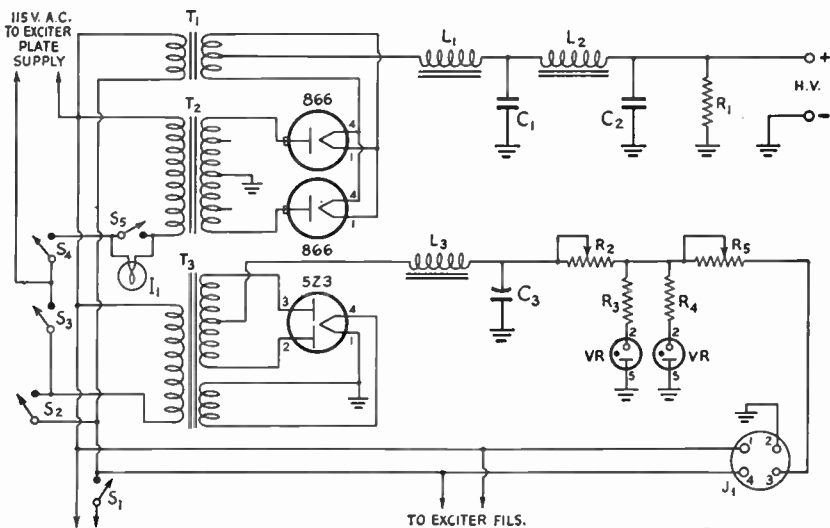


Fig. 6-87 — Circuit diagram of a power supply and control system for the 450-watt bandswitching amplifier.

- $C_1, C_2$  — 4- $\mu$ fd. 2000-volt oil-filled.
- $C_3$  — 8- $\mu$ fd. 450-volt electrolytic.
- $R_1$  — 25,000 ohms, 100 watts.
- $R_2$  — 20,000 ohms, 25 watts, with slider.
- $R_3, R_4$  — 100 ohms, 1 watt.
- $R_5$  — 2500 ohms, 10 watts, with slider.
- $L_1$  — 5/25-hy. 400-ma. swinging choke.
- $L_2$  — 20-hy. 400-ma. smoothing choke.
- $L_3$  — 30-hy. 50-ma. filter choke.
- $I_1$  — 150-watt 115-volt lamp.

- $J_1$  — 4-prong socket connector.
- $S_1, S_2, S_3, S_4$  — 10-amp. switch.
- $S_5$  — 5-amp. switch.
- $T_1$  — 2.5-volt 10-ampere filament transformer, 10,000-volt insulation.
- $T_2$  — Plate transformer, 1500/1250 v. d.c., 400 ma.
- $T_3$  — Power transformer, 650 volts c.t., 50 ma.; 5 volts, 3 amp.
- VR — Voltage-regulator tubes — VR75 (see text).



num sheet is cut to form end plates for a sub-assembly which includes the switch,  $S_2$ , the two coil sockets, and a mounting for the padder,  $C_{10}$ . As viewed from the rear,  $L_4$  is to the left and  $L_3$  to the right. Pillar-type ceramic insulators form spacers for the mounting angles that support the cartridge-fuse clips in which the vacuum-type padding condenser,  $C_{10}$ , is mounted. The assembly is spaced from the panel on  $1\frac{1}{4}$ -inch cone stand-offs, placed so that the shaft comes  $5\frac{1}{2}$  inches from the right-hand edge of the panel and  $2\frac{3}{4}$  inches below the top edge. The Millen safety terminal for the high-voltage connection, the link output terminals and the insulating condenser,  $C_8$ , are fastened to the rear end plate of the assembly. The plate r.f. choke is fastened to the panel between the plate tank condenser and the switch assembly.

Reference should be made to earlier sections in this chapter for tuning and adjusting procedures.

### Power Supply

Fig. 6-87 shows the circuit of a suitable power supply and control system for this amplifier. The plate-supply transformer,  $T_2$ , is tapped for either 1500 or 1250 volts d.c. output from the filter, making it suitable for operating the amplifier at maximum ratings, 'phone or c.w. The bias supply employs a

small transformer and the output voltage is regulated. A pair of VR tubes are used in parallel to carry the required grid current. The resistor,  $R_2$ , should be adjusted, without excitation to the amplifier, until the VR tubes just ignite. The voltage of the pack should then hold constant over a wide range of grid-current values. VR tubes should be selected with voltage ratings between the value required to cut off plate current and the recommended value of operating bias for the amplifier tubes used. The difference between the VR-tube voltage and the recommended operating value then is made up by grid-leak action through  $R_5$ .  $R_5$  should be adjusted so that the operating bias is the recommended value with rated grid current flowing and the amplifier loaded to rated plate current.

The control system is arranged so that  $S_1$  turns on the 866 filaments in the power supply, amplifier and exciter filaments, and sets up circuit for  $S_2$  which turns on the bias supply.  $S_2$  also sets up circuit for  $S_3$  which turns on the exciter plate supply and sets up circuit for  $S_4$  which controls the high-voltage supply. When  $S_5$  is open, power is reduced for adjustments since  $I_1$  is in series with the primary of  $T_2$ . In operating the transmitter, all switches except  $S_3$  are closed.  $S_3$  then serves as the stand-by switch, controlling all plate power supplies simultaneously.


## A 500-Watt Beam-Tube Amplifier

The photographs of Figs. 6-88, 6-90, 6-91 and 6-92 show the construction of a single-tube screen-grid amplifier using a Type 813 which will handle an input of up to 500 watts. The circuit is shown in Fig. 6-89. The amplifier is designed for link coupling in both input and output circuits. Bandswitching is employed in the grid circuit principally because of the problem of providing plug-in coils with

satisfactory shielding. To assure good stability, the amplifier is neutralized.

The triode-connected 6Y6 is used to protect the tube against overload in case of removal or failure of excitation. This system is used in preference to protective bias because of the difficulty of limiting the input to a safe value without exceeding the recommended operating bias for operating conditions when screen

◆  
Fig. 6-88 — Front-panel view of the stabilized 813 amplifier. In addition to the meter and the plate and grid tuning controls, the panel contains the r.f. input jack, the key jack, a three-position meter switch, and a four-position bandswitch for the grid circuit.  
◆

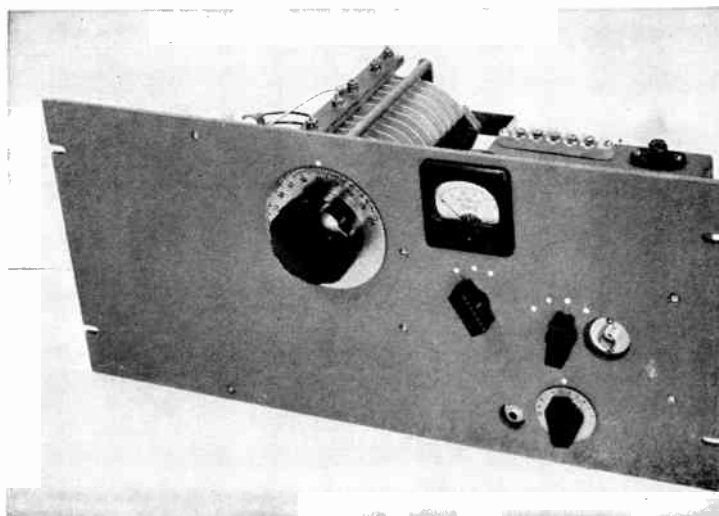

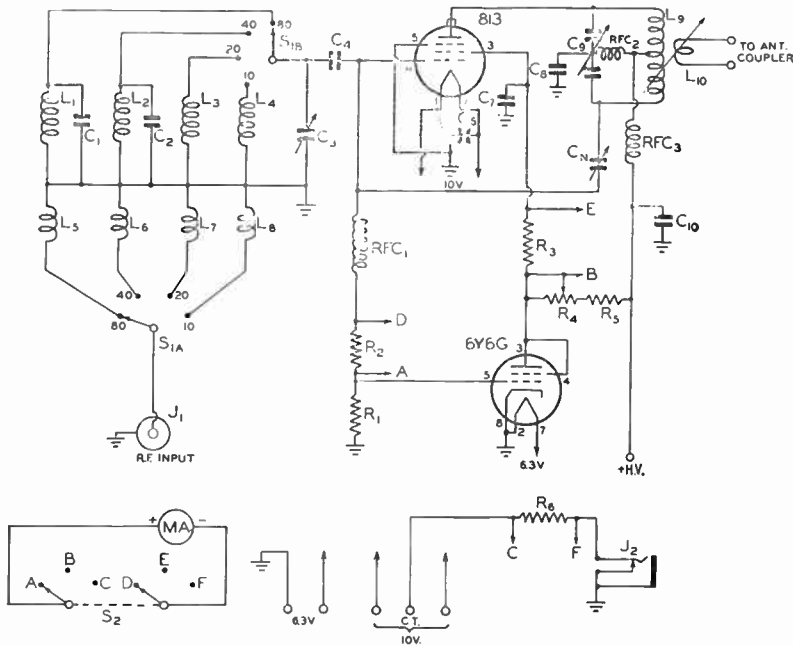


Fig. 6-89 — Schematic diagram of the 813 amplifier.

- C<sub>1</sub> — 100- $\mu$ fd. mica.  
 C<sub>2</sub> — 68- $\mu$ fd. mica.  
 C<sub>3</sub> — 50- $\mu$ fd. receiving-type variable (Millen Type 19050).  
 C<sub>4</sub> — 0.0022- $\mu$ fd. mica.  
 C<sub>5</sub>, C<sub>6</sub> — 0.01- $\mu$ fd. paper.  
 C<sub>7</sub> — 0.001- $\mu$ fd. 2500-volt mica.  
 C<sub>8</sub> — 0.001- $\mu$ fd. 5000-volt mica.  
 C<sub>9</sub> — 50- $\mu$ fd.-per-section dual transmitting type, 0.171-inch spacing (Cardwell XG-50-X1).  
 C<sub>10</sub> — 0.001- $\mu$ fd. 5000-volt mica.  
 C<sub>N</sub> — See text.  
 R<sub>1</sub> — 10,000 ohms, 5 watts. (See text.)  
 R<sub>2</sub>, R<sub>3</sub> — 100 ohms,  $\frac{1}{2}$  watt.  
 R<sub>4</sub> — 35,000 ohms, 50 watts, with slider.  
 R<sub>5</sub> — 15,000 ohms, 50 watts.  
 R<sub>6</sub> — Meter shunt. Wound with No. 30 d.s.c. wire, length as required to multiply meter scale by ten.  
 L<sub>1</sub> — 26 turns No. 22 d.s.c. spaced to occupy  $1\frac{1}{4}$  inches on a 1-inch diam. form.  
 L<sub>2</sub> — 15 turns No. 18 d.c.c. spaced to occupy  $1\frac{1}{4}$  inches on a 1-inch diam. form.  
 L<sub>3</sub> — 10 turns No. 18 d.c.c. spaced to occupy  $1\frac{1}{4}$  inches on a 1-inch diam. form.  
 L<sub>4</sub> — 5 turns No. 18 d.c.c. spaced to occupy  $1\frac{1}{4}$  inches on a 1-inch diam. form.  
 L<sub>5</sub>, L<sub>6</sub>, L<sub>7</sub>, L<sub>8</sub> — Two-turn links, No. 18 insulated stranded wire, wound over ground ends of L<sub>1</sub> through L<sub>4</sub> inclusive.

- L<sub>9</sub> — NOTE: These coils are B & W TVII series, for use with the B & W TVII swinging-link assembly. The coils are modified as described below.  
 80 meters: B & W 160-TVII with 4 turns removed from each end. (54 turns No. 18 enameled,  $2\frac{1}{2}$  inches diameter, winding length  $4\frac{7}{8}$  inches.)  
 40 meters: B & W 80-TVII with 8 turns removed from each end. (22 turns No. 14 enameled,  $2\frac{1}{2}$  inches diameter, winding length  $3\frac{3}{8}$  inches.)  
 20 meters: B & W 20-TVII with 1 turn removed from each end. (12 turns No. 12 enameled,  $2\frac{1}{2}$  inches diameter, winding length  $4\frac{1}{2}$  inches.)  
 10 meters: B & W 10-TVII with 1 turn removed from each end. (6 turns  $\frac{1}{8}$ -inch copper tubing,  $2\frac{1}{2}$  inches diameter, winding length  $5\frac{1}{4}$  inches.) (Winding lengths specified above include  $\frac{5}{8}$ -inch separation between halves of the coil for entrance of swinging link coil.)  
 L<sub>10</sub> — 3-turn link assembly, part of B & W TVII swinging-link assembly.  
 J<sub>1</sub> — Coaxial connector.  
 J<sub>2</sub> — Closed-circuit jack.  
 MA — 0-50 d.c. milliammeter.  
 RFC<sub>1</sub> — 2.5 mh. (Millen Type 34104).  
 RFC<sub>2</sub> — 2.5 mh. (National R-100).  
 RFC<sub>3</sub> — 2.5 mh. (National R-300).  
 S<sub>1</sub> — Single-gang 2-pole 5-position ceramic wafer switch. (Centralab S-2505.)  
 S<sub>2</sub> — Two-gang 2-pole 5-position ceramic wafer switch. (Centralab S-2511).

voltage is obtained from a series resistance — recommended practice if the amplifier is to be plate-screen modulated. So long as normal grid current flows to the 813, the 6Y6 is biased to cut-off, so that it has no effect. However, when excitation is removed from the amplifier, the bias on the 6Y6 disappears and it draws current through the screen resistor, causing the screen voltage to drop to a value that reduces both plate and screen currents to safe values.


The single milliammeter may be switched by

S<sub>2</sub> to read grid current, screen current or cathode current. A multiplier shunt increases the range of the 50-ma. meter to 500 ma. when it is switched to read cathode current. A jack, J<sub>2</sub>, is provided so that the amplifier may be keyed in the center-tap.
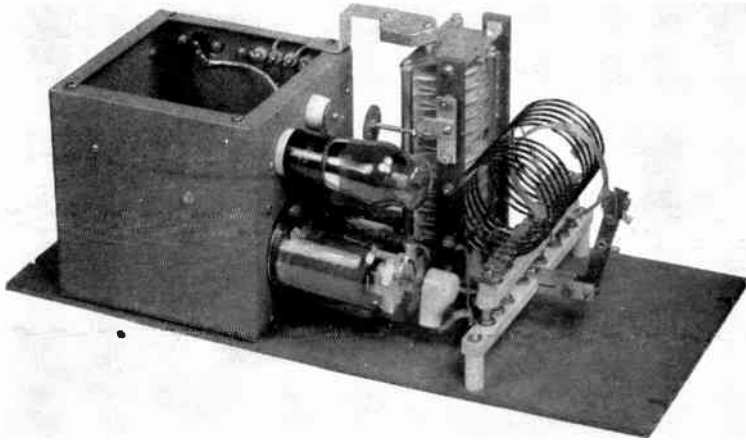
### Construction

The entire amplifier unit is suspended from a standard  $19 \times 8\frac{3}{4}$ -inch panel. The grid-circuit components are housed in the  $6 \times 6 \times 6$ -inch steel box to the left in Fig. 6-90.

◆  
 Fig. 6-90 — Rear view of the 813 amplifier. The steel utility box used to shield the input circuits is bolted to the rear of the panel. The home-built neutralizing condenser is below the mica bypass condenser which forms a part of the rear support for the plate condenser. The plate condenser and the swinging-link assembly are mounted directly on the panel with ceramic stand-off insulators.




◆  
 while the plate tank condenser and coil are mounted on the panel to the right. The 813 protrudes horizontally from the right-hand side of the box, its socket being submounted on brackets inside the box so that that portion of the tube which extends above its internal shielding plate is exposed. The 6Y6 is mounted alongside the 813.

The r.f. input jack, the grid coils, grid tuning condenser, bandswitch, key jack, and the meter switch are built as one assembly constructed on one of the cover plates of the box as shown in Fig. 6-92. All ground connections in this assembly are made to soldering lugs slipped under the screws which mount the coil forms. The coils themselves are held away from the chassis by National GS-10 stand-off insulators. Care should be taken in locating the mounting holes for the coils and the bandswitch to be

sure that they will clear the lip of the utility box when the time comes for final assembly. If required, additional clearance may be obtained by filing semicircular notches in the lips of the box. The coils should be connected to the bandswitch before the coupling links are wound. This keeps the assembly clear of obstructions and makes wiring easier. Padding condensers  $C_1$  and  $C_2$ , used with the 40- and 80-meter coils respectively, are connected from the grid end of the coil to the same soldering lugs used for grounding the cold ends of the coils. When the links are wound on later, their ground connections are also made to these same lugs.

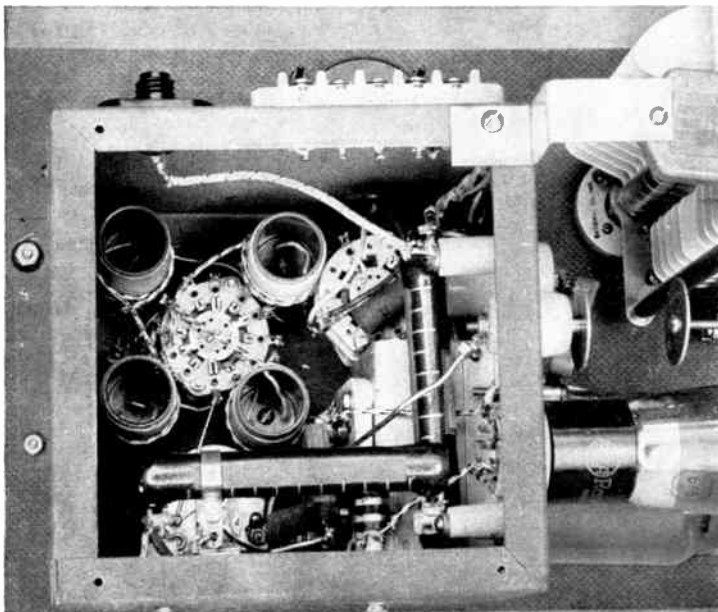The meter switch provides mounting terminals for meter shunts  $R_2$ ,  $R_3$  and  $R_6$ , and for the grid resistor,  $R_1$ . The leads to the meter itself are passed through the top of the box through



◆  
 Fig. 6-91 — The interior of the shield box. The socket for the 813 is mounted on a bracket visible to the right of the four grid coils. The two large resistors are the screen-dropping units. This view also shows the construction of the neutralizing condenser, one plate of which mounts on a ceramic bushing on the wall of the box, the other being supported by a bracket from the plate tuning condenser.

a grommet-lined hole after assembly. The other leads to the metered circuits are cabled and are run along the top of the box.

All of the by-pass condensers associated with the screen and filament circuits are mounted on the socket and should be grounded at a common point. All of this wiring, together with the filament and screen leads, should be soldered in place before the 813 socket bracket is mounted within the box. The grid blocking condenser,  $C_3$ , may also be soldered in position, leaving one end free to be connected to the stator plates of the grid tuning condenser after assembly. The mounting of the screen dropping resistors is shown in Fig. 6-91. Both are supported by small ceramic stand-off insulators. High voltage for the plate-and-screen supply enters the top of the box through a Millen safety connector, and is passed through the side of the box to the plate coil through a ceramic bushing. A bushing requiring a  $\frac{3}{4}$ -inch hole was used to provide maximum insulation. The fixed plate of the neutralizing condenser is mounted on a similar bushing just above the socket for the 6Y6G. The exact location of this hole should be determined after temporarily assembling the panel, the plate tuning condenser, and the box, because the fixed plate must be aligned with the variable plate, which is supported by the plate tuning condenser.

The plate tuning condenser is mounted on the front panel by three ceramic stand-off insulators. This is necessary because the condenser rotor is at full plate potential above ground. The rotor shaft is cut off about  $\frac{1}{4}$  inch from the rotor bushing, to permit the insertion of a high-voltage type shaft coupling. An insulated shaft made of  $\frac{1}{4}$ -inch bakelite rod couples the rotor of the condenser to the dial. Both r.f. chokes used in the plate tank circuit are mounted on the jack-bar into which the coils plug. The high-voltage lead runs from the center-tap of the coil to the ceramic bush-

ing on the side of the box, at which point the plate by-pass condenser,  $C_{10}$ , is mounted. The ground end of this condenser is mounted on a spacer which is held in place by one of the screws which passes through the side of the box to hold the socket mounting bracket in place. The rear of the plate tuning condenser is held to the rear of the box by a small aluminum bracket, bent to provide adequate clearance between itself and the rotor. Blocking condenser  $C_8$  is made a part of this bracket.

The variable plate of the neutralizing condenser is supported by a small bracket bolted to the stator connectors of the tuning condenser. The copper disks used are each 1 inch in diameter. A hole is drilled in the center of each disk to pass a mounting screw. The "stator" disk is bolted to the ceramic feed-through bushing, and is held away from it by a  $\frac{1}{4}$ -inch spacer. The other end of the screw which goes through the bushing is fitted with a soldering lug to which the grid connection is soldered. The "rotor" disk is fastened to a 2-inch machine screw with a nut. The threaded end of the screw is then passed through the mounting bracket and is held in position firmly by two nuts, one on each surface of the bracket. This plate should be put in position first, after which the location of the hole for the bushing can be determined to provide proper alignment of the two plates.

After the three separate assemblies have been built and wired, the few remaining interconnections should be made. These include the connection of the metering leads to the proper points of the circuit, the connection of the grid coupling condenser to the stator plates of the grid tuning condenser, and the connection of the leads between the common terminals of the meter switch and the meter itself. The entire box assembly is then fastened to the front panel using angle brackets and 6-32 machine screws.


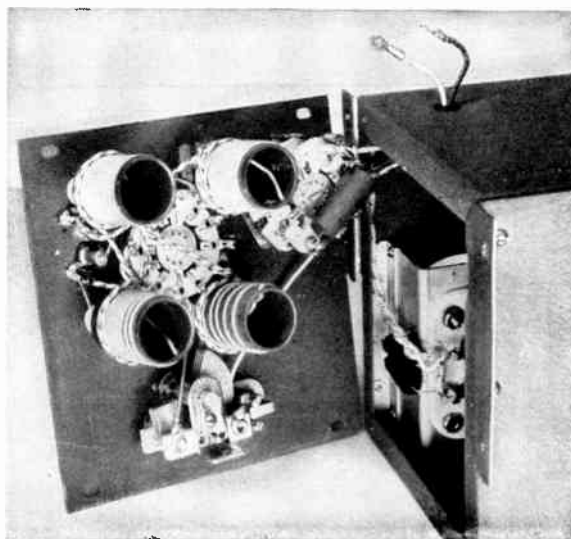


Fig. 6-92 — The grid coils are grouped around their handswitch on one of the covers of the utility box. The coaxial input jack is mounted between the two coils at the left. The meter switch is in the upper right-hand corner, and the grid tuning condenser is at the bottom. The two leads coming through the top of the box run from the meter switch to the meter.

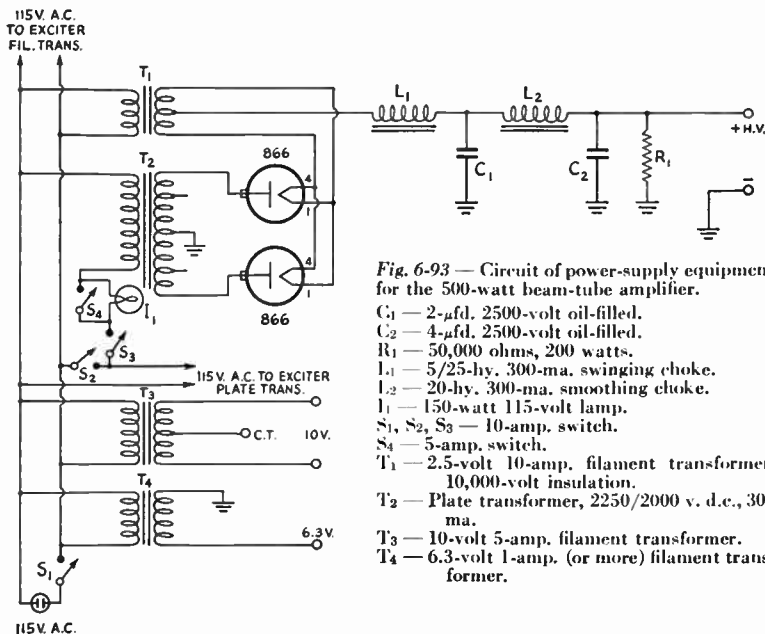

**Fig. 6-93** — Circuit of power-supply equipment for the 500-watt beam-tube amplifier.  
 C<sub>1</sub> — 2- $\mu$ fd. 2500-volt oil-filled.  
 C<sub>2</sub> — 4- $\mu$ fd. 2500-volt oil-filled.  
 R<sub>1</sub> — 50,000 ohms, 200 watts.  
 L<sub>1</sub> — 5/25-hy. 300-ma. swinging choke.  
 L<sub>2</sub> — 20-hy. 300-ma. smoothing choke.  
 I<sub>1</sub> — 150-watt 115-volt lamp.  
 S<sub>1</sub>, S<sub>2</sub>, S<sub>3</sub> — 10-amp. switch.  
 S<sub>4</sub> — 5-amp. switch.  
 T<sub>1</sub> — 2.5-volt 10-amp. filament transformer, 10,000-volt insulation.  
 T<sub>2</sub> — Plate transformer, 2250/2000 v. d.c., 300 ma.  
 T<sub>3</sub> — 10-volt 5-amp. filament transformer.  
 T<sub>4</sub> — 6.3-volt 1-amp. (or more) filament transformer.

### Power Supply

The circuit diagram of a plate and filament supply and a suggested control system is shown in Fig. 6-93. The plate transformer is tapped so that voltage may be reduced to keep within the tube ratings when modulating the amplifier.

The control system is arranged to take care of the exciter as well as the amplifier. S<sub>1</sub> turns on all filaments in the exciter, amplifier and power supply, and sets up circuit for S<sub>2</sub> which turns on the exciter plate supply. Closing S<sub>2</sub> also sets up circuit for S<sub>3</sub> which turns on the high-voltage supply. When S<sub>4</sub> is open, I<sub>1</sub> is in series with the primary of T<sub>2</sub> to reduce voltage while adjustments are being made. When the transmitter is in operation, all switches except S<sub>2</sub> are closed. S<sub>2</sub> then serves as the stand-by switch, controlling both exciter and amplifier plate-voltage supplies simultaneously.

### Adjustment

The amplifier is neutralized most accurately by applying excitation with the positive high-voltage lead disconnected and checking for r.f. in the plate tank circuit with an absorption-type indicator (see Chapter Sixteen). Starting with the neutralizing condenser wide open, the capacitance should be increased slowly. At some point within the range of the neutralizing condenser, the indicator should show minimum indication (or no indication) of r.f. as the plate tank condenser is swung through its range. If further increase in the capacitance of the neutralizing condenser causes an increase in the reading of the indicator, the setting of the neutralizing condenser should be brought back to the minimum point.

Tube data sheets furnish proper operating values for a choice of several plate voltages and these should be followed closely. For operating at maximum c.w. ratings, the plate voltage should be 2250. A screen resistor of 46,000 ohms and a grid leak of 10,000 ohms should be used. When the amplifier is loaded to a plate current of 220 ma. and the excitation adjusted to give a grid current of 15 ma., the d.c. grid voltage should be -155 volts and the screen voltage 400 at a

screen current of 40 ma. For maximum plate/screen-modulated ratings, the plate voltage should be 2000, the screen resistor 41,000 ohms and the grid leak 11,000 ohms. When the amplifier is loaded to the maximum rated plate current of 200 ma. and the grid current adjusted to 16 ma., the bias should be 175 volts and the screen voltage 350 at 40 ma. The driver should be capable of an output of 15 to 20 watts to allow for coupling losses. For c.w. operation with a 1500-volt supply and a plate current of 180 ma., the recommended screen voltage is 300. The screen current should be 30 ma. and the required screen voltage-dropping resistor 40,000 ohms. The grid current under load should be 12 ma. through a 7500-ohm grid leak. For 'phone operation at 1600 volts, the following values are recommended: plate current 150 ma., screen voltage 400 at 20 ma., grid bias 130 volts at 6 ma., screen voltage-dropping resistor 60,000 ohms, grid leak 22,000 ohms.

Perhaps the most critical adjustment is that of obtaining proper excitation. Overdriving results in excessive screen current. Excessive screen current causes abnormal voltage drop in the screen resistor, resulting in reduced output from the tube. Since both screen and control-grid current will vary with the loading of the amplifier, it is important that the excitation adjustment be made with the amplifier loaded to rated plate current. Underloading can quite readily result in excessive screen dissipation unless the screen resistor and excitation are readjusted to suit the conditions.

If the amplifier is properly neutralized, it should be possible to remove both load and excitation without encountering any indication of self-oscillation. Under this condition, the cathode current should fall to a low value.

## A Push-Pull Amplifier for 200 to 500 Watts Input

Figs. 6-95, 6-96 and 6-97 show various views of a compact push-pull amplifier using tubes of the 1500-volt 150-ma. class, although the design is also suitable for use with tubes of the 1000-volt 100-ma. class. With the lower plate voltages a plate tank condenser with a spacing between plates of 0.05 inch, and smaller tank coils, may be used.

The circuit, shown in Fig. 6-94, is quite conventional, with link coupling at both input and output. The tuned circuits,  $L_3C_6$  and  $L_4C_5$ , are traps important for the prevention of v.h.f. parasitic oscillations. The 100-ma. meter may be shifted between the grid and cathode circuits for reading either grid current or cathode current. When shifted to read cathode current,

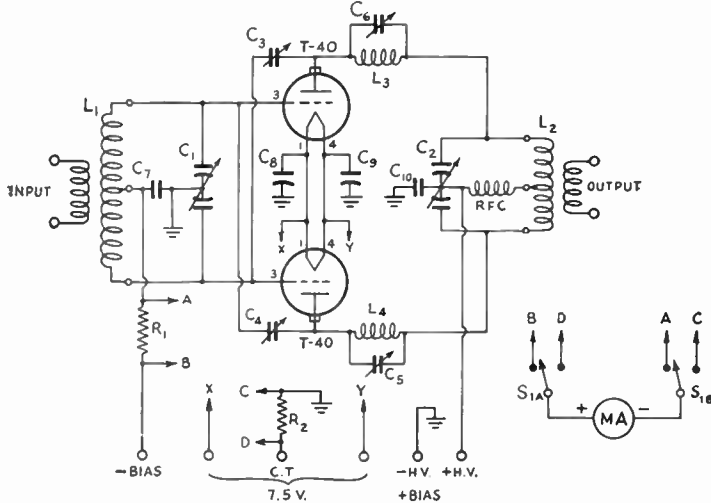


Fig. 6-94 — Circuit diagram of the 450-watt push-pull amplifier.

- $C_1$  — 100  $\mu$ fd. per section, 0.03-inch spacing (Hammarlund HFA0-100-B).  
 $C_2$  — 100  $\mu$ fd. per section, 0.07-inch spacing (Hammarlund HFBD-100-F).  
 $C_3, C_4$  — Neutralizing condenser (National NC-800).  
 $C_5, C_6$  — 3-30- $\mu$ fd. mica trimmer (National M-30).  
 $C_7, C_8, C_9$  — 0.01- $\mu$ fd. paper.  
 $C_{10}$  — 0.001- $\mu$ fd. mica, 7500-volt rating (Aerovox 1653).  
 $R_1$  — 22 ohms, 1 watt.  
 $R_2$  — See text.  
 $L_1$  — B & W JCL series, dimensions as follows:  
 — 3.5 Mc. — 44 turns No. 20,  $2\frac{1}{8}$  inches long.  
 — 7 Mc. — 26 turns No. 16,  $2\frac{1}{8}$  inches long.  
 — 14 Mc. — 14 turns No. 16,  $1\frac{7}{8}$  inches long (remove 2 turns from B & W coil).  
 — 28 Mc. — 6 turns No. 16,  $1\frac{7}{8}$  inches long (remove 2 turns from B & W coil).  
 (All  $1\frac{1}{2}$ -inch diam. 3-turn links.)

- $L_2$  — B & W TCCL series, dimensions as follows:  
 — 3.5 Mc. — 26 turns No. 12,  $3\frac{1}{2}$ -inch diam.,  $4\frac{1}{2}$  inches long.  
 — 7 Mc. — 22 turns No. 12,  $2\frac{1}{2}$ -inch diam.,  $4\frac{1}{2}$  inches long.  
 — 14 Mc. — 10 turn- No. 12,  $2\frac{1}{2}$ -inch diam.,  $4\frac{1}{4}$  inches long. Remove one turn from each end of coil.  
 — 28 Mc. — 4 turns  $\frac{1}{4}$ -inch copper tubing,  $2\frac{1}{2}$ -inch diam.,  $4\frac{1}{2}$  inches long. Remove one turn from each end.  
 (All coils fitted with 2-turn links.)  
 $L_3, L_4$  — 4 turns No. 14,  $\frac{1}{2}$ -inch diam.,  $\frac{3}{4}$  inch long.  
 MA — 100-ma. milliammeter.  
 RFC — 1-mh. r.f. choke (National R-154U).  
 $S_1$  — 2-section 2-position rotary switch.

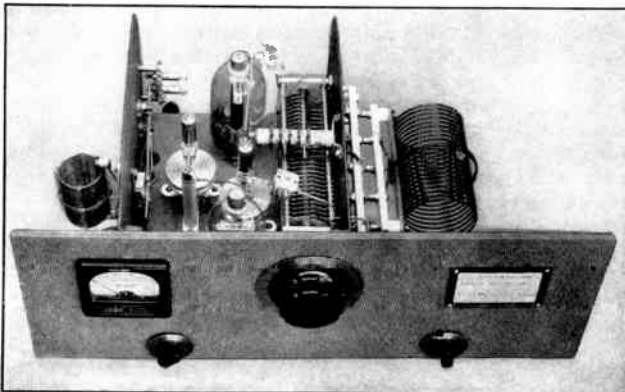


Fig. 6-95 — A general view of the compact 450-watt push-pull amplifier, showing the front-panel and top-of-chassis arrangement. Mounted on a standard relay rack, the height is only 7 inches and the depth 9 inches. Grid and plate tank circuits are isolated from each other by the double shielding partitions. On the panel are the 0-100-ma. milliammeter, which is switched to read current in all circuits, the plate-tank tuning dial, and a chart giving coil and tuning data. The small knob at the left below is the grid-circuit tuning control, while the one to the right is for the meter switch.

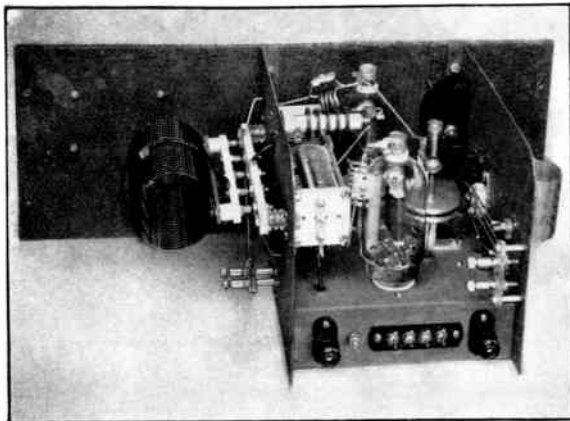


Fig. 6-96 — Rear view of the 450-watt push-pull amplifier. The plate tank condenser is mounted on the left-hand partition. The plate tank-coil jack-bar is mounted centrally, opposite the condenser. The socket for the grid tank coil is mounted to the right just above the chassis line.

the meter is shunted by a resistor,  $R_2$  which multiplies the scale reading by five. This resistor is wound with No. 26 copper wire, the length being determined experimentally to give the desired scale multiplication.

#### Construction

The mechanical arrangement shown in the photographs results in a compact unit requiring a minimum of panel space. All components are assembled around a small metal chassis  $7 \times 2 \times 9$  inches deep. The partitions are standard  $6\frac{1}{2} \times 10$ -inch interstage shields. The tank condenser is mounted on the left-hand partition (Fig. 6-96) at a height which brings its shaft down  $2\frac{3}{8}$  inches from the top of the panel. The plate-tank-coil jack-bar is mounted centrally with the condenser on spacers which give a  $\frac{1}{2}$ -inch clearance between the strip and the partition.  $C_{10}$  is mounted with a small angle on the partition under the center of  $C_2$ . Leads from both ends of the rotor shaft are brought to one side of  $C_{10}$  for symmetry.

The two tube sockets are mounted in a line through the center of the chassis and at opposite ends of the plate tank condenser. They are spaced about one inch below the chassis on long machine screws. The neutralizing condensers are placed between the two tubes, so that the leads from the plate of one tube to the

grid of the other are short. The r.f. choke is mounted just above the tank condenser.

The right-hand partition is cut out at the forward edge to clear the meter. This cut-out can be readily made with a socket punch and a hack saw. The socket for the grid tank coil is mounted  $4\frac{1}{2}$  inches behind the panel, just above the chassis line.


The grid tank condenser,  $C_1$ , is mounted under the chassis without insulation. Large clearance holes, lined with rubber grommets, are drilled for connecting wires which must be run through the chassis or partitions. The parasitic traps are made self-supporting in the plate leads from the tank condenser to the tube caps. The panel is placed so that the plate tank-condenser shaft comes at the center. The meter switch is mounted to balance the knob controlling  $C_1$ . Power-supply connections are made at the rear of the chassis.

#### Power Supply and Excitation

To operate the T40s shown in the photographs at maximum ratings, the driver should be capable of an output of 25 to 40 watts.

The circuit diagram of a suitable plate and bias supply with control switches is shown in Fig. 6-98. The bias supply should be adjusted as described in connection with the power supply for the 450-watt bandswitching amplifier

Fig. 6-97 — Bottom view of the 450-watt push-pull amplifier. The grid tank condenser is mounted between the two tube sockets which are set below the chassis on brackets. Connections between the condenser terminals and the coil socket above pass through grommet-lined holes in the chassis. The partitions provide shielding between input and output tank coils.

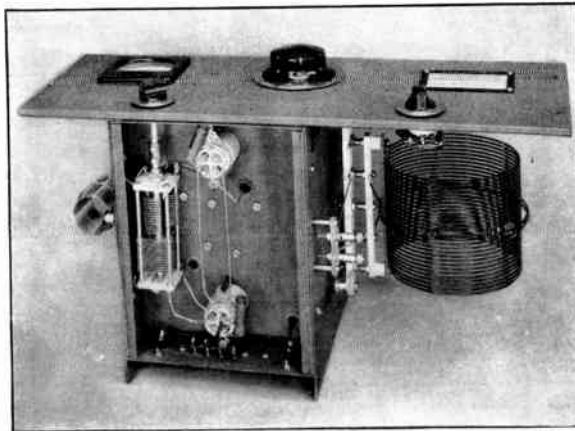

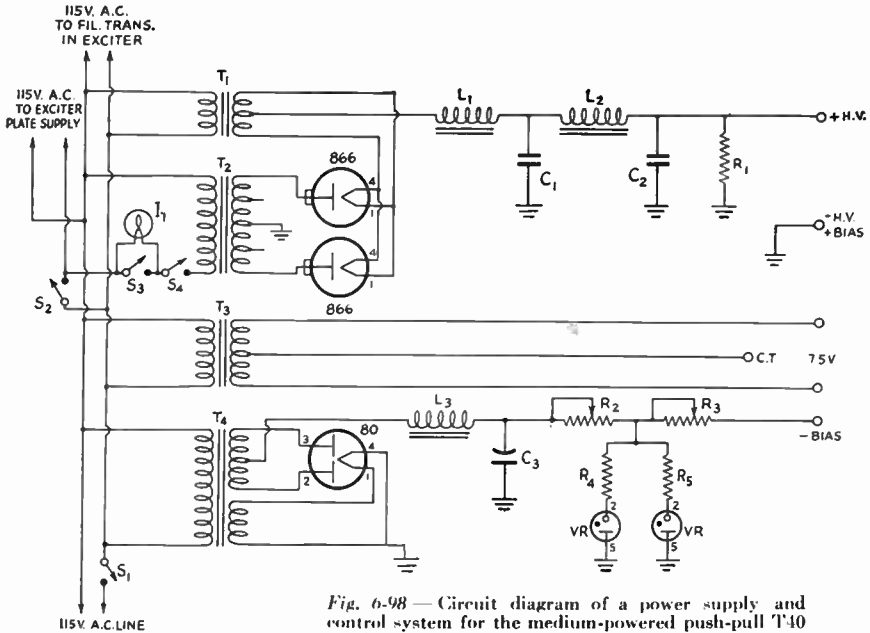


Fig. 6-98 — Circuit diagram of a power supply and control system for the medium-powered push-pull T40 amplifier.

- C<sub>1</sub>, C<sub>2</sub> — 4 μfd. 2000-volt oil-filled.
- C<sub>3</sub> — 8 μfd. 150-volt electrolytic.
- R<sub>1</sub> — 25,000 ohms, 100 watts.
- R<sub>2</sub> — 25,000 ohms, 25 watts, with slider.
- R<sub>3</sub> — 3000 ohms, 25 watts, with slider.
- R<sub>4</sub>, R<sub>5</sub> — 100 ohms, 1 watt.
- L<sub>1</sub> — 5/25-hy. 400-ma. swinging choke.
- L<sub>2</sub> — 20-hy. 100-ma. smoothing choke.
- L<sub>3</sub> — 30-hy. 50-ma. filter choke.
- I<sub>1</sub> — 150-watt 115-volt lamp.

- S<sub>1</sub>, S<sub>2</sub> — 10-amp. switch.
- S<sub>3</sub>, S<sub>4</sub> — 5-amp. switch.
- T<sub>1</sub> — 2.5-volt 10-amp. filament transformer, 10,000-volt insulation.
- T<sub>2</sub> — Plate transformer, 1500/1250 v. d.c., 400 ma.
- T<sub>3</sub> — 7.5-volt 5-amp. filament transformer.
- T<sub>4</sub> — Power transformer, 650 v. a.c., e.t., 50 ma. or more, 5 volts, 2 amp.
- VR — See text.

of Fig. 6-87. For T40s, VR-90 regulators may be used. For operating at maximum c.w. ratings, an additional 50 volts of bias should be obtained from the grid leak, R<sub>3</sub>. At the rated grid current of 30 ma. per tube, a resistance of about 850 ohms will be required at R<sub>3</sub>.

**Tuning**

After the amplifier has been neutralized, a test should be made for parasitic oscillation. The bias should be reduced until the amplifier draws a plate current of about 100 ma. without excitation. With C<sub>1</sub> adjusted to various settings, C<sub>2</sub> should be varied through its range and the plate current watched closely for any abrupt change. Any change will indicate oscillation, in which case C<sub>5</sub> and C<sub>6</sub> should be adjusted simultaneously in slight steps until the oscillation disappears. Unless the wiring differs appreciably from the original, complete sup-

pression will be obtained with the two condensers at full capacity.

The amplifier should now be tuned up and the excitation adjusted so that a grid current of 60 ma. is obtained with the amplifier fully loaded. Full loading will be indicated when the cathode-current meter registers 360 ma. Under these conditions the biasing voltage should rise to 150 volts, dropping to 90 volts without excitation when the plate current will fall to zero.

If the amplifier is to be plate-modulated, the plate voltage should be reduced to 1250 and the loading decreased to reduce the plate current to 250 ma. The same bias-supply adjustment will be satisfactory for this type of operation but excitation may be reduced to give a grid current of 40 ma., bringing the total cathode current to 290 ma.

For operating conditions for tubes of other types tube data should be consulted.

**A Compact 450-Watt Push-Pull Amplifier**

The photographs of Figs. 6-99, 6-101 and 6-102 show an amplifier designed along the lines of the type of construction often referred to as "dish type." This style of construction

has many advantages, although its use normally is confined to components of moderate physical dimensions and weight.

The tank coils may be mounted so that very



little metal of the normal rack structure is in the immediate fields of the tank coils — a condition almost impossible to approach in the usual form of construction with metal panels and side brackets. Plug-in coils are made much more accessible for changing and the direction of “pull” in removing coils is outward away from the rack rather than upward into the next rack unit above. Terminals may be mounted so that the wiring between rack units may be made inconspicuous and so that the chances of personal injury from accidental contact with exposed terminals at the rear are greatly reduced. Lastly, this form of construction usually reduces the required height of the unit which is a particular advantage in table racks where vertical space is at a premium.

The circuit of the amplifier shown in the diagram of Fig. 6-100 is standard in every way except in the method of metering. By means of the two-gang six-position switch it is possible to measure the individual grid and cathode currents of each tube as well as total grid or total cathode currents. To accomplish this, two small filament transformers are used, one for each tube, instead of a single large transformer. The meter is switched across shunting resistances in each circuit to simplify switch-

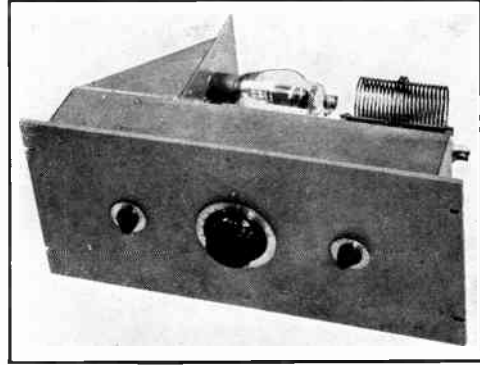


Fig. 6-99 — The three controls of the 450-watt “dish-type” amplifier are arranged symmetrically. The meter switch is at the right, the control for the plate tank condenser at the center and the grid-circuit control at the left. The panel which is  $8\frac{3}{4} \times 19$  inches is fitted with panel bearings for the condenser-shaft extensions. It is fastened to the chassis by flat-head screws after the bottom edges of the chassis have been drilled and tapped.

ing. In the cathode circuits, the shunting resistors should be carefully adjusted to provide a scale multiplication of ten, giving a full-scale reading of 1000 ma.

In doing the r.f. wiring, care should be taken


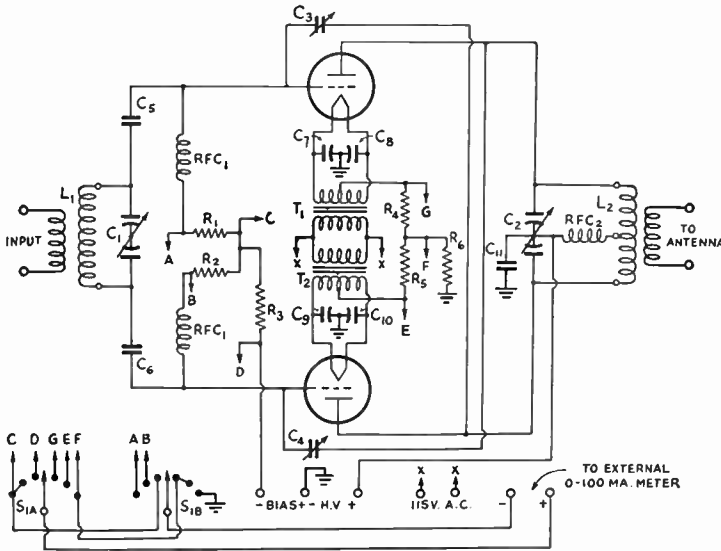


Fig. 6-100 — Circuit diagram of the “dish-type” push-pull 450-watt amplifier.

- C<sub>1</sub> — 100  $\mu$ fd. per section (Hammarlund MCD100M).
  - C<sub>2</sub> — 100  $\mu$ fd. per section (Cardwell MT100GD), 0.07-inch spacing.
  - C<sub>3</sub>, C<sub>4</sub> — Neutralizing condenser, 10 to 15  $\mu$ fd. (Hammarlund N10).
  - C<sub>5</sub>, C<sub>6</sub> — 470- $\mu$ fd. 600-volt mica.
  - C<sub>7</sub>, C<sub>8</sub>, C<sub>9</sub>, C<sub>10</sub> — 0.01- $\mu$ fd. 600-volt paper.
  - C<sub>11</sub> — 0.002- $\mu$ fd. 5000-volt mica.
  - R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub> — 25 to 50 ohms, 2 watts.
  - R<sub>4</sub>, R<sub>5</sub>, R<sub>6</sub> — Cathode-current meter shunts (see text).
  - L<sub>1</sub> — National AR series coils with center link (variable-link type recommended).
- Substitute coils may be wound on  $1\frac{1}{2}$ -inch diam. form as follows:

- 3.5 Mc. — 44 turns, 2 inches long.
  - 7 Mc. — 22 turns, 2 inches long.
  - 14 Mc. — 10 turns,  $1\frac{1}{2}$  inches long.
  - 28 Mc. — 6 turns,  $1\frac{1}{2}$  inches long.
- L<sub>2</sub> — B & W T.L. series with center links.  
Substitute coils may be wound as follows on  $2\frac{1}{2}$ -inch diam. forms:
- 3.5 Mc. — 36 turns, 4 inches long.
  - 7 Mc. — 18 turns, 4 inches long.
  - 14 Mc. — 10 turns, 3 inches long.
  - 28 Mc. — 6 turns, 3 inches long.
- RFC<sub>1</sub> — 2.5-mh. r.f. choke.  
RFC<sub>2</sub> — 1-mh. r.f. choke (National 154-U).  
S<sub>1</sub> — 2-gang 6-position rotary switch (Mallory).  
T<sub>1</sub>, T<sub>2</sub> — 6.3 volts, 6 amp.

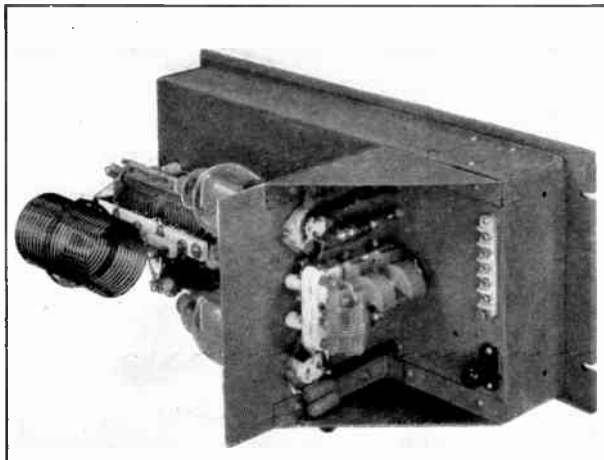

*Fig. 6-101* — The grid-circuit components of the "dish-type" 450-watt amplifier are mounted on this side of the partition which is braced by standard 5-inch triangular brackets. The tank condenser is mounted by means of a screw in the hole which remains when the shield between the stators is removed. The ceramic terminal strip is for all external connections except for positive high voltage for which a special safety terminal is provided. A large clearance hole should be cut in the chassis for the condenser shaft. The shaft, which should come at the center line of the chassis, should be provided with a flexible insulating coupling.

to keep it as symmetrical as possible. In forming the long wires between the neutralizing condensers and the tank-condenser stators, the lengths should be made identical. The wire connecting to the rear condenser stator should go directly in a straight line, while the one going to the front stator section may be bent to make up for the difference in distance between the neutralizing condensers and the two stators. The plate leads to the tubes should be tapped on these long wires at points which will make the wire length between neutralizing condenser and plate and between tank condenser and plate equal on each side.

The positive high-voltage lead, run inside the chassis with high-voltage cable, comes up through a feed-through insulator near the plate choke.

The rotors of the grid tank condenser are not grounded, since experience has shown that an amplifier of this type usually neutralizes more readily without the ground connection and excitation usually divides more evenly between the two tubes.

The leads from the neutralizing condensers to the grid terminals are crossed over before they pass through small feed-through points


mounted in the partition. The grid r.f. chokes are self-supporting between the tube grid terminals and the feed-through points in the chassis which carry the biasing leads inside to the individual meter shunts. Filament wires are run through  $\frac{3}{8}$ -inch holes lined with rubber grommets.

Inside the chassis, the separate meter-shunting resistances are supported on fiber lug strips. The leads going to the switch should be soldered in place, formed into cables, and the other ends connected to the switch on the panel as the last operation before putting the panel in place.

This amplifier is suitable for use with any of the 1000-volt 100-ma. to 1500-volt 150-ma. triodes. Those shown in the photographs are 812s.

For 1500-volt tubes, the power supply shown in Fig. 6-103 is suitable for use with this amplifier. The bias supply should be adjusted following the suggestions given in connection with Fig. 6-87. For 812s, VR-90 regulators will provide adequate protective bias. If these tubes are to be operated at maximum e.w. ratings, an operating bias of 175 volts is required. The difference between the fixed voltage (90

*Fig. 6-102* — The plate tank-coil jack strip of the 450-watt push-pull amplifier is fastened to the tank-condenser frame with strip-metal brackets. The assembly, mounted on  $\frac{3}{8}$ -inch stand-off insulators is placed at the center of the chassis as far to the left as possible. The condenser shaft is extended at right angles through the bearing in the center of the chassis by means of two Milen 45-degree shaft joints connected together by a short length of bakelite shafting. The sockets for the tubes are submounted on the 6 × 8-inch partition, 3½ inches up from the chassis and 1⅞ inches from each edge and are orientated so that the plates of the tubes will be in a vertical plane.

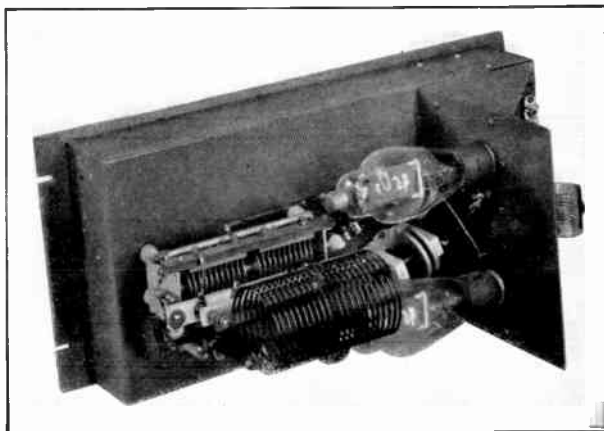

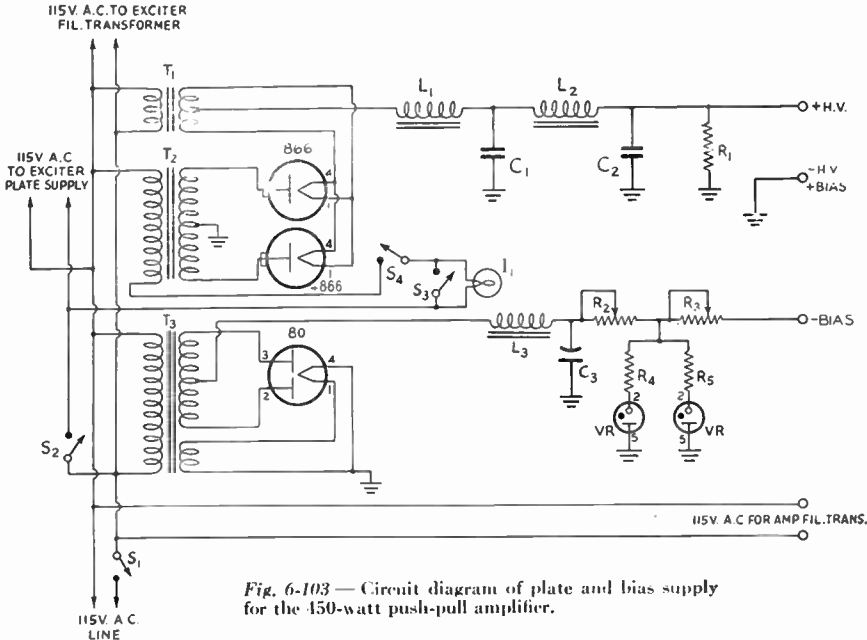


Fig. 6-103 — Circuit diagram of plate and bias supply for the 450-watt push-pull amplifier.

- |   |   |
|---|---|
| <p><math>C_1, C_2</math> — 4-<math>\mu</math>fd. 2000-volt oil-filled.<br/> <math>C_3</math> — 8-<math>\mu</math>fd. 450-volt electrolytic.<br/> <math>R_1</math> — 25,000 ohms, 100 watts.<br/> <math>R_2</math> — 25,000 ohms, 25 watts, with slider.<br/> <math>R_3</math> — 5000 ohms, 25 watts, with slider.<br/> <math>R_4, R_5</math> — 100 ohms, 1 watt.<br/> <math>L_1</math> — 5/25-hy. 400-ma. swinging choke.<br/> <math>L_2</math> — 20-hy. 400-ma. smoothing choke.<br/> <math>L_3</math> — 30-hy. 50-ma. filter choke.</p> | <p><math>I_1</math> — 150-watt 115-volt lamp.<br/> <math>S_1, S_2, S_3</math> — 10-amp. switch.<br/> <math>S_4</math> — 5-amp. switch.<br/> <math>T_1</math> — 2.5-volt 10-amp. filament transformer, 10,000-volt insulation.<br/> <math>T_2</math> — 1500/1250-v. d.c. 400-ma. plate transformer.<br/> <math>T_3</math> — Power transformer, 650 v. a.c., c.t., 50 ma. or more; 5 volts, 2 amp.<br/> <math>VR</math> — Voltage-regulator tubes (see text).</p> |
|---|---|

volts) and the operating bias, 85 volts, is obtained from the grid leak,  $R_3$ . At the rated grid current of 50 ma. for the two tubes,  $R_3$  should be adjusted to 1700 ohms.  $R_2$  should be adjusted so that the VR tubes just ignite without excitation applied to the amplifier.

The control switching system is similar to the ones previously described. The amplifier requires a driver delivering 25 to 40 watts output.

If the layout and wiring have been followed carefully, no difficulties should be encountered in neutralizing nor with parasites. Both grid and plate currents should check the same within ten per cent.

The meter, when switched to read grid current, forms a good neutralizing indicator. Both neutralizing condensers should be kept at equal settings and adjusted simultaneously until the grid current remains perfectly steady as the plate tank condenser is tuned through resonance. Neutralizing is always done with the plate-voltage lead removed. Operating voltages and currents for other tubes or operating conditions for lower plate voltages should be taken from tube data sheets.

Link output is provided for connecting directly to a "flat" line or coupling to any type of antenna system through an antenna tuner (see Chapter Ten).

## A 1-Kw. Push-Pull Amplifier

The push-pull amplifier shown in the photographs of Figs. 6-104, 6-106 and 6-107 is built around a pair of Eimac 250T11 triodes. It will handle a full kw. input at a plate voltage of 2000 or less, although the plate tank-condenser spacing is sufficient for 3000-volt operation with plate modulation. The driving stage should be capable of delivering approximately 100 watts. The amplifier may be shifted to any amateur band by a system of plug-in coils.

The circuit, shown in Fig. 6-105, is standard for a push-pull link-coupled neutralized am-

plifier. The only departure from strict conventionality is the use of the fixed vacuum-type padding condenser ( $C_9$ ) across the plate tank coil when operating at 3.5 Mc. A filament transformer is included on the chassis to permit short leads which must carry the high heating current.

The components are mounted on a standard 10 × 17 × 3-inch chassis, with the 10-inch side against the panel to provide the necessary depth. The B & W "butterfly"-type plate tank condenser is mounted on heavy 2-inch

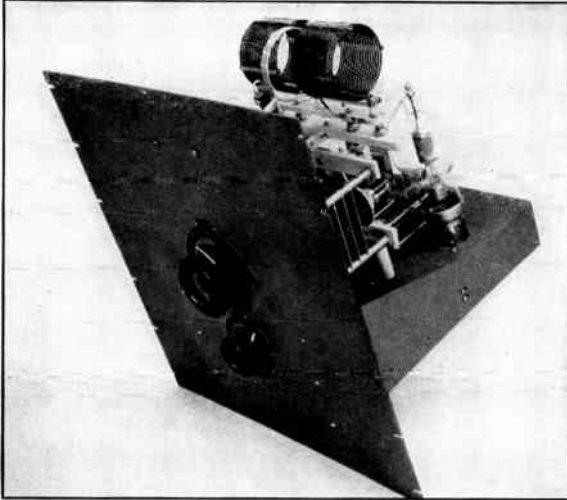


Fig. 6-104 — Front view of the kilowatt amplifier. The panel is 21 inches high and of standard 19-inch width.

stand-off insulators, with its shaft along the center line of the chassis and its front mounting feet centered 2 inches from the panel. Since its rotor is connected to the high-voltage supply, use of a good insulating shaft coupling is of utmost importance as a safety measure. The output tank-coil base assembly, with its adjustable link, is fastened to the two upper-rear stator nuts of the condenser by means of a pair of aluminum angle pieces. Similarly, the clips for the 3.5-Mc. vacuum-type padding condenser are mounted at the front of the condenser. Link output terminals are provided by the large stand-off insulators fastened to the rear of the panel near the top.

The neutralizing condensers are special units designed as accessories to the tank condenser. Each consists of a single disk connected to the grids, the rear stator plates of the plate tank condenser serving as the other side of the neutralizing condenser, for a compact unit. The by-pass condenser,  $C_7$ , is located under the rear end of the tank condenser and is fastened to the chassis with a small metal angle piece which makes the ground connection.

The sockets for the 250THs are submounted. They are spaced 5 inches, center to center, and 4 inches in from the rear edge of the chassis. The grid tank condenser is mounted between the tubes with an extension shaft to the front of the panel. The rotor plates are grounded to the chassis. The high-voltage line to the plate tank condenser and the plate r.f. choke is brought up through the chassis via a large ceramic feed-through insulator.

Underneath, the jack-bar for the grid coil is centered between the tube sockets. Connections between this coil mounting and the condenser on top are made through large clearance holes lined with rubber grommets. Short, direct leads connect the tank circuit to the grid terminals of the tubes.

The filament transformer is mounted directly underneath the plate tank condenser. Since this transformer, as well as the grid coil, protrudes from the underside of the chassis, the chassis is set with its bottom edge  $2\frac{1}{2}$  inches above the bottom edge of the panel. The transformer shown in the photographs, and listed under Fig. 6-105, is one designed for rectifier service and has high-voltage insulation. If

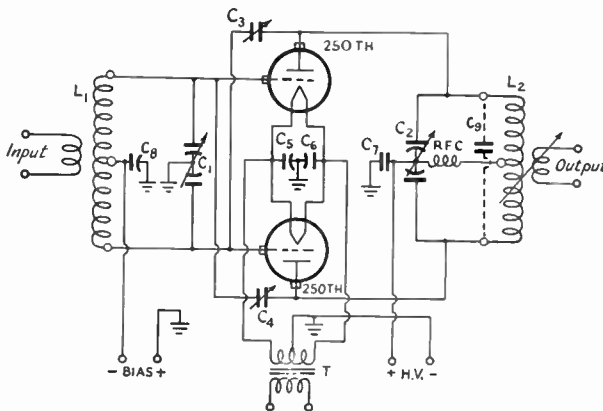


Fig. 6-105 — Circuit diagram of the high-power push-pull amplifier.

$C_1$  — 100  $\mu$ fd. per section, 0.05-inch spacing (Hammarlund HFD-100-C).

$C_2$  — 60  $\mu$ fd. per section, 0.25-inch spacing (B & W CX62-C).

$C_3, C_4$  — Disk-type neutralizing condenser (B & W N-3).

$C_5, C_6, C_8$  — 0.01- $\mu$ fd. paper, 600 volts.

$C_7$  — 0.001- $\mu$ fd. mica, 10,000 volts.

$C_9$  — 25  $\mu$ fd., 16,000 volts (GE GL122).

$L_1$  — B & W BCL coils.

$L_2$  — B & W HDVL coils.

RFC — 1-mh. r.f. choke (Hammarlund CH-500).

T — 5 volts, 22 amperes (Stancor P6302, see text).

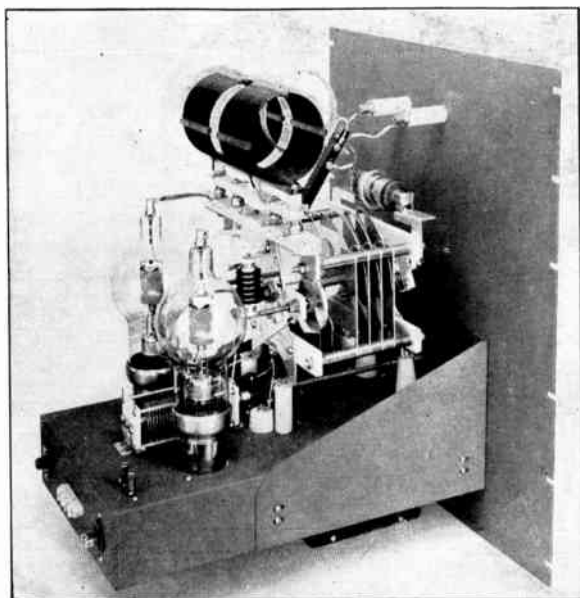


Fig. 6-106 — Rear view of the push-pull 250TH amplifier showing the mounting of the plate tank coil and 3.5-Mc. padding condenser.

one with 1600- or 2000-volt insulation is available it may be substituted, of course. A Millen safety terminal for the positive high-voltage connection, a three-terminal ceramic strip for bias and ground connections, and a male power plug for the 115-volt connection to the filament transformer are set in the rear edge of the chassis while a pair of insulated terminals in the left rear corner are for the excitation input.

### Power Supply

Fig. 6-108 shows the details of a suitable high-voltage plate and biasing supply for this amplifier. For a plate voltage of 2500, VR-90s in the bias supply will provide adequate voltage for plate-current cut-off. Five of them in parallel should be used to handle the necessary grid current.  $R_2$  should be adjusted so that the tubes just ignite without excitation to the 250THs. For an operating bias of 150 volts, 60 volts must be obtained from the grid leak,  $R_3$ . At a grid current of 150 ma. under operating conditions, this will require a resistance of 400 ohms for  $R_3$ . The control switching system operates as described in connection with previously-mentioned supplies.

### Adjustment

When the amplifier is completed and ready for operation, the first step in adjustment is the neutralization. This may be done with the amplifier set up with all external connections made, except for the antenna and high voltage.

With the coils for the desired band plugged in, the tuning of the grid tank circuit should be adjusted until a grid-current reading is obtained. Then the neutralizing condensers should be adjusted simultaneously, bit by bit, keeping the spacing equal. When the amplifier is not

neutralized, a dip in grid current will be found as the plate tank condenser is tuned through resonance. The neutralizing condensers should be adjusted until no change in grid current occurs as the plate tank condenser is swung through its range. This should occur with the adjustable plates of the neutralizing condensers spaced about  $1\frac{3}{16}$  inches away from the rear stator plates of the tank condenser.

Although plenty of plate dissipation is available, it is desirable to do the preliminary tun-



Fig. 6-107 — The filament transformer and grid coil are mounted underneath the chassis.

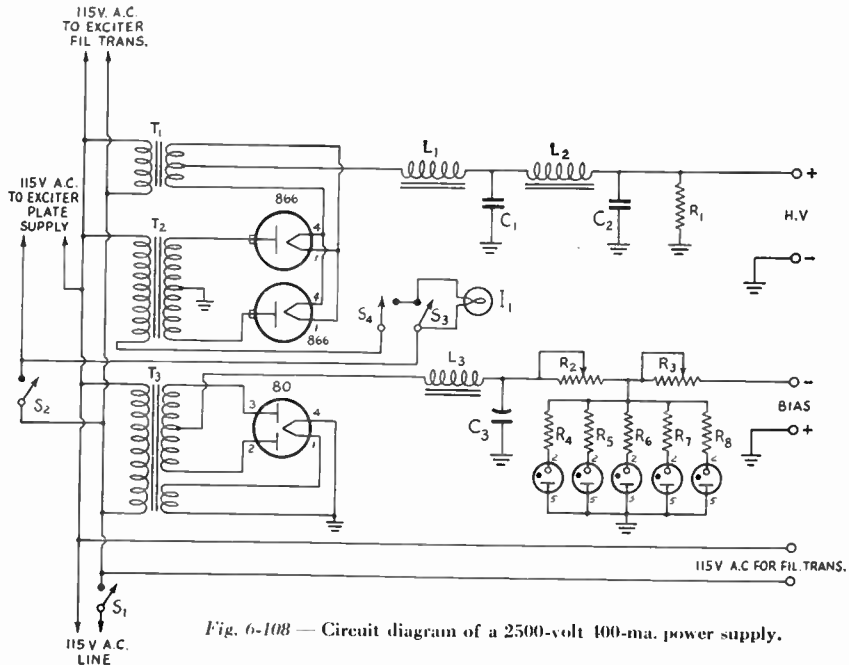


Fig. 6-108 — Circuit diagram of a 2500-volt 400-ma. power supply.

- C<sub>1</sub>, C<sub>2</sub> — 4- $\mu$ fd. 300-volt oil-filled.
- C<sub>3</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- R<sub>1</sub> — 50,000 ohms, 200 watts.
- R<sub>2</sub> — 10,000 ohms, 25 watts, with slider.
- R<sub>3</sub> — 1000 ohms, 25 watts, with slider.
- R<sub>4</sub>, R<sub>5</sub>, R<sub>6</sub>, R<sub>7</sub>, R<sub>8</sub> — 100 ohms, 1 watt.
- L<sub>1</sub> — 5-25-hy. 500-ma. swinging choke.
- L<sub>2</sub> — 20-hy. 500-ma. smoothing choke.
- L<sub>3</sub> — 30-hy. 50-ma. filter choke.

- I<sub>1</sub> — 150-watt 115-volt lamp.
  - S<sub>1</sub>, S<sub>2</sub>, S<sub>4</sub> — 15-amp. switch.
  - S<sub>3</sub> — 5-amp. switch.
  - T<sub>1</sub> — 2.5-volt 10-amp. filament transformer, 10,000-volt insulation.
  - T<sub>2</sub> — 2500-v. d.c. 500-ma. plate transformer.
  - T<sub>3</sub> — Power transformer, 650 v. a.c., c.t., 50 ma. or more; 5 volts, 2 amp.
- See text for voltage-regulator tube data.

ing and loading of the amplifier at reduced plate voltage. Before plate voltage is applied, a grid-current reading of at least 150 to 200 ma. should be possible. The antenna link should be swung out to the minimum-coupling position. As soon as plate voltage and excitation are applied, the plate tank condenser should be adjusted for minimum plate current. Grid current still should be above 150 ma. When the excitation is removed, there should be no indication of oscillation at any setting of the grid- or plate-tank condenser.

The output link may be connected directly to a properly-terminated low-impedance line, or through a link-coupled antenna tuner to the

feeders of any antenna system. With excitation and plate power applied, the plate current should increase as the link coupling is tightened and the antenna system tuned to resonance. With each adjustment of coupling or antenna tuning, the plate tank condenser should be retuned for minimum plate current. The minimum reading will increase as the coupling is tightened with the antenna tuned to resonance. The loading may be increased up to the point where the minimum reading is 400 ma., when the input will be 1 kw. at 2500 volts. With the amplifier loaded, the excitation should be adjusted to about 150 ma. for the two tubes.

## A Complete 350-Watt 'Phone-C.W. Transmitter

The 350-watt 'phone-c.w. transmitter shown in Fig. 6-109 is made up in three sections. The center section contains a bandswitching exciter and speech amplifier, each on a separate chassis. The top section is shared by a plate modulator and a push-pull final amplifier with grid bandswitching and plug-in plate coils. The bottom unit contains the two power supplies from which the transmitter is operated. All bands from 3.5 to 28 Mc. are covered and the entire apparatus is housed in a standard-

rack-width cabinet 36 $\frac{3}{4}$  inches high overall.

### Bandswitching Exciter

The bandswitching exciter and speech amplifier are shown in Figs. 6-111 and 6-112. The circuit of the exciter, shown in Fig. 6-110, follows quite closely that of the exciter unit of Fig. 6-79. The tube line-up consists of a 6V6 Tri-tet crystal oscillator giving fundamental or second-harmonic output using 3.5-Mc. crystals or fundamental output using 7-Mc.

crystals, a 6N7 dual-triode frequency multiplier with the first section doubling from 7 Mc. to 14 Mc., the second section of the same tube doubling from 14 Mc. to 28 Mc., and an 807 buffer-driver stage.

A 12-position wafer switch,  $S_1$ , is used to select one of 12 crystal sockets or to switch to external VFO input. The Tri-tet cathode coil may be switched out of the circuit by  $S_4$  to permit straight-through crystal-oscillator operation of the 6V6 with either 3.5- or 7-Mc. crystals. For 27-Mc. band output, suitable crystals must of course be selected.

Provision is made in the bandswitching circuit, controlled by the 4-section switch,  $S_2$ , to disconnect grids of unused triode sections of the 6N7 from the preceding stage and to ground them, thus avoiding applying excitation to idle stages. Both 3.5 and 7 Mc. are covered with one coil,  $L_1$ , an extra condenser (air-padder  $C_3$ ) being connected across it in parallel to extend the tuning range to cover the 3.5-Mc. band.

The output of the 807 is link-coupled to the

grid of the final amplifier but all exciter stages are capacitance-coupled. Parallel feed is used in the first three stages so that the tuning condensers,  $C_4$ ,  $C_5$  and  $C_6$ , need not be insulated from the metal panel. The coupling to the 807 grid is through a tap on each plate coil; this provides proper loading of the various driver stages.  $C_{23}$ , connected across the 3.5-Mc. output link winding, was found necessary to detune the link, which resonated at 28 Mc., absorbing a considerable amount of power when operating in the ten-meter band. Grid-leak bias is used in the 807 stage. Screen voltage for the 807 is obtained from the 600-volt supply through a dropping resistor,  $R_7$ , and approximately 300 volts is applied to the driver plates from a tap on the voltage divider,  $R_{10}R_{11}$ , across the 600-volt supply. Excitation to the 807 may be adjusted by  $R_2$  which varies the oscillator screen voltage.

The d.c. cathode returns of both the oscillator and the 807 stage are connected to closed-circuit jacks, offering a choice of keying the 807 stage only or keying both oscillator and

◆

*Fig. 6-109* — A bandswitching medium-power 'phone-c.w. transmitter, completely self-contained and compactly housed in a metal cabinet 36 $\frac{3}{4}$  inches high, 21 $\frac{1}{2}$  inches wide and 15 inches deep. The panels are standard 19-inch width and total 35 inches in height. The meter at the left in the row at the top of the panel reads filament voltage. The milliammeter on the right measures modulator plate current while that in the center can be switched to read final-amplifier grid current and plate currents in each r.f. stage. The final-amplifier plate-tank tuning control is centrally located in the top panel and the dial in line at the left is for grid-tank tuning. The 'phone-c.w. switch is at the bottom right of the top panel and the bandswitch for the final grid is at the left. The knob in the middle is for the meter switch. The tuning control for the 807 plate is located high on the left of the middle panel under which are controls, left to right, for oscillator, first doubler, second doubler and bandswitch for the 807 output tanks. The crystal-selector switch is at the lower left, with the cathode coil switch at its right. The excitation control next to the right is flanked by the two key jacks. Under the bandswitch for the output tanks is the one for the earlier stages. The audio gain control is on the extreme right lower corner. On the power-supply panel, switches in the a.c. circuits to control filament, 600-volt and 1250-volt supplies are matched at the top with panel lights.

◆



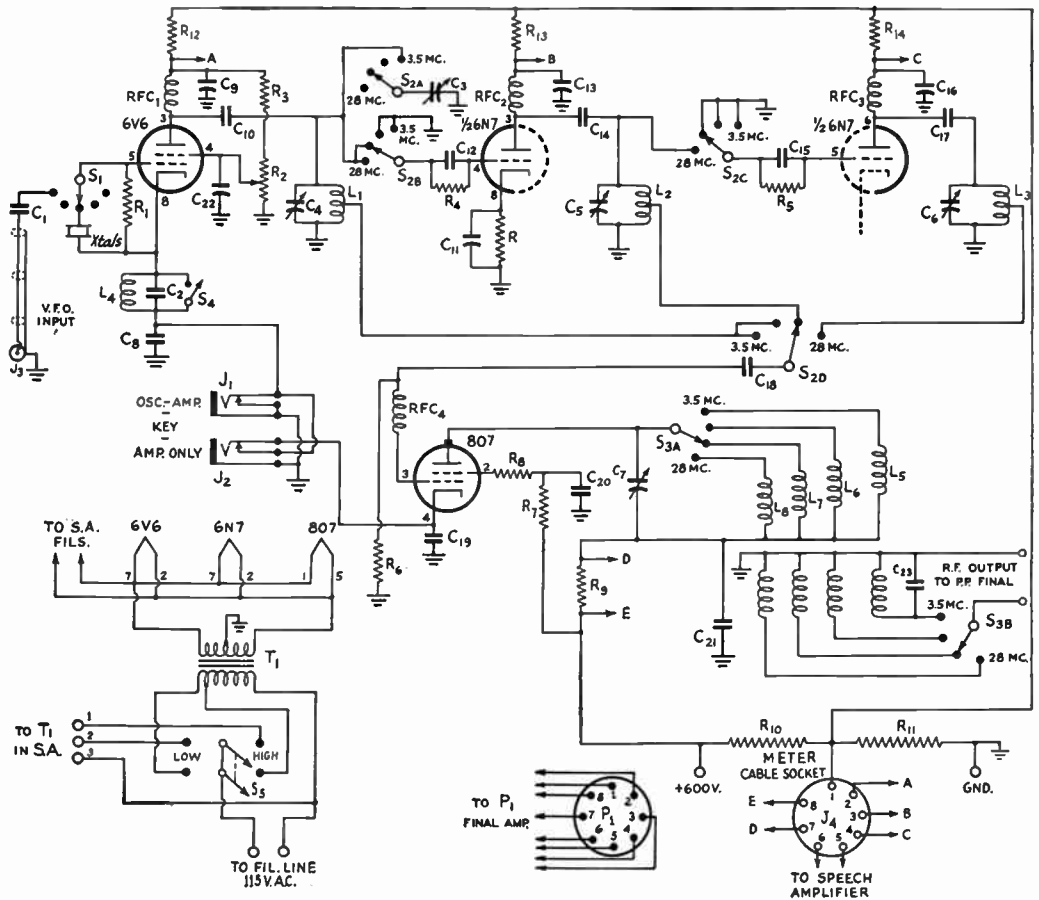


Fig. 6-110 — Circuit diagram of the r.f.-exciter unit.

- C<sub>1</sub>, C<sub>10</sub>, C<sub>14</sub>, C<sub>17</sub> — 0.0022- $\mu$ fd. mica.
- C<sub>2</sub> — 220- $\mu$ fd. mica.
- C<sub>3</sub> — 140- $\mu$ fd. air padder.
- C<sub>4</sub>, C<sub>5</sub>, C<sub>6</sub> — 100- $\mu$ fd. variable (National ST-100).
- C<sub>7</sub> — 100- $\mu$ fd. variable (Hammarlund MC-100-SX).
- C<sub>8</sub>, C<sub>19</sub> — 0.0047- $\mu$ fd. mica.
- C<sub>9</sub>, C<sub>11</sub>, C<sub>13</sub>, C<sub>16</sub>, C<sub>22</sub> — 0.01- $\mu$ fd. 600-volt paper.
- C<sub>12</sub>, C<sub>15</sub>, C<sub>18</sub> — 100- $\mu$ fd. mica.
- C<sub>20</sub> — 500- $\mu$ fd. 2500-volt mica.
- C<sub>21</sub> — 0.002- $\mu$ fd. 2500-volt mica.
- C<sub>23</sub> — 22- $\mu$ fd. mica.
- R — 470 ohms, 1 watt.
- R<sub>1</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.
- R<sub>2</sub> — 50,000-ohm potentiometer, 10 watts.
- R<sub>3</sub> — 47,000 ohms, 1 watt.
- R<sub>4</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>5</sub> — 22,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>6</sub> — 22,000 ohms, 1 watt.
- R<sub>7</sub> — 50,000 ohms, 10 watts.
- R<sub>8</sub> — 47 ohms (carbon),  $\frac{1}{2}$  watt.
- R<sub>9</sub>, R<sub>12</sub>, R<sub>13</sub>, R<sub>14</sub> — 22 ohms,  $\frac{1}{2}$  watt.
- R<sub>10</sub> — 3000 ohms, 50 watts.
- R<sub>11</sub> — 15,000 ohms, 25 watts.
- L<sub>1</sub> — 21 turns No. 18 on 1-inch diam. form, length 1 inch; tapped 15 turns from ground.

- L<sub>2</sub> — 10 turns No. 18 on 1-inch diam. form, length 1 inch; tapped 7 turns from ground.
- L<sub>3</sub> — 5 turns No 18 on 1-inch diam. form, length 1 inch; tapped 2 turns from ground.
- L<sub>4</sub> — 13 turns No. 18 on 1-inch diameter form, length 1 inch.

- NOTE — L<sub>1</sub>, L<sub>2</sub>, L<sub>3</sub> and L<sub>4</sub> are wound on Millen Type 45000 forms.
- L<sub>5</sub>, L<sub>6</sub>, L<sub>7</sub>, L<sub>8</sub> — Millen 43082, 43042, 43022 and 43012.
  - J<sub>1</sub>, J<sub>2</sub> — Closed-circuit jack.
  - J<sub>3</sub> — Coaxial-cable socket (Amphenol).
  - J<sub>4</sub> — Octal socket.
  - P<sub>1</sub> — Octal plug.
  - RFC<sub>1</sub>, RFC<sub>2</sub>, RFC<sub>3</sub> — 2.5-mh. r.f. choke (National R-100U).
  - RFC<sub>4</sub> — 20 turns No. 20 d.c.c. close-wound on 1-watt resistor (any high value of resistance may be used).
  - S<sub>1</sub> — Single-gang 12-position wafer switch.
  - S<sub>2</sub> — Four-gang four-position ceramic wafer switch.
  - S<sub>3</sub> — Two-gang four-position ceramic wafer switch.
  - S<sub>4</sub> — S.p.s.t. toggle switch.
  - S<sub>5</sub> — D.p.d.t. toggle switch.
  - T<sub>1</sub> — 6.3-volt 4-amp. filament transformer (Stancor P-4019).


buffer-amplifier stages simultaneously. With no fixed bias on the 807, the oscillator alone may not be keyed since the 807 is not provided with protective bias. The 6N7 is protected by cathode bias.

**Exciter Construction**

The exciter chassis is shown in Figs. 6-111 and 6-112. It is built on a 14 × 10 × 3-inch chassis and is mounted, with the speech-amplifier chassis, on a standard rack panel 8 $\frac{3}{4}$  inches



Fig. 6-111 — Top view of the speech-amplifier r.f.-exciter unit. The speech-amplifier equipment is mounted on the  $3 \times 5 \times 10$ -inch standard chassis to the left. The r.f. unit is spaced two inches from it with interconnections cabled through a grommetted hole in the side of each chassis. The coil assembly for the plate circuit of the 807 stage is mounted on a bracket bent from sheet aluminum. It is  $3\frac{1}{2}$  inches wide,  $6\frac{1}{2}$  inches long, and  $2\frac{1}{2}$  inches high.

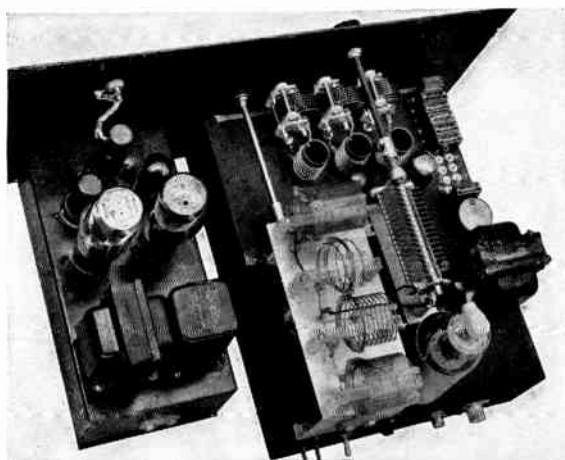

high. In Fig. 6-111, the row of eleven crystal sockets to accommodate new-style crystal holders is mounted along the right-hand edge of the chassis. A spare socket to the rear of the others is provided for old-style crystals with  $\frac{3}{4}$ -inch pin spacing and is wired in parallel with the eleventh socket from the panel. The 6.3-volt transformer to supply the heaters in both the r.f. exciter and the speech amplifier is located to the rear of the crystal sockets.

Coils for the crystal-oscillator stage and the first two doublers are wound on Millen 1-inch diameter forms and secured to the chassis with small machine screws. The leads from these coils are fed to the 4-gang bandswitch,  $S_2$ , below, through small insulating bushings immediately in front of the coils. The 6V6 crystal-oscillator tube is slightly to the right of the oscillator coil and the 6N7 is directly to the left.

The tuning condenser for the 807 driver stage is mounted on small ceramic stand-offs on a bracket formed of sheet aluminum, to permit the fiber shaft extension rod to clear the oscillator and doubler coils and condensers.

In line with this condenser and immediately to the rear of it are the socket and shield can for the 807. A short length of braid connects the plate cap of the tube to the stator terminal of the condenser.

The coils for the bandswitching assembly for the 807 stage are mounted on small ceramic stand-off insulators and fastened to another sheet-aluminum platform below which is mounted the 2-gang 807-stage bandswitch,  $S_3$ . The wafers of  $S_3$  are spaced about  $2\frac{1}{2}$  inches so that one section is almost directly under the 28-Mc. coil, to permit shortest possible leads to that coil. The 14-Mc. coil is placed next in line to the rear and the 7-Mc. coil is farthest to the rear of the subbase. The 3.5-Mc. coil is nearest the panel. The switch section at the front is used to switch the links for the various coils. The National Type FWJ banana-jack terminal for r.f. output is set in the rear end of the coil-supporting subbase.

Looking at the bottom of the exciter in Fig. 6-112, the crystal-selector switch is in the lower right-hand corner below the row of crystal sockets. The voltage-divider resistors,  $R_{10}$  and

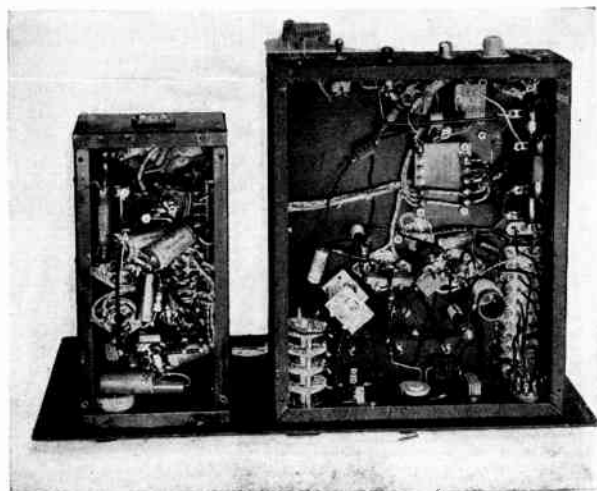


Fig. 6-112 — Bottom of the r.f.-exciter/speech-amplifier unit, with covers removed.



Fig. 6-113 — The final amplifier and modulator. The grid tank condenser and neutralizing condensers are to the right of the tubes. The plate-tank components with the coil mounted on top of the condenser are to the left. Grid coils are located underneath the chassis. The modulator occupies the left-hand end of the chassis. All meters in the transmitter are mounted on the panel of this unit.

$R_{11}$ , are mounted toward the rear of the chassis on angle brackets. The crystal-oscillator tube socket is at right center, with the cathode coil and condenser toward the panel and slightly to the right. The switch to short out the cathode coil is mounted on the panel immediately to the left of the crystal-selector switch. The excitation-control potentiometer,  $R_2$ , is mounted centrally just to the right of the two key jacks. The bandswitch  $S_2$  is at the extreme left-hand front of the chassis with the 3.5-Mc. plate-tank padding condenser,  $C_3$ , mounted at an angle to the right. The shaft of the latter extends through the chassis for screwdriver adjustment from above.

Related components are mounted wherever convenient to permit leads to be as short as possible. Much of the non-r.f. wiring, including connections to the speech amplifier, is cabled and placed around the edge of the chassis. The terminal board, mounted on small pillars, facilitates wiring. The parasitic-suppressor choke,  $RPC_4$ , is wound using a 1-watt resistor of 0.1 megohm as a form. The 115-volt male connector at the left of the back side of the chassis is the input terminal for the filament-transformer primaries. The high-low line-voltage switch,  $S_3$ , is next to the right. The Millen safety terminal is for 600-volt supply with a banana-plug jack ground connection next to it. An octal socket at the extreme right rear edge of the chassis is for the cable containing metering leads and other interunit connections. To its left is an Amphenol coaxial connector for VFO input. A length of RG-58U cable leads along the lip of the chassis to the blocking condenser,  $C_1$ , soldered to the No. 12 crystal selector-switch lug. A chassis bottom plate, removed for the picture, forms part of the shielding for the unit.

#### Final Amplifier and Modulator

The final amplifier shares the top chassis with the modulator. The wiring of this chassis is shown in Fig. 6-114.

Bandswitching is employed only in the grid circuit of the final amplifier because of the bulk that plate-coil switching would involve. One side of each link joins a common line and the other side is switched in automatically when a band is selected. Both ends of the grid tank coils are switched. The individual 500-ohm resistances at the center-tap of each coil help to isolate unused coils. The common resistor,  $R_5$ , makes up the balance of the grid leak.  $L_5C_1$  and  $L_6C_2$  are trap circuits to suppress v.h.f. parasitic oscillation.

The plate spacing of the plate tank condenser is reduced to a minimum by arranging the circuit so that d.c. and audio voltages do not appear across the condenser section. This requires that the condenser rotor be insulated from the chassis and that the shaft be provided with a high-voltage insulating coupling. The 5514s require no protective bias so they may be operated safely with grid-leak bias only.

Hytron 5514s are used also in the Class B modulator; its circuit is included in Fig. 6-114. High-frequency response is limited by shunting condensers  $C_7$  and  $C_8$  across the primary and secondary of the modulation transformer. This added capacitance acts in conjunction with the leakage reactance of the transformer windings to form a low-pass filter which attenuates the highs, including those arising because of modulator distortion. Since transformers vary, the proper value of capacitance must be determined experimentally. In this particular case, a capacitance of 0.003  $\mu$ fd. results in a rather sharp cut-off above 3000 cycles.

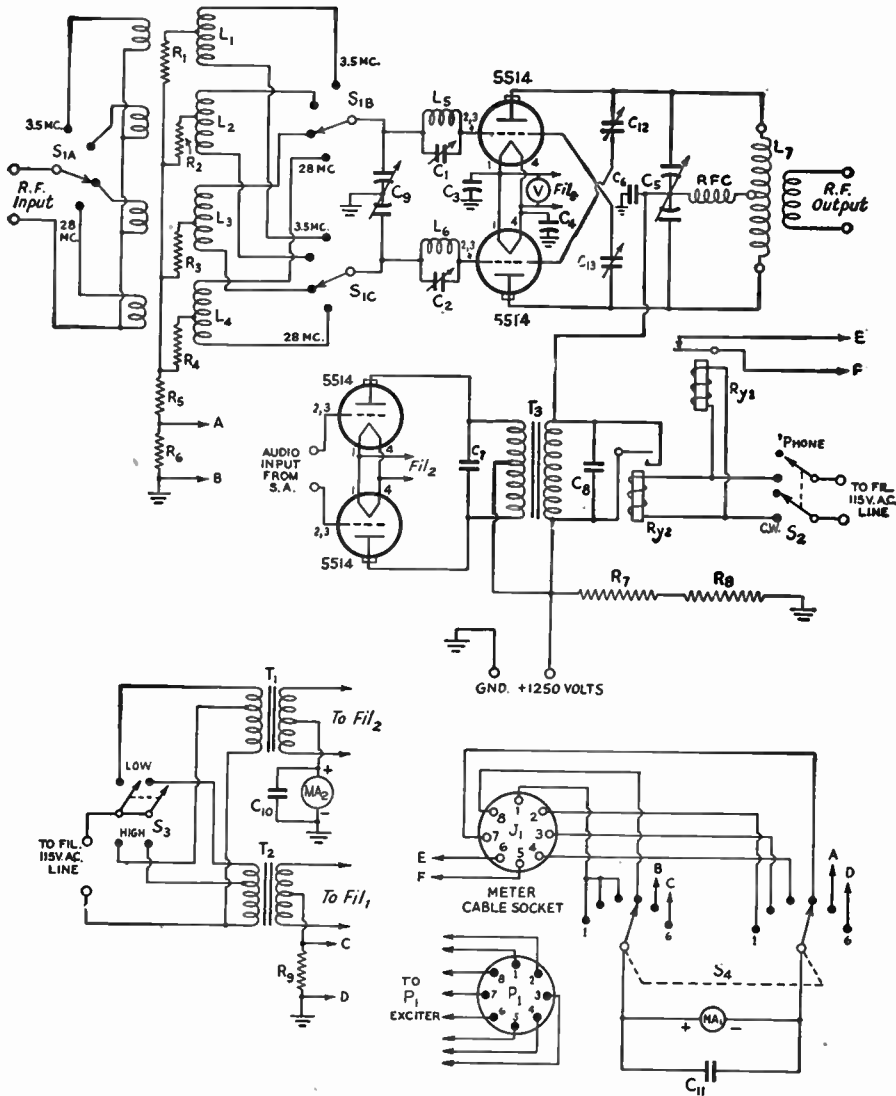


Fig. 6-114 — Circuit diagram of the final-amplifier-and-modulator unit.

- C<sub>1</sub>, C<sub>2</sub> — 3-30- $\mu$ fd. mica trimmers.
- C<sub>3</sub>, C<sub>4</sub> — 0.01- $\mu$ fd. 600-volt paper.
- C<sub>5</sub> — 100- $\mu$ fd.-per-section variable, 0.07-inch spacing (Cardwell PL7030).
- C<sub>6</sub> — 0.02- $\mu$ fd. 2500-volt mica.
- C<sub>7</sub>, C<sub>8</sub> — 0.003- $\mu$ fd. 2500-volt mica (see text).
- C<sub>9</sub> — 100- $\mu$ fd.-per-section variable, 0.047-inch spacing (National TMK-100D).
- C<sub>10</sub>, C<sub>11</sub> — 0.001- $\mu$ fd. mica.
- C<sub>12</sub>, C<sub>13</sub> — Neutralizing condenser (National NC-800).
- R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub>, R<sub>4</sub> — 500 ohms, 10 watts.
- R<sub>5</sub> — 1300 ohms, 10 watts.
- R<sub>6</sub> — 22 ohms,  $\frac{1}{2}$  watt.
- R<sub>7</sub>, R<sub>8</sub> — 10,000 ohms, 75 watts.
- R<sub>9</sub> — 22 ohms,  $\frac{1}{2}$  watt, shunted by a length of No. 30 copper wire wound around the resistor. The wire length should be adjusted to make the millimeter read one-tenth its normal value, increasing the full-scale range to 1000 ma.
- L<sub>1</sub>, L<sub>2</sub>, L<sub>3</sub>, L<sub>4</sub> — Millen Types 43081, 43041, 43021 and 43011 coils.

- L<sub>5</sub>, L<sub>6</sub> — 5 turns No. 14 bare copper wire,  $\frac{3}{4}$ -inch diameter,  $\frac{3}{4}$  inch long.
- L<sub>7</sub> — B & W BXL series.
- J<sub>1</sub> — Octal socket.
- MA<sub>1</sub> — 0-100 d.c. milliammeter.
- MA<sub>2</sub> — 0-300 d.c. milliammeter.
- P<sub>1</sub> — Octal plug.
- RFC — 1-mh. r.f. choke (National R-300).
- R<sub>y1</sub> — D.p.d.t. 115-volt coil relay (Ward-Leonard 507-549 used as s.p.s.t.).
- R<sub>y2</sub> — D.p.d.t. 115-volt coil relay (Ward-Leonard 507-531 used as s.p.s.t.).
- S<sub>1</sub> — 3-gang 4-position ceramic wafer switch.
- S<sub>2</sub> — D.p.s.t. toggle switch.
- S<sub>3</sub> — D.p.d.t. toggle switch.
- S<sub>4</sub> — 2-gang 6-position ceramic wafer switch.
- T<sub>1</sub>, T<sub>2</sub> — 7.5-volt 5-amp. filament transformer (Stancor P-4091).
- T<sub>3</sub> — Modulation transformer, 5514s to Class C (Thor-darson T-14M49).
- V — 0-10 a.c. voltmeter.

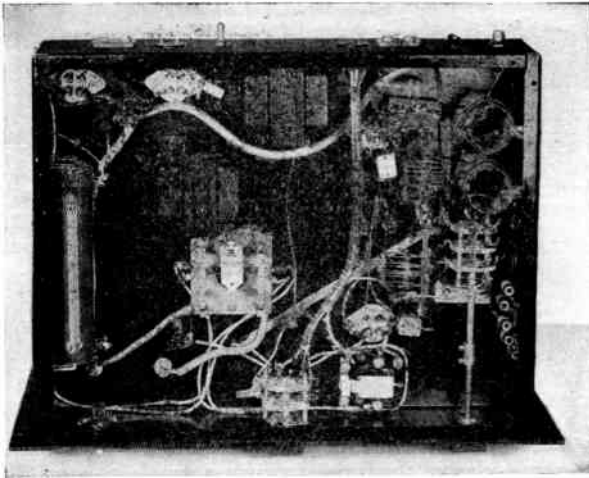


Fig. 6-113 — Under the final-amplifier/modulator chassis. The toggle switch controlling the 'phone-c.w. relays is shown in the lower left-hand corner of the chassis.

**Metering System**

A single milliammeter and switching system is used to check the plate current of all exciter stages as well as the grid and cathode currents of the final amplifier. The double-gang switch, *S*<sub>4</sub>, Fig. 6-114, connects the meter *MA*<sub>1</sub> across low-value resistors in each circuit. The resistance of *R*<sub>9</sub>, *R*<sub>12</sub>, *R*<sub>13</sub> and *R*<sub>14</sub>, Fig. 6-110, and *R*<sub>6</sub> in Fig. 6-114, is sufficiently high so that it does

not affect the reading of the meter. However, *R*<sub>9</sub>, Fig. 6-114, in the filament center-tap of the final amplifier, is a lower-resistance shunt that multiplies the meter-scale reading by ten. A separate milliammeter, *MA*<sub>2</sub>, is provided for checking modulator cathode current, while the a.c. voltmeter, *V*, Fig. 6-114, serves as a check on filament voltage.

Switch *S*<sub>2</sub> is the 'phone-c.w. switch. When it

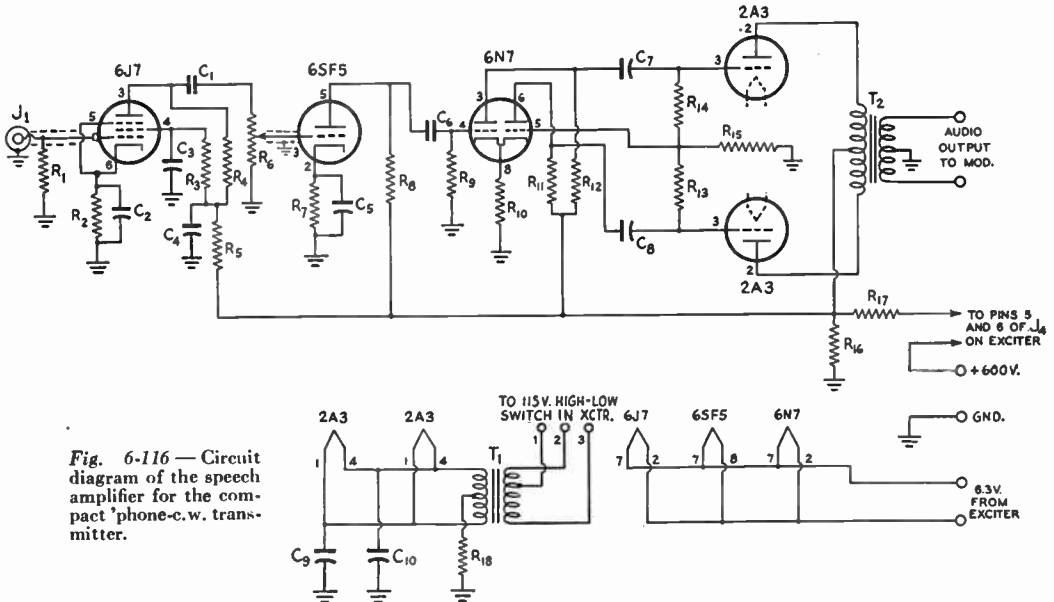


Fig. 6-116 — Circuit diagram of the speech amplifier for the compact 'phone-c.w. transmitter.

- C*<sub>1</sub>, *C*<sub>6</sub> — 0.0047- $\mu$ fd. mica.
- C*<sub>2</sub>, *C*<sub>5</sub> — 25- $\mu$ fd. 50-volt electrolytic.
- C*<sub>3</sub>, *C*<sub>7</sub>, *C*<sub>8</sub>, *C*<sub>9</sub>, *C*<sub>10</sub> — 0.1- $\mu$ fd. 440-volt paper.
- C*<sub>4</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- R*<sub>1</sub> — 4.7 megohms, 1 watt.
- R*<sub>2</sub> — 2200 ohms, 1 watt.
- R*<sub>3</sub> — 2.2 megohms, 1 watt.
- R*<sub>4</sub>, *R*<sub>8</sub> — 0.47 megohm, 1 watt.
- R*<sub>5</sub> — 47,000 ohms, 1 watt.
- R*<sub>6</sub> — 0.5-megohm potentiometer, 1 watt.
- R*<sub>7</sub> — 4700 ohms, 1 watt.
- R*<sub>9</sub> — 0.47 megohm, 1 watt.

- R*<sub>10</sub> — 1500 ohms, 1 watt.
- R*<sub>11</sub>, *R*<sub>12</sub> — 0.1 megohm, 1 watt.
- R*<sub>13</sub>, *R*<sub>14</sub>, *R*<sub>15</sub> — 0.22 megohm, 1/2 watt.
- R*<sub>16</sub> — 15,000 ohms, 15 watts.
- R*<sub>17</sub> — 4500 ohms, 35 watts.
- R*<sub>18</sub> — 750 ohms, 10 watts.
- J*<sub>1</sub> — Microphone jack.
- T*<sub>1</sub> — Filament transformer, 2.5 volts, 2.5 amperes (Stancor P-4082).
- T*<sub>2</sub> — Output transformer to match p.p. 2A3s to Class B grids (Stancor A-4212).

is closed for c.w. operation,  $Ry_2$  short-circuits the output of the modulator and  $Ry_1$  opens the high-voltage line to the speech amplifier.

#### Building the Final Amplifier

In Fig. 6-113, the dual-section variable condenser for the plate circuit,  $C_5$ , Fig. 6-114, is mounted centrally on the chassis on small ceramic stand-off insulators. A large ceramic-insulated coupling must be used between the shaft of this condenser and the dial. The jack-bar for the plug-in plate coils is fastened to the condenser frame with small angle pieces. Sockets for the 5514s are mounted just far enough apart to permit mounting the neutralizing condensers in between, while the grid tank condenser is fastened directly to the chassis at the right. The plate by-pass condenser,  $C_6$ , and r.f. choke are to the left of the plate tuning condenser.

The amplifier grid-tank coils are grouped closely around the triple-gang selector switch,  $S_1$ , shown at the right-hand side in Fig. 6-115. The switch is mounted on a metal bracket about halfway back to the rear edge. The 7- and 3.5-Mc. coils are mounted on ceramic stand-off insulators on the side of the chassis and to the rear. The 28-Mc. coil is mounted on small angle brackets just to the left of the bandswitch and the 14-Mc. coil to the rear of the switch. The parasitic-trap circuits,  $L_5C_1$  and  $L_6C_2$ , supported by the grid leads, are placed as close as possible to the grid pins of the tube sockets. The grid resistors are mounted on a terminal board fastened to the side of the chassis, just forward of the coil-selector switch.

The modulator occupies the left-hand side of the chassis in Fig. 6-113. The modulation transformer,  $T_3$ , Fig. 6-114, is placed as close to the edge of the chassis as possible with the two 5514s directly to the rear. Two 0.0015- $\mu$ fd. condensers in parallel make up the required

0.003- $\mu$ fd. capacitors for  $C_7$  and  $C_8$  and these are fastened directly across the transformer input and output terminals. The high-voltage connection is made to the center-tap of the primary of  $T_3$  and fed through a ceramic feed-through insulator in the chassis. The two filament transformers for the 5514s,  $T_1$  and  $T_2$ , and the bleeder resistors for the 1250-volt supply,  $R_7$  and  $R_8$ , Fig. 6-114, also are mounted underneath the chassis of this unit.

The relay just below the filament transformers is  $Ry_2$  which short-circuits the modulation transformer during c.w. operation. The smaller relay at the bottom is  $Ry_1$ , the supply-voltage control relay for the speech amplifier.


The three meters are mounted above the tuning controls on the final-amplifier panel, while the meter switch,  $S_4$ , is located under the chassis at the center of the front edge of the same unit. Connections between the switch and the exciter unit are made through the cabling system.

Banana-plug jacks for r.f. link input and audio input to the modulator, a 115-volt line plug for the filament transformers, the high-low filament switch,  $S_3$ , Fig. 6-114, a Millen safety terminal for the high-voltage connection and another banana-plug jack for ground connection are mounted along the rear edge.

#### Speech Amplifier

The speech amplifier is a separate unit built on a 5 × 10 × 3-inch chassis that shares the same panel as the exciter unit. It is designed for use with a crystal microphone but, by altering slightly the circuit shown in Fig. 6-116, any type of microphone may be used. A 6J7 input stage is followed by a high-gain triode stage with a 6SF5. A 6N7 phase inverter feeds a pair of 2A3s in push-pull which drive the 5514 modulator stage. The gain control is inserted in the grid of the second stage. Low-capaci-

Fig. 6-117 — A 1250-volt 550-ma. and 600-volt 200-ma. dual power supply. Components are mounted both above and below the 17 × 13 × 4-inch chassis. Close to the panel are the filter choke,  $L_4$ , the filter condensers,  $C_1$  and  $C_2$ , and the 1250-volt transformer,  $T_1$ . Along the rear are the 866 Jr., the choke,  $L_3$ , and the 866s. The female socket at the left is for the a.c. line to the filament transformers on the other chassis. The toggle switch selects the proper tap on the primaries of the filament transformers to partially compensate for low or high line voltage and the male Amphenol socket is for the a.c. input line from the safety switches on the top and back doors. The Millen safety terminal to the right of the toggle switch is the 600-volt output terminal while the one near the right-hand edge of the chassis is for the high-voltage output. At the extreme right-hand edge of the chassis is the ground connection, a banana jack mounted on a small spacer.

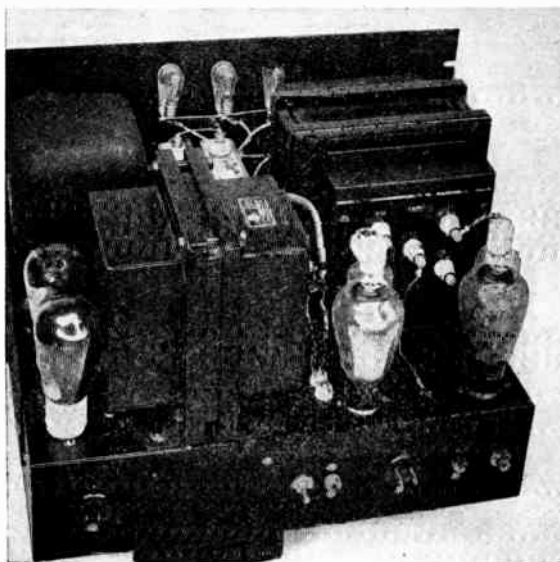

tance coupling condensers are used throughout to reduce low-frequency response.

In Fig. 6-111, the 6J7 input tube is at the

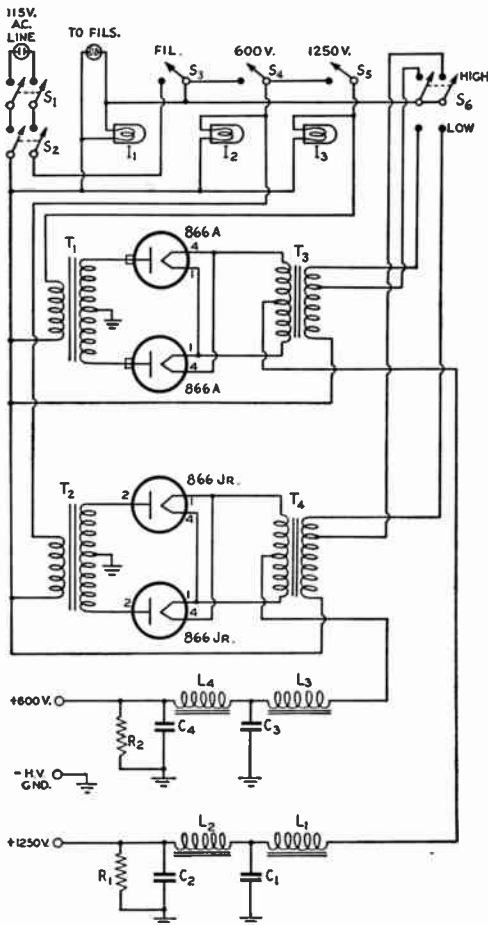


Fig. 6-118 — Circuit diagram of the dual power supply for the medium-power bandswitching transmitter, delivering 1250 volts at 550 ma. and 600 volts at 200 ma.  $C_1$ ,  $C_2$  — 4- $\mu$ fd. 2000-volt filter condenser (C-D TJU 20040).

$C_3$  — 2- $\mu$ fd. 1000-volt filter condenser (C-D TJU 10020).  
 $C_4$  — 4- $\mu$ fd. 1000-volt filter condenser (C-D TJU 10040).

$R_1$  — 0.5 megohm, 5 watts.

$R_2$  — 0.5 megohm, 2 watts.

$L_1$  — Smoothing choke, 5–20 hy., 550 ma., 75 ohms (Thordarson T-19C38).

$L_2$  — Smoothing choke, 8 hy., 550 ma., 75 ohms (Stancor C1415).

$L_3$  — Smoothing choke, 6–19 hy., 300 ma., 125 ohms (Thordarson T-19C36).

$L_4$  — Smoothing choke, 11 hy., 300 ma., 125 ohms (Thordarson T-15C46).

$I_1$ ,  $I_2$ ,  $I_3$  — 115-volt indicator lamps.

$S_1$ ,  $S_2$  — D.p.s.t. push-button interlock switch.

$S_3$ ,  $S_4$ ,  $S_5$  — S.p.s.t. toggle switch.

$S_6$  — D.p.d.t. toggle switch.

$T_1$  — Plate transformer, 1250 volts each side of center, 550 ma. (Stancor P8027).

$T_2$  — Plate transformer, 600 volts each side of center, 200 ma. (Stancor P8042).

$T_3$ ,  $T_4$  — Rectifier filament transformer, 2.5 volts, center-tapped, 10 amperes; 10,000-volt insulation (Stancor P3025).

front of the speech-amplifier chassis with its input resistor and shielded lead to the microphone terminal. The 6SF5 is located a little to the rear and to the left of the 6N7 phase inverter. The two 2A3 driver tubes occupy the center of the chassis, directly in front of the driver transformer and the 2½-volt transformer for the 2A3 filaments,  $T_1$ , Fig. 6-116. The National FWJ output terminal is at the center of the back end of the chassis.

Under the chassis, the gain control,  $R_6$ , is at the lower left as viewed from the rear. The voltage-divider resistors,  $R_{16}$  and  $R_{17}$ , are mounted along the left-hand side of the chassis and the internal terminal strip along the right-hand side. Holes in the rear cut with a socket punch allow entrance of the leads from the two transformers mounted above.

The grid lead of the 6SF5 is run through grounded shielding braid. Connections to the terminal strip are cabled and fed through rubber-grommetted holes in the sides of the chassis to appropriate external terminals. A bottom plate covers the chassis of this unit.

#### Power Supplies


Two power supplies provide plate voltage for all tubes in the transmitter. A 600-volt 200-ma. section supplies voltage for the 807 and, through voltage dividers and series voltage-dropping resistors, voltage for the exciter and speech-amplifier tubes as well. A single 1250-volt 550-ma. section provides plate voltage for the four 5514s in the final amplifier and modulator. Both supplies are assembled on a single 17 × 13 × 4-inch chassis behind a 14-inch panel that occupies the lower part of the transmitter cabinet.

The circuits are shown in Fig. 6-118.  $S_1$  and  $S_2$  are interlock switches that operate when the rear door and hinged top lid of the cabinet are opened and closed. The control switches,  $S_3$ ,  $S_4$  and  $S_5$ , are arranged so that neither of the high-voltage transformers can be turned on before the filament switch,  $S_3$ , is closed, nor can the 1250-volt supply be turned on until the 600-volt switch,  $S_4$ , has been thrown. In operation,  $S_5$  is closed and then  $S_4$  serves to control both plate supplies simultaneously. Signal lamps  $I_1$ ,  $I_2$  and  $I_3$  are provided for each switch.

Figs. 6-117 and 6-119 show the general placement of parts, which will probably vary somewhat in individual cases depending upon the available components. The chassis is fastened to the panel 2 inches up from the bottom edge, and large side brackets are used to add strength to the assembly. To provide sufficient room, it may be necessary to cut and bend the chassis lip at certain points so that the unit may be fastened to the edge of the cabinet. Wire with high-voltage insulation should be used for all except the primary circuits.

The three pilot lamps are mounted in the upper part of the panel, while the three toggle switches,  $S_3$ ,  $S_4$  and  $S_5$ , are along the bottom edge. Line a.c. input and high-voltage output

Fig. 6-119 — Bottom view of the dual power supply. The two rectifier filament transformers,  $T_3$  and  $T_4$ , are at the right with sockets for the 866As to the rear. The sockets for the 866 Jrs. in the 600-volt supply are located under the filter condensers,  $C_3$  and  $C_4$ , in the upper left-hand corner. Switches for control of the a.c. lines are set in the front edge of the chassis. The lip of the chassis is turned down to make room for mounting of the 600-volt transformer,  $T_2$ , at the lower left. The filter choke for the low-voltage supply,  $L_3$  — lower center — is supported on an aluminum bracket near the panel to allow space for switches and associated wiring. The choke  $L_1$  is above.

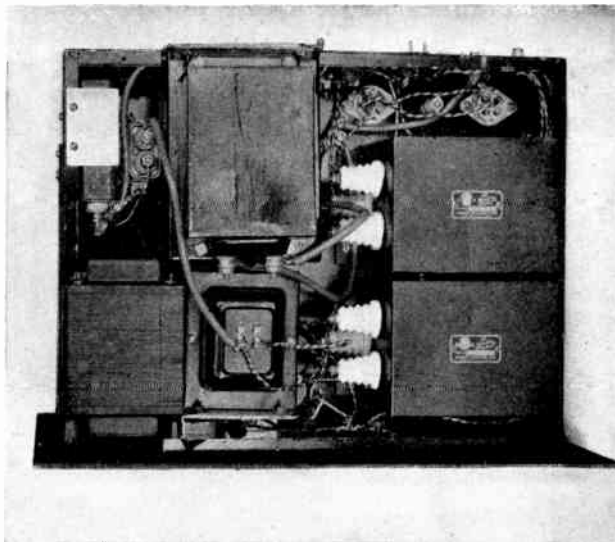

connections are made at the back, Millen safety terminals being provided for the latter.

#### Tuning Procedure

The tuning procedure is quite simple. The 'phone-c.w. switch should be in the c.w. position. With the key connected to the buffer only, set the exciter and final-grid band-switches for 28-Mc. output. Set the meter switch to read oscillator plate current (Position 1). With a 3.5-Mc. crystal, the cathode-coil switch should be open; for a 7-Mc. crystal, it should be closed. Switch on the 600-volt supply and, *without closing the key*, rotate the oscillator plate tank condenser to resonance as indicated by a dip in plate current. Switch the meter to the first doubler (Position 2) and rotate the first-doubler tank condenser for a similar resonance-indicating dip. Check the 28-Mc. doubler stage in like manner.

With these driver stages tuned to resonance, close the key and rapidly rotate the 807 tank condenser for resonance. Then adjust the grid

current to the final amplifier by rotating the final-amplifier grid condenser. It may be necessary to retune the plate circuit of the 807 to bring it back to resonance after adjusting the final-grid tuning. Grid current to the final should read 80 to 100 ma.

The final amplifier should then be neutralized in the usual manner. After neutralizing, voltage may be applied to the final and the output tank resonated and the amplifier loaded in conventional manner.

#### 'Phone Operation

For 'phone operation the plate supplies are switched off and the 'phone-c.w. switch changed to the 'phone position. The key should be closed or the keying plug removed entirely from the jack. First the 600-volt and then the 1250-supply should be switched on, then the gain control adjusted to proper level after which the 600-volt supply switch alone may be used to control the transmitter by leaving the high-voltage supply switch in the "on" position.

## Rack Construction

Most of the units described in the constructional chapters of this *Handbook* are designed for standard rack mounting. The assembly of a selected group of units to form a complete transmitter is, therefore, a relatively simple matter. While standard metal racks are available on the market, many amateurs prefer to build their own less expensively from wood. With care, an excellent substitute can be made.

The plan of a rack of standard dimensions is shown in Fig. 6-120. The rack is constructed entirely of 1 × 2-inch stock of smooth pine, spruce or redwood, with the exception of the trimming strips, *M*, *N*, *O* and *P*. Since the actual size of standard 1 × 2-inch stock runs appreciably below these dimensions, a much

sturdier job will result if pieces are obtained cut to the full dimensions.

Each of the main vertical supporting members of the wooden rack is comprised of two pieces (*A* and *B*, and *I* and *J*) joined together at right angles. Each pair of these members is fastened together by No. 8 flat-head screws, with heads countersunk.

Before fastening these pairs together, pieces *A* and *J* should be made exactly the same length and drilled in the proper places for the mounting screws, using a No. 30 drill. The length of pieces *A*, *J*, *B* and *I* should equal the total height of all panels required for the transmitter plus *twice* the sum of the thickness and width of the material used. If the dimensions

of the stock are exactly  $1 \times 2$  inches, then 6 inches must be added to the sum of the panel heights. An inspection of the top and bottom of the rack in the drawing will reveal the reason for this. The first mounting hole should come at a distance of  $\frac{1}{4}$  inch plus the sum of the thickness and width of the material from either end of pieces *A* and *J*. This distance will be  $3\frac{1}{4}$  inches for stock exactly  $1 \times 2$  inches. The second hole will come  $1\frac{1}{4}$  inches from the first, the third  $\frac{1}{2}$  inch from the second, the fourth  $1\frac{1}{4}$  inches from the third and so on, alternating spacings between  $\frac{1}{2}$  inch and  $1\frac{1}{4}$  inches (see detail drawing Fig. 6-121). All holes should be placed  $\frac{3}{8}$  inch from the inside edges of the vertical members. Accompanying Table 6-V shows standard panel heights and drilling dimensions.

The two vertical members are fastened together by cross-member *K* at the top and *L* at the bottom. These should be of such a length that the inside edges of *A* and *J* are exactly  $17\frac{1}{2}$  inches apart at all points. This will bring the lines of mounting holes  $18\frac{1}{4}$  inches center to center. Extending back from the bottoms of the vertical members are pieces *G* and *D* connected together by cross-members *L*, *Q* and *E*, forming the base. The length of the pieces *D* and *G* will depend upon space requirements of the largest power-supply unit which will rest upon it. The vertical members are braced against the base by diagonal members *C* and *H*. Rear support for heavy units placed above the base may be provided by mounting angles on *C* and *H* or by connecting these members with cross-braces as shown at *F*.

To finish off the front of the rack pieces of  $\frac{1}{4}$ -inch oak strip (*M*, *N*, *O*, *P*) are fastened around the edges with small-head finishing nails. The heads are set below the surface and the holes plugged with putty or plastic wood.

The top and bottom edges of *M* and *O* should be  $\frac{1}{4}$  inch from the first mounting holes, and the distance between the inside edges of the vertical strips, *N* and *P*,  $19\frac{1}{16}$  inches. To prevent the screw holes from wearing out when panels are changed frequently,  $\frac{1}{2} \times \frac{1}{16}$  or  $\frac{1}{32}$ -inch iron or brass strip may be used to back up the vertical members of the frame.

The outside surfaces should be sanded thoroughly and given one or two coats of flat black, sandpapering between coats. A finishing surface of two coats of glossy black "Duco" is then applied, again sandpapering between coats. It is very important to allow each coat to dry thoroughly before applying the next, or sandpapering.

Since the combined weights of power supplies, modulator equipment, etc., may total to a surprising figure, the rack should be provided with rollers or wheels so that it may be moved about when necessary after the transmitter has been assembled. Ball-bearing roller-skate wheels are suitable for the purpose.

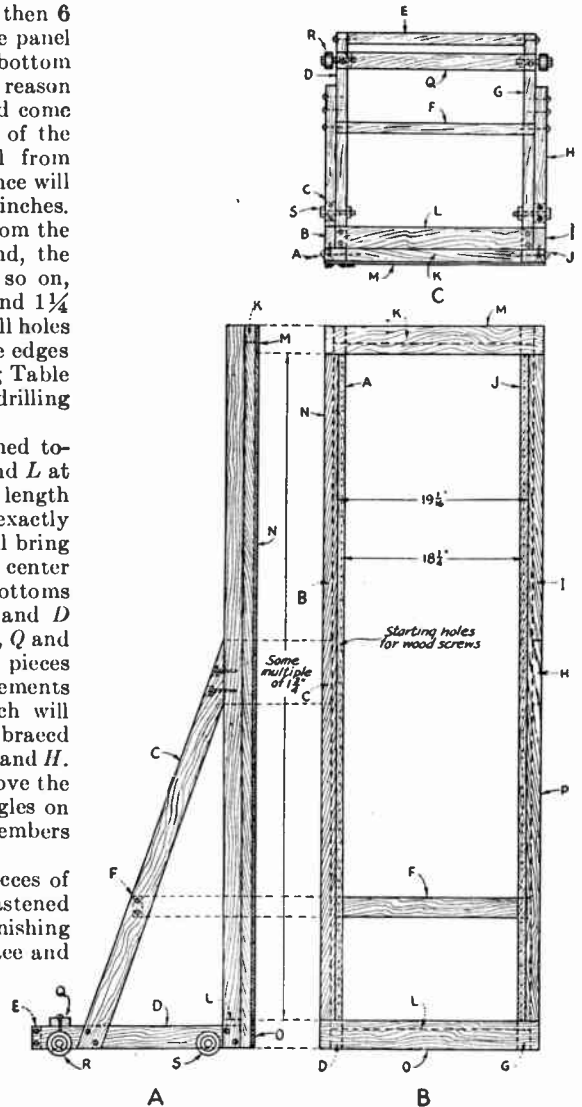



Fig. 6-120 — Detail drawing of a standard rack made of wood. A — Side view. B — Front view. C — Top view.

Standard metal chassis are 17 inches wide. Standard panels are 19 inches wide and multiples of  $1\frac{3}{4}$  inches high. Panel mounting holes start with the first one  $\frac{1}{4}$  inch from the edge of the panel, the second  $1\frac{1}{4}$  inches from the first, the third  $\frac{1}{2}$  inch from the second, the fourth  $1\frac{1}{4}$  inches from the third, and the distances between holes from there on alternated between  $\frac{1}{2}$  inch and  $1\frac{1}{4}$  inches. (See Fig. 6-121.) In a panel higher than two or three rack units ( $1\frac{3}{4}$  inches per unit), it is common practice to drill only sufficient holes to provide a secure mounting. All panel holes should be drilled  $\frac{3}{8}$  inch in from the edge.

If desired, the rack may be enclosed by completing a framework of one-by-two strip, using  $\frac{1}{4}$ -inch plywood for the panels. The panels



Fig. 6-121 — Detail sketch showing proper drilling for standard rack and panels. As shown for the 3½- and 5¼-inch panels, only sufficient holes are drilled in the panel to provide the necessary strength. When the panels are drilled as shown, they may be moved up and down in steps of 1¼ inches and the holes will always match.

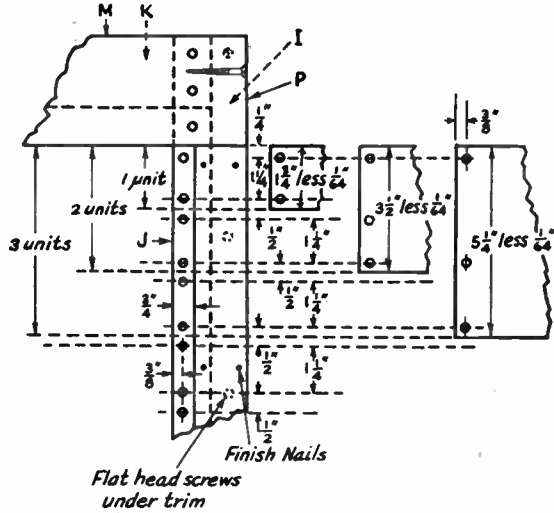

may be hinged so that three sides are made accessible for servicing. If the transmitter is to be operated in an enclosure, provision should be made for a small amount of forced-air ventilation; otherwise the panels should be open while the transmitter is in operation.

TABLE 6-V

Panel Height (Inches)	1¾	3½	5¼	7	8¾	10½	12¼	14	15¾
Panel* Drilling (Inches)	1¼ 1½	2 3¼	3¾ 5	5½ 6¾	7¼ 8½	9 10¼	10¾ 12	12½ 13¾	14¼ 15½
Panel Height (Inches)	17½	19¼	21	22¾	24½	26¼	28	29¾	31½
Panel* Drilling (Inches)	16 17¼	17¾ 19	19½ 20¾	21¼ 22½	23 24¼	24¾ 26	26½ 27¾	28¼ 29½	30 31¼

\* Additional holes for this size panel. Any or all holes given for panels smaller than this size may be added, as required for support.

# Power Supplies

Essentially pure direct-current plate supply is required for receivers to prevent hum in the output. Government regulations require the use of d.c. plate supply for transmitters to prevent modulation of the carrier by the supply, which would result in undesired hum in the case of voice transmissions and an unnecessarily broad c.w. signal.

use except where commercial a.c. lines are not available. Wherever such lines are available, it is universal practice to obtain low a.c. voltage for filaments and heaters from a step-down transformer, and the required high-voltage d.c. by means of a transformer-rectifier-filter system. Such a system is shown in the block diagram of Fig. 7-1. Power from the

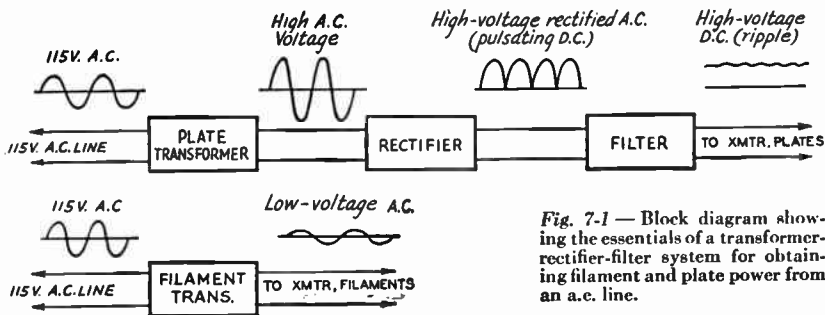


Fig. 7-1 — Block diagram showing the essentials of a transformer-rectifier-filter system for obtaining filament and plate power from an a.c. line.

The filaments of tubes in a transmitter may be operated from a.c. Those in a receiver, excepting the power audio tubes, may be a.c. operated only if the cathodes are indirectly heated.

The comparative high cost and inconvenience of batteries and d.c. generators preclude their

a.c. line is fed to a transformer which steps the voltage up to that required. The stepped-up voltage is changed to pulsating d.c. by passing through a rectifier — usually of the vacuum-tube type. The pulsations then are smoothed out to the required extent by a filtering system.

## Rectifier Circuits

### Half-Wave Rectifier

Fig. 7-2 shows three rectifier circuits covering most of the common applications in amateur equipment. Fig. 7-2A is the circuit of a half-wave rectifier. During that half of the a.c. cycle when the rectifier plate is positive with respect to the cathode, current will flow through the rectifier and load. But during the other half of the cycle, when the plate is negative in respect to the cathode, no current can flow. The shape of the output wave is shown at the right. It shows that the current always flows in the same direction but that the flow of current is not continuous and is pulsating in amplitude.

The average output voltage — the voltage read by the usual d.c. voltmeter — with this circuit is 0.45 times the r.m.s. value of the a.c. voltage delivered by the transformer secondary. Because the frequency of the pulses in the output wave is relatively low, considerable filtering is required to provide adequately

smooth d.c. output, and for this reason this circuit is usually limited to applications where the current involved is small, such as in supplies for cathode-ray tubes and for protective bias in a transmitter.

### Full-Wave Center-Tap Rectifier

The most universally-used rectifier circuit is shown in Fig. 7-2B. Being essentially an arrangement in which the outputs of two half-wave rectifiers are combined, it makes use of both halves of the a.c. cycle. A transformer with a center-tapped secondary, or two identical transformers with their secondaries connected in series (with proper polarization), is required with the circuit. When the plate of rectifier No. 1 is positive, current flows through the load to the center-tap. Current cannot flow through rectifier No. 2 because at this instant its cathode is positive in respect to its plate. When the polarity reverses, rectifier No. 2 conducts and current again flows through the



Fig. 7-2 — Fundamental vacuum-tube rectifier circuits.

load to the center-tap, this time through rectifier No. 2.

The average output voltage is 0.9 times the r.m.s. value of the voltage across *half* of the transformer secondary. For the same *total* secondary voltage, the average output voltage will be the same as that delivered with a half-wave rectifier. However, as can be seen from the sketch of the output waveform, the frequency of the output pulses is twice that of the half-wave rectifier. Therefore much less filtering is required. Since the rectifiers work alternately, each handles half of the average load current. Therefore the load current which may be drawn from this circuit is twice the rated load current of a single rectifier.

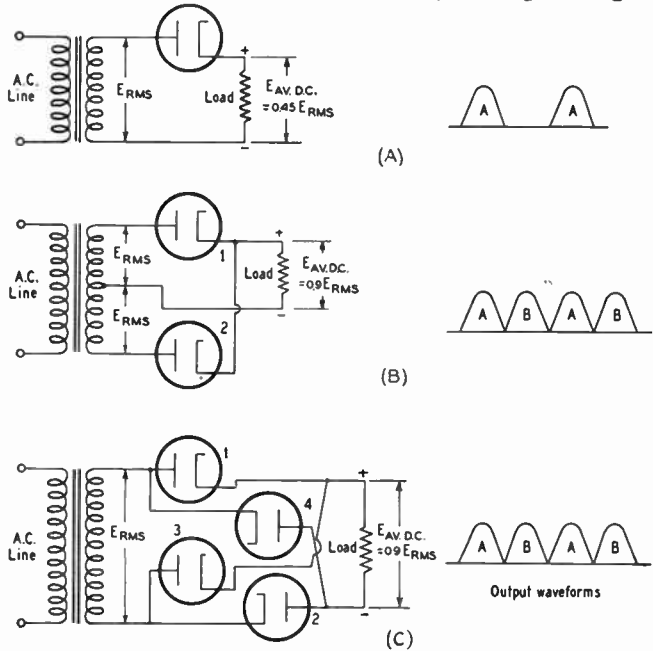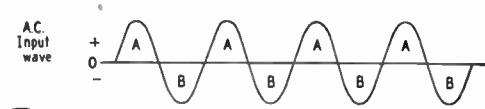**Full-Wave Bridge Rectifier**

Another full-wave rectifier circuit is shown in Fig. 7-2C. In this arrangement, two rectifiers operate in series on each half of the cycle, one rectifier being in the lead to the load, the other being in the return lead. Over that portion of the cycle when the upper end of the transformer secondary is positive in respect to the other end, current flows through rectifier No. 1, through the load and thence through rectifier No. 2. During this period current cannot flow through rectifier No. 4 because its plate is negative in respect to its cathode. Over the other half of the cycle, current flows through rectifier No. 3, through the load and thence through rectifier No. 4. The crossover connection keeps the current flowing in the same direction through the load. The output waveform is the same as that from the simple



center-tap rectifier circuit. The output voltage obtainable with this circuit is 0.9 times the r.m.s. voltage delivered by the transformer secondary. For the same total transformer-secondary voltage, the average output voltage when using the bridge rectifier will be twice that obtainable with the center-tap rectifier circuit. However, when comparing rectifier circuits for use *with the same transformer*, it should be remembered that the *power* which a given transformer will handle remains the same regardless of the rectifier circuit used. If the output voltage is doubled by substituting the bridge circuit for the center-tap rectifier circuit, only half the rated load current can be taken from the transformer without exceeding its normal rating. The value of load current which may be drawn from the bridge rectifier circuit is twice the rated d.c. load current of a single rectifier.

**Rectifiers**

**Cold-Cathode Rectifiers**

Tube rectifiers fall into three general classifications as to type. The cold-cathode type of rectifier is a diode which requires no cathode heating. Certain types will handle up to 350 ma. at 200 volts d.c. output. The internal voltage drop in most types lies between 60 and 90 volts. Rectifiers of this kind are produced in both half-wave (single diode) and full-wave (double diode) types.

**High-Vacuum Rectifiers**

High-vacuum rectifiers depend entirely upon the thermionic emission from a heated cathode and are characterized by a relatively high internal resistance. For this reason, their application usually is limited to low power, although there are a few types designed for medium and high power in cases where the relatively high internal voltage drop may be tolerated. This high internal resistance makes

them less susceptible to damage from temporary overload and they are free from the bothersome electrical noise sometimes associated with other types of rectifiers.

Some rectifiers of the high-vacuum full-wave type in the so-called receiver-tube classification will handle up to 250 ma. at 400 to 500 volts d.c. output. Those in the higher-power class can be used to handle up to 500 ma. at 2000 volts d.c. in full-wave circuits. Most low-power high-vacuum rectifiers are produced in the full-wave type, while those for greater power are invariably of the half-wave type.

#### Mercury-Vapor Rectifiers

In mercury-vapor rectifiers the internal resistance is reduced by the introduction of a small amount of mercury which vaporizes un-

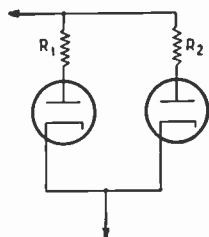


Fig. 7-3 — Connecting rectifiers in parallel for heavier currents.  $R_1$  and  $R_2$  should have the same value, between 50 and 100 ohms.

der the heat of the filament, the vapor ionizing upon the application of voltage. The voltage drop through a rectifier of this type is practically constant at approximately 15 volts regardless of the load current. Tubes of this type are produced in sizes that will handle any voltage or current likely to be encountered in amateur transmitters. For high power they have the advantage of cheapness. Rectifiers of this type, however, have a tendency toward a certain type of oscillation which produces noise in near-by receivers. When encountered, this can usually be eliminated by suitable filtering.

#### Selenium Rectifiers

Selenium rectifiers for power applications are a comparatively recent development. Units are now available with which it is possible to design a power supply capable of delivering up to 400 or 450 volts, 200 ma. These units have the advantage of compactness as well as low internal voltage drop (about 5 volts). Since they develop little heat if operated within their ratings, they are especially suitable for use in equipment requiring minimum temperature variation. Electrical noise filtering sometimes is required.

#### Rectifier Ratings

Vacuum-tube rectifiers are subject to limitations as to breakdown voltage and current-handling capability. Some types are rated in terms of the maximum r.m.s. voltage which should be applied to the rectifier plate, while

others, particularly mercury-vapor types, are rated according to maximum inverse peak voltage — the peak voltage which appears between plate and cathode during the time the tube is not conducting. In all of the circuits shown in Fig. 7-2, the inverse peak voltage across each rectifier is 1.4 times the r.m.s. value of the voltage delivered by the entire transformer secondary.

The maximum d.c. output current is the maximum load current which can be drawn safely from the output of the filter. The value listed in tube tables is the value considered to be the safe maximum under average conditions. The exact value is dependent to a considerable extent, however, upon the nature of the filter that follows the rectifier.

A more significant rating is the maximum peak plate current. It is the peak value of the current pulses passing through the rectifier. This peak value can be much greater than the load current, especially if a large condenser is placed across the output of the rectifier as part of the filtering system, because of the large instantaneous charging current drawn by the condenser if there is no impedance between the rectifier and the condenser. These peaks do not run as high with high-vacuum-type rectifiers as they do with rectifiers of the mercury-vapor type because of the relatively high series resistance of the former.

Rectifiers may be connected in parallel for current higher than the rated current of a single unit. This includes the use of the sections of a double diode for this purpose. Equalizing resistors of 50 to 100 ohms should be connected in series with each plate, as shown in Fig. 7-3, as a measure toward maintaining an equal division of current between the two rectifiers.

#### Operation of Rectifiers

In operating rectifiers requiring filament or cathode heating, care should be taken to provide the correct filament voltage at the tube terminals. Low filament voltage can cause excessive voltage drop in high-vacuum rectifiers and a considerable reduction in the inverse peak voltage which a mercury-vapor tube will withstand without breakdown. Filament connections to the rectifier socket should be firmly soldered, particularly in the case of the larger mercury-vapor tubes whose filaments operate at low voltage and high current. The socket should be selected with care, not only as to contact surface but also as to insulation, since the filament usually is at full output voltage to ground. Bakelite sockets will serve at voltages up to 500 or so, but ceramic sockets, well spaced from the chassis, always should be used at the higher voltages. Special filament transformers with high-voltage insulation between primary and secondary are required for rectifiers operating at voltages in excess of 1000 volts inverse peak.

The rectifier tubes should be placed in the

equipment with adequate free space surrounding them to provide for proper ventilation. When mercury-vapor tubes are first placed in

service, they should be allowed to run only with filament voltage for ten minutes before applying high voltage.

## Filters

The pulsating d.c. wave shown in Fig. 7-2 is not sufficiently smooth to prevent modulation. A filter consisting of chokes and condensers, as shown in Fig. 7-4, is connected between the rectifier output and the load circuit (transmitter or receiver) to smooth out the wave to the required degree.

The filter makes use of the energy-storage properties of the inductance of the choke and the capacitance of the condenser, energy being stored over the period during which the voltage and current are rising and releasing it to the load circuit during the period when the amplitude of the pulse is falling, thus leveling off the output by both lopping off the peaks and filling in the valleys.

### Ripple Frequency and Voltage

The pulsations in the output of the rectifier can be considered to be the resultant of an alternating current superimposed upon a steady direct current. From this viewpoint, the filter may be considered to consist of shunting condensers which short-circuit the a.c. component while not interfering with the flow of the d.c. component, and series chokes which pass d.c. readily but which impede the flow of the a.c. component.

The alternating component is called the ripple. The effectiveness of the filter can be expressed in terms of per cent ripple which is the ratio of the r.m.s. value of the ripple to

with 60-cycle supply. Since the output pulses are doubled with a full-wave rectifier, the ripple frequency is doubled — to 120 cycles with 60-cycle supply.

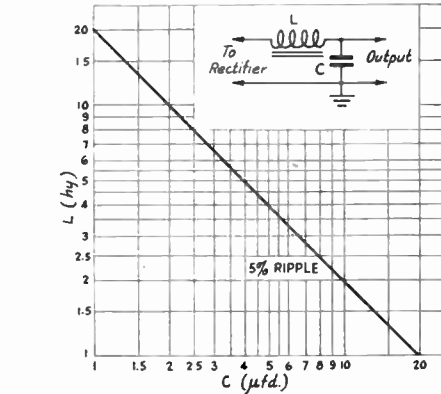


Fig. 7-5 — Graph showing combinations of inductance and capacitance that may be used to reduce ripple to 5 per cent with a single-section choke-input filter.

The amount of filtering (values of inductance and capacitance) required to give adequate smoothing depends upon the ripple frequency, more filtering being required as the ripple frequency is lower.

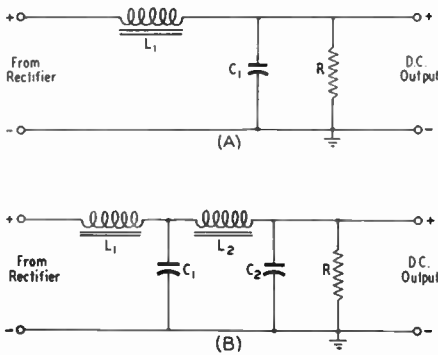


Fig. 7-4 — Choke-input filter circuits. A — Single section. B — Double section.

the d.c. value in terms of percentage. For c.w. transmitters, a reduction of the ripple to 5 per cent is considered adequate. The ripple in the output of power supplies for voice transmitters and VFOs should be reduced to 0.25 per cent or less. High-gain speech amplifiers and receivers may require a reduction to as low as 0.1 per cent to avoid objectionable hum,

### CHOKE-INPUT FILTERS

The filters shown in Fig. 7-4 are known as choke-input filters because the first element in the filter is a choke. This term is used in contrast to a condenser-input filter in which the first element is a condenser.

The percentage ripple output from a single-section filter (Fig. 7-4A) made up of any values of inductance and capacitance may be determined to a close approximation from the following formula:

$$\left. \begin{array}{l} \text{Single-} \\ \text{Section} \\ \text{Filter} \end{array} \right\} \text{Percentage ripple} = \frac{100}{LC}$$

where  $L$  is in hy. and  $C$  in  $\mu\text{fd.}$

Example:  $L = 5 \text{ hy.}, C = 4 \mu\text{fd.}$   
 Percentage ripple =  $\frac{100}{(5)(4)} = \frac{100}{20} = 5 \text{ per cent}$

Fig. 7-5 shows various other combinations

of inductance and capacitance which will reduce the ripple to 5 per cent — the required minimum reduction for a supply for a c.w. transmitter.

Example: With a 10-hy. choke, what capacitance is required to reduce the ripple to 5 per cent?

Referring to Fig. 7-5, following the 10-hy. line horizontally, it intersects the ripple line at the 2- $\mu$ fd. vertical line. Therefore the filter capacitance should be 2  $\mu$ fd.

Example: With a 4- $\mu$ fd. condenser, what choke inductance is required to reduce the ripple to 5 per cent?

Follow the vertical  $C = 4$ - $\mu$ fd. line to the point where it intersects the ripple line; then follow the horizontal line at that point to read 5 hy., the required inductance.

### Double-Section Filter

If sufficient smoothing cannot be obtained with a single set of inductance and capacitance of reasonable value (Fig. 7-4A), another section of filter may be added as shown at B. In cases where the ripple must be reduced to less than 5 per cent, the required smoothing usually can be obtained most economically by the use of a two-section filter.

The ripple percentage in the output of a double-section filter, when the ripple frequency is 120 cycles, is given by:

$$\left. \begin{array}{l} \text{Double-} \\ \text{Section} \\ \text{Filter} \end{array} \right\} \text{Percentage ripple} = \frac{650}{L_1 L_2 (C_1 + C_2)^2}$$

$L$  being in hy. and  $C$  in  $\mu$ fd.

Example:  $L_1 = 5$  hy.,  $L_2 = 20$  hy.,  $C_1 = 2$   $\mu$ fd.,  $C_2 = 4$   $\mu$ fd.

$$\text{Percentage ripple} = \frac{650}{(5)(20)(2+4)^2} = \frac{650}{3600} = 0.18 \text{ per cent}$$

The curves of Fig. 7-6 show the product of the inductances and sum of the capacitances which will reduce the ripple to 5 per cent, 0.25 per cent or 0.1 per cent. In the above example, the product of the inductances is  $5 \times 20 = 100$ , and the sum of the capacitances is  $2 + 4 = 6$ . In Fig. 7-6 the horizontal line from  $C_1 + C_2 = 6$  intersects the vertical line from  $L_1 \times L_2 = 100$  at a point between the 0.25 and 0.1 per-cent-ripple line.

Reversing the process, select any point on the desired ripple-percentage line, follow the horizontal graph line out to the left to find the required product of inductances and the vertical line down from the same point to find the required sum of the capacitances.

Example: Suppose two filter chokes are at hand, one with an inductance of 5 hy. and the other an inductance of 10 hy. The product is  $5 \times 10 = 50$ . If it is desired to reduce the ripple to 0.25 per cent, follow the horizontal line at 50 to the right until it intersects the 0.25 per cent line. At this point, follow the vertical line down to 7.5, which is the required sum of the capacitances. Two 4- $\mu$ fd. condensers (sum 8) will be suitable.

When the line frequency is other than 60

cycles, the values of both inductance and capacitance should be multiplied by the ratio of 60 to the actual line frequency to obtain the same degree of filtering.

Example: Line frequency = 25 cycles. Multiplying factor to be applied to values of inductance and capacitance based on 60 cycles =  $60/25 = 2.4$ . For a line frequency of 50 cycles the factor would be  $60/50 = 1.2$ .

In the case of a half-wave rectifier, the value of each inductance and capacitance in the filter arrived at on the basis of a ripple frequency of 120 cycles must be doubled. It requires twice as much inductance and capacitance for the same degree of filtering with the half-wave circuit.

From the consideration of ripple reduction, any combination of inductances and capacitances which will give the required product and sum respectively will give the same ripple reduction. However, two other factors must be taken into consideration in the design of the filter. These are the peak rectifier current and voltage regulation.

### Voltage Regulation

Unless the power supply is designed to prevent it, there may be a considerable difference between the output-terminal voltage of the supply when it is running free without an external load and the value when the external load is connected. Application of the load usually will be accompanied by a reduction in terminal voltage and this must be taken into consideration in the design of the supply. Regulation is commonly expressed as the percentage change in output voltage between no-load and full-load conditions in relation to the full-load voltage.

$$\text{Per cent regulation} = \frac{100(E_1 - E_2)}{E_2}$$

Example: No-load voltage =  $E_1 = 1550$  volts.  
Full-load voltage =  $E_2 = 1230$  volts.

$$\text{Percentage regulation} = \frac{100(1550 - 1230)}{1230} = \frac{32,000}{1230} = 26 \text{ per cent}$$

With proper design and the use of conservatively-rated components, a regulation of 10 per cent or less at the output terminals of the supply unit is possible. Good voltage regulation may or may not be of primary importance depending upon the nature of the load. If the load is constant, as in the case of a receiver, speech amplifier or the stages of a transmitter which are not keyed, voltage regulation, so far as that contributed by filter design is concerned, may be of secondary importance. The highly-stabilized voltage desirable for high frequency-stability of oscillators in receivers and transmitters is obtained by other means. Power supplies for the keyed stage of a c.w. transmitter and the stages following, and for Class B modulators, should have good regulation.

**The Input Choke**

The rectifier peak current and the power-supply voltage regulation depend almost entirely upon the inductance of the input choke in relation to the load resistance. The function of the choke is to raise the ratio of average to peak current (by its energy storage), and to prevent the d.c. output voltage from rising above the average value of the a.c. voltage ap-

plied to the rectifier. For both purposes, its impedance to the flow of the a.c. component must be high.

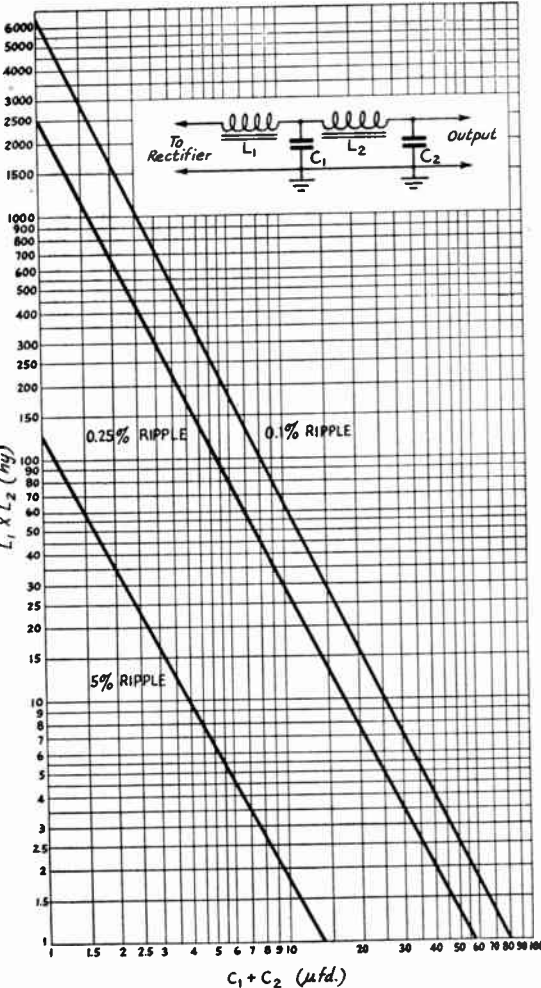


Fig. 7-6 — Chart which may be used in determining values of inductance and capacitance necessary to reduce ripple to 5, 0.25 or 0.1 per cent with a 2-section choke-input filter. Conversely, the approximate ripple to be expected with any combination of inductance and capacitance may be found. The vertical axis is in terms of the sum of the two condenser capacitances used, while the horizontal axis is in terms of the product of the inductances of the two filter chokes.

plied to the rectifier. For both purposes, its impedance to the flow of the a.c. component must be high.

The value of input-choke inductance which prevents the d.c. output voltage from rising above the average of the rectified a.c. wave is

$$L_{crit.} = \frac{\text{Load resistance (ohms)}}{1000}$$

the critical inductance. For 120-cycle ripple, it is given by the approximate formula:

For other ripple frequencies, the inductance required will be the above value multiplied by the ratio of 120 to the actual ripple frequency. With inductance values less than critical, the d.c. output voltage will rise because the filter tends to act as a condenser-input filter. With critical inductance, the peak plate current of one tube in a center-tap rectifier will be approximately 10 per cent higher than the d.c. load current taken from the supply.

An inductance of twice the critical value is called the optimum value. This value gives a further reduction in the ratio of peak-to-average plate current, and represents the point at which further increase in inductance does not give correspondingly improved operating characteristics.

**Swinging Chokes**

The formula for critical inductance indicates that the minimum inductance required varies widely with the load resistance. In the case where there is no load except the bleeder on the power supply, the critical inductance required is the highest; much lower values are satisfactory when the full-load current is being delivered. Since the inductance of a choke tends to rise as the direct current flowing through it is decreased, it is possible to effect an economy in materials by designing the choke to have a "swinging" characteristic so that it has the required critical inductance value with the bleeder load only, and about the optimum inductance value at full load. If the bleeder resistance is 20,000 ohms and the full-load resistance (including the bleeder) is 2500 ohms, a choke which swings from 20 henrys to 5 henrys over the full output-current range will fulfill the requirements. With any given input choke, the bleeder resistance (or other steady minimum load) should be 1000 times the maximum inductance of the choke in henrys.

Example: With a swinging choke of 5 to 20 hy., the bleeder resistance (or the resultant of the bleeder plus other steady load in parallel) should not exceed  $(20) (1000) = 20,000$  ohms.

**Output Condenser**

If the supply is intended for use with an audio-frequency amplifier, the reactance of the last filter condenser should be small (20 per cent or less) compared to the other a.f. resistance or impedance in the circuit, usually the tube plate resistance and load resistance. On the basis of a lower a.f. limit of 100 cycles for speech amplification, this condition usually is satisfied when the output capacitance (last filter capacitance) of the filter

is 4 to 8  $\mu\text{f.}$ , the higher value of capacitance being used in the case of lower tube and load resistances.

### Resonance

Resonance effects in the series circuit across the output of the rectifier which is formed by the first choke ( $L_1$ ) and first filter condenser ( $C_1$ ) must be avoided, since the ripple voltage would build up to large values. This not only is the opposite action to that for which the filter is intended, but also may cause excessive rectifier peak currents and abnormally-high inverse peak voltages. For full-wave rectification the ripple frequency will be 120 cycles for a 60-cycle supply, and resonance will occur when the product of choke inductance in henrys times condenser capacitance in microfarads is equal to 1.77. The corresponding figure for 50-cycle supply (100-cycle ripple frequency) is 2.53, and for 25-cycle supply (50-cycle ripple frequency), 13.5. At least twice these products should be used to ensure against resonance effects.

### Output Voltage

Provided the input-choke inductance is at least the critical value, the output voltage may be calculated quite closely by the following equation:

$$E_o = 0.9E_t - \frac{(I_b + I_L)(R_1 + R_2)}{1000} - E_r$$

where  $E_o$  is the output voltage;  $E_t$  is the r.m.s. voltage applied to the rectifier (r.m.s. voltage between center-tap and one end of the secondary in the case of the center-tap rectifier);  $I_b$  and  $I_L$  are the bleeder and load currents, respectively, in milliamperes;  $R_1$  and  $R_2$  are the resistances of the first and second filter chokes; and  $E_r$  is the drop between rectifier plate and cathode. These voltage drops are

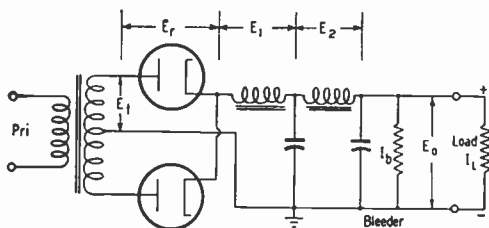


Fig. 7-7—Diagram showing various voltage drops that must be taken into consideration in determining the required transformer voltage to deliver the desired output voltage.

shown in Fig. 7-7. At no load  $I_L$  is zero, hence the no-load voltage may be calculated on the basis of bleeder current only. The voltage regulation may be determined from the no-load and full-load voltages.

## CONDENSER-INPUT FILTERS

The conventional condenser-input filter is

shown in Fig. 7-8A. No simple formulas are available for computing the ripple voltage, but it will be smaller as both capacitance and inductance are made larger. Adequate smoothing for transmitting purposes usually can be secured by using 4 to 8  $\mu\text{f.}$  at  $C_1$  and  $C_2$  and 20 to 30 hy. at  $L_1$ , for full-wave 60-cycle rectifiers.

As in the case of choke-input filters, if additional smoothing is required, another filter section may be added as shown in Fig. 7-8B. In such supplies the three condensers generally are 8  $\mu\text{f.}$  each, although the input condenser,  $C_1$ , sometimes is reduced to 4  $\mu\text{f.}$  Inductances of 10 to 20 hy. each will give satisfactory filtering, for receivers and similar applications, with these capacitance values.

For ripple frequencies other than 120 cycles, the inductance and capacitance values should be multiplied by the ratio of  $120/f$ , where  $f$  is the actual ripple frequency.

The bleeder resistance,  $R$ , should be chosen to draw about 10 per cent or less of the rated output current of the supply. Its value is equal to  $1000E/I$ , where  $E$  is the output voltage and  $I$  the bleeder current in milliamperes.

The ratio of rectifier peak current to average load current is high with a condenser-input filter. Small rectifier tubes designed for low-voltage supplies (Type 80, etc.) generally carry load-current ratings based on the use of condenser-input filters. With rectifiers for higher power, such as the 866/866-A, the load current should not exceed 25 per cent of the rated peak plate current for one tube when a full-wave rectifier is used, or one-eighth the half-wave rating.

The d.c. output voltage from a condenser-input supply will, with light loads or no load, approach the peak transformer voltage. This is 1.41 times the r.m.s. voltage of the transformer secondary, in the case of Fig. 7-2A and C or 1.41 times the voltage from the center-tap to one end of the secondary in Fig. 7-2B. At heavy loads, it may decrease to the average value of secondary voltage or about 90 per cent of the r.m.s. voltage, or even less. Because of this wide range of output voltage with load current, the voltage regulation is inherently poor.

The output voltage obtainable from a given supply with condenser input cannot readily be calculated, since it depends critically upon the load current and filter constants. Under average conditions the voltage will be approximately equal to or somewhat less than the r.m.s. voltage between the center-tap and one end of the secondary in the full-wave center-tap rectifier circuit.

### Ratings of Components

Although filter condensers in a choke-input filter are subjected to smaller variations in d.c. voltage than in the condenser-input filter, it is advisable to use condensers rated for the peak transformer voltage in case the bleeder resistor



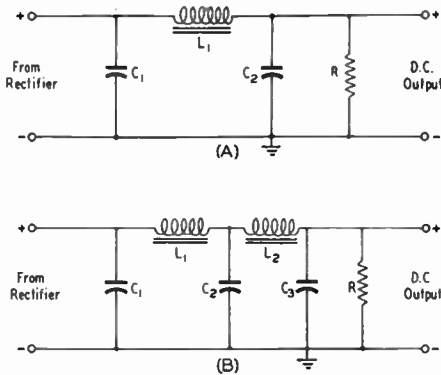


Fig. 7-8 — Condenser-input filter circuits. A — Single section. B — Double section.

should burn out when there is no external load on the power supply, since the voltage then will rise to the same maximum value as with a condenser-input filter.

In a condenser-input filter, the condensers should have a working-voltage rating at least as high and preferably somewhat higher, as a safety factor. Thus, in the case of a center-tap rectifier having a transformer delivering 550 volts each side of the center-tap, the minimum safe condenser voltage rating will be  $550 \times 1.41$  or 775 volts. An 800-volt condenser should be used, or preferably a 1000-volt unit to allow a margin of safety.

Filter condensers are made in several different types. Electrolytic condensers, which are

available for voltages up to about 800, combine high capacitance with small size, since the dielectric is an extremely-thin film of oxide on aluminum foil. Condensers for higher voltages usually are made with a dielectric of thin paper impregnated with oil. The working voltage of a condenser is the voltage that it will withstand continuously.

The input choke may be of the swinging type, the required no-load and full-load inductance values being calculated as described above. The second choke (smoothing choke) should have constant inductance with varying d.c. load currents. Values of 10 to 20 henrys ordinarily are used. Since chokes usually are placed in the positive leads, the negative being grounded, the windings should be insulated from the core to withstand the full d.c. output voltage of the supply and be capable of handling the required load current.

Filter chokes or inductances are wound on iron cores, with a small gap in the core to prevent magnetic saturation of the iron at high currents. When the iron becomes saturated its permeability decreases, consequently the inductance also decreases. Despite the air gap, the inductance of a choke usually varies to some extent with the direct current flowing in the winding; hence it is necessary to specify the inductance at the current which the choke is intended to carry. Its inductance with little or no direct current flowing in the winding may be considerably higher than the value when full load current is flowing.

## The Plate Transformer

### Output Voltage

The output voltage which the plate transformer must deliver depends upon the required d.c. load voltage and the type of rectifier circuit. With condenser-input filters, the r.m.s. secondary voltage usually is made equal to or slightly more than the d.c. output voltage, allowing for voltage drops in the rectifier tubes and filter chokes as well as in the transformer itself. The full-wave center-tap rectifier requires a transformer giving this voltage each side of the secondary center-tap, the total secondary voltage being twice the desired d.c. output voltage.

With a choke-input filter, the required r.m.s. secondary voltage (each side of center-tap for a center-tap rectifier) can be calculated by the equation:

$$E_t = 1.1 \left[ E_o + \frac{I(R_1 + R_2)}{1000} + E_r \right]$$

where  $E_o$  is the required d.c. output voltage,  $I$  is the load current (including bleeder current) in ma.,  $R_1$  and  $R_2$  are the resistances of the chokes, and  $E_r$  is the voltage drop in the rectifier.  $E_t$  is the full-load r.m.s. secondary voltage; the open-circuit voltage usually will be 5 to 10 per cent higher than the full-load value.

### Volt-Ampere Rating

The volt-ampere rating of the transformer depends upon the type of filter (condenser or choke input). With a condenser-input filter the heating effect in the secondary is higher because of the high ratio of peak to average current, consequently the volt-amperes consumed by the transformer may be several times the watts delivered to the load. With a choke-input filter, provided the input choke has at least the critical inductance, the secondary volt-amperes can be calculated quite closely by the equation:

$$\text{Sec. V.A.} = 0.00075EI$$

where  $E$  is the total r.m.s. voltage of the secondary (between the outside ends in the case of a center-tapped winding) and  $I$  is the d.c. output current in milliamperes (load current plus bleeder current). The primary volt-amperes will be 10 to 20 per cent higher because of transformer losses.

### Building Small Transformers and Chokes

Power transformers for both filament heating and plate supply for all transmitting and rectifying tubes are available commercially, but occasionally the amateur wishes to build a

transformer for some special purpose or has a core from a burned-out transformer on which he wishes to put new windings.

Most transformers that amateurs build are for use on 115-volt 60-cycle supplies. The number of turns necessary on the 115-volt winding depends on the kind of iron used in the core and on the cross-sectional area of the core. Silicon steel is best, and a flux density of about 50,000 lines per square inch can be used. This is the basis of the table of cross-sections given.

An average value for the number of primary turns to be used is 7.5 turns per volt per square inch of cross-sectional area. This relation may be expressed as follows:

$$\text{No. primary turns} = 7.5 \left( \frac{E}{A} \right)$$

where  $E$  is the primary voltage and  $A$  the number of square inches of cross-sectional area of the core. For 115-volt primary transformers the equation becomes:

$$\text{No. primary turns} = \frac{863}{A}$$

When a small transformer is built to handle a continuous load, the copper wire in the windings should have an area of 1500 circular mils for each ampere carried. (See Wire Table in Chapter Twenty-Four.) For intermittent use, 1000 circular mils per ampere is permissible.

The primary wire size is given in Table 7-1; the secondary wire size should be chosen according to the current to be carried, as previously described. The Wire Table in Chapter Twenty-Four shows how many turns of each wire size can be wound into a square inch of window area, assuming that the turns are wound regularly and that no insulation is used between layers. The primary winding of a 200-watt transformer, which has 270 turns of No. 17 wire, would occupy 270/329 or 0.82 square inch if wound with double-cotton-covered wire, for example. This makes no allowance for a layer of insulation between the windings (in general, it is good practice to wind a strip of paper between each layer) so that the winding area allowance should be increased if layer insulation is to be

used. The figures also are based on accurate winding such as is done by machines; with hand-winding it is probable that somewhat more area would be required. An increase of 50 per cent should take care of both hand-winding and layer thickness. The area to be taken by the secondary winding should be estimated, as should also the area likely to be occupied by the insulation between the core

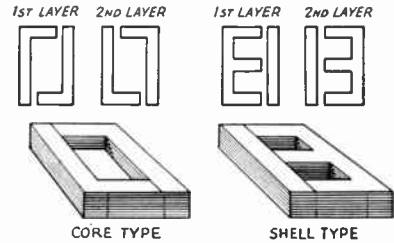


Fig. 7-9 — Two different types of transformer cores and their laminations.

and windings and between the primary and secondary windings themselves. When the total window area required has been figured — allowing a little extra for contingencies — laminations having the desired leg-width and window area should be purchased. It may not be possible to get laminations having exactly the dimensions wanted, in which case the nearest size should be chosen. The cross-section of the core need not be square but can be rectangular in shape so long as the core area is great enough. It is easier to wind coils for a core of square cross-section, however.

Transformer cores are of two types, "core" and "shell." In the core type, the core is simply a hollow rectangle formed from two "L"-shaped laminations, as shown in Fig. 7-9. Shell-type laminations are "E"- and "I"-shaped, the transformer windings being placed on the center leg. Since the magnetic path divides between the outer legs of the "E," these legs are each half the width of the center leg. The cross-sectional area of a shell-type core is the cross-sectional area of the center leg. The shell-type core makes a better trans-

TABLE 7-1  
Transformer Design

Input (Watts)	Full-Load Efficiency	Size of Primary Wire	No. of Primary Turns	Turns Per Volt	Cross-Section Through Core
50	75%	23	528	4.80	1 1/4" x 1 1/4"
75	85	21	437	3.95	1 3/8" x 1 3/8"
100	90	20	367	3.33	1 1/2" x 1 1/2"
150	90	18	313	2.84	1 5/8" x 1 5/8"
200	90	17	270	2.45	1 3/4" x 1 3/4"
250	90	16	248	2.25	1 7/8" x 1 7/8"
300	90	15	248	2.25	1 7/8" x 1 7/8"
400	90	14	206	1.87	2 x 2
500	95	13	183	1.66	2 1/4" x 2 1/4"
750	95	11	146	1.33	2 3/4" x 2 3/4"
1000	95	10	132	1.20	2 1/2" x 2 1/2"
1500	95	9	109	0.99	2 3/4" x 2 3/4"

TABLE 7-II  
Filter-Choke Design

L (Hy.)	Ma.	Stack Size (Inches)	Core Length		Gap (Inches)	Winding Form		Turns	Wire Size	Feet
			Long Piece	Short Piece		b	c			
15	50	1/2 x 1/2	1/2 x 2.2	1/2 x 0.85	0.035	1	0.68	9500	33	3500
10	100	3/4 x 3/4	3/4 x 2.6	3/4 x 0.95	0.03	1	0.67	5000	30	2250
15	100	1 x 1	1 x 3.1	1 x 0.9	0.035	0.96	0.65	4800	30	2550
10	250	2 x 2	2 x 5.2	2 x 1	0.4	1.05	0.68	2000	26	1750
20	250	2 x 2	2 x 5.6	2 x 1.2	0.28	1.43	0.95	4000	26	3820
5	500	2 x 2	2 x 5.5	2 x 1.15	0.17	1.35	0.9	1800	23	1700
10	500	2 x 2	2 x 6.2	2 x 1.5	0.4	2	1.3	3800	23	4100

former than the core type, because it tends to prevent leakage of the magnetic flux. Calculations are the same for both types.

Fig. 7-10 shows the method of putting the windings on a shell-type core. The primary is usually wound on the inside — next to the core — on a form made of fiber or several layers of cardboard. This form should be slightly larger than the core leg on which it is to fit so that it will be an easy matter to slip in the laminations after the coils are completed and ready for mounting. The terminals are brought out to the side. After the primary is finished, the secondary is wound over it, several layers of insulating material being put between. If the transformer is for high voltages, the high-voltage winding should be carefully insulated from the primary and core by a few layers of Empire Cloth or tape. A protective covering of heavy cardboard or thin fiber should be put over the outside of the secondary

should be inserted, one lamination at a time. Fig. 7-9 shows the method of building up the core. Alternate "E"-shaped laminations are pushed through the core opening from opposite sides. The "I"-shaped laminations are used to fill the end spaces, butting against the open ends of the "E"-shaped pieces. This method of building up the core ensures a good magnetic path of low reluctance. All laminations should be insulated from each other to prevent eddy currents from flowing. If there is iron rust or a scale on the core material, that will serve the purpose very well — otherwise one side of each piece can be coated with thin shellac. It is essential that the joints in the core be well made and be square and even. After the transformer is assembled, the joints can be hammered up tight using a block of wood between the hammer and the core to prevent damaging the laminations. If the winding form does not fit tightly on the core, small wooden wedges may be driven between it and the core to prevent vibration. Transformers built by the amateur can be painted with insulating varnish or waxed to make them rigid and moistureproof. A mixture of melted beeswax and rosin makes a good impregnating mixture. Melted paraffin should not be used because it has too low a melting point. Double-cotton-covered wire can be coated with shellac as each layer is put on. However, enameled wire should never be treated with shellac as it may dissolve the enamel and hurt the insulation, and it will not dry because the moisture in the shellac will not be absorbed by the insulation. Small transformers can be treated with battery compound after they are wound and assembled. Strips of thin paper between layers of small enameled wire are necessary to keep each layer even and to give added insulation. Thick paper must be avoided since it keeps in the heat generated in the winding so that the temperature may become dangerously high.

Keep watch for shorted turns and layers. If just a single turn should become shorted in the entire winding, the voltage set up in it would


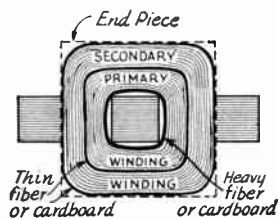


Fig. 7-10 — A convenient method of assembling the windings of a shell-type core. Windings can be similarly mounted on core-type cores, in which case the coils are placed on one of the sides. High-voltage core-type transformers sometimes are made with the primary on one core leg and the secondary on the opposite.

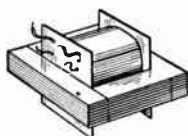

to protect it from damage and to prevent the core from rubbing through the insulation. Square-shaped end pieces of fiber or cardboard usually are provided to protect the sides of the windings and to hold the terminal leads in place. High-voltage terminal leads should be enclosed in Empire Cloth tubing or spaghetti.

After the windings are finished the core

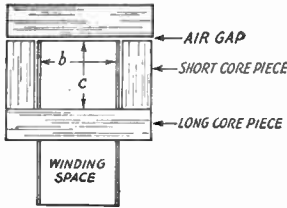


Fig. 7-11 — Core arrangement for filter choke coils. The dimensions  $b$  and  $c$  refer to Table 7-II.

cause a heavy current to flow which would burn it up, making the whole transformer useless.

Taps can be taken off as the windings are made if it is desired to have a transformer giving several voltages. Taps should be arranged whenever possible so that they come at the ends of the layers.

After leaving the primary winding connected to the line for several hours it should be only slightly warm. If it draws much current or gets

hot there is something wrong. Some short-circuited turns are probably responsible and will continue to cause overheating.

**Building Filter Chokes**

Filter choke coils may be either of the core or shell type. The laminations should not be interleaved, a butt joint being used instead. An air gap must be provided at some point in the core circuit to prevent magnetic saturation by the d.c. flowing through the winding.

Table 7-II may be used as an approximate guide in winding choke coils. For the same core size, air gap and ampere turns, the inductance will vary approximately as the square of the number of turns. The arrangement of the core is shown in Fig. 7-11 and the dimensions  $b$  and  $c$  in the table refer to this sketch. The core may be built from straight pieces as shown or with "L"-shaped laminations.

**Voltage Dropping**

**Series Voltage-Dropping Resistor**

Certain plates and screens of the various tubes in a transmitter or receiver often require a variety of operating voltages differing from the output voltage of available power supplies. In most cases, it is not economically feasible to provide a separate power supply for each of the required voltages. If the current drawn by an electrode, or combination of electrodes operating at the same voltage, is reasonably constant, under normal operating conditions, the required voltage may be obtained from a supply of higher voltage by means of a voltage-dropping resistor in series, as shown in Fig. 7-12A. The value of the series resistor,  $R_1$ , may

be obtained from Ohm's Law,  $R = \frac{E_d}{I}$ , where

$E_d$  is the voltage drop required from the supply voltage to the desired voltage and  $I$  is the total rated current of the load.

Example: The plate of the tube in one stage and the screens of the tubes in two other stages require an operating voltage of 250. The nearest available supply voltage is 400 and the total of the rated plate and screen currents is 75 ma. The required resistance is

$$R = \frac{400 - 250}{0.075} = \frac{150}{0.075} = 2000 \text{ ohms.}$$

The power rating of the resistor is obtained from  $P$  (watts) =  $I^2R = (0.075)^2(2000) = 11.2$  watts. A 25-watt resistor is the nearest safe rating to be used.

**Voltage Dividers**

The regulation of the voltage obtained in this manner obviously is poor, since any change in current through the resistor will cause a directly-proportional change in the voltage drop across the resistor. The regulation can be improved somewhat by connecting a second resistor from the low-voltage end of the first to the negative power-supply terminal, as shown in Fig. 7-12B. Such an arrangement constitutes

a voltage divider. The second resistor,  $R_2$ , acts as a constant load for the first,  $R_1$ , so that any variation in current from the tap becomes a smaller percentage of the total current through  $R_1$ . The heavier the current drawn by the resistors when they alone are connected across the supply, the better will be the voltage regulation at the tap.

Such a voltage divider may have more than

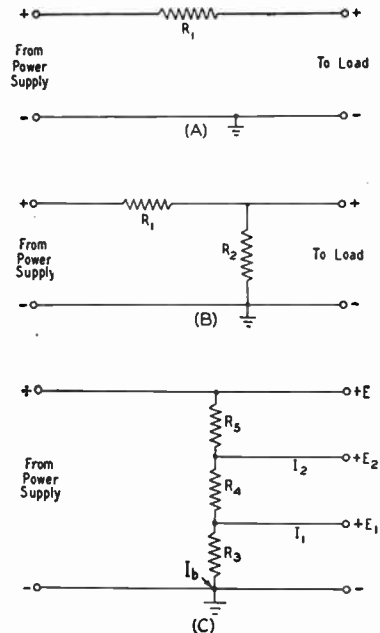


Fig. 7-12 — A — Series voltage-dropping resistor. B — Simple voltage divider. C — Multiple divider circuit.

$$R_3 = \frac{E_1}{I_b}; R_4 = \frac{E_2 - E_1}{I_b + I_1}; R_5 = \frac{E - E_2}{I_b + I_1 + I_2}$$

a single tap for the purpose of obtaining more than one value of voltage. A typical arrangement is shown in Fig. 7-12C. The terminal voltage is  $E$ , and two taps are provided to give lower voltages,  $E_1$  and  $E_2$ , at currents  $I_1$  and  $I_2$  respectively. The smaller the resistance between taps in proportion to the total resistance, the smaller the voltage between the taps. For convenience, the voltage divider in the figure is considered to be made up of separate resistances  $R_3, R_4, R_5$ , between taps.  $R_3$  carries only the bleeder current,  $I_b$ ;  $R_4$  carries  $I_1$  in addition to  $I_b$ ;  $R_5$  carries  $I_2, I_1$  and  $I_b$ . To cal-

culate the resistances required, a bleeder current,  $I_b$ , must be assumed; generally it is low compared to the total load current (10 per cent or so). Then the required values can be calculated as shown in Fig. 7-12C,  $I$  being in amperes.

The method may be extended to any desired number of taps, each resistance section being calculated by Ohm's Law using the voltage drop across it and the total current through it. The power dissipated by each section may be calculated either by multiplying  $I$  and  $E$  or  $I^2$  and  $R$ .

### Voltage Stabilization

#### Gaseous Regulator Tubes

There is frequent need for maintaining the voltage applied to a low-voltage low-current circuit (such as the oscillator in a superhet receiver or the frequency-controlling oscillator in a transmitter) at a practically constant

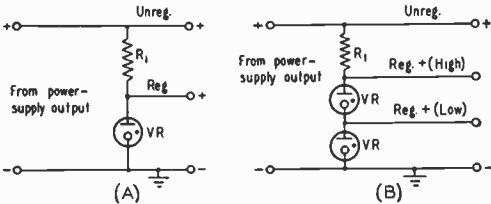


Fig. 7-13 — Voltage-stabilizing circuits using VR tubes.

value, regardless of the voltage regulation of the power supply or variations in load current. In such applications, gaseous regulator tubes (VR105-30, VR150-30, etc.) can be used to good advantage. The voltage drop across such tubes is constant over a moderately wide current range. Tubes are available for regulated voltages of 150, 105, 90 and 75 volts and will carry a maximum current of 40 ma.

The fundamental circuit for a gaseous regulator is shown in Fig. 7-13A. The tube is connected in series with a limiting resistor,  $R_1$ , across a source of voltage that must be higher than the starting voltage. The starting voltage is about 30 per cent higher than the operating voltage. The load is connected in parallel with the tube. For stable operation, a minimum tube current of 5 to 10 ma. is required. The maximum permissible current with most types is 40 ma.; consequently, the load current cannot exceed 30 to 35 ma. if the voltage is to be stabilized over a range from zero to maximum load current.

The value of the limiting resistor must lie between that which just permits minimum tube current to flow and that which just passes the maximum permissible tube current when there is no load current. The latter value is generally used. It is given by the equation:

$$R = \frac{1000 (E_s - E_r)}{I}$$

where  $R$  is the limiting resistance in ohms,  $E_s$  is the voltage of the source across which the tube and resistor are connected,  $E_r$  is the rated voltage drop across the regulator tube, and  $I$  is the maximum tube current in milliamperes (usually 40 ma.).

Fig. 7-13B shows how two tubes may be used in series to give a higher regulated voltage than is obtainable with one, and also to give two values of regulated voltage. The limiting resistor may be calculated as above, using the sum of the voltage drops across the two tubes for  $E_r$ . Since the upper tube must carry more current than the lower, the load connected to the low-voltage tap must take small current. The total current taken by the loads on both the high and low taps should not exceed 30 to 35 milliamperes.

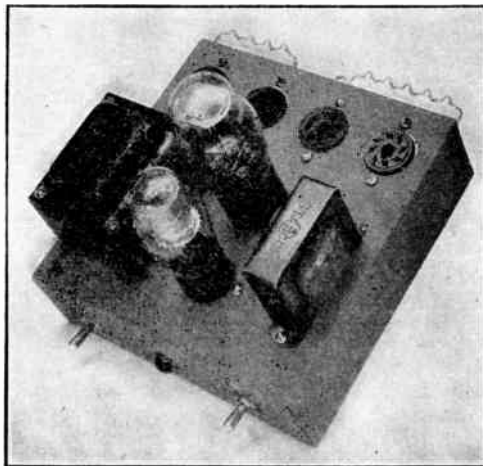


Fig. 7-14 — A receiver-type supply that delivers 250 volts at 35 ma. and a regulated potential of 150 volts at 15 ma. The amount of current which can be drawn from the 150-volt tap can be made higher or lower by selecting a suitable limiting resistor for the regulator tube; the current output will increase as the resistance value is reduced. The total current drain imposed on the supply should not exceed 50 ma. unless a transformer of greater current capacity is used. The four octal tube sockets on top of the chassis are wired in parallel with screw-type terminals and pin jacks at the rear to provide an assortment of terminals to which external circuits may be connected. The wiring diagram for the supply is shown in Fig. 7-15.

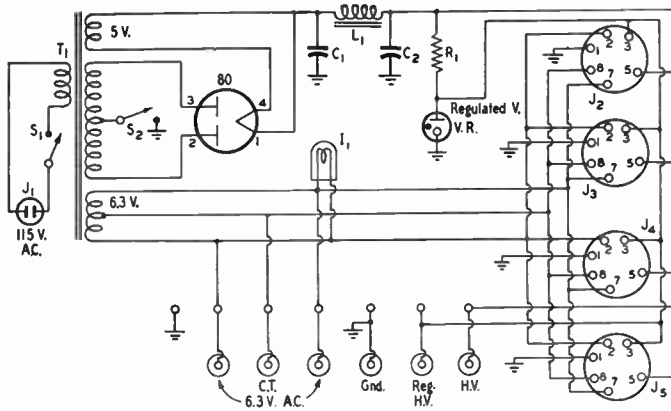


Fig. 7-15 — Circuit diagram of the receiver-type power supply.

- C<sub>1</sub>, C<sub>2</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- R<sub>1</sub> — 15,000 ohms, 10 watts.
- L<sub>1</sub> — 10-hy. 130-ma. 100-ohm filter choke.
- I<sub>1</sub> — 6.3-volt pilot lamp.
- J<sub>1</sub> — Panel-mounting a.c. plug (Amphenol 61M1).
- J<sub>2</sub>, J<sub>3</sub>, J<sub>4</sub>, J<sub>5</sub> — Octal socket.
- S<sub>1</sub>, S<sub>2</sub> — S.p.s.t. toggle switch.
- T<sub>1</sub> — Replacement-type power transformer: 290 volts each side of center-tap, 50 ma.; 5 volts, 3 amp.; 6.3 volts c.t., 2 amp.

A dual-unit electrolytic condenser may be used. The filter choke should have a fairly high current rating as suggested above in order that the output voltage of the supply will not be reduced because of high resistance in the filter. Most available low-current chokes have a d.c. resistance of 500 ohms or more.

Voltage regulation of the order of 1 per cent can be obtained with circuits of this type.

A small receiver-type power supply with a regulated tap is shown in Fig. 7-14 and the circuit diagram appears in Fig. 7-15.

**Electronic Voltage Regulation**

A voltage-regulator circuit suitable for higher voltages and currents than the gaseous tubes, and also having the feature that the output voltage can be varied over a rather wide range, is shown in Fig. 7-16. A high-gain voltage-amplifier tube, usually a sharp cut-off pentode, is connected in such a way that a small change in the output voltage of the power supply causes a change in grid bias, and thereby a corresponding change in plate current. Its plate current flows through a resistor (R<sub>5</sub>), the voltage drop across which is used to bias a second tube — the “regulator” tube — whose plate-cathode circuit is connected in series with the load circuit. The regulator tube therefore functions as an automatically-variable series resistor. Should the output voltage increase slightly the bias on the control tube will become more positive, causing the plate current of the control tube to increase and the drop across R<sub>5</sub> to increase correspondingly. The bias on the regulator tube therefore becomes more negative and the effective resistance of the regulator tube increases, causing the terminal voltage to drop. A decrease in output voltage causes the reverse action. The time lag in the action of the system is negligible, and with proper circuit constants the output voltage can be held within a fraction of a per cent throughout the useful range of load currents

and over a wide range of supply voltages.

An essential in this system is the use of a constant-voltage bias source for the control tube. The voltage change which appears at the grid of the tube is the difference between a fixed negative bias and a positive voltage which is taken from the voltage divider across the output. To get the most effective control, the negative bias must not vary with plate current. The most satisfactory type of bias is a dry battery of 45 to 90 volts, but a gaseous regulator tube (VR75-30) or a neon bulb of the type without a resistor in the base may be used instead. If the gas tube or neon bulb is used, a negative-resistance type of oscillation may take place at audio frequencies or higher, in which case a condenser of 0.1  $\mu$ fd. or more should be

connected across the tube. A similar condenser between the control-tube grid and cathode also is frequently helpful in this respect.

The variable resistor, R<sub>3</sub>, is used to adjust the bias on the control tube to the proper operating value. It also serves as an output-voltage control, setting the value of regulated voltage within the existing operating limits.

The maximum output voltage obtainable is equal to the power-supply voltage minus the minimum drop through the regulator tube. This drop is of the order of 50 volts with the tubes ordinarily used. The maximum current also is limited by the regulator tube; 100 milli-


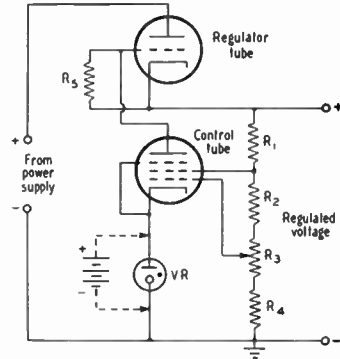


Fig. 7-16 — Electronic voltage regulator. The regulator tube is ordinarily a 2A3 or a number of them in parallel, the control tube a 6SJ7 or similar type. The filament transformer for the regulator tube must be insulated for the plate voltage, and cannot supply current to other tubes when a filament-type regulator tube is used. Typical values: R<sub>1</sub>, 10,000 ohms; R<sub>2</sub>, 22,000 ohms; R<sub>3</sub>, 10,000-ohm potentiometer; R<sub>4</sub>, 4700 ohms; R<sub>5</sub>, 0.47 megohm.

Fig. 7-17 — A heavy-duty regulated power supply capable of delivering 150 ma. over a range of 120 to 310 volts. The output, without regulation, is 435 volts. A negative potential of 150 volts is also available. Two 6B4G tubes are connected in parallel to provide regulation and a 6SJ7GT is used as the control tube. The negative voltage is obtained by connecting a 1-V rectifier tube between the secondary of the power transformer and a VR-150 regulator tube. This front view of the supply shows the placement of the power and filament transformers, tubes, and filter choke. The pilot light, on-off switches, and voltage-control potentiometer are mounted on the front wall of the chassis. The wiring diagram for the supply is shown in Fig. 7-18.

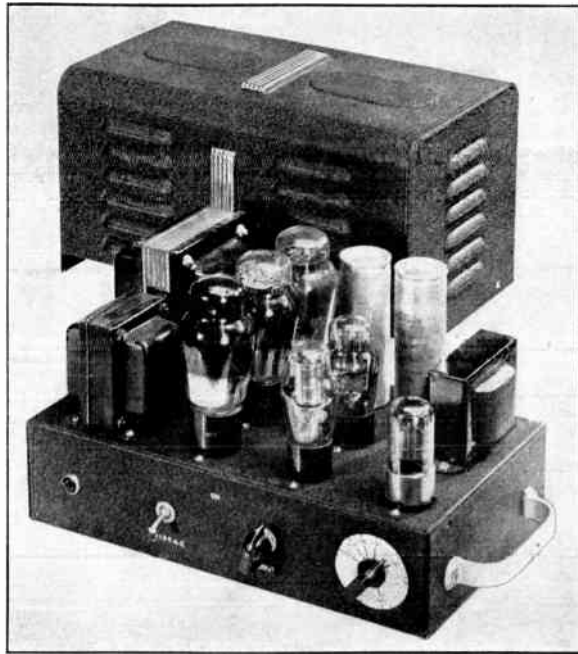

amperes is a safe value for the 2A3. Two or more regulator tubes may be connected in parallel to increase the current-carrying capacity, with no change in the circuit. A heavy-duty supply of this type is shown in Fig. 7-17 and the circuit is shown in Fig.

7-18. The unit is built on a 7 × 12 × 3-inch chassis. The transformers are to the left in Fig. 7-17. The 83 and 6B4Gs are immediately to the right followed by the 1-V, VR150 and the 6SJ7GT. Condensers C<sub>1</sub> and C<sub>2</sub> and the choke, L<sub>1</sub>, are placed along the rear edge.

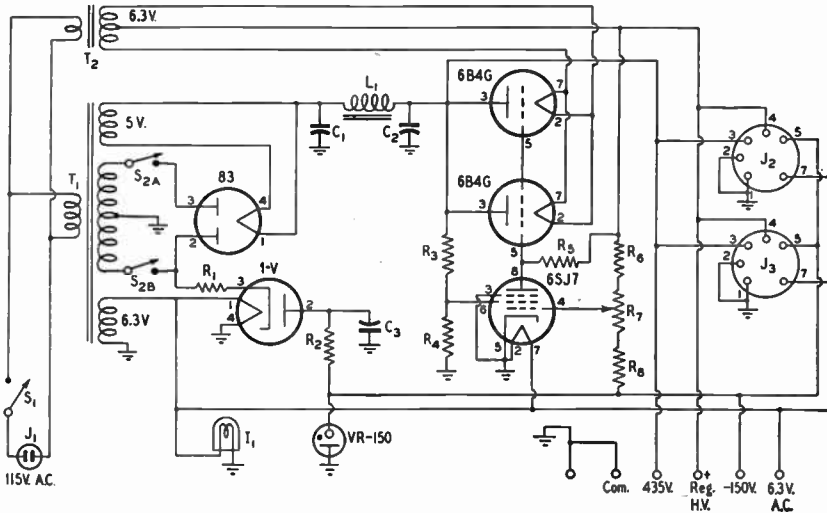


Fig. 7-18 — Circuit diagram of the heavy-duty regulated power supply.

- C<sub>1</sub>, C<sub>2</sub> — 8- $\mu$ fd. 600-volt electrolytic.
- C<sub>3</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- R<sub>1</sub> — 2500 ohms, 10 watts.
- R<sub>2</sub> — 7500 ohms, 10 watts.
- R<sub>3</sub> — 50,000 ohms, 10 watts.
- R<sub>4</sub> — 25,000 ohms, 2 watts.
- R<sub>5</sub> — 0.47 megohm,  $\frac{1}{2}$  watt.
- R<sub>6</sub> — 0.18 megohm,  $\frac{1}{2}$  watt.
- R<sub>7</sub> — 75,000-ohm potentiometer.
- R<sub>8</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.

- L<sub>1</sub> — 8-hy. 160-ma. 100-ohm filter choke.
- I<sub>1</sub> — 6.3-volt pilot lamp.
- J<sub>1</sub> — Panel-mounting a.c. plug (Amphenol 61 M1).
- J<sub>2</sub>, J<sub>3</sub> — Octal socket.
- S<sub>1</sub> — S.p.s.t. toggle switch.
- S<sub>2</sub> — 2-gang 2-position ceramic rotary switch.
- T<sub>1</sub> — Power transformer: 400 volts a.c. each side of center-tap, 160 ma.; 5 volts, 3 amp.; 6.3 volts, 6 amp.
- T<sub>2</sub> — 6.3-volt 2-amp. e.t. filament transformer.

Miscellaneous Power-Supply Circuits

Duplex Plate Supplies

In some cases it may be advantageous economically to obtain two plate-supply voltages from a single power supply, making one or more of the components serve a double purpose. Circuits of this type are shown in Figs. 7-19 and 7-20.

In Fig. 7-19, a bridge rectifier is used to obtain the full transformer voltage, while a connection is also brought out from the center-tap to obtain a second voltage corresponding to half the total transformer secondary voltage. The sum of the currents drawn from the two

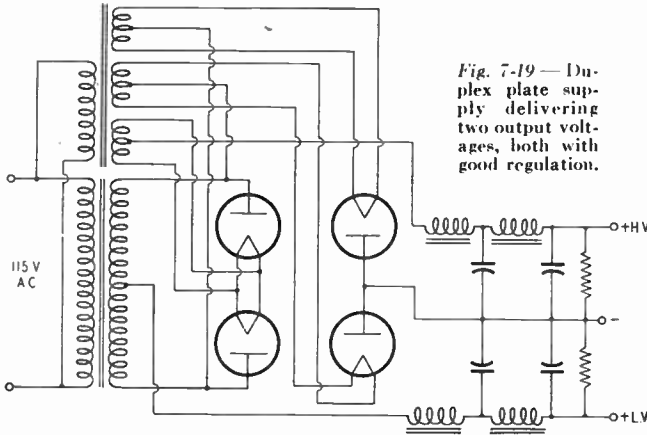


Fig. 7-19 — Duplex plate supply delivering two output voltages, both with good regulation.

taps should not exceed the d.c. ratings of the rectifier tubes and transformer. Filter values for each tap are computed separately.

Fig. 7-20 shows how a transformer with multiple secondary taps may be used to obtain both high and low voltages simultaneously. A separate full-wave rectifier is used at each pair of taps. The filter chokes are placed in the common negative lead, but separate filter condensers are required. The sum of the currents drawn from each pair of taps must not exceed the transformer rating, and the chokes must carry the total load current. Each bleeder should have a value in ohms 1000 times the maximum rated inductance in henrys of the swinging choke,  $L_1$ , for best regulation. A power supply of this type is shown in Figs. 7-21 and 7-22. In this case two sets of chokes are used to divide the load current.

Transformerless Plate Supplies

The line voltage is rectified directly, without a step-up power transformer, for certain applications (such as some types of receivers) where the low voltage so obtained is satisfactory. A simple power supply of this variety, often called the "a.c.-d.c." type, is shown in Fig. 7-23. Rectifier tubes for

this purpose have heaters operating at relatively high voltages (12.6, 25, 35, 45, 50, 70 or 115 volts), which can be connected across the a.c. line in series with other tube heaters and/or a resistor,  $R$ , of suitable value to limit the heater current to the rated value for the tubes.

The half-wave circuit shown has a fundamental ripple frequency equal to the line frequency and hence requires more inductance and capacitance in the filter for a given ripple percentage than the full-wave rectifier. A condenser-input filter generally is used. The input condenser should be at least 16  $\mu$ f. and preferably 32 or 40  $\mu$ f., to keep the output voltage high and to improve voltage regulation. Frequently a second filter section is required to provide additional smoothing.

No ground connection can be used on the power supply unless the grounded side of the power line is connected to the grounded side of the supply. Receivers using an a.c.-d.c. supply usually are grounded through a low-capacitance (0.05  $\mu$ f.) condenser, to avoid short-circuiting the line should the line plug be inserted in the socket the wrong way.

Voltage-Multiplier Circuits

Transformerless voltage-multiplier circuits make it possible to obtain d.c. voltages higher than the line voltage without using step-up transformers. By alternately charging two or more condensers to the peak line voltage and allowing them to discharge in series, the total output voltage becomes the sum of the voltages appearing across the individual condensers. The required switching operation is performed automatically by rectifiers associated with the condensers provided they are connected in the proper relationship.


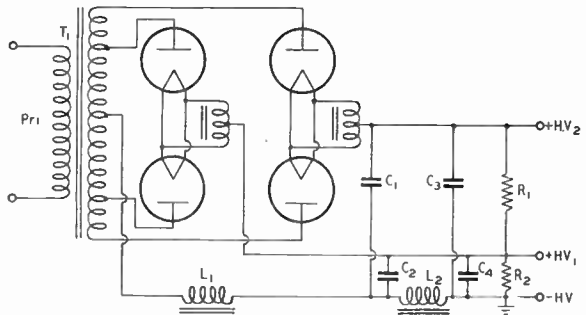


Fig. 7-20 — Power supply in which a single transformer and set of chokes serve for two different output voltages.

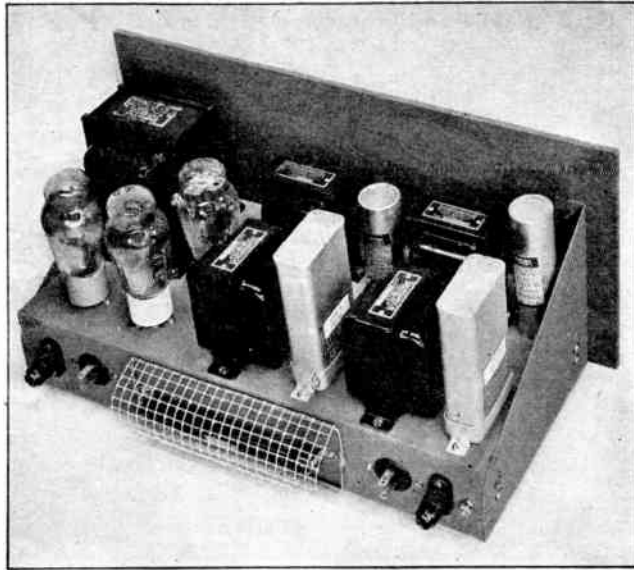

Fig. 7-21 — This power supply makes use of a combination transformer and a dual filter system, delivering 1000 volts at 125 ma. and 400 volts at 150 ma., or 400 volts and 750 volts simultaneously, depending upon the transformer selected. The circuit diagram is given in Fig. 7-22. The 1000-volt bleeder resistor is mounted on the rear edge of the chassis, with a protective guard made of a piece of galvanized fencing material to provide ventilation. Millen safety terminals are used for the two high-voltage terminals. Ceramic sockets should be used for the 866 Jrs. The chassis measures 8 × 17 × 3 inches and the standard rack panel is 8¾ inches high.



A half-wave voltage doubler is shown in Fig. 7-24A. In this circuit when the plate of the lower diode is positive the tube passes current, charging  $C_1$  to a voltage equal to the peak line voltage less the tube drop. When the

popular than the half-wave type. One diode charges  $C_1$  when the polarity between its plate and cathode is positive while the other section charges  $C_2$  when the line polarity reverses. Thus each condenser is charged separately to the same d.c. voltage, and the two discharge in series into the load circuit. The ripple frequency with the full-wave doubler is twice the line frequency. The voltage regulation is inherently poor and depends upon the capacitances of  $C_1$  and  $C_2$ , being better as these capacitances are made larger. A supply with 16  $\mu$ d. at  $C_1$  and  $C_2$  will have an output voltage of approximately 300 at light loads, as shown in Fig. 7-25.

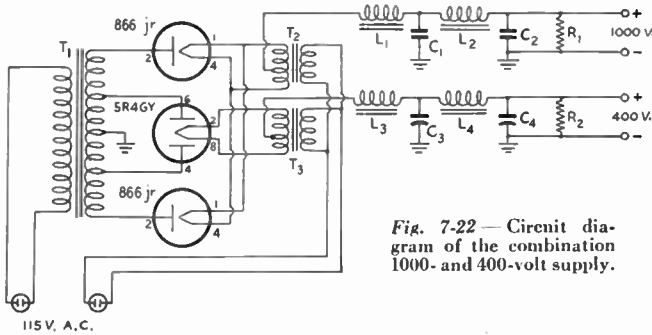


Fig. 7-22 — Circuit diagram of the combination 1000- and 400-volt supply.

- $C_1, C_2$  — 2- $\mu$ d. 1000-volt paper (Mallory TX805).
- $C_3$  — 4- $\mu$ d. 600-volt electrolytic (C-D 604).
- $C_4$  — 8- $\mu$ d. 600-volt electrolytic (C-D 608).
- $R_1$  — 20,000 ohms, 75 watts.
- $R_2$  — 20,000 ohms, 25 watts.
- $L_1, L_2$  — 5/20-hy. swinging choke, 150 ma. (Thordarson T-19C39).
- $L_3, L_4$  — 12-hy. smoothing choke, 150 ma. (Thordarson T-19C16).
- $T_1$  — High-voltage transformer, 1075 and 500 volts r.m.s. each side, 125- and 150-ma. simultaneous current rating (Thordarson T-19P57).
- $T_2$  — 2.5 volts, 5 amp. (Thordarson T-19F88).
- $T_3$  — 5 volts, 4 amp. (Thordarson T-63F99).

line polarity reverses at the end of the half-cycle the voltage resulting from the charge in  $C_1$  is added to the line voltage, the upper diode meanwhile similarly charging  $C_2$ .  $C_2$ , however, does not receive its full charge because it begins discharging into the load resistance as soon as the upper diode becomes conductive. For this reason, the output is somewhat less than twice the line peak voltage. As with any half-wave rectifier, the ripple frequency corresponds to the line frequency.

The full-wave voltage doubler at B is more

voltage, and the regulation is better than in other voltage-multiplier arrangements, as shown in Fig. 7-25.

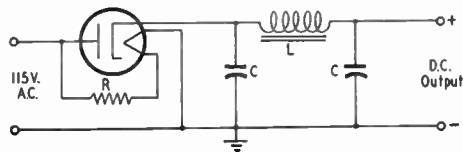


Fig. 7-23 — Transformerless plate supply with half-wave rectifier. Other heaters are connected in series with R.

Fig. 7-24D is a voltage quadrupler with two half-wave doublers connected in series, discharging the sum of the accumulated voltages in the associated condensers into the filter input. The quadrupler is by no means the ultimate limit in voltage multiplication. Practical power supplies have been built using up to twelve doubler stages in series.

Selenium rectifiers can be used in these circuits to arrive at a very compact and lightweight power unit for portable work.

In the circuits of Fig. 7-24,  $C_2$  should have a working voltage rating of 350 volts and  $C_1$  of 250 volts for a 115-volt line. Their capacitances

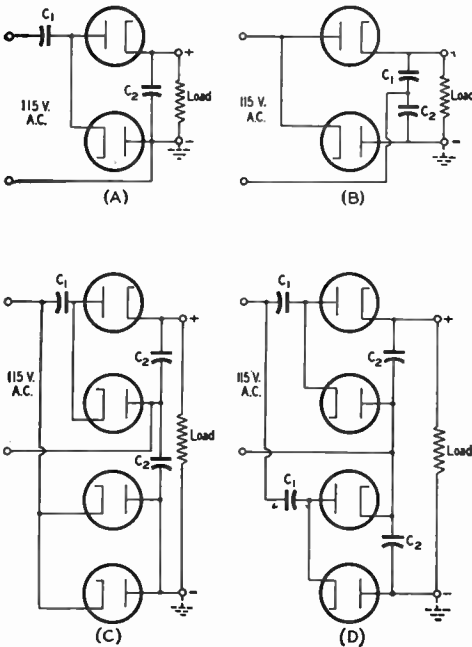


Fig. 7-24 — Voltage-multiplier circuits. A, half-wave voltage doubler. B, full-wave doubler. C, tripler. D, quadrupler. Dual-diode rectifier tubes may be used.

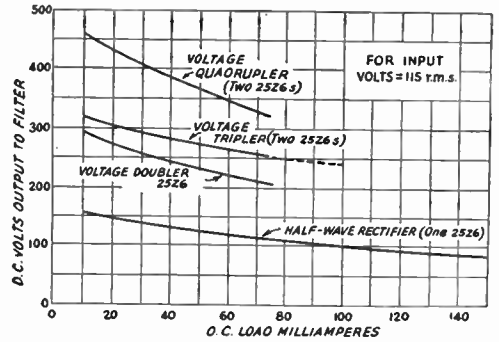


Fig. 7-25 — Curves showing the d.c. output voltage and the regulation under load for voltage-multiplier circuits.

should be at least 16  $\mu$ f. each. Subsequent filter condensers must, however, withstand the peak total output voltage — 450 volts in the case of the tripler and 600 for the quadrupler.

No direct ground can be used on any of these supplies or on associated equipment. If an r.f. ground is made through a condenser the capacitance should be small (0.05  $\mu$ f.), since it is in shunt from plate to cathode of one rectifier. In addition to the fact that care must be exercised in avoiding direct ground connection or observation of proper line polarization to prevent short-circuiting the power line, transformerless supplies frequently give rise to other difficulties. For this reason their application is recommended only where economy or space is a prime consideration. A regenerative receiver operating from a transformerless supply has a greater tendency toward "tunable hum" than when operating from a supply equipped with a transformer. Apparatus operating from a transformerless supply often is the source of a rough hum when a near-by broadcast receiver is tuned to a carrier. A line filter in the supply, or a switch of line polarization, when this is permissible, sometimes will eliminate trouble of this type, but sometimes only the use of a transformer will be effective.

## Bias Supplies

As discussed in Chapter Six, the chief function of a bias supply for the r.f. stages of a transmitter is that of providing protective bias, although under certain circumstances, a bias supply, or pack, as it is sometimes called, can provide the operating bias if desired.

### Simple Bias Packs

Fig. 7-26A shows the diagram of a simple bias supply.  $R_1$  should be the recommended grid leak for the amplifier tube. No grid leak should be used in the transmitter with this type of supply. The output voltage of the supply, when amplifier grid current is not flowing, should be some value between the bias required for plate-current cut-off and the recom-

mended operating bias for the amplifier tube. The transformer peak voltage (1.4 times the r.m.s. value) should not exceed the recommended operating-bias value, otherwise the output voltage of the pack will soar above the operating-bias value when rated grid current flows.

This soaring can be reduced to a considerable extent by the use of a voltage divider across the transformer secondary, as shown at B. Such a system can be used when the transformer voltage is higher than the operating-bias value. The tap on  $R_2$  should be adjusted to give amplifier cut-off bias at the output terminals. The lower the total value of  $R_2$ , the less the soaring will be when grid current flows.

A full-wave circuit is shown in Fig. 7-26C.  $R_3$  and  $R_4$  should have the same total resistance and the taps should be adjusted symmetrically. In all cases, the transformer must be designed to furnish the current drawn by these resistors plus the current drawn by  $R_1$ .

**Regulated Bias Supplies**

The inconvenience of the circuits shown in Fig. 7-26 and the difficulty of predicting values in practical application can be avoided in most cases by the use of gaseous voltage-regulator tubes across the output of the bias supply, as shown in Fig. 7-27A. A VR tube with a voltage rating anywhere between the biasing-voltage value which will reduce the input to the amplifier to a safe level when excitation is removed, and the operating value of bias, should be chosen.  $R_1$  is adjusted, without amplifier excitation, until the VR tube just ignites and draws about 5 ma. Any additional voltage to bring the bias up to the operating value when excitation is applied can be obtained from a grid leak, as discussed in Chapter Six. If the VR-tube voltage rating is the same as the required operating voltage, no grid leak need be used.

Each VR tube will handle 40 ma. of grid current. If the grid current exceeds this value under any condition, similar VR tubes should be added in parallel, as shown in Fig. 7-27B, for each 40 ma., or less, of additional grid current. The resistors  $R_2$  are for the purpose of helping to maintain equal currents through each VR tube.

If the voltage rating of a single VR tube is not sufficiently high for the purpose, other VR tubes may be used in series (or series-parallel if required to satisfy grid-current requirements) as shown in Fig. 7-27C and D.

If a single value of fixed bias will serve for more than one stage, the biasing terminal of each such stage may be connected to a single supply of this type, provided only that the total grid current of all stages so connected does not exceed the current rating of the VR tube or tubes. Alternatively, other separate VR-tube branches may be added in any desired combination to the same supply, as shown in Fig. 7-27E, to suit the requirements of each stage.

Providing the VR-tube current rating is not exceeded, a series arrangement may be tapped for lower voltage, as shown at F.

**Other Sources of Biasing Voltage**

In some cases, it may be convenient to obtain the biasing voltage from a source other than a separate supply. A half-wave rectifier may be connected with reversed polarization to obtain biasing voltage from a low-voltage plate supply, as shown in Fig. 7-28A. In another arrangement, shown at B, a spare filament winding can be used to operate a filament transformer of similar voltage rating in reverse to obtain a voltage of about 130 from the

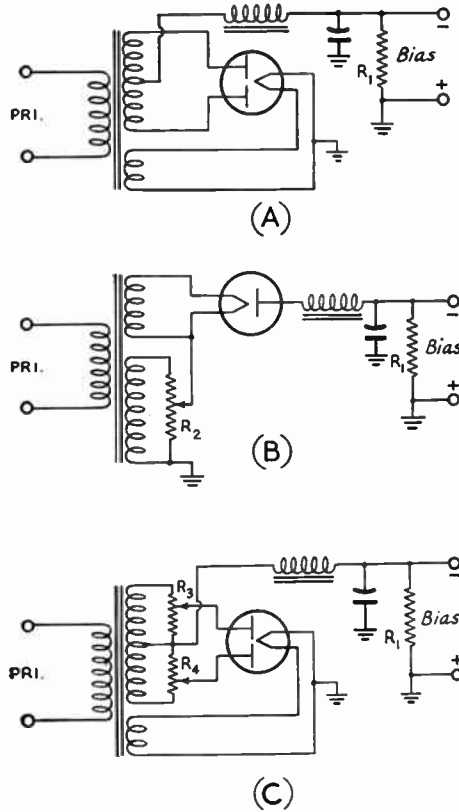


Fig. 7-26 — Simple bias-supply circuits. In A, the peak transformer voltage must not exceed the operating value of bias. The circuits of B (half-wave) and C (full-wave) may be used to reduce transformer voltage to the rectifier.  $R_1$  is the recommended grid-leak resistance.

winding that is customarily the primary. This will be sufficient to operate a VR75 or VR90. If a selenium rectifier is used, no additional filament voltage for the bias rectifier is needed.

A bias supply of any of the types discussed requires relatively little filtering, if the peak output-terminal voltage does not approach the operating-bias value, because the effect of the supply is entirely or largely "washed out" when grid current flows.

● **FILAMENT SUPPLY**

Except for tubes designed for battery operation, the filaments or heaters of vacuum tubes used in both transmitters and receivers are universally operated on alternating current obtained from the power line through a step-down transformer delivering a secondary voltage equal to the rated voltage of the tubes used. The transformer should be designed to carry the current taken by the number of tubes which may be connected in parallel across it. The filament or heater transformer generally is center-tapped, to provide a balanced circuit for eliminating hum.

For medium- and high-power r.f. stages of

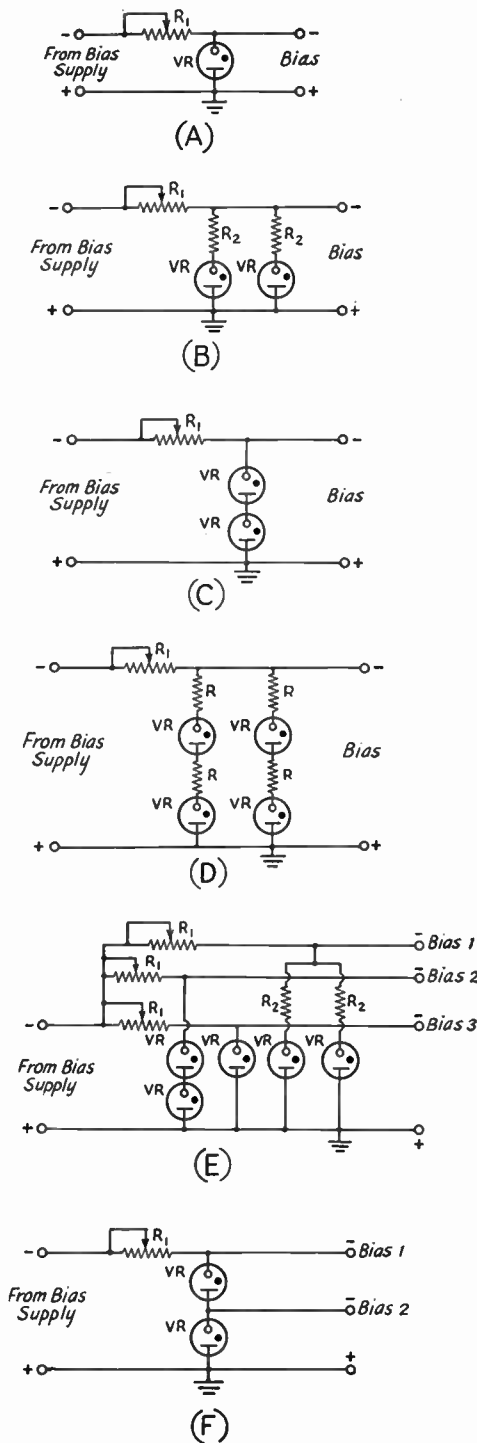


Fig. 7-27 — Illustrating the use of VR tubes in stabilizing protective-bias supplies.  $R_1$  is a resistor whose value is adjusted to limit the current through each VR tube to 5 ma. before amplifier excitation is applied.  $R$  and  $R_2$  are current-equalizing resistors of 50 to 100 ohms.

transmitters, and for high-power audio stages, it is desirable to use a separate filament transformer for each section of the transmitter, installed near the tube sockets. This avoids the necessity for abnormally large wires to carry the total filament current for all stages without appreciable voltage drop. Maintenance of rated filament voltage is highly important, especially with thoriated-filament tubes, since under- or over-voltage may reduce filament life.

● LINE-VOLTAGE ADJUSTMENT

In certain communities trouble is sometimes experienced from fluctuations in line voltage. Usually these fluctuations are caused by a variation in the load on the line and, since most of the variation comes at certain fixed times of the day or night, such as the times when lights are turned on and off at evening, they may be taken care of by the use of a manually-operated compensating device. A simple arrangement is shown in Fig. 7-29A. A toy transformer is used to boost or buck the line voltage as required. The transformer should have a tapped secondary varying between 6 and 20 volts in steps of 2 or 3 volts and its secondary should be capable of carrying the full load current of the entire transmitter, or that portion of it fed by the toy transformer.

The secondary is connected in series with the line voltage and, if the phasing of the windings is correct, the voltage applied to the primaries of the transmitter transformers can be brought up to the rated 115 volts by setting the toy-transformer tap switch on the right tap. If the phasing of the two windings of the toy transformer happens to be reversed, the voltage will be reduced instead of increased. This connection may be used in cases where the line voltage may be above 115 volts. This method is preferable to using a resistor in the primary of a power transformer since it does not affect the voltage regulation as seriously. The circuit of 7-29B illustrates the use of a variable transformer (Variac) for adjusting line voltage to the desired value.

Another scheme by which the primary voltage of each transformer in the transmitter may be adjusted to deliver the desired secondary voltage, with a master control for compensating for changes in line voltage, is described in Fig. 7-30.

This arrangement has the following features:

1) Adjustment of the switch  $S_1$  to make the voltmeter read 105 volts automatically adjusts all transformer primaries to the predetermined correct voltage.

2) The necessity for having all primaries work at the same voltage is eliminated. Thus, 110 volts can be applied to the primary of one transformer, 115 to another, etc.

3) Independent control of the plate transformer is afforded by the tap switch  $S_2$ . This permits power-input control and does not require an extra autotransformer.

● CONSTRUCTION OF POWER SUPPLIES

The length of most leads in a power supply is unimportant so that the arrangement of components from this consideration is not a factor in construction. More important are the points of good high-voltage insulation, adequate conductor size for filament wiring, proper ventilation for rectifier tubes and — most important of all — safety to the operator. Exposed high-voltage terminals or wiring which might be bumped into accidentally should not be permitted to exist. They should be covered

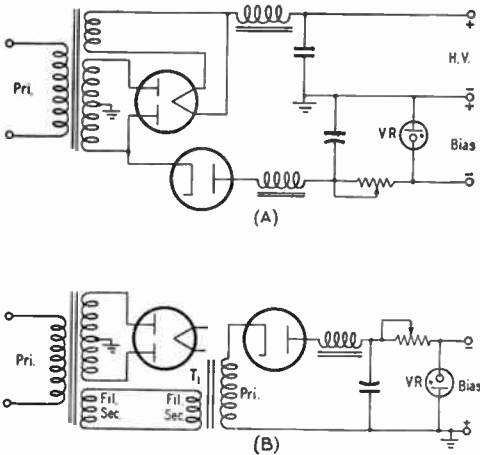


Fig. 7-28 — Convenient means of obtaining biasing voltage. A — From a low-voltage plate supply. B — From spare filament winding.  $T_1$  is a filament transformer, of a voltage output similar to that of the spare filament winding, connected in reverse to give 115 volts r.m.s. output. If cold-cathode or selenium rectifiers are used, no additional filament supply is required.

with adequate insulation or placed inaccessible to contact during normal operation and adjustment of the transmitter.

Rectifier filament leads should be kept short to assure proper voltage at the rectifier socket, and the sockets should have good insulation and adequate contact surface. Plate leads to mercury-vapor tubes should be kept short to minimize the radiation of noise.

Where high-voltage wiring must pass through a metal chassis, grommet-lined clearance holes will serve for voltages up to 500 or 750, but ceramic feed-through insulators should be used for higher voltages. Bleeder and voltage-dropping resistors should be placed where they are open to air circulation. Placing them in confined space reduces the power rating.

It is highly preferable from the standpoint of operating convenience to have separate filament transformers for the rectifier tubes, rather than to use combination transformers, such as those used in receivers. This permits the plate voltage to be switched on without the

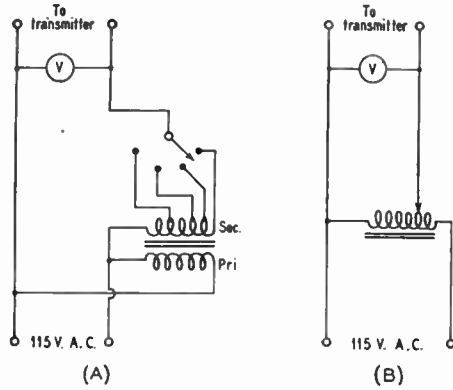


Fig. 7-29 — Two methods of transformer primary control. At A is a tapped toy transformer which may be connected so as to boost or buck the line voltage as required. At B is indicated a variable transformer or autotransformer (Variac) in series with the transformer primaries.

necessity for waiting for rectifier filaments to come up to temperature after each time the high voltage has been turned off.

A bleeder resistor with a power rating giving a considerable margin of safety should be used across the output of all transmitter power supplies so that the filter condensers will be discharged when the high-voltage transformer is turned off. To guard against the possibility of danger to the operator should the bleeder resistor burn out without his knowledge, a relay with its winding connected in parallel with the high-voltage transformer primary and its contacts in series with a 1000-ohm resistor across the output of the power supply sometimes is used. The relay should be arranged so that the contacts open when the relay is energized.

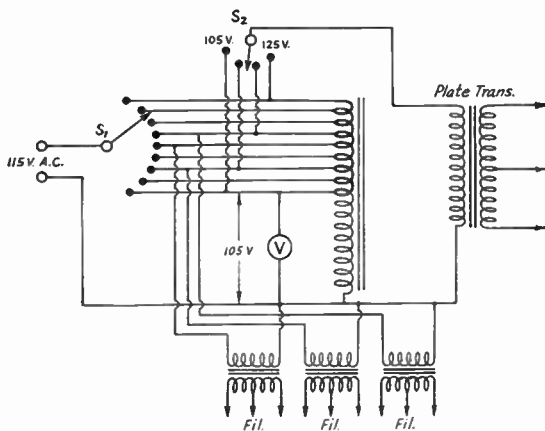


Fig. 7-30 — With this circuit, a single adjustment of the tap switch  $S_1$  places the correct primary voltage on all transformers in the transmitter. Information on constructing a suitable autotransformer at negligible cost is contained in the text. The light winding represents the regular primary winding of a revamped transformer, the heavy winding the voltage-adjusting section.

## Control Systems

A well-planned system of controlling power-supply equipment is not only a matter of safety to the operator but also a factor in the convenient and efficient operation of the station while on the air.

The diagrams of power supplies suggested for use with transmitters described in Chapter

Six include a suitable control system for each. In general principle they are the same, varying only in the details of special considerations for the specific case at hand.

As a minimum, except possibly in the case of simple transmitters employing a single power supply, there should be a filament switch that controls simultaneously all filaments in the power supplies as well as in the transmitter. This switch sometimes also controls the bias supply if one is used. There should be a separate switch for each plate-voltage supply and one that controls all plate supplies simultaneously. This latter switch is the "stand-by" switch by which power to the transmitter may be turned off quickly during receiving periods. The switches should be arranged in series, so that the plate voltage cannot be applied before filament and bias voltages have been turned on.

Figs. 7-31 and 7-32 show a complete control system for a multistage c.w. and 'phone transmitter. Indicator lamps, proper line fusing and automatic protective features are included. These circuits are more or less basic and will cover all requirements of most transmitters. They are similar except that the circuit of Fig. 7-31 is for use with a 115-volt line, while that of Fig. 7-32 is suitable for a 3-wire 220-volt line.

The system starts out with a polarized plug,  $P_1$ , for the line connection. The side of the line indicated should be the grounded side. One or more utility outlets which are not affected by the switching may be connected at  $J_1$ . The line-fuse indicator lamp,  $I_1$ , should not light unless the line fuse,  $F_1$ , is blown.

Turning on  $S_1$  at the transmitter or  $S_2$  at the operating position turns on all r.f. and r.f. power-supply filament transformers, which are connected in parallel at  $T_1$ , and the indicator lamp,  $I_2$ , lights. If the 'phone-c.w. switch,  $S_3$ , is thrown to the 'phone position, all audio and a.f.-supply filament transformers, which are connected in parallel at  $T_2$ , will also be turned on by  $S_1$  and the 'phone indicator lamp,  $I_3$ , will light. If  $S_3$  is in the c.w. position, the c.w. indicator lamp,  $I_4$ , will light, and the a.f. power supplies will be cut off.  $S_{3B}$  short-circuits the modulation-transformer secondary.

If the safety interlock switch,  $S_4$ , is closed, the bias-supply plate and filament voltages ( $T_3$ ) will be turned on. As soon as the rectifier of this supply (an indirectly-heated rectifier such as a 6X5G) warms up, and the supply delivers full voltage, the delay relay,  $Ry_2$ , will close, extinguishing the bias-indicator lamp,  $I_7$ , and setting up the circuit for the plate-supply relay,  $Ry_3$ . The time which the bias rectifier takes to come up to temperature provides the required delay between the application of filament voltage and the time when it becomes possible to turn on the plate voltages on the r.f. and a.f. tubes.

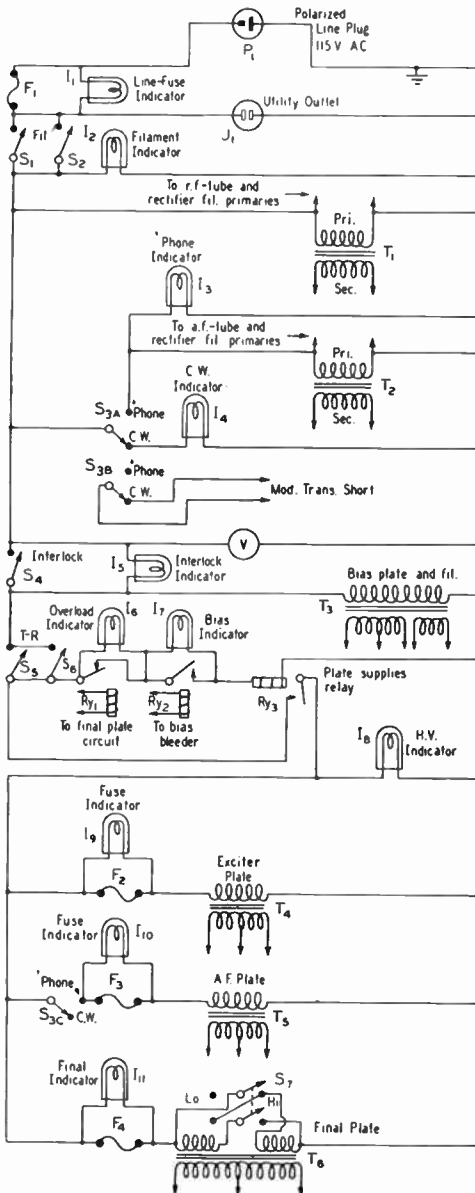


Fig. 7-31 — 115-volt control circuit used at W4DCW. All switches, except  $S_3$ , may be 5 amp.  $S_3$  should be a ceramic rotary switch. The indicator lamps are  $\frac{5}{8}$ -in. panel type.

With the contacts of  $Ry_2$  closed, the plate-supply relay,  $Ry_3$ , can be operated by closing the transmit-receive switch,  $S_5$ , or its extension,  $S_6$ , at the operating position.  $Ry_3$  turns on all plate voltages, lights the high-voltage indicator,  $I_8$ , and the transmitter is ready for operation.

Should the interlock switch  $S_4$  be open, the indicator lamp,  $I_5$ , will light. This lamp, in series with the primary of the bias-supply transformer, has sufficient resistance to prevent lighting of the rectifier filament and thus voltage output from the bias pack, and therefore  $Ry_2$  does not close so that  $Ry_3$  cannot be operated and high voltage cannot be applied, making the transmitter safe so long as the interlock switch is open.

$Ry_1$  is an overload breaker which breaks off the line to the plate-supply relay whenever the plate current to the final amplifier exceeds a value to which it has been set. The winding of this relay is in the filament center-tap of the final-amplifier tubes. It should be of the reset type so that it will not continue to close and open repeatedly until  $S_5$  is opened as it would do if it were not of the reset type.  $I_9$ ,  $I_{10}$  and  $I_{11}$  are fuse-indicator lamps which light when their associated fuses blow.  $S_7$  is a switch for changing to low power for tune-up. This system is, of course, applicable only to transformers with dual primaries. With single-primary transformers a switch can be arranged to short-circuit a 150- to 200-watt lamp connected in series with the primary winding for reducing power.

The only switch which need be thrown for stand-by is  $S_5$ . Only  $S_3$  need be thrown in changing from 'phone to c.w. No other switching is necessary.

The only difference in Fig. 7-32 is that the filament and bias transformers are operated from one side of the line, while the plate supplies are operated from the other. This connection is preferable whenever it can be applied, since it helps to equalize the loads drawn from each side of a 3-wire line. For high power, or in cases where light blinking is experienced, the plate transformer,  $T_6$ , should have a 220-volt primary connected to the two outside wires.

All indicator lamps and panel switches should be marked plainly so that there will be no question as to which circuit each belongs, to facilitate switching and localizing of trouble.

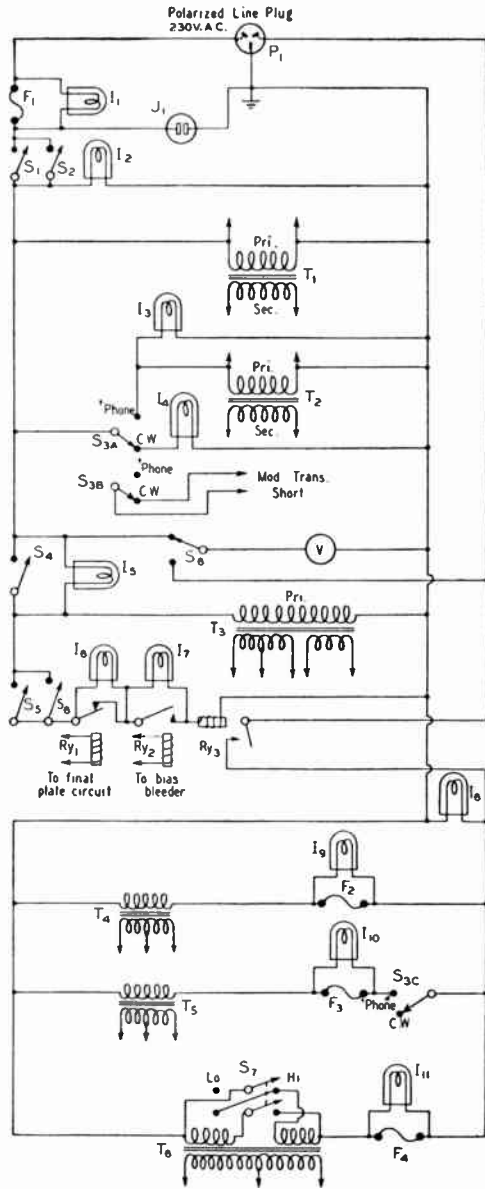


Fig. 7-32 — 230-volt control circuit.  $Ry_1$  is an overload type,  $Ry_2$  is a light-current relay and  $Ry_3$  is a 115-volt a.c. relay with heavy contacts.

## Emergency and Independent Power Sources

Emergency power supply which operates independently of a.c. lines is available, or can be built in a number of different forms, depending upon the requirements of the service for which it is intended.

The most practical supply for the average individual amateur is one that operates from a 6-volt car storage battery. Such a supply may take the form of a small motor generator

(often called a genemotor), a rotary converter or a vibrator-transformer-rectifier combination.

### Dynamotors

A dynamotor differs from a motor generator in that it is a single unit having a double armature winding. One winding serves for the driving motor, while the output voltage is taken from the other. Dynamotors usually are

TABLE 7-III—DYNAMOTORS

Manufacturer's Type No.			Input		Output		Weight
Carrier	Eicor	Duty	Volts	Amp.	Volts	Ma.	Lb.
210A		Continuous	6	6.1	200	100	7
	3412 <sup>1</sup>		6	4.2	200	100	4 $\frac{5}{8}$
	3415 <sup>1</sup>		6	6.1-9.7	200-300	100	5
MA250		Continuous	6	4.2	250	50	4 $\frac{3}{4}$
251A		Continuous	6	7.9	250	100	7
MA301		Continuous	6	9.0	300	100	4 $\frac{3}{4}$
315A			6	13.4	300	150	7 $\frac{7}{8}$
320A			6	18.2	300	200	9 $\frac{1}{2}$
	3420 <sup>1</sup>			18.2	300	200	
					15.0	350	150
41520 <sup>1</sup>			6	31.0	400	300	
				40.0	600	250	7 $\frac{7}{8}$
351A			6	10	350	100	6 $\frac{1}{2}$
MAS355		Intermittent	6	15	350	150	4 $\frac{3}{4}$
352AR			6	22	350	200	9 $\frac{1}{2}$
401A			6	13	400	100	7 $\frac{7}{8}$
			6	14.2	400	125	9 $\frac{1}{4}$
415A		Continuous	6	18.2	400	150	8
420A		Continuous	6	23.4	400	200	10
425A			6	30	400	225	9 $\frac{1}{2}$
AF450		Continuous	6	27	400	250	13
AF430		Continuous	6	31	400	300	13
520AS		Intermittent	6	28	500	200	10
650AS		Intermittent	6	39	600	250	10
VSF630		Intermittent	5.5	56	600	300	13

<sup>1</sup> Characteristics are typical for frame size given.

operated from 6-, 12-, 28- or 32-volt storage batteries and deliver from 300 to 1000 volts or more at various current ratings.

Genemotor is a term popularly used when making reference to a dynamotor designed especially for automobile-receiver, sound-truck and similar applications. It has good regulation and efficiency, combined with economy of operation. Standard models of genemotors have ratings ranging from 135 volts at 30 ma. to 300 volts at 200 ma. or 600 volts at 300 ma. (See Table 7-III.) The normal efficiency averages around 50 per cent, increasing to better than 60 per cent in the higher-power units. The voltage regulation of a genemotor is comparable to that of well-designed a.c. supplies.

Successful operation of dynamotors and genemotors requires heavy, direct leads, mechanical isolation to reduce vibration, and thorough r.f. and ripple filtration. The shafts and bearings should be thoroughly "run in" before regular operation is attempted, and thereafter the tension of the bearings should be checked occasionally to make certain that no looseness has developed.

In mounting the genemotor, the support should be in the form of rubber mounting blocks, or equivalent, to prevent the transmission of vibration mechanically. The frame of the genemotor should be grounded through a heavy flexible connector. The brushes on the high-voltage end of the shaft should be bypassed with 0.002- $\mu$ fd. mica condensers to a common point on the genemotor frame, preferably to a point inside the end cover close to the brush holders. Short leads are essential.

It may prove desirable to shield the entire unit, or even to remove the unit to a distance of three or four feet from the receiver and antenna lead.

When the genemotor is used for receiving, a filter should be used similar to that described for vibrator supplies. A 0.01- $\mu$ fd. 600-volt (d.c.) paper condenser should be connected in shunt across the output of the genemotor, followed by a 2.5-mh. r.f. choke in the positive high-voltage lead. From this point the output should be run to the receiver power terminals through a smoothing filter using 4- to 8- $\mu$ fd. condensers and a 15- or 30-henry choke having low d.c. resistance.

#### A.C.-D.C. Converters

In some instances it is desirable to utilize existing equipment built for 115-volt a.c. operation. To operate such equipment with any of the power sources outlined above would require a considerable amount of rebuilding. This can be obviated by using a rotary converter capable of changing the d.c. from 6-, 12- or 32-volt batteries to 115-volt 60-cycle a.c. Such converter units are built to deliver outputs ranging from 40 to 300 watts, depending upon the battery power available.

The conversion efficiency of these units averages about 50 per cent. In appearance and operation they are similar to genemotors of equivalent rating. The over-all efficiency of the converter will be lower, however, because of losses in the a.c. rectifier-filter circuits and the necessity for converting heater (which is supplied directly from the battery in the case of the genemotor) as well as plate power.



Vibrator Power Supplies

The vibrator type of power supply consists of a special step-up transformer combined with a vibrating interrupter (*vibrator*). When the unit is connected to a storage battery, plate power is obtained by passing current from the battery through the primary of the transformer. The circuit is made and reversed rapidly by the vibrator contacts, interrupting the current at regular intervals to give a changing magnetic field which induces a voltage in the secondary. The resulting square-wave d.c. pulses in the primary of the transformer cause an alternating voltage to be developed in the secondary. This high-voltage a.c. in turn is rectified, either by a vacuum-tube rectifier or by an additional synchronized pair of vibrator contacts. The rectified output is pulsating d.c., which may be filtered by ordinary means. The smoothing filter can be a single-section affair, but the filter output capacitance should be fairly large — 16 to 32  $\mu\text{fd}$ .

Fig. 7-33 shows the two types of circuits. At A is shown the *nonsynchronous* type of vibrator. When the battery is disconnected the reed is midway between the two contacts, touching neither. On closing the battery circuit the magnet coil pulls the reed into contact with one contact point, causing current to flow through the lower half of the transformer primary winding. Simultaneously, the magnet coil is short-circuited, deenergizing it, and the reed swings back. Inertia carries the reed into contact with the upper point, causing current to flow through the upper half of the transformer primary. The magnet coil again is energized, and the cycle repeats itself.

The synchronous circuit of Fig. 7-33B is provided with an extra pair of contacts which rectify the secondary output of the transformer, thus eliminating the need for a separate rectifier tube. The secondary center-tap furnishes the positive output terminal when the relative polarities of primary and secondary windings are correct. The proper connections may be determined by experiment.

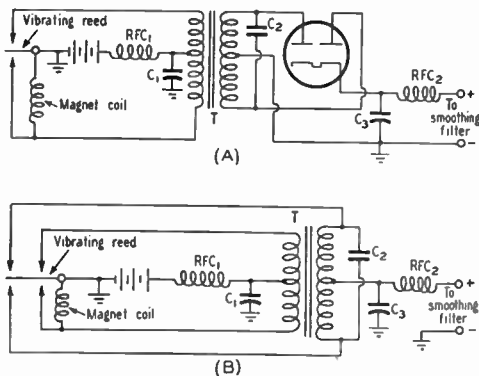


Fig. 7-33 — Basic types of vibrator power-supply circuits. A—Nonsynchronous, B—Synchronous.

The buffer condenser,  $C_2$ , across the transformer secondary absorbs the surges that occur on breaking the current, when the magnetic field collapses practically instantaneously and hence causes very high voltages to be induced in the secondary. Without this condenser excessive sparking occurs at the vibrator contacts, shortening the vibrator life. Correct values usually lie between 0.005 and 0.03  $\mu\text{fd}$ ., and for 250–300-volt supplies the condenser

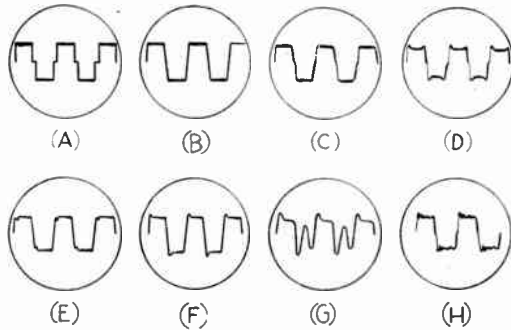


Fig. 7-34 — Characteristic vibrator waveforms as viewed on the oscilloscope. A, ideal theoretical trace for resistive load; current flow stops instantly when vibrator contacts open and resumes approximately 1 microsecond later (for standard 115-cycle vibration frequency) after interrupter arm moves across for the next half-cycle. B, ideal practical waveform for inductive load (transformer primary) with correct buffer capacitance. C, practical approximation of B for loaded nonsynchronous vibrator. D, satisfactory practical trace for synchronous (self-rectifying) vibrator under load; the peaks result from voltage drop in the primary when the secondary load is connected, not from faulty operation.

Faulty operation is indicated in E through H: E, effect of insufficient buffering capacitance (not to be mistaken for "bouncing" of contacts). The opposite condition — excessive buffering capacitance — is indicated by slow build-up with rounded corners, especially on "open." F, overclosure caused by too-small buffer condenser (same condition as in E) with vibrator unloaded. G, "skipping" of worn-out or misadjusted vibrator, with interrupter making poor contact on one side. H, "bouncing" resulting from worn-out contacts or sluggish reed. G and H usually call for replacement of the vibrator.

should be rated at 1500 to 2000 volts d.c. The exact capacitance is critical, and should be determined experimentally. The optimum value is that which results in least battery current for a given rectified d.c. output from the supply. In practice the value can be determined by observing the degree of vibrator sparking as the capacitance is changed. When the system is operating properly there should be practically no sparking at the vibrator contacts. A 5000-ohm resistor in series with  $C_2$  will limit the secondary current to a safe value should the condenser fail.

A more exact check on the operation can be secured with an oscilloscope having a linear sweep circuit that can be synchronized with the vibrator. The vertical plates should be connected across the outside ends of the transformer primary winding to show the input voltage waveshape. Fig. 7-34C shows an idealized trace of the optimum waveform when the

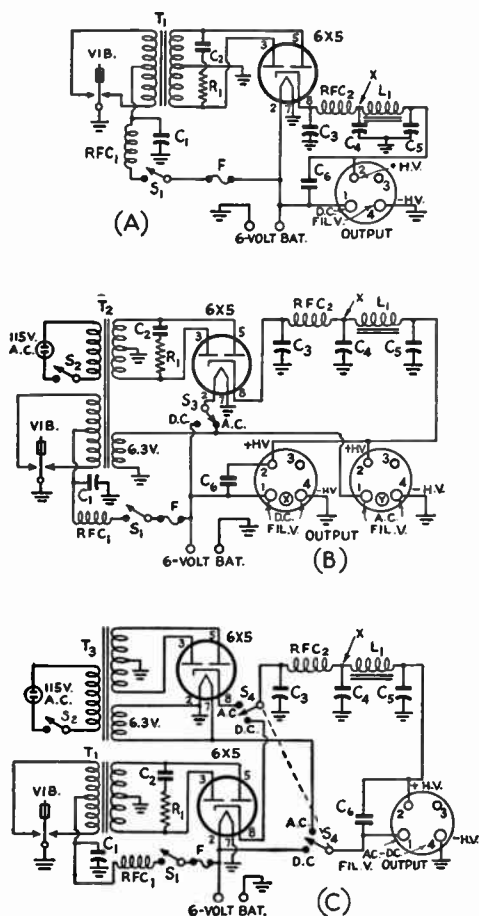


Fig. 7-35 — Typical vibrator-transformer power-supply circuits. The circuit at A shows a simple arrangement for 6-volt d.c. input; the one at B illustrates the use of a combination transformer for operation from either 6 volts d.c. or 115 volts a.c. The circuit of C is similar to that of B but uses separate transformers.

C<sub>1</sub> — 0.5- $\mu$ fd. paper, 50-volt rating or higher.

C<sub>2</sub> — 0.005 to 0.01  $\mu$ fd., 1600 volts.

C<sub>3</sub> — 0.01- $\mu$ fd. 600-volt paper.

C<sub>4</sub> — 8- $\mu$ fd. 450-volt electrolytic.

C<sub>5</sub> — 32- $\mu$ fd. 450-volt electrolytic.

C<sub>6</sub> — 100- $\mu$ fd. mica.

R<sub>1</sub> — 4700 ohms,  $\frac{1}{2}$  or 1 watt.

L<sub>1</sub> — 10–12-henry 100-ma. filter choke, not over 100 ohms (Stancor C-2303 or equivalent).

F — 15-ampere fuse.

RFC<sub>1</sub> — 55 turns No. 12 on 1-inch form, close-wound.

RFC<sub>2</sub> — 2.5-mh. r.f. choke.

S<sub>1</sub> — S.p.s.t. toggle — battery switch.

S<sub>2</sub> — S.p.s.t. toggle — a.c. power switch.

S<sub>3</sub> — S.p.d.t. toggle — rectifier-heater change-over switch.

S<sub>4</sub> — D.p.d.t. toggle — a.c.-d.c. switch.

T<sub>1</sub> — Vibrator transformer.

T<sub>2</sub> — Special vibrator transformer with 115-volt and 6-volt primaries, to give approximately 300 volts at 100 ma. d.c. (Stancor P-6166 or equivalent).

T<sub>3</sub> — A.c. transformer, 275 to 300 volts each side of center-tap, 100 to 150 ma.; 6.3-volt filament.

VIB — Vibrator unit (Mallory 500P, 294, etc.)

X — Insert a series resistor of suitable value to drop the output voltage to 300 at 100 ma. load, if necessary. If transformer gives over 300 volts d.c., a second filter choke may be used to give additional voltage drop as well as more smoothing.

buffer capacitor is adjusted to give proper operation throughout the life of the vibrator. The horizontal lines in the trace represent the voltage during the time the vibrator contacts are closed, which should be approximately 90 per cent of the total time. When the contacts are open the trace should be partly tilted and partly vertical, the tilted part being 60 per cent of the total connecting trace. The oscilloscope will show readily the effect of the buffer condenser on the percentage of tilt. In actual patterns the horizontal sections are likely to droop somewhat because of the resistance drop in the battery leads as the current builds up through the primary inductance (Fig. 7-34D).

### "Hash" Elimination

Sparking at the vibrator contacts causes r.f. interference ("hash," which can be distinguished from hum by its harsh, sharper pitch) when used with a receiver. To minimize this, r.f. filters are incorporated, consisting of RFC<sub>1</sub> and C<sub>1</sub> in the battery circuit, and RFC<sub>2</sub> with C<sub>3</sub> in the d.c. output circuit.

Equally as important as the hash filter is thorough shielding of the power supply and its connecting leads, since even a small piece of wire or metal will radiate enough r.f. to cause interference in a sensitive receiver.

Testing in connection with hash elimination should be carried out with the supply operating a receiver. Since the interference usually is picked up on the receiving antenna leads by radiation from the supply itself and from the battery leads, it is advisable to keep the supply and battery as far from the receiver as the connecting cables will permit. Three or four feet should be ample. The microphone cord likewise should be kept away from the supply and leads.

The power supply should be built on a metal chassis, with all unshielded parts underneath. A bottom plate to complete the shielding is advisable. The transformer case, vibrator cover and the metal shell of the tube all should be grounded to the chassis. If a glass tube is used it should be enclosed in a tube shield. The battery leads should be evenly twisted, since these leads are more likely to radiate hash than any other part of a well-shielded supply. Experimenting with different values in the hash filters should come *after* radiation from the battery leads has been reduced to a minimum. Shielding the leads is not particularly helpful.

### ● PRACTICAL VIBRATOR-SUPPLY CIRCUITS

A vibrator-type power supply may be designed to operate from a six-volt storage battery only, or in a combination unit which may be operated interchangeably from either battery or 115 volts a.c.

Typical circuits are shown in Fig. 7-35. The one shown at A is the simplest, although it operates from a 6-volt d.c. source only. S<sub>1</sub> turns the high voltage on and off.

The circuit of B provides for either 6-volt d.c. or 115-volt a.c. operation with a dual-primary transformer.  $S_2$  is the a.c. on-off switch while  $S_3$  switches the heater of the 6X5 rectifier from the storage battery to the 6.3-volt winding on the transformer. Filament supply for the transmitter or receiver is switched by shifting the power plug to the correct output socket, X when operating from a 6-volt d.c. source and Y when 115-volt a.c. input is used.

The circuit of Fig. 7-35C may be used when a dual-primary transformer is not available. The filter is switched from one rectifier output to the other by means of the d.p.d.t. switch,  $S_4$ , which also shifts filament connections from a.c. to d.c. The filter section of the switch could be eliminated if desired by connecting the filtering circuit permanently to the output terminals of both rectifiers and removing the unused rectifier tube from its socket. Similarly, the filament section of  $S_4$  could be dispensed with by providing two output sockets as in the circuit at B. If a separate rectifier filament winding is available on  $T_3$ , directly-heated rectifier types may be substituted for the 6X5 in the a.c. supply. In some cases where the required filament windings are not available, a rectifier of the cold-cathode type, such as the OZ4, which requires no heater voltage, sometimes may be used to advantage.

If suitable filament windings are available, a regular a.c. transformer will make an acceptable substitute for a vibrator transformer. If the a.c. transformer has two 6.3-volt windings, they may be connected in series, their junction forming the required center-tap. A 6.3-volt and a 5-volt winding may be used in a similar manner even though the junction of the two

windings does not provide an accurate center-tap. A better center-tap may be obtained if a 2.5-volt winding also is available, since half of this winding may be connected in series with the 5-volt winding to give 6.25 volts.

R.f. filters for reducing hash are incorporated in both primary and secondary circuits. The secondary filter consists of a 0.01- $\mu$ fd. paper condenser directly across the rectifier output, with a 2.5-mh. r.f. choke in series ahead of the smoothing filter. In the primary circuit a low-inductance choke and high-capacitance condenser are needed because of the low impedance of the circuit. A choke of the specifications given should be adequate, but if there is trouble with hash it may be beneficial to experiment with other sizes. The wire should be large — No. 12, preferably, or No. 14 as a minimum. Manufactured chokes such as the Mallory RF583 are more compact and give higher inductance for a given resistance because they are bank-wound, and may be substituted if obtainable.  $C_1$  should be at least 0.5  $\mu$ fd.; even more capacitance may help in bad cases of hash.

The smoothing filter for battery operation can be a single-section affair, but there will be some hum (readily distinguishable from hash because of its deeper pitch) unless the filter output capacitance is fairly large — 16 to 32  $\mu$ fd.

The compactness of selenium rectifiers and the fact that they do not require filament voltage make them particularly suited to compact light-weight power supplies for portable-emergency work.

Fig. 7-36 shows the circuit of a vibrator pack which will deliver an output voltage of 400 at 200 ma. It will work with either 115-volt a.c. or 6-volt battery input. The circuit is that of the familiar voltage tripler whose d.c. output voltage is as a rough approximation, three times the peak voltage delivered by the transformer or line. An interesting feature of the circuit is the fact that the single transformer serves as the vibrator transformer when operating from 6-volt d.c. supply and as the filament transformer when operating from an a.c. line. This is accomplished without complicated switching.

The vibrator transformer,  $T_1$ , is a dual-secondary 6.3-volt filament transformer connected in reverse. It may also consist of two single transformers of the same type with their primaries connected in series and secondaries in parallel, both windings being properly polarized. In either event, the filament windings must have a rating of 10 amperes if the full load current of 200 ma. is to be used. Some excellent surplus transformers that will handle the required current are now available on the surplus market. The vibrator also must be capable of handling the current. The hash-filter choke,  $L_1$ , must carry a current of 20 amperes.

The following table shows the output voltage

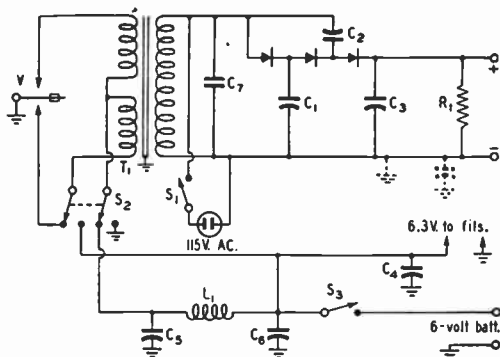


Fig. 7-36 — Circuit diagram of a compact vibrator-a.c. portable power supply suggested by W9CO.

- $C_1$  — 60- $\mu$ fd. 200-volt electrolytic.
- $C_2$  — 60- $\mu$ fd. 400-volt electrolytic.
- $C_3$  — 60- $\mu$ fd. 600-volt electrolytic.
- $C_4$  — 25- $\mu$ fd. 25-volt electrolytic.
- $C_5, C_6$  — 0.5- $\mu$ fd. 25-volt paper.
- $C_7$  — 0.007- $\mu$ fd. 1500-volt paper.
- $R_1$  — 25,000 ohms, 10 watts.
- $L_1$  — 25- $\mu$ hy. 20-amp. choke.
- $S_1$  — 115-volt toggle switch.
- $S_2$  — 1-p.d.t. heavy-duty knife switch.
- $S_3$  — 25-amp. switch.
- $T_1$  — See text.
- V — Heavy-duty vibrator.

to be expected at various load currents, depending upon the size of condensers used at  $C_1$ ,  $C_2$  and  $C_3$ .

$C_1, C_2, C_3$ ( $\mu\text{fd.}$ )	Output Voltage at			
	50 ma.	100 ma.	150 ma.	200 ma.
60	455	430	415	395
40	425	390	360	330
20	400	340	285	225

In operating the supply from an a.c. line, it is always wise to determine the plug polarity in respect to ground. Otherwise the rectifier part of the circuit and the transformer circuit cannot be connected to actual ground except through by-pass condensers.

**Vibrator-Supply Construction**

Table 7-IV contains a list of some of the currently-available vibrator-type power supplies on the market. However, supplies of this type are not difficult to construct.

A typical example of vibrator-supply construction is shown in the photographs of Figs. 7-37 and 7-38.

All components in the supply with the exception of the four-prong outlet socket are mounted on a piece of quarter-inch tempered Masonite measuring  $3\frac{3}{4} \times 9$  inches. This fits into a plywood box having inside dimensions ( $3\frac{3}{4} \times 9 \times 5\frac{1}{2}$  inches) just large enough to

TABLE 7-IV—VIBRATOR SUPPLIES

American Television and Radio Co.	Manufacturer's Type Number				Input		Output									
	Electronic Labs	Hallcrafters	Mallory	Radiart	Volts	Volts <sup>7</sup>	Ma.	Watts	Rectifier	Output Filter						
VPM-F-7			VP-551 <sup>4</sup>	4201B <sup>6</sup>	6.3 D.C.	90	10	—	Syn.	Yes						
					6.3 D.C.	125-150-175-200	25-30-35-40 (100 Max.)	—	Syn.	No						
					6.3 D.C.	250	50	—	Syn.	Yes						
					6.3 D.C.	250	60	—	Syn.	Yes						
					605A	6.3 D.C.	150-200-250-275	35-40-50-65	19	Syn.	No					
						604A	6.3 D.C.	225-250-275-300	50-65-80-100	30	Syn.	No				
							6.3 D.C.	225-250-275-300	50-65-80-100	30	Tube	No				
					616	6.3 D.C. and 115 A.C.	115 A.C. 325-350-375-400	125-150-175-200	15	Tube	Input Cond.					
						619	6.3 D.C. and 115 A.C.	300 6.3 A.C.	100 4.85 Amp.	60	Tube	Yes				
					2606		6.3 D.C.	300	100	30	Tube	Yes				
					VPM-6			VP-552 <sup>5</sup>		6.3 D.C.	250-275-300-325	50-75-100-125	—	Tube	Yes	
										6.3 D.C.	225-250-275-300	50-65-80-100	—	Syn.	No	
										VP-2	6.3 D.C.	300	170	—	Tube	No
											VP-4	6.3 D.C.	320	70	—	Tube
										VP-555	6.3 D.C.	300	200	—	Tube	Yes
VP-557	6.3 D.C.	400	150	—							Tube	Input cond.				
451	6.0 D.C. or 12 D.C.	250-180	60-40	15						Syn.	Yes					
	452	6.0 D.C.	300-275-250-225	100-100-100-100						30	Tube	Yes				
452-12		12 D.C.	Same as model 452													
453	6.0 D.C.	300-275-250-225	100-100-100-100	30						Syn.	Yes					
	453-12	12 D.C.	Same as model 453													
454	6.0 D.C.	300	200	60						Tube	Yes					
454-12	12 D.C.	Same as model 454														
455	6.0 D.C.	400	150	60						Tube	Yes					
	455-12	12 D.C.	Same as model 455													
456	6 D.C. and 110 A.C.	300-275-250-225 6.3 A.C.	100-110-100-100 5 Amp.	30	Tube	Yes										
	INVERTERS															
6RSB <sup>1</sup>					6.0 D.C.	110 A.C.	—	75 <sup>2</sup>	—	—						
12RSB <sup>1</sup>					12 D.C.	110 A.C.	—	100 <sup>2</sup>	—	—						
6ISO <sup>2</sup>					6 D.C.	110 A.C.	—	75 <sup>2</sup>	—	—						
12ISO <sup>2</sup>					12 D.C.	110 A.C.	—	100 <sup>2</sup>	—	—						
6LIC <sup>2</sup>					6 D.C.	110 A.C.	—	25 <sup>2</sup>	—	—						
12LIC <sup>2</sup>					12 D.C.	110 A.C.	—	35 <sup>2</sup>	—	—						

All a.c. voltages are 60-cycle.  
<sup>1</sup> For use with power factors as low as 80%.  
<sup>2</sup> For use with power factors as low as 60%.

<sup>3</sup> Continuous service.  
<sup>4</sup> VP-553 same with tube rect.  
<sup>5</sup> VP-554 same with tube; VP-G556 same with 12-volt d.c. input.  
<sup>6</sup> 4201B2 same with tube rect.  
<sup>7</sup> D.c. unless specified.

TABLE 7-V — GASOLINE-ENGINE DRIVEN GENERATORS, AIR-COOLED

Manufacturer			Output				Weight Lb.	Starting Method
Kato	Onan	Pioneer	Volts A.C.	Watts	Volts D.C.	Watts		
		BD-6 <sup>1</sup>	110	300	6	200	100	Push-Button
JRA-3 <sup>2</sup>			110	350	6	30	65	Rope Crank
	03AAE-1E		115	350	6	—	77	Push-Button
	358RSAL <sup>1</sup>		115	350	12	—	79	Push-Button <sup>2</sup>
	05AH-1R <sup>1</sup>		115	500	12	—	126	Push-Button <sup>2</sup>
23HAB4			115	500	12	13	125	Push-Button
		BA-6 <sup>1</sup>	110	600	—	—	135	Push-Button
14HAB4			115	600	12	13	170	Push-Button
	07AH-1R <sup>1</sup>		115	750	12	—	136	Push-Button <sup>2</sup>
		BA-10 <sup>1</sup>	110	1000	—	—	170	Push-Button
	10LS <sup>1</sup>		115	1000	12	—	210	Push-Button <sup>2</sup>
26HAB4			115	1000	12	10	265	Remote Contr.
28HAB4			115	1500	18	6	350	Remote Contr.
	105BH-1R <sup>1</sup>		115	1500	12	—	187	Push-Button <sup>2</sup>
		BA-15	110	1500	—	—	365	Push-Button
	2CK-1R <sup>1</sup>		115	2000	12	—	258	Push-Button <sup>2</sup>
41HAB4			115	2500	32	5	450	Remote Contr.
	3CK-1R <sup>1</sup>		115	3000	12	—	266	Push-Button <sup>2</sup>

<sup>1</sup> Available with remote control.

<sup>2</sup> Manual starting available.

<sup>3</sup> Postwar model expected to be produced.

contain the equipment. The Masonite shelf rests on 3/4-inch-square strips, 1 1/4 inches long, glued to the corners of the box at the bottom. The top and bottom of the box are removable. To provide shielding and thus reduce hash troubles, the box is covered with thin iron salvaged from 5-quart oil cans. Where the edges bend around the box to make a joint, the lacquer is rubbed off with steel wool so the pieces make electrical contact, and the metal is tacked to the plywood with escutcheon pins.

To make sure that the shielding will be complete, the top and bottom of the box slide into place from the side, with the metal covering extending out so that it fits tightly under a lip bent over from the metal on the sides. These lips also are cleaned of lacquer to permit good electrical contact. The general construction should be quite apparent from the photographs. The bottom is provided with rubber feet, and the top has a small knob at each end so that it can be pulled out. This is essential,

since the fit is good and there is no way to get either the top or bottom off, once on, without having some sort of handle to grip.

● GASOLINE-ENGINE DRIVEN GENERATORS

For higher-power installations, such as for communications control centers during emergencies, the most practical form of independent power supply is the gasoline-engine driven generator which provides standard 115-volt 60-cycle supply.

Such generators are ordinarily rated at a minimum of 250 or 300 watts. They are available up to two kilowatts, or big enough to handle the highest-power amateur rig. Most are arranged to charge automatically an auxiliary 6- or 12-volt battery used in starting. Fitted with self-starters and adequate mufflers and filters, they represent a high order of performance and efficiency. Many of the larger models are liquid-cooled, and they will operate

Fig. 7-37 — A view inside a typical vibrator-type power supply. The rectifier tube is at the upper left with the filter choke just below. The primary fuse socket and vibrator are at the right. A synchronous-type vibrator may be substituted for the interrupter type if it is desired to eliminate the rectifier tube.

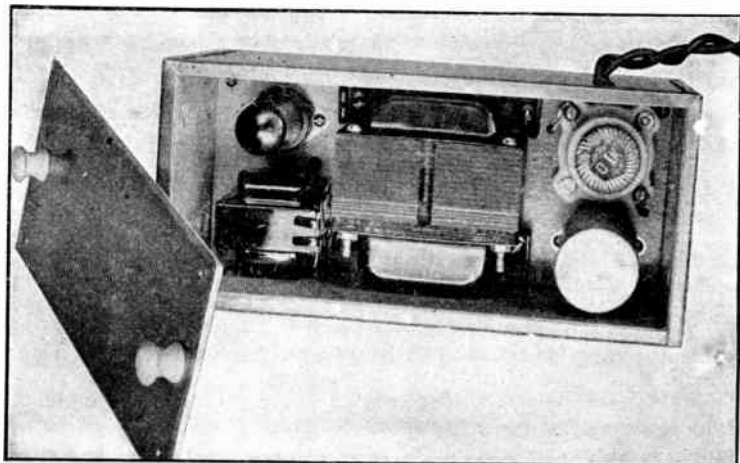


TABLE 7-VI—PLATE-BATTERY SERVICE HOURS

Estimated to 34-volt end-point per nominal 45-volt section.  
Based on intermittent use of 3 to 4 hours daily at room temp. of 70° F.  
(For batteries manufactured in U. S. A. only.)

Manufacturer's Type No.		Weight		Current Drain in Ma.											
Burgess	Eveready	Lb.	Oz.	5	10	15	20	25	30	40	50	60	75	100	150
—	758	14	8	Suggested current range = 7 to 12 Ma.											
21308	—	12	8	1600	1100	690	490	—	300	200	—	130	—	60	30
10308	—	11	4	1300	750	520	350	—	—	130	—	90	—	45	22
—	754	6	8	Suggested current range = 5 to 15 Ma.											
2308	—	8	3	1100	500	330	200	—	150	65	—	34	—	—	—
—	487	4	2	Suggested current range = 7 to 12 Ma.											
B30	—	2	8	350	170	90	50	—	21	17	—	—	—	—	—
A30	—	2	—	260	100	48	28	—	17	7	—	—	—	—	—
—	482	1	14	400	208	122	80	—	—	—	—	—	—	—	—
Z30N	—	1	4	155	70	30	20	15	9.5	—	—	—	—	—	—
—	467	—	12	82	30	—	—	—	—	—	—	—	—	—	—
—	738	1	2	160	70	30	20	10	7	—	—	—	—	—	—
W30FL	—	—	11	70	20	12	7	—	3.5	—	—	—	—	—	—
—	455	—	8	82	30	—	—	—	—	—	—	—	—	—	—
XX30	—	—	9	70	20	12	7	—	3.5	—	—	—	—	—	—

TABLE 7-VII—FILAMENT-BATTERY SERVICE HOURS

Estimated to 1-volt end-point per nominal 1.5-volt unit. Based on intermittent use of 3 to 4 hours per day at room temperature. (For batteries manufactured in U. S. A. only.)

Manufacturer's Type No.		Weight		Volt- age	Current Drain in Ma.											
Burgess	Eveready	Lb.	Oz.		30	50	60	120	150	175	180	200	240	250	300	350
—	A-1300	8	4	1.25	—	—	—	—	2000	1715	1500	1333	1250	1200	1000	854
—	740	6	4	1.5	—	—	—	—	—	—	870	—	—	—	—	—
—	741 <sup>1</sup>	2	13	1.5	—	—	—	—	—	—	460	—	—	270	—	—
—	743	2	1	1.5	—	—	—	—	—	—	300	—	225	175	—	—
—	742	1	6	1.5	—	—	—	—	—	—	170	—	120	90	—	—
8F <sup>2</sup>	—	2	10	1.5	—	—	1100	600	450	—	400	—	320	230	190	—
4F	—	1	4	1.5	—	—	600	340	230	—	160	—	110	95	60	—
—	A-2300	11	—	2.5	—	—	—	—	2000	1715	1500	1333	1250	1200	1000	854
20F <sup>2</sup>	—	13	12	3.0	—	—	—	—	1100	—	850	—	775	600	500	—
2F2H	—	1	6	3.0	600	—	340	130	95	—	60	—	42	30	—	—
2F2BP <sup>3</sup>	—	1	5	3.0	600	—	340	130	95	—	60	—	42	30	—	—
F2BP	—	—	12	3.0	340	—	130	45	30	—	—	—	—	—	—	—
G3 <sup>4</sup>	—	1	5	4.5	370	200	150	50	35	—	—	—	—	—	—	—
—	746	1	4	4.5	—	225	—	—	—	—	—	—	—	—	—	—
—	718 <sup>5</sup>	2	13	6.0	—	415	—	—	—	—	—	—	—	—	—	—
F4PI	—	1	6	6.0	340	150	130	45	30	—	—	—	—	—	—	—

<sup>1</sup> Same life figures apply to 745, wt. 2 lb. 13 oz.  
<sup>2</sup> Same life figures apply to 8FL, wt. 2 lb. 15 oz.

<sup>3</sup> Same life figures apply to 2F4, volts 6, wt. 2 lb. 11 oz.  
<sup>4</sup> Same life figures apply to G5, volts 7½, wt. 2 lb. 2 oz.  
<sup>5</sup> Same life figures apply to 747, wt. 2 lb. 13 oz.

If batteries of another make are to be used, locate ones of similar size and weight on these tables and comparable performance may be expected.


continuously at full load. Ratings of typical engine-driven units are given in Table 7-V.

A variant on the generator idea is the use of fan-belt-drive. The disadvantage of requiring that the automobile must be running throughout the operating period has not led to general popularity of this idea among amateurs. Such generators are similar in construction and capacity to the small gas-driven units.

The output frequency of an engine-driven generator must fall between the relatively narrow limits of 50 to 60 cycles if standard 60-cycle transformers are to operate efficiently from this source. A 60-cycle electric clock provides a means of checking the output frequency with a fair degree of accuracy. The clock is

connected across the output of the generator and the second hand is checked closely against the second hand of a watch. The speed of the engine is adjusted until the two second hands are in synchronism. If a 50-cycle clock is used to check a 60-cycle generator, it should be remembered that one revolution of the second hand will be made in 50 seconds and the clock will gain 4.8 hours in each 24 hours.

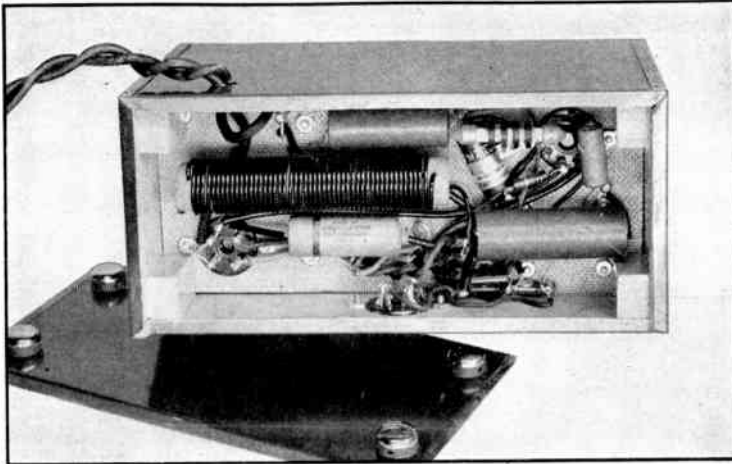Output voltage should be checked with a voltmeter since a standard 115-volt lamp bulb, which is sometimes used for this purpose, is very inaccurate. Tests have shown that what appears to be normal brilliance in the lamp may occur at voltages as high as 150 if the check is made in bright sunlight.



◆  
**Fig. 7-38** — Hash and smoothing filter components are mounted in the bottom of the low-voltage vibrator power supply. The 4-prong outlet socket is mounted on the side.  
 ◆

**Noise Elimination**

Electrical noise which may interfere with receivers operating from engine-driven a.c. generators may be reduced or eliminated by taking proper precautions. The most important point is that of grounding the frame of the generator *and* one side of the output. The ground lead should be short to be effective, otherwise grounding may actually increase the noise. A water pipe may be used if a short connection can be made near the point where the pipe enters the ground, otherwise a good separate ground should be provided.

The next step is to loosen the brush-holder locks and slowly shift the position of the brushes while checking for noise with the re-

ceiver. Usually a point will be found (almost always different from the factory setting) where there is a marked decrease in noise.


From this point on, if necessary, by-pass condensers from various brush holders to the frame, as shown in Fig. 7-39, will bring the hash down to within 10 to 15 per cent of its original intensity, if not entirely eliminating it. Most of the remaining noise will be reduced still further if the high-power audio stages are cut out and a pair of headphones is connected into the second detector.

● **POWER FOR PORTABLES**

Dry-cell batteries are the only practical source of supply for equipment which must be transported on foot. From certain considerations they may also be the best source of voltage for a receiver whose filaments may be operated from a storage battery, since no problem of noise filtering is involved.

Their disadvantages are weight, high cost, and limited current capability. In addition, they will lose their power even when not in use if allowed to stand idle for periods of a year or more. This makes them uneconomical if not used more or less continuously.

Tables 7-VI and 7-VII give service life of representative types of batteries for various current drains, based on intermittent service simulating typical operation. The continuous-service life will be somewhat greater at very low current drains and from one-half to two-thirds the intermittent life at higher drains.

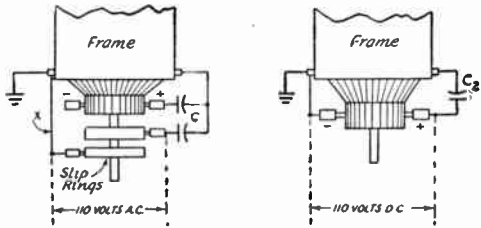

**Fig. 7-39** — Connections used for eliminating interference from gas-driven generator plants. *C* should be 1  $\mu$ fd., 300 volts, paper, while *C*<sub>2</sub> may be 1  $\mu$ fd. with a voltage rating of twice the d.c. output voltage delivered by the generator. *X* indicates an added connection between the slip ring on the grounded side of the line and the generator frame.

# Keying and Break-In

If the proper keying of a transmitter entailed only the ability to turn on and off the output, keying would be a simple matter. Unfortunately, perfect keying is as difficult to obtain as perfect voice quality, and so is not a matter to be dismissed lightly. The keying of a transmitter can be considered satisfactory if the power output is reduced to zero with the key open, or "up," and reaches full output when

the key is closed, or "down." The keying system should accomplish this without producing objectionable transients or "clicks," which cause interference with other amateur stations and with local broadcast reception. Furthermore, the keying process should cause no "chirp," which means that the transmitter output frequency should not be affected by the keying process.

## Keying Principles and Characteristics

### *Back-Wave*

When the transmitter output is not reduced to zero under key-up conditions, the signal is said to have a **back-wave**. If the amount of back-wave is appreciable, the keying will be difficult to read. A pronounced back-wave may result when the amplifier feeding the antenna is keyed, as a result of the excitation energy feeding through an incompletely-neutralized stage. Magnetic coupling between antenna coils and one of the driver stages on the operating frequency is also a cause of back-wave. Direct radiation from a driver stage ahead of the keyed stage will result in a back-wave, but this type is generally heard only within a few miles of the transmitter, unless the driver stage is fairly high powered.

A back-wave also may be radiated if the keying system does not reduce the input to the keyed stage to zero during keying spaces. This trouble will not occur in keying systems that completely cut off the plate voltage when the key is open. It will occur in grid-block keying systems if the blocking voltage is not great enough, or in power-supply primary keying systems if only the final-stage power-supply primary is keyed. A vacuum-tube keyer will give a back-wave if the "open" key resistance is too low.

### *Key Clicks*

If a transmitter is keyed in such a manner that the power output rises instantly to its full value or drops immediately to zero, the resultant short rise and decay times produce signals (at the times of closing and opening the key) extending from the signal frequency to several hundred kilocycles on either side.

These signals are called "key clicks," and they will cause interference to other amateurs and other services. Consequently, keying systems must be used that increase the rise and decay times of the keyed characters, since this results in less click energy removed from the signal frequency.

The simple process of making and breaking any circuit with current flowing through it will produce a brief burst of r.f. energy. This effect can be noticed in a radio receiver when an electric light or other appliance in the house is turned on or off. It is, therefore, not only necessary to delay the rise and decay times of the keyed transmitter to prevent interference with other services, but it may be necessary to filter the r.f. energy generated at the key contacts if this energy is found to interfere with broadcast reception in the amateur's house or vicinity. This interference is also called "key clicks."

Getting back to the discussion of rise and decay times, tests have shown that practically all operators prefer to copy a signal that is "solid" on the "make" end of each dot or dash; i.e., one that does not build up too slowly but just slowly enough to have a slight click when the key is closed. On the other hand, the most-pleasing and least-difficult signal to copy, particularly at high speeds, is one that has a fairly soft "break" characteristic; i.e., one that has practically no click as the key is opened. A signal with heavy clicks on both make and break is difficult to copy at high speeds and also causes considerable interference. If it is too "soft" the dots and dashes will tend to run together and the characters will be difficult to copy. The keying should be



adjusted so that for all normal hand speeds (15 to 35 w.p.m.) the readability will be satisfactory without causing unnecessary interference to the reception of other signals near the transmitter frequency.

### Chirps

Keying should have no effect upon the frequency of the transmitter. In many cases where sufficient pains have not been taken, keying will cause a frequency change, or "chirp," at the instant of opening or closing the key. The resultant signal is unpleasant and, in cases of extreme chirp, difficult to copy. Multistage transmitters keyed in a stage following the oscillator are generally free from chirp, unless the keying causes line-voltage changes which in turn affect the oscillator frequency. When the oscillator is keyed, as is done for "break-in" operation, particular care must be taken to insure that the signal does not have keying chirps.

### Break-In Operation

In code transmission, there are intervals between dots and dashes, and slightly longer intervals between letters and words, when no power is being radiated by the transmitter. If the receiver can be made to operate at normal sensitivity during these intervals, it is possible for the receiving operator to signal the transmitting operator, by holding his key down. This is useful during the handling of messages, since the receiving operator can immediately signal the transmitting operator if he misses part of the message. It is also useful in reducing the time necessary for calling in

answer to a "CQ." The ability to hear signals during the short "key-up" intervals is called break-in operation.

### Selecting the Stage To Key

It is highly advantageous from an operating standpoint to design the c.w. transmitter for break-in operation. In most cases this requires that the oscillator be keyed, since a continuously-running oscillator will create interference in the receiver and prevent break-in on or near one's own frequency. On the other hand, it is easier to avoid a chirpy signal by keying a stage or two following the oscillator. Since the effect of a chirp is multiplied with frequency, it is quite difficult to obtain chirpless oscillator keying in the 14- and 28-Mc. bands. In any case, however, the stages following the keyed stage (or stages) must be provided with sufficient fixed bias to limit the plate currents to safe values when the key is up and the tubes are receiving no excitation voltage. Complete cut-off reduces the possibility of a back-wave if a stage other than the oscillator is keyed, but the keying waveform is not well preserved and some clicks can be introduced, even though the keyed stage itself produces no clicks. *It is a good general rule to bias the tubes following the keyed stage so that they draw a key-up current of about 5 per cent of the normal key-down value.*

The power broken by the key is an important consideration, both from the standpoint of safety to the operator and that of sparking at the key contacts. Keying of the oscillator or a low-power stage is favorable on both counts. The use of a keying relay is recommended when a high-power circuit is keyed.

## Keying Circuits

Only general circuits can be shown for keying, since the final decision on where and how to key rests with the amateur and depends upon the power level and type of operation.

### ● PLATE-CIRCUIT KEYING

Any stage of the transmitter can be keyed by opening and closing the plate-power circuit. Fig. 8-1 shows how the key can be connected to key the plate circuit (A) or the screen circuit (B). The circuit in Fig. 8-1A shows the key in the negative power lead, although it could be placed in the positive lead, at the point marked "X." Either system is recommended only for low-voltage circuits, on the order of 300 or less, unless a relay is used, because of the danger of accidental electrical shock.

Fig. 8-1B shows the key in the screen lead of an electron-coupled oscillator, and can be considered a variation of 8-1A that has the desirable advantage of breaking less current at a lower voltage.

Both of the circuits shown in Fig. 8-1 respond well to the use of key-click filters, and

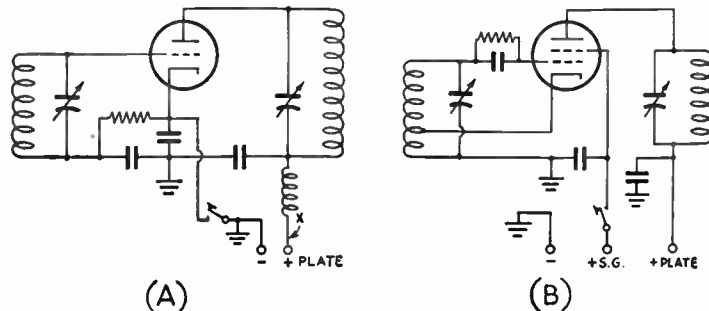


Fig. 8-1 — Plate-circuit keying is shown at A, and screen-grid keying is shown in B. Oscillator circuits are shown in both cases, but the same keying methods can be used with amplifier circuits. Notice the similarity between A and Fig. 8-5 — the only difference is in the way the grid return is connected.

are particularly suitable for use with crystal- and self-controlled oscillators, which are generally operated at low voltage and low power.

● PRIMARY KEYING

A popular method of keying high-powered amplifiers is shown in Fig. 8-2. In its simplest form, as shown in 8-2A, it consists of keying the primary of the plate transformer supplying power to one or more of the driver stages. It has the advantage that the filter, *LC*, acts as a keying filter and prevents clicks. However, too much filter cannot be used or the keying will be too soft, and a single section is all that can normally be used. Since this will introduce some a.c. modulation on the keyed stages, it is essential that the amplifier driven by the keyed stage have sufficient excitation to operate as a Class C amplifier, which tends to eliminate the modulation existing in the excitation voltage. Primary keying of the final plate power supply alone is not recommended, since it is practically impossible to comply with the FCC regulations about "adequately-filtered power supply" and still avoid keying that is too soft.

Primary keying of the driver power supply requires that the following amplifier stage (or stages) be biased to prevent excessive cur-

rent under key-up conditions. If this bias exceeds the cut-off value for the tube (or tubes) a slightly more elaborate version of primary keying can be used, as shown in Fig. 8-2B. The primaries of both driver and final-amplifier plate supplies are keyed, and the system has the advantage that the final-amplifier plate voltage remains substantially constant under key-up or key-down conditions, and thus no clicks can be introduced by the sudden changes in final-amplifier plate voltage as the excitation is applied or removed. The final-amplifier plate supply will remain charged for several minutes after the last transmission, however, and extreme caution must be exercised. As a safety measure, the final-amplifier power supply can be discharged by a relay that shorts the supply through a 1000-ohm resistor, or the bias can be removed and the final-amplifier tube will discharge the power supply.

The keying system shown in Fig. 8-2B has been used to key an entire transmitter for break-in operation. The oscillator and multiplier/driver stages take their plate power from the supply with the small filter, while the final amplifier is powered from the heavily-filtered supply. It is essential, however, in a transmitter keyed for break-in in this manner,

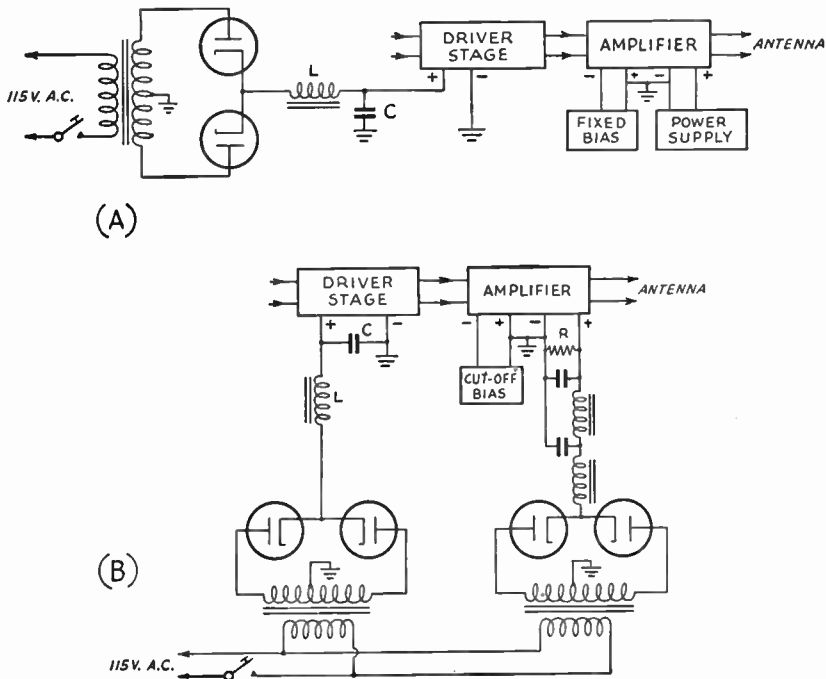


Fig. 8-2 — Primary-keying circuits. The circuit at A shows primary keying of the driver-stage (or stages) power supply, followed by an amplifier biased to or close to cut-off. The circuit of B uses primary keying of both driver and final supplies, and has the advantage that the key-up and key-down voltage on the final amplifier remains substantially constant, thus eliminating the chance of clicks being introduced by the final-amplifier plate-supply regulation. In either case, *L* and *C* should be as small as possible, consistent with sufficient filtering and rectifier-tube limits. *R* in B need be only about 1000 ohms per volt. If a plate voltmeter is used, the bleed through it is sufficient, since the only function is to remove any long-standing charge from the power supply. A heavy bleed current will reduce the effectiveness of the keying system. See text for other bleeder suggestions.

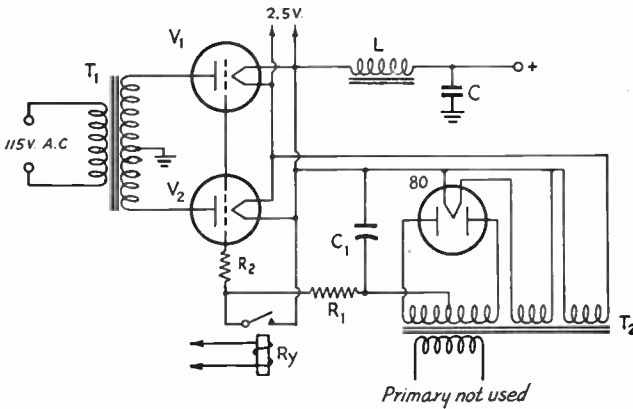


Fig. 8-3 — Grid-controlled rectifier keying. Circuit is similar to Fig. 8-2, and the values of  $L$  and  $C$  are the same. A well-insulated keying relay,  $Ry$ , is used to control the bias on the rectifiers  $V_1$  and  $V_2$ . The bias voltage is obtained from a small receiver power-supply transformer,  $T_2$ , the 80 rectifier and filter condenser  $C_1$ .  $T_2$  does not need to be insulated for the full plate-supply voltage (obtained from  $T_1$ ) because it is excited from the filament transformer for  $V_1$  and  $V_2$ . It should be well insulated to ground, however.  $R_1$  limits the short-circuit on the bias supply and can be approximately 50,000 ohms in value.

that the oscillator be free from chirp, and this point should be checked carefully before using the system on the air.

In using primary keying up to several hundred watts, direct keying in the primary circuit is satisfactory. For higher powers, however, a keying relay should be used, because of the arcing at the contacts.

Fig. 8-3 shows grid-controlled rectifier tubes in the power supply. By applying suitable bias to the tubes when the key is up, no current flows through the tubes. When the key is closed, the bias is removed and the tubes conduct. The system can be used in the same way that primary keying was used in Fig. 8-2A and B. This system is used only in high-powered high-voltage supplies.

**● BLOCKED-GRID KEYING**

An amplifier tube can be keyed by applying sufficient negative bias voltage to the control

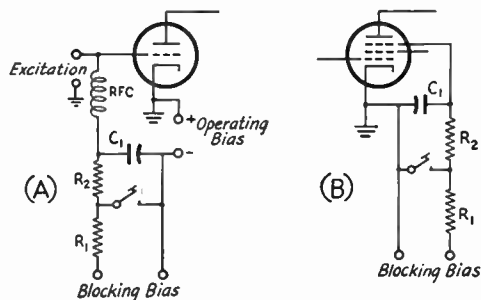


Fig. 8-4 — Blocked-grid keying.  $R_1$ , the current-limiting resistor, should have a value of about 50,000 ohms.  $C_1$  may have a capacity of 0.1 to 1  $\mu\text{fd.}$ , depending upon the keying characteristic desired.  $R_2$  also depends upon the performance characteristic desired, values being of the order of 5000 to 10,000 ohms in most cases.

or suppressor grid to cut off plate-current flow when the key is up, and by removing this blocking bias when the key is down. When the bias is applied to the control grid, its value will be considerably higher than the nominal cut-off bias for the tube, since the r.f. excitation voltage must be overcome. The fundamental circuits are shown in Fig. 8-4A and B. The circuits can be applied to oscillator tubes as well as amplifiers. Suppressor-grid keying will not completely turn off a Tri-tet crystal oscillator or electron-coupled self-controlled oscillator, and is likely to cause serious chirps with the latter.

In both circuits the key is connected in series with a resistor,  $R_1$ , which limits the current drain on the blocking-bias source when the key is closed.  $R_2C_1$  is a resistance-capacitance

filter that controls the rise time on make, the rise time increasing as  $R \times C$  is made larger.  $C \times (R_1 + R_2)$  controls the decay time on break in the same manner. Since grid current flows through  $R_2$  in Fig. 8-4A when the key is

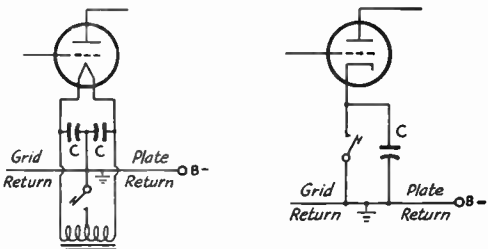


Fig. 8-5 — Center-tap and cathode keying. The condensers,  $C$ , are r.f. by-pass condensers. Their capacity is not critical, values of 0.001 to 0.01  $\mu\text{fd.}$  ordinarily being used.

closed, operating bias is developed, and  $R_2$  is usually the normal grid leak for the tube. Thus  $C_1$  only is varied to obtain the proper rise time.

With blocked-grid keying only a small current is broken compared with other systems, and sparking at the key is slight.

**● CATHODE KEYING**

Keying the cathode circuit of a tube simultaneously opens the grid and plate circuits of the tube. This is shown in Fig. 8-5. The condenser  $C$  serves as a short path for the r.f. energy, since the keying leads are often long. When a filament-type tube is keyed in this manner, the key is connected in the filament-transformer center-tap lead, as in Fig. 8-5, and the system is called center-tap keying. The condensers  $C$  serve the same purpose as in cathode keying.

Cathode (or center-tap) keying results in less sparking at the key contacts than does plate-supply keying, for the same plate power. When used with an oscillator it does not respond as readily to key-click filtering as does plate-circuit keying, but it is an excellent method for amplifier keying. If plate voltages above 300 are used, it is highly advisable to use a keying relay, to avoid accidental electrical shock at the key.

● KEYING RELAYS

A keying relay can be substituted for a key in any of the keying circuits shown in this chapter. Most keying relays operate from 6.3 or 115 volts a.c., and they should be selected for their speed of operation and adequate insulation for the job to be done. Adequate current-handling capability is also a factor. A

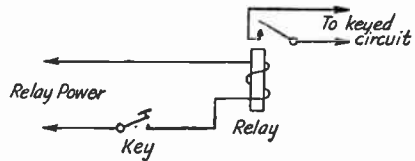


Fig. 8-6—A keying relay can always be substituted for the key, to provide better isolation from the keyed circuit. An r.f. filter is generally required at the key, and the keying filter is connected in the keyed circuit at the relay contacts.

typical circuit is shown in Fig. 8-6.

The relay-coil current that is broken by the key will cause clicks in the receiver, and an r.f. filter (see later in this chapter) is often necessary across the key. The normal keying filter connects at the relay armature contacts in the usual manner.

### Key-Click Reduction

As pointed out earlier, interference caused by the key breaking current and the fast rise and decay times of the keyed characters is called "key clicks." The elimination of the interference depends upon its type.

● R.F. FILTERS

Key clicks caused by the spark (often very minute) at the key contacts can be minimized by isolating the key from the rest of the wiring by a small r.f. filter. Such a filter usually consists of an r.f. choke in each key lead, placed right at the key terminals and by-passed on the line side by a small condenser. Such a circuit is shown in Fig. 8-7. Suitable values are best found by experiment, although 2.5-mh. r.f. chokes and an 0.001- $\mu$ fd. condenser represent good starting points. The chokes must be capable of carrying the current that is broken, and the condenser must have a voltage rating equal at least to the voltage across the key under key-up conditions. Sometimes a small

amateur band and adjacent services, is called a keying filter or lag circuit. In its simplest form it consists of a condenser and an inductance, connected as in Fig. 8-8. This type of keying

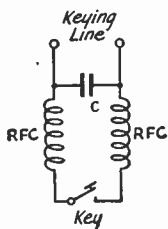


Fig. 8-7—R.f. filter used for eliminating the radiation effects of sparking at the key contacts. Suitable values for best results with individual transmitters must be determined by experiment. Values for RFC range from 2.5 to 80 millihenrys and for C from 0.001 to 0.1  $\mu$ fd.

condenser directly across the key terminals is also necessary to remove the last trace of click.

This type of r.f. filter is required in nearly every keying installation, in addition to the circuits to be described in the following few paragraphs.

**Keying Filters**

A filter used to give a desired shape to the keyed character, to eliminate clicks in the

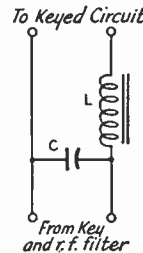


Fig. 8-8—Lag circuit used for shaping the keying character to eliminate unnecessary sidebands. Actual values for any given circuit must be determined by experiment, and may range from 1 to 30 henrys for L and from 0.05 to 0.5  $\mu$ fd. for C, depending on the keyed current and voltage.

filter is suitable for use in the circuits shown in Figs. 8-1 and 8-5. The optimum values of capacitance and inductance must be found by experiment but are not very critical. If a high-voltage low-current circuit is being keyed, a small condenser and a large inductance will be required, while a low-voltage high-current circuit needs a large condenser and small inductance to reduce the clicks properly. For example, a 300-volt 6-ma. circuit will require about 30 henrys and 0.05  $\mu$ fd., while a 300-volt 50-ma. circuit needs about 1 henry and 0.5  $\mu$ fd. For any given set of conditions, increasing the inductance will reduce the clicks on "make" and increasing the capacitance will reduce the clicks on "break."

Primary keying is adjusted by changing the filter values (L or C in Fig. 8-2). Since it is unlikely that a variety of chokes will be available to the operator, capacitance changes are usually all that can be made. If the keying is found too "soft," the value of C must be reduced.

Blocked-grid keying is adjusted by changing the values of resistors and condensers in the circuit, as outlined under the description of the

circuit. The values required for individual installations will vary with the amount of blocking voltage and the value of grid leak.

### Tube Keying

A tube keyer is a convenient device for keying the transmitter, because it allows the keying characteristic to be adjusted easily and also removes all dangerous voltages from the key itself. The current broken by the key is negligible and usually no r.f. filter is required at the key. A tube keyer uses a tube (or tubes in parallel) to control the current in the plate

or cathode circuit of the stage being keyed. The keyer tube turns off the current flow when a high negative voltage is applied to the grid of the keyer tube. The keying characteristic is shaped through the time constants of the grid circuit of the keyer tube, in exactly the same way that it is controlled in blocked-grid keying. When a tube keyer is used to replace the key in a plate or cathode circuit, the power output of the stage may be reduced somewhat because of the voltage drop across the keyer tube but this is of little importance because the effect is not large.

## A Vacuum-Tube Keyer

A tube-keyer unit is shown in Figs. 8-9 and 8-10.  $T_1$ , the 80 rectifier, and  $C_1$  and  $R_1$  form the power-supply section that furnishes the blocking voltage for the keyer tubes.



Fig. 8-9 — A vacuum-tube keyer, built up on a 7 × 9 × 2-inch chassis with space for four or less keyer tubes and the power-supply rectifier. The resistors and condensers which produce the lag are underneath, controlled by the knobs at the right. The jack is for the key, while terminals at the left are for the keyed circuit.

$S_1$  and  $S_2$  and their associated resistors and condensers are included to allow the operator to select the keying characteristic he wants. A simplified version could omit the switches and extra components, since once the values have been selected the components can be soldered permanently in place. The rule for adjusting the keying characteristic is the same as for blocked-grid keying. However, large values of resistors and small values of condensers can be used, since there is no value of grid leak determined by the tube that dictates a starting point.

As many 45s may be added in parallel as desired. The voltage drop through a single tube varies from about 90 volts at 50 ma. to 50 volts at 20 ma. Tubes added in parallel will reduce the drop in proportion to the number of tubes used.

When connecting the output terminals of the keyer to the circuit to be keyed, the grounded output terminal of the keyer must be connected to the transmitter ground. Thus the keyer can be used only in negative-lead or cathode keying.

When the key or keying lead has poor insulation, the resistance may become low enough (particularly in humid weather) to reduce the blocking voltage and allow the keyer tube to pass some current. This may cause a slight back-wave on the signal.

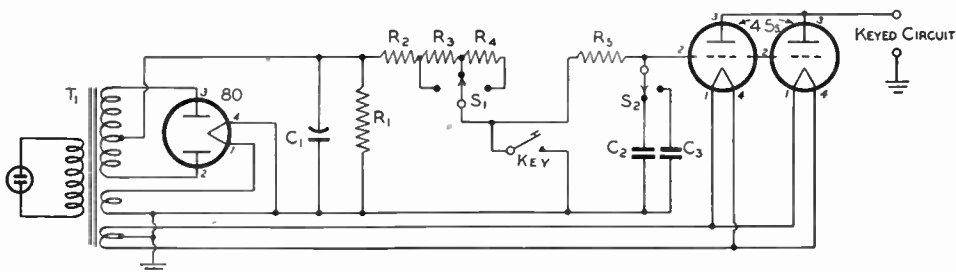


Fig. 8-10 — Wiring diagram of the practical vacuum-tube keyer unit and power supply shown in Fig. 8-9.

$C_1$  — 2- $\mu$ fd. 600-volt paper.  
 $C_2$  — 0.0033- $\mu$ fd. mica.  
 $C_3$  — 0.0047- $\mu$ fd. mica.  
 $R_1$  — 0.22 megohm, 1 watt.  
 $R_2$  — 50,000 ohms, 10 watts.

$R_3, R_4$  — 4.7 megohms, 1 watt.  
 $R_5$  — 0.47 megohm, 1 watt.  
 $S_1, S_2$  — 3-position 1-circuit rotary switch.  
 $T_1$  — 325-0-325 volts, 5 volts and 2.5 volts (Thordarson T-13R01).

## Checking Transmitter Keying

One of the best ways to check your transmitter keying is to enlist the aid of a near-by amateur and trade stations with him for a short time. Not only will you be able to check your own key clicks and chirps, if they exist, but if you have any complaint about the other fellow's signal this is a convenient way to let him know!

### ● A SIGNAL MONITOR

Lacking a conveniently-local amateur, your next best bet is to check your signals with a signal monitor. This consists of a completely-shielded battery-operated simple receiver. The complete shielding reduces the signal from the transmitter to the point where it is possible to listen without having the signal "block" the monitor. The monitor can be used to listen to a harmonic of the transmitter, in the case of high-powered transmitters, or the monitor can be used at some distance from the transmitter and remote keying leads run out for the test. A typical signal monitor is shown in Figs. 8-11, 8-12, 8-13 and 8-14.

The monitor is a two-tube regenerative receiver, as can be seen from the circuit diagram, Fig. 8-12. The 1T4 detector has a medium-*C* tank circuit and low value of grid leak ( $R_1$ ) to reduce blocking effects. Capacitance control of regeneration is obtained through  $C_5$ . The 1S4 audio amplifier gives reasonable headphone volume with the 45-volt plate supply. By-pass condensers across the headphone jack attenuate signals picked up by the 'phone cords.

The jack,  $J_1$ , is insulated from the panel by fiber washers to avoid shorting the plate-supply battery.

The monitor is built in a  $5 \times 9 \times 6$ -inch "utility cabinet." The chassis is a small piece of sheet aluminum supported by the two variable condensers. The variable condensers fasten to the front panel (cover) of the cabinet by their single-hole mountings, and the tapped mounting brackets of the condensers then serve as two brackets to support the chassis. The side walls of the cabinet bearing on the chassis contribute to the rigidity of the assembly.

A shield can is mounted over the antenna post, and is only removed when the signal isn't strong enough to be heard otherwise. Normally the shield can will be left in place. The can is one of the small aluminum cans 35-mm. film is packed in. The cover of the can is fastened to the panel with two screws, and a National XS-7 steatite bushing serves as a feed-through and antenna terminal.

The coils are wound on Silver Type 125 coil forms, which are low-loss tube bases. The winding data are given in Fig. 8-12. For any one range, both coils are wound in the same direction, and the grid and plate leads are taken off at the outside ends of the coils. It isn't necessary to wind coils for every amateur band, since one's listening should be done on the band in use or a higher-frequency one. Running one's hands over the 'phone cords or touching the cabinet at any point should result in no change in frequency. If any is noted, it indicates that the shielding and filtering are not adequate, and the grounding of  $C_6$  and  $C_7$  and the bonding of the cabinet should be thoroughly checked.

### ● SIGNAL CHECKING WITH A RECEIVER

If keying the transmitter does not affect the line voltage, the station communications receiver can be used to check keying. The antenna should be disconnected from the receiver and the antenna posts shorted to ground. This method is satisfactory only when the line voltage is not affected by keying, since any changes in line voltage will probably affect the receiver frequency. Receivers with

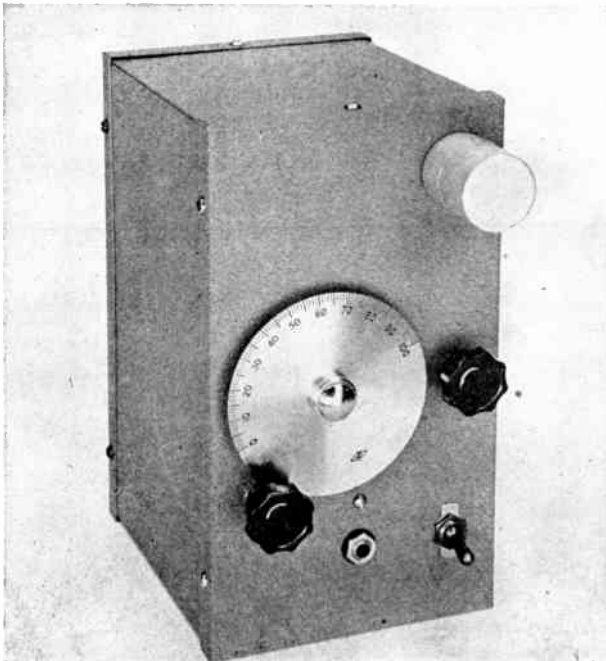


Fig. 8-11 — A two-tube battery-operated monitor. The extra knob is a regeneration control, and the little aluminum box in the upper corner is a shield can for the antenna terminal.

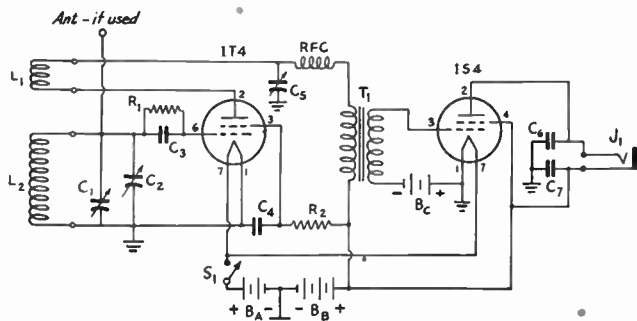


Fig. 8-12 — Wiring diagram of the battery-powered monitor.

- C<sub>1</sub> — 10- $\mu$ fd. midget variable (Bud LC-1648).  
 C<sub>2</sub> — 3-30- $\mu$ fd. mica trimmer.  
 C<sub>3</sub> — 47- $\mu$ fd. mica.  
 C<sub>4</sub>, C<sub>6</sub>, C<sub>7</sub> — 0.001- $\mu$ fd. mica.  
 C<sub>5</sub> — 75- $\mu$ fd. midget variable (Hammarlund HF-75 or Bud LC-1645).  
 R<sub>1</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.  
 R<sub>2</sub> — 10,000 ohms,  $\frac{1}{2}$  watt.  
 L<sub>1</sub> — 7 Mc.: 5 turns. 14 Mc.: 3 turns. 28 Mc.: 2 turns.  
 L<sub>2</sub> — 7 Mc.: 14 $\frac{1}{2}$  turns. 14 Mc.: 6 $\frac{1}{2}$  turns. 28 Mc.: 2 $\frac{3}{4}$  turns. L<sub>1</sub> and L<sub>2</sub> are close-wound with No. 24 d.c.c. on 1 $\frac{3}{8}$ -inch diameter tube-base forms. Final adjustment of tuning range made by spacing top turns of L<sub>2</sub> and/or setting C<sub>2</sub>.  
 B<sub>A</sub> — 1 $\frac{1}{2}$ -volt dry cell (Eveready No. 6 or equiv.).  
 B<sub>B</sub> — 45-volt "B" battery, small size (Burgess XX30).  
 B<sub>C</sub> — 4 $\frac{1}{2}$  volts. Three "penlite" cells connected in series and wrapped with friction tape.  
 J<sub>1</sub> — Open-circuit jack.  
 RFC — 2.5-mh. r.f. choke (National R-100S).  
 T<sub>1</sub> — Interstage audio transformer, 3:1 ratio (Thordarson T13A34).

good shielding will be more satisfactory than those that allow signals to leak in through the receiver wiring.

### Key Clicks

When checking for key clicks, the b.f.o. and a.v.c. of the monitoring receiver should be turned off. If the monitor of Fig. 8-11 is used, the regeneration control should be backed off until the detector is out of oscillation. The keying should be adjusted so that a slight click is heard as the key is closed but practically none heard as the key is opened. When the keying constants have been adjusted to meet this condition, the clicks will be about optimum for all normal amateur work. The receiver gain should be reduced during these tests, since false clicks can be generated in the receiver if the receiver is overloaded. No clicks should be heard off the signal frequency. Checks should be made with no r.f. power but with the key breaking its normal current, to insure that local clicks are not gen-

erated by sparking at the key. To do a good job of checking clicks, those caused by sparking at the key must be eliminated independently of those generated by the keyed r.f. carrier.

### Chirps

Keying chirps may be checked by tuning in the signal or one of its harmonics on the highest frequency range of the receiver or monitor and listening to the beat-note in the normal manner. The gain should be sufficient to give moderate signal strength, but it should be low enough to avoid overloading. Adjust the tuning to give a low-frequency beat-note and key the transmitter at several different speeds. Any chirp introduced by the keying will show up. The signal should be tuned in on either side of zero beat and at various beat frequencies for a complete check. Listening to a harmonic magnifies the effect of any chirp and makes it easier to detect.

### Oscillator Keying

The keying of an amplifier is relatively straightforward and requires no special treatment, but considerable care may be necessary with oscillator keying. Any oscillator, either crystal or self-controlled, should oscillate at low voltages (on the order of two or three volts) and have negligible change in frequency with plate voltage, if it is to key without chirps or clicks. A crystal oscillator will oscillate at low voltages if a regenerative type such as the Tri-

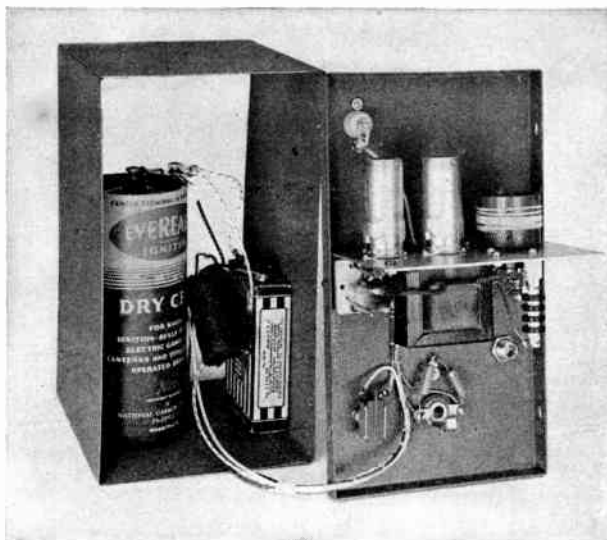


Fig. 8-13 — A view of the monitor disassembled, giving an idea of the arrangement of parts and the batteries. The tube shields cover the audio amplifier (left) and the oscillating detector (center).

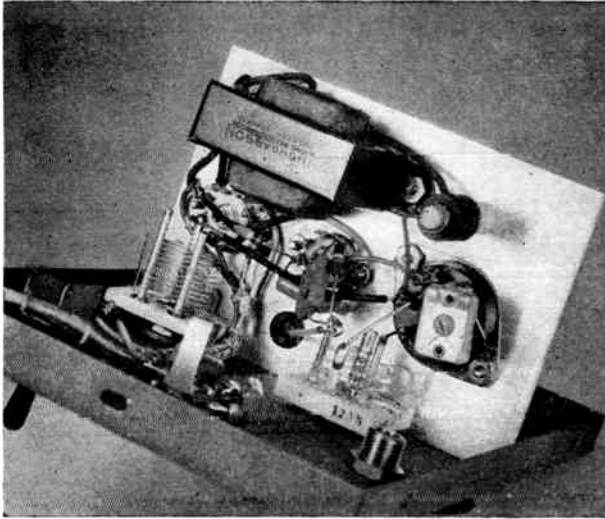


Fig. 8-14 — A close-up view of the underside of the monitor chassis, showing the main tuning condenser (right), the padding condenser mounted on the coil socket, and the feed-back control condenser.

tet or grid-plate is used and if an r.f. choke is connected in series with the grid-leak resistor, to reduce loading on the crystal. Crystal oscillators of this type are generally free from chirp unless the crystal is a poor one or if there is too much air gap in the crystal holder.

Self-controlled oscillators are more difficult to operate without chirp, but the important requirements are a high  $C$  to  $L$  ratio in the tank circuit, low plate (and screen) currents, and careful adjustment of the feed-back. A self-controlled oscillator intended to be keyed should be designed for best keying rather than maximum output.

#### Stages Following Keying

When a keying filter is being adjusted, the stages following the keyed stage should be made inoperative by removing the plate voltage. This allows the keying to be checked without masking by effects caused in the later stages. The following stages should then be connected in, one at a time, and the keying checked after each addition. An increase in click intensity (for the same carrier strength in the receiver) indicates that the clicks are being added in the stages following the one being keyed. The fixed bias on such stages should be sufficient to reduce the idling plate current (no excitation) to a low value, but not to zero. Under these conditions, any instability or tendency toward parasitic oscillations will show up. The output condensers on the filters of the power supplies feeding these later stages can often be increased to good advantage in reducing clicks introduced by these stages.

Low-frequency parasitic oscillations in later stages can cause key clicks removed from the signal frequency by 50 or 100 kc. These clicks are often difficult to track down, but they cause considerable interference and cannot be tolerated. They are most common in beam-tetrode stages, and

often can only be eliminated by neutralizing the tetrode stage. Since the parasitic oscillations are of a transient nature, and exist only during the make and break periods of keying, they are much harder to find than parasitics that are not transient.

#### MONITORING OF KEYING

Most operators find a keying monitor helpful in developing and maintaining a good "fist," especially if a "bug" or semiautomatic key is used. The most popular type of monitor is an audio oscillator which is keyed simultaneously with the transmitter. The output of the audio oscillator is coupled to the receiver headphones or loudspeaker. The circuit diagram for a simple monitor of this type is shown in Fig. 8-15. The plate voltage, as well as the heater voltage, is supplied by a 6.3-volt filament transformer. One section of the 6F8G dual triode is used as the rectifier to supply d.c. for the plate of the other section, and this latter section is used as the oscillator. A change in the value of  $R_1$  will alter the output tone. The output post marked "GND" should be connected directly to the receiver chassis, while "P<sub>1</sub>" should be connected to the "hot" side of the headphones. Shunting the headphones with the oscillator may cause some loss in volume from the receiver, unless the cou-

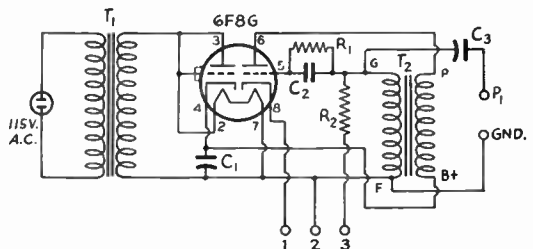


Fig. 8-15 — Circuit diagram of a keying monitor of the audio-oscillator type, with self-contained power supply.

$C_1$  — 25- $\mu$ fd. 25-volt electrolytic.

$C_2$  — 220- $\mu$ fd. mica.

$C_3$  — Approximately 0.01  $\mu$ fd. (see text).

$R_1$  — 0.15 megohm,  $\frac{1}{2}$  watt.

$R_2$  — Approximately 0.1 megohm, 1 watt.

$T_1$  — 6.3-volt 1-ampere filament transformer.

$T_2$  — Small audio transformer, interstage type.



pling capacitor,  $C_3$ , is made small. However, the capacitor should be made large enough to provide good transfer of the oscillator signal to the headphones or 'speaker.

If the transmitter oscillator is keyed for break-in, the keying terminals of the oscillator may be connected in parallel with those of the

transmitter. With cathode or negative-plate-supply keying, Terminals 1 and 2 should be connected across the key, with Terminal 2 going to the ground side. If blocked-grid keying is used, Terminals 1 and 2 should be connected to the ground side of the key and Terminal 3 to the "hot" (negative) side of the key.

## Break-In Operation

Break-in operation requires a separate receiving antenna, since none of the available antenna change-over relays is fast enough to follow keying. The receiving antenna should be installed as far as possible from the transmitting antenna. It should be mounted at right

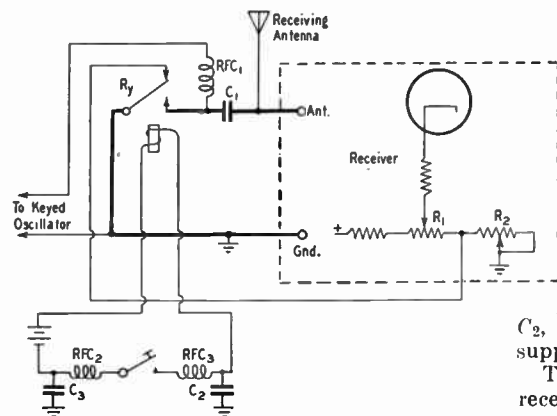


Fig. 8-16 — Wiring diagram for smooth break-in operation. The leads shown as heavy lines should be kept as short as possible, for minimum pick-up of the transmitter signal.

$C_1, C_2, C_3$  — 0.001  $\mu\text{f}$ .

$R_1$  — Receiver manual gain control.

$R_2$  — 5000- or 10,000-ohm wire-wound potentiometer.

$\text{RFC}_1, \text{RFC}_2, \text{RFC}_3$  — 2.5-mh. r.f. choke.

$R_y$  — S.p.d.t. keying relay.

angles to the transmitting antenna and fed with low-pick-up lead-in material such as coaxial cable or 300-ohm Twin-Lead, to minimize pick-up.

If a low-powered transmitter is used, it is often quite satisfactory to use no special equipment for break-in operation other than the separate receiving antenna, since the transmitter will not block the receiver too seriously. Even if the transmitter keys without clicks, some clicks will be heard when the receiver is tuned to the transmitter frequency because of overload in the receiver. An output limiter, as described in Chapter Five, will wash out these clicks and permit good break-in operation even on your transmitter frequency.

When powers above 25 or 50 watts are used, special treatment is required for quiet break-in on the transmitter frequency. A means should be provided for shorting the input of the receiver when the code characters are sent, and a means for reducing the gain of the receiver at

the same time is often necessary. The system shown in Fig. 8-16 permits quiet break-in operation for higher-powered stations. It requires a simple operation on the receiver but otherwise is perfectly straightforward.  $R_1$  is the regular receiver r.f. and i.f. gain control.

The ground lead is lifted on this control and run to a rheostat,  $R_2$ , that goes to ground. A wire from the junction runs outside the receiver to the keying relay,  $R_y$ . When the key is up, the ground side of  $R_1$  is connected to ground through the relay arm, and the receiver is in its normal operating condition. When the key is closed, the relay closes, which breaks the ground connection from  $R_1$  and applies additional bias to the tubes in the receiver. This bias is controlled by  $R_2$ . When the relay closes, it also closes the circuit to the transmitter oscillator.

$C_2, C_3, \text{RFC}_2$  and  $\text{RFC}_3$  is a keying filter to suppress the clicks caused by the relay current. The keying relay should be mounted on the receiver as close to the antenna terminals as possible, and the leads shown heavy in the diagram should be kept short, since long leads will allow too much signal to get through into the receiver. A good high-speed keying relay should be used. If a two-wire line is used from the receiving antenna, another r.f. choke,  $\text{RFC}_4$ , will be required. The revised portion of the schematic is shown in Fig. 8-17.

### ● A DE LUXE BREAK-IN SYSTEM

In many instances it is quite difficult to key an oscillator without clicks and chirps. Most oscillators will key without apparent chirp

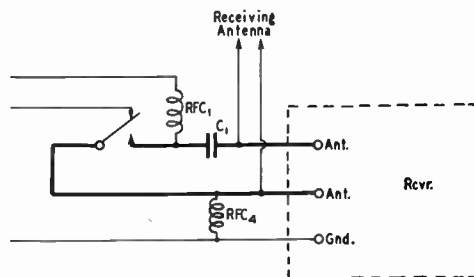


Fig. 8-17 — Necessary circuit revision of Fig. 8-16 if a two-wire lead from the receiving antenna is used.  $\text{RFC}_4$  is a 2.5-mh. r.f. choke — other values are the same as in Fig. 8-16.

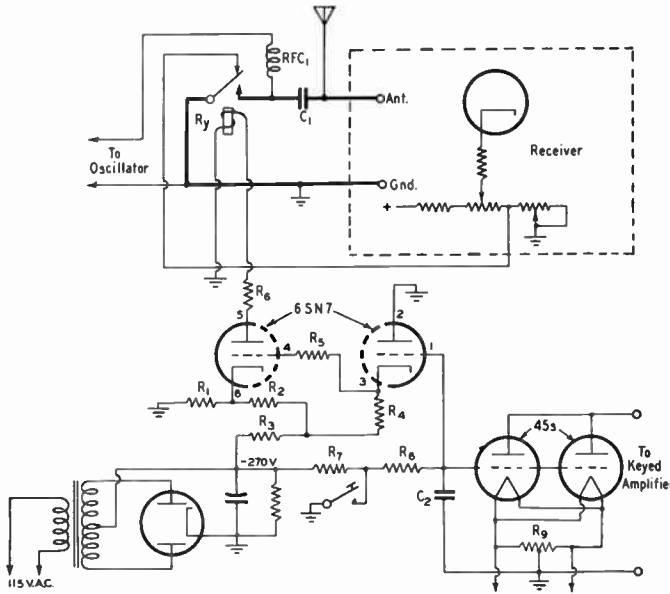


Fig. 8-18 — A de luxe break-in system that holds the oscillator circuit closed (and the receiver input shorted) during a string of fast dots but opens between letters or words.

- $C_1$  — 0.001  $\mu$ fd.  
 $C_2$  — 0.005  $\mu$ fd.  
 $R_1$  — 20,000 ohms, 10 watts, wire-wound.  
 $R_2$  — 1800 ohms.  
 $R_3$  — 1500 ohms.  
 $R_4, R_5$  — 1.0 megohm.  
 $R_6$  — 4700 ohms.  
 $R_7$  — 6.8 megohm.  
 $R_8$  — 0.47 megohm.  
 $R_9$  — 50-ohm center-tapped resistor, 2 watts.  
 All resistors 1-watt composition unless otherwise noted.  
 $RFC_1$  — 2.5-mh. r.f. choke.  
 $Ry$  — High-speed relay, 1400-ohm 18-volt coil (Stevens-Arnold Type 172 Millisec relay).

if the rise and decay times are made very short, but this introduces key clicks that cannot be avoided. The system shown in Fig. 8-18 avoids this trouble by turning on the oscillator quickly, keying an amplifier with a vacuum-tube keyer, and turning off the oscillator after the amplifier keying is finished. The oscillator is turned on and off without lag, but the resultant clicks are not passed through the transmitter. Actually, with keying speeds faster than about 15 w.p.m., the oscillator will stay turned on for a letter or even a word, but it turns off between words and allows the transmitting station to hear the "break" signal of the other station. It requires one tube more than the ordinary vacuum-tube keyer and a special high-speed relay.

As can be seen from Fig. 8-18, the circuit is a combination of the break-in system of Fig. 8-16 and the tube keyer of Fig. 8-9, with a 6SN7 tube and a few resistors added. Normally the left-hand portion of the 6SN7 is biased to a low value of plate current by the drop through  $R_2$  (part of the bleeder  $R_1R_2R_3$ ) and the relay is open. When the key is closed and  $C_2$  starts to discharge, the right-hand portion

of the 6SN7 draws current and this in turn puts a less-negative voltage on the grid of the left-hand portion. The tube draws current and the relay closes. The relay will stay closed until the negative voltage across  $C_2$  is close to the supply voltage, and consequently a string of dots or dashes (which don't give  $C_2$  a chance to charge to full negative) will keep the relay closed. In adjusting the system,  $R_2$  controls the amount of idling current through the relay and  $R_6$  determines the voltage across the relay.  $R_7, R_8$  and  $C_2$  are the normal resistors and condenser for the tube keyer. When adjusted properly, the relay will close without delay on the first dot and open quickly during the spaces between words or slower letters. When idling,

the voltage across the relay should be one or two volts — with the key down it should be 18 volts.

The oscillator should be designed to key as fast as possible, which means that series resistances and shunt capacitances should be held to a minimum. Negative-plate-lead keying is slightly faster than cathode keying and should be used in the oscillator. The keyer tubes are connected in the cathode circuit of an amplifier following the oscillator, far enough removed in the circuit to avoid reaction on the oscillator.

## ● ELECTRONIC KEYS

Electronic keys, as contrasted with mechanical automatic keys, use vacuum tubes (and possibly relays) to form automatic dashes as well as automatic dots. Full descriptions of such devices can be found in the following *QST* articles:

- Beecher, "Electronic Keying," April, 1940.  
 Grammer, "Inexpensive Electronic Key," May, 1940.  
 Savage, "Improved Switching Arrangement for Simplified Electronic Key," March, 1942.  
 Gardner, "New Electronic-Key Circuits," March, 1944.  
 Wiley, "Simplifying the Electronic Key," July, 1944.  
 "Electronic Bug Movement," Feb., 1945.  
 Snyder, "Versatile Electronic Key," March, 1945; correction, page 82, May, 1945.  
 Beecher, "Better Electronic Keyer," August, 1945.  
 DeHart, "De luxe Electronic Key," Sept., 1946; correction, page 27, Jan., 1947.

# Radiotelephony

To transmit intelligible speech by radio it is necessary to **modulate** the normally-constant output of the radio-frequency section of a transmitter. **Modulation**, defined in the most simple terms, is the process of varying the transmitter output in a desired fashion. In the case of radiotelephony, it means varying the radio-frequency output in a way that follows the spoken word.

The unmodulated r.f. output of the transmitter is called the **carrier**. In itself, the carrier conveys no information to the receiving operator — other than that the transmitting station is “on the air.” It is only when the carrier is modulated that it becomes possible to transmit a message.

## ● METHODS OF MODULATION

The carrier as generated by the transmitter is a simple form of alternating current — practically a sine wave. As such, it has three “dimensions” that can be varied — its amplitude, its frequency, and its phase. Modulation can be applied successfully to any of the three.

In **amplitude modulation (AM)** the amplitude of the carrier is made to vary upward and downward, following similar variations in audio-frequency currents generated by a microphone. In this type of modulation the frequency and phase of the carrier are unaffected by the modulation. Amplitude modulation is today the most widely-used system in amateur stations.

In **frequency modulation (FM)** the frequency of the carrier is made to vary above and below the unmodulated carrier frequency, the frequency variations being made to follow the a.f. currents. The power output of the transmitter does not change in frequency modulation. The *phase* of the carrier does change, however, since frequency and phase are intimately related.

In **phase modulation (PM)** the phase of the carrier is advanced and retarded by the modulating audio-frequency current. The transmitter power does not vary with modulation, but the carrier frequency changes.

These definitions are quite broad, and detailed explanations of the three systems are given later in this chapter.

## ● SIDEBANDS

No matter what the method of modulation, the process of modulating a carrier sets up new groups of radio frequencies both above and below the frequency of the carrier itself. These new frequencies that accompany the modulation are called **side frequencies**, and the frequency bands occupied by a group of them when the modulating signal is complex (as it is with voice modulation) are called **sidebands**. Sidebands always appear on *both* sides of the carrier; the band higher than the carrier frequency is called the **upper sideband** and the band lower than the carrier frequency is called the **lower sideband**. The modulation (that is, the intelligence) in the signal is carried in the sidebands, not in the carrier itself.

The result of this is that a modulated signal occupies a group or band of frequencies (**channel**) rather than the single frequency of the carrier alone. Just how much of a frequency band (that is how wide a channel) is occupied depends upon the method of modulation and the frequency characteristics of the modulating signal itself.

A normal voice contains frequencies or tones ranging from perhaps a hundred cycles at the low end to several thousand cycles at the high end. Vowel sounds (*a, e, i, o, u*) are in general fairly low in frequency and contain most of the voice power. Consonants usually are characterized by higher frequencies, and the hissing sound of the letter “S” is particularly high up in the audio-frequency range. The timbre of a voice, or the thing that makes it possible for us to distinguish the voices of different individuals, results principally from overtones or harmonics. All these things add up to the fact that a fairly wide range of audio frequencies is needed for the accurate reproduction of a *particular* voice.

On the other hand, the frequency range required for good *intelligibility* is not nearly so wide as that needed for accurate reproduction or “fidelity.” For the latter, an audio system that is “flat” — that is, has the same amplification at all frequencies — over the range up to about 10,000 cycles is required. But a system that “cuts off” above 2500 cycles — that is, has comparatively little output above that

figure — will transmit everything that is necessary for *understandable* speech. The speech may sound a little less like the speaker's actual voice, but it will be thoroughly intelligible to the receiving operator.

This distinction between intelligibility and "quality" is extremely important. The *minimum* channel occupied by a 'phone transmitter, no matter what the system of modulation, is equal to *twice the highest audio frequency present in the modulation*. If audio frequencies up to 10,000 cycles are contained in the modulation, the channel will be at least twice 10,000 or 20,000 cycles (20 kc.) wide. But if there are no frequencies above 2500 cycles in the modulation, the channel will be only 5000 cycles (5 kc.) wide. In amateur bands where there is a great deal of congestion it is in everybody's interest that each transmitter should occupy no more than the minimum channel needed for transmitting *intelligible* speech. Taking up a wider frequency channel than that simply creates unnecessary interference.

## Amplitude Modulation

In amplitude modulation, as we have already stated, the amplitude or strength of the carrier is varied up and down from the unmodulated value. The several methods of making the carrier strength vary are discussed in a later section; for the moment let us look only at the end result that is the object of all the various amplitude-modulation systems.

In Fig. 9-1, the drawing at A shows the unmodulated r.f. carrier, assumed to be a sine wave of the desired radio frequency. The graph can be taken to represent either voltage or current, and each cycle has just the same height as the preceding and following ones.

In B, the carrier wave is assumed to be modulated by a signal having the shape shown in the small drawing above. The frequency of the modulating signal is much lower than the carrier frequency, so quite a large number of carrier cycles can occur during each cycle of the modulating signal. This is a necessary condition for good modulation, and always is the case in radiotelephony because the audio frequencies used are very low compared with the radio frequency of the carrier. (Actually, there would be very many times more r.f. cycles in each modulation cycle than are shown in the drawing; so many that it is impossible to make the drawing to actual scale.) When the modulating signal is "positive" (above its axis) the carrier amplitude is increased *above* its unmodulated amplitude; when the modulating signal is "negative" the carrier amplitude is *decreased*. Thus the carrier grows larger and smaller with the polarity and amplitude of the modulating signal.

The drawing at C shows what happens with a stronger modulating signal. In this case the

Also, transmitting a wide range of audio frequencies in a congested band actually accomplishes nothing, insofar as "fidelity" is concerned; the receiving operator has to use so much receiver selectivity — in order to "copy" the signal at all — that the higher-frequency sidebands are rejected by the receiver. Those sidebands do, however, continue to interfere with stations operating on near-by carrier frequencies.

We have said that the *minimum* channel is equal to twice the highest audio frequency in the modulation. The actual channel occupied, may be several times the minimum necessary channel-width. This depends on the system of modulation used, for one thing. For another, it depends on whether the system is operated properly or whether it is misadjusted. Improper operation of any sort invariably increases the channel-width. Since the amount of frequency space available for amateur operation is limited, no operator of an amateur 'phone station can avoid the obligation to confine his transmissions to the least possible space.

strength of the modulation is such that on the "up" modulation the carrier amplitude is doubled at the instant the modulating signal reaches its positive peak. On the negative peak of the modulating signal the carrier amplitude just reaches zero; in other words, the carrier is "all used up."

### Percentage of Modulation

When a modulated wave is detected in a receiver the sound that comes out of the loud-

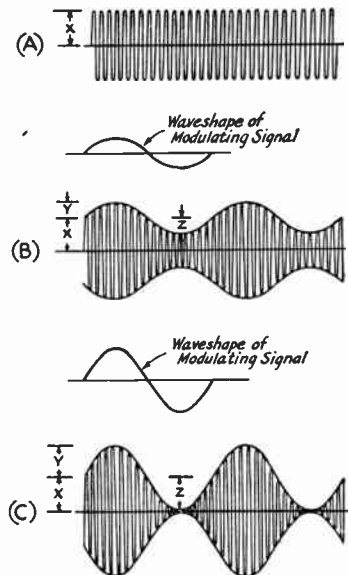


Fig. 9-1 — Graphical representation of (A) carrier unmodulated, (B) modulated 50%, (C) modulated 100%.

speaker or headset is caused by the modulation, not by the carrier. In other words, in detecting the signal the receiver eliminates the carrier and takes from it the modulating signal. The stronger the modulation, therefore, the greater is the useful receiver output. Obviously, it is desirable to make the modulation as strong or "heavy" as possible. A wave modulated as in Fig. 9-1C would produce considerably more useful signal than the one shown at B.

The "depth" of the modulation is expressed as a percentage of the unmodulated carrier amplitude. In either B or C, Fig. 9-1, *X* represents the unmodulated carrier amplitude, *Y* is the maximum increase in amplitude on the modulation up-peak, and *Z* is the maximum decrease in amplitude on the modulation down-peak. Assuming that *Y* and *Z* are equal, then the *percentage of modulation* can be found by dividing either *Y* or *Z* by *X* and multiplying the result by 100. In the wave shown in Fig. 9-1C, *Y* and *Z* are both equal to *X*, so the wave is modulated 100 per cent. In case the modulation is not symmetrical (*Y* and *Z* not equal), the larger of the two should be used for calculating the percentage of modulation.

The outline of the modulated wave is called the **modulation envelope**. It is shown by the thin line outlining the patterns in Figs. 9-1 and 9-2.

### Power in Modulated Wave

The amplitude values shown in Fig. 9-1 correspond to current or voltage, so the drawings may be taken to represent instantaneous values of either. Now power varies as the square of either the current or voltage (so long as the resistance in the circuit is unchanged), so at the peak of the modulation up-swing the instantaneous power in the wave of Fig. 9-1C is four times the unmodulated carrier power (because the current and voltage are doubled). At the peak of the down-swing the power is zero, since the amplitude is zero. With a sine-wave modulating signal, the *average* power in a 100-per-cent modulated wave is one and one-half times the value of unmodulated carrier power; that is, the power output of the transmitter increases 50 per cent with 100-per-cent modulation.

The complex waveform of speech does not contain as much power as there is in a pure tone or sine wave of the same peak amplitude. On the average, speech waveforms will contain only about half as much power as a sine wave, both having the same peak amplitude. The average power output of the transmitter therefore increases only about 25 per cent with 100-per-cent speech modulation. However, the *instantaneous* power output must quadruple on the peak of 100-per-cent modulation regardless of the modulating waveform. Therefore, the peak output-power capacity of the transmitter must be the same for any type of modulating signal.

### Overmodulation

If the carrier is modulated more than 100 per cent, a condition such as is shown in Fig. 9-2 occurs. Not only does the peak amplitude exceed twice the carrier amplitude, but there actually may be a considerable period during which the output is entirely cut off. Therefore the modulated wave is distorted, and the modulation contains harmonics of the audio modulating frequency.


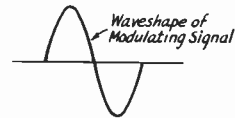


Fig. 9-2 — An over-modulated r.f. carrier wave.

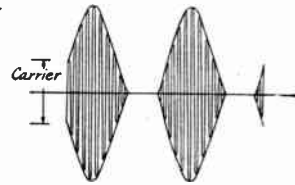

The sharp "break" when the carrier is suddenly cut off on the modulation down-swing produces a type of distortion that contains a large number of harmonics. For example, it is easily possible for harmonics up to the fifth to be produced by a relatively small amount of overmodulation. If the modulating frequency is 2000 cycles, this means that the actual modulated wave will have sidebands not only at 2000 cycles, but also at 4000, 6000, 8000 and 10,000 cycles each side of the carrier frequency. The signal thus occupies five times the needed channel-width. It is obviously of first importance to prevent the modulation from exceeding 100 per cent, and thus prevent the generation of spurious sidebands — commonly called "splatter."

### Carrier Requirements

For satisfactory amplitude modulation, the carrier *frequency* should be entirely unaffected by the application of modulation. If modulating the amplitude of the carrier also causes a change in the carrier frequency, the frequency will wobble back and forth with the modulation. This causes distortion and widens the channel taken by the signal. Thus unnecessary interference is caused to other transmissions. In practice, this undesirable frequency modulation is prevented by applying the modulation to an r.f. amplifier stage that is isolated from the frequency-controlling oscillator by a **buffer amplifier**. Amplitude modulation applied directly to an oscillator always is accompanied by frequency modulation. Under existing regulations amplitude modulation of an oscillator is permitted only on frequencies above 144 Mc. Below that frequency the regulations require that an amplitude-modulated transmitter be completely free from frequency modulation.

### Plate Power Supply

The d.c. power supply for the plate or plates of the modulated amplifier must be well filtered; if it is not, the plate-supply ripple will modulate the carrier and cause annoying hum. To be substantially hum-free, the ripple voltage should not be more than about 1 per cent of the d.c. output voltage.

In amplitude modulation the plate current varies at an audio-frequency rate; in other words, an alternating current is superimposed on the d.c. plate current. The output filter condenser in the plate supply must have low reactance, at the lowest audio frequency in the modulation, if the transmitter is to modulate equally well at all audio frequencies. The condenser capacitance required depends on the ratio of d.c. plate current to plate voltage in the modulated amplifier. The requirements will be met satisfactorily if the capacitance of the output condenser is at least equal to

$$C = 25 \frac{I}{E}$$

where  $C$  = Capacitance of output condenser in  $\mu\text{fd}$ .

$I$  = D.c. plate current of modulated amplifier in milliamperes

$E$  = Plate voltage of modulated amplifier

Example: A modulated amplifier operates at 1250 volts and 275 ma. The capacitance of the output condenser in the plate-supply filter should be at least

$$C = 25 \frac{I}{E} = 25 \times \frac{275}{1250} = 25 \times 0.22 = 5.5 \mu\text{fd}.$$

### Linearity

Up to the limit of 100-per-cent modulation, the amplitude of the r.f. output should be directly proportional to the amplitude of the modulating signal. Fig. 9-3 is a graph of an ideal modulation characteristic, or curve, showing the relationship between r.f. output amplitude and modulating-signal amplitude. The modulation swings the amplitude back and forth along the curve  $A$  as the modulating signal alternately swings positive and negative. Assuming that the negative peak of the modulating signal is just sufficient to reduce the carrier amplitude to zero (modulating signal equal to  $-1$  in the drawing), the same modulating signal peak in the *positive* direction ( $+1$ ) should cause the r.f. amplitude to reach twice its unmodulated-carrier value. The ideal modulation characteristic is a straight line, as shown by curve  $A$ . Such a modulation characteristic is perfectly linear.

A nonlinear characteristic is shown by curve  $B$ . The r.f. amplitude does not reach twice the unmodulated carrier amplitude when the modulating signal reaches its positive peak. A modulation characteristic of this type gives a modulation envelope that is "flattened" on the up-peak; in other words, the modulation envelope is not an exact reproduction of the

modulating signal. It is therefore distorted and harmonics are generated, causing the transmitted signal to occupy a wider channel than is necessary. A nonlinear modulation characteristic can easily result when a transmitter is not properly designed or is misadjusted.

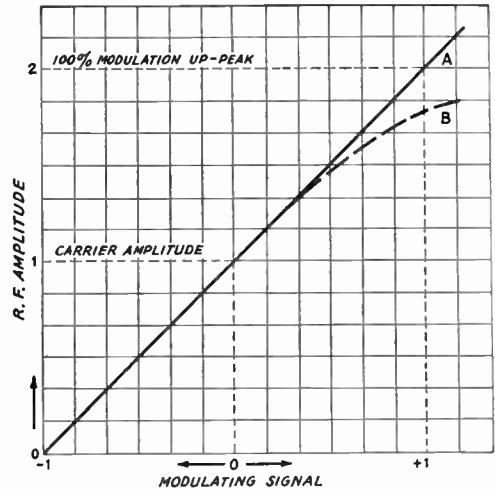


Fig. 9-3—The modulation characteristic shows the relationship between the instantaneous amplitude of the r.f. output and the instantaneous amplitude of the modulating signal. The ideal characteristic is a straight line, as shown by curve  $A$ .

The modulation capability of the transmitter is the maximum percentage of modulation that is possible without objectionable distortion from nonlinearity. The maximum capability is 100 per cent on the down-peak but can be higher on the up-peak. The modulation capability should be as high as possible, so that the most effective signal can be transmitted for a given carrier power.

### Types of Amplitude Modulation

The most widely-used amplitude-modulation system is that in which the modulating signal is applied in the plate circuit of a radio-frequency power amplifier (**plate modulation**). In a second type the audio signal is applied to a control grid (**grid-bias modulation**). A third system, involving variation of both plate and grid voltages, is called **cathode modulation**.

## ● PLATE MODULATION

The most popular system of amplitude modulation is plate modulation. It is the simplest to apply, gives the highest efficiency in the modulated amplifier, and is the easiest to adjust for proper operation.

Fig. 9-4 shows the most widely-used system of plate modulation. A balanced (push-pull Class A, Class AB or Class B) modulator is transformer-coupled to the plate circuit of the modulated r.f. amplifier. The audio-frequency power generated by the modulator is com-

bined with the d.c. power in the modulated-amplifier plate circuit by transfer through the coupling transformer, *T*. For 100-per-cent modulation the audio-frequency output of the modulator and the turns ratio of the coupling transformer must be such that the voltage at the plate of the modulated amplifier varies between zero and twice the d.c. operating plate voltage, thus causing corresponding variations in the amplitude of the r.f. output.

As stated earlier, the average power output of the modulated stage must increase during modulation. The modulator must be capable of supplying to the modulated r.f. stage sine-wave audio power equal to 50 per cent of the d.c. plate input. For example, if the d.c. plate power input to the r.f. stage is 100 watts, the sine-wave audio power output of the modulator must be 50 watts.

### Modulating Impedance; Linearity

The modulating impedance, or load resistance presented to the modulator by the modulated r.f. amplifier, is equal to

$$\frac{E_b}{I_p} \times 1000$$

where  $E_b$  = D.c. plate voltage  
 $I_p$  = D.c. plate current (ma.)

$E_b$  and  $I_p$  are measured without modulation.

The power output of the r.f. amplifier must vary as the square of the plate voltage (the r.f. voltage must be proportional to the applied plate voltage) in order for the modulation to be linear. This will be the case when the amplifier operates under Class C conditions. The linearity then depends upon having sufficient grid excitation and proper bias, and upon the adjustment of circuit constants to the proper values.

### Adjustment of Plate-Modulated Amplifiers

The general operating conditions for Class C operation have been described in Chapter Six. The grid bias and grid current required for plate modulation usually are given in the operating data supplied by the tube manufacturer; in general, the bias should be such as to give an operating angle of about 120 degrees at carrier plate voltage, and the grid excitation should be great enough so that the amplifier's plate efficiency will stay constant when the plate voltage is varied over the range from zero to twice the unmodulated value. For best linearity, the grid bias should be obtained partly from a fixed source of about the cut-off value, and then supplemented by grid-leak bias to supply the remainder of the required operating bias.

The maximum permissible d.c. plate power input for 100-per-cent modulation is twice the sine-wave audio-frequency power output of the modulator. This input is obtained by varying the loading on the amplifier (keeping its tank circuit tuned to resonance) until the product

of d.c. plate voltage and plate current is the desired power. The modulating impedance under these conditions must be transformed to the proper value for the modulator by using the correct output-transformer turns ratio. This point is considered in detail later in this chapter in the section on Class B modulator design.

Neutralization, when triodes are used, should be as nearly perfect as possible, since regeneration may cause nonlinearity. The amplifier also must be completely free from parasitic oscillations.

Although the *effective* value of power input increases with modulation, as described above, the *average* d.c. plate power input to a plate-modulated amplifier does not change. This is because each increase in plate voltage and plate current is balanced by an equivalent decrease in voltage and current on the next half-cycle of the modulating signal. The d.c. plate current to a properly-modulated amplifier is always constant, with or without modulation. On the other hand, an r.f. ammeter connected in the antenna or transmission line will show an increase in r.f. current with modulation.

### Screen-Grid Amplifiers

Screen-grid tubes of the pentode or beam-tetrode type can be used as Class C plate-modulated amplifiers by applying the modula-

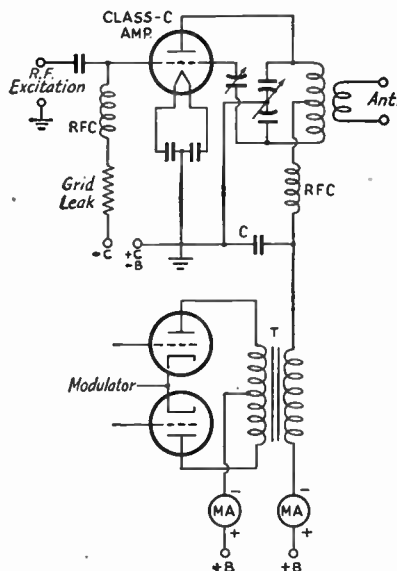


Fig. 9-4 — Plate modulation of a Class C r.f. amplifier. The r.f. plate by-pass condenser, *C*, in the amplifier stage should have reasonably high reactance at audio frequencies. (See section on Class B modulators.)

tion to both the plate and screen grid. The usual method of feeding the screen grid with the necessary d.c. and modulation voltage is shown in Fig. 9-5. The dropping resistor, *R*, should be of the proper value to apply normal d.c. voltage to the screen under steady carrier

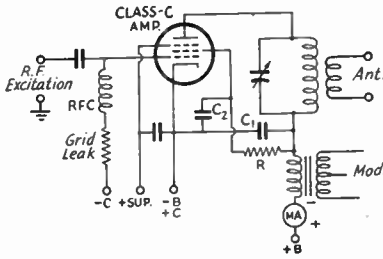


Fig. 9-5 — Plate and screen modulation of a Class C r.f. amplifier using a pentode tube. The plate r.f. by-pass condenser,  $C_1$ , should have reasonably high reactance at all audio frequencies. (See section on Class B modulators.) The screen by-pass,  $C_2$ , should be 0.002  $\mu$ fd. or less in the usual case.

conditions. Its value can be calculated by taking the difference between plate and screen voltages and dividing it by the rated screen current.

The modulating impedance is found by dividing the d.c. plate voltage by the sum of the plate and screen currents. The plate voltage multiplied by the sum of the two currents gives the power input to be used as the basis for determining the audio power required from the modulator.

Modulation of the screen along with the plate is necessary because both elements affect the plate current in a power-type screen-grid tube, and a linear modulation characteristic cannot be obtained by modulating the plate alone. However, at least some types of beam tetrodes (the 4-250A and 4-125A, for example) can be modulated satisfactorily by applying the modulating power to the plate circuit alone, provided the screen is "floating" at audio frequencies — that is, is not grounded for a.f. but is connected to its d.c. supply through an audio impedance. The circuit is shown in Fig. 9-6. The choke coil  $L_1$  is the audio impedance in the screen circuit; its inductance should be large enough to have a reactance (at the lowest desired audio frequency) that is not less than the impedance of the screen. The latter can be taken to be approximately equal to the d.c. screen voltage divided by the d.c. screen current.

**Choke Coupling**

Fig. 9-7 shows the circuit of the choke-coupled system of plate modulation. The d.c. plate power for both the modulator tube and modulated amplifier is furnished from a common source through the modulation choke,  $L$ . This choke must have high impedance, compared to the modulating impedance of the Class C amplifier, for audio frequencies. The modulator operates as a power amplifier with the plate circuit of the r.f. amplifier as its load, the audio output of the modulator being superimposed on the d.c. power supplied to the amplifier.

For 100-per-cent modulation, the audio volt-

age applied to the r.f. amplifier plate circuit across the choke,  $L$ , must have a peak value equal to the d.c. voltage on the modulated amplifier. To obtain this without distortion the r.f. amplifier must be operated at a lower d.c. plate voltage than the modulator. The extent of the voltage difference is determined by the type of modulator tube used. The necessary drop in voltage is provided by the resistor,  $R_1$ , which is by-passed for audio frequencies by the by-pass condenser,  $C_1$ .

This type of modulation seldom is used except in very low-power portable sets, because a Class A modulator is required. The output of a Class A modulator is very low compared to the power obtainable from a pair of tubes of the same size operated Class B, so only a small amount of r.f. power can be modulated.

● **GRID-BIAS MODULATION**

Fig. 9-8 is the diagram of a typical arrangement for grid-bias modulation. In this system, the secondary of an audio-frequency output transformer, the primary of which is connected in the plate circuit of the modulator tube, is connected in series with the grid-bias supply for the modulated amplifier. The audio voltage varies the grid bias, and thereby the power output of the r.f. stage. The r.f. stage is operated as a Class C amplifier.

In this system the plate voltage is constant, and the increase in power output with modulation is obtained by making both the plate current and plate efficiency vary with the mod-

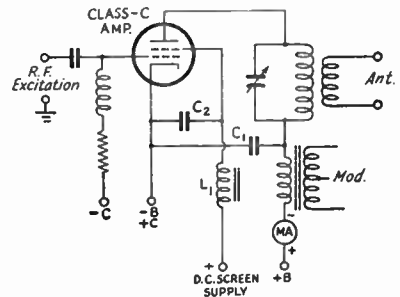


Fig. 9-6 — Plate modulation of a beam tetrode, using an audio impedance in the screen circuit. The value of  $L_1$  is discussed in the text. See Fig. 9-5 for data on by-pass capacitors  $C_1$  and  $C_2$ .

ulating signal. For 100-per-cent modulation, both plate current and efficiency must, at the peak of the modulation up-swing, be twice their carrier values. Thus at the modulation peak the power input is doubled, and since the plate efficiency also is doubled at the same instant the peak output power will be four times the carrier power. The maximum efficiency obtainable in practicable circuits is of the order of 70 to 80 per cent, so the carrier efficiency ordinarily cannot exceed about 35



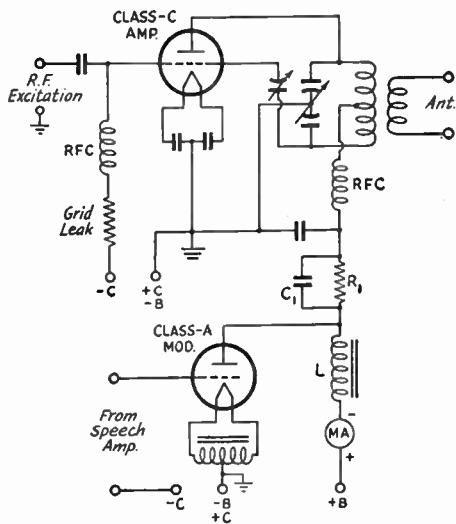


Fig. 9-7—Choke-coupled plate modulation.

to 40 per cent. For a given r.f. tube, the carrier output is about one-fourth the power obtainable from the same tube plate-modulated.

### Modulator Power

The increase in average carrier power with modulation is secured by varying the plate efficiency and d.c. plate input of the amplifier, so the modulator need supply only such power losses as may be occasioned by connecting it in the grid circuit. Since these are quite small, a modulator capable of only a few watts output will suffice.

The load on the modulator varies over the a.f. cycle as the rectified grid current of the modulated amplifier changes, so the modulator must have good voltage regulation. The purpose of the resistor  $R$  across the primary of the modulation transformer in Fig. 9-8 is to "swamp" such load changes by dissipating most of the audio power in the resistor. Generally, this resistor should be approximately equal to the load resistance required by the particular type of modulator tube used. The turns ratio of transformer  $T$  should be about 1-to-1 in most practical cases.

### Grid-Bias Source

The change in instantaneous bias voltage with modulation causes the rectified grid current of the amplifier also to vary, the r.f. excitation being fixed. If the bias source has appreciable resistance, the change in grid current will cause a change in bias in a direction opposite to that caused by the modulation. It is necessary, therefore, to use a grid-bias source having low resistance, so that these bias variations will be negligible. Battery bias is satisfactory. If a rectified a.c. bias supply is used, the type having regulated output should be chosen (see Chapter Seven). Grid-leak bias for a grid-modulated amplifier is un-

satisfactory, and its use should never be attempted.

### Driver Regulation

The load on the r.f. driving stage varies with modulation, and a linear modulation characteristic cannot be obtained if the r.f. voltage from the driver does not stay constant with changes in load. Driver regulation (ability to maintain constant output voltage with changes in load) may be improved by using a driving stage having two or three times the power output necessary for excitation of the amplifier (which is less than the power required for ordinary Class C operation), and dissipating the extra power in a constant load such as a resistor. The variations caused by changes in load with modulation are thereby reduced because the variable load is only a fraction of the total load.

### Operating Conditions

The d.c. plate input to the modulated amplifier, assuming a round figure of  $\frac{1}{3}$  (33 per cent) for the plate efficiency, should not exceed  $1\frac{1}{2}$  times the plate dissipation rating of the tube or tubes used in the modulated stage. On the modulation up-peaks the d.c. plate current doubles instantaneously but the d.c. plate voltage does not change. The problem, therefore, is to choose a set of operating conditions that will give normal Class C efficiency when the plate current is twice the carrier value.

Example: Two tubes having plate dissipation ratings of 55 watts each are to be used with grid-bias modulation. With plate modulation, the ratings are 1250 volts and 250 ma. for the two tubes, so the plate-voltage/plate-current ratio is

$$\frac{E \text{ (volts)}}{I \text{ (ma.)}} = \frac{1250}{250} = 5$$

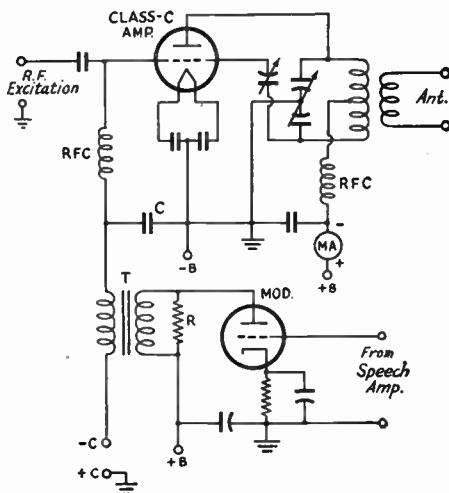


Fig. 9-8—Grid-bias modulation of a Class C amplifier. The r.f. grid by-pass condenser,  $C$ , should have high reactance at audio frequencies (0.005  $\mu$ f. or less).

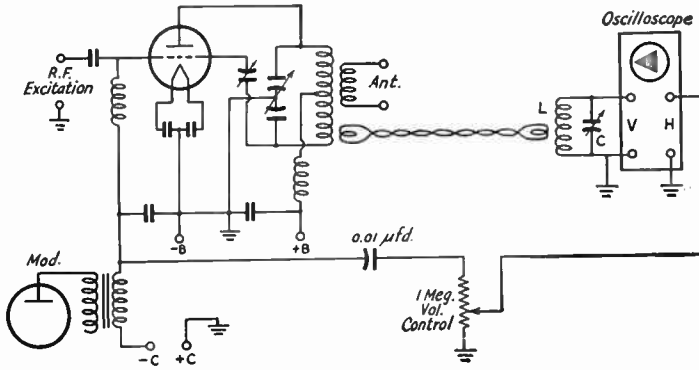


Fig. 9-9 — Adjustment set-up for grid-bias modulation. *L* and *C* should tune to the operating frequency, and may be coupled to the transmitter tank circuit through a twisted pair or other low-impedance line, using single-turn links at each end. The 0.01-μfd. blocking condenser that couples the audio voltage to the horizontal plates of the oscilloscope should have a voltage rating equal to about three times the grid bias.

With grid-bias modulation the maximum power input, at 33% efficiency, is  
 $P = 1.5 \times (2 \times 55) = 1.5 \times 110 = 165$  watts  
 The maximum recommended plate voltage for these tubes is 1500 volts. Using this figure, the plate current for the two tubes will be

$$I = \frac{P}{E} = \frac{165}{1500} = 0.11 \text{ amp.} = 110 \text{ ma.}$$

The plate-voltage/plate-current ratio at *twice* carrier plate current is

$$\frac{1500}{220} = 6.8$$

This is quite satisfactory. In this case it would be possible to use a lower plate voltage without having the plate-voltage/plate-current ratio drop to too low a value. At 1300 volts, for example, the ratio would be slightly over 5. However, at 1000 volts it would be only 3.

At 33% efficiency, the carrier output to be expected is 55 watts.

The tank-circuit *L/C* ratio should be chosen on the basis of *twice* the carrier plate current. In the example above, it would be based on a plate-voltage/plate-current ratio of 6.8. Note that if *carrier* conditions are used the ratio is 13.6, and a tank *L/C* ratio based on this figure would have a *Q* much too low for good coupling to the output circuit.

Since the amplifier operates in normal Class C fashion on the modulation up-peaks, the grid bias should be chosen for Class C operation at the plate voltage used. It may be higher if desired, but should never be lower. It is convenient to have an adjustable bias source for arriving at optimum operating conditions.

**Adjustment**

This type of modulated amplifier should be adjusted with the aid of an oscilloscope. The oscilloscope should be connected as shown in Fig. 9-9. A tone source for modulating the transmitter is a convenience, since a steady tone will give a steady pattern on the oscilloscope. A steady pattern is easier to study than one that flickers with voice modulation.

Having determined the permissible carrier plate current as previously described, apply r.f. excitation and plate voltage and, without modulation, adjust the plate loading to give the required plate current (keeping the plate tank circuit tuned to resonance). Next, apply

modulation and increase the modulating signal until the modulation characteristic shows curvature (see later section in this chapter for use of the oscilloscope). If curvature occurs well below 100-per-cent modulation, the plate efficiency is too high. Increase the plate loading slightly and reduce the excitation to maintain the same plate current; then apply modulation and check the characteristic again. Continue this process until the characteristic is linear from the horizontal axis to twice the carrier amplitude. It is usually easier to obtain a more linear characteristic with high plate voltage and low current (carrier conditions) than with relatively low plate voltage and high plate current.

**Suppressor Modulation**

The circuit arrangement for suppressor-grid modulation of a pentode tube is shown in Fig. 9-10. The operating principles are the same as for grid-bias modulation. However, the r.f. excitation and modulating signals are applied to separate grids; this makes the system somewhat simpler to operate because best adjustment for proper excitation requirements and proper modulating-circuit requirements are more or less independent. The carrier plate efficiency is approximately the same as for grid-bias modulation, and the modulator power requirements are similarly small. With tubes having suitable suppressor-grid charac-

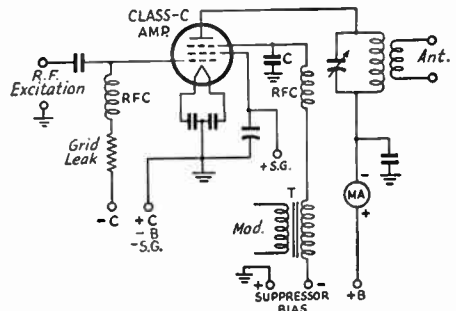


Fig. 9-10 — Suppressor-grid modulation of an r.f. amplifier using a pentode-type tube. The suppressor-grid r.f. by-pass condenser, *C*, should be the same as the grid by-pass condenser in grid-bias modulation (Fig. 9-8).

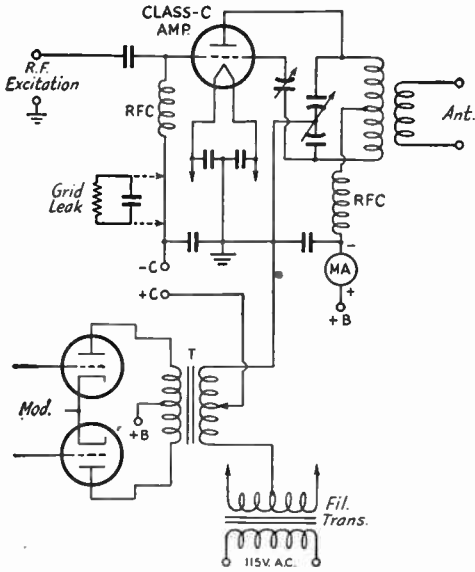


Fig. 9-11 — Circuit arrangement for cathode modulation of a Class C r.f. amplifier.

teristics, linear modulation up to practically 100 per cent can be obtained with negligible distortion.

The method of adjustment of this system is essentially the same as that described in the preceding paragraph.

**CATHODE MODULATION**

**Circuit**

The fundamental circuit for cathode or "center-tap" modulation is shown in Fig. 9-11. This type of modulation is a combination of the plate and grid-bias methods, and permits a carrier efficiency midway between the two. The audio power is introduced in the cathode circuit, and both grid bias and plate voltage vary during modulation.

Because part of the modulation is by the grid-bias method, the plate efficiency of the modulated amplifier must vary during modulation. The carrier efficiency therefore must be lower than the efficiency at the modulation peak. The required reduction in efficiency depends upon the proportion of grid modulation to plate modulation; the higher the percentage of plate modulation, the higher the permissible carrier efficiency, and vice versa. The audio power required from the modulator also varies with the percentage of plate modulation, being greater as this percentage is increased.

The way in which the various quantities vary is illustrated by the curves of Fig. 9-12. In these curves the performance of the cathode-modulated r.f. amplifier is plotted in terms of the tube ratings for plate-modulated telephony, with the percentage of plate modulation as a base. As the percentage of plate modulation is decreased, it is assumed that

the grid-bias modulation is increased to make the over-all percentage of modulation reach 100 per cent. The limiting condition, 100-per-cent plate modulation and no grid-bias modulation, is at the right (A); pure grid-bias modulation is represented by the left-hand ordinate (B and C).

Example: Assume that the r.f. tube to be used has a 100% plate-modulation rating of 250 watts input and will give a carrier power output of 190 watts at that input. Cathode modulation with 40% plate modulation is to be used. From Fig. 9-12, the carrier efficiency will be 56% with 40% plate modulation, the permissible d.c. input will be 65% of the plate-modulation rating, and the r.f. output will be 48% of the plate-modulation rating. That is,

Power input = 250 × 0.65 = 162.5 watts  
 Power output = 190 × 0.48 = 91.2 watts

The required audio power, from the chart, is equal to 20% of the d.c. input to the modulated amplifier. Therefore

Audio power = 162.5 × 0.2 = 32.5 watts

The modulator should supply a small amount of extra power to take care of losses in the grid circuit. These should not exceed four or five watts.

**Modulating Impedance**

The modulating impedance of a cathode-modulated amplifier is approximately equal to

$$m \frac{E_b}{I_b}$$

where  $m$  = Percentage of plate modulation (expressed as a decimal)

$E_b$  = D.c. plate voltage on modulated amplifier

$I_b$  = D.c. plate current of modulated amplifier

Example: Assume that the modulated amplifier in the example above is to operate at a plate

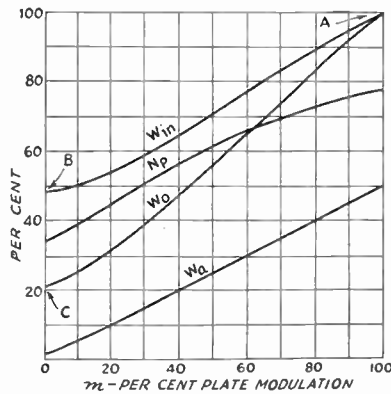


Fig. 9-12 — Cathode-modulation performance curves, in terms of percentage of plate modulation plotted against percentage of Class C telephony tube ratings.  $W_{in}$  — D.c. plate input watts in terms of percentage of plate-modulation rating.  $W_0$  — Carrier output watts in per cent of plate-modulation rating (based on plate efficiency of 77.5%).  $W_a$  — Audio power in per cent of d.c. watts input.  $\eta_p$  — Plate efficiency of the amplifier in percentage.

potential of 1250 volts. Then the d.c. plate current is

$$I = \frac{P}{E} = \frac{162.5}{1250} = 0.13 \text{ amp. (130 ma.)}$$

The modulating impedance is

$$m \frac{E_b}{I_b} = 0.4 \frac{1250}{0.13} = 3846 \text{ ohms}$$

The modulating impedance is the load into which the modulator must work, just as in the case of pure plate modulation. This load must be matched to the load required by the modulator tubes by proper choice of the turns ratio of the modulation transformer.

#### Conditions for Linearity

R.f. excitation requirements for the cathode-modulated amplifier are midway between those for plate modulation and grid-bias modulation. More excitation is required as the percentage of plate modulation is increased. Grid bias should be considerably beyond cut-off; fixed bias from a supply having good voltage regulation is preferred, especially when the percentage of plate modulation is small and the amplifier is operating more nearly like a grid-bias modulated stage. At the higher percentages of plate modulation a combination of fixed and grid-leak bias can be used, since the variation in rectified grid current is smaller. The grid leak should be by-passed for audio frequencies. The percentage of grid modulation

may be regulated by choice of a suitable tap on the modulation-transformer secondary.

The cathode circuit of the modulated stage must be independent of other stages in the transmitter. That is, when directly-heated tubes are modulated their filaments must be supplied from a separate transformer. The filament by-pass condensers should not be larger than about 0.002  $\mu$ fd., to avoid by-passing the audio-frequency modulation.

#### Adjustment of Cathode-Modulated Amplifiers

In most respects, the adjustment procedure is similar to that for grid-bias modulation. The critical adjustments are antenna loading, grid bias, and excitation. The proportion of grid-bias to plate modulation will determine the operating conditions.

Adjustments should be made with the aid of an oscilloscope connected in the same way as for grid-bias modulation. With proper antenna loading and excitation, the normal wedge-shaped pattern will be obtained at 100-per-cent modulation. As in the case of grid-bias modulation, too-light antenna loading will cause flattening of the upward-peaks of modulation as also will too-high excitation. The cathode current will be practically constant with or without modulation when the proper operating conditions have been established.

## Speech Equipment

In designing speech equipment it is necessary to "work from both ends." That is, we must know, simultaneously, (1) the amount of audio power the modulation system must furnish and (2) the output voltage developed by the microphone when it is spoken into from normal distance (a few inches) with ordinary loudness. It then becomes possible to choose the number and type of amplifier stages needed to generate the required audio power without overloading or distortion anywhere along the line.

The starting point is the microphone.

### ● MICROPHONES

In this age, no one needs an introduction to the microphone. However, there are several different types of them, considerably different in characteristics. Before considering the various types, it is necessary to define a few terms used in connection with microphones.

The level of a microphone is its electrical output for a given sound intensity. Level varies greatly with microphones of different basic types, and also varies between different models of the same type. The output is also greatly dependent on the character of the individual voice (that is, the audio frequencies present in the voice) and the distance of the

speaker's lips from the microphone. It decreases approximately as the square of the distance. Because of these variables, only approximate values based on averages of "normal" speaking voices can be given. The values in the following paragraphs are based on close talking; that is, with the microphone about an inch from the speaker's lips.

The frequency response or fidelity of a microphone is its relative ability to convert sounds of different frequencies into alternating current. With fixed sound intensity at the microphone, the electrical output may vary considerably as the sound frequency is varied. For understandable speech transmission only a limited frequency range is necessary, and intelligible speech can be obtained if the output of the microphone does not vary more than a few decibels at any frequency within a range of about 200 to 2500 cycles. When the variation expressed in terms of decibels is small between two frequency limits, the microphone is said to be flat between those limits.

#### Carbon Microphones

The carbon microphone consists of a metal diaphragm placed against an insulating cup containing loosely-packed carbon granules (microphone button). Current from a battery flows through the granules, the diaphragm be-

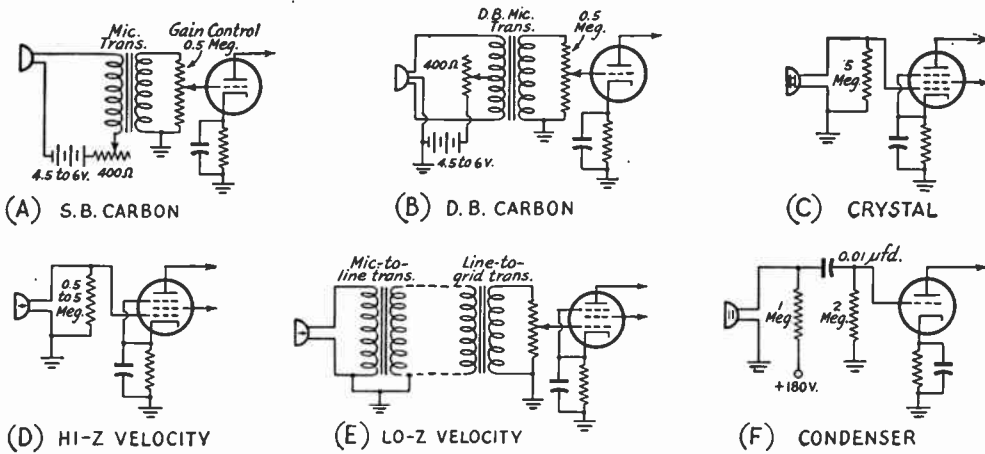


Fig. 9-13 — Speech input circuits for various types of microphones.

ing one connection and the metal backplate the other. Fig. 9-13A and B shows connections for single- and double-button carbon microphones, with a rheostat included in each circuit for adjusting the button current to the correct value as specified with each microphone. The primary of a transformer is connected in series with the battery and microphone.

As the diaphragm vibrates, its pressure on the granules alternately increases and decreases, causing a corresponding increase and decrease of current flow through the circuit, since the pressure changes the resistance of the mass of granules. The resulting change in the current flowing through the transformer primary causes an alternating voltage, of corresponding frequency and intensity, to be set up in the transformer secondary. In the double-button type the two buttons are in push-pull.

Good quality single-button carbon microphones give outputs ranging from 0.1 to 0.3 volt across 50 to 100 ohms; that is, across the primary winding of the microphone transformer. With the step-up of the transformer, a peak voltage of between 3 and 10 volts can be assumed to be available at the grid of the amplifier tube. The usual button current is 50 to 100 ma.

The level of good-quality double-button microphones is considerably less, ranging from 0.02 volt to 0.07 volt across 200 ohms. With this type of microphone and the usual push-pull input transformer, a peak voltage of 0.4 to 0.5 can be assumed available at the first speech-amplifier grid. The button current with this type of microphone ranges from 5 to 50 ma. per button. Double-button microphones have better frequency response and less distortion than the single-button type.

**Crystal Microphones**

The crystal microphone makes use of the piezoelectric properties of Rochelle salts crystals. This type of microphone requires no battery or transformer and can be connected

directly to the grid of an amplifier tube. It is the most popular type of microphone among amateurs, for these reasons as well as the fact that it has good frequency response and is available in inexpensive models.

The "communications-type" crystal microphone uses a diaphragm mechanically coupled to a crystal. This type of construction gives good sensitivity and adequate frequency response for speech. In higher-fidelity types the sound acts directly on a pair of crystals cemented together, with plated electrodes. The level with the latter construction is considerably less. The input circuit for either model of crystal microphone is shown in Fig. 9-13C.

Although the level of crystal microphones varies with different models, an output of 0.03 volt or so is representative for communication types. The level is affected by the length of the cable connecting the microphone to the first amplifier stage; the above figure is for lengths of 6 or 7 feet. The frequency characteristic is unaffected by the cable, but the load resistance (amplifier grid resistor) does affect it; the lower frequencies are attenuated as the value of load resistance is lowered. A grid-resistor value of at least 1 megohm should be used for reasonably flat response, 5 megohms being a customary figure.

**Velocity and Dynamic Microphones**

In a velocity or "ribbon" microphone, the element acted upon by the sound waves is a thin corrugated metallic ribbon suspended between the poles of a magnet. When vibrating, the ribbon cuts the lines of force between the poles, first in one direction and then the other, thus generating an alternating voltage. The movement of the ribbon is proportional to the velocity of the air particles set in motion by the sound.

Velocity microphones are built in two types, high impedance and low impedance, the former being used in most applications. A high-impedance microphone can be directly connected

to the grid of an amplifier tube, shunted by a resistance of 0.5 to 5 megohms (Fig. 9-13D). Low-impedance microphones are used when a long connecting cable (75 feet or more) must be employed. In such a case the output of the microphone is coupled to the first amplifier stage through a suitable step-up transformer, as shown in Fig. 9-13E.

The level of the velocity microphone is about 0.03 to 0.05 volt. This figure applies directly to the high-impedance type, and to the low-impedance type when the voltage is measured directly across the coupling-transformer secondary.

The **dynamic microphone** somewhat resembles a dynamic loudspeaker. A light weight voice coil is rigidly attached to a diaphragm, the coil being placed between the poles of a permanent magnet. Sound causes the diaphragm to vibrate, thus moving the coil back and forth between the magnet poles and generating an alternating voltage. The frequency of the generated voltage is proportional to the frequency of the sound waves and the amplitude is proportional to the sound pressure.

The dynamic microphone usually is built with high-impedance output, suitable for working directly into the grid of an amplifier tube. If the connecting cable must be unusually long, a low-impedance type should be used, with a step-up transformer at the end of the cable.

A small permanent-magnet 'speaker can be used as a dynamic microphone, although the fidelity is not as good as is obtainable with a properly-designed microphone.

#### Condenser Microphones

The **condenser microphone** consists of a two-plate capacitance, with one plate stationary. The other, which is separated from the first by about a thousandth of an inch, is a thin metal membrane serving as a diaphragm. This condenser is connected in series with a resistor and a d.c. voltage source, as shown in Fig. 9-13F. When sound waves cause the diaphragm to vibrate, the change in capacitance causes a small charging current to flow through the circuit. The resulting audio voltage that appears across the resistor is fed to the grid of the tube through the coupling condenser.

The output of condenser microphones varies with different models, the high-quality type being about one-hundredth to one-fiftieth as sensitive as the double-button carbon microphone. The first speech-amplifier stage must be built into the microphone, since the capacity of a connecting cable would impair both output and frequency range. Also, this "pre-amplifier" must be battery operated, because the microphone output is so low that the least hum would be objectionable. This is cumbersome, and the microphone itself is expensive in construction because of the high precision required. As a result, the condenser microphone finds little present-day application.

### THE SPEECH AMPLIFIER

In common terminology, the audio-frequency amplifier stage that actually causes the r.f. carrier output to be varied is called the **modulator**, and all the amplifier stages preceding it comprise the **speech amplifier**. Depending on what sort of modulator is used, the speech amplifier may be called upon to deliver a power output ranging from practically zero (only voltage required) to 20 or 30 watts.

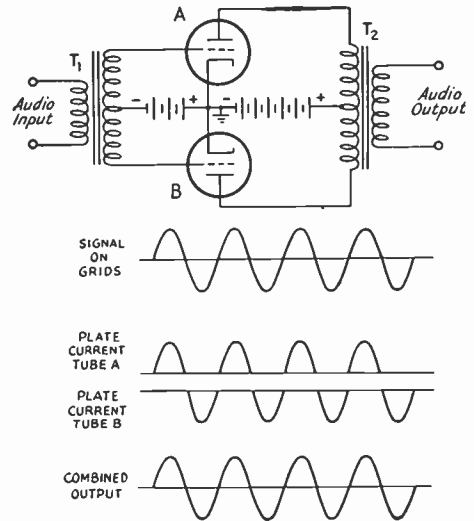


Fig. 9-14 — Class B amplifier operation.

Before starting the design of a speech amplifier, therefore, it is necessary to have selected a suitable modulator for the transmitter. This selection must be based on the power required to modulate the transmitter 100 per cent, and this power in turn depends on the type of modulation system selected, as already described. With the modulator picked out, its **driving-power** requirements (audio power required to excite the modulator to full output) can be determined from the tube tables in Chapter Twenty-Five. Generally speaking, it is advisable to choose a tube or tubes for the last stage of the speech amplifier that will be capable of developing at least 50 per cent more power than the rated driving power of the modulator. This will provide a factor of safety so that losses in coupling transformers, etc., will not upset the calculations. A "skippy" driver, or one designed without a safety factor, usually cannot excite the modulator to full output without being itself overloaded. The inevitable result is speech distortion, generation of unnecessary sidebands, and a "broad" transmitter.

#### Audio-Amplifier Classifications

The description of amplification as outlined in Chapter Three covered only one — the simplest — way of operating an amplifier

tube. There are several other ways of operating tubes to obtain higher power output and greater plate efficiency (ratio of useful power output to d.c. plate-power input).

Fig. 9-14 shows two tubes connected in a push-pull circuit. If the grid bias is set at the point where (when no signal is applied) the plate current is just cut off, then a signal can cause plate current to flow in either tube *only* when the signal voltage applied to that particular tube is positive. In the balanced grid circuit, the signal voltages on the grids of the two tubes always have opposite polarities; that is, when the signal swings the instantaneous voltage in the positive direction on the grid of tube *A*, it is at the same time swinging the grid of tube *B* more negative. On the next half-cycle the polarities reverse and the grid of tube *B* is more positive and that of tube *A* more negative. Since the fixed bias is just at the cut-off point, this means that plate current flows only in one tube at a time.

The graphs show the operation of such an amplifier. The plate current of tube *B* is drawn inverted to show that it flows in the opposite direction, through the primary of the output transformer, to the plate current of tube *A*. Thus each half of the output-transformer primary works alternately to induce a half-cycle of voltage in the secondary. In the secondary of  $T_2$ , the original waveform is restored. This type of operation is called **Class B amplification**.

The Class B amplifier is considerably more efficient than the Class A amplifier described in Chapter Three. As a matter of fact, the plate efficiency is in the neighborhood of 65 to 75 per cent, as compared to 20 to 30 per cent for a Class A power amplifier. Furthermore, the d.c. plate current of a Class B amplifier is proportional to the signal voltage on the grids, so the power input is small with small signals. The d.c. plate power input to a Class A amplifier is the same whether the signal is large, small, or absent altogether; therefore the maximum input that can be applied to a Class A amplifier is the rated plate dissipation of the tube or tubes. The result is that two tubes in a Class B amplifier can deliver approximately twelve times as much audio power as the same two tubes in a Class A amplifier.

A Class B amplifier usually is operated in such a way as to secure the maximum possible power output. This requires that the grids be driven positive with respect to the cathode during at least part of the cycle, so grid current flows and the grid circuit consumes power. While the power requirements are fairly low (as compared to the power output), the fact that the grids are positive during only *part* of the cycle means that the load on the driver stage varies in magnitude during the cycle; the effective load resistance is high when the grids are not drawing current and relatively low when they do take current. This must be allowed for when designing the driver. One

essential is that the driver must be capable of delivering more power than actually is required by the Class B grids.

Certain types of tubes have been designed specifically for Class B service and can be operated without fixed or other form of grid bias ("zero-bias" tubes). The amplification factor is so high that the plate current is small without signal. Because there is no fixed bias, the grids start drawing current immediately whenever a signal is applied, so the grid-current flow is continuous throughout the cycle. This makes the load on the driver much more constant than is the case with tubes of lower  $\mu$  biased to plate-current cut-off.

The amplifier that drives a Class B modulator usually is a **Class AB amplifier**. As the name indicates, this type of amplifier is operated midway between Class A and Class B conditions. A Class AB amplifier is a push-pull amplifier with higher bias than would be normal for pure Class A operation, but less than the cut-off bias required for Class B. At low signal levels the tubes operate practically as Class A amplifiers, and the plate current is the same with or without signal. At higher signal levels, the plate current of one tube is cut off during part of the *negative* cycle of the signal applied to its grid, and the plate current of the other tube rises with the signal. The plate current for the whole amplifier also rises above the no-signal level when a large signal is applied.

In a properly-designed Class AB amplifier the distortion is as low as with a Class A stage, but the efficiency and power output are considerably higher than with pure Class A operation. A Class AB amplifier can be operated either with or without driving the grids into the positive region. A **Class AB<sub>1</sub> amplifier** is one in which the grids are never positive with respect to the cathode; therefore, no driving power is required — only voltage. A **Class AB<sub>2</sub> amplifier** is one that has grid-current flow during part of the cycle, when the applied signal is large; it takes a small amount of driving power. The Class AB<sub>2</sub> amplifier will deliver somewhat more power (using the same tubes) but the Class AB<sub>1</sub> amplifier avoids the problem of designing a driver for it that will deliver power, without distortion, into a load of highly-variable resistance. It is advisable to use a Class AB<sub>1</sub> amplifier rather than the Class AB<sub>2</sub> type, whenever the circumstances permit.

#### Voltage Amplifiers

If the last stage in the speech amplifier is a Class AB<sub>2</sub> or Class B amplifier, the stage ahead of it must be capable of sufficient power output to drive it. However, if the last stage is a Class AB<sub>1</sub> or Class A amplifier the preceding stage can be simply a voltage amplifier.

From there on back to the microphone, all stages are voltage amplifiers. These are always operated Class A, not only to simplify the

design by avoiding driving power, but because just as much *voltage* can be secured from a Class A amplifier as from any other type.

The important characteristics of a voltage amplifier are its **voltage gain**, maximum undistorted **output voltage**, and its **frequency response**. The voltage gain is the voltage-amplification ratio of the stage. The output voltage is the maximum a.f. voltage that can be secured from the stage without distortion; we cannot figure on any greater output voltage than this, no matter what the gain of the stage, without running into the overload region. The amplifier frequency response should be adequate for voice reproduction; this requirement is easily satisfied.

The voltage gain and maximum undistorted output voltage depend on the operating conditions of the amplifier. Data on the popular types of tubes used in speech amplifiers are given in Table 9-I, for resistance-coupled amplification. The output voltage is in terms of *peak* voltage rather than r.m.s.; this method of rating is preferable because it makes the rating independent of the waveform. The ratio of peak to r.m.s. voltage varies widely with different waveforms and, in general, is known accurately only for a sine wave. On the other hand, exceeding the peak value causes

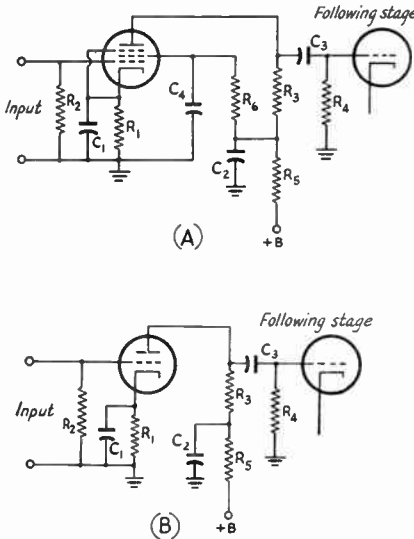


Fig. 9-15 — Resistance-coupled voltage-amplifier circuits. A, pentode; B, triode. Designations are as follows:

- C<sub>1</sub> — Cathode by-pass condenser.
- C<sub>2</sub> — Plate by-pass condenser.
- C<sub>3</sub> — Output coupling condenser (blocking condenser).
- C<sub>4</sub> — Screen by-pass condenser.
- R<sub>1</sub> — Cathode resistor.
- R<sub>2</sub> — Grid resistor.
- R<sub>3</sub> — Plate resistor.
- R<sub>4</sub> — Next-stage grid resistor.
- R<sub>5</sub> — Plate decoupling resistor.
- R<sub>6</sub> — Screen resistor.

Values for suitable tubes are given in Table 9-I. Values in the decoupling circuit, C<sub>2</sub>R<sub>5</sub>, are not critical. R<sub>5</sub> may be about 10% of R<sub>3</sub>; an 8- or 10- $\mu$ fd. electrolytic condenser is usually large enough at C<sub>2</sub>.

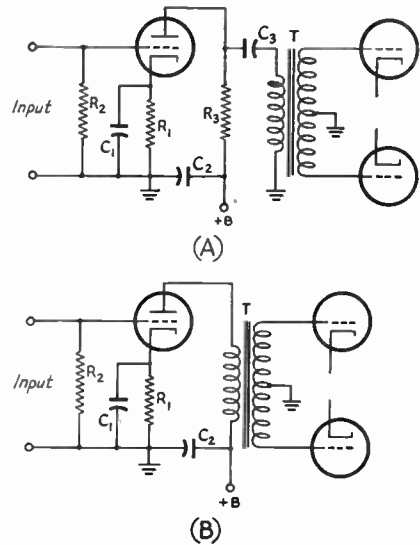


Fig. 9-16 — Transformer-coupled amplifier circuits for driving a push-pull amplifier. A is for resistance-transformer coupling; B, for transformer coupling. Designations correspond to those in Fig. 9-15. In A, values can be taken from Table 9-I. In B, the cathode resistor is calculated from the rated plate current and grid bias as given in the tube tables for the particular type of tube used.

the amplifier to distort, so it is more useful to consider only peak values in working with amplifiers.

### Resistance Coupling

Resistance coupling generally is used in voltage-amplifier stages. It is relatively inexpensive, good frequency response can be secured, and there is little danger of hum pick-up from stray magnetic fields associated with heater wiring. It is the only type of coupling suitable for the output circuits of pentodes and high- $\mu$  triodes, because with transformers a sufficiently high load impedance cannot be obtained without considerable frequency distortion. Typical circuits are given in Fig. 9-15 and design data in Table 9-I.

### Transformer Coupling

Transformer coupling between stages ordinarily is used only when power is to be transferred (in such a case resistance coupling is very inefficient), or when it is necessary to couple between a single-ended and a push-pull stage. Triodes having an amplification factor of 20 or less are used in transformer-coupled voltage amplifiers. With transformer coupling, tubes should be operated under the Class A conditions given in the tube tables in Chapter Twenty-Five.

Representative circuits for coupling single-ended to push-pull stages are shown in Fig. 9-16. The circuit at A combines resistance and transformer coupling, and may be used for exciting the grids of a Class A or AB<sub>1</sub> following



### TABLE 9-1—RESISTANCE-COUPLED VOLTAGE-AMPLIFIER DATA

Data are given for a plate supply of 300 volts, departures of as much as 50 per cent from this supply voltage will not materially change the operating conditions or the voltage gain, but the output voltage will be in proportion to the new voltage. Voltage gain is measured at 400 cycles; condenser values given are based on 100-cycle cut-off. For increased low-frequency response, all condensers may be made larger than specified (cut-off frequency in inverse proportion to condenser values provided all are changed in the same proportion). A variation of 10 per cent in the values given has negligible effect on the performance.

	Plate Resistor Megohms	Next-Stage Grid Resistor Megohms	Screen Resistor Megohms	Cathode Resistor Ohms	Screen By-pass $\mu$ f.	Cathode By-pass $\mu$ f.	Blocking Condenser $\mu$ f.	Output Volts (Peak) <sup>1</sup>	Voltage Gain <sup>2</sup>
6SJ7	0.1	0.1	0.35	500	0.10	11.6	0.019	72	67
		0.25	0.37	530	0.09	10.9	0.016	96	98
		0.5	0.47	590	0.09	9.9	0.007	101	104
	0.25	0.25	0.89	850	0.07	8.5	0.011	79	139
		0.5	1.10	860	0.06	7.4	0.004	88	167
		1.0	1.18	910	0.06	6.9	0.003	98	185
0.5	0.5	2.0	1300	0.06	6.0	0.004	64	200	
	1.0	2.2	1410	0.05	5.8	0.002	79	238	
	2.0	2.5	1530	0.04	5.2	0.0015	89	263	
6J7, 7C7	0.1	0.1	0.44	500	0.07	8.5	0.02	55	61
		0.25	0.5	450	0.07	8.3	0.01	81	82
		0.5	0.53	600	0.06	8.0	0.006	96	94
	0.25	0.25	1.18	1100	0.04	5.5	0.008	81	104
		0.5	1.18	1200	0.04	5.4	0.005	104	140
		1.0	1.45	1300	0.05	5.8	0.005	110	185
0.5	0.5	2.45	1700	0.04	4.2	0.005	75	161	
	1.0	2.9	2200	0.04	4.1	0.003	97	200	
	2.0	2.95	2300	0.04	4.0	0.0025	100	230	
6AU6, 6SH7	0.1	0.1	0.2	500	0.13	18.0	0.019	76	109
		0.25	0.24	600	0.11	16.4	0.011	103	145
		0.47	0.26	700	0.11	15.3	0.006	129	168
	0.22	0.22	0.42	1000	0.1	12.4	0.009	92	164
		0.47	0.5	1000	0.098	12.0	0.007	108	230
		1.0	0.55	1100	0.09	11.0	0.003	122	262
0.47	0.47	1.0	1800	0.075	8.0	0.0045	94	248	
	1.0	1.1	1900	0.065	7.6	0.0028	105	318	
	2.2	1.2	2100	0.06	7.3	0.0018	122	371	
6AQ6, 6AT6, 6Q7, 6SL7GT (one triode)	0.1	0.1	—	1500	—	4.4	0.027	40	34
		0.22	—	1800	—	3.6	0.014	54	38
		0.47	—	2100	—	3.0	0.0065	63	41
	0.22	0.22	—	2600	—	2.5	0.013	51	42
		0.47	—	3200	—	1.9	0.0065	65	46
		1.0	—	3700	—	1.6	0.0035	77	48
0.47	0.47	—	5900	—	1.2	0.006	61	48	
	1.0	—	6300	—	1.0	0.0035	74	50	
	2.2	—	7200	—	0.9	0.002	85	51	
6F5, 6SF5, 7B4	0.1	0.1	—	1300	—	5.0	0.025	33	42
		0.25	—	1600	—	3.7	0.01	43	49
		0.5	—	1700	—	3.2	0.006	48	52
	0.25	0.25	—	2600	—	2.5	0.01	41	56
		0.5	—	3200	—	2.1	0.007	54	63
		1.0	—	3500	—	2.0	0.004	63	67
0.5	0.5	—	4500	—	1.5	0.006	50	65	
	1.0	—	5400	—	1.2	0.004	62	70	
	2.0	—	6100	—	0.93	0.002	70	70	
6SC7 <sup>3</sup> (one triode)	0.1	0.1	—	750	—	—	0.033	35	29
		0.25	—	930	—	—	0.014	50	34
		0.5	—	1040	—	—	0.007	54	36
	0.25	0.25	—	1400	—	—	0.012	45	39
		0.5	—	1680	—	—	0.006	55	42
		1.0	—	1840	—	—	0.003	64	45
0.5	0.5	—	2330	—	—	0.006	50	45	
	1.0	—	2980	—	—	0.003	62	48	
	2.0	—	3280	—	—	0.002	72	49	
6J5, 7A4, 7N7, 6SN7GT (one triode)	0.05	0.05	—	1020	—	3.56	0.06	41	13
		0.1	—	1270	—	2.96	0.034	51	14
		0.25	—	1500	—	2.15	0.012	60	14
	0.1	0.1	—	1900	—	2.31	0.035	43	14
		0.25	—	2440	—	1.42	0.0125	56	14
		0.5	—	2700	—	1.2	0.0065	64	14
0.25	0.25	—	4590	—	0.87	0.013	46	14	
	0.5	—	5770	—	0.64	0.0075	57	14	
	1.0	—	6950	—	0.54	0.004	64	14	
6C4	0.047	0.047	—	870	—	4.1	0.065	38	12
		0.1	—	1200	—	3.0	0.034	52	12
		0.22	—	1500	—	2.4	0.016	68	12
	0.1	0.1	—	1900	—	1.9	0.032	44	12
		0.22	—	3000	—	1.3	0.016	68	12
		0.47	—	4000	—	1.1	0.007	80	12
0.22	0.22	—	5300	—	0.9	0.015	57	12	
	0.47	—	800	—	0.52	0.007	82	12	
	1.0	—	11000	—	0.46	0.0035	92	12	

<sup>1</sup> Voltage across next-stage grid resistor at grid-current point.

<sup>2</sup> At 5 volts r.m.s. output.

<sup>3</sup> Cathode-resistor values are for phase-inverter service.

stage. The resistance coupling is used to keep the d.c. plate current from flowing through the transformer primary, thereby preventing a reduction in primary inductance below its no-current value; this improves the low-frequency response. With low- $\mu$  triodes (6C5, 6J5, etc.), the gain is equal to that with resistance coupling multiplied by the secondary-to-primary turns ratio of the transformer.

In B the transformer primary is in series with the plate of the tube, and thus must carry the tube plate current. When the following amplifier operates without grid current, the voltage gain of the stage is practically equal to the  $\mu$  of the tube multiplied by the transformer ratio. This circuit also is suitable for transferring power (within the capabilities of the tube) to a following Class AB<sub>2</sub> or Class B stage.

### Phase Inversion

Push-pull output may be secured with resistance coupling by using an extra tube, as shown in Fig. 9-17. The extra tube is used purely to provide a 180-degree phase shift without additional gain. The outputs of the two tubes are then added to provide push-pull excitation for the following amplifier.

The circuit shown in Fig. 9-17 is known as the "self-balancing" type. The amplified voltage from  $V_1$  appears across  $R_5$  and  $R_7$  in series. The drop across  $R_7$  is applied to the grid of  $V_2$ , and the amplified voltage from  $V_2$  appears across  $R_6$  and  $R_7$  in series. This voltage is 180 degrees out of phase with the voltage from  $V_1$ , thus giving push-pull output. The part that appears across  $R_7$  therefore opposes the voltage from  $V_1$  across  $R_7$ , thus reducing the signal applied to the grid of  $V_2$ . The negative feedback so obtained tends to automatically regulate the voltage applied to the phase-inverter tube so that the output voltages from both tubes

are substantially equal — as they must be for distortionless reproduction. Other circuits usually require careful adjustment (preferably with the aid of an oscilloscope) for satisfactory operation. The self-balancing circuit also has the advantage of compensating for variations in the characteristics of the two tubes.

It is common practice to use a double triode when a phase inverter is to be built. This provides two identical tubes in one bulb, and saves space and cost.

### Gain Control

A means for varying the over-all gain of the amplifier is a practical necessity. Without it, there would be no way to keep the final output down to the proper level for modulating the transmitter except to talk at just the right intensity. The common method of gain control is to adjust the value of a.c. voltage applied to the grid of one of the amplifiers by means of a voltage divider or potentiometer.

The gain-control potentiometer should be near the input end of the amplifier, at a point where the a.c. voltage level is so low that there is no danger of overloading in the stages ahead of the gain control. With carbon microphones the gain control may be placed directly across the microphone-transformer secondary. With other types of microphones, however, the gain control usually will affect the frequency response of the microphone when connected directly across it. The control therefore is usually placed in the grid circuit of the second stage.

## DESIGNING THE SPEECH AMPLIFIER

The steps in designing a speech amplifier are as follows:

1) Determine the power needed to modulate the transmitter and select the modulator. In the case of plate modulation, this will nearly always be a Class B amplifier. Select a suitable tube type and determine from the tube tables in Chapter Twenty-Five the driving power required.

2) As a safety factor, multiply the required driver power by at least 1.5.

3) Select a tube, or pair of tubes, that will deliver the power determined in the second step. This is the last speech-amplifier stage. Receiver-type power tubes can be used (beam tubes such as the 6L6 may be needed in some cases) so the receiving-tube tables in Chapter Twenty-Five may be consulted. (If the speech amplifier is to drive a Class B modulator, use a Class A or AB<sub>1</sub> amplifier if it will give enough power output. If the last speech-amplifier stage has to operate Class AB<sub>2</sub>, use a medium- $\mu$  triode (such as the 6J5 or corresponding types) to drive it. In the extreme case of driving 6L6s to maximum output, two triodes should be used in push-pull in the driver. In either

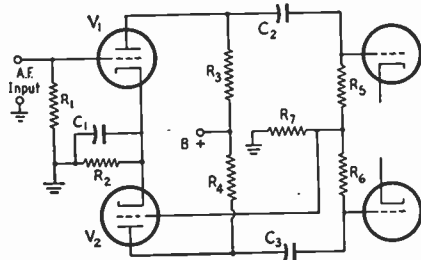


Fig. 9-17 — Self-balancing phase-inverter circuit.  $V_1$  and  $V_2$  may be a double triode such as the 6SN7GT or 6SL7GT.

$R_1$  — Grid resistor (1 megohm or less).

$R_2$  — Cathode resistor; use one-half value given in Table 9-I for tube and operating conditions chosen.

$R_3, R_4$  — Plate resistor; select from Table 9-I.

$R_5, R_6$  — Following-stage grid resistor (0.22 to 0.47 megohm).

$R_7$  — 0.22 megohm.

$C_1, C_3$  — 10- $\mu$ fd. electrolytic.

$C_2, C_3$  — 0.01- to 0.1- $\mu$ fd. paper.

case transformer coupling will have to be used, and transformer manufacturers' catalogs should be consulted for a suitable type.)

4) If the last speech-amplifier stage operates Class A or AB<sub>1</sub>, it may be driven by a voltage amplifier. If the last stage is push-pull, the driver may be a single tube coupled through a transformer with a balanced secondary, or may be a dual-triode phase inverter. Determine the signal voltage required for full output from the last stage. If the last stage is a single-tube Class A amplifier, the peak signal is equal to the grid-bias voltage; if push-pull Class A, the peak signal voltage is equal to twice the grid bias; if Class AB<sub>1</sub>, twice the bias voltage when fixed bias is used; if cathode bias is used, twice the bias figured from the cathode resistance and the no-signal plate current.

5) From Table 9-I, select a tube capable of giving the required output voltage and note its rated voltage gain. A phase inverter (using two tubes of the type selected) will have approximately twice the output voltage and twice the gain of one tube operating as an ordinary amplifier. If the driver is to be transformer-coupled to the last stage, select a medium- $\mu$  triode and calculate the gain and output voltage as previously described.

6) Divide the voltage required to drive the last stage by the gain of the preceding stage. This gives the peak voltage required at the grid of the next-to-the-last stage.

7) Find the output voltage, under ordinary conditions, of the microphone to be used. This information should be obtained from the manufacturer's catalog. If not available, the figures given in the section on microphones in this chapter will serve.

8) Divide the voltage found in (6) by the output voltage of the microphone. The result is the over-all gain required from the microphone to the grid of the next-to-the-last stage. To be on the safe side, double or triple this figure.

9) From Table 9-I, select a combination of tubes whose gains, when multiplied together, give approximately the figure arrived at in (8). These amplifiers will be used in cascade. In general, if high gain is required it is advisable to use a pentode for the first speech-amplifier stage, but it is *not* advisable to use a second pentode because of the possibility of feedback and self-oscillation. In most cases a triode will give enough gain, as a second stage, to make up the total gain required. If not, a third stage, also a triode, may be used.

## ● SPEECH-AMPLIFIER CONSTRUCTION

Once a suitable circuit has been selected for a speech amplifier, the construction problem resolves itself into avoiding two difficulties — excessive hum, and unwanted feedback. For reasonably humless operation, the hum voltage should not exceed about 1 per cent of the maximum audio output voltage — that is, the hum

should be about 40 db. below the output level. Unwanted feedback, if negative, will reduce the gain below the calculated value; if positive, is likely to cause self-oscillation or "howls." Feedback can be minimized by isolating each stage with "decoupling" resistors and condensers, by avoiding layouts that bring the first and last stages near each other, and by shielding of "hot" points in the circuit, such as grid leads in low-level stages.

Speech-amplifier equipment, especially voltage amplifiers, should be constructed on metal chassis, with all wiring kept below the chassis to take advantage of the shielding afforded. Exposed leads, particularly to the grids of low-level high-gain tubes, are likely to pick up hum from the electrostatic field that usually exists in the vicinity of house wiring. Even with the chassis, additional shielding of the input circuit of the first tube in a high-gain amplifier usually is necessary. In addition, such circuits should be separated as much as possible from power-supply transformers and chokes and also from any audio transformers that operate at fairly-high power levels; this will minimize magnetic coupling to the grid circuit and thus reduce hum or audio-frequency feedback. It is always a safe plan, although not an absolutely necessary one, to build the speech amplifier and its power supply as separate units.

If a low-level microphone such as the crystal type is used, the microphone, its connecting cable, and the plug or connector by which it is attached to the speech amplifier, all should be shielded. The microphone and cable usually are constructed with suitable shielding. The cable shield should be connected to the speech-amplifier chassis, and it is advisable — as well as usually necessary — to connect the chassis to a ground such as a water pipe.

Heater wiring should be kept as far as possible from grid leads, and either the center-tap or one side of the heater-transformer secondary winding should be connected to the chassis. If the center-tap is grounded, the heater leads to each tube should be twisted together to reduce the magnetic field from the heater current. With either type of connection, it is advisable to lay heater leads in the corner formed by a fold in the chassis, bringing them out from the corner to the tube socket by the shortest possible path.

In a high-gain amplifier it is sometimes helpful if the first tube has its grid connection brought out to a top cap rather than to a base pin; in the latter type the grid lead is exposed to the heater leads inside the tube and hence may pick up more hum. With the top-cap tubes, complete shielding of the grid lead and grid cap is a necessity.

When metal tubes are used, always ground the shell connection to the chassis. Glass tubes used in the low-level stages of high-gain amplifiers must be shielded; tube shields are obtainable for that purpose. It is a good

plan to enclose the entire amplifier in a metal box, or at least provide it with a cane-metal cover, to avoid feed-back difficulties caused by the r.f. field of the transmitter; r.f. picked up on exposed wiring leads or tube elements causes overloading, distortion, and frequently oscillation.

When using paper condensers as by-passes, be sure that the terminal marked "outside foil" is connected to ground. This utilizes the outside foil of the condenser as a shield around the "hot" foil. When paper condensers are used as coupling condensers between stages, always connect the outside-foil terminal to the side of the circuit having the lowest impedance to ground. Usually, this will be the plate side rather than the following-grid side.

For low-power transmitters, it is often possible to construct the speech amplifier and modulator as a single unit. In high-power equipment the modulator (for plate modulation) takes up so much space that it is usually impracticable to build it on the same chassis with the speech amplifier. In the following section representative designs are given for combination units as well as for speech amplifiers alone.

The speech amplifiers described in the following pages are all designed for use with crystal microphones, since that type of micro-

phone is the most popular. If a carbon microphone is to be used, the secondary of the transformer used with it may be connected directly to the gain control in any of the amplifier circuits given. The stage or stages of amplification preceding the gain control may be omitted in that case. An alternative method is to build the amplifier just as described and connect the

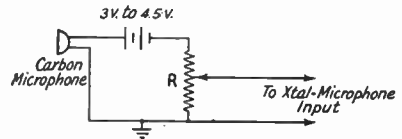


Fig. 9-18 — Input connections for using a carbon microphone with a high-gain speech amplifier, omitting the usual microphone transformer.  $R$  is a 100-ohm potentiometer, wire-wound. The arm should be set at the point that gives normal output from the amplifier when the amplifier gain control is set at  $\frac{1}{3}$  to  $\frac{1}{2}$  full scale.

carbon microphone as shown in Fig. 9-18. With this method of connection there is no need for a microphone transformer, because a speech amplifier designed for use with a crystal microphone has more than enough gain to compensate for the omission of the microphone transformer.

## Speech Amplifier with Push-Pull Triode Output

The speech amplifier shown in Fig. 9-19 is a general-purpose unit of conventional design, suitable either as a driver for a medium-power Class B modulator or as a grid-bias modulator. As shown in the circuit diagram, Fig. 9-20, it has a pentode first stage using a 6SJ7, a medium- $\mu$  triode second stage (6J5) followed by a 6SL7 phase inverter, and a pair of 6B4Gs in push-pull as Class AB<sub>1</sub> output amplifiers. The power supply for the unit is included on the same chassis. The measured

power output is approximately 8 watts from the output-transformer secondary. A tone control is provided to reduce the response of the amplifier above about 2500 cycles.

The speech section occupies the left-hand side of the chassis and the power-supply section the right. Controls along the front chassis edge are the tone-control switch,  $S_1$ , gain control,  $R_5$ , microphone connector, "B" switch,  $S_3$ , and a.c. switch,  $S_2$ . The 6SJ7 is behind the microphone connector on the chassis, and the 6J5 is to its left, near the gain control. The 6SL7 phase inverter and 6B4G output tubes are located behind the 6J5.

At the right, the power transformer is at the rear of the chassis, the 5Y3GT rectifier in front, and the first filter choke,  $L_1$ , is to the left of the rectifier tube. The output transformer is at the rear center of the chassis.

The bottom view shows the cathode resistor,  $R_{17}$ , for the 6B4Gs at the lower right, together with its

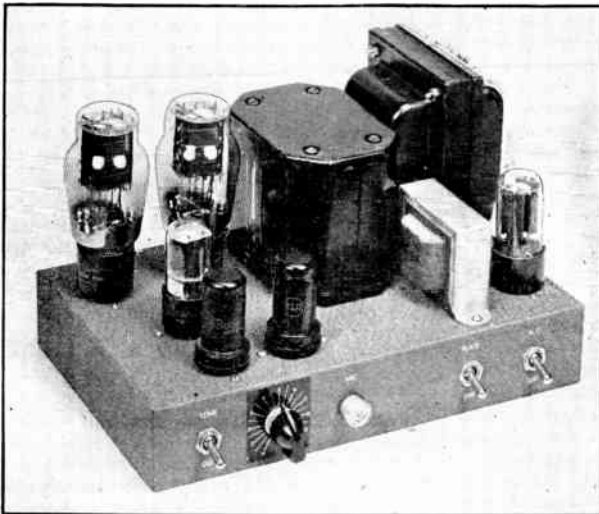


Fig. 9-19 — This amplifier uses 6B4Gs (equivalent to 6A3s) as output tubes and will deliver 8 watts of undistorted power. It is complete with power supply on a  $7 \times 11 \times 2$ -inch chassis.

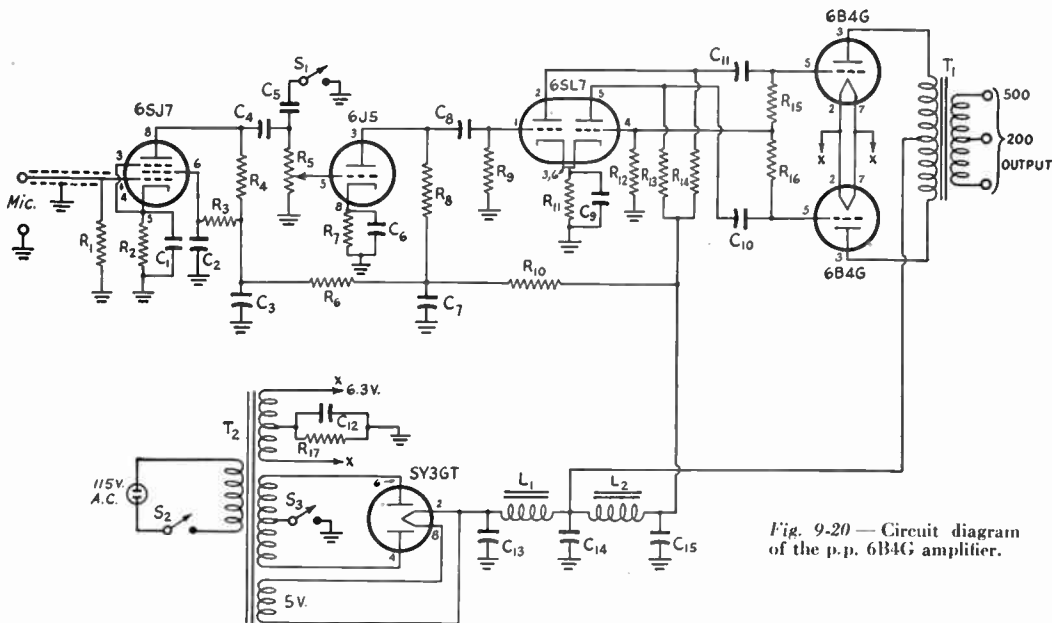


Fig. 9-20 — Circuit diagram of the p.p. 6B4G amplifier.

- C<sub>1</sub>, C<sub>6</sub>, C<sub>9</sub> — 20- $\mu$ fd. 25-volt electrolytic.
- C<sub>2</sub> — 0.1- $\mu$ fd. 400-volt paper.
- C<sub>3</sub>, C<sub>7</sub>, C<sub>13</sub>, C<sub>14</sub>, C<sub>15</sub> — 10- $\mu$ fd. 450-volt electrolytic.
- C<sub>4</sub>, C<sub>8</sub>, C<sub>10</sub>, C<sub>11</sub> — 0.01- $\mu$ fd. 600-volt paper.
- C<sub>5</sub> — 0.001- $\mu$ fd. 500-volt mica.
- C<sub>12</sub> — 50- $\mu$ fd. 100-volt electrolytic.
- R<sub>1</sub> — 1 megohm,  $\frac{1}{2}$  watt.
- R<sub>2</sub>, R<sub>7</sub> — 1500 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 1.5 megohms,  $\frac{1}{2}$  watt.
- R<sub>4</sub>, R<sub>12</sub>, R<sub>13</sub>, R<sub>14</sub>, R<sub>15</sub>, R<sub>16</sub> — 0.22 megohm,  $\frac{1}{2}$  watt.
- R<sub>5</sub> — 0.5-megohm volume control.
- R<sub>6</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.

- R<sub>8</sub> — 82,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>9</sub> — 0.47 megohm,  $\frac{1}{2}$  watt.
- R<sub>10</sub> — 10,000 ohms, 1 watt.
- R<sub>11</sub> — 1500 ohms, 1 watt.
- R<sub>17</sub> — 750 ohms, 10 watts.
- L<sub>1</sub> — 8-hy. 160-ma. filter choke (UTC R-20).
- L<sub>2</sub> — 10-hy. 35-ma. filter choke (UTC R-55).
- S<sub>1</sub>, S<sub>2</sub>, S<sub>3</sub> — S.p.s.t. toggle.
- T<sub>1</sub> — Output transformer, p.p. plates (5000 ohms) to line (UTC PA-16).
- T<sub>2</sub> — 700 volts e.t., 110 ma.; 5 volts, 3 amp.; 6.3 volts, 4.5 amp. (Stancor P-1080).

by-pass condenser, C<sub>12</sub>. Just above is the second filter choke, L<sub>2</sub>. The filter condensers, C<sub>13</sub>, C<sub>14</sub> and C<sub>15</sub>, are the larger tubular units located to the left. The resistors and condensers associated with individual stages are grouped about the appropriate tube sockets. The terminals of the output transformer, T<sub>1</sub>, project through a cut-out in the chassis, and secondary leads are brought out to a terminal strip.

A shielded lead should be used from the microphone connector to the grid prong on the 6SJ7 socket, but there are otherwise no special constructional precautions to observe other than those mentioned in the section on general considerations in speech-amplifier construction.

The output transformer shown in the photographs is designed for working into a 500- or 200-ohm line. This type of transformer may be used when the speech amplifier is

located at some distance from the Class B modulator or other unit it is to drive. If desired, a Class B input transformer can be substituted at T<sub>1</sub>. In that case, the leads to the modulator-tube grids should be shielded as a precaution against hum or r.f. pick-up. The transformer selected should be designed for working from a 5000-ohm plate-to-plate load to the grids of the modulator tubes selected. The amplifier has ample gain for communications-type crystal microphones.

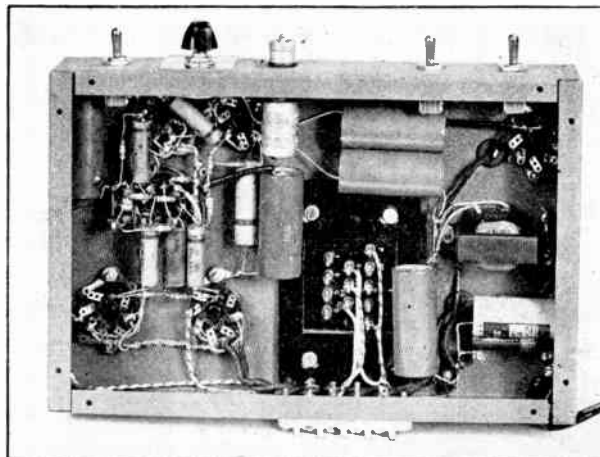


Fig. 9-21 — Bottom view of the push-pull 6B4G amplifier. Output-transformer terminals are brought out to a connection strip on the rear edge of the chassis.

Speech Amplifiers with Output Limiting

It is obviously desirable to modulate the transmitter as completely as possible — without, of course, overmodulating and setting up spurious sidebands. However, it is difficult to maintain constant voice intensity when speaking into the microphone. To overcome this

ing the rectified and filtered d.c. to a control electrode in an early stage in the amplifier.

A practical circuit for this purpose is shown in Fig. 9-22. The rectifier must be connected, through the transformer, to a tube capable of delivering some power output (a small part of the output of the power stage may be used) or else a separate power amplifier for the rectifier circuit alone may have its grid connected in parallel with that of the last voltage amplifier.

Resistor  $R_4$ , in series with  $R_5$  across the plate supply, provides an adjustable positive bias on the rectifier cathodes. This prevents the limiting action from beginning until a desired microphone input level is reached.  $R_2$ ,  $R_3$ ,  $C_2$ ,  $C_3$  and  $C_4$  filter the audio frequencies from the rectified output. The output of the rectifier may be connected to the suppressor grid of a pentode first stage of the speech amplifier.

A step-down transformer with a turns ratio such as to give about 50 volts when its primary is connected to the output circuit of the power stage should be used. If a transformer having a center-tapped secondary is not available, a half-wave rectifier may be used instead of the full-wave circuit shown, but it will be harder to get satisfactory filtering.

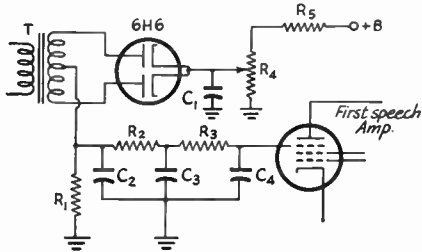


Fig. 9-22 — Speech-amplifier output-limiting circuit.  $C_1, C_2, C_3, C_4$  — 0.1- $\mu$ f.  $R_1, R_2, R_3$  — 0.22 megohm.  $R_4$  — 25,000-ohm pot.  $R_5$  — 0.1 megohm. T — See text.

variable output level, it is possible to use automatic gain control that follows the *average* (not instantaneous) variations in speech amplitude. This can be done by rectifying and filtering some of the audio output and apply-

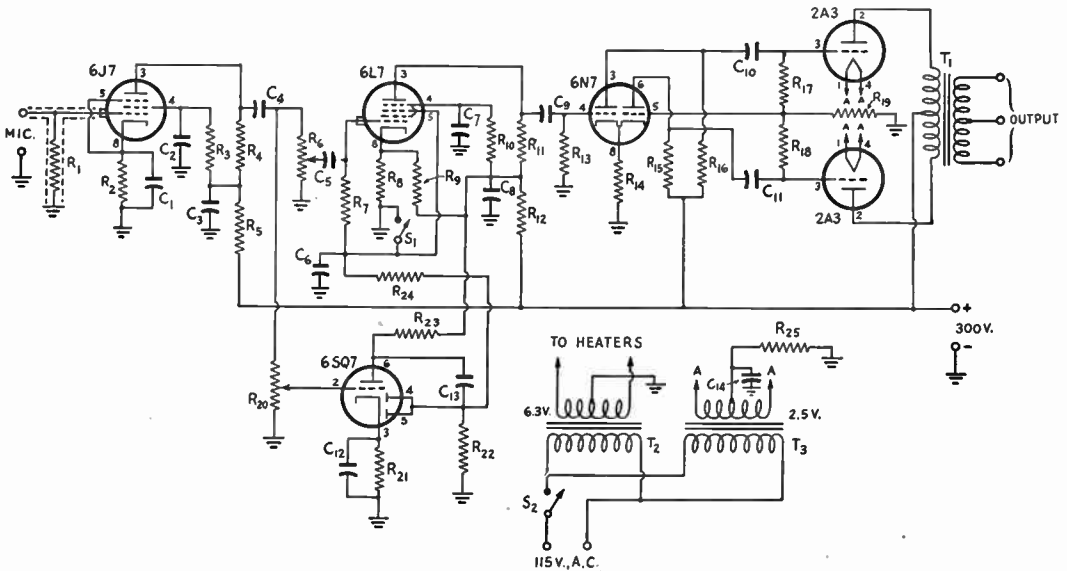


Fig. 9-23 — Circuit diagram of the Class-A 2A3 volume-compression speech amplifier.

- |   |  |   |
|---|--|---|
| $C_1, C_{12}$ — 10- $\mu$ f. 50-volt electrolytic.                                | $R_4, R_{13}, R_{22}, R_{24}$ — 0.47 megohm, $\frac{1}{2}$ watt. | $R_{17}, R_{18}, R_{19}$ — 0.22 megohm, $\frac{1}{2}$ watt.     |
| $C_2, C_4, C_5, C_6, C_9, C_{10}, C_{11}, C_{13}$ — 0.1- $\mu$ f. 400-volt paper. | $R_5$ — 47,000 ohms, $\frac{1}{2}$ watt.                         | $R_{21}$ — 4700 ohms, $\frac{1}{2}$ watt.                       |
| $C_3, C_8$ — 8- $\mu$ f. 450-volt electrolytic.                                   | $R_6, R_{20}$ — 0.5-megohm variable.                             | $R_{25}$ — 750 ohms, 10 watts.                                  |
| $C_7$ — 0.5- $\mu$ f. 400-volt paper.   | $R_9$ — 0.22 megohm, 1 watt.                                     | $S_1, S_2$ — S.p.s.t. switch.                                   |
| $C_{14}$ — 50- $\mu$ f. 100-volt electrolytic.                                    | $R_{10}, R_{11}, R_{23}$ — 0.1 megohm, $\frac{1}{2}$ watt.       | $T_1$ — Output transformer to match p.p. 2A3s to Class B grids. |
| $R_1$ — 4.7 megohms, $\frac{1}{2}$ watt.  | $R_{12}$ — 10,000 ohms, $\frac{1}{2}$ watt.                      | $T_2$ — Filament transformer, 6.3 volts, 2 amperes.             |
| $R_2, R_8$ — 1200 ohms, $\frac{1}{2}$ watt.                                       | $R_{14}$ — 1500 ohms, $\frac{1}{2}$ watt.                        | $T_3$ — Filament transformer, 2.5 volts, 5 amperes.             |
| $R_3, R_7$ — 2.2 megohms, $\frac{1}{2}$ watt.                                     | $R_{15}, R_{16}$ — 0.1 megohm, 1 watt.                           |   |

## Volume-Limiting Circuit

Fig. 9-23 is the circuit diagram of a complete speech amplifier using a slightly different volume-limiting circuit than that given in Fig. 9-22. It has sufficient gain for working from a crystal microphone and has a power output (6 watts or more, depending upon the efficiency of the output transformer) sufficient to drive a Class B modulator to an output of about 250 watts. The automatic gain-control circuit uses a separate amplifier and rectifier combined in one tube, a 6SQ7. The rectified output of this circuit is filtered and applied to the Nos. 1 and 3 grids of a pentagrid amplifier tube, thereby varying its gain in inverse proportion to the signal strength. With proper adjustment, an average increase in modulation level of about 7 db. can be secured without exceeding 100-per-cent modulation on peaks.

The amplifier proper consists of a 6J7 first stage followed by a 6L7 amplifier-compressor. The 2A3 grids are driven by a 6N7 self-balancing phase inverter. The operation of the 2A3s is Class AB<sub>1</sub>, without grid current.

The amount of compression is controlled by the potentiometer,  $R_{20}$ , in the grid circuit of the 6SQ7. A switch,  $S_1$ , is provided to short-circuit the rectified output of the compressor

when normal amplification is required.

Adjustment of the compressor control is rather critical. First set  $R_{20}$  at zero and adjust the gain control,  $R_6$ , for full modulation with the particular microphone used. Then advance the compressor control until the amplifier just "cuts off" (output decreases to a low value) on peaks. When this point is reached, back off the compressor control until the cut-off effect is gone but an obvious decrease in gain follows each peak.

Because of the necessity for filtering out the audio-frequency component in the rectifier output, there will be a slight delay (amounting to a fraction of a second) before the decrease in gain "catches up" with the peak. This is caused by the time constant of the circuit, and so is unavoidable.

When a satisfactory setting is secured, as indicated by good speech quality with a definite reduction in gain on peaks, the gain control,  $R_6$ , should be advanced to give full output with normal operation. Too much volume compression, indicated by the cut-off effect following each peak, is definitely undesirable, and the object of adjustment of the compressor control should be to use as much compression as possible without danger of overcompression.

## Speech Clipping and Filtering

Earlier in this chapter it was pointed out that with sine-wave 100-per-cent modulation the average power increases to 150 per cent of the unmodulated carrier power, but that in speech waveforms the average power content is considerably less than in a sine wave, when both waveforms have the same peak amplitude. Nevertheless, it is the peak conditions that count in modulation. This is shown in the drawings of Fig. 9-24. The upper drawing, A, represents a sine wave having a maximum amplitude that just modulates a given transmitter 100 per cent. The same maximum amplitude will modulate the same transmitter 100 per cent regardless of the waveform of the modulating signal. The speech wave at B, therefore, also represents 100-per-cent modulation.

In the speech wave, 100-per-cent modulation is reached only on occasional peaks. The average modulation is obviously much lower. But if the gain is increased to raise the average modulation level, the transmitter will immediately be overmodulated on the peaks, with the result that splatter-producing sidebands will be generated.

Now suppose that the amplitude of the wave shown at B is increased so that its power is comparable to — or even higher than — the power in a sine wave, but that everything above the 100-per-cent modulation mark is cut off. We then have a wave

such as is shown at C, which is the wave at B increased in amplitude but with its peaks "clipped." This signal will not modulate the transmitter more than 100 per cent, but the voice power will be several times as great. The wave is not exactly like the one at B, so the result will not sound exactly like the original. However, such clipping can be used to secure a worth-while increase in modulation

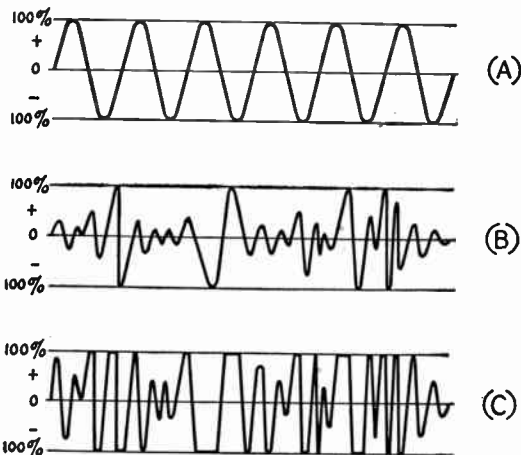


Fig. 9-24 — The normal speech wave (B) has high peaks but low average energy content. When the peaks are clipped from the wave the signal may be increased to a considerably-higher power level without causing overmodulation (C).

power without sacrificing *intelligibility*. The clipping can be done in the speech amplifier, and once the system is properly adjusted it *will be impossible to overmodulate the transmitter* no matter how much gain is used ahead of the clipper — because the clipper will hold the maximum output amplitude to the same value no matter what the amplitude of the signal applied to it.

But by itself the clipper is not enough. Although the clipping takes place in the audio system, the signal applied to the modulated r.f. amplifier has practically the same wave-shape that the modulation envelope *would have had* if the signal were unclipped and the transmitter were badly overmodulated. In other words, clipping generates the same high-order harmonics that overmodulation does. So far as the end effect is concerned, it does not matter whether the distortion takes place in the audio system or in the modulated amplifier; both cause splatter. It is therefore necessary to prevent the higher audio frequencies from reaching the modulator. In other words, the frequencies above those needed for intelligible speech must be filtered out, *after* clipping and *before* modulation. The filter required for this purpose should have relatively little attenuation at frequencies below about 2500 cycles, but very great attenuation for all frequencies above 3000 cycles.

It is possible to use as much as 25 db. of clipping before intelligibility is lost; that is, if the original peak amplitude is 10 volts, the signal can be clipped to such an extent that the resulting maximum amplitude is less than one volt. If the original 10-volt signal represented the amplitude that caused 100-per-cent modulation on peaks, the clipped and filtered signal can then be amplified up to the same 10-volt peak level for modulating the transmitter, with a very considerable increase in modulation power. The price to be paid for the increased voice power is loss in naturalness.

Before drastic clipping can be used, the

speech signal must be amplified up to 10 times more than is necessary for normal modulation. Also, the hum and noise must be much lower than the tolerable level in ordinary amplification, because the noise in the output of the amplifier increases in proportion to the gain. These factors need not be given so much attention if the clipper-filter is used chiefly as a means for preventing *occasional* overmodulation, and not primarily to obtain more modulation power.

### ● A CLIPPER-FILTER SPEECH AMPLIFIER

The amplifier shown in Fig. 9-25 has a usable output of about 4 watts (sine wave) and includes a clipper-filter for increasing the effectiveness of the modulator and for confining the channel-width to the frequencies needed for intelligible speech. The output stage uses a 6V6 with negative feed-back; this reduces the effective plate resistance of the tube to a low value. The unit therefore can be used to drive a Class B modulator that does not require more than 4 watts on the grids. It can also be used as a complete modulator unit for grid-bias modulation.

As shown in the circuit diagram, Fig. 9-26, the first tube is a 6SJ7. The second stage is one section of a 6SL7GT. With  $S_3$  thrown to the left-hand position, the output of this stage is connected to the grid of a 6J5, which in turn drives the 6V6. Under these conditions the amplifier operates conventionally and has fairly wide frequency response. With  $S_3$  thrown to the right, the output of the first 6SL7GT section is fed to the 6AL5 clipper, and the clipped output is then fed to the grid of the second section of the 6SL7GT. The output of this tube goes through a low-pass filter and thence through a second gain control,  $R_{15}$ , to the grid of the 6J5. Thus the clipper-filter feature can be used or not as desired.

The first two stages are resistance-coupled amplifiers following ordinary practice. In the last stage, use is made of the center-tap on the primary of the output transformer to obtain feed-back voltage that is applied to the grid of the 6V6 through the plate resistor,  $R_{18}$ , of the 6J5. If a different type of transformer is used, not having a center-tap, a voltage divider can be connected across the primary to obtain the feed-back voltage, as

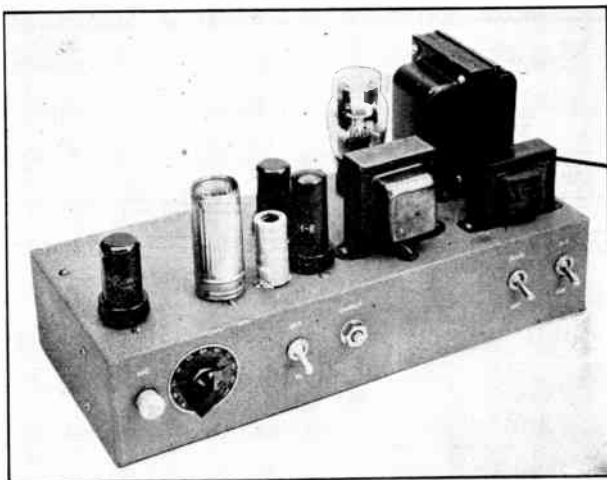


Fig. 9-25 — A 4-watt output amplifier with speech clipping and filtering. It uses a 6V6 output tube with negative feed-back, and has its power supply on the same chassis.



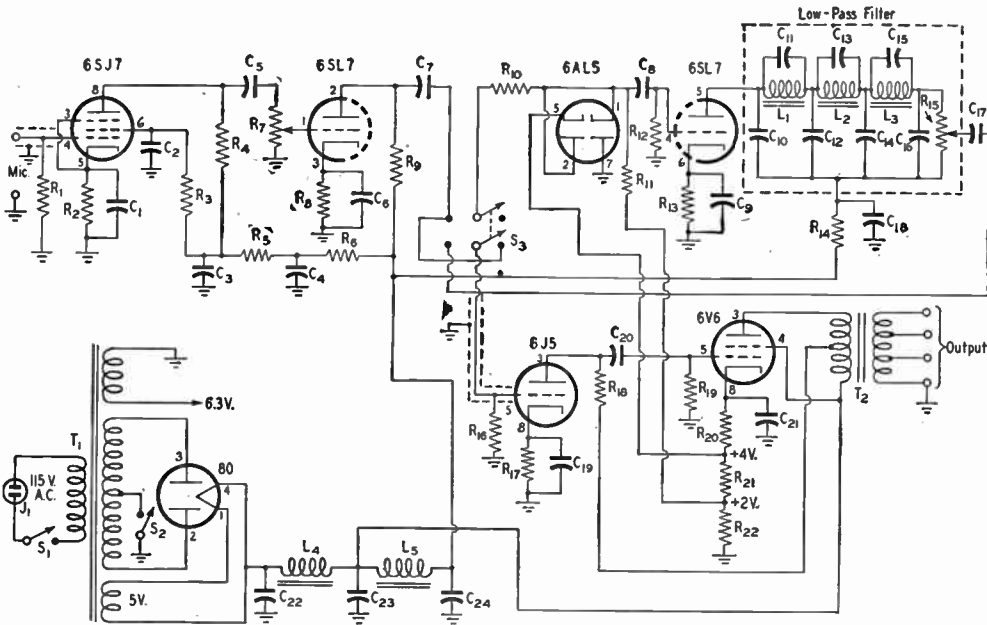


Fig. 9-26 — Circuit diagram of the clipper-filter speech amplifier.

- C<sub>1</sub>, C<sub>6</sub>, C<sub>9</sub>, C<sub>10</sub> — 10- $\mu$ fd. 25-volt electrolytic.
- C<sub>2</sub> — 0.1- $\mu$ fd. 400-volt paper.
- C<sub>3</sub>, C<sub>4</sub>, C<sub>18</sub>, C<sub>22</sub>, C<sub>23</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- C<sub>5</sub>, C<sub>7</sub>, C<sub>8</sub>, C<sub>17</sub>, C<sub>20</sub> — 0.01- $\mu$ fd. 600-volt paper.
- C<sub>10</sub>, C<sub>11</sub>, C<sub>13</sub> — 0.015- $\mu$ fd. paper.
- C<sub>12</sub> — 0.03- $\mu$ fd. paper.
- C<sub>14</sub> — 0.05- $\mu$ fd. paper.
- C<sub>15</sub> — 0.003- $\mu$ fd. mica.
- C<sub>16</sub> — 0.06- $\mu$ fd. paper.
- C<sub>21</sub> — 50- $\mu$ fd. 50-volt electrolytic.
- C<sub>24</sub> — 16- $\mu$ fd. 450-volt electrolytic.
- R<sub>1</sub> — 1 megohm,  $\frac{1}{2}$  watt.
- R<sub>2</sub>, R<sub>13</sub> — 1000 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 1.2 megohms,  $\frac{1}{2}$  watt.
- R<sub>4</sub> — 0.22 megohm,  $\frac{1}{2}$  watt.
- R<sub>5</sub>, R<sub>10</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>6</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.
- R<sub>7</sub> — 2-megohm volume control.
- R<sub>8</sub> — 3300 ohms,  $\frac{1}{2}$  watt.
- R<sub>9</sub>, R<sub>12</sub>, R<sub>19</sub> — 0.47 megohm,  $\frac{1}{2}$  watt.
- R<sub>11</sub> — 0.15 megohm,  $\frac{1}{2}$  watt.
- R<sub>14</sub> — 10,000 ohms, 1 watt.
- R<sub>15</sub> — 2000-ohm wire-wound volume control.
- R<sub>16</sub> — 0.33 megohm,  $\frac{1}{2}$  watt.
- R<sub>17</sub> — 1500 ohms,  $\frac{1}{2}$  watt.
- R<sub>18</sub> — 82,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>20</sub> — 150 ohms, 10 watts.
- R<sub>21</sub>, R<sub>22</sub> — 39 ohms, 2 watts.
- L<sub>1</sub>, L<sub>2</sub>, L<sub>3</sub> — 125 mh.
- L<sub>4</sub> — 10 henrys, 60 ma.
- L<sub>5</sub> — 10 henrys, 35 ma.
- J<sub>1</sub> — 115-v. a.c. connector.
- S<sub>1</sub>, S<sub>2</sub> — S.p.s.t. toggle.
- S<sub>3</sub> — D.p.d.t. toggle.
- T<sub>1</sub> — Power transformer, 350 volts each side c.t., 70 ma.; 5 volts, 2 amp.; 6.3 volts, 3 amp. (Stancor P-4078).
- T<sub>2</sub> — Output transformer, 5000 ohms (total primary) to line or voice coil.

described in the section on negative feed-back in this chapter.

The amplifier has its own power supply, as shown in the diagram and photographs.

**Clipper-Filter Considerations**

The clipper circuit resembles those used for noise limiting in receivers, as described in Chapter Five. It uses two diodes, one to clip positive and the other to clip negative peaks, in shunt with a load resistor, R<sub>11</sub>. The diodes are biased so that they are nonconducting (and therefore have no effect on the signal) until the signal amplitude reaches about 2 volts. When the amplitude rises above 2 volts, signal current flows through the diodes. When conducting, the diode resistance is low compared to the resistance of R<sub>11</sub>, and also compared to the series resistor R<sub>10</sub>. Under these conditions, all of the voltage in excess of the 2-volt bias appears as a voltage drop in R<sub>10</sub> (and in the

plate resistance of the preceding stage), with the result that the voltage across R<sub>11</sub> cannot exceed 2 volts.

For convenience, the bias for the diodes is taken from the cathode resistor of the 6V6 by a voltage-dividing arrangement. As shown in Fig. 9-26, the plate of one diode is connected to ground, R<sub>11</sub> is returned to a point 2 volts above ground, and the cathode of the second diode is returned to a point 4 volts above ground. This makes the plate of each diode 2 volts negative with respect to its own cathode.

The filter shown in Fig. 9-27 is constructed of standard components, the chokes being 125-mh. units usually sold as r.f. chokes. The design of a filter using this value of inductance requires a fairly high capacitance and a low value of load resistance. The constants listed give a sharp cut-off between 2500 and 3000 cycles, with very large attenuation (averaging

45 db. below the response at 1000 cycles) at all frequencies above 3000 cycles. However, the low value of load or terminating resistor, 2000 ohms, greatly decreases the voltage amplification of the 6SL7GT section as compared to what could be obtained with a normal load. The over-all gain with  $R_{15}$  at maximum is about the same as with  $S_3$  in the "normal-amplifier" position, despite the extra stage, when the input signal is below the clipping level. Once clipping begins, of course, the output voltage cannot rise above the clipping level no matter how high the amplitude of the input signal.

#### Construction

The amplifier is built on a  $6 \times 14 \times 3$ -inch chassis. The input end of the speech amplifier is at the left end and the power supply is at the right. A shield is placed over the 6SL7GT to prevent hum pick-up and to protect the tube from r.f. fields from the transmitter. The 6AL5 is between the 6SL7GT and the 6V6. The 6J5 is just to the rear of the 6V6, and the output transformer,  $T_2$ , is to its right. Along the front edge of the chassis are the microphone connector; gain control,  $R_7$ ; clipper-filter switch,  $S_3$ ; the "output" control,  $R_{15}$ ; and — at the far right — the "B" voltage and a.c. toggle switches.

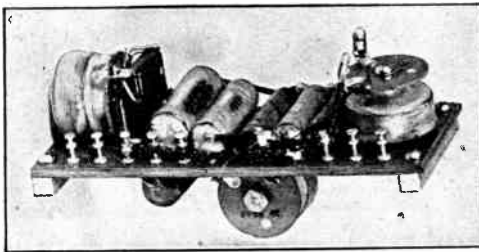


Fig. 9-27 — The low-pass filter is assembled as a unit on its own mounting board. Readily-available parts are used throughout.

The low-pass filter is built as a unit on a  $2 \times 5$ -inch mounting board, as shown in Fig. 9-27. The coils are kept well separated and are mounted so that their axes are all at right angles. This prevents magnetic coupling between them, and is essential to good filter performance. In other respects the placement of parts in the filter is not critical. If the proper values of capacitance are not at hand, they can be made up by connecting smaller units in parallel (a  $0.01\text{-}\mu\text{fd.}$  paper and  $0.005\text{-}\mu\text{fd.}$  mica can be paralleled to make  $0.015\text{-}\mu\text{fd.}$ , for example). The filter unit occupies the upper right-hand corner in the bottom-view photograph, Fig. 9-28.

Particular care should be taken to reduce hum. The 6SJ7 grid lead must be shielded, and the heater wiring in the vicinity of the first two tubes should be kept in the corners of the chassis except where it is necessary to bring

the ungrounded wire out to the socket terminal. It is worth while to try reversing the heater connections on the 6SJ7 to reduce hum. Reducing the gain at the lower frequencies also will reduce the hum in the output, and this may be done by decreasing the capacitance of  $C_5$  and  $C_7$  to  $0.002\text{-}\mu\text{fd.}$  instead of the  $0.01\text{-}\mu\text{fd.}$  specified.

The output transformer,  $T_2$ , in this unit is a low-impedance output type, with 500- and 200-ohm line taps as well as taps for a 'speaker voice coil. A Class B driver transformer can be substituted, if desired, or a 1-to-1 transformer can be used for grid-bias modulation.


#### Adjusting the Clipper-Filter Amplifier

The good effect of the low-pass filter in eliminating splatter can be entirely nullified if the amplifier stages following the filter can introduce appreciable distortion. That is a primary reason for the use of negative feedback in the output stage of the amplifier described. Amplifier stages following the unit must be operated well within their capabilities; in particular, the Class B output transformer (if a Class B modulator is to be driven) should be shunted by condensers to reduce the high-frequency response as described in the section on Class B modulators.

The setting of  $R_{15}$  is most important. It is most easily done with the aid of an oscilloscope (one having a linear sweep) and an audio oscillator, using the test set-up shown in the section on testing of speech equipment. Use a resistance load on the output transformer to reflect the proper load resistance (5000 ohms) at the plate of the 6V6. First set  $R_{15}$  at about  $\frac{1}{4}$  the resistance from the ground end, switch in the clipper-filter, and apply a 500-cycle sine-wave signal to the microphone input. Increase the signal amplitude until clipping starts, as shown by flattening of both the negative and positive peaks of the wave. To check whether the clipping is taking place in the clipper or in the following amplifiers, throw  $S_3$  to the "normal" or "out" position; the waveshape should return to normal. If it does not, return  $S_3$  to the "in" position and reduce the setting of  $R_{15}$  until it does. Then reduce the amplifier gain by means of  $R_7$  until the signal is just below the clipping level. At this point the signal should be a sine wave. Increase  $R_{15}$ , without touching  $R_7$ , until the wave starts to become distorted, and then reduce the setting of  $R_{15}$  until the distortion just disappears.

Next, change the input-signal frequency to 2000 cycles, without changing the signal level. Slowly increase  $R_7$  while observing the pattern. At this frequency it should be almost impossible to get anything except a sine wave through the filter, so if distortion appears it is the result of overloading in the amplifiers following the filter. Reduce the setting of  $R_{15}$  until the distortion disappears, even when  $R_7$  is set at maximum and the maximum available signal

Fig. 9-28 — Bottom view of the clipper-filter speech amplifier. Resistors and condensers are grouped around the sockets to which they connect.

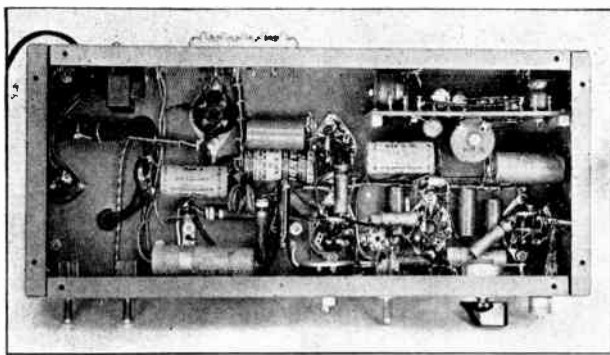

from the audio oscillator is applied to the amplifier. The position of  $R_{15}$  should be marked at this point and the marked setting should never be exceeded.

To find the *operating* setting of  $R_{15}$ , leave the audio-oscillator signal amplitude at the value just under the clipping level and set up the complete transmitter for a modulation check, using the oscilloscope to give the trapezoidal pattern. With the Class C amplifier and modulator running, find the setting of  $R_{15}$  (keeping the audio signal just under the clipping level) that just gives 100-per-cent modulation. This setting should be below the maximum setting of  $R_{15}$  as previously determined; if it is not, the driver and modulator are not capable of modulating the transmitter 100 per cent and must be redesigned — or the Class C amplifier input must be lowered. Assuming a satisfactory setting is found, connect a microphone to the amplifier and set the amplifier gain control,  $R_7$ , so that the transmitter is modulated 100 per cent. Observe the pattern closely at different settings of  $R_7$  to see if it is possible to overmodulate. If overmodulation does not occur at any setting of  $R_7$ , the transmitter is ready for operation and  $R_{15}$  may be locked in position; it need never be touched subsequently. If some overmodulation does occur,  $R_{15}$  should be backed off until it disappears and then locked.

In the absence of an oscilloscope the other methods of checking distortion described in

the section on speech-amplifier testing may be used. The object is to prevent any distortion in all stages following the filter, so that when the clipping level is exceeded the following stages will still be working within their capabilities.

As a final check, the signal should be monitored by another station a short distance away. A receiver with a sharp crystal filter is needed for this purpose. The signal input to the receiver should be kept low enough (by using a small antenna) so that there is no danger of overloading any stage of the receiver. When the transmitter is modulated 100 per cent by a tone of about 2500 cycles, the receiving operator should be able to find only one pair of sidebands, each 2500 cycles from the carrier, even when the speech-amplifier gain control ( $R_7$ , not  $R_{15}$ ) is set well beyond the level at which 100-per-cent modulation is reached. If additional sidebands are in evidence there may be distortion in the modulator (use condensers across the modulation transformer to cut high-frequency response), or the low-pass filter in the speech amplifier may not be properly built.

## 6L6 Modulators for Low-Power Transmitters

Plate modulation for transmitters operating at final-stage plate power inputs up to 75 or 80 watts can be provided at relatively small cost by using Class AB 6L6s as modulators. The combined speech amplifier and modulator shown in Fig. 9-29 uses the 6L6s as Class AB<sub>2</sub> amplifiers and has an output (from the transformer secondary) of about 40 watts. The input amplifier is a 6J7 (a 6SJ7 can be substituted if a single-ended tube is preferred to the type with the top grid cap). It is resistance-coupled to a 6J5 second amplifier, and the 6J5 is in turn coupled through a transformer to a pair of 6J5s in push-pull. These two tubes supply the power necessary to drive the 6L6s into the grid-current region. (A 6SN7GT can be substituted for the pair of 6J5s in the push-pull stage if desired; no changes in circuit constants will be necessary.)

The amplifier is built on a 6 × 14 × 3-inch chassis. The photographs show the arrangement of parts. About the only constructional precaution that must be observed is to use a short lead from the microphone socket (a jack may be used instead of the screw-on type) and to shield the entire input circuit to the grid of the 6J7. This shielding is necessary to reduce hum pick-up. In this amplifier the 6J7 grid resistor,  $R_1$ , is enclosed along with the input jack in a National Type JS-1 jack shield, and a shielded lead is run from the jack shield to the grid of the 6J7. A metal slip-on shield covers the grid cap of the tube. The amplifier has more than enough gain for typical crystal microphones.

This unit may be used to plate-modulate 80 watts input to an r.f. amplifier. For cathode modulation, the input that can be modulated

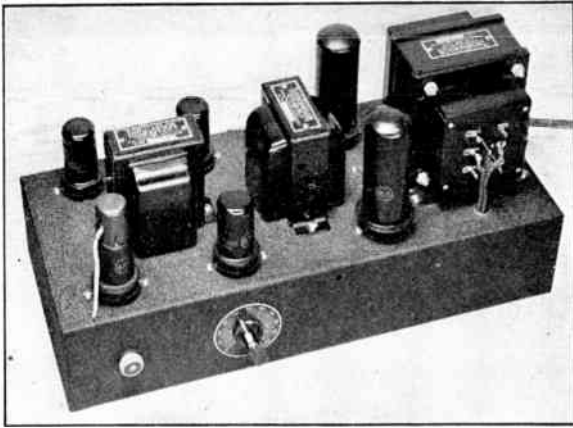


Fig. 9-29 — A 40-watt speech amplifier or modulator of inexpensive construction. The 6J7 and first 6J5 are at the front, near the microphone socket and volume control, respectively.  $T_1$  is behind them, and the push-pull 6J5s are at the rear of the chassis behind  $T_1$ .  $T_2$ , in the center, the push-pull 6L6s, and  $T_3$  follow in order to the right.

will depend upon the type of operation chosen, as described earlier. For instance, with 55-per-cent plate efficiency in the r.f. stage the input may be of the order of 200 watts, making an allowance for the small amount of audio power taken by the grid circuit. The

output transformer shown in the photograph is a universal Class B output type suitable for coupling to a plate-modulated amplifier; other types may be substituted if the r.f. amplifier is to be cathode-modulated. Whatever the type of service, the output-transformer turns

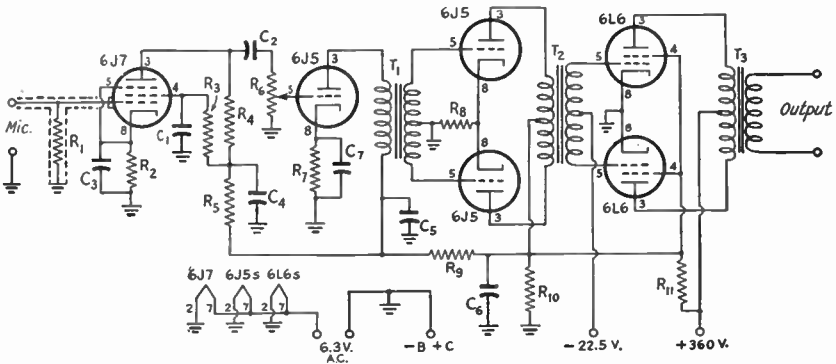



Fig. 9-30 — Circuit diagram of the Class AB<sub>2</sub> push-pull-6L6 40-watt speech amplifier or modulator.

- $C_1$  — 0.1- $\mu$ fd. 200-volt paper.
- $C_2$  — 0.01- $\mu$ fd. 400-volt paper.
- $C_3, C_7$  — 20- $\mu$ fd. 50-volt electrolytic.
- $C_4, C_6, C_6$  — 8- $\mu$ fd. 450-volt electrolytic.
- $R_1$  — 4.7 megohms,  $\frac{1}{2}$  watt.
- $R_2$  — 1500 ohms,  $\frac{1}{2}$  watt.
- $R_3$  — 1.5 megohms,  $\frac{1}{2}$  watt.
- $R_4$  — 0.22 megohm,  $\frac{1}{2}$  watt.

- $R_5$  — 47,000 ohms,  $\frac{1}{2}$  watt.
- $R_6$  — 1-megohm volume control.
- $R_7$  — 1500 ohms, 1 watt.
- $R_8$  — 750 ohms, 1 watt.
- $R_9$  — 12,000 ohms, 1 watt.
- $R_{10}$  — 20,000 ohms, 25 watts.
- $R_{11}$  — 1500 ohms, 10 watts.
- $T_1$  — Interstage audio, single plate to p.p. grids, 3:1 ratio

- (Thordarson T-57A41).
- $T_2$  — Driver transformer, p.p. 6J5s to 6L6s, Class AB<sub>2</sub> (Thordarson T-84D59).
- $T_3$  — Output transformer, type depending on requirements. A multitap modulation transformer (Thordarson T-19M15) is shown.

Fig. 9-31 — Underneath the chassis of the 40-watt speech amplifier-modulator.

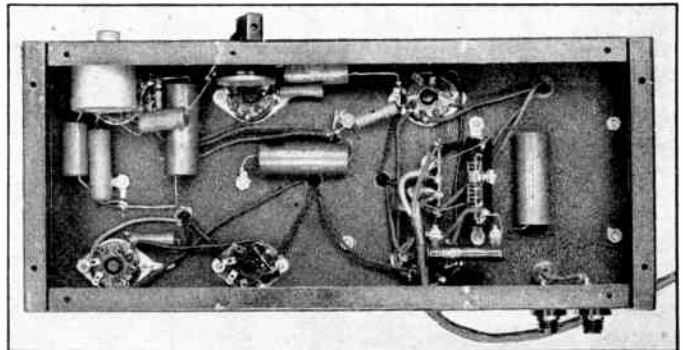

ratio should be chosen to couple properly between 3800 ohms (the plate-to-plate load required by the 6L6s) and the modulating impedance of the r.f. amplifier.

The power supply should have good voltage regulation, since the total "B" current varies from approximately 140 ma. with no signal to 265 ma. at full output. A heavy-duty choke-input plate supply should be used; general design data will be found in Chapter Seven. Heater requirements are 6.3 volts at 3 amperes. Bias for the 6L6 stage can be supplied conveniently by a 22.5-volt "B"-battery block; a small-sized unit will be satisfactory.

Fig. 9-32 is the circuit of a speech amplifier and modulator that has an output of approximately 20 watts. This circuit also uses 6L6s as output tubes, but the amplifier operates Class AB<sub>1</sub> and thus requires no driving power. Aside from the fact that there is one less voltage-amplifier stage than in the 40-watt unit, the same general construction may be followed. The first two stages are identical in circuit with the first two stages in the 40-watt amplifier, and the same constructional precautions should be observed with respect to shielding the grid circuit of the first tube. This amplifier can be used to plate-modulate an input of 40 watts to the r.f. amplifier. It is necessary, of course, to choose the proper output-transformer turns ratio to couple the modulator and modulated ampli-

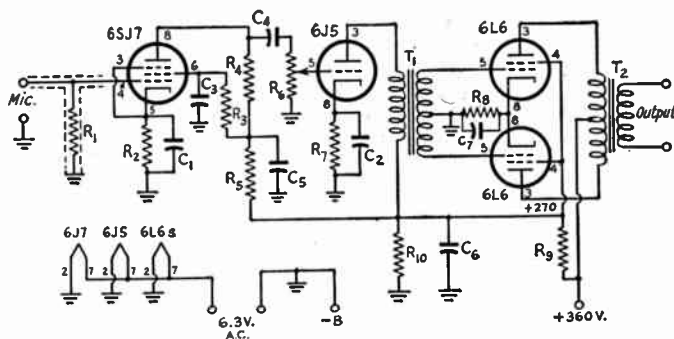


Fig. 9-32 — Circuit diagram of the low-cost speech amplifier or modulator capable of power outputs up to 20 watts.

- C<sub>1</sub>, C<sub>2</sub> — 20- $\mu$ fd. 50-volt electrolytic.
- C<sub>3</sub> — 0.1- $\mu$ fd. 200-volt paper.
- C<sub>4</sub> — 0.01- $\mu$ fd. 400-volt paper.
- C<sub>5</sub>, C<sub>6</sub> — 8- $\mu$ fd. 450-volt electrolytic.
- C<sub>7</sub> — 50- $\mu$ fd. 50-volt electrolytic.
- R<sub>1</sub> — 4.7 megohms,  $\frac{1}{2}$  watt.
- R<sub>2</sub> — 1500 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 1.5 megohms,  $\frac{1}{2}$  watt.
- R<sub>4</sub> — 0.22 megohm,  $\frac{1}{2}$  watt.
- R<sub>5</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>6</sub> — 1-megohm volume control.

- R<sub>7</sub> — 1500 ohms, 1 watt.
- R<sub>8</sub> — 250 ohms, 10 watts.
- R<sub>9</sub> — 2000 ohms, 10 watts.
- R<sub>10</sub> — 20,000 ohms, 25 watts.
- T<sub>1</sub> — Interstage audio transformer, single plate to p.p. grids, ratio 3:1 (Thordarson T-57A41).
- T<sub>2</sub> — Output transformer, type depending on requirements. A multitap transformer (Thordarson T-19M14) is shown in photos.

fier. The output stage of the unit is designed to work into a plate-to-plate load of 9000 ohms.

For the maximum power output of 20 watts, the plate supply for the amplifier must deliver 145 ma. at 360 volts. A condenser-input supply of ordinary design (Chapter Seven) may be used. The total plate current is approximately 120 ma. with no signal and 145 ma. at full output. If a power output of no more than 12 or 13 watts is needed, R<sub>9</sub> and R<sub>10</sub> may be left out of the circuit and all tubes fed directly from a "B" supply giving approximately 175 ma. at 270 volts.

## An 807 Modulator and Speech Amplifier

The combined speech amplifier and modulator unit shown in Fig. 9-33 is simple and inexpensive in design and, with the exception of the plate supply for the modulator tubes, is contained on a chassis measuring 3 × 8 × 17 inches. With a 750-volt plate supply, it is capable of a tube output of 120 watts, or enough to plate-modulate a Class C stage with 200 watts input, allowing for moderate losses in the modulation transformer. The output tubes, 807s, will develop this amount of audio power when operated as Class AB<sub>2</sub> amplifiers, but require only a small amount of grid driving power.

As shown in Fig. 9-34 the first tube in the speech amplifier is a 6J7 (a 6SJ7 may be substituted). A 6SN7GT is used in the second stage, one section serving as a voltage amplifier and the other as a phase inverter of the self-balancing type. The gain control for the amplifier

is in the grid circuit of the first half of the tube. The third tube, also a 6SN7GT, is a push-pull amplifier, transformer-coupled to the grids of the 807s.

A power supply for the three tubes preceding the 807s is built on the same chassis. Voltage for the 807 screens is taken from this same supply. The negative return of the supply goes to the chassis through the adjustable arm of potentiometer R<sub>17</sub>, which is connected in series with the bleeder resistor, R<sub>16</sub>. The voltage developed in the section of R<sub>17</sub> below the adjustable arm is negative with respect to chassis, and is used to provide fixed bias for the 807s. C<sub>11</sub> is connected across this section of R<sub>17</sub> to by-pass any a.f. current that might flow through the resistor. A separate filament transformer is provided for the 807 heaters, since the total heater power required by all the tubes in the amplifier is somewhat in ex-



Fig. 9-33 — A speech amplifier and 807 modulator for plate modulation of transmitters up to 200 watts input. The microphone jack and the gain control are at the left end of the chassis. The audio components and tubes occupy the front section and the power supply for the driver tubes is laid out along the rear edge.

cess of the rating of the 6.3-volt winding on the ordinary small power transformer.

Resistors  $R_{14}$  and  $R_{15}$  and condenser  $C_8$  are

The frequency response of this unit is maximum in the range from about 200 to 2500 cycles, for greatest voice effectiveness and mini-

placed in the 807 screen circuit to suppress the r.f. parasitic oscillations that sometimes occur with these tubes. Their use is principally a precautionary measure, and they may not be required in most installations.


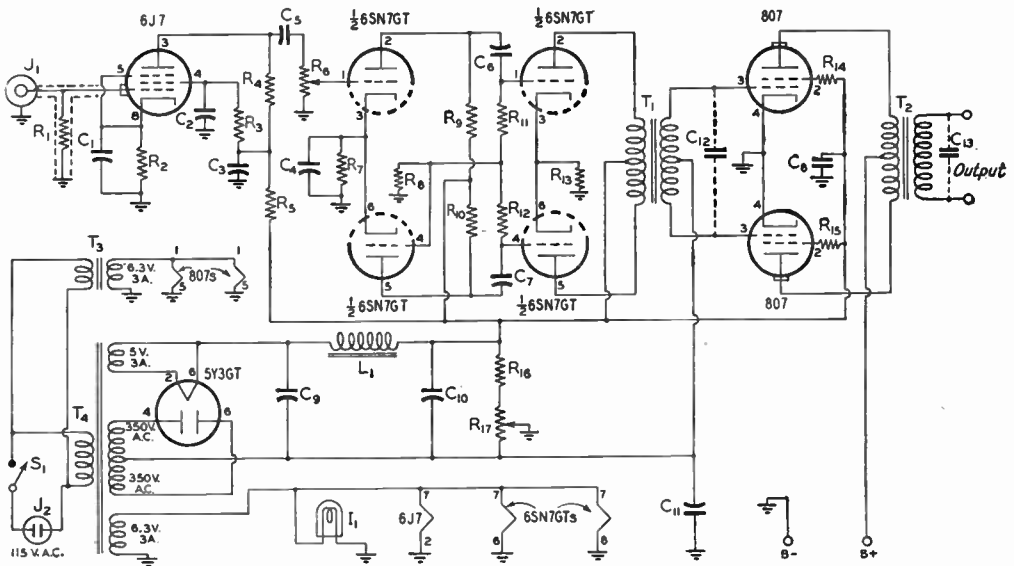


Fig. 9-34 — Circuit diagram of the p.p. 807 speech amplifier-modulator.

- $C_1$  — 10- $\mu$ fd. 50-volt electrolytic.
- $C_2$  — 0.1- $\mu$ fd. 400-volt paper.
- $C_3, C_9, C_{10}$  — 8- $\mu$ fd. 450-volt electrolytic.
- $C_4, C_{11}$  — 50- $\mu$ fd. 50-volt electrolytic.
- $C_5, C_6, C_7$  — 0.01- $\mu$ fd. 400-volt paper.
- $C_8$  — 0.0068- $\mu$ fd. mica.
- $C_{12}$  — 0.001- $\mu$ fd. mica (see text).
- $C_{13}$  — 0.02- $\mu$ fd. mica (see text).
- $R_1$  — 1 megohm.
- $R_2, R_7$  — 1500 ohms.
- $R_3$  — 1.5 megohms.
- $R_4, R_8, R_{11}, R_{12}$  — 0.22 megohm.
- $R_5$  — 47,000 ohms.
- $R_6$  — 1-megohm volume control.
- $R_9, R_{10}$  — 0.1 megohm.
- $R_{13}$  — 470 ohms.
- $R_{14}, R_{15}$  — 100 ohms.
- $R_{16}$  — 15,000 ohms, 10 watts.

- $R_{17}$  — 1000-ohm wire-wound potentiometer.
- (All resistors  $\frac{1}{2}$  watt unless otherwise noted.)
- $L_1$  — Smoothing choke, 30 hy., 75 ma., 340-ohm d.c. resistance (Utah 4002).
- $I_1$  — 6.3-volt a.c. pilot-lamp-and-socket assembly.
- $J_1$  — Microphone-cable jack.
- $J_2$  — Panel-mounting a.c. plug (Amphenol 61-M1).
- $S_1$  — S.p.s.t. switch.
- $T_1$  — Push-pull plates to push-pull grids (UTC S-9).
- $T_2$  — Output transformer, type depending on requirements. A multitap transformer (UTC VM-3) is shown in photos.
- $T_3$  — Filament transformer, 6.3 volts, 3 amp. (Thorndarson T-21F10).
- $T_4$  — Power transformer, 350 volts a.c. each side of center-tap, 70-ma. rating. Filament windings: 5 v., 3 amp.; 6.3 v., 3 amp. (Stancor P-4078).

Fig. 9-35 — Below-chassis view of the 807 modulator. The shielded microphone jack is in the upper left-hand corner. The filter choke is mounted in the lower left-hand corner and the 807 filament transformer is to the rear and slightly to the right of the 807 tube sockets. The condenser for attenuating the high audio frequencies, shown at the right-hand end of the chassis, is supported by No. 12 wire leads which connect to the output terminals of the modulation transformer.

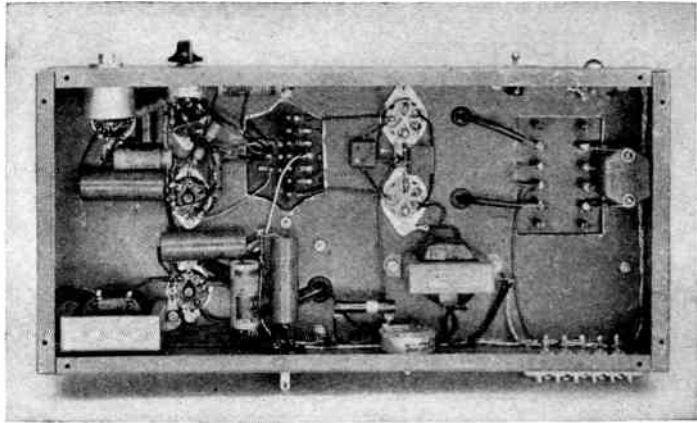

imum width of the r.f. channel. Frequencies above 2500 cycles are attenuated by condensers  $C_{12}$  and  $C_{13}$ , the former across the secondary of the driver transformer and the latter across the secondary of the output transformer. The capacitance values given are about optimum for the types of transformers specified and should be close to optimum for other transformers of similar ratings. The voltage rating of  $C_{13}$  should be at least equal to the d.c. voltage on the modulated r.f. amplifier.

**Construction**

The photographs show the general layout of components. The 6J7 and 6SN7GT phase inverter are in line at the left-hand front edge of the chassis. The 6SN7GT driver and 5Y3GT rectifier are to the rear of the phase inverter. The driver transformer,  $T_1$ , is at the front and the power transformer,  $T_4$ , is at the rear. Plate leads for the 807s run through rubber grommets in the chassis.

The bottom view shows the by-pass condensers and resistors grouped around the sockets to which they connect. The bias-control potentiometer,  $R_{17}$ , is mounted on the rear edge of the chassis, and the power-supply

bleeder,  $R_{16}$ , is mounted between  $R_{17}$  and an insulated tie-point on the chassis near the a.c. input socket (also on the rear chassis edge). A jack shield (National JS-1) covers the microphone jack, and the first-stage grid resistor,  $R_1$ , is mounted inside this shield. The lead to the 6J7 grid cap must be shielded and the shield grounded.

The No. 1 terminals of the driver transformer specified should be connected to the grids of the 807s. If a different transformer is used, it should have a primary-to-secondary ratio (total) of about 1-to-1 to couple the 6SN7GT and 807 grids properly. The output-transformer turns ratio will depend on the type of operation selected and the modulating impedance of the Class C amplifier. Operated at ICAS ratings, the 807s will deliver a tube output of 120 watts into a plate-to-plate load of 6950 ohms. This requires a plate supply capable of delivering 240 ma. at 750 volts. At CCS ratings the tubes will deliver 80 watts into a 6400-ohm load and require a 600-ma. plate supply. The bias should be set, by means of  $R_{17}$ , to give -32 volts between the potentiometer arm and chassis for ICAS operation, and to -30 volts for CCS operation.

**Drivers for Class-B Modulators**

**Driving Power**

Class B amplifiers are driven into the grid-current region, so power is consumed in the grid circuit. The preceding stage or driver must be capable of supplying this power at the required peak audio-frequency grid-to-grid voltage. Both of these quantities are given in the manufacturer's tube ratings. The grids of the Class B tubes represent a variable load resistance over the audio-frequency cycle, because the grid current does not increase directly with the grid voltage. To prevent distortion, therefore, it is necessary to have a driving source that will maintain the waveform of the signal without distortion even though the load varies. That is, the driver stage must have good

regulation. To this end, it should be capable of delivering somewhat more power than is consumed by the Class B grids, as previously described in the discussion on speech amplifiers. It is also desirable to use an input coupling transformer having a turns ratio giving the largest step-down in the voltage between the driver plate or plates and the Class B grids that will permit obtaining the specified grid-to-grid a.f. voltage.

The peak output voltage at the primary of the driver transformer is

$$E_o = 1.4\sqrt{PR}$$

where  $E_o$  = Peak value of a.f. output voltage  
 $P$  = Rated power output of driver  
 $R$  = Rated load impedance for driver

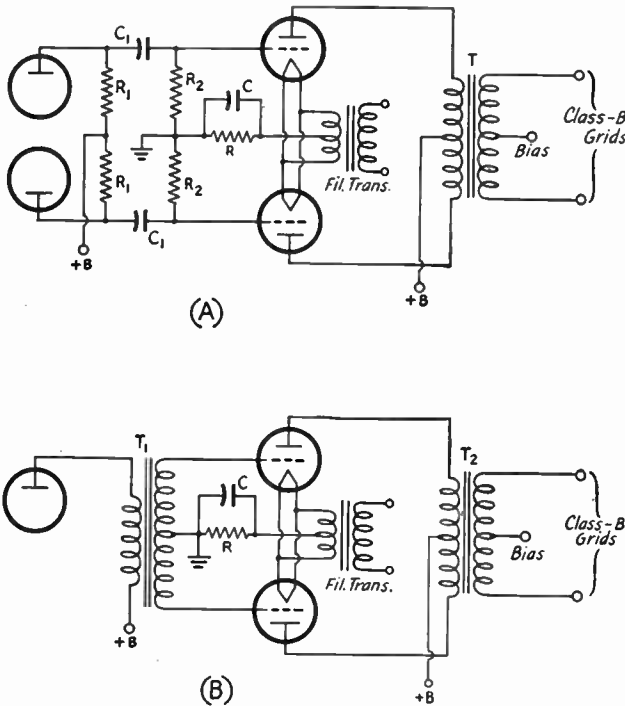


Fig. 9-36 — Triode driver circuits for Class B modulators. A, resistance coupling to grids; B, transformer coupling.  $R_1$  in A is the plate resistor for the preceding stage, value determined by the type of tube and operating conditions as given in Table 9-1.  $C_1$  and  $R_2$  are the coupling condenser and grid resistor, respectively; values also may be taken from Table 9-1.

In both circuits the output transformer,  $T_2$ , should have the proper turns ratio to couple between the driver tubes and the Class B grids.  $T_1$  in B is usually a 2:1 transformer, secondary to primary.  $R$ , the cathode resistor, should be calculated for the particular tubes used. The value of  $C$ , the cathode bypass, is determined as described in the text.

This is correct when the driver is working into its rated load. When the load is the grid circuit of a Class B modulator, the impedance varies over the audio-frequency cycle. It reaches a minimum value when the signal reaches a positive peak and the grid current has its maximum instantaneous value. The best that can be done is to assume that, if the driver has more than enough power output, the turns ratio of the driver transformer should be

$$N = \frac{E_o}{E}$$

where  $N$  = Driver-transformer turns ratio, primary to secondary

$E_o$  = Peak output voltage of driver

$E$  = Peak grid-to-grid voltage required by Class B tubes.

Example: A pair of Class B tubes requires a driving power of 7 watts and a peak a.f. grid-to-grid voltage of 200 for maximum output. The driver has a maximum output of 10 watts when working into a 5000-ohm load. The peak output voltage at the primary of the driver transformer is

$$E_o = 1.4 \sqrt{PR} = 1.4 \sqrt{10 \times 5000} = 1.4 \times 224 = 314 \text{ volts}$$

The driver-transformer turns ratio, primary to secondary, should be

$$N = \frac{E_o}{E} = \frac{314}{200} = 1.57 \text{ to } 1$$

Commercial transformers frequently are designed for specific driver-modulator combinations, and the turns ratio is chosen to give as good driver regulation as the conditions will permit.

The driver transformer,  $T$  or  $T_2$  in Fig. 9-36, may couple directly between the driver tube and the modulator grids or may be designed to work into a low-impedance (200- or 500-ohm) line. In the latter case, a tube-to-line output transformer must be used at the output of the driver stage. This type of coupling is recommended only when the driver must be at a considerable distance from the modulator; the second transformer not only introduces additional losses but also impairs the voltage regulation of the driver stage.

### Driver Tubes

The variation in grid resistance of a Class B amplifier over the audio-frequency cycle poses a special problem in the driver stage. To avoid distortion, the driver output voltage (not power) must stay constant (for a fixed signal voltage on its grid) regardless of the variations in load resistance.

The fundamental requirement for good voltage regulation in any electrical generator is that the internal resistance must be low. In a vacuum-tube amplifier, this means that the tubes must have a low value of plate resistance. The best tubes in this respect are low- $\mu$  triodes (the 6A3 is an example) and the worst are tetrodes and pentodes as represented by the 6V6 and 6L6. This does not mean that tetrodes (or pentodes) cannot be used, but it does mean that they should not be used without taking measures to reduce the effective plate resistance (see next section).

In selecting a driver stage always choose Class A or AB<sub>1</sub> operation in preference to Class AB<sub>2</sub>. This not only simplifies the speech-amplifier design but also makes it easier to apply negative feed-back to tetrodes for reduction of plate resistance. It is possible to obtain a tube power output of approximately 25 watts (from 6L6s) without going beyond Class AB<sub>1</sub> operation; this is ample driving power for the popular Class B modulator tubes, even when a



kilowatt transmitter is to be modulated.

The rated tube output (as shown by the tube tables) should be reduced by about 20 per cent to allow for losses in the Class B input transformer. If two transformers are used, tube-to-line and line-to-grids, allow about 35 per cent for transformer losses. Another 25 per cent should be allowed, if possible, as a safety factor and to improve the voltage-regulation.

Fig. 9-36 shows representative circuits for a push-pull triode driver using cathode bias. If the amplifier operates Class A, the cathode resistor need not be by-passed, because the a.f. currents from each tube flowing in the cathode resistor are out of phase and cancel each other. However, in Class AB operation this is not true; considerable distortion will be generated at high signal levels if the cathode resistor is not by-passed. The by-pass capacitance required can be calculated by a simple rule: the cathode resistance in ohms multiplied by the by-pass capacitance in microfarads should equal at least 25,000. The voltage rating of the condenser should be equal to the maximum bias voltage. This can be found from the maximum-signal plate current and the cathode resistance.

Example: A pair of 6A3s is to be used in Class AB<sub>1</sub> self-biased. From the tube tables, the cathode resistance should be 780 ohms and the maximum-signal plate current 120 ma. From Ohm's Law,

$$E = RI = 780 \times 0.12 = 93.6 \text{ volts}$$

From the rule mentioned previously, the by-pass capacitance required is  
 $C = 25,000/R = 25,000/780 = 32 \mu\text{fd.}$   
 A 40- or 50- $\mu\text{fd.}$  100-volt electrolytic condenser would be satisfactory.

**Negative Feed-Back**

Whenever tetrodes or pentodes are used as drivers for Class B modulators, negative feed-back should be used in the driver stage. This will reduce the distortion caused by the variable load resistance represented by the Class B grids. It also reduces the distortion inherent in the driver stage itself, when properly applied. The effect of feed-back is to reduce the apparent plate resistance of the driver, and this in turn helps to maintain the a.f. output voltage at a more constant level (for a constant signal on the grid) when the load resistance varies. It is readily possible to reduce the plate resistance to a value comparable to or lower than that of low- $\mu$  triodes such as the 6A3.

Suitable circuits for single-ended and push-pull tetrodes are shown in Fig. 9-37. Fig. 9-37A shows resistance coupling between the preceding stage and a single tetrode, such as the 6V6, that operates at the same plate voltage as the preceding stage. Part of the a.f. voltage across the primary of the output transformer is fed back to the grid of the tetrode,  $V_2$ , through the plate resistor of the preceding tube,  $V_1$ . The amount of voltage so fed back is determined by the voltage divider,  $R_4R_5$ . The total resistance of  $R_4$  and  $R_5$  in series should be large compared to the rated load resistance of  $V_2$ . Instead of the voltage divider, a tap on the transformer primary can be used to supply the feed-back voltage, if such a tap is available.

The amount of feed-back voltage that appears at the grid of tube  $V_2$  is determined by  $R_1$ ,  $R_2$  and the plate resistance of  $V_1$ , as well as by the relationship between  $R_4$  and  $R_5$ . Calculation of the feed-back voltage, although not mathematically difficult, is not ordinarily practicable because the plate resistance of  $V_1$  is seldom known at the particular operating conditions used. Circuit values for a typical tube combination are given in detail in Fig. 9-37.

The push-pull circuit in Fig. 9-37B requires an audio transformer with a split secondary. The feed-back voltage is obtained from the plate of each output tube by means of the voltage divider,  $R_1R_2$ . The blocking condenser,  $C_1$ , prevents the d.c. plate voltage from being applied to  $R_1R_2$ ; the reactance of this condenser should be low, compared to the sum of  $R_1$  and  $R_2$ , at the lowest audio frequency to be amplified. Also, the sum of  $R_1$  and  $R_2$  should be high compared to the rated load resistance for  $V_2$  and  $V_3$ .

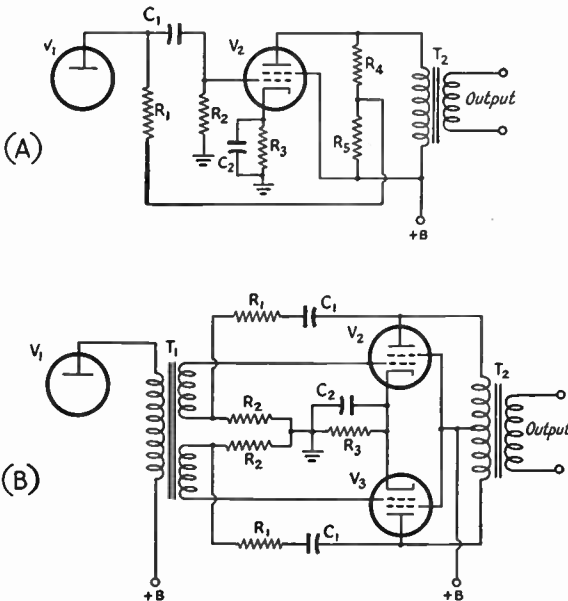


Fig. 9-37 — Negative feed-back circuits for drivers for Class B modulators. A — Single-ended beam-tetrode driver. If  $V_1$  and  $V_2$  are a 6J5 and 6V6, respectively, the following values are suggested:  $R_1$ , 47,000 ohms;  $R_2$ , 0.47 megohm;  $R_3$ , 250 ohms;  $R_4$ ,  $R_5$ , 22,000 ohms;  $C_1$ , 0.01  $\mu\text{fd.}$ ;  $C_2$ , 50  $\mu\text{fd.}$   
 B — Push-pull beam-tetrode driver. If  $V_1$  is a 6J5 and  $V_2$  and  $V_3$  6L6s, the following values are suggested:  $R_1$ , 0.1 megohm;  $R_2$ , 22,000 ohms;  $R_3$ , 250 ohms;  $C_1$ , 0.1  $\mu\text{fd.}$ ;  $C_2$ , 100  $\mu\text{fd.}$

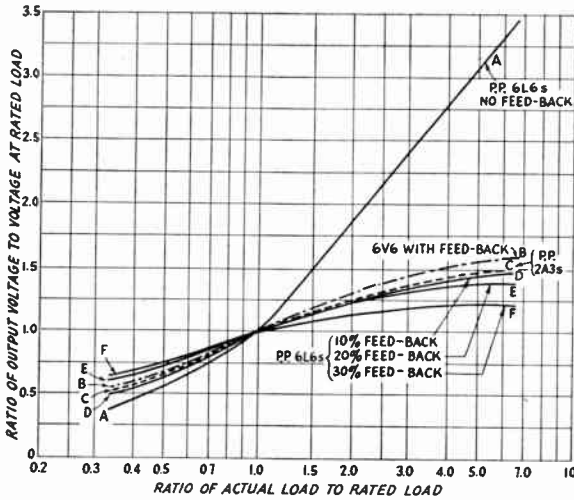


Fig. 9-38 — Output voltage regulation of two types of beam-tetrode drivers with negative feed-back. For comparison, the regulation with a pair of 2A3s (no feed-back) also is shown.

In this circuit the feed-back voltage that is developed across  $R_2$  also appears at the grid of  $V_2$  (or  $V_3$ ) because there is no appreciable current flow (in the usual audio range) through the transformer secondary and grid-cathode circuit of the tube, provided the tubes are not driven to grid current. The circuit should not be used with tubes that are operated Class AB<sub>2</sub>. The per cent feed-back is

$$n = \frac{R_2}{R_1 + R_2} \times 100$$

where  $n$  is the feed-back percentage, and  $R_1$  and  $R_2$  are connected as shown in the diagram. The higher the feed-back percentage, the lower the effective plate resistance. However, if the percentage is made too high the preceding tube,  $V_1$ , may not be able to develop enough voltage, through  $T_1$ , to drive the push-pull stage to maximum output without itself generating harmonic distortion. Distortion in  $V_1$  is not compensated for by the feed-back circuit. If  $V_2$  and  $V_3$  are 6L6s operated self-biased in Class AB<sub>1</sub> with a load resistance of 9000 ohms,  $V_1$  is a 6J5, and  $T_1$  has a turns ratio of 2-to-1, total secondary to primary, it is possible to use over 30-per-cent feed-back without going beyond the output-voltage capabilities of the 6J5. Actually, it is unnecessary to use more than about 20-per-cent feed-back. This value reduces the effective plate resistance to the point where the output voltage regulation is better than that of 6A3s or 2A3s without feed-back.

Instead of the voltage-divider arrangement shown in Fig. 9-37B for obtaining feed-back voltage, a separate winding on the output transformer can be used, provided it has the proper number of turns to give the desired feed-back percentage. Special transformers are available for this purpose.

The improvement in constancy of output voltage resulting from the use of negative feed-back is shown graphically in Fig. 9-38.

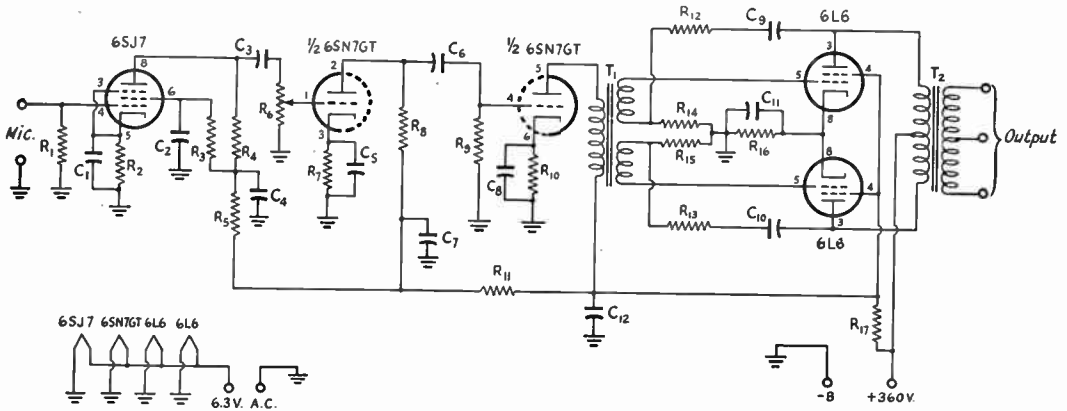


Fig. 9-39 — Circuit diagram of speech amplifier using 6L6s with negative feed-back, suitable for driving Class B modulators up to 500 watts output.

- C<sub>1</sub>, C<sub>5</sub>, C<sub>8</sub> — 20- $\mu$ f. 25-volt electrolytic.
- C<sub>2</sub>, C<sub>9</sub>, C<sub>10</sub> — 0.1- $\mu$ f. 400-volt paper.
- C<sub>3</sub>, C<sub>6</sub> — 0.01- $\mu$ f. 600-volt paper.
- C<sub>4</sub>, C<sub>7</sub>, C<sub>12</sub> — 10- $\mu$ f. 450-volt electrolytic.
- C<sub>11</sub> — 100- $\mu$ f. 50-volt electrolytic.
- R<sub>1</sub> — 2.2 megohms, 1/2 watt.
- R<sub>2</sub>, R<sub>7</sub> — 1500 ohms, 1/2 watt.
- R<sub>3</sub> — 1.5 megohms, 1/2 watt.
- R<sub>4</sub> — 0.22 megohm, 1/2 watt.
- R<sub>5</sub>, R<sub>8</sub> — 47,000 ohms, 1/2 watt.
- R<sub>6</sub> — 1-megohm volume control.

- R<sub>9</sub> — 0.47 megohm, 1/2 watt.
- R<sub>10</sub> — 1500 ohms, 1 watt.
- R<sub>11</sub> — 10,000 ohms, 1/2 watt.
- R<sub>12</sub>, R<sub>13</sub> — 0.1 megohm, 1 watt.
- R<sub>14</sub>, R<sub>15</sub> — 22,000 ohms, 1/2 watt.
- R<sub>16</sub> — 250 ohms, 10 watts.
- R<sub>17</sub> — 2000 ohms, 10 watts.
- T<sub>1</sub> — Interstage audio, 2:1 secondary (total) to primary, with split secondary winding.
- T<sub>2</sub> — Class B input transformer to suit modulator tubes.

In order to compare the various types of tubes, the variation in output voltage is shown as a percentage of the output voltage when the tubes are working into the rated load. The load resistance also is expressed as a percentage of the rated load resistance for the particular tube, or pair of tubes, used.

A circuit for a speech-amplifier suitable for driving a Class B modulator is given in Fig. 9-39. In this amplifier the 6L6s are operated Class AB<sub>1</sub> and will deliver up to 20 watts to the grids of the Class B amplifier. The feedback circuit requires no adjustment, but does require an interstage transformer with two separate secondary windings (split secondary).

This amplifier may be constructed along the same lines as in Fig. 9-29, observing the same precautions with respect to shielding the

6SJ7 grid circuit. Although the power output is the same as from the amplifier of Fig. 9-32, an additional voltage-amplifier stage is incorporated in the circuit. This is necessary because the voltage fed back from the plates to the grids of the 6L6s opposes the voltage from the preceding stage, so the latter must be increased in order to maintain the same power output from the 6L6s. In turn, this necessitates more over-all voltage gain than is required to drive Class AB<sub>1</sub> push-pull 6L6s without feedback.

The output transformer, T<sub>2</sub>, should be selected to work between a 9000-ohm plate-to-plate load and the grids of whatever Class B tubes will be used. The power-supply requirements for this amplifier are essentially the same as for the amplifier of Fig. 9-32.

### Class-B Modulators

Plate modulation of all but low-power transmitters requires so much audio power that the Class B amplifier is the only practical type to use. (Included in the Class B category are high-power modulators of the Class AB<sub>2</sub> type; whether the operation is in one class or the other is principally a matter of degree.)

Class B modulator circuits are practically identical no matter what the power output of the modulator. The diagrams of Fig. 9-40 therefore will serve for any modulator of this type that the amateur may elect to build. The triode circuit is given at A and the circuit for tetrodes at B. When small tubes with indirectly-heated cathodes are used, the cathodes should be connected to ground.

#### Modulator Tubes

Class B audio ratings of various types of transmitting tubes are given in the tube tables of Chapter Twenty-Five. Choose a pair of tubes that is capable of delivering sine-wave audio power equal to somewhat more than half the d.c. input to the modulated Class C amplifier. It is sometimes convenient to use tubes that will operate at the same plate voltage as that applied to the Class C stage, because one power supply of adequate current capacity may then suffice for both stages. However, available power-supply components do not always permit this, and better over-all performance and economy may result from the use of separate power supplies.

In estimating the output of the modulator, remember that the figures given in the tables are for the tube output only, and do not include output-transformer losses. The efficiency of the output transformer will vary with its construction, and may be assumed to be in the vicinity of 80 per cent for the less-expensive units

and somewhat higher for higher-priced transformers. To be adequate for modulating the transmitter, therefore, the modulator should have a theoretical power capability about 25 per cent greater than the actual power needed for modulation.

It is always desirable to provide more power capability in the modulator than actually is

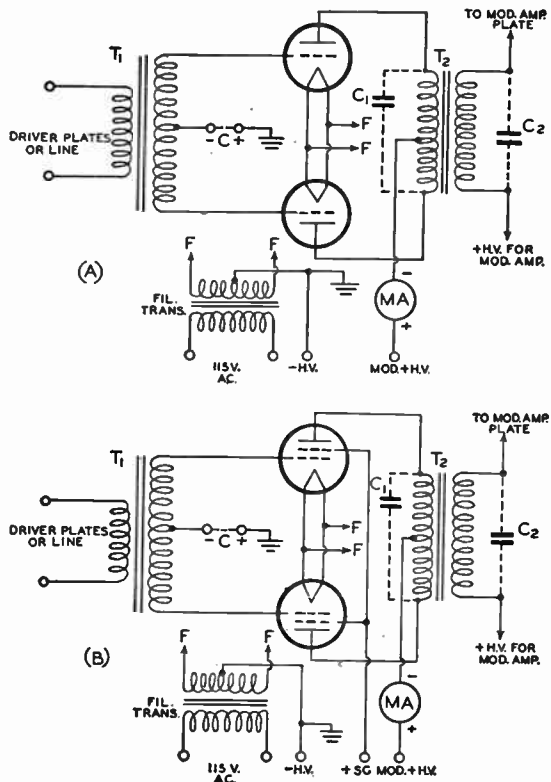


Fig. 9-40 — Class B modulator circuit diagrams. Tubes and circuit considerations are discussed in the text.

needed. Then the tubes need not be worked to the limit of their capacity, with the result that there is minimum distortion and therefore no audio harmonics — and no consequent broadening of the r.f. channel.

#### Matching to Load

In giving Class B ratings on power tubes, manufacturers specify the plate-to-plate load impedance into which the tubes must operate to deliver the rated audio power output. This load impedance seldom is the same as the modulating impedance of the Class C r.f. stage, so a match must be brought about by adjusting the turns ratio of the coupling transformer. The required turns ratio, primary to secondary, is

$$N = \sqrt{\frac{Z_p}{Z_m}}$$

where  $N$  = Turns ratio, primary to secondary

$Z_m$  = Modulating impedance of Class C r.f. amplifier

$Z_p$  = Plate-to-plate load impedance for Class B tubes

Example: The modulated r.f. amplifier is to operate at 1250 volts and 0.25 ma. The power input is

$$P = EI = 1250 \times 0.25 = 312 \text{ watts}$$

so the modulating power required is  $312/2 = 156$  watts. Increasing this by 25% to allow for losses and a reasonable operating margin gives  $156 \times 1.25 = 195$  watts. The modulating impedance of the Class C stage is

$$Z_m = \frac{E}{I} = \frac{1250}{0.25} = 5000 \text{ ohms.}$$

From the tube tables a pair of Class B tubes is selected that will give 200 watts output when working into a 6900-ohm load, plate-to-plate. The primary-to-secondary turns ratio of the modulation transformer therefore should be

$$N = \sqrt{\frac{Z_p}{Z_m}} = \sqrt{\frac{6900}{5000}} = \sqrt{1.38} = 1.175 \text{ to } 1.$$

Commercial Class B output transformers usually are rated to work between specified primary and secondary impedances and fre-

quently are designed for specific Class B tubes. In such a case, it will be unnecessary to calculate the turns ratio when the recommended tube combination is used. Many transformers are provided with primary and secondary taps, so that various turns ratios can be obtained to meet the requirements of various tube combinations.

It may be that the exact turns ratio required by a particular tube combination cannot be secured, even with a tapped modulation transformer. *Small* departures from the proper turns ratio will have no serious effect if the modulator is operating well within its capabilities; if the actual turns ratio is within 10 per cent of the ideal value the system will operate satisfactorily. Where the discrepancy is larger, it is always possible to choose a new set of operating conditions for the Class C stage to give a modulating impedance that can be matched by the turns ratio of the available transformer. This may require operating the Class C amplifier at higher voltage and less plate current, if the modulating impedance must be increased, or at lower voltage and higher current if the modulating impedance must be decreased. However, this process cannot be carried too far without exceeding the ratings of the Class C tubes for either plate voltage or current, even though the power input is kept at the same figure. In such a case the only solution is to operate at reduced input and use less of the power available from the modulator.


#### Suppressing Audio Harmonics

Distortion in either the driver or Class B modulator itself will cause a.f. harmonics that may lie outside the frequency band needed for intelligible speech transmission. While it is almost impossible to avoid some distortion, it is possible to cut down the amplitude of the higher-frequency harmonics. The purpose of condensers  $C_1$  and  $C_2$  across the primary and secondary, respectively, of the Class B output transformer in Fig. 9-40 is to



Fig. 9-41 — A conventional chassis arrangement for low- and medium-power Class B modulator stages. The mechanical layout in general follows the typical circuit diagrams given in Fig. 9-40.

Fig. 9-42—A chassis arrangement for a higher-power Class B modulator. This unit has the filament transformer for the tubes mounted on the chassis. Where the input transformer is included with the speech amplifier, less chassis space will be needed. The tubes are placed near the rear, where the ventilation is good. The plate milliammeter is provided with a small plate over the adjusting screw, to prevent touching the screw accidentally. A Presdwood panel was used for this modulator; with a metal panel, the meter should be mounted behind glass on a well-insulated mount (the meter insulation is not intended for voltages above a few hundred) or connected in the filament center-tap rather than in the high-voltage lead.

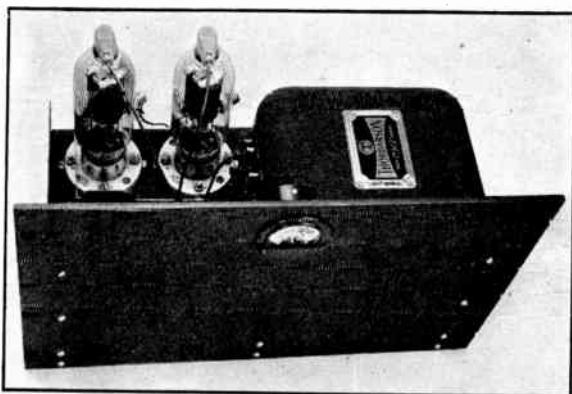

reduce the strength of harmonics and unnecessary high-frequency components existing in the modulation.

The condensers act with the leakage inductance of the transformer winding to form a rudimentary low-pass filter. The values of capacitance required will depend on the load resistance (modulating impedance of the Class C amplifier) and the leakage inductance of the particular transformer used. In general, capacitances between about 0.001 and 0.006  $\mu\text{fd.}$  will be required; the larger values are necessary with the lower values of load resistance. A test set-up for measuring frequency response (described in a later section in this chapter) will quickly show the optimum values to use, if a small assortment of condensers is on hand for experimenting. The object is to find the combination of  $C_1$  and  $C_2$  that will give the most rapid reduction in response as the signal frequency is raised above about 2500 cycles.

The voltage rating of each condenser should at least be equal to the d.c. voltage at the transformer winding with which it is associated. In the case of  $C_2$ , part of the total capacitance required usually is supplied by the plate by-pass or blocking condenser of the modulated amplifier, so  $C_2$  need only be large enough to make up the difference.

#### Grid Bias

Many modern transmitting tubes designed for Class B audio work can be operated without grid bias. Besides eliminating the need for a grid-bias supply, this reduces the variation in grid impedance over the audio-frequency cycle and thus gives the driver a more constant load into which to work. With these tubes, the grid return lead from the center-tap of the driver transformer secondary is simply connected to the filament center-tap or cathode ground.

When the tubes require bias, it should always be supplied from a fixed voltage source. Neither cathode bias nor grid-leak bias can be used with a Class B amplifier; with both types the bias changes with the amplitude of the signal voltage, whereas proper operation demands that the bias voltage be unvarying

no matter what the strength of the signal. When only a small amount of bias is required it can be obtained conveniently from a few dry cells. When greater values of bias are required, a heavy-duty "B" battery may be used if the grid current does not exceed 40 or 50 milliamperes on voice peaks. Even though the batteries are charged by the grid current rather than discharged, a battery will deteriorate with time and its internal resistance will increase. When the increase in internal resistance becomes appreciable, the battery tends to act like a grid-leak resistor and the bias varies with the applied signal. Batteries should be checked with a voltmeter occasionally while the amplifier is operating. If the bias varies more than 10 per cent or so with voice excitation the battery should be replaced.

As an alternative to batteries, a regulated bias supply may be used. This type of supply is described in Chapter Seven.

#### Plate Supply

The plate supply for a Class B modulator should be sufficiently well filtered to prevent hum modulation of the r.f. stage. An additional requirement is that the output condenser of the supply should have low reactance, at 100 cycles or less, compared to the load into which each tube is working. (This load is one-fourth of the plate-to-plate load resistance.) A 4- $\mu\text{fd.}$  output condenser with a 1000-volt supply, or a 2- $\mu\text{fd.}$  condenser with a 2000-volt supply, usually will be satisfactory. With other plate voltages, condenser values should be in inverse proportion to the plate voltage.

To keep distortion at a minimum, the voltage regulation of the plate supply should be as good as it can be made. If the d.c. output voltage of the supply varies with the amount of current taken, it should be kept in mind that the voltage at maximum current determines the amount of power that can be taken from the modulator without distortion. A supply whose voltage drops from 1500 at no load to 1250 at the full modulator plate current is a 1250-volt supply, so far as the modulator is concerned, and any estimate of the power output available should be based on the lower figure.

It is particularly important, in the case of a tetrode Class B stage, that the screen-voltage power-supply source have excellent regulation, to prevent distortion. The screen voltage should be set as exactly as possible to the recommended value for the tube.

## ● IMPROPER OPERATION

### Overexcitation

When a Class B amplifier is overdriven in an attempt to secure more than the rated power, distortion increases rapidly. The high-frequency harmonics which result from the distortion modulate the transmitter, producing spurious sidebands which can cause serious interference over a band of frequencies several times the channel-width required for speech. This may happen even though the transmitter is not being overmodulated. It *will* happen if the modulator is incapable of delivering the power required to modulate the transmitter fully, or if the Class C amplifier is not adjusted to give the proper modulating impedance.

As previously stated, the tubes used in the Class B modulator should be capable of somewhat more than the power output nominally required. In addition, the Class C amplifier should be adjusted to give the proper modulat-

ing impedance and the correct output transformer turns ratio should be used. Even though means may be incorporated in the speech amplifier to attenuate frequencies above those necessary for intelligible speech, it is still possible for high-frequency sidebands to be radiated if distortion occurs in the modulator, or if the transmitter is overmodulated. Such high-frequency harmonics as may be generated in the modulator can be reduced by connecting condensers across both the primary and secondary of the output transformer as previously described.

### Operation Without Load

Excitation should never be applied to a Class B modulator until after the Class C amplifier is turned on and is drawing the value of plate current required to present the rated load to the modulator. With no load to absorb the power, the primary impedance of the transformer rises to a high value and excessive audio voltages are developed across it — frequently high enough to break down the transformer insulation. If the modulator is to be tested separately from the transmitter, a resistance of the same value as the modulating impedance, and capable of dissipating the full power output of the modulator, should be connected across the transformer secondary.

## Checking Speech Equipment

One way to check the performance of speech equipment is to put the complete transmitter on the air and depend on the comments of other amateurs. If it turns out that anything is wrong, fixing it becomes a slow and rather painful process not only to those concerned but to those who have to put up with the interference it causes. It is also a not altogether reliable method, since the reports are necessarily biased by the receiving operator's opinions of what is good or bad, to say nothing of the reluctance of most operators to be wholly frank — they don't want to hurt your feelings or appear to be casting doubt on your abilities.

The other method is to check it yourself, with the help of some measuring gear. An

adequate job can be done with equipment that is neither elaborate nor expensive. A simple set-up is shown in Fig. 9-43. The only equipment that is not likely to be already at hand is the audio oscillator (the construction of a very simple one is described in Chapter Sixteen). The voltmeter — one that operates at audio frequencies is necessary — is available in any multirange volt-ohm-milliammeter that has a rectifier-type a.c. range. The headset is included for aural checking of the amplifier performance.

A two-step attenuator for the output of the audio oscillator is recommended so that a wide range of output voltages can be smoothly controlled. Also,  $R_3$  should have relatively low resistance — 500 ohms or less; operating at low impedance will minimize stray hum pick-up, which might cause false results when the amplifier gain is high.

As a preliminary check, cover the microphone input terminals with a metal shield (with the audio oscillator and attenuator disconnected) and, while listening in the headset, note the hum level with the amplifier gain control in the off position. The hum should be very low under these conditions. Then increase the gain-control setting to maximum and observe the hum; it will no doubt increase. Then connect the audio oscillator and attenuator and, starting from minimum

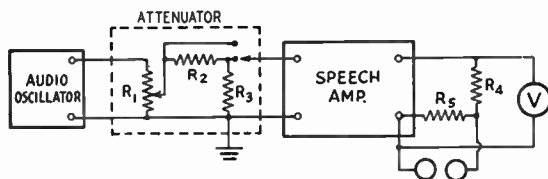


Fig. 9-43 — Simple test set-up for checking a speech amplifier. The audio-oscillator frequency range should be from about 100 to 5000 cycles. It is not necessary that it be continuously variable; a number of "spot" frequencies will be satisfactory. Suitable resistor values are:  $R_1$ , 50,000-ohm potentiometer;  $R_2$ , 4700 ohms;  $R_3$ , 470 ohms;  $R_4$ , rated load resistance for amplifier output stage;  $R_5$ , determine by trial for comfortable headphone level (25 to 100 ohms, ordinarily).  $V$  is a high-resistance a.c. voltmeter, multirange rectifier type.

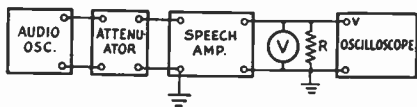


Fig. 9-44 — Test set-up using an oscilloscope for checking waveform.

signal, increase the setting of  $R_1$  until the voltmeter indicates full power output. (The voltage should equal  $\sqrt{PR}$ , where  $P$  is the expected power output in watts and  $R$  is the load resistance —  $R_4$  in the diagram.) Listen carefully to the tone while increasing  $R_1$  to see if there is any change in its character. When it begins to sound like a musical octave instead of a single tone, distortion is beginning. Assuming that the output is substantially without audible distortion at full output, substitute the microphone for the audio oscillator and speak into it in a normal tone while watching the voltmeter. Reduce the gain-control setting until the meter "kicks" nearly up to the full-power reading on voice peaks. Note the hum level, as read on the voltmeter, at this point; the hum level should not exceed one or two per cent of the voltage at full output.

If the hum level is too high, the amplifier stage that is causing the trouble can be located by temporarily short-circuiting the grid of each tube, in turn, to ground. When shorting a particular grid makes a marked decrease in hum, the hum presumably is coming from a preceding stage, although it is possible that it is getting its start in that particular grid circuit. If shorting a grid does not decrease the hum, the hum is originating either in the plate circuit of that tube or the grid circuit of the next. Aside from wiring errors or a defective tube, objectionable hum usually originates in the first stage of the amplifier.

If distortion occurs below the point at which the expected power output is secured, the stage in which it is occurring can be located by working from the last stage toward the front end of the amplifier, applying a signal to each grid in turn from the audio oscillator and adjusting the signal voltage for maximum output. In the case of push-pull stages, the signal may be applied to the primary of the interstage transformer — after disconnecting it from the plate-voltage source. Assuming that normal design principles have been followed and that all stages are theoretically working within their capabilities, the probable causes of distortion are wiring errors (such as accidental short-circuit of a cathode resistor), defective components, or use of wrong values of resistance in cathode and plate circuits.

An oscilloscope having amplifiers and a linear sweep circuit is a useful instrument in testing audio amplifiers because it provides a ready check on waveform and thus shows distortion instantly. It may be connected across the output circuit as shown in Fig. 9-44, and also may be moved from stage to stage to

check the waveform at the grid as well as at the plate. When connected to circuits that are not at ground potential for d.c., a condenser (about 0.1  $\mu$ fd.) should be connected in series with the "hot" oscilloscope lead. The hot lead preferably should be shielded so that it will not pick up stray hum and introduce it into the amplifier.

## ● CLASS-B MODULATORS

Once the speech amplifier is in satisfactory working condition, a Class B modulator can be checked by similar means. A circuit is shown in Fig. 9-45. The resistance of  $R_1$  should be equal to the modulating impedance of the Class C amplifier to be modulated, and the resistor should have a power rating equal to the rated power output of the modulator. Calculate the voltage to be expected across  $R_1$  at full output; if it exceeds the range of the meter the meter may be connected across say half or one-fourth of  $R_1$  and the readings multiplied by 2 or 4, respectively. Only a few ohms will be needed at  $R_2$ , in the average case, to give a good signal in the headphones. As a safety precaution, ground the output terminal to which the headphones are connected and use a resistor at  $R_2$  that has ample current-carrying capacity.

Hum will seldom be a problem in the modulator. Distortion may be checked as described

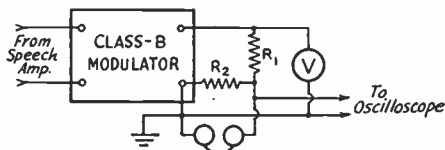


Fig. 9-45 — Set-up for checking a Class B modulator.

previously; the oscilloscope is excellent for this purpose. If a variable-frequency audio oscillator is used, a check on the frequency response of the over-all system can be obtained by varying its frequency (check its output voltage at each frequency change) and observing the variation in the modulator output voltage. The high-frequency response of the system can be attenuated by trying condensers of various values across the primary and secondary of the output transformer, as pointed out in the discussion on Class B modulators. The response above 3000 cycles should be small compared to the response in the 200- to 2500-cycle region so that the channel occupied by the transmitter will not be excessive. A simple way to check this is to apply a sine-wave signal of about 1500 cycles and increase its amplitude until distortion becomes noticeable; when this occurs the tone no longer sounds pure but sounds like a musical octave. The condenser values should then be adjusted until the tone sounds pure again at the same signal amplitude.

## Checking 'Phone-Transmitter Operation

Proper adjustment of a 'phone transmitter is aided immeasurably by the oscilloscope; it will give more information, more accurately, than almost any collection of other instruments that might be named. Furthermore, an oscilloscope that is entirely satisfactory for the purpose is not necessarily an expensive instrument; the cathode-ray tube and its power supply are about all that are needed. Amplifiers and linear sweep circuits are by no means necessary. They do, however, give a different type of pattern than is obtained without them.

When using the tube without a sweep circuit, radio-frequency voltage from the modulated amplifier is applied directly to the vertical deflection plates of the tube, and audio-frequency voltage from the modulator is applied to the horizontal deflection plates. As the amplitude of the horizontal signal varies, the r.f. output of the transmitter also varies, and this produces a wedge-shaped pattern or **trapezoid** on the screen. If the oscilloscope has a horizontal sweep, the r.f. voltage is applied to the vertical plates as before (never through an amplifier) and the sweep produces

coil. As shown in the alternative drawing, a resonant circuit tuned to the operating frequency may be connected to the vertical plates, using link coupling between it and the transmitter. This will eliminate r.f. harmonics, and the tuning control provides a means for adjustment of the pattern height.

To get a wave-envelope pattern the position of the pick-up coil should be varied until a carrier pattern, Fig. 9-47B, of suitable height is obtained. The horizontal sweep voltage should be adjusted to make the width of the pattern somewhat more than half the diameter of the screen. When voice modulation is applied, a rapidly-changing pattern of varying height will be obtained. When the maximum height of this pattern is just twice that of the carrier alone, the wave is being modulated 100 per cent. This is illustrated by Fig. 9-47D, where the point *X* represents the sweep line (reference line) alone, *YZ* is the carrier height, and *PQ* is the maximum height of the modulated wave. If the height is greater than the distance *PQ*, as illustrated in *E*, the wave is overmodulated in the upward direction. Overmodulation in the downward direction is indicated by a gap in the pattern at the reference axis, where a single bright line appears on the screen. Overmodulation in either direction may take place even when the modulation is in the other direction is less than 100 per cent.

Assuming that the modulation is symmetrical, any modulation percentage can be measured directly from the screen by measuring the maximum height with modulation and the height of the carrier alone; calling these two heights  $h_1$  and  $h_2$  respectively, the modulation percentage is

$$\frac{h_1 - h_2}{h_2} \times 100$$

Connections for the trapezoidal pattern are shown in Fig. 9-46B. The vertical plates are coupled to the transmitter tank circuit through a pick-up loop; alternatively, the tuned input circuit to the oscilloscope may be used. The horizontal plates are coupled to the output of the modulator through a voltage divider,  $R_1R_2$ .  $R_2$  should be a potentiometer so the audio voltage can be adjusted to give a satisfactory horizontal sweep on the screen.  $R_2$  may be a 0.25-megohm volume control. The value of  $R_1$  will depend upon the audio output voltage of the modulator. This voltage is equal to  $\sqrt{PR}$ , where  $P$  is the audio power output of the modulator and  $R$  is the modulating impedance of the modulated r.f. amplifier. In the case of grid-bias modulation with a 1:1 output transformer, it will be satisfactory to assume that the a.c. output voltage of the modulator is equal to  $0.7E$  for a single tube, or to  $1.4E$  for a push-pull stage, where  $E$  is the

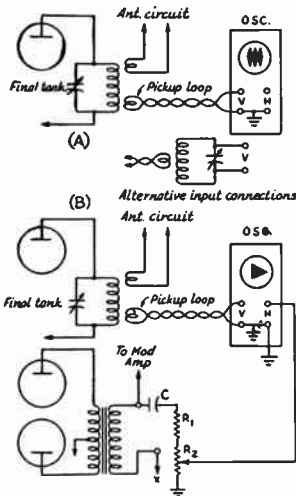


Fig. 9-46 — Methods of connecting an oscilloscope to the modulated r.f. amplifier for checking modulation.

a pattern that follows the modulation envelope of the transmitter output, provided the sweep frequency is lower than the modulation frequency. This produces a **wave-envelope** modulation pattern.

Oscilloscope connections for both types of patterns are shown in Fig. 9-46. The connections for the wave-envelope pattern are somewhat simpler than those for the trapezoidal figure. The vertical deflection plates are coupled to the amplifier tank coil (or an antenna coil) through a twisted-pair line and pick-up



d.c. plate voltage on the modulator. If the transformer ratio is other than 1:1, the voltage so calculated should be multiplied by the actual secondary-to-primary turns ratio.

The total resistance of  $R_1$  and  $R_2$  in series should be 0.25 megohm for every 150 volts of modulator output; for example, if the modulator output voltage is 600, the total resistance should be four (600/150) times 0.25 megohm, or 1 megohm. Then, with 0.25 megohm at  $R_2$ ,  $R_1$  should be 0.75 megohm. The blocking condenser,  $C$ , should be 0.1  $\mu$ fd. or more, and its voltage rating should be greater than the maximum voltage in the circuit. With plate modulation, this is twice the d.c. voltage applied to the plate of the modulated amplifier.

Trapezoidal patterns for various conditions of modulation are shown in Fig. 9-47 at F to J, each alongside the corresponding wave-envelope pattern. With no signal, only the cathode-ray spot appears on the screen. When the unmodulated carrier is applied, a vertical line appears; the length of the line should be adjusted, by means of the pick-up coil coupling, to a convenient value. When the carrier is modulated, the wedge-shaped pattern appears; the higher the modulation percentage, the wider and more pointed the wedge becomes. At 100-per-cent modulation it just makes a point on the axis,  $X$ , at one end, and the height,  $PQ$ , at the other end is equal to twice the carrier height,  $YZ$ . Overmodulation in the upward direction is indicated by increased height over  $PQ$ , and in the downward direction by an extension along the axis  $X$  at the pointed end. The modulation percentage may be found by measuring the modulated and unmodulated carrier heights, in the same way as with the wave-envelope pattern.

### Nonsymmetrical Waveforms

In voice waveforms the maximum amplitude in one direction from the axis frequently is greater than in the other direction (although the average energy on both sides is the same). For this reason the percentage of modulation in the "up" direction frequently differs from that in the "down" direction. With a given voice and microphone, this difference in modulation percentage is usually always in the same direction. Overmodulation in the downward direction causes more out-of-channel interference than overmodulation upward, because of the sharp break — generating high-order harmonics — when the carrier goes to zero.

It is therefore advisable to "phase" the modulation so that the side of the voice waveform having the larger excursions causes the instantaneous carrier power to increase — that is, modulate upward. This reduces the likelihood of overmodulation on the "down" peak. The direction of the larger excursions can readily be found by careful observation of the oscilloscope pattern. The phase can be reversed by reversing the connections of one winding of

any transformer in the speech amplifier or modulator.

### Modulation Monitoring

It is always desirable to modulate as fully as possible, but 100-per-cent modulation should not be exceeded — particularly in the downward direction — because harmonic distortion will be introduced and the channel-width in-


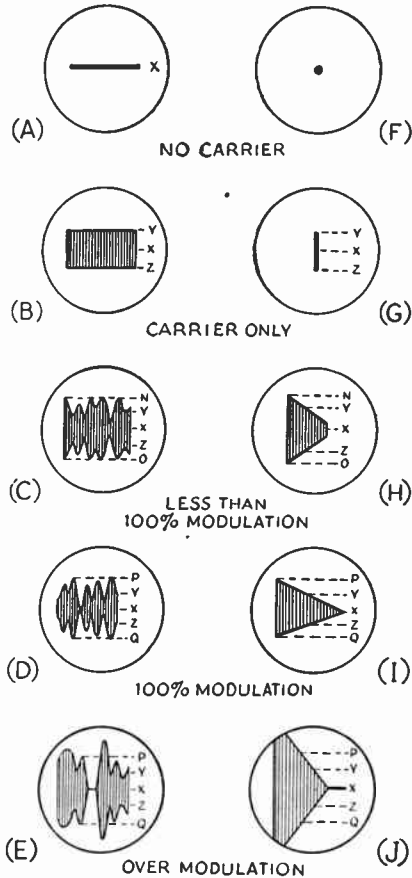



Fig. 9-47 — Wave-envelope and trapezoidal patterns representing different conditions of modulation.

creased: This causes unnecessary interference to other stations. The oscilloscope is the best instrument for continuously checking the modulation. However, simpler indicators may be used for the purpose, once calibrated.


A convenient indicator, when a Class B modulator is used, is the plate milliammeter in the Class B stage, since plate current fluctuates with the voice intensity. Using the oscilloscope, determine the gain-control setting and voice intensity that give 100-per-cent modulation on voice peaks, and simultaneously observe the maximum Class B plate-milliammeter reading on the peaks. When this maximum reading is obtained, it will suffice to adjust the gain so that it is not exceeded.

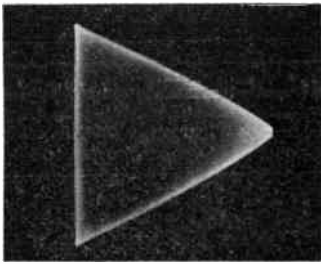

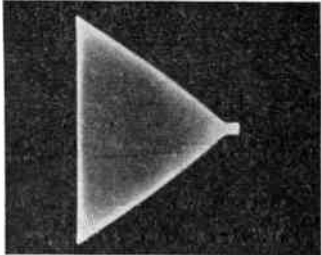
Properly-operated 'phone transmitter modulated 100 per cent.



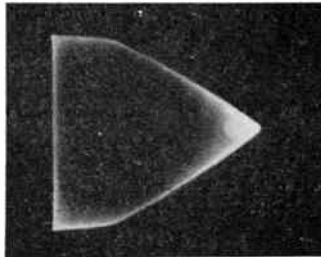
Overmodulation of a transmitter having high modulation capability. Distortion occurs only on the down-peaks.



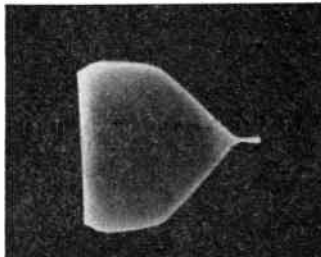
Nonlinearity in modulated r.f. stage, frequently caused by insufficient excitation of a plate-modulated amplifier or overexcitation of a grid-bias modulated amplifier. The amplifier modulates linearly in the downward direction but the up-peaks are flattened.








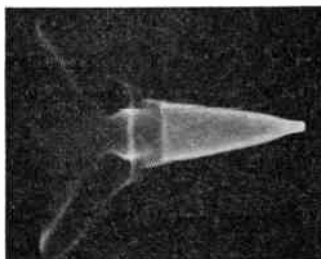
Overmodulation and non-linear operation (insufficient modulation capability). These patterns are similar to those directly above, but with the modulation carried beyond 100 per cent in the downward direction.



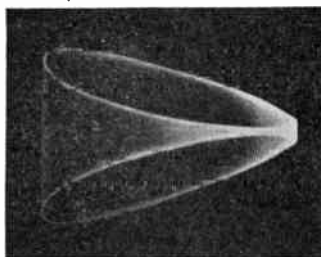Overmodulation and parasitic oscillations in the modulated amplifier. The trapezoidal pattern also shows phase distortion caused by incorrect coupling between the oscilloscope and audio system.



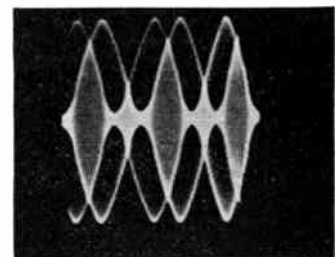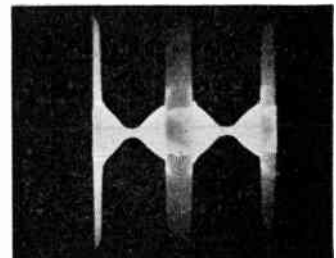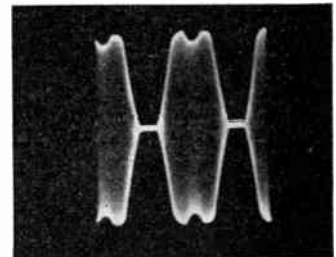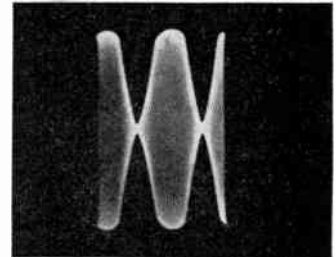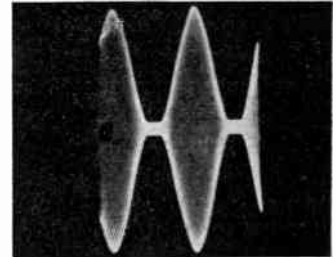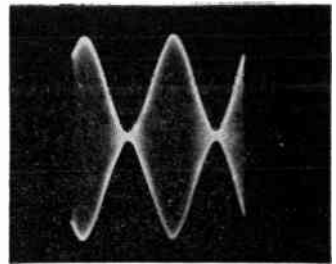Left — Phase distortion caused by incorrect coupling between audio system and oscilloscope. Right — Multiple pattern caused by incorrect setting of oscilloscope time-base control. In both cases the wave is modulated 100 per cent.



### PHOTOGRAPHS OF TYPICAL OSCILLOSCOPE PATTERNS

These photographs show various conditions of modulation as displayed by the wedge or trapezoidal patterns in the left-hand column and the wave-envelope patterns in the right-hand column.

(Photographs reproduced through courtesy of the Allen B. DuMont Laboratories, Inc., Passaic, N. J.)

A sensitive rectifier-type voltmeter (copper-oxide type) also can be used for modulation monitoring. It should be connected across the output circuit of an audio driver stage where the power level is a few watts, and similarly calibrated against the oscilloscope to determine the reading that represents 100-per-cent modulation.

The plate milliammeter of the modulated r.f. stage also is of some value as an indicator of overmodulation. The average plate current stays constant if the amplifier is linear, so the reading will be the same whether or not the transmitter is modulated. When the amplifier is overmodulated, especially in the downward direction, the operation is no longer linear and the average plate current will change. A flicker of the pointer may therefore be taken as an indication of overmodulation or non-linearity. However, it is possible that under some operating conditions the average plate current will remain constant even though the amplifier is considerably overmodulated. Therefore an indicator of this type is not wholly reliable unless it has been checked previously against an oscilloscope.

#### *Linearity*

The linearity of a modulated amplifier may readily be checked with the oscilloscope. The trapezoidal pattern is more easily interpreted than the wave-envelope pattern, and less auxiliary equipment is required. The connections are the same as for measuring modulation percentage (Fig. 9-46B). If the amplifier is perfectly linear, the sloping sides of the trapezoid will be perfectly straight from the point at the axis up to at least 100-per-cent modulation in the upward direction. Nonlinearity will be shown by curvature of the sides. Curvature near the point, causing it to approach the axis more slowly than would occur with straight sides, indicates that the output power does not decrease rapidly enough in this region; it may also be caused by imperfect neutralization (a push-pull amplifier is recommended because better neutralization is possible than with single-ended amplifiers) or by r.f. leakage from the exciter through the final stage. The latter condition can be checked by removing the plate voltage from the modulated stage, when the carrier should disappear, leaving only the beam spot remaining on the screen (Fig. 9-47F). If a small vertical line remains, the amplifier should be reneutralized; if this does not eliminate the line, it is an indication that r.f. is being picked up from lower-power stages, either by coupling through the final tank or via the oscilloscope pick-up loop.

Inward curvature at the large end of the pattern is caused by improper operating conditions of the modulated amplifier — usually improper bias or insufficient excitation, or both, with plate modulation. In grid-bias and cathode-modulated systems, the bias, excita-

tion and plate loading are not correctly proportioned when such curvature occurs. The usual reason is that the amplifier has been adjusted to have too-high carrier efficiency without modulation.

For the wave-envelope pattern, it is necessary to have a linear horizontal-sweep circuit in the oscilloscope and a source of sine-wave audio signal voltage (such as an audio oscillator or signal generator) that can be synchronized with the sweep circuit. The linearity can be judged by comparing the wave envelope with a true sine wave. Distortion in the audio circuits will affect the pattern in this case (such distortion has no effect on the trapezoidal pattern, which shows the modulation characteristic of the r.f. amplifier alone), and it is also readily possible to misjudge the shape of the modulation envelope, so that the wave envelope is less useful than the trapezoid for checking linearity of the modulated amplifier.

Fig. 9-48 shows typical patterns of both types. The cause of the distortion is indicated for grid-bias and suppressor modulation. The patterns at A, although not truly linear, are representative of properly-operated grid-bias modulation systems. Better linearity can be obtained with plate modulation of a Class C amplifier.

#### *Faulty Patterns*

The drawings of Figs. 9-47 and 9-48 show what is normally to be expected in the way of pattern shapes when the oscilloscope is used to check modulation. If the actual patterns differ considerably from those shown, it may be that the pattern is faulty rather than the transmitter. It is important that only r.f. from the modulated stage be coupled to the oscilloscope, and then only to the vertical plates. The effect of stray r.f. from other stages in the transmitter has been mentioned in the preceding paragraph. If r.f. is present also on the horizontal plates, the pattern will lean to one side instead of being upright. If the oscilloscope cannot be moved to a spot where the unwanted pick-up disappears, a small by-pass condenser (10  $\mu\text{mf.}$ ) should be connected across the horizontal plates as close to the cathode-ray tube as possible. An r.f. choke (2.5 mh. or smaller) may also be connected in series with the ungrounded horizontal plate.

"Folded" trapezoidal patterns, and patterns in which the sides of the trapezoid are elliptical instead of straight, occur when the audio sweep voltage is taken from some point in the audio system other than that where the a.f. power is applied to the modulated stage. Such patterns are caused by a phase difference between the sweep voltage and the modulating voltage. The connections should always be as shown in Fig. 9-46B.

#### *Plate-Current Shift*

As mentioned above, the d.c. plate current of a modulated amplifier will be the same with

and without modulation so long as the amplifier operation is perfectly linear and other conditions remain unchanged. This also assumes that the modulator is working within its capabilities. Because there is usually some curvature of the modulation characteristic with grid-bias modulation there is normally a slight upward change in plate current of a stage so modulated, but this occurs only at high modulation percentages and is barely detectable under the usual conditions of voice modulation.

With plate modulation, a downward shift in plate current may indicate one or more of the following:

- 1) Insufficient excitation to the modulated r.f. amplifier.
- 2) Insufficient grid bias on the modulated stage.
- 3) Wrong load resistance for the Class C r.f. amplifier.
- 4) Insufficient output capacitance in the filter of the modulated-amplifier plate supply.
- 5) Heavy overloading of the Class C r.f. amplifier tube or tubes.

Any of the following may cause an upward shift in plate current:

- 1) Overmodulation (excessive audio power, audio gain too great).
- 2) Incomplete neutralization of the modulated amplifier.
- 3) Parasitic oscillation in the modulated amplifier.

When a common plate supply is used for both a Class B (or Class AB) modulator and a modulated r.f. amplifier, the plate current of the latter may "kick" downward because of poor power-supply voltage regulation with the

varying additional load of the modulator on the supply. The same effect may occur with high-power transmitters because of poor regulation of the a.e. supply mains, even when a separate power-supply unit is used for the Class B modulator. Either condition may be detected by measuring the plate voltage applied to the modulated stage; in addition, poor line regulation also may be detected by observing if there is any downward shift in filament or line voltage.

With grid-bias modulation, any of the following may be the cause of a plate current shift greater than the normal mentioned above:

**Downward kick:** Too much r.f. excitation; insufficient operating bias; distortion in modulator or speech amplifier; too-high resistance in bias supply; insufficient output capacitance in plate-supply filter to modulated amplifier; amplifier plate circuit not loaded heavily enough; plate-circuit efficiency too high under carrier conditions.

**Upward kick:** Overmodulation (excessive audio voltage); distortion in audio system; regeneration because of incomplete neutralization; operating grid bias too high.

A downward kick in plate current will accompany an oscilloscope pattern like that of Fig. 9-48B; the pattern with an upward kick will look like Fig. 9-48A, with the shaded portion extending farther to the right and above the carrier, for the "wedge" pattern.

#### Noise and Hum on Carrier

Noise and hum may be detected by listening to the signal on a receiver, provided the receiver is far enough away from the transmitter to avoid overloading. The hum level should be low compared to the voice at 100-per-cent modulation. Hum may come either from the speech amplifier and modulator or from the r.f. section of the transmitter. Hum from the r.f. section can be detected by completely shutting off the modulator; if hum remains when this is done, the power-supply filters for one or more of the r.f. stages have insufficient smoothing. With a hum-free carrier, hum introduced by the modulator can be checked by turning on the modulator but leaving the speech amplifier off; power-supply filtering is the likely source of such hum. If carrier and modulator are both clean, connect the speech amplifier and observe the increase in hum level. If the hum disappears with the gain control at minimum, the hum is being introduced in the stage or stages preceding the gain control. The microphone also may pick up hum, a condition that can be checked by removing the microphone from the circuit but leaving the first speech-amplifier grid circuit otherwise unchanged. A good ground on the microphone and speech system usually is essential to hum-free operation.

Hum can be checked with the oscilloscope, where it has the same appearance as ordinary modulation on the carrier. While the percentage usually is rather small, if the carrier shows

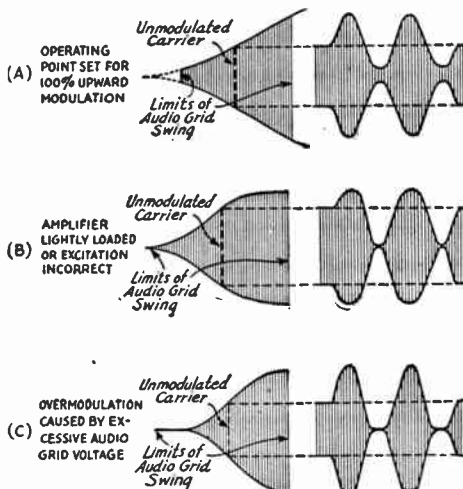


Fig. 9-48 — Oscilloscope patterns representing proper and improper adjustments for grid-bias or cathode modulation. The pattern obtained with a correctly-adjusted amplifier is shown at A. The other drawings indicate nonlinear modulation from typical causes.

modulation with no speech input hum is the likely cause. The various parts of the transmitter may be checked through as described above.

### Spurious Sidebands

A superheterodyne receiver having a crystal filter is needed for checking spurious sidebands outside the normal communication channel. The r.f. input to the receiver must be kept low enough, by removing the antenna or by adequate separation from the transmitter, to avoid overloading and consequent spurious receiver responses. With the crystal filter in its sharpest position and the beat oscillator turned on, tune through the region outside the normal channel limits (3 to 4 kilocycles each side of the carrier) while another person talks into the microphone. Spurious sidebands will be observed as intermittent beat-notes coinciding with voice peaks — or, in bad cases of distortion or overmodulation, as “clicks” or crackles well away from the carrier frequency. Sidebands more than 3 to 4 kilocycles from the carrier should be of negligible strength in a properly-modulated phone transmitter. The causes are overmodulation or nonlinear operation.

### R.F. in Speech Amplifier

A small amount of r.f. current in the speech amplifier — particularly in the first stage, which is most susceptible to such r.f. pick-up — will cause overloading and distortion in the low-level stages. Frequently also there is a regenerative effect which causes an audio-frequency oscillation or “howl” to be set up in the audio system. In such cases the gain control cannot be advanced very far before the howl builds up, even though the amplifier may be perfectly stable when the r.f. section of the transmitter is not turned on.

Complete shielding of the microphone, microphone cord, and speech amplifier is necessary to prevent r.f. pick-up, and a ground connection separate from that to which the transmitter is connected is advisable. Direct coupling or unsymmetrical coupling to the antenna (single-wire feed, feeders tapped on final tank circuit, etc.) may be responsible because these systems sometimes cause the transmitter chassis to take an r.f. potential above ground. Inductive coupling to a two-wire transmission line is advisable. This antenna effect can be checked by disconnecting the antenna and dissipating the r.f. power in a dummy antenna, when it usually will be found that the r.f. feed-back disappears. If it does not, the speech amplifier and microphone shielding are at fault.

### Overmodulation Indicators

The most positive method of preventing overmodulation is the clipper-filter system described earlier, when properly set up and adjusted. In the absence of such a system — or

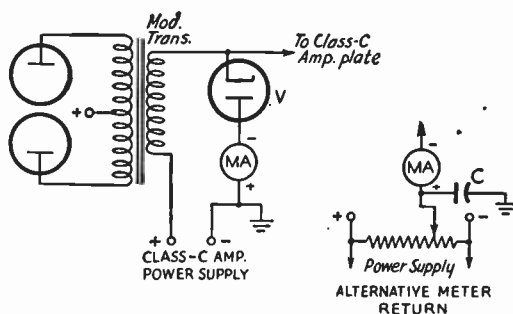


Fig. 9-49 — A negative-peak overmodulation indicator. Milliammeter MA may be any low-range instrument (up to 0-50 ma. or so). The inverse peak-voltage rating of the rectifier, V, must be at least equal to the d.c. voltage applied to the plate of the r.f. amplifier. The alternative meter-return circuit can be used to indicate modulation in excess of any desired value below 100 per cent.

even with it, just to be safe — some form of overmodulation indicator should be in constant use when the transmitter is on the air.

The best device for this purpose is the cathode-ray oscilloscope. The trapezoidal and wave-envelope patterns are equally useful. A 60-cycle sinusoidal sweep will be quite satisfactory for the wave-envelope pattern. Either pattern should be watched particularly for the bright spots at the axis that accompany overmodulation in the downward direction. The speaking-voice intensity should be kept below the level that shows 100-per-cent modulation on the 'scope.

Overmodulation on negative peaks is more likely to result in spurious sidebands than overmodulation in the upward direction because of the sharp break that occurs when the carrier is suddenly cut off and on. The milliammeter in the negative-peak indicator of Fig. 9-49 will show a reading on each overmodulation peak that carries the instantaneous voltage on the plate of the Class C modulated amplifier “below zero” — that is, negative. The rectifier, V, cannot conduct so long as the negative half-cycle of audio output voltage is less than the d.c. voltage applied to the r.f. tube. The rectifier tube must be of a type suitable for the Class C plate voltage employed, and its filament transformer must have similarly-rated insulation.

The effectiveness of the monitor is improved if it indicates at somewhat less than 100-per-cent modulation, as it will then warn of the danger of overmodulation before it actually occurs. It can be adjusted to indicate at any desired modulation percentage by making the meter return to a point on the power-supply bleeder as shown in the alternative diagram. The by-pass condenser, C, insures that the full audio voltage appears across the indicator circuit. The modulation percentage at which the system indicates is determined by the ratio of the d.c. voltage between the meter tap and the positive terminal to the total d.c. voltage.

## Frequency and Phase Modulation

The primary advantage of frequency or phase modulation over amplitude modulation comes from the fact that noise or "static," whether natural or set up by electrical machines, is fundamentally an amplitude effect. An AM detector responds to noise just as readily as to the desired modulation on a signal. However, if the receiving system responds only to frequency or phase changes and is insensitive to amplitude variations, it will give normal reception of an FM or PM signal but will not receive noise.

This statement, although an oversimplification, conveys the basic idea. In practice it is only partially accurate; the improvement that can be realized by using FM or PM instead of AM depends on the strength of the received signal, the character of the noise, and the way the noise is distributed over the receiver passband. In general, the wider the channel occupied by the signal the better the noise suppression — if the signal strength is above a certain threshold value. The wider the channel occupied by the signal, the stronger the signal required to reach the threshold. The noise suppression in the receiver is most effective when the noise is evenly distributed over the receiver passband and least so when the noise appears on one side or the other of the incoming carrier. (The noise itself usually is properly distributed, but misalignment in receiver circuits will cause uneven response over the passband.) The noise suppression also is most marked when the noise is of the "impulse" type, having a high peak amplitude but short duration.

In amateur work, FM and PM have been used not so much because of the possibility of an improved signal-to-noise ratio but because of more-or-less incidental advantages. For example, in the ultrahigh and superhigh fre-

quency ranges some tubes do not lend themselves well to amplitude modulation, but can easily be frequency-modulated. On the lower frequencies FM and PM are often used because they cause less interference than AM in unshielded broadcast receivers in the vicinity.

### Frequency Modulation

The fundamental principle of frequency modulation is easy to understand. Suppose we have an oscillator operating at a frequency of, say, 3900 kc. Further suppose that we vary the oscillator tuning control back and forth so that at one extreme the frequency is 3905 kc. and at the other, 3895 kc.; that is, plus and minus 5 kc. on either side of the carrier frequency. Imagine that the tuning is varied back and forth in that fashion at 1000 times per second. Then we are *frequency modulating* the oscillator at an audio frequency of 1000 cycles.

The *frequency deviation* is the maximum change in frequency from the carrier frequency; in this example it is 5 kc. So long as the tuning control is varied between the same two extremes, the frequency deviation is the same no matter how rapidly the control is varied; i.e., no matter what the modulating frequency. In other words, we can make the deviation any reasonable figure we want, whether it is a few hundred cycles or tens of kilocycles, and it is not affected by the modulating frequency.

Fig. 9-50 is a representation of frequency modulation. In the unmodulated carrier each cycle occupies the same time as the preceding one. When a modulating signal is applied, the carrier frequency is increased during one half-cycle of the modulating signal and decreased during the half-cycle of opposite polarity. This is indicated in the drawing by the fact that the r.f. cycles occupy less time (higher frequency) when the modulating signal is positive, and more time (lower frequency) when the modulating signal is negative. The change in the carrier frequency is proportional to the instantaneous amplitude of the modulating signal — or, to use the analogy above, to the position of the oscillator tuning control — so the frequency deviation is small when the instantaneous amplitude of the modulating signal is small, and is greatest when the modulating signal reaches its peak, either positive or negative. That is, the frequency deviation follows the changes in the amplitude of the modulating signal.

### Phase and Frequency

Phase modulation is a little more difficult. To understand the difference between FM and PM it is necessary to appreciate that the frequency of an alternating current is determined by the *rate at which its phase changes*. A current in which the phase changes rapidly has a higher

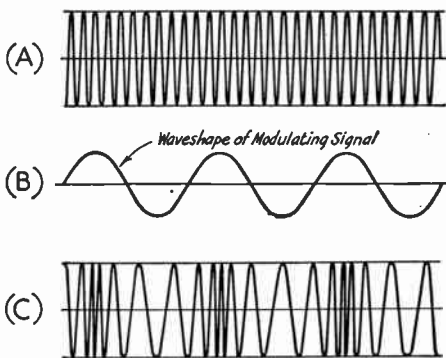


Fig. 9-50 — Graphical representation of frequency modulation. In the unmodulated carrier at A, each r.f. cycle occupies the same amount of time. When the modulating signal, B, is applied, the radio frequency is increased and decreased according to the amplitude and polarity of the modulating signal.

frequency than one in which the phase changes slowly. For example, if the phase moves through 360 degrees in one second the frequency is one cycle per second, but if the phase moves through 1080 degrees in one second ( $3 \times 360$  degrees) there are three complete cycles in one second.

If the phase moves along at a constant speed the frequency also is constant. But if the rate of phase change is speeded up or slowed down there is an accompanying shift in the frequency. If the speed is increased the frequency becomes higher; if the speed is decreased the frequency becomes lower.

Now suppose we have a transmitter operating at a fixed frequency; a frequency that is unaffected by tuning an amplifier that is a few stages removed from the frequency-controlling oscillator. We cannot change the *frequency*, but we can *shift the phase* of the r.f. current by adjusting the tuning control of the amplifier. We might, for example, shift the phase of the current in that circuit 10 degrees by detuning the tank circuit from resonance. Once the detuning is finished the phase shift is permanent, but there is still just exactly the same number of cycles per second as before — so the frequency is exactly the same as it was in the first place. *But during the time that the phase shift is taking place there is a change in frequency.* If the phase is advanced (moved forward) the frequency increases; if it is retarded (slowed down) the frequency decreases.

This “instantaneous” frequency change would never be noticed in tuning an amplifier tank circuit, because the frequency deviation depends on the *speed* with which the phase is shifted. Any manual adjustment would be too slow to make an observable frequency change. But when the phase is shifted back and forth at an audio-frequency rate the frequency deviation is observable, and it is directly proportional to the rate at which the phase is shifted. The rate of phase shift is naturally proportional to the total number of degrees through which the phase is shifted; it is also proportional to the amplitude of the modulating signal (a large signal will shift the phase more, in the same time, than a small signal), and to the frequency of the modulating signal because the phase shift is more rapid the greater the number of times it is shifted per second.

To summarize, then, in FM the carrier frequency deviation is proportional to the amplitude of the modulating signal but not to its frequency. In PM the deviation is proportional to *both* the amplitude and frequency of the modulating signal. Fig. 9-50 is just as representative of PM as it is of FM, because it is impossible to tell the two apart when there is only one modulating frequency.

### Modulation Depth

In FM or PM there is no condition that corresponds exactly to overmodulation in AM. “Percentage of modulation” has to be defined

a little differently for these systems. Practically, “100-per-cent modulation” is reached when the transmitted signal occupies a channel just equal to the bandwidth for which the receiver is designed. If the channel occupied is wider than the receiver can accept, the receiver distorts the signal and the end effect is much the same as overmodulation in AM. However, on another receiver designed for a different bandwidth the same signal might be equivalent to only 25-per-cent modulation. Until the maximum width is set for the channel, percentage of modulation has no meaning.

In amateur work no specifications have been set up for channel-width except in the case of “narrow-band” FM or PM (frequently abbreviated NFM), where the channel-width is defined as being the same as that of a properly-modulated AM signal. That is, the channel-width for NFM does not exceed twice the highest audio frequency in the modulating signal. NFM transmissions based on an upper audio limit of 3000 cycles therefore should occupy a channel no wider than 6 kc.

### FM and PM Sidebands

From the descriptions given above of the fundamentals of frequency and phase modulation it might be concluded that the channel occupied by the transmission would be no greater than the frequency deviation on each side of the carrier. However, if we applied the same line of reasoning to amplitude modulation we should reach the conclusion that an AM signal takes up no more space than the carrier alone, since only the *amplitude* of the carrier varies. Both conclusions would be wrong; the fact is that both FM and PM set up sidebands, just as AM does. In the case of FM and PM, single-tone modulation sets up a whole series of pairs of sidebands that are harmonically related to the modulating frequency, whereas in AM there is only one pair of sidebands.

The number of “extra” sidebands that occur in FM and PM depends on the relationship between the modulating frequency and the carrier frequency deviation. The ratio between the frequency deviation, in cycles per second, and the modulating frequency, also in cycles per second, is called the **modulation index**. That is,

$$\text{Modulation index} = \frac{\text{Carrier frequency deviation}}{\text{Modulating frequency}}$$

Example: The maximum frequency deviation in an FM transmitter is 3000 cycles either side of the carrier frequency. The modulation index when the modulating frequency is 1000 cycles is

$$\text{Modulation index} = \frac{3000}{1000} = 3$$

At the same deviation with 3000-cycle modulation the index would be 1; at 100 cycles it would be 30, and so on.

The modulation index is also equal to the phase shift (in radians). In PM the index is constant regardless of the modulating fre-

quency; in FM it varies with the modulating frequency, as shown in the previous example. To identify any particular FM system, the limiting modulation index — that is, the ratio of the *maximum* carrier-frequency deviation to the *highest* modulating frequency used — is called the deviation ratio.

Fig. 9-51 shows how the amplitudes of the carrier and the various sidebands vary with the modulation index. This is for single-tone modulation; the first sideband (actually a pair, one above and one below the carrier) is displaced from the carrier by an amount equal to the modulating frequency, the second is twice the modulating frequency away from the carrier, and so on. For example, if the modulating frequency is 2000 cycles and the carrier frequency is 29,500 kc., the first sideband pair is at 29,498 kc. and 29,502 kc., the second pair

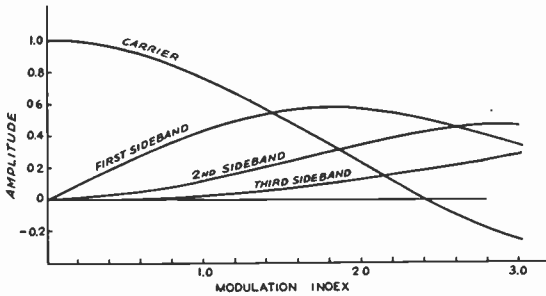


Fig. 9-51 — How the amplitude of the pairs of sidebands varies with the modulation index in an FM or PM signal. If the curves were extended for greater values of modulation index it would be seen that the carrier amplitude goes through zero at several points. The same statement also applies to the sidebands.

is at 29,496 kc. and 29,504 kc., the third at 29,494 kc. and 29,506 kc., etc. The amplitudes of these sidebands depend on the modulation index, not on the frequency deviation. In AM, regardless of the percentage of modulation (so long as it does not exceed 100 per cent) the sidebands would appear *only* at 29,498 and 29,502 kc. under the same conditions.

Note that, as shown by Fig. 9-51, the carrier strength varies with the modulation index. (In amplitude modulation the carrier strength is constant; only the sideband amplitude varies.) At a modulation index of approximately 2.4 the carrier disappears entirely and then becomes "negative" at a higher index. This simply means that its phase is reversed as compared to the phase without modulation. In FM and PM the energy that goes into the sidebands is taken from the carrier, the *total* power remaining the same regardless of the modulation index. In AM the sideband power is supplied by the modulator in the case of plate modulation, and by changing the power input and efficiency in the case of grid-bias modulation.

Fig. 9-51 can be carried out to considerably-higher modulation indexes, in which case it will

be found that more and more additional sidebands are set up and that the carrier goes through several "zeros" and reversals in phase.

### Frequency Multiplication

In amplitude modulation it is customary amateur practice to apply the modulation to the final r.f. stage of the transmitter. If a lower-level stage is modulated, a special type of operation is necessary in the following r.f. stages to pass the modulation envelope without distortion. These "linear" amplifiers are rather difficult to adjust properly and must be operated at low plate efficiency. Consequently, the simplest and most economical transmitter design results when the final stage is modulated.

In frequency or phase modulation there is no change in the amplitude of the signal with modulation. Consequently, an FM or PM signal can be amplified by an ordinary Class C amplifier without distortion. The modulation can take place in a very low-level stage and the signal can then be amplified by either frequency multipliers or straight amplifiers. In fact, this is the usual practice. The audio power required for modulating an FM or PM transmitter is negligible.

If the modulated signal is passed through one or more frequency multipliers, the modulation index is multiplied by the same factor that the carrier frequency is multiplied. For example, suppose that the controlling oscillator in the transmitter is on 3.5 Mc. and the final output is on 28 Mc. The total frequency multiplication is 8 times, and any FM or PM applied to the oscillator will likewise be multiplied by 8 in the 28-Mc. output. If the frequency deviation is 500 cycles at 3.5 Mc., it will be 4000 cycles at 28 Mc.

Frequency multiplication offers a means for obtaining practically any desired amount of frequency deviation, whether or not the modulator itself is capable of giving that much deviation without distortion. Also, if the same oscillator is modulated in a transmitter that operates on several bands, the frequency deviation is different on each band. The amount of frequency multiplication after modulation always must be taken into account in determining whether or not the final frequency deviation is the desired value on a given band.

### ● NARROW-BAND FM OR PM

Where FM or PM is used in crowded 'phone bands (particularly below 27 Mc.) it is of utmost importance that the transmissions should occupy no greater channel-width than would be occupied by an AM signal. It is evident from Fig. 9-51 that this requirement can be met only by using a relatively small modulation index. It must be realized that the higher-



order sidebands always are present, even at very small indexes. It is therefore necessary to set an arbitrary level above which the extra sidebands should not go. If the modulation index (with single-tone modulation) does not exceed about 0.6 the most important extra sideband, the second, will be at least 20 db. below the unmodulated carrier level, and this should represent an effective channel-width about equivalent to that of an AM signal. In the case of speech, a somewhat higher modulation index can be used. This is because the energy distribution in a complex wave is such that the modulation index for any one frequency component is reduced, as compared to the index with a sine wave having the same peak amplitude as the voice wave.

The chief advantage of narrow-band FM or PM for frequencies below 30 Mc. is that it eliminates or reduces certain types of interference

to broadcast reception. Also, the modulating equipment is relatively simple and inexpensive. However, assuming the same unmodulated carrier power in all cases, narrow-band FM or PM is not as effective as AM. As shown by Fig. 9-51, at an index of 0.6 the amplitude of the first sideband is about 25 per cent of the unmodulated-carrier amplitude; this compares with a sideband amplitude of 50 per cent in the case of a 100-per-cent modulated AM transmitter. In other words, so far as effectiveness is concerned a narrow-band FM or PM transmitter is about equivalent to a 100-per-cent modulated AM transmitter operating at one-fourth the power input. This assumes that the receiving system is equally efficient in all cases. This very often is not true on the low-frequency bands, since communications receivers are designed primarily for AM reception.

## Methods of Frequency and Phase Modulation

### ● FREQUENCY MODULATION

The simplest and most satisfactory device for amateur FM is the reactance modulator. This is a vacuum tube connected to the r.f. tank circuit of an oscillator in such a way as to act as a variable inductance or capacitance. Fig. 9-52 is a representative circuit. The control-grid circuit of the 6L7 tube is connected across the small capacitance,  $C_1$ , which is in series with the resistor,  $R_1$ , across the oscillator tank circuit. Any type of oscillator circuit may be used. The resistance of  $R_1$  is made large compared to the reactance of  $C_1$ , so the r.f. current through  $R_1C_1$  will be practically in phase with the r.f. voltage appearing at the terminals of the tank circuit. However, the voltage across  $C_1$  will lag the current by 90 degrees. The r.f. current in the plate circuit of the 6L7 will be in phase with the grid voltage, and consequently is 90 degrees behind the current through  $C_1$ , or 90 degrees behind the r.f. tank voltage. This lagging current is drawn through the oscillator tank, giving the same effect as though an inductance were connected across the tank. The frequency increases in proportion to the amplitude of the lagging plate current of the modulator. The value of plate current is determined by the voltage on the No. 3 grid of the 6L7; hence the oscillator frequency will vary when an audio signal voltage is applied to the No. 3 grid.

If, on the other hand,  $C_1$  and  $R_1$  are interchanged and the reactance of  $C_1$  is made large compared to the resistance of  $R_1$ , the r.f. current in the 6L7 plate circuit will lead the oscillator-tank r.f. voltage, making the reactance capacitive rather than inductive.

A circuit using a receiving-type r.f. pentode of the high-transconductance type, such as the 6SG7, is shown in Fig. 9-53. In this case, both r.f. and audio are applied to the control grid. The audio voltage, introduced through a radio-frequency choke,  $RFC$ , varies the transconductance of the tube and thereby varies the r.f. plate current. The capacitance  $C_8$  corresponds to  $C_1$  in Fig. 9-52; it represents the input capacitance of the tube. (It is possible, also, to omit  $C_1$  from Fig. 9-52 and depend upon the input capacitance of the 6L7 instead; the only disadvantage is that there is then no control over the modulator sensitivity. Likewise, a 3-30- $\mu$ fd. trimmer condenser can be connected at  $C_8$  in Fig. 9-53 to permit controlling the sensitivity.) In Fig. 9-53 the r.f. circuit is

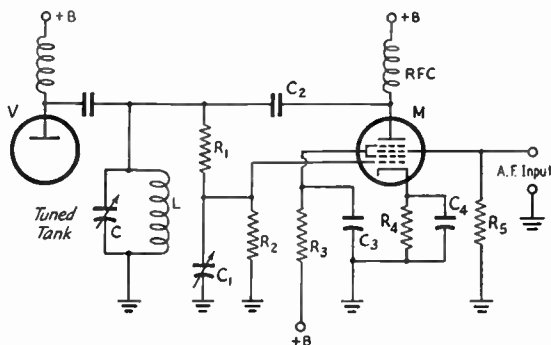


Fig. 9-52 — Reactance-modulator circuit using a 6L7 tube.  
 C — R.f. tank capacitance.  $C_1$  — 3-30  $\mu$ fd.  $C_2$  — 220  $\mu$ fd.  
 $C_3$  — 8- $\mu$ fd. electrolytic (a.f. by-pass) in parallel with 0.01- $\mu$ fd. paper (r.f. by-pass).  
 $C_4$  — 10- $\mu$ fd. electrolytic in parallel with 0.01- $\mu$ fd. paper.  
 L — R.f. tank inductance.  $R_2, R_5$  — 0.47 megohm.  
 $R_1$  — 47,000 ohms.  $R_4$  — 330 ohms.  
 $R_3$  — 33,000 ohms. RFC — 2.5 mh.

series-fed, which is advantageous if the r.f. tube and the modulator can be operated at the same plate voltage. The use of different plate voltages on the two tubes calls for the parallel-feed arrangement shown in Fig. 9-52.

The modulated oscillator usually is operated on a relatively low frequency, so that a high order of carrier stability can be secured. Frequency multipliers are used to raise the frequency to the final frequency desired. The frequency deviation increases with the number of times the initial frequency is multiplied; for instance, if the oscillator is operated on 6.5 Mc. and the output frequency is to be 52 Mc., an oscillator frequency deviation of 1000 cycles will be raised to 8000 cycles at the output frequency.

A reactance modulator can be connected to a crystal oscillator as well as to the self-controlled type. However, the resulting signal is more phase-modulated than it is frequency-modulated, for the reason that the frequency deviation that can be secured by varying the tuning of a crystal oscillator is quite small.

#### Design Considerations

The sensitivity of the modulator (frequency change per unit change in grid voltage) depends on the transconductance of the modulator tube. It increases when  $C_1$  is made smaller, for a fixed value of  $R_1$ , and also increases with an increase in  $L/C$  ratio in the oscillator tank circuit. Since the carrier stability of the oscillator depends on the  $L/C$  ratio, it is desirable to use the highest tank capacitance that will permit the desired deviation to be secured while keeping within the limits of linear operation. When the circuit of Fig. 9-53 is used in connection with a 7-Mc. oscillator, a linear deviation of 1500 cycles above and below the carrier frequency can be secured when the oscillator tank capacitance is approximately 200  $\mu\mu\text{fd}$ . A peak a.f. input of two volts is required for full deviation.

A change in *any* of the voltages on the modulator tube will cause a change in r.f. plate current, and consequently a frequency change. Therefore it is advisable to use a regulated plate power supply for both modulator and oscillator. At the low voltages used (250 volts), the required stabilization can be secured by means of gaseous regulator tubes.

#### Speech Amplification

The speech amplifier preceding the modulator follows ordinary design, except that no power is required from it and the a.f. voltage taken by the modulator grid usually is small — not more than 10 or 15 volts, even with large modulator tubes. Because of these modest requirements, only a few speech-amplifier stages are needed; a two-stage amplifier consisting of a pentode followed by a triode, both resistance-coupled, will more than suffice for crystal microphones.

### ● PHASE MODULATION

The same type of reactance-tube circuit that is used to vary the tuning of the oscillator tank in FM can be used to vary the tuning of an amplifier tank and thus vary the phase of the tank current for PM. Hence the modulator circuits of Figs. 9-52 and 9-53 can be used for PM if the reactance tube works on an amplifier tank instead of directly on a self-controlled oscillator.

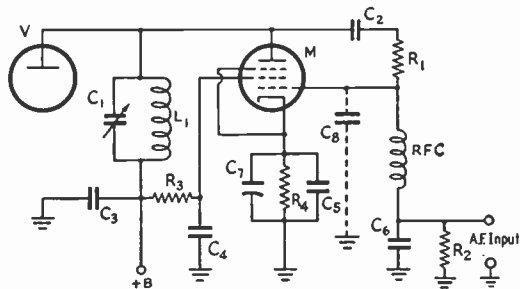


Fig. 9-53 — Reactance modulator using a high-transconductance pentode (6SG7, 6AG7, etc.).

$C_1$  — R.f. tank capacitance (see text).

$C_2, C_3$  — 0.001- $\mu\text{fd}$ . mica.

$C_4, C_5, C_6$  — 0.0047- $\mu\text{fd}$ . mica.

$C_7$  — 10- $\mu\text{fd}$ . electrolytic.

$C_8$  — Tube input capacitance (see text).

$R_1, R_2$  — 0.47 megohm.

$R_3$  — Screen dropping resistor; select to give proper screen voltage on type of modulator tube used.

$R_4$  — Cathode bias resistor; select as in case of  $R_3$ .

$L_1$  — R.f. tank inductance.

RFC — 2.5-mh. r.f. choke.

The phase shift that occurs when a circuit is detuned from resonance depends on the amount of detuning and the  $Q$  of the circuit. The higher the  $Q$ , the smaller the amount of detuning needed to secure a given number of degrees of phase shift. If the  $Q$  is at least 10, the relationship between phase shift and detuning (in kilocycles either side of the resonant frequency) will be substantially linear over a range of about 25 degrees. From the standpoint of modulator sensitivity, the  $Q$  of the tuned circuit on which the modulator operates should be as high as possible. On the other hand, the effective  $Q$  of the circuit will not be very high if the amplifier is delivering power to a load, since the load resistance reduces the  $Q$ . There must therefore be a compromise between modulator sensitivity and r.f. power output from the modulated amplifier. An optimum figure for  $Q$  appears to be about 20; this allows reasonable loading of the modulated amplifier and the necessary tuning variation can be secured from a reactance modulator without difficulty.

It is advisable to modulate at a very low power level — preferably in a transmitter stage where receiving-type tubes are used. A practical phase-modulator unit is described later in this chapter.

## A Frequency-Control and FM-Modulator Unit

The accompanying photographs show a complete VFO/reactance-modulator unit designed to work into a normally crystal-controlled transmitter using either 7- or 14-Mc. crystals. It has its own power supply, using a small "broadcast-replacement" power transformer. The VFO uses a 6SJ7 as the oscillator tube, and is followed by a 6SJ7 buffer that may be used as a straight amplifier for 7-Mc. output, or as a frequency doubler for 14-Mc. output. The reactance modulator is a 6L7. There are two stages of speech amplification, a 6SJ7 followed by a 6C5, a combination that provides ample gain for a crystal microphone. The r.f. output of the unit is intended to be fed through a link to a tuned circuit that substitutes for the crystal in the transmitter's regular crystal-oscillator circuit. This tuned circuit should be resonant at the same frequency as the output tank circuit in the control unit ( $L_2C_3$  in Fig. 9-54) and can be identical in construction.

The constants of the oscillator tank circuit are chosen so that the frequency range 6000-7425 kc. can be covered. In the transmitter, the

output can be multiplied in frequency to the 14-, 28-, 50- and 144-Mc. bands when the 6SJ7 oscillator is set to the appropriate frequency.

The sensitivity of the modulator is controlled by the setting of  $C_{11}$ . The higher the capacitance of this condenser the smaller the frequency deviation for a given audio input voltage to the modulator. At maximum sensitivity, with  $C_{11}$  at minimum capacitance, the linear deviation is approximately 1.5 kc.; this deviation requires a signal of 2 volts peak at the No. 3 grid of the 6L7. The actual deviation at the output frequency depends on the amount of frequency multiplication following the oscillator. The maximum linear deviation is 3 kc. at 14 Mc., 6 kc. at 28 Mc., 12 kc. at 50 Mc., and 36 kc. at 144 Mc. The unit is therefore suitable for narrow-band frequency modulation on 14 and 28 Mc., and for wide-band FM on 50 and 144 Mc. For narrow-band FM the speech-amplifier gain should be set so that the deviation does not exceed about 2 kc. at the output frequency.


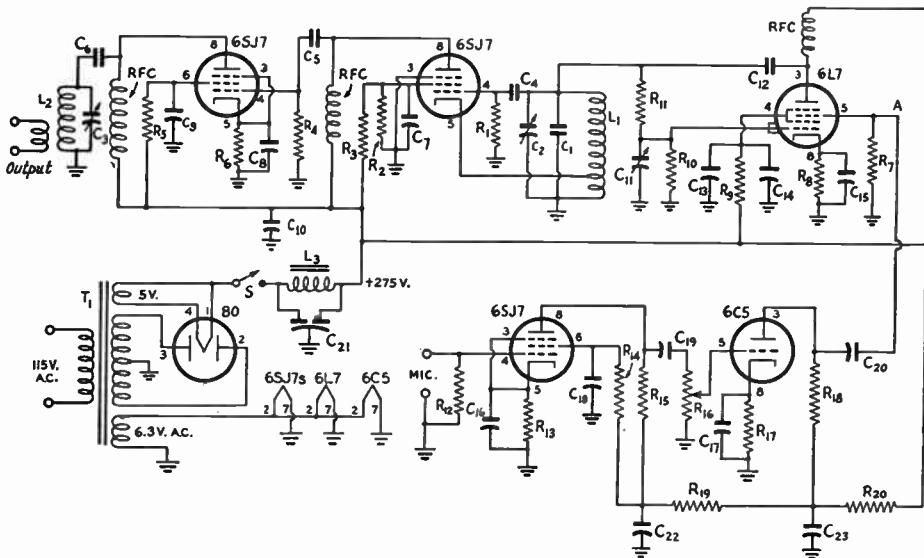


Fig. 9-54 — Circuit diagram of the FM control unit for use with normally crystal-controlled v.h.f. transmitters.

- $C_1$  — 150- $\mu$ fd. silvered mica (for 7 Mc.)
- $C_2$  — 100- $\mu$ fd. variable (National SE-100).
- $C_3$  — 50- $\mu$ fd. variable (Hammarlund HF-50).
- $C_4$  — 100- $\mu$ fd. mica.
- $C_5, C_{12}$  — 220- $\mu$ fd. mica.
- $C_6$  — 0.001- $\mu$ fd. mica.
- $C_7, C_8, C_9, C_{10}, C_{13}, C_{15}, C_{19}, C_{20}$  — 0.01- $\mu$ fd. paper.
- $C_{11}$  — 3-30- $\mu$ fd. mica trimmer.
- $C_{14}, C_{22}, C_{23}$  — 8- $\mu$ fd. 450-volt electrolytic.
- $C_{16}, C_{17}$  — 10- $\mu$ fd. 25-volt electrolytic.
- $C_{18}$  — 0.1- $\mu$ fd. 200-volt paper.

- $C_{21}$  — Dual 450-volt 8- $\mu$ fd. electrolytic.
- $R_1$  — 0.1 megohm, 1 watt.
- $R_2$  — 22,000 ohms, 1 watt.
- $R_3, R_4, R_5, R_{11}$  — 47,000 ohms, 1 watt.
- $R_6, R_8$  — 330 ohms,  $\frac{1}{2}$  watt.
- $R_7, R_{10}$  — 0.47 megohm,  $\frac{1}{2}$  watt.
- $R_9$  — 33,000 ohms, 1 watt.
- $R_{12}$  — 4.7 megohms,  $\frac{1}{2}$  watt.
- $R_{13}$  — 1000 ohms,  $\frac{1}{2}$  watt.
- $R_{14}$  — 1 megohm,  $\frac{1}{2}$  watt.
- $R_{15}, R_{19}$  — 0.22 megohm,  $\frac{1}{2}$  watt.
- $R_{16}$  — 0.5-megohm volume control.
- $R_{17}$  — 2200 ohms,  $\frac{1}{2}$  watt.
- $R_{18}$  — 47,000 ohms,  $\frac{1}{2}$  watt.
- $R_{20}$  — 0.15 megohm, 1 watt.

- $L_1$  — 7 Mc.: 11 turns No. 18 e., length  $\frac{3}{4}$  inch, 1-inch diameter, tapped 3rd turn from ground.
- $L_2$  — 3.5 Mc.: see text; 7 Mc.: 23 t. No. 24 e. close-wound on 1-inch diam. form; 14 Mc.: 11 t. No. 24 e. spaced wire diam. on 1-inch diam. form. Link: 3 to 5 turns (not critical).
- $L_3$  — Filter choke, 10 hy., 40 ma.
- RFC — 2.5-mh. r.f. choke.
- S — S.p.s.t. toggle switch.
- $T_1$  — 500 volts c.t., 40 ma.; 6.3 volts at 2 amp.; 5 volts at 2 amp. (Thordarson T-13R11).

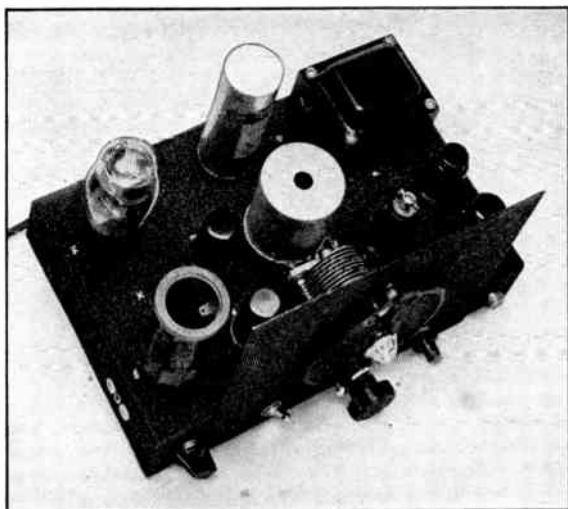

◆

*Fig. 9-55* — This modulator-oscillator unit is used with normally crystal-controlled v.h.f. transmitters for frequency-modulated output. It contains a speech amplifier and power supply, so that no additional equipment is needed. The oscillator coil is in the round shield can in the center. The coil in the left foreground is the buffer output circuit. The speech amplifier and modulator are at the right, with the power supply along the rear. A 7 × 11-inch chassis is used.

◆

In the top view of the unit, the 6SJ7 oscillator tube is alongside the aluminum shield that covers the oscillator coil. The 6SJ7 r.f. amplifier is between the oscillator tuning condenser (at the center) and its output coil at the left. The tubes along the right-hand edge of the chassis are the 6SJ7 and 6C5 speech amplifiers, with the former in front. The 6L7 modulator is between the speech-amplifier tubes and the oscillator tuned circuit. The r.f. leads in the oscillator circuit, including the connections to  $R_{11}$ ,  $C_{11}$ , and the No. 1 grid of the 6L7, should be kept short and rigid. The usual precautions as to wiring in r.f. and audio circuits should be observed.

For narrow-band FM in the portion of the 3.5-Mc. band in which such operation is permitted, it is advisable to operate the oscillator at half the desired frequency and use the r.f. output stage as a doubler to 3.5 Mc. For this purpose it is suggested that a 470- $\mu$ fd. silvered

mica condenser be substituted at  $C_1$ , and that  $L_1$  consist of 29 turns of No. 20 enameled wire close-wound on a 1-inch diameter form. The oscillator cathode tap should be at the 9th turn from ground. The r.f. output coil,  $L_2$ , should have 46 turns of No. 24 enameled wire close-wound on a 1-inch diameter form. The frequency range of the oscillator will be sufficient to cover the frequencies assigned for 'phone.


Somewhat more r.f. output can be obtained by substituting a 6AC7 for the 6SJ7 output amplifier. This substitution should be necessary only if the 6SJ7 is incapable of driving the crystal-oscillator tube in the transmitter. The considerations involved in coupling a VFO to various types of crystal-oscillator circuits are discussed in Chapter Six.

Before putting the unit on the air the carrier frequency stability and frequency deviation should be checked by the methods outlined later.

◆

*Fig. 9-56* — In this bottom view of the FM modulator unit, the r.f. section is at the right and the audio at the left. The oscillator socket is to the right of the coil socket in the center.

◆

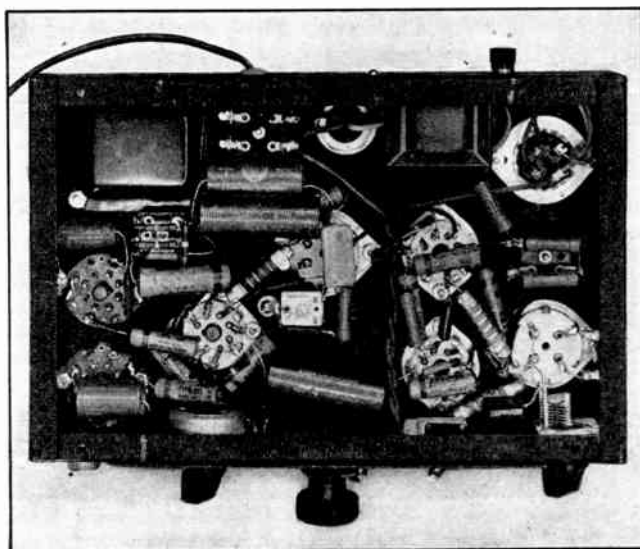

## A Narrow-Band PM Exciter Unit

The unit shown in Figs. 9-57, 9-58 and 9-59 will deliver from 10 to 20 watts of phase-modulated output, depending upon the plate voltage used, and it can be used to replace the crystal oscillator of that power level in any existing transmitter. It can also be used with an existing VFO to obtain a phase-modulated signal. A low-pass filter is incorporated to limit the modulation frequencies to those below 3000 cycles, thus making it easier to comply with the regulations on narrow-band FM and PM.

As can be seen in the wiring diagram, Fig. 9-57, a 6J5 Pierce-type oscillator circuit is used to excite a 6SK7 r.f. amplifier. If VFO control is used, the 6J5 can be removed from its socket and the VFO output introduced at  $J_1$ . To accommodate various output levels from the VFO, a gain control,  $R_3$ , is included in the cathode circuit of the 6SK7 amplifier. The plate circuit of the 6SK7 amplifier is reactance-modulated (to give the PM signal) by a 6SG7 reactance modulator, and the output of the 6SK7 drives a 2E26 r.f. amplifier. With 500 volts on the

plate of the 2E26, 15 watts output can be obtained, and the plate voltage can be raised to 600 if more output is required. The microphone input at  $J_4$  is amplified through a 6SJ7 and a 6J5, and the low-pass filter is connected between the 6J5 and the 6SK7 modulator tube. The degree of modulation is controlled by the setting of  $R_{16}$ , the audio gain control.

### Construction

The unit is built on a 7 × 12 × 3-inch chassis, and the location of the components can be seen from Figs. 9-58 and 9-59. A shield can (Millen 80016) is used over  $L_1$ , to avoid regeneration, and a small shield extends up 1 inch around the 2E26 for the same reason. No special care is necessary in wiring the unit, except that  $C_5$  or  $C_6$  should be mounted across the 6SK7 socket, to shield the grid pin from the plate pin, and the audio-circuit wiring should be kept away from the r.f. circuits. The r.f. input and output, from  $J_1$  and  $J_3$ , is most conveniently run in short pieces of RG-58/U

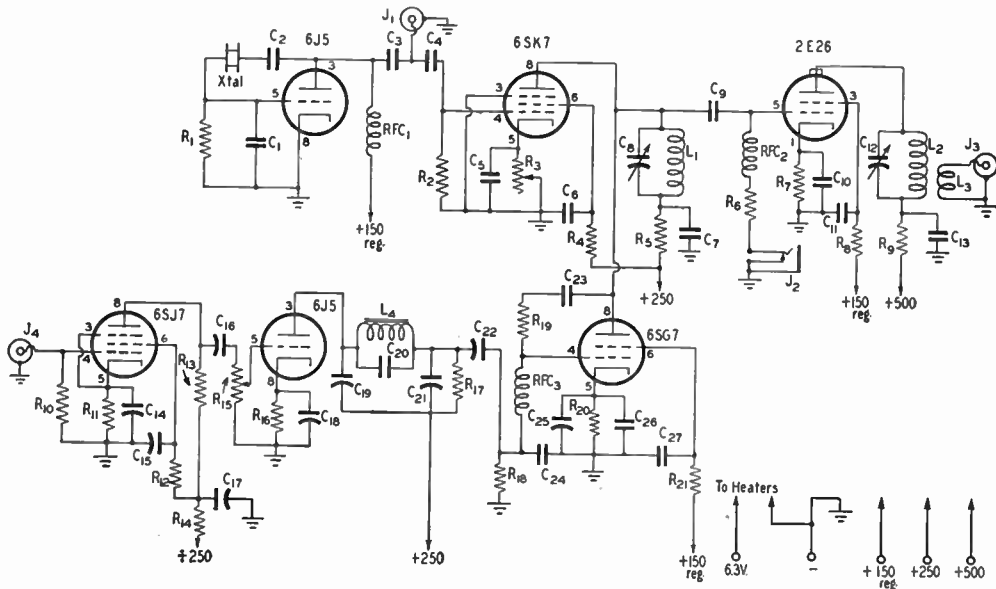


Fig. 9-57 — Wiring diagram of the narrow-band phase-modulation unit.

- $C_1$  — 22- $\mu$ fd. mica.
- $C_2, C_5, C_6, C_7, C_{10}, C_{11}, C_{13}, C_{23}, C_{24}, C_{26}, C_{27}$  — 0.001- $\mu$ fd. mica.
- $C_3, C_4, C_9$  — 100- $\mu$ fd. mica.
- $C_8$  — 50- $\mu$ fd. midget variable (Millen 21050).
- $C_{12}$  — 50- $\mu$ fd. variable (Millen 22050).
- $C_{14}, C_{18}, C_{25}$  — 10- $\mu$ fd. electrolytic, 25 volts.
- $C_{15}$  — 0.1- $\mu$ fd. paper, 200 volts.
- $C_{16}$  — 0.05- $\mu$ fd. 400-volt paper.
- $C_{17}$  — 8- $\mu$ fd. electrolytic, 450 volts.
- $C_{19}, C_{21}, C_{22}$  — 0.01- $\mu$ fd. 400-volt paper.
- $C_{20}$  — 0.006- $\mu$ fd. 200-volt paper.
- $R_1, R_2, R_4, R_{14}$  — 47,000 ohms.
- $R_3$  — 5000-ohm potentiometer, wire-wound.
- $R_5, R_8, R_{21}$  — 470 ohms.
- $R_6$  — 12,000 ohms.
- $R_7$  — 330 ohms, 1 watt.
- $R_9$  — 100 ohms.

- $R_{10}, R_{12}$  — 1.0 megohm.
- $R_{11}$  — 820 ohms.
- $R_{13}$  — 0.22 megohm.
- $R_{15}$  — 0.25-megohm volume control.
- $R_{16}$  — 1000 ohms.
- $R_{17}$  — 3900 ohms.
- $R_{18}$  — 0.1 megohm.
- $R_{19}$  — 22,000 ohms.
- $R_{20}$  — 220 ohms.

- Resistors  $\frac{1}{2}$  watt unless otherwise specified.
- $L_1, L_2$  — 3.5 Mc.: 40 turns No. 26 e., 1" d., close-wound.
- $L_3$  — 9 turns No. 22 enam., close-wound next to cold end of  $L_2$ .
- $L_4$  — 0.25 henry (Millen 34400-250).
- $J_1, J_3$  — Cable connector (Jones S-201).
- $J_2$  — Closed-circuit midget jack.
- $J_4$  — Microphone-cable connector (Amphenol PC1M).
- $RFC_1, RFC_2$  — 2.5 mh.

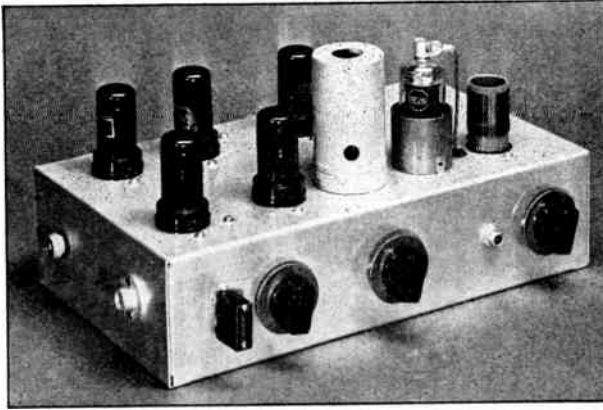



Fig. 9-58 — The narrow-band PM exciter is built in simple style. The r.f. stages are mounted along the front, and from left to right the tubes are 6J5, 6SK7 and 2E26. Note the shield can for the 6SK7 plate coil. The tubes at the rear, from left to right, are 6SJ7, 6J5 and 6SG7.

cable, but no other shielding should be necessary. The excitation control,  $R_3$ , was made to be adjusted by a screwdriver, since ordinarily there is little need for changing the setting once it has been established.

The power-supply requirements are 500

to warm up and apply plate power. If the crystal oscillator is being used, the circuit will work without adjustment and, with  $R_3$  set at minimum resistance, a meter plugged in at  $J_2$  should read 3 or 4 ma. when  $C_3$  is tuned to resonate the 6SK7 plate circuit. With VFO input, the excitation may be more than this. The 2E26 plate circuit can be tuned using a milliammeter in the 500-volt lead or by reading grid current on the following stage. When the two r.f. circuits have been resonated, the gain of the 6SK7 stage should be reduced, by increasing the resistance at  $R_3$  until the grid current is be-

Fig. 9-59 — The r.f. and audio wiring of the PM exciter are kept separated as much as possible. To carry out this scheme, the audio gain control is mounted on a small bracket, and a long shaft is brought out to the panel.

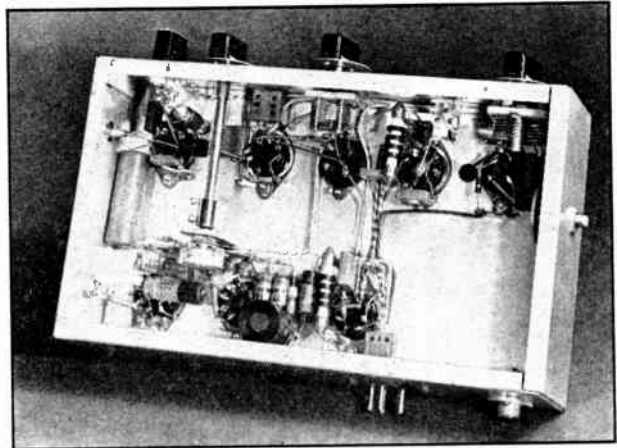

volts at 60 ma. (or whatever is required for input to the 2E26 plate), 250 volts at 25 ma., 150 volts regulated (by a VR-150) at about 12 ma., and 6.3 volts a.c. at 2.3 amperes. If the 150-volt supply is not regulated,  $C_{27}$  should be shunted with an 8- $\mu$ fd. electrolytic condenser, to avoid audio degeneration.

#### Tuning

To set the unit in operation after the power supply has been connected, allow the heaters

tween 2.5 and 3 ma. Monitoring the signal in a receiver (at reduced gain and with no antenna connected), the proper setting of  $R_{16}$  for the microphone in use can be found. The audio gain control,  $R_{15}$ , will normally be set near maximum for work on 3.9 Mc., but it will be necessary to reduce the setting for 14- and 29-Mc. operation. Working with a 3.9-Mc. crystal or VFO, best results on 75-meter 'phone will be obtained when the receiving operator uses his crystal filter for pure PM reception.

## Checking FM and PM Transmitters

Accurate checking of the operation of an FM or PM transmitter is considerably more difficult than the corresponding checks on an AM set. This is because the common forms of measuring devices either indicate amplitude variations only (a d.c. milliammeter, for ex-

ample), or because their indications are most easily interpreted in terms of amplitude. There is no simple instrument that indicates frequency deviation in a modulated signal directly, in the same fashion that an oscilloscope will indicate the instantaneous modulation percentage of an

AM signal. To check an FM signal we must first establish the relationship between frequency deviation and the amplitude of the speech signal that is causing the deviation. Then the amplitude of the speech signal becomes a measure of the frequency deviation.

There is one very favorable feature in FM or PM checking. The modulation takes place at a very low level and the stages following the one that is modulated do not affect the frequency deviation so long as they are properly tuned. Therefore the modulation may be checked *without putting the transmitter on the air*, or even on a dummy antenna. The power is simply cut off the amplifiers following the modulated stage. This not only avoids unnecessary interference to other stations during testing periods, but also keeps the signal at such a low level that it may be observed quite easily on the station receiver. A good receiver with a crystal filter is an essential part of the checking equipment of an FM or PM transmitter, particularly for narrow-band FM or PM.

The quantities to be checked in an FM or PM transmitter are the linearity and frequency deviation. Because of the essential difference between FM and PM the methods of checking differ in detail.

### Reactance-Tube FM

It was explained earlier that in FM the frequency deviation is the same at any audio modulation frequency if the audio signal amplitude does not vary. Since this is true at *any* audio frequency it is true at zero frequency. Consequently it is possible to calibrate a reactance modulator by applying an adjustable d.c. voltage to the modulator grid and noting the change in oscillator frequency as the voltage is varied. A suitable circuit for applying the adjustable voltage is shown in Fig. 9-60. The battery, *B*, should have a voltage of 3 to 6 volts (two or more dry cells in series). The arrows indicate clip connections so that the battery polarity can be reversed.

The oscillator frequency deviation should be measured by using a receiver in conjunction with an accurately-calibrated frequency meter,

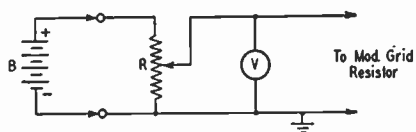


Fig. 9-60 — D.c. method of checking frequency deviation of a reactance-tube modulated oscillator. A 500- or 1000-ohm potentiometer may be used at *R*.

or by any means that will permit accurate measurement of frequency differences of a few hundred cycles. One simple method is to tune in the oscillator on the receiver (disconnect the receiving antenna, if necessary, to keep the signal strength well below the overload point) and then set the receiver b.f.o. to zero beat.

Then increase the d.c. voltage applied to the modulator grid from zero in steps of about  $\frac{1}{2}$  volt and note the beat frequency at each change. Then reverse the battery terminals and repeat. The frequency of the beat-note may be measured by comparison with a calibrated audio-frequency oscillator, or by comparison with a piano or other musical instrument (see Chapter Twenty-Four for frequen-

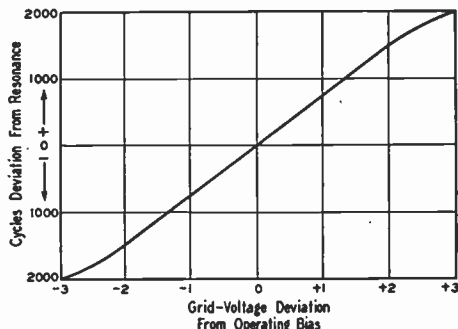


Fig. 9-61 — A typical curve of frequency deviation vs. modulator grid voltage. This curve was taken on the FM modulator unit described in this chapter (6L7 modulator and oscillator operating on 7 Mc.).

cies of musical tones). Note that with the battery polarity positive with respect to ground the radio frequency will move in one direction when the voltage is increased, and in the other direction when the battery terminals are reversed. When a number of readings has been taken a curve may be plotted to show the relationship between grid voltage and frequency deviation.

A sample curve is shown in Fig. 9-61. The usable portion of the curve is the center part which is essentially a straight line. The bending at the ends indicates that the modulator is no longer linear; this departure from linearity will cause harmonic distortion and will broaden the channel occupied by the signal. In the example, the characteristic is linear 1.5 kc. on either side of the center or carrier frequency. This is the maximum deviation permissible at the frequency at which the measurement is made. At the final output frequency the deviation will be multiplied by the same number of times that the measurement frequency is multiplied. This must be kept in mind when the check is made at a frequency that differs from the output frequency.

A good modulation indicator is a "magic-eye" tube such as the 6E5. This should be connected across the grid resistor of the reactance modulator as shown in Fig. 9-62. Note its deflection (using the d.c. voltage method as in Fig. 9-60) at the maximum deviation to be used. This deflection represents "100-per-cent modulation" and with speech input the gain should be kept at the point where it is just reached on voice peaks. If the transmitter is used on more than one band, the gain control

should be marked at the proper setting for each band, because the signal amplitude that gives the correct deviation on one band will be either too great or too small on another. For narrow-band FM the proper deviation is approximately 2000 cycles (based on an upper a.f. limit of 3000 cycles and a deviation ratio of 0.7) at the final *output* frequency. If the output frequency is in the 29-Mc. band and the oscillator is on 7 Mc., the deviation at the *oscillator* frequency should not exceed 2000/4, or 500 cycles.

#### Checking with a Crystal-Filter Receiver

With PM the d.c. method of checking just described cannot be used, because the frequency deviation at zero frequency also is zero. For narrow-band PM it is necessary to check the actual channel-width occupied by the

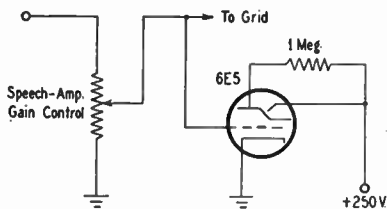


Fig. 9-62 — 6E5 modulation indicator for FM or PM modulators. To insure sufficient grid voltage for a good deflection, it may be necessary to connect the gain control in the modulator grid circuit rather than in an earlier speech-amplifier stage.

transmission. (The same method also can be used to check FM.) For this purpose it is necessary to have a crystal-filter receiver and an a.f. oscillator that generates a 3000-cycle sine wave.

Keeping the signal intensity in the receiver at a medium level, tune in the carrier at the *output* frequency. Do not use the a.v.c. Switch on the beat oscillator, and set the crystal filter at its sharpest position. Peak the signal on the crystal and adjust the b.f.o. for any convenient beat-note. Then apply the 3000-cycle tone to the speech amplifier (use the connections shown in Fig. 9-43 to avoid overloading) and increase the audio gain until there is a small amount of modulation. Tuning the receiver on either side of the carrier frequency will show the presence of sidebands 3 kc. from the carrier on both sides. With low audio input, these two should be the *only* sidebands detectable.

Now increase the audio gain and tune the receiver over a range of about 10 kc. on both sides of the carrier. When the gain becomes high enough, a second set of sidebands spaced 6 kc. on either side of the carrier will be detected. The signal amplitude at which these sidebands become detectable is the maximum speech amplitude that should be used. If the 6E5 modulation indicator is incorporated in the modulator, its deflection with the 3000-cycle tone will be the "100-per-cent modulation" deflection for speech.

When this method of checking is used with a reactance-tube modulated FM (not PM) transmitter, the linearity of the system can be checked by observing the *carrier* as the a.f. gain is slowly increased. The beat-note frequency will stay constant so long as the modulator is linear, but nonlinearity will be accompanied by a shift in the average carrier frequency that will cause the beat-note to change in frequency. If such a shift occurs at the same time that the 6-kc. sidebands appear, the extra sidebands may be caused by modulator distortion rather than by an excessive modulation index. This means that the modulator is not able to shift the frequency over a wide-enough range — a situation comparable to an AM transmitter that is not capable of 100-per-cent modulation. The 6-kc. sidebands should appear *before* there is any shift in the carrier frequency.

#### R.F. Amplifiers

The r.f. stages in the transmitter that follow the modulated stage may be designed and adjusted as in ordinary operation. In fact, there are no special requirements to be met except that all tank circuits should be carefully tuned to resonance (to prevent unwanted r.f. phase shifts that might interact with the modulation and thereby introduce hum, noise and distortion). In neutralized stages, the neutralization should be as exact as possible, also to minimize unwanted phase shifts. With FM and PM, all r.f. stages in the transmitter can be operated at the manufacturer's maximum c.w.-telegraphy ratings, since the average power input does not vary with modulation as it does in AM 'phone operation.

The output of the transmitter should be checked for amplitude modulation by observing the antenna current. It should not change from the unmodulated-carrier value when the transmitter is modulated. If there is no antenna ammeter in the transmitter, a flashlight lamp and loop can be coupled to the final tank coil to serve as a current indicator. If the carrier amplitude is constant, the lamp brilliance will not change with modulation.

Amplitude modulation accompanying FM or PM is just as much to be avoided as frequency or phase modulation that accompanies AM. A mixture of AM with either of the other two systems results in the generation of spurious sidebands and consequent widening of the channel. If the presence of AM is indicated by variation of antenna current with modulation, the cause is almost certain to be nonlinearity in the modulator. In very wide-band FM, it is possible for the selectivity of the tank circuits in the transmitter to cause the amplitude to decrease at high deviations, but this is not likely to occur on the amateur frequencies at which wide-band FM would be used. It is a practical certainty that it cannot occur with narrow-band FM or PM, except when an amplifier stage is on the verge of self-oscillation.



# Antennas and Transmission Lines

The radio-frequency power that is generated by a transmitter serves a useful purpose only when it is radiated out into space in the form of electromagnetic waves. It is the antenna's job to convert the power into radio waves as efficiently as possible, and to direct the waves where they will do the most good in communication. To do so, the antenna usually must be located well above the ground and kept as far as possible from buildings, trees, and other objects that might absorb energy. This raises a problem, because by some means or another the power that is generated inside the station, in the transmitter, must be conveyed to the antenna. The usual means is a **transmission line**.

There is thus a natural association between antennas and transmission lines — an association that has frequently led to the quite mistaken belief that an antenna fed by a particular type of transmission line is a better (or worse) radiator than exactly the same type of antenna fed by a different type of transmission line. The fact is that a transmission line can be used to carry power to any sort of device — not just an antenna — capable of receiving it. Nor does the antenna care by what means it gets the power; the amount it receives will be radiated just as well no matter by what system it was conveyed to the antenna.

While it would be dangerous to carry the comparison very far, there are nevertheless some similarities between transmission lines at radio frequencies and the lines used for carrying 60-cycle power from the generating station to the consumer. Some lines are best adapted to carrying power at high voltage and relatively low current; the reverse is true of others. Like

a lot of other electrical devices, some antennas want a relatively large current at low voltage, while others want high voltage at low current. We connect a 115-volt lamp, for example, to a 115-volt power line, but if we have a 6-volt lamp and want to run it from the 115-volt line we have to use a transformer to reduce the voltage. Similarly, if an antenna wants high current at low voltage (low impedance) and the transmission line is of a type that is best adapted to carrying power at low current and high voltage (high impedance), we need a transforming device comparable to the transformer used with the 6-volt lamp.



Fig. 10-1 — The principal elements in the system connecting the transmitter and antenna.

The power company's generators usually do not generate the voltage that is wanted on the power line, so an appropriate transformer is connected between the generator and the line. Similarly, the voltage generated in the tank circuit of the final amplifier in the transmitter usually has to be transformed to a value that "fits" the transmission line used. At radio frequencies, it is more convenient to talk in terms of impedance rather than voltage, so we speak of "impedance transformations" rather than "voltage transformations." In general, we have a complete system like that shown in block form in Fig. 10-1. Perhaps this looks complicated, but the power-line analogy should help make it understandable. The equipment itself is not particularly complex, and seems even less so when the underlying necessity for it is appreciated.

## Transmission Lines

At power-line frequencies — and even at rather high radio frequencies when we are dealing with tuned circuits that are physically rather small — it is habitual to think of current as flowing "around" the circuit. In a series circuit, for example, it is assumed that the current has the same value at every point

in the circuit. Indeed, all the explanations of circuit action in Chapter Two are based on this assumption.

The assumption can be true only if electrical and magnetic effects take place instantaneously all around the circuit. The fact is, though, that the action is *not* instantaneous. The

fastest that an electromagnetic field can travel is 300,000,000 meters, or 186,000 miles, per second. This is a tremendous speed, and is so great that in many circuits the action *appears* to be instantaneous. When that is so we can ignore the fact that it takes a certain amount of time for an electrical effect that occurs at one point to be felt at another a short distance away.

But there are other circuits in which time becomes an all-important factor. The transmission lines used to carry radio-frequency power are typical circuits in which time cannot be neglected.

### ● CURRENT FLOW IN LONG LINES

Suppose we have a battery connected to a pair of parallel wires that extends to a very great distance, as in Fig. 10-2. At the moment

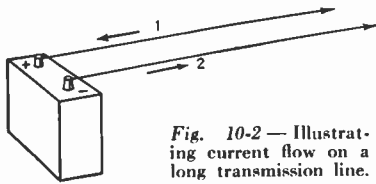


Fig. 10-2 — Illustrating current flow on a long transmission line.

the battery is connected to the wires, electrons in wire No. 1 near the positive terminal of the battery will be attracted to the battery, and the same number of electrons in wire No. 2, near the battery terminal, will be repelled outward along the wire. The directions are shown by the arrows. Thus a current flows in both wires at the instant the battery is connected. These currents do *not* flow throughout the entire length of both wires simultaneously. They start instantaneously in both wires at the battery terminals, but a definite time interval will elapse before they are evident at a distance from the battery.

The time interval may be very small. For example, one-millionth of a second (one microsecond) after the connection is made the currents in the wires will have traveled 300 meters, or nearly 1000 feet, from the battery terminals. Note that they flow in both wires simultaneously, even though there may be no connection between the two wires at the end (which is infinitely far away) to form what we ordinarily think of as a closed circuit.

The current is in the nature of a charging current, flowing to charge the capacitance between the two wires. But unlike an ordinary condenser, the conductors of this "linear" condenser have appreciable inductance. In fact, we may think of the line as being composed of a whole series of small inductances and capacitances connected as shown in Fig. 10-3, where each coil is the inductance of a very short section of one wire and each condenser is the capacitance between two such short sections.

### Characteristic Impedance

An indefinitely-long chain of coils and condensers connected as in Fig. 10-3, where each  $L$  is the same as all others and all the  $C$ s have the same value, has an interesting and important peculiarity. To an electrical impulse applied to one end, the combination (or transmission line) appears to have an impedance that is approximately equal to  $\sqrt{L/C}$ , where  $L$  and  $C$  are the inductance and capacitance per unit length. Furthermore, this impedance is purely resistive. The line will "look like" such an impedance only when it is infinitely long, but even a short line can be made to "think" it is infinitely long by means to be described a little later.

This inherent line impedance is called the **characteristic impedance** or **surge impedance** of the line. Its value is determined by the inductance and capacitance per unit length. These quantities in turn depend upon the size of the line conductors and the spacing between them. The closer the two conductors of the line and the greater their diameter, the higher the capacitance and the lower the inductance. A line with large conductors closely spaced will have low impedance, while one with small conductors widely spaced will have relatively high impedance.

The characteristic impedance of the line is a very important property. For one thing, it determines the amount of current that can flow when a voltage is applied to the line. When a line is infinitely long, the current is simply equal to  $E/Z_0$ , where  $E$  is the voltage applied to the line and  $Z_0$  is the characteristic impedance. This has nothing to do with the *resistance* of the conductors; in fact, in this simplified picture of a transmission line we

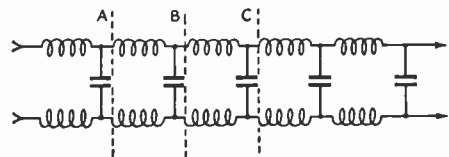


Fig. 10-3 — Equivalent of a transmission line in lumped circuit constants.

have tacitly assumed that the conductors do not have any resistance. The line is an impedance (like any circuit composed of  $L$  and  $C$ , without any  $R$ ) that does not consume power. Actually, of course, the conductors do have resistance, so power cannot be transmitted along the line without some loss. But if the line is properly constructed and operated, this loss will be small compared with the amount of power carried to the load to do useful work.

### R.F. on Lines

Bearing in mind that *time* must elapse before the currents initiated at the "input" end of the line — that is, the end to which the source of

power is connected — can appear some distance away, consider now what happens when a radio-frequency voltage is applied to a transmission line. Suppose an r.f. generator is connected to a long line as shown in Fig. 10-4. To make the figures easy, assume that the frequency is 10 Mc., or 10,000,000 cycles per second. Then each cycle will occupy 0.1 microsecond, as shown by the drawing of the applied voltage. Suppose that the points *B* and *D* along the line are 30 meters away from *A* and *C*, respectively. If the current travels with the velocity of light, in 0.1 microsecond (one cycle) it will move 30 meters (300,000,000 meters divided by 10,000,000 cycles) along the line. This is a distance of one wavelength. Thus any currents observed at *B* and *D* occur just one cycle later in time than the currents at *A* and *C*. To put it another way, the currents initiated at *A* and *C* do not appear at *B* and *D*, one wavelength away, until the applied voltage has had time to go through a complete cycle.

Since the applied voltage is always changing, the currents at *A* and *C* are changing in proportion. The current a short distance away from *A* and *C* — for instance, at *X* and *Y* — is not the same as the current at *A* and *C* because the current at *X* and *Y* was caused by a value of voltage that occurred slightly earlier in the cycle. This is true all along the line; at any instant the current anywhere along the line from *A* to *B* and *C* to *D* is different from the current at every other point in that same distance. The series of drawings shows how the instantaneous currents might be distributed if we could snapshot them at intervals of one-quarter cycle. The current travels out from the input end of the line in waves.

At any selected point on the line the current goes through its complete range of a.c. values in the time of one cycle just as it does at the input end. Therefore (if there are no losses) an ammeter inserted in either conductor would read exactly the same current at any point along the line, because the ammeter averages the current over a whole cycle. The phases of the currents at any two separated points would be different, but an ammeter would not show this.

### “Matched” Lines

In this picture of current traveling along a transmission line we have assumed that the line was infinitely long. Lines have a definite length, of course, and they are connected to or terminated in a load at the “output” end, or end to which the power is delivered. If the load is a pure resistance of a value equal to the characteristic impedance of the line, the current traveling along the line to the load does not find conditions changed in the least when it meets the load; in fact, the load just looks like still more transmission line of the same

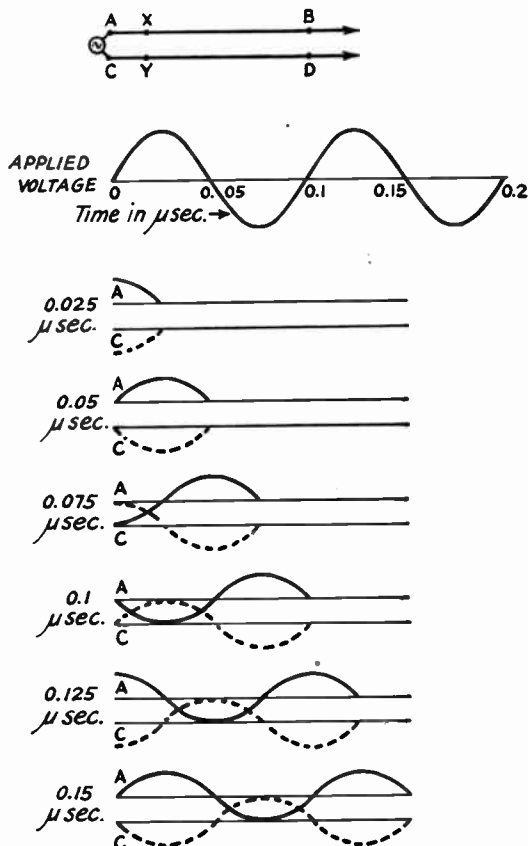


Fig. 10-4 — Progression of radio-frequency current flow in a transmission line.

characteristic impedance. Consequently, connecting such a load to a short transmission line allows the current to travel in exactly the same fashion as it would on an infinitely-long line.

In other words, a short line terminated in a purely-resistive load equal to the characteristic impedance of the line acts just as though it were infinitely long. Such a line is said to be **matched**. In a matched transmission line, power travels outward along the line from the source until it reaches the load, where it is completely absorbed.

### ● STANDING WAVES

Now suppose that the line is terminated in a load that is not equal to the line's characteristic impedance. To take an extreme case, suppose that the output end of the line is short-circuited, as in Fig. 10-5.

With the infinitely-long line (or its matched counterpart) the impedance was the same at any point on the line and therefore the ratio of voltage to current was the same at any point on the line. However, the impedance at the end of the line in Fig. 10-5 is zero — or at least extremely small. A given amount of

power in a very low impedance will result in a very large current and a very small voltage, as compared with the current-voltage ratio that exists in a few hundred ohms — which is a typical impedance value for some types of transmission lines. Something has to happen, therefore, when the power traveling along the transmission line meets the short-circuit at the end.

What happens is that the outgoing power, on meeting the short-circuit, simply reverses its direction of flow and goes back along the transmission line toward the input end. It has nowhere else to go. There is a very large current in the short-circuit, but substantially no voltage across the line at this point. We now have a voltage and current representing the power going outward toward the short-circuit, and a second voltage and current representing the reflected power traveling back toward the source.

Consider only the two current components

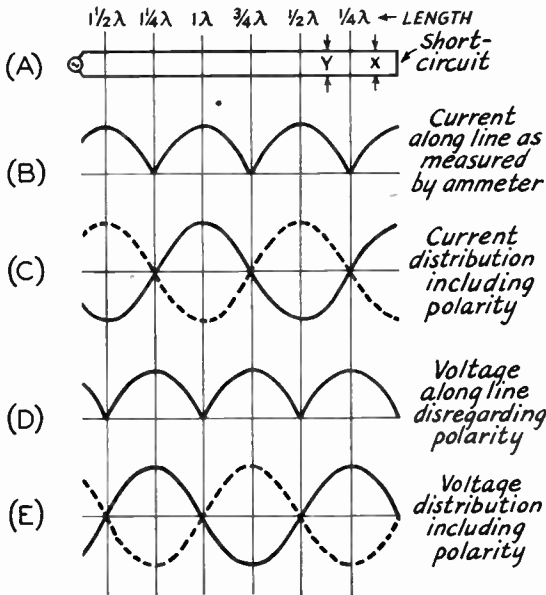


Fig. 10-5 — Standing waves of voltage and current along a short-circuited transmission line.

for the moment. The reflected current travels at the same speed as the outgoing current, so its instantaneous value will be different at every point along the line, in the distance represented by the time of one cycle. At some points along the line the outgoing and reflected currents will be in phase while at other points they will be completely out of phase. At the out-of-phase points the currents cancel each other (if the outgoing and reflected currents have the same value, as they will if all the power is reflected) and so at those points the resultant current is zero. At the in-phase points the two currents add numerically. At in-between points the two currents are neither

completely in nor completely out of phase and so their sum is not equal to their numerical sum, but is something less.

The points at which the currents are in and out of phase depend only on the *time* required for them to travel and so depend only on the *distance* along the line from the point of reflection. The phase is completely reversed when the current travels for one-half cycle — that is, a distance of one-half wavelength — and is back in the in-phase condition when the current has traveled for one whole cycle, or one wavelength.

In the short-circuit at the end of the line the total current is high and the two current components are in phase. Therefore at a distance of *one-half* wavelength back along the line from the short-circuit the outgoing and reflected components will again be in phase and the current will have its maximum value. This is also true at any point that is a multiple of a half-wavelength from the short-circuited end of the line. The distance along the line is one-half wavelength because the current has to travel the distance twice in order to “meet itself coming back.”

Since a total distance of one-half wavelength gives a complete reversal of phase, the outgoing and reflected currents will cancel at a point *one-quarter* wavelength, along the line, from the short-circuit. At this point, then, the current will be zero. It will also be zero at all points that are an *odd* multiple of one-quarter wavelength from the short-circuit.

If the current along the line is measured at successive points with an ammeter, it will be found to vary about as shown in Fig. 10-5B. The same result would be obtained by measuring the current in either wire, since the ammeter cannot measure phase. However, if the phase could be checked, it would be found that in each successive half-wavelength section of the line the currents at any given instant are flowing in opposite directions, as indicated by the solid line in Fig. 10-5C. Furthermore, the current in the second wire is flowing in the opposite direction to the current in the adjacent section of the first wire, as a result of the

electron movement discussed in connection with Fig. 10-2. This is indicated by the broken curve in Fig. 10-5C. The variations in current intensity along the transmission line are referred to as **standing waves**. The point of maximum line current is called a **current loop** and the point of minimum line current a **current node**.

**Voltage Relationships**

Since the end of the line is short-circuited, the voltage at that point has to be zero. This can only be so if the voltage in the outgoing wave is met, at the end of the line, by an equal voltage of opposite polarity. In other words,

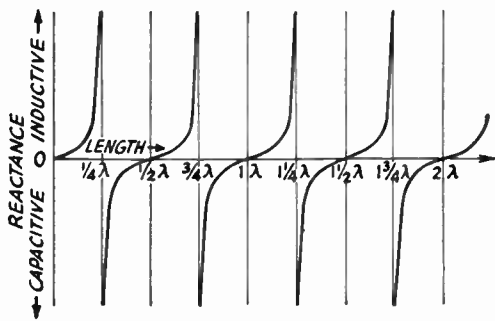


Fig. 10-6 — Input reactance vs. length of a short-circuited transmission line. Actual values of reactance depend upon the characteristic impedance of the line as well as its length. For a given line length, the input reactance is directly proportional to the characteristic impedance.

the phase of the voltage wave is reversed when reflection takes place from the short-circuit. This reversal is equivalent to an extra half-cycle or half-wavelength of travel. As a result, the outgoing and returning voltages are in phase a quarter wavelength from the end of the line, and again out of phase a half-wavelength from the end. The standing waves of voltage, shown at D in Fig. 10-5, are therefore displaced by one-quarter wavelength from the standing waves of current. The drawing at E shows the voltages on both wires when phase is taken into account. The polarity of the voltage on each wire reverses in each half-wavelength section of transmission line. A voltage maximum on the line is called a voltage loop and a voltage minimum is called a voltage node.

**Input Impedance**

It is apparent, from examination of B and D in Fig. 10-5, that at points that are a multiple of a half-wavelength — i.e.,  $\frac{1}{2}$ , 1,  $1\frac{1}{2}$  wavelengths, etc. — from the short-circuited end of the line the current and voltage have the same values that they do at the short-circuit. In other words, if the line were an exact multiple of a half-wavelength long the generator or source of power would “look into” a short-circuit. On the other hand, at points that are an odd multiple of a quarter wavelength — i.e.,  $\frac{1}{4}$ ,  $\frac{3}{4}$ ,  $1\frac{1}{4}$ , etc. — from the short-circuit the voltage is maximum and the current is zero. Since  $Z = E/I$ , the impedance at these points is theoretically infinite. (Actually it is very high, but not infinite. This is because the current does not actually go to zero when there are losses in the line. Losses are always present, but usually are small enough so that the impedance is of the order of tens or hundreds of thousands of ohms.)

At either the odd or even multiples of a quarter wavelength the impedance is a pure resistance, because at these points the current and voltage in the transmission line are exactly in phase.

A detailed study of the outgoing and reflected components of voltage and current will show that at a point such as X in Fig. 10-5, lying anywhere in the section of line between the short-circuit and the first quarter-wavelength point, the current lags behind the voltage. This is exactly what happens in an inductance, so it can be said that a section of short-circuited transmission line less than a quarter wavelength long has inductive reactance. The value of reactance is determined by the ratio of voltage to current at the input end of such a line. It is evident from B and D in Fig. 10-5 that the reactance is low when the line is quite short, and highest when the line is nearly a quarter wavelength long. The line also has inductive reactance when its length is between one-half and three-quarter wavelengths, between one and one-and-one-quarter wavelengths, and so on.

On the other hand, in the section of line between one-quarter and one-half wavelength from the short-circuit the current leads the voltage, so a short-circuited line having a length between these two limits “looks like” a capacitive reactance to the generator to which it is connected. The reactance is highest when the line is just over one-quarter wavelength long, and lowest when the line is just less than one-half wavelength long. Fig. 10-6 shows the general way in which the reactance varies with different line lengths.

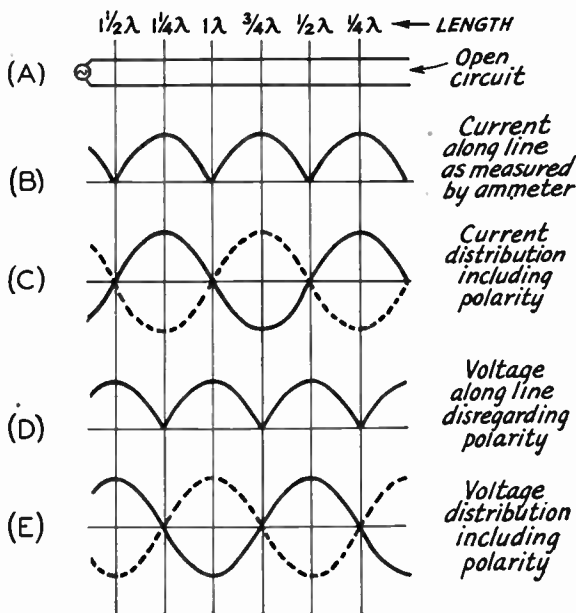


Fig. 10-7 — Standing waves of current and voltage along an open-circuited transmission line.

**Open-Circuited Line**

If the end of the line is open-circuited instead of short-circuited, there can be no current at the end of the line but a large voltage can exist. Again the outgoing power is reflected back toward the source because it has nowhere else to go. In this case, the outgoing and reflected components of *current* must be equal and opposite in phase in order for the total current at the end of the line to be zero. The outgoing and reflected components of voltage

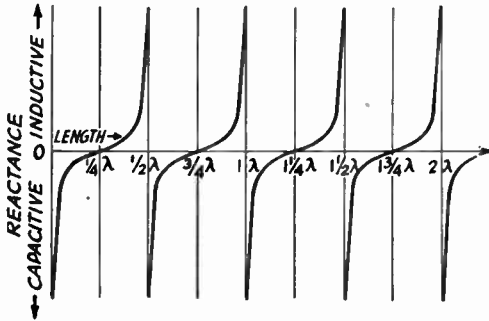


Fig. 10-8 — Input reactance vs. length of an open-circuited transmission line. Actual values of reactance depend upon the characteristic impedance of the line as well as its length. For a given line length, the input reactance is directly proportional to the characteristic impedance.

are in phase, however, and add together. The result is that we again have standing waves, but the conditions are reversed. Fig. 10-7 shows the open-circuited line case. It may be compared directly with Fig. 10-5. The impedance looking into the line toward the open end is purely resistive at each multiple of one-quarter wavelength. It is very low at odd multiples of one-quarter wavelength, and very high at even multiples. In fact, an open-circuited line and short-circuited line behave just alike if the length of one differs by one-quarter wavelength from the length of the other.

Fig. 10-8 shows how the reactance varies with line length for the open-circuited line. Comparing this with Fig. 10-6 shows that the reactance of any given length of line is of the opposite type to that obtained with a short-circuited line of the same length.

**Lines Terminated in Resistive Load**

An open- or short-circuited line does not deliver any power to a load, and for that reason is not, strictly speaking, a "transmission" line. However, the fact that a line of the proper length has an extremely high resistive input impedance at a given frequency or wavelength makes such lines useful as substitutes for the more common coil-and-condenser resonant circuits. With proper design, the effective *Q* of such a "linear" resonant circuit is much higher than is obtainable with coils and condensers. Linear circuits are particularly useful at v.h.f., and their application in that field is discussed

in later chapters. In this chapter we are concerned with lines delivering power to a load such as an antenna.

Fig. 10-9 shows a line terminated in a resistive load. In such a case at least part of the outgoing power is absorbed in the load, and so is not available to be reflected back toward the source. Because only part of the power is reflected, the reflected components of voltage and current do not have the same magnitude as the outgoing components. Therefore there is no such thing as complete cancellation of either voltage or current at any point along the line. However, the *speed* at which the outgoing and reflected components travel is not affected by their amplitude, so the phase relationships are similar to those in open- or short-circuited lines.

It was pointed out earlier that if the load resistance, which we will call  $Z_r$ , is equal to the characteristic impedance,  $Z_0$ , of the line all the power is absorbed in the load. In such a case there is no reflected power and therefore no standing waves of current and voltage. This is a special case that represents the changeover point between "short-circuited" and "open-circuited" lines. If  $Z_r$  is less than  $Z_0$ , the current is largest at the load and the reflected component of voltage is out of phase with the outgoing component at the load. If  $Z_r$  is greater than  $Z_0$ , the voltage is largest at the load and the reflected component of current is out of phase with the outgoing component. Thus, if  $Z_r$  is less than  $Z_0$  the current will be minimum at a point one-quarter wavelength from the load and at every point an odd number of quarter wavelengths away, while the voltage will be maximum at these same points. The current will be maximum and the voltage minimum at points that are multiples of one-half wavelength from the load. If  $Z_r$  is greater

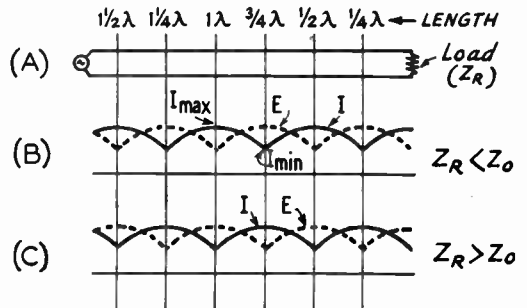


Fig. 10-9 — Standing waves on a transmission line terminated in a resistive load.

than  $Z_0$ , the opposite is true. The two conditions are shown at B and C, respectively, in Fig. 10-9.

The impedance looking into the line toward the load will be purely resistive (if  $Z_r$  is a pure resistance) when the line length is a multiple of a quarter wavelength, just as in the open- and short-circuited cases. The input imped-

ance is equal to  $Z_r$  when the line is an even multiple of a quarter wavelength long. If  $Z_r$  is less than  $Z_o$  the impedance is maximum when the line is an odd multiple of a quarter wavelength long. In such a case the impedance looking into the line is

$$Z_s = \frac{Z_o^2}{Z_r} \quad (10-A)$$

where  $Z_s$  = Impedance looking into line (line length an odd multiple of one-quarter wavelength)

$Z_r$  = Impedance of load (must be pure resistance)

$Z_o$  = Characteristic impedance of line

Example: A quarter-wavelength line having a characteristic impedance of 500 ohms is terminated in a resistive load of 75 ohms. The impedance looking into the input or sending end of the line is

$$Z_s = \frac{Z_o^2}{Z_r} = \frac{(500)^2}{75} = \frac{250,000}{75} = 3333 \text{ ohms}$$

When  $Z_r$  is greater than  $Z_o$ , the input impedance reaches its minimum value when the line is an odd multiple of a quarter wavelength long. The value of input impedance in this case also is given by the equation above.

Example: A quarter-wavelength line is terminated in a resistive load of 1200 ohms. The characteristic impedance of the line is 600 ohms. Then the input impedance of the line is

$$Z_s = \frac{Z_o^2}{Z_r} = \frac{(600)^2}{1200} = \frac{360,000}{1200} = 300 \text{ ohms}$$

### Impedance Transformation

If the formula in the preceding discussion is rearranged, we have

$$Z_o = \sqrt{Z_s Z_r} \quad (10-B)$$

This means that if we have two values of impedance that we wish to "match," we can do so if we connect them together by a quarter-wave transmission line having a characteristic impedance equal to the square root of their product. A quarter-wave line, in other words, has the characteristics of a transformer. This is a very useful attribute of transmission lines.

Example: A 600-ohm transmission line is to be used to feed an antenna that has a resistive impedance of 75 ohms. It is desired that the line operate without standing waves, and it must therefore be terminated in a resistive load equal to its characteristic impedance; i.e., 600 ohms. A quarter-wave line or "linear transformer" is to be used to match the 75-ohm load to the line impedance. To do this, the characteristic impedance of the quarter-wave transformer must be

$$Z_o = \sqrt{Z_s Z_r} = \sqrt{75 \times 600} = \sqrt{45,000} = 223 \text{ ohms}$$

### Reactance of Terminated Lines

We have seen that a short-circuited line less than one-quarter wavelength long exhibits inductive reactance. Also, a line of any length terminated in a resistive load equal to its characteristic impedance always looks like a pure resistance to the source of power. When the

load is purely resistive and has any value between zero and  $Z_o$ , a line less than a quarter wave long will show inductive reactance, but the reactive effects decrease the closer the value of  $Z_r$  approaches  $Z_o$ .

On the other hand, an open-circuited line less than one-quarter wavelength long exhibits capacitive reactance. If the line is terminated in a resistive load larger than  $Z_o$ , it continues to show capacitive reactance but the reactive effects are less the closer  $Z_r$  approaches  $Z_o$  in value.

In general, then, a line terminated in a resistive impedance less than  $Z_o$  will show reactance variations with length similar to those of a short-circuited line as given in Fig. 10-6. A line terminated in a resistive impedance greater than  $Z_o$  will show reactance variations with length similar to those of an open-circuited line as given in Fig. 10-8. The magnitudes of the reactances will be smaller the closer  $Z_r$  approaches  $Z_o$  in value.

### Loads That Are Not Pure Resistance

In most amateur applications of transmission lines the load is — or should be — a pure resistance. At least, every attempt is made to make it so. However, there are cases where the load has reactance as well as resistance, and recognizing the symptoms of reactance in the load is of value in indicating what steps should be taken to convert the load to a pure resistance.

The situation is easier to visualize if a line terminated in a pure reactance is considered first. For example, suppose the line is terminated in a capacitive reactance as shown in Fig. 10-10A. It does not matter to the line what physical form the reactance takes; the important thing is that in it the current leads the voltage. The reactance might be a condenser, for example — or it might simply be an additional section of transmission line that exhibits capacitive reactance at its input end, as indicated in Fig. 10-10B.

From Fig. 10-8, we can see that a section of open-circuited transmission line less than one-quarter wavelength long will have capacitive reactance. By proper choice of line length, any desired value of reactance can be obtained. Conversely, any "lumped" reactance, such as a condenser, connected to the end of the transmission line can be replaced by a section of open-circuited line of appropriate length. If the condenser capacitance is small and its reactance therefore is high, only a short length of line is required. If the condenser capacitance is large and its reactance consequently is low, the additional line section must be nearly a quarter wavelength long. In other words, connecting a condenser across the end of the transmission line is equivalent to lengthening the line, electrically. The amount of effective lengthening depends on the capacitance of the condenser.

Once the equivalent lengthening is determined, we can simply look upon the line as one having the new length and apply all that has been said previously. In the case just considered, this would mean that the point of maximum current, instead of appearing exactly a quarter wavelength from the end of the open-circuited line, would appear at something less than a quarter wavelength from the end. This is shown in Fig. 10-10C. The larger the capacitance of the terminating condenser the closer the current loop comes to the physical end of the line. All the other loops and nodes of both current and voltage would be changed accordingly.

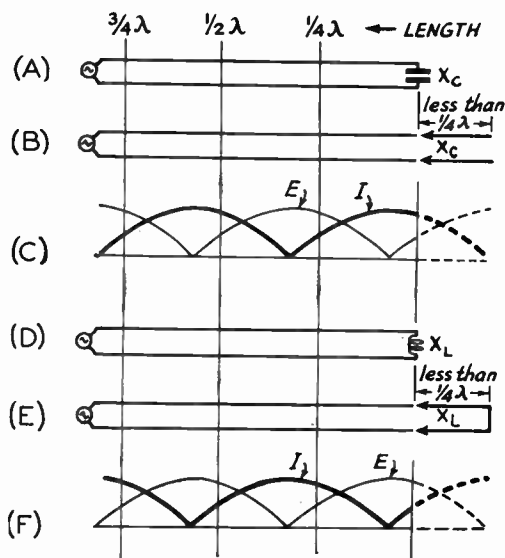


Fig. 10-10 — Lines terminated in reactance. A reactive load is equivalent to a change in the length of the line.

If the line is terminated in an inductance, we can substitute a short-circuited section of line less than one-quarter wavelength long for the lumped inductance. Thus, terminating a line in an inductance is equivalent to extending its length by something less than one-quarter wavelength and short-circuiting it. This is shown at D, E and F in Fig. 10-10. The larger the inductance, the greater the length of line, up to one-quarter wavelength, that must be added to obtain the electrical equivalent. When the equivalent section of line is substituted for the inductance, all that has been said about shorted lines applies, based on the new equivalent length.

When the load has both resistance and reactance the apparent length of the line is again increased. However, the amount of the apparent increase is affected by the resistance component of the load together with the reactive component. Inductive reactance will cause the first voltage maximum to appear less than one-quarter wavelength from the load, just as

in Fig. 10-10F. Capacitive reactance will cause the first current maximum to appear less than one-quarter wavelength from the load, as in Fig. 10-10C. If the positions of either the voltage or current loops can be determined, it is always possible to tell whether the reactive component of the load is inductive or capacitive. When the load has both resistance and reactance, the voltage and current nodes do not reach zero because not all the outgoing power is reflected. The actual standing waves would be more like those shown in 10-9, but with the positions of the nodes and loops shifted as indicated in Fig. 10-10.

### Standing-Wave Ratio

The ratio of maximum current to minimum current along a line, as indicated in Fig. 10-11, is called the standing-wave ratio. It is a measure of the mismatch between the load and the line, and is equal to 1 when the line is perfectly matched. (In that case the "maximum" and "minimum" current are the same, since the current does not vary along the line.) When the line is terminated in a purely-resistive load, the standing-wave ratio is

$$S.W.R. = \frac{Z_r}{Z_o} \text{ or } \frac{Z_o}{Z_r} \quad (10-C)$$

Where *S.W.R.* = Standing-wave ratio

$Z_r$  = Impedance of load (must be pure resistance)

$Z_o$  = Characteristic impedance of line

Example: A line having a characteristic impedance of 300 ohms is terminated in a resistive load of 25 ohms. The s.w.r. is

$$S.W.R. = \frac{Z_o}{Z_r} = \frac{300}{25} = 12 \text{ to } 1$$

It is customary to put the larger of the two quantities,  $Z_r$  or  $Z_o$ , in the numerator of the fraction so that the s.w.r. will be expressed by a number larger than 1.

It is easier to measure the standing-wave ratio than some of the other quantities (such as the impedance of an antenna) that enter into transmission-line computations. Consequently, the s.w.r. is a convenient basis for work with lines. The higher the s.w.r., the greater the mismatch between line and load. Also, the higher the s.w.r. the more marked are the reactive effects when the line length is not an exact multiple of a quarter-wavelength. In practical lines, the loss in the line itself increases with the s.w.r.

### Resonant and Nonresonant Lines

A transmission line terminated in a resistive load equal to its characteristic impedance is commonly called a **flat, nonresonant or untuned** line. The line is "flat" because there are no standing waves, hence a graph of the current along the line is a straight line. It is "nonresonant" because the input impedance of



such a line is pure resistance and does not change when the line length is changed.

When there are standing waves the line is said to be **resonant** or **tuned**. In this case the input impedance depends critically on the length of the line and the characteristics of the load. The input impedance is a pure resistance only when the line length is such that a current or voltage loop appears at the input end. The previous discussion has shown that the positions of these loops depends upon the characteristics of the load. At all other lengths the input impedance consists of both reactance and resistance. Under these conditions the line acts something like a circuit that is not tuned to resonance; it is difficult to make it "take power" until something is done to "tune" it — that is, to eliminate the reactance. When this is done the input impedance of the line is purely resistive and its resistance may be matched to the transmitter for optimum power transfer.

It should be noted that if there are standing waves on the line the input impedance, even when the reactance is tuned out, is never equal to the characteristic impedance of the line. Depending on the length of the line, the characteristics of the load, and the s.w.r., the input resistance may be considerably higher or considerably lower than the line's characteristic impedance. This introduces an element of uncertainty in coupling to the transmitter. In one special case, when the load is a pure resistance and the line is exactly one-half wavelength long, the input impedance of the line is a pure resistance equal to the load impedance.

The reactive or resonance effects increase with the s.w.r., as previously pointed out. Generally speaking, a line is satisfactorily flat if the s.w.r. does not exceed about 1.5 to 1, but if the s.w.r. is much larger it becomes necessary to tune out the input reactance.

### Radiation

Whenever a wire carries alternating current the electromagnetic fields travel away into space with the velocity of light. At power-line frequencies the field that "grows" when the current is increasing has plenty of time to return or "collapse" about the conductor when the current is decreasing, because the alternations are so slow. But at radio frequencies fields that travel only a relatively short distance do not have time to get back to the conductor before the next cycle commences. The consequence is that some of the electromagnetic energy is prevented from being restored to the conductor; in other words, energy is radiated into space in the form of electromagnetic waves.

The amount of energy radiated depends, among other things, on the length of the conductor in relation to the frequency or wavelength of the r.f. current. If the conductor is very short compared to the wavelength the energy radiated will be small. However, a transmission line used to feed power to an

antenna is not short in this sense; in fact, it is almost always an appreciable fraction of a wavelength long and may have a length of several wavelengths.

The lines previously considered have consisted of two parallel conductors of the same diameter. Provided there is nothing in the system to destroy symmetry, at every point along the line the current in one conductor has the same intensity as the current in the other conductor at that point, but the currents flow in opposite directions. This was shown in Figs. 10-5C and 10-7C. This means that the fields set up about the two wires have the same intensity, but *opposite directions*. The consequence is that the total field set up about such a transmission line is zero; the two fields "cancel out." Hence no energy is radiated.

Actually, the fields do not completely cancel out because for them to do so the two conductors would have to occupy the same space, whereas they are slightly separated. However, the cancellation is substantially complete if the distance between the conductors is very small compared to the wavelength. Radiation will be negligible if the distance between the conductors is 0.01 wavelength or less, provided the currents in the two actually are balanced as described.

The amount of radiation also is proportional to the current flowing in the line. Because of the way in which the current varies along the line when there are standing waves, the effective current, for purposes of radiation, becomes greater as the s.w.r. is increased. For this reason the radiation is least when the line is flat. However, if the conductor spacing is small and the currents are balanced, the radiation from a line with even a high s.w.r. is inconsequential. A small unbalance in the line currents is far more serious.

There is no factual basis for the common belief that the presence of standing waves on a transmission line always means that the line is radiating a great deal of r.f. energy. Tuned lines are perhaps more subject to the stray coupling effects described later in this chapter, simply because they are frequently cut to resonant lengths while any random length can be used for a flat line. It is the stray coupling that gives rise to excessive line radiation, not the presence of the normal type of standing wave on the transmission line.

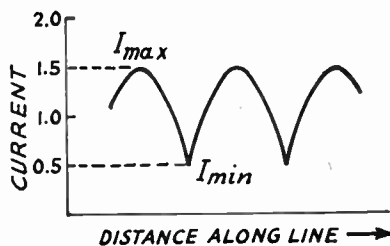


Fig. 10-11 — Measurement of standing-wave ratio. In this drawing,  $I_{max}$  is 1.5 and  $I_{min}$  is 0.5, so the s.w.r. =  $I_{max}/I_{min} = 1.5/0.5 = 3$ .

## Practical Line Characteristics

The foregoing discussion of transmission lines has been based on a line consisting of two parallel conductors. Actually, the parallel-conductor line is but one of two general types. The other is the coaxial or concentric line. The coaxial line consists of a round conductor placed in the center of a circular tube. The inside surface of the tube and the outside surface of the smaller inner conductor form the two conducting surfaces of the line.

In the coaxial line the fields are entirely inside the tube, because the tube acts as a shield to prevent them from appearing outside. This reduces radiation to the vanishing point. So far as the electrical behavior of coaxial lines is concerned, all that has previously been

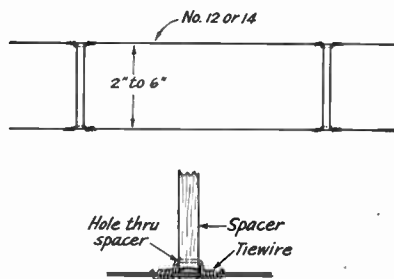


Fig. 10-12 — Typical construction of open-wire line. The line conductor fits in a groove in the end of the spacer, and is held in place by a tie-wire anchored in a hole near the groove.

said about the operation of parallel-conductor lines applies. There are, however, practical differences in their construction and use.

### Types of Construction

There are several constructional variations in both the basic types of transmission lines mentioned in the preceding section. Probably the most common type of transmission line used in amateur installations is a parallel-conductor line in which two wires (ordinarily No. 12 or No. 14) are supported a fixed distance apart by means of insulating rods called "spacers." The spacings used vary from two to six inches, the smaller spacings being necessary at frequencies of the order of 28 Mc. and higher so that radiation will be minimized. The construction is shown in Fig. 10-12. Such a line is said to be air-insulated. Typical spacers are shown in Fig. 10-13. The characteristic impedance of such "open-wire" lines runs between about 400 and 600 ohms, depending on the wire size and spacing.

Parallel-conductor lines also are sometimes constructed of metal tubing of a diameter of  $\frac{1}{4}$  to  $\frac{1}{2}$  inch. This reduces the characteristic impedance of the line. Such lines are mostly used as quarter-wave transformers, when different values of impedance are to be matched.

Two forms of "Twin-Lead" or "ribbon" transmission line are shown in Fig. 10-13. This is a parallel-conductor line with stranded conductors imbedded in low-loss insulating material (polyethylene). It has the advantages of light weight, compactness and neat appearance, together with close and uniform spacing. However, losses are higher in the solid dielectric than in air, and dirt or moisture on the line tends to change the characteristic impedance. Twin-Lead line is available in characteristic impedances of 75, 150 and 300 ohms.

The most common form of coaxial line consists of either a solid or stranded-wire inner conductor surrounded by polyethylene dielectric. Copper braid is woven over the dielectric to form the outer conductor, and a waterproof vinyl covering is placed on top of the braid. This cable is made in a number of different diameters. It is moderately flexible, and so is convenient to install. Some different types are shown in Fig. 10-13. This solid coaxial cable is commonly available in impedances approximating 50 and 70 ohms.

Air-insulated coaxial lines have lower losses than the solid-dielectric type, but are less used in amateur work because they are expensive and difficult to install as compared with the flexible cable. The common type of air-insulated coaxial line uses a solid-wire conductor inside a copper tube, with the wire held in the center of the tube by means of insulating "beads" at regular intervals.

### Characteristic Impedance

The characteristic impedance of an air-insulated parallel-conductor line is given by:

$$Z_0 = 276 \log \frac{b}{a} \quad (10-D)$$

where  $Z_0$  = Characteristic impedance

$b$  = Center-to-center distance between conductors

$a$  = Radius of conductor (in same units as  $b$ )

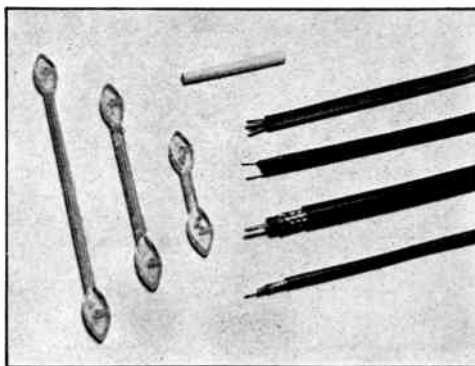


Fig. 10-13 — Typical manufactured transmission lines and spacers.

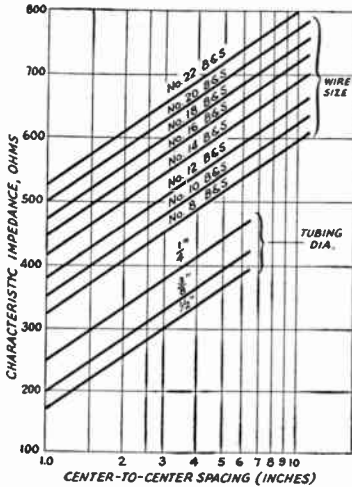


Fig. 10-14 — Chart showing the characteristic impedance of typical spaced-conductor parallel transmission lines. Tubing sizes given are for outside diameters.

It does not matter what units are used for *a* and *b* so long as they are the same units. Both quantities may be measured in centimeters, inches, etc. Since it is necessary to have a table of common logarithms to solve practical problems, the solution is given in graphical form in Fig. 10-14 for a number of common conductor sizes.

The characteristic impedance of an air-insulated coaxial line is given by the formula

$$Z_0 = 138 \log \frac{b}{a} \quad (10-E)$$

where *Z*<sub>0</sub> = Characteristic impedance  
*b* = Inside diameter of outer conductor  
*a* = Outside diameter of inner conductor (in same units as *b*)

Again it does not matter what units are used for *b* and *a*, so long as they are the same. Curves for typical conductor sizes are given in Fig. 10-15.

The formula for coaxial lines is approximately correct for lines in which bead spacers are used, provided the beads are not too closely spaced. When the line is filled with a solid dielectric, the characteristic impedance as given by the chart should be multiplied by  $1/\sqrt{K}$ , where *K* is the dielectric constant of the material. In solid-dielectric parallel-conductor lines such as Twin-Lead the characteristic impedance cannot be calculated readily, because part of the electric field is in air as well as in the solid dielectric.

**Electrical Length**

In the discussion of line operation earlier in this chapter it was assumed that currents traveled along the conductors at the speed of light. Actually, the velocity is somewhat less, the reason being that electromagnetic fields travel more slowly in dielectric materials than they do in free space. In air the velocity is

practically the same as in empty space, but a practical line always has to be supported in some fashion by solid insulating materials. The result is that the fields are slowed down; the currents travel a shorter distance in the time of one cycle than they do in space, and so the wavelength along the line is less than the wavelength would be in free space at the same frequency. (Wavelength is equal to velocity divided by frequency.)

Whenever reference is made to a line as being so many wavelengths (such as a "half-wavelength" or "quarter wavelength") long, it is to be understood that the electrical length of the line is meant. Its actual physical length as measured by a tape always will be somewhat less. The physical length corresponding to an electrical wavelength is given by

$$\text{Length in feet} = \frac{984}{f} \cdot V \quad (10-F)$$

where *f* = Frequency in megacycles  
*V* = Velocity factor

The velocity factor is the ratio of the actual velocity along the line to the velocity in free space. Values of *V* for several common types of lines are given in Table 10-I.

Example: A 75-foot length of 300-ohm Twin-Lead is used to carry power to an antenna at a frequency of 7150 kc. From Table 10-I, *V* is 0.82. At this frequency (7.15 Mc.) a wavelength is

$$\begin{aligned} \text{Length (feet)} &= \frac{984}{f} \cdot V = \frac{984}{7.15} \times 0.82 \\ &= 137.6 \times 0.82 = 112.8 \text{ ft.} \end{aligned}$$

The line length is therefore  $75/112.8 = 0.665$  wavelength.

Because a quarter-wavelength line is frequently used as a linear transformer, it is convenient to calculate the length of a quarter-wave line directly. The formula is

$$\text{Length (feet)} = \frac{246}{f} \cdot V \quad (10-G)$$

where the symbols have the same meaning as above.

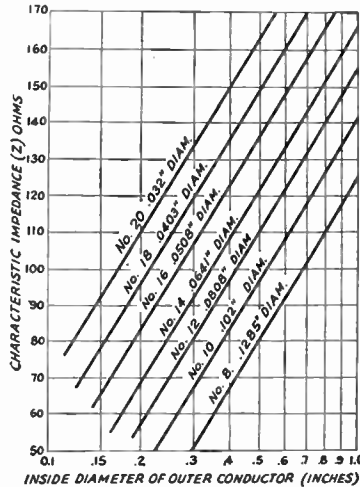


Fig. 10-15 — Chart showing characteristic impedance obtained with various air-insulated concentric lines.

**Losses in Transmission Lines**

There are three ways by which power may be lost in a transmission line: by radiation, by heating of the conductors ( $I^2R$  loss), and by heating of the dielectric, if any. Loss by radiation will occur if the line is unbalanced and, particularly with open-wire lines, may greatly exceed the heat losses. It can be reduced to a minimum by properly terminating the line in a balanced load and by symmetrical, uniform construction.

Heat losses in both the conductor and the dielectric increase with frequency. Conductor losses also are greater the lower the characteristic impedance of the line, because a higher current flows in a low-impedance line for a given power input. The converse is true of dielectric losses because these increase with the voltage, which is greater on high-impedance lines. The dielectric loss in air-insulated lines is negligible (the only loss is in the insulating spacers) and such lines operate at high efficiency when radiation losses are low. In solid-dielectric lines most of the loss is in the dielectric, the conductor losses being small.

It is convenient to express the loss in a transmission line in decibels per unit length, since the loss in db. is directly proportional to the line length. Losses in various types of lines operated without standing waves (that is, terminated in a resistive load equal to the characteristic impedance of the line) are given in Table 10-I. In these figures the radiation loss is assumed to be negligible.

When there are standing waves on the line

the power loss increases as shown in Fig. 10-16. Whether or not the increase in loss is serious depends on what the original loss in watts would have been if the line were perfectly matched. If the line loss with perfect matching is very low, a large standing-wave ratio will not greatly affect the efficiency of the line — that is, the ratio of the power delivered to the load to the power put into the line.

Example: A 150-foot length of RG-11/U cable is operating at 7 Mc. with a 5-to-1 s.w.r. If perfectly matched, the loss from Table 10-I would be  $1.5 \times 0.41 = 0.615$  db. Under these conditions the power delivered to the load would be 86.8% of the power input to the line. If the power input is 100 watts, the line loss is  $100 - 86.8 = 13.2$  watts. From Fig. 10-16, the loss is increased by a factor of 2.6 when the s.w.r. is 5 to 1, so the loss at this s.w.r. is  $2.6 \times 13.2 = 34.3$  watts. Under these conditions the power delivered to the load is  $100 - 34.3 = 65.7$  watts. Therefore,  $65.7/86.8 = 0.757$ , or approximately 76% as much power is delivered to the load with an s.w.r. of 5 as compared with perfect matching. The standing waves therefore cause the output power to be reduced by 1.2 db. (See discussion of the decibel in Chapter Twenty-Four.) With an open-wire line the loss caused by such an s.w.r. would be negligible, provided the line is well balanced to prevent radiation.

An appreciable s.w.r. on a solid-dielectric line may result in excessive loss of power at the higher frequencies. Such lines, whether of the parallel-conductor or coaxial type, should be operated as nearly flat as possible, particularly when the line length is more than 50 feet or so. As shown by Fig. 10-16, the increase in line loss is not too serious so long as the s.w.r. is below 2 to 1, but increases rapidly when the s.w.r. rises above 2.5 or 3 to 1. Tuned transmission lines such as are used with multiband antennas always should be air-insulated, in the interests of highest efficiency.

**Unbalance in Parallel-Conductor Lines**

When installing parallel-conductor lines care should be taken to avoid introducing electrical unbalance into the system. If for some reason the current in one conductor is higher than in the other, or if the currents in the two wires are not exactly out of phase with each other, the electromagnetic fields will not cancel completely and a considerable amount of power may be radiated by the line.

Maintaining good line balance requires, first of all, a balanced load at its end. For this reason the antenna should be fed, whenever possible, at a point where each conductor "sees" exactly the same thing. Usually this means that the antenna system should be fed at its electrical center. Even though the antenna appears to be symmetrical, physically, it can be unbalanced electrically if the part con-

**TABLE 10-I**  
**Transmission-Line Velocity Factors and Attenuation**

Type of Line	Velocity Factor V	** Attenuation, db./100 ft., Mc.						Capacitance per foot $\mu\text{mfd.}$
		3.5	7	14	28	50	144	
Open-wire, 400 to 600 ohms	0.975*	0.03	0.05	0.07	0.1	0.13	0.25	
Parallel-tubing	0.95*	***						
Coaxial, air-insulated	0.85*	0.2	0.28	0.42	0.55	0.7	1.4	
RG-8/U (53 ohms)	0.66	0.28	0.42	0.64	1.0	1.4	2.6	29.5
RG-58/U (53 ohms)	0.66	0.53	0.8	1.2	1.9	2.7	5.1	28.5
RG-11/U (75 ohms)	0.66	0.27	0.41	0.61	0.92	1.3	2.4	20.5
Twin-Lead, 300 ohms	0.82	0.18	0.3	0.5	0.84	1.3	2.8	5.8
Twin-Lead, 150 ohms	0.77	0.2	0.35	0.6	1.0	1.6	3.5	10
Twin-Lead, 75 ohms	0.68	0.37	0.64	1.1	1.9	3.0	6.8	19
Transmitting Twin-Lead, 75 ohms	0.71	0.29	0.49	0.82	1.4	2.1	4.8	
Rubber-insulated twisted-pair or coaxial ****	0.56 to 0.65	0.96	1.6	2.5	4.2	6.2	13	

\* Average figures for air-insulated lines taking into account effect of insulating spacers.  
 \*\* For lines terminated in characteristic impedance.  
 \*\*\* Losses between open-wire line and air-insulated coaxial cable. Actual loss with both open-wire and parallel-tubing lines is higher than listed because of radiation, especially at higher frequencies.  
 \*\*\*\* Approximate figures for good-quality rubber insulation.

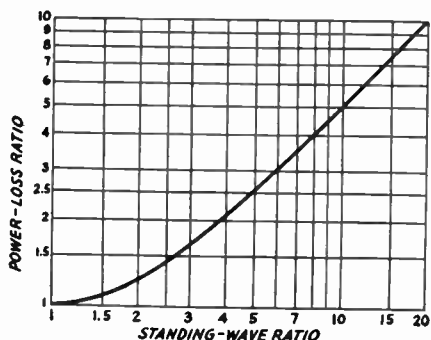


Fig. 10-16 — Effect of standing-wave ratio on line loss. The power-loss ratio given by the curve, multiplied by the power that would be lost in the same line if perfectly matched, gives the actual power lost in the line when standing waves are present.

nected to one of the line conductors is inadvertently coupled to something (such as house wiring or a metal pole or roof) that is

not duplicated on the other part of the antenna. Every effort should be made to keep the antenna as far as possible from other wiring or sizeable metallic objects. The transmission line itself will cause some unbalance if it is not brought away from the antenna at right angles to it for a distance of at least a quarter wavelength.

In installing the line conductors take care to see that they are kept away from metal. The minimum separation between either conductor and all other wiring should be at least four or five times the conductor spacing. The shunt capacitance introduced by close proximity to metallic objects can drain off enough current (to ground) to unbalance the line currents, resulting in increased radiation. A shunt capacitance of this sort also constitutes a reactive load on the line, causing an impedance "bump" that will prevent making the line actually flat.

## Coupling the Transmitter to the Line

In very general terms, the problem of coupling the transmission line and transmitter together is one of transforming the input impedance of the line into a value of impedance that will "load" the transmitter properly — that is, cause it to deliver the desired power output at as high efficiency as the transmitter design will permit. This is a question of impedance matching, and the impedance that must be matched is the value of resistance into which the tubes in the final stage of the transmitter should work. The value of this resistance is determined by the choice of tube operating conditions. The tubes are working into the proper resistance when the final tank circuit is tuned to resonance and the loading is such that the tubes are drawing rated plate current, as described in Chapter Six. The proper value of load resistance is thus reached automatically when the coupling is adjusted to bring the plate current up to the normal operating value. It is therefore not at all necessary to know what value of resistance is required. It is sufficient to note that, in general, it is in the neighborhood of a few thousand ohms, and is higher the higher the plate-voltage/plate-current ratio of the final stage.

The input impedance of the line can assume a wide range of values. As described earlier, it may be very much higher or very much lower than the impedance of the load at the end of the line, unless the line is matched to the load. Furthermore, it may or may not be a pure resistance, depending on the s.w.r., the line length, and the characteristics of the load.

### Transforming Impedances

It was explained in Chapter Two that a resistive load tapped across part of a tuned circuit is equivalent to a higher value of resistance connected in parallel with the whole circuit. In other words, there is a transformer action in such an arrangement that enables us to change the value of a given resistance, such as  $R$  in Fig. 10-17A, into a new and higher value when the source of power looks into the terminals  $AB$ . Given reasonable values for  $L$  and  $C$ , the resistance looking into  $AB$  is determined practically wholly by the value of  $R$  and the position of the tap, so long as  $LC$  is tuned to resonance with the applied frequency. This is because the resonant impedance of  $LC$  alone (with  $R$  disconnected) is usually very high

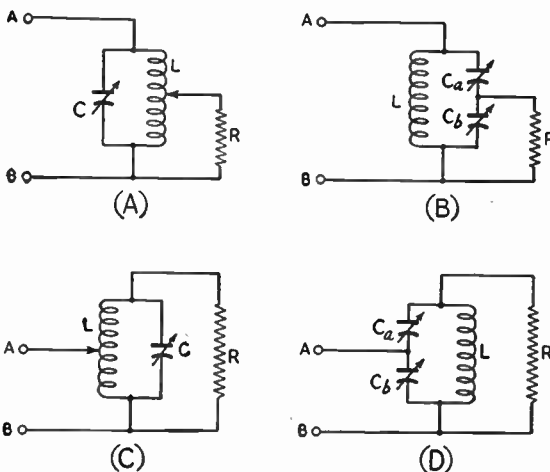


Fig. 10-17 — Using a resonant circuit for matching impedances.

compared with the resistance,  $R$ , of any practical load likely to be used, and also compared with any resistance that might be required between the terminals  $AB$ .

Fig. 10-17B shows a circuit that also provides a method for impedance transformation, using a capacitance voltage divider instead of tapping on the inductance. In this case, decreasing the capacitance of  $C_b$  (while increas-

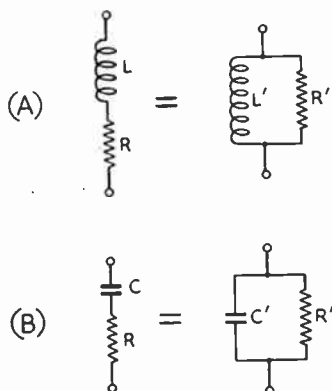


Fig. 10-18 — Series and parallel equivalents of a line whose input impedance has both reactive and resistive components.

ing the capacitance of  $C_a$  correspondingly to maintain resonance) has the same effect as moving the tap toward the top of the coil in Fig. 10-17A. This type of circuit gives very smooth control. However, variable condensers of impracticable size would be necessary, to give as wide a range of impedance transformation as the circuit at A.

When an r.f. amplifier is coupled to a transmission line the line impedance very seldom is larger than the load impedance required by the amplifier. However, should such a case arise the same circuits can be used by reversing the terminals. This is shown at C and D in Fig. 10-17. With  $R$  connected across the whole circuit, its resistance can be transformed to a lower value when the input terminals are tapped across part of the coil, as at A, or across  $C_b$  in Fig. 10-17B. The nearer the tap is to the bottom end of the coil, or the larger the capacitance of  $C_b$  compared with  $C_a$ , the smaller the resistance between terminals  $AB$ .

#### Complex Loads

In the foregoing it was assumed that the load,  $R$ , was a pure resistance. However, the input impedance of a line is more likely than not to have a reactive as well as a resistive component. This means, basically, that the current flowing into the line is not in phase with the voltage applied to the line. To represent such a condition by circuit symbols we can assume the input impedance of the line to consist either of a reactance (coil or condenser) in series with a resistance, or a

reactance in parallel with a resistance. It does not matter which we choose, so long as the values assigned to the resistance and reactance are such that if the voltage were applied to the circuit instead of to the line, the current that flows would have exactly the same amplitude and phase angle as it actually does at the input terminals of the line.

These equivalent circuits are shown in Fig. 10-18. In practical work with lines it is not necessary to know the values of  $R$ ,  $L$  or  $C$ . It is sufficient to know that they *symbolize* a condition that exists at the input end of the line — and then to know what to do about them. A few general points are worth noting: Given a fixed value of voltage, if the current at the input end of the line is high, then the impedance is relatively low; if the current is low, the impedance is relatively high. If the current is very nearly in phase with the voltage the reactance in the *series* equivalent circuit is small, but the reactance in the *parallel* equivalent circuit is large. On the other hand, if there is a considerable phase difference between current and voltage the reactance is large in the equivalent series circuit and is low in the equivalent parallel circuit. (In visualizing these reactances as coils and condensers it must be remembered that “large” and “small” are relative terms; for example, a “large” inductance at 28 Mc. would be a “small” inductance at 3.5 Mc. Also, the larger the capacitance of a condenser the smaller its reactance.)

Now suppose that a reactive line is to be connected to our impedance-transforming resonant circuit. Let us choose the parallel equivalent circuit, since it is somewhat easier to picture what happens. Fig. 10-19A shows a load with inductive reactance tapped across part of the resonant circuit (corresponding to Fig. 10-17A), and a load with capacitive reactance is shown in Fig. 10-19B. Imagine for the moment that the load has only reactance; the resistive component,  $R$ , is disconnected. Then, just as in the pure-resistance case previously

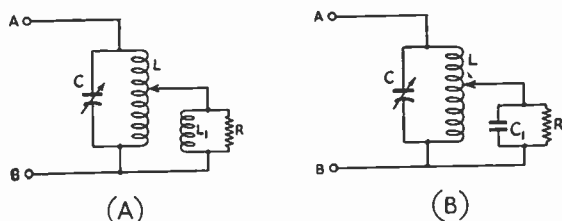


Fig. 10-19 — Circuit equivalent of a reactive line connected to a resonant circuit for impedance matching.

discussed, a small reactance tapped across the coil  $L$  will appear as a larger reactance across the whole circuit, or between the input terminals  $AB$ . Thus, connecting a coil,  $L_1$ , across part of  $L$  is equivalent to connecting a larger coil across the whole circuit. Connecting a condenser,  $C_1$ , across part of  $L$  is equivalent to connecting a *smaller* condenser (larger reactance) across the whole circuit.

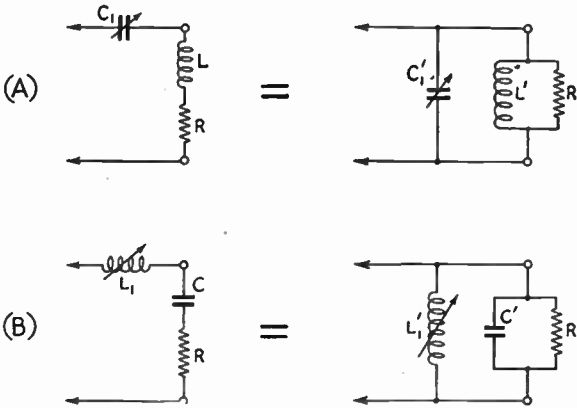


Fig. 10-20 — Methods for canceling the reactive component of the input impedance of a transmission line. In A the line input impedance is represented by  $L$  and  $R$  in series, or by  $L'$  and  $R'$  in parallel, and in B by  $C$  and  $R$  in series, or by  $C'$  and  $R'$  in parallel.

In either case this equivalent shunting reactance detunes the  $LC$  circuit from resonance, and  $C$  must be readjusted to bring it back. In the case of Fig. 10-19A, the capacitance of  $C$  must be increased because the "reflected" reactance in parallel with  $L$  decreases the total inductance (inductances in parallel) and so tunes the circuit to a higher frequency. The opposite is the case in Fig. 10-19B; the shunting reactance is capacitive and increases the total capacitance. Consequently the capacitance of  $C$  must be decreased to bring the circuit back to resonance.

The over-all effect, then, of coupling a reactive load to the circuit is to cause detuning as well as to cause the desired resistance loading. If the reflected reactance is large, corresponding to connecting a very large coil or a very small condenser across the whole  $LC$  circuit, it is readily possible to retune the circuit to resonance by adjusting  $C$ . The nearer the tap to the top end of  $L$ , the greater the change required in the tuning. But this simple method of compensating for the reactive component of the load is not always sufficient. In some cases the tap has to be moved so far up the coil, in order to obtain the right value of resistance loading, that the tuning condenser,  $C$ , no longer has sufficient range to compensate for the reflected reactance. When such a condition exists it is difficult, and sometimes impossible, to couple the desired amount of power to the transmission line.

**Canceling Line Reactance**

The remedy for this condition is to make the input end of the line look like a pure resistance before it is tapped on the impedance-transforming circuit. This can be done by "tuning out" the reactance of the line, by inserting a reactance of the same value but of the opposite kind. Again we have our choice between considering the line to be represented by react-

ance and resistance in series, or by reactance and resistance in parallel. The circuits are shown in Fig. 10-20. In A, a condenser,  $C_1$ , is used to cancel out the inductive reactance of the line, and in B an inductance,  $L_1$ , is used to cancel capacitive reactance. The same value of capacitance cannot be used for  $C_1$  and  $C_1'$  under a given set of conditions because, as explained earlier,  $L$  and  $L'$  do not have the same values. For example, if  $L$  is small its parallel equivalent,  $L'$ , is large, so a large capacitance would be required at  $C_1$  and a small capacitance at  $C_1'$ . Because of limitations in practicable components (particularly in the capacitance range of variable condensers), there are conditions where the series circuit is the easiest to set up, from a practical standpoint. In others, the parallel circuit is easier

to get working. For the large majority of cases either circuit will work equally well; from the standpoint of convenience, the parallel circuit is probably better.

To summarize, then, we have three general cases as shown in Fig. 10-21. If the line is purely resistive, or so nearly so that such reactance as is reflected across the  $LC$  circuit can be tuned out by readjusting  $C$ , the circuit at A may be used. Where the line shows more pronounced reactive effects, the line reactance can be tuned out, as indicated at B and C, so that the load tapped on  $L$  is purely resistive. It is easy to tell which should be used, inductance or capacitance, to compensate for the line reactance. If the line only (Fig. 10-21A)

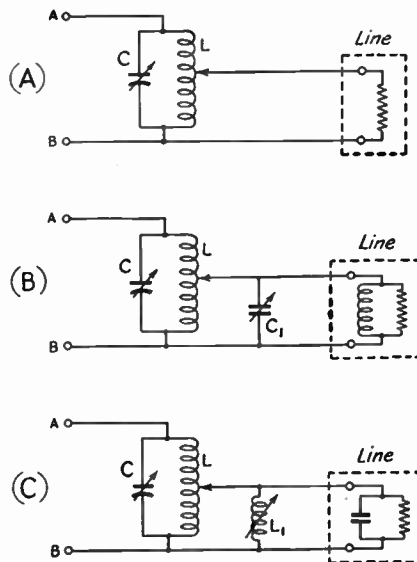


Fig. 10-21 — Methods of canceling line input reactance combined with impedance transformation.

is tapped across a very small portion of  $L$ ,  $C$  will have to be readjusted slightly to bring the  $LC$  circuit back to resonance. If the capacitance of  $C$  has to be increased, a condenser,  $C_1$ , should be connected across the input terminals of the line. If the capacitance of  $C$  has to be decreased, an inductance,  $L_1$ , should be connected across the line. In either case the compensating reactance,  $C_1$  or  $L_1$ , should be adjusted in value until the setting of  $C$ , for resonance with the applied frequency, is the same whether or not the line is tapped on  $L$ . When this condition is reached the loading may be adjusted by changing the tap position until the amplifier takes the desired plate current.

### ● PRACTICAL COUPLING SYSTEMS

In practical work the two primary functions that a coupling system must perform — tuning out the line reactance, if any, and providing a method for control of loading on the transmitter — are not always enough. For one thing, it is desirable that the coupling system be such that the transmission line will operate only in the way it is intended that it should. For another, the coupling system should prevent transfer of any of the harmonic energy that always is present in the output of a transmitting amplifier. Both these points will be considered later in this section. For the moment, let us take a look at some of the simpler coupling systems.

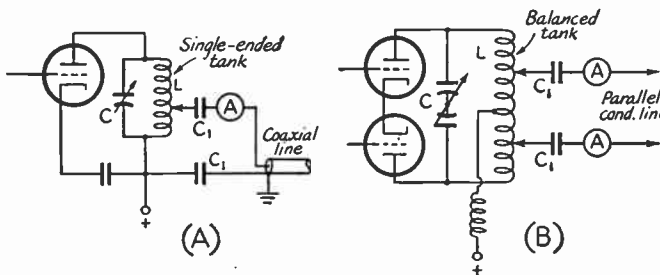


Fig. 10-22 — Simple methods of coupling to a transmission line. The blocking condensers,  $C_1$ , should be 0.001- $\mu$ fd. (or larger) mica condensers having a voltage rating in excess of the maximum d.c. voltage applied to the final amplifier (including the voltage applied on modulation up-peaks). The coaxial line can be coupled to a balanced tank circuit by connecting the grounded shield to the center of the coil (through a blocking condenser) and tapping the inner conductor on one side of the center. The parallel-conductor line requires a balanced tank circuit.

The possibility of tapping the input end of the transmission line directly on the final-amplifier tank suggests itself from the discussion earlier. This method will work when the input impedance of the line is purely resistive, or nearly so. It can therefore be used with nonresonant or untuned lines, or with a resonant line when the line has the right length. As explained earlier, the input impedance of the line will be resistive when its length is a multiple of a quarter wavelength, provided the load at the output end of the line is a pure

resistance. This will be so if the antenna itself is resonant, but will not be true if the antenna length is not correct for the operating frequency. The circuits are shown in Fig. 10-22. If the final amplifier is series-fed so that the tank circuit is "hot" with the plate voltage, it is necessary to connect a blocking condenser between the tank and the line. These circuits, although simple, are not recommended except perhaps in emergencies; there is little or no discrimination against harmonic frequencies.

Adjustment of this type of coupling is simple. First, resonate the amplifier tank circuit, with the line disconnected, by setting the tank condenser,  $C$ , to the minimum plate current point. Then tap the line across a turn or two of the tank coil, and readjust  $C$  for minimum plate current. The new minimum will be higher than with no load on the tank. Continue increasing the number of turns between the line taps, readjusting  $C$  each time, until the minimum plate current is the desired full-load value.

### R.F. Ammeters

The r.f. ammeters shown in Fig. 10-22 and subsequent coupling circuits are useful accessories. The input impedance of the line is unaffected by any adjustments made in the coupling system (except for the effects of stray capacitance, as discussed later) so the greater the current flowing into the line the larger the amount of power delivered to the load. Measurement of r.f. current thus gives a check on the adjustment procedure and indicates when the largest power output is being obtained. Obviously, an adjustment that increases the input to the final stage of the transmitter without causing the line current to increase has simply increased the losses without increasing the output.

In the case of parallel-conductor lines two ammeters are shown, one in each conductor. This gives a check on line balance, since the two currents should be the same. It is not actually necessary to use two instruments; one ammeter can be switched from one side of the line to the other for comparative measurements. Also, it is to be understood that any current-indicating device (such as a flashlight lamp) that will work at r.f. may be used as a substitute for an actual ammeter.

The scale range required depends on the input impedance of the line and the power. The current to be expected can readily be calculated from Ohm's Law when the line is flat. In other cases the s.w.r. and the length of the line must be considered. The maximum current



will occur when there is a current loop at the input end of the line, and if the load impedance and line impedance are known the input impedance at a current loop can be calculated from the formulas given earlier.

The ammeters are less useful when the input impedance of the line is high, because in that case the input current is quite small. It is to be noted that the value of current does not indicate, in any absolute sense, how well the system as a whole is working unless the actual value of the resistance component of the line input impedance is known. Current measurements taken on different lines, or on the same line if its length in wavelengths is changed, are not directly comparable.

### Inductive Coupling

The circuits shown in Fig. 10-23, like those in Fig. 10-22, are useful only with lines having purely-resistive input impedance. The pick-up coil, which is inductively-coupled to the tank coil, is in fact simply a substitute for the tapped portion of the tank coil in Fig. 10-22. The number of turns required in the pick-up coil depends upon the resistance represented by the input end of the line. For flat lines, the number is governed by the characteristic impedance of the line. For 50- or 70-ohm lines it may range from one or two turns, at frequencies of the order of 14 to 28 Mc., to several turns at 3.5 Mc. For higher-impedance lines it may take half as many turns as there are in the tank coil, to get adequate coupling. In both cases the coupling between the coils will have to be very tight. The link windings provided on commercial coils are not usually adequate for this type of coupling except for low-impedance lines at the higher frequencies. When the number of turns on the pick-up coil is fixed, the loading on the final amplifier can be varied by varying the coupling between the two coils. Inductive coupling of this type is somewhat better than direct coupling from the standpoint of harmonic transfer.

Pick-up coil coupling introduces some reactance into the tank circuit, because of the leakage reactance of the coupling coil. This must be compensated for by retuning the final tank circuit when the desired degree of coupling is reached. If very much retuning is required, or if the amplifier loads with loose coupling between the two coils, it is an excellent indication that the line is not actually flat.

When a "swinging-link" assembly is used to obtain this type of coupling, the loading on the final amplifier can be adjusted to the desired value by varying the coupling between the two coils. The tank condenser,  $C$ , should be readjusted to minimum plate current each time the coupling is changed. If the desired loading cannot be obtained there is no alternative but to use a different coupling system.

The pick-up coil may be wound directly over the final tank coil, in which case the correct number of turns may be determined by

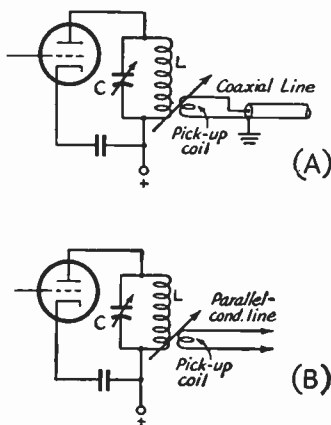


Fig. 10-23 — Using an untuned pick-up coil to couple to a transmission line. The method of adjustment is discussed in the text.

trial. The insulation between the coils must be adequate for the plate voltage used, if the amplifier is series-fed.

### Series and Parallel Tuning

The circuits shown in Fig. 10-24 are useful with parallel-conductor lines operating at a relatively-high standing-wave ratio, particularly when the line length is such as to make the input impedance substantially a pure resistance. Assuming that the antenna is resonant, the optimum line lengths will be multiples of a quarter wavelength at the operating frequency. When the s.w.r. is high, the impedance at such points is considerably higher or considerably lower than the characteristic impedance of the line.

In these circuits the secondary, consisting of  $L_1$ ,  $C_1$  (and  $C_2$ , in the series circuit) and the input impedance of the line, is tuned to the operating frequency. As explained in Chapter Two, the degree of coupling between two resonant circuits is determined by their  $Q$ 's, and it is necessary to keep the  $Q$ 's fairly high (of the order of 10 or so). Assuming that the input impedance of the line is purely resistive, it can be inserted in series with the circuit (as in A) if its value is below about 100 ohms. The  $Q$  of the secondary circuit then can be brought to the proper value by making the reactance of  $L_1$  of the order of 500 to 1000 ohms and setting the total capacitance of  $C_1$  and  $C_2$  to tune the circuit to resonance. With this type of tuning the current flowing into the line is rather large; in other words, the system is suitable for coupling into the line at a current loop.

On the other hand, if the line impedance is of the order of a few thousand ohms or more — which it will be at a voltage loop when the s.w.r. is high — the secondary circuit cannot be made to take power from the transmitter if the line resistance is inserted in series. The  $Q$  of the secondary circuit would be far too low to give adequate coupling. In such a case the parallel-tuned circuit at B may be used. As ex-

mitter. To take care of cases where the input impedance of the line has a considerable reactive component, provision is made for switching in either a shunt capacitance or inductance, both of which are variable (see earlier discussion). The coupling should be variable at least at one end of the link circuit.

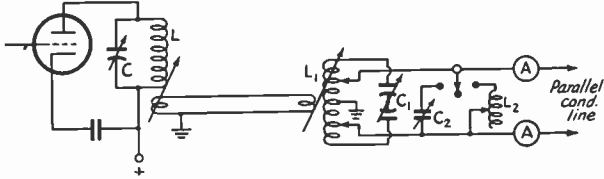


Fig. 10-26 — "Universal" antenna-coupling system. This circuit can be used with both resonant and nonresonant parallel-conductor lines.

In general, it is advisable to make the inductance of  $L_1$  about the same as that of  $L$ , and to use for  $C_1$  a condenser of the same capacitance as that used for  $C$ . The voltage rating for  $C_1$  also should be the same as that of  $C$ . In other words,  $L_1C_1$  may be a duplicate of  $LC$  for the operating frequency in use. The link coils can consist of two or three turns at each end. Provision should be made for tapping  $L_1$  at frequent intervals — every turn, if possible.  $C_2$  should have as large a maximum capacitance as is convenient — 250 to 500  $\mu\text{mfd}$ . — but its voltage rating need not be high in the average case. For most installations where the power output does not exceed a few hundred watts a plate spacing of the order of 0.025 to 0.05 inch is sufficient. The inductance  $L_2$  can consist of 20 or 25 turns approximately 2 inches in diameter and spaced 8 to 10 turns to the inch. The coil should be tapped every few turns.

The tuning procedure is as follows: First, disconnect the feeder taps on  $L_1$  and use the loosest possible coupling, through the variable link coupling, to the final tank circuit. Tune  $C_1$  until the plate current rises to a peak, indicating that  $L_1C_1$  is resonated, and note the setting of  $C_1$ . Cut  $C_2$  and  $L_2$  out of the circuit and then connect the line taps across a turn or two at the center of  $L_1$ . Readjust  $C_1$  to resonance, as indicated by a rise in plate current. It should be necessary to use closer coupling to get an observable change in plate current with the line connected. Note the new setting of  $C_1$ . If the capacitance is lower, switch in  $L_2$  and find the tap that permits returning  $C_1$  as nearly as possible to its original setting; if the capacitance is higher, switch in  $C_2$  and adjust it to bring  $C_1$  back to the original setting. Then increase the coupling, keeping  $C_1$  at resonance as indicated by maximum plate current, and keeping  $C$  at resonance as indicated by minimum plate current. Continue until the minimum plate current reaches the desired load value. If  $C_1$  flashes over as the coupling is increased, or if tuning  $C_1$  back and forth a small amount either side of resonance makes it

necessary to change the setting of  $C$  appreciably to maintain the final tank in resonance, the taps on  $L_1$  are too close together. Move each tap one turn toward the ends of  $L_1$ , and again try increasing the coupling for rated load on the amplifier. When the proper loading is obtained, the tuning of  $L_1C_1$  will be reasonably sharp, and changing the coupling will not necessitate more than "touching up"  $C$  to maintain resonance. If the taps on  $L_1$  are too far apart the antenna tank circuit,  $L_1C_1$ , will be loaded heavily and its tuning will be broad. Under these conditions it may also be impossible to load the amplifier to rated plate current, even with the tightest available coupling. On the other hand, if

the taps on  $L_1$  are too close together the antenna tank will be too lightly loaded; its tuning will be critical and will affect the tuning of the plate tank circuit to a marked degree, and  $L_1$  may overheat when the coupling is adjusted to make the amplifier take normal input.

When the reactive effects at the input end of the line are small, neither  $C_2$  nor  $L_2$  will be required. When this is the case, the setting of  $C_1$  for resonance will not change much when the line is tapped on  $L_1$ . The greater the number of turns between the taps, the greater the detuning of the antenna tank by a given amount of reactance in the transmission-line input impedance.

This coupling system is equally effective with flat lines or those operating at a high s.w.r. If the line is actually flat,  $C_2$  and  $L_2$  will not be needed and the resonance setting of  $C_1$  will not be affected by connecting the line. Regardless of the s.w.r., the positions of the line taps will depend on the resistive component of the line input impedance. If the resistance is low, the taps will be close together; if it is very high, the taps may have to be set right at the ends of  $L_1$ .

#### Coupling to Coaxial Lines

The principles of coupling to coaxial lines are just the same as for coupling to parallel-conductor lines. However, this type of line is unbalanced to ground, has inherently low impedance, and always should be operated with a low standing-wave ratio. The input impedance of a properly-operated coaxial transmission line therefore will be principally resistive, and of a value varying between perhaps 30 to 100 ohms, depending on the type of line and the s.w.r.

It is possible to couple such a line by means of a small coil inductively coupled to the final tank coil, as shown in Fig. 10-23A. The small amount of reactance introduced by the pick-up coil — and by the line, if the s.w.r. is slightly greater than 1 — can readily be tuned out by adjustment of the final tank condenser. However, additional selectivity is desirable for the

Two condensers are used in the series-tuned circuit in order to keep the line balanced to ground. This is because two identical condensers, both connected with either their stators or rotors to the line, will have the same capacitance to ground. A single condenser will slightly unbalance the circuit, since the frame has more capacitance to ground than the stator, but the unbalance is not serious unless the condenser is mounted near a large mass of metal, such as a chassis.

### Adjustment of Parallel Tuning

Coupling and tuning adjustments with parallel tuning are carried out in much the same way as with series tuning. There is only one condenser to adjust, of course. Start with very loose coupling between  $L$  and  $L_1$ , resonate the secondary circuit by adjusting  $C_1$  to make the final-amplifier plate current rise, then readjust  $C$  for minimum plate current. Increase the coupling in small steps, reresonating  $C_1$  and  $C$  each time, until the desired loading is obtained.

Just as in the case of series tuning, it should be possible to tune through resonance with  $C_1$ . If the resonant point is at either maximum or minimum capacitance on  $C_1$ , change the number of turns on  $L_1$  to bring the resonant point well on the condenser scale. In general,  $L_1$  and  $C_1$  will have about the same values as  $L$  and  $C$ , respectively, when the input impedance of the line is purely resistive. If the line shows reactance, the reactance can be tuned out, within limits, by adjustment of  $C_1$  and, if necessary, by changing the number of turns on  $L_1$  to achieve a combination that will permit the secondary circuit to resonate at the operating frequency.

If the input resistance of the line is very high, the secondary circuit will tune quite sharply. On the other hand, if the input resistance is relatively low the tuning will be broad and the resonance point will not be well marked. In such a case the number of turns in  $L_1$  should be reduced and the capacitance of  $C_1$  increased, to increase the  $Q$  of the circuit. This will permit power transfer with relatively loose coupling between  $L$  and  $L_1$ . Should it not be possible to load the transmitter properly with any combination of  $L_1$  and  $C_1$ , the input resistance of the line is too low for parallel tuning.

In the parallel-tuned circuit  $C_1$  is shown as a balanced or split-stator condenser. This type of condenser is used so that the system will be balanced to ground for stray capacitances. This is particularly desirable in the case of parallel tuning, because the voltage at the input end of the line is high, causing a relatively large current to flow through a small stray capacitance. An alternative scheme to maintain balance is to use two single-ended condensers in parallel, but with the frame of one connected to one side of the line and the

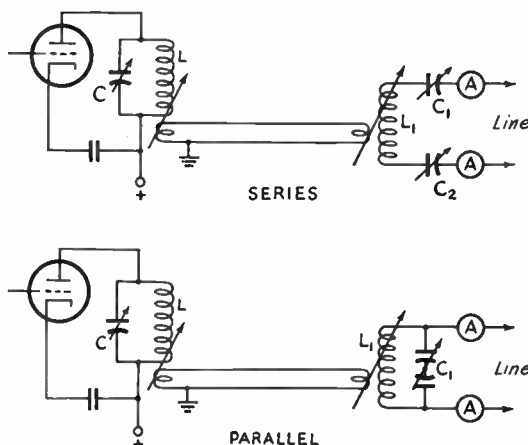


Fig. 10-25 — Link-coupled series and parallel tuning.

frame of the other connected to the other side of the line. The same two condensers may be switched in series, as in Fig. 10-24A, when series tuning is to be used.

### Link Coupling

The circuits shown in Fig. 10-24 require a means for varying the coupling between two sizable coils, a thing that is somewhat inconvenient constructionally. It is easier to use separate fixed mountings for the final tank and antenna coils and couple them by means of a link. As explained in Chapter Two, a short length of link line is equivalent to providing mutual inductance between two tuned circuits. Typical arrangements for series and parallel tuning are shown in Fig. 10-25. Although these drawings show variable coupling at both ends of the link circuit, a fixed link can be used at either end so long as a variable link is used at the other.

There is no essential difference between the tuning procedures with these circuits and those of Fig. 10-24. The only change is that the coupling is adjusted by means of a link instead of by varying the spacing between  $L$  and  $L_1$ .

### "Universal" Antenna Couplers

An antenna-coupling system that is adaptable to a wide range of line input impedances can be constructed on the basis of the coupling principles described earlier. Combined with link coupling to the final tank circuit and provision for tuning out the input reactance of the line, such a system is suitable for working into either resonant or nonresonant lines, and introduces additional selectivity into the coupling system that helps discriminate against harmonics.

The circuit diagram is given in Fig. 10-26. The final tank is coupled to a second tuned circuit,  $L_1C_1$ , through a link. Taps are provided on  $L_1$  so that the resistive component of the line impedance can be matched to the trans-

mitter. To take care of cases where the input impedance of the line has a considerable reactive component, provision is made for switching in either a shunt capacitance or inductance, both of which are variable (see earlier discussion). The coupling should be variable at least at one end of the link circuit.

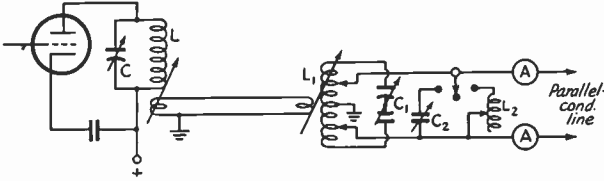


Fig. 10-26 — "Universal" antenna-coupling system. This circuit can be used with both resonant and nonresonant parallel-conductor lines.

In general, it is advisable to make the inductance of  $L_1$  about the same as that of  $L$ , and to use for  $C_1$  a condenser of the same capacitance as that used for  $C$ . The voltage rating for  $C_1$  also should be the same as that of  $C$ . In other words,  $L_1C_1$  may be a duplicate of  $LC$  for the operating frequency in use. The link coils can consist of two or three turns at each end. Provision should be made for tapping  $L_1$  at frequent intervals — every turn, if possible.  $C_2$  should have as large a maximum capacitance as is convenient — 250 to 500  $\mu\text{fd}$ . — but its voltage rating need not be high in the average case. For most installations where the power output does not exceed a few hundred watts a plate spacing of the order of 0.025 to 0.05 inch is sufficient. The inductance  $L_2$  can consist of 20 or 25 turns approximately 2 inches in diameter and spaced 8 to 10 turns to the inch. The coil should be tapped every few turns.

The tuning procedure is as follows: First, disconnect the feeder taps on  $L_1$  and use the loosest possible coupling, through the variable link coupling, to the final tank circuit. Tune  $C_1$  until the plate current rises to a peak, indicating that  $L_1C_1$  is resonated, and note the setting of  $C_1$ . Cut  $C_2$  and  $L_2$  out of the circuit and then connect the line taps across a turn or two at the center of  $L_1$ . Readjust  $C_1$  to resonance, as indicated by a rise in plate current. It should be necessary to use closer coupling to get an observable change in plate current with the line connected. Note the new setting of  $C_1$ . If the capacitance is lower, switch in  $L_2$  and find the tap that permits returning  $C_1$  as nearly as possible to its original setting; if the capacitance is higher, switch in  $C_2$  and adjust it to bring  $C_1$  back to the original setting. Then increase the coupling, keeping  $C_1$  at resonance as indicated by maximum plate current, and keeping  $C$  at resonance as indicated by minimum plate current. Continue until the minimum plate current reaches the desired load value. If  $C_1$  flashes over as the coupling is increased, or if tuning  $C_1$  back and forth a small amount either side of resonance makes it

necessary to change the setting of  $C$  appreciably to maintain the final tank in resonance, the taps on  $L_1$  are too close together. Move each tap one turn toward the ends of  $L_1$ , and again try increasing the coupling for rated load on the amplifier. When the proper loading is obtained, the tuning of  $L_1C_1$  will be reasonably sharp, and changing the coupling will not necessitate more than "touching up"  $C$  to maintain resonance. If the taps on  $L_1$  are too far apart the antenna tank circuit,  $L_1C_1$ , will be loaded heavily and its tuning will be broad. Under these conditions it may also be impossible to load the amplifier to rated plate current, even with the tightest available coupling. On the other hand, if

the taps on  $L_1$  are too close together the antenna tank will be too lightly loaded; its tuning will be critical and will affect the tuning of the plate tank circuit to a marked degree, and  $L_1$  may overheat when the coupling is adjusted to make the amplifier take normal input.

When the reactive effects at the input end of the line are small, neither  $C_2$  nor  $L_2$  will be required. When this is the case, the setting of  $C_1$  for resonance will not change much when the line is tapped on  $L_1$ . The greater the number of turns between the taps, the greater the detuning of the antenna tank by a given amount of reactance in the transmission-line input impedance.

This coupling system is equally effective with flat lines or those operating at a high s.w.r. If the line is actually flat,  $C_2$  and  $L_2$  will not be needed and the resonance setting of  $C_1$  will not be affected by connecting the line. Regardless of the s.w.r., the positions of the line taps will depend on the resistive component of the line input impedance. If the resistance is low, the taps will be close together; if it is very high, the taps may have to be set right at the ends of  $L_1$ .

#### Coupling to Coaxial Lines

The principles of coupling to coaxial lines are just the same as for coupling to parallel-conductor lines. However, this type of line is unbalanced to ground, has inherently low impedance, and always should be operated with a low standing-wave ratio. The input impedance of a properly-operated coaxial transmission line therefore will be principally resistive, and of a value varying between perhaps 30 to 100 ohms, depending on the type of line and the s.w.r.

It is possible to couple such a line by means of a small coil inductively coupled to the final tank coil, as shown in Fig. 10-23A. The small amount of reactance introduced by the pick-up coil — and by the line, if the s.w.r. is slightly greater than 1 — can readily be tuned out by adjustment of the final tank condenser. However, additional selectivity is desirable for the

purpose of reducing harmonic transfer from the final tank. Circuits are shown in Fig. 10-27. Except that it is adapted for single-ended rather than balanced operation, the circuit at A operates in much the same way as the circuit in Fig. 10-26. Also, because the load is known to be in the region of 100 ohms or less, it is possible to tap it across a capacitance voltage divider (see earlier discussion) for impedance matching. This avoids the necessity for tapping  $L_1$ .

The circuit of Fig. 10-27B is similar in operation to that at A, but dispenses with the link circuit. For convenience, it uses a link coil on the final tank for inductive transfer of energy, the rest of the inductance in the antenna tank circuit being made up by  $L_1$ .

In the circuit at A,  $L_1$  may be the same as  $L$ ; in B,  $L_1$  plus the pick-up coil should have about the same inductance as  $L$ . Except at perhaps 28 Mc., it is satisfactory, practically, to make  $L_1$  the same as  $L$  in this circuit also, since the pick-up coil will not ordinarily have much inductance itself. In both circuits  $C_2$  should have about the same capacitance as  $C$ , and  $C_1$  should have approximately the value suggested in Fig. 10-27.

To adjust the circuit, set  $C_1$  at maximum, loosen the coupling between  $L$  and the link or pick-up coil, and tune  $C_2$  to resonance. This will be indicated, as usual, by a rise in the amplifier plate current. Adjust  $C$  to minimum plate current and increase the coupling in small steps, re-resonating  $C_2$  and  $C$  each time, until the amplifier plate current is normal. The loading on the antenna tank circuit is least when  $C_1$  is at maximum capacitance, and increases when the capacitance of  $C_1$  is decreased (with  $C_2$  increased correspondingly to maintain resonance). The symptoms of under- and over-loading of the antenna tank are the

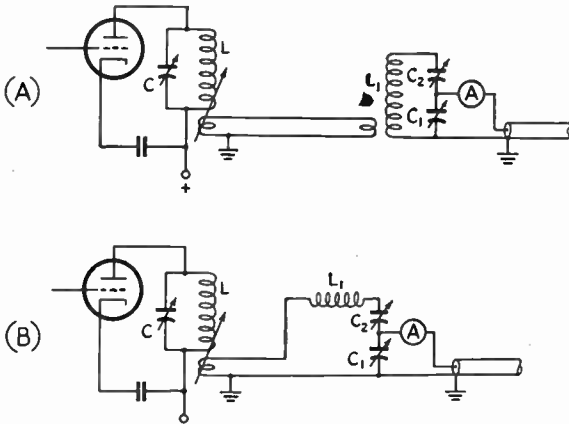


Fig. 10-27 — Coupling to coaxial lines. These circuits are used for harmonic suppression when working into a nonresonant coaxial line. Recommended capacitance values for  $C_1$  are as follows: 28 Mc., 100  $\mu\text{fd.}$ ; 14 Mc., 200  $\mu\text{fd.}$ ; 7 Mc., 400  $\mu\text{fd.}$ ; 3.5 Mc., 800  $\mu\text{fd.}$

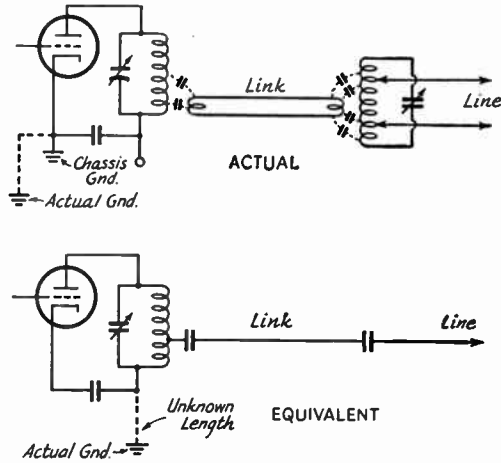


Fig. 10-28 — The stray capacitive coupling between coils in the upper circuit leads to the equivalent circuit shown below. The effect on the performance of the antenna system is discussed in the text.

same as described in connection with the universal antenna coupler. Adjust the loading by means of  $C_1$ , so that at normal plate input the antenna tank tuning is reasonably sharp and the setting of  $C$  is not greatly affected when  $C_2$  is tuned a small amount either side of resonance.

**Stray Coupling**

In most of the circuits in Figs. 10-22 to 10-27, inclusive, a single-ended tank circuit has been indicated for the final amplifier. The amplifier itself has been shown only sketchily. The fact is that any type of antenna coupling circuit can be used with any type of amplifier — screen grid or neutralized triode, single-ended or push-pull. However, the actual arrangement, physically, of the circuit elements usually has an important bearing on the performance of the system. As it happens, a coupling system that is poorly designed, constructionally speaking, usually will do what it is supposed to do. But, equally important, it may do a lot of things it is not supposed to do.

Most of the unwanted effects that occur on transmission lines can be traced to stray capacitances in the system. Fig. 10-28 is an illustration. The upper drawing shows the ordinary link-coupled system as it might be used to couple into a parallel-conductor line. Inasmuch as a coil is a sizeable metallic object, it will have capacitance to any other metallic objects in its vicinity, including other coils. Consequently there is capacitance between the final tank coil and its associated link coil, and between the antenna tank coil and its link. These capacitances

are small, but not negligible. In addition, the transmitter, particularly with metal-chassis construction, has appreciable capacitance to ground. Even if it did not, there is always a path from the transmitter to ground through the power wiring and the many stray capacitances associated with it.

There is a fundamental difference between the inductive coupling between coils and the capacitive coupling between them. Inductive coupling induces a voltage in the secondary coil that causes a current to flow, in common terminology, "around" the circuit. In Fig. 10-28, this means that the same current flows in both conductors of the link but, if the wires are parallel, the current flows in opposite directions in the two as it completes its travel around the loop. The same is true of the currents in the two conductors of the line. But with stray capacitive coupling the voltages at all points on the secondary coil are essentially in phase; for this type of coupling the secondary coil is just a mass of metal. Consequently, whatever current flows in the link (or in the line) flows in the *same* direction in both wires. Although both the link and line have two conductors and apparently form an ordinary go-and-return circuit, to the currents that flow as a result of capacitive coupling they simply look like a pair of conductors in parallel — in effect, that is, like a single conductor. The equivalent circuit is shown in the lower drawing in Fig. 10-28.

This single-wire circuit is an antenna system in itself, working in conjunction with a ground lead of unknown composition and length. It includes the regular antenna as well as the entire transmission line. If the various lengths hap-

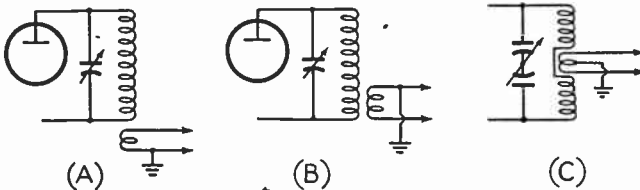


Fig. 10-29 — Methods of coupling and grounding link circuits to reduce energy transfer through stray capacitance.

pen to be just right, a fairly-large "parallel" current of this type can flow in it. This means that a considerable proportion of the total power output of the transmitter can be wasted in losses and radiation from a very undesirable sort of antenna system. Furthermore, despite the tuned tank circuits in the amplifier and antenna coupler, harmonic currents will flow in such an "antenna" even more readily than the fundamental current.

There are other undesirable results, too. The fact that the power wiring becomes part of an "antenna" system means that the transmitter itself may perforce be at a considerable r.f. potential above ground. The chassis becomes "hot" with r.f., r.f. feed-back is prone

to occur in speech equipment, and a considerable amount of r.f. power may be pumped into receiving and other equipment connected to the same a.c. power outlet. (A similar type of coupling in the input circuits of a receiver leads to stray pick-up of signals that may partially or completely mask the directive effects of the proper antenna.) On top of all this, it is

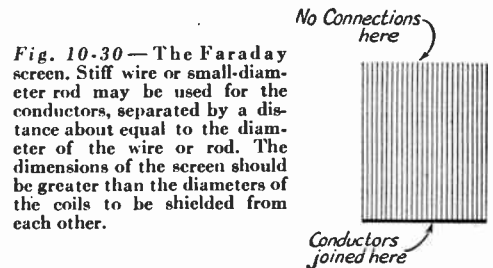


Fig. 10-30 — The Faraday screen. Stiff wire or small-diameter rod may be used for the conductors, separated by a distance about equal to the diameter of the wire or rod. The dimensions of the screen should be greater than the diameters of the coils to be shielded from each other.

impossible to tell much about the operation of the transmission line because the parallel current is more or less in phase with the regular line current in one wire and out of phase with it in the other. Thus the resultant currents in the two wires are unbalanced, and there is no way to separate the "parallel" and "line" currents in measurement.

These effects can only be eliminated if the stray capacitances are eliminated. However, they can be reduced by arranging the coils so the amount of energy coupled from the primary to the secondary is small, even though the capacitance itself still exists. This can be done by using a link coil that is physically small — that is, has few turns — and coupling it to the "cold" point on the tank coil. The cold point

will be at the end of the coil that is grounded for r.f., either directly or through a by-pass condenser, in the case of single-ended tanks. In balanced tank circuits, the cold point is at the center. The coupling is further reduced if one side of the link circuit is grounded to the transmitter chassis as close as possible to the point where the tank itself is grounded. If the link is at the

end of the tank coil the side farthest from the tank should be grounded, as indicated in Fig. 10-29A. If the link is wound *over* one end of the tank coil, ground the side toward the hot end of the tank, as indicated in Fig. 10-29B. With a balanced tank circuit the link should be at the center of the coil. In this case the best point to ground is the center of the link coil, but if this is impracticable good results will be secured by grounding either end of the coil. Ground directly to the chassis and keep the lead as short as possible.

This treatment of link circuits does not eliminate capacitive coupling. It simply makes it less troublesome, by making certain that the coupling occurs between parts of circuits that

are not at high r.f. voltage. However, there are cases, particularly with balanced tank circuits, where the point on the tank coil that is cold for the fundamental frequency is hot at the even harmonics. This means that even though the transmitter and line behave properly on the fundamental frequency, harmonics still can be radiated at considerable intensity. The only way to be sure that these effects do not exist is to eliminate the stray capacitance entirely.

Capacitive coupling between coils can be eliminated by means of a Faraday screen. This is a shield that prevents the electric field from one coil from reaching the other, but which has no effect on the magnetic field. As shown in Fig. 10-30, it consists of a group of parallel conductors, insulated from each other, and connected together at one end only. This forms an effective shield for the electric field, but since the conductors are open-circuited the voltages induced in them by the magnetic field cannot cause any current to flow. (Such current flow is essential to magnetic shielding with nonmagnetic materials, as explained in Chapter Two.)

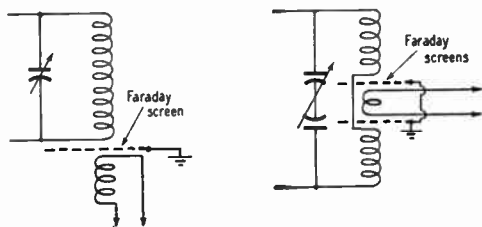


Fig. 10-31 — Installation of Faraday screens to eliminate capacitive coupling between coils.

The Faraday screen should be somewhat larger than the diameter of the coils with which it is used. It is simply mounted between the two coils that are to be shielded from each other, and then grounded to the chassis through a short lead, as indicated in Fig. 10-31. In the case of a balanced tank circuit with a shielding link, two shields must be used, one

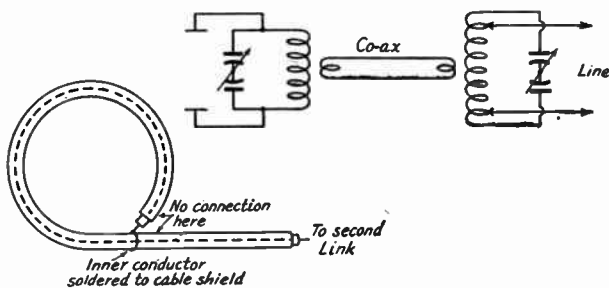


Fig. 10-32 — A shielded link coil constructed from coaxial cable. The smaller sizes of cable such as RG-59/U are most convenient, except when the coils have a diameter of 3 inches or more. For larger coils, RG-8/U or RG-11/U can be used.

on each side of the link coil. In the case of fixed links wound over the tank coil, a satisfactory screen can be made by using several turns of the same type of coil, cutting them parallel to the axis to open-circuit the conductors, and then soldering them together at one end only. This shield can then be inserted between the tank coil and link, making sure that it is adequately insulated from both.

An alternative, and perhaps simpler, type of screening is shown in Fig. 10-32. In this case the inner conductor of a piece of coaxial cable is used to form a one-turn link. The outer conductor serves as an open-circuited shield around the turn, this shield being grounded to the chassis. The circuit to the link line is made by connecting the inner conductor to the outer conductor at the finish of the turn, as shown, and from there on the coaxial line is used to transfer the power to a second, and similar, link coil at the antenna tuner. This type of shielded link is simpler to make than the regular Faraday screen.

Aside from the adverse effects on the performance of the antenna system, stray capacitive coupling frequently is responsible for interference to near-by broadcast receivers. It is not difficult to appreciate that radiation taking place from transmission lines and power wiring is, in general, more likely to get into a broadcast receiver than radiation from an antenna that is intentionally kept away from other antennas — particularly when the receivers are connected to that same power wiring.

## Antenna-Coupler Construction

The apparatus used to cancel line reactance and match the line resistance to the transmitter is commonly called an "antenna coupler" or "antenna tuner." (The name is really a misnomer, because the coupling and tuning equipment at the input end of the line does not have any effect on the antenna itself; if there is any antenna tuning to be done it must be done at the antenna, independently of the line.) The design principles and the important construc-

tional points have been covered earlier in this chapter; in this section we show a few examples of typical construction.

Bearing in mind the precautions mentioned earlier as to maintaining balance in parallel-conductor transmission lines, it is usually good practice to install the coupling equipment close to the point where the line enters the station. This is a simple matter when the tuning equipment is link-coupled to the trans-

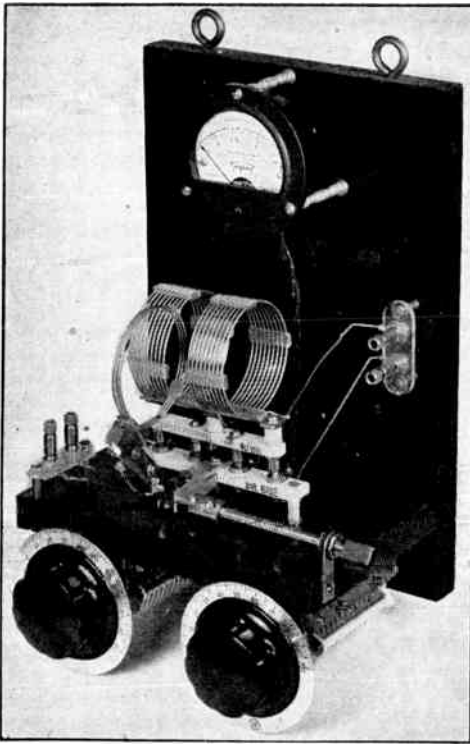


Fig. 10-33—A wall-mounting antenna coupler for medium-power transmitters. This unit provides a choice of either series or parallel tuning for resonant feeders. Standard transmitting coils of the variable-link type are used.

mitter, since there are no particular restrictions on the length of the link that can be used. However, if the link line is fairly long it should be treated as a transmission line rather than merely as a means of providing mutual inductance between two separated coils. In such a case it is advisable to have variable coupling at both ends of the link. This permits matching the link line to the line tank circuit, and once the match is obtained the power output of the transmitter can be varied by changing the coupling at the transmitter tank. If the link line is not properly matched its current may be excessive, leading to unnecessary power loss.

The most desirable form of link line is coaxial cable. Properly handled, its losses are low; and since it is shielded it can be on or near metal objects with impunity.

### ● SERIES-PARALLEL COUPLER FOR WALL MOUNTING

Fig. 10-33 shows a link-coupled coupler designed for series or parallel tuning of a resonant line. It is suitable for transmitters having a power output in the neighborhood of 250 watts. A higher-power version easily could be made using a similar layout, but substituting heavier coils and condensers with greater plate spacing.

As shown in Fig. 10-34, the change from series to parallel tuning is made by means of jumpers and extra pins on the coil plug-bar. A separate coil is used for each band, and after determining which should be used, series or parallel tuning, on a particular band, the jumpers may be installed permanently or left off as required. The tuning condensers specified, together with a set of standard plug-in transmitting coils, should provide adequate coupling if the transmission-line length is such as to bring a voltage or current loop near the input end.

The unit is mounted on an  $8 \times 12 \times \frac{7}{8}$ -inch board for hanging on the wall in any convenient location near the entrance point of the feeders. The 2.5-ampere r.f. ammeter is mounted centrally by long wood screws through spacers at the top of the unit. A short length of twisted pair connects it to the thermocouple, secured in a horizontal position at the bottom of the backboard. The tuning condensers are mounted on the underside of a 4-inch shelf extending the width of the unit. Atop the shelf, the jack-bar for the coil is supported on pillars by wood screws. An extension shaft to vary the degree of coupling is supported by a bushing fastened to a short strip of brass at the right of the shelf. A short length of 300-ohm ribbon (coaxial cable can be used instead) connects the input terminals to the movable link, while the output terminals are located at the middle right of the backboard. Two screw eyes at the top permit the unit to be hung from screws or nails in the wall.

### ● RACK-MOUNTING SERIES-PARALLEL COUPLER

The rack-mounting coupling unit shown in Fig. 10-35 is suitable for power outputs of 25 to 50 watts, and provides either series or parallel tuning for resonant lines. Separate condensers are used for this purpose, and while

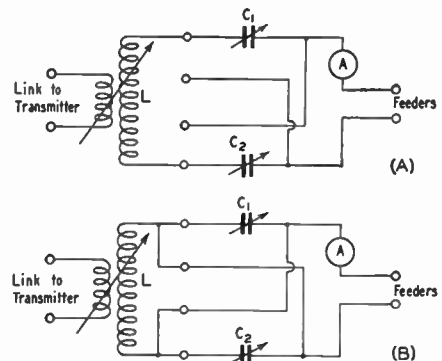


Fig. 10-34—Circuit diagram of an antenna coupler for use with a medium-power transmitter. A—Series tuning. B—Parallel tuning.

$C_1, C_2$ —100- $\mu$ fd. single section variable, 0.070-inch spacing (Cardwell MT-100-GS).

L—B & W BVL series.

A—0-2.5 thermocouple r.f. ammeter.



three are required, this system has the advantage that no switching is necessary when changing from series to parallel tuning. It is also possible to cover a somewhat wider range of line input impedances with parallel tuning because the series condensers can be used to help cancel out inductive reactance that cannot be handled by the parallel circuit alone.

The coupler is mounted on a  $5\frac{1}{4} \times 19$ -inch panel. The parallel condenser,  $C_1$ , is in the center, with  $C_2$  and  $C_3$  on either side. The variable condensers are mounted on National GS-1 stand-off insulators which are fastened to the condenser tie-rods by means of machine screws with the heads cut off. Small ceramic shaft couplings are used to insulate the control knobs from the condenser shafts.

Clips with flexible leads attached are provided for the parallel condenser,  $C_1$ , so that the sections may be used either in series or parallel to form either a high- $C$  or low- $C$  tank circuit, as required. When the high- $C$  tank is necessary the two stators are connected together by means of the clips, as indicated by the dotted lines in the circuit diagram, Fig. 10-36. When the two sections are connected in series for low- $C$  operation the breakdown voltage is increased.

Two sets of variable condensers are suggested in the list of parts. The smaller receiving-type condensers with 0.03-inch air gap are satisfactory for transmitter power outputs up to 50 watts. The larger condensers, with 0.045-inch spacing, are required for transmitter outputs of the order of 100 watts.

**BANDSWITCHING UNIVERSAL COUPLER**

The coupling unit shown in Figs. 10-37 and 10-39 is of the "universal" type discussed earlier. It is a bandswitching unit using commercially-available coils. Provision is made for switching either capacitance or inductance across the transmission line to compensate for its input reactance. Impedance matching is achieved by tapping the tank coils at the proper points.

In the circuit diagram, Fig. 10-38, only one

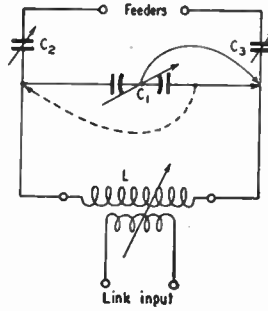


Fig. 10-36 — Circuit of the rack-mounting antenna tuner for use with transmitters having final amplifiers that are operated at less than 1000 volts on the plate.

All coils are  $1\frac{1}{8}$  inches in diameter and  $2\frac{1}{4}$  inches long, with the variable link located at the center. For series tuning, use the coil specified for the next-higher frequency band, which will be approximately correct.

- $C_1$  — 100  $\mu$ fd. per section, 0.045-inch spacing (National TMK-100-D) for high voltages; receiving type for low voltages (Hammarlund MCD-100).
- $C_2, C_3$  — 250  $\mu$ fd., 0.026-inch spacing (National TMS-250) for high voltages; receiving type for low voltages (Hammarlund MC-250).
- $L$  — B & W JVL-series coils. Approximate dimensions for parallel tuning for each band are as follows:  
 3.5-Mc. band — 40 turns No. 20.  
 7-Mc. band — 24 turns No. 16.  
 14-Mc. band — 14 turns No. 16.  
 28-Mc. band — 8 turns No. 16.

set of coils is shown. For other bands the connections shown for  $L_1$  and  $L_2$  would be duplicated. Bandswitching is accomplished by a five-gang switch,  $S_1$ . Compensating reactances can be switched in or out of the circuit by  $S_2$ . The coupling links,  $L_2$ , are the shielded type using coaxial cable described earlier in this chapter (Fig. 10-32).

The coupler is wholly supported by a  $7 \times 19$ -inch relay-rack panel. The variable condensers are mounted from the panel by small stand-off insulators, and insulated couplings are used between the condenser shafts and the National Type AM dials. The tank condenser,  $C_1$ , is mounted at the right-hand end of the panel with the bandswitch,  $S_1$ , to its left. The four coils are grouped around the bandswitch, with the 28-Mc. coil placed so that the leads to it are the shortest. The coils are Millen 44000 series with the plug bases removed from the

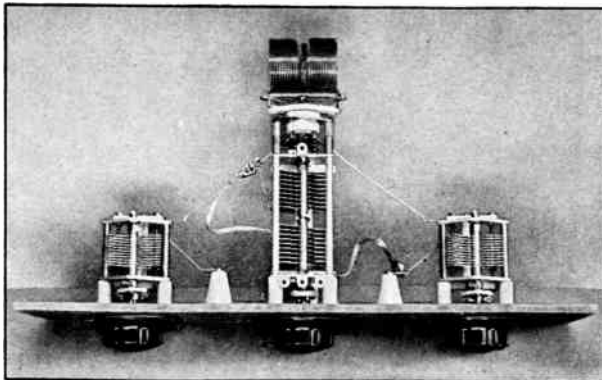


Fig. 10-35 — Rack-mounted coupler for low-power transmitters. This unit uses three variable condensers to provide either series or parallel tuning without condenser switching.

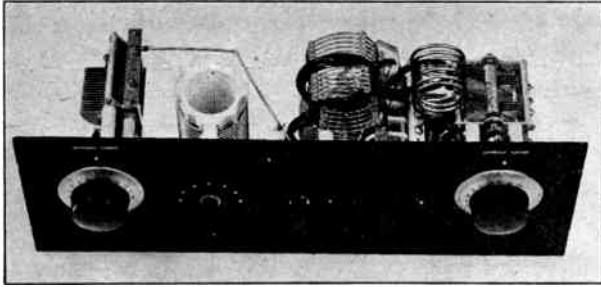


Fig. 10-37 — Bandswitching universal-type coupler for parallel-conductor lines. This unit can be used with transmitters having power outputs of the order of 100 watts.

3.5-, 7- and 14-Mc. coils. It is not practicable to remove the base from the 28-Mc. coil because it does not have the polystyrene supporting strip that is part of the lower-frequency coil

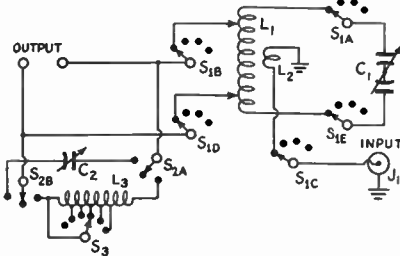


Fig. 10-38 — Circuit diagram of the bandswitching coupler. In this diagram the ground symbol indicates points that are connected together. Wiring to coils is shown for one band only, to avoid complicating the diagram; the wiring for other coils is identical.

$C_1$  — 100- $\mu\text{fd.}$  per-section variable (Cardwell MR-100-B11).

$C_2$  — 335- $\mu\text{fd.}$  variable (Cardwell MR-335-BS).

$L_1$  — Millen 44000-series coils (see text).

$L_2$  — Shielded link; one turn for 28 and 14 Mc.; 2 turns for 7 and 3.5 Mc.

$L_3$  — 26 turns No. 12 on 2½-inch diameter form (National XR-10A), 7 turns per inch. Tapped 8, 14, 18, 22 and 24 turns from end to which arm of  $S_3$  is connected.

$J_1$  — Coaxial-cable connector (Amphenol).

$S_1$  — 5-section 4-position ceramic wafer switch (Centralab 2546).

$S_2$  — 2-section 4-position ceramic wafer switch (Centralab 2543).

$S_3$  — 1-section 6-position ceramic wafer switch (Centralab 2501).

assemblies. The coils are partly supported by the wiring to the switch and partly by the polystyrene plate mounted on the back of the switch. The ends of the coil mounting strips are cemented into holes cut in the plate.

The compensating condenser,  $C_2$ , is mounted at the left-hand end of the panel.  $L_3$  is mounted vertically to its right, with  $S_3$  directly in front of it on the panel.  $S_2$  is mounted centrally on the panel. The output terminals to the line are mounted above  $S_3$ . The link input terminal is a coaxial cable socket mounted on a small bracket in the lower right-hand corner.

The link coils,  $L_2$ , are supported by the wiring, and the coupling is changed by bending the link into or out of its associated tank coil. Since the links fit rather tightly in the tank coils, the pressure helps hold them in place once the proper coupling is determined. The link shields are all connected together and to the input connector; the inner conductors go to the switch contacts. The link coils are made from RG-59/U cable.

With the coils and condensers specified, this coupler can handle power outputs of the order of 100 to 150 watts. The method of adjustment is covered earlier in this chapter.

### ● A WIDE-RANGE ANTENNA COUPLER

The photograph of Fig. 10-40 shows the constructional details of a wide-range antenna coupler suitable for use with high-power transmitters. Various combinations of parallel and series tuning, with high- and low- $C$  tanks and high- and low-impedance outputs, are available. Diagrams of the various circuit combinations possible with this arrangement are given in Fig. 10-41.

A separate coil is used for each band, and the desired connections for series or parallel tuning with high or low  $C$ , or for low-impedance output

Fig. 10-39 — Rear view of the bandswitching coupler. Details of coil mountings are shown in this view.


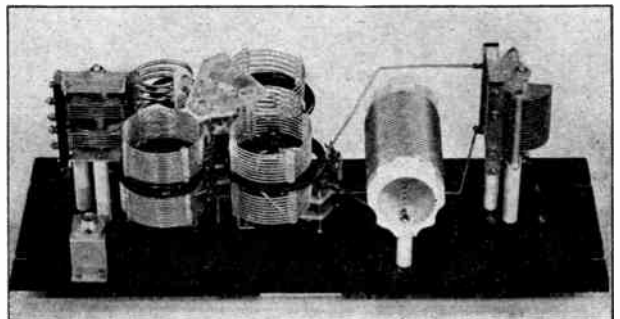


Fig. 10-40 — Wide-range antenna coupler. The unit is assembled on a metal chassis measuring 10 × 17 × 2 inches, with a panel 8<sup>3</sup>/<sub>4</sub> × 19 inches in size. The variable condenser is a split-stator unit with a capacitance of 200 μμfd. per section and 0.07-inch plate spacing (Johnson 200ED30). The plug-in coils are the B & W TVL series. The r.f. ammeter has a 4-ampere scale.

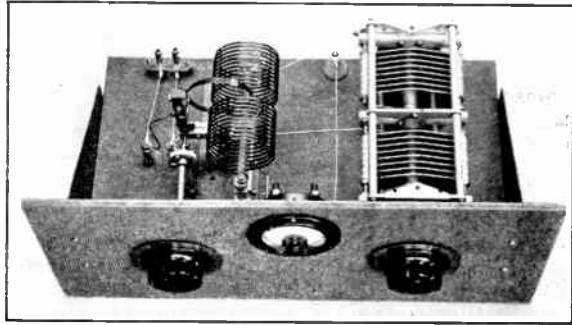

with high or low C, are automatically made when the coil is plugged in. Coil connections to the pins for various circuit arrangements are shown in Fig. 10-41.

The tuning condenser specified, together with a set of standard plug-in transmitting coils, should cover nearly all coupling conditions likely to be encountered.

Because the switching connections require the use of a central pin, a slight alteration in the B & W coil-mounting unit is required. The central link-mounting unit should be removed from the jack-bar and an extra jack placed in the central hole thus made available. The link assembly should then be mounted on a 2-inch cone insulator to one side of the jack bar.

Correspondingly, the central nut on each coil plug base must be removed and a Johnson tapped plug, similar to those furnished with

the coils, substituted. An extension shaft may then be fitted on the link shaft and a control brought out to a knob on the panel.

The split-stator tank condenser is mounted by means of angle brackets on four 1-inch cone-type ceramic insulators, and an insulated flexible coupling is provided for the shaft.

If desired, the coils may be wound with fixed links on ceramic transmitting coil forms. The links should be provided with flexible leads which can be plugged into a pair of jack-top insulators mounted near the coil jack strip, unless a special mounting is made providing for seven connections.

The unit as described should be satisfactory for transmitters having an output of 500 watts with plate modulation and somewhat more on c.w. For higher-power 'phone, a tank condenser with larger plate spacing should be used.

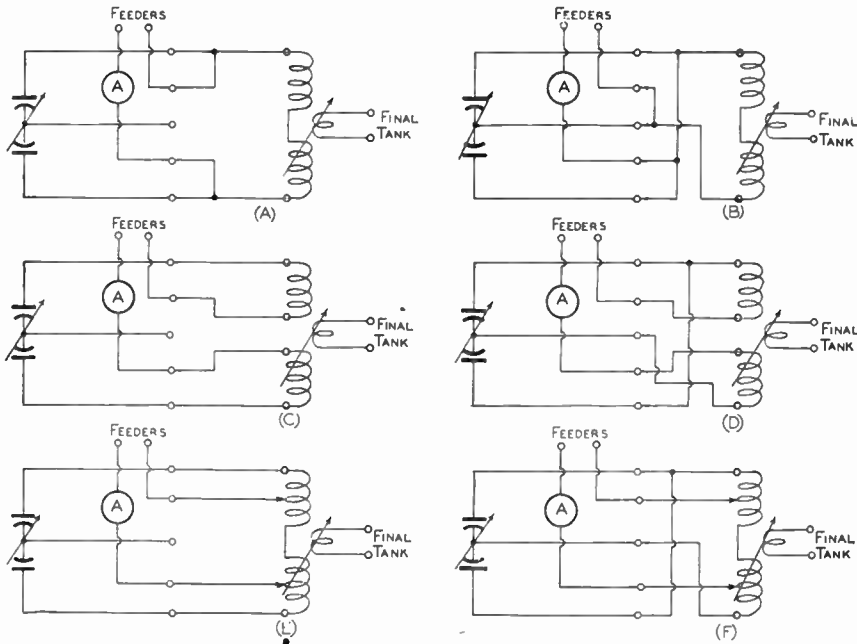


Fig. 10-41 — Circuit diagram of the wide-range rack-type antenna coupler. A — Parallel tuning, low C. B — Parallel tuning, high C. C — Series tuning, low C. D — Series tuning, high C. E — Parallel tank, low-impedance output, low C. F — Parallel tank, low-impedance output, high C. After the inductance required for each of the various bands has been determined experimentally, the connections to the coils can be made permanent. Then it will be necessary only to plug in the right coil for each band, tune the condenser for resonance, and adjust the link loading.

## Antennas

In selecting the type of antenna to use, the propagation characteristics of the frequency band or bands to be used should be given due consideration. These are outlined in Chapter Four. In general, antenna construction and location become more critical and important on the higher frequencies. On the lower frequencies (3.5 and 7 Mc.) the angle of radiation and plane of polarization may be of relatively little importance; at 28 Mc. and higher they may be all-important. On a given frequency, the particular type of antenna best suited for long-distance transmission may not be as good for shorter-range work as would a different type. The important properties of an antenna or antenna system are its polarization, angle of radiation, impedance, directivity and gain.

### Polarization

The polarization of a straight-wire antenna is its position with respect to the earth. That is, a vertical wire transmits vertically-polarized waves and a horizontal antenna generates horizontally-polarized waves in its direction of maximum radiation (broadside). The wave from an antenna in a slanting position contains both horizontal and vertical components.

### Angle of Radiation

The wave angle (or vertical angle) at which an antenna radiates best is determined by its polarization, height above ground, and the nature of the ground. Radiation is not all at one well-defined angle, but rather is generally dispersed over a more or less large angular region, depending upon the type of antenna. The angle is measured in a vertical plane with respect to a tangent to the earth at that point.

### Impedance

The impedance of the antenna at any point is the ratio of the voltage to the current at that point. It is important in connection with feeding power to the antenna, since it constitutes the load represented by the antenna. It is a pure resistance only at current loops (maxima) and nodes (minima) on resonant antennas. The antenna impedance is high at the current node and low at the current loop.

### Directivity

All antennas radiate more power in certain directions than in others. This characteristic, called *directivity*, must be considered in three dimensions, since directivity exists in the vertical plane as well as in the horizontal plane. Thus the directivity of the antenna will affect the wave angle as well as the actual compass directions in which maximum transmission takes place.

### Current

The field strength produced by an antenna is proportional to the current flowing in it. When there are standing waves on an antenna, the parts of the wire carrying the higher current have the greater radiating effect. All resonant antennas have standing waves — only terminated types, like the terminated rhombic and terminated "V," have substantially uniform current along their lengths.

### Power Gain

The ratio of power required to produce a given field strength, with a "comparison" antenna, to the power required to produce the same field strength with a specified type of antenna is called the **power gain** of the latter antenna. The field is measured in the optimum direction of the antenna under test. In amateur work, the comparison antenna is generally a half-wave antenna at the same height and having the same polarization as the antenna under consideration. Power gain usually is expressed in decibels.

### Front-to-Back Ratio

In unidirectional beams (antenna systems with maximum radiation in only one direction) the front-to-back ratio is the ratio of power radiated in the maximum direction to power radiated in the opposite direction. It is also a measure of the reduction in received signal when the beam direction is changed from that for maximum response to the opposite direction. Front-to-back ratio is usually expressed in decibels.

## Ground Effects

The radiation pattern of any antenna that is many wavelengths distant from the ground and all other objects is called the **free-space pattern** of that antenna. The free-space pattern of an antenna is almost impossible to obtain in practice, except in the v.h.f. and u.h.f. ranges. Below 30 Mc., the location of the antenna with respect to ground plays an important part in determining the actual radiation pattern of the antenna.

When any antenna is near the ground the free-space pattern is modified by reflection of radiated waves from the ground, so that the actual pattern is the resultant of the free-space pattern and ground reflections. This resultant is dependent upon the height of the antenna, its position or orientation with respect to the surface of the ground, and the electrical characteristics of the ground. The effect of a perfectly-reflecting ground is such that the

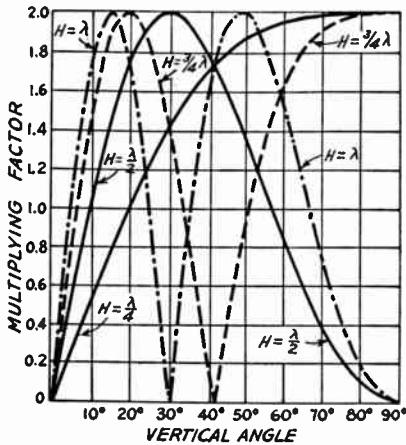


Fig. 10-42 — Effect of ground on radiation of horizontal antennas at vertical angles for four antenna heights. This chart is based on perfectly-conducting ground.

original free-space field strength may be multiplied by a factor which has a maximum value of 2, for complete reinforcement, and having all intermediate values to zero, for complete cancellation. These reflections only affect the radiation pattern in the vertical plane — that is, in directions upward from the earth's surface — and not in the horizontal plane, or the usual geographical directions.

Fig. 10-42 shows how the multiplying factor varies with the vertical angle for several representative heights for horizontal antennas. As the height is increased the angle at which complete reinforcement takes place is lowered, until for a height equal to one wavelength it occurs at a vertical angle of 15 degrees. At still greater heights, not shown on the chart, the first maximum will occur at still smaller angles.

**Radiation Angle**

The vertical angle, or angle of radiation, is of primary importance, especially at the higher frequencies. It is advantageous, therefore, to erect the antenna at a height that will take advantage of ground reflection in such a way as to reinforce the space radiation at the most desirable angle. Since low radiation angles usually are desirable, this generally means that the antenna should be high — at least one-half wavelength at 14 Mc., and preferably three-quarter or one wavelength; at least one wavelength, and preferably higher, at 28 Mc. and the very-high frequencies. The physical height required for a given height in wavelengths decreases as the frequency is increased, so that good heights are not impracticable; a half-wavelength at 14 Mc. is only 35 feet, approximately, while the same height represents a full wavelength at 28 Mc. At 7 Mc. and lower frequencies the higher radiation angles are effective, so that again a reasonable antenna height is not difficult of attainment. Heights between 35 and 70 feet are suitable for all bands, the higher figures being preferable.

**Imperfect Ground**

Fig. 10-42 is based on ground having perfect conductivity, whereas the actual earth is not a perfect conductor. The principal effect of actual ground is to make the curves inaccurate at the lowest angles; appreciable high-frequency radiation at angles smaller than a few degrees is practically impossible to obtain over horizontal ground. Above 15 degrees, however, the curves are accurate enough for all practical purposes, and may be taken as indicative of the sort of result to be expected at angles between 5 and 15 degrees.

The effective ground plane — that is, the plane from which ground reflections can be considered to take place — seldom is the actual surface of the ground but is a few feet below it, depending upon the character of the soil.

**Impedance**

Waves that are reflected directly upward from the ground induce a current in the antenna in passing, and, depending on the antenna height, the phase relationship of this induced current to the original current may be such as either to increase or decrease the total current in the antenna. For the same power input to the antenna, an increase in current is equivalent to a decrease in impedance, and vice versa. Hence, the impedance of the antenna varies with height. The theoretical curve of variation of radiation resistance for an antenna above perfectly-reflecting ground is shown in Fig. 10-43. The impedance approaches the free-space value as the height becomes large, but at low heights may differ considerably from it.

**Choice of Polarization**

Polarization of the transmitting antenna is generally unimportant on frequencies between 3.5 and 30 Mc. However, the question of whether the antenna should be installed in a horizontal or vertical position deserves consideration for other reasons. A vertical half-wave or quarter-wave antenna will radiate

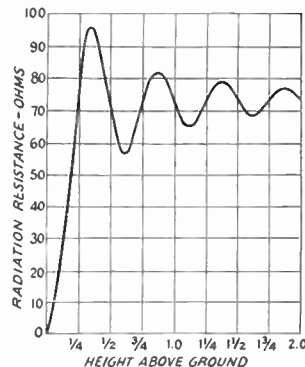


Fig. 10-43 — Theoretical curve of variation of radiation resistance for a half-wave horizontal antenna, as a function of height in wavelength above perfectly-reflecting ground.

equally well in all *horizontal* directions, so that it is substantially nondirectional, in the usual sense of the word. If installed horizontally, however, the antenna will tend to show directional effects, and will radiate best in the direction at right angles, or broadside, to the wire. The radiation in such a case will be least in the

direction toward which the wire points.

The vertical angle of radiation also will be affected by the position of the antenna. If it were not for ground losses at high frequencies, the vertical half-wave antenna would be preferred because it would concentrate the radiation horizontally.

## The Half-Wave Antenna

The fundamental form of antenna is a single wire whose length is approximately equal to half the transmitting wavelength. It is the unit from which many more-complex forms of antennas are constructed. It is variously known as a **half-wave dipole**, **half-wave doublet**, or **Hertz antenna**.

The length of a half-wavelength in space is:

$$\text{Length (feet)} = \frac{492}{\text{Freq. (Mc.)}} \quad (10-H)$$

The actual length of a half-wave antenna will not be exactly equal to the half-wave in space, but depends upon the thickness of the conductor in relation to the wavelength as shown in Fig. 10-44, where *K* is a factor that must be multiplied by the half-wavelength in free space to obtain the resonant antenna

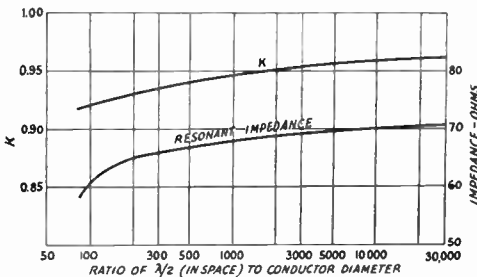


Fig. 10-44 — Effect of antenna diameter on length for half-wave resonance, shown as a multiplying factor, *K*, to be applied to the free-space half-wavelength (Equation 10-H). The effect of conductor diameter on the impedance measured at the center also is shown.

length. An additional shortening effect occurs with wire antennas supported by insulators at the ends because of the capacitance added to the system by the insulators (**end effect**). Under average conditions the following formula is sufficiently accurate for wire antennas at frequencies up to 30 Mc.:

$$\text{Length of half-wave antenna (feet)} = \frac{492 \times 0.95}{\text{Freq. (Mc.)}} = \frac{468}{\text{Freq. (Mc.)}} \quad (10-I)$$

Example: A half-wave antenna for 7150 kc. (7.15 Mc.) is  $\frac{468}{7.15} = 65.45$  feet, or 65 feet 5 inches.

Above 30 Mc. the following formulas should be used, particularly for antennas constructed from rod or tubing. The factor *K* is taken from Fig. 10-44.

$$\text{Length of half-wave antenna (feet)} = \frac{492 \times K}{\text{Freq. (Mc.)}} \quad (10-J)$$

$$\text{or length (inches)} = \frac{5905 \times K}{\text{Freq. (Mc.)}} \quad (10-K)$$

Example: Find the length of a half-wavelength antenna at 29 Mc., if the antenna is made of 2-inch diameter tubing. At 29 Mc., a half-wavelength in space is  $\frac{492}{29} = 16.97$  feet, from Eq.

10-H. Ratio of half-wavelength to conductor diameter (changing wavelength to inches) is  $\frac{16.97 \times 12}{2} = 101.8$ . From Fig. 10-44, *K* = 0.92

for this ratio. The length of the antenna, from Eq. 10-J, is  $\frac{492 \times 0.92}{29} = 15.6$  feet, or 15 feet

7 inches. The answer is obtained directly in inches by substitution in Eq. 10-K:  $\frac{5905 \times 0.92}{29} = 187$  inches.

### Current and Voltage Distribution

When power is fed to such an antenna, the current and voltage vary along its length. The current is maximum at the center and nearly zero at the ends, while the opposite is true of the r.f. voltage. The current does not actually reach zero at the current nodes, because of the end effect; similarly, the voltage is not zero at its node because of the resistance of the antenna, which consists of both the r.f. resistance of the wire (*ohmic resistance*) and the **radiation resistance**. The radiation resistance is an *equivalent* resistance, a convenient conception to indicate the radiation properties of an antenna. The radiation resistance is the equivalent resistance that would dissipate the power the antenna radiates, with a current flowing in it equal to the antenna current at a current loop (maximum). The ohmic resistance of a half-wavelength antenna is usually small enough, in comparison with the radiation resistance, to be neglected for all practical purposes.

### Impedance

The radiation resistance of an infinitely-thin half-wave antenna in free space — that is, sufficiently removed from surrounding objects so that they do not affect the antenna's characteristics — is 73 ohms, approximately. The value under practical conditions is commonly taken to be in the neighborhood of 70 ohms. It is pure resistance, and is measured at the center of the antenna. The impedance

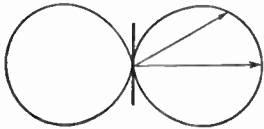


Fig. 10-45 — The free-space radiation pattern of a half-wave antenna. The antenna is shown in the vertical position. This is a cross-section of the solid pattern described by the figure when rotated on its vertical axis. The "doughnut" form of the solid pattern can be more easily visualized by imagining the drawing glued to a piece of cardboard, with a short length of wire fastened on it to represent the antenna. Twirling the wire will give a visual representation of the solid radiation pattern.

is minimum at the center, where it is equal to the radiation resistance, and increases toward the ends. The actual value at the ends will depend on a number of factors, such as the height, the physical construction, the insulators at the ends, and the position with respect to ground.

**Conductor Size**

The impedance of the antenna also depends upon the diameter of the conductor in relation to the wavelength, as shown in Fig. 10-44. If the diameter of the conductor is made large, the capacitance per unit length increases and the inductance per unit length decreases. Since the radiation resistance is affected relatively little, the decreased  $L/C$  ratio causes the  $Q$  of the antenna to decrease, so that the resonance curve becomes less sharp. Hence, the antenna is capable of working over a wide frequency range. This effect is greater as the diameter is increased, and is a property of some importance at the very-high frequencies where the wavelength is small.

**Radiation Characteristics**

The radiation from a half-wave antenna is not uniform in all directions but varies with the angle with respect to the axis of the wire. It is most intense in directions perpendicular to the wire and zero along the direction of the wire, with intermediate values at intermediate angles. This is shown by the sketch of Fig. 10-45, which represents the radiation pattern in free space. The relative intensity of radiation is proportional to the length of a line drawn from the center of the figure to the perimeter. If the antenna is vertical, as shown in the figure, then the field strength will be uniform in all horizontal directions; if the antenna is horizontal, the relative field strength will depend upon the direction of the receiving point with respect to the direction of the antenna wire. The variation in radiation at vari-

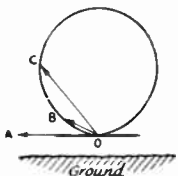


Fig. 10-46 — Illustrating the importance of vertical angle of radiation in determining antenna directional effects. Ground reflection is neglected in this drawing of the free-space field pattern of a horizontal antenna.

ous vertical angles from a half-wavelength horizontal antenna is indicated in Figs. 10-46 and 10-47.

**FEEDING THE HALF-WAVE ANTENNA**

**Direct Feed**

If possible, it is advisable to locate the antenna at least a half-wavelength from the transmitter and use a transmission line to carry the power from the transmitter to the antenna. However, in many cases this is impossible, particularly on the lower frequencies, and direct feed must be used. Three examples of direct feed are shown in Fig. 10-48. In the method shown at A,  $C_1$  and  $C_2$  should be about  $150 \mu\text{fd.}$  each for the 3.5-Mc. band,  $75 \mu\text{fd.}$  each at 7 Mc., and proportionately smaller at the higher frequencies. The antenna coil

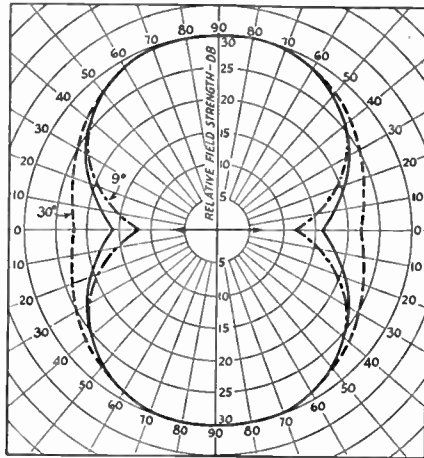


Fig. 10-47 — Horizontal pattern of a horizontal half-wave antenna at three vertical radiation angles. The solid line is relative radiation at 15 degrees. Dotted lines show deviation from the 15-degree pattern for angles of 9 and 30 degrees. The patterns are useful for shape only, since the amplitude will depend upon the height of the antenna above ground and the vertical angle considered. The patterns for all three angles have been proportioned to the same scale, but this does not mean that the maximum amplitudes necessarily will be the same. The arrow indicates the direction of the horizontal antenna wire.

connected between them should resonate to 3.5 Mc. with about 60 or  $70 \mu\text{fd.}$ , for the 80-meter band, for 40 meters it should resonate with 30 or  $35 \mu\text{fd.}$ , and so on. The circuit is adjusted by using loose coupling between the antenna coil and the transmitter tank coil and adjusting  $C_1$  and  $C_2$  until resonance is indicated by an increase in plate current. The coupling between the coils should then be increased until proper plate current is drawn. It may be necessary to reresonate the transmitter tank circuit as the coupling is increased, but the change should be small.

The circuits in Fig. 10-48B and C are used when only one end of the antenna is accessible. In B, the coupling is adjusted by moving the

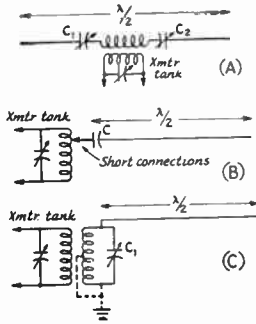


Fig. 10-48 — Methods of directly exciting the half-wave antenna. A, current feed, series tuning; B, voltage feed, capacitance coupling; C, voltage feed, with inductively-coupled antenna tank. In A, the coupling circuit is not included in the effective electrical length of the antenna system proper.

tap toward the “hot” or plate end of the tank coil — the condenser *C* may be of any convenient value that will stand the voltage, and it doesn’t have to be variable. In the circuit at *C*, the antenna tuned circuit (*C*<sub>1</sub> and the antenna coil) should be similar to the transmitter tank circuit. The antenna tuned circuit is adjusted to resonance with the antenna connected but with loose coupling to the transmitter. Heavier loading of the tube is then obtained by tightening the coupling between the antenna coil and the transmitter tank coil.

Of the three systems, that at *A* is preferable because it is a symmetrical system and generally results in less r.f. power “floating” around the shack. The system of *B* is undesirable be-

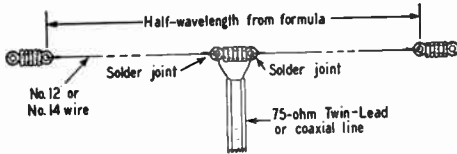


Fig. 10-49 — Construction of a half-wave doublet fed with 75-ohm line. The length of the antenna is calculated from Equation 10-1.

cause it provides practically no protection against the radiation of harmonics, and it should only be used in emergencies.

**Transmission-Line Feed for Half-Wave Antennas**

Since the impedance at the center of a half-wavelength antenna is in the vicinity of 75 ohms, it offers a good match for 75-ohm two-wire transmission lines. Several types are available on the market, with different power-handling capabilities. They can be connected in the center of the antenna, across a small strain insulator to provide a convenient connection point. Coaxial line of 75-ohms impedance can also be used, but it is heavier and thus not as convenient. In either case, the transmission line should be run away at right angles to the antenna for at least one-quarter wavelength, if possible, to avoid current unbalance in the line caused by pick-up from the antenna. The antenna length is calculated from Equation 10-1, for a half-wavelength antenna. When

No. 12 or No. 14 enameled wire is used for the antenna, as is generally the case, the length of the wire is the over-all length measured from the loop through the insulator at each end. This is illustrated in Fig. 10-49.

The use of 75-ohm line results in a “flat” line over most of any amateur band. However, by making the half-wave antenna in a special manner, called the two-wire or folded doublet, a good match is offered for a 300-ohm line. Such an antenna is shown in Fig. 10-50, with another version in Fig. 10-79B. The two differ only in the construction of the antenna

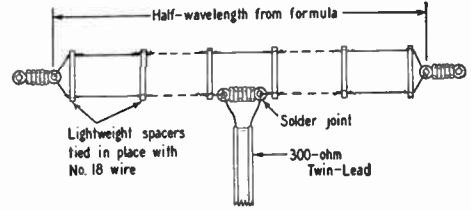


Fig. 10-50 — The construction of an open-wire folded doublet fed with 300-ohm line. The length of the antenna is calculated from Equation 10-1.

proper. The open-wire line shown in Fig. 10-50 is made of No. 12 or No. 14 enameled wire, separated by lightweight spacers of Lucite or other material (it doesn’t have to be a low-loss insulating material), and the spacing can be on the order of from 4 to 8 inches, depending upon what is convenient and what the operating frequency is. At 14 Mc., 4-inch separation is satisfactory, and 8-inch or even greater spacing can be used at 3.5 Mc.

If a half-wavelength antenna is fed at the center with other than 75-ohm line, or if a folded doublet is fed with other than 300-ohm line, standing waves will appear on the line and coupling to the transmitter may become awkward for some line lengths, as described earlier in this chapter. However, in many cases it is not convenient to feed the half-wave antenna with the correct line (as is the case where multiband operation of the same antenna is desired), and sometimes it is not convenient to feed the antenna at the center. Where multiband operation is desired (to be discussed later) or when the antenna must be

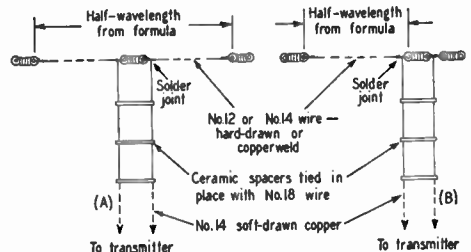


Fig. 10-51 — The antenna can be fed at the center or at the end with an open-wire line. The antenna length is obtained from Equation 10-1.



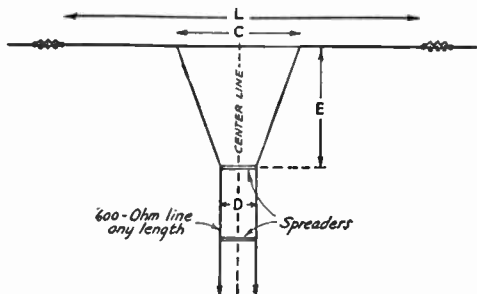


Fig. 10-52 — Delta-matched antenna system. The dimensions  $C$ ,  $D$ , and  $E$  are found by formulas given in the text. It is important that the matching section,  $E$ , come straight away from the antenna without any bends.

fed at one end by a transmission line, an open-wire line of from 450 to 600 ohms impedance is generally used. The impedance at the end of a half-wavelength antenna is in the vicinity of several thousand ohms, and hence a standing-wave ratio of 4 or 5 is not unusual when the line is connected to the end of the antenna. It is advisable, therefore, to keep the losses in the line as low as possible. This requires the use of ceramic or Micalex feeder spacers, if any appreciable power is used. For low-power installations in dry climates, dry wood spacers that have been boiled in paraffin are satisfactory. Mechanical details of half-wavelength antennas fed with open-wire lines are given in Fig. 10-51. If the power level is low, below 100

watts or so, 300-ohm Twin-Lead can be used in place of the open line.

One method for offering a match to a 600-ohm open-wire line with a half-wavelength antenna is shown in Fig. 10-52. The system is called a **delta match**. The line is "fanned" as it approaches the antenna, to have a gradually-increasing impedance that equals the antenna impedance at the point of connection. The dimensions are fairly critical, but careful measurement before installing the antenna and matching section is generally all that is necessary. The length of the antenna,  $L$ , is calculated from Equation 10-I. The length of section  $C$  is computed from:

$$C \text{ (feet)} = \frac{118}{\text{Freq. (Mc.)}} \quad (10-L)$$

The feeder clearance,  $E$ , is found from

$$E \text{ (feet)} = \frac{148}{\text{Freq. (Mc.)}} \quad (10-M)$$

Example: For a frequency of 7.1 Mc., the length

$$L = \frac{468}{7.1} = 65.91 \text{ feet, or } 65 \text{ feet } 11 \text{ inches.}$$

$$C = \frac{118}{7.1} = 16.62 \text{ feet, or } 16 \text{ feet } 7 \text{ inches.}$$

$$E = \frac{148}{7.1} = 20.84 \text{ feet, or } 20 \text{ feet } 10 \text{ inches.}$$

Since the equations hold only for 600-ohm line, it is important that the line be close to this value. This requires  $4\frac{3}{4}$ -inch spaced No. 14 wire, 6-inch spaced No. 12 wire, or  $3\frac{3}{4}$ -inch spaced No. 16 wire.

## Long-Wire Antennas

An antenna will be resonant so long as an integral number of standing waves of current and voltage can exist along its length; in other words, so long as its length is some integral multiple of a half-wavelength. When the antenna is more than a half-wave long it usually is called a long-wire antenna, or a harmonic antenna.

### Current and Voltage Distribution

Fig. 10-53 shows the current and voltage distribution along a wire operating at its fundamental frequency (where its length is equal to a half-wavelength) and at its second, third and fourth harmonics. For example, if the fundamental frequency of the antenna is 7 Mc., the current and voltage distribution will be as shown at A. The same antenna excited at 14 Mc. would have current and voltage distribution as shown at B. At 21 Mc., the third harmonic of 7 Mc., the current and voltage distribution would be as in C; and at 28 Mc., the fourth harmonic, as in D. The number of the harmonic is the number of half-waves contained in the antenna at the particular operating frequency.

The polarity of current or voltage in each standing wave is opposite to that in the ad-

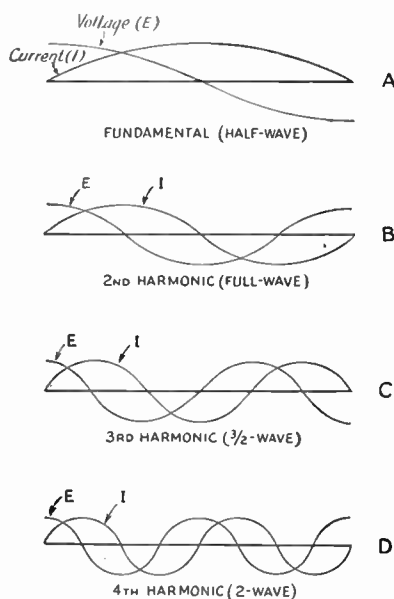


Fig. 10-53 — Standing-wave current and voltage distribution along an antenna when it is operated at various harmonics of its fundamental resonant frequency.

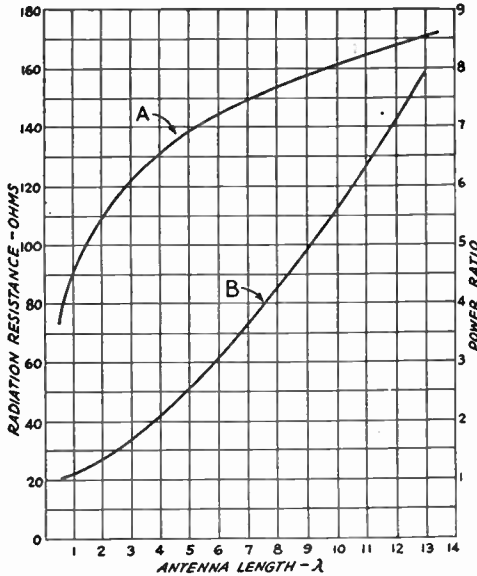


Fig. 10-54 — Curve A shows variation in radiation resistance with antenna length. Curve B shows power in lobes of maximum radiation for long-wire antennas as a ratio to the maximum radiation for a half-wave antenna.

adjacent standing waves. This is shown in the figure by drawing the current and voltage curves successively above and below the antenna (taken as a zero reference line), to indicate that the polarity reverses when the current or voltage goes through zero. Currents flowing in the same direction are *in phase*; in opposite directions, *out of phase*.

It is evident that one antenna may be used for harmonically-related frequencies, such as the various amateur bands. The long-wire or harmonic antenna is the basis of multiband operation with one antenna.

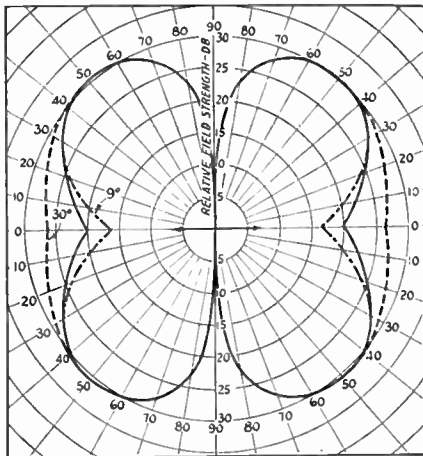


Fig. 10-55 — Horizontal patterns of radiation from a full-wave antenna. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. All three patterns are drawn to the same relative scale; actual amplitudes will depend upon the height of the antenna.

**Physical Lengths**

The length of a long-wire antenna is not an exact multiple of that of a half-wave antenna because the end effects operate only on the end sections of the antenna; in other parts of the wire these effects are absent, and the wire length is approximately that of an equivalent portion of the wave in space. The formula for the length of a long-wire antenna, therefore, is

$$\text{Length (feet)} = \frac{492 (N - 0.05)}{\text{Freq. (Mc.)}} \quad (10-N)$$

where *N* is the number of half-waves on the antenna.

Example: An antenna 4 half-waves long at 14.2 Mc. would be  $\frac{492 (4 - 0.05)}{14.2} = \frac{492 \times 3.95}{14.2} = 136.7$  feet, or 136 feet 8 inches.

It is apparent that an antenna cut as a half-wave for a given frequency will be slightly off

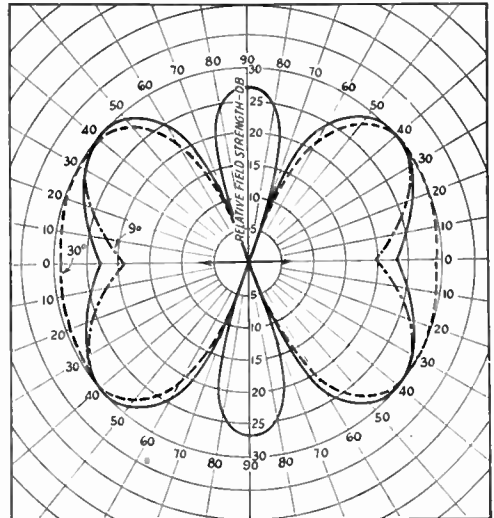


Fig. 10-56 — Horizontal patterns of radiation from an antenna three half-waves long. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. Minor lobes coincide for all three angles.

resonance at exactly twice that frequency (the second harmonic), because of the decreased influence of the end effects when the antenna is more than one-half wavelength long. The effect is not very important, except for a possible unbalance in the feeder system and consequent radiation from the feedline. If the antenna is fed in the exact center, no unbalance will occur at any frequency, but end-fed systems will show an unbalance in all but one frequency band, the band for which the antenna is cut.

**Impedance and Power Gain**

The radiation resistance as measured at a current loop becomes larger as the antenna length is increased. Also, a long-wire antenna radiates more power in its most favorable di-

rection than does a half-wave antenna in its most favorable direction. This power gain is secured at the expense of radiation in other directions. Fig. 10-54 shows how the radiation resistance and the power in the lobe of maximum radiation vary with the antenna length.

**Directional Characteristics**

As the wire is made longer in terms of the number of half-wavelengths, the directional effects change. Instead of the "doughnut" pattern of the half-wave antenna, the directional characteristic splits up into "lobes" which make various angles with the wire. In general, as the length of the wire is increased the direction in which maximum radiation occurs tends to approach the line of the antenna itself.

Directional characteristics for antennas one wavelength, three half-wavelengths, and two wavelengths long are given in Figs. 10-55, 10-56 and 10-57, for three vertical angles of radiation. Note that, as the wire length increases, the radiation along the line of the antenna becomes more pronounced. Still longer antennas can be considered to have practically "end-on" directional characteristics, even at the lower radiation angles.

**Methods of Feeding**

In a long-wire antenna, the currents in adjacent half-wave sections must be out of phase, as shown in Fig. 10-53. The feeder system must not upset this phase relationship. This requirement is met by feeding the antenna at either end or at any current loop. A two-wire feeder cannot be inserted at a current node, however, because this invariably brings the currents in two adjacent half-wave sections in

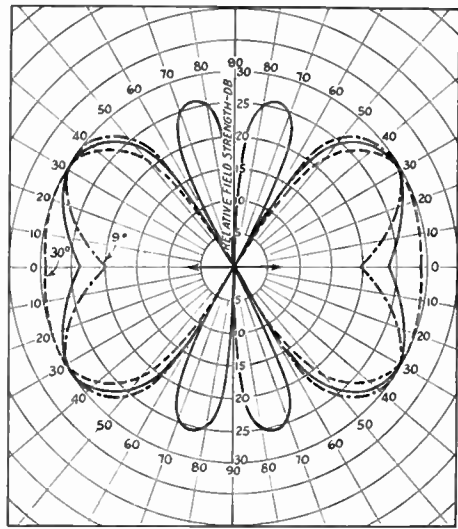


Fig. 10-57 — Horizontal patterns of radiation from an antenna two wavelengths long. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. The minor lobes coincide for all three angles.

phase; if the phase in one section could be reversed, then the currents in the feeders necessarily would have to be in phase and the feeder radiation would not be canceled out.

No point on a long-wire antenna offers a reasonable impedance for a direct match to any of the common types of transmission lines. The most common practice is to feed the antenna at one end or at a current loop with a low-loss open-wire line and accept the resulting standing-wave ratio of 4 or 5. When a better match is required, "stubs" are generally used (described later in this chapter).

**Multiband Antennas**

As suggested in the preceding section, the same antenna may be used for several bands by operating it on harmonics. When this is done it is necessary to use resonant feeders, since the impedance matching for nonresonant feeder operation can be accomplished only at one frequency unless means are provided for changing the length of a matching section and shifting the point at which the feeder is attached to it.

Furthermore, the current loops shift to a new position on the antenna when it is operated on harmonics, further complicating the feed situation. It is for this reason that a half-wave antenna which is center-fed by a rubber-insulated line is practically useless for harmonic operation; on all even harmonics there is a voltage maximum occurring right at the feed point, and the resultant impedance mismatch is so bad that there is a large standing-wave ratio and consequently high losses arise in the rubber dielectric. It is also wise not to attempt to use a half-wave

antenna center-fed with coaxial cable on its harmonics. Higher-impedance solid-dielectric lines such as 300-ohm Twin-Lead may be used, however, provided the power does not exceed a few hundred watts.

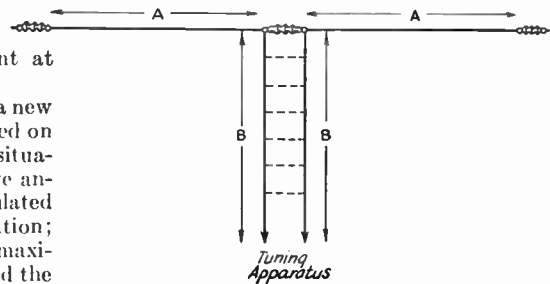


Fig. 10-58 — Practical arrangement of a shortened antenna. The total length,  $A + B + B + A$ , should be a half-wavelength for the lowest-frequency band, usually 3.5 Mc. See Table 10-III for lengths and tuning data.

**TABLE 10-II**  
**Multiband Resonant-Line Fed Antennas**

Antenna Length (ft.)	Feeder Length (ft.)	Band	Type of Tuning
With end feed: 120	60	4-Mc. 'phone	series
136	67	3.5-Mc. c.w. 7 Mc. 14 Mc. 28 Mc.	series parallel parallel parallel
134	67	3.5-Mc. c.w. 7 Mc.	series parallel
67	33	7 Mc. 14 Mc. 28 Mc.	series parallel parallel
With center feed: 137	67	3.5 Mc. 7 Mc. 14 Mc. 28 Mc.	parallel parallel parallel parallel
67.5	34	7 Mc. 14 Mc. 28 Mc.	parallel parallel parallel

The antenna lengths given represent compromises for harmonic operation because of different end effects on different bands. The 136-foot end-fed antenna is slightly long for 3.5 Mc., but will work well in the region that quadruples into the 14-Mc. band (3500-3600 kc.). Bands not listed are not recommended for the particular antenna. The center-fed systems are less critical as to length.

On harmonics, the end-fed and center-fed antennas will not have the same directional characteristics, as explained in the text.

When the same antenna is used for work in several bands, it must be realized that the directional characteristic will vary with the band in use.

**Simple Systems**

The most practical simple multiband antenna is one that is a half-wavelength long at the lowest frequency and is fed either at the center or one end with an open-wire line. Although the standing-wave ratio on the feedline will not approach 1.0 on any band, if the losses in the line are low the system will be efficient. From the standpoint of reduced feedline radiation, a center-fed system is superior to one that is end-fed, but the end-fed arrangement is often more convenient and should not be ignored as a possibility. The center-fed antenna will not have the same radiation pattern as an end-fed one of the same length, except on frequencies where the over-all length of the antenna is a half-wavelength or less. The end-fed antenna acts like a long-wire antenna on all bands (for which it is longer than a half-wavelength), but the center-fed one acts like two antennas of half that length fed in phase. For example, if a full-wavelength antenna is fed at one end, it will have a radiation

pattern as shown in Fig. 10-55, but if it is fed in the center the pattern will be somewhat similar to Fig. 10-47, with the maximum radiation broadside to the wire. Either antenna is a good radiator, but if the radiation pattern is a factor, the point of feed must be considered.

Since multiband operation of an antenna does not permit matching of the feedline, some attention must be paid to the length of the feedline if convenient transmitter-coupling arrangements are to be obtained. Table 10-II gives some suggested antenna and feeder lengths for multiband operation. In general, the length of the feedline should be some integral multiple of a quarter wavelength at the lowest frequency.

**Antennas for Restricted Space**

If the space available for the antenna is not large enough to accommodate the length necessary for a half-wave at the lowest frequency to be used, quite satisfactory operation can be secured by using a shorter antenna and making up the missing length in the feeder system. The antenna itself may be as short as a quarter wavelength and still radiate fairly well, although of course it will not be as effective as one a half-wave long. Nevertheless, such a system is useful where operation on the desired band otherwise would be impossible.

Resonant feeders are a practical necessity with such an antenna system, and a center-fed antenna will give best all-around performance. With end feed the feeder currents become badly unbalanced.

With center feed practically any convenient length of antenna can be used, if the feeder length is adjusted to accommodate at least

**TABLE 10-III**  
**Antenna and Feeder Lengths for Short Multiband Antennas, Center-Fed**

Antenna Length (ft.)	Feeder Length (ft.)	Band	Type of Tuning
100	38	3.5 Mc. 7 Mc. 14 Mc. 28 Mc.	parallel series series series or parallel
67.5	34	3.5 Mc. 7 Mc. 14 Mc. 28 Mc.	series parallel parallel parallel
50	13	7 Mc. 14 Mc. 28 Mc.	parallel parallel parallel
33	51	7 Mc. 14 Mc. 28 Mc.	parallel parallel parallel
33	31	7 Mc. 14 Mc. 28 Mc.	parallel series parallel

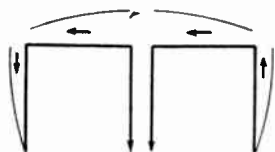


Fig. 10-59 — Folded arrangement for shortened antennas. The total length is a half-wave, not including the feeders. The horizontal part is made as long as convenient and the ends dropped down to make up the required length. The ends may be bent back on themselves like feeders to cancel radiation partially. The horizontal section should be at least a quarter wave long.

one half-wave around the whole system.

A practical antenna of this type can be made as shown in Fig. 10-58. Table 10-III gives a few recommended lengths. However, the antenna can be made any convenient length, provided the total length of wire is a half-wavelength at the lowest frequency, or an integral multiple of a half-wavelength.

### Bent Antennas

Since the field strength at a distance is proportional to the current in the antenna, the

high-current part of a half-wave antenna (the center quarter wave, approximately) does most of the radiating. Advantage can be taken of this fact when the space available does not permit erecting an antenna a half-wave long. In this case the ends may be bent, either horizontally or vertically, so that the total length equals a half-wave, even though the straightaway horizontal length may be as short as a quarter wave. The operation is illustrated in Fig. 10-59. Such an antenna will be a somewhat better radiator than a quarter-wavelength antenna on the lowest frequency, but is not so desirable for multiband operation because the ends play an increasingly important part as the frequency is raised. The performance of the system in such a case is difficult to predict, especially if the ends are vertical (the most convenient arrangement) because of the complex combination of horizontal and vertical polarization which results as well as the dissimilar directional characteristics. However, the fact that the radiation pattern is incapable of prediction does not detract from the general usefulness of the antenna.

## Long-Wire Directive Arrays

### THE "V" ANTENNA

It has been emphasized that, as the antenna length is increased, the lobe of maximum radiation makes a more acute angle with the

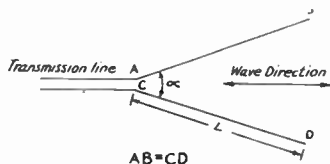


Fig. 10-60 — The basic "V" antenna, made by combining two long wires.

wire. Two such wires may be combined in the form of a horizontal "V" so that the main lobes from each wire will reinforce along a line bisecting the angle between the wires. This increases both gain and directivity, since the lobes in directions other than along the bisector cancel to a greater or lesser extent. The horizontal "V" antenna therefore transmits best in either direction (is bidirectional) along a line bisecting the "V" made by the two wires. The power gain depends upon the length of the wires. Provided the necessary space is available, the "V" is a simple antenna to build and operate. It can also be used on harmonics, so that it is suitable for multiband work. The "V" antenna is shown in Fig. 10-60.

Fig. 10-61 shows the dimensions that should be followed for an optimum design to obtain maximum power gain for different-sized "V" antennas. The longer systems

give good performance in multiband operation. Angle  $\alpha$  is approximately equal to twice the angle of maximum radiation for a single wire equal in length to one side of the "V."

The wave angle referred to in Fig. 10-61 is the vertical angle of maximum radiation. Tilting the whole horizontal plane of the "V" will tend to increase the low-angle radiation off the low end and decrease it off the high end.

The gain increases with the length of the

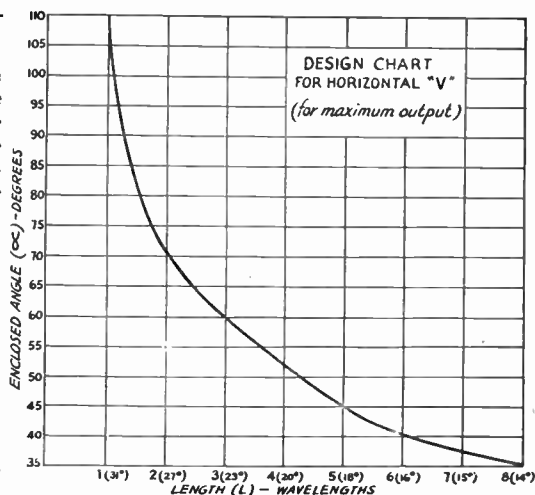


Fig. 10-61 — Design chart for horizontal "V" antennas, giving the enclosed angle between sides vs. the length of the wires. Values in parentheses represent approximate wave angle for height of one-half wavelength.

wires, but is not exactly twice the gain for a single long wire as given in Fig. 10-54. In the longer lengths the gain will be somewhat increased, because of mutual coupling between the wires. A "V" eight wavelengths on a leg, for instance, will have a gain of about 12 db. over a half-wave antenna, whereas twice the gain of a single eight-wavelength wire would be only approximately 9 db.

The two wires of the "V" must be fed out of phase, for correct operation. A resonant line may simply be attached to the ends, as shown in Fig. 10-60. Alternatively, a quarter-wave matching section may be employed and the antenna fed through a nonresonant line. If the antenna wires are made multiples of a half-wave in length (use Equation 10-N for computing the length), the matching section will be closed at the free end. A stub can be connected across the resonant line to provide a match, as described later.

● THE RHOMBIC ANTENNA

The horizontal rhombic or "diamond" antenna is shown in Fig. 10-62. Like the "V," it requires a great deal of space for erection, but it is capable of giving excellent gain and directivity. It also can be used for multiband operation. In the terminated form shown in Fig. 10-62, it operates like a nonresonant transmission line, without standing waves, and is unidirectional. It may also be used without the terminating resistor, in which case there are standing waves on the wires and the antenna is bidirectional.

The important quantities influencing the design of the rhombic antenna are shown in Fig. 10-62. While several design methods may be used, the one most applicable to the conditions existing in amateur work is the so-called "compromise" method. The chart of Fig. 10-63 gives design information based on a given length and wave angle to determine the remaining optimum dimensions for best operation. Curves for values of length of two, three

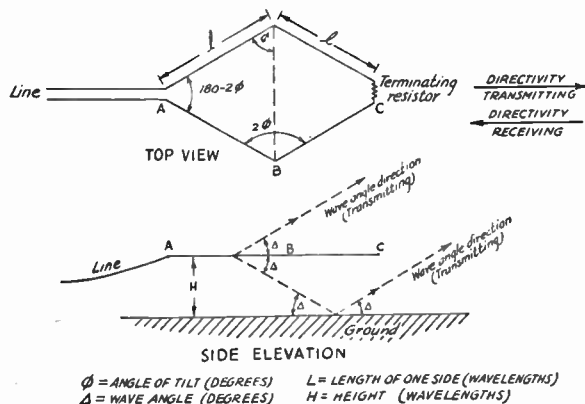


Fig. 10-62 — The horizontal rhombic or diamond antenna, terminated. Important design dimensions are indicated; details in text.

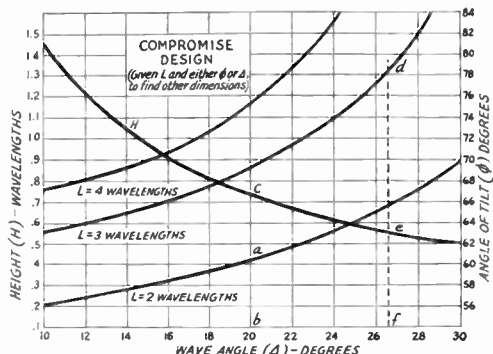


Fig. 10-63 — Compromise-method design chart for rhombic antennas of various leg lengths and wave angles. The following examples illustrate the use of the chart:

- (1) Given:
  - Length ( $L$ ) = 2 wavelengths.
  - Desired wave angle ( $\Delta$ ) =  $20^\circ$ .
  - To Find:  $H, \phi$ .
  - Method: Draw vertical line through point  $a$  ( $L = 2$  wavelengths) and point  $b$  on abscissa ( $\Delta = 20^\circ$ ). Read angle of tilt ( $\phi$ ) for point  $a$  and height ( $H$ ) from intersection of line  $ab$  at point  $c$  on curve  $H$ .
  - Result:
    - $\phi = 60.5^\circ$ .
    - $H = 0.73$  wavelength.
- (2) Given:
  - Length ( $L$ ) = 3 wavelengths.
  - Angle of tilt ( $\phi$ ) =  $78^\circ$ .
  - To Find:  $H, \Delta$ .
  - Method: Draw a vertical line from point  $d$  on curve  $L = 3$  wavelengths at  $\phi = 78^\circ$ . Read intersection of this line on curve  $H$  (point  $e$ ) for height, and intersection at point  $f$  on the abscissa for  $\Delta$ .
  - Result:
    - $H = 0.56$  wavelength.
    - $\Delta = 26.6^\circ$ .

and four wavelengths are shown, and any intermediate values may be interpolated.

With all other dimensions correct, an increase in length causes an increase in power gain and a slight reduction in wave angle. An increase in height also causes a reduction in wave angle and an increase in power gain, but not to the same extent as a proportionate increase in length. For multiband work, it is satisfactory to design the rhombic antenna on the basis of 14-Mc. operation, which will permit work from the 7- to 28-Mc. bands as well.

A value of 800 ohms is correct for the terminating resistor for any properly-constructed rhombic, and the system behaves as a pure resistive load under this condition. The terminating resistor must be capable of safely dissipating one-half the power output (to eliminate the rear pattern), and should be noninductive. Such a resistor may be made up from a long 800-ohm transmission line using

resistance wire. If the carbon rod or a similar form of lumped resistance is used, the device should be suitably protected from weather effects, i.e., it should be covered with a good asphaltic compound and sealed in a small lightweight box or fiber tube. Suitable nonreactive terminating resistors are also available commercially.

For feeding the antenna, the antenna impedance will be matched by an 800-ohm line, which may be constructed from No. 16 wire spaced 20 inches or from No. 18 wire spaced 16 inches. The 800-ohm line is somewhat ungainly to install, however, and may be replaced by an ordinary 600-ohm line with only a negligible mismatch. Alternatively, a matching section may be installed between the antenna terminals and a low-impedance

line. However, when such an arrangement is used, it will be necessary to change the matching-section constants for each different band on which operation is contemplated.

The same design details apply to the unterminated rhombic as to the terminated type. When used without a terminating resistor, the system is bidirectional. Resonant feeders are preferable for the unterminated rhombic. A nonresonant line may be used by incorporating a matching section at the antenna, but is not readily adaptable to satisfactory multiband work.

Rhombic antennas will give a power gain of 8 to 12 db. or more for log lengths of two to four wavelengths, when constructed according to the charts given. In general, the larger the antenna, the greater the power gain.

## Directive Arrays with Driven Elements

By combining individual half-wave antennas into an array with suitable spacing between the antennas (called **elements**) and feeding power to them simultaneously, it is possible to make the radiated fields from the individual elements add in a favored direction, thus increasing the field strength in that direction as compared to that produced by one antenna element alone. In other directions the fields will more or less oppose each other, giving a reduction in field strength. Thus a power gain in the desired direction is secured at the expense of a power reduction in other directions.

Besides the spacing between elements, the instantaneous direction of current flow (*phase*)

increases with the number of elements. The proportionality between gain and number of elements is not simple, however. The gain depends upon the effect that the spacing and phasing has upon the radiation resistance of the elements, as well as upon their number.

### Collinear Arrays

Simple forms of collinear arrays, with the current distribution, are shown in Fig. 10-64. The two-element array at A is popularly known as "two half-waves in phase." It will be recognized as simply a center-fed antenna operated at its second harmonic. The way in which the number of elements may be extended for increased directivity and gain is shown in Fig. 10-64B. Note that quarter-wave phasing sections are used between elements; these give the reversal in phase necessary to make the currents in individual antenna elements all flow in the same direction at the same instant.

Any phase-reversing section may be used as a quarter-wave matching section for attaching a nonresonant feeder, or a resonant transmission line may be substituted for any of the quarter-wave sections. Also, the antenna may be ended by any of the systems previously described, or any element may be centered. It is best to feed at the center of the array, so that the energy will be distributed as uniformly as possible among the elements.

The gain and directivity depend upon the number of elements and their spacing, center-to-center. This is shown by Table 10-IV. Although three-quarter wave spacing gives greater gain, it is difficult to construct a suitable phase-reversing system when the ends of the antenna elements are widely separated. For this reason, the half-wave spacing is most generally used in actual practice.

Collinear arrays may be mounted either horizontally or vertically. Horizontal mount-

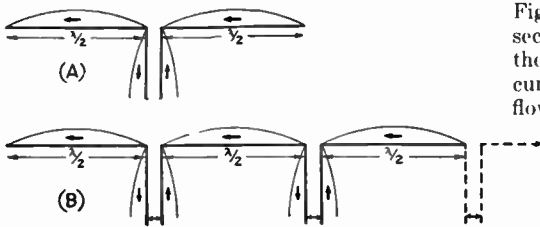


Fig. 10-64 — Collinear half-wave antennas in phase. The system at A is generally known as "two half-waves in phase." B is an extension of the system; in theory the number of elements may be carried on indefinitely, but practical considerations usually limit the elements to four.

in individual elements determines the directivity and power gain. There are several methods of arranging the elements. If they are strung end to end, so that all lie on the same straight line, the elements are said to be **collinear**. If they are parallel and all lying in the same plane, the elements are said to be **broadside** when the phase of the current is the same in all, and **end-fire** when the currents are not in phase. Elements that receive power from the transmitter through the transmission line are called **driven elements**.

The power gain of a directive system in-

**TABLE 10-IV**  
**Theoretical Gain of Collinear Half-Wave Antennas**

Spacing between centers of adjacent half-waves	Number of half-waves in array vs. gain in db.				
	2	3	4	5	6
$\frac{1}{2}$ wave	1.8	3.3	4.5	5.3	6.2
$\frac{3}{4}$ wave	3.2	4.8	6.0	7.0	7.8

ing gives increased horizontal directivity, while the vertical directivity remains the same as for a single element at the same height. Vertical mounting gives the same horizontal pattern as a single element, but concentrates the radiation at low angles. It is seldom practicable to use more than two elements vertically at frequencies below 14 Mc. because of the excessive height required.

**Broadside Arrays**

Parallel antenna elements with currents in phase may be combined as shown in Fig. 10-65 to form a broadside array, so named because

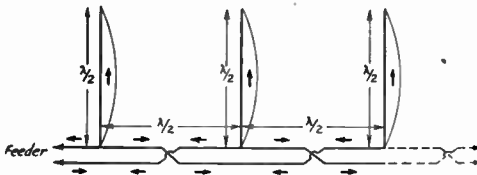


Fig. 10-65 — Broadside array using parallel half-wave elements. Arrows indicate the direction of current flow. Transposition of the feeders is necessary to bring the antenna currents in phase. Any reasonable number of elements may be used. The array is bidirectional, with maximum radiation "broadside" or perpendicular to the antenna plane (perpendicularly through this page).

the direction of maximum radiation is broadside to the plane containing the antennas. Again the gain and directivity depend upon the number of elements and the spacing, the gain for different spacings being shown in Fig. 10-66. Half-wave spacing generally is used, since it simplifies the problem of feeding the system when the array has more than two elements. Table 10-V gives theoretical gain as a function of the number of elements with half-wave spacing.

Broadside arrays may be suspended either with the elements all vertical or with them horizontal and one above the other (stacked). In the former case the horizontal pattern becomes quite sharp, while the vertical pattern is the same as that of one element alone. If the array is suspended horizontally, the horizontal pattern is equivalent to that of one element while the vertical pattern is sharpened, giving low-angle radiation.

Broadside arrays may be fed either by resonant transmission lines or through quarter-wave matching sections and nonresonant lines. In Fig. 10-65, note the "crossing over" of the

feeders, which is necessary to bring the elements into proper phase relationship.

**Combined Broadside and Collinear Arrays**

Broadside and collinear arrays may be combined to give both horizontal and vertical directivity, as well as additional gain. The general plan of constructing such antennas is shown in Fig. 10-67. The lower angle of radiation resulting from stacking elements in the vertical plane is desirable at the higher frequencies. In general, doubling the number of elements in an array by stacking will raise the gain from 2 to 4 db., depending upon whether vertical or horizontal elements are used — that is, whether the stacked elements are of the broadside or collinear type.

The arrays in Fig. 10-67 are shown fed from one end, but this is not especially desirable in the case of large arrays. Better distribution of energy between elements, and hence better over-all performance, will result when the feeders are attached as nearly as possible to the center of the array. Thus, in the eight-element array at A, the feeders could be introduced at the middle of the transmission line between the second and third set of elements, in which case the connecting line would not be transposed between the second and third set of elements. Alternatively, the antenna could be constructed with the transpositions as shown and the feeder connected between the adjacent ends of either the second or third pair of collinear elements.

A four-element array of the general type shown in Fig. 10-67B, known as the "lazy-H" antenna, has been quite frequently used. This arrangement is shown, with the feed point indicated, in Fig. 10-68.

**End-Fire Arrays**

Fig. 10-69 shows a pair of parallel half-wave elements with currents out of phase. This is known as an end-fire array, because it radiates best along the line of the antennas, as shown.

The end-fire array may be used either ver-

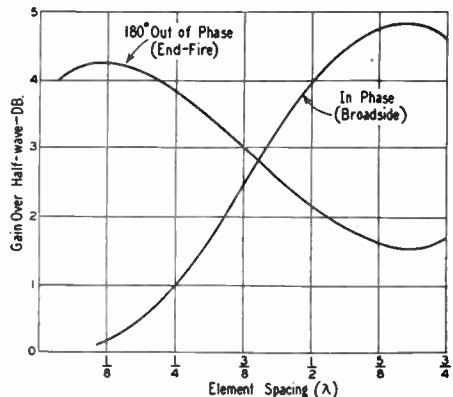


Fig. 10-66 — Gain vs. spacing for two parallel half-wave elements combined as either broadside or end-fire arrays.



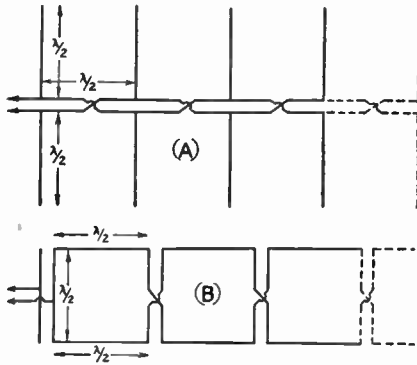


Fig. 10-67 — Combination broadside and collinear arrays. A, with vertical elements; B, with horizontal elements. Both arrays give low-angle radiation. Two or more sections may be used. The gain in db. will be equal, approximately, to the sum of the gain for one set of broadside elements (Table 10-V) plus the gain of one set of collinear elements (Table 10-IV). For example, in A each broadside set has four elements (gain 7 db.) and each collinear set two elements (gain 1.8 db.), giving a total gain of 8.8 db. In B, each broadside set has two elements (gain 4 db.) and each collinear set three elements (gain 3.3 db.), making the total gain 7.3 db. The result is not strictly accurate, because of mutual coupling between the elements, but is good enough for practical purposes.

tically or horizontally (elements at the same height), and is well adapted to amateur work because it gives maximum gain with relatively close element spacing. Fig. 10-66 shows how the gain varies with spacing. End-fire elements may be combined with additional collinear and broadside elements to give a further increase in gain and directivity.

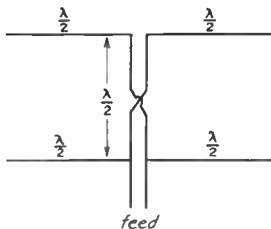


Fig. 10-68 — A four-element combination broadside-collinear array, popularly known as the "lazy-11" antenna. A closed quarter-wave stub may be used at the feed point to match into a 600-ohm transmission line, or resonant feeders may be attached at the point indicated. The gain over a half-wave antenna is 5 to 6 db.

Either resonant or nonresonant lines may be used with this type of array. Nonresonant lines preferably are matched to the antenna through a quarter-wave matching section or phasing stub.

**Phasing**

Figs. 10-67 and 10-69 illustrate a point in connection with feeding a phased antenna system which sometimes is confusing. In Fig. 10-69, when the transmission line is connected as at A there is no crossover in the line connecting the two antennas, but when the transmission line is connected to the center of the

connecting line the crossover becomes necessary (B). This is because in B the two halves of the connecting line are simply branches of the same line. In other words, even though the connecting line in B is a half-wave in length, it is not actually a half-wave line but two quarter-wave lines in parallel. The same thing is true of the untransposed line of Fig. 10-67. Note that, under these conditions, the antenna elements are in phase when the line is not transposed, and out of phase when the transposition is made. The opposite is the case when the half-wave line simply joins two antenna elements and does not have the feedline connected to its center, as in Fig. 10-65.

**Adjustment of Arrays**

With arrays of the types just described, using half-wave spacing between elements, it

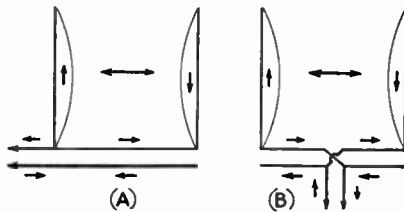


Fig. 10-69 — End-fire arrays using parallel half-wave elements. The elements are shown with half-wave spacing to illustrate feeder connections. In practice, closer spacings are desirable, as shown by Fig. 10-66. Direction of maximum radiation is shown by the large arrows.

will usually suffice to make the length of each element that given by Equations 10-I or 10-J. The half-wave phasing lines between the parallel elements should be of open-wire construction, and their length can be calculated from:

$$\text{Length of half-wave line (feet)} = \frac{480}{\text{Freq. (Mc.)}} \tag{10-O}$$

Example: A half-wavelength phasing line for 28.8 Mc. would be  $\frac{480}{28.8} = 16.66$  feet = 16 feet 8 inches.

The spacing between elements can be made equal to the length of the phasing line. No special adjustments of line or element length or spacing are needed, provided the formulas are followed closely.

TABLE 10-V Theoretical Gain vs. Number of Broadside Elements (Half-Wave Spacing)	
No. of elements	Gain
2	4 db.
3	5.5
4	7
5	8
6	9

With collinear arrays of the type shown in Fig. 10-64B, the same formula may be used for the element length, while the length of the quarter-wave phasing section can be found from the following formula:

$$\text{Length of quarter-wave line (feet)} = \frac{240}{\text{Freq. (Mc.)}} \quad (10-P)$$

Example: A quarter-wavelength phasing line for 14.25 Mc. would be  $\frac{240}{14.25} = 16.84$  feet = 16 feet 10 inches.

If the array is fed in the center it should not be necessary to make any particular adjustments, although, if desired, the whole system can be resonated by connecting an r.f. ammeter in the shorting link of each phasing section and moving the link back and forth to find the maximum-current position. This refinement is hardly necessary in practice, however, so long as all elements are the same length and the system is symmetrical.

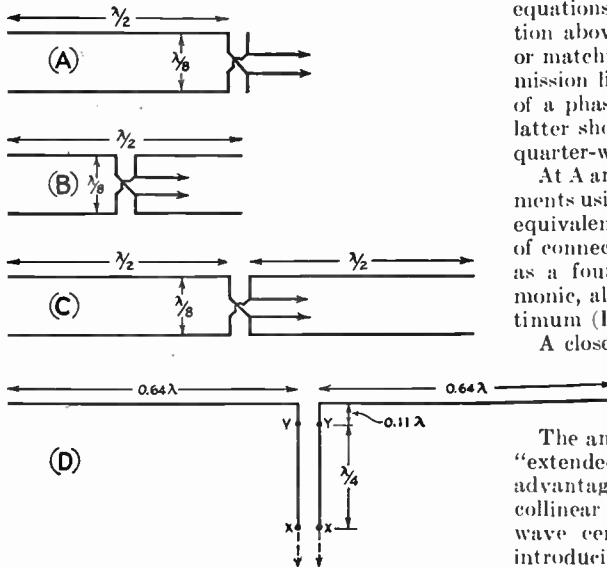


Fig. 10-70 — Simple directive-antenna systems. A is a two-element end-fire array; B is the same array with center feed, which permits use of the array on the second harmonic, where it becomes a four-element array with quarter-wave spacing. C is a four-element end-fire array with  $\frac{1}{8}$ -wave spacing. D is a simple two-element broadside array using extended in-phase antennas ("extended double-Zepp"). The gain of A and B is slightly over 4 db. On the second harmonic, B will give about 5-db. gain. With C, the gain is approximately 6 db., and with D, approximately 3 db. In A, B and C, the phasing line contributes about  $\frac{1}{16}$  wavelength to the transmission line; when B is used on the second harmonic, this contribution is  $\frac{1}{8}$  wavelength. Alternatively, the antenna ends may be bent to meet the transmission line, in which case each feeder is simply connected to one antenna. In D, points Y-Y indicate a quarter-wave point (high current) and X-X a half-wave point (high voltage). The line may be extended in multiples of quarter waves if resonant feeders are to be used. A, B and C may be suspended on wooden spreaders. The plane containing the wires should be parallel to the ground.

The phasing sections can be made of 300-ohm Twin-Lead, if low power is used. However, the lengths of the phasing sections must be only 84 per cent of the length obtained in the two formulas above.

Example: The half-wavelength line for 28.8 Mc. would become  $0.84 \times 16.66 = 13.99$  feet = 14 feet 0 inches.

Using Twin-Lead for the phasing sections is most useful in arrays such as that of Fig. 10-64B, or any other system in which the element spacing is not controlled by the length of the phasing section.

**Simple Arrays**

Several simple directive-antenna systems using driven elements have achieved rather wide use among amateurs. Four of these systems are shown in Fig. 10-70. Tuned feeders are assumed in all cases; however, a matching section readily can be substituted if a non-resonant transmission line is preferred. Dimensions given are in terms of wavelength; actual lengths can be calculated from the equations for the antenna and from the equation above for the resonant transmission line or matching section. In cases where the transmission line proper connects to the midpoint of a phasing line, only half the length of the latter should be added to the line to find the quarter-wave point.

At A and B are two-element end-fire arrangements using close spacing. They are electrically equivalent; the only difference is in the method of connecting the feeders. B may also be used as a four-element array on the second harmonic, although the spacing is not quite optimum (Fig. 10-66) for such operation.

A close-spaced four-element array is shown at C. It will give about 2 db. more gain than the two-element array.

The antenna at D, commonly known as the "extended double-Zepp," is designed to take advantage of the greater gain possible with collinear antennas having greater than half-wave center-to-center spacing, but without introducing feed complications. The elements are made longer than a half-wave in order to bring this about. The gain is 3 db. over a single half-wave antenna, and the broadside directivity is fairly sharp.

The antennas of A and B may be mounted either horizontally or vertically; horizontal suspension (with the elements in a plane parallel to the ground) is recommended, since this tends to give low-angle radiation without an unduly sharp horizontal pattern. Thus these systems are useful for coverage over a wide horizontal angle. The system at C, when mounted horizontally, will have a sharper horizontal pattern than the two-element arrays because of the effect of the collinear arrangement. The vertical pattern, however, will be the same as that of the antennas in A and B.

Matching the Antenna to the Line

Except in the several cases of half-wave antennas mentioned earlier, most antenna systems do not have center impedances that readily match open-wire lines or available solid-dielectric ones. However, any antenna can be matched to practically any line by any of the several means to be described. The matching is accomplished by first resonating the antenna to the proper frequency and then introducing either a matching transformer between the antenna and the line or by applying corrective stubs to the line.

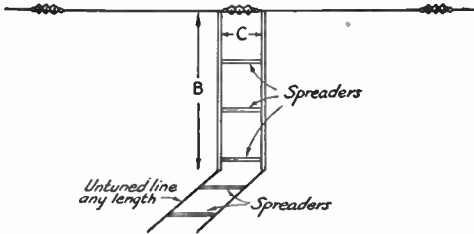


Fig. 10-71 - The "Q" antenna, using a quarter-wave impedance-matching section with close-spaced conductors.

An impedance mismatch of 10 or 20 per cent is of little consequence so far as power transfer to the antenna is concerned. It is relatively easy to get the standing-wave ratio down to 1.5- or 2-to-1, a perfectly satisfactory condition in practice. Of considerably greater importance is the necessity for getting the currents in the two wires balanced, both as to amplitude and phase. If the currents are not the same at corresponding points on adjacent wires and the loops and nodes do not also occur at corresponding points, there will be considerable radiation loss. Perfect balance can be brought about only by perfect symmetry in the line, particularly with respect to ground. This symmetry should extend to the coupling apparatus at the transmitter.

In the following discussion of ways in which different types of lines may be matched to the antenna, a half-wave antenna is used as an example. Other types of antennas may be treated by the same methods, making due allowance for the order of impedance that appears at the end of the line when more elaborate systems are used.

"Q"-Section Transformer

The impedance of a two-wire line of ordinary construction (400 to 600 ohms) can be matched to the impedance of the center of a half-wave antenna by utilizing the impedance-transforming properties of a quarter-wave line, Equation 10-B. The matching section must have low surge impedance and therefore is commonly constructed of large-diameter conductors such as aluminum or copper tubing, with fairly-close spacing. This system is known as the "Q"

antenna. It is shown in Fig. 10-71. Important dimensions are the length of the antenna itself, the length of the matching section, *B*, the spacing between the two conductors of the matching section, *C*, and the impedance of the untuned transmission line connected to the lower end of the matching section.

The required characteristic impedance for the matching section is

$$Z_m = \sqrt{Z_1 Z_2} \quad (10-B)$$

where *Z*<sub>1</sub> and *Z*<sub>2</sub> are the antenna and feedline impedances.

Example: To match a 600-ohm line to an antenna presenting a 72-ohm load, the quarter-wave matching section would require a characteristic impedance of  $\sqrt{72 \times 600} = \sqrt{43,200} = 208$  ohms.

The spacings between conductors of various sizes of tubing and wire for different surge impedances are given in graphical form in Fig. 10-14. With 1/2-inch tubing, the spacing should be 1.5 inches for an impedance of 208 ohms.

The length of the matching section, *B*, should be equal to a quarter wavelength, and is given by Equation 10-G. The length of the antenna can be calculated from Equations 10-I or 10-J.

This system has the advantage of the simplicity of adjustment of the 75-ohm feeder

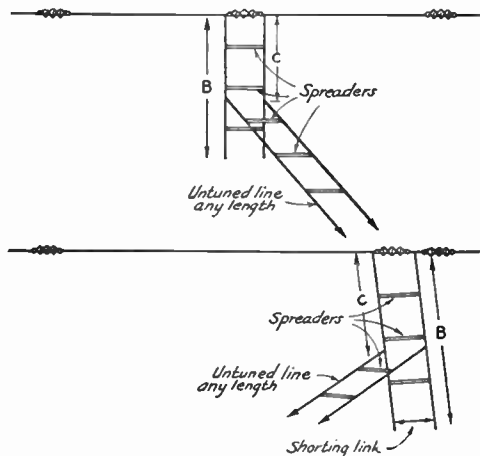


Fig. 10-72 - Antenna systems with quarter-wave open-wire linear impedance-matching transformers.

system and at the same time the superior insulation of an open-wire system.

Linear Transformers

Fig. 10-72 shows two methods of coupling a nonresonant line to an antenna through a quarter-wave linear transformer or matching section. In the case of the center-fed antenna, the free end of the matching section, *B*, is open (high impedance) if the other end is connected

to a low-impedance point (current loop) on the antenna. With the end-fed antenna, the free end of the matching section is closed through a shorting bar or link; this end of the section has low impedance, since the other end is connected to a high-impedance point on the antenna.

When the connection between the matching section and the antenna is unbalanced, as in the end-fed system, it is important that the antenna be the right length for the operating frequency if a good match is to be obtained. The balanced center-fed system is less critical in this respect. The shorting-bar method of tuning the center-fed system to resonance may be used if the matching section is extended to a half-wavelength, bringing a current loop at the free end.

In the center-fed system, the antenna and matching section should be cut to lengths found from Equations 10-I, 10-N and 10-P. Any necessary on-the-ground adjustment can be made by adding to or clipping off the open ends of the matching section. In the end-fed system the matching section can be adjusted

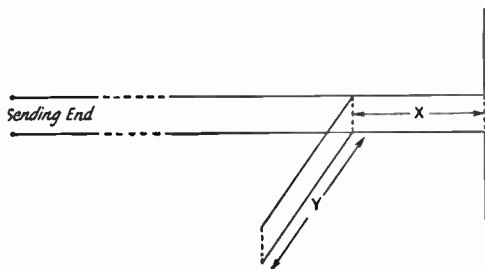


Fig. 10-73 — When antenna and transmission line differ in impedance, they may be matched by a short length of transmission line, *Y*, called a stub. Determination of the critical dimensions, *X* and *Y*, for proper matching depends on whether the stub is open or closed at the end.

by making the line a little longer than necessary and adjusting the system to resonance by moving the shorting link up and down. Resonance can be determined by exciting the antenna at the proper frequency from a temporary antenna near by and measuring the current in the shorting bar by a low-range r.f. ammeter or galvanometer using one of the devices of this type described in the chapter on measurements. The position of the bar should be adjusted for maximum current reading. This should be done before the transmission line is attached to the matching section.

The position of the line taps will depend upon the impedance of the line as well as on the antenna impedance at the point of connection. The procedure is to take a trial point, apply power to the transmitter, and then check the transmission line for standing waves. This can be done by measuring the current in, or voltage along, the wires. At any one position along the line the currents in the two wires should be identical. Readings taken at intervals of a

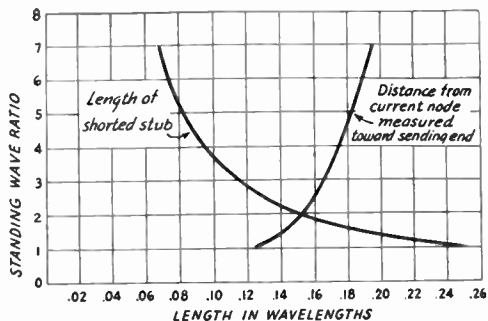


Fig. 10-74 — Graph for determining position and length of a shorted stub. Dimensions may be converted to linear units after values have been taken from the graph.

quarter wavelength will indicate whether or not standing waves are present.

It will not usually be possible to obtain complete elimination of standing waves when the matching stub is exactly resonant, but the line taps should be adjusted for the smallest obtainable standing-wave ratio. Then a further "touching up" of the matching-stub tuning will eliminate the remaining standing waves, provided the adjustments are carefully made. The stub must be readjusted, because when resonant it exhibits some reactance as well as resistance at all points except at the ends, and a slight lengthening or shortening of the stub is necessary to tune out this reactance.

**Matching Stubs**

The operation of the quarter-wave matching transformer of Fig. 10-72 may be considered from another — and more general — viewpoint. Suppose that section *C* is looked upon simply as a continuation of the transmission line. Then the "free" end of the transformer becomes a "stub" line, shunting a section of the main transmission line. From this viewpoint, matching the line to the antenna becomes a matter of selecting the right type and length of stub and attaching it to the proper spot along the line.

Referring to Fig. 10-73, at any distance (*X*) from the antenna, the line will have an imped-

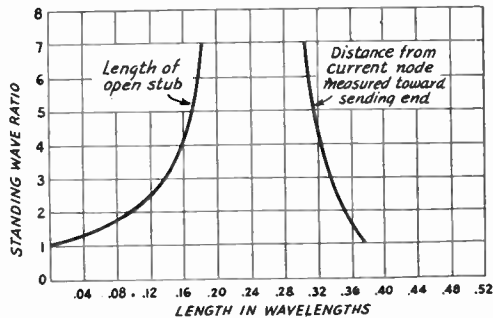


Fig. 10-75 — Graph for determining position and length of an open stub. Dimensions may be converted to linear units after values have been taken from the graph.

ance that may be considered to be made up of reactance (either inductive or capacitive) and resistance, in parallel. The reactive component can be eliminated by shunting the line at distance  $X$  from the antenna with another reactance equal in value but opposite in sign to the reactance presented by the line at that point. If distance  $X$  is such that the line presents an inductive reactance, a corresponding shunting capacitive reactance will be required.

The required compensating reactance may be supplied by shunting the line with a stub cut to proper length,  $Y$ . With the reactances canceled only a pure resistance remains as a termination for the remainder of the line between the sending end and the stub, and this resistance can be adjusted to match the characteristic impedance of the line by adjusting the distance  $X$ .

Distances  $X$  and  $Y$  may be determined experimentally, but since their values are interdependent the cut-and-try method is somewhat laborious. If the standing-wave ratio and the positions of the current loops and nodes can be measured, the length and position of the stub can be found from Figs. 10-74 and 10-75.

While it is relatively easy to locate the position of the current (or voltage) loops and nodes by examining the line with a neon bulb, r.f. galvanometer, or pick-up loop and crystal detector, other means are more direct for determining the standing-wave ratio. Several devices of this type are described in Chapter

Sixteen, and the use of these also affords a simple method for determining the location of current loops (voltage nodes). With the meter or indicator in the line near the transmitter, points will be found on the transmission line where touching the line with a screwdriver will have a minimum effect on the meter indication. These points correspond to voltage nodes.

Once the standing-wave ratio is known, the length and position of the stub, in terms of wavelength, can be found directly from Figs. 10-74 and 10-75. The wavelength in feet for any frequency can be found from Equation 10-0.

### Measuring Standing Waves

In adjusting a "Q-match" or linear transformer, or a delta or "T"-match to an antenna, one of the standing-wave indicators described in Chapter Sixteen should be used. If 300-ohm Twin-Lead is used, the simple "twin-lamp" indicator is the most convenient and the simplest to use. For lines of other impedance, or for coaxial line, the Micro-Match type or the bridge type should be used. In any event, the absolute value of standing-wave ratio is not as important as the proper adjustment for a minimum ratio, since ratios of 1.5-to-1 or less represent good amateur practice.

Where two-wire lines are used, the standing-wave-ratio indicator should give the same reading regardless of the polarity of the transmission line — any discrepancy indicates an unbalance in the line.

## Directive Arrays with Parasitic Elements

### Parasitic Excitation

The antenna arrays previously described are bidirectional; that is, they will radiate in directions both to the "front" and to the "back" of the antenna system. If radiation is wanted in only one direction, it is necessary to use different element arrangements. In most of these arrangements the additional elements receive power by induction or radiation from the driven element, generally called the "antenna," and reradiate it in the proper phase relationship to achieve the desired effect. These elements are called *parasitic* elements, as contrasted to the driven elements which receive power directly from the transmitter through the transmission line. They are widely used to give additional gain and directivity to simple antennas.

The parasitic element is called a *director* when it reinforces radiation on a line pointing to it from the antenna, and a *reflector* when the reverse is the case. Whether the parasitic element is a director or reflector depends upon the parasitic-element tuning (which usually is adjusted by changing its length) and, particularly when the element is self-resonant, upon the spacing between it and the antenna.

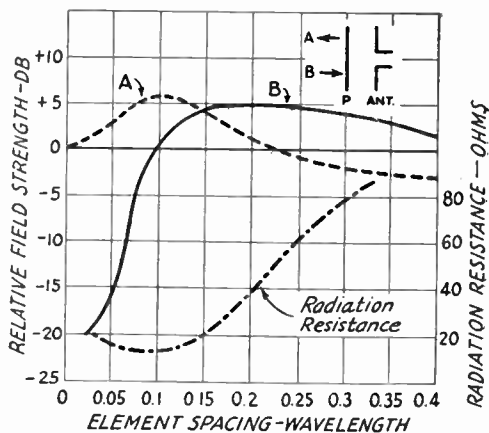


Fig. 10-76 — Gain vs. element spacing for an antenna and one parasitic element. The reference point, 0 db., is the field strength from a half-wave antenna alone. The greatest gain is in direction  $A$  at spacings of less than 0.14 wavelength, and in direction  $B$  at greater spacings. The front-to-back ratio is the difference in db. between curves  $A$  and  $B$ . Variation in radiation resistance of the driven element also is shown. These curves are for a self-resonant parasitic element. At most spacings the gain as a reflector can be increased by slight lengthening of the parasitic element; the gain as a director can be increased by shortening. This also improves the front-to-back ratio.

**Gain vs. Spacing**

The gain of an antenna-reflector or an antenna-director combination varies chiefly with the spacing between the elements. The way in which gain varies with spacing is shown in Fig. 10-76, for the special case of self-resonant parasitic elements. This chart also shows how the attenuation to the "rear" varies with spacing. The same spacing does not necessarily give both maximum forward gain and maximum backward attenuation. Backward attenuation is desirable when the antenna is used for receiving, since it greatly reduces interference coming from the opposite direction to the desired signal.

**Element Lengths**

The antenna length is given by the formula for a half-wavelength antenna. The director and reflector lengths must be determined experimentally for maximum performance. The preferable method is to aim the antenna at a receiver a mile or more distant and have an observer check the signal strength (on the receiver S-meter) while the reflector or director is adjusted a few inches at a time, until the length which gives maximum signal is found. The attenuation may be similarly checked, the length being adjusted for minimum signal. In general, for best front-to-back ratio the length of a director will be about 4 per cent less than that of the antenna. The reflector will be about 5 per cent longer than the antenna.

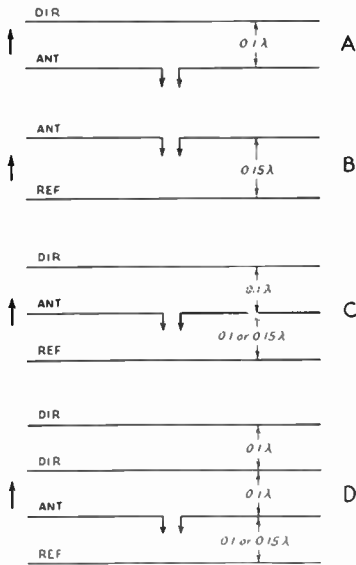


Fig. 10-77 — Half-wave antennas with parasitic elements. A, with director; B, with reflector; C, with both director and reflector; D, two directors and one reflector. Gain is approximately as shown by Fig. 10-76, in the first two cases, and depends upon the spacing and length of the parasitic element. In the three- and four-element arrays a reflector spacing of 0.15 wavelength will give slightly more gain than 0.1-wavelength spacing. Arrows show the direction of maximum radiation.

**Simple Systems: the Rotary Beam**

Four practical combinations of antenna, reflector and director elements are shown in Fig. 10-77. Spacings which give maximum gain or maximum front-to-back ratio (ratio of power radiated in the desired direction to power radiated in the opposite direction) may be taken from Fig. 10-76. In the chart, the front-to-back ratio in db. will be the sum of gain and attenuation at the same spacing.

Systems of this type are popular for rotary-beam antennas, where the entire antenna system is rotated, to permit its gain and directivity to be utilized for any compass direction. They may be mounted either horizontally (with the plane containing the elements parallel to the earth) or vertically.

Arrays using more than one parasitic element, such as those shown at C and D in Fig. 10-77, will give more gain and directivity than is indicated for a single reflector or director by the curves of Fig. 10-76. The gain with a properly-adjusted three-element array (antenna, director and reflector) will be 5 to 7 db. over a half-wave antenna. Somewhat higher gain still can be secured by adding a second director to the system, making a four-element array. The front-to-back ratio is correspondingly improved as the number of elements is increased.

The elements in close-spaced (less than one-quarter wavelength element spacing) arrays preferably should be made of tubing of one-half to one-inch diameter. A conductor of large diameter not only has less ohmic resistance but also has lower Q; both these factors are important in close-spaced arrays because the impedance of the driven element usually is quite low compared to that of a single half-wave dipole. With 3- and 4-element arrays the radiation resistance of the driven element may be as low as 6 or 8 ohms, so that ohmic losses in the conductor can consume an appreciable fraction of the power. Low radiation resistance means that the antenna will work over only a small frequency range without retuning unless large-diameter conductors are used. In addition, the antenna elements should be rigid because if they are free to move with respect to each other, the array will tend to show troublesome detuning effects under windy conditions.

**Feeding Close-Spaced Arrays**

While any of the usual methods of feed may be applied to the driven element of a parasitic array, the fact that, with close spacing, the radiation resistance as measured at the center of the driven element drops to a very low value makes some systems more desirable than others. The preferred methods are shown in Fig. 10-78. Resonant feeders are not recommended for lengths greater than a half-wavelength.

The quarter- or half-wave matching stubs shown at A and B in Fig. 10-78 preferably

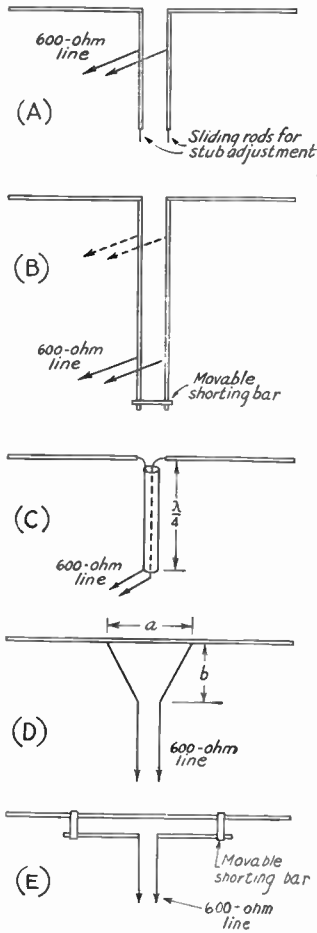


Fig. 10-78 — Recommended methods of feeding the driven antenna element in close-spaced parasitic arrays. The parasitic elements are not shown. A, quarter-wave open stub; B, half-wave closed stub; C, concentric-line quarter-wave matching section; D, delta matching transformer; E, “F” matching transformer. Adjustment details are discussed in the text.

should be constructed of tubing with rather close spacing, in the manner of the “Q” section. This lowers the impedance of the matching section and makes the position of the line taps somewhat less difficult to determine accurately. The line adjustment should be made only with the parasitic elements in place, and after the correct element lengths have been determined it should be checked to compensate for changes likely to occur because of element tuning.

The concentric-line matching section at C will work with fair accuracy into a close-spaced parasitic array of 2, 3 or 4 elements without necessity for adjustment. The line is used as an impedance-inverting transformer, and, if its characteristic impedance is 70 ohms (RG-11/U), it will give a good match to a 600-ohm line when the resistance at the termination is about 8.5 ohms. Over a range of 5 to 15 ohms

the mismatch, and therefore the standing-wave ratio, will be less than 2-to-1. The length of the quarter-wave section may be calculated from Equation 10-G.

The delta matching transformer shown at D is probably easier to install, mechanically, than any of the others. The positions of the taps (dimension *a*) must be determined experimentally, along with the length, *b*, by checking the standing-wave ratio on the line as adjustments are made. Dimension *b* should be about 15 per cent longer than *a*.

The system shown at E (“F”-match) resembles the delta match in principles of operation. It has the advantage that, with close spacing between the two parallel conductors, line radiation from the matching section is negligible whereas radiation from a delta may be considerable. It is adjusted by moving the shorting bars, keeping them equidistant from the center, until there are no standing waves on the line. The matching section may be made of the same type of conductor used for the driven element and spaced a few inches from it.

The “folded-dipole” type of antenna may be used as the driven element of a close-spaced parasitic array to secure an impedance step-up to the transmission line and also to broaden the resonance curve of the antenna. The folded dipole consists of two or more half-wave antennas connected together at the ends with the feeder connected to the center of only one of the antennas. The spacing between the parallel antennas should be small — of the order of the spacing used between wires of a transmission line. The current in the system divides in approximate proportion to the areas of the conductors, resulting in an impedance step-up at the input terminals. With two similar conductors (equal areas) the impedance step-up is 4-to-1; if there are three similar conductors (or if the one not connected to the transmission line has twice the diameter of the other) the step-up is 9-to-1; if the ratio of the areas is 3-to-1 the step-up is 16-to-1, and so on. Thus if a 3-conductor dipole (all conductors the same diameter) is used as the driven element of a four-element parasitic array the center impedance of approximately 8 ohms is multiplied by 9 and appears as approximately 72 ohms at the input terminals. Such a system therefore can be fed directly from a 70-ohm line with no additional means for matching.

Fig. 10-80 shows the impedance step-up obtained in a folded dipole when conductors of different sizes are used.

**Sharpness of Resonance**

Peak performance of a multielement parasitic array depends upon proper phasing or tuning of the elements, which can be exact for one frequency only. In the case of close-spaced arrays, which because of the low radiation resistance usually are quite sharp-tuning, the frequency range over which optimum results can be secured is only of the order of 1 or 2


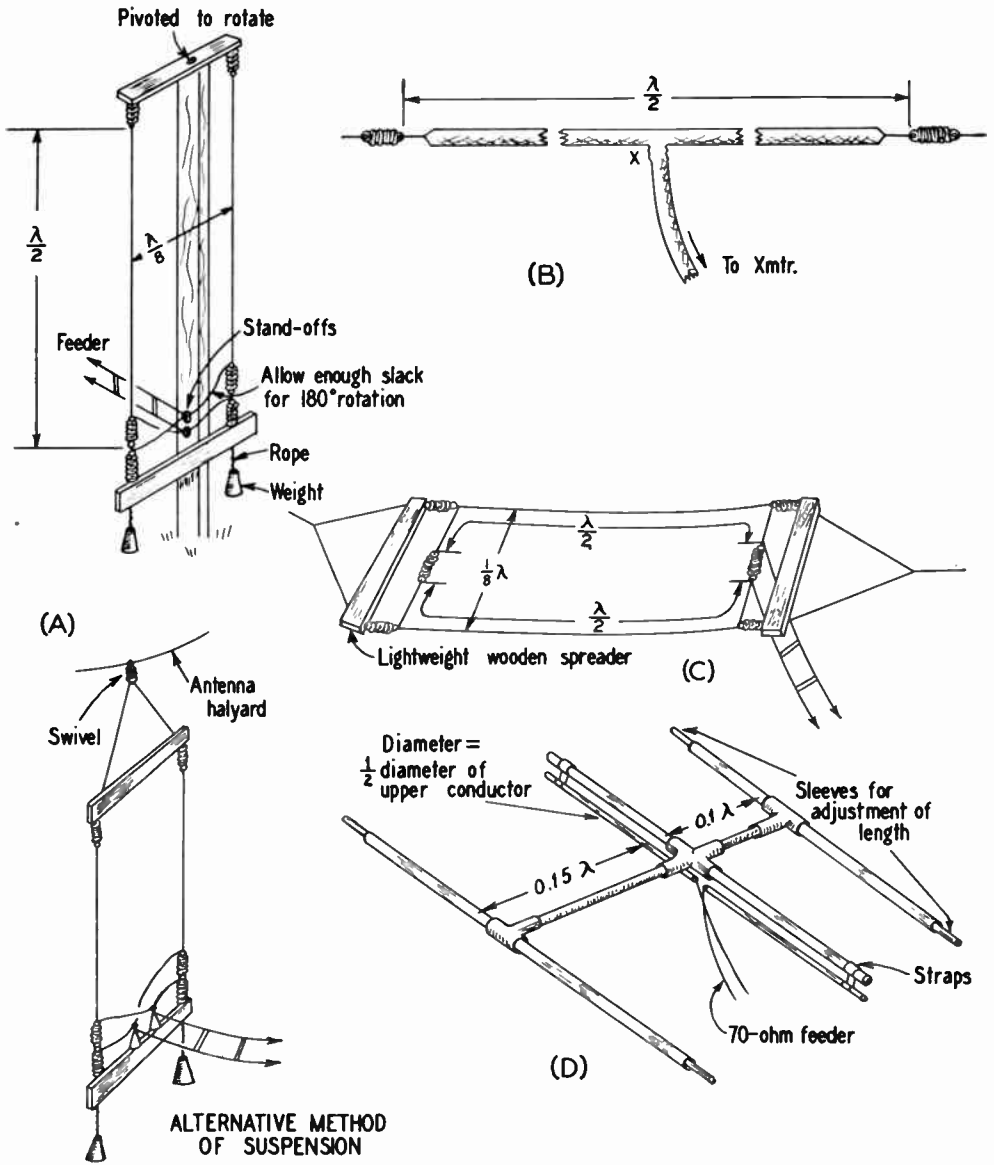


Fig. 10-79—Some suggested antenna systems. A — Simple bidirectional rotatable end-fire array using  $\frac{1}{8}$ -wave spacing between out-of-phase elements. It is suitable for either 14 or 28 Mc. and can be hand-rotated. It can also be suspended from the halyard holding another antenna, as suggested in the lower drawing. B — Folded dipole using 300-ohm Twin-Lead for both antenna and feeder. The junction X at the center is made by opening one conductor of the antenna section and soldering to the feeder leads. The joint may be made mechanically firm by heating the dielectric with a soldering iron, using extra bits of dielectric for a good bond. C — An end-fire array for use where space is

limited. The ends of the two half-wave elements are folded to meet at an insulator in the center. The antenna may be made still shorter by increasing the spacing: spacings up to  $\frac{1}{4}$  wavelength may be used. D — Pipe-assembly three-element beam ("plumber's delight") with folded-dipole driven element. Because all three elements are at the same r.f. potential at their centers it is possible to join them electrically as well as mechanically with no effect on the performance. Provision is made for adjusting the element lengths for optimum performance at a given frequency. E — An extension of the folding principle shown in C. The collinear in-phase elements give additional gain and directivity. F — End-

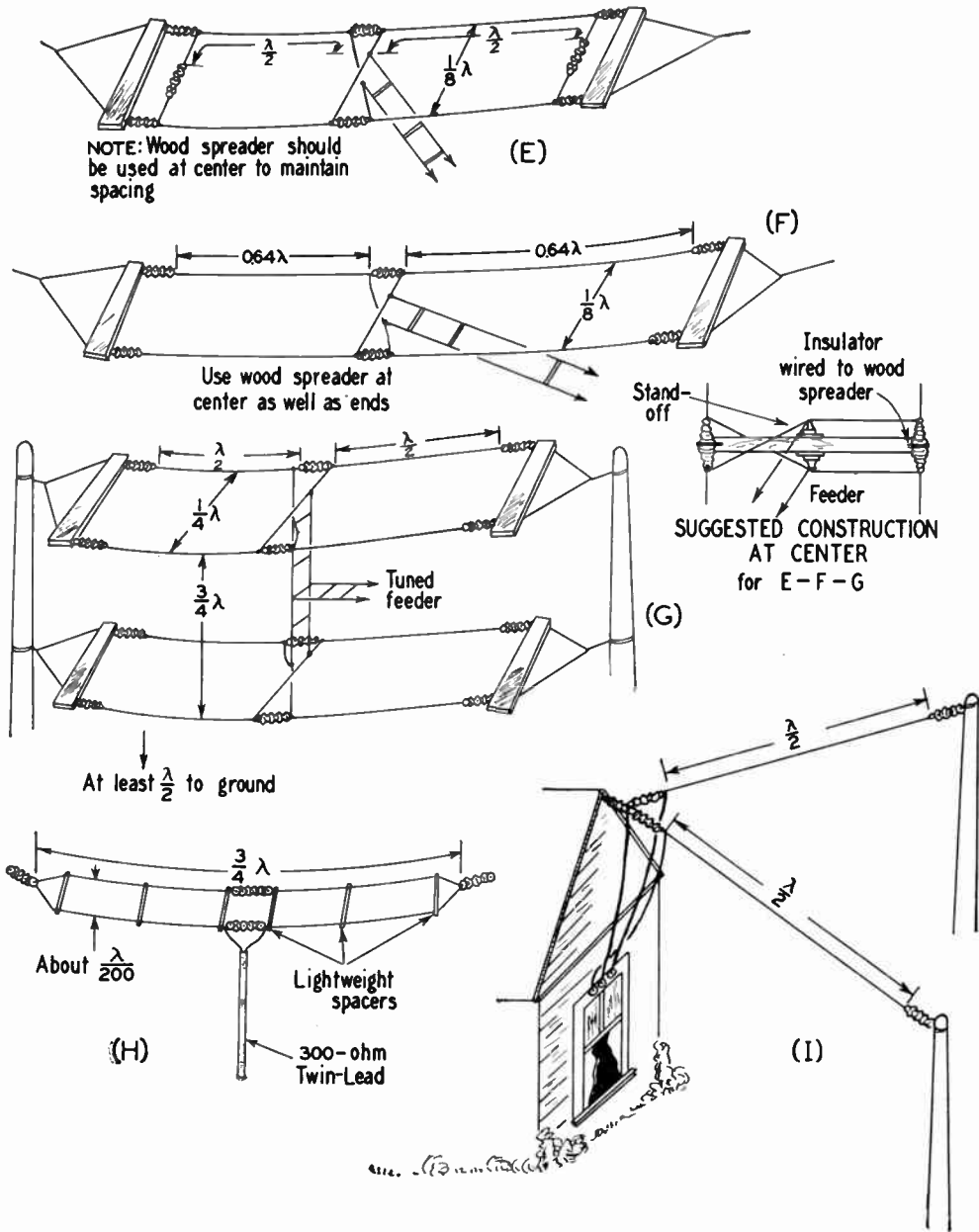



fire array with extended double-Zepps. This antenna should give a gain of about 7 db. in the direction perpendicular to the line of the antenna. G — An 8-element array combining broadside, end-fire and collinear elements. The gain of an antenna of this type is about 10 db. This antenna also can be used at half the frequency for which it is designed. H — A three-quarter wavelength folded antenna offers a fairly-close match for a 500- or 600-ohm open-wire line. Its pattern is quite similar to a half-wavelength antenna. Note that, unlike the half-wavelength folded dipole, the far side is open at the center. I — Using two half-wave antennas at right angles to change direction. With the three feeders indi-

cated, either antenna alone can be fed as a Zepp and will radiate best perpendicular to its direction. By feeding the two together, leaving the third feeder wire idle, the optimum direction is the bisector of the angle between the wires. This system is most useful at high frequencies. In these drawings, wavelength dimensions on conductors refer to lengths calculated for the conductor size as described in Equation 10-J. Dimensions between elements are free-space dimensions. The feeders to the various directive systems in A, C, E, F and G must be tuned if used as shown. For one-band operation, matching stubs may be attached to the feeders if a matched line is desired.

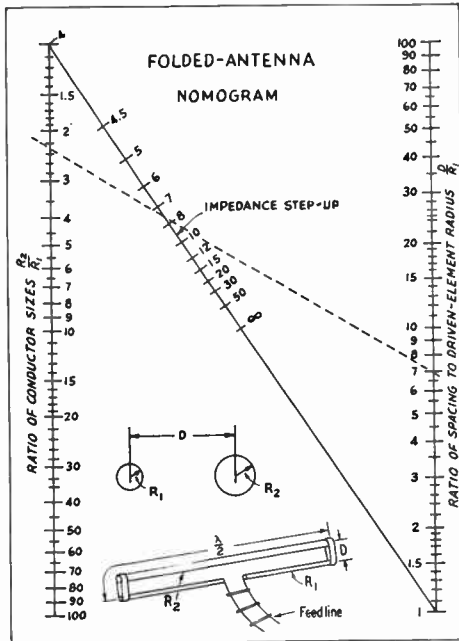


Fig. 10-80 — Nomogram for computing impedance step-up in a folded dipole with dissimilar conductors. The line at the left is the ratio of conductor diameters, and the line at the right is the ratio of conductor spacing (center-to-center) to the driven-element radius. The solid slanting line is the impedance step-up ratio. Laying a straightedge between any two known quantities will give the value of the third.

Example: Find the diameter of the large conductor when the driven-element diameter is 0.5 inch, line impedance 300 ohms, antenna impedance 40 ohms, and spacing 1.75 inches.

Impedance step-up required =  $300/40 = 7.5$   
 Spacing-to-element-radius ratio =  $1.75/0.25 = 7$

Laying a straightedge across the figure (dashed line), ratio of conductor diameters = 2.3  
 Diameter of large conductor =  $2.3 \times 0.5 = 1.15$  inches

per cent of the resonant frequency, or up to about 500 ke. at 28 Mc. However, the antenna can be made to work satisfactorily over a wider frequency range by adjusting the director or directors to give maximum gain at the highest frequency to be covered, and by adjusting the reflector to give optimum gain at the lowest frequency. This sacrifices some gain at all frequencies, but maintains more uniform gain over a wider frequency range.

As mentioned in the preceding paragraphs, the use of large-diameter conductors will broaden the response curve of an array because the larger diameter lowers the *Q*. This causes the reactances of the elements to change rather slowly with frequency, with the result that the tuning stays near the optimum over a considerably-wider frequency range than is the case with wire conductors.

**Combination Arrays**

It is possible to combine parasitic elements with driven elements to form arrays composed

of collinear driven and parasitic elements and combination broadside-collinear-parasitic elements. Thus two or more collinear elements might be provided with a collinear reflector or director set, one parasitic element to each driven element. Or both directors and reflectors might be used. A broadside-collinear array could be treated in the same fashion.

When combination arrays are built up, a rough approximation of the gain to be expected may be obtained by adding the gains for each type of combination. Thus the gain of two broadside sets of four collinear arrays with a set of reflectors, one behind each element, at quarter-wave spacing for the parasitic elements, would be estimated as follows: From Table 10-IV, the gain of four collinear elements is 4.5 db. with half-wave spacing; from Fig. 10-66 or Table 10-V, the gain of two broadside elements at half-wave spacing is 4.0 db.; from Fig. 10-76, the gain of a parasitic reflector at quarter-wave spacing is 4.5 db. The total gain is then the sum, or 13 db. for the sixteen elements. Note that using two sets of elements in broadside is equivalent to using two elements, so far as gain is concerned; similarly with sets of reflectors, as against one antenna and one reflector. The actual gain of the combination array will depend, in practice, upon the way in which the power is distributed between the various elements and upon the effect which mutual coupling between elements has upon the radiation resistance of the array, and may be somewhat higher or lower than the estimate.

A great many directive-antenna combinations can be worked out by combining elements according to these principles.

● **RECEIVING ANTENNAS**

Nearly all of the properties possessed by an antenna as a radiator also apply when it is used for reception. Current and voltage distribution, impedance, resistance and directional characteristics are the same in a receiving antenna as if it were used as a transmitting antenna. This reciprocal behavior makes possible the design of a receiving antenna of optimum performance based on the same considerations that have been discussed for transmitting antennas.

The simplest receiving antenna is a wire of random length. The longer the wire, the more energy it abstracts from the wave. Because of the high sensitivity of modern receivers, a large antenna is not necessary for picking up signals at good strength. An indoor wire only 15 to 20 feet long will serve at frequencies below the v.h.f. range, although a longer wire outdoors is better.

The use of a tuned antenna improves the operation of the receiver, however, because the signal strength is raised more in proportion to the stray noises picked up than is the case with wires of random length. Since the transmitting antenna usually is given the best loca-

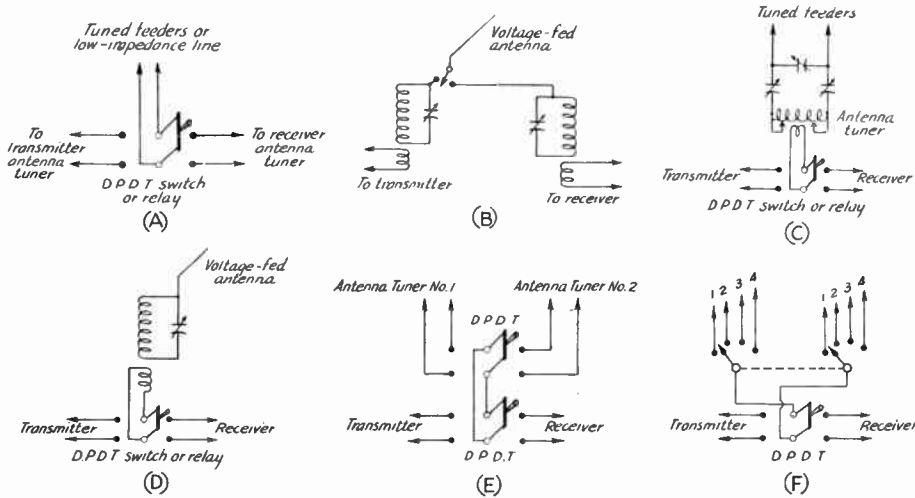


Fig. 10-81 — Antenna-switching arrangements for various types of antennas and coupling systems. A — For tuned lines with separate antenna tuners or low-impedance lines. B — For a voltage-fed antenna. C — For a tuned line with a single antenna tuner. D — For a voltage-fed antenna with a single tuner. E — For two tuned-line antennas with a tuner for each antenna or for two low-impedance lines. F — For combinations of several two-wire lines.

tion, it can also be expected to serve best for receiving. This is especially true when a directive antenna is used, since the directional effects and power gain of directive transmitting antennas are the same for receiving as for transmitting.

In selecting a directional receiving antenna it is preferable to choose a type that gives very little response in all but the desired direction (small minor lobes). This is even more important than high gain in the desired direction, because the cumulative response to noise and unwanted-signal interference in the smaller lobes may offset the advantage of increased desired-signal gain. The feedline from the antenna should be balanced so that it will not pick up signals and destroy the directivity.

**Antenna Switching**

Switching of the antenna from receiver to transmitter is commonly done with a change-over relay, connected in the antenna leads or the coupling link from the antenna tuner. If the relay is one with a 115-volt a.c. coil, the switch or relay that controls the transmitter plate power will also control the antenna relay. If the convenience of a relay is not desired, porcelain knife switches can be used and thrown by hand.

Typical arrangements are shown in Fig. 10-81. If coaxial line is used, the use of a coaxial relay is recommended, although on the lower-frequency bands a regular switch or change-over relay will work almost as well.

**Antenna Construction**

The use of good materials in the antenna system is important since the antenna is exposed to wind and weather. To keep electrical losses low, the wires in the antenna and feeder system must have good conductivity and the insulators must have low dielectric loss and surface leakage, particularly when wet.

For short antennas, No. 14 gauge hard-drawn enameled copper wire is a satisfactory conductor. For long antennas and directive arrays, No. 14 or No. 12 enameled copper-clad steel wire should be used. It is best to make feeders and matching stubs of ordinary soft-drawn No. 14 or No. 12 enameled copper wire, since hard-drawn or copper-clad steel wire is difficult to handle unless it is under considerable tension at all times. The wires should be all in one piece; where a joint cannot be avoided, it should be carefully soldered.

In building a resonant two-wire feeder, the

spacer insulation should be of as good quality as in the antenna insulators proper. For this reason, good ceramic spacers are advisable. Wooden dowels boiled in paraffin may be used with untuned lines, but their use is not recommended for tuned lines. The wooden dowels can be attached to the feeder wires by drilling small holes and binding them to the feeders with wire.

At points of maximum voltage, insulation is most important, and Pyrex glass, Isolantite or steatite insulators with long leakage paths are recommended for the antenna. Glazed porcelain also is satisfactory. Insulators should be cleaned once or twice a year, especially if they are subjected to much smoke and soot.

In most cases poles or masts are desirable to lift the antenna clear of surrounding buildings, although in some locations the antenna will be sufficiently in the clear when strung

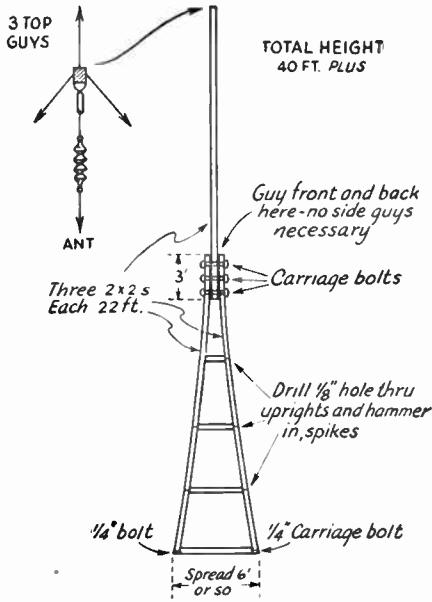


Fig. 10-82 — Details of a simple 40-foot "A"-frame mast suitable for erection in locations where space is limited.

from one chimney to another or from a chimney to a tree. Small trees usually are not satisfactory as points of suspension for the antenna because of their movement in windy weather. If the antenna is strung from a point near the center of the trunk of a large tree, this difficulty is not so serious. Where the antenna wire must be strung from one of the smaller branches, it is best to tie a pulley firmly to the branch and run a rope through the pulley to the antenna, with the other end of the rope attached to a counterweight near the ground. The counterweight will keep the tension on the antenna wire reasonably constant even when the branches sway or the rope tightens and stretches with varying climatic conditions.

● "A"-FRAME MAST

The simple and inexpensive mast shown in Fig. 10-82 is satisfactory for heights up to 35 or 40 feet. Clear, sound lumber should be selected. The completed mast may be protected by two or three coats of house paint.

If the mast is to be erected on the ground, a couple of stakes should be driven to keep the bottom from slipping and it may then be "walked up" by a pair of helpers. If it is to go on a roof, first stand it up against the side of the building and then hoist it from the roof, keeping it vertical. The whole assembly is light enough for two men to perform the complete operation — lifting the mast, carrying it to its permanent berth and fastening the guys — with the mast vertical all the while. It is entirely practicable, therefore, to erect this type of mast on any small, flat area of roof.

By using 2 × 3s or 2 × 4s, the height may be extended up to about 50 feet. The 2 × 2 is too flexible to be satisfactory at such heights.

● SIMPLE 40-FOOT MAST

The mast shown in Fig. 10-83 is relatively strong, easy to construct, readily dismantled, and costs very little. Like the "A"-frame, it is suitable for heights of the order of 40 feet.

The top section is a single 2 × 3, bolted at the bottom between a pair of 2 × 3s with an overlap of about two feet. The lower section thus has two legs spaced the width of the narrow side of a 2 × 3. At the bottom the two legs are bolted to a length of 2 × 4 which is set in the ground. A short length of 2 × 3 is placed between the two legs about halfway up the bottom section, to maintain the spacing.

The two back guys at the top pull against the antenna, while the three lower guys prevent buckling at the center of the pole.

The 2 × 4 section should be set in the ground so that it faces the proper direction, and then made vertical by lining it up with a plumb bob. The holes for the bolts should be drilled beforehand. With the lower section laid on the ground, bolt A should be slipped in place through the three pieces of wood and tightened just enough so that the section can turn freely on the bolt. Then the top section may be bolted in place and the mast pushed up, using a ladder or another 20-foot 2 × 3 for the job. As the mast goes up, the slack in the guys can be taken up so that the whole structure is in some meas-

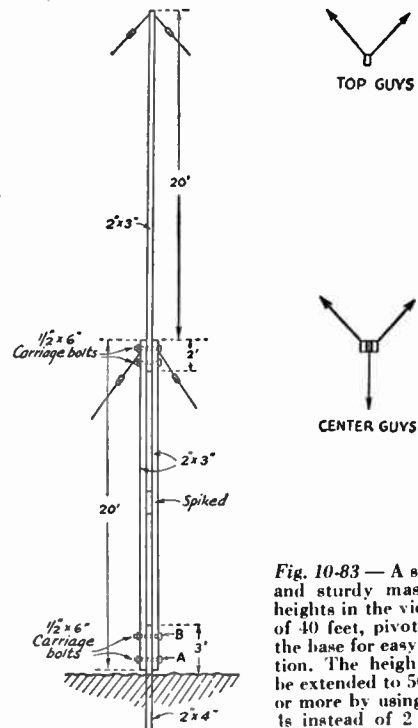


Fig. 10-83 — A simple and sturdy mast for heights in the vicinity of 40 feet, pivoted at the base for easy erection. The height can be extended to 50 feet or more by using 2 × 4s instead of 2 × 3s.

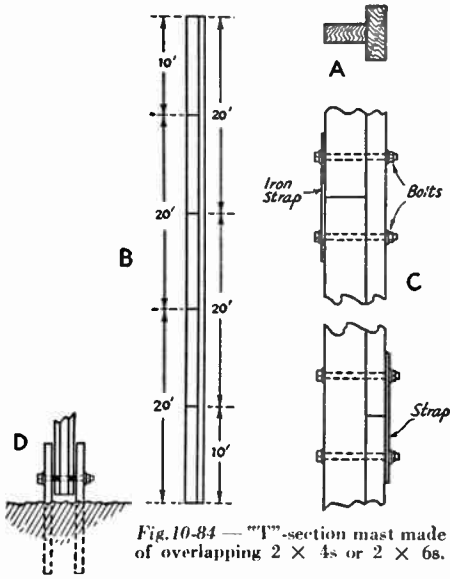


Fig. 10-84 — "I"-section mast made of overlapping 2 x 4s or 2 x 6s.

ure continually supported. When the mast is vertical, bolt B should be slipped in place and both A and B tightened. The lower guys can then be given a final tightening, leaving those at the top a little slack until the antenna is pulled up, when they should be adjusted to pull the top section into line.

● "T"-SECTION MAST

A type of mast suitable for heights up to about 80 feet is shown in Fig. 10-84. The mast is built up by butting 2 x 4 or 2 x 6 timbers flatwise against a second 2 x 4, as shown at A, with alternating joints in the edgewise and flatwise sections. The construction can be carried out to greater lengths simply by continuing the 20-foot sections. Longer or shorter sections may be used.

The method of making the joints is shown at C. Quarter-inch or 3/16-inch iron, 1 1/2 to 2 inches wide, is recommended for the straps, with 1/2-inch bolts to hold the pieces together. One bolt should be run through the pieces midway between joints, to provide additional rigidity.

Although there are many ways in which such a mast can be secured at the base, the "cradle" illustrated at D has many advantages. Heavy timbers set firmly in the ground, spaced far enough apart so the base of the mast will pass between them, hold a large carriage bolt or steel bar which serves as a bearing. The bolt goes through a hole in the mast so that it is pivoted at the bottom.

Half of the guys can be put in place and tightened up before the mast leaves the ground. Four sets of guys should be used, one in front, one directly in the rear, and two on each side at right angles to the direction in which the mast will face. A set of guys should be used at each of the joints in the edgewise sections, the guy wires being wrapped around the pole for added strength.

For heights up to 50 feet, 2 x 4-inch members may be used throughout. For greater heights, use 2 x 4s for the edgewise sections; 2 x 6-inch pieces will do for the flat sections.

● POLE AND TOWER SUPPORTS

Poles, which often may be purchased at a reasonable price from the local telephone or power company, have the advantage that they do not require guying unless they are called upon to carry a very heavy load. The life of a pole can be extended many years by proper precautions before erecting, and regular maintenance thereafter.

Before setting the pole, it should be given four or five coats of creosote, applying it liberally so it can soak into and preserve the wood. The bottom of the pole and the part that will be buried in the ground should have a generous coating of hot pitch, poured on while the pole is warm. This will keep termites out and prevent rotting.

The pole should be set in the ground four to eight feet depending upon the height. It is a good idea to pour concrete around the bottom three feet of the base, packing the rest of the excavation with soil. The concrete will help hold the pole against strong winds. After filling the hole with dirt, a stream from a hose should be played on the dirt slowly for several hours.

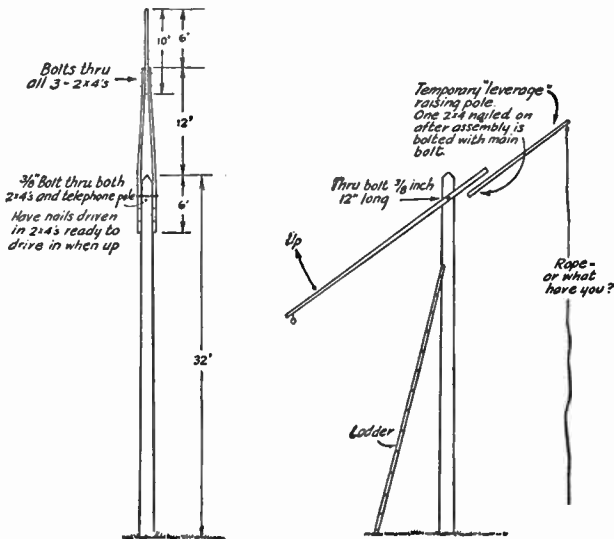


Fig. 10-85 — This type of mast may be carried to a height of fifty feet or more. No guy wires are required.

This will help to settle the soil quickly.

If desired, the pole may be extended by the arrangement shown in Fig. 10-85. Three  $2 \times 4$ s are required for the top section, two being 18 feet long and one 10 feet long. The 10-foot section is placed between the other two and bolted in place. A half-inch hole should be bored through the pole about 2 feet from its top and through both 18-foot  $2 \times 4$ s about 5 feet from their bottom ends, which are spread apart to fit the top of the pole. The bottom end of the extension is then hauled up to the top of the pole and bolted loosely so that the section can be swung up into place by the leverage of another  $2 \times 4$  temporarily fastened to the section, as shown in Fig. 10-85.

Lattice towers built of wood should be assembled with brass screws and casein glue, rather than with nails which work loose in a short time. A tower constructed in this manner will give trouble-free service if treated with a coat of paint every year.

In painting outside structures, use pure white lead, thinned with three parts of pure linseed oil to one part of turpentine, for the first coat on new wood. The use of a drier is not recommended if the paint will possibly dry without it, since it may cause the paint to peel after a short time. For the second and third coats pure white lead thinned only with pure

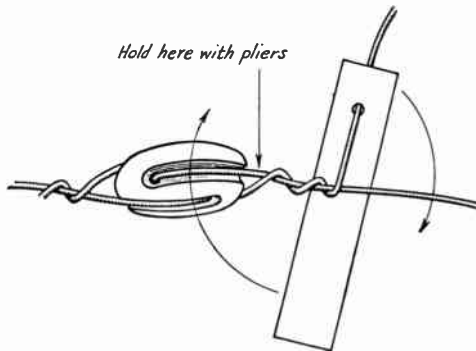


Fig. 10-86 — Using a lever for twisting heavy guy wires.

linseed oil is recommended. Plenty of time for drying should be allowed between coats. White paint will last fifty per cent longer than any colored paint.

### ● GUYS AND GUY ANCHORS

For masts or poles up to about 50 feet, No. 12 iron wire is a satisfactory guy-wire material. Heavier wire or stranded cable may be used for taller poles or poles installed in locations where the wind velocity is high.

More than three guy wires in any one set usually are unnecessary. If a horizontal antenna is to be supported, two guy wires in the top set will be sufficient in most cases. These should run to the rear of the mast about 100 degrees apart to offset the pull of the antenna.

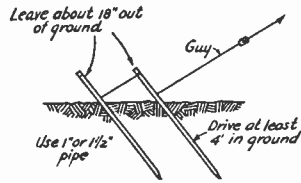


Fig. 10-87 — Pipe guy anchors. One pipe is sufficient for small masts, but two installed as shown will provide the additional strength required for the larger poles.

Intermediate guys should be used in sets of three, one running in a direction opposite to that of the antenna, while the other two are spaced 120 degrees either side. This leaves a clear space under the antenna. The guy wires should be adjusted to pull the pole slightly back from vertical before the antenna is hoisted so that when the antenna is pulled up tight the mast will be straight.

When raising a mast that is big enough to tax the facilities available, it is some advantage to know nearly exactly the length of the guys. Those on the side on which the pole is lying can then be fastened temporarily to the anchors beforehand, which assures that when the pole is raised, those holding opposite guys will be able to pull it into nearly-vertical position with no danger of its getting out of control. The guy lengths can be figured by the right-angled-triangle rule that "the sum of the squares of the two sides is equal to the square of the hypotenuse." In other words, the distance from the base of the pole to the anchor should be measured and squared. To this should be added the square of the pole length to the point where the guy is fastened. The square root of this sum will be the length of the guy.

Guy wires should be broken up by strain insulators, to avoid the possibility of resonance at the transmitting frequency. Common practice is to insert an insulator near the top of each guy, within a few feet of the pole, and then cut each section of wire between the insulators to a length which will not be resonant either on the fundamental or harmonics. An insulator every 25 feet will be satisfactory for frequencies up to 30 Mc. The insulators should be of the "egg" type with the insulating material under compression, so that the guy will not part if the insulator breaks.

Twisting guy wires onto "egg" insulators may be a tedious job if the guy wires are long and of large gauge. The simple time- and finger-saving device shown in Fig. 10-86 can be made from a piece of heavy iron or steel by drilling a hole about twice the diameter of the guy wire about a half inch from one end of the piece. The wire is passed through the insulator, given a single turn by hand, and then held with a pair of pliers at the point shown in the sketch. By passing the wire through the hole in the iron and rotating the iron as shown, the wire may be quickly and neatly twisted.

Guy wires may be anchored to a tree or building when they happen to be in convenient spots. For small poles, a 6-foot length of 1-inch pipe driven into the ground at an angle will

suffice. Additional bracing will be provided by using two pipes, as shown in Fig. 10-87.

## ● HALYARDS AND PULLEYS

Halyards or ropes and pulleys are important items in the antenna-supporting system. Particular attention should be directed toward the choice of a pulley and halyards for a high mast since replacement, once the mast is in position, may be a major undertaking if not entirely impossible.

Galvanized-iron pulleys will have a life of only a year or so. Especially for coastal-area installations, marine-type pulleys with hardwood blocks and bronze wheels and bearings should be used.

An arrangement that has certain advantages over a pulley when a mast is used is shown in Fig. 10-88. In case the rope breaks, it may be possible to replace it by heaving a line over the brass rod, making it unnecessary to climb or lower the pole.

For short antennas and temporary installations, heavy clothesline or window-sash cord may be used. However, for more permanent jobs,  $\frac{3}{8}$ -inch or  $\frac{1}{2}$ -inch waterproof hemp rope should be used. Even this should be replaced about once a year to insure against breakage.

Nylon rope, used during the war as glider tow rope, is, of course, one of the best materials for halyards, since it is weatherproof and has extremely long life.

It is advisable to carry the pulley rope back up to the top in "endless" fashion in the manner of a flag hoist so that if the antenna breaks close to the pole, there will be a means for pulling the hoisting rope back down.

## ● BRINGING THE ANTENNA OR FEEDLINE INTO THE STATION

The antenna or transmission line should be anchored to the outside wall of the building, as shown in Fig. 10-89, to remove strain from the lead-in insulators. Holes cut through the walls of the building and fitted with feed-through insulators are undoubtedly the best means of

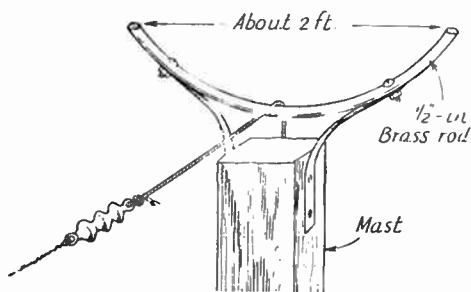


Fig. 10-88 — This device is much easier than a pulley to "rethread" when the rope breaks.

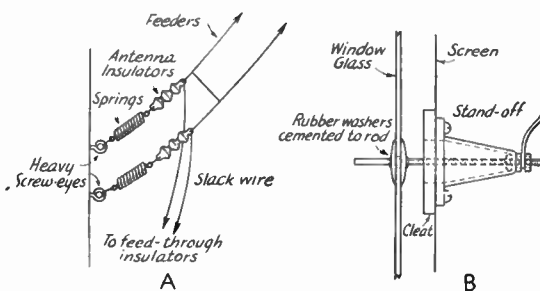


Fig. 10-89 — A — Anchoring feeders takes the strain from feed-through insulators or window glass. B — Going through a full-length screen, a cleft is fastened to the frame of the screen on the inside. Clearance holes are cut in the cleft and also in the screen.

bringing the line into the station. The holes should have plenty of air clearance about the conducting rod, especially when using tuned lines that develop high voltages. Probably the best place to go through the walls is the trimming board at the top or bottom of a window frame which provides flat surfaces for lead-in insulators. Either cement or rubber

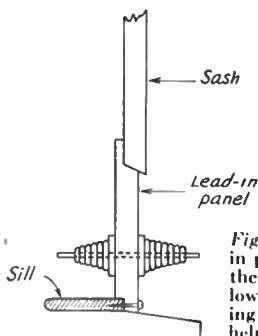


Fig. 10-90 — An antenna lead-in panel may be placed over the top sash or under the lower sash of a window. Sealing the overlapping joint will help make it weatherproof.

gaskets may be used to waterproof the exposed joints.

Where such a procedure is not permissible, the window itself usually offers the best opportunity. One satisfactory method is to drill holes in the glass near the top of the upper sash. If the glass is replaced by plate glass, a stronger job will result. Plate glass may be obtained from automobile junk yards and drilled before placing in the frame. The glass itself provides insulation and the transmission line may be fastened to bolts fitting the holes. Rubber gaskets will render the holes waterproof. The lower sash should be provided with stops to prevent damage when it is raised. If the window has a full-length screen, the scheme shown in Fig. 10-89B may be used.

As a less permanent method, the window may be raised from the bottom or lowered from the top to permit insertion of a board which carries the feed-through insulators. This lead-in arrangement can be made weatherproof by making an overlapping joint between the board and window sash, as shown in Fig. 10-90, and

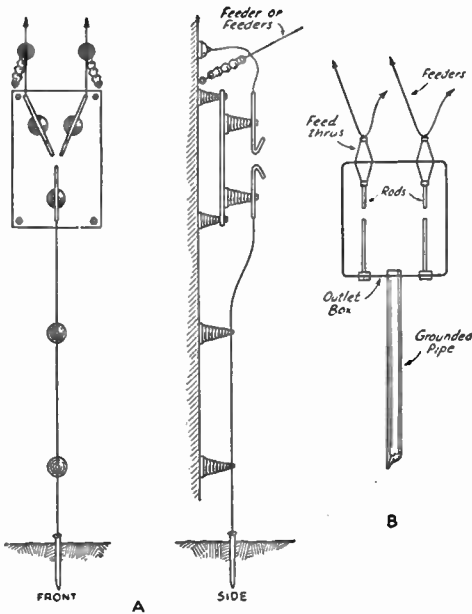


Fig. 10-91 — Low-loss lightning arresters for transmitting-antenna installations.

covering the opening between sashes with a sheet of soft rubber from a discarded inner tube.

● LIGHTNING PROTECTION

An ungrounded radio antenna, particularly if large and well elevated, is a lightning hazard. When grounded, it provides a measure of protection. Therefore, grounding switches or lightning arresters should be provided. Examples of construction of low-loss arresters are shown in Fig. 10-91. At A, the arrester electrodes are mounted by means of stand-off insulators on a fireproof asbestos board. At B, the electrodes are enclosed in a standard steel outlet box. The gaps should be made as small as possible without danger of breakdown during operation. Lightning-arrester systems require the best ground connection obtainable.

The most positive protection is to ground the antenna system when it is not in use; grounded flexible wires provided with clips for connection to the feeder wires may be used. The ground lead should be short and run, if possible, directly to a driven pipe or water pipe where it enters the ground outside the building.

Rotary-Beam Construction

It is a distinct advantage to be able to shift the direction of a beam antenna at will, thus securing the benefits of power gain and directivity in any desired compass direction. A favorite method of doing this is to construct the antenna so that it can be rotated in the horizontal plane. Obviously, the use of such rotatable antennas is limited to the higher frequencies — 14 Mc. and above — and to the simpler-antenna element combinations if the

structure size is to be kept within practicable bounds. For the 14- and 28-Mc. bands such antennas usually consist of two to four elements and are of the parasitic-array type described earlier in this chapter. At 50 Mc. and higher it becomes possible to use more elaborate arrays because of the shorter wavelength and thus obtain still higher gain. Antennas for these bands are described in Chapter Fourteen.

The problems in rotary-beam construction are those of providing a suitable mechanical support for the antenna elements, furnishing a means of rotation, and attaching the transmission line so that it does not interfere with the rotation of the system.

Elements

The antenna elements usually are made of metal tubing so that they will be at least partially self-supporting, thus simplifying the supporting structure. The large diameter of the conductor is beneficial also in reducing resistance, which becomes an important consideration when close-spaced elements are used.

Dural tubes often are used for the elements, and thin-walled corrugated steel tubes with copper coating also are available for this purpose. The elements frequently are constructed of sections of telescoping tubing, making length adjustments for tuning quite easy. Electricians' thin-walled conduit also is suitable for rotary-beam elements.

If steel elements are used, special precautions

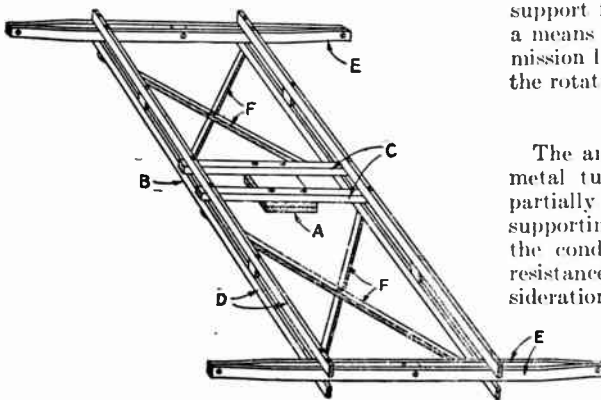


Fig. 10-92 — Easily-built supporting structure for horizontal rotary beams. Made chiefly of 1 X 2" wood strip, it is strong yet lightweight. Antenna elements are supported on stand-off insulators on the arms, E. The length of the D sections will depend upon the element spacing, while the length of the E sections and the spacing between the D sections should be 1/4 to 1/2 the length of the antenna elements.



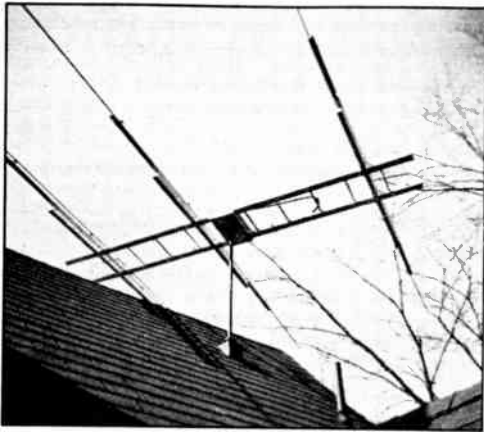


Fig. 10-93 — A ladder-supported 3-element 28-Mc. beam. It is mounted on a pipe mast that projects through a bearing in the roof and is turned from the attic operating room. (WIMRK in August, 1916, QST.)

should be taken to prevent rusting. Even copper-coated steel does not stand up indefinitely, since the coating usually is too thin. The elements should be coated both inside and out with slow-drying aluminum paint. For coating the inside, a spray gun may be used, or the paint may be poured in one end while rotating the tubing. The excess paint may be caught as it comes out the bottom end and poured through again until it is certain that the entire inside wall has been covered. The ends should then be plugged up with corks sealed with glyptal varnish.

**Supports**

The supporting framework for a rotary beam usually is made of wood but sometimes of metal, using as lightweight construction as is consistent with the required strength. Generally, the frame is not required to hold much weight, but it must be extensive enough so that the antenna elements can be supported near enough to their ends to prevent excessive sag, and it must have sufficient strength to stand up under the maximum wind in the locality. The design of the frame will depend chiefly on the size of the antenna elements, whether they are mounted horizontally or vertically, and the method to be employed for rotating the antenna.

The general preference is for horizontal polarization, primarily because less height is required to clear surrounding obstructions when all the antenna elements are in the horizontal plane. This is important at 14 and 28 Mc. where the elements are fairly long.

An easily-constructed supporting frame for a horizontal array is shown in Fig. 10-92. It may be made of 1 X 2-inch lumber, preferably oak, for the center sections B, C, and D. The outer arms, E, and cross braces, F, may be of white pine or cypress. The square block, A, at the

center supports the whole structure and may be coupled to the pole by any convenient means which permits rotation. Alternatively, the block may be firmly fastened to the pole and the latter rotated in bearings affixed to the side of the house.

Another type of construction is shown in Fig. 10-93, with details in Figs. 10-94 and 10-95. This method, suitable for 28-Mc. beams, uses a section of ordinary ladder as the main support, with crosspieces to hold the tubing antenna elements. Fig. 10-94 also indicates a method of adjusting the lengths of the parasitic elements and bringing the transmission line down through the supporting pole from a delta match. The latter is especially adapted to construction in which the pole rather than the framework alone is rotated.

**Metal Booms**

Metal can be used to support the elements of the rotary beam. For 28 Mc., a piece of 2-inch diameter duraluminum tubing makes a good "boom" for supporting the elements. The elements can be made to slide through suitable holes in the boom, or special clamps and brackets can be fashioned to support the elements. The antenna of Fig. 10-79D shows one example of such construction.

Generally it is not practicable to support the elements of a 14-Mc. beam by a single-piece boom, because the size of the elements requires a stronger structure. However, by making use of tubing or duraluminum angle, a lightweight support for a 20-meter antenna can be built. The four-element beam shown in

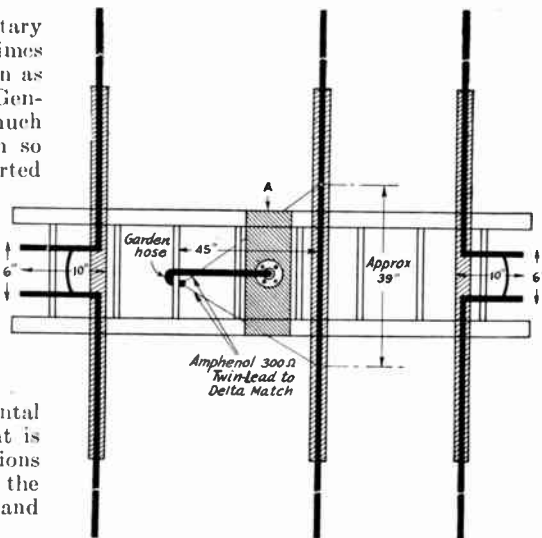


Fig. 10-94 — Top-view drawing of the ladder support and mounted elements. Lengths of director and reflector are adjusted by means of the shorting bars on the small stubs at the center. The drawing also shows a method for pulling off the wires of a delta match and feeding 300-ohm Twin-Lead transmission line through the pipe support.

Figs. 10-96, 10-97 and 10-98 is an example. It uses  $1\frac{3}{4}$ -inch angle for the main pieces and  $\frac{3}{4}$ -inch angle for the other framework members, and the entire framework plus elements weighs only forty pounds. This simplifies considerably the problem of supporting the beam.

The following aluminum pieces are required:

- 4 — 1-inch diameter tubing, 12 feet long,  $\frac{1}{16}$ -inch wall
- 8 —  $\frac{7}{8}$ -inch diameter tubing, 12 feet long,  $\frac{1}{32}$ -inch wall. Must fit snugly into 1-inch tubing.
- 2 —  $1\frac{3}{4}$ -inch angle, 21 feet long
- 2 —  $\frac{3}{4}$ -inch angle, 21 feet long
- 4 —  $\frac{3}{4}$ -inch angle, 1 foot long
- 2 —  $\frac{1}{2}$ -inch diameter tubing, 6 feet long

Aluminum tubing and angle corresponding to the above sizes can possibly be bought from scrap dealers at reasonable prices, if not directly from the manufacturer. If the sections of the elements do not fit snugly, insert shims or

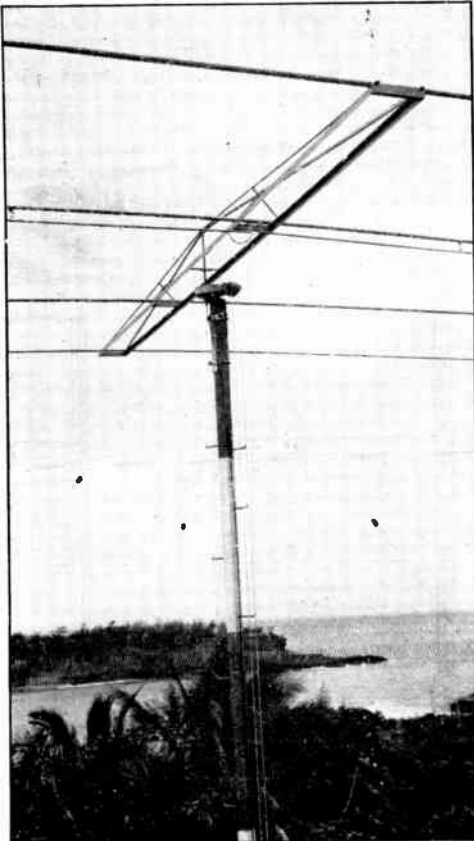


Fig. 10-96 — A four-element 14-Mc. beam of lightweight all-metal construction. Fed by coaxial cable and hand-rotated, the antenna and boom assembly weighs only 40 pounds. (KH6JJ, Dec., 1947, QST.)

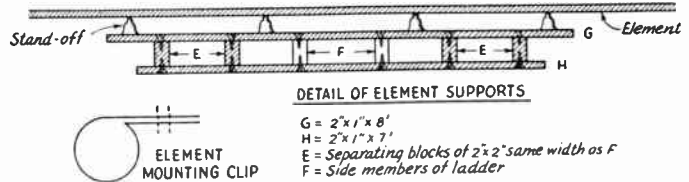


Fig. 10-95 — Detail of element supports for the ladder beam.

make some other provision for a tight fit, since the appearance of the beam will be spoiled by sagging elements. Some amateurs reinforce their beam elements with copper-clad steel wire supported a foot above the elements at the boom and tied to the extreme ends of the elements.

As shown in Fig. 10-97A, two  $1\frac{3}{4}$ -inch aluminum angles 21 feet long serve as the main members of the boom. They are spaced one foot apart. The elements are spaced 7 feet apart. Wooden spacers of  $2 \times 2$  are placed at the end of the boom and screwed on with brass screws. These spacers are also placed under each element where it crosses the boom. These spacers may be unnecessary if the elements are bolted to the boom, but if the construction is as in Fig. 10-97B the spacers are recommended.

The cross braces shown in Fig. 10-98 are put into position at the very last, after the beam is hung in position on the central pivot, since they offer a means for truing up minor sag in the elements.

The central pivot consists of structure made from  $\frac{3}{4}$ -inch angle iron and  $\frac{1}{2}$ -inch pipe, as shown in Fig. 10-97C. It has to be brazed. The crossbar rest is made separate from the boom and central pivot, and affords a means for tilting the beam when unbolted from these structures. The  $\frac{1}{2}$ -inch pipe is drilled for the coaxial line that is fed through this pipe. The pinion gear on the  $\frac{1}{2}$ -inch pipe should be brazed on.

A washing-machine gear train is well suited for this type of beam. Another possibility (used in this instance) is a discarded forge blower. It was fitted with a  $\frac{1}{2}$ -inch pipe which serves as the central pivot. The gear train ends up in a "V"-pulley, and the beam is easily rotated by a system of ropes and pulleys that ends up in an automobile steering wheel at the operating position. A plumb bob attached to the shaft of the steering wheel serves as a direction indicator. A small cardboard scale mounted along the line of plumb-bob travel can be readily calibrated to show the direction of the beam.

The supporting structure for this beam consists of a  $4 \times 4$  pole 30 feet long, with ten-foot extensions of  $2 \times 4$  bolted to both sides of the bottom, making the total length about 36 feet. Two sets of guy wires should be used, approximately 2 feet and 15 feet from the top. As an alternative, the pole can be set against the side of the house, and only the top set of guys used to provide additional support.

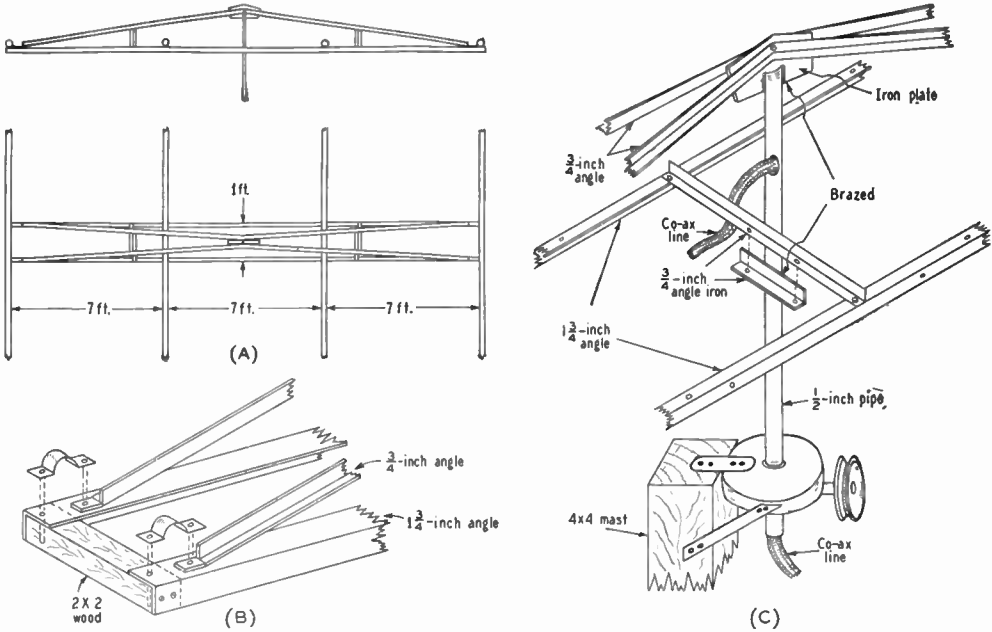


Fig. 10-97 — Details of the 4-element beam construction. The general dimensions and arrangement of the beam are given in A, the detail of the ends of the boom is shown at B, and C shows the construction of the central pivot. A discarded-forge blower gear train is used to drive the assembly.

With all-metal construction, delta match or "T"-match are the only practical matching methods to use to the line, since anything else requires opening the driven element at the center, and this complicates the support problem for that element.

**A Wooden Boom for 14 Mc.**

Many amateurs prefer to build their beam booms from standard pieces of lumber, and the beam shown in Figs. 10-99 and 10-100 is an example of excellent design in wooden-boom construction. The boom members are two 20-foot 2 x 4s fastened to the 4 x 12 x 24-inch center block with six lag screws. The two center screws serve as the axis for tilting — the other four lock the boom in position after final assembly and adjustment have been completed. The blocks midway from each end are 2 x 4s spaced about six inches apart, with a long bolt between them. When this bolt is drawn tight, a very sturdy box brace is formed.

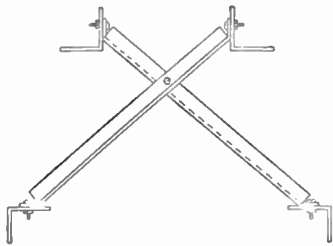


Fig. 10-98 — The boom for the 4-element beam is cross-braced at two points, about 6 1/2 feet in from the ends.

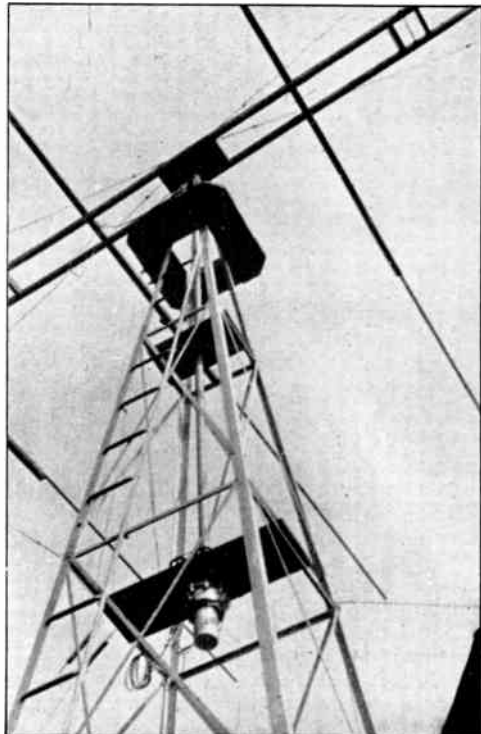


Fig. 10-99 — A wooden boom for a 4-element 14-Mc. boom can be made quite strong by judicious use of guy wires. This installation is made on a windmill tower, and the drive motor is mounted halfway down on the tower. (W6MJB, Nov., 1947, QST.)

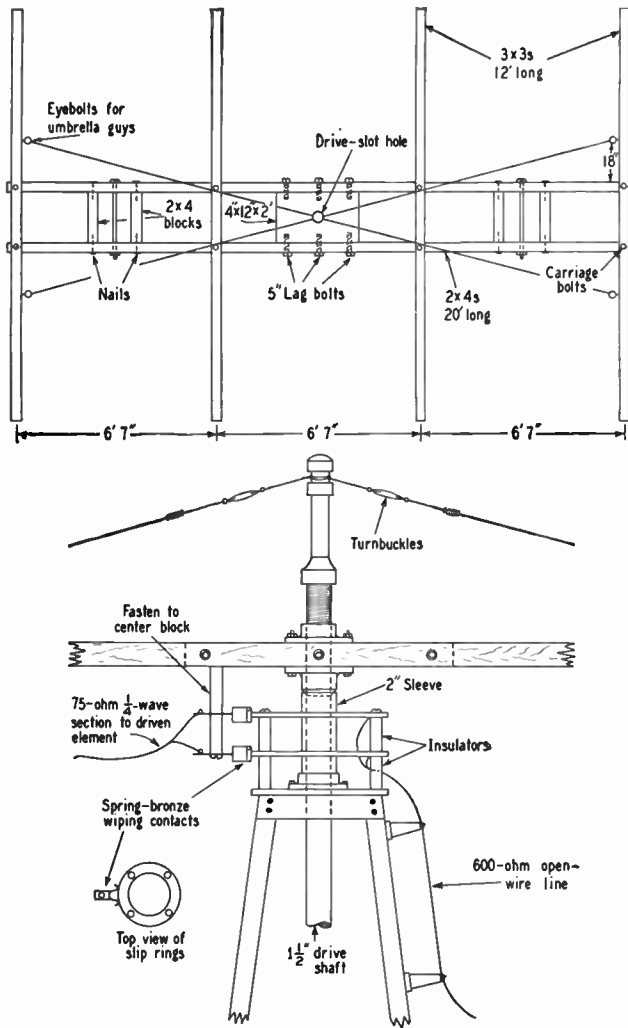


Fig. 10-100 — Details of the wooden boom, its method of support and the construction of the slip rings.

The crossarms are 3 × 3s twelve feet long, bolted to the boom with carriage bolts.

The umbrella guys should have turnbuckles in them, and the guys are fastened to the center support after the beam has been permanently locked in its horizontal position. With the turnbuckles properly adjusted, there will be no sag in the boom, the elements will be parallel and neat, and weaving in the wind will be eliminated.

The elements are 1 3/8- and 1 1/2-inch diameter duralumin tubing, supported by 1 1/2-inch stand-off insulators. Hose clamps are used to hold the elements on the insulators. Final adjustment of element lengths is possible through "hairpin" loops. The tower, for the beam shown in Fig. 10-99, was a Sears-Roebuck windmill tower. The driving motor for the beam was located halfway down the tower, the torque being transmitted through a length of

1 1/2-inch drive shaft. A pipe flange is welded to the drive shaft and bolted to the center block. A cone bearing is obtained by turning both the flange and a sleeve of 2-inch pipe to match, as shown in Fig. 10-100.

One method of matching the line to the antenna is to use a quarter wavelength of 75-ohm Twin-Lead between the radiator and the slip-ring contacts, to match a 600-ohm line from the slip rings to the transmitter.

A 600-ohm open-wire line is run to a point about halfway up on the tower, then up the side of the tower to the slip rings. The slip rings are mounted on the top of the tower, directly under the center block. A quarter-wave-length matching section of transmitting-type 75-ohm Amphenol Twin-Lead hangs in a loop between the driven element and the slip-ring contacts.

**Feeder Connections**

For beams that rotate only 180 degrees, it is relatively simple to bring off feeders by making a short section of the feeder, just where it leaves the rotating member, of flexible wire. Enough slack should be left so that there is no danger of breaking or twisting on the rotating shaft of the antenna so that the feeders cannot "wind up." This method also can be used with antennas that rotate the full 360 degrees, but again a stop is necessary to avoid jamming the feeders.

For continuous rotation, the sliding contact is simple and, when properly built, quite practicable. Fig. 10-101 shows two methods of making sliding contacts. The chief points to keep in mind are that the contact surfaces should be wide enough to take care of wobble in the rotating shaft, and that the contact surfaces should be kept clean. Spring contacts are essential, and an "umbrella" or other scheme for keeping rain off the contacts is a desirable addition. Sliding contacts preferably should be used with nonresonant open lines where the impedance is of the order of 500 to 600 ohms, so that the current is low.

The possibility of poor connections in sliding contacts can be avoided by using inductive coupling at the antenna, with one coil rotating on the antenna and the other fixed in position, the two coils being arranged so that the coupling does not change when the antenna is rotated. Such an arrangement is shown in Fig. 10-102,

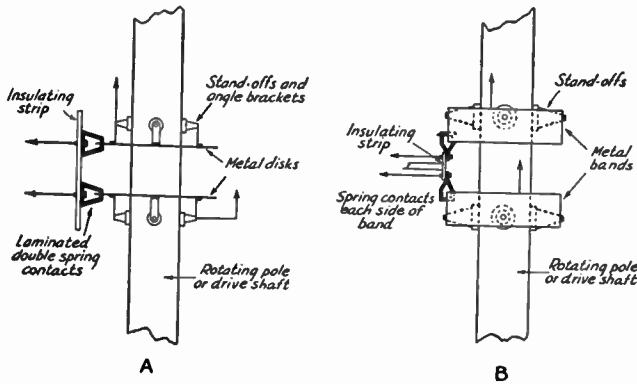


Fig. 10-101 — Ideas in sliding contacts for rotatable antenna feeder connection to permit continuous rotation. The broad bearing surfaces take care of any wobble in the rotating mast or driving shaft.

adapted to an antenna system in which the pole itself rotates. A quarter-wave feeder system is connected to a tuned pick-up circuit whose inductance is coupled to a link. In the drawing, the link coil connects to a twisted-pair transmission line, but any type of line such as flexible coaxial cable can be used. The circuit would be adjusted in the same way as any link-coupled circuit, and the number of turns in the link should be varied to give proper loading on the transmitter. The rotating coupling circuit of course tunes to the transmitting frequency. The whole thing is equivalent to a link-coupled antenna tuner mounted on the pole, using a parallel-tuned tank at the end of a quarter-wave line to center feed the antenna. To maintain constant coupling, the two coils should be quite rigid and the pole should rotate without wobble. The two coils might be made a part of the upper bearing assembly holding the rotating pole in position.

Other variations of the inductive-coupled system can be worked out. The tuned circuit might, for instance, be placed at the end of a 600-ohm line, and a one-turn link used to couple directly to the center of the antenna, if the construction of the rotary member permits. In this case the coupling can be varied by changing the  $L/C$  ratio in the tuned circuit. For mechanical strength the coils preferably should be made of copper tubing, well braced with insulating strips to keep them rigid.

**Rotation**

It is convenient to use a motor to rotate the beam, but it is not always necessary, especially if a rope-and-pulley arrangement can be brought into the operating room. If the pole can be mounted near a window in the operating room, hand rotation of the beam will work out quite well, as has been proven by many amateur installations.

If the use of a rope and pulleys is impracticable, motor drive is about the only alternative. There are several complete motor-driven rotators on the market, and they are easy to

mount, convenient to use, and require little or no maintenance. However, to many the cost of such units puts them out of reach, and a homemade unit must be considered. Generally speaking, lightweight units are better because they reduce the load on the mast or tower.

The speed of rotation should not be too great — one or two r.p.m. is about right. This requires a considerable gear reduction from the usual 1750-r.p.m. speed of small induction motors; a large reduction is advantageous because the gear train will prevent the beam from turning in weather-vane fashion in a wind. The ordinary

structure does not require a great deal of power for rotation at slow speed, and a  $\frac{1}{8}$ -hp. motor will be ample. Even small series motors of the sewing-machine type will develop enough power to turn a 28-Mc. beam at slow speed. If possible, a reversible motor should be used so that it will not be necessary to go through nearly 360 degrees to bring the beam back to a direction only slightly different, but in the opposite direction of rotation, to the direction to which it may be pointed at the moment. In cases where the pole is stationary and only the supporting framework rotates, it will be necessary to mount the motor and gear train in a housing on or near the top of the pole. If the pole rotates, the motor can be installed in a

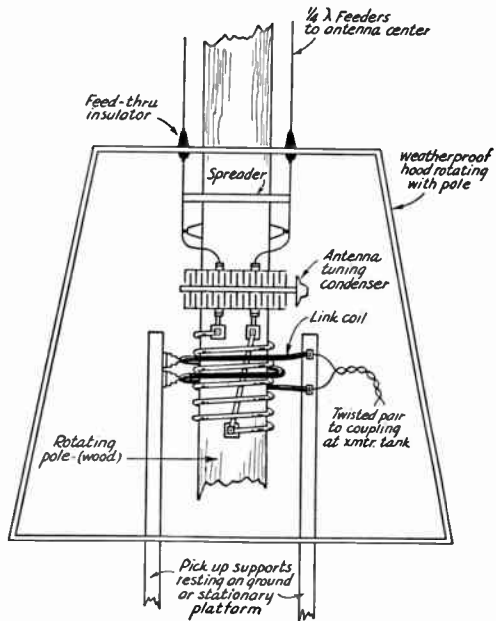


Fig. 10-102 — One method of transmission line-antenna system coupling which eliminates sliding contacts. The low-impedance line is link-coupled to a tuned line.

more accessible location (see Fig. 10-99).

Parts from junked automobiles often provide gear trains and bearings for rotating the antenna. Rear axles, in particular, can readily be adapted to the purpose. Driving motors and gear housings will stand the weather better if given a coat of aluminum paint followed by two coats of enamel and a coat of glyptal varnish. Even commercial units will last longer if treated with glyptal varnish. Be sure, of course, that the surfaces are clean and free from grease before painting them. Grease can be removed by brushing it with kerosene and then squirting the surface with a solid stream of water. The work can then be wiped dry with a rag.

If hand rotation of the beam is used, or if the rotating motor drives the beam through a pulley system, bronze cable or chain drive is preferable to rope. However, if you must use rope, be sure to soak it overnight in pure linseed oil and then let it dry for several days before installation.

The power and control leads to the rotator should be run in electrical conduit or in lead covering, and the metal should be grounded. Often r.f. appearing in power leads can be reduced by suitable filtering, but running wires in conduit is generally easier and more satisfactory. Any r.f. in the wiring can sometimes be responsible for feed-back in a 'phone transmitter. "Hash" from the motor is also reduced by shielding the wires, but it is often necessary to install a small filter at the motor to reduce this source of interference. Motor noise appearing in the receiver is a nuisance, since it is usual practice to determine the proper direction for the beam by rotating it while listening to the station it is desired to work and setting the antenna at the point that gives maximum signal strength.

The outside electrical connections should be soldered, bound with rubber tape followed by regular friction tape, and then given a coat of glyptal varnish.

# About V.H.F.

In the days when DX activity first burgeoned on our lower frequencies the assignments above 30 Mc. were not too highly regarded. It was assumed that propagation on these frequencies was limited to distances only slightly beyond the visual horizon, and thus the bands allocated to amateurs in this region were used principally in areas where large concentrations of population brought hundreds of workers within local range of one another. In the early thirties activity boomed on 56 Mc. in the larger cities of the United States, but there were few stations elsewhere. Use of frequencies higher than 60 Mc. was confined to a few experimentally-inclined amateurs here and there.

In 1934, '35 and '36, new types of propagation were discovered by amateurs, and the opportunities for v.h.f. DX so brought to light caused a tremendous growth in activity, particularly in areas where it had not previously existed. Up to this time, practically all v.h.f. work had been done with the simplest sort of gear, mainly modulated-oscillator transmitters and superregenerative receivers; but when our available space began to fill with DX signals it became obvious that, if we were to realize anything like the possibilities inherent in this type of work, we must have improved techniques, whereby more stations could be accommodated in a given area. Crystal-controlled transmitters and superheterodyne receivers, permitting utilization of the 56-Mc. band on a scale comparable with that obtain-

ing on lower frequencies, became the order of the day, and by the end of 1938 stabilization of transmitters used on all frequencies up to 60 Mc. became mandatory. Our 5-meter band had grown up!

With the impetus of improved techniques, operating ranges on 56 Mc. grew by leaps and bounds. Meanwhile the use of the simplest form of equipment was transferred to the next higher band, then 112 Mc; and this band, in turn, took over the burden of heavy urban occupancy formerly carried by the 5-meter band. Soon our principal cities were teeming with 112-Mc. activity, and before long it was found that this band, too, had much of interest to offer. Even more than had been the case on 56 Mc., it was found that weather conditions had a profound effect on 112-Mc. propagation, and before the close-down of amateur activity, at the entry of our country into the war, the record for 112-Mc. work had passed the 300-mile mark. There was a smattering of activity on the still higher frequencies of 224 and 400 Mc. as well.

During the war years the vast use of v.h.f., u.h.f. and s.h.f. equipment in countless war applications demonstrated that these frequencies, once thought to be almost useless, were of untold importance. In the postwar world the v.h.f. amateur need no longer apologize for his interests. His frequencies are among the most highly prized in the whole radio-frequency spectrum, and his is now regarded as one of the major fields of amateur endeavor.

## Propagation Phenomena

A thorough understanding of the basic principles of wave propagation, outlined in Chapter Four, is a most useful tool for the v.h.f. worker. Much of the pleasure and satisfaction to be derived from v.h.f. endeavor lie in making the best possible use of propagation vagaries resulting from natural phenomena. Contrary to the impression of many newcomers to the field, a working knowledge of v.h.f. propagation is not difficult of attainment. Below are listed the principal ways by which v.h.f. waves may be propagated over abnormal distances.

### *F<sub>2</sub>-Layer Reflection*

The "normal" contacts made on 28 Mc. and lower frequencies are the result of reflection of

the transmitted wave by the  $F_2$  layer, the ionization density of which varies with solar activity, the highest frequencies being reflected at the peak of the 11-year solar cycle. The maximum usable frequency (m.u.f.) for  $F_2$  reflection also rises and falls with other well-defined cycles, including daily, monthly, and seasonal variations, all related to conditions on the sun and its position with respect to the earth.

At the low point of the 11-year cycle, such as the period we were entering at the outbreak of war, the m.u.f. may reach 28 Mc. only during a short period each spring and fall, whereas it may go to 60 Mc. or higher at the peak of the cycle. The fall of 1946 saw the first authentic

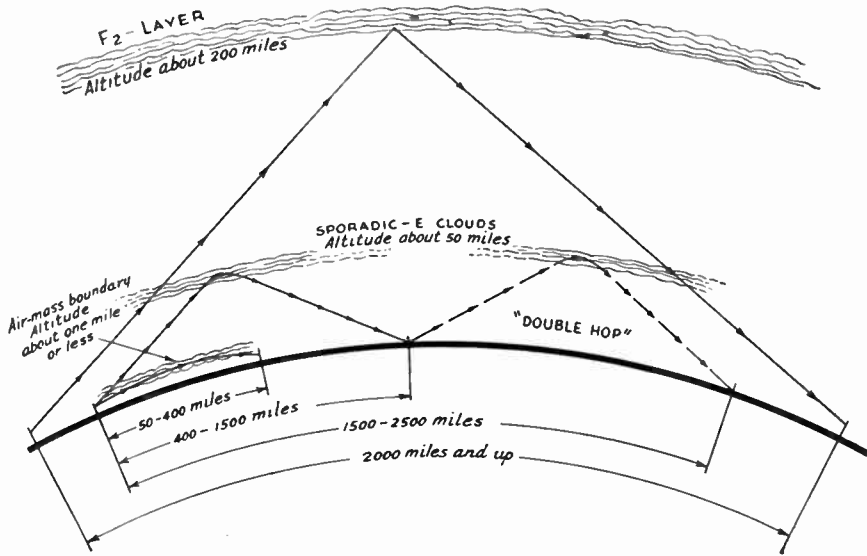


Fig. 11-1 — The principal means by which v.h.f. waves may be returned to earth. The  $F_2$  layer, highest of the known ionospheric layers, is capable of reflecting 50-Mc. signals during the period around the peak of the 11-year solar cycle, and may support communication over world-wide distances. Sporadic ionization of the  $E$  layer produces "short-skip" contacts at medium distances. It is a fairly frequent occurrence regardless of the solar cycle, but is most common in May through August. Refraction of v.h.f. waves also takes place at air-mass boundaries in the lower atmosphere, making possible reception of signals at distances up to 300 miles or more without a skip zone.

instances of long-distance 50-Mc. work by this medium, and it is probable that  $F_2$  DX will be workable on 50 Mc. until about 1950. In the northern latitudes there are peaks of m.u.f. each spring and fall, with a low period during the summer and a slight dropping off during the midwinter months. At or near the Equator conditions are more or less constant at all seasons.

Fortunately the  $F_2$  m.u.f. is quite readily determined by observation, and means are available whereby it may be estimated quite accurately for any path at any time. It is predictable for months in advance,<sup>1</sup> enabling the v.h.f. worker to arrange test schedules with distant stations at propitious times. As there are numerous signals, both harmonics and fundamental transmissions, on the air in the range between 28 and 50 Mc., it is possible for the listener to determine the approximate m.u.f. by careful listening in this range. A series of daily observations will serve to show if the m.u.f. is rising or falling from day to day, and once the peak for a given month is determined it can be assumed that the peak for the following month will occur about 27 days later, this cycle coinciding with the turning of the sun on its axis. The working range, via  $F_2$  skip, will be roughly comparable to that on 28 Mc., though the *minimum* distance is somewhat longer. Two-way work on 50 Mc. by

means of reflection from the  $F_2$  layer has been accomplished over distances ranging from 2200 to 10,500 miles. The maximum frequency for  $F_2$  reflection is believed to be in the vicinity of 70 Mc.

#### Sporadic-E Skip

Patchy concentrations of ionization in the  $E$ -layer region are often responsible for reflection of signals on 28 and 50 Mc. This is the popular "short skip" that provides fine contacts on both bands in the range between 400 and 1300 miles. It is most common in May, June and July, during the early evening hours, but it may occur at any time or season. Since it is largely unpredictable, at our present state of knowledge, sporadic- $E$  skip is of high "surprise value." Multiple-hop effects may appear, when ionization develops simultaneously over large areas, making possible work over distances of more than 2500 miles. As far as is known, no 144-Mc. effects have yet been observed, the known limit for sporadic- $E$  skip being in the vicinity of 100 Mc.

#### Aurora Effect

Low-frequency communication is occasionally wiped out by absorption of these frequencies in the ionosphere, when ionospheric storms, associated with variations in the earth's magnetic field, occur. During such disturbances, however, 50-Mc. signals may be reflected back to earth, making communication possible over distances not normally workable on this band. Magnetic storms may be accompanied by an aurora-borealis display, if the

<sup>1</sup> *Basic Radio Propagation Predictions*, issued monthly, three months in advance, by the Central Radio Propagation Laboratory of the National Bureau of Standards. Order from the Supt. of Documents, Washington 25, D. C.; \$1.50 per year.



disturbance occurs at night and visibility is good. When the aurora is confined to the northern sky, aiming a directional array at the auroral curtain will bring in 50-Mc. signals strongest, regardless of the true direction to the transmitting station. When the display is widespread there may be only a slight improvement noted when the array is aimed north. The latter condition is often noticed during the period around the peak of the 11-year cycle, when solar activity is spread well over the sun's surface, instead of being concentrated extensively in the region near the solar equator.

Aurora-reflected signals are characterized by a rapid flutter, which lends a "dribbling" sound to 28-Mc. carriers and may render modulation on 50-Mc. signals completely unreadable. The only satisfactory means of communication then becomes straight c.w. The effect may be noticeable on signals from any distance other than purely local, and stations up to about 500 miles in any direction may be worked at the peak of the disturbance. Unlike the two methods of propagation previously described, aurora effect exhibits no skip zone. It has been observed, to date, only on the frequencies up to about 60 Mc.

**Reflections from Meteor Trails**

Probably the least-known means of v.h.f. wave propagation is that resulting from the passage of meteors across the signal path. Reflections from the ionized meteor trails may be noted as a Doppler-effect whistle on the carrier of a signal already being received, or they may cause bursts of reception from stations not normally receivable. Sudden large increases in strength of normally-weak signals are another manifestation of this effect. Ordinarily such reflections are of little value in extending communication ranges, since the increases in signal strength are of short duration, but meteor showers of considerable magnitude and duration may provide fluttery 50-Mc. signals from distances up to 1000 miles or more. Signals so reflected have a combination

of the characteristics of aurora and sporadic-E skip.

**Tropospheric Bending**

Refraction of radio waves takes place whenever a change in refractive index is encountered. This may occur at one of the ionized layers of the ionosphere, as mentioned above, or it may exist at the boundary area between two different types of air masses, in the region close to the earth's surface. A warm, moist air mass from over the Gulf of Mexico, for instance, may overrun a cold, dry air mass which may have had its origin in northern Canada. Each tends to retain its original characteristics for considerable periods of time, and there may be a well-defined boundary between the two for as much as several days. When such an air-mass boundary exists near the midpoint between two v.h.f. stations separated by 50 to 300 miles or more, a considerable degree of refraction takes place, and signals run high above the average value. Under ideal conditions there may be almost no attenuation, and signals from far beyond the visual horizon will come through with strength comparable to that of local stations.

Many factors other than air-mass movement of a continental character may provide increased v.h.f. operating range. The convection that takes place along our coastal areas in warm weather is a good example. The rapid cooling of the earth after a hot day in summer, with the air aloft cooling more slowly, is another, producing a rise in signal strength in the period around sundown. The early-morning hours, when the sun heats the air aloft, before the temperature of the earth's surface begins its daily rise, may frequently be the best hours of the day for extended v.h.f. range, particularly in clear calm weather, when the barometer is high and the humidity low.

Any weather condition that produces a pronounced boundary between air masses of different temperature and humidity characteristics provides the medium by which v.h.f. signals cover abnormal distances. The ambi-

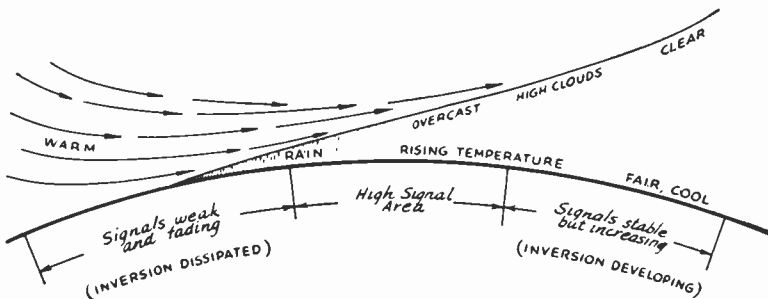


Fig. 11-2 — Illustrating a typical weather sequence, with associated variations in v.h.f. propagation. At the right is a cold air mass (fair weather, high or rising barometer, moderate summer temperatures). Approaching this from the left is a warm moist air mass, which overruns the cold air at the point of contact, creating a temperature inversion and considerable bending of v.h.f. waves. At the left, in the storm area, the inversion is dissipated and signals are weak and subject to fading. Barometer is low or falling at this point.

tious v.h.f. enthusiast soon learns to correlate various weather manifestations with radio-propagation phenomena. By watching temperature, barometric pressure, changing cloud formations, wind direction, visibility, and other easily-observed weather signs, he is able to tell with a reasonable degree of accuracy what is in prospect on the v.h.f. bands.

The responsiveness of radio waves to varying weather conditions increases with frequency. Our 50-Mc. band is considerably more sensitive to weather variations than is the 28-Mc. band, and the 144-Mc. band may show strong signals from far beyond visual distances when the lower frequencies are relatively inactive. It is probable that this tendency continues on up through the microwave range, and that our assignments in the u.h.f. and s.h.f. portions of the frequency spectrum may someday support communication over distances far in excess of the optical range. Already 144-Mc. communication by amateurs has passed the 600-mile mark, and even greater distances are believed possible on this and higher frequencies.

### ● STATION LOCATIONS

In line with our early notions of v.h.f. wave propagation, it was once thought that only highly-elevated v.h.f. stations had any chance of working beyond a few miles. Almost all the work was done by portable stations operating from mountain tops, and only hilltop home sites were considered suitable for fixed-station work. It is still true that the fortunate amateur who lives at the top of a hill enjoys a certain advantage over his fellows on the v.h.f. bands,

but high elevation is not the all-important factor it was once thought to be.

Improvements in equipment, the wide use of high-gain antenna systems, and an awareness of the opportunities afforded by weather phenomena have enabled countless v.h.f. workers to achieve excellent results from seemingly poor locations. In 50-Mc. DX work particularly, elevation has ceased to be an important factor, though it may help in extending the range of operation somewhat under normal conditions. A high elevation is somewhat more helpful on 144 Mc. and higher frequencies, particularly when no unusual propagation factors are present, as during the winter months. Other factors, such as close proximity to large bodies of water, may more than compensate for lack of elevation during the other seasons of the year, however.

Stations situated in sea-level locations along our coasts have been consistent in their ability to set distance records on 144 Mc.; weather variations provide interesting propagation effects over our Middle Western plain areas; and even the worker situated in mountainous country need not necessarily feel that he is prevented by the nature of his horizon from doing interesting work. Contacts have been made on 50 and 144 Mc. over distances in excess of 100 miles in all kinds of terrain.

The consistently-reliable nature of 50 and 144 Mc. for work over such a radius and more, regardless of weather, time or season, and the occasional opportunities these frequencies afford for exciting DX, have caused an increasing number of amateurs to migrate to the v.h.f. bands for extended-local communication, once thought possible only on the lower frequencies.

## V.H.F. Techniques

Recognition of the value of the very-high frequencies has resulted in the development of many tubes and other components especially suited for use at these frequencies. Where, not so many years ago, it was necessary to remove the bases from available tubes, and otherwise cut down components designed for use at lower frequencies, we now have tubes and circuit components specifically designed for high-efficiency operation, not only on the v.h.f. bands, but on up through the microwave range. Examples of transmitting tubes especially made for v.h.f. work are shown in Fig. 11-3.

The higher frequencies are rapidly becoming the primary field of interest for those amateurs who like to design and build their own equipment. While there is an increasing tendency to the purchase of commercially-built equipment, both transmitting and receiving, for low-frequency operation, most gear used for v.h.f. and higher bands is still a product of the amateur's own ingenuity.

In the field of antenna design, too, the v.h.f. bands offer much to the amateur who is inter-

ested in experimental work. With their smaller physical size making for greater ease of construction and adjustment, the development of high-gain directional antennas continues to occupy much of the time devoted by the v.h.f. enthusiast to experimental work.

### ● TRANSMITTER DESIGN

The use of crystal control, or its equivalent in stability, is standard for 50-Mc. work. The design of transmitters for this band differs hardly at all from that employed for lower amateur frequencies, except that much more care must be exercised in the selection of component parts and their placement in the equipment, in order to avoid more than the absolute minimum length in the connecting leads. Customary procedure is to start with a crystal or variable-frequency oscillator, operating at 6, 8, or 12 Mc., and follow with such frequency-multiplying stages as may be required to reach 50 Mc. The power level is not particularly important, as interference is not a critical factor

in 50-Mc. communication. Much good work has, in fact, been accomplished with power inputs under 100 watts and even stations in the 10-watt class are quite capable of working out well, particularly if equipped with well-designed antenna systems.

At 144 Mc. crystal control is becoming more popular daily. It is somewhat more difficult of attainment than at 50 Mc., but the construction of a crystal-controlled transmitter for 144 Mc. is not beyond the capabilities of the average amateur. The number of usable tube types is limited, however, and only those specifically designed for v.h.f. applications can be used successfully. Even with such tubes, great care must be exercised to keep leads and circuit capacitances down. Conventional coil-and-condenser combinations designed for lower frequencies are generally unsatisfactory, and only well-designed tank circuits will operate efficiently at this frequency. High power is seldom employed in 144-Mc. operation, most workers preferring to use high-gain antenna systems rather than high-powered transmitters, at this and higher frequencies.

For 235 Mc. and higher, crystal control may be employed, and its use is desirable where possible, but the modulated-oscillator type of transmitter still bears the brunt of operation on 235 Mc., and is used almost exclusively for 420 Mc. and higher. Since occupancy is relatively low, the broader signals radiated by such equipment and the inefficiencies of the superregenerative receivers necessary to accommodate them, are not major problems.

● RECEIVER CONSIDERATIONS

Even more than in work on lower frequencies, a good receiver is all-important in the v.h.f. station. Though commercial receivers that cover the 50-Mc. band are slowly appearing on the amateur market, the most satisfactory and inexpensive solution to the receiver problem is still that of a converter that works into a communications receiver



Fig. 11-3 — Vacuum tubes designed especially for high-efficiency operation at very-high frequencies are now available for amateur use. Several such tubes are shown above, in comparison to typical low-frequency tubes, the 813 and V-70-D at the left. The v.h.f. types are the 6L-592, 35TG, 21G, 11Y-75-A, all triodes; and the 829-B, 11K-57, and 832-A, all tetrodes.

designed for the lower frequencies. Such a combination is almost certain to give better results on 50 Mc. than a complete receiver, unless the latter is designed especially for v.h.f. use.

Converters are replacing the once-popular superregenerative receivers for 144-Mc. use also, particularly for fixed-station work in localities where the use of stabilized transmitters has become more or less standard procedure. Many types of superhet receivers used for radar and aircraft service during the war are convertible to amateur use, and hundreds of such surplus units are now employed by amateurs working on 144 Mc.

For portable or emergency use, where small size and low battery drain are important, the simple superregenerative receiver is still popular. For the number of tubes and parts required, it is still an efficient receiving system, especially in areas where there is not extensive activity. For frequencies higher than 148 Mc. it is still the principal receiving system, though the converter approach is practical for any frequency. To accommodate the broader signals generally found on these frequencies, a converter may be used in conjunction with a wide-band i.f. system, such as a receiver designed for FM broadcast reception.

# V.H.F. Receivers

In its essentials most modern receiving equipment for the 28- and 50-Mc. bands differs very little from that used on lower frequencies. The 28-Mc. band serves as the meeting ground between what are ordinarily termed "communications frequencies" and the very-highs, and it will be found that most of the receivers described in Chapter Five are capable of working on 28 Mc. In this chapter are described receivers and converters capable of good performance on 50 Mc. and higher.

Federal regulations impose identical requirements on all frequencies below 54 Mc. respecting stability of frequency and, when amplitude modulation is used, freedom from frequency modulation. Thus receivers for 50-Mc. AM reception may have the same selectivity as those designed for the lower frequencies. This order of selectivity is not only possible but desirable, since it permits a considerable increase in the number of transmitters that can work in the band without undue interference. High selectivity also aids greatly in improving the signal-to-noise ratio, both as concerns noise originating in the receiver itself and in its response to external noise. The effective sensitivity of such a receiver can be made considerably higher than is possible with nonselective receivers.

## *Superheterodynes for V.H.F.*

The superheterodyne system of reception is used almost universally on 50 Mc., and to a considerable extent on 144 Mc., because it is the only type that fulfills the stability, selectivity and sensitivity requirements. AM superheterodynes and those for FM reception differ only in the i.f. amplifier and second detector, so that a single high-frequency converter may be used for either AM or FM.

Superheterodynes for 50 Mc. and higher should have fairly-high intermediate frequencies to reduce both image response and oscillator "pulling." For example, a difference between signal and image frequencies of 900 kc. (the difference when the i.f. is 450 kc.) is a very small percentage of the signal frequency; consequently, the response of the r.f. circuits to the image frequency is nearly as great as to the desired frequency. To obtain discrimination against the image equal to that obtainable at 3.5 Mc. would require an i.f. 16 times as high, or about 7 Mc. However, the  $Q$  of tuned circuits is less in the v.h.f. range than it is at lower frequencies, chiefly because the tube

loading is considerably greater, and thus still higher intermediate frequencies are desirable. A practical compromise is reached at about 10 Mc., and the standard i.f. for converters and commercial v.h.f. receivers is 10.7 Mc.

To obtain high selectivity with a reasonable number of i.f. stages, the double-superheterodyne principle is often employed. A 10-Mc. intermediate frequency, for example, is changed to a second i.f. of perhaps 450 kc. by an additional oscillator-mixer combination.

Few amateurs build complete 50-Mc. superheterodyne receivers. General practice in this band has been to use a conventional communications receiver to handle the i.f. output of a simple 50-Mc. frequency converter. Even an all-wave broadcast receiver may be used with excellent results on 50 Mc. by the addition of a relatively simple converter.

The superheterodyne type of receiver is finding increased favor for 144-Mc. work also, as the occupancy of that band increases. Especially in heavily-populated areas, stabilization of transmitters and an improvement in the selectivity of receivers are becoming almost mandatory, particularly for those operators who are interested in exploiting the full possibilities of this band.

With a well-designed converter, a considerable improvement in signal-to-noise ratio can be achieved in 144-Mc. reception by using such a converter in conjunction with a communications receiver. Only crystal-controlled or other stable signals can be received in this manner, but the effective sensitivity will be better than is possible with a less critical broad-band receiver. An example of a simple but effective converter for 2-meter use is shown in Figs. 12-16 through 12-19.

In any superheterodyne for 144 Mc. a primary problem is that of oscillator stability. One satisfactory solution is the use of a crystal-controlled oscillator and frequency multiplier to supply the injection voltage, the method used in the converter shown in Figs. 12-13-12-15. All r.f. circuits are then fixed-tuned, and coverage of the band is attained by tuning the communications receiver (or i.f. system) over a range of 4 Mc. This can be 14 to 18 Mc. in the case of certain war-surplus receivers, or it may be any higher frequency within the range of the communications receiver.

A converter working into an FM receiver, or into a broad-band i.f. channel designed for

either AM or FM reception, provides a quite satisfactory means of reception of signals, not only at 144 Mc., but on up through the microwave range. This approach has been used in most of the recent pioneering efforts by amateurs working in the microwave field.

### The Superregenerative Receiver

The simplest type of v.h.f. receiver is the **superregenerator**, long favored in amateur work. It affords good sensitivity with few tubes and elementary circuits. Its disadvantages are lack of selectivity and, if the oscillating detector is coupled to an antenna, a tendency to radiate a signal which may cause severe interference to other receivers. To some extent the lack of selectivity is advantageous, since it makes for easy tuning, and permits reception of all signals within its tuning range, however unstable they may be. To reduce radiation, a superregenerative detector should be preceded by an r.f. stage, or, if the detector is coupled directly to the antenna, it should be operated at the lowest plate voltage that will permit superregeneration.

From a practical aspect, superregenerative receivers may be divided into two general types. In the first the quenching voltage is developed by the detector tube functioning as a "self-quenched" oscillator. In the second, a separate oscillator tube is used to generate the quench voltage. Self-quenched superregenerators have found wide favor in amateur work. The simpler types are particularly suited for portable equipment, which must be kept as simple as possible. Many amateurs have "pet" circuits claimed to be superior to all others, but the probability is that the arrangement of a particular circuit has led to correct operating conditions. Time spent in minor adjustments will result in a smooth-working receiver.

### Superregeneration Principles

The limit to which ordinary regenerative amplification can be carried is the point at which oscillations commence, since at that point further amplification ceases. The *superregenerative* detector overcomes this limitation by introducing into the detector circuit an alternating voltage of a frequency somewhat above the audible range (of the order of 20 to 200 kilocycles), in such a way as to vary the

detector's operating point. As a consequence of the introduction of this **quench** or **interruption** frequency, the detector can oscillate only when the varying operating point is in a region suitable for the production of oscillations. Because the oscillations are constantly being interrupted, the regeneration can be greatly increased, and the amplified signal will build up to tremendous proportions. A one-tube superregenerative detector is capable of an inherent sensitivity approaching the thermal-agitation noise level of the tuned circuit, and may have an antenna input sensitivity of two microvolts or better.

Because of its inherent characteristics, the superregenerative circuit is suitable only for the reception of modulated signals, and operates best on the very-high frequencies. Typical superregenerative circuits for v.h.f. are shown in Fig. 12-1, but the basic circuit may be any of the various arrangements used for straight regenerative detectors.

In Fig. 12-1A the quench frequency is obtained from a separate oscillator and introduced into the plate circuit of the detector.

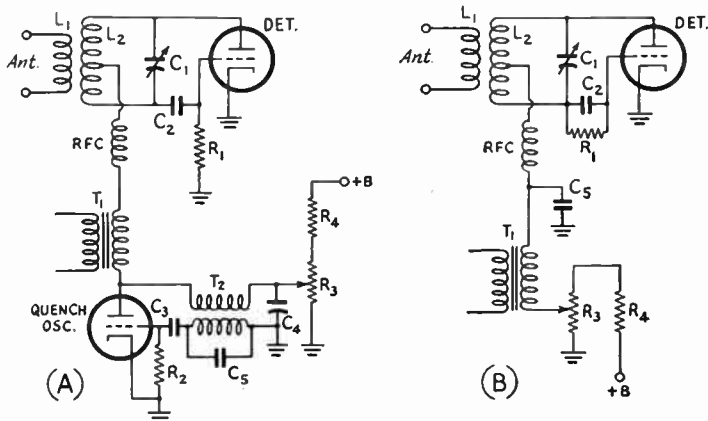


Fig. 12-1 — (A) Superregenerative detector circuit using a separate quench oscillator. (B) Self-quenched superregenerative detector circuit.  $L_2C_1$  is tuned to the signal frequency. Typical values for other components are:

- $C_2 = 17 \mu\text{fd.}$
- $C_3 = 170 \mu\text{fd.}$
- $C_4 = 0.1 \mu\text{fd.}$
- $C_5 = 0.001\text{--}0.005 \mu\text{fd.}$
- $R_1 = 2\text{--}10 \text{ megohms.}$
- $R_2 = 17,000 \text{ ohms.}$
- $R_3 = 50,000\text{-ohm potentiometer.}$

- $R_1 = 47,000 \text{ ohms.}$
- RFC — R.F. choke, value depending upon frequency. Small low-capacitance chokes are required for v.h.f. operation.
- $T_1$  — Audio transformer, plate-to-grid type.
- $T_2$  — Quench-oscillator transformer.

The quench oscillator, operating at a low radio frequency, alternately allows oscillations to build up in the regenerative circuit and then causes them to die out. In the absence of a signal, the thermal-agitation noise in the input circuit produces the voltage that initiates the build-up process. However, when an incoming signal provides the initiating pulse, it has the effect of advancing the starting time of the oscillations. This causes the area within the envelope to increase, as indicated in Fig. 12-2C.

If regeneration in an ordinary regenerative circuit is carried sufficiently far, the circuit will

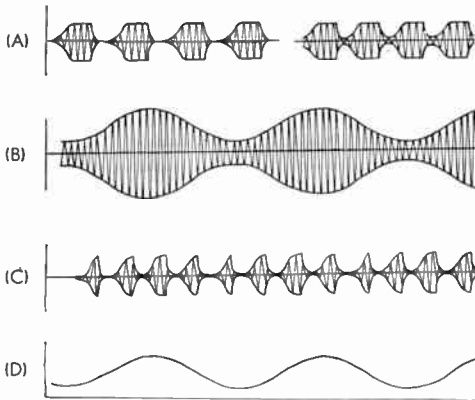


Fig. 12-2 — R.f. oscillation envelopes in a self-quenched superregenerative detector. Without signal (A at left) oscillations are completely quenched after each period, resuming in random phase depending on momentary noise voltages. At right, when the initiating pulses are supplied by a received signal the starting time of the oscillations is advanced causing the build-up period to begin before damping is complete. This advance is proportional to the carrier amplitude when modulated (B). Since the building-up period varies in accordance with modulation (C), when these wave trains are rectified the average rectified current is proportional to the amplitude of the signal. Amplitude modulation is therefore reproduced as an audio wave in the output circuit (D).

break into a low-frequency oscillation simultaneously with that at the operating radio frequency. This low-frequency oscillation has much the same quenching effect as that from a separate oscillator, hence a circuit so operated is called a *self-quenching* superregenerative de-

tector. The frequency of the quench oscillation depends upon the feed-back and upon the time constant of the grid leak and condenser, the oscillation being a "blocking" or "squegging" in which the grid accumulates a strong negative charge which does not leak off rapidly enough through the grid leak to prevent a relatively slow variation of the operating point.

The greater the difference between the quenching and signal frequencies the greater the amplification, because the signal then has a longer period in which to build up during the nonquenching half-cycle when the resistance of the circuit is negative. This ratio should not exceed a certain limit, however, for during the quenched or nonregenerative intervals the input selectivity is merely that of the  $Q$  of the tuned circuit alone.

Because of the greater amplification, the hiss noise when a superregenerative detector goes into oscillation is much stronger than with the ordinary regenerative detector. The most sensitive condition is at the point where the hiss first becomes marked. When a signal is tuned in, the hiss will disappear to a degree that depends upon the signal strength.

Lack of hiss indicates insufficient feed-back at the signal frequency, or inadequate quench voltage. Antenna-loading effects will cause dead spots that are similar to those in regenerative detectors and can be overcome by the same methods. The self-quenching detector may require critical adjustment of the grid-leak and grid-condenser values for smooth operation, since these determine the frequency and amplitude of the quench voltage.

## T.R.F. Superregenerative Receiver

The 144-Mc. receiver in Figs. 12-3-12-7 uses miniature tubes throughout and is intended for either home or portable/mobile use. The r.f. amplifier stage furnishes some additional gain over a straight superregenerative detector, affords freedom from antenna effects, and — most important of all — prevents radiation from the receiver. Although the r.f. and detector circuits are individually tuned, the broad tuning of the r.f. stage makes the receiver essentially a single-dial affair — important in mobile work — and the miniature tubes permit compact assembly and low current consumption. Total heater current is 625 ma. at 6.3 volts, and the total plate-current drain from 135 volts of "B" battery is less than 10 ma.

The tuned r.f. amplifier stage uses a 6AK5 pentode which is coupled through  $C_5$  to the 6C4 superregenerative triode detector. This in turn is transformer-coupled to a 6C4 audio stage which drives the 6AK6 output stage. A plate coupling choke,  $L_4$ , and the coupling condenser  $C_{12}$  remove d.c. from the output jack,  $J_2$ , and eliminate the possibility of short-circuiting the plate supply at this point.

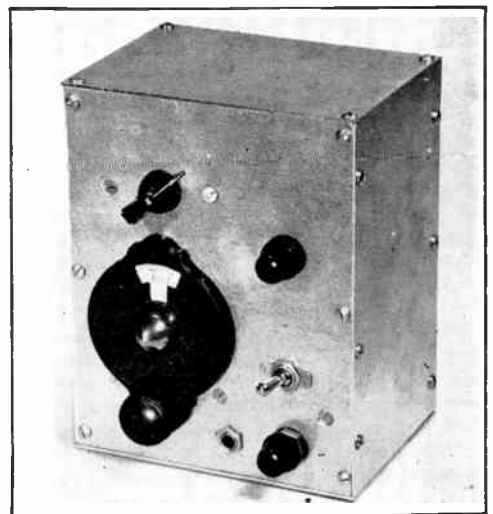


Fig. 12-3 — Front view of the 144-Mc. t.r.f. receiver. The pointer knob above the vernier dial tunes the r.f. stage. The small round knobs are for audio volume (lower right) and detector plate-voltage variation. Dimensions of the handmade case are  $7 \times 5\frac{1}{2} \times 4$  inches.

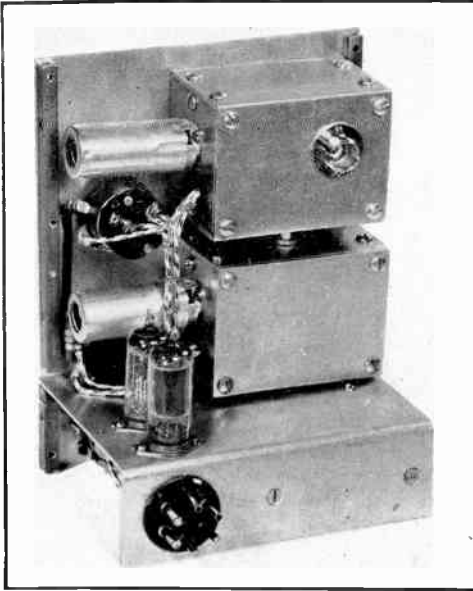


Fig. 12-4 — Rear view of the complete receiver. Note that the r.f. stage and superregenerative-detector circuit components are in separate completely-enclosed compartments, for elimination of radiation. Miniature tubes are used throughout, for compactness and low current consumption.

boxes are completely assembled. The wire between  $C_5$  and  $L_3$  runs through two Millen 32150 bushings in the walls of the two shield compartments. This interconnection, the only one except for the power circuits, is made by running separate leads from the condenser and coil through the bushings and then soldering the two ends together after the two units are mounted on the front panel.

The detector tuning condenser,  $C_5$ , is a regular Cardwell ZV-5-TS modified by adding a single circular plate to the regular one-plate rotor. This additional constant capacitance across the circuit increases the bandsread and, because it decreases the  $L$ -to- $C$  ratio, smooths out the regeneration so that the regeneration control,  $R_{10}$ , does not have to be readjusted within the 144-Mc. band.

### Mechanical Details

The receiver chassis and partitions are built from pieces of  $\frac{1}{16}$ -inch aluminum held together at the corners with machine screws and strips of  $\frac{1}{4}$ -inch-square brass rod. The over-all dimensions are  $7 \times 5\frac{1}{2} \times 4$  inches — the chassis that mounts the audio components is  $4 \times 5$  inches with a  $1\frac{3}{4}$ -inch folded lip. To eliminate oscillation in the r.f. stage and radiation from the detector, completely-separate compartments are used for the r.f. and detector stages. These compartments consist of identical boxes that measure  $1\frac{7}{8}$  inches square and 3 inches long. The tube sockets are mounted on the end plates, and all of the connections to the sockets are made before the

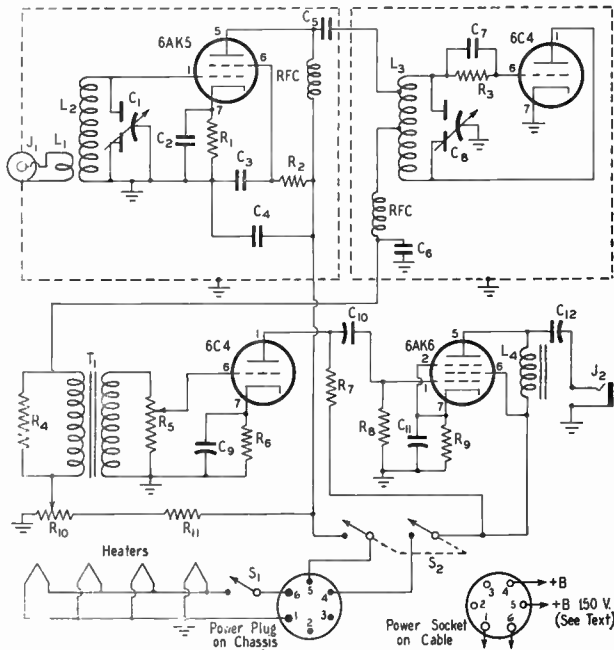


Fig. 12-5 — Wiring diagram of the 4-tube r.f. superregenerative receiver. Shield compartments housing r.f. and detector stages are shown by dotted lines.

- $C_1, C_8$  — Split-stator condenser (Cardwell ZV-5-TS). See text.
- $C_2, C_3, C_4$  — 470- $\mu$ fd. midget mica.
- $C_5, C_7$  — 17- $\mu$ fd. midget mica.
- $C_6$  — 0.0022- $\mu$ fd. midget mica.
- $C_9, C_{11}$  — 10- $\mu$ fd. 25-volt midget electrolytic.
- $C_{10}, C_{12}$  — 0.1- $\mu$ fd. paper.
- $R_1$  — 1500 ohms,  $\frac{1}{2}$  watt.
- $R_2, R_7, R_8$  — 0.1 megohm,  $\frac{1}{2}$  watt.
- $R_3$  — 3.3 megohms,  $\frac{1}{2}$  watt.
- $R_4$  — 39,000 ohms,  $\frac{1}{2}$  watt. See text.
- $R_5$  — 0.5-megohm potentiometer.
- $R_6$  — 2200 ohms,  $\frac{1}{2}$  watt.
- $R_9$  — 680 ohms,  $\frac{1}{2}$  watt.

- $R_{10}$  — 50,000-ohm potentiometer.
- $R_{11}$  — 22,000 ohms, 1 watt.
- $L_1$  — 2 t.  $\frac{3}{8}$ -inch i.d. No. 18 enam. inserted between turns of  $L_2$  at cold end.
- $L_2$  — 4 t.  $\frac{3}{8}$ -inch i.d.,  $\frac{3}{4}$  inch long, No. 18 tinned.
- $L_3$  — 5 t. center-tapped,  $\frac{1}{2}$  inch long, No. 18 tinned. R.f. coupling tap 1 t. from grid end.
- $L_4$  — Midget audio or filter choke (Inca D-92).
- $J_1$  — Coaxial socket (Jones S-201). Matching plug for antenna is P-101 or P-201.
- $J_2$  — Headphone or speaker jack.
- RFC — See text.
- $S_1$  — S.p.s.t. switch on  $R_{10}$ .
- $S_2$  — D.p.s.t. toggle switch.
- $T_1$  — Midget audio transformer (Thordarson T-13A34).

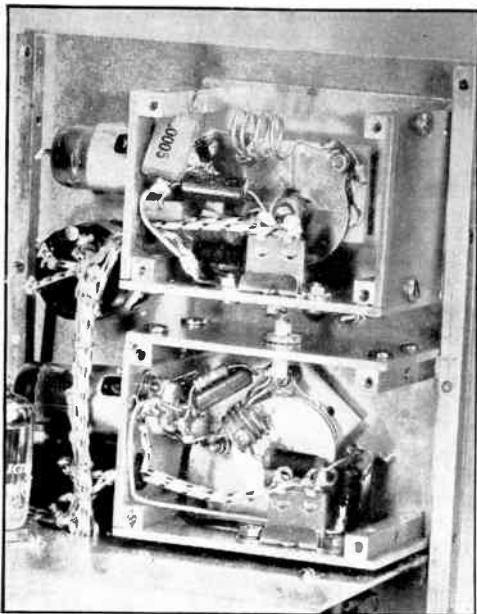


Fig. 12-6 — Close-up view of the r.f. and superregenerative-detector compartments, with back plates removed to show details. Top, back, and right side may be removed from either assembly, providing accessibility despite compact design.


The two r.f. chokes, *RFC*, are homemade affairs wound on 1-watt IRC composition resistors — 0.22 megohm or higher — of the insulated type that is  $\frac{1}{4}$  inch in diameter and  $2\frac{1}{32}$  inch long. The ends are notched with a small file or saw, to prevent the ends of the coil wire from slipping after they have been soldered to the pigtail leads of the resistor, and then a single layer of No. 30 d.s.c. is wound on for a length of  $1\frac{7}{32}$  inch. No lacquer or dope should be used on the winding because of the increased distributed capacitance that would result.

#### Adjustments

When the receiver is completely wired the first move should be to check detector operation. With the 6AK5 in its socket, but with no plate or screen voltage applied to it, apply the plate voltage to the detector and check for the customary hiss. Try the regeneration control,  $R_{10}$ , to determine whether the detector goes in and out of superregeneration smoothly. Some variation in values of  $R_3$ ,  $R_4$  and  $C_6$  may be necessary to attain this end, and some 6C4s work better than others in this respect.



Fig. 12-7 — Bottom view, showing audio-component arrangement.

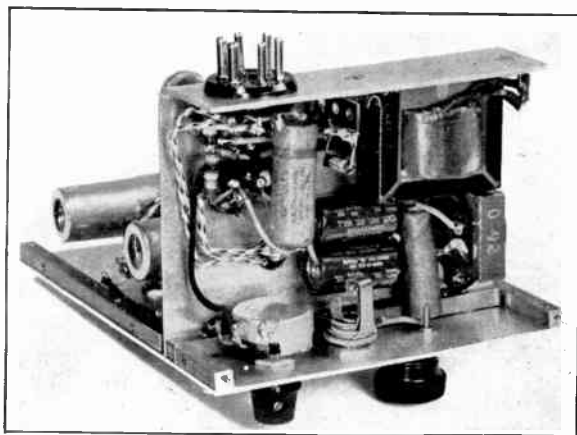

Next, the tuning range should be checked by means of Lecher wires or an absorption-type wavemeter. With the values given, 144 Mc. should fall at about 80 on the dial, with 148 Mc. at around 60. The position of the r.f. coupling tap on  $L_3$  will have considerable effect on the resonant frequency of the combination. Its position is not critical, except for its effect on the tuning range of the detector circuit, but the spacing of the turns in the coil will have to be changed if the position of the tap is materially different from that given.

When the detector is found to be in the band, the r.f. stage may be put into operation. With any of the shields removed, or with no antenna connected, the 6AK5 will probably oscillate, blocking the detector, but this effect will disappear when the two compartments are completely assembled and an antenna attached by means of the coaxial connector. If the r.f. stage is operating properly there will be slight change in the character of the hiss when the stage is tuned through resonance. Using a signal generator (the harmonic of any oscillator which falls in the 144-Mc. band will do) or the signal of a 144-Mc. station, there will be a pronounced drop in background noise and a slight change in dial setting of the detector when the r.f. stage is tuned "on the nose." Once the r.f. tuning is adjusted for maximum response, preferably on a weak signal near the middle of the band, it may be left at that setting for all except the very weakest signals at either end.

#### Power Supply

Power-supply filtering and regulation are important factors in attaining smooth and efficient performance with superregenerative detectors. The power plug mounted on the back of the chassis provides a separate connection (Pin 5) for the detector and r.f. +B, in order that this may be drawn from a regulated source, such as a VR-150. The other pin marked "+B" (Pin 4) supplies the audio tubes, and the voltage used here need not be regulated. If "B" batteries are used — and they are highly recommended for mobile oper-



ation — Pins 4 and 5 may be connected together in the power socket on the cable. The use of "B" batteries in mobile work will result in better sensitivity and more quiet operation than will be available with any sort of mobile power supply, vibrator or dynamotor, and the drain from the car battery will be negligible

during receiving periods. Medium-size "B" batteries will last through a year or more of normal operation. When batteries are used, the on-off switch,  $S_2$ , should be thrown to the "off" position when the receiver is not in use, otherwise there will be a small continuous drain on the batteries through the  $R_{10}$ - $R_{11}$  bleeder.

### Simple Two-Tube Converter for 50 Mc.

When a high intermediate frequency is used, image rejection is not a problem, and r.f. selectivity in the converter is not particularly important, especially when the converter is used in conjunction with a highly-selective communications receiver. Thus quite satisfactory performance can be obtained without the use of an r.f. amplifier stage. The new high-transconductance miniature pentodes, such as the 6AK5, are excellent as mixers, and a two-tube converter incorporating the 6AK5 in an appropriate circuit will give a degree of performance formerly obtainable only with more complex designs. Such a converter is shown in Figs. 12-8-12-12. It was designed by Richard W. Houghton, WINKLE, and was described in detail in *QST* for June, 1946. Though it was laid out particularly for use with an HRO it may be used effectively with any communications receiver capable of tuning to 10.5 Mc.

As shown in the schematic diagram, Fig. 12-10, the oscillator voltage is injected at the screen grid of the mixer tube. The coupling condenser,  $C_9$ , has sufficient capacitance to act as the 6AK5 screen by-pass condenser as well. The grid tank circuit, comprised of  $L_2$  in parallel with  $C_1$ ,  $C_2$  and  $C_3$ , resonates over the operating frequency range, 49.5 to 54.8 megacycles. Ca-

pacitor  $C_3$  is ganged with the oscillator tuning condenser,  $C_6$ .

The oscillator operates over a range 10.5 Mc. higher than that of the mixer, and the mixer plate circuit is tuned to this intermediate frequency. With this i.f., the fifth harmonic of the receiver's local oscillator ( $10.955 \times 5 = 54.775$  Mc.) appears just outside the high end



Fig. 12-8 — This two-tube 50-Mc. converter incorporates miniature tubes and obtains its power from the communications receiver with which it is used. The toggle switch at the left cuts the filament circuit when the unit is not in use. The control at the lower right transfers the antenna from the converter to the receiver for normal reception.

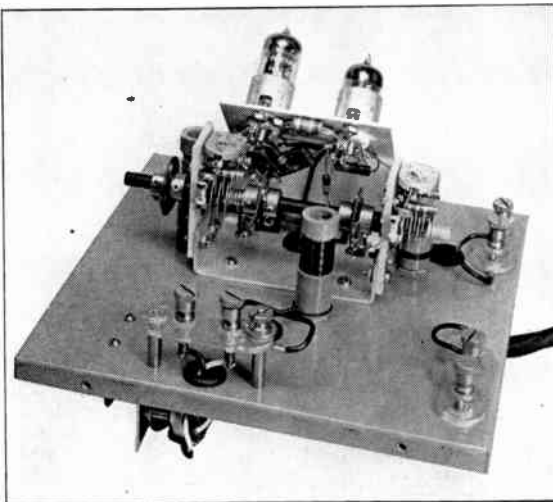


Fig. 12-9 — The r.f. construction of the 50-Mc. converter is shown in this above-chassis view. The 6CA oscillator is at the left and 6AK5 mixer at the right on the subchassis. The 10.5-Mc. i.f. output coil is in the foreground. Flexible ground leads are shown connected to their binding posts in the position normally used for grounded antenna systems.

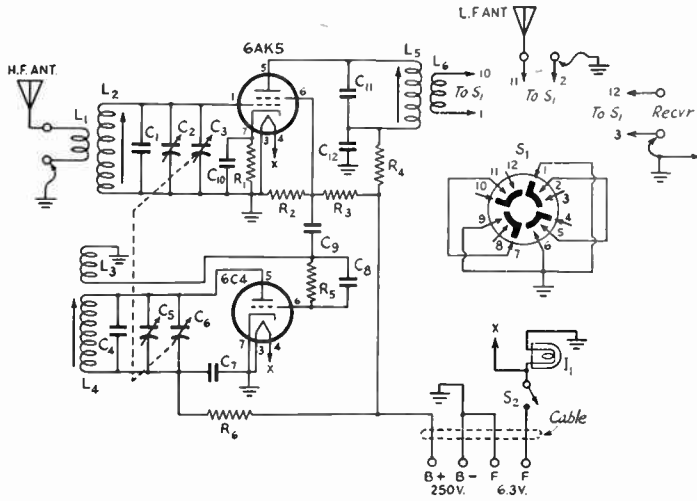


Fig. 12-10 — Circuit diagram of the 50-Mc. converter.

- C<sub>1</sub> — 15- $\mu$ fd. fixed ceramic, zero temp. coef. (Eric NPOA).
- C<sub>2</sub>, C<sub>5</sub> — 2-6- $\mu$ fd. ceramic trimmer (Centralab 820-A).
- C<sub>3</sub> — 11- $\mu$ fd. variable (National UMA-10 with 1-stator plate removed).
- C<sub>4</sub> — 12- $\mu$ fd. fixed ceramic, zero temp. coef. (Eric NPOA).
- C<sub>6</sub> — 9- $\mu$ fd. variable (National UMA-10 with 1-stator and 1-rotor plate removed).
- C<sub>7</sub>, C<sub>8</sub>, C<sub>9</sub> — 100- $\mu$ fd. mica or ceramic.
- C<sub>10</sub>, C<sub>12</sub> — 47- $\mu$ fd. mica or ceramic.
- C<sub>11</sub> — 35- $\mu$ fd. fixed ceramic, zero temp. coef. (Eric NPOA).
- R<sub>1</sub> — 6800 ohms,  $\frac{1}{2}$  watt.
- R<sub>2</sub> — 1.5 megohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 0.17 megohm,  $\frac{1}{2}$  watt.
- R<sub>4</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.
- R<sub>5</sub> — 22,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>6</sub> — 10,000 ohms, 1 watt.
- L<sub>1</sub> to L<sub>6</sub>, inc. — See Fig. 12-11.
- I<sub>1</sub> — 6.3-volt pilot lamp.
- S<sub>1</sub> — 4-pole double-throw switch, preferably with ceramic wafers (Oak Type 11C).
- S<sub>2</sub> — S.p.s.t. toggle.

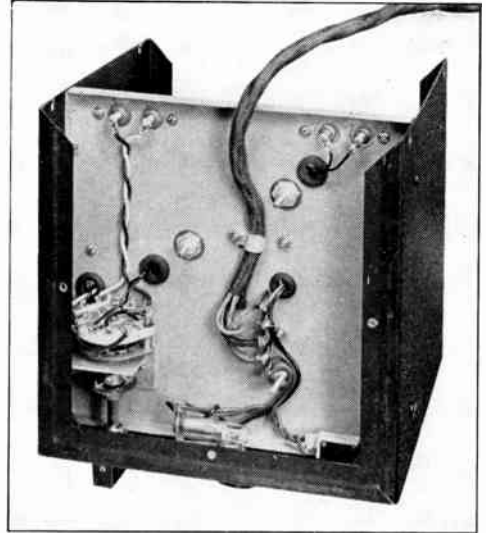


Fig. 12-12 — A bottom view of the converter. S<sub>1</sub>, the antenna-transfer switch, is at the lower left. Low-impedance antenna leads should be twisted loosely as shown. The three adjusting screws for the iron-core inductances protrude from the chassis on either side of the power cord.

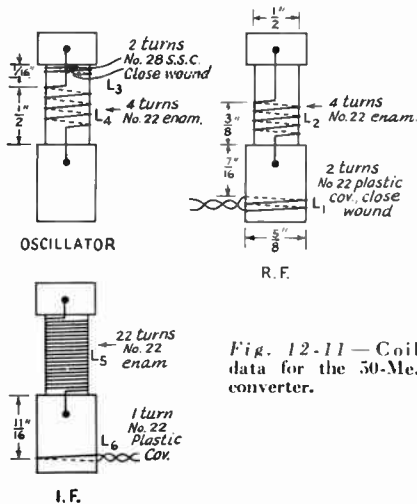


Fig. 12-11 — Coil data for the 50-Mc. converter.

mixer. Sufficient fixed padding capacitance, using a zero-temperature-coefficient ceramic for low over-all temperature drift, is added to give the required range. The coil forms used are provided with adjustable cores of high-frequency powdered iron, providing an easily-accessible inductance adjustment.

The wafer-type switch, S<sub>1</sub>, provides a convenient means of channeling either the converter output or a low-frequency antenna into the antenna terminals of the receiver. When the converter is in use both low-frequency antenna terminals are switched to ground, thus minimizing direct receiver pick-up at the intermediate frequency. Single-wire or doublet

antennas may be used at either high- or low-frequency inputs.

When operating the receiver over its normal frequency range, the converter filaments may be turned off by means of switch  $S_2$ . This function also could be accomplished by means of an additional wafer on  $S_1$ .

A four-prong-to-four-prong adapter, of the sort used for making tube substitutions, is used

on the power cord to enable both it and the receiver cord to be plugged into the IRO power pack simultaneously. With receivers having integral power packs a different arrangement would be required, one possibility being to use a similar plug adapter under one of the power tubes in the receiver, picking up the "B" voltage at the screen-grid pin. A separate supply may be used if desired.

## Crystal-Controlled Converter for 144 Mc.

While most converters are used in the manner described above (by leaving the communications receiver set at a given intermediate frequency and tuning the converter over the desired frequency range), it is quite possible to reverse the procedure, using a fixed-frequency oscillator in the converter and tuning the receiver. This approach is particularly advantageous at 144 Mc. and higher, where the selectivity of the tuned circuits is such that no adjustment of the converter circuits is required when the i.f. (in this case usually a broad-band receiver) is varied over a four-megacycle range.

Several converters employing this principle were described by Calvin F. Hadlock, W1CTW, in the May 1946 issue of *QST*. The simplest is shown in Figs. 12-13, 12-14 and 12-15. It uses a 6J6 oscillator-doubler, operating with a 28-Mc. crystal, followed by a 6C4 doubler and a 6AK5 mixer, the grid circuit of which is tuned to 146 Mc. and coupled to the antenna. The plate circuit of the mixer is the input circuit of a receiver (see Fig. 12-14) that tunes the range between 30 and 34 Mc. The converter

was designed for use with the National One-Ten, a superregenerative receiver, but it should provide excellent results when used with any

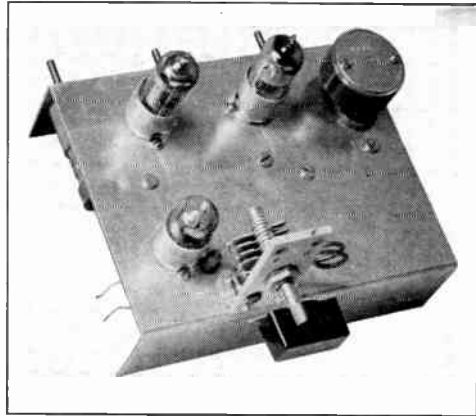


Fig. 12-13 — Top view of the three-tube 144-Mc. converter using a 10-meter crystal. Space is provided at the right of the mixer for addition of an r.f. stage.

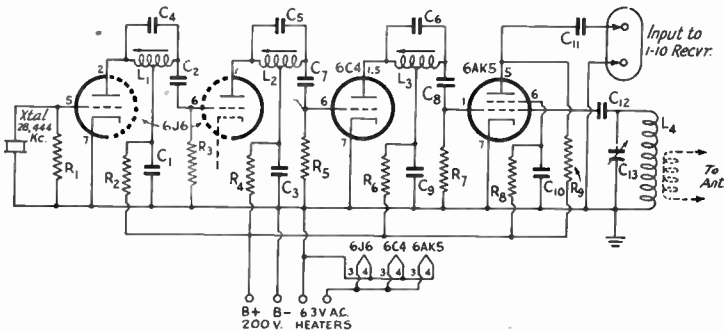


Fig. 12-14 — Schematic of the 3-tube 2-meter converter, using a 28-Mc. crystal.

- $C_1, C_3, C_9$  — 470- $\mu$ fd. mica.
- $C_2, C_7$  — 100- $\mu$ fd. mica.
- $C_4, C_6$  — 15- $\mu$ fd. (10 to 20) ceramic or mica.\*
- $C_5$  — 22- $\mu$ fd. (15 to 25) ceramic or mica.\*
- $C_8$  — 2.2- $\mu$ fd. ceramic or mica.
- $C_{10}, C_{12}$  — 47- $\mu$ fd. mica.
- $C_{11}$  — 100- $\mu$ fd. mica.
- $C_{13}$  — 15- $\mu$ fd. variable, National UMA-15.
- $R_1$  — 22,000 ohms,  $\frac{1}{2}$  watt.
- $R_2$  — 4700 ohms,  $\frac{1}{2}$  watt.
- $R_3$  — 0.1 megohm,  $\frac{1}{2}$  watt.
- $R_4$  — 4700 ohms,  $\frac{1}{2}$  watt.
- $R_5$  — 0.1 megohm,  $\frac{1}{2}$  watt.
- $R_6$  — 2200 ohms,  $\frac{1}{2}$  watt.

- $R_7$  — 0.25 megohm,  $\frac{1}{2}$  watt.
  - $R_8$  — 0.75 megohm,  $\frac{1}{2}$  watt.
  - $R_9$  — 4700 ohms,  $\frac{1}{2}$  watt.
  - $L_1$  — XR-50 coil form, ungrooved, 11 turns No. 22 enam., close-wound, center-tapped.
  - $L_2$  — XR-50 coil form, ungrooved, 5 turns No. 16 enam., spaced  $\frac{1}{2}$  inch dia. of wire, center-tapped.
  - $L_3$  — XR-50 coil form, ungrooved, 3 turns copper strip,  $\frac{3}{32}$  inch wide, spaced  $\frac{3}{32}$  inch, center-tapped.
  - $L_4$  — 1  $\frac{1}{2}$  turns of No. 14 copper wire,  $\frac{1}{2}$  inch in diameter.
- \*  $C_4, C_5$  and  $C_6$  should be selected in value so that plugs extend fairly well out from center of coil at resonance.

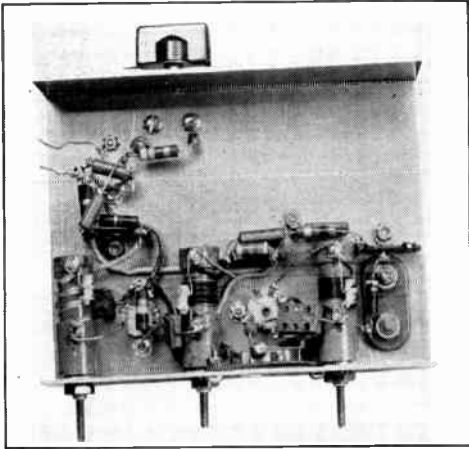


Fig. 12-15 — Bottom view of the three-tube 2-meter converter. Note the fixed-tuned tank circuits mounted along the back edge of the chassis. The two short leads at the upper left connect to the antenna terminals of a One-Ten receiver.

of several AM-FM receivers that are capable of tuning this range.

It is built on a chassis of folded aluminum  $6 \times 4\frac{1}{2} \times 1\frac{1}{2}$  inches in size. Space is left on the chassis for addition of an r.f. stage, if desired. The first half of the 6J6 is a conventional triode crystal oscillator, the second half acting as a doubler, driving a 6C4 doubler. With the values shown, the second 6J6 grid will have about 20 volts of excitation, as measured with a high-resistance voltmeter across  $R_3$ . The voltage developed across  $R_5$  will be about 25 to 30 volts. The 6C4 doubler provides about 10 volts on the mixer grid before the r.f. input circuit is connected. With the input circuit connected and adjusted to approximately the middle of the 2-meter band, the excitation voltage drops to about 1 volt, which is sufficient for good conversion with the grid-leak injection shown. A very high-resistance voltmeter should be used for these measurements. A 100-microampere meter with a 0.5-megohm resistor in series is suitable.

## One-Tube Converter for 144 Mc.

A simple converter employing a single 7F8 tube is shown in Figs. 12-16-12-19. It is designed to work into a communications receiver on either 10.7 or 27.9 Mc., the latter frequency being provided so that the converter may be used with v.h.f. superheterodynes such as the Five-Ten, NHU, S-27, S-36, and others which do not tune to the lower frequency. While it was designed for maximum simplicity, it is capable of outperforming the best superregenerative receivers in weak-signal work. If greater sensitivity is desired, one or two stages of r.f. amplification (Figs. 12-20-12-22) may be added.

From the schematic diagram, Fig. 12-18, it may be seen that one section of the 7F8 dual triode is used as a mixer and the other as a

Colpitts oscillator. Stability, an important factor in v.h.f.-converter design, is assured as the result of several precautions. The tuned circuit has a high  $C/L$  ratio, the coil is mounted rigidly on the tuning condenser, and the tube is mounted below the chassis to minimize heating effects. The Colpitts oscillator circuit permits grounding the cathode, preventing a.c. hum modulation, a common trouble when the cathode is operated above ground in v.h.f. circuits.

### Mechanical Details

No attempt was made to gang the oscillator and mixer tuning controls, as the mixer setting is sufficiently broad so that it may be peaked at 146 Mc. and left in that position for the whole


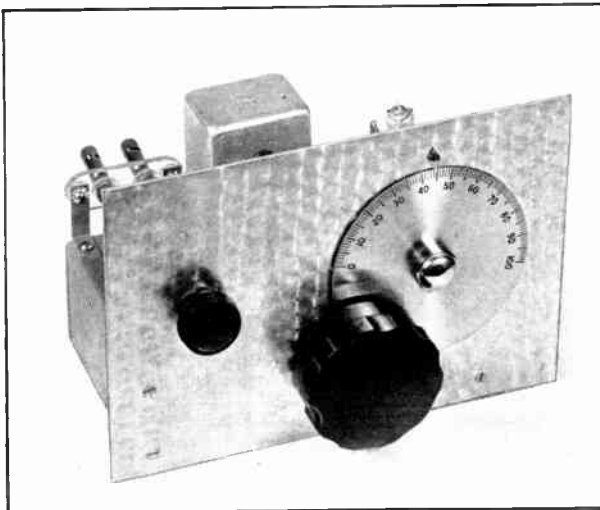


Fig. 12-16 — Front-panel view of the simple 2-meter converter.

Fig. 12-17—Top view of the simple 2-meter converter. At the right are the mixer tuned circuit and antenna coupling coil. Oscillator components are at the left. The shield at the rear of the chassis houses the output coupling transformer. The trimmer attached to the 7F8 socket terminals is the oscillator injection condenser,  $C_4$ .

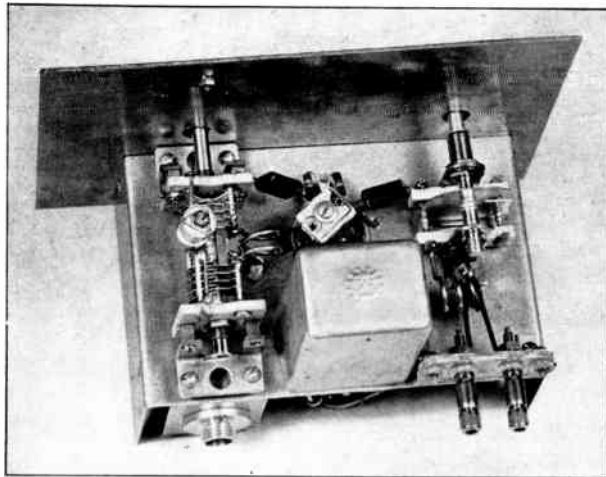

band. The oscillator tuning condenser,  $C_2$ , a split-stator variable, was made from a Millen Type 21935, originally a 35- $\mu\text{f}$ d. single-section double-spaced midget variable. A section of the stator bars  $\frac{1}{4}$  inch long is sawed out of the center of the condenser, leaving four stator and five rotor plates in each section. The three

extra rotor plates, at the center of the rotor shaft, may be removed with long-nosed pliers. The condenser is mounted with the stator bars at the top, permitting the two-turn coil to be soldered directly to the sawed ends of the bars, for solid mounting. The parallel padder,  $C_3$ , is an air trimmer of new design (Silver Type 619), or a mica trimmer may be substituted, if necessary.

The vernier dial used is a National Type K, but a large knob is substituted for the small one with which the dial is equipped, giving the converter tuning a communications-receiver quality. The appearance of the converter was further dressed up by giving the panel a "watch-case" finish. This is done with a small wad of steel wool in a drill press, or it may be done by hand with somewhat more effort.

The tube is mounted with its socket above the chassis, providing short r.f. leads. The arrangement of the smaller parts should be obvious from the photographs. Oscillator injection is controlled by the mica trimmer,  $C_4$ , which is mounted directly on the oscillator-plate and mixer-grid prongs of the tube socket. Its setting is not critical; it may be left near the minimum capacitance of the condenser.

The output coupling transformer is housed in a cut-down i.f. shield can, with the mixer plate lead coming out of a hole in the side. Winding data for both 10.7- and 27.9-Mc. transformers are given. The higher frequency is recommended for use wherever possible. The fixed padder,  $C_7$ , and the by-pass condenser,  $C_8$ , are mounted inside the i.f. shield. Converter output is taken off through a coaxial cable and fitting, though the latter may be eliminated if desired.

Ordinarily the receiver with which the converter is to be used will be capable of supplying the 6.3 volts a.e. at 0.3 amp. and 150 volts d.c. at 5 ma., but a separate supply may be used if desired. If the supply voltage is much over 150 volts, a dropping resistor should be used to bring it down to about that value.

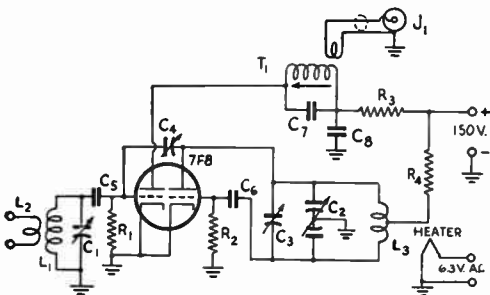


Fig. 12-18—Schematic diagram of the 7F8 converter for 144 Mc.

- $C_1$  — 10- $\mu\text{f}$ d. variable.
- $C_2$  — 15- $\mu\text{f}$ d. per section, split stator. See text.
- $C_3$  — 3-30- $\mu\text{f}$ d. air trimmer (Silver Type 619).
- $C_4$  — 3-30- $\mu\text{f}$ d. mica trimmer.
- $C_5, C_6$  — 47- $\mu\text{f}$ d. mica or ceramic.
- $C_7$  — 27- $\mu\text{f}$ d. mica or ceramic.
- $C_8$  — 470- $\mu\text{f}$ d. mica.
- $R_1$  — 1 megohm,  $\frac{1}{2}$  watt.
- $R_2, R_3$  — 10,000 ohms,  $\frac{1}{2}$  watt.
- $R_4$  — 2200 ohms,  $\frac{1}{2}$  watt.
- $L_1$  — 3 turns No. 12,  $\frac{3}{8}$ -inch i.d.,  $\frac{1}{2}$  inch long.
- $L_2$  — 2 turns "push-back,"  $\frac{3}{8}$ -inch i.d., inserted in cold end of  $L_1$ .
- $L_3$  — 2 turns No. 12,  $\frac{1}{2}$ -inch i.d., spaced  $\frac{1}{4}$  inch, center-tapped.
- $J_1$  — Coaxial jack (Jones S-201).
- $T_1$  — 29.7-Mc. i.f.: 9 turns No. 22 d.s.c. wire, spaced one diameter, on National NR-50 form (slug-tuned). Coupling winding: 2 turns No. 22 d.s.c. wire, interwound in cold end of main winding.
- 10.7-Mc. i.f.: 22 turns No. 22 enameled wire, close-wound on National NR-50 form (slug-tuned). Coupling winding: 3 turns No. 22 enameled wire wound over cold end of main winding. Insulate between two windings with poly-styrene or other insulating tape.

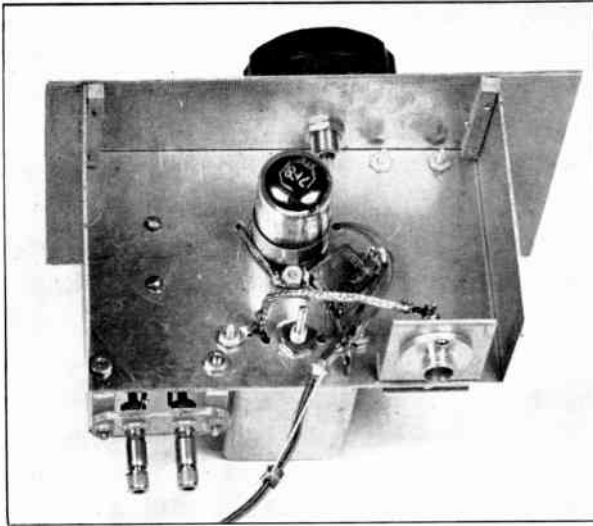


Fig. 12-19 — Bottom view of the converter shows the 7F8 tube mounted below the chassis. The i.f. core adjusting screw is in front of the tube. At the right, on a bracket, is the coaxial fitting for i.f. output.

The converter is built on a folded aluminum chassis made from a sheet  $4 \times 10$  inches in size, 2 inches being folded over on either end. The panel is  $5 \times 8$  inches. The coaxial fitting and the antenna terminals are mounted on small aluminum brackets. The panel is fastened to the chassis by means of  $\frac{1}{4}$ -inch-square rods, but small angle brackets would serve equally well.

#### Adjustments

Adjustment and testing of the converter are simple enough, if a calibrated signal generator is available. Lacking this, harmonics of a VFO, or even the radiation from a receiver oscillator, may be used. A superregenerative receiver, the tuning range of which is known, may also be used as a signal generator. First, the i.f. output transformer should be tuned to 27.9 or 10.7 Mc. by means of its adjustable core. The exact frequency employed is, of course, unimportant, as the coaxial cable between the converter and receiver will prevent

appreciable pick-up at the i.f. frequency. If any strong signals are present, the i.f. may be shifted to any clear frequency.

Next, the tuning range of the oscillator should be checked. When the converter is to be used with a 27.9-Mc. i.f., the tuning range of the oscillator will be 116.1 to 120.1 Mc. With a 10.7-Mc. i.f. it will be 133.3 to 137.3 Mc. Either of these ranges can be reached by adjustment of the parallel air trimmer,  $C_3$ . Bandspread, with the higher i.f., will be about 80 divisions. With the low i.f. it will be somewhat less. The oscillator may be checked with a calibrated absorption-type wavemeter, or by listening to it in a calibrated receiver.

A strong signal near 146 Mc. should then be tuned in, and the mixer condenser adjusted for maximum response. As the oscillator frequency varies when the mixer tuning is changed, it will be necessary to rock the oscillator dial back and forth across the signal as the mixer tuning is adjusted. Once the proper setting of  $C_1$  has been determined, it may be left set for the entire band. When a sensitive receiver is used as an i.f. system quite good sensitivity will be obtained, and a signal of one microvolt or less will produce a plainly-audible response.

#### ● A 144-MC. GROUNDED-GRID R.F. AMPLIFIER

The two-stage r.f. amplifier unit shown in Figs. 12-20 through 12-22 may be used with the simple converter described above, or with any other 2-meter receiver where an improvement in sensitivity and image rejection is desired. It employs two 6J4 triodes in a grounded-grid circuit. Other tubes might also be used, but the 6J4 was designed especially for this service and has internal shielding which reduces the likelihood of self-oscillation troubles. In the grounded-grid circuit, the signal input is to the cathode of the tube instead of the grid, which is connected directly to ground, as the name implies.

In the unit shown, the antenna is coupled to a tuned circuit in the cathode of the first tube, the plate circuit of which is also tuned. Coupling between stages is effected by a small capacity,  $C_9$ , which is tapped down on the plate coil,  $L_2$ . The cathode of the second stage is

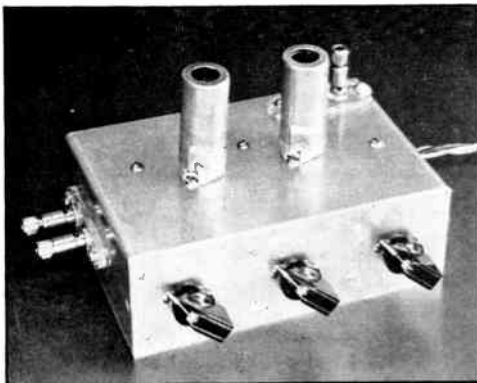


Fig. 12-20 — A two-stage grounded-grid r.f. amplifier for 144 Mc.

returned to ground through an r.f. choke and a bias resistor,  $R_3$ . Both cathodes are maintained above ground for r.f. by insertion of r.f. chokes in the heater leads. The plate circuit of the second stage is link-coupled to the mixer, the coupling line being brought out through two National FWG terminals at the back of the chassis. All three tuned circuits are provided with front-panel controls, for ease of adjustment, but only the plate tuning of the second stage will require any readjustment in tuning over the band. The other two controls may be set at 146 Mc. and no noticeable change in signal strength will be obtained if they are repeated for a signal at either end.

The r.f. amplifier is mounted on a chassis similar to that used in the simple converter. It is  $2 \times 4 \times 6$  inches in size, and was bent from a  $4 \times 10$ -inch piece of aluminum. The front panel is cut to fit, being approximately  $2 \times 6$  inches in size. Interstage shields are sheets of copper, notched to fit closely over the center of the 6J4 tube sockets, which are mounted in such a position that the cathode and plate terminals come on opposite sides of the shield. The three grid pins (1, 5, 6) are soldered directly to the shield itself, or grounded to soldering lugs under the screws with which the sockets are mounted. All leads should be as short as possible.

The amplifier unit may be operated from the same power supply as that used with the converter, but care should be taken to see that the plate voltage on the 6J4s does not exceed 150 volts. The performance of the unit does not change materially with a considerably-lower voltage, and it was found advisable to operate it from a bleeder tap ( $R_5$ ,  $R_6$ ) as shown in the schematic diagram, when the amplifier was

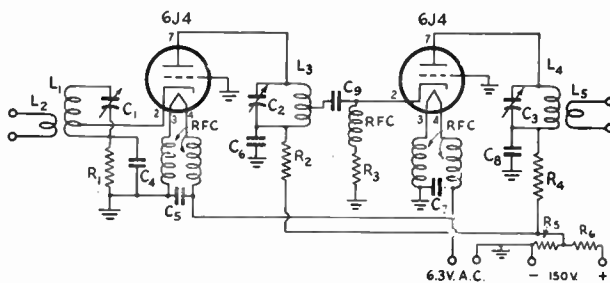



Fig. 12-21 — Schematic diagram of the 6J4 r.f. amplifier.

- $C_1$ ,  $C_2$ ,  $C_3$  — 15- $\mu$ fd. midget variable (Millen 20015).
- $C_4$ ,  $C_5$ ,  $C_6$ ,  $C_7$ ,  $C_8$  — 170- $\mu$ fd. midget mica.
- $C_9$  — 47- $\mu$ fd. mica.
- $R_1$ ,  $R_3$  — 220 ohms,  $\frac{1}{2}$  watt.
- $R_2$ ,  $R_4$  — 170 ohms,  $\frac{1}{2}$  watt.
- $R_5$ ,  $R_6$  — 10,000 ohms, 10 watts.
- $L_1$  — 1 turns No. 11,  $\frac{3}{8}$ -inch inside diameter,  $\frac{1}{2}$  inch long, tapped  $1\frac{1}{2}$  turns from cold end.
- $L_2$  — 2 turns "push-back," interwound in  $L_1$ .
- $L_3$  — 3 turns No. 11,  $\frac{3}{8}$ -inch inside diameter,  $\frac{3}{8}$  inch long, center-tapped.
- $L_4$  — Same as  $L_3$ , but without tap.
- $L_5$  — 2 turns "push-back," interwound in  $L_4$ .
- RFC — No. 22 d.s.c. wire close-wound on 1-watt carbon resistor. Winding length  $1\frac{1}{32}$  inch.

used in conjunction with the 7F8 converter and a 150-volt supply.

With the constants shown, the circuits will tune near minimum capacitance. Tuning the circuits to resonance produces a different result for each circuit. The noise output drops appreciably as the first circuit hits resonance; in the second there is only a slight noise change; while in the third the noise *increases* noticeably at resonance. Best results will be obtained if each circuit is adjusted while listening to a signal. If the receiver has an S-meter, the amplifier should be tuned for maximum reading on a medium-strength signal; if no S-meter is available, the adjustments should be made with the a.v.c. off, otherwise small changes in signal level will be difficult to detect. Once  $C_1$  and  $C_2$  have been set near the middle of the band they require no further adjustment, and  $C_3$  may be re-peaked for maximum noise as the converter is tuned across the band.

Fig. 12-22 — Bottom view of the grounded-grid r.f. amplifier. At the left are the cathode input circuit and antenna coupling. The center compartment contains the plate circuit of the first stage and cathode circuit of the second. The right-hand compartment houses the plate circuit of the second stage, and the output coupling.

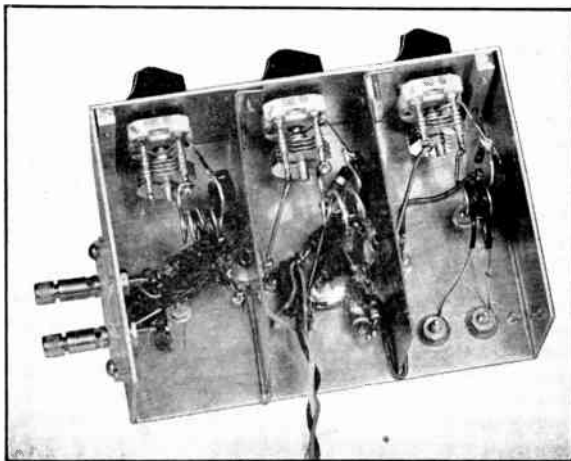

## Mobile Receiving Equipment

Probably the most satisfactory method of obtaining reception on 50 and 28 Mc., in cars equipped with broadcast receivers, is the use of a converter of simple design, working into the car receiver at 1600 kc. Some other arrangement must be made for 144 Mc. and higher, however, as the i.f. used for these frequencies must be higher than 2 Mc., to avoid image troubles. One solution, in areas where there is extensive use of crystal-controlled transmitters, would be a converter having an i.f. of about 30 Mc., working into a second mixer-oscillator whose output would be 1600 kc., for working into the car broadcast receiver.

Most mobile reception on frequencies from 144 Mc. up has been done with simple superregenerative units, or, in a few cases, complete receivers designed especially for 144-Mc. work. With either of these approaches it is difficult to achieve satisfactory performance on all three of the popular mobile bands, 2, 6 and 10 meters. One way of attaining this end involves the use of a superheterodyne converter (or converters) and a high-frequency i.f. (in the vicinity of 10-20 Mc.) working into a superregenerative second detector. This is particularly useful for installations where no broadcast receiver is available.

### ● A SUPERREGENERATIVE I.F. AND AUDIO UNIT

The high sensitivity, noise rejection, and a.v.c. characteristics of the superregenerative detector make it useful in mobile operation. The chief difficulties inherent in this type of receiver, broadness of tuning and radiation of an interfering signal, can be overcome at least partially through the use of a superregenerative stage as the second detector in a superheterodyne receiver. The i.f. amplifier and audio unit shown in Figs. 12-23-12-26 was designed especially for mobile operation. Two converters, shown in Figs. 12-23 and 12-27-12-31, working with this unit, provide mobile reception on 2,

6, 10 and 11 meters. The space available in a particular make of car will influence the form factor of the units, but these are representative designs. The two converters, one for 6-11 meters and one for 2 meters, are intended for steering-post mounting, while the i.f.-audio unit is shaped to fit into either a glove or radio compartment.

Little need be said about the i.f. unit, as there are few critical factors, and mechanical layout is relatively unimportant. Only four tubes are used: a 6AG5 11-Mc. i.f. amplifier, a 6C4 superregenerative second detector, a 6C4 first audio amplifier, and a 6AK6 second audio. Note that both audio stages are transformer-coupled, this method having been used in preference to resistance coupling, as experience has shown that the former makes for smooth, quiet operation when superregenerative detectors are employed.

The input stage of the unit should be well shielded, not only to prevent oscillation, but to reduce pick-up on 11 Mc. When the unit is installed in a car this is not troublesome, but in home-station work, 11-Mc. interference can become quite severe, especially during evening hours.

The tuned circuits used in the 11-Mc. amplifier, the superregenerative detector, and as output coupling units in the two converters, are all similar. The coils are wound of No. 22 enameled wire on National XR-50 core-tuned forms, the secondary winding occupying the entire winding space. A simple way of securing the primary is to wrap a layer of Scotch Tape, sticky side *out*, around the ground end of the secondary. The primary winding will then stick as it is wound on, and holding it in place will be no problem. A small tab of tape, or household cement, will suffice.

### ● A CONVERTER FOR 50 AND 28 MC.

The three tube converter shown in Figs. 12-23, 12-27 and 12-28 covers the 50-54 Mc.

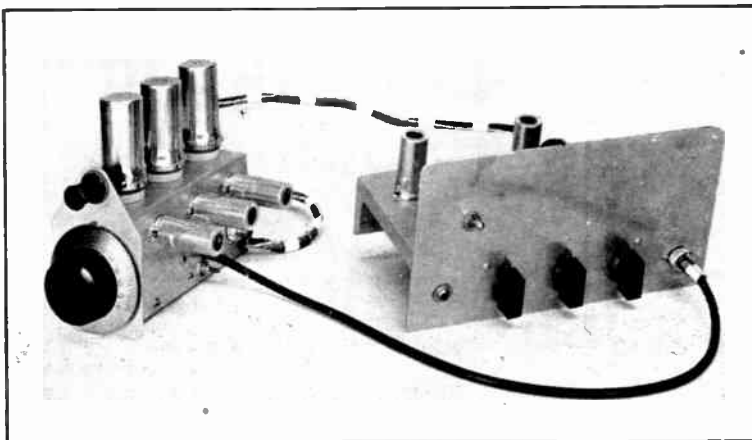


Fig. 12-23 — The three-tube converter for 6 and 10 meters connected to the 11-Mc. i.f. amplifier and audio system. The converter is mounted on the steering post, while the i.f. unit is designed for glove-compartment mounting. The object above the converter dial is an adjustable-beam dial light.



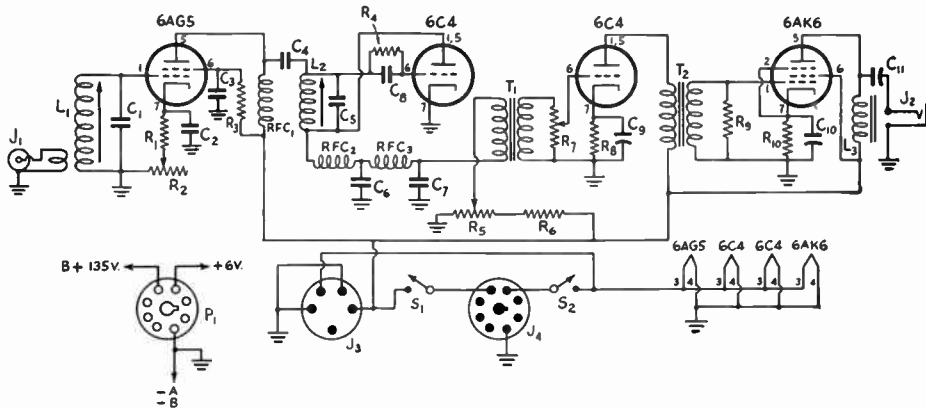


Fig. 12-24 — Wiring diagram of the i.f. unit using a superregenerative second detector and two audio stages.


- C<sub>1</sub>, C<sub>5</sub> — 47- $\mu$ fd. ceramic.
  - C<sub>2</sub>, C<sub>3</sub> — 170- $\mu$ fd. midget mica.
  - C<sub>4</sub>, C<sub>8</sub> — 100- $\mu$ fd. midget mica.
  - C<sub>6</sub>, C<sub>7</sub> — 0.0068- $\mu$ fd. mica.
  - C<sub>9</sub>, C<sub>10</sub> — 25- $\mu$ fd. 50-volt electrolytic.
  - C<sub>11</sub> — 0.1- $\mu$ fd. 600-volt tubular.
  - R<sub>1</sub> — 270 ohms, carbon.
  - R<sub>2</sub> — 10,000-ohm potentiometer.
  - R<sub>3</sub> — 1000 ohms.
  - R<sub>4</sub> — 1.7 megohms.
  - R<sub>5</sub> — 50,000-ohm potentiometer.
  - R<sub>6</sub> — 47,000 ohms, 1 watt.
  - R<sub>7</sub> — 0.25-megohm potentiometer.
  - R<sub>8</sub> — 2200 ohms.
  - R<sub>9</sub> — 0.22 megohm.
  - R<sub>10</sub> — 680 ohms.
- All resistors  $\frac{1}{2}$ -watt type unless otherwise indicated.  
 L<sub>1</sub>, L<sub>2</sub> — 22 turns No. 22 enam., close-wound on Na-
- tional XR-50 form. Primary: 3 turns No. 22 enam. close-wound on layer Scotch Tape over ground end of L<sub>1</sub>.
  - L<sub>3</sub> — Midget filter or audio choke.
  - J<sub>1</sub> — Coaxial socket (Jones S-201).
  - J<sub>2</sub> — Speaker or headphone jack.
  - J<sub>3</sub> — 5-prong plug for converter power, mounted on back of chassis.
  - J<sub>4</sub> — Octal plug, mounted on back of chassis.
  - P<sub>1</sub> — Octal socket on power cable.
  - RFC<sub>1</sub> — 2.5-mh. r.f. choke (National R-100).
  - RFC<sub>2</sub> — One "pie" from National R-100, mounted on 1-watt resistor.
  - RFC<sub>3</sub> — 80-mh. r.f. choke.
  - S<sub>1</sub> — S.p.s.t. toggle switch, bat-handle type.
  - S<sub>2</sub> — S.p.s.t. switch, mounted on R<sub>7</sub>.
  - T<sub>1</sub>, T<sub>2</sub> — Midget interstage audio transformers.


and 27-30 Mc. ranges by means of plug-in coils. Using the 11-Mc. intermediate frequency, it is possible to cover the two bands with a common oscillator coil, the oscillator running on the low side of the signal frequency for 50-54 Mc. and on the high side for 27-30 Mc. It is thus merely necessary to change the mixer and r.f. coils when changing bands. Three tubes are used: a 6AK5 r.f. amplifier, a 6AK5 mixer, and a 6C4 oscillator.

The converter layout, shown in Fig. 12-27, makes some sacrifices in accessibility for the sake of compactness; however, by planning the construction carefully, the builder should have no trouble in assembling or adjusting the converter. Parts are mounted on an "L"-shaped aluminum chassis, with a cover of the same general shape, making a case that is 2 inches wide, 3 inches high, and 6 $\frac{1}{2}$  inches long.

Octal sockets for the plug-in coils (Millen

Fig. 12-25 — Rear view of the 11-Mc.-i.f./audio unit. The tubes nearest the panel are the i.f. amplifier, left, and the superregenerative detector. The octal plug on the back of the chassis is for the power cable, while the 5-prong plug connects through another cable to the converter. The toggle switch is the B+ stand-by switch.

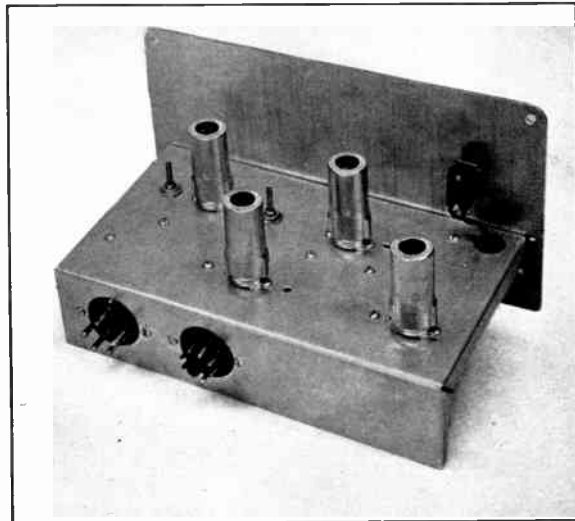

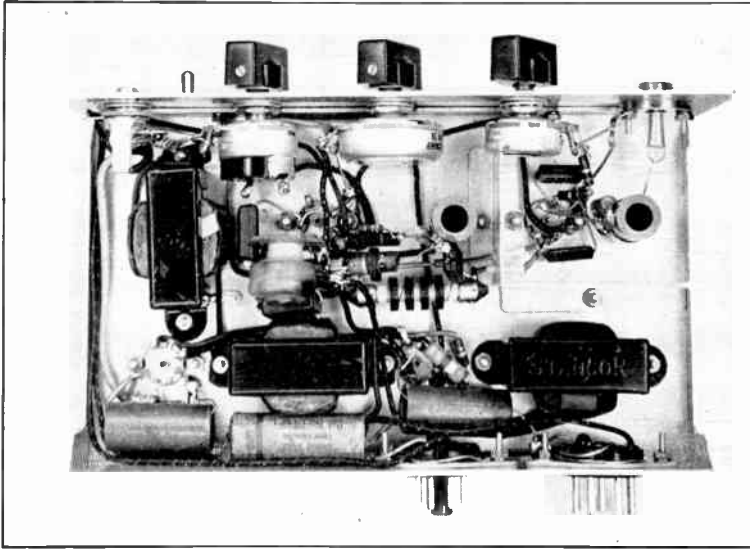


◆  
 Fig. 12-26 — Bottom view of the i.f.-audio unit, showing arrangement of parts. At the upper right, in a partially-shielded compartment, are the parts comprising the i.f.-amplifier input circuit. In the center are the detector socket and associated parts. At the left and rear are the audio components.  
 ◆

74001 shielded core-tuned forms) are mounted along the top edge, with the corresponding tube sockets projecting from the right side. The oscillator compartment is at the front, nearest the dial — a “must” when flexible couplings are used for ganging. The middle compartment houses the mixer-stage components, including the core-tuned i.f. output coupling transformer. Coupling between the oscillator and mixer is obtained by means of a piece of “push-back” wire which is soldered to the oscillator tuned circuit and then wrapped around the r.f.-plate or mixer-grid lead. The coupling should be set at the lowest value that will provide maximum signal strength. At the back is the r.f. section, which is pro-

vided with a coaxial input jack for antenna connection.

As this converter may be used with conventional i.f. systems, provision was made for incorporating a.v.c. Instead of grounding the grid returns from the r.f. and mixer tubes, these returns are brought out, through resistors  $R_1$  and  $R_5$ , to a separate pin on the power-cable socket. The corresponding pin in the i.f. unit is connected to ground.

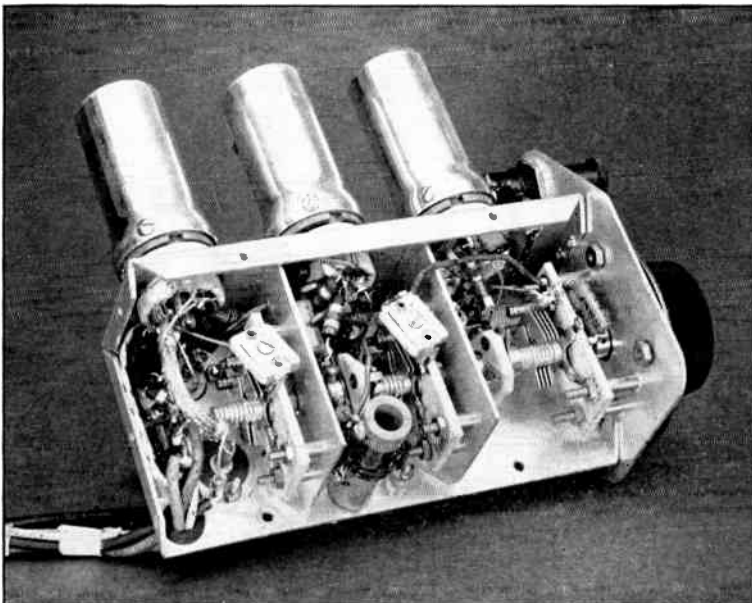The oscillator circuit is high  $C$ , for maximum stability, the capacitance other than that of the variable condenser being supplied by a ceramic padder, consisting of 20- $\mu\text{fd.}$  and 27- $\mu\text{fd.}$  units in parallel with the tuning condenser. Adjustable padders are used in the



◆  
 Fig. 12-27 — Interior view of the 28- and 50-Mc. converter, with cover removed. The mica trimmers are adjusted through small holes in the chassis cover. The oscillator compartment is at the front (right), the mixer in the middle, and the r.f. amplifier at the left.  
 ◆

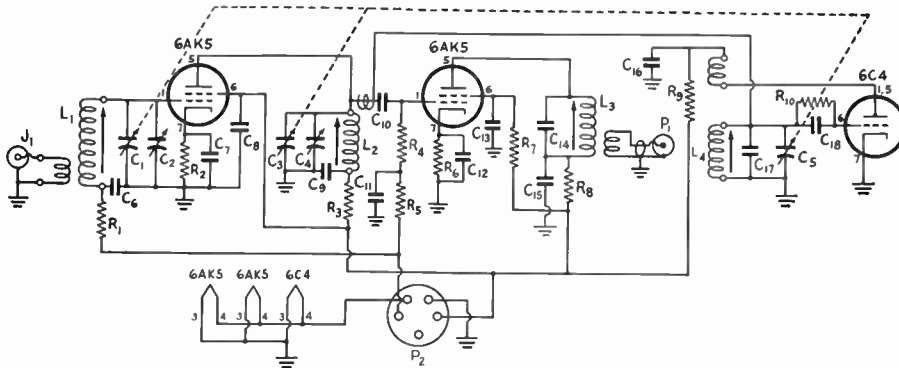


Fig. 12-28 — Schematic diagram of the mobile converter for 27 to 54 Mc.

- C<sub>1</sub>, C<sub>3</sub> — R.f. and mixer tuning condensers (National UM-15 reduced to 2 stator and 2 rotor plates).
  - C<sub>2</sub>, C<sub>4</sub> — 3-30- $\mu$ fd, mica trimmer.
  - C<sub>5</sub> — Oscillator tuning condenser (National UM-35 reduced to 1 stator and 1 rotor plates).
  - C<sub>6</sub>, C<sub>7</sub>, C<sub>8</sub>, C<sub>9</sub>, C<sub>11</sub>, C<sub>12</sub>, C<sub>13</sub>, C<sub>15</sub>, C<sub>16</sub> — 470- $\mu$ fd. midget mica.
  - C<sub>10</sub>, C<sub>18</sub> — 100- $\mu$ fd, mica.
  - C<sub>14</sub> — 17- $\mu$ fd, ceramic.
  - C<sub>17</sub> — 17- $\mu$ fd, ceramic (20 and 27  $\mu$ fd. in parallel).
  - R<sub>1</sub>, R<sub>5</sub> — 0.22 megohm.
  - R<sub>2</sub>, R<sub>3</sub>, R<sub>8</sub>, R<sub>9</sub> — 270 ohms, carbon.
  - R<sub>4</sub>, R<sub>7</sub> — 1.0 megohm.
  - R<sub>6</sub> — 6800 ohms.
  - R<sub>10</sub> — 47,000 ohms.
- (All resistors  $\frac{1}{2}$ -watt rating.)

- L<sub>1</sub> — R.f. coil, 28 Mc.: 10 turns No. 22 enam.,  $\frac{3}{4}$  inch long. Primary: 2 turns No. 28 d.s.c. interwound in cold end of L<sub>1</sub>. 50 Mc.: 5 turns No. 22 enam.,  $\frac{3}{8}$  inch long. Primary similar to 28-Mc. coil.
- L<sub>2</sub> — Mixer coil, 28 Mc.: 9 turns No. 22 e.,  $\frac{3}{4}$  inch long. 50 Mc.: 4 turns No. 22 e.,  $\frac{3}{8}$  inch long.
- L<sub>3</sub> — I.f. output transformer, 22 turns No. 22 enam., close-wound on National NR-50 form. Coupling winding: 2 turns No. 20 "push-back," wound at cold end of L<sub>3</sub>.
- L<sub>4</sub> — Oscillator coil, 21.4 turns No. 22 enam.,  $\frac{9}{16}$  inch long. Feed-back winding: 2 turns No. 28 d.s.c. interwound between turns of L<sub>4</sub>.
- J<sub>1</sub> — Coaxial socket (Jones S-201).
- P<sub>1</sub> — Coaxial plug (Jones P-201).
- P<sub>2</sub> — 5-prong socket on power cable.

mixer and r.f. circuits to facilitate tracking. These are mica trimmers, but the coil inductance is adjusted so that the trimmers tune nearly wide open, and small changes in plate spacing have a negligible effect on the capacitance. Tracking is made easy by the adjustable-inductance feature of the coil forms.

In putting the converter into operation it is best to start by establishing the tuning range of the oscillator, which may be checked with an absorption wavemeter or monitored by a receiver that is capable of tuning from 37 to 43 Mc. It is useful to have the receiver capable of tuning in the high end of the old FM band, so the oscillator may be made to hit 37 Mc. or so at the low-frequency end of its range. If the inductance of the coil is properly adjusted, 43 Mc. (oscillator frequency) will come at the high end. This gives a spread of about 70 divisions for the 50-Mc. band, and about 50 divisions for 27 to 30 Mc. If more spread is desired for the 10-meter band, a separate oscillator coil for that band may be made, and additional padder capacitance built into the r.f. and mixer coils for 10 meters.

Once the oscillator is tuning the desired range, the mixer should be put into operation. For test purposes, a temporary primary may be wound on the mixer coil, using two of the spare pins on the coil and socket for bringing out the leads thereto. From here on, a signal generator which tunes the desired frequency ranges is useful, but it is not absolutely necessary. A signal from a VFO, or the harmonics of several crystals, can be made to serve the same purpose. The signal from the oscillator in a communications receiver can be used also.

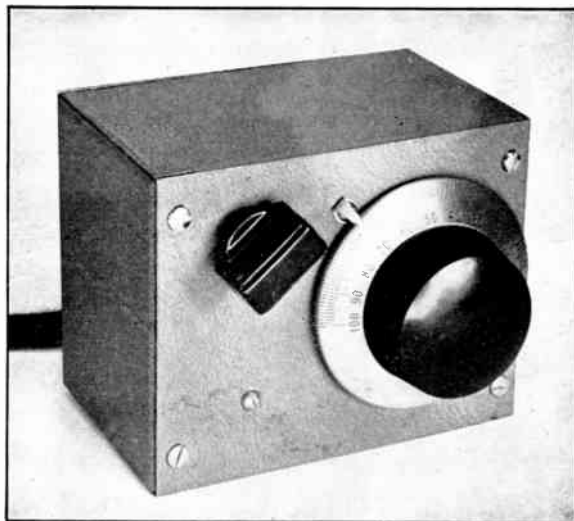


Fig. 12-29 — Front view of the 114-Mc. converter. The entire unit is contained in a standard 3 x 4 x 5-inch case.

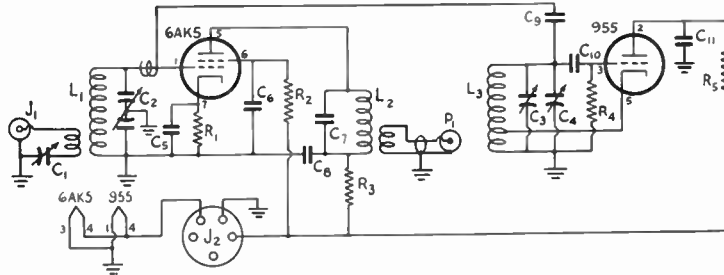


Fig. 12-30 — Schematic diagram of the 144-Mc. converter with 11-Mc. output.

- C<sub>1</sub> — 3–30- $\mu$ fd. mica trimmer.  
 C<sub>2</sub> — Cardwell "butterfly" condenser, 1 rotor plate with 1 stator plate on each side. See text.  
 C<sub>3</sub> — 25- $\mu$ fd. trimmer with screwdriver adjustment (Millen 26025).  
 C<sub>4</sub> — Oscillator tuning condenser (Millen 20015 reduced to 1 stator and 1 rotor plate).  
 C<sub>5</sub>, C<sub>6</sub>, C<sub>8</sub>, C<sub>11</sub> — 470- $\mu$ fd. mica midget.  
 C<sub>7</sub> — 47- $\mu$ fd. ceramic.  
 C<sub>9</sub> — 4.7- $\mu$ fd. ceramic.  
 C<sub>10</sub> — 100- $\mu$ fd. mica midget.  
 R<sub>1</sub> — 10,000 ohms.  
 R<sub>2</sub> — 1.0 megohm.  
 R<sub>3</sub> — 270 ohms.

R<sub>4</sub> — 22,000 ohms.

R<sub>5</sub> — 10,000 ohms.

All resistors  $\frac{1}{2}$ -watt carbon.

L<sub>1</sub> — 3 turns No. 12 tinned,  $\frac{3}{8}$  inch long,  $\frac{3}{8}$ -inch inside diameter. Primary: 2 turns No. 20 "push-back" interwound at cold end of L<sub>1</sub>.

L<sub>2</sub> — 22 turns No. 22 enam., close-wound on National XR-50 form. Coupling winding: 3 turns No. 22 enam. wound on layer of Scotch Tape over cold end of L<sub>2</sub>.

L<sub>3</sub> — 3 turns No. 12 tinned,  $\frac{1}{2}$  inch long,  $\frac{1}{4}$ -inch inside diameter, tapped 1 turn from cold end.

J<sub>1</sub> — Coaxial socket (Jones S-201).

J<sub>2</sub> — 5-prong socket on power cable.

P<sub>1</sub> — Coaxial plug (Jones P-201).

The signal source should be fed into the converter by direct connection to the temporary primary or by means of a pick-up antenna, and the output of the converter fed into a communications receiver tuned to 11 Mc. If the converter is working there will be an appreciable increase in receiver noise as the plate voltage is applied to the mixer, and this will increase as the mixer grid and plate circuits are resonated.

Tracking is accomplished in the usual way, except that no squeezing of turns is required for inductance adjustment. With a signal near the high end of the band, adjust the trimmer, C<sub>4</sub>, for maximum signal or noise. Tune to near the low end, and recheck the setting of C<sub>4</sub>. If the trimmer capacitance has to be increased, the coil inductance is low; if the capacitance has to be decreased the inductance is too high.

Adjust the inductance by moving the core (moving the core inward increases the inductance) and repeat the trimmer-setting process until the band can be tuned without any re-adjustment of C<sub>4</sub>. When the mixer is functioning properly the same procedure should be followed with the r.f. coil. It is well to note the performance of the mixer alone, as this will serve to determine whether the r.f. stage is performing as it should. There should be a noticeable increase in sensitivity when the r.f. stage is added, but if the mixer is functioning correctly it should be possible to get quite good performance with the mixer alone.

It is well to make all converter adjustments with a communications receiver serving as the i.f., as it is difficult to observe minor changes when the superregenerative detector is used, because of its strong a.v.c. characteristics.

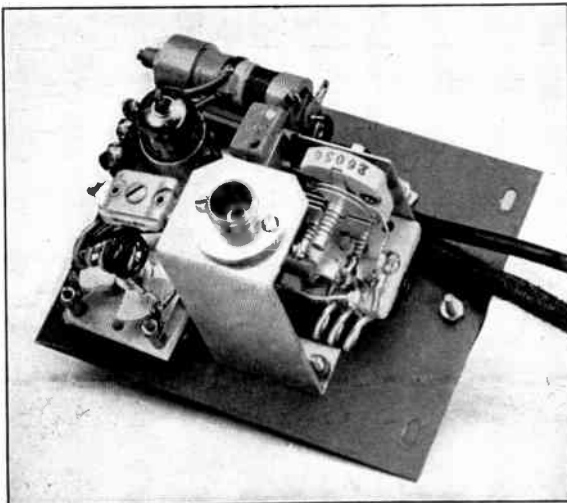


Fig. 12-31 — Back view of the 2-meter converter. Two similar condensers mounted at right angles comprise the tuning assembly for the oscillator stage.

The i.f. system should be peaked at 11 Mc. with a signal generator, and then the converter connected to it for an over-all check. The performance using the superregenerative i.f. unit will be somewhat lower than that of the converter-receiver combination, but ordinarily it should be possible to copy any signal on the mobile set-up that is solidly readable when the communications receiver is used for an i.f. system.

### ● A MOBILE CONVERTER FOR 144 MC.

The circuit of the two-tube 144-Mc. converter, shown in Figs. 12-29-12-31, is similar to the lower-frequency unit, except that the r.f. stage is omitted for the sake of simplicity. Even without the r.f. stage, performance well above that of the better superregenerative receivers is obtainable. The 2-meter converter uses a 6AK5 mixer and a 955 oscillator. Because the mixer tuning is fairly broad, no attempt was made to gang the tuned circuits, and only the oscillator is tuned by the vernier dial. The mixer tuning condenser is provided with a front-panel knob, but once set for maximum signal at 146 Mc., it can be left in the same position for both ends of the band with a negligible sacrifice in sensitivity.

From the schematic diagram, Fig. 12-30, it may be seen that the circuits of the converters are somewhat similar except for the elimination of the r.f. stage and the use of a cathode-tapped coil in the oscillator circuit of the 2-meter unit. The converter was originally laid out using a 6J6 push-push mixer, but because of the difficulty of obtaining satisfactory performance with this arrangement, it was changed to the 6AK5. The "butterfly" tuning condenser used is a hangover from the 6J6 set-up — an ordinary Trim-Aire, with its stator sawed in half, would do.

All the parts are mounted on the front panel, so that the complete unit can be removed from the case intact. Sections of the folded-over edge of the case were sawed out at several points to provide space for easy removal. The oscillator and mixer assemblies are mounted on individual subpanels of folded aluminum, and most of the wiring can be done before these assemblies are fastened to the front panel. The coaxial socket for the antenna connection is mounted on a separate aluminum bracket, and projects through a hole located in the back of the case.

Injection of oscillator voltage is accomplished in a manner similar to that used in the other converter, except that a smaller capacitor must be used, otherwise the oscillator will "pull out" when the mixer circuit is tuned to resonance. A 4.7- $\mu$ fd. ceramic condenser is connected to the hot end of the oscillator tuned circuit, and the coupling lead is run from this condenser to the mixer grid lead. By bringing the two tuned circuits closer together, it would be

unnecessary to provide any coupling other than that between the two coils.

The oscillator tuning condensers,  $C_3$  and  $C_4$ , are similar mechanically, except that one has a shaft to which is affixed the vernier dial, and the other a screwdriver adjustment. It is important that two similar condensers be used in this arrangement, where the two are mounted at right angles, in order that the stators and rotors line up for direct connection without leads. With the condensers and coil used here, the 144-Mc. band covers about 50 divisions on the dial, permitting coverage up to 150 Mc. This is useful, as commercial signals are available in this range in many locations, and they are quite helpful in making necessary receiver adjustments and in judging the condition of the band.

To do a completely-effective job of mobile operation requires considerable attention to noise reduction. With this sort of receiver, the worst interference comes, not from the car's ignition system, but from the generator. The superregenerative detector provides effective silencing for noise pulses of short duration, such as ignition interference, but its inherent a.v.c. characteristics make it respond to a continuous noise such as the whine of the generator, to the exclusion of any weaker signal. It is for this reason that the use of "B" batteries for receiver plate supply is recommended. There is almost certain to be enough noise from any vibrator or generator plate supply to effect at least a slight reduction in the over-all sensitivity of a receiver of this type.

#### *Modes of Operation*

Several types of reception are possible through variation in the setting of the regeneration control. With the plate voltage on the detector near maximum, the loudest "shush" and widest bandwidth are obtained. This is the setting normally used for 144-Mc. reception of nonstabilized signals. Backing off the regeneration control reduces the hiss level and sharpens the response, and best all-around reception on 28 or 50 Mc. is usually obtained in this position. Further reduction of the plate voltage results in a whistle being heard as carriers are tuned in, and quite satisfactory c.w. reception is possible at this setting. From here down, the detector is operating in a condition in between superregeneration and straight regeneration for a considerable variation in the plate voltage. It goes into straight oscillation and then out of oscillation entirely as the voltage is reduced nearly to zero. Reception of modulated signals is possible when the detector is operated in a manner similar to that used with regenerative detectors, and "hissless" reception is possible at this point. Sensitivity is considerably lower, however, giving striking proof of the value of superregeneration as a means of attaining high performance with a few tubes.

## A Mobile Converter for the Car Receiver

The converter shown in Figs. 12-32-12-36 is designed for use with a mobile broadcast receiver. Two sets of plug-in coils cover 6, 10 and 11 meters, the set not in use being plugged into a pair of dummy sockets in the base of the converter. Power for the unit is obtained from the car-receiver power supply, and a switching arrangement allows a standard car antenna to be used for either broadcast or amateur reception. The performance of the converter may be somewhat below that of more advanced types employing r.f. stages, but it is adequate for mobile operation, where high noise level and the low power of the transmitter are limiting factors.

### Circuit Details

As may be seen from the diagram, Fig. 12-36, the converter uses a single 6BE6 pentagrid converter tube, employing electronic injection. A Colpitts oscillator is used, permitting the rotor of the tuning condenser to be grounded and doing away with the need for a cathode tap or tickler coil. The mixer section also uses a grounded-rotor condenser. The output transformer,  $C_5$ ,  $L_4$  and  $L_5$ , is made as a plug-in unit. Switch sections  $S_{1A}$  and  $S_{1B}$  transfer the antenna from the receiver input circuit to the converter, and, at the same time, connect the transformer output winding,  $L_5$ , to the receiver input. Toggle switches  $S_2$  and

$S_3$  are used for heater and stand-by purposes. A VR-105 regulates the oscillator plate voltage, preventing oscillator frequency fluctuation which would otherwise result from the voltage variation usually encountered in mobile equipment.

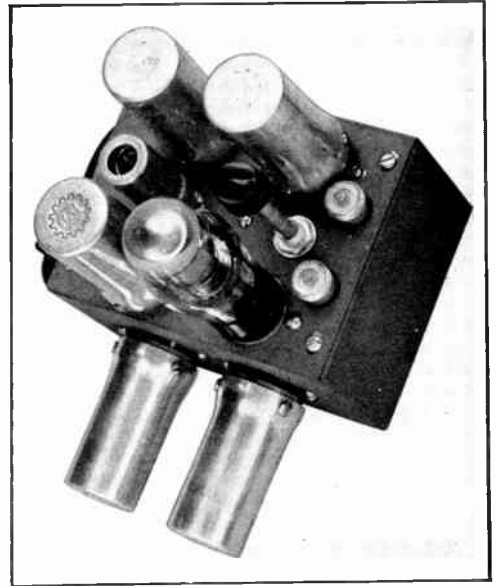


Fig. 12-33 — A side view of the mobile converter. The long shaft on the antenna change-over switch allows the switch to be operated without reaching down in among the other components.

### Physical Layout

A side view of the converter, Fig. 12-33, shows most of the components mounted on one of the detachable plates of a  $3 \times 4 \times 5$ -inch utility box. From top to bottom on the left side of the cover plate are the oscillator coil, the 6BE6 tube, and the mixer coil. The output transformer, the antenna switch, and the regulator tube are next in line, with the output jack,  $J_2$ , just to the right of the output transformer, and the input jack,  $J_1$ , directly below  $J_2$ .

The inside view of the unit, Fig. 12-35, shows the parts closely grouped around the tuning condenser,  $C_{1A}$ ,  $C_{1B}$ , the mounting of which requires care in order that the control shaft can be made to line up with the vernier dial which is mounted on the small surface of the case. It is suggested that the layout drawing, Fig. 12-34, be followed as closely as possible. The condenser, mounted after other components have been fastened in place, is equipped with the brackets that are supplied with the Trim-Aire type of condenser. These brackets are attached to the outer surfaces of the ceramic end plates, with the mounting lips

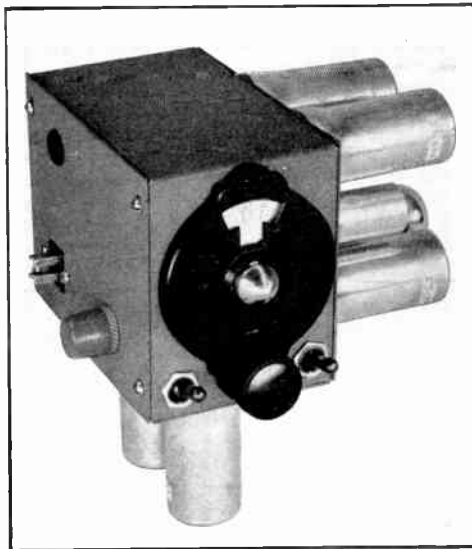


Fig. 12-32 — Front view of the mobile converter. The heater- and plate-voltage switches are to the left and right of the vernier-dial control knob. The pilot light and input connector are at the left side of the case. A hole for screwdriver adjustment of the output transformer is located above the input plug. Tube sockets, mounted in the bottom of the case, are used as holders for the extra set of coils.

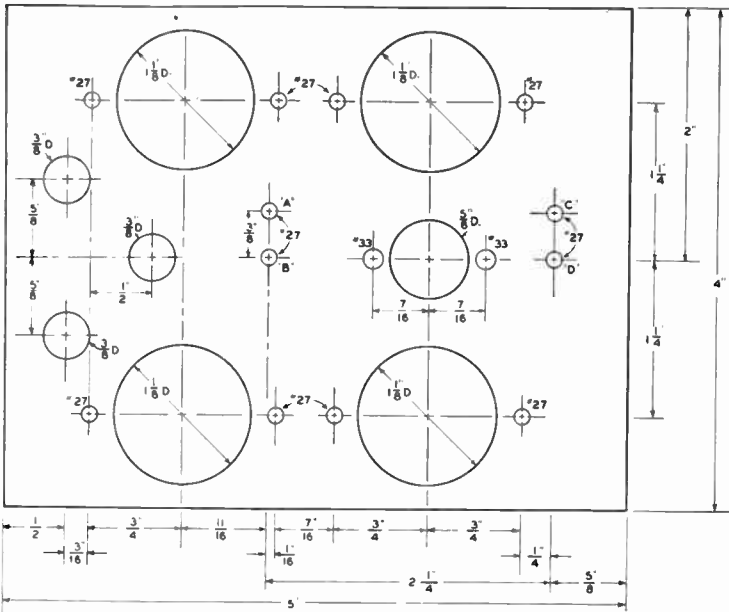


Fig. 12-34 — A mechanical drawing of the subchassis layout.

facing toward the back of the condenser. Between the brackets and the panel are metal pillars  $1\frac{1}{16}$  inch long. The position of the condenser is such that the stator terminals are just above the tube- and coil-socket prongs.

It should be possible to follow the layout shown, as there is no excessive crowding of parts. Looking at Fig. 12-35, the oscillator components are at the left of the tuning condenser, with the mixer parts at the right. The output transformer is at the lower left and the regulator tube socket at the right, with the antenna switch in between. The band-set condensers are soldered directly to the coil-socket prongs. All four sockets have extra prongs, which may be used as tie-points for other components.


The main part of the utility box needs some modification before the dial, switches and spare-coil sockets are mounted. It is necessary to fold back the two  $\frac{1}{2}$ -inch flanges which are at the top and bottom edges of the right side of the case, and the flange at the rear must be filed out in two places to provide clearance for jacks  $J_1$  and  $J_2$ .

Details of the coils are given in Fig.



Fig. 12-35 — Inside view of the 6-, 10- and 11-meter mobile converter. Practically all of the construction and wiring can be completed before the subchassis is attached to the case.

12-36. The oscillator and mixer coils employ Millen No. 74002 shielded plug-in forms, and the output transformer uses the No. 74001 permeability-tuned form of similar construction. These were selected because of the protection their design affords against the rough handling to which such equipment is subjected. The output transformer is designed to resonate near 1500 kc., and is core-adjusted to this frequency.

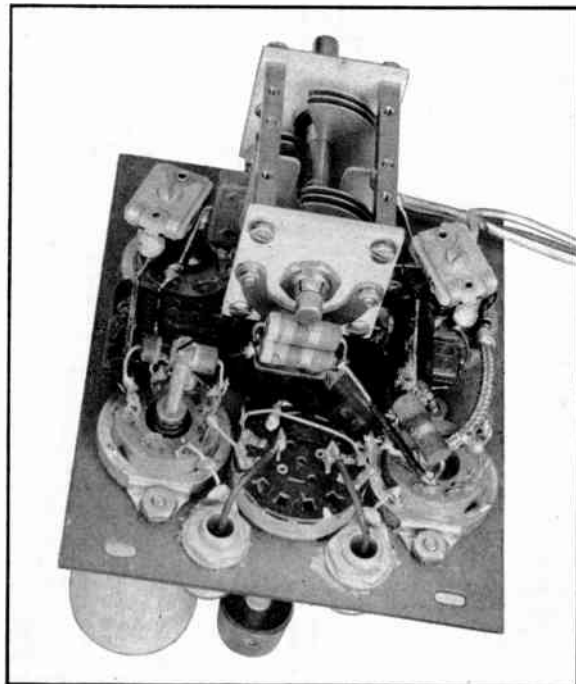

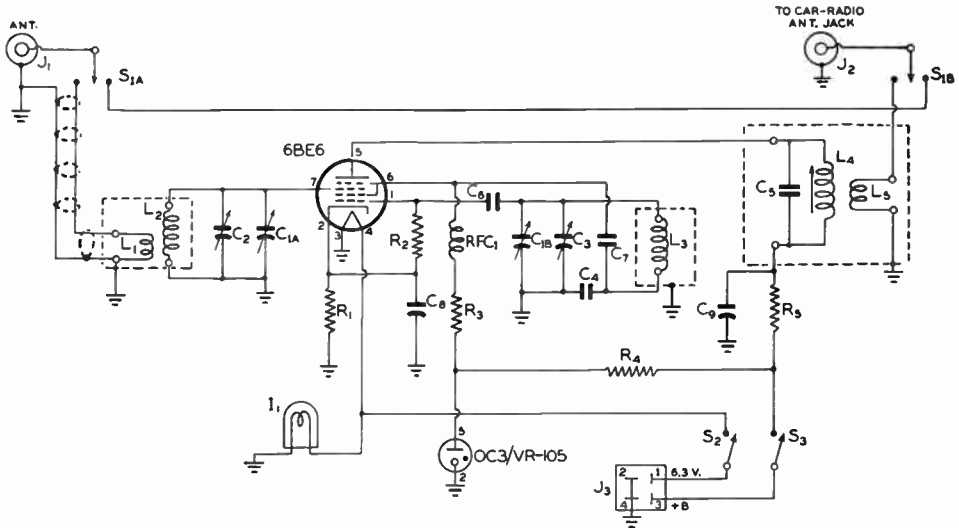


Fig. 12-36 — Wiring diagram of the mobile converter for 6, 10 and 11 meters.

- C<sub>1A</sub>, C<sub>1B</sub> — Split-stator condenser, 15  $\mu$ fd. per section (Cardwell ER-15-AD).
- C<sub>2</sub>, C<sub>3</sub> — 3-30- $\mu$ fd. ceramic trimmer.
- C<sub>4</sub>, C<sub>5</sub> — 100- $\mu$ fd. midget mica.
- C<sub>6</sub>, C<sub>7</sub> — 0.0022- $\mu$ fd. mica.
- C<sub>8</sub>, C<sub>9</sub> — 0.01- $\mu$ fd. paper tubular.
- R<sub>1</sub> — 150 ohms, 1/2 watt.
- R<sub>2</sub> — 22,000 ohms, 1/2 watt.
- R<sub>3</sub> — 680 ohms, 1 watt.
- R<sub>4</sub> — 2200 ohms, 2 watts.
- R<sub>5</sub> — 1000 ohms, 1 watt.
- I<sub>1</sub> — 6.3-volt pilot lamp.
- J<sub>1</sub>, J<sub>2</sub> — Coaxial-cable jack.
- J<sub>3</sub> — 4-prong male plug.
- S<sub>1A</sub>, S<sub>1B</sub> — 2-pole 2-circuit selector switch.
- S<sub>2</sub>, S<sub>3</sub> — S.p.s.t. toggle switches.
- L<sub>1</sub> — 50 Mc.; 2 1/2 turns No. 18 d.c.c. wire, interwound in cold end of L<sub>2</sub>.
- 28 Mc.; 3 1/4 turns No. 18 d.c.c. wire at cold end of L<sub>2</sub>.
- L<sub>2</sub>, L<sub>3</sub> — 50 Mc.; 4 1/2 turns No. 18 enameled wire, spaced one diameter.
- 28 Mc.; 11 1/2 turns No. 18 enameled wire, 3/8 inch long.
- L<sub>4</sub> — No. 36 d.s.c. wire, close-wound, one inch long.
- L<sub>5</sub> — 15 turns No. 36 d.s.c. wire, close-wound over B-plus end of L<sub>4</sub>. Note that condenser C<sub>5</sub> is mounted inside the coil shield.

**Alignment and Installation**

The converter may be lined up using an a.c. power supply and a communications receiver. A good signal generator simplifies this task, but if none is available the job may be done as follows: Turn on the receiver, set the volume control at maximum, and with the receiver dial at 1500 kc. adjust the output transformer on the converter for greatest noise. With the 10-meter coils in place and the tuning condenser set at about half capacitance, set the oscillator trimmer near maximum capacitance. With the aid of a signal, which may be noise from ignition or an electric razor, adjust the mixer trimmer for maximum response. Final adjustments can be made using amateur signals, resetting the oscillator trimmer as may be required to bring the band at the desired dial settings. The procedure outlined should be followed for the 6-meter range as well. Bandspread will be approximately 60 divisions for the 50-Mc. band and 85 for 27-29.7 Mc.

The exact anode voltage for the 6BE6 will not be known until the converter is actually tested in the car installation. The tube is designed to operate with 250 volts on the output plate and 100 volts on the oscillator plate. With a 150-ohm cathode resistor the cathode current is approximately 10 ma. It is important that the regulator tube be allowed to

function normally at all times, and in cases where the receiver voltage is abnormally low it may be necessary to change the value of the limiting resistor, R<sub>4</sub>. The proper value will permit the tube to regulate (as indicated by a constant glow) over the complete voltage range, as the input voltage varies with the condition of the car battery and the charging rate of the car generator.

In modifying the car receiver it is necessary to remove it from its case and install a power plug for carrying the heater and plate voltages and the ground lead to the converter. The heater lead should be connected directly to one of the receiver tube sockets, to take advantage of any 6-volt line filtering which may be incorporated in the receiver. Similarly, it is wise to tap for plate power at a point where the r.f. circuits are most heavily decoupled. This may result in a somewhat lower plate voltage than the maximum obtainable, but the extra filtering aids in eliminating hum and vibrator hash.

Antenna and power cables should be made up at this time. One coaxial cable must reach from the car antenna to the converter and the second from the converter to the receiver antenna connection. The 3-wire shielded power cable will connect between the receiver output plug and the 4-prong plug at the converter end.



In-putting the converter into operation in the car it may be necessary to readjust the output transformer slightly, and retune the r.f. trimmer in the broadcast receiver slightly to compensate for loading effect of the converter. It may also be found that, although the broadcast receiver may be quiet in its operation, there may be considerable noise from ignition

and the car generator when the converter is used. Even with the best available filters and suppressors the ignition noise may still be excessive, in which case the best solution to the problem is the installation of some form of noise silencer in the car receiver. Suitable noise silencers are completely described in Chapter Five.

### Wide-Band FM Reception

Wide-band FM may be used in the 50-Mc. band above 52.5 Mc., and elsewhere throughout the v.h.f. and higher bands. It represents an excellent means of obtaining high-quality noise-free reception at these frequencies, where the width of the passband required is not a problem. It shares with narrow-band FM an almost complete freedom from the broadcast-interference problems that plague the urban amateur who uses amplitude modulation. A receiver designed for wide-band FM is also useful in work with stations using modulated-oscillator type transmitters, on 144 Mc. and higher. Standard FM broadcast receivers may be used in conjunction with suitable converters for wide-band FM reception on any frequency. This technique is applicable up through the microwave range, and several of the workers in the amateur microwave bands have used wide-band FM detection in their pioneering efforts in this field. Receiving techniques for narrow-band FM are detailed in Chapter Five.

### FM RECEIVERS

A frequency-modulation receiver differs in circuit design from one designed for amplitude modulation chiefly in the arrangement used for detecting the signal. Detectors for amplitude-modulated signals do not respond to frequency modulation. It is also necessary, for full realization of the noise-reducing benefits of the FM system, that the signal applied to the detector be completely free from amplitude modulation. In practice, this is attained by preventing the signal from rising above a given amplitude by means of a limiter. Since the weakest signal must be amplitude-limited, high gain must be provided ahead of the limiter; the superheterodyne type of circuit almost invariably is used to provide the necessary gain.

The r.f. and i.f. stages in a superheterodyne for FM reception are practically identical in circuit arrangement with those in an AM receiver. Since the use of FM is confined to the very-high frequencies (above 29 Mc.) a high intermediate frequency is employed, usually between 4 and 5 Mc. This not only reduces image response but also provides the greater bandwidth necessary to accommodate wide-band frequency-modulated signals.

#### Receiver Requirements

The primary requirements are sufficient r.f. and i.f. gain to "saturate" the limiter even with a weak signal, sufficient bandwidth to accommodate the full frequency deviation either side of the carrier frequency without undue attenuation at the edges of the band, a limiter circuit that functions properly on both rapid and slow variations in amplitude, and a detector that gives a linear relationship between frequency deviation and amplitude output. The audio circuits are the same as in other receivers, except that in communications-type receivers it is desirable to cut off the upper audio range by a low-pass filter because higher-frequency noise components have the greatest amplitude in an FM receiver

#### The Limiter

Limiter circuits generally are of the plate-saturation type, where low plate and screen voltage are used to limit the plate-current flow at high signal amplitudes. Fig. 12-37A is a typical circuit. The tube is self-biased by a

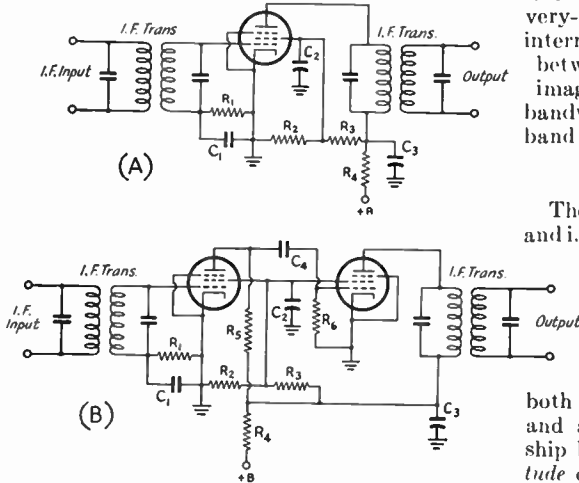


Fig. 12-37 — FM limiter circuits. A, single-tube plate-saturation limiter; B, cascade limiter. Typical values are:

Circuit A	Circuit B
C <sub>1</sub> — 100 μfd.	100 μfd.
C <sub>2</sub> , C <sub>3</sub> — 0.1 μfd.	0.1 μfd.
C <sub>4</sub> —	220 μfd.
R <sub>1</sub> — 0.1 megohm.	47,000 ohms.
R <sub>2</sub> — 2200 ohms.	2200 ohms.
R <sub>3</sub> — 47,000 ohms.	47,000 ohms.
R <sub>4</sub> — 0-50,000 ohms.	0-50,000 ohms.
R <sub>5</sub> —	3900 ohms.
R <sub>6</sub> —	0.22 megohm.

Plate-supply voltage is 250 in both circuits.

grid leak,  $R_1$ , and condenser,  $C_1$ .  $R_2$ ,  $R_3$  and  $R_4$  form a voltage divider which puts the desired voltages on the screen and plate. The lower the voltages the lower the signal level at which limiting occurs, but the r.f. output voltage of the limiter also is lower.  $C_2$  and  $C_3$  are the plate and screen by-pass condensers, of conventional value for the intermediate frequency used. The time constant of  $R_1C_1$  determines the behavior of the limiter with respect to rapid and slow amplitude variations. For best operation on impulse noise the time constant should be small, but a too-small time constant limits the range of signal strengths the limiter can handle without departing from the constant-output condition. A larger time constant is better in this respect but is not so effective for rapid variations. Compromise constants are shown in Fig. 12-37.

The cascade limiter, Fig. 12-37B, overcomes this by making the time constant in the first grid circuit suitable for effective operation on impulse noise, and that in the second grid ( $C_4R_6$ ) optimum for a wide range of input signal strengths. This results, in addition, in more constant output over a very wide range of input signal amplitudes because the voltage at

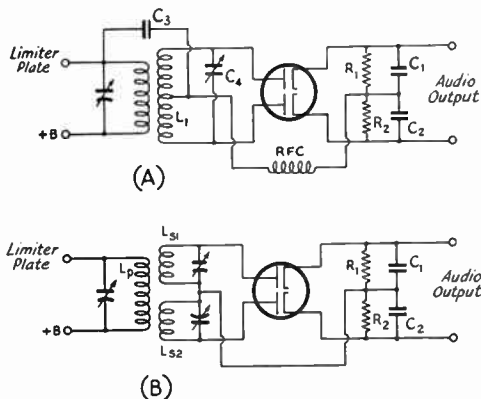


Fig. 12-38 — FM discriminator circuits. In both circuits typical values for  $C_1$  and  $C_2$  are 100  $\mu\text{mfd.}$  each;  $R_1$  and  $R_2$ , 0.1 megohm each.  $C_3$  in A is approximately 50  $\mu\text{mfd.}$ , depending upon the intermediate frequency; RFC should be of a type designed for the i.f. in use (2.5 millihenrys is satisfactory for intermediate frequencies of 4 to 5 Mc.).

the grid of the second stage already is partially amplitude-limited. Resistance coupling ( $R_5C_4R_6$ ) is used for simplicity and to prevent unwanted regeneration, additional gain at this point being unnecessary.

The rectified voltage developed across  $R_1$  in either circuit may be applied to the i.f. amplifier for a.v.c.

#### Discriminator Circuits and Operation

The FM detector commonly is called a *discriminator*, because of its ability to discriminate between frequency deviations above and below the carrier frequency.

A rectifier connected to an ordinary tuned circuit adjusted so that the signal frequency falls on one side of the response curve constitutes an elementary discriminator, because the rectifier output will vary with a change in the carrier frequency. If two such circuits are used with a balanced rectifier, one tuned above and the other below the signal frequency, amplitude variations are balanced out and the combined rectified current is proportional to the frequency deviation.

The circuit most widely used is the "series" or center-tuned discriminator shown in Fig. 12-38A. A special i.f. coupling transformer is used between the limiter and detector. Its secondary,  $L_1$ , is center-tapped and is connected back to the plate side of the primary circuit, which otherwise is conventional.  $C_4$  is the tuning condenser. The load circuits of the two diode rectifiers ( $R_1C_1R_2C_2$ ) are connected in series; constants are the same as in ordinary diode detector circuits. Audio output is taken from across the two load resistances.

The primary and secondary circuits are both adjusted to resonance in the center of the i.f. passband. The voltage applied to the rectifiers consists of two components, that induced in the secondary by the inductive coupling and that fed to the center of the secondary through  $C_3$ . The phase relations between the two are such that at resonance the rectified load currents are equal in amplitude but flow in opposite directions through  $R_1$  and  $R_2$ , hence the net voltage across the terminals marked "audio output" is zero. When the carrier deviates from resonance the induced secondary current either lags or leads, depending upon whether the deviation is to the high- or low-frequency side, and this phase shift causes the induced current to combine with that fed through  $C_3$  in such a way that one diode gets more voltage than the other when the frequency is below resonance, while the second diode gets the larger voltage when the frequency is higher than resonance. The voltage appearing across the output terminals is the difference between the two diode voltages. Thus a characteristic like that of Fig. 12-39 results, where the net rectified output voltage has opposite polarity for frequencies on either side of resonance, and up to a certain point becomes greater in amplitude as the frequency deviation is greater. The straight-line portion of the curve is the useful detector characteristic. The separation between the peaks that mark the ends of the linear portion of the curve depends upon the  $Q$ s of the primary and secondary circuits and the degree of coupling. The separation becomes greater with low  $Q$ s and close coupling. The circuit ordinarily is designed so that the peaks fall just outside the limits of the pass-band, thus utilizing most of the straight portion of the curve. Since the audio output is proportional to the change in d.c. voltage with deviation, it is advantageous for maximum output to keep the frequency separation between peaks

down to the minimum value necessary for a linear characteristic.

A second type of discriminator is shown in Fig. 12-38B. Two secondary circuits are used, one tuned above the center frequency of the i.f. passband and the other below. They are coupled equally to the primary, which is tuned to the center frequency. As the carrier frequency deviates the voltages induced in the secondaries will change in amplitude, the larger voltage appearing across the secondary being nearer resonance with the instantaneous fre-

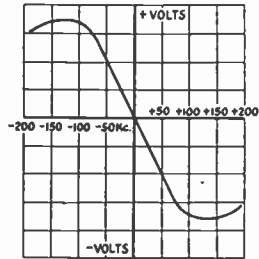


Fig. 12-39 — Characteristic of a typical FM detector. The vertical axis represents the voltage developed across the load resistor as the frequency varies from the exact resonance frequency. This detector would handle FM signals up to a bandwidth of 150 kc. over the linear portion of the curve.

quency. The detection characteristic is similar to that of the center-tuned discriminator. The peak separation is determined by the  $Q$ s of the circuits, the coefficient of coupling, and the tuning of the secondaries. High  $Q$ s and loose coupling are required for close peak separation.

A simple self-quenched superregenerative receiver may be used as a frequency detector if it is tuned so that the carrier frequency falls along the slope of the resonance curve. Two such detectors, off-tuned on either side of the carrier, may be used in push-pull. An alternative arrangement employing a superregenerative stage as a first i.f. amplifier at 75 Mc., following a converter unit, provides high gain and linear response with relatively few stages.

### FM-Receiver Alignment


Alignment of FM receivers up to the limiter is similar to other superheterodynes. For output measurement, a 0-1 milliammeter or 0-500 microammeter should be connected in series with the limiter grid resistor ( $R_1$  in Fig. 12-37A) at the grounded end; or, if the voltage drop across  $R_1$  is used for a.v.c. and the receiver is provided with a tuning meter, the tuning meter may be used as an output meter. An accurately-calibrated signal generator or test oscillator is desirable, since the i.f. should be aligned to be as symmetrical as possible; that is, the output reading should be the same for any two test-oscillator settings the same number of kilocycles above or below resonance. It is not necessary to have uniform response over the whole band to be received, although the output at the edges of the band (limit of deviation of the transmitted signals) should not be less than 25 per cent of the voltage at resonance. In communications work, a bandwidth of 30 kc. or less (15 kc. or less deviation)

is commonly used. Output readings should be taken with the oscillator set at intervals of a few kilocycles either side of resonance up to the band limits.

After the i.f. (and front-end) alignment, the limiter operation should be checked. This can be done by temporarily disconnecting  $C_3$ , if the discriminator circuit of Fig. 12-38A is used, disconnecting  $R_1$  and  $C_1$  on the cathode side, and inserting the milliammeter or microammeter in series with  $R_2$  at the low end. This converts the discriminator into an ordinary diode rectifier. Varying the signal-generator frequency over the channel, with the discriminator transformer adjusted to resonance, should show no change in output (at the bandwidths used for communications purposes) as indicated by the rectified current read by the meter. At this point various plate and screen voltages can be tried on the limiter tube or tubes, to determine the set of conditions that gives maximum output with adequate limiting (no change in rectified current).

When the limiter has been checked the discriminator connections can be restored, leaving the meter connected in series with  $R_2$ . Provision should be made for reversing the connections to the meter terminals, to take care of the reversal in polarity of the net rectified current. Set the signal generator to the center frequency of the band and adjust the discriminator-transformer trimmer condensers to resonance, which will be indicated by zero rectified current. Then set the test oscillator at the deviation limit on one side of the center frequency, and note the meter reading. Reverse the meter terminals and set the test oscillator at the deviation limit on the other side. The two readings should be the same. If they are not, they can be made so by a slight adjustment of the primary trimmer. This will necessitate rechecking the response at resonance to make sure it is still zero. Generally, the secondary trimmer will chiefly affect the zero-response frequency, while the primary trimmer will have most effect on the symmetry of the discriminator peaks. A detector curve

Fig. 12-40 — Oscilloscope patterns in FM i.f. alignment. A — I.f.-amplifier response. B — Overall characteristic through the FM detector.

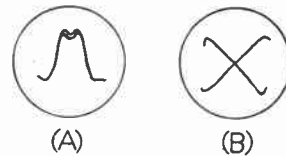

having satisfactory linearity can be obtained by cut-and-try adjustment of both trimmers.

A visual curve tracer is particularly advantageous in aligning the wide-band i.f. amplifiers of FM receivers. The i.f. is first aligned with the discriminator circuit converted into an AM diode detector, as described above, the pattern appearing as in Fig. 12-40A. The over-all characteristic, including the FM detector, is shown in Fig. 12-40B.

# V.H.F. Transmitters

Beginning with the v.h.f. region, frequency assignments are no longer in direct harmonic relationship. This fact, coupled with the necessity for extreme care in selection and arrangement of components for low circuit capacitance and minimum lead inductance, makes it highly desirable to construct separate r.f. equipment for v.h.f. work, rather than attempt to adapt for v.h.f. use a transmitter designed for the lower frequencies.

Transmitter stability requirements for 50 Mc. are the same as for the lower-frequency bands, and, by careful attention to component placement, a rig may be made to serve well on 50, 28, and even 14 Mc., but incorporation of 50 Mc. and higher in the usual "all-band" transmitter is not generally feasible.

At 144 Mc. and higher, no restrictions are imposed on transmitter stability, except that the whole emission must be kept within the band limits. This permits the use of modulated-oscillator transmitters, and many of the stations now working on 144 Mc. and above still employ this simple type of gear. By proper choice of tubes and circuits, crystal control is applicable to 144 Mc. however, and the greatly-increased occupancy of the band in metropolitan areas makes stabilization of at least the higher-powered stations almost mandatory, if the full possibilities of the band are to be realized. Crystal control, or its equivalent, may even be employed on 235 and 420 Mc., but the use of these frequencies has not reached

the point where stabilization is particularly important.

Above 51 Mc., and higher throughout the v.h.f. and u.h.f. regions, frequency modulation as well as amplitude modulation is permitted by the amateur regulations. The 200-watt transmitter for 50 and 144 Mc. described in this chapter makes provision for the use of FM, and any crystal-controlled transmitter can be adapted for FM by using a frequency-modulated oscillator to replace the crystal, in the manner described in Chapter Nine.

At 420 Mc. and higher, most standard transmitting tubes cannot be used with any degree of success. Instead, special tubes designed for these frequencies must be employed. Such tubes have extremely-close electrode spacing, to reduce transit-time effects, and are constructed with leads having virtually no inductance. Several more-or-less-conventional tubes are now available which will operate with fair efficiency up to above 500 Mc., and the disk-seal or "lighthouse" variety will function up to about 3000 Mc.

Above about 2000 Mc. the most useful types of tubes are the klystron and magnetron. These are essentially one-band devices, the frequency-determining circuits being an integral part of the tube itself. Tuning over a small frequency range, such as an amateur band, is possible, usually by warping the cavity employed, but the tubes are not independent of frequency in the conventional sense.

## A 60-Watt AM-FM 50-Mc. Transmitter or Exciter

The transmitter shown in Figs. 13-1-13-3, inclusive, has an output of approximately 40 watts in the 50-Mc. band and is so designed that either frequency or amplitude modulation may be used. Aside from power supplies, no auxiliary apparatus is needed for FM transmission, since the primary frequency control is a variable-frequency oscillator and a reactance modulator is included in the unit. For amplitude modulation, a modulator having an audio power output of about 30 watts is required.

As an alternative to electron-coupled VFO control, provision also is made for crystal control, using a Tri-tet oscillator. As shown in the circuit diagram, Fig. 13-2, the crystal oscillator and e.c. oscillator have a common plate circuit, the frequency being doubled in this

circuit in both cases. The oscillators are followed by a 6V6 doubler, and this in turn drives the final amplifier, an 815.

The tuned circuits are designed to cover a little more than the range required for the 50-Mc. band so that the transmitter as shown can be used to drive a power frequency multiplier tripling into the 144-Mc. band. The VFO grid circuit tunes from 12 to 13.5 Mc., the range from 12.5 to 13.5 Mc. being used for the 50-Mc. band, and the range from 12 to 12.35 Mc. being available for the 144-Mc. band. When crystal control is to be used, frequencies within the appropriate ranges should be selected, since the oscillator portion of the Tri-tet circuit works over the same frequency range as the grid circuit of the VFO. Appropriate

crystals in the 6-, 8-, or 12-Mc. ranges may be used, as the 6AG7 crystal oscillator will operate effectively as a quadrupler or tripler, as well as a doubler.

The common oscillator plate circuit tunes from 24 to 27 Mc., with the 6V6 doubling to 48 to 54 Mc. Either oscillator may be selected by means of a switch,  $S_{1A-B-C}$ , which closes the cathode circuit of the desired oscillator. To prevent any possibility of accidental frequency modulation when amplitude modulation is being used, a three-position switch is employed, giving a front-panel selection of crystal or VFO control (for AM or c.w.) and VFO control with FM.

Stability under changes in supply voltage is attained by supplying the VFO screen from a VR-150. This holds the screen voltage at 150 when the plate potential is varied from 150 to 600 volts. The cathode current to the oscillator, measured in  $J_2$ , remains practically constant when the plate voltage is varied over this wide range, and the total frequency shift is only a few hundred cycles. With variations in plate voltage which would result from even the most severe line-voltage fluctuations, the frequency shift in the oscillator is only a few cycles.

The transmitter is built on a  $10 \times 17 \times 3$ -inch chassis, with all components except tubes, crystal and the final-stage output circuit mounted below the deck. Viewing the unit from the top front, the microphone transformer and 6SA7 reactance modulator are at the right front, with the VR-150 at the rear, adjacent to the antenna-coupling assembly. The crystal, crystal oscillator and VFO are grouped near the middle of the chassis, with the doubler and final tubes at the left.

The front panel is a standard  $8\frac{3}{4} \times 19$ -inch crackle-finished Masonite unit. The VFO tuning dial is centrally placed, with the oscillator and doubler tuning condensers at the left and the AM/FM switch and deviation control at

the right. The final plate tuning knob is above the VFO dial, at the left, and the swinging-link adjustment is at the right. Jacks, from left to right, are  $J_4$ ,  $J_3$ ,  $J_2$  and  $J_1$ .


The two wires protruding through the chassis close to the 815 are neutralizing "condensers," labeled  $C_{N1}$  and  $C_{N2}$  on the schematic diagram. They consist of two pieces of No. 14 enameled wire soldered to the grid prongs of the 815 socket, crossed under the chassis, and brought through the chassis and held in position by two small Isolantite feed-through bushings (Millen 32150).

#### Adjustment Procedure

Adjustment is simple and straightforward. The tuning range of the VFO should be checked first. This may be done with only the two oscillator tubes in place and the AM/FM switch in the VFO position. The oscillator plate condenser should be tuned for maximum r.f. indication in a neon bulb adjacent to  $L_2$ , and the frequency checked in a receiver having a fairly-accurate calibration for the region around 12, 24, or 48 Mc.

The size of the VFO grid coil,  $L_1$ , is extremely critical, and if some pruning of this coil is to be avoided it would be advisable to make the  $50\text{-}\mu\text{fd.}$  section of  $C_{10}$  an adjustable padder condenser, such as a Hammarlund APC-50, which can then be adjusted until 12 Mc. appears at about 90 on the VFO vernier dial. The high-frequency limit, 13.5 Mc., should then come at approximately 10, giving a spread of about 18 divisions for the 144-Mc. band and 54 divisions for the 50-Mc. band. Without such a variable condenser, the number of turns on  $L_1$  must be adjusted by cut-and-try until the proper tuning range is secured. In either case, the final adjustment of band coverage should be made with the 6SA7 reactance modulator in its socket so that its plate-to-ground capacitance will be across the tuned circuit.

◆  
Fig. 13-1 — Front view of the 50-Mc. AM/FM transmitter. The r.f. section of the unit occupies the left-hand portion of the chassis. The VR-150, 6SA7 reactance modulator, and microphone transformer are at the right. Note the neutralizing-capacitance wires at the left of the 815.  
◆

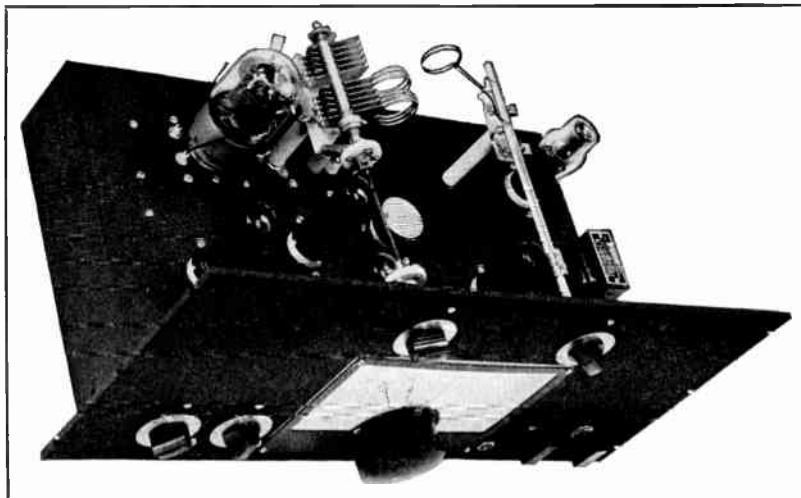

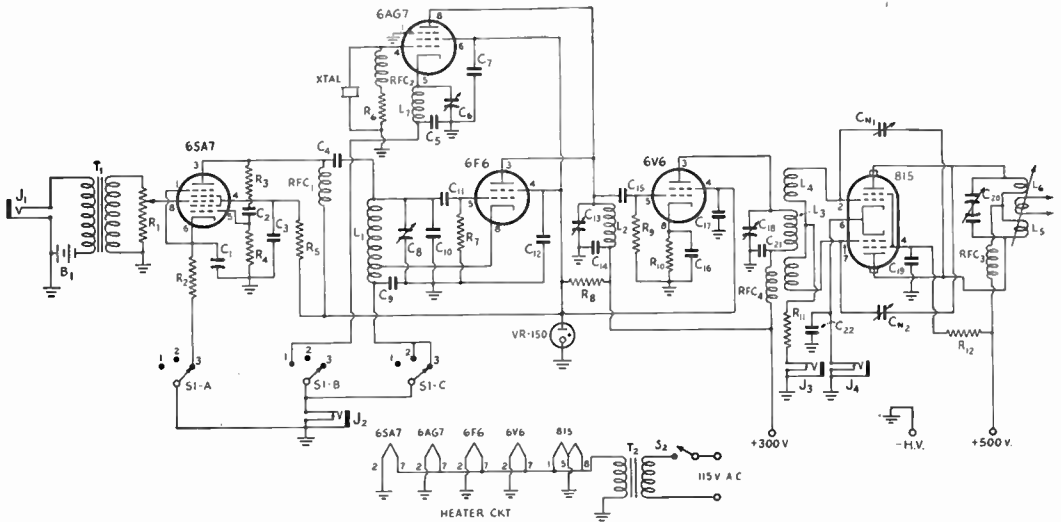


Fig. 13-2 — Wiring diagram of a 50-Mc. AM/FM transmitter.

$C_1$  — 0.01- $\mu$ fd. 400-volt paper tubular.  
 $C_2$  — 0.001- $\mu$ fd. mica.  
 $C_3$  — 8- $\mu$ fd. 450-volt electrolytic and 0.0047- $\mu$ fd. mica in parallel.  
 $C_4, C_{19}$  — 470- $\mu$ fd. mica.  
 $C_5, C_7, C_9, C_{12}, C_{14}, C_{16}, C_{17}, C_{21}, C_{22}$  — 0.0022- $\mu$ fd. mica.  
 $C_6$  — 100- $\mu$ fd. midget variable, screwdriver adjustment (Hammarlund APC-100).  
 $C_8$  — 50- $\mu$ fd. variable, "straight-line-frequency" type (Hammarlund MC-50-M).  
 $C_{10}$  — 100- $\mu$ fd. and 50- $\mu$ fd. in parallel (Siekles Silver-cap). See text.  
 $C_{11}$  — 100- $\mu$ fd. mica.  
 $C_{13}, C_{18}$  — 50- $\mu$ fd. variable (Hammarlund MC-50-S).  
 $C_{15}$  — 47- $\mu$ fd. mica.  
 $C_{20}$  — 35  $\mu$ fd. per section, split stator (Hammarlund MCD-35-MX).  
 $C_{N1}, C_{N2}$  — Neutralizing capacitors. See text.  
 $R_1$  — 0.5-megohm volume control, switch type.  
 $R_2$  — 680 ohms,  $\frac{1}{2}$  watt.  
 $R_3$  — 47,000 ohms,  $\frac{1}{2}$  watt.  
 $R_4, R_6$  — 0.22 megohm,  $\frac{1}{2}$  watt.  
 $R_5$  — 4700 ohms,  $\frac{1}{2}$  watt.  
 $R_7, R_9$  — 0.1 megohm,  $\frac{1}{2}$  watt.  
 $R_8$  — 5000 ohms, 5 watts.  
 $R_{10}$  — 220 ohms, 1 watt.  
 $R_{11}$  — 15,000 ohms, 1 watt.  
 $R_{12}$  — 15,000 ohms, 5 watts.

$L_1$  — 8 turns No. 18 tinned,  $\frac{3}{8}$ -inch diameter, 1-inch length on National PRF-2 form. Tapped 2 t. from ground end.  
 $L_2$  — 10 turns No. 14 e.,  $\frac{1}{2}$ -inch diameter, spaced one diameter, air-wound.  
 $L_3$  — 4 turns No. 14 e.,  $\frac{1}{2}$ -inch diameter, spaced one diameter, air-wound.  
 $L_4$  — 5 turns each section, No. 14 e.,  $\frac{1}{2}$ -inch diameter. Adjust spacing for best coupling. See text.  
 $L_5$  — 3 turns each section, No. 12, tinned,  $1\frac{1}{8}$ -inch diameter, spaced one diameter.  
 $L_6$  — 2 turns No. 14 e., 1-inch diameter, swinging link. See photos and text.  
 $L_7$  — 35 turns No. 24 d.c.e., close-wound on 9/16-inch diameter form (National PRF-3).  
 $B_1$  — Microphone battery (Burgess).  
 $J_1$  — Open-circuit jack.  
 $J_2, J_3, J_4$  — Closed-circuit jack.  
 $RFC_1, RFC_2, RFC_4$  — 2.5-mh. r.f. choke (National R-100).  
 $RFC_3$  — 2.5-mh. r.f. choke, end-mounting (National R-100-U).  
 $S_{1A-B-C}$  — 3-position 3-contact rotary switch (Mallory).  
 $S_2$  — Switch on deviation control,  $R_1$ .  
 $T_1$  — Single-button microphone transformer (Thordarson T-83A78).  
 $T_2$  — 6.3-volt 4-amp. filament transformer.


Operation of the crystal oscillator may next be checked. With a 100-ma. meter connected through  $J_2$ , and the AM/FM switch in the "crystal" position, adjust the crystal-oscillator cathode tuning,  $C_6$ , until the current dips sharply, indicating oscillation. This control should be set at the point that gives the lowest cathode current consistent with easy crystal starting. Cathode current should be similar for both oscillators — about 20 ma.

The doubler stage may next be tested by installing the 6V6 and 815 tubes, leaving the plate power off the 815. A meter having a 10-ma. range should be used to measure the grid current in the 815, at  $J_3$ . The current should come up to about 6 ma. when the spacing between  $L_3$  and  $L_4$  is optimum, though this is more than is actually needed for satisfactory operation of the 815.

Next the position of the neutralizing wires can be adjusted. The 815 plate tuning condenser,  $C_{20}$ , should be rotated slowly, meanwhile watching the grid current for any variation. The position of the neutralizing wires should be adjusted until there is no sign of fluctuation in grid current as the tuning condenser is rotated. A length of wire extending about one inch above the metal ring on the 815, at a position about  $\frac{1}{8}$  inch from the glass envelope, should be sufficient. If this should be inadequate, small tabs of copper or brass can be soldered to the ends of the wires to afford additional capacitance to the tube plates. The neutralizing capacitance is necessary in order to ensure completely-stable operation.

After neutralization, power may be applied to the 815 plates, while noting the cathode current as indicated on a 200-ma. meter plugged

Fig. 13-3 — Under-chassis view of the 50-Mc. AM/FM transmitter. At the lower center are the VFO grid coil and associated components. Over these are the crystal and cathode circuit for the 6AG7 crystal oscillator. At the upper right are the inductively-coupled doubler plate coil and final grid coil. The coil and condenser at the lower right comprise the plate circuit which is common to both oscillators. The doubler plate tuning condenser is at the extreme right.

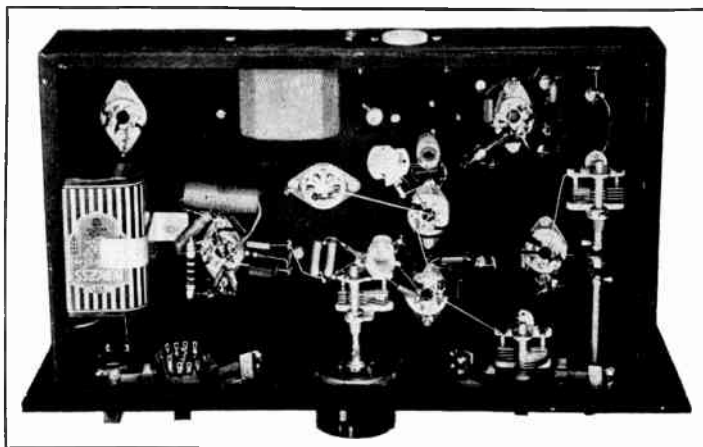

into  $J_4$ . The dip at resonance should bring the current to about 50 ma. with no load. A 40-watt lamp connected across the swinging-link terminals should then give a full-brilliance indication when the link is adjusted for maximum coupling. This is with 500 volts applied, which should be used only after it has been determined that everything is functioning properly. If trouble is encountered, further tests should be made with reduced voltage to avoid damaging the tube.

When the transmitter is put on the air, the full 500 volts at 150 ma. may be used for FM or c.w. operation. For plate modulation, the voltage should be reduced to about 400 for maximum tube life, even though the tube plates may show no color at the higher plate voltage.

For frequency modulation, the 6SA7 reactance modulator provides the simplest possible means of obtaining the desired swing in frequency. It may be operated with a single-button microphone plugged into  $J_1$ , or the modulator may be driven from a speech amplifier and crystal or dynamic microphone. The output of the speech amplifier should then be connected across potentiometer  $R_1$ , and  $T_1$  may

be omitted. In either case, potentiometer  $R_1$  serves as a deviation control, the frequency swing being adjusted to suit the receiver at the station being worked.

For 144-Mc. work, or for operation above 52.5 Mc. in the 6-meter band, wide-band FM may be used if desired, in which case the setting of  $R_1$  may be anything up to full-on. The transmitter may also be used for narrow-band FM on any frequency above 51 Mc. Considerable care should then be used in adjusting the deviation, to be certain that the swing is within the prescribed limits. The procedure outlined in Chapter Nine may be followed for checking the deviation in NFM operation.

In addition to the filament transformer,  $T_2$ , indicated in the circuit diagram, the transmitter requires two plate power supplies. One, for the 815, should have an output of 400 to 500 volts at 175 ma.; the other, for the remaining tubes, should deliver 300 volts at approximately 100 milliamperes.

If more power is desired, an 829 may be substituted for the 815. In this case an input of 100 watts or more may be run, the output being as high as 85 watts at maximum operating conditions.

## 200-Watt Driver-Amplifier for 50 and 144 Mc.

A companion medium-power driver-amplifier for the 815 rig just described is shown in Figs. 13-4 to 13-7. The amplifier uses a pair of 24G triodes in push-pull, while the driver, a frequency tripler used for 144-Mc. operation only, is a single 829-B. If operation on 144 Mc. is not contemplated, all to the left of the final grid coil,  $L_3$  in Fig. 13-6, may be omitted.

Looking at the front-panel view, Fig. 13-4, the two large dials are the plate tuning controls for both stages. The small dial at the left controls the swinging link, the center one is the grid tuning control for the final, and the one at the far right is the tripler grid tuning.

The rear view shows the general placement

of parts. At the left rear is a jack-bar, containing terminals  $AA$  and  $BB$ , into which the link from the exciter is plugged to furnish excitation for the tripler (terminals  $AA$ ) or final stage (terminals  $BB$ ). The tripler grid-circuit components,  $L_1C_1$ , are adjacent to the jack-bar.  $C_1$  is mounted with its shaft parallel to the panel, in order to permit short leads, and is tuned by means of a flexible shaft. The 829-B and its plate-circuit components are mounted in such position as to permit inductive coupling between the plate coil of the tripler and the grid coil of the final, when the transmitter is used on 144 Mc. For 50-Mc. work the 829-B is inoperative, and the 50-Mc. grid coil (the same

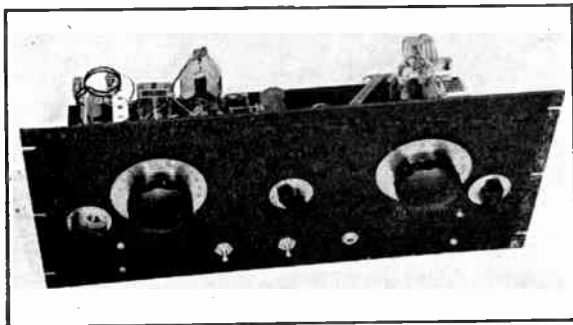


Fig. 13-4 — Front view of the 200-watt driver-amplifier for 50 and 144 Mc. The two large dials are the plate tuning controls. The small dial at the left adjusts the position of the output coupling link, the center dial is the grid tuning control for the final, and the third small dial is the tripler grid-tuning control. Across the lower center are the filament switches and grid-current meter jack.

coil is used in both tripler and final) just clears the plate coil of the 829-B. Care must be used in parts placement to work this out correctly.

Between the grid tuning condenser,  $C_3$ , and the 24G tubes are the two neutralizing condensers. These are triple-spaced midgets, mounted back-to-back, with coupled shafts. The stator plates had to be filed out to reduce the minimum capacitance to the small value needed to neutralize the 24Gs. The final tank condenser,  $C_5$ , and the jack-bar for the final plate coil are positioned for the short leads that are required if satisfactory performance on 144 Mc. is to be attained. R.f. leads in the final stage are made with  $\frac{1}{4}$ -inch silver ribbon, which is appreciably better than braid at these frequencies. Thin copper strip may also be used. All connections in the plate circuit of the 21Gs should be made with bolts and nuts, as the tank circuit will heat sufficiently during 144-Mc. operation to melt soldered connections and increase losses. Plate connections to the 829-B are made by means of small Fahnestock clips. The tripler plate coil is supplied with two of these clips (Millen 36021), so that it may be removed separately from the condenser leads, in replacing the tube.

#### Operation on 50 Mc.


When the amplifier is to be used on 50 Mc. the switch,  $S_1$ , is left open, so that the heater of the tripler will not be energized when  $S_2$  is

closed. The link from the exciter is plugged into terminals  $BB$  in the jack-bar, which is a Millen 41205 coil socket. The output of the exciter is thus connected to the link terminals of the final grid-coil socket, a National XB-16.

The final stage should be tested on 50 Mc. before attempting 144-Mc. operation. With the proper coils inserted at  $L_3$  and  $L_4$ , and with power on the exciter but no plate voltage on the final, rotate  $C_3$  for maximum grid current. Set the neutralizing condensers at maximum capacitance and rotate  $C_5$ . If the plate circuit is capable of being resonated there will be a kick in the grid current as the circuit passes through resonance. The neutralizing condensers should be rotated, a small amount at a time, until the kick in the grid current disappears. This will probably occur close to the minimum-capacitance setting of  $C_{3a}$  and  $C_{3b}$ .

Power may now be applied to the plate circuit. It is advisable to make initial tuning adjustments at low voltage, preferably 750 volts or less. If everything is in order, the plate current will drop to about 20 ma. at resonance, at this voltage. A load of some sort should now be connected across the output terminals and the operation tested at increasingly higher voltages. The final tubes should be capable of an input of 250 watts or more on 50 Mc. without exceeding their normal plate dissipation of 50 watts for the pair, indicated by a bright orange color.

Fig. 13-5 — Rear view of the driver-amplifier for 50 and 144 Mc., with coils in place for 144-Mc. operation. At the lower left are the link socket and the grid circuit of the tripler stage. The plate coil of the tripler is inductively-coupled to the final grid coil, a single turn. All parts are grouped as closely as possible, for efficient performance on 144 Mc. R.f. leads in the final stage are made of  $\frac{1}{4}$ -inch silver ribbon.

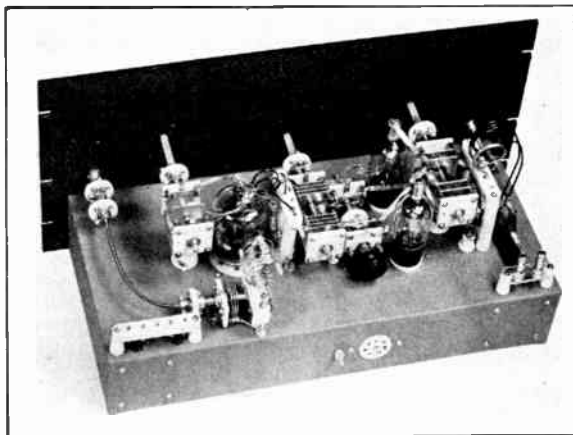



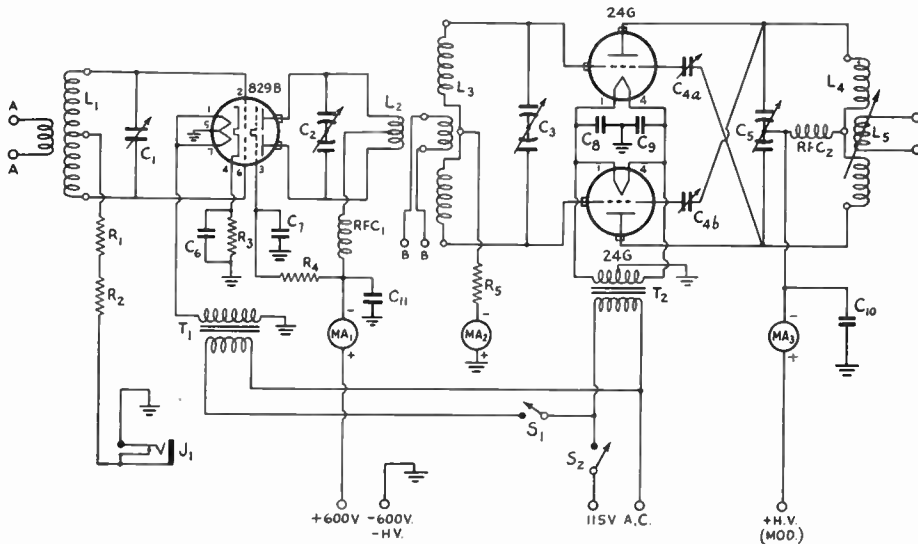


Fig. 13-6 — Schematic diagram of the 200-watt driver-amplifier.

- C<sub>1</sub> — 15- $\mu$ fd. variable (Cardwell ZR-15-AS).
- C<sub>2</sub> — 10- $\mu$ fd. per-section split stator (Cardwell ER-10-AD).
- C<sub>3</sub> — 15- $\mu$ fd. per-section split stator (Cardwell ET-15-AD).
- C<sub>4a</sub>, C<sub>4b</sub> — 2-plate triple-spaced midget variable (Cardwell ZS-4-SS with stator plates filed to reduce minimum capacitance).
- C<sub>5</sub> — 4- $\mu$ fd. per-section split stator (Cardwell ES-4-SI).
- C<sub>6</sub>, C<sub>7</sub> — 470- $\mu$ fd. midget mica.
- C<sub>8</sub>, C<sub>9</sub> — 0.001- $\mu$ fd. mica.
- C<sub>10</sub> — 500- $\mu$ fd. 2500-volt mica.
- C<sub>11</sub> — 500- $\mu$ fd. 1000-volt mica.
- R<sub>1</sub> — 1700-ohm 2-watt carbon.
- R<sub>2</sub> — 50,000 ohms, 10 watts.
- R<sub>3</sub> — 250 ohms, 10 watts.
- R<sub>4</sub> — 15,000 ohms, 10 watts.
- R<sub>5</sub> — 3000 ohms, 10 watts.
- L<sub>1</sub> — 4 turns No. 18, 1 1/4-inch diameter, 1 inch long, 3-turn center link (National AR-16, 10-C, with 2 turns removed from each end).

- L<sub>2</sub> — 2 turns No. 12 enameled, 7/8-inch diameter, spaces 1/4 inch.
- L<sub>3</sub> — 50 Mc.: Use L<sub>1</sub>. 144 Mc.: Center-tapped "U" made from No. 12 enameled wire, 5/8 inch high, 3/4 inch wide. See rear-view photograph. Sockets for L<sub>1</sub> and L<sub>3</sub> are National XB-16.
- L<sub>4</sub> — 50 Mc.: 4 turns each side of center-tap, spaced diameter of wire, on Millen No. 40205 base.  
— 144 Mc.: 2 turns 1/8-inch brass rod, spaced to fit into socket terminals, 1 1/4-inch inside diameter. May be silver-plated for best results.
- L<sub>5</sub> — Swinging link: 3 turns No. 12 enameled wire, 1 3/8-inch diam. Mount for adjustment on polystyrene rod; see rear-view photograph.
- J<sub>1</sub> — Closed-circuit jack.
- MA<sub>1</sub> — 0-200 d.c. milliammeter.
- MA<sub>2</sub> — 0-100 d.c. milliammeter.
- MA<sub>3</sub> — 0-300 d.c. milliammeter.
- RFC<sub>1</sub>, RFC<sub>2</sub> — Ohmite Z-0.
- S<sub>1</sub>, S<sub>2</sub> — S.p.s.t. toggle switch.
- T<sub>1</sub> — 6.3 volts, 2.5 amp.
- T<sub>2</sub> — 6.3 volts, 6 amp.


**Checking on 144 Mc.**

For operation on 144 Mc., the switch, S<sub>1</sub>, should be closed, energizing the heater of the 829-B tripler. The link from the exciter should be plugged into terminals AA on the jack-bar, so that drive is applied to the tripler grid circuit. The 144-Mc. coils should be inserted at L<sub>3</sub> and L<sub>4</sub>. It will be noted that these coils have no bases. The grid coil (merely a center-tapped "U") is made of No. 12 wire, which fits snugly in the coil-socket terminals. It should be bent

slightly toward the 829-B plate coil. L<sub>2</sub>, so that it fits between the turns at a position that provides optimum inductive coupling. The final plate coil is made of 1/8-inch brass rod, which provides a tight fit in the jack-bar. The coil may be silver-plated, if desired.

The grid coil for the tripler (L<sub>1</sub>) may be the same coil as is used for 50-Mc. operation at L<sub>3</sub>. With this coil in place and the output of the exciter on 48 Mc., the operation of the tripler may be checked, using a voltage of around 400

Fig. 13-7 — Bottom view of the 50-144-Mc. driver-amplifier.

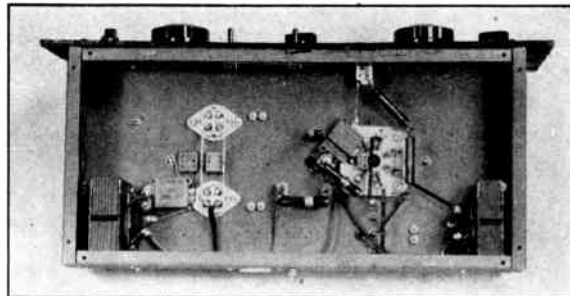

on the plates of the 829-B initially. The grid circuit of the final should then be tuned to resonance as indicated by maximum grid current. The plate voltage on the tripler may be raised to 600 volts, if necessary, to assure adequate grid drive for the final stage. Typical operating conditions are as follows: tripler plate voltage — 600; plate current — 125 ma.; tripler grid current (read in  $J_1$ ) — 10 ma. or more; final grid current — 35 to 50 ma.

Neutralization of the final should be rechecked, as the position of  $C_{4a}$  and  $C_{4b}$  may be slightly different from the 50-Mc. setting. Power may then be applied to the final stage, using low voltages at first. The final stage should not be operated without load, except with low plate voltages, as tank-circuit losses will cause excessive heating otherwise. The dip in plate current at resonance will be less than at 50 Mc., and minimum current at 1000 volts will probably not drop below about 65 ma. The maximum recommended plate potential for 144-Mc. operation is about 1250 volts, though tests have been made on this amplifier at voltages as high as 1700.

A safe check on the operation of the tubes is to adjust the plate voltage (with no excitation

applied) until an input of 50 watts is being run to the pair. Note the color of the plates at this input — a bright orange. If this color is not exceeded in normal operation, one may be sure that the tubes are being operated within safe limits. An input of 200 watts can be handled safely on 144 Mc. if the stage is running properly.

The transmitter may be used for c.w. work on either band by keying the cathode of the driving stage. If the 829-B tripler cathode is to be keyed a jack will have to be added. Provision should be made to add fixed bias in series between the final grid meter,  $MA_2$ , and ground. A 45-volt "B" battery will suffice to hold the 24G plate current to a safe value when the excitation is removed.

The three meters shown in the schematic diagram, but not in the photographs, are mounted on a separate meter panel. Another useful addition, not shown, is a 3500-ohm 10-watt potentiometer, connected in series with  $R_6$ , so that the final-stage bias can be varied to suit different operating conditions. This is particularly useful if the transmitter is to be used on c.w. and FM, as well as AM voice operation.

## A 60-Watt Transmitter for 50, 28 and 14 Mc.

The transmitter-exciter shown in Figs. 13-8, 13-9 and 13-10 is a three-stage unit designed for use in the 50-, 28- and 14-Mc. bands. It employs a 6V6GT Tri-tet oscillator, a 6V6GT frequency multiplier, and an 815 operating as a straight amplifier without neutralization. It is capable of an input of 75 watts when being operated as an exciter or c.w. transmitter, but the power should be reduced to 60 watts input if the amplifier is modulated. Plug-in coils are employed for simplicity and flexibility.

### Circuit Features

The Tri-tet oscillator has a fixed-frequency cathode circuit which resonates at approximately 21.5 Mc. With the cathode circuit so

tuned, it is possible to employ a wide variety of crystal frequencies. For operation on 14 Mc., 3.5-Mc. crystals may be used, with the oscillator plate circuit tuned to 7 Mc., doubling in the second 6V6GT to 14 Mc. Most 3.5-Mc. crystals will deliver sufficient output from the oscillator on 7 Mc. to permit operating the second stage as a quadrupler to 28 Mc. also. Crystals between 7000 and 7200 kc. can be used with the oscillator working straight-through, provided that the oscillator plate circuit is not resonated at exactly the crystal frequency. Crystals from 7000 to 7425 kc. are used for operation of the amplifier in the 28-Mc. band, the oscillator doubling in this case.

For 50-Mc. operation crystals between 6250 and 6750 kc. are recommended. The oscillator

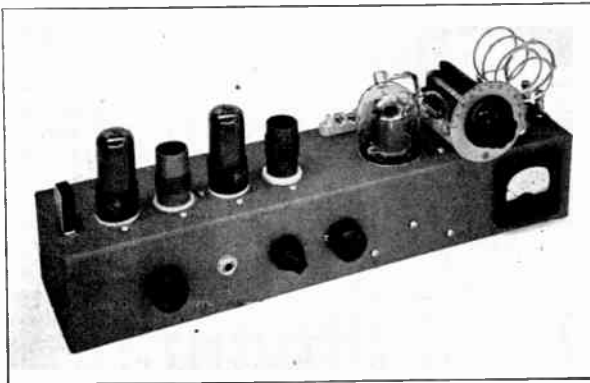


Fig. 13-8 — A front view of the 815 transmitter-exciter for 50, 28 and 14 Mc. Coils for 50-Mc. operation are in place.

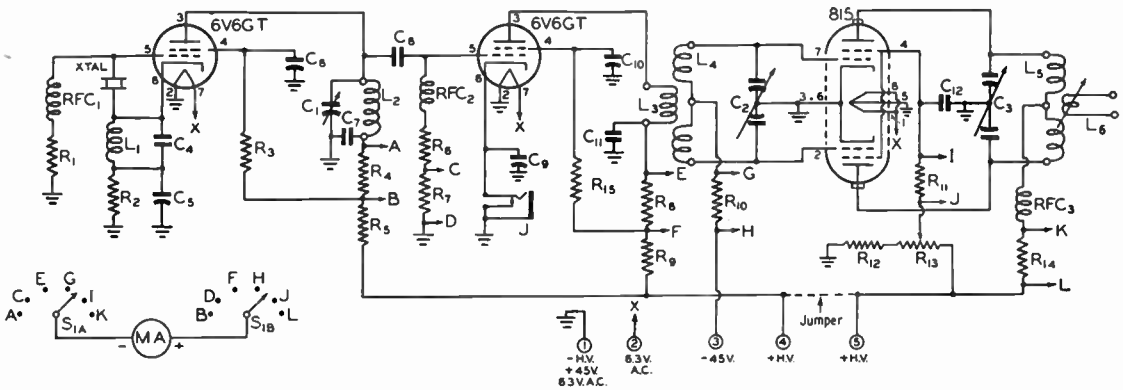


Fig. 13-9 — Circuit diagram of the 815 transmitter-exciter.

- C<sub>1</sub> — 25- $\mu$ fd. variable (Cardwell ZR-25-AS).
- C<sub>2</sub> — 50- $\mu$ fd. per-section variable (Bud LC-1662).
- C<sub>3</sub> — 35- $\mu$ fd. per-section variable (Hammarlund MCD-35-SX).
- C<sub>4</sub> — 68- $\mu$ fd. mica.
- C<sub>5</sub>, C<sub>6</sub>, C<sub>9</sub>, C<sub>10</sub> — 0.01- $\mu$ fd. paper.
- C<sub>7</sub> — 0.0022- $\mu$ fd. mica.
- C<sub>8</sub> — 100- $\mu$ fd. mica.
- C<sub>11</sub>, C<sub>12</sub> — 470- $\mu$ fd. mica.
- R<sub>1</sub> — 0.12 megohm, 1/2 watt.
- R<sub>2</sub> — 220 ohms, 1/2 watt.
- R<sub>3</sub> — 15,000 ohms, 1 watt.
- R<sub>4</sub>, R<sub>7</sub>, R<sub>8</sub>, R<sub>10</sub>, R<sub>11</sub>, R<sub>14</sub> — 100 ohms, 1/2 watt.
- R<sub>5</sub>, R<sub>9</sub> — 5,000 ohms, 10 watts, adjustable.
- R<sub>6</sub> — 47,000 ohms, 1/2 watt.
- R<sub>12</sub>, R<sub>13</sub> — 5,000 ohms, 10 watts, adjustable.
- R<sub>15</sub> — 40,000 ohms, 10 watts.
- L<sub>1</sub> — 8 turns No. 18 enameled, close-wound, 1/2-inch dia.
- L<sub>2</sub> — 7 Mc. — 25 turns No. 20 d.c.c., close-wound, 1 inch long.
- 14 Mc. — 12 turns No. 20 d.c.c., space-wound, 1 inch long.
- 28 Mc. — 5 turns No. 18 enameled, space-wound, 1/2 inch long.
- L<sub>3</sub> — 14 Mc. — 9 turns No. 20 d.c.c., close-wound, 3/8 inch long.
- 28 Mc. — 6 turns No. 20 d.c.c., space-wound, 3/8 inch long.

- 50 Mc. — 3 turns No. 18 enameled, space-wound, 1/4 inch long.
  - L<sub>4</sub> — 14 Mc. — 14 turns No. 20 d.c.c., close-wound, 7 turns each side of primary.
  - 28 Mc. — 6 turns No. 20 d.c.c., spaced diam. wire, 3 turns each side of primary.
  - 50 Mc. — 4 turns No. 18 enameled, spaced diam. wire, 2 turns each side of primary.
- Above coils are wound on 1-inch diameter forms (Millen 15004 for L<sub>2</sub>; Millen 45005 for L<sub>3</sub>-L<sub>4</sub>). Approximately 1/8 inch between L<sub>3</sub> and L<sub>4</sub>.
- L<sub>5</sub> — 14 Mc. — 14 turns No. 16, 1 1/8-inch diameter, 2 inches long. (B & W 20-JVL.)
  - 28 Mc. — 8 turns No. 12, 1 1/8-inch diameter, 2 inches long. (B & W 10-JVL.)
  - 50 Mc. — 4 turns No. 12, 1 1/8-inch diameter, 2 inches long. (B & W 10-JVL) with 2 turns removed from each end.)
- Above coils are wound in two sections with half the total number of turns each side of center. A 1/2-inch space is left at the center to permit the use of a swinging link (L<sub>6</sub>). The Barker & Williamson coils are mounted on five-prong bases of the type which plug into tube sockets.
- J — Closed-circuit jack.
  - MA — 0-50 milliammeter.
  - RFC<sub>1</sub>, RFC<sub>2</sub>, RFC<sub>3</sub> — 2.5-mh. r.f. choke.
  - S<sub>1A</sub>, S<sub>1B</sub> — 2-circuit 6-position selector switch (Mallory 3226J).

is then operated as a quadrupler and the second stage as a doubler. The oscillator may also be operated as a tripler, using crystals between 8334 and 9000 kc., or as a doubler with 12.5-13.5-Mc. crystals. The complete unit may also be used as a driver for a 144-Mc. tripler stage by using the above crystal types, except that the ranges would then be 6000-6166, 8000-8222, or 12,000-12,333 kc.

Cathode bias is used on the oscillator stage, maintaining the plate current at a reasonable figure. The common-power-supply voltage is lowered to 300 volts by the dropping resistor, R<sub>5</sub>, and the screen voltage of 250 is obtained from resistor R<sub>3</sub>. The by-pass condenser, C<sub>7</sub>, is inserted between the cold end of the plate coil, L<sub>2</sub>, and ground, in order to permit grounding of the tuning-condenser rotor. Capacitive coupling, through C<sub>8</sub>, is used between the oscillator and the multiplier stage.

The multiplier stage has a self-resonant plate circuit which is inductively-coupled to the grid circuit of the final amplifier. This arrangement was found to give better balance of excitation to the final-stage grids than did the

use of a self-resonant grid circuit in the final stage and a tuned plate circuit for the 6V6GT. Resistors R<sub>9</sub> and R<sub>15</sub> drop the screen and plate voltages to the proper values. Grid bias is developed across R<sub>6</sub>. The cathode by-pass condenser, C<sub>9</sub>, is required because of the lengthening of the cathode lead by the insertion of the keying jack, J. No neutralization is required in this stage, since it is operated as a frequency multiplier at all times.

Bias for the final amplifier is obtained from a 45-volt "B" battery, permitting the preceding stage to be keyed for c.w. operation. The voltage-divider network, R<sub>12</sub> and R<sub>13</sub>, can be adjusted to provide the proper screen voltage for either type of operation. The plate tuning-condenser rotor is connected directly to ground. Power output is taken from the plate circuit by means of the adjustable link, L<sub>6</sub>, which is part of the plug-in plate-coil assembly.

A switching system is provided for measuring all the necessary currents with one 50-ma. meter, connecting it across shunt resistors R<sub>4</sub>, R<sub>7</sub>, R<sub>8</sub>, R<sub>10</sub>, R<sub>11</sub> and R<sub>14</sub>. The range of the meter is extended to 300 ma. by means of R<sub>14</sub>,

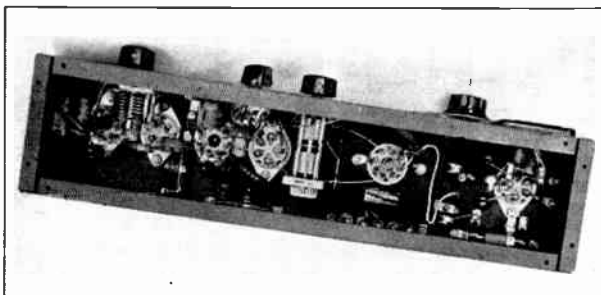


Fig. 13-10 — A bottom-inside view of the 815 transmitter.

which consists of about 31 inches of No. 30 insulated wire scramble-wound on a 100-ohm resistor. The length of wire required for this shunt may vary with different types of meters.

#### Mechanical Details

The front-view photograph, Fig. 13-8, shows the arrangement of the principal components. The chassis measures  $3 \times 4 \times 17$  inches. It is suggested that this layout be followed closely, particularly as regards the arrangement of parts in the 815 plate and grid circuits, since this layout permits operation of the 815 without neutralization. Components, along the top of the chassis, from left to right, are the crystal, oscillator tube, oscillator plate coil, multiplier tube, multiplier plate and final grid coil, final-amplifier tube, and amplifier tank circuit. A 5-connector terminal strip may be seen just to the rear of the 815. Across the front wall are the oscillator tuning knob, the keying jack, meter switch, multiplier tuning knob, and meter.

The 815 socket is mounted on a subchassis which can be seen in the bottom view, Fig. 13-10. This unit, Millen No. 80009, also includes the tube shield, which was cut off in this case so that, with the shield just flush with the chassis, the tube socket is  $1\frac{1}{2}$  inches below. Arrangement of other components is apparent from the bottom view. Resistors  $R_{12}$  and  $R_{13}$  are at the right end near the coil socket. The amplifier plate choke,  $RFC_3$ , is on a stand-off adjacent to the coil socket, and the meter shunt,  $R_{14}$ , is connected between the choke and one end of  $R_{13}$ . The dropping resistor,  $R_9$ , is parallel to the rear wall of the chassis, and  $R_5$  is at right angles to it, both below, and to the left of, the sockets for the 6V6GT and its associated plug-in coil.  $RFC_1$  and  $RFC_2$  are mounted on stand-off insulators at the rear of the tube sockets. The cathode coil,  $L_1$ , is self-supporting, and is mounted directly on the tube-socket terminals. All other small parts are grouped closely adjacent to their respective tube sockets.

Coil information is given in full detail under Fig. 13-9. The number of turns specified should be satisfactory for the frequencies of operation referred to, though some adjustment of the coupling between windings of  $L_3$  and  $L_4$  may be required. Since variation in

spacing of these windings affects the tuning range of the  $L/C$  combination to a noticeable degree, the setting of  $C_2$  should be checked as the coupling adjustment is being carried on.

#### Testing Procedure

The power supply for the transmitter should be capable of delivering 275 to 300 ma. at 400 or 500 volts. The filament transformer should supply 6.3 volts at 2.5 amperes or more. It is advisable to test the oscillator and multiplier stages before applying plate and screen voltage to the 815. The jumper between Terminals 4 and 5 on the terminal strip should be left off during this operation. With plate voltage applied to the oscillator and doubler, the oscillator plate circuit should be tuned to resonance as indicated by maximum grid current in the next stage. The amplifier grid circuit should then be tuned for maximum grid current. With the coil specifications given it is unlikely that the circuits will tune to an incorrect harmonic; nevertheless, it is wise to check with a calibrated absorption-type wavemeter to be sure that such is not the case. Dropping resistors  $R_5$  and  $R_9$  should be set at their full value of 5000 ohms during this operation, final setting of the adjustments being made after the power supply is loaded by the entire transmitter. Grid current to the final stage should be about 15 ma. for all bands at this point. This may be adjusted by changing the turns on  $L_3$ , or by detuning  $C_2$ , if the grid current is excessive. Detuning of  $C_2$  is recommended as the more satisfactory of the two methods.

The final amplifier may now be put into operation. The screen voltage should be tapped in between the screen divider,  $R_{12}$  and  $R_{13}$ , and the jumper connected between Terminals 4 and 5. With plate voltage and grid excitation applied, the off-resonance plate current should be about 250 ma., dropping to about 25 ma. when the plate circuit is tuned to resonance. A dummy load such as a lamp should be connected across the output terminals, and the coupling adjusted to bring the plate current up to 150 ma. at resonance.

The oscillator and multiplier plate voltages and the amplifier screen voltage should now be adjusted to 300 and 200 volts, respectively, by adjusting the taps on  $R_5$ ,  $R_9$  and  $R_{13}$ . It is probable that the amplifier plate current will

change appreciably at this point, so it will be desirable to readjust the coupling so that the current is again 150 ma., and readjust the resistor taps as required to secure the correct voltages on the various tube elements. Adjustment for 'phone operation is similar, except that the amplifier screen and plate voltages should be 175 and 400 volts, respectively.

With all voltages set for the proper values, the currents will run about as follows: oscillator and doubler plates — 35 ma.; doubler grid — 1 to 3 ma.; 815 grid — 5 to 6 ma.; 815 screen — 17 ma.; 815 plate — 150 ma. The 815 screen current should drop to 15 ma. for 'phone operation. A grid current of 4 to 6 ma. in the 815

is adequate. Though more grid current is usually available, an increase beyond 6 ma. does not improve the output. In c.w. operation, it will be noticed that the 815 plate current does not drop completely off when the excitation is removed. This is no cause for concern, so long as the plate and screen dissipation are held to recommended levels.

The amplifier plate coils are provided with links designed for working into a low-impedance line. The amplifier may thus be used for direct feed in the case of antenna systems having matched lines, or it may work into a line feeding an antenna-coupling unit, in case tuned-feeder antenna systems are employed.

### A 3-Stage Stabilized Transmitter

A three-stage transmitter in which frequency-modulation effects are quite small is shown in Figs. 13-11-13-14, inclusive. It includes a 6C4 oscillator, 6C4 neutralized buffer amplifier, and 815 final amplifier, as shown in the circuit diagram, Fig. 13-12. The oscillator and buffer are built as a unit on a "U"-shaped piece of aluminum  $6\frac{1}{2}$  inches long on top,  $2\frac{3}{8}$  inches high, and  $2\frac{1}{8}$  inches deep on the top. The 815 is mounted on a vertical aluminum piece measuring  $4\frac{1}{4}$  inches high and 3 inches wide, reinforced by bending side lips as shown in the photographs. The two sections are assembled on a  $6 \times 14 \times 3$ -inch chassis.


The oscillator circuit is "high-C," using a butterfly-type condenser with three circular rotor plates, two butterfly rotors, and four split-stator plates. This condenser has a high minimum capacitance and a small tuning range.

The construction of the buffer amplifier is quite similar to that of the oscillator. The buffer tuning condenser consists of a rotor having three butterfly plates and two stators each having two 90-degree plates. The grid circuit of the buffer is self-resonant, the tuning being adjusted by squeezing the turns of the grid coil  $L_2$  together, or prying them apart. The buffer

neutralizing condenser,  $C_7$ , mounted directly between the grid of the 6C4 and the lower set of stator plates of  $C_8$ , is a 3-30- $\mu$ fd. trimmer with the movable plate removed and a washer soldered under the head of the adjusting screw. The washer, by replacing the movable plate, reduces the capacitance of the condenser to a value suitable for neutralizing the 6C4. This capacitor may be conveniently adjusted through the open end of the chassis. Its location is clearly shown in Fig. 13-13.

The grid coil of the final amplifier also is resonant with the input capacitance of the 815, just as the buffer grid circuit is self-resonant. For best operation, the 815 requires neutralization at this frequency. The neutralizing "condensers,"  $C_9$  and  $C_{10}$  in the circuit diagram, are simply pieces of No. 14 wire extending from the grid of one section of the 815 to the vicinity of the plate of the other section. The wires are crossed at the bottom of the tube socket and go through Millen 32150 bushings in the metal partition. The screen and filament by-pass condensers are mounted so that the leads between the socket prongs and the nearest ground point are as short as possible. This wiring should be done before mounting the partition.

◆  
 Fig. 13-11 — A three-stage transmitter using a 6C4 master oscillator, 6C4 buffer amplifier, and 815 final amplifier for stabilized transmission in the 141-Mc. band. The oscillator and buffer are built as a unit on the folded-aluminum chassis at the right. The transmitter develops a carrier output of about 40 watts.  
 ◆

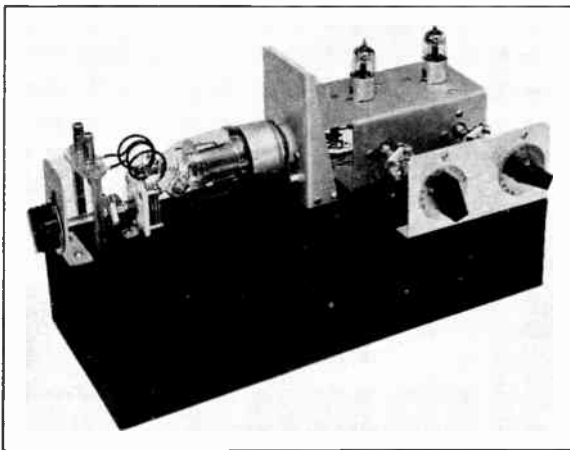

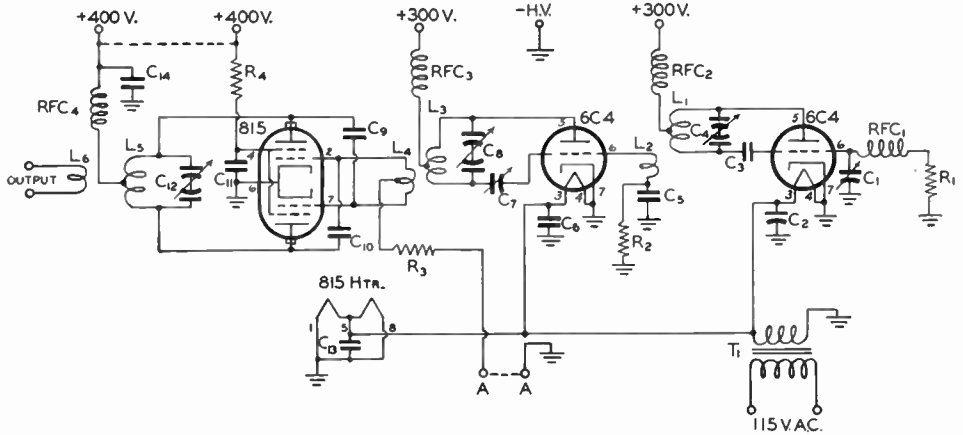


Fig. 13-12 — Circuit diagram of the stabilized 144-Mc. transmitter.

- C<sub>1</sub> — 3-30- $\mu$ fd. trimmer.
- C<sub>2</sub>, C<sub>6</sub>, C<sub>11</sub>, C<sub>13</sub> — 470- $\mu$ fd. midget mica.
- C<sub>3</sub>, C<sub>5</sub> — 47- $\mu$ fd. midget mica.
- C<sub>4</sub> — Oscillator tuning; Cardwell ER-14-BF/S1.
- C<sub>7</sub> — Neutralizing capacitor; see text.
- C<sub>8</sub> — Buffer tuning; Cardwell ER-6-BF/S.
- C<sub>9</sub>, C<sub>10</sub> — Amplifier neutralizing; see text.
- C<sub>12</sub> — Amplifier tuning; Cardwell ER-6-BF/S.
- C<sub>14</sub> — 100  $\mu$ fd., 2500 volts.
- R<sub>1</sub>, R<sub>2</sub> — 22,000 ohms, 1/2 watt.
- R<sub>3</sub> — 15,000 ohms, 1 watt.
- R<sub>4</sub> — 15,000 ohms, 10 watts.
- T<sub>1</sub> — 6.3-volt 2-amp. filament transformer.

- L<sub>1</sub> — 2 turns No. 12 bare wire; inside diameter 3/16 inch, length 1 inch; plate-supply tap at center.
- L<sub>2</sub> — 2 turns No. 14, inside diameter 1/2 inch; turns spaced wire diameter.
- L<sub>3</sub> — 4 turns No. 11, inside diameter 3/4 inch, length 1 inch; plate-supply tap at center.
- L<sub>4</sub> — 2 turns No. 14, inside diameter 1/2 inch; turns spaced diameter of wire; tapped at center.
- L<sub>5</sub> — 2 turns No. 12, inside diameter 1 inch, length 1 inch; plate-supply tap at center.
- L<sub>6</sub> — 2 turns No. 12, inside diameter 3/4 inch.
- RFC<sub>1</sub>, RFC<sub>2</sub>, RFC<sub>3</sub>, RFC<sub>4</sub> — 1-inch winding No. 21 d.s.c. on 1/4-inch diam. polystyrene rod.

The amplifier plate tank circuit uses a condenser of the same construction as that used in the buffer tank. It is mounted as closely as possible to the plate caps on the 815, and to preserve circuit symmetry the condenser is tuned from the left-hand edge of the chassis. If the transmitter is to be equipped with a regular panel this condenser may be operated by a right-angle drive from the front.


The output terminals are a standard binding-post assembly on polystyrene, mounted on metal posts 2 3/8 inches high to bring the coupling coil in proper relation to the amplifier plate tank coil, L<sub>5</sub>. Antenna coupling is ad-

justed by bending L<sub>6</sub> toward or away from L<sub>5</sub>.

The plate by-pass condenser and screen-dropping resistor are mounted underneath the chassis, as shown in Fig. 13-14, together with the filament transformer. Separate power-supply terminals are provided for the oscillator plate, buffer plate, amplifier grid (terminals A.A), amplifier screen, and amplifier plate so that the currents can be measured separately. An external 0-200 d.c. milliammeter will serve in making all adjustments. However, if a meter of lower range is available, it may be used profitably in the low-current circuits.

In putting the transmitter into operation,

Fig. 13-13 — A rear view of the three-stage 144-Mc. transmitter. The oscillator is at the left, with the buffer amplifier in the center. The 815 final is at the right.

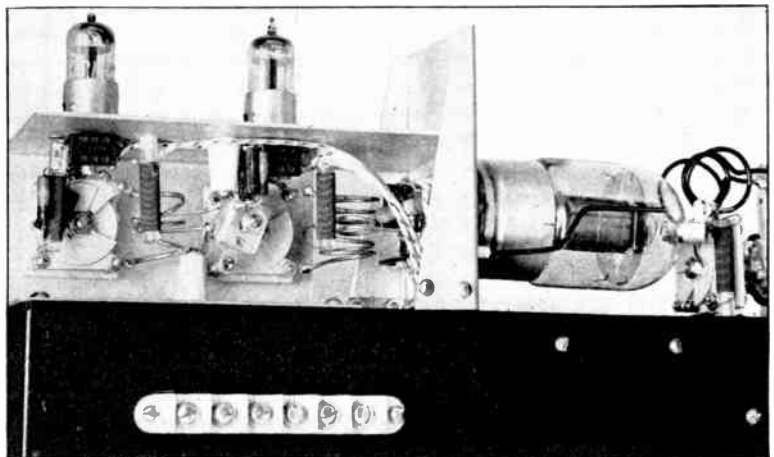

The first step is to adjust the frequency range of the oscillator, using Lecher wires or a calibrated absorption-type wavemeter. This should be done after  $C_1$  has been adjusted for maximum output. Then, using loose coupling between the buffer grid coil,  $L_2$ , and the oscillator tank coil,  $L_1$  (the coupling may be adjusted by bending  $L_2$  away from  $L_1$  on its mounting lugs), adjust  $L_2$  by changing the turn spacing until the grid circuit is resonant. Resonance will be indicated by maximum oscillator plate current; it can also be checked by measuring the voltage across the buffer grid leak,  $R_2$ , with a high-resistance voltmeter. The maximum voltmeter reading (about 40 volts) indicates resonance. The buffer should next be neutralized by varying the capacitance of  $C_7$  until there is no change in the voltage across  $R_2$  when the buffer tank condenser,  $C_8$ , is tuned through resonance. The point of correct neutralization also can be determined by coupling a sensitive absorption wavemeter such as is described in the chapter on Measuring Equipment to the buffer plate coil, and adjusting  $C_7$  for minimum reading. With this method, care must be used to avoid coupling between the wavemeter and the oscillator; link coupling between  $L_3$  and the wavemeter, with the latter far enough away so that it does not give a reading from the oscillator alone, should be used. Another method of checking neutralization is to adjust the turn spacing of the amplifier grid coil,  $L_4$ , to resonance and measure the 815 grid current (with no plate or screen voltage on the tube) and adjust  $C_7$  for zero grid current.

After the buffer is neutralized, plate voltage may be applied and  $C_8$  adjusted to resonance, as indicated by minimum plate current. If the coupling to the final amplifier is quite loose, the minimum plate current should be approximately 17 ma. The amplifier grid coil may next be resonated (by adjusting the spacing between turns) and the coupling increased until the maximum grid current is secured. The grid cur-

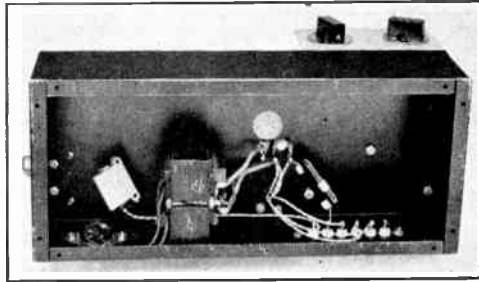


Fig. 13-14 — Underneath the chassis of the 144-Mc. MOPA transmitter. The filament transformer, amplifier plate by-pass condenser, and screen-dropping resistor are mounted here.

rent should be 4 milliamperes or more and the buffer plate current should rise to about 28 ma.

Neutralization of the 815 is the next step. The process is similar to that outlined for the 815 transmitter described at the beginning of the chapter. Plate and screen voltage may then be applied. With no load on the amplifier the plate current should dip to approximately 65 ma. at resonance. Loading the amplifier to a plate current of 150 ma. should not cause the grid current to drop below about 3.5 ma. A 40-watt lamp used as a dummy load should light to practically normal brightness at this input, using a plate-supply voltage of 400.

For greatest stability, the coupling between the oscillator and buffer should be as loose as possible. It is better to obtain the rated 815 grid current of 3 milliamperes by using tight coupling between the buffer and amplifier and loose coupling between the oscillator and buffer than vice versa. With normal operation the oscillator plate current should be approximately 25 ma. and the buffer plate current 28 ma., at 300 volts.

A modulator for the transmitter should have an audio output of 35 watts, using a coupling transformer designed to work into a 2500-ohm load. This transmitter is described in greater detail in *QST* for April, 1946.

## 144-Mc. Double Beam-Tetrode Power Amplifier

An amplifier set-up suitable for use with double beam-tetrode tubes is shown in Figs. 13-15, 13-16 and 13-17. The tube in the photographs is an 829, but an 815 or 832 can be used in the same layout. The only change that might be required would be in the inductances of the grid and plate coils,  $L_2$  and  $L_3$ ; these may have to be made slightly smaller or larger in diameter to compensate for the differences in input and output capacitances in the various types. The physical arrangement of the components is similar to that used for the 815 amplifier incorporated in the three-stage transmitter described above. When an 829 is used, the amplifier is well suited for use as an outboard unit with war-surplus transmitters such as the SCR-522.

The amplifier is built on an aluminum chassis formed by bending the long edges of a  $5 \times 10$ -inch piece of aluminum to form vertical lips  $\frac{3}{4}$  inch high, so that the top-of-chassis dimensions are  $3\frac{1}{2}$  by 10 inches. The tube socket is mounted on a vertical aluminum partition measuring  $3\frac{1}{2}$  inches high by  $3\frac{1}{4}$  inches wide on the flat face, with the sides bent as shown in the photographs to provide bracing. The partition is mounted to the chassis by right-angle brackets fastened to the sides. The socket is mounted with the cathode connection at the top, the cathode prong being directly grounded to the nearest mounting screw for the socket. The heater by-pass condenser,  $C_6$ , is mounted directly over the center of the tube socket, extending between the

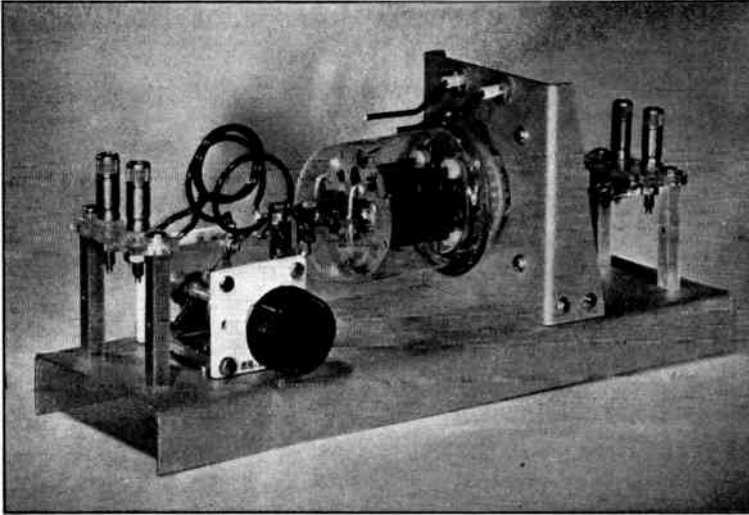


Fig. 13-15 — A 144-Mc. amplifier using a double beam tetrode. This type of construction is suitable for the 815 and 832 as well as the 829 shown. The vertical partition provides support for the tube as well as shielding between the input and output circuits. Note the neutralizing "condensers" formed by the wires near the tube plates.

paralleled heater prongs at the bottom and the cathode prong at the top. The screen by-pass is connected with short leads between the screen prong and the nearest socket screw.

The grid coil,  $L_2$ , is supported by the grid prongs on the socket. The two turns of the coil are spaced about one-half inch to allow room for the input coupling coil  $L_1$  to be inserted between them. The coupling is adjusted by bending  $L_1$  into or out of  $L_2$ . The grid tuning condenser,  $C_1$ , is mounted between the socket prongs; although the condenser has mica insulation it is used essentially as an air-dielectric condenser since the movable plate does not actually contact the mica at any setting inside the band. The coupling link is soldered to lugs under binding posts on a National FWG strip, the strip being mounted on metal pillars  $1\frac{1}{2}$  inches high to bring the link to the same height as the grid coil.

Although the shielding between the input and output circuits of the tube is sufficiently good so that the circuit will not self-oscillate, tuning of the plate circuit will react on the grid circuit to some extent because the grid-plate capacitance, while small, is not zero. To eliminate this reaction it is necessary to neutralize the tube. The neutralizing "condensers" are lengths of No. 12 wire soldered to the grid prongs on the socket. The wires are crossed over the socket and then go through small ceramic feed-throughs at the top of the vertical shield, projecting over the tube plates on the other side as shown in Fig. 13-15.

Connections between the plate tank condenser,  $C_7$ , and the tube plate terminals are made by means of small Fahnestock clips soldered to short lengths of flexible wire. The tank coil,  $L_3$ , is mounted on the same condenser

terminals to which the plate clips make connection. The output link,  $L_4$ , is mounted similarly to the grid link except that the posts are  $1\frac{1}{8}$  inches high. The plate choke,  $RFC_1$ , is mounted vertically on the chassis midway between the plate prongs of the tube, the mounting means being a short machine screw threaded into the end of the polystyrene rod. The "cold" lead of the choke is by-passed by  $C_5$  underneath the chassis.

Supply connections are made through a 5-post strip on the rear edge of the chassis. The dotted lines between connections in Fig. 13-16 indicate that these connections are normally short-circuited: leads are brought out so that the grid and screen currents can be measured separately.

In adjusting the amplifier, the plate and


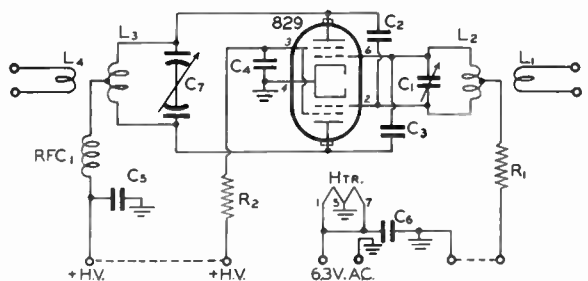


Fig. 13-16 — Circuit of the 829 amplifier for 144 Mc.

- $C_1$  — 3–30- $\mu$ fd. ceramic trimmer.
- $C_2, C_3$  — Neutralizing condensers; see text.
- $C_4$  — 500- $\mu$ fd. mica, 1000 volts.
- $C_5$  — 500- $\mu$ fd. mica, 2500 volts.
- $C_6$  — 470- $\mu$ fd. mica.
- $C_7$  — Split stator, 15  $\mu$ fd. per section (Cardwell ER-15-AD).
- $R_1$  — 4700 ohms, 1 watt.
- $R_2$  — 10,000 ohms, 10 watts.
- $L_1$  — 2 turns No. 12, diameter  $\frac{1}{2}$  inch.
- $L_2$  — 2 turns No. 12, diameter  $\frac{1}{2}$  inch, length  $\frac{1}{2}$  inch.
- $L_3$  — 2 turns No. 12, diameter  $1\frac{1}{8}$  inches, length 1 inch.
- $L_4$  — 2 turns No. 12, diameter 1 inch.
- $RFC_1$  — 1-inch winding of No. 24 d.s.e. or s.c.e. on  $\frac{1}{4}$ -inch diameter polystyrene rod.

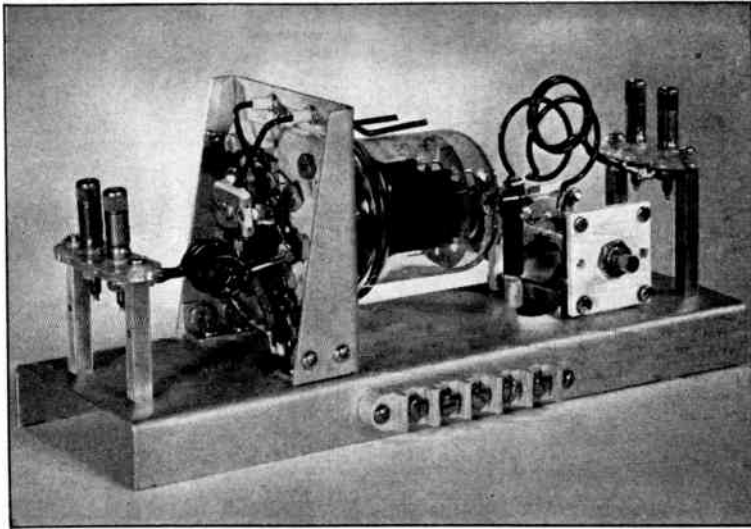

◆  
 Fig. 13-17 — Another view of the 144-Mc. amplifier. The neutralizing wires are crossed over the socket before going through the feed-through insulators. The input circuit is designed for link coupling to the driver stage.  
 ◆



screen voltages should be left off and the d.c. grid circuit closed through a milliammeter of 0-25 or 0-50 range. The driver should be coupled to the amplifier input circuit through a link (Amphenol Twin-Lead is suitable, because of its constant impedance and low r.f. losses). Use loose coupling between  $L_1$  and  $L_2$  at first, and adjust  $C_1$  to make the grid circuit resonate at the driver frequency, as indicated by maximum grid current. The coupling between  $L_1$  and  $L_2$  may then be increased to make the grid current slightly higher than the rated load value for the tube used — approximately 12 ma. for the 829. If the driver is an oscillator, the coupling between  $L_1$ - $L_2$  should be as loose as possible with proper grid current.

After neutralization, the procedure for which has been given in connection with other similar amplifiers, plate and screen voltage may be applied. If possible, the plate voltage should be low at first trial so there will be no danger of overloading the tube. Adjust  $C_7$  to resonance, as indicated by minimum plate current (this

should be measured independently of the screen); with the 829, the minimum plate current should be in the neighborhood of 80 milliamperes with 400 volts on the plate and no load on the circuit. A dummy load such as a 60-watt lamp should light to something near full brilliance when the coupling between  $L_3$  and  $L_4$  is adjusted to make the tube draw a plate current of 200 ma. When the loading is set, the grid current should be checked to make sure it is up to the rating for the tube. If it has decreased, the coupling between  $L_1$  and  $L_2$  should be increased to bring it back to normal.

Power-supply and modulator requirements will depend upon the particular tube used. For the 829, the plate supply should have an output voltage of 400 to 500 with a current capacity of 250 milliamperes. With a 400-volt supply the modulator power required is 50 watts, with an output transformer designed to work into a 1600-ohm load; with a 500-volt supply slightly over 60 watts of audio power is needed, the load being 2000 ohms.

## A Low-Cost 2-Meter Transmitter

Until very recently, most 144-Mc. stations employed simple transmitters of the modulated-oscillator type. Since the superregenerative receiver was also widely used, the instability of the transmitters was not a matter of great importance; but with the rapid swing to stabilized transmitters and selective receivers now in evidence, most of the modulated-oscillator signals are no longer readable. It is, however, still possible, by careful design and proper operation, to use the simple and economical oscillator rig and yet radiate a signal that can be copied on all but the most selective receivers. Such a transmitter is shown in Figs. 13-18, 13-21 and 13-22.

### Oscillator Ills and Their Treatment

There are two principal faults in most simple 2-meter transmitters. Many use filament tubes with a.c. applied to the filaments, causing severe hum modulation. Others, through poor design, have insufficient feed-back (as evidenced by low grid current) so that they are unable to sustain strong oscillation under load. Lack of sufficient excitation also renders them incapable of maintaining oscillation at low plate voltages, causing them to go out of oscillation over a considerable portion of the modulation cycle. Such oscillators suffer from extreme frequency modulation, making their signals unreadable on all but the very broadest



**Fig. 13-18** — Front view of the simple 144-Mc. transmitter. The jacks at each side of the antenna terminals are for insertion of a meter in the oscillator grid (left) and plate (right) circuits. The microphone jack is at the lower left and the on-off switch is at the right. The calibration scale is drawn with India ink on heavy white paper.

oscillator, employing the familiar "unity-coupled" circuit. This arrangement, wherein the grid coil is fed through the inside of a plate tank made of copper tubing, provides adequate excitation. Stability over wide ranges of plate voltage is quite good, and the degree of frequency modulation is not too severe if the modulation is held to 75 per cent or less. It is laid out so that it is stable mechanically, reducing possible frequency changes from vibration.


**Mechanical Details**

The transmitter is designed for use with a plate supply of 250 to 300 volts, making it useful for

receivers, and even on these the quality is poor indeed.

No simple transmitter can hope to overcome these faults entirely, but they are materially reduced in the rig described herewith. A.c. hum modulation is reduced through the use of indirectly-heated tubes; and stability is improved through the use of a high-C push-pull

mobile or low-powered home-station operation. It employs a pair of 2C22 tubes (also known as 7193s) as oscillators, a 6V6GT modulator, and a 6C4 as a speech amplifier and source of microphone voltage. It is housed in a standard 5 x 6 x 8-inch utility cabinet, the back and front of which are removable. The schematic diagram is shown in Fig. 13-19.

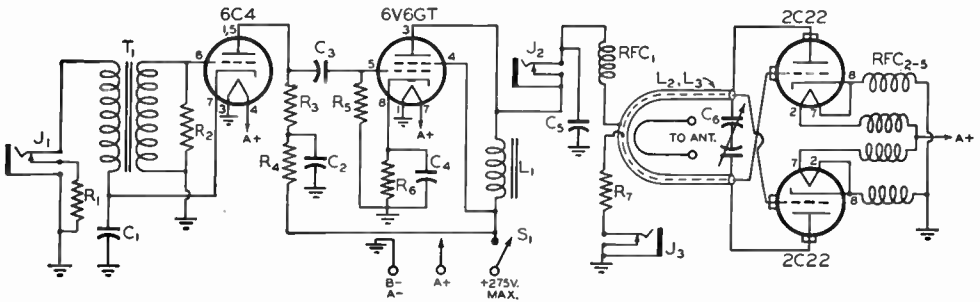

**Fig. 13-19** — Schematic diagram of the simple 144-Mc. transmitter.

- C<sub>1</sub>, C<sub>4</sub> — 10-μfd. 25-volt electrolytic.
- C<sub>2</sub> — 8-μfd. 450-volt electrolytic.
- C<sub>3</sub>, C<sub>5</sub> — 0.01-μfd. 600-volt paper.
- C<sub>6</sub> — "Butterfly" variable (Cardwell ER-14-BF/S modified; see text).
- R<sub>1</sub> — 470 ohms, 1 watt.
- R<sub>2</sub> — 0.33 megohm, ½ watt.
- R<sub>3</sub>, R<sub>4</sub> — 5000 ohms, 5 watts.
- R<sub>5</sub> — 0.47 megohm, ½ watt.
- R<sub>6</sub> — 680 ohms, 1 watt.
- R<sub>7</sub> — 10,000 ohms, 1 watt.

- L<sub>1</sub> — Midget filter choke.
- L<sub>2</sub>, L<sub>3</sub> — Unity-coupled grid and plate coils. See text and Fig. 13-20.
- J<sub>1</sub>, J<sub>2</sub>, J<sub>3</sub> — Closed-circuit jack.
- RFC<sub>1</sub> — No. 28 d.s.c. wire, close-wound on 1-watt resistor, ¼-inch diam., ⅝ inch long.
- RFC<sub>2</sub>, RFC<sub>3</sub>, RFC<sub>4</sub>, RFC<sub>5</sub> — 20 turns No. 20 d.s.c. wire close-wound on ¼-inch polystyrene rod.
- S<sub>1</sub> — S.p.s.t. toggle switch.
- T<sub>1</sub> — Single-button microphone transformer (UTC "Ouncer" — surplus).

The plate tank "coil" is made of  $\frac{3}{16}$ -inch copper tubing, bent into a "U" which is two inches long overall. The ends of the "U" are made into spade lugs, as shown in Fig. 13-20, the slotted ends providing a small range of inductance adjustment. The lug ends are fastened directly to two of the stator terminals of the butterfly-type tank condenser,  $C_6$ . Part of the "U" is cut out at the curved end, to provide an opening for the center-tap of the

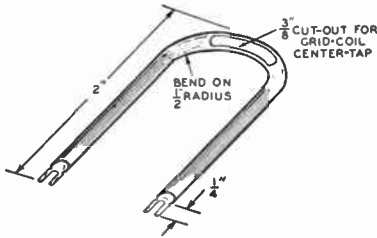


Fig. 13-20 — Detail drawing of the oscillator plate inductance. It is made from  $\frac{3}{16}$ -inch copper tubing, bent into a "U" shape. Ends of the "U" are formed into spade lugs, the slots in which provide a means of slight inductance adjustment. It is mounted directly on the stator terminals of the tuning condenser.


grid coil. An easy way to make the grid coil is to cut two pieces of flexible insulated wire, about four inches long, and feed them into the "U" through the center opening. The protruding tap, made by twisting the ends of the wires

together, should be coated with household cement after the grid resistor has been soldered to it. Note that the grid leads are transposed. The 2C22s will not oscillate if these are improperly connected. The plate leads may be made of  $\frac{1}{4}$ -inch copper braid, or copper or silver ribbon is even better, if available. If braid is used, it may be made solid at the end by flowing solder over the last half inch, after which it may be drilled, to pass the stator terminal screw.

Provision is made for reading both grid and plate current to the oscillator, two meter jacks being mounted on either side of the plate tank. Their terminals make convenient mounting places for  $R_7$  and  $RFC_1$ . Note that the jacks are connected so that the meter leads need not be reversed when changing from one jack to the other. The plate-meter jack must, of course, be insulated from the metal panel.

No battery is required for microphone current, this being obtained by running the cathode current of the 6C4 speech amplifier through the microphone transformer. The 6C4 cathode is by-passed with a large electrolytic condenser, and the plate is decoupled and by-passed to reduce hum. Since the 6C4 stage is used principally as a source of microphone current, resistance coupling to the 6V6GT modulator gives adequate drive. No gain control is included, as the full output of the modulator is insufficient for overmodulation.

Fig 13-21 — Back view of the 2-meter transmitter, showing the symmetrical arrangement of components. Note that the "U"-shaped tank inductance is mounted directly on the stator terminals of the butterfly tuning condenser.

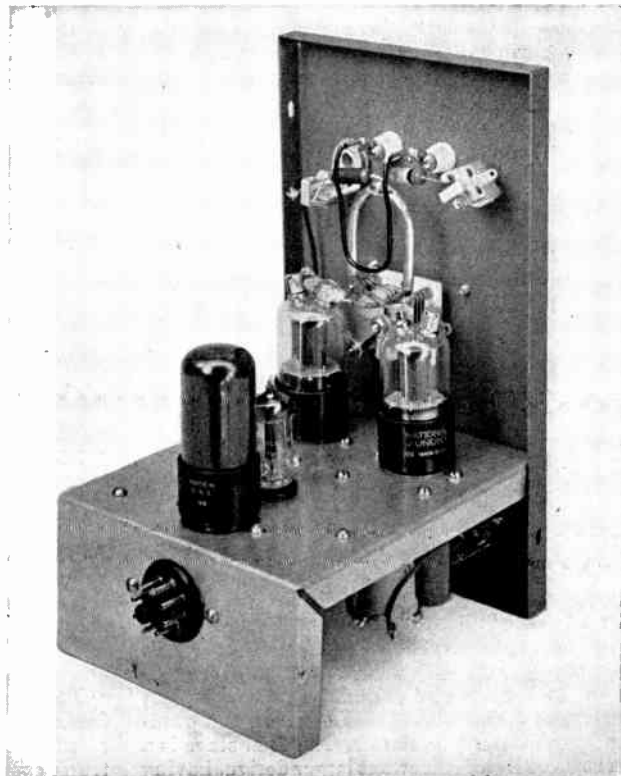

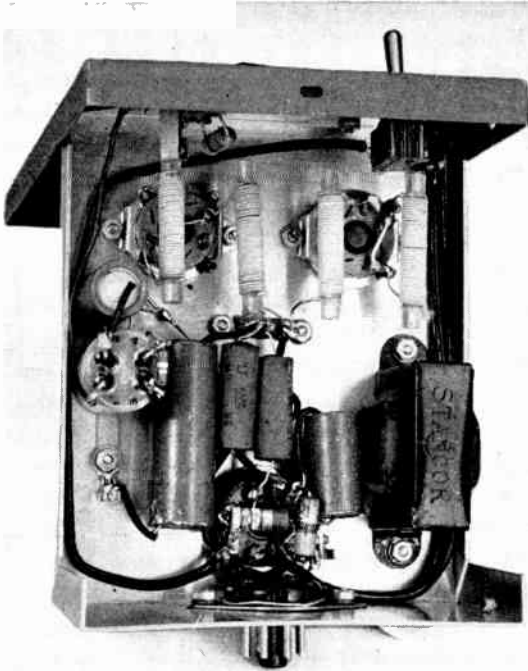


Fig. 13-22 — Under-chassis view shows the four heater chokes and audio components. The small round object, left center, is the microphone transformer, a surplus midget unit. The audio choke is at the right.

#### Testing

Since the grid is the controlling element in the operation of any Class C stage, it is important that the grid current be observed in adjust-

ing the oscillator. The plate current may be almost meaningless, as an indication of the proper functioning of such a stage, but the grid current shows plainly if the oscillator is functioning correctly. If the grid current and bias are normal for the tubes used, the plate current can be ignored, except to see that the input is not excessive. Grid current in this oscillator should run about 8 ma. when a plate voltage of 275 or so is used and the oscillator is loaded by a lamp or antenna. The "U"-shaped antenna-coupling loop should be adjusted until the grid current is approximately this value. The plate current will be about 60 ma. with 275 volts on the plates.

The transmitter frequency should be checked with Lecher wires, or by listening to the signal in a calibrated receiver. In either case there should be a load across the antenna terminals, as the frequency may be appreciably different between loaded and unloaded operation.

The rough calibration scale shown was first roughed on a white card using pencil, and afterward drawn over in India ink. The calibration card is glued to the panel, and further held in place by the condenser mounting nut and two small machine screws.

## Mobile Transmitters

In most respects, gear designed for mobile operation is similar to that used for home-station service, except for the additional considerations imposed by space and current-drain limitations and the need to withstand constant vibration. Though there are various types of power supplies capable of delivering more power, the most satisfactory arrangement for most mobile installations is the generator or vibrator supply that furnishes 300 volts at

100 to 150 ma. This power is within the capability of the average family-car battery, making unnecessary the separate batteries and special generators usually needed when higher-powered systems are employed. The transmitters described below are designed for 300-volt service, though in several instances they may be modified readily for use at higher power levels, if the car battery and generator will handle the extra load imposed.

### A Mobile Transmitter for 50 and 28 Mc.


Low over-all battery drain in mobile operation is best obtained through the use of filament-type tubes which are lighted only during transmission periods. The mobile unit for 6, 10 and 11 meters, shown in Figs. 13-23-13-27, employs filament-type beam tetrodes throughout. Five 2E30s are used, as crystal oscillator, frequency multiplier, Class A driver, and push-pull Class AB modulators. The final stage is a 2E25, a tube of somewhat larger design, having

its plate connection at the top of the envelope. Total filament current is only 4.3 amperes, and there is no drain whatever when the rig is not actually on the air.
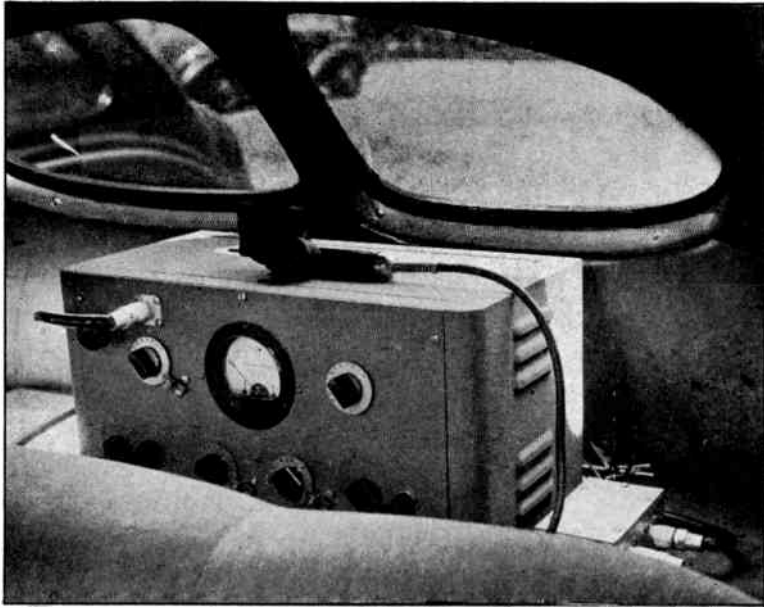
#### Mechanical Details

The transmitter is housed in a crackle-finished cabinet which may be mounted in back of the seat in coupé-type vehicles or in the trunk compartment of sedans.

◆  
 Fig. 13-23 — A typical installation of the 6- and 10-meter mobile transmitter. The small aluminum box at the right of the unit houses the antenna change-over relay. The genemotor and its starting relay are mounted under the hood, adjacent to the car battery. Operation of the transmitter is controlled entirely by the push-to-talk switch on the hand microphone.  
 ◆




Special attention is paid to ruggedness of construction, all leads being made as short and direct as possible. Small components are supported with terminal strips at each end where possible, and tuning controls are equipped with dial locks (National ODL). The meter (a Marion 0-10-ma. sealed unit) is back-of-panel mounted, with a sheet of Lucite serving as a protecting window. This method of mounting the meter, about 1/2 inch in back of the panel, also provides a convenient method for illuminating the meter face. Dial lights are mounted at either side of the meter, as shown in Figs. 13-24 and 13-26.

By using 100- $\mu$ fd. variable condensers for  $C_2$  and  $C_3$ , the range of the oscillator and multiplier plate circuits is extended, so that it is unnecessary to change these coils in changing bands. Only the crystal and the final plate coil,

$L_5$ , need be changed. Complete push-to-talk operation is made possible through the use of two relays.  $Ry_1$  starts the genemotor and applies the filament voltage to the transmitter.  $Ry_2$  transfers the antenna from receiver to transmitter. Both are controlled by the switch on the microphone, which may be any single-button type that has a control switch. The Army T-17-B, now currently available as government surplus, is shown with the rig.

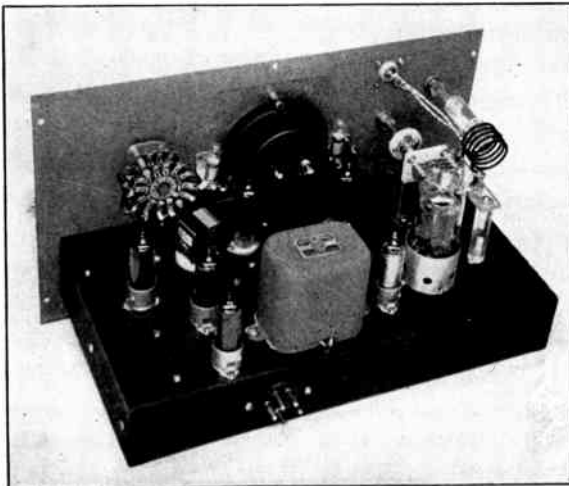**The Circuit**

The crystal oscillator is a Tri-tet, modified for filament-type tubes. Interwound coils are inserted in the filament leads, and one of these is tuned. The setting of this adjustment is not critical and may be left near maximum setting, for both 7- and 8.4-Mc. crystals. The oscillator doubles in its plate circuit for both bands.



◆  
 Fig. 13-24 — The plate circuit of the final stage of the mobile transmitter is the only r.f. circuit above the chassis. The three tubes at the left are the driver and audio stages, with the oscillator and multiplier tubes directly in back of the meter. The tube to the right of the modulation transformer is the 0A2 voltage regulator. Chassis size is 7 x 13 x 2 inches.  
 ◆

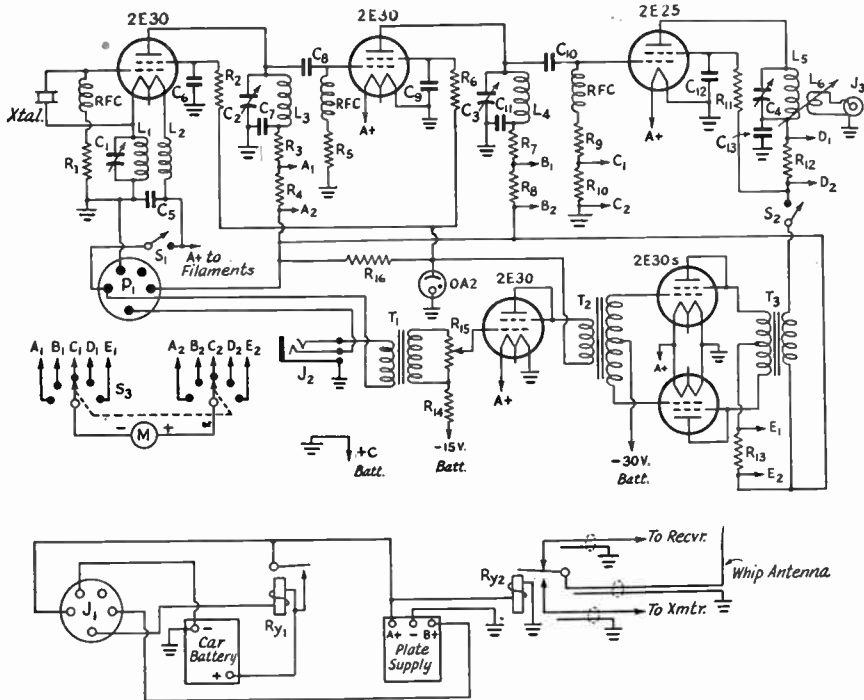


Fig. 13-25 — Wiring diagram of the mobile rig for 6 and 10 meters.

- C<sub>1</sub> — 100- $\mu$ fd. midget, screwdriver-adjustment type (Hammarlund APC-100).
- C<sub>2</sub>, C<sub>3</sub> — 100- $\mu$ fd. midget, shaft type (Hammarlund HF-100).
- C<sub>4</sub> — 15  $\mu$ fd., double spaced (Hammarlund HFA-15-F).
- C<sub>5</sub> — 0.001- $\mu$ fd. mica.
- C<sub>6</sub>, C<sub>7</sub>, C<sub>8</sub>, C<sub>11</sub>, C<sub>12</sub>, C<sub>13</sub> — 170- $\mu$ fd. midget mica.
- C<sub>9</sub>, C<sub>10</sub> — 100- $\mu$ fd. midget mica.
- R<sub>1</sub> — 82,000 ohms, 1 watt.
- R<sub>2</sub>, R<sub>6</sub> — 1000 ohms, 1/2 watt.
- R<sub>3</sub>, R<sub>7</sub>, R<sub>10</sub> — 100 ohms, 1/2 watt.
- R<sub>4</sub>, R<sub>8</sub>, R<sub>12</sub>, R<sub>13</sub> — Special shunts. (See text.)
- R<sub>5</sub> — 150,000 ohms, 1 watt.
- R<sub>9</sub> — 33,000 ohms, 1 watt.
- R<sub>11</sub>, R<sub>16</sub> — 5000 ohms, 10 watts.
- R<sub>14</sub> — 10,000 ohms, 1/2 watt.
- R<sub>15</sub> — 0.5-megohm potentiometer.
- L<sub>1</sub>, L<sub>2</sub> — 7 turns each, No. 20 d.c.c., 3/8 inch long on 1-inch dia. form, windings interwound.
- L<sub>3</sub> — 10 turns No. 12 enam., close-wound on 1-inch diam. form.

- L<sub>4</sub> — 6 turns No. 12 enam., 3/4 inch long, 1/2-inch inside diam., self-supporting.
- L<sub>5</sub> — 28 Mc.: 10 turns No. 12 enam., 1 1/2 inches long, 1-inch inside diam., self-supporting.  
50 Mc.: 5 turns No. 12 enam., 1 inch long, 1-inch inside diam., self-supporting.
- L<sub>6</sub> — 3 turns on 1/2-inch polystyrene rod — see text and detail photo.
- J<sub>1</sub> — Socket on power cable, 5 prong.
- J<sub>2</sub> — Double-button microphone jack. If T-17-B microphone is used, a special jack designed for this microphone must be obtained.
- J<sub>3</sub> — Coaxial fitting (Amphenol 83-1R. Matching plug is 83-1SPN).
- M — 0-10-ma. scaled unit (Marion).
- P<sub>1</sub> — Power plug on transmitter chassis.
- RFC — 2.5-mh. r.f. choke, National R-100.
- R<sub>y1</sub>, R<sub>y2</sub> — See text.
- S<sub>1</sub>, S<sub>2</sub> — S.p.s.t. snap switch.
- S<sub>3</sub> — 2-section 5-position wafer type switch.
- T<sub>1</sub> — Single-button microphonic transformer.
- T<sub>2</sub> — Driver transformer (Stancor A-4752).
- T<sub>3</sub> — Modulation transformer (UTC S-18).

The stage following the oscillator is operated as a doubler for 27- and 28-Mc. work, and as a tripler for 50 Mc. The 2E30 is an effective frequency multiplier, and there is adequate excitation for the final in either case. Screen voltage on the exciter stages is stabilized with a miniature voltage-regulator tube, an OA2. With a screen voltage of 150, the plate input to both 2E30s is held to about 6 watts per tube.

The final stage uses a 2E25, whose top-cap plate connection permits the mounting of the plate circuit above the chassis, well isolated from the other tuned circuits. A small shield, cut from an old-style tube shield to a length of about one inch, comes up to the bottom of

the 2E25 plate assembly. These precautions are sufficient to provide completely-stable operation without neutralization.

The antenna coupling coil, L<sub>6</sub>, is wound on a short length of polystyrene rod 1/2 inch in diameter, into which is inserted a 1/4-inch rod of the same material. This shaft projects through the front panel, where a shaft-locking panel bushing (Bud PB-532 bushing, Millen 10061 shaft lock) holds it in the desired position. Coupling is adjusted by pushing or pulling the knob affixed to the shaft, following which the bushing may be tightened for permanent setting. The bushing may also be set finger-tight, allowing the coupling to be ad-

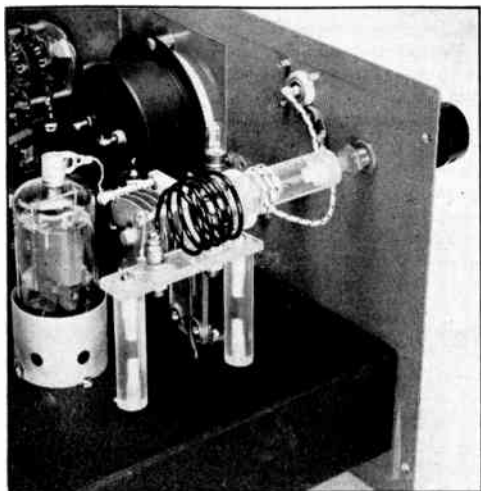


Fig. 13-26 — Detail photo of the 2E25 final stage, showing method of coupling to the antenna. The coupling coil, wound on a polystyrene rod, is adjustable from the front panel. The plate coil is mounted by means of G.R. plugs.

justed, yet holding it with sufficient firmness to prevent its being jarred out of position.

Three 2E30s are used for the modulator, one as a Class A driver and two in push-pull as Class AB modulators. All three are triode-connected. Bias is supplied by a 30-volt hearing-aid battery, which can be tapped at 15 volts by opening up the cardboard case and soldering on a lead at the point where the two 15-volt sections are joined together. This lead is brought out to the unused terminal on the battery socket and plug.

Metering of all circuits is provided by a 10-ma. meter, a 2-section 5-position switch, and a set of shunts. The shunts are made from small 100-ohm resistors, on which is wound about 7 feet of No. 30 enameled wire. The shunts should be wound with an excess of wire, the length of which may be reduced until the multiplication of the meter scale is just right. The resistor  $R_{10}$  in the final grid circuit is left without a shunt, giving direct reading on the 10-ma. scale for measuring the final grid current.

◆

Fig. 13-27 — Bottom view of the mobile rig. At the left center are the interwound coil and tuning condenser which are part of the oscillator filament circuit. Audio components are at the left, with oscillator and multiplier plate circuits near the front panel.

◆

### Testing


Except for the speech stages, the unit may be tested using 6.3 volts a.c. on the filaments and an a.c. power supply. A storage battery must be used for filament supply when the speech equipment is to be tested, as a.c. on the filaments will produce excessive hum. Initial testing should be carried on with about 200 volts on the tube plates. When operation has been found to be satisfactory, this may be raised to 300.

To place the unit in operation, set  $S_1$  to the "on" position, leaving  $S_2$  "off." With the meter switch in position *A*, apply plate voltage and note meter reading, which is the oscillator plate current. This will be about 20 ma., dipping slightly at resonance as  $C_2$  is adjusted. Next switch to position *B* and adjust  $C_3$ . The dip here may not be as pronounced as in the oscillator, and the final grid current, position *C*, 10-ma. scale, is the best indication of resonance in the preceding adjustments. This reading should be about 4 ma., dropping to 3 ma. under load. With  $S_2$  turned on, the final plate current, position *D*, should drop to below 10 ma. at resonance, and coupling of the antenna should raise it to 50 to 60 ma. Modulator plate current will be about 20 ma., rising to 60 ma. or more on audio peaks. No metering position is provided for the Class A driver current, but this should be approximately 10 ma.

With the coil and condenser values given, it is impossible to get output from the final stage on a wrong frequency, but excitation to the final may be obtained on incorrect harmonics; hence it is advisable to check the frequency of each stage with a calibrated absorption-type wavemeter.
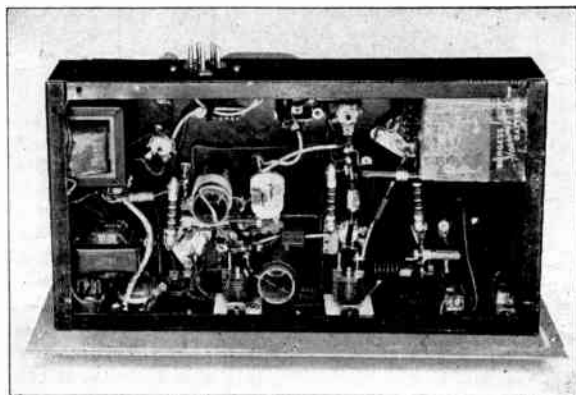
### Installation

For maximum convenience, the same antenna should be used for both transmission and reception. Antenna change-over is handled with a conventional 6-volt antenna relay which is mounted in a small box made up for the purpose from folded sheet aluminum. Amphenol coaxial fittings, mounted on the sides



of the relay box as close to the relay contacts as possible, provide for connection to the transmitter, the receiver, and the antenna by means of coaxial line. The relay case is grounded and only the inner conductor of the coaxial line is switched.

A headlight relay for genemotor starting may be purchased from any auto-accessory store, and this and the genemotor should be mounted as close to the car battery as possible, in order to minimize voltage drop. Battery wiring and filament cables should be as heavy

wire as possible, with No. 12 as the minimum for the genemotor leads.

For actual mobile operation, the quarter-wave telescoping "whip" antenna, operating as a<sup>1</sup> Marconi in the manner shown in Fig. 14-11, is convenient. Much greater range in stationary operation from high locations may be had with half-wave radiators or multielement arrays, either of which may be arranged for easy on-the-spot assembly. An example of such a portable array for 50 Mc. is shown in Fig. 14-12, Chapter Fourteen.

## Mobile Transmitter for 144-Mc.

A crystal-controlled transmitter designed for mobile operation on 2 meters is shown in Figs. 13-28 through 13-31. It includes a modulator and will handle 15 watts input when used with a 300-volt power supply.

The circuit diagram of the transmitter, Fig. 13-29, shows a Type 6V6GT tube used in a Tri-tet oscillator, with a 24-Mc. crystal. The oscillator has a fixed-tuned cathode circuit and a self-resonant plate tank coil that tunes to 48 Mc. A series-dropping resistor,  $R_2$ , maintains the screen voltage at the proper level, when a 300-volt supply is used. The oscillator, like the other stages of the transmitter, includes a

jack wired in the cathode lead for metering purposes.

A 7F8 dual triode serves as a push-pull tripler to 144 Mc. The tripler grid coil,  $L_3$ , is tuned by the trimmer condenser,  $C_1$ , and its plate coil,  $L_4$ , is self-resonant. Cathode bias, developed across  $R_4$ , prevents excessive plate current flow during off-resonant adjustment of either the oscillator or the tripler circuits.

The final stage employs an 832A dual tetrode as a neutralized amplifier on 144 Mc. Grid bias is developed by the flow of grid current through resistor  $R_5$ . If desired, protective bias can be used by decreasing the value of  $R_5$  and by connecting a battery in series with the grid resistor.

A small amount of neutralization was required to assure completely-stable operation. The neutralizing condensers,  $C_{11}$  and  $C_{12}$  in the circuit diagram, are pieces of No. 12 wire extending from the grid of one section of the 832A to the vicinity of the plate of the other section. The wires are crossed at the bottom of the tube socket and go through Millen 32150 bushings mounted in the chassis between the 7F8 and the 832A sockets. It is possible that use of a shielded tube socket would eliminate the tendency toward oscillation in the 832A.

A series-tuned antenna circuit, consisting of  $C_3$  and  $L_7$ , is intended for use with any of the low-impedance antenna feed systems commonly used for mobile work. The amount of loading is adjusted by varying the position of the pick-up link,  $L_7$ .

The modulator employs a pair of 6V6 tubes working Class AB. A speech-amplifier stage is not required as long as a single-button carbon microphone is used. Voltage for the microphone is taken from the junction of the two cathode-biasing resistors,  $R_7$  and  $R_8$ , thus eliminating the need for a microphone battery.

The microphone and modulation transformers used are both large and expensive for the job at hand and were used only because they happened to be available. The microphone transformer can be any single-button-microphone-to-push-pull-grids transformer and the modulation transformer need not be rated at more than 10 watts. It should be capable of matching a pair of 6V6 tubes to an r.f. load of

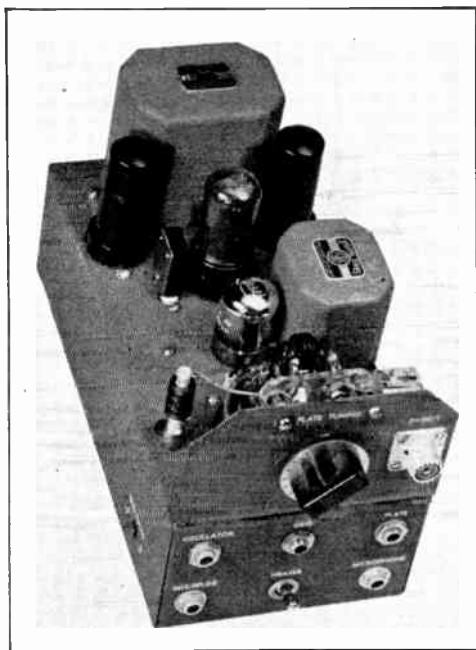


Fig. 13-28 — Crystal-controlled transmitter for 144-Mc. mobile use. The amplifier plate tuning condenser and the antenna jack are mounted on the front panel along with the pick-up link assembly and the antenna trimmer condenser. The microphone jack, the metering jacks, and the filament on-off switch are mounted on the front wall of the chassis. A hole to permit screwdriver adjustment of the amplifier grid condenser is located at the left side of the chassis.



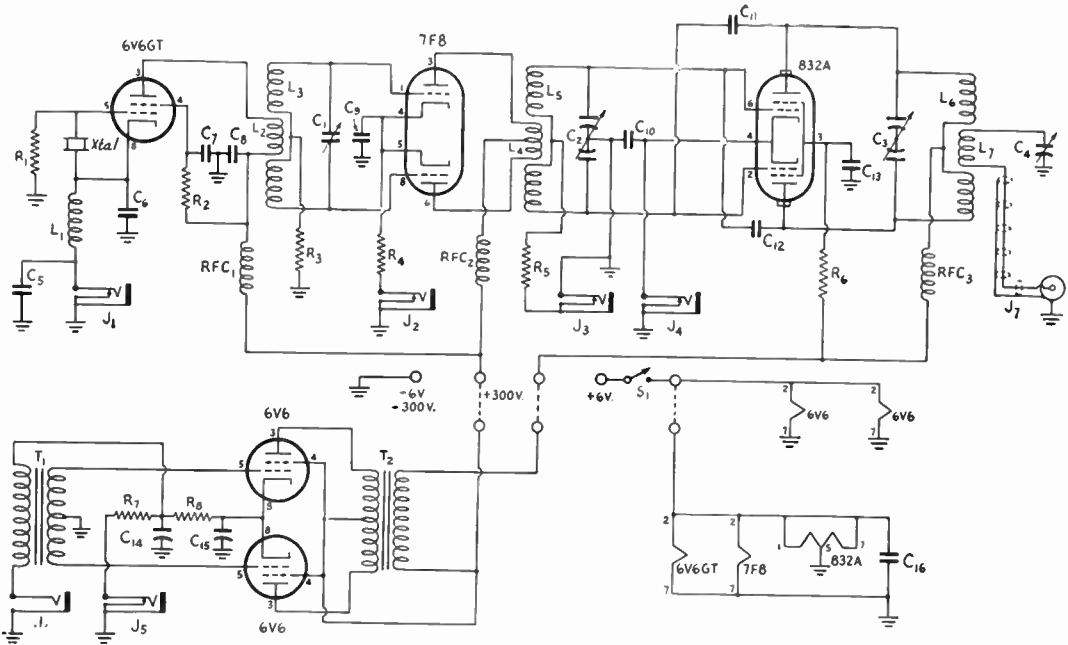


Fig. 13-29 — Circuit diagram of the mobile transmitter for 144 Mc.

- C<sub>1</sub>, C<sub>4</sub> — 3-30- $\mu$ fd. mica trimmer.
- C<sub>2</sub> — 15- $\mu$ fd. per-section split stator (Bud LC-1660).
- C<sub>3</sub> — "Butterfly" condenser, 6  $\mu$ fd. per section (Cardwell ER-6-BF/S).
- C<sub>5</sub>, C<sub>7</sub>, C<sub>8</sub> — 0.0047- $\mu$ fd. mica.
- C<sub>6</sub> — 100- $\mu$ fd. midget mica.
- C<sub>9</sub>, C<sub>10</sub>, C<sub>13</sub>, C<sub>16</sub> — 470- $\mu$ fd. midget mica.
- C<sub>11</sub>, C<sub>12</sub> — Neutralizing wires. (See text.)
- C<sub>14</sub>, C<sub>15</sub> — 10- $\mu$ fd. 25-volt electrolytic.
- R<sub>1</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.
- R<sub>2</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 33,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>4</sub> — 470 ohms,  $\frac{1}{2}$  watt.
- R<sub>5</sub> — 22,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>6</sub> — 25,000 ohms, 10 watts.
- R<sub>7</sub> — 100 ohms, 1 watt.
- R<sub>8</sub> — 150 ohms, 1 watt.
- L<sub>1</sub> — 3 turns No. 18 enam., close-wound,  $\frac{1}{2}$ -inch diam.
- L<sub>2</sub> — 4 turns No. 18 enam.,  $\frac{3}{8}$  inch long.
- L<sub>3</sub> — 10 turns No. 18 enam.; coil wound in two sections with 5 turns each side of L<sub>2</sub>, each section  $\frac{3}{8}$  inch long. A  $\frac{1}{2}$  inch is left between windings.

- Form for L<sub>2</sub>L<sub>3</sub> is a Millen 30003 Quartz-Q stand-off insulator,  $\frac{3}{4}$ -inch diam.
- L<sub>4</sub> — 3 turns No. 18 enam.,  $\frac{1}{2}$  inch long,  $9/16$ -inch diameter.
- L<sub>5</sub> — 2 turns No. 18 enam., interwound with turns of L<sub>4</sub>. L<sub>4</sub> and L<sub>5</sub> are wound on a National PRE-3 coil form.
- L<sub>6</sub> — 4 turns No. 12 enam.,  $\frac{1}{2}$ -inch i.d., wound in two sections with 2 turns each side of center-tap and a  $\frac{1}{2}$ -inch space at the center, turns spaced wire diameter.
- L<sub>7</sub> — 3 turns No. 12 enam.,  $\frac{1}{2}$ -inch diam., turns spaced wire diameter.
- J<sub>1</sub>-J<sub>5</sub> — Closed-circuit jack.
- J<sub>6</sub> — Open-circuit jack.
- J<sub>7</sub> — Coaxial-cable connector.
- RFC<sub>1</sub>, RFC<sub>2</sub> — 300- $\mu$ h. r.f. choke (Millen 31300).
- RFC<sub>3</sub> — 2.5-mh. r.f. choke (Millen 31102).
- S<sub>1</sub> — S.p.s.t. toggle.
- T<sub>1</sub> — Single-button microphone transformer (UTC S-7).
- T<sub>2</sub> — Modulation transformer (UTC S-19).


5000 to 7000 ohms, depending upon the input at which the 832A is operated.

It will be noticed that the modulator input and output connections are not wired directly into the transmitter proper and that separate terminal blocks are used for the r.f. and audio sections. When the modulator is used with the 144-Mc. transmitter, jumper connections are made between the two sets of terminals as shown by the circuit diagram. Removal of the jumpers will allow the modulator to be used with another transmitter, which might very well be the 50-Mc. rig shown in Figs. 13-32 to 13-35. S<sub>1</sub>, the filament switch, will open and close the modulator- and r.f.-section filament circuits when the jumper connections are made, and will operate with the modulator alone when the jumpers are removed.

The photographs of the transmitter show

how the parts are mounted on a metal chassis measuring 3 x 5 x 10 inches. The front panel measures 3 x 5 inches and has a  $\frac{1}{2}$ -inch lip for fastening to the chassis. The construction of the antenna assembly and the method of mounting the components on the panel are identical to the 50-Mc. transmitter. A recommended system of mounting the 832A tube socket is also detailed in the text referring to the 50-Mc. unit.


No special care need be given to the wiring of the audio circuit, but the r.f. leads should be kept as short as possible. The use of four tie-point strips will simplify the mounting and wiring of parts. A single tie-point is mounted to the rear of the oscillator tube socket and is used as the junction of R<sub>7</sub>, R<sub>8</sub>, C<sub>14</sub> and the primary lead of the microphone transformer. A double tie-point strip is mounted to the right

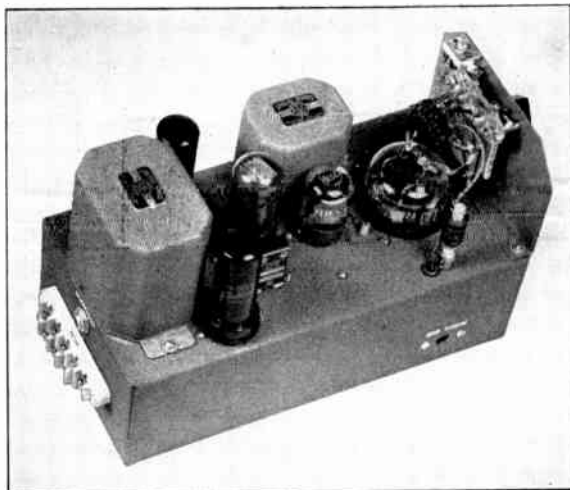

*Fig. 13-30* — A top view of the mobile transmitter. The modulation transformer and the modulator tubes are at the left end of the chassis. The 6V6GT crystal oscillator, the 7F8 frequency multiplier, and the 832A amplifier are in line along the center of the chassis. The microphone transformer is in back of the 7F8.  $J_5$ , the modulator metering jack, is mounted on the rear wall of the chassis just above the terminal strips.

of the crystal socket (as seen in Fig. 13-31); one lug is used as the connecting point for the positive high-voltage lead and the bottom ends of  $RFC_1$  and  $RFC_2$ ; the bottom of  $L_1$  and the top ends of  $C_5$  and  $J_1$  are connected to the second terminal. The cathode end of  $L_1$  is connected to the cathode side of the crystal socket. The third tie-point strip is mounted on the 832A tube socket and serves as the connecting point between  $R_4$  and  $J_2$ ; the bottom end of  $R_6$  connects to the high-voltage lead at the second lug. The fourth strip (single lug) is mounted on the frame of  $C_2$  and the leads between  $R_5$  and  $J_3$  join at this point.

The construction of the driver-stage coils is not difficult if the coil forms are properly prepared in advance. A study of Fig. 13-31 will show how the windings are placed on the forms, and the lengths of the windings are given in the parts list. The forms should be marked and drilled to accommodate the windings with the holes for the ends of the windings passing directly through the forms.  $L_3$  should be wound in two sections with the inside ends being soldered together after the winding of  $L_2$  has been completed. The center-taps for  $L_4$  and  $L_5$  are made by cleaning and twisting the wire at the center of each winding. Condenser  $C_1$  is soldered across the grid ends of  $L_3$  before the coil is connected to the tube socket.

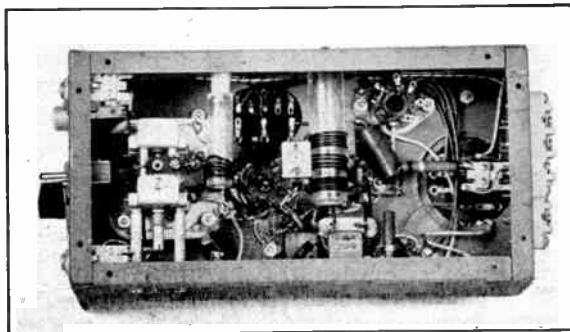

*Fig. 13-31* — Bottom view of the 144-Mc. transmitter. The coil forms for  $L_2$ ,  $L_3$  and  $L_4$ ,  $L_5$  are mounted on the side wall of the chassis; the form for  $L_4$ ,  $L_5$  is mounted on a small stand-off insulator so that the windings can be brought out to the center line of the chassis.  $C_1$ , the grid condenser for the frequency multiplier, is soldered across the grid ends of  $L_3$ . The amplifier grid tuning condenser,  $C_2$ , is mounted on metal pillars having a length of  $1\frac{5}{8}$  inches.

### Adjustment and Testing

When testing the transmitter, it is advisable to start with the high voltage applied to the first two stages only. With a 100-ma. meter plugged in  $J_1$  the oscillator cathode current at resonance should be approximately 30 ma. A low-range milliammeter should now be plugged in  $J_3$  and the final grid circuit should be brought into resonance by adjustment of  $C_2$ . Proper operation of the tripler stage will be indicated by a cathode current of approximately 20 ma. and a final-amplifier-grid current of 2.5 to 3 ma. The tripler grid condenser,  $C_1$ , should be retuned after the amplifier grid circuit has been peaked, to assure maximum overall operating efficiency.

The amplifier should be tested for neutralizing requirements after adequate grid drive has been obtained. If a well-shielded tube socket has been used, it is possible that the amplifier grid current will not be affected by tuning the 832A plate circuit through resonance. However, if the grid current does kick down as the plate circuit is tuned, it will be necessary to add the neutralizing wires referred to in the text and parts list as  $C_{11}$  and  $C_{12}$ . After installation these wires should be adjusted until no kick in grid current is seen as the 832-A plate circuit is tuned through resonance.

Plate and screen voltage can now be applied to the 832A and the plate circuit tuned to resonance, as indicated by a dip in the cathode current to 40 ma. or less. Then a dummy load (a 15-watt light bulb will do) is connected to the antenna jack and the loading adjusted by varying the position of  $L_7$  and the capacitance of  $C_4$ , to cause a cathode current of 60 to 70 ma. Approximately 10 ma. of the total cathode current will be drawn by the screen of the 832A and this value should be subtracted from the cathode current in determining the plate input.

Amplifier grid-current should be 1.5 to 2 ma. under load.

The jumper connections can now be made between the r.f. and modulator terminal blocks and, with power applied to the entire transmitter, the modulator cathode current should be 75 ma.; 85 ma. with modulation.

The cathode meter reading will decrease slightly when the microphone is plugged into the circuit. This is caused by the parallel current path that exists when the microphone circuit is completed.

## A Mobile Low-Power 50-Mc. Transmitter

The transmitter shown in Figs. 13-32 through 13-35 is designed for mobile operation with a power input of 12 to 20 watts, as a companion unit to the 144-Mc. rig described above. However, the rating of the amplifier tube used is such that the unit can be used at higher levels, delivering an output of approximately 20 watts if a 500-volt supply is available.

As may be seen from the circuit diagram, in Fig. 13-33, a Tri-tet oscillator-doubler, employing a 6V6GT tube and a 25-Mc. crystal, is used to drive an 832A amplifier. The oscillator requires no manual adjustment, once set, as the cathode circuit is fixed-tuned and the plate circuit has a self-resonant coil. The screen voltage for the 6V6 is reduced to the proper value by the dropping resistor,  $R_2$ .

The push-pull amplifier employs split-stator input and output circuits. The grid circuit is inductively-coupled to the oscillator plate coil, and grid bias is developed across resistor  $R_3$ . Usually, for the sake of convenience, it is desirable to employ self-bias during mobile operation and the amplifier, as shown, is set up for this type of operation. The grid leak should be reduced in value, and a battery or bias supply should be connected between the upper end of the grid-metering jack,  $J_1$ , and ground, if the unit is to be operated at maximum rated power input. Because of the isolation afforded by the placement of the grid-circuit components below the chassis and the plate circuit above, the amplifier has no tendency toward self-oscillation. This may not be true if the parts layout differs from that shown. Screen voltage for the 832A is maintained at the proper level for both low and maximum power input to the amplifier, by the dropping resistor,  $R_4$ . A jack,  $J_2$ , provides for metering of the cathode current of the tube. If the transmitter is to be keyed for c.w. operation, the key can be plugged into this cathode jack.

An antenna tuning assembly, intended for operation with coaxial feed systems normally used in mobile installations, is included as part of the transmitter circuit. The degree of antenna loading can be regulated by adjustment of the coupling between the plate coil,  $L_4$ , and the output link,  $L_5$ . A short length of coaxial

cable completes the circuit between the antenna tuning components and the output jack.

The photographs show how a metal box measuring  $3 \times 4 \times 5$  inches serves as the chassis for the transmitter. The bottom plate of the box is removed and used as a panel, and is held in place by the screws and nuts that hold the top cover and the box together. In Figs. 13-32 and 13-35 the condenser,  $C_2$ , and the antenna jack may be seen mounted on the panel. Metal pillars,  $\frac{1}{4}$  inch long, are used to space the condenser away from the panel. A National FWB polystyrene insulator is used as a mounting support for the antenna coil,  $L_5$ , and the insulator is mounted on  $\frac{3}{4}$ -inch metal posts. The antenna tuning condenser,  $C_3$ , is supported by its own mounting tabs, and is connected between one end of the pick-up link and ground.

The rear and bottom views of the transmitter show how the rest of the components are laid out on the top plate of the metal box.



Fig. 13-32 — A compact mobile transmitter or exciter unit for 50 Mc.

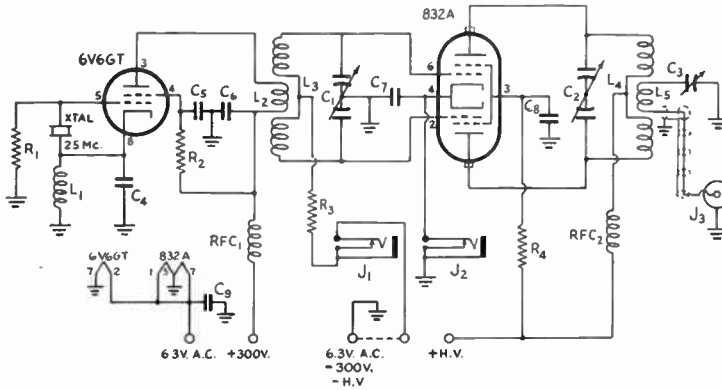


Fig. 13-33 — Circuit diagram of the mobile transmitter for 6 meters.

- C<sub>1</sub> — 15- $\mu$ fd. per section (Bud I.C.-1660).
- C<sub>2</sub> — "Butterfly" condenser, 15  $\mu$ fd. total (Cardwell ER-15-BF/S).
- C<sub>3</sub> — 3-30- $\mu$ fd. mica trimmer.
- C<sub>4</sub> — 100- $\mu$ fd. midget mica.
- C<sub>5</sub>, C<sub>6</sub> — 0.0047- $\mu$ fd. mica.
- C<sub>7</sub>, C<sub>9</sub> — 170- $\mu$ fd. midget mica.
- C<sub>8</sub> — 0.001- $\mu$ fd. mica.
- R<sub>1</sub> — 0.12 megohm,  $\frac{1}{2}$  watt.
- R<sub>2</sub> — 47,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 22,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>4</sub> — 25,000 ohms, 10 watts.
- L<sub>1</sub> — 3 turns No. 18 enameled wire, close-wound,  $\frac{1}{2}$ -inch diam.
- L<sub>2</sub> — 5 turns.
- L<sub>3</sub> — 9 turns, 4 $\frac{1}{2}$  each side of center, with a  $\frac{7}{8}$ -inch space between sections.
- L<sub>4</sub> — 10 turns, 5 each side of center, with a  $\frac{3}{4}$ -inch space between sections.
- L<sub>5</sub> — 3 turns. L<sub>2</sub> through L<sub>5</sub> have an inside diameter of  $\frac{3}{4}$  inch; No. 12 enameled wire, turns spaced wire diameter.
- J<sub>1</sub>, J<sub>2</sub> — Midget closed-circuit jack.
- J<sub>3</sub> — Coaxial-cable connector.
- RFC<sub>1</sub> — 10- $\mu$ h. r.f. choke (Millen 34300).
- RFC<sub>2</sub> — 2.5-mh. r.f. choke (Millen 34102).

This plate should be removed from the box while the construction and wiring are being carried on. All of the wiring, with the exception of the d.c. leads to the metering jacks and the input terminals, can be completed in convenient fashion before the top plate is attached to the metal box.

The socket for the amplifier tube is centered on the chassis plate at a point 2 $\frac{3}{8}$  inches in from the front edge, and is mounted below the plate on metal pillars  $\frac{5}{8}$  inch long. A clearance hole for the 832A, 2 $\frac{1}{4}$  inches in diameter, is directly above the tube socket. Sockets for the oscillator tube and the crystal are mounted toward the rear of the chassis.

The oscillator coil, L<sub>2</sub>, is mounted on the 6V6 socket; the spare pin, No. 6, of the socket being used as the tie-point for the cold end of the plate coil and the other connections that must be made at this part of the circuit. The oscillator cathode coil is mounted between the cathode pin of the 6V6 and a soldering lug placed under the mounting screw of the crystal socket. C<sub>5</sub> and C<sub>6</sub> can be seen to the rear of the crystal socket, and RFC<sub>1</sub> is mounted between the tube socket and a bakelite tie-point strip located at the left of the chassis.

The method employed to assure good r.f. grounding of the amplifier components is visible in Fig. 13-35. Soldering lugs are placed beneath

the mounting nuts of the 832A socket, and these lugs are joined together with a No. 12 lead which, in turn, is carried on to the common ground point for the oscillator circuit. The filament, cathode, and screen by-pass condensers are all returned to the common ground. These three condensers, C<sub>7</sub>, C<sub>8</sub> and C<sub>9</sub>, all rest on the 832A tube socket.

The amplifier grid coil, L<sub>3</sub>, is self-supporting, with the ends connected to the grid pins of the 832A socket. The tuning condenser, C<sub>1</sub>, is actually supported on metal pillars at the right-hand side of the metal box, but the condenser can be wired in place if the operation is carried out in the proper order. First, mount the chassis plate on the box and locate the proper place for the condenser. Next, determine the length of the leads to connect the condenser to the tube socket, and then re-

move the chassis from the case. The condenser may now be wired into the circuit, and the


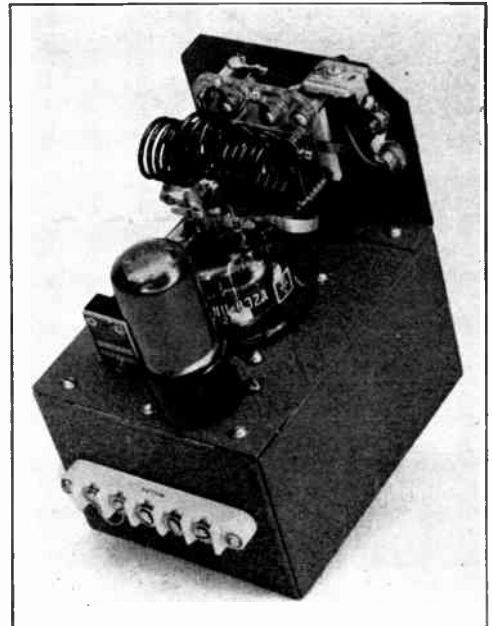


Fig. 13-34 — Top view of the 50-Mc. mobile transmitter

Fig. 13-35 — Bottom view of the mobile transmitter, showing all major components attached to the top plate.

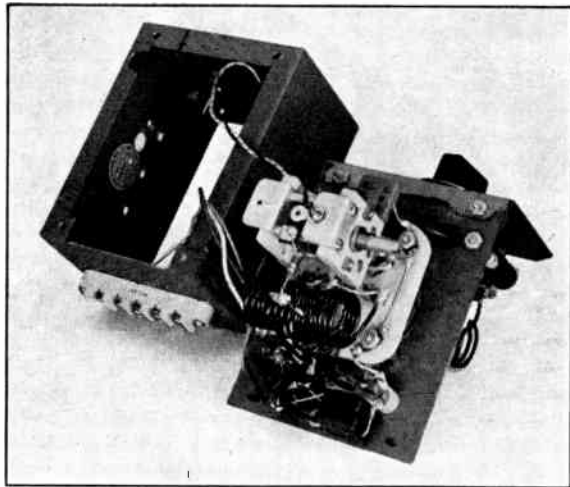

rigid mounting of  $C_1$ , by means of metal posts  $1\frac{1}{4}$  inches long, can be done during the final assembly of the unit.

The grid leak,  $R_3$ , is connected between the center-tap of  $L_3$  and a tie-point strip that is mounted on the condenser frame.  $RFC_2$  is mounted toward the front of the chassis, and the grommet-fitted hole to the left of the choke (Fig. 13-35) carries the lead between the plate-voltage terminal and the choke.

The metering jacks and the power terminal strip may now be mounted on the front and rear walls of the metal box. Holes to permit mounting and adjustment of  $C_1$  should also be drilled at this time. Portions of top flanges of the metal case must be cut away in order to provide clearance for the oscillator section and the mounting nut for the amplifier plate choke. After the case, chassis and panel have been fastened together, the wiring of the amplifier plate circuit may be completed.

#### Test Procedure

A power supply capable of delivering 300 volts at 100 ma. and 6.3 volts at 2 amp. may be used for testing the transmitter. The high voltage should not be applied to the 832A plates until the oscillator has been checked. For initial tests the input voltage can be reduced to approximately 150 volts while the circuits are checked for resonance and proper operation. Squeezing or spreading the turns of the coils should bring the circuits into resonance, as indicated by maximum grid current to the 832A. If the oscillator is performing correctly, the 6V6 plate current will be between 1 and 4 ma., rising to the latter value when the circuits are tuned to the second harmonic of the crystal by adjustment of  $C_1$ . The grid current should fall to zero, and the plate current of the oscillator tube should rise consid-

erably when the crystal is removed from the socket.

The amplifier plate and screen voltage can be applied at this point. The unloaded cathode current of the amplifier should be about 15 ma., rising to a maximum of 75 or 80 ma. under load, which may be a 15-watt light bulb connected to the antenna jack.  $C_3$  should be adjusted along with the coupling between  $L_4$  and  $L_5$  until maximum output is obtained. The correct degree of loading has been obtained when the plate current at resonance is 10 to 15 ma. below the off-resonance value. The plate tuning condenser,  $C_2$ , should be reset each time that a loading adjustment is made.

A final check of voltages and currents should show the following: oscillator and amplifier plate, 300 volts; oscillator screen, 200 volts; amplifier screen, 150 volts; amplifier bias (read at the grid-coil center-tap with a high-resistance voltmeter), 65 volts, negative.

The oscillator plate current should be 28 to 30 ma. and amplifier grid current should be about 3 ma. Under load, the amplifier cathode current should be approximately 60 ma. with 8 or 10 ma. of this amount being drawn by the 832A screen.

Modulation can be supplied by the audio system used in the 2-meter rig shown in Fig. 13-28, or a similar unit may be added, if only 50-Mc. operation is desired.

## Transceivers

The transceiver is a combination transmitter-receiver in which, by suitable switching of d.c. and audio circuits, the same tube and r.f. circuit functions either as a modulated transmitting oscillator or as a superregenerative detector. This makes for extreme compactness and light weight, making the transceiver popular for hand-carried portable equipment. It is a compromise with respect to other features, however. The transceiver can be a source of serious interference, and its efficiency

is not equal to that of other types of gear wherein separate tubes and circuits are used for transmission and reception.

As a matter of good amateur practice the use of transceivers should be confined to very low-power operation — as in “walkie-talkie” or “handie-talkie” equipment — in the 144-Mc. band, and to experimental low-power operation in the higher-frequency bands. The use of transceivers should be avoided entirely for regular operation on the 144-Mc. band.

# V.H.F. Antennas

While the basic principles of antenna operation are essentially the same for all frequencies, certain factors peculiar to v.h.f. work call for changes in antenna technique for the frequencies above 50 megacycles. Here the physical size of multielement arrays is reduced to the point where an antenna system having some gain over a simple dipole is possible in nearly every location, and experimentation with various types of arrays is an important part of the program of most progressive amateurs. The importance of high-gain antennas in v.h.f. work cannot be overemphasized. A good antenna system is often the sole difference between routine operation and outstanding success in this field. By no other means can so large a return be obtained from a small investment as results from the erection of a good directional array.

## Design Factors

Beginning with the 50-Mc. band, the frequency range over which antenna arrays should operate effectively is often wider in percentage than that required of lower-frequency systems; thus greater attention must be paid to designing arrays for maximum frequency response, possibly to the extent of sacrificing other factors such as high front-to-back ratio.

As the frequency of operation is increased, losses in the transmission line rise sharply; hence it becomes more important that the line be matched to the antenna system correctly. Because any v.h.f. transmission line is long, in terms of wavelength, it is often more effective to use a high-gain array at relatively low height, rather than to employ a low-gain system at great height above ground, particularly if the antenna location is not completely shielded by heavy foliage, buildings, or other obstructions in the *immediate* vicinity.

This concept is in direct contrast to early notions of what was most desirable in a v.h.f. antenna system. An appreciable clearance above surrounding terrain is desirable, but great height is by no means so all-important as it was once thought to be. Outstanding results have been obtained by many v.h.f. workers, especially on 50 and 144 Mc., with antennas not more than 25 to 40 feet above ground. DX can be worked on 50 Mc. with arrays as low as a half-wave above the ground level.

## Polarization

Practically all the early work on frequencies above 30 Mc. was done with vertical antennas, probably because of the somewhat stronger field in the immediate vicinity of a vertical system. When v.h.f. work was confined to almost pure line-of-sight distances, the vertical dipole produced a stronger signal at the edge of the working range than did the same antenna turned over to a horizontal position. With the advent of high-gain antennas and extended operating ranges, horizontal systems began to assume importance in v.h.f. work, especially in parts of the country where a considerable degree of activity had not already been established with verticals.

Numerous tests have shown that there is very little difference in the effective working range with either polarization, *if* the most effective element arrangements are used and the same polarization is employed at both ends of the path. Vertical polarization still has its adherents among 50-Mc. enthusiasts and much fine work has been done with vertical antennas, but an effective horizontal array is somewhat easier to build and rotate. Simple 2-, 3- or 4-element horizontal arrays have proven extremely effective in 50-Mc. work, and the postwar era has seen an increase in the use of such arrays which has amounted to standardization on horizontal polarization.

The picture is somewhat different when one goes to 144 Mc. and higher. At these frequencies, the most effective vertical systems (those having two or more half-wave elements, vertically stacked) are more easily erected than on 50 Mc. Important, in considering the polarization question, is the existence of countless 144-Mc. mobile stations, whose antenna systems must, of necessity, be vertical. While horizontal polarization will undoubtedly find increased favor at 144 Mc. and higher, particularly for point-to-point work in rural areas, it is probable that vertical polarization will continue in use for some years to come, particularly in areas where activity has been established with vertical systems. Under certain conditions, notably a station directly in the shadow of a hill, there may be a considerable degree of polarization shift, but ordinarily it may be assumed that best results in 144-Mc. work will be obtained by matching the polarization of the stations one desires to contact.

## Impedance Matching

Because line losses tend to be much higher in v.h.f. antenna systems, it becomes increasingly important that feedlines be made as nearly "flat" as possible. Transmission lines commonly used in v.h.f. work include the open-wire line of 500 to 600 ohms impedance, usually spaced about two inches; the polyethylene-insulated flexible lines, available in impedances of 300, 150, 100, and 72 ohms; and coaxial lines of 50 to 90 ohms impedance. These may be matched to dipole or multielement antennas by any of several arrangements detailed below.

### The "J"

Used principally as a means of feeding a stationary vertical radiator, around which parasitic elements are rotated, the "J" consists of a half-wave vertical radiator fed by a quarter-wave matching section, as shown at A, Fig. 14-1. The spacing between the two sides of the matching section should be two inches or less, and the point of attachment of the feedline will depend on the impedance of the line used. The feeder should be slid along the matching section until the point is found that gives the best operation. The bottom of the matching section may be grounded for lightning protection. A variation of the "J" for use with coaxial-line feed is shown at B in Fig. 14-1. The "J" is also useful in mobile applications.

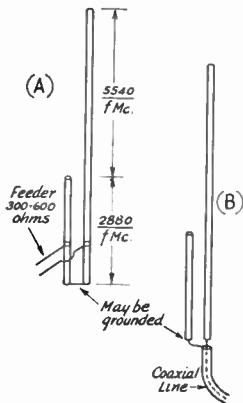


Fig. 14-1 — Two versions of the "J" antenna, often used in mobile installations, or in vertical arrays where parasitic elements may rotate around a fixed radiator.

### The Delta or "Y"-Match

Probably the simplest arrangement for feeding a dipole or parasitic array is the familiar delta, or "Y"-match, in which the feeder system is fanned out and attached to the radiator at a point where the impedance along the element is the same as that of the line used. Information on figuring the dimensions of the delta may be found in Chapter Ten. Chief weakness of the delta is the likelihood of radiation from the matching section, which may interfere with the effectiveness of a multielement array. It is also somewhat unstable

mechanically, and quite critical in adjustment.

### The "Q" Section

An effective arrangement for matching an open-wire line to a dipole, or to the driven element in a 2- or 3-element array having wide (0.25 wavelength or greater) spacing, is the "Q" section (Chapter Ten). This consists of a quarter-wave line, usually of 1/2-inch or larger tubing, the spacing of which is determined by the impedance at the center of the array. The parallel-pipe "Q" section is not practical for matching multielement arrays to lines of lower impedances than about 600 ohms, nor can it be used effectively with close-spaced parasitic arrays. The impedance of the "Q" section required in these

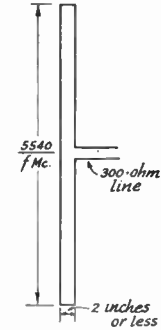


Fig. 14-2 — Details of the folded dipole.

cases is lower than can be obtained with parallel sections of tubing of practical dimensions. A quarter-wave section of coaxial or other low-impedance line is a commonly-used means of matching a line of 300 to 600 ohms impedance to the low center impedance of a 3- or 4-element array. The length of such a line will depend on the velocity of propagation (propagation factor) of the line used. The propagation factors of all the commonly-used lines are given in table form in Chapter Ten.

In some installations it may be more convenient to use a line of greater length than a single quarter wave for matching purposes, in which case any odd multiple of a quarter wavelength may be used. The exact length required may be determined experimentally by shorting one end of the line and coupling it to a source of r.f., and trimming the line length until maximum loading is obtained at the center frequency of the operating range.

### The "T"-Match

The principal disadvantages of the delta system can be overcome through the use of the arrangement shown in Figs. 14-5 and 14-13, commonly called the "T"-match. It has the advantage of providing a means of adjustment (by sliding the clips along the parallel conductors), yet the radiation from the matching arrangement is lower than with the delta, and its rigid construction is more suitable for rotatable arrays. It may be used with coaxial lines of any impedance, or with the various other forms of transmission lines up to 300 ohms. The position of the clips should, of course, be adjusted for maximum loading and minimum standing-wave ratio, the latter being most important as an indication of

proper setting. The "T" system is particularly well suited for use in all-metal "plumbing" arrays.

**The Folded Dipole**

Probably the most effective means of matching various lines to the wide range of antenna impedances encountered in v.h.f. antenna work is the folded dipole, shown in its simplest form in Fig. 14-2. When all portions of the dipole are of the same conductor size, the impedance at the feed-point is equal to the square of the number of elements in the folded dipole times the normal center impedance which would be present if only a conventional split half-wave radiator were used. Thus, the simple folded dipole of Fig. 14-2 has a feed-point impedance of  $4 \times 72$ , or approximately 288 ohms. It may be fed with the popular 300-ohm

line without appreciable mismatch. If a three-wire dipole were used, the step-up in impedance would be nine times. Note that this step-up occurs *only* if all portions of the folded dipole are the same conductor size.

The impedance at the feed-point of a folded dipole may also be raised by making the fed portion of the dipole smaller than the parallel section. Thus, in the 50-Mc. array shown in Fig. 14-4 the relatively low center impedance of a 4-element array is raised to a point where it may be fed directly with 300-ohm line by making the fed portion of the dipole of  $\frac{1}{4}$ -inch tubing, and the parallel section of 1-inch. A 3-element array of similar dimensions could be matched by substituting  $\frac{3}{4}$ -inch tubing in the unbroken section. Conductor ratios and spacings may be obtained from Fig. 10-80, Chapter Ten.

**Antenna Systems for 50 Mc.**

Since the same basic principles apply to all antennas regardless of frequency, little discussion is given here of the various simple dipoles that may be used when nondirectional systems are desired. Details of such antennas may be found in Chapter Ten, and the only modification necessary for adaptation to use on 50 Mc. or higher is the reduction in length necessary for increased conductor diameter at these frequencies.

**A Simple 2-Element Array**

A simple but effective array which requires no matching arrangement is shown in Fig. 14-3. Its design takes into account the drop in center impedance of a half-wave radiator when a parasitic element is placed a quarter wavelength away. A director element is shown, as the drop in impedance using a slightly-shortened parasitic element is just about right to provide a good match to a 50-ohm coaxial line. The element lengths are not extremely critical in such a simple system, and the figures presented may be used with satisfactory results.

**A 4-Element Array**

The importance of broad frequency response in any antenna designed for v.h.f. work cannot be overlooked. The disadvantage of all parasitic systems is that they tend to tune

quite sharply, and thus are often effective over only a small portion of a given band. One way in which the response of a system can be broadened out is to increase the spacing between the

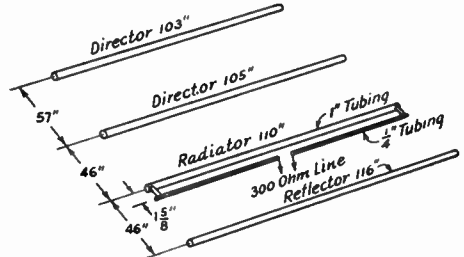


Fig. 14-4 — Dimensional drawing of a 4-element 50-Mc. array. Element length and spacing were derived experimentally for maximum forward gain at 50.5 Mc.

parasitic elements to somewhat more than the 0.1 or 0.15 wavelength normally considered to provide optimum front-to-back ratio. Some broadening may also be obtained by making the directors slightly shorter and the reflector slightly longer than the optimum value. The folded dipole is useful as the radiator in such an array, as its over-all frequency response is somewhat broader than other types of driven elements.

A 4-element array for 50 Mc. having an effective operating range of about 2 Mc. is shown in Figs. 14-4 and 14-5. It employs a folded dipole having nonuniform conductor size. Reflector and first director are spaced 0.2 wavelength from the driven element, while the forward director is spaced 0.25 wavelength. The spacing and element lengths given were derived experimentally, and are those that give optimum forward gain at the expense of some front-to-back ratio. As the latter quality is not of great value in 50-Mc. work, it can be neglected entirely in the tuning procedure for such an array.


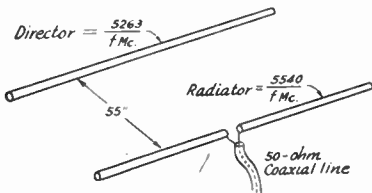


Fig. 14-3 — A simple 2-element array for 50 Mc. No matching devices are needed with this arrangement.

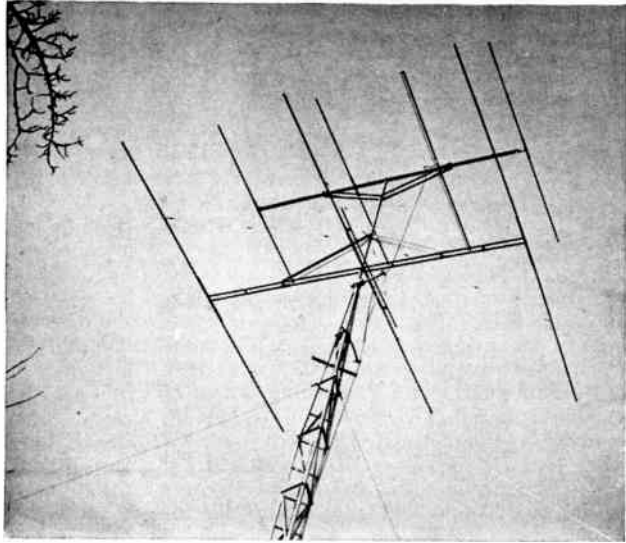

◆  
 Fig. 14-5 — An example of stacking two arrays for different bands on the same support. The top section is a 4-element array for 50 Mc.; the lower a 3-element system for 28 Mc. All-metal construction is employed.



The dimensions given are for peak performance at 50.5 Mc. For other frequencies, the length of the folded dipole in inches should be figured according to the formula

$$L = \frac{5540}{f_{Mc.}}$$

The reflector will be 5 per cent longer, the first director 5 per cent shorter, and the second director 6 per cent shorter than the driven element. A broadening of the response may be obtained, at a slight sacrifice in forward gain, by adding to the reflector length and subtracting from the director lengths. For those interested in experimenting with element lengths, slotted extensions may be inserted in the ends of the various elements, other than the dipole, as shown in Fig. 14-7. A 3-element array may

be built, using the same general dimensions, except that the unbroken section of the folded dipole, in this case, should have a 3/4-inch diameter element in place of the 1-inch tubing used in the 4-element array.


**Stacked Antennas**

Excellent results in long-distance work are being obtained by 50-Mc. stations using various more-complex directional arrays than the ones described above. The most important factor in such work is the attainment of the lowest-possible radiation angle, and this purpose is well served by stacking of elements, in either vertical or horizontal systems. The use of two parasitic arrays, one a half-wavelength above the other, fed in phase, provides a gain of 3 db. or more over that of a single array. The system shown (for 144 Mc.) in Fig. 14-8 is excellent for either vertical or horizontal polarization, as is the "H" array, using four half-wave elements, with or without parasitic elements.

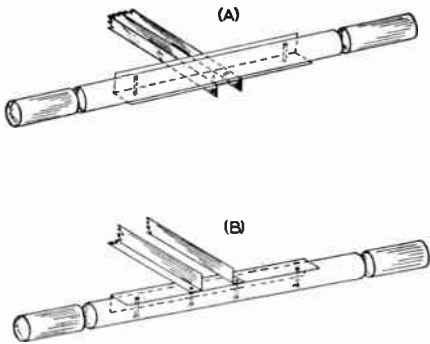**Stacked Arrays for Two Bands**

As many 50-Mc. enthusiasts also operate on 28 Mc., it is often desirable to stack arrays for the two bands on a common tower and rotating device. Such a dual array, combining a 4-element system for 50 Mc. with a 3-element array for 28 Mc., is shown in Fig. 14-5.

If space limitations make it absolutely necessary, the two arrays may be mounted with but a few inches separating them, but experience has shown that some effectiveness is sacrificed, particularly in the array for the higher frequency. A separation of at least three feet is recommended as the minimum for avoiding harmful interaction. In the example shown the separation is six feet, at which distance each array performs equally as well as it would if mounted alone.



◆  
 Fig. 14-6 — Detail sketches showing method of mounting elements in the dual array for 28 and 50 Mc. A — The 50-Mc. boom is comprised of two pieces of angle stock mounted edge-to-edge to form a channel. The elements are fastened to the boom by means of a cradle, also of angle stock. B — In the 10-meter array, the two portions of the boom are separated, and mount on either side of the vertical support. The elements and their supporting crossarms are attached to the lower surface of the boom,

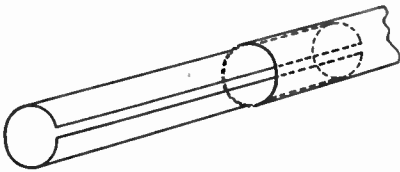


Fig. 14-7 — Detail drawing of inserts which may be used in the ends of the elements of a parasitic array to permit accurate adjustment of element length.

In this dual array all-metal construction is employed, doing away with the use of insulators in mounting the elements. The booms are made of two pieces of 1-inch angle stock (24ST aluminum), with supporting braces of the same material. The method of assembling the booms and mounting the elements is shown in Fig. 14-6. The booms are 150 inches and 160 inches in length for the 6- and 10-meter arrays respectively. To prevent swaying of the 10-

meter elements, they are braced with guy wires, which are broken up with small insulators. These sway-brace wires are attached to the elements at approximately the midpoint between the boom and the outer end, and are brought up to the vertical support at the point of attachment of the horizontal fore-and-aft braces.

The 50-Mc. portion of the array is similar in element length and spacing to the 4-element array already described. The element spacing for the 10-meter array is 0.2 wavelength, or 80 inches. The driven element is 198 inches long, the director 188 inches, and the reflector 208 inches. It is fed by means of a "T"-match and a 300-ohm line. These dimensions give quite uniform performance and low standing-wave ratio over the range from 28 to 29.1 Mc., and the array will take power and show appreciable gain over a half-wave from 27.2 to 29.7 Mc. Complete details of this dual array will be found in *QST* for July, 1947.

## Antenna Systems for 144 Mc.

The antennas already described may, of course, be used for 144 as well as 50 Mc., but since they are designed for maximum effectiveness in a horizontal position, other designs may be used more effectively where vertical polarization is desired. With either polarization, the stacking of elements vertically lowers the radiation angle and extends the operating range. The smaller size of 144-Mc. arrays makes such stacking of elements a much simpler procedure than on 50 Mc. Another advantage of the array employing elements fed in phase is that its frequency response is likely to be less critical than an array that achieves the same gain with but one driven element and parasitic directors and reflectors. Thus the element lengths, even in such complex systems as the 16-element array shown in Fig. 14-9, are not at all critical.

Plane reflectors are usable at 144 Mc., their size at this frequency being within reason. An interesting possibility in connection with this

type of reflector is its use with two different sets of driven elements, one on each side of the reflecting screen. A set of elements arranged for vertical polarization may be used on one side, and a set of horizontally-polarized elements on the other, or the plane reflector may be made to serve on two different bands by a similar arrangement of elements for two frequencies, on opposite sides of the reflector. The screen need not be a solid sheet of metal, or even a close-mesh screen. A set of wires or rods arranged in back of the driven elements will work almost equally well. The dimensions of the reflector are not critical. For maximum effectiveness, the plane reflector should extend at least one-quarter wavelength beyond the area occupied by the elements, but reflecting curtains no larger than the space occupied by the reflectors shown in Fig. 14-9 have been used with good results.

### A 6-Element Array

In designing directional arrays having more than one driven element it is advisable to arrange for feeding the array at a central point. A simple 6-element array of high performance, incorporating this principle, is shown in Fig. 14-8. All the elements may be made of soft-copper tubing,  $\frac{1}{4}$  inch in diameter. The driven elements are comprised of two pieces which are bent into two "U"-shaped sections and arranged in the form of a half-wave "H." The horizontal portion of the "H" is then a double quarter-wave "Q" section, matching the impedance of the two radiators to that of the feedline. With the wide spacing used, the position of the parasitic elements is not particularly critical, except as it affects the impedance of the system, and the spacing of the elements may be varied to provide the best


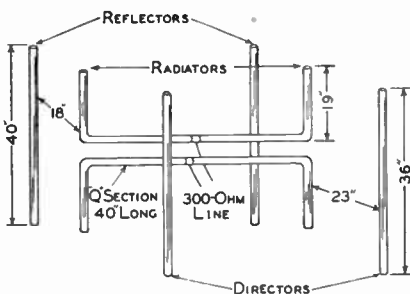


Fig. 14-8 — A double-"Q" array for 144 Mc. The horizontal portion of the half-wave "H" acts as a "Q" section, matching the antenna impedance to the 300-ohm line attached at the center of the array. This array works well in either vertical or horizontal positions.

**Fig. 14-9** — A 16-element array for 144 Mc., showing supporting structure and "rotating mechanism." Sash cord wrapped three times around the crisscross pulley permits 360-degree rotation.

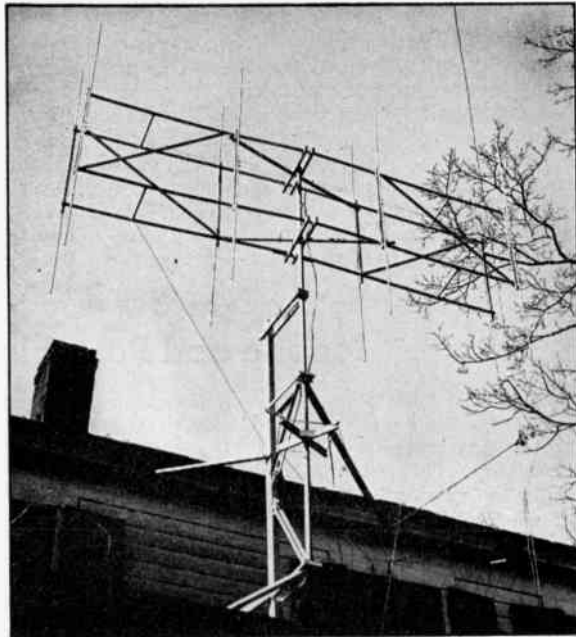

match. The spacing of the horizontal section may be varied for the same purpose. With the dimensions given, a spacing of one inch between centers is about right for feeding with a 300-ohm line. The radiation pattern of this array is similar in both horizontal and vertical planes; thus it will work with equal effectiveness in either position, provided the polarization is the same as that of the stations to be contacted.

### A 16-Element Array

By using a curtain of eight half-wave elements, arranged as shown in Figs. 14-9 and 14-10, backed up by eight reflectors, a degree of performance can be obtained which is truly outstanding. A gain of as much as 15 db. can be realized with such an arrangement, effecting an improvement in operating range which could never be obtained by any other means. Such an array is neither difficult nor expensive to construct, and its performance will more than repay the builder for the trouble involved in its construction.


The cumbersome nature of the structure required to support such an array would make its construction out of the question for a lower frequency, but for 144 Mc. the outside dimensions are only  $1\frac{1}{2} \times 7 \times 10$  feet, and the supporting frame can be made quite light.

The center pole (a  $1\frac{1}{2}$ -inch rug pole 10 feet long) turns in three bearings which are mounted on braced arms extending out about two feet from a "two by three," which is

braced in a vertical position. An improvised pulley made of two pieces of  $1 \times 2$ -inch "furring" notched in the ends and fastened criss-cross fashion near the bottom of the center pole serves as a "rotating mechanism." Sash cord wrapped three times around this "pulley" and run over to the window on small pulleys allows the beam to be rotated more than 360 degrees before reversal is required. To keep the array from twisting in high winds light sash cords are attached near each end of the supporting structure. These cords are brought through the window near the rotating ropes and are pulled up tight and fastened when the antenna is not in use.

The elements are of  $\frac{3}{16}$ -inch soft-aluminum tubing for light weight. To stiffen the structure, and to help maintain alignment, inserts were turned down from  $\frac{1}{2}$ -inch polystyrene rod to fit tightly into the elements at the point where the crossover or phasing wires are connected. Similar inserts are used for the reflector elements also. The interconnecting phasing sections are of No. 16 wire, spaced about  $1\frac{1}{2}$  inches. The feedline, connected at the center of the system, is Amphenol 21-056 Twin-Lead, 300 ohms impedance. The impedance at the center of the array is about right for direct connection of the 300-ohm line, without the necessity for a matching section of any kind. It is probably somewhat lower than 300 ohms, actually, and if a perfect match is desired, a "Q" section may be used. The performance is not greatly affected by such a change, however, as the standing-wave ratio is relatively low with the connection as shown.

The center section of the array may be used without the outside 8 elements, if space is lim-

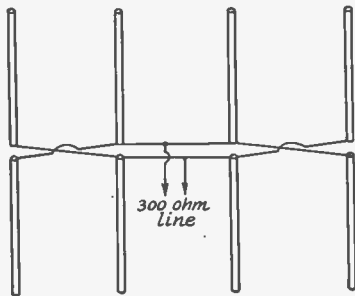

**Fig. 14-10** — Schematic of the radiating portion of the 16-element 144-Mc. array. Reflectors are omitted for clarity. Radiators are 38 inches long, reflectors 40.5 inches. Crossover or phasing sections are also 40.5 inches long. Reflectors are mounted 17 inches in back of each radiator.

ited, and a simpler array of good performance is desired. The simple "H" with reflectors may also be fed with 300-ohm line without the necessity for special matching devices.

Desiring still further gain, ambitious 144-Mc. enthusiasts have doubled and even tripled the 16-element array with worth-while improvements in gain. The same general arrangement, but using four rows of 4 driven elements, with 16 reflectors, has been particularly effective in improving the gain and sharpening the pattern.

## Mobile and Portable Antennas

A common type of antenna employed for mobile operation on 50 and 144 Mc. is the quarter-wave radiator which is fed with a coaxial line. The antenna, which may be a flexible telescoping "fish pole," is mounted in any of several places on the car. The inner

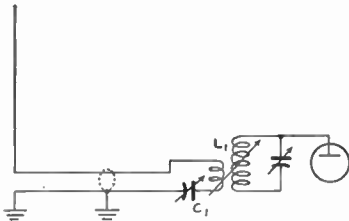


Fig. 14-11 — Method of feeding quarter-wave mobile antennas with coaxial line.  $C_1$  should have a maximum capacitance of 75 to 100  $\mu\text{fd.}$  for 28- and 50-Mc. work.  $L_1$  is an adjustable link.

conductor of the coaxial line is connected to the antenna, and the outer conductor is grounded to the frame of the car. Quite a good match may be obtained by this method with the 50-ohm coaxial line now available; however, it is well to provide some means of tuning the system, so that all variables can be taken care of. The simplest tuning arrangement consists of a variable condenser connected between the low side of the transmitter coupling coil and ground, as shown in Fig. 14-11. This condenser should have a maximum capacitance of 75 to 100  $\mu\text{fd.}$  for 50 Mc., and should be adjusted for maximum loading with the least coupling to the transmitter. Some method of varying the coupling to the transmitter should be provided.

The short antenna required for 144 Mc. (approximately 19 inches) permits mounting the antenna on the top of the car. Such an arrangement provides good coverage in all directions, the car body acting as a ground plane. When the antenna is mounted elsewhere on the car, it is apt to show quite marked directional characteristics. Because of this it is desirable to make provisions for the use of the same antenna for both transmitting and receiving.

### Long-Wire Antennas

Where space permits their use, the possibilities of long-wire antenna systems, particularly the rhomboid, should not be overlooked. Design problems are similar to those for lower frequencies, and data contained in Chapter Ten may be applied to systems for the v.h.f. bands. A vertical rhomboid for 144 Mc. or higher is of practical size, and such antennas have been used with outstanding results. At still higher frequencies the stacking of such arrays a half-wave apart presents interesting possibilities.

### A Collapsible Array for 50 Mc.


The best antenna possible for operation under mobile conditions is not particularly effective, as compared with antenna systems normally used in fixed-station work. To make the most of the fine opportunities for DX work afforded by countless high-altitude locations which are accessible by car, it is helpful to have some sort of collapsible antenna array which can be assembled "on the spot." Even a simple array like the one shown in Figs. 14-12 and 14-13 will effect a great improvement in the operating range of the low-powered gear normally used for mobile operation. This one is designed for 50-Mc. use, but similar arrangements can be made for other frequencies.

The array shown is a 2-element system, comprised of a radiator which is fed with coaxial line by means of a "T"-match, and a reflector which is spaced 0.15 wavelength in back of the



Fig. 14-12 — A 2-element collapsible array for 50-Mc. portable use.

Fig. 14-13 — Detail drawing of the collapsible 50-Mc. array shown in Fig. 14-12. All parts except the vertical support, which is 1 inch in diameter, are made of 3/4-inch duralumin tubing. For carrying purposes, it is taken apart at points A and B, inserts of slotted dural tubing being used at points A to hold the sections together. All extensions are the same length, the difference in element length being provided by the length of the center sections.

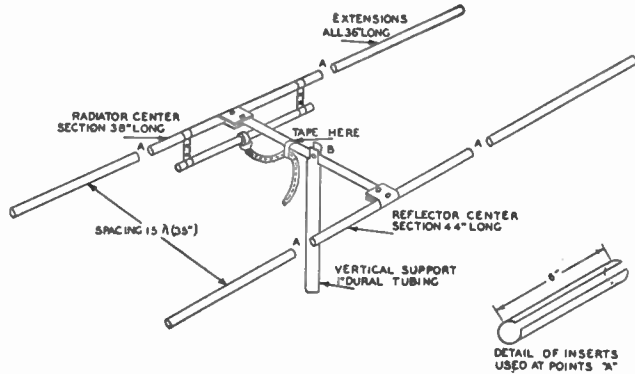

driven element. It is made entirely of 3/4-inch dural tubing, except for the vertical support, which is 1-inch tubing of the same material. A suggested method of mounting is shown in Fig. 14-12. A short length of 1 X 2-inch or larger wood is bolted to the car bumper. A piece of 3/4-inch dural tubing is bolted to this upright, and the 1-inch vertical section of the array slips over the top of the 3/4-inch section. The array is turned by means of ropes attached to the reflector element. Height of the array may be increased over that shown by using a longer wooden support, in which case it is desirable to use a 2 X 2 for greater strength. An anchoring pin made from a spike inserted in the bottom end of the wooden support is helpful to prevent tilting of the array. With such a device embedded in the ground, the whole assembly will remain rigid, which is helpful in the high winds usually encountered in mountain-top locations. Portability is provided by making the elements in three sections, with

the end sections all the same length. The center section of the radiator is 6 inches shorter than that of the reflector.

The fed section of the "T" matching device is composed of two pieces of 3/4-inch dural tubing about 14 inches long. The two sections are held together mechanically, but insulated electrically, by a piece of polystyrene rod which is turned down just enough to make a tight fit in the tubing. The inner and outer conductors of the coaxial line are fastened to the two inside ends of the matching section. Clips made of spring bronze are used for connection between the radiator and the "T." The position of these should be adjusted for maximum loading and minimum standing-wave ratio on the line.

This antenna system may be used as a dipole on 29 Mc. by plugging the reflector sections into the driven element, thus bringing its over-all length to approximately that of a half-wave for the high end of the 10-meter band.

## Miscellaneous Antenna Systems

### Coaxial Antennas

With the "J" antenna radiation from the matching section and the transmission line tends to combine with the radiation from the antenna in such a way as to raise the angle of radiation. At v.h.f. the lowest possible radiation angle is essential, and the coaxial antenna shown in Fig. 14-14 was developed to eliminate feeder radiation. The center conductor of a 70-ohm concentric transmission line is extended one-quarter wave beyond the end of the line, to act as the upper half of a half-wave antenna. The lower half is provided by the quarter-wave sleeve, the upper end of which is connected to the outer conductor of the concentric line. The sleeve acts as a shield about the transmission line and very little current is induced on the outside of the line by the antenna field. The line is nonresonant, since its characteristic impedance is the same as the center impedance of the half-wave antenna. The sleeve may be made of copper or brass tubing of suitable diameter to clear the trans-

mission line. The coaxial antenna is somewhat difficult to construct, but is superior to simpler systems in its performance at low radiation angles.

### Cylindrical Antennas

Radiators such as are used for television and broad-band FM are of interest in amateur v.h.f. operation because they work at high efficiency without adjustment throughout the width of an amateur band.

At the very-high frequencies an ordinary dipole or equivalent antenna made of small wire is purely resistive only over a very small frequency range. Its Q, and therefore its selectivity, is sufficient to limit its optimum performance to a narrow frequency range, and readjustment of the length or tuning is required for each narrow slice of the spectrum. With tuned transmission lines, the effective length of the antenna can be shifted by retuning the whole system. However, in the case of antennas fed by matched-impedance lines, any appreciable frequency change requires an

actual mechanical adjustment of the system. Otherwise, the resulting mismatch with the line will be sufficient to cause significant reduction in power input to the antenna.

A properly designed and constructed wide-band antenna, on the other hand, will exhibit very nearly constant input impedance over several megacycles.

The simplest method of obtaining a broad-band characteristic is the use of what is termed a "cylindrical" antenna. This is no more than a conventional doublet in which large-diameter tubing is used for the elements. The use of a relatively large diameter-to-length ratio lowers the  $Q$  of the antenna, thus broadening the resonance characteristic.

As the diameter-to-length ratio is increased, end effects also increase, with the result that the antenna must be made shorter than a thin-wire antenna resonating at the same frequency. The reduction factor may be as much as 20 per cent with the tubing sizes commonly used for amateur antennas at v.h.f.

### Cone Antennas

From the cylindrical antenna various specialized forms of broadly-resonant radiators have been evolved, including the ellipsoid, spheroid, cone, diamond and double diamond. Of these, the conical antenna is perhaps the most interesting. With large angles of revolution the characteristic impedance can be reduced to a very low value suitable for extremely wide-band operation. The cone may be made up either of sheet metal or of multiple wire spines, as in Fig. 14-15.

### Plane Sheet Reflectors

The small physical size of v.h.f. antennas makes practical many methods not feasible on lower frequencies. For example, a plane flat-sheet reflector may be used with a half-wave dipole, obtaining gains of 5 to 7 db. Much higher gains are attainable with a number of stacked dipoles, spaced one-quarter or three-quarter wavelength apart, and a larger reflecting sheet; such an arrangement is called a "billboard" array.

Plane reflectors need not be constructed of solid sheets. Wire mesh, or a grid of closely-spaced parallel-wire spines, is more easily erected and offers lower wind resistance.

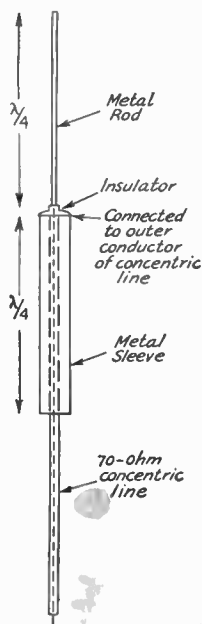


Fig. 14-14 — Coaxial antenna. The insulated inner conductor of the 70-ohm concentric line is connected to the quarter-wave metal rod which forms the upper half of the antenna.

### Parabolic Reflectors

A plane sheet may be formed into the shape of a parabolic curve and used with a driven radiator situated at its focus, to provide a highly-directive antenna system. If the parabolic reflector is sufficiently large so that the distance to the focal point is a number of wavelengths, optical conditions are approached and the wave across the mouth of the reflector is a plane wave. However, if the reflector is of the same order of dimensions as the operating wavelength, or less, the driven radiator is appreciably coupled to the reflecting sheet and minor lobes occur in the pattern. With an aperture of the order of 10 or 20 wavelengths, a beam-width of 5 degrees may be achieved.

A reflecting paraboloid must be carefully designed and constructed to obtain ideal performance. The antenna must be located at the focal point. The most desirable focal length of the parabola is that which places the radiator along the plane of the mouth; this length is equal to one-half the mouth radius. At other focal distances interference fields may deform the pattern or cancel a sizable portion of the radiation.

### Corner Reflectors

The "corner" reflector consists of two flat conducting sheets which intersect at a designated angle. The corner-reflector antenna is particularly useful at v.h.f. where structures one or two wavelengths in maximum dimensions are more practical to build than larger systems.

The plane surfaces are set at an angle of 90 degrees, with the antenna set on a line bisecting this angle. For maximum performance, the distance of the antenna from the vertex should be 0.5 wavelength, but compromise designs can be built with closer spacings. The plane surfaces need not be solid sheets; spines spaced about 0.1 wavelength apart will serve as well. The spines do not have to be connected together electrically.

If the driven radiator is situated on a line bisecting the corner angle, as shown in Fig. 14-16, maximum radiation is in the direction of this line. There is no focus point for the driven radiator, as with a parabolic reflector, and the radiator can be placed at a variety of positions along the bisecting line.

Corner angles larger than 90 degrees can be

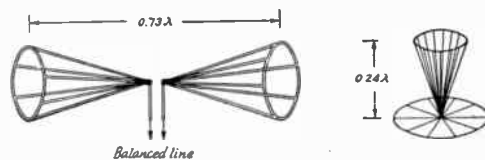


Fig. 14-15 — Conical broad-band antennas have relatively constant impedance over a wide frequency range. The three-quarter wavelength dipole at left and the quarter-wave vertical with ground plane at right have the same input impedance — approximately 65 ohms. Sheet-metal or spine-type construction may be used.

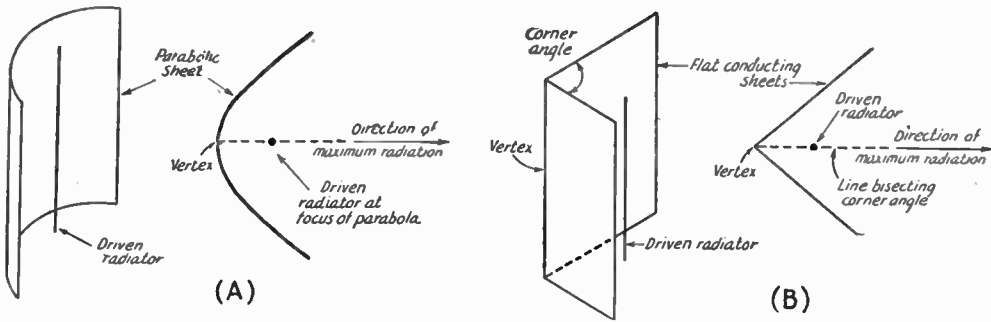


Fig. 14-16 — Plane sheet reflectors for v.h.f. and u.h.f. A shows a parabolic sheet and B a square-corner reflector.

used, with some decrease in gain. A 180-degree "corner" is equivalent to a single flat-sheet reflector. With angles smaller than 90 degrees, the gain theoretically increases as the corner angle is decreased. However, to realize this gain the size of the reflecting sheets must also be increased.

At a spacing of 0.5 wavelength from the driven dipole to the vertex, the radiation resistance of the driven dipole is approximately

twice the radiation resistance of the same dipole in free space. Smaller spacings of driven dipole and vertex are practical, but at a slight sacrifice in efficiency. The alternative design for the 144- and 50-Mc. square-corner reflector has a dipole-to-vertex spacing of 0.4 wavelength. At this spacing the driven-dipole radiation resistance is still somewhat higher than its free-space value, but is considerably less than when the spacing is 0.5 wavelength.

# U.H.F. and Microwaves

Once the amateur passes the 144-Mc. band on the way up through the radio-frequency spectrum, he encounters a distinct change of technique. So far he has been operating in a region where various modifications make usable the familiar coils and condensers, the crystal-controlled transmitters, selective superhet receivers, and other more-or-less standard items of the amateur field.

The boundary line beyond which such conventional gear is no longer usable has moved ever higher and higher in frequency as new developments and improvements in existing equipment have come along. In the early '30s the boundary line was our 28-Mc. band; then, as that band filled, the line moved up to 56 Mc., which remained border territory until 1938, when stabilization of transmitters used was made a legal requirement of operation in the old 5-meter band. For some years, then, the 112-Mc. band, and since the war the 144-Mc. band, constituted the dividing line, but even the latter band has now swung into the stabilized-transmitter-and-superhet-receiver field.

In the light of current developments, it may be said that the 235-Mc. band is now true borderline territory. The multistage transmitter can be used successfully, as can the superheterodyne receiver of semiconventional design, but special tank circuits must be employed and extreme care in mechanical layout must be used, in order to achieve satisfactory results. For these reasons, equipment for the 235-Mc. band is included in this "microwave" chapter, though current nomenclature designates it as a v.h.f. band.

The 235- and 420-Mc. bands are fruitful territory for the experimentally-minded amateur. Most of the gear used will have to be made by the worker himself, but the techniques

employed are such that construction of the necessary equipment will not be outside his capabilities. There is enough interest in a number of areas to support regular activity in both bands, and more can be generated with a little organizational effort.

Antenna work on these frequencies is particularly intriguing. The antenna systems are so small in size that arrays having a gain of 10 db. or more can be erected in almost any location. Experimentation with models built for 420 Mc. is a fine way of checking the performance of arrays for lower frequencies. The experimenter who starts to work with u.h.f. antenna systems is bound to find himself spending many interesting hours checking his pet antenna ideas. Since u.h.f. or microwave experimentation is best accomplished in groups of interested workers, it is a fine project for cooperative effort by radio clubs.

The communication possibilities of the u.h.f. region should not be overlooked. Recent experience in the 144-Mc. band has demonstrated the possibilities of that band for long-distance work, and it is reasonable to assume that propagation vagaries, as regards tropospheric effects, will continue on up through the microwave range. With suitable antenna systems, it is probable that operating ranges on the frequencies above 200 Mc. may equal or approach those now being covered in the 70-160-Mc. region.

At least some amateur work has been done in all the microwave bands now assigned. The work of the pioneers in adapting these frequencies to communication purposes has been in line with the best amateur tradition, and it is hoped that the almost unknown territory from 500 Mc. up will see much amateur exploration in the near future.

## U.H.F. Tank Circuits

In resonant circuits as employed at the lower frequencies it is possible to consider each of the reactance components as a separate entity. A coil is used to provide the required inductance and a condenser is connected across it to provide the needed capacitance. The fact that the coil itself has a certain amount of self-capacitance, as well as some resistance, while the condenser also possesses a small self-inductance, can usually be disregarded.

At the very-high and ultrahigh frequencies, however, it is no longer possible to separate these components. The connecting leads which,

at lower frequencies, would serve merely to join the condenser to the coil now may have more inductance than the coil itself. The required inductance coil may be no more than a single turn of wire, yet even this single turn may have dimensions comparable to a wavelength at the operating frequency. Thus the energy in the field surrounding the "coil" may in part be radiated. At a sufficiently high frequency the loss by radiation may represent a major portion of the total energy in the circuit. Since energy which cannot be utilized as intended is wasted, regardless of whether it is



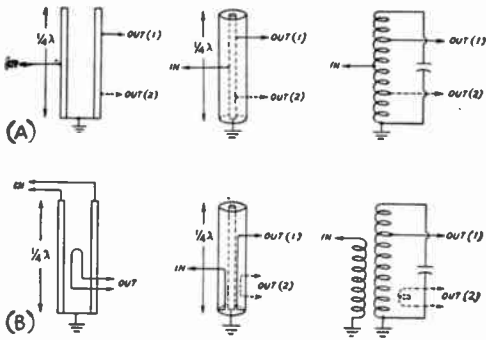


Fig. 15-1 — Equivalent coupling circuits for parallel-line, coaxial-line and conventional resonant circuits.

consumed as heat by the resistance of the wire or simply radiated into space, the effect is as though the resistance of the tuned circuit were greatly increased and its  $Q$  greatly reduced.

For this reason, it is common practice to utilize resonant sections of transmission line as tuned circuits at frequencies above 100 Mc. A quarter-wavelength line, or any odd multiple thereof, shorted at one end and open at the other, exhibits large standing waves. When a voltage of the frequency at which such a line is resonant is applied to the open end, the response is very similar to that of a parallel resonant circuit; it will have very high input impedance at resonance and a large current flowing at the short-circuited end. The input impedance may be as high as 0.4 megohm for a well-constructed line.

The action of a resonant quarter-wavelength line can be compared with that of a coil-and-condenser combination whose constants have been adjusted to resonance at a corresponding frequency. Around the point of resonance, in fact, the line will display very nearly the same characteristics as those of the tuned circuit. The equivalent relationships are shown in Fig. 15-1. At frequencies off resonance the line displays qualities comparable to the inductive and capacitive reactances of the coil-and-condenser circuit, although the exact relationships involved are somewhat different. For all practical purposes, however, sections of resonant wire or transmission line can be used in much the same manner as coils or condensers.

In circuits operating above 300 Mc., the spacing between conductors becomes an appreciable fraction of a wavelength. To keep the radiation loss as small as possible the

parallel conductors should not be spaced farther apart than 10 per cent of the wavelength, center to center. On the other hand, the spacing of large-diameter conductors should not be reduced to much less than twice the diameter because of what is known as the *proximity effect*, whereby another form of loss is introduced through eddy currents set up by the adjacent fields. Because the cancellation is no longer complete, radiation from an open line becomes so great that the  $Q$  is greatly reduced. Consequently, at these frequencies coaxial lines must be used.

**Construction**

Practical information concerning the construction of transmission lines for such specific uses as feeding antennas and as resonant circuits in radio transmitters will be found in this and other chapters of this *Handbook*. Certain basic considerations applicable in general to resonant lines used as circuit elements may be considered here, however.

While either parallel-line or coaxial sections may be used, the latter are preferred for higher-frequency operation. Representative methods for adjusting the length of such lines to resonance are shown in Fig. 15-2. At the left, a slid-

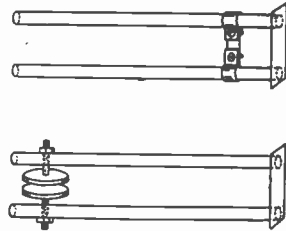


Fig. 15-3 — Methods of tuning parallel-type resonant lines.

ing shorting disk is used to reduce the effective length of the line by altering the position of the short-circuit. In the center, the same effect is accomplished by using a telescoping tube in the end of the inner conductor to vary its length and thereby the effective length of the line. At the right, two possible methods of mounting parallel-plate condensers, used to tune a "foreshortened" line to resonance, are illustrated. The arrangement with the loading capacitor at the open end of the line has the greatest tuning effect per unit of capacitance; the alternative method, which is equivalent to "tapping" the condenser down on the line, has less effect on the  $Q$  of the circuit. Lines with capacitive "loading" of the sort illustrated will be shorter, physically, than an unloaded line resonant at the same frequency.

The short-circuiting disk at the end of the line must be designed to make perfect electrical contact. The voltage is a minimum at this end of the line; therefore, it will not break down some of the thinnest insulating films. Usually a soldered connection or a tight clamp is used to secure good contact. When the length of line

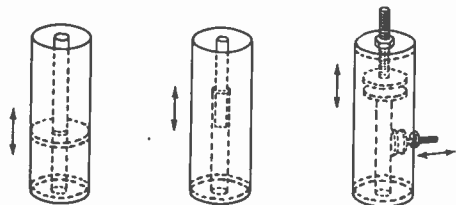


Fig. 15-2 — Methods of tuning coaxial resonant lines.

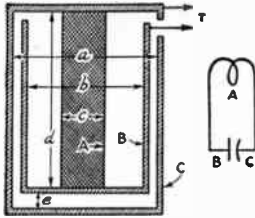


Fig. 15-4 — Concentric-cylinder or "pot" type tank for v.h.f. The equivalent circuit diagram is also shown. Connections are made to the terminals marked T. For maximum Q the ratio of b to c should be between 3 and 5.

must be readily adjustable, the shorting plug is provided with spring collars which make contact on the inner and outer conductors at some distance away from the shorting plug at a point where the voltage is sufficient to break down the film between the collar and conductor.

Two methods of tuning parallel-conductor lines are shown in Fig. 15-3. The sliding short-circuiting strap can be tightened by means of screws and nuts to make good electrical contact. The parallel-plate condenser in the second drawing may be placed anywhere along the line, the tuning effect becoming less as the condenser is located nearer the shorted end of the line. Although a low-capacitance variable condenser of ordinary construction can be used, the circular-plate type shown is symmetrical and thus does not unbalance the line. It also has the further advantage that no insulating material is required.

Equivalent impedance points, for coupling or impedance-transformation purposes, are shown in Fig. 15-1 for parallel-line, coaxial-line, and conventional coil-and-condenser circuits.

**Lumped-Constant Circuits**

At the very-high frequencies the low values of L and C required make ordinary coils and condensers impracticable, while linear circuits offer mechanical difficulties in making tuning adjustments over a wide frequency range, and radiation from unshielded lines may reduce their effectiveness materially.

To overcome these difficulties, special high-Q lumped-constant circuits have been developed in which connections from the "condenser" to the "coil" are an inherent part of the structure. Integral design minimizes both resistance and inductance and increases the C/L ratio.

The simplest of these circuits is based on the use of disks combining half-turn inductance loops with semicircular condenser plates. By connecting several of these half-turn coils in parallel, the effective inductance is reduced to a value appreciably below that for a single turn. Tuning is accomplished by interleaving grounded rotor plates between the turns. Both by shielding action and short-circuited-turn effect, these further reduce the inductance.

Another type of high-C circuit is a single-turn toroid, commonly termed the "hat" resonator. Two copper shells with wide, flat "brims" are mounted facing each other on an axially-aligned copper rod. The capacitance in the circuit is that between the wide shells, while the central rod comprises the inductance.

**"Pot"-Type Tank Circuits**

The lumped-constant concentric-element tank in Fig. 15-4, commonly referred to as the "pot" circuit, is equivalent to a very short coaxial line (no linear dimension should exceed 1/20 wavelength), loaded by a large integral capacitor.

The inductance is supplied by the copper rod, A. Capacitance is provided by the concentric cylinders, B and C, plus the capacitance between the plates at the bottoms of the cylinders.

Approximate values of capacitance and inductance for tank circuits of the "pot" type can be determined by the following:

$$L = 0.0117 \log \frac{b}{c} \mu h.$$

$$C = \left( \frac{0.6225 d}{\log \frac{a}{b}} \right) + \left( \frac{0.1775 b^2}{e} \right) \mu \mu f d.$$

where the symbols are as indicated in Fig. 15-4, and dimensions are in inches. The left-hand term for capacitance applies to the concentric cylinders, B and C, while the second term gives capacitance between the bottom plates.

**"Butterfly" Circuits**

The tank circuits described in the preceding section are primarily fixed-frequency devices. The "butterfly" circuits shown in Fig. 15-5 are capable of being tuned over an exceptionally wide range, while still having high Q and reasonable physical dimensions. The circuit at A is derived from a conventional balanced-type variable condenser. The inductance is in the wide circular band connecting the stator plates. At its minimum setting the rotor plate fills the opening of the loop, reducing the inductance to a minimum. Connections are made to points 1 and 2. This basic structure eliminates all connecting leads and avoids all sliding or wiping electrical contacts to a rotating member. A disadvantage is that the electrical midpoint shifts

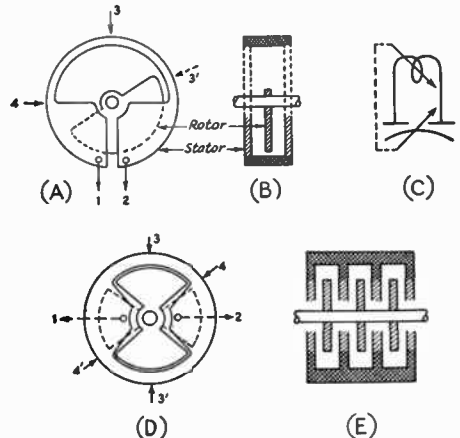


Fig. 15-5 — "Butterfly" tank circuits for v.h.f., showing front and cross-section views and the equivalent circuit.

from point 3 to point 3' as the rotor is turned. Constant magnetic coupling may be obtained by a coupling loop located at point 4, however.

In the modification shown at D, two sectoral stators are spaced 180 degrees, thereby achieving the electrical symmetry required to permit tapping for balanced operation. Connections to the circuit should be made at points 1 and 2 and it may be tapped at points 3 and 3', which are the electrical midpoints. Where magnetic coupling is employed, points 4 and 4' are suitable locations for coupling links.

The capacitance of any butterfly circuit may be computed by the standard formula for parallel-plate condensers given in Chapter Twenty-Four. The maximum inductance can be obtained approximately by finding the inductance of a full ring of the same diameter and multiplying the result by a factor of 0.17. The ratio of minimum to maximum inductance

varies between 1.5 and 4 with conventional construction.

Any number of butterfly sections may be connected in parallel. In practice, units of four to eight plates prove most satisfactory. The ring and stator sections may either be made in a single piece or with separate sectoral stator plates and spacing rings assembled with machine screws.

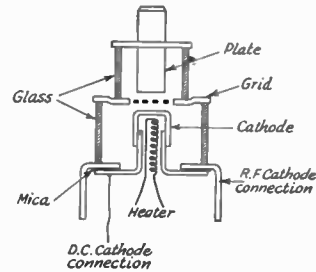


Fig. 15-6—Sectional view of the "lighthouse" tube's construction. Close electrode spacing reduces transit time while the disk electrode connections reduce lead inductance.

### V.H.F. and U.H.F. Tubes

At very-high frequencies, interelectrode capacitance and the inductance of internal leads determine the highest possible frequency to which a vacuum tube can be tuned. The tube usually will not oscillate up to this limit, however, because of dielectric losses, grid emission, and "transit-time" effects. In low-frequency operation, the actual time of flight of electrons

made as little as 0.005 inch, are capable of operation up to about 700–800 Mc. The normal frequency limit is around 600 Mc., although output may be obtained up to 800 Mc.

Very low interelectrode capacitance and lead inductance have been achieved in the newer tubes of modified construction. In multiple-lead types the electrodes are provided with up to three separate leads which, when connected in parallel, have considerably-reduced effective inductance. In double-lead types the plate and grid elements are supported by heavy single wires which run entirely through the envelope, providing terminals at either end of the bulb. When a resonant circuit is connected to each pair of leads, the shunting capacitance divides between the two circuits. With linear circuits the leads become a part of the line and have distributed rather than lumped constants. Radiation loss is minimized and the effect of the transit time is reduced. In "lighthouse" tubes or *megatrons* the plate, grid and cathode are assembled in parallel planes, as shown in Fig. 15-6, instead of coaxially. The uniform coplanar electrode design and disk-seal terminals permit low interelectrode capacitance.

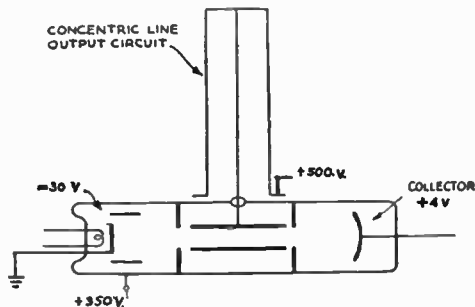


Fig. 15-7—Simple form of cylindrical-grid velocity-modulated tube with retarding-field collector and coaxial-line output circuit, used as a superheterodyne high-frequency oscillator or as a superregenerative detector. Similar tubes can also be used as r.f. amplifiers and frequency converters in the 5–50-cm. region.

between the cathode and the anode is negligible in relation to the duration of the cycle. At 1000 kc., for example, transit time of 0.001 microsecond, which is typical of conventional tubes, is only 1/1000 cycle. But at 100 Mc., this same transit time represents 1/10 of a cycle, and a full cycle at 1000 Mc. These limiting factors establish about 3000 Mc. as the upper frequency limit for negative-grid tubes.

With tubes of ordinary construction, the upper limit of oscillation is about 150 Mc. For higher frequencies, v.h.f. tubes of special construction are used. The "acorn" and "door-knob" types and the special v.h.f. "miniature" tubes, in which the grid-cathode spacing is

#### Velocity Modulation

In negative-grid operation the potential on the grid tends to reduce the electron velocity during the more negative half of the oscillation cycle, while on the other half-cycle the positive potential on the grid serves to accelerate them. Thus the electrons tend to separate into groups, those leaving the cathode during the negative half-cycle being collectively slowed down, while those leaving on the positive half are accelerated. After passing into the grid-plate space only a part of the electron stream follows the original form of the oscillation cycle, the remainder traveling to the plate at differing velocities. Since these contribute nothing to the

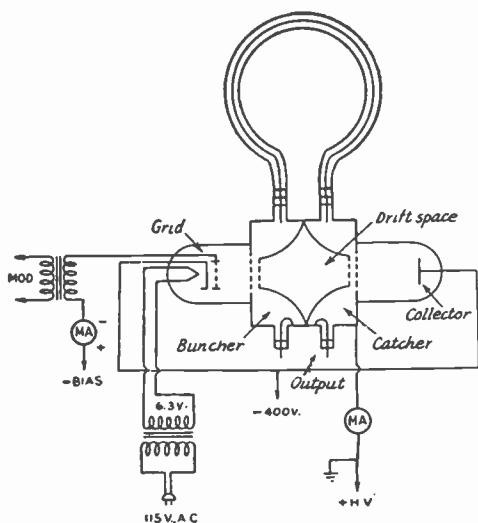


Fig. 15-8 — Circuit diagram of the klystron oscillator, showing the feed-back loop coupling the frequency-controlling rhumbatrons and the output loop in the catcher.

power output at the operating frequency, the efficiency is reduced in direct proportion to the variation in velocity, the output reaching a value of zero when the transit time approaches a half-cycle.

This effect, such a disadvantage in conventional tubes, is an advantage in velocity-modulated tubes in that the input signal voltage on the grid is used to change the velocity of the electrons in a constant-current electron beam, rather than to vary the intensity of a constant-velocity current flow as is the method in ordinary tubes.

A simple form of velocity-modulation oscillator tube is shown in Fig. 15-7. Electrons emitted from the cathode are accelerated through a negatively-biased cylindrical grid by a constant positive voltage applied to a sleeve electrode, shown in heavy lines. This electrode, which is the velocity-modulation control grid, consists of two hollow tubes, with a small space at each end between the inner tube, through which the electron beam passes, and the disks at the ends of the larger tube portion. With r.f. voltage applied across these gaps, which are small compared to the distance traveled by the electrons in one half-cycle, electrons entering the tube will be accelerated on positive half-cycles and decelerated on the negative half-cycles. The length of the tube is made equal to the distance covered by the electrons in one-half cycle, so that the electrons will be further accelerated or decelerated as they leave the tube.

As the beam approaches the collector electrode, which is at nearly zero potential, the electrons are retarded, brought to rest, and ultimately turned back by the attraction of the positive sleeve electrode. The collector electrode is, therefore, also termed a reflector.

The point at which electrons are returned depends on their velocity. Thus the velocity modulation is again translated into current modulation.

Velocity-modulated tubes operate satisfactorily up to 6000 Mc. (5 cm.) and higher, with outputs of 100 watts or more.

### The Klystron

In the *klystron* velocity-modulated tube, the electrons emitted by the cathode are accelerated or retarded during their passage through an electric field established by two grids in a cavity resonator, or *rhumbatron*, called the "buncher." The high-frequency electric field between the grids is parallel to the electron stream. This field accelerates the electrons at one moment and retards them at another, in accordance with the variations of the r.f. voltage applied. The resulting velocity-modulated beam travels through a field-free "drift space," where the slowly-moving electrons are gradually overtaken by the faster ones. The electrons emerging from the pair of grids therefore are separated into groups or bunched along the direction of motion. The velocity-modulated electron stream is passed to a "catcher" rhumbatron. Again the beam passes through two parallel grids; the r.f. current created by the bunching of the electron beam induces an r.f. voltage between the grids. The catcher cavity is made resonant at the frequency of the

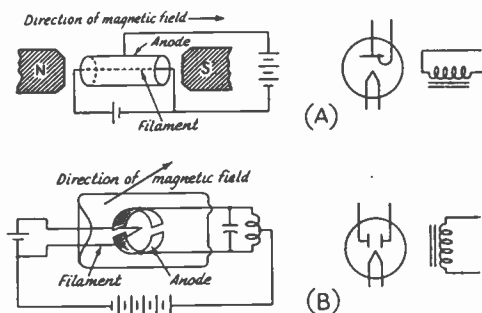


Fig. 15-9 — Conventional magnetrons, with equivalent schematic symbols at the right. A, simple cylindrical magnetron. B, split-anode negative-resistance magnetron.

velocity-modulated electron beam, so that an oscillating field is set up within it by the passage of the electron bunches through the grid aperture.

If a feed-back loop is provided between the two rhumbatrons, as shown in Fig. 15-8, oscillations will occur. The resonant frequency depends on the electrode voltages and on the shape of the cavities, and may be adjusted by varying the supply voltage and altering the dimensions of the rhumbatrons. The bunched beam current is rich in harmonics, but the output waveform is remarkably pure because the high Q of the catcher rhumbatron suppresses the unwanted harmonics.

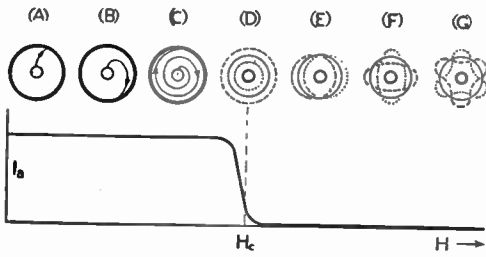


Fig. 15-10 — Electron trajectories for increasing values of magnetic field strength,  $H$ . Below is shown the corresponding curve of plate current,  $I_b$ . Oscillations commence when  $H$  reaches a critical value,  $H_c$ ; progressively higher-order modes of oscillation occur beyond this point.

**Magnetrons**

A magnetron is fundamentally a diode with cylindrical electrodes placed in a uniform magnetic field with the lines of electromagnetic force parallel to the elements. The simple cylindrical magnetron consists of a filamentary cathode surrounded by a concentric cylindrical anode. In the more efficient split-anode magnetron the cylinder is divided longitudinally.

Magnetron oscillators are operated in two different ways. Electrically the circuits are similar, the difference being in the relation between electron transit time and the frequency of oscillation.

In the negative-resistance or dynatron type of magnetron oscillator, the element dimensions and anode voltage are such that the transit time is short compared with the period of the oscillation frequency. Electrons emitted from the cathode are driven toward both halves of the anode. If the potentials of the two halves are unequal, the effect of the magnetic field is such that the majority of the electrons travel to that half of the anode that is at the lower potential. In other words, a decrease in the potential of either half of the anode results in an increase in the electron current flowing to that half. The magnetron consequently exhibits negative-resistance characteristics. Negative-resistance magnetron oscillators are useful between 100 and 1000 Mc. Under the best operating conditions efficiencies of 20 to 25 per cent may be obtained. Since the power loss in the tube appears as heat in the anode, where it is readily dissipated, relatively large power-handling capacity can be obtained.

In the transit-time magnetron the frequency is determined primarily by its dimensions and

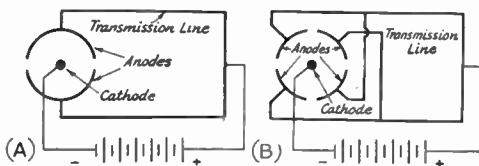



Fig. 15-11 — S.h.f. magnetron circuits. A, split-anode type. B, 4-anode type, opposite electrodes paralleled.

by the electric and magnetic field intensities rather than by the tuning of the tank circuits. The efficiency is much better than that of a positive-grid oscillator and good power output can be obtained even on the superhigh.

In a nonoscillating magnetron with a weak magnetic field, electrons traveling from the cathode to the anode move almost radially, their trajectories being bent only slightly by the magnetic field. With increased magnetic field the electrons tend to spiral around the filament, their radial component of velocity being much smaller than the angular component. Under critical conditions of magnetic field strength, a cloud of electrons rotates about the filament. It extends up to the anode but does not actually reach it.

The nature of these electron trajectories is shown in Fig. 15-10. Cases A, B and C correspond to the nonoscillating condition. For a small magnetic field (A) the trajectory is bent slightly near the anode. This bending increases for a higher magnetic field (B) and the electron moves through quite a large angle near the anode before reaching it, signifying a large increase of space charge near the anode. For a

Fig. 15-12 — Split-anode magnetron with integral resonant anode cavity for use at u.h.f.

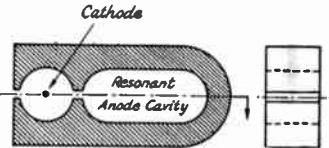

strong magnetic field (C) electrons start radially from the cathode but are soon bent and curl about the filament in the form of a long spiral before reaching the anode. This means a very long transit time and a very large space charge in the whole region where the spiraling takes place. Under critical conditions (D), no current flows to the anode and no electron is able to move from cathode to anode, but a large space charge still exists between the cathode and anode. The spiraling becomes a set of concentric circles, and the entire space-charge distribution rotates about the filament.

Fig. 15-10E, F and G depicts higher-order (harmonic-type) modes of operation in which the space charge oscillates not only symmetrically but in transverse directions contrasting to the vibrations of the fundamental.

In a transit-time magnetron oscillator the intensity of the magnetic field is adjusted so that, under static conditions, electrons leaving the cathode move in curved paths which just fail to reach the anode. All electrons are therefore deflected back to the cathode, and the anode current is zero. When an alternating voltage is applied between the two halves of the anode, causing the potentials of these halves to vary about their average positive values, the conditions in the tube become analogous to those in a positive-grid oscillator. If the period of the alternating voltage is made equal to the


time required for an electron to make one complete rotation in the magnetic field, the a.c. component of the anode voltage reverses direction twice with each electron rotation. Some electrons will lose energy to the electric field, with the result that they are unable to reach the cathode and continue to rotate about it. Meanwhile other electrons gain energy from the field and are returned to the cathode. Since those electrons that lose energy remain in the interelectrode space longer than those that gain energy, the net effect is a transfer of energy from the electrons to the electric field. This energy can be applied to sustain oscillations in a resonant transmission line connected between the two halves of the anode.

Split-anode magnetrons for u.h.f. are constructed with a cavity resonator built into the tube structure, as illustrated in Fig. 15-12. The assembly is a solid block of copper which assists in heat dissipation. At extremely high

frequencies operation is improved by subdividing the anode structure into from 4 to 16 or more segments, the resonant cavities for each anode coupled by slots of critical dimensions to the common cathode region, as in Fig. 15-13.

The efficiency of multisegment magnetrons

Fig. 15-13 — Multisegment magnetron with four resonant cavities. This construction is used for extremely high frequencies.

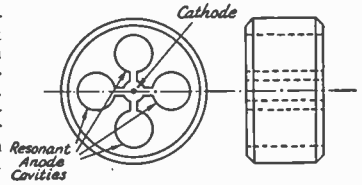

reaches 65 or 70 per cent. Slotted-anode magnetrons with four segments function up to 30,000 Mc. (1 cm.), delivering up to 100 watts at efficiencies greater than 50 per cent. Using larger multiples of anodes and higher-order modes, performance can be attained at 0.2 cm.

## Equipment for 235 Mc.

While the serious experimenter, who is interested in fully exploring the possibilities of the 235-Mc. band, will undoubtedly wish to employ the most advanced techniques possible, there are many who will want to work the band with simple gear. The modulated oscillator and the superregenerative receiver are in disrepute among 144-Mc. enthusiasts principally because they were improperly used by many on that band, resulting in extremely bad-sounding signals and much needless interference. The simple-oscillator type of rig is capable of radiating a signal that is not unduly broad, and which sounds well when received on a not-too-sharp receiver. With proper attention to a few important details, the simplest form of equipment can be used on 235-Mc. with good results.

In the transmitter, it is a relatively simple matter to avoid the faults that have been so common in past experience. If an a.c. power supply is used on the transmitter, we should use heater-type tubes, to avoid hum modula-

tion of the signal. Special attention should be paid to the design of the oscillator, making certain that sufficient feed-back (as indicated by the *grid* current) is provided so that the oscillator will function over a wide range of plate voltages. This assures that the carrier will stand up well under reasonable percentages of modulation, and that the degree of frequency modulation will be minimized. The loading of the oscillator should not be excessive, otherwise the signal will be broad and of poor quality. The tubes must be operated at considerably-lower ratings than would be used on lower frequencies, otherwise there will be severe drift, and shortened tube life.

If the receiver is the superregenerative type, we should avoid coupling the detector to the antenna, if there is appreciable other activity within a few miles, as nothing is more troublesome than receiver radiation. The superheterodyne principle can be used without excessive complication, and it should be employed wherever possible. A simple solution to this problem


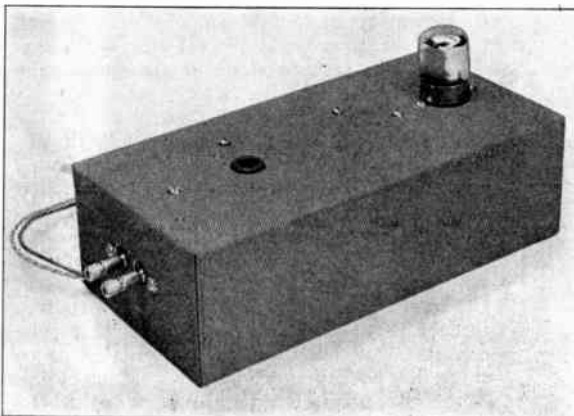


Fig. 15-14 — A one-tube transmitter for 235 Mc. The oscillator is a 7F8 dual triode. Lines and antenna coupling are below the chassis.


*Fig. 15-15 — Under-chassis view of the 235-Mc. transmitter. Note the method of making the shorting bar and mounting the trimmer condenser — both by the use of spring grid clips, permitting adjustment of the position of either along the line.*

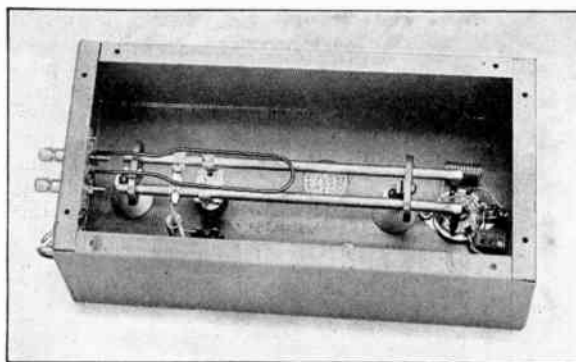

is the use of a converter working into a super-regenerative detector on some lower frequency, or into a broad-band i.f. system, such as an FM broadcast receiver.

### A 10-Watt Transmitter for 235 Mc.

A line oscillator which is suitable for low-power experimental work is shown in Figs. 15-14, 15-15 and 15-16. It is built entirely of readily-obtainable standard parts, and may be

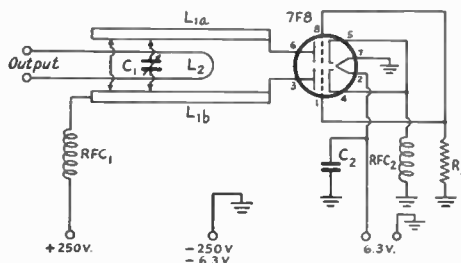


*Fig. 15-16 — Schematic of the 235-Mc. transmitter. R.f. chokes are 12 turns No. 18 d.c.c. wire, 1/4-inch diam. C<sub>2</sub> is 0.0047 μfd. See text for other values.*

constructed at very low cost. The tube is a 7F8 dual triode, working as a push-pull oscillator, with parallel lines in the plate circuit. The frequency is varied by means of a mica trimmer which is connected across the line near the cold end, so that a vernier effect is attained. A rough adjustment of frequency is made by means of an adjustable shorting bar. When the proper setting of the shorting bar is found, the 235-240-Mc. band will be covered by about two complete turns of the trimmer.

The transmitter is mounted on a 3 × 5 × 10-inch chassis. Only the oscillator tube is above the chassis, with the lines and antenna coupling below. The antenna coupling loop is connected to a National FWG terminal assembly which projects through the end of the chassis. The plate lines are 7 1/2 inches long and made of 1/4-inch copper tubing spaced 3/4 inch, center to center. They are held in position by two halves of a National FWH or FWJ terminal block. These blocks are of low-loss insulating material, and the hole spacing is right for this application. The connection

between the plates and the lines should be made with 1/4-inch-wide copper strip. They are mounted on two cone stand-offs 6 inches apart. Self-supporting r.f. chokes, one in the cathode lead and the other in the B-plus lead, a 1000-ohm resistor from grids to ground, and a small by-pass condenser from the hot heater terminal to ground, complete the circuit. The antenna coupling is a "U"-shaped loop 4 1/2 inches long.

The transmitter may be placed in operation by applying 6.3 volts a.c. and about 250 volts d.c. Plate current, under load, should be under 40 ma. A lamp load should be used across the antenna terminals until the frequency is adjusted to within the band limits. The shorting bar is made from two National No. 8 grid clips, which make a tight fit on the 1/4-inch tubing, and the trimmer condenser is also connected to the line by means of a pair of these clips, making it possible to adjust the position of the condenser along the line to give the desired degree of frequency coverage. The shorting bar and the trimmer should be set in such positions

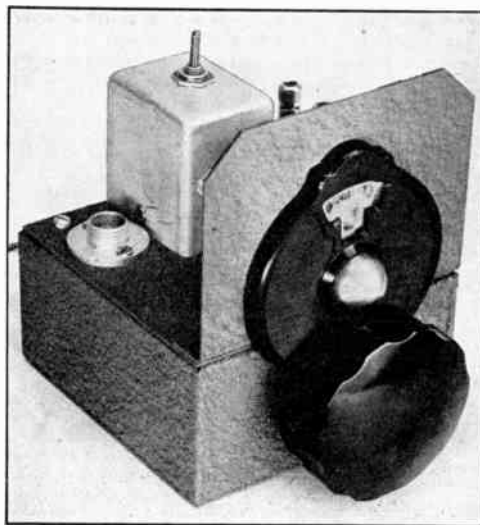

*Fig. 15-17 — A simple converter for 235-Mc. reception. The large knob was substituted for the customary small one to facilitate slow tuning.*

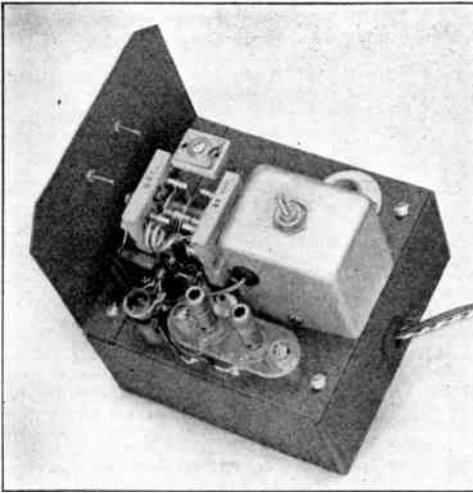


Fig. 15-18 — Top view of the 235-Mc. converter. At the lower left is the slug-tuned mixer input circuit. The output transformer, also slug-tuned, is in the shield. Just visible over the top of the shield is the coaxial i.f. output fitting. Oscillator tuning is by means of the split-stator condenser attached to the vernier dial.

that, with the trimmer set near maximum capacitance, the frequency of the oscillator is 235 Mc.

The antenna coupling may then be adjusted,

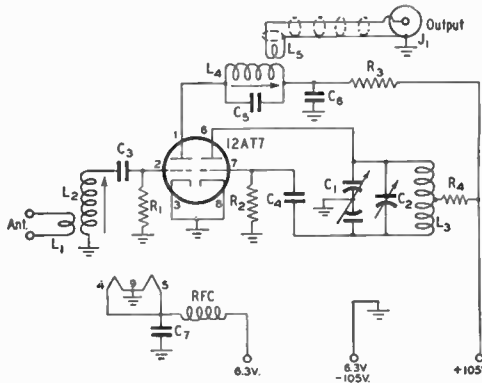


Fig. 15-19 — Circuit diagram of the 235-Mc. converter.

- C<sub>1</sub> — 15- $\mu$ fd.-per-section split stator (Bud LC-1660 reduced to 1 stator and 1 rotor plate per section).
- C<sub>2</sub> — 3-30- $\mu$ fd. mica trimmer (National M-30).
- C<sub>3</sub>, C<sub>4</sub> — 22- $\mu$ fd. mica.
- C<sub>5</sub> — 27- $\mu$ fd. mica.
- C<sub>6</sub>, C<sub>7</sub> — 470- $\mu$ fd. mica.
- R<sub>1</sub> — 1 megohm,  $\frac{1}{2}$  watt.
- R<sub>2</sub> — 10,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub>, R<sub>4</sub> — 1000 ohms,  $\frac{1}{2}$  watt.
- L<sub>1</sub> — 1 turn insulated wire,  $\frac{3}{8}$ -inch diam., wound at cold end of L<sub>2</sub>.
- L<sub>2</sub> — 1 turn No. 18 e. wire,  $\frac{3}{8}$ -inch diam.
- L<sub>3</sub> — 2 turns No. 12 tinned wire,  $\frac{1}{4}$ -inch diam., turns spaced wire diam.
- L<sub>4</sub> — 9 turns No. 18 e. wire,  $\frac{1}{2}$ -inch diam.,  $\frac{5}{8}$  inch long.
- L<sub>5</sub> — 2 turns insulated wire, close-wound over bottom end of L<sub>4</sub>. L<sub>1</sub> and L<sub>2</sub> are wound on a Cambridge Thermionic Corp. Type LS-3 slug-tuned coil form,  $\frac{3}{8}$ -inch diameter. L<sub>4</sub> and L<sub>5</sub> are wound on a National Type XR-50 slug-tuned form.
- J<sub>1</sub> — Coaxial-cable connector (Jones S-201).
- RFC — 12 turns No. 18 wire,  $\frac{1}{4}$ -inch diameter, 1 inch long.

with the antenna connected. The position of the loop should be adjusted for maximum power transfer (a field-strength meter close to the antenna is a good indication), using the minimum coupling that will give satisfactory output. The frequency should be checked again after the antenna is on and the coupling adjusted, as this operation may have shifted the frequency slightly.

The transmitter can be run at 10 watts input without endangering the tube. The useful output is in the vicinity of 2 watts. The rig may be modulated with a single 6V6 tube.

#### A Simple 235-Mc. Converter

A simple one-tube converter for 235 Mc. is shown in Figs. 15-17-15-20. It uses the new 9-pin miniature 12AT7 dual triode, but a 7F8 or 6J6 might work equally well. Its circuit is similar to that of the 7F8 converter for 144 Mc., described in Chapter Twelve. One section of the tube is used as the oscillator, and is tuned by means of a small split-stator condenser and the vernier dial. The mixer input circuit is untuned, except for the slug adjustment. Mixer output is on 27.9 Mc., but it could be changed to suit the i.f. to be used. The converter was designed for use with superregenerative receivers such as the National One-Ten, or with other broad-band receivers capable of tuning to the i.f. frequency. It has also been used successfully in reception of crystal-controlled transmitters, in conjunction with conventional low-frequency communications receivers, though the selectivity of such an arrangement is excessively sharp for most signals. Its sensitivity, with any of the above arrangements, is appreciably better than is obtainable

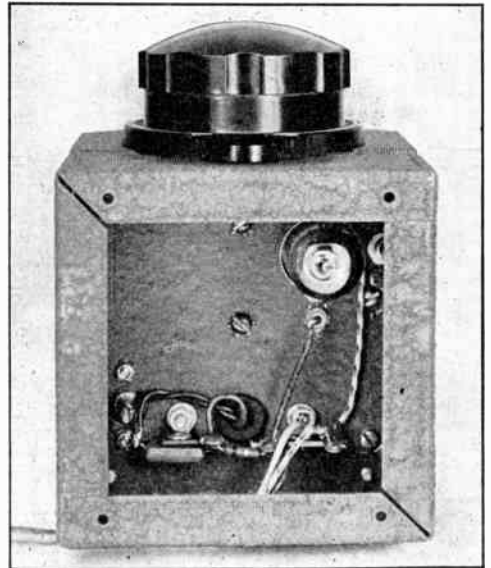


Fig. 15-20 — Bottom view of the 235-Mc. converter, showing the 12AT7 tube mounted below the chassis.



with superregenerative detectors operating on 235 Mc., and the radiation and other disadvantages of the superregen are eliminated.

The converter is built on the smallest-size standard utility box, with the bottom plate removed and used for a front panel. The tube is mounted with its socket above the chassis.

## 420-Mc. Gear

Though it is entirely possible to use crystal control, even on 420 Mc., it is highly improbable that many amateurs will care to go to the trouble necessary to accomplish it. For some time to come, at least, most work on this band will be done with simple oscillators supplying the r.f. power. Superheterodyne-receiver design is not too difficult, and a considerable number of experimenters will find the superhet the most satisfactory receiving system, especially when broad-band i.f. systems are employed. The i.f. strips used in radar work are readily adapted to 420-Mc. amateur work, as their extreme broadness is not important at the present state of activity on this frequency. Broadness in both the transmitter and receiver need not be troublesome in this band, which is considerably wider than any of our lower v.h.f. assignments.

### A 420-Mc. Transmitter

Not too many tubes are available which can be made to function at 420 Mc. Of these, the 6J6 is a logical choice. The transmitter shown in Figs. 15-21 through 15-24 uses a pair of 6J6s in push-pull-parallel. It can be operated at 15 watts input and is capable of delivering about 2 watts output at 420 Mc., the output dropping off slightly toward the 450-Mc. end of the band.

The circuit and shorting-bar details were suggested by a war-surplus transmitter-receiver known as the AN/APS-13. Details of the tank

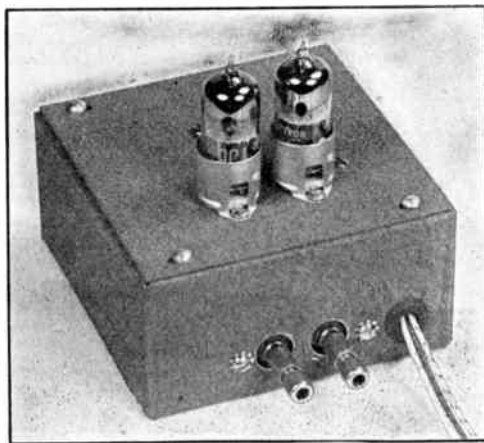


Fig. 15-21 — A transmitter for 420 Mc. using two 6J6 tubes in push-pull-parallel. Antenna coupling terminals project through the front of the chassis.

permitting short leads to all r.f. components. Leads must, of course, be practically non-existent at these frequencies. The general parts arrangement is visible in the photographs, and putting the converter into operation is similar to the process detailed for the 7F8 converter described in Chapter Twelve.

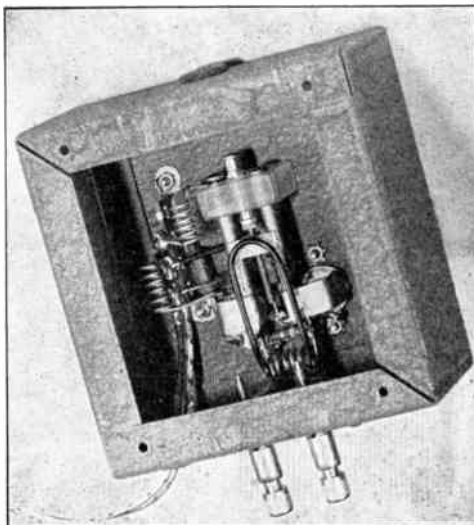


Fig. 15-22 — Bottom view of the 420-Mc. transmitter, showing the plate-line assembly. Note wide strips used to make connection to the tube plates.

circuit may be seen in the under-chassis photograph, and the drawing, Fig. 15-23. It is made of two pieces of  $\frac{3}{16}$ -inch copper tubing, this size being used because it can be tapped

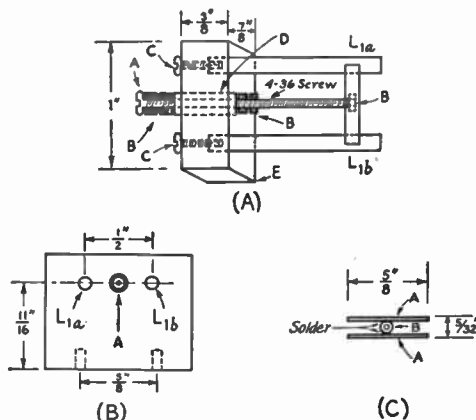


Fig. 15-23 — Detail drawing of the plate-line assembly used in the 420-Mc. transmitter. A shows the lines and method of mounting in the polystyrene block, which is shown in detail at B. The shorting bar, for frequency adjustment, is shown at C. In view A parts B are 4-36 nuts which are tightened on shaft A, a  $1\frac{1}{2}$ -inch 4-36 screw. Part D is a bushing which is embedded in the polystyrene block. It serves as a bearing. Lines  $L_{1a}$  and  $L_{1b}$  are  $1\frac{1}{2}$  inches long.

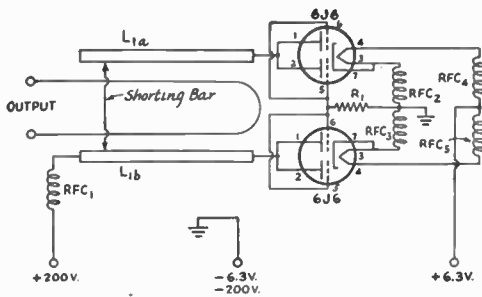


Fig. 15-24 — Circuit diagram of the 420-Mc. push-pull-parallel transmitter.

$R_1$  — 2700 ohms,  $\frac{1}{2}$  watt.

$L_{1a}$ ,  $L_{1b}$  — Plate line; see Fig. 15-23.

$RFC_1$ ,  $RFC_2$ ,  $RFC_3$ ,  $RFC_4$ ,  $RFC_5$  — 6 turns No. 20,  $\frac{3}{8}$ -inch inside diameter,  $\frac{5}{8}$  inch long.

merely by running a 6-32 tap into the end of the tube, providing a simple means of mounting. The shorting bar is made of two pieces of spring bronze which are soldered to opposite faces of a 4-36 nut. A long screw, mounted in the polystyrene block which also acts as a support for the two portions of the line, serves as a means of frequency adjustment, its head being reached through a rubber-grommetted access hole in the end of the chassis. With the dimensions shown, movement of the shorting bar the whole length of the line just about covers the 420-450-Mc. range. Output drops off slightly at the high end, as might be expected, with most of the tank circuit shorted out. Note that the two plates of each 6J6 are connected to the tank circuit by means of  $\frac{3}{8}$ -inch-wide copper strip, for negligible lead inductance.

The unit is mounted on the top plate of a small-sized utility box, with antenna terminals (National FWG) coming out through one side. Small self-supporting r.f. chokes are inserted in each heater lead, and the cathode is connected to the heater (be sure it's the grounded side) at the socket. Another r.f. choke is in the B-plus lead from the cold end of the tank circuit. A grid

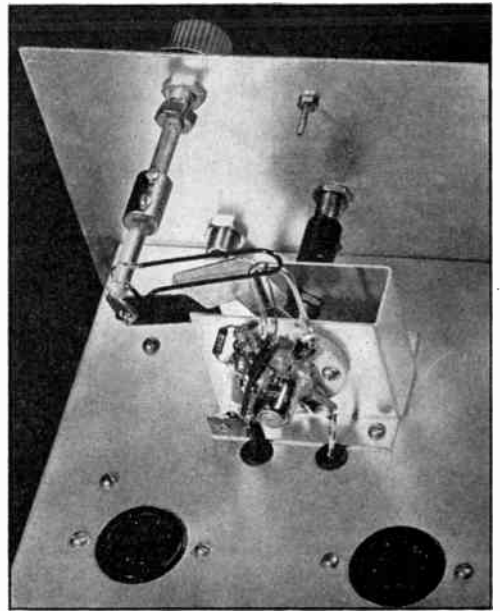


Fig. 15-26 — Close-up view of the detector assembly used in the 420-Mc. receiver. The frequency coverage is attained by moving a copper vane across the "U"-shaped detector tank circuit, maximum frequency being reached when the loop is covered by the vane. Antenna coupling is varied by means of the hairpin loop at the left. The two audio tubes were removed from their sockets to permit a clear view of the tuning system.

resistor is the only additional circuit component required.

The transmitter should be checked at low voltage, preferably 200 or under, until it is determined that it is operating correctly. At 250 volts it can run as high as 60 ma. without damaging the 6J6s, provided a load is kept across the antenna terminals. Since few experimenters will have an absorption-type wavemeter for 420 Mc., it is best to check the frequency with Lecher wires. Antenna coupling should be adjusted until maximum output is obtained, the least amount of coupling possible being used. Frequency checks should be made with the antenna attached, once the frequency of the oscillator is found to be close to the band.

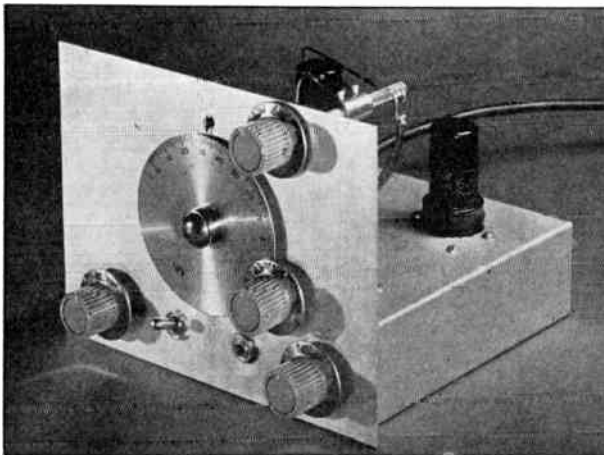


Fig. 15-25 — A superregenerative receiver for 420 Mc. The two lower controls are for variation of detector voltage and audio gain. The vernier dial controls the position of the tuning vane, while the knob at the top adjusts the antenna coupling.

Though the output of this little transmitter is less than two watts, it is sufficient for much interesting work. Since it is a simple matter to attain antenna gains of 15 db. or more at this frequency, a small amount of power can be made to produce surprising results.

### Superregenerative Receiver for 420 Mc.

Though the advanced experimenter will wish to use something more elaborate, the simple superregen is a good start on 420 Mc. The tuning system used in the receiver, see Fig. 15-26, could, however, be adapted to the tuning of the oscillator in a converter, if a suitable broad-band i.f. system is available.

It is obvious that coils and condensers, in the normal sense, are incapable of operation at 420 Mc. The tuning arrangement used in this receiver is the vane type, wherein a self-resonant loop of wire has its inductance reduced by passing a copper vane across the plane of the loop. The three-tube receiver shown in Figs. 15-25-15-28 uses a 955 superregenerative detector, with a loop of stiff wire connected between the plate and the grid-blocking condenser, in a manner similar to the conventional circuit used on lower frequencies. In details other than the tuning arrangement, the receiver is similar to self-quenched detectors used for years on lower v.h.f. bands.

The 955 socket is mounted on one side of a "U"-shaped bracket, with the grid and plate terminals at the top, so that the inductor extends above the top of the mounting bracket. The vane is attached to a 1/4-inch polystyrene rod which extends through a shaft bearing on the opposite side of the bracket from the tube

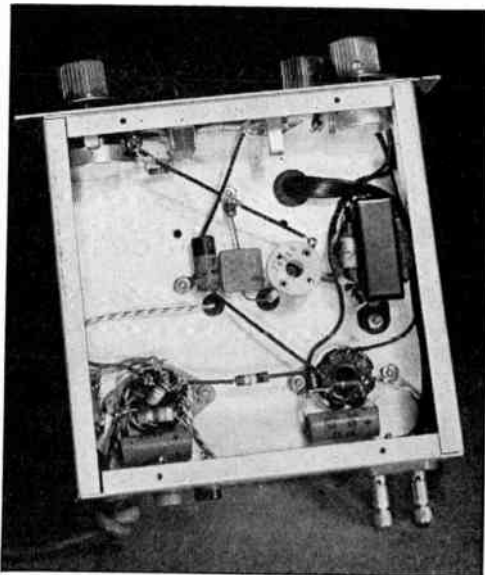


Fig. 15-27 — Bottom view of the 420-Mc. receiver. Loudspeaker terminals are at the lower left. At the right are the antenna terminals, from which a length of 300-ohm line runs up through the chassis to the antenna coupling loop.

socket. The vane is moved across the coil by means of a vernier dial, providing slightly more than 30 Mc. tuning range. The vane is not grounded, so that if it accidentally touches the coil it will not short the B-plus to ground.

Adjustable antenna coupling, absolutely necessary at this frequency, is provided by a hairpin loop which is attached to a front-panel

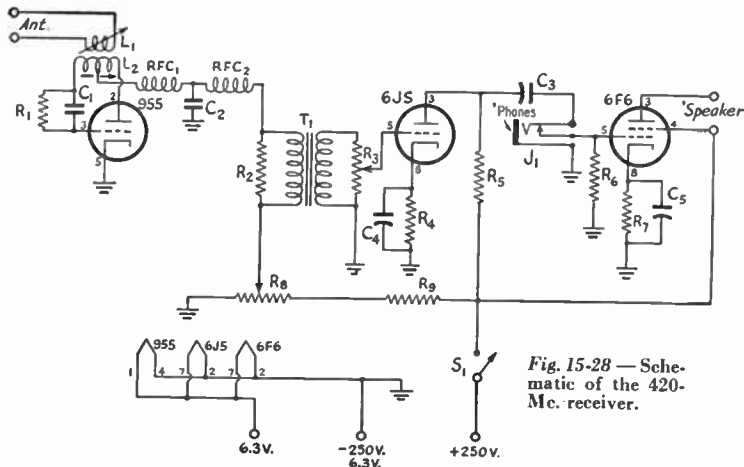


Fig. 15-28 — Schematic of the 420-Mc. receiver.

- C<sub>1</sub> — 47- $\mu$ fd. trimmer (National XLA-C).
- C<sub>2</sub> — 0.0033- $\mu$ fd. mica.
- C<sub>3</sub> — 0.01- $\mu$ fd. 400-volt paper.
- C<sub>4</sub>, C<sub>5</sub> — 10- $\mu$ fd. 25-volt electrolytic.
- R<sub>1</sub> — 1.2 megohms, 1/2 watt.
- R<sub>2</sub> — 47,000 ohms, 1/2 watt.
- R<sub>3</sub> — 0.5-megohm potentiometer.
- R<sub>4</sub> — 2200 ohms, 1/2 watt.
- R<sub>5</sub>, R<sub>6</sub> — 0.1 megohm, 1/2 watt.
- R<sub>7</sub> — 470 ohms, 1 watt.
- R<sub>8</sub> — 50,000-ohm potentiometer.

- R<sub>9</sub> — 22,000 ohms, 1/2 watt.
- L<sub>1</sub> — Hairpin loop; No. 12 wire with an inside diameter of 3/8 inch and a length of 2 1/2 inches.
- L<sub>2</sub> — Hairpin loop; No. 12 wire with an inside diameter of 1/2 inch and a length of 2 inches. Vane-tuned — see text and photograph.
- J<sub>1</sub> — Closed-circuit jack.
- RFC<sub>1</sub> — 4- $\mu$ h. r.f. choke (Millen 34300).
- RFC<sub>2</sub> — 10-mh. r.f. choke (Millen 34210).
- S<sub>1</sub> — S.p.s.t. toggle switch.
- T<sub>1</sub> — Interstage transformer.

control in a manner that will be clear from the front- and rear-view photographs. A length of 300-ohm line runs from the hairpin through a hole in the chassis to the antenna terminals on the back of the chassis.

Critical points in attaining smooth operation of the detector are the values of  $R_1$ ,  $C_2$  and

$R_2$ , and the condition of the 955 tube. Tubes which work satisfactorily on lower frequencies may fail to operate entirely on 420 Mc. The addition of r.f. chokes in the heater and cathode leads may be necessary in some cases. They should be similar to those used in the 420-Mc. transmitter.

## Wave Guides and Cavity Resonators

A wave guide is a conducting tube through which energy is transmitted in the form of electromagnetic waves. The tube is not considered as carrying a current in the same sense that the wires of a two-conductor line do, but rather as a *boundary* which confines the waves to the enclosed space. Skin effect prevents any electromagnetic effects from being evident outside the guide. The energy is injected at one end, either through capacitive or inductive coupling or by radiation, and is received at the other end. The wave guide then merely confines the energy of the fields, which are propagated through it to the receiving end by means of reflections against its inner walls.

The difficulty of visualizing energy transfer without the usual closed circuit can be relieved somewhat by considering the guide as being evolved from an ordinary two-conductor line.

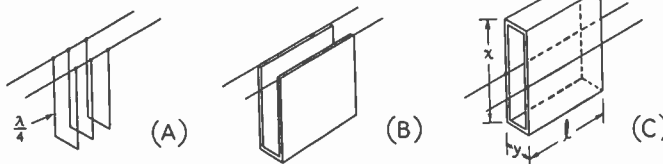


Fig. 15-29 — Evolution of a wave guide from a two-wire transmission line.

In Fig. 15-29A, several closed quarter-wave stubs are shown connected in parallel across a two-wire transmission line. Since the open end of each stub is equivalent to an open circuit, the line impedance is not affected by their presence. Enough stubs may be added to form a "U"-shaped rectangular tube with solid walls, as at B, and another identical "U"-shaped tube may be added edge-to-edge to form the rectangular pipe shown in Fig. 15-29C. As before, the line impedance still will not be affected. But now, instead of a two-wire transmission line, the energy is being conducted within a hollow rectangular tube.

This analogy to wave-guide operation is not exact, and therefore should not be taken too literally. In the evolution from the two-wire line to the closed tube the electric and magnetic field configurations undergo considerable change, with the result that the guide does not actually operate like a two-conductor line shunted by an infinite number of quarter-wave stubs. If it did, only waves of the proper length to correspond to the stubs would be propagated through the tube, but the fact is that such waves do *not* pass through the guide.

Only waves of shorter length — that is, higher frequency — can go through. The distance  $x$  represents half the *cut-off wavelength*, or the shortest wavelength that is unable to go through the guide. Or, to put it another way, waves of length equal to or greater than  $2x$  cannot be propagated in the guide.

A second point of difference is that the apparent length of a wave along the direction of propagation through a guide always is greater than that of a wave of the same frequency in free space, whereas the wavelength along a two-conductor transmission line is the same as the free-space wavelength (when the insulation between the wires is air).

### Operating Principles of Wave Guides

Analysis of wave-guide operation is based on the assumption that the guide material is a perfect conductor of electricity. Typical distributions of electric and magnetic fields in a rectangular guide are shown in Fig. 15-30. It will be observed that the intensity of the electric field is greatest at the center along the  $x$  dimension, diminishing to zero at the end walls. The latter

is a necessary condition, since the existence of any electric field parallel to the walls at the surface would cause an infinite current to flow in a perfect conductor. This represents an impossible situation.

Zero electric field at the end walls will result if the wave is considered to consist of two separate waves moving in zigzag fashion down the guide, reflected back and forth from the end walls as shown in Fig. 15-31. Just at the walls, the positive crest of one wave meets the negative crest of the other, giving complete cancellation of the electric fields. The angle of reflection at which this cancellation occurs depends upon the width  $x$  of the guide and the length of the waves; Fig. 15-31A illustrates the case of a wave considerably shorter than the cut-off wavelength, while B shows a longer wave. When the wavelength equals the cut-off value, the two waves simply bounce back and forth between the walls and no energy is transmitted through the guide.

The two waves travel with the speed of light, but since they do not travel in a straight line the energy does not travel through the guide as rapidly as it does in space. A further conse-

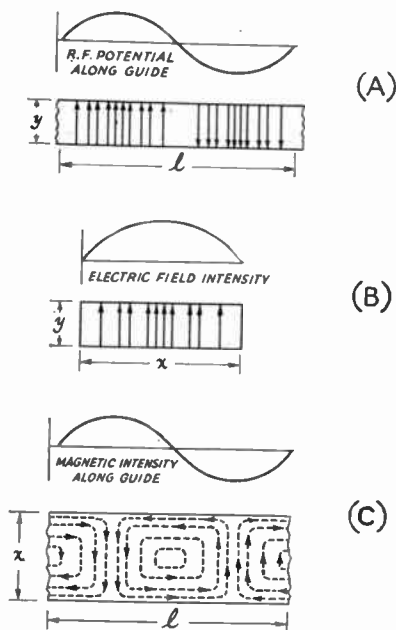


Fig. 15-30 — Field distribution in a rectangular wave guide. The  $TE_{1,0}$  mode of propagation is depicted.

quence of the repeated reflections is that the points of maximum intensity or wave crests are separated more along the line of propagation in the guide than they are in the two separate waves. In other words, the wavelength in the guide is greater than the free-space wavelength. This is also shown in Fig. 15-31.

**Modes of Propagation**

Fig. 15-30 represents a relatively simple distribution of the electric and magnetic fields. There is in general an infinite number of ways in which the fields can arrange themselves in a guide so long as there is no upper limit to the frequency to be transmitted. Each field configuration is called a *mode*. All modes may be separated into two general groups. One group, designated *TM* (*transverse magnetic*), has the magnetic field entirely transverse to the direction of propagation, but has a component of electric field in that direction. The other type, designated *TE* (*transverse electric*) has the electric field entirely transverse, but has a component of magnetic field in the direction of propagation. *TM* waves are sometimes called *E* waves, and *TE* waves are sometimes called *H* waves, but the *TM* and *TE* designations are preferred.

The particular mode of transmission is identified by the group letters followed by two subscript numerals; for example,  $TE_{1,0}$ ,  $TM_{1,1}$ , etc. The number of possible modes increases with frequency for a given size of guide. There is only one possible mode (called the *dominant mode*) for the lowest frequency that can be transmitted. The dominant mode is the one generally used in practical work.

**Wave-Guide Dimensions**

In the rectangular guide the critical dimension is  $x$  in Fig. 15-29; this dimension must be more than one-half wavelength at the lowest frequency to be transmitted. In practice, the  $y$  dimension usually is made about equal to  $\frac{1}{2}x$  to avoid the possibility of operation at other than the dominant mode.

Other cross-sectional shapes than the rectangle can be used, the most important being the circular pipe. Much the same considerations apply as in the rectangular case.

Wavelength formulas for rectangular and circular guides are given in the following table, where  $x$  is the width of a rectangular guide and  $r$  is the radius of a circular guide. All figures are in terms of the dominant mode.

	Rectangular	Circular
Cut-off wavelength.....	$2x$	$3.41r$
Longest wavelength transmitted with little attenuation.....	$1.6x$	$3.2r$
Shortest wavelength before next mode becomes possible.....	$1.1x$	$2.8r$

**Cavity Resonators**

At low and medium radio frequencies resonant circuits usually are composed of "lumped" constants of  $L$  and  $C$ ; that is, the inductance is concentrated in a coil and the capacitance concentrated in a condenser. However, as the frequency is increased, coils and condensers must be reduced to impractically small physical dimensions. Up to a certain point this difficulty may be overcome by using linear circuits but even these fail at extremely high frequencies. Another kind of circuit particularly applicable at wavelengths of the order of centimeters is the *cavity resonator*, which may be looked upon as a section of a wave guide with the dimensions chosen so that waves of a given length can be maintained inside.

The derivation of one type of cavity resonator from an ordinary  $LC$  circuit is shown in Fig. 15-32. As in the case of the wave-guide derivation, this picture must be accepted with some reservations, and for the same reasons.

Considering that even a straight piece of wire has appreciable inductance at very-high fre-

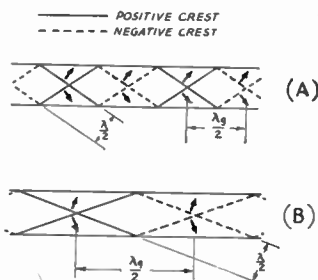


Fig. 15-31 — Reflection of two component waves in a rectangular guide.  $\lambda$  = wavelength in space,  $\lambda_g$  = wavelength in guide. Direction of wave motion is perpendicular to the wave front (crests) as shown by the arrows.

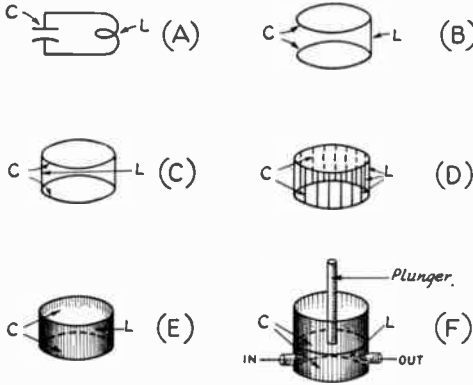


Fig. 15-32 — Steps in the derivation of a cavity resonator from a conventional coil-and-condenser tuned circuit.

quencies, it may be seen in Fig. 15-32A and B that a direct short across a two-plate condenser with air dielectric is the equivalent of a tuned circuit with a typical coiled inductance. With two wires between the plates, as shown in Fig. 15-32C, the circuit may be thought of as a resonant-line section. For d.c. or even low frequency r.f., this line would appear as a short across the two condenser plates. At the ultra-high frequencies, however, such a section of line a quarter wavelength long would appear as an open circuit when viewed from one of the plates with respect to the other end of the section.

Increasing the number of parallel wires between the plates of the condenser would have no effect on the equivalent circuit, as shown at D. Eventually, the closed figure at E will be developed. Since each wire which is added in D is like connecting inductances in parallel, the total inductance across the condenser becomes increasingly smaller as the solid form is approached, and the resonant frequency of the figure therefore becomes higher.

If energy now is introduced into the cavity in a manner such as that shown at F, the circuit will respond like any equivalent coil-condenser tank circuit at its resonant frequency. A cavity resonator may therefore be used as a u.h.f. tuning element, along with a vacuum tube of suit-

able design, to form the main components of an oscillator circuit which will be capable of functioning at frequencies considerably beyond the maximum limits possible when conventional tubes, coils and condensers are employed.

Other shapes than the cylinder may be used as resonators, among them the rectangular box, the sphere, and the sphere with re-entrant cones, as shown in Fig. 15-33. The resonant frequency depends upon the dimensions of the cavity and the mode of oscillation of the waves (comparable to the transmission modes in a wave guide). For the lowest modes the resonant wavelengths are as follows:

Cylinder.....	2.61r
Square box.....	1.41l
Sphere.....	2.28r
Sphere with re-entrant cones.....	4r

The resonant wavelengths of the cylinder and square box are independent of the height when the height is less than a half-wavelength. In other modes of oscillation the height must be a multiple of a half-wavelength as measured inside the cavity. Fig. 15-32F shows how a cylindrical cavity can be tuned when operating in such a mode. Other tuning methods include placing adjustable tuning paddles or "slugs" inside the cavity so that the standing-wave pattern of the electric and magnetic fields can be varied.

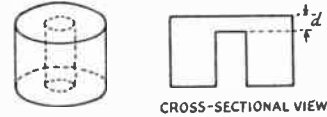


Fig. 15-31 — Re-entrant cylindrical cavity resonator.

A form of cavity resonator in wide practical use is the re-entrant cylindrical type shown in Fig. 15-34. It is useful in connection with vacuum-tube oscillators of the types described for u.h.f. use earlier in this chapter. In construction it resembles a concentric line closed at both ends with capacitance loading at the top, but the actual mode of oscillation may differ considerably from that occurring in coaxial lines. The resonant frequency of such a cavity depends upon the diameters of the two cylinders and the distance *d* between the ends of the inner and outer cylinders.

Compared to ordinary resonant circuits, cavity resonators have extremely-high *Q*. A value of *Q* of the order of 1000 or more is readily obtainable, and *Q* values of several thousand can readily be secured with good design and construction.

**Coupling to Wave Guides and Cavity Resonators**

Energy may be introduced into or abstracted from a wave guide or resonator by means of either the electric or magnetic field. The energy transfer frequently is through a coaxial line, two methods for coupling to which

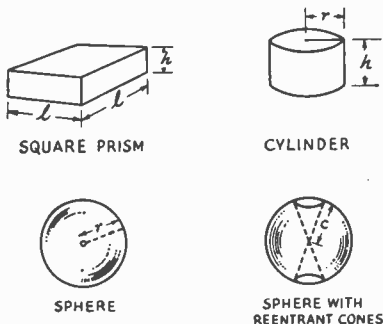


Fig. 15-33 — Forms of cavity resonators.

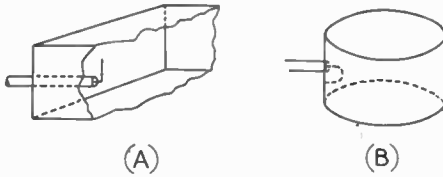


Fig. 15-35 — Coupling to wave guides and resonators.

are shown in Fig. 15-35. The probe shown at A is simply a short extension of the inner conductor of the coaxial line, so oriented that it is parallel to the electric lines of force. The

loop shown at B is arranged so that it encloses some of the magnetic lines of force. The point at which maximum coupling will be secured depends upon the particular mode of propagation in the guide or cavity; the coupling will be maximum when the coupling device is in the most intense field.

Coupling can be varied by turning either the probe or loop through a 90-degree angle. When the probe is perpendicular to the electric lines the coupling will be minimum; similarly, when the plane of the loop is parallel to the magnetic lines the coupling will have its least possible value.

### Amateur Microwave Technique

All the microwave bands allotted to amateurs have been used experimentally for communication purposes. Complete description of the equipment used is beyond the scope of this text, but reference is made to various articles which have appeared in *QST*, describing the gear devised by the amateur pioneers in this field.

For the experimentally inclined, our microwave assignments represent a challenge to amateur ingenuity. Who can say but greater use of these frequencies will repeat past history, turning up propagation peculiarities and potential uses which will make these bands as coveted a region as our "communication frequencies" are considered today?

The first amateur microwave communication was carried on by Merchant and Harrison, W6BMS/2 and W2LGF, who assembled the gear shown in Fig. 15-36 in time to communicate with each other on November 15, 1945 — the date that the microwave bands were officially opened to amateur experimentation. They used two klystron tubes, one as a frequency-modulated transmitter oscillator, the other as a local oscillator for receiving. The latter worked in conjunction with a crystal mixer, into a 30-Mc. i.f. in the form of an FM receiver.

The 2300-Mc. amateur assignment was first used for communication by Koch and Floyd, W9WHM/2 and W6OJK/2, who used light-house tubes in simple transceivers, both of which are shown in Fig. 15-37. Their antenna systems used parabolic reflectors, one being made of wire screening attached to a wooden frame, and the other, also shown in the photograph, was simply an electric-heater assembly, with the microwave dipole substituted for the heater element.

Amateur communication on 10,000 Mc. was first accomplished by Atwater and McGregor, W2JN and W2RJM, who modified 723-A/B klystrons to permit their operation in the amateur band. They are shown, with one of their equipment set-ups, in Fig. 15-38. A somewhat similar arrangement was used by

W4HPJ/3 and W6IFE/3 to extend the distance record, and has since been employed by W6IFE in opening the 3300-Mc. band to amateur use, except that the tube used in the latter instance was a 707-B with an external cavity.

The highest frequency ever used in amateur work is 21,000 Mc., first employed by Sharbaugh and Watters, W1NVL/2 and W9SAD/2, whose laboratory set-up is shown in Fig. 15-39. The r.f. generator, for transmitting and receiving, was a developmental tube designated as the Z-668, a velocity-modulated tube of the reflex type. Communication was carried on, two-way, over a distance of 800 feet.

A list of *QST* references, arranged according to the amateur band concerned, follows. It should be emphasized that the equipment



Fig. 15-36 — The first amateur microwave communication was accomplished by W6BMS (left) and W2LGF, who used two sets of similar equipment to open the 5300-Mc. amateur band on November 15, 1945, the date that the first microwave bands were released for amateur use.

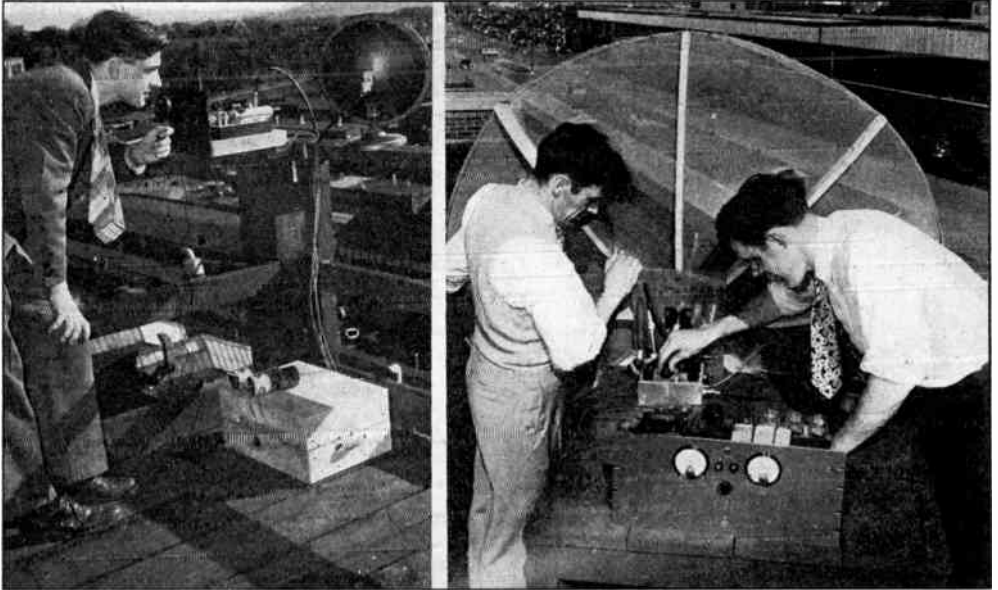


Fig. 15-37—The 2300-Mc. band was first employed for amateur communication by W6OJK (left) and W9WHM (extreme right). Antenna systems employed a standard electric-heater unit and a handmade screen-lined parabola.

described in these reports is experimental in nature. In most instances it represents only one of several ways in which microwave communication equipment might be built. The distances covered in the pioneering work just mentioned are not, for the most part, indicative of the maximum working range, since exploration of the particular band in question was the end in view when the experiments were conducted, rather than the covering of any long distances.

#### Bibliography

1215 Mc. — "World Above 50 Mc." (W1BBM), May 1947 *QST*, page 136. Also July 1947 *QST*, page 136.



Fig. 15-38 — W2RJM (left) and W2JN, with one of the equipments used in pioneering work on 10,000 Mc.

2300 Mc. — Koch and Floyd, "CQ — 2400 Mc.," July 1946 *QST*, page 32. Also "World Above 50 Mc." (W6IFE), Aug. 1947 *QST*, page 128.  
3300 Mc. — "World Above 50 Mc." (W6IFE), Aug. 1947 *QST*, page 128.

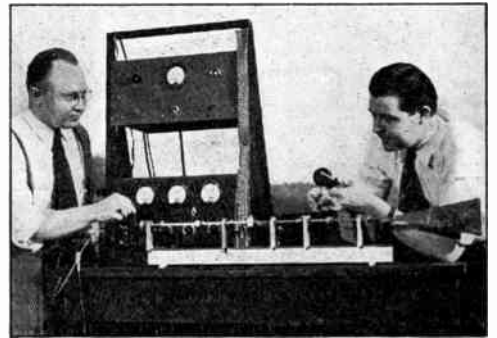


Fig. 15-39 — W1NVL (left) and W9SAD with the equipment used to work a distance of 800 feet on the highest frequency ever used for amateur communication — 21,000 Mc. Antenna systems employed a parabolic reflector at one end and a horn radiator at the other.

5250 Mc. — Merchant and Harrison, "Duplex 'Phone on 5300 Mc.," Jan. 1946 *QST*, page 19.  
10,000 Mc. — McGregor and Atwater, "Dishing Out the Milliwatts on 10 KMc.," Feb. 1947 *QST*, page 58. Also "World Above 50 Mc." (W4HPJ/3, W6IFE/3), Sept. 1946 *QST*, page 152.  
21,000 Mc. — Sharbaugh and Watters, "Our Best DX — 800 Feet!" Aug. 1946 *QST*, page 19.



# Measuring Equipment

To comply with FCC regulations it is necessary that the amateur station be equipped to make a few relatively simple measurements. For example, the regulations require that means be available for checking the transmitter frequency to make sure that it is inside the band. This means must be independent of the frequency control of the transmitter itself; it is not enough to depend on, say, the calibration of a crystal in the crystal-controlled oscillator that drives the transmitter. In addition, it is necessary to make sure that the plate power input to the final stage of the transmitter does

not exceed one kilowatt. The regulations also impose certain requirements with respect to plate-supply filtering, stability and purity of the transmitted signal, and depth of modulation in the case of 'phone transmission.

In many cases all these measurements can be made to a satisfactory degree of accuracy with no more auxiliary equipment than the regular station receiver. However, a better job usually can be done by building and calibrating some relatively simple test gear. Too, the progressive amateur is interested in instruments as an aid to better performance.

## Frequency Measurement

Frequency-measuring equipment can be divided into two broad classes: oscillators of various types generating signals of known frequency that can be compared with the signal whose frequency is unknown, and adjustable resonant circuits.

Instruments in the first classification are the more accurate. Two types are commonly used by amateurs, the **secondary frequency standard** and the **heterodyne frequency meter**. The secondary frequency standard, nearly always crystal-controlled, usually generates a frequency of 100 kc. and employs a circuit that is rich in harmonic output. As a result, it supplies a series of frequencies, all multiples of 100 kc., which provides accurate calibration points throughout the communications spectrum. The more elaborate instruments of this type are provided with frequency dividers (multivibrators) to supply intermediate calibration points; a divisor commonly used is 10, thus furnishing signals at intervals of 10 kc. when the fundamental frequency is 100 kc.

The heterodyne frequency meter is a variable-frequency oscillator which is calibrated in frequency against a secondary standard or by other means. The oscillator usually is designed to cover the lowest frequency band in which measurements are to be made; measurements then can be made in higher-frequency bands by using the harmonic output of the oscillator. For example, when the oscillator is set to 3560 kc. its second harmonic is 7120 kc., its fourth harmonic is 14,240 kc., and so on. The proper frequency reading is determined by knowing the fundamental frequency of the oscillator and the number of the harmonic that falls in the desired frequency range.

Both the secondary standard and the heterodyne meter are ordinarily used in conjunction with a receiver, the signals from the instruments being picked up just as though they were from distant stations. In the case of the secondary standard, the frequency of the unknown signal can be determined by locating it between two known 100-kc. or 10-kc. multiples. With the heterodyne meter, the frequency is measured by adjusting the frequency meter until its signal is at zero beat with the signal of unknown frequency, after which the frequency can be read from the frequency-meter calibration.

Since the secondary standard operates on a fixed frequency and can be crystal-controlled, its accuracy can be quite high. However, it simply establishes a series of known frequencies at regular intervals, and thus auxiliary methods must be used for determining frequencies between the known points. The series of fixed frequencies, when they mark the edges of amateur bands (as they do if they are multiples of 100 kc.), is quite sufficient for amateur work because the information that is required is whether or not the transmitter frequency is *inside* the band limits, rather than the exact frequency itself. On the other hand, the heterodyne frequency meter, while capable of giving readings at any point in its calibrated range, is inherently less accurate than the crystal-controlled standard because of the lower stability of the variable-frequency oscillator.

In the absence of more elaborate frequency-measuring equipment, a calibrated receiver may be used to indicate the approximate frequency of the transmitter. If the receiver is well made and has good inherent stability, a

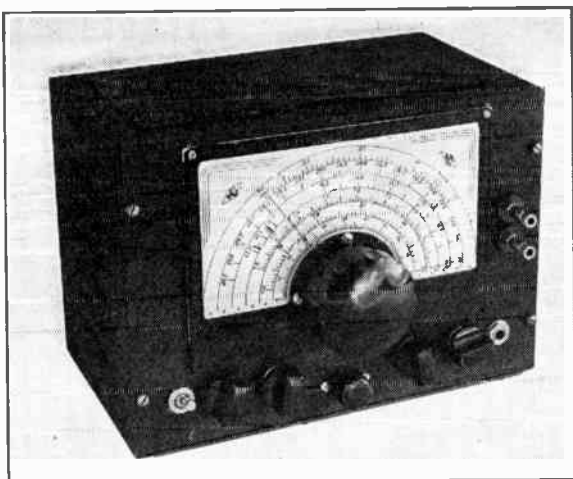


Fig. 16-1 — Heterodyne frequency meter with built-in harmonic amplifier, crystal calibrator, and detector, usable on all amateur bands up to 144 Mc. Controls along the bottom of the panel are, from left to right, crystal-oscillator on-off switch, 100/1000-kc. crystal-selector switch, calibration range switch, drift compensator, harmonic-amplifier range switch, output control, headphone jack. The two output terminals are along the right-hand edge.

bandspread dial calibration can be relied upon to within perhaps 0.2 per cent. For most accurate measurement maximum response in the receiver should be determined by means of a carrier-operated tuning indicator (such as an S-meter), the receive beat oscillator being turned off.

When checking the transmitter frequency the receiving antenna should be disconnected, so that the signal will not overload or "block" the receiver. If the receiver still blocks without an antenna the frequency may be checked by turning off the power amplifier and tuning in the oscillator alone.

### ● HETERODYNE FREQUENCY METER AND CRYSTAL CALIBRATOR

The basis of the heterodyne frequency meter is a completely-shielded oscillator with a precise frequency calibration. The oscillator must be so designed and constructed that it can be accurately calibrated and will retain its calibration over long periods of time.

The oscillator used in the frequency meter must be very stable. Mechanical considerations are most important in its construction. No matter how good the instrument may be electrically, its accuracy cannot be depended upon if the mechanical construction is flimsy. Inherent frequency stability can be improved by avoiding the use of phenolic compounds and thermoplastics (bakelite, polystyrene, etc.) in the oscillator circuit, employing only high-grade ceramics instead. Plug-in coils ordinarily are not acceptable; instead, a solidly-built and firmly-mounted tuned circuit should be permanently installed. The oscillator panel and chassis should be as rigid as possible.

A stable oscillator circuit suitable for use in a heterodyne frequency meter is the electron-coupled circuit. It is possible to take output from the plate with but negligible effect on the frequency of the oscillator, and strong harmonics are generated in the plate circuit.

The heterodyne frequency meter shown in Figs. 16-1 to 16-4, inclusive, combines a number of features that make it suitable for accurate frequency measurement in the amateur bands from 3.5 to 144 Mc. As shown in the circuit diagram, Fig. 16-3, it consists of a 6SK7 electron-coupled oscillator followed by a 6AC7 amplifier that is used to intensify the higher-frequency harmonics. A second 6SK7 oscillator, using a crystal of the type that operates at either 100 or 1000 kc., provides check-points and a means for calibration of the frequency meter. A 6SL7 is incorporated to amplify the crystal harmonics and to provide a detector circuit in which the outputs of the

crystal and e.c. oscillators can be mixed for calibration purposes. The detector also enables direct checking of the transmitter frequency.

The fundamental tuning range of the heterodyne oscillator is from 3500 to 4000 kc. By means of  $S_1$  this range can be changed to 3500-3720 kc., approximately, so that the eighth harmonic just covers the 28-29.7-Mc. band. This avoids excessively critical tuning at the higher frequencies. The main tuning condenser,  $C_2$ , is connected across all of  $L_1$  for the larger range and is connected to a tap on  $L_1$  for the smaller to increase the bandspread. Simultaneously, an adjustable padding condenser,  $C_1$ , is switched in so that the oscillator frequency will be exactly 3500 kc. with  $C_2$  set at maximum capacitance regardless of the switch position.  $C_4$  is a fixed padding condenser to make the circuit fairly high  $Q$ , and  $C_5$  is the band-setting condenser.  $C_3$  is a small padder adjustable from the panel; its function is to permit resetting the oscillator frequency to the calibration points provided by the crystal oscillator and thus take care of drift effects.

The 6AC7 plate circuit is broadly tuned by means of switched coils resonating, with the circuit capacitances, at 144, 50 and 28 Mc., and thus increases the harmonic strength on those bands. A radio-frequency choke is connected to the fourth switch position; this gives ample signal strength at 14 Mc. and lower frequencies.  $R_5$  makes it possible to reduce the strength of the signal from the meter to the value desired for measurement purposes.

In the crystal-oscillator circuit,  $S_2$  changes the frequency from 100 to 1000 kc. or vice versa. In the 100-kc. position  $C_{14}$  is connected across the crystal to provide means for adjusting the frequency to exactly 100 kc.

## WWV SCHEDULES

Standard radio and audio frequencies are broadcast from WWV, the station of the Central Radio Propagation Laboratory, National Bureau of Standards, Washington, D. C., on the following schedule:

Freq. in Mc.	Time, EST	Modulation, c.p.s.
2.5	7 P.M. to 9 A.M.	1 and 440
5	7 P.M. to 7 A.M.	1 and 440
5	7 A.M. to 7 P.M.	1, 440 and 4000
10	Continuously	1, 440 and 4000
15	Continuously	1, 440 and 4000
20	Continuously	1, 440 and 4000
25	Continuously	1, 440 and 4000
30	Continuously	1 and 440
35	Continuously	1

The 1-c.p.s. modulation is a 0.005-second pulse, the beginning of which marks each second to an accuracy of one part in 1,000,000. The pulse is omitted on the 59th second of every minute.

The accuracy of the radio and audio frequencies is within one part in 50,000,000. The audio frequencies are interrupted exactly on the hour and each five minutes thereafter; they are resumed in precisely one minute. During each silent interval the time is given in telegraphic code. A station announcement is given in voice on the hour and half hour.

As shown in Figs. 16-2 and 16-4, the frequency meter is built on a chassis folded from a piece of sheet aluminum, the dimensions being 9 inches wide by  $5\frac{1}{2}$  inches deep by 2 inches high. Half-inch lips are bent along the bottom edges of the walls to make the chassis more rigid. The cabinet into which the meter fits is  $10 \times 7 \times 6$  inches. The main tuning condenser,  $C_2$ , is mounted on an aluminum bracket above the chassis and the coil,  $L_1$ , is similarly mounted below it. The band-setting condenser,  $C_6$ , is mounted on the chassis behind the coil, with its shaft protruding through the chassis for screwdriver adjustment. Trimmer  $C_3$  is mounted on the panel and is adjusted by a knob underneath the main tuning dial. The coil is shielded from the amplifier section by the small aluminum baffle shown in Fig. 16-4. The bandspread padder,  $C_1$ , is mounted to the left of the oscillator range switch and, like  $C_6$ , is screwdriver-adjusted from the top of the chassis. Wiring in the oscillator tuned circuit, including the switch, should be short, direct, and as rigid as possible.

The 100-kc. oscillator trimmer,  $C_{14}$ , does not require frequent adjustment and is therefore mounted on the rear edge of the chassis, close to the crystal unit.  $C_{16}$ , the plate tuning condenser for 1000 kc., is adjusted from the top of the chassis and is mounted to the right of the crystal-oscillator socket in Fig. 16-4.

In putting the instrument into operation, the crystal oscillator should

be checked first. Connect a length of wire to the crystal output terminal (from  $C_{18}$ ) and listen on a receiver over the range from 3.5 to 5 Mc. With  $S_2$  in the 1000-kc. position, signals should appear at 4000 and 5000 kc., and with  $S_2$  in the 100-kc. position signals should be heard every 100 kc. Tune in WWV on 5000 kc., wait for the modulation to go off, and then adjust  $C_{14}$  for zero beat. This sets the oscillator to precisely 100 kc. In the 1000-kc. position there may be a difference of a few kilocycles between the frequency of WWV and the 5-Mc. harmonic, but this is not a serious condition since the 1000-kc. crystal oscillator is used only as an aid in identification of the 100-kc. harmonics.

To set the range of the e.c. oscillator, put  $S_2$  in the 1000-kc. position, plug a pair of 'phones into  $J_1$ , set  $S_2$  on the maximum range position ( $C_2$  across all of  $L_1$ ), and set  $C_2$  near minimum capacitance. Adjust  $C_6$  until the 4000-kc. harmonic is heard. Then switch  $S_2$  to 100 kc. and tune  $C_2$  toward maximum, counting off five additional 100-kc. signals.  $C_6$  may then be re-adjusted to bring the 3500-kc. marker close to the end of the tuning-dial scale. The 100-kc. points may then be marked off on the scale or the readings recorded. The second tuning range is adjusted by setting  $C_2$  at 3500 kc. on the first range, then setting  $S_1$  so that  $C_2$  is connected to the tap, and adjusting  $C_1$  (without touching  $C_2$ ) so that the 3500-kc. marker is brought to the same point on the dial. The second range may be calibrated by the 100-kc. points in the same way as the first.

Calibration points may be obtained between the 100-kc. markers on both ranges by

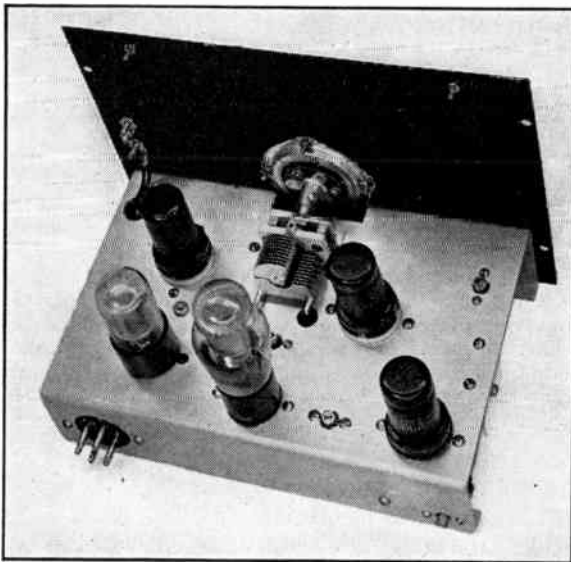


Fig. 16-2 — Inside view of the heterodyne frequency meter. The main tuning condenser is in the center with the e.c. oscillator tube to its right. The crystal-oscillator tube is at the upper left, and the twin-triode amplifier-detector is in line with it at the rear edge (foreground) of the chassis. The 6AC7 is in the lower-right corner.

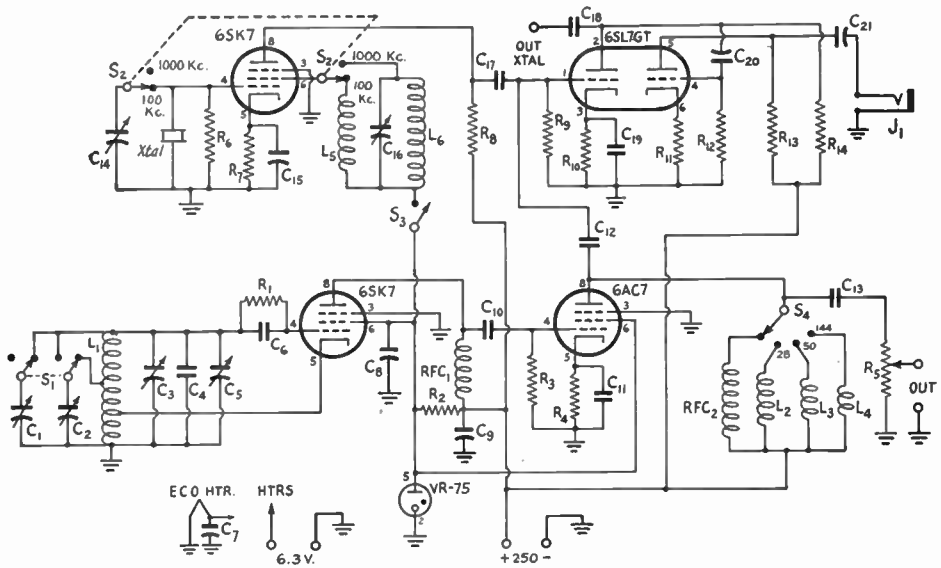


Fig. 16-3 — Circuit diagram of the heterodyne frequency meter.

C<sub>1</sub>, C<sub>5</sub> — 75- $\mu$ fd. variable.  
 C<sub>2</sub>, C<sub>16</sub> — 100- $\mu$ fd. variable.  
 C<sub>3</sub>, C<sub>14</sub> — 25- $\mu$ fd. variable.  
 C<sub>4</sub> — 220- $\mu$ fd. mica.  
 C<sub>6</sub>, C<sub>10</sub>, C<sub>13</sub> — 100- $\mu$ fd. mica.  
 C<sub>7</sub>, C<sub>8</sub>, C<sub>9</sub>, C<sub>15</sub>, C<sub>20</sub>, C<sub>21</sub> — 0.01- $\mu$ fd. paper.  
 C<sub>11</sub>, C<sub>19</sub> — 470- $\mu$ fd. mica.  
 C<sub>12</sub> — 10- $\mu$ fd. mica.  
 C<sub>17</sub> — 0.001- $\mu$ fd. mica.  
 C<sub>18</sub> — 47- $\mu$ fd. mica.  
 R<sub>1</sub>, R<sub>3</sub>, R<sub>9</sub>, R<sub>12</sub> — 0.47 megohm,  $\frac{1}{2}$  watt.  
 R<sub>2</sub> — 10,000 ohms, 1 watt.  
 R<sub>4</sub> — 330 ohms, 1 watt.  
 R<sub>5</sub> — 25,000-ohm potentiometer.  
 R<sub>6</sub> — 4.7 megohms,  $\frac{1}{2}$  watt.  
 R<sub>7</sub> — 470 ohms, 1 watt.  
 R<sub>8</sub> — 0.22 megohm, 1 watt.  
 R<sub>10</sub> — 10,000 ohms, 1 watt.  
 R<sub>11</sub> — 1500 ohms, 1 watt.

R<sub>13</sub>, R<sub>14</sub> — 0.1 megohm,  $\frac{1}{2}$  watt.  
 L<sub>1</sub> — 18 turns No. 18 on 1-inch form, length  $1\frac{1}{2}$  inches. Cathode tap 5 turns from ground end; band-spread tap 11 turns from ground.  
 L<sub>2</sub> — 24 turns No. 18 enam. close-wound on  $\frac{1}{4}$ -inch form.  
 L<sub>3</sub> — 11 turns No. 18 enam. close-wound on  $\frac{1}{4}$ -inch form.  
 L<sub>4</sub> — 2 turns No. 16 spaced  $\frac{1}{2}$  inch, diameter  $\frac{1}{4}$  inch.  
 L<sub>5</sub> — 8-mh. coil (r.f. choke).  
 L<sub>6</sub> — 1 pie of 4-pie 2.5-mh. r.f. choke.  
 J<sub>1</sub> — Open-circuit jack.  
 RFC<sub>1</sub>, RFC<sub>2</sub> — 2.5-mh. r.f. choke.  
 S<sub>1</sub> — 2-position 2-pole ceramic wafer switch.  
 S<sub>2</sub> — 2-position 2-pole switch (bakelite insulation satisfactory).  
 S<sub>3</sub> — S.p.s.t. toggle.  
 S<sub>4</sub> — 4-position 1-pole ceramic wafer switch.  
 XTAL — 100/1000-kc. crystal unit (Bliley SMC-100).

using a receiver as an auxiliary. For example, if the receiver is adjusted to pick up the fifth harmonic of the e.c. oscillator (17.5 to 20 Mc.) and the harmonic is beat against 100-kc. points from the crystal oscillator in that range, 100-kc. intervals on the fifth harmonic will give 20-kc. intervals on the fundamental. With a straight-line capacitance condenser at C<sub>2</sub>, the relationship between dial divisions and frequency is almost linear, and marking off the dial at the proper intervals between actual calibration points will result in a calibration of sufficient accuracy.

The various amateur bands are covered by the following harmonics: 3.5-4 Mc., fundamental; 7-7.3 Mc., 2nd harmonic; 14-14.4 Mc., 4th; 27.185-27.245 Mc., 7th; 28-29.7 Mc., 8th; 50-54 Mc., 14th; 144-148 Mc., 40th. At lower frequencies a short length of wire connected to the output terminal will give ample signal strength under average conditions, but in the v.h.f. range closer coupling — such as running the wire in close proximity to the receiving antenna lead, or actually connecting it

to the antenna post through a small fixed condenser — may be necessary to get a good signal.

With an instrument of this type the edges of amateur bands may be quite accurately determined, if care is used in setting the 100-kc. oscillator to WWV and equal care is used in setting the e.c. oscillator scale to the 100-kc. crystal points. C<sub>3</sub> may be used for the latter purpose each time the meter is used, and particularly during the first 30 minutes or so of operation when the temperature of the equipment is rising. The accuracy at intermediate points will depend upon the accuracy of the original calibration; it should be possible to read within 0.05 per cent under normal conditions by using the "drift corrector," C<sub>3</sub>.

### ● ABSORPTION FREQUENCY METERS

The simplest possible frequency-measuring device is a resonant circuit, tunable over the desired frequency range and having its tuning dial calibrated in terms of frequency. Such a

frequency meter operates by extracting a small amount of energy from the oscillating circuit to be measured, the frequency then being determined by tuning the frequency-meter circuit to resonance and reading the frequency from the calibrated scale. This method is not capable of as high accuracy as the heterodyne methods for two reasons: First, the resonance indication is relatively "broad" as compared to the zero beat of a heterodyne; second, the necessarily close coupling between the frequency meter and the circuit being measured causes some detuning in both circuits, with the result that the calibration of the frequency-meter circuit depends to some degree on the coupling to the circuit being measured.

It is necessary to have some means for indicating resonance with an absorption frequency meter. When such a meter is used for checking a transmitter, the plate current of the tube connected to the circuit being checked can provide the resonance indication. When the frequency meter is tuned through resonance the plate current will rise, and if the frequency meter is loosely coupled to the tank circuit the plate current will simply give a slight upward flicker as the meter is tuned through resonance. The greatest accuracy is secured when the loosest possible coupling is used.

A receiver oscillator may be checked by tuning in a steady signal and heterodyning it to give a beat-note as in ordinary c.w. reception. When the frequency meter is coupled to the oscillator coil and tuned through resonance the beat-note will change. Again, the coupling should be made loose enough so that a just-perceptible change in beat-note is observed when the meter is tuned through resonance.

Although the absorption-type frequency meter should not be depended upon for accurate measurement, it is a highly-useful instrument to have in the station even when better frequency-measuring equipment is available. Since it generates no harmonics itself, it will respond only to the frequency to which it is tuned. It is therefore indispensable for distinguishing between fundamental and various harmonics, and for detecting harmonics and parasitic oscillations. When provided with a sensitive resonance indicator it is also useful for detecting r.f. in undesired places such as power wiring, for making rough measurements of field strength in adjustment of antennas, and can likewise be used as a modulation monitor.

An approximate calibration — usually sufficient — may be obtained by comparison with a calibrated receiver. The usual receiver dial calibration is

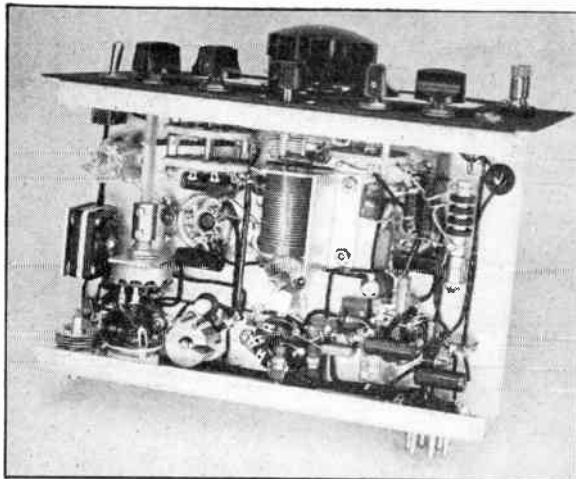


Fig. 16-4 — Underneath the chassis of the heterodyne frequency meter. The parts layout is discussed in the text.

sufficiently accurate. A simple oscillator circuit covering the same range as the frequency meter will be useful in calibration. Set the receiver to a given frequency, tune the oscillator to zero beat at the same frequency, and adjust the frequency meter to resonance with the oscillator as described above. This gives one calibration point. When a sufficient number of such points has been obtained a graph may be drawn to show frequency vs. dial settings on the frequency meter.

## ● A SENSITIVE ABSORPTION FREQUENCY METER

Figs. 16-5 to 16-7, inclusive, show an absorption frequency meter or "wavemeter" with a crystal-detector/milliammeter resonance indicator that provides a relatively high degree of sensitivity. As shown in Fig. 16-6, a

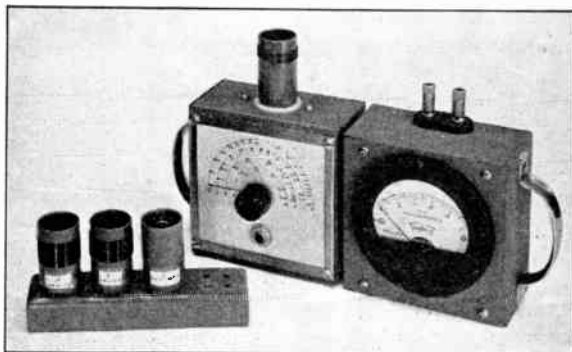


Fig. 16-5 — A sensitive absorption-type frequency meter with a crystal-detector rectifier and a d.c. milliammeter indicating circuit. The meter is housed in a separate compartment so that it may be used with other measuring devices. The cabinet and front cover are drilled and tapped to accommodate the mounting screws for a large-size chart frame; frequency calibrations are marked on cardboard held in place by the chart frame. A short strip of wood, drilled to match the coil-form prongs, is used as a rack for the coils. Meter-box connections are shown in Fig. 16-15.

resonant circuit is connected in series with a crystal detector and a 0-1 milliammeter. The tank coil,  $L_1$ , serves as the pick-up coil, and the crystal is tapped down on the inductance in order to improve the sensitivity and selectivity of the meter. Plug-in coils are provided so that the unit covers a frequency range from about 1 megacycle to 165 megacycles. Any type of fixed crystal detector may be used, but the v.h.f. types are recommended. The meter box shown at the right in Fig. 16-5 is the same unit

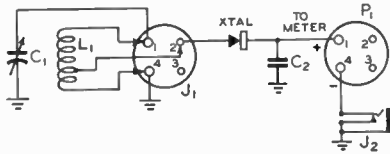


Fig. 16-6 — Circuit diagram of the absorption-type frequency meter.

$C_1$  — 140- $\mu$ fd. variable (Millen 22140).

$C_2$  — 0.0015- $\mu$ fd. midget mica.

$L_1$  — 1.22-4.0 Mc.: 70 turns No. 32 enameled wire, 1-inch diam.,  $\frac{1}{2}$  inch long. Tap 12 $\frac{1}{2}$  turns from grounded end.

— 4.0-13.5 Mc.: 20 turns No. 20 enameled wire, 1-inch diam.,  $\frac{9}{16}$  inch long. Tap 4 $\frac{1}{2}$  turns from grounded end.

— 13.2-44.0 Mc.: 5 turns No. 20 enameled wire, 1-inch diam.,  $\frac{5}{16}$  inch long. Tap 1 $\frac{1}{2}$  turns from grounded end.

— 39.8-165 Mc.: Hairpin loop of No. 14 wire,  $\frac{1}{2}$ -inch spacing, 2 inches long (total length including ends which fit down into the coil-form prongs). Tap 1 $\frac{1}{2}$  inches from grounded end.

All four coils wound on Millen 45004 coil forms.

$J_1$  — 4-prong tube socket.

$J_2$  — Closed-circuit jack.

$P_1$  — 4-prong male plug.

XTAL — Type 1N34.

that is used with the volt-ohm-milliammeter described later in this chapter.

The frequency meter is housed in a 2  $\times$  4  $\times$  4-inch metal box, the milliammeter being mounted in a separate box of the same size. The coil socket is on the top near the front edge, with the tuning condenser just below it inside the case. This arrangement keeps the tuned-circuit leads short. A handle is mounted on the side of the box for convenience in handling. A headphone jack is provided for monitoring 'phone transmissions. The unit may be calibrated as described in the preceding section.

A two- or three-foot antenna rod may be added to the unit to permit using the instrument for field-strength measurements. The antenna should be connected to the top end of the tank coil,  $L_1$ . The rod antenna is not required for ordinary frequency measurement, and its use may be undesirable when the frequencies of individual simultaneously-operating circuits are to be checked — as in the case of a multistage transmitter with frequency multipliers — because the antenna increases the sensitivity to such an extent that it may be difficult to identify the output of a particular circuit. It may be convenient to intercon-

nect the two units by means of a length of lamp cord or coaxial cable of any reasonable length (up to several hundred feet) when the meter is being used as a field-strength measuring device.

In addition to the uses mentioned in the preceding section, a meter of this type may be used for final adjustment of neutralization in r.f. amplifiers when loosely coupled to the plate tank coil.

## LECHER WIRES

At very-high and ultrahigh frequencies it is possible to determine frequency by actually measuring the length of the waves generated. The measurement is made by observing standing waves on a two-wire parallel transmission line or Lecher wires. Such a line shows pronounced resonance effects, and it is possible to determine quite accurately the current loops (points of maximum current). The physical distance between two consecutive current loops is equal to one-half wavelength. Thus the wavelength can be read directly in meters (39.37 inches = 1 meter; 0.3937 inch = 1 cm.), or in centimeters for the very-short wavelengths.

The Lecher-wire line should be at least a wavelength long — that is, 7 feet or more on 144 Mc. — and should be entirely air-insulated except where it is supported at the ends. It may be made of copper tubing or of wires stretched tightly. The spacing between wires should be about one to one-and-one-half inches. The positions of the current loops are found by means of a "shorting bar," which is simply a metal strip or knife edge which can be slid along the line to vary its effective length. The system can be used more conveniently and with greater accuracy if it is built up in per-

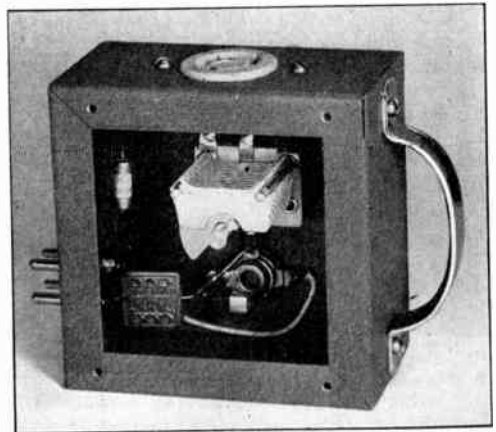


Fig. 16-7 — A rear view of the absorption-type frequency meter. The crystal is wired between the connector plug at the left and the coil socket at the top. The meter by-pass condenser is mounted between the plug and the grounded side of the 'phone jack. The variable-condenser terminals are connected directly to the coil socket.

manent fashion and provided with a shorting bar maintained at right angles to the wires (Fig. 16-8). The support may consist of two pieces of "1-by-2" pine fastened together with wood screws to form a "T"-girder, this arrangement being used to minimize bending of the wood when the wires are tightened.

A slider holds the shorting bar and acts as a guide to keep the wire spacing constant. A piece of wood hold in the hand can be used; it is an easy matter to regulate the pressure so that free movement is secured. A spring device may be arranged for the same purpose.

For convenience in measuring lengths directly in the metric system used for wavelength, the supporting beam may be marked off in decimeter (10-centimeter) units. A 10-centimeter transparent scale (obtainable at 5 & 10 cent stores) may be cemented to the slider, extending out from the front, so that readings can be taken to the nearest millimeter. The difference between any two readings gives the half-wavelength directly.

### Making Measurements

Resonance indications can be obtained in several different ways. Let us suppose the frequency of a transmitter is to be measured. A convenient and fairly sensitive indicator can be made by soldering the ends of a one-turn loop of wire, of about the same diameter as the transmitter tank coil, to a low-current flashlight bulb, then coupling the loop to the tank coil to give a moderately bright glow. A similar coupling loop should be connected to the ends of the Lecher wires and brought near the tank coil, as shown in Fig. 16-9. Then the shorting bar should be slid along the wires outward from the transmitter until the lamp gives a sharp dip in brightness. This point should be marked and the shorting bar moved out until a second dip is obtained. Marking the second spot, the distance between the two points can be measured and will be equal to half the wavelength. If the measurement is made in inches, the frequency will be

$$F_{Mc.} = \frac{5905}{\text{length (inches)}}$$

If the length is measured in meters,

$$F_{Mc.} = \frac{150}{\text{length (meters)}}$$

In checking a superregenerative receiver, the Lecher wires may be similarly coupled to the receiver coil. In this case the resonance indication may be obtained by setting the receiver just to the point where the hiss is obtained, then as the bar is slid along the wires a spot will be found where the receiver goes out of oscillation. The distance between two such spots is equal to a half-wavelength.

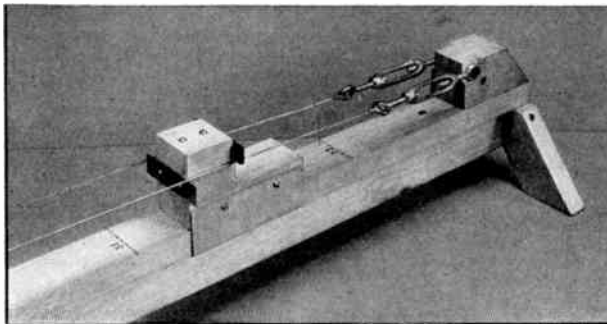


Fig. 16-8 — One end of a typical Lecher-wire system. The feet at each end keep the assembly from tipping over when in use. The wires terminate in airplane-type strain insulators at one end, and at the other in small turnbuckles for maintaining tension. The wire is No. 16 bare solid-copper antenna wire (hard-drawn). The turnbuckles are held in place by a  $\frac{3}{8} \times 2$ -inch bolt through the anchor block. This end of the line is thus short-circuited; it does not matter whether it is open or shorted, since the other end is the one connected to the pick-up loop.

In either case, the most accurate readings result only when the loosest possible coupling is used between the line and the tank coil. After taking a preliminary reading to find the regions along the line in which resonance occurs, loosen the coupling until the indications are just discernible and repeat the measurement. Unless this is done the tuning of the line will affect the frequency of the oscillator and inaccurate indications will be obtained. As the coupling is loosened the resonance points will become sharper, which is a further aid to accurate determination of the wavelength.

The shorting bar must be kept at right angles to the two wires. A sharp edge on the bar is desirable, since it not only helps make good contact but also definitely locates the *point* of contact.

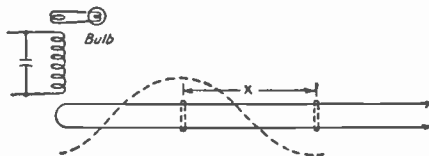


Fig. 16-9 — Coupling a Lecher-wire system to a transmitter tank coil. Typical standing-wave distribution is shown by the dashed line. The distance, *X*, between the positions of the shorting bar at the current loops equals one-half wavelength.

The accuracy with which frequency can be measured by such a system depends principally upon the technique of measurement. The necessity for using very loose coupling to the transmitter or receiver has already been mentioned. In addition, careful measurement of the exact distance between two current loops also is essential. Even if all other sources of error are eliminated, measurements within 0.1 per cent require an accuracy within 1 part in 1000, or 1 millimeter in one meter, in measuring the distance along the wires. This means that an accurate standard of length is necessary — a good steel tape, for instance — and that care must be used in determining the length exactly.

## Signal Monitoring

Every amateur station should make provision for checking the quality of the transmitter output. This requires that some means be available in the station for reproducing the conditions existing at a distant receiving station; that is, for reducing the strength of the signal from the transmitter to such a point that its characteristics can be examined without danger of false indications from overloading the receiving equipment.

The simplest method of checking the quality of c.w. transmissions is to use the regular station receiver. If the receiver is a superheterodyne the process may simply be that of reducing the r.f. gain to minimum and tuning to the transmitter frequency. If distant signals are stable and have "pure-d.c." tone in normal reception, then the local transmitter should too, when the receiver gain is reduced to the point where the receiver does not overload. If the signal is too strong with the r.f. gain "off," shorting the receiver antenna input terminals may reduce it to suitable proportions, or the mixer circuit in the receiver may be temporarily detuned to arrive at the same result.

An alternative method is to set the receiver on the next lower-frequency band than the one in use, then tune the receiver so that the second harmonic of its oscillator beats with the transmitter signal to produce the intermediate frequency. Higher-order harmonics also may be used for this purpose. With this harmonic method there is ordinarily no danger that the receiver will overload, because the r.f. and mixer tuned circuits are so far from resonance with the transmitter frequency. The setting of the tuning dial bears no direct relation to the transmitter frequency under these conditions, since the oscillator harmonic must maintain a constant difference with the transmitter to produce the i.f. beat.

A 'phone signal may be monitored in the same way, provided a headset is used for reception. Use of a loudspeaker is not usually practicable because the sound output feeds back to the microphone and causes howling.

A crystal detector and headset may also be used for the same purpose, as described in preceding sections. In monitoring a 'phone signal the best plan is to have another person speak into the microphone rather than to listen to one's own voice. It is difficult to judge quality when speaking and listening at the same time.

### ● C.W. SIGNAL MONITOR

One trouble with checking a c.w. signal on the station receiver is that receivers frequently have hum and instability, particularly on the higher frequencies, that cause the signal to sound worse than it really is. The best way to get a true picture of the signal is to monitor it with a battery-operated oscillator. With battery plate and filament supplies, the monitor cannot introduce hum. If the oscillator is mechanically and electrically stable and is well shielded, a true replica of the signal can be obtained.

The construction of a shielded, battery-operated monitor is described in Chapter Eight. Instructions for its use also will be found in that chapter.

### ● MODULATION MONITOR

Fig. 16-10 is the circuit of a 'phone monitor that can be used both for aural checking and for measuring modulation percentage. When a small r.f. voltage is applied to the input circuit it is rectified by the crystal. With switch  $S_1$  in the "r.f." position the average value of the rectified current is measured by the 0-1 milliammeter,  $MA$ . With the switch in the "a.f." position, the audio modulation on the signal is transferred through  $T_1$  to a second rectifier. The average value of the rectified audio is again read by the milliammeter. The circuit constants are chosen so that if the input is adjusted to make the meter read full scale on r.f., the a.f. meter readings will be directly proportional to percentage of modulation (for voice modulation), 100-percent modulation being represented by a cur-

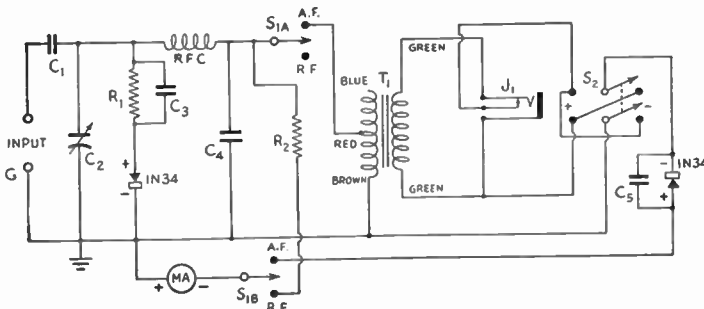


Fig. 16-10 — Circuit of direct-reading modulation meter.

- C<sub>1</sub>, C<sub>4</sub> — 1000- $\mu$ fd. ceramic.
- C<sub>2</sub> — 100- $\mu$ fd. variable midget.
- C<sub>3</sub> — 12- $\mu$ fd. mica.
- C<sub>5</sub> — 470- $\mu$ fd. mica.
- R<sub>1</sub> — 1100 ohms, 5%, 1 watt.
- R<sub>2</sub> — 16,000 ohms, 5%, 1 watt.
- J<sub>1</sub> — Closed-circuit jack.
- MA — 0-1 ma., 100 ohms.
- RFC — 20  $\mu$ h.
- S<sub>1A</sub>-B, S<sub>2</sub> — D.p.d.t. toggle.
- T<sub>1</sub> — Push-pull interstage transformer, 1:1 ratio (Stancor A-4711).



rent of 1 milliampere. Switch  $S_2$  provides for reversing the "polarity" of the modulation, giving a qualitative indication of the up and down peaks. A headphone jack,  $J_1$ , is provided for listening to the quality of the modulation. (The percentage modulation cannot be read with 'phones plugged into  $J_1$ , so the 'phones must be removed when readings are to be taken.)

In constructing such an instrument, care should be used to prevent r.f. pick-up in the audio rectifier circuit. This can be checked by testing the instrument on an unmodulated carrier (which must be substantially hum-free); with a full-scale reading when  $S_1$  is in the "r.f." position, the meter should read zero when  $S_1$  is switched to "a.f." The values of  $R_1$  and  $R_2$  are critical and should be within 5 per cent of the recommended values.

## Measurement of Current, Voltage and Power

The amateur regulations require that when the power input to the final stage is above 900 watts, means must be provided for measuring the power input. This may be done by measuring the d.c. voltage applied to the final-stage plates and the d.c. current flowing to them. The instruments required are a milliammeter and voltmeter.

Although in lower-power transmitters power-input measurements are not required, it is nevertheless true that a milliammeter is an almost indispensable instrument in the amateur station. It is invaluable in the adjustment of transmitting amplifier stages; tuning a transmitter without measuring grid and plate currents is like working in the dark. A d.c. voltmeter, although not essential, is useful in conjunction with the milliammeter in determining whether tube ratings are being exceeded or not and thus is helpful in prolonging tube life.

Besides d.c. measurements, it is also well to measure the filament voltages applied to transmitting tubes. Tube performance is dependent upon proper cathode emission, which in turn depends upon the voltage applied to the filament or heater. Also, the life of some transmitting tubes, particularly the thoriated-tungsten filament types, is critically dependent upon maintaining the filament voltage within rather close limits. Since most transmitting-tube filaments are operated on a.c., an a.c. voltmeter is a worth-while addition to amateur transmitting equipment.

Adjustment of a transmitter for maximum power output to the antenna or transmission line is facilitated by the use of instruments which measure radio-frequency current. Such instruments, although not actually essential, round out the measuring equipment used in transmitter adjustment.

A sample of the modulated carrier may be coupled into the instrument through a one-turn link and a length of Twin-Lead, the link being placed within a few inches of the final tank circuit of the transmitter. The coupling between the link and final tank coil must be adjusted to give a full-scale r.f. reading, after  $C_2$  has been set for maximum reading. Alternatively, a coil that will resonate with  $C_2$  at the operating frequency may be connected to the input terminals and the instrument located so that a suitable full-scale reading will be obtained.

Besides indicating modulation percentage, the instrument will show carrier shift (as shown by a change in the reading, when modulating, with  $S_1$  in the "r.f." position) and thus detect nonlinearity in the modulated amplifier.

### D.C. Instruments

D.c. ammeters and voltmeters are basically identical instruments, the difference being in the method of connection. An ammeter is connected in series with the circuit and measures the current flow. A voltmeter is a milliammeter that measures the current through a high resistance connected across the source to be measured; its calibration is in terms of the voltage drop in the resistance or multiplier.

If a single instrument must be used for measuring widely-different values of current or voltage, it is advisable to purchase one which will read, at about 75 per cent of full scale, the *smallest* value of current or voltage

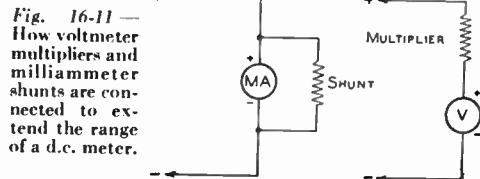


Fig. 16-11 — How voltmeter multipliers and milliammeter shunts are connected to extend the range of a d.c. meter.

to be measured. Small currents cannot be read with any degree of precision on a high-scale instrument; on the other hand, the range of a low-scale instrument can be extended as desired to take care of larger values. The ranges of both voltmeters and ammeters can be extended by the use of external resistors, connected in series with the instrument in the case of a voltmeter or in shunt in the case of an ammeter. Fig. 16-11 shows at the left the manner in which a shunt is connected to extend the range of an ammeter and at the right the connection of a voltmeter multiplier.

To calculate the value of a shunt or multiplier it is necessary to know the resistance of the meter. If it is desired to extend the range of a voltmeter, the value of resistance which must

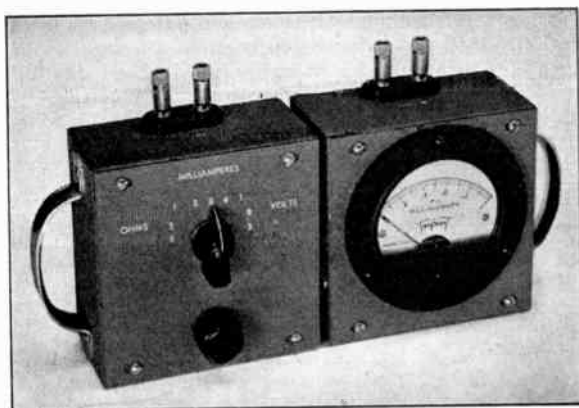


Fig. 16-12 — An inexpensive multirange volt-ohm-milliammeter. The 2 × 4 × 4-inch cabinet at the left houses the multipliers, shunts, switch and zero-adjustment resistor. The meter is mounted in the metal cabinet shown at the right. The units are provided with plugs and jacks so that the meter can be used independently or as the indicator component for other instruments. Connections to the volt-ohm-milliammeter, or to the meter alone, are made to the terminals mounted at the top of both boxes. Handles are mounted on the cabinets to facilitate handling.

be added in series is given by the formula:

$$R = R_m (n - 1)$$

where  $R$  is the multiplier resistance,  $R_m$  the resistance of the voltmeter, and  $n$  the scale multiplication factor. For example, if the range of a 10-volt meter is to be extended to 1000 volts,  $n$  is equal to 1000/10 or 100.

If a milliammeter is to be used as a voltmeter, the value of series resistance can be found by Ohm's Law:

$$R = \frac{1000E}{I}$$

where  $E$  is the desired full-scale voltage and  $I$  the full-scale reading of the instrument in milliamperes.

To increase the current range of a milliammeter, the resistance of the shunt is

$$R = \frac{R_m}{n - 1}$$

where the symbols have the same meanings as above.

Homemade milliammeter shunts can be constructed from any of the various special kinds of resistance wire, or from ordinary copper magnet wire if no resistance wire is available. The Copper Wire Table in Chapter Twenty-Four gives the resistance per 1000 feet for various sizes of copper wire. After computing the resistance required, determine the smallest wire size that will carry the full-scale current (at 250 circular mils per ampere). Measure off enough wire (pulled tight but not stretched) to provide the required resistance. Accuracy can be checked by causing enough current to flow through the meter to make it read full scale without the shunt; connecting the shunt should then give the correct reading on the new full-scale range.

Precision wire-wound resistors used as voltmeter multipliers cannot readily be made by the amateur because of the much higher resistance required (as high as several megohms). As an economical substitute, standard fixed resistors may be used. Such resistors are sup-

plied in tolerances of 5, 10 or 20 per cent ± the marked values. By obtaining matched pairs from the dealer's stock, one of which is, for example, 4 per cent low while the other is 4 per cent high, and using the pairs in parallel or series to obtain the required value of resistance, good accuracy can be obtained at small cost. High-voltage multipliers are preferably made up of several resistors in series; this not only raises the breakdown voltage but tends to average out errors in the individual resistors attributable to manufacturing tolerances.

When d.c. voltage and current are known, the power in a d.c. circuit can be stated by simple application of Ohm's Law:  $P = EI$ . Thus the voltmeter and ammeter are also the instruments used in measuring d.c. power.

### Multirange Voltmeters and Ohmmeters

A combination voltmeter-milliammeter having various ranges is extremely useful for experimental purposes and for trouble shooting in receivers and transmitters. As a voltmeter

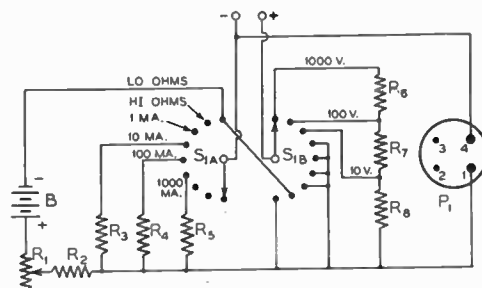


Fig. 16-13 — Diagram of the volt-ohm-milliammeter.

- R<sub>1</sub> — 2000-ohm wire-wound variable.
- R<sub>2</sub> — 3000 ohms, ½ watt.
- R<sub>3</sub> — 10-ma. shunt, 6.11 ohms (see text).
- R<sub>4</sub> — 100-ma. shunt, 0.555 ohm (see text).
- R<sub>5</sub> — 1000-ma. shunt, 0.055 ohm (see text).
- R<sub>6</sub> — 1000-volt multiplier, 0.9 megohm, ½ watt.
- R<sub>7</sub> — 100-volt multiplier, 90,000 ohms, ½ watt.
- R<sub>8</sub> — 10-volt multiplier, 10,000 ohms, ½ watt.
- B — 4.5-volt dry battery (Burgess 5360).
- P<sub>1</sub> — 4-prong male plug (for milliammeter).
- S<sub>1A-B</sub> — 9-point 2-pole selector switch (Mallory 3229J).

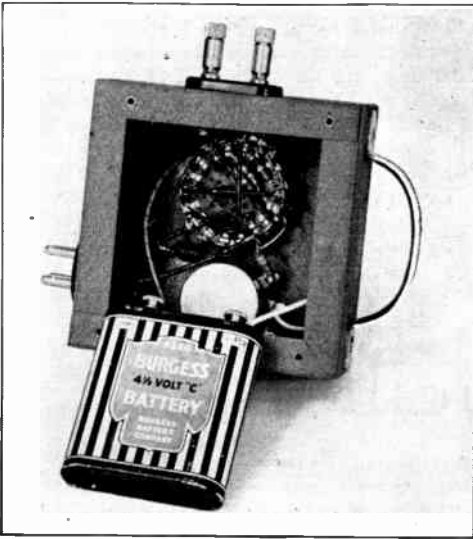


Fig. 16-14 — A rear view of the volt-ohm-milliammeter. The range-selector switch is mounted above the zero-adjustment potentiometer, and the shunts and multipliers are connected across the switch terminals. A four-prong male plug, for connection to the meter box, is shown at the left of the cabinet. The ohmmeter battery fits inside the case; the battery terminals should be insulated with tape or paper before the battery is installed in the box.

such an instrument should have high resistance so that very little current will be drawn in making voltage measurements. A voltmeter taking considerable current will give inaccurate readings when connected across a high-resistance source — as is often the case in various parts of a receiver circuit. For such purposes the instrument should have a resistance of at least 1000 ohms per volt; a 0-1 milliammeter or 0-500 microammeter (0-0.5 ma.) is the basis of most multirange meters of this type. Microammeters having a range of 0-50  $\mu$ a., giving a sensitivity of 20,000 ohms per volt, also are used.

The various current ranges on a multirange instrument can be obtained by using a number of shunts individually switched in parallel with the meter. Care should be used to minimize contact resistance in the switch.

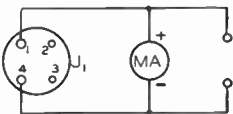


Fig. 16-15 — Wiring diagram of the 0-1 milliammeter shown in Figs. 16-5 and 16-12.  $J_1$  is a 4-prong tube socket.

It is often necessary to check the value of a resistor or to find the value of an unknown resistance, particularly in receiver servicing. An ohmmeter is used for this purpose. The ohmmeter is simply a low-current d.c. voltmeter provided with a source of voltage (usually dry cells), the meter and battery being

connected in series with the unknown resistance. If a full-scale deflection is obtained with the connections to the external resistance shorted, insertion of the resistance under measurement will cause the meter reading to decrease. The meter scale can be calibrated in ohms. When the resistance of the voltmeter is known, the following formula can be applied:

$$R = \frac{eR_m}{E} - R_m$$

where  $R$  is the resistance under measurement,  $E$  is the voltage read on the meter,  $e$  is the series voltage applied, and  $R_m$  is the resistance of the voltmeter.

Since the resistance of a voltmeter is usually rather high, this method is not well adapted to measuring low values of resistance. For very low resistances, the unknown may be connected in shunt with the instrument (not including the multiplier) instead of in series.

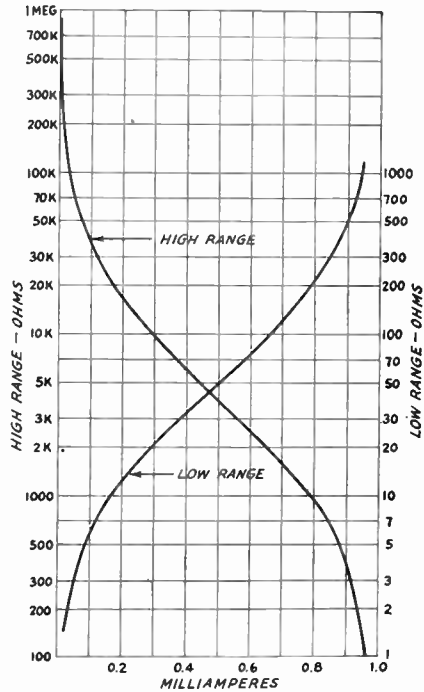


Fig. 16-16 — Calibration curve for the high- and low-resistance ranges of the volt-ohm-milliammeter.

● AN INEXPENSIVE V.O.M.

A combination multirange volt-ohm-milliammeter, reduced to simple and inexpensive terms, is shown in Figs 16-12 to 16-15. Using a 0-1 milliammeter, the voltmeter has three ranges at 1000 ohms per volt: 0-10, 100 and 1000 volts. Current ranges of 0-1, 10, 100 and 1000 ma. are provided. There are two resis-

tance-measurement ranges, a series range that is useful up to about 0.5 megohm, and a shunt range of 0-1000 ohms.

For economy, ordinary carbon resistors are used as voltmeter multipliers. These can be obtained with an accuracy within 5 per cent. However, standard resistors of 10-per-cent tolerance can be used without introducing undue error. The 1000-volt multiplier,  $R_6$ , is two 1.8-megohm resistors in parallel, and the 100-volt multiplier,  $R_7$ , is two 0.18-megohm resistors in parallel.

The 10-, 100- and 1000-ma. shunts are made

of ordinary copper magnet wire wound on  $\frac{1}{2}$ -watt resistors of high resistance value — 10,000 ohms or higher. The approximate lengths and sizes of the wire for the shunts are as follows:  $R_3$ , 9 inches No. 38 enameled;  $R_4$ , 5 inches No. 30 enameled;  $R_5$ , 3 inches No. 18.

A calibration curve for the ohmmeter ranges is given in Fig. 16-16. With instruments having different internal resistance than the one shown in the photograph (Triplett Model 0321-1) the "low-ohms" curve will not apply exactly.

## Test Oscillators and Grid-Dip Meters

A useful and inexpensive general-purpose instrument is an oscillator covering a wide frequency range. When it generates frequencies in the audio range it can be used as a signal source for checking the performance of audio amplifiers. As a radio-frequency oscillator it may be made to generate signals that can be used for receiver alignment, for calibrating absorption wavemeters as described earlier in this chapter, and for furnishing small r.f. voltages for whatever purpose may be required. When equipped with a low-range milliammeter connected to read the oscillator grid current, it becomes a grid-dip meter and may be used for checking the resonant frequencies of tuned circuits, and as a means for measuring inductance and capacitance as described in a later section.


The grid-dip meter is so called because when its oscillator is coupled to a tuned circuit, the oscillator grid current will show a decrease or "dip" when the oscillator is tuned through resonance with the unknown circuit. The reason for this is that the external circuit will absorb energy from the oscillator when both it and the oscillator are tuned to the same fre-

quency, and the loss of energy from the oscillator circuit causes the feed-back to decrease. The decrease in feed-back is accompanied by a decrease in grid current. The dip in grid current is quite sharp when the circuit to which the oscillator is coupled has reasonably high  $Q$ .
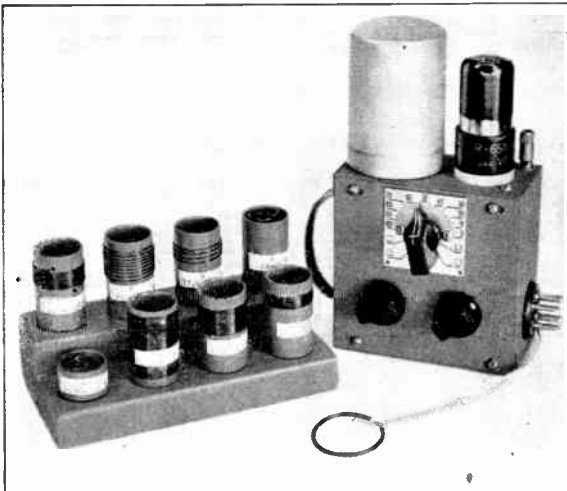
### ● GENERAL-PURPOSE OSCILLATOR AND GRID-DIP METER

A general-purpose test oscillator is shown in Figs. 16-17 and 16-19. This simple unit can be used as an audio oscillator, an r.f. signal generator, a grid-dip meter, a field-strength indicator, or as an absorption wavemeter, and has a frequency range of 200 cycles to 56 Mc.

As shown by the circuit diagram, Fig. 16-18, a Type 6SN7GT tube is used in a cathode-coupled oscillator circuit. The only critical values are those of the cathode resistor,  $R_2$ , and the coupling condenser,  $C_4$ . Use of a cathode resistor of less than 1000 ohms will result in a poor waveform at audio frequencies, and the oscillator output will be greatly reduced if the cathode resistor is larger than 3000 ohms. The audio attenuator,  $R_4$ , loads the circuit to some



◆  
Fig. 16-17 — The general-purpose test oscillator. The variable condenser, sensitivity control and audio-output potentiometer are mounted on the front panel of a 2 × 4 × 1-inch metal box. A handle at the left of the box, and a meter jack at the right, are provided so that the oscillator may be used with the meter unit shown in Fig. 16-12. Sockets for the oscillator tube and the plug-in coils are mounted on the top of the box. The coil shield is necessary only when the oscillator is being used as a signal generator. The r.f. coils are shown mounted in a wooden rack which has been drilled to fit the prongs of the coil forms.  
◆

extent, and will prevent oscillation if the coupling condenser,  $C_4$ , is made much smaller than  $0.1 \mu\text{fd}$ . The oscillator requires a filament supply of 6.3 volts at 0.6 amp., and the plate supply should deliver 150 to 250 volts at 14 ma. (the plate-current drain will be less than 10 ma. at the audio and the low radio frequencies).

The frequency of the oscillator is controlled by the values of inductance and capacitance connected across points  $C$  and  $D$  in Fig. 16-18. The coil chart lists values of capacitance and inductance that can be used for either audio- or radio-frequency output. At audio frequencies, the  $LC$  combination is connected across terminals  $C$  and  $D$ , and at radio frequencies the coils plug into the socket provided for this purpose. The variable condenser,  $C_1$ , is used as the frequency adjustment over the r.f. range of the oscillator, and can be used as a vernier adjustment at audio frequencies.

A potentiometer,  $R_3$ , serves as the sensitivity control when the oscillator is used as a grid-dip meter, an absorption wavemeter, or as a field-strength indicator. This control also acts as an output attenuator when the oscillator is used as a signal generator. It should be noticed that the audio-output attenuator,  $R_4$ , in series with the output coupling condenser,  $C_5$ , is connected to the resonant circuit by means of a jumper connected between terminals  $A$  and  $C$ . This jumper must be removed when the oscillator is used at radio frequencies; otherwise the circuit will not oscillate.

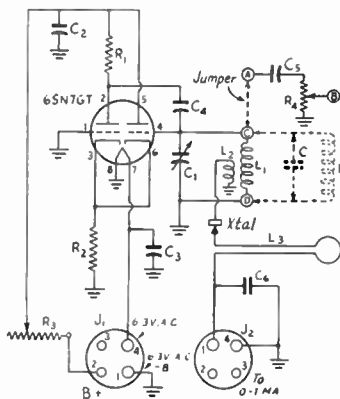


Fig. 16-18 — Simple general-purpose test oscillator.  
 $C_1$  — 100- $\mu\text{fd}$ , midget variable (Millen 20100).  
 $C_2, C_3$  — 0.01- $\mu\text{fd}$ , 400-volt paper.  
 $C_4, C_5$  — 0.1- $\mu\text{fd}$ , 400-volt paper.  
 $C_6$  — 100- $\mu\text{fd}$ , midget mica.  
 $R_1$  — 68,000 ohms, 1 watt.  
 $R_2$  — 1500 ohms, 1 watt.  
 $R_3$  — 0.2-megohm carbon potentiometer.  
 $R_4$  — 50,000-ohm carbon potentiometer.  
 $L_1, L_2, L_3$  — See text and coil table.  
 $J_1, J_2$  — 4-prong plug (Amphenol 86-CP4).  
 XTAL — Type 1N34,

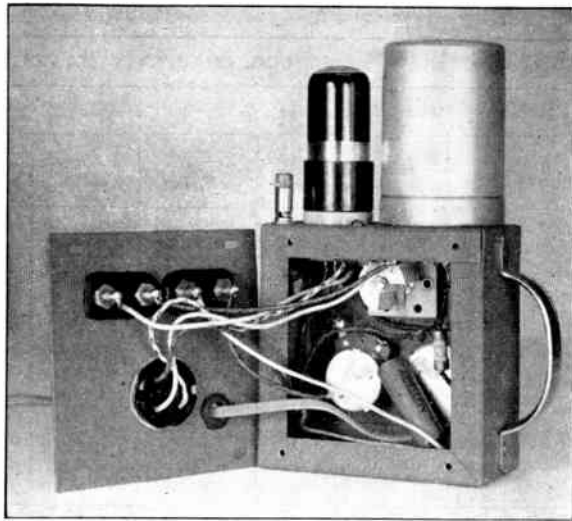


Fig. 16-19 — A rear view of the general-purpose test oscillator. The low impedance link for the pick-up loop feeds through a rubber grommet mounted in the rear cover. Input and output jacks are also located on the backplate. The arrangement of components inside the box is not critical. The 1N34 crystal and the meter bypass condenser,  $C_6$ , are mounted inside the box.

The rectifier system consists of coil  $L_2$ , the 1N34 crystal, a pick-up loop, and a meter bypass condenser. R.f. current generated by the oscillator circuit is coupled to the crystal rectifier by means of  $L_2$ . The current is rectified by the crystal and flows through the pick-up loop to an external meter (any 0-1 milliammeter will do). The pick-up loop, if placed in series with the crystal as shown, will not overload the oscillator circuit.

For output in the audio-frequency range, the desired  $LC$  combination is connected across the circuit and output connections are made to terminals  $B$  and  $D$  (the jumper is connected between  $A$  and  $C$ ). If a test signal of radio frequency is desired, the jumper connection is removed and a coil is plugged in the coil socket. Terminal  $C$  will then serve as a short antenna from which the signal is radiated. The strength of the signal being radiated can be increased by adding a short length of wire to the output terminal. It is advisable to shield the r.f. coil for this type of operation so that hand-capacitance effects will be minimized.

To use the oscillator as a grid-dip meter, connect a 0-1 milliammeter to the meter jack,  $J_2$ . With the proper r.f. coil in place, and with power turned on, adjust the sensitivity control for maximum meter deflection (full deflection will be approximately 0.5 ma. on the highest frequency range). The pick-up loop can then be coupled to the circuit under measurement and, if the oscillator frequency is varied by means of the tuning condenser,  $C_1$ , there will be a pronounced dip in grid current as the resonant frequency of the external circuit is passed.

COIL CHART FOR THE TEST OSCILLATOR							
Audio Frequencies			Radio Frequencies				
Frequency (Cycles)	Inductance (hy.) (L)	Capacitance (μfd.) (C)	Freq. (Mc.)	Coil	No. Turns	Wire Size	Length of Winding (Inches)
200	1.2	0.02	0.955-1.75	L <sub>1</sub>	120	No. 30 enam.	1 1/16
400	"	0.06		L <sub>2</sub>	12	" 18 "	
600	"	0.15	1.72-3.1	L <sub>1</sub>	50	" 30 "	3/16
1000	"	0.5		L <sub>2</sub>	6	" 18 "	
1300	0.125 (Meissner) No. 19-6848.	0.1	3.0-5.4	L <sub>1</sub>	23	" 30 "	1/4
1800		0.05		L <sub>2</sub>	2	" 18 "	
2000	"	0.04	5.3-9.8	L <sub>1</sub>	15	" 22 "	7/16
2300	"	0.03		L <sub>2</sub>	6	" 18 "	
2800	"	0.02	9.7-17.8	L <sub>1</sub>	9	" 22 "	3/8
3300	"	0.015		L <sub>2</sub>	2	" 18 "	
4000	"	0.01	17.6-31.5	L <sub>1</sub>	4	" 22 "	3/8
5200	"	0.0068		L <sub>2</sub>	2	" 18 "	
6250	"	0.005	31.0-56.0	L <sub>1</sub>	3	" 12 "	1/2
10,000	"	0.002		L <sub>2</sub>	1	" 18 "	

*L*<sub>1</sub> and *L*<sub>2</sub> for 0.33 to 0.6 Mc. are the primary and secondary windings of a 456-ke. i.f. transformer, closely coupled, and mounted inside the coil form. *L*<sub>1</sub> for 31.0 to 56.0 Mc. has a diameter of 3/8 inch and is mounted inside the form. For all other frequencies *L*<sub>1</sub> is wound on the outside of the coil form. All *L*<sub>2</sub> windings are close-wound, have a diameter of 3/8 inch, and are mounted inside the forms. Millen Type 45004 forms are used throughout. *L*<sub>3</sub>, the pick-up coil, is one turn of No. 12 enameled wire, 1 1/4 inches in diameter, connected to a length of 75-ohm Twin-Lead.

The 0-1 milliammeter is also required when the unit is used as an absorption wavemeter or as a field-strength indicator. However, the power supply is not required for these types of operation. It is only necessary that the proper r.f. coil be selected and that the coil (or the pick-up loop) be placed in the field of the frequency-generating device that is being measured. The sensitivity, during field-strength measurements, can be increased by attaching a short antenna to terminal C.

Because of the large frequency range covered by this instrument, it is not practical to employ a dial calibrated directly in terms of frequency. Therefore, an ordinary 0-100 degree dial is used and the actual frequency calibrations are marked on a separate chart. The r.f. ranges can be calibrated by using a calibrated re-

ceiver for listening to the oscillator output signal. An alternative method is to use the unit as a grid-dip meter coupled to a calibrated absorption wavemeter. The audio-frequency range can be calibrated by feeding the oscillator output to the vertical amplifier of an oscilloscope while the horizontal amplifier of the 'scope is being excited by the output of a calibrated audio oscillator. A circular pattern will be registered on the screen of the 'scope when the outputs of the two audio oscillators are adjusted to the same frequency. An alternative method of a.f. calibration is to connect a headset to the oscillator output terminals and compare the tone to the notes of a piano, determining which piano note is nearest. The approximate frequency then can be found from the table in Chapter Twenty-Four.

## Measuring Inductance and Capacitance

The ability to measure the inductance of coils, the capacitance of condensers, or the resonant frequency of a tuned circuit frequently saves time that might otherwise be spent in cut-and-try. A convenient instrument for this purpose is the grid-dip oscillator, described earlier in this chapter.

For measuring inductance, the coil to be measured is connected to a condenser of known capacitance as shown at A in Fig. 16-20. A mica condenser may be used as a standard; a 100-μμfd. 5-per-cent tolerance unit will serve for most purposes. With the unknown coil connected to the standard condenser, the pick-up loop is coupled to the coil and the oscillator frequency adjusted for the grid-current dip, using the loosest coupling that gives a de-

tectable indication. The inductance is then given by the formula

$$L_{\mu h.} = \frac{25,300}{C_{\mu\mu fd.} f_{Mc.}^2}$$

A calibrated variable condenser is required for measuring capacitance. The circuit used is shown at B in Fig. 16-20. The frequency of the circuit, using any convenient coil, is first measured with the unknown capacitance disconnected and the calibrated condenser set near maximum. The unknown is then connected and the calibrated condenser readjusted to resonance. The unknown capacitance is then equal to the difference between the capacitances at the two settings of the calibrated condenser. Obviously only capacitances smaller

than the maximum capacitance of the calibrated condenser can be measured by this method. Since high accuracy in capacitance measurement is not ordinarily required, a satisfactory standard is any condenser of the straight-line capacitance type, for which a sufficiently good calibration curve can be constructed by noting the dial divisions at which the plates just start to mesh and are completely meshed, and assuming that the capacitance change is linear within those limits. The minimum and maximum capacitance (corresponding closely enough to these condenser settings) can be obtained from the manufacturer's data on the particular condenser used.

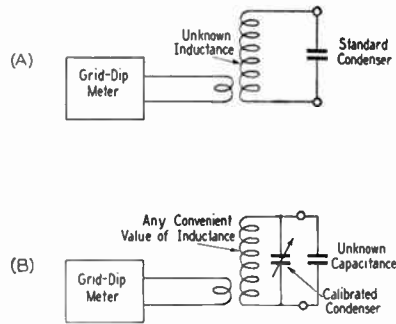


Fig. 16-20 — Set-ups for measuring inductance and capacitance with the grid-dip meter.

### The Oscilloscope

The cathode-ray oscilloscope is an instrument of great versatility, and in conjunction with the instruments herein described, should be a valuable addition to the practical amateur station. The oscilloscope is useful on d.c., and audio and radio frequencies, and is particularly suited to a.f. and r.f. measurements because, compared to other types of measuring equipment, it introduces relatively little error at such frequencies.

#### ● CATHODE-RAY TUBES

The heart of the oscilloscope is the **cathode-ray tube**, a vacuum tube in which the electrons emitted from a hot cathode are first accelerated to give them considerable velocity, then formed into a beam, and finally allowed to strike a special translucent screen which *fluoresces*, or gives off light at the point where the beam strikes. A narrow beam of moving electrons is analogous to a wire carrying current, and can be moved laterally, or **deflected**, by electric or magnetic fields.

Since the cathode-ray beam consists only of moving electrons, its weight and inertia are negligibly small. For this reason, it can be made to follow instantly the variations in periodically-changing fields at both audio and radio frequencies.

The electrode arrangement that forms the electrons into a beam is called the **electron gun**. In the simple tube structure shown in Fig. 16-21, the gun consists of the cathode, grid, and anodes Nos. 1 and 2. The intensity of the electron beam is regulated by the grid in the same way as in an ordinary tube. Anode No. 1 is operated at a positive potential with respect to the cathode, thus accelerating the electrons that pass through the grid, and is provided with small apertures through which the electron stream passes. On emerging from the apertures the electrons are traveling in practically parallel straight-line paths. The electrostatic fields set up by the potentials on anode No. 1 and anode No. 2 form an **electron lens** system which makes the electron paths converge to a point at the fluorescent screen. The potential on anode No. 2 is usually fixed, while that on anode No. 1 is varied to bring the beam into focus. Anode No. 1 is, therefore, called the **focusing electrode**.

Sharpest focus is obtained when the electrons of the beam have high velocity, so that relatively high d.c. potentials are common with cathode-ray tubes. However, the current required is small, so that the power consumption is negligible. A second grid may be placed between the control grid and anode No. 1, for additional acceleration of the electrons.

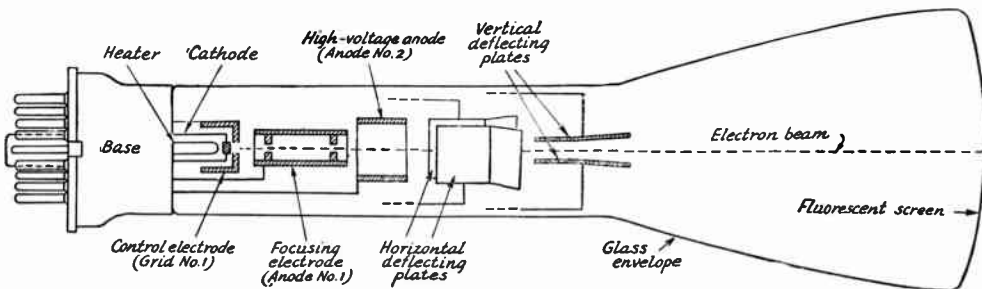


Fig. 16-21 — Typical construction for a modern cathode-ray tube of the electrostatic-deflection type. The envelope is made of glass, with the fluorescent screen at one end. Leads for the high-voltage anode, the deflection plates, and other electrodes are insulated low-capacitance conductors carried inside the envelope to the base.

**Methods of Deflection**

When focused, the beam from the gun produces only a small spot on the screen, as described above. However, if after leaving the gun the beam is deflected by either magnetic or electrostatic fields, the spot will move across the screen in accordance with the force exerted on the beam. If the motion is rapid, the path of the spot (trace) appears as a continuous line.

Electrostatic deflection, the type generally used in the smaller tubes, is produced by **deflecting plates**. Two sets of plates are placed at right angles to each other, as indicated in Fig. 16-21. The fields are created by applying suitable voltages between the two plates of each pair. Usually one plate of each pair is connected to anode No. 2, to establish the polarities of the vertical and horizontal fields with respect to the beam and to each other.

**Formation of Patterns**

When periodically-varying voltages are applied to the two sets of deflecting plates, the path traced by the fluorescent spot forms a **pattern** that is stationary so long as the amplitude and phase relationships of the voltages remain unchanged. Fig. 16-22 shows how such

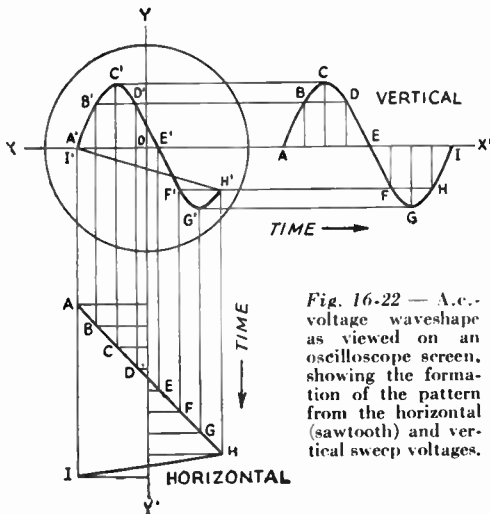


Fig. 16-22 — A.c. voltage waveshape as viewed on an oscilloscope screen, showing the formation of the pattern from the horizontal (sawtooth) and vertical sweep voltages.

patterns are formed. The horizontal sweep voltage is assumed to have the "sawtooth" waveshape indicated. With no voltage applied to the vertical plates the trace simply sweeps from left to right across the screen along the horizontal axis  $X-X'$  until the instant  $H$  is reached, when it reverses direction and returns to the starting point. The sine-wave voltage applied to the vertical plates similarly would trace a line along the axis  $Y-Y'$  in the absence of any deflecting voltage on the horizontal plates. However, when both voltages are present the position of the spot at any instant depends upon the voltages on both sets of plates at that instant. Thus at time  $B$  the horizontal voltage has moved the spot a short

distance to the right and the vertical voltage has similarly moved it upward, so that it reaches the actual position  $B'$  on the screen. The resulting trace is easily followed from the other indicated positions, which are taken at equal time intervals.

**Types of Sweeps**

A sawtooth sweep-voltage waveshape, such as is shown in Fig. 16-22, is called a **linear sweep**, because the deflection in the horizontal direction is directly proportional to time. If the sweep were perfect the **fly-back** time, or time taken for the spot to return from the end ( $H$ ) to the beginning ( $I$  or  $A$ ) of the horizontal trace, would be zero, so that the line  $III'$  would be perpendicular to the axis  $Y-Y'$ . Although the fly-back time cannot be made zero in practicable sweep-voltage generators it can be made quite small in comparison to the time of the desired trace  $AH$ , at least at most frequencies within the audio range. The fly-back time is somewhat exaggerated in Fig. 16-22, to show its effect on the pattern. The line  $III'$  is called the **return trace**; with a linear sweep it is less brilliant than the pattern, because the spot is moving much more rapidly during the fly-back time than during the time of the main trace. If the fly-back time is short enough, the return trace will be invisible.


The linear sweep has the advantage that it shows the shape of the wave in the same way that it is usually represented graphically. If the time of one cycle of the a.c. voltage applied to the vertical plates is a fraction of the time taken to sweep horizontally across the screen, several cycles of the vertical or "signal" voltage will appear in the pattern. The shape of only the last cycle (or the last few cycles, depending upon the number in the pattern and the characteristics of the sweep) to appear will be affected by the fly-back in such a case.

The shape of the pattern obtained, with a given signal waveshape on the vertical plates, obviously will depend upon the shape of the horizontal sweep voltage. If the horizontal sweep is sinusoidal, the main and return sweeps each occupy the same time and the spot moves faster horizontally in the center of the pattern than it does at the ends. When two sinusoidal voltages of the same frequency are applied to both sets of plates, the pattern may be a straight line, an ellipse, or a circle, depending upon the amplitudes and phase relationships of the two voltages.

For many amateur purposes a satisfactory horizontal sweep is simply a 60-cycle voltage of adjustable amplitude. In modulation monitoring (described in Chapter Nine) audio-frequency voltage can be taken from the modulator to supply the horizontal sweep. For examination of audio-frequency waveforms, the linear sweep is essential. Its frequency should be adjustable over the entire range of audio frequencies to be inspected on the oscilloscope.



Fig. 16-23 — Front view of a rack-mounting oscilloscope for modulation monitoring. All components are mounted on the rear of a 19 × 5½-inch rack panel. The power-supply components are built into a utility box bolted on the left side of the panel, and the 'scope circuits are mounted on the right-hand side, enclosed by a shield box. The a.c. switch is on the left. All other controls are on the right, as follows: top row, l. to r., sweep switch, intensity control, focus control; bottom row, sweep-amplitude control, horizontal centering, vertical centering.

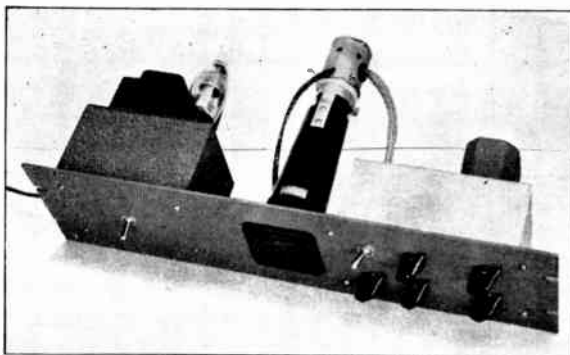

## ● A SIMPLE OSCILLOSCOPE FOR MODULATION MONITORING

Figs. 16-23 through 16-25 show the circuit and constructional details of a simple 2-inch oscilloscope that is suitable for use as a modulation monitor. It is designed to be mounted in the transmitter rack, becoming a permanent part of the 'phone station. Inexpensive parts are used throughout, and the circuits themselves are simple to build and operate.

The 2AP1 cathode-ray tube is mounted with its screen protruding through a 2-inch hole in the 19 × 5½-inch aluminum rack panel. The cathode-ray tube is enclosed in a Millen shield, and its screen is covered by a Millen Type 80072 bezel. The power-supply components are housed in a standard 3 × 4 × 5-inch utility box that is bolted to the left rear of the

rack panel. An inexpensive replacement-type transformer is used with a 2X2 half-wave rectifier to deliver about 800 volts at the required 4 or 5 ma. drain.

The voltage-divider circuit components and the sweep-circuit controls are mounted on the right-hand side of the panel, and are enclosed by a 6 × 4½ × 2½-inch three-sided box folded from sheet aluminum. A small audio transformer, mounted on the rear of this box, serves to provide 60-cycle sweep voltage. The by-pass condensers, C<sub>2</sub>, C<sub>3</sub> and C<sub>4</sub>, used to eliminate a.c. components from the d.c. control circuits, are connected directly to the rotor arms of their respective potentiometers, R<sub>1</sub>, R<sub>8</sub> and R<sub>9</sub>.

The socket for the cathode-ray tube is not fastened to any of the structural members of the unit, but is used as a plug, with the socket terminals enclosed in a tubular aluminum shield made by cutting down a National Type T-78 tube shield. The base plate of this assembly is used as the support for a two-terminal tie-

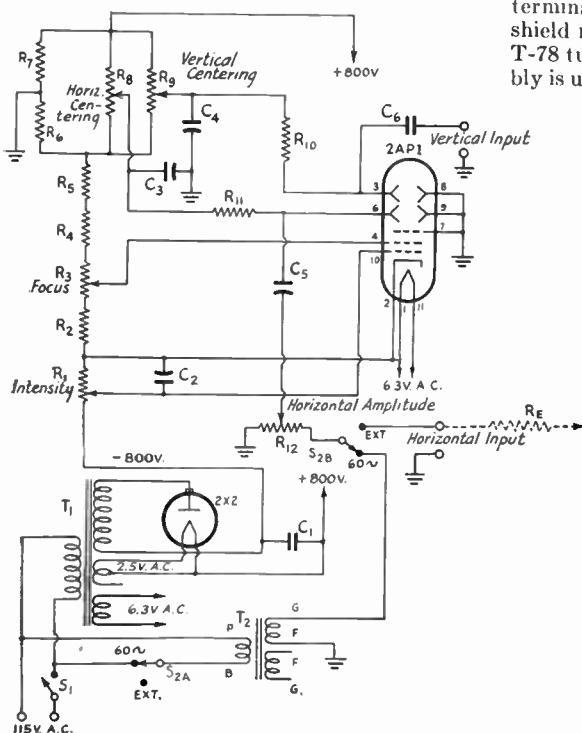


Fig. 16-24 — Circuit diagram of the simple oscilloscope for modulation monitoring.

- C<sub>1</sub> — 1 μfd., 1000 volts, oil-filled.
- C<sub>2</sub>, C<sub>3</sub>, C<sub>4</sub> — 0.01-μfd. 600-volt paper.
- C<sub>5</sub> — 0.1 μfd., 1000 volts, paper.
- C<sub>6</sub> — 0.001 μfd., 600 volts, mica.
- R<sub>1</sub> — 20,000-ohm potentiometer, linear taper.
- R<sub>2</sub> — 4700 ohms, ½ watt.
- R<sub>3</sub> — 50,000-ohm potentiometer, linear taper.
- R<sub>4</sub>, R<sub>5</sub> — 33,000 ohms, 1 watt.
- R<sub>6</sub>, R<sub>7</sub> — 47,000 ohms, 1 watt.
- R<sub>8</sub>, R<sub>9</sub> — 50,000-ohm potentiometer, linear taper.
- R<sub>10</sub>, R<sub>11</sub> — 1 megohm, ½ watt.
- R<sub>12</sub> — 0.25-megohm potentiometer, linear taper.
- S<sub>1</sub> — S.p.s.t. toggle switch.
- S<sub>2</sub> — D.p.d.t. toggle switch.
- T<sub>1</sub> — Replacement-type receiver transformer, 350 v. each side of c.t., 70 ma. (Stancor P-6011.)
- T<sub>2</sub> — Interstage audio transformer. (UTC S-2, with half of secondary unused, to produce approx. 1:1 turns ratio.)

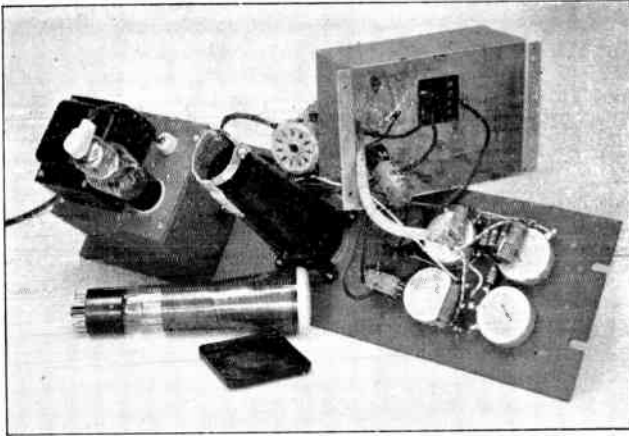


Fig. 16-25 — Rear view of the rack-mounting oscilloscope. The shield covering the voltage-divider components has been removed to show wiring. Mounted on the shield are the audio transformer and the horizontal input terminals. The scope tube and its socket have been removed.

point that holds isolating resistors  $R_{10}$  and  $R_{11}$ . These resistors are mounted inside the socket shield, as close to the tube base as possible. A  $\frac{1}{2}$ -inch hole is drilled through the side of the shield to pass the cabled and shielded d.c. leads that run from the tube socket into the divider network in the aluminum shield box. A ceramic feed-through bushing requiring a  $\frac{3}{8}$ -inch clearance hole passes through the opposite side of the socket shield to serve as the vertical input terminal.  $C_6$  is connected between this bushing and the vertical deflection-plate pin on the tube socket.  $C_5$ , the coupling condenser for the horizontal plates, is mounted inside the larger shield box, near the horizontal-amplitude control,  $R_{12}$ .

The horizontal input terminals of the 'scope are mounted on the rear of the shield box, alongside of the audio transformer. The transformer secondary is connected to produce a turns ratio of approximately 1-to-1, which is sufficient to produce more than enough sweep voltage. A double-pole toggle switch is used to open the primary circuit of the audio transformer and to connect the external terminal to the amplitude control when the 'scope is used for transmitter monitoring. In this case sweep voltage is obtained from the audio system of the transmitter.  $R_{12}$  is connected on the tube side of the sweep switch, so that it remains in the circuit at all times to give control of voltage applied to the horizontal plates.

Details for using this oscilloscope to monitor a 'phone transmitter and to check both linearity and percentage modulation are contained in Chapter Nine. It should be remembered that an external resistor,  $R_E$  in Fig. 16-24, must be used in series with the lead to the horizontal input terminals to reduce the audio voltage to the desired level. Instructions for selection of this resistor are given in Chapter Nine.

### ● LINEAR SWEEPS AND AMPLIFIERS

Probably the chief use of the oscilloscope in amateur work is in measuring the percentage

modulation in 'phone transmitters and in serving as a continuous monitor of modulation percentage. An oscilloscope for this purpose may be quite simple and inexpensive, consisting only of a small cathode-ray tube and an appropriate power supply as described above. However, by providing amplifiers for the deflection plates and furnishing a linear sweep circuit, the possibilities of the instrument are greatly extended. It then becomes possible, for example, to examine audio-frequency waveforms and to check and locate the causes of distortion in a.f. amplifiers.

#### Gas-Tube Sweep Generator

A typical circuit for a linear sweep generator and amplifier is shown in Fig. 16-26. The tube is a gas triode or grid-control rectifier. The striking or breakdown voltage, which is the plate voltage at which the tube ionizes or "fires" and starts conducting, is determined by the grid bias. When plate voltage,  $E_b$  in Fig. 16-27, is applied, the condenser between plate and cathode acquires a charge through  $R_6R_7$ . The charging voltage rises relatively slowly, as shown by the solid line, until the breakdown or flashing point,  $V_f$ , is reached. Then the condenser discharges rapidly through the comparatively low plate-cathode resistance of the tube. When the voltage drops to a value too low to maintain plate-current flow,  $E_a$ , the ionization is extinguished and the condenser once more charges through  $R_6R_7$ . If they are large enough, the voltage across the condenser rises linearly with time up to the breakdown point. This linear voltage change is used for the sweep. The fly-back time is the time required for discharge through the tube; to keep this time small, the resistance during discharge must be low.

The "sawtooth" rate is controlled by varying the capacitance between plate and cathode and the resistance of  $R_6R_7$ . To obtain a stationary pattern, the sweep is synchronized by introducing some of the voltage being observed on the vertical plates into the grid circuit of the 884 tube. This voltage "triggers" the tube into

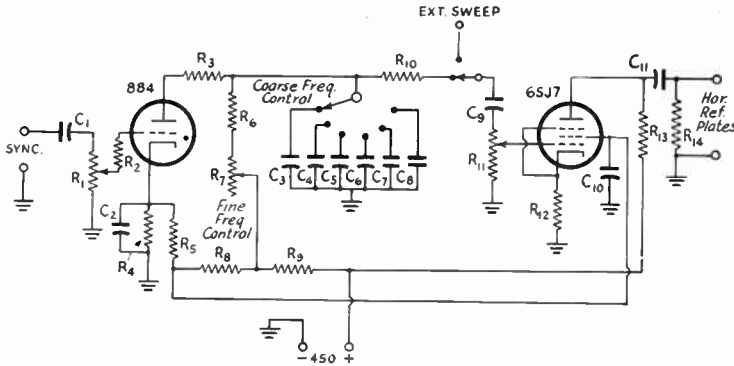


Fig. 16-26 — Linear sweep generator and horizontal amplifier.

- C<sub>1</sub> — 0.1- $\mu$ fd. paper.
- C<sub>2</sub> — 25- $\mu$ fd. 25-volt electrolytic.
- C<sub>3</sub> — 0.25- $\mu$ fd. paper, 600 volts.
- C<sub>4</sub> — 0.1- $\mu$ fd. paper, 600 volts.
- C<sub>5</sub> — 0.01- $\mu$ fd. paper, 600 volts.
- C<sub>6</sub> — 0.015- $\mu$ fd. paper, 600 volts.
- C<sub>7</sub> — 0.005- $\mu$ fd. paper or mica, 600 volts.
- C<sub>8</sub> — 0.0022- $\mu$ fd. mica.
- C<sub>9</sub>, C<sub>10</sub> — 0.5- $\mu$ fd. paper, 600 volts.
- C<sub>11</sub> — 8- $\mu$ fd. electrolytic, 450 volts.
- R<sub>1</sub> — 0.25-megohm potentiometer.
- R<sub>2</sub> — 22,000 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 170 ohms,  $\frac{1}{2}$  watt.
- R<sub>4</sub> — 2200 ohms,  $\frac{1}{2}$  watt.
- R<sub>5</sub> — 22,000 ohms, 1 watt.
- R<sub>6</sub> — 0.33 megohm,  $\frac{1}{2}$  watt.
- R<sub>7</sub> — 1-megohm potentiometer.
- R<sub>8</sub>, R<sub>9</sub> — 62,000 ohms, 1 watt.
- R<sub>10</sub> — 1 megohm,  $\frac{1}{2}$  watt.
- R<sub>11</sub> — 0.5-megohm potentiometer.
- R<sub>12</sub> — 820 ohms,  $\frac{1}{2}$  watt.
- R<sub>13</sub> — 0.1 megohm, 1 watt.
- R<sub>14</sub> — Bleed resistor for horizontal deflection plates.

operation in synchronism with the signal frequency. Synchronization will occur so long as the signal frequency is nearly the same as, or a multiple of, the self-generated sweep frequency.

The pentode amplifier in Fig. 16-26 can be used either to amplify the sweep-voltage output of the 884 oscillator, or to amplify any external voltage that it may be desired to use as a horizontal sweep. The gain control, R<sub>11</sub>,

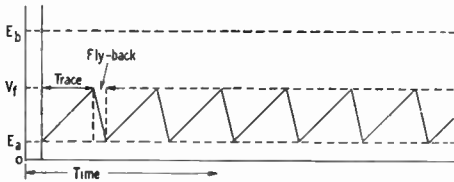


Fig. 16-27 — Condenser charging curves showing how a sawtooth wave is produced by a gaseous-tube linear sweep oscillator.

provides a means for adjusting the width of the pattern on the cathode-ray tube screen. The output of the amplifier should be connected to the horizontal deflection plates of the tube. If this circuit is to be used with the oscilloscope previously described, the output terminals may be connected directly to Terminals 6 and 9 on the 2A1P socket. In such case C<sub>5</sub> in Fig. 16-24 should be disconnected, but all other connections should be left unchanged.

**Vertical Amplifiers**

When using an oscilloscope for checking audio-frequency waveforms a "vertical" amplifier is a practical necessity. For most pur-

poses the amplifier will be satisfactory if its frequency-response characteristic is flat over the a.f. range and if it has a gain of 100 or so. A typical circuit is shown in Fig. 16-28. It will be recognized as being practically similar to the "horizontal" amplifier of Fig. 16-26. A high-resistance gain control is desirable, to avoid loading the audio circuits to which the amplifier is connected.

When such an amplifier is used with the oscilloscope of Fig. 16-24, the output terminals should be connected between Terminals 3 and 8 on the 2A1P socket. It is advisable to connect Terminal 3 to the arm of a 2-position ceramic switch, one contact going to the vertical amplifier and the other to C<sub>6</sub> in Fig. 16-24. This permits using either r.f. or a.f. input to the vertical deflection plates, disconnecting the a.f. amplifier circuit when r.f. is to be applied.

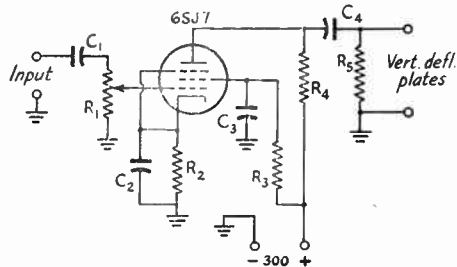


Fig. 16-28 — Circuit diagram of vertical amplifier.

- C<sub>1</sub>, C<sub>3</sub>, C<sub>4</sub> — 0.1- $\mu$ fd. paper, 400 volts.
- C<sub>2</sub> — 25- $\mu$ fd. 25-volt electrolytic.
- R<sub>1</sub> — 1-megohm potentiometer.
- R<sub>2</sub> — 1500 ohms,  $\frac{1}{2}$  watt.
- R<sub>3</sub> — 2.2 megohms, 1 watt.
- R<sub>4</sub> — 0.17 megohm, 1 watt.
- R<sub>5</sub> — Bleed resistor for vertical deflection plates.

### Constructional Considerations

In building an oscilloscope, care should be taken to see that the tube is shielded from stray electric and magnetic fields that might deflect the beam, and means should be provided to protect the operator from accidental shock, since the voltages employed with the larger tubes are quite high. In general, the preferable form of construction is to enclose the instrument completely in a metal cabinet. It is good practice to provide an interlock switch that automatically disconnects the high-voltage supply when the cabinet is opened for servicing or other reasons.

In laying out the unit, the cathode-ray tube must be placed so that the alternating magnetic field from the power transformer has no effect

on the electron beam. The transformer should be mounted directly behind the base of the tube, with the axes of the transformer windings and of the tube on a common line.

It is important that provision be included either for switching off the electron beam or reducing the spot intensity when no signal voltage is being applied. A thin, bright line or a spot of high intensity will "burn" the tube screen.

If trouble is experienced in obtaining a clean pattern from a high-power transmitter because of r.f. voltage introduced by the 115-volt line, by-pass condensers (0.01 or 0.1  $\mu$ fd.) should be connected in series across the primary of the power transformer, the common connection between the two being grounded to the case.

## Antenna Measurements

Antenna measurements are made for the purpose (a) of securing maximum transfer of power to the antenna from the transmitter, and (b) of adjusting directional antennas to conform with design conditions. Measurements of the antenna system include the measurement of transmission-line performance.

### ● FIELD-INTENSITY METERS

In adjusting antenna systems for maximum radiation and in determining radiation patterns, use is made of field-intensity meters. Fundamentally the field-intensity meter consists of a pick-up antenna and an indicating device such as a rectifier and microammeter, or a vacuum-tube voltmeter provided with a tuned input circuit. It is used to indicate the relative intensity of the radiation field under actual radiating conditions. It is particularly useful on the very-high frequencies and in adjusting directional antennas. Field-intensity

checks should be made at points at least several wavelengths distant from the antenna and at heights corresponding with the desired angle of radiation.

The absorption frequency meter shown in Fig. 16-5 may be used as a field-strength meter if provided with a pick-up antenna. It is convenient to have the indicating device separate from the actual pick-up. This arrangement allows the pick-up unit to be set up out in the field to pick up radiation from the antenna under test, while the meter unit is near where adjustments are to be made. Antenna adjustment thus becomes a one-man job.

The unit shown in Figs. 16-29 to 16-31, inclusive, is particularly suitable for measurements in the v.h.f. range. It is constructed in two sections, one containing a tuned circuit, crystal rectifier, and antenna connection, and the other housing a microammeter for registering the rectified current from the crystal. The two units are fitted with matching plug and socket, permitting them to be used together, or they may be interconnected by means of a cable which can be any length up to several hundred feet. Three coils are used, so that measurements may be made on 28, 50 and 144 Mc. A resistor is inserted in series with the crystal and meter, to lessen the loading effect on the tuned circuit and to make the response of the crystal more linear with variations in radiated power. As the resistor reduces the sensitivity somewhat, a switch is provided to short it out in case measurements are to be made with extremely low power or at large distances from the transmitting antenna. A 100-micro-ampere meter is used to give high sensitivity, and a shunt is

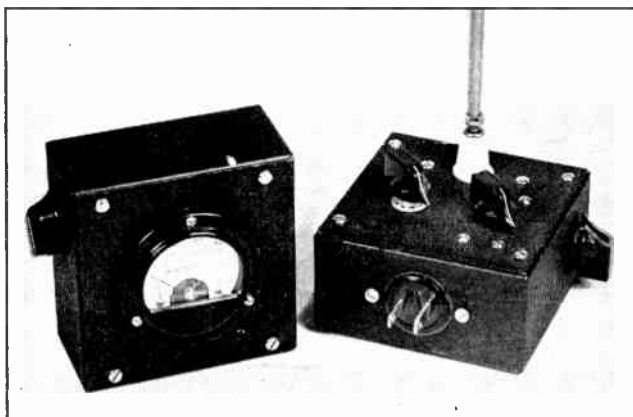


Fig. 16-29 — Remote-indicating field-strength meter, consisting of an r.f. pick-up and rectifier unit, and a meter unit. The knob on the left side of the meter unit is the switch for the shunt. On the pick-up unit the two controls are the bandswitch (left) and tuning. The knob at the right is for the resistor-shorting switch.

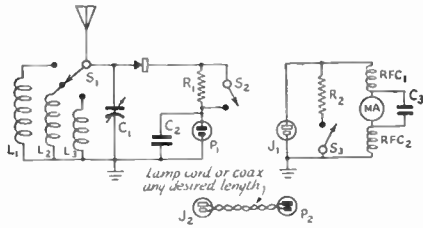


Fig. 16-30 — Wiring diagram of the remote-indicating field-strength meter.

- C<sub>1</sub> — 25- $\mu$ fd. midget variable.
- C<sub>2</sub>, C<sub>3</sub> — 0.001- $\mu$ fd. mica.
- R<sub>1</sub> — 1000 ohms,  $\frac{1}{2}$  watt.
- R<sub>2</sub> — 220 ohms,  $\frac{1}{2}$  watt.
- L<sub>1</sub> — 28-Mc. coil — 7 turns No. 22 enamel,  $\frac{1}{4}$  inch long, on  $\frac{3}{4}$ -inch dia. form (National PRF-1).
- L<sub>2</sub> — 50-Mc. coil — 6 turns No. 22 enamel,  $\frac{1}{4}$  inch long, on 9/16-inch dia. form (National PRF-1).
- L<sub>3</sub> — 144-Mc. coil — 3 turns No. 18 enamel,  $\frac{1}{4}$  inch long,  $\frac{3}{8}$ -inch dia., self-supporting.
- J<sub>1</sub>, J<sub>2</sub> — Universal receptacle, two-pole retainer-ring type (Amphenol 61-F).
- MA — 0-100 microammeter (0-500 microammeter or 0-1 milliammeter may be used, with reduced sensitivity).
- P<sub>1</sub>, P<sub>2</sub> — Polarized plug, two-pole retainer-ring type (Amphenol 61-MP).
- S<sub>1</sub> — 3-position wafer-type switch.
- S<sub>2</sub>, S<sub>3</sub> — S.p.s.t. snap switch.
- RFC<sub>1</sub>, RFC<sub>2</sub> — 2.5 mh. choke (National R-100).

available to multiply the range of the meter by three. This shunt is also provided with a switch so that low or high readings can be taken without making a trip to the pick-up unit. The crystal is the 1N21 type. Germanium crystals (1N34) also may be used with good results.

The two units are housed in 2 × 4 × 4-inch steel boxes with front and back removable. In the pick-up unit all parts except the resistor-shorting switch and connecting plug are mounted on the top panel, permitting easy wiring of the assembly. The interconnecting plug and socket are the polarized type, with one prong on the plug slightly larger than the other. The plug will fit a standard a.c. outlet, so the interconnecting cable (ordinary rubber-covered lamp cord) doubles as a long a.c. extension cord when not in use for its intended purpose.

The antenna connection is a seatite feed-through bushing fitted with a "banana-plug" socket. A convenient pick-up antenna is made by drilling and tapping a  $\frac{1}{4}$ -inch rod for 6/32 thread to take the threaded end of a banana plug. The length of the anten-

na will vary the sensitivity of the unit. If measurements are to be made with high power levels, a rod a few inches in length will suffice, but for ordinary work a length of 24 inches or so will be about right.

## ● CHECKING STANDING WAVES

Standing waves on a transmission line can be measured if it is possible to measure the current at every point along the line, or the voltage between the two conductors at every point along the line. Rough checks can be made by going along the line with an absorption wavemeter having a crystal rectifier, taking care to keep the pick-up coil (or pick-up antenna) at the same distance from the line at every measurement. With such a device the milliammeter usually will indicate current loops if a small pick-up coil is used, and voltage loops if a short pick-up antenna is used.

On two-conductor lines the current can be checked by means of the device shown in Fig. 16-32. The hooks, which should be sharp enough to cut through the insulation (if any) on the wires, are placed on one of the wires. The spacing between the hooks should be adjusted to give a suitable reading on the meter. The standing-wave ratio can be determined by taking readings to determine the maximum and minimum currents along the line. At any one position along the line the currents in the two wires should be identical. If they are not, the line is carrying current either induced by the field of the antenna or coupled into the line through stray capacitance at the transmitter end.

## ● BRIDGE-TYPE STANDING-WAVE INDICATORS

The standing-wave ratio on a transmission line can be found without actually going along

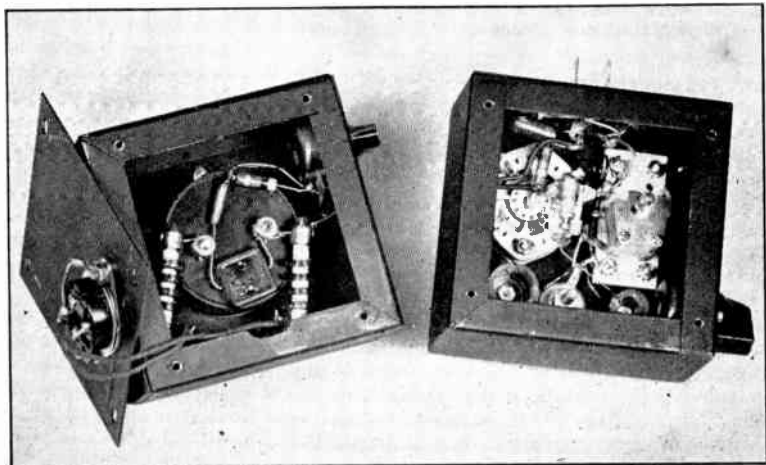


Fig. 16-31 — Inside view of the two units of the remote-indicating field-strength meter.

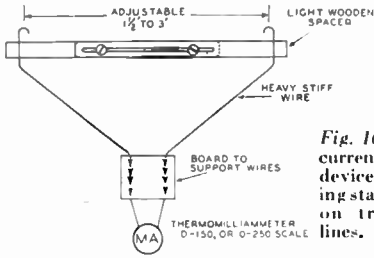


Fig. 16-32 — Line-current measuring device for checking standing waves on transmission lines.

the line and measuring the current or voltage. The basis of such measurement is the separation of the power traveling outward along the transmission line to the load from the power reflected back from the load toward the source. At any point along the line the following relationship is true:

$$S.W.R. = \frac{V_o + V_r}{V_o - V_r}$$

where *S.W.R.* = Standing-wave ratio

$V_o$  = Outgoing component of voltage

$V_r$  = Reflected component of voltage

$V_o$  and  $V_r$  are both taken at the point where the s.w.r. measurement is made.

An ordinary voltage measurement on the

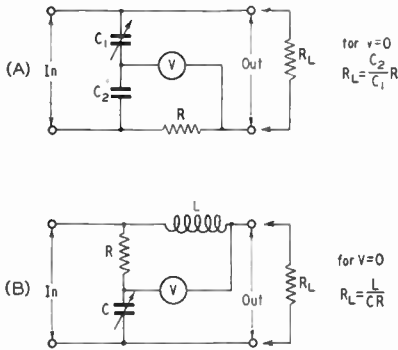


Fig. 16-33 — Fundamental circuits of two bridge-type standing-wave indicators. The upper circuit is used in the "Micro-Match" unit; the lower is a Maxwell bridge.

line simply shows the resultant of the two voltage components, but by using special bridge-type circuits it is possible to obtain voltage readings that are proportional to each component. Two circuits of this type are shown in Fig. 16-33. The one at A is a resistance-capacitance bridge and that at B a Maxwell-type bridge. Both bridges are theoretically independent of the applied frequency, and are practically so up to the frequency where stray inductance, capacitance, and coupling between circuit elements and wiring become of importance. In both circuits the radio-frequency voltmeter, *V*, must be a high-impedance device. The conditions for "balance" — that is, for the voltmeter to read zero regardless of the voltage applied to the input terminals — are given in the equations to the right of each

diagram.  $C_1$  in Fig. 16-33A, and  $C$  in the circuit at B, are made adjustable so that the ratio of the bridge can be varied for various load resistances,  $R_L$ .

If the load,  $R_L$ , is a transmission line, it will look like a pure resistance equal to its characteristic impedance when the line is correctly terminated. Consequently, the voltmeter will read zero when the line is perfectly matched, if the bridge has previously been balanced for that same value of resistance. If the line is not matched, the reflected power will cause the voltmeter to register a reading that is proportional to the reflected voltage. If the load is connected to the "input" terminals and the source of power to the "output" side, the voltmeter reading will be proportional to the outgoing component of voltage. Substituting the two voltmeter readings in the formula above will then give the standing-wave ratio.

Practical circuits corresponding to the two

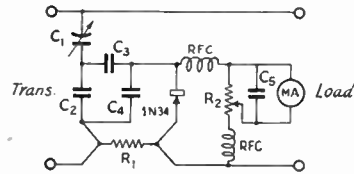


Fig. 16-34 — Circuit diagram of the "Micro-Match" standing-wave indicator.

- $C_1$  — 3–15- $\mu$ fd. midget variable.
- $C_2, C_4$  — 220- $\mu$ fd. mica.
- $C_3$  — 82- $\mu$ fd. mica.
- $C_5$  — 0.0047- $\mu$ fd. mica.
- $R_1$  — 1.1-ohm resistor (9 10-ohm 1-watt carbon resistors in parallel).
- $R_2$  — 5000-ohm potentiometer.
- MA — 0–1 d.c. milliammeter.
- RFC — 2.5-mh. r.f. choke.

in Fig. 16-33 are given in Figs. 16-34 and 16-35. The r.f. voltmeter is a crystal rectifier and 0–1 d.c. milliammeter (or microammeter) with chokes and resistors for keeping the r.f. out of the meter circuit. In order to keep the voltmeter impedance high and to improve the linearity, it is advisable to use as much resist-

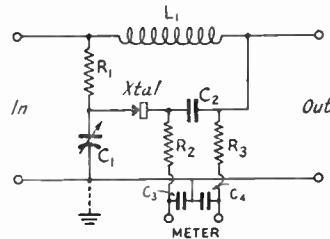


Fig. 16-35 — Circuit diagram of the Maxwell-bridge standing-wave indicator. The meter should have a full-scale range of 1 milliamper or less.

- $C_1$  — 10–100- $\mu$ fd. Ceramicon variable.
- $C_2$  — 470- $\mu$ fd. mica.
- $C_3, C_4$  — (Optional) 100- $\mu$ fd. mica.
- $R_1$  — 500 ohms, nonreactive.
- $R_2, R_3$  — 10,000 ohms, 1/2-watt carbon.
- $L_1$  — Approx. 29 turns No. 18, diameter 0.6 inch, 2.5 inches long.
- XTAL — 1N34 or equivalent.

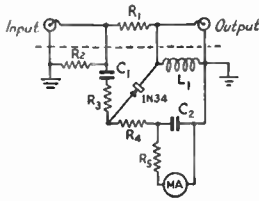


Fig. 16-36 — Circuit diagram of resistance bridge for measuring s.w.r., as adapted for coaxial lines. This circuit operates at very low power level and provision must be made for reducing the transmitter power to a low value when using it.

- C<sub>1</sub>, C<sub>2</sub> — 470- $\mu$ fd. mica.
- R<sub>1</sub> — 1-watt composition resistor, value equal to impedance of line being measured.
- R<sub>2</sub> — 10 ohms, 1 watt.
- R<sub>3</sub>, R<sub>4</sub> — 56-ohm 1-watt composition. Exact value not important but the two resistors must have the same value.
- R<sub>5</sub> — 470 ohms,  $\frac{1}{2}$  watt.
- L<sub>1</sub> — Good r.f. choke at operating frequency. Not required if antenna system is closed type that offers d.c. return. At 28 Mc., 40 turns of No. 36 d.c.c. wound on a 1-watt 0.1-megohm resistor is satisfactory, or a regular 2.5-mh. choke may be used.
- MA — 0-1 milliammeter.

ance in series with the meter as possible while still obtaining full-scale indications at the r.f. power level used.

Several precautions must be observed in constructing and using such instruments. The leads must be kept short, to avoid introducing reactance that would prevent obtaining proper balance. The rectifier-circuit wiring should be kept out of the fields of the other components insofar as possible, since stray pick-up in this wiring will give a "residual" voltmeter reading that will not balance out. It is absolutely essential that the resistors have negligible capacitance and inductance; wire-wound resistors cannot be used with any success.

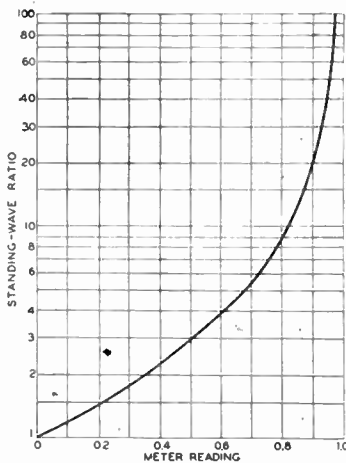


Fig. 16-37 — Standing-wave ratio in terms of meter reading (relative to full scale) after setting outgoing voltage to full scale. This graph is a plot of the formula

$$S.W.R. = \frac{V_o + V_r}{V_o - V_r}$$

To calibrate such a bridge, connect a non-inductive resistor equal to the characteristic impedance of the line to be used to the output terminals, apply an r.f. voltage to the input terminals, and adjust the variable condenser for minimum reading. Then reverse the bridge so that the power source is connected to the output terminals and the resistor load to the input. Adjust the r.f. voltage (by changing the coupling to the transmitter) to make the meter read full scale. Then reverse the bridge connections and check the reading. If it is more than one or two per cent of the full-scale reading it will be necessary to try different arrangements of the wiring until the null reading can be brought as close to zero as possible. The variable condenser can be calibrated in terms of various line impedances by substituting load resistances of the appropriate values, noting the setting for balance at each resistance

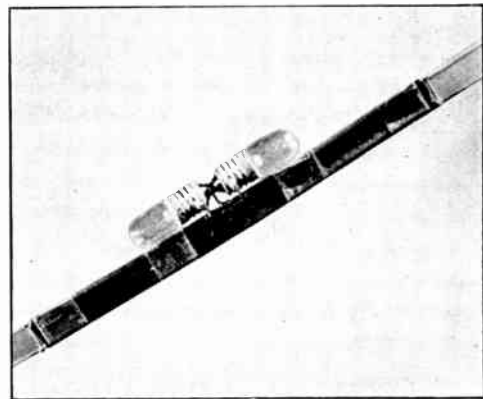


Fig. 16-38 — The "twin-lamp" standing-wave indicator.

value. Both circuits can be used over the range of 50 to 300 ohms, approximately.

In using standing-wave indicators, the readings will be reliable only when there are no "antenna" currents on the transmission line. (See Chapter Ten.) If there is no stray pick-up on the line, it will not matter which line conductor is connected to which output terminal; the meter reading will be the same both ways. The same is true of the connections to the power source. If the way the line or source is connected does make a difference in the readings the results can be considerably in error. Coaxial lines usually are less troublesome in this respect than parallel-conductor lines.

**Resistance Bridge**

The bridge circuit in Fig. 16-36 uses equal resistance arms and can be used with only one value of line impedance. However, it is not necessary to reverse the line and power source to obtain a standing-wave reading. When properly constructed (noninductive resistors must be used) the meter reading will be zero when a noninductive resistance equal to the

line impedance is connected to the output terminals.

To use the bridge, the output terminals are first short-circuited and the input voltage adjusted to give a full-scale reading on the milliammeter. When the short-circuit is removed and the line connected to the output terminals, the meter reading (relative to the full-scale reading) indicates the s.w.r. as shown in Fig. 16-37.

#### The "Twin-Lamp"

A simple and inexpensive standing-wave indicator for 300-ohm line is shown in Fig. 16-38. It consists only of two flashlight lamps and a short piece of 300-ohm line. When laid flat against the line to be checked, the combination of inductive and capacitive coupling is such that outgoing power on the line causes the lamp nearest to the transmitter to light, while reflected power lights the lamp nearest the load. When the line is matched and no power is reflected, the lamp toward the antenna will be dark. The power input to the line should be adjusted to make the lamp nearest the transmitter light to full brilliance. When the lamp nearest the load just begins to glow, the s.w.r. is about 1.5 to 1.

To construct the "twin-lamp," take a short length (a foot or two) of 300-ohm line and remove about  $\frac{1}{4}$  inch of insulation from one wire at the center of the piece. Then take a second piece, 4 to 10 inches long (depending on the frequency and the transmitter power) and short-circuit both ends. Cut one wire in the exact center of the piece and peel the ends back on either side just far enough to provide

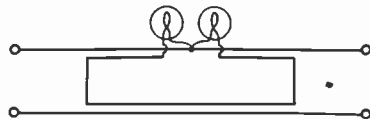


Fig. 16-39 — Wiring diagram of the "twin-lamp" standing-wave indicator.

leads to the flashlight lamps. Use the lowest-current flashlight bulbs or dial lamps available. Solder the tips of the bulbs together and connect them to the bare point in the long section of line, then solder the ends of the cut portion of the short piece to the shells of the bulbs. Figs. 16-38 and 16-39 should make the construction clear. The whole unit forms a "test section" that can be inserted in series with the line to be measured.

While the "twin-lamp" cannot readily be used for quantitative measurement of s.w.r., it is very useful in checking the effect of load adjustments on the standing-wave ratio, when 300-ohm line is used.

#### References

The construction of a bridge-type standing-wave indicator is critical both as to layout and materials. Additional information will be found in the following *QST* articles:

Jones and Sontheimer, "The 'Micromatch,'" April, 1947; "Additional Notes on the 'Micromatch,'" July, 1947.

Pattison, Morris and Smith, "A Standing-Wave Meter for Coaxial Lines," July, 1947.

Wright, "The 'Twin-Lamp,'" October, 1947.

Tiffany, "A Universal Transmission Bridge," December, 1947.



# Assembling a Station

An amateur station is generally far better known by its signal and good operation than by its physical appearance. Good operating and a clean signal will build a reputation faster than thousands of dollars invested in special equipment and an elaborate "shack," and it is this very fact that makes amateur radio the democratic hobby that it is. However, most amateurs take pride in the arrangement of their stations, in the same way that they are careful of the appearance and arrangement of anything else which is part of the household. An antenna installation is the only external indication of the amateur station, and the degree of neatness required is generally determined by the district where the amateur lives and the attitude of the neighbors.

The actual location inside the house of the "shack" — the room where the transmitter and receiver are located — depends, of course, on the free space available for amateur activities. Fortunate indeed is the amateur with a separate room that he can devote to his amateur station, or the few who can have a special small building separate from the main house. However, most amateurs must share a room with other domestic activities, and amateur stations will be found tucked away in a corner of the living room, a bedroom, a large closet, or even under the kitchen stove! A spot in the cellar or the attic can almost be classed as a separate room, although it may lack the "finish" of a normal room.

Regardless of the location of the station, however, it should be designed for maximum operating convenience and safety. It is foolish to have the station arranged so that the throwing of several switches is required to go from "receive" to "transmit," just as it is silly to have the equipment arranged so that the operator is in an uncomfortable and cramped position during his operating hours. The reasons for building the station as safe as possible are obvious, if you are interested in spending a number of years with your hobby!


## ● CONVENIENCE

The first consideration in any amateur station is the operating position, which includes the operator's table and chair and the

pieces of equipment that are in constant use (the receiver, send-receive switch, and key or microphone). The table should be as large as possible, to allow sufficient room for the receiver or receivers, frequency-measuring equipment, monitoring equipment, control switches, and keys and microphones, with enough space left over for the logbook, a pad and pencil, and perhaps a *large* ash tray. Suitable space should be included for radiogram blanks and a call book, if these accessories are in frequent use. If the table is small, or the number of pieces of equipment is large, it is often necessary to build a shelf or rack for the auxiliary equipment, or to mount it in some less convenient location in or under the table. If one has the facilities, a semicircular "console" can be built of wood, or a simpler solution is to use two small wooden cabinets to support a table top of wood or Masonite. Home-built tables or consoles can be finished in any of the available oil stains, varnishes, paints or lacquers. Many operators



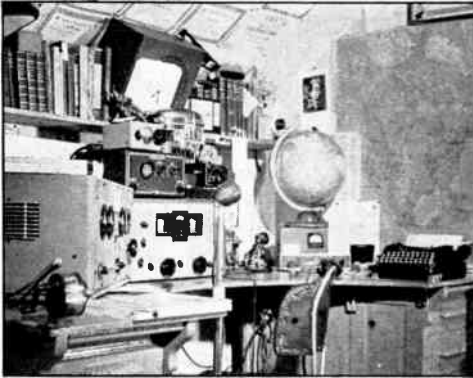This station is tucked away in a corner of the attic, and everything is accessible to the operator without his leaving the chair. The second-hand furniture was not an attempt to be fancy, but simply the only way the operator could find any lumber during a shortage. (W4JIZ/W4KFC, Annandale, Va.)




A convenient operating position can be obtained by building a "horseshoe-type" operating desk as shown here. Considerably more equipment can be placed on the desk around the operator than if an ordinary desk is used. (W9AND, Dixon, Ill.)

use a large piece of plate glass over part of their table, since it furnishes a good writing surface and can cover miscellaneous charts and tables, prefix lists, operating aids, calendar, and similar accessories.

If the major interests never require frequent band changing, or frequency changing within a band, the transmitter can be located some distance from the operator, in a location where the meters can be observed from time to time (and the color of the tube plates noted!). If frequent band or frequency changes are a part of the usual operating procedure, the transmitter should be mounted close to the operator, either along one side or above the receiver, so that the controls are easily accessible without the need for leaving the operating position.

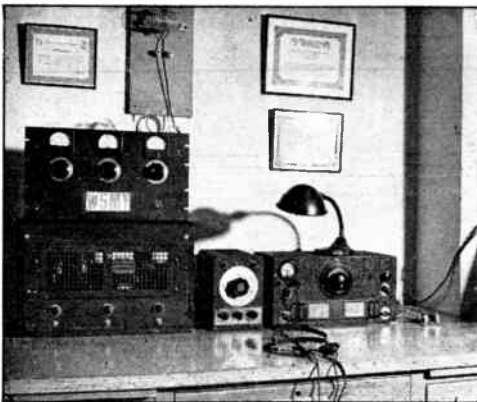A compromise arrangement would place the VFO or crystal-switched oscillator at the operating position and the transmitter in some convenient location not adjacent to the op-




When one specializes in clean-cut c.w. operation on all bands, he is likely to come up with a neat arrangement like this. The transmitter runs 400 watts, despite its small size. The small unit between transmitter and receiver is the VFO. (W5MY, San Antonio, Texas)

erator. Since it is usually possible to operate over a portion of a band without retuning the transmitter stages, an operating position of this type is an advantage over one in which the operator must leave his position to make a change in frequency.

### Controls

The operator has an excellent chance to exercise his ingenuity in the location of the operating controls. The most important controls in the station are the receiver tuning dial and the send-receive switch. The receiver tuning dial should be located four to eight inches above the operating table, and if this requires mounting the receiver off the table, a small

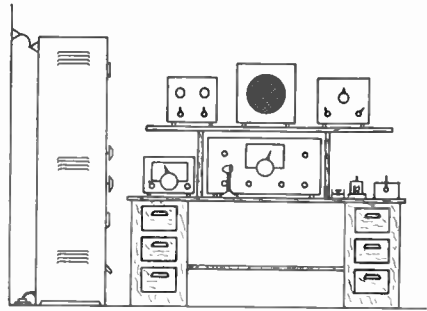

*Fig. 17-1* — In a station assembled for maximum ease in frequency or band changing, the transmitter should be located next to the operating position, as shown above. On the operating table, the receiver is in front of the operator and the VFO or crystal-switching oscillator on the left. (The VFO or crystal oscillator could be part of the transmitter proper, but most operators seem to prefer a separate VFO.)

The frequency standard and other auxiliary equipment can be mounted on a shelf above the receiver. The operating table can be an old desk, or a top supported by two small wooden cabinets. The "send-receive" switch is to the right of the telegraph keys — other switches are on the transmitter or the individual units.

The above arrangement can be made to look cleaner by arranging all of the equipment on the table behind a single panel or a set of panels. In this case, provision must be made for getting behind the panel for servicing the units.

shelf or bracket will do the trick. With the single exception of the amateur whose work is almost entirely in traffic or rag-chew nets, which require little or no attention to the receiver, it will be found that the operator's hand is on the receiver tuning dial most of the time. If the tuning knob is too high or too low, the hand gets cramped after an extended period of operating, hence the importance of a properly-located receiver. The majority of c.w. operators tune with the left hand, preferring to leave the right hand free for copying messages and handling the key, and so the receiver should be mounted where the knob can be reached by the left hand. 'Phone operators aren't tied down this way, and tune the communications receiver with the hand that is more convenient.


The hand-key should be fastened securely to the table, in a line just outside the right

shoulder and far enough back from the front edge of the table so that the elbow can rest on the table. A good location for the semiautomatic or "bug" key is right next to the hand-key, although some operators prefer to mount the automatic key in front of them on the left, so that the right forearm rests on the table parallel to the front edge.

The best location of the microphone is directly in front of the operator, so that he doesn't have to shout across the table into it, or run up the speech-amplifier gain so high that all manner of external sounds are picked up.

In any amateur station worthy of the name, it should be necessary to throw no more than one switch to go from the "receive" to the "transmit" condition. In 'phone stations, this switch should be located where it can be easily reached by the hand that isn't on the receiver. In the case of c.w. operation, this switch is most conveniently located to the right or left of the key, although some operators prefer to have it mounted on the left-hand side of the operating position and work it with the left hand while the right hand is on the key. Either location is satisfactory, of course, and the choice depends upon personal preference. Some operators use a foot-controlled switch, which is a convenience but doesn't allow too much freedom of position during long operating periods.

If the microphone is hand-held during 'phone operation, a "push-to-talk" switch on the microphone is convenient, but hand-held microphones tie up the use of one hand and

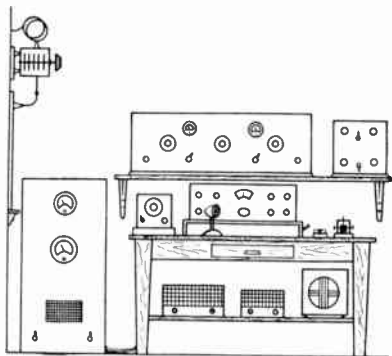

*Fig. 17-2* — When little space is available for the amateur station, the equipment has to be spotted where it will fit. In the above arrangement, the transmitter, modulator and power supplies (separate units) are sandwiched in alongside the operating table and on a shelf above the table. The antenna tuning unit is mounted over the feed-through insulators that bring the antenna line into the "shack," and loudspeaker and small power supplies are mounted under the table. The operating position is clean, however, with the VFO, receiver and keys at table level. The tuning knob of this receiver would be uncomfortably low if the receiver weren't raised by the wooden arch, and the "send-receive" switch is mounted on the right-hand side of this arch, next to the hand-key. Interconnecting leads should be cabled along the back of the table and table legs, to keep them inconspicuous.



A high-powered station in a room with enough space to locate the transmitters along one wall and the operating table along another. Note the convenient location of the control switches, and the receiver raised above the table. (WICH, Worcester, Mass.)

are not too desirable, although they are widely used in mobile and portable work. A breast, chin or throat microphone is safer for mobile work, if the operator is also the driver of the vehicle.

The location of other switches, such as those used to control power supplies, filaments, 'phone/c.w. change-over and the like, is of no particular importance, and they can be located on the unit with which they are associated. This is not strictly true in the case of the 'phone/c.w. DX man, who sometimes has need to change in a hurry from c.w. to 'phone. In this case, the change-over switch should be at the operating table, although the actual change-over should be done by a relay that the switch controls.

If a rotary beam is used the control of the beam should be convenient to the operator. The beam-direction indicator, however, can be located anywhere within sight of the operator, and does not have to be located on the operating table unless it is small, or included with the beam control.

When several fixed beams are used, the selection of any one should be possible from the operating position, to minimize the time required to select the proper one. This generally means using a series of antenna relays or a stepping switch.

### Frequency Spotting

In a station where a VFO is used, or where a number of crystals is available, the operator should be able to turn on only the oscillator of his transmitter, so that he can spot accurately his location in the band with respect to other stations. This allows him to see if he has anything like a clear channel (if such a thing exists in the amateur bands!), or to see what his frequency is with respect to another station. Such a provision can be part of the "send-receive" switch. Switches are available with a center "off" position, a "hold" position on one side,

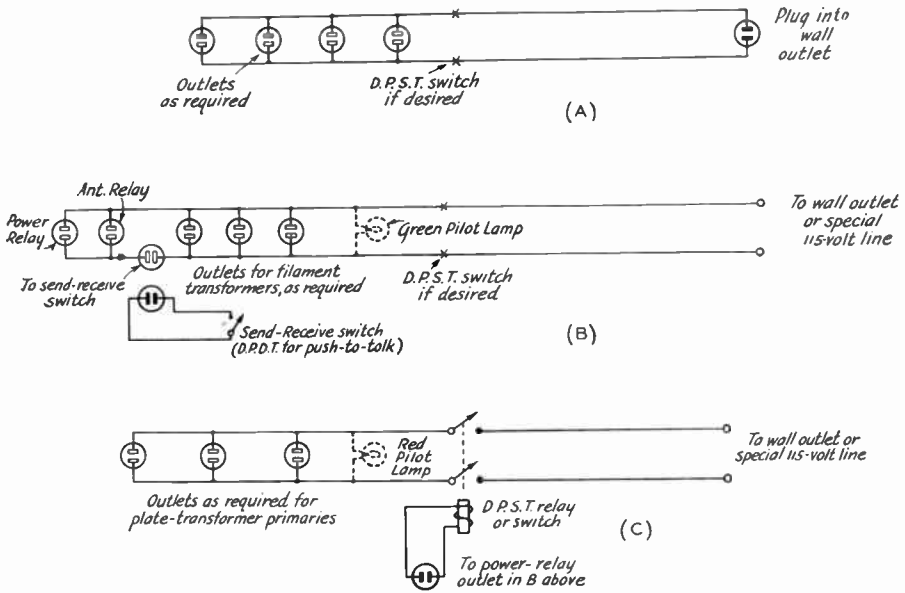


Fig. 17-3 — Power circuits for a high-power station. A shows the outlets for the receiver, monitoring equipment, speech amplifier and the like. The outlets should be mounted inconspicuously on the operating table. B shows the transmitter filament circuits and control-relay circuits, if the latter are used. C shows the plate-transformer primary circuit, controlled by the power relay. A heavy-duty switch can be used instead of the relay, in which case the antenna relay would be connected in circuit C.

If 115-volt pilot lamps are used, they can be connected as shown. Lower-voltage lamps must be connected across suitable windings on transformers.

With "push-to-talk" operation, the "send-receive" switch can be a d.p.d.t. affair, with the second pole controlling the "on-off" circuit of the receiver.

for turning on the oscillator only, and a "lock" position on the other side for turning on the transmitter and antenna relays. If oscillator keying is used, the key serves the same purpose, provided a "send-receive" switch is available to turn off the high-voltage supplies and prevent a signal going out on the air during adjustment of the oscillator frequency.

For 'phone operation, the telegraph key or an auxiliary switch can control the transmitter oscillator, and the "send-receive" switch can then be wired into the control system so as to control the oscillator as well as the other circuits.

**Comfort**

Of prime importance is the comfort of the operator. If you find yourself getting tired after a short period of operating, examine your station to find what causes the fatigue. It may be that the chair is too soft or hasn't a straight back or is the wrong height for you. The key or receiver may be located so that you assume an uncomfortable position while using them. If you get sleepy fast, the ventilation may be at fault. (Or you may need sleep!)

● **POWER CONNECTIONS AND CONTROL**

Following a few simple rules in wiring your power supplies and control circuits will make it an easy job to change units in the station. If the station is planned in this way from the start, or if the rules are recalled when you are rebuilding, you will find it a simple matter to revise your station from time to time without a major rewiring job.

The regular wall outlets in a home are generally rated at 15 amperes at 115 volts, and so will furnish sufficient power for receivers, monitoring equipment, speech amplifiers, and anything that doesn't draw too high an intermittent load (such as a keyed transmitter or Class B modulator). A low-powered transmitter, under one or two hundred watts, can be supplied by an ordinary wall outlet. To make a neat installation, it is better to run a single pair of wires from the outlet over to the



An example of the compact station, complete on the operating table. The receiver is mounted on the left side of the table, for left-hand tuning. The beam-direction indicator and switches are housed in a small box sitting on the YFO. (W2NFL, Forest Hills, N. Y.)

operating table or some central point, rather than to use a number of adapters at the wall outlet.

In a high-powered station, the receiver and auxiliary equipment can get their power from the wall outlet, but it is advisable to run in a special, heavy three-wire line from the meter box for the transmitter. This three-wire line will, of course, be 115 volts either side of neutral (ground), or 230 volts across the outside. In many cases it is possible to run the filaments and constant loads from one side of this three-wire line and the intermittent loads (plate transformers) from the other side. In this case the filament voltages will rise slightly with the application of load, because of the reduced net current in the neutral. However, this procedure often unbalances the system too much, resulting in considerable "blinking" of the lights, and the load must be distributed equally across the 230-volt circuit. This can be done by using plate transformers with 230-volt primaries, by dividing the load as equally as possible across both 115-volt circuits, or by using autotransformers that step down the 230 volts to 115 volts and connecting the plate-transformer primaries across the autotransformer secondaries. Obviously balancing the load is the cheapest "out" and the first one to try.

If the lights blink with keying or modulation of a low-powered transmitter that gets its power from a regular wall outlet, taking some of the power from another outlet may help to improve the regulation and is always worth a try.

When a special heavy line is run into the shack for a high-powered transmitter, it will generally be done by a licensed electrician who can advise you on the various types of outlets that are available. Some amateurs terminate their special lines in switch boxes, while others end the line in an electric-stove receptacle. In case you do the work yourself, it is wise to find out if there are any special regulations in your area covering the type of wire, insulation and outlet which must be used. The power companies are always willing to advise you if it looks as though you will be using more power!

#### Interconnections

The wiring of any station will entail two or three common circuits. The circuit for the receiver, monitoring equipment and the like, assuming it to be taken from a wall outlet should be run from the wall to an inconspicuous point on the operating table, where it terminates in a multiple outlet large enough to handle the required number of plugs. A single switch between the wall outlet and the receptacle will then turn on all of this equipment at one time, or the plug can simply be pulled out at the wall when leaving the shack.

The second common circuit in the station is that supplying voltage to rectifier- and transmitter-tube filaments, bias supplies, and any-

thing else that is not switched on and off during transmit and receive periods. The coil power for control relays should also be obtained from this circuit. The power for this circuit can come from a wall outlet or from the transmitter line, if a special one is used.

The third circuit is the one that furnishes power for the power-supply transformers for the r.f. stages and for the modulator. When it is opened, the transmitter is disabled except for the filaments, and the transmitter should be safe to work on. However, one always feels safer when working on the transmitter if he has turned off everything pertaining to the transmitter.


With these three circuits established, it becomes a simple matter to arrange the station for different conditions and with new units. Anything on the operating table (which runs all the time) ties into the first circuit. Any new power supply or r.f. unit gets its filament power from the second circuit. Since the third circuit is controlled by the send-receive switch (or relay), any power-supply primary that is to be switched on and off for send and receive connects to circuit No. 3.
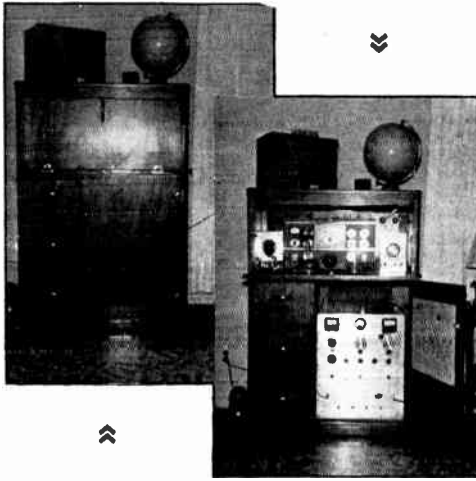
#### Break-In and Push-To-Talk

In c.w. operation, "break-in" is any system that allows the transmitting operator to hear the other fellow's signal during the "key-up" periods between characters and letters. This allows the sending station to be "broken" by the receiving station at any time, to shorten calls, ask for "fills" in messages, and speed up operation in general. With present techniques, it requires the use of a separate receiving antenna and, with high power, some means for protecting the receiver from the transmitter when the key is "down." Several methods, applicable to high-powered stations, are described in Chapter Eight. If the transmitter is low-powered (50 watts or so), no special



In this example of a compact high-powered station, the operating table folds up when not in use and covers the receiver and speech amplifier. Special furniture, like this homemade operating table, goes a long way toward solving the space problem for many amateurs. (W4HAY, Fort Thomas, Ky.)



This station goes all the way in concealment by housing the entire station in a special cabinet. When the cabinet is opened, the operating table is formed and all pieces of gear are accessible. (W6YNN, Mountain View, Calif.)

equipment is required except the separate receiving antenna and a receiver that "recovers" fast. Where break-in operation is used, there should be a switch on the operating table to turn off the plate supplies when adjusting the oscillator to a new frequency, although during all break-in work this switch will be closed.

"Push-to-talk" is an expression derived from the "push" switch on some microphones, and it means a 'phone station with a single control for all change-over functions. Strictly speaking, it should apply only to a station where this single send-receive switch must be held in place during transmission periods, but any fast-acting switch will give practically the same effect. A control switch with a center "off" position, and one "hold" and one "lock" position, will give more flexibility than a straight "push" switch. The one switch must control the antenna change-over relay, the transmitter power supplies, and the receiver "on-off" circuit. This latter is necessary to disable the receiver during transmit periods, to avoid acoustic feed-back.

#### Switches and Relays

It is dangerous to use an overloaded switch in the power circuits. After it has been used for some time, it may fail, leaving the power on the circuit even after the switch is thrown to the "off" position. For this reason, large switches, or relays with adequate ratings, should be used to control the plate power. Relays are rated by coil voltages (for their control circuits) and by their contact ratings (what they will carry safely).

When relays are used, the send-receive switch closes the circuit to their coils, thus closing the relay contacts. The relay contacts are in the power circuit being controlled, and thus the switch handles only the relay-coil current.

#### SAFETY

Of prime importance in the layout of the station is the personal safety of the operator and of visitors, invited or otherwise, during normal operating practice. If there are small children in the house, every step must be taken to prevent their accidental contact with power leads of any voltage. A locked room is a fine idea, if it is possible, otherwise, housing the transmitter and power supplies in metal cabinets is an excellent, although expensive, solution. Lacking a metal cabinet, a wooden cabinet or a wooden framework covered with wire screen is the next best solution. Many stations have the power supplies housed in metal cabinets in the operating room or in a closet or basement, and this cabinet or entry is kept locked — with the key out of reach of everyone but the operator. The power leads are run through conduit to the transmitter, using ignition cable for the high-voltage leads. If the power supplies and transmitter are in the same cabinet, a lock-type main switch for the incoming line power is a good precaution.

A simple substitute for a lock-type main switch is an ordinary line plug with a short connecting wire between the two pins. By wiring a female receptacle in series with the main power line in the transmitter, the shorting plug will act as the main safety lock. When the plug is removed and hidden, it will be impossible to energize the transmitter, and a stranger or child isn't likely to spot or suspect the open receptacle.

An essential adjunct to any station is a **shorting stick** for discharging any high voltage to ground before any work or coil changing is done in the transmitter. Even if interlocks and power-supply bleeders are used, the failure of one or more of these components may leave the transmitter in a dangerous condition. The shorting stick is made by mounting a small metal hook, of wire or rod, on one end of a dry stick or bakelite rod. A piece of ignition cable or other well-insulated wire is then run from the hook on the stick to the chassis or common ground of the transmitter, and the stick is hung alongside the transmitter. Whenever the power is turned off in the transmitter to work on the rig, or to change coils, the shorting stick is first used to touch the several high-voltage leads (tank condenser, filter condenser, tube plate connection, etc.) to insure that there is no high voltage at any of these points. Most commercial installations require the use of this simple device, and it has saved many a life. Use it!

#### Fusing

A minor hazard in the amateur station is the possibility of fire through the failure of a component. If the failure is complete and the component is large, the house fuses will generally blow. However, it is unwise and inconvenient to depend upon the house fuses to

protect the lines running to the radio equipment, and every power supply should have its own set of fuses, with the fuse ratings selected at about 150 or 200 per cent of the maximum rating of the supply. If, for example, a power transformer is rated at 600 watts, it would draw about 5 amperes from the a.c. line ( $600 \div 115 = 5.2$ ), and a 10-ampere fuse should be used in the primary circuit of the transformer. Circuit breakers can be used instead of fuses if desired.

### *Wiring*

Control-circuit wires running between the operating position and a transmitter in another part of the room should be hidden if possible. This can be done by running the wires under the floor or behind the base molding, bringing the wires out to terminal boxes or regular wall fixtures. Such construction, however, is generally only possible in elaborate installations, and the average amateur must content himself with trying to make the wires as inconspicuous as possible. If several pairs of leads must be run from the operating table to the transmitter, as is generally the case, a single piece of rubber- or vinyl-covered multiconductor cable will always look neater than several pieces of rubber-covered lamp cord.

The antenna wires always present a problem, unless coaxial-line feed is used. Open-wire line from the point of entry of the antenna line should always be arranged neatly, and it is generally best to support it at several points. Many operators prefer to mount their antenna-tuning assemblies right at the point of entry of the feedline, together with an antenna change-over relay (if one is used), and then the link from the tuning assembly to the transmitter can be made of inconspicuous coaxial line or Twin-Lead. If the transmitter is mounted near the point of entry of the antenna line, it sim-



There was enough room at this station to build the transmitter into the wall, and to protect it with glass doors. In an installation like this, it is convenient to have access to the rear of the transmitter units, for making connection to them and for testing. If the rear cannot be reached, all power leads should be cabled up along the side walls, at the rear. (W6NY, Whittier, Calif.)

plifies the problem of "what to do with the feeders."

### *General*

You can check your station arrangement by asking yourself the following questions. If all of your answers are an honest "Yes," your station will be one of which you can be proud.

- 1) Is your station safe, under normal operating conditions, both for the operator and the visitor?
- 2) Is the operating position comfortable, even after several hours of operating?
- 3) Do you throw not more than one switch to go from "receive" to "transmit"?
- 4) Does it take only a short time to explain to another amateur how to work your station?
- 5) Do you show your station to visiting amateurs or laymen without apologizing for its appearance?

# The Amateur's Workshop

## ● TOOLS AND MATERIALS

While an easier, and perhaps a better, job can be done with a greater variety of tools available, by taking a little thought and care it is possible to turn out a fine piece of equipment with only a few of the common hand tools. A list of tools which will be indispensable in the construction of radio equipment will be found on this page. With these tools it should be possible to perform any of the required operations in preparing

panels and metal chassis for assembly and wiring. It is an excellent idea for the amateur who does constructional work to add to his supply of tools from time to time as finances permit.

Several of the pieces of light woodworking machinery, often sold in hardware stores and mail-order retail stores, are ideal for amateur radio work, especially the drill press, grinding head, band and circular saws, and joiner. Although not essential, they are desirable should you be in a position to acquire them.

### *Twist Drills*

Twist drills are made of either high-speed steel or carbon steel. The latter type is more common and will usually be supplied unless specific request is made for high-speed drills. The carbon drill will suffice for most ordinary equipment construction work and costs less than the high-speed type.

While twist drills are available in a number of sizes those listed in bold-faced type in Table 18-1 will be most commonly used in construction of amateur equipment. It is usually desirable to purchase several of each of the commonly-used sizes rather than a quantity of odd sizes, most of which will be used infrequently, if at all.

### *Care of Tools*

The proper care of tools is not alone a matter of pride to a good workman. He also realizes the energy which may be saved and the annoyance which may be avoided by the possession of a full kit of well-kept sharp-edged tools.

Drills should be sharpened at frequent intervals so that grinding is kept at a minimum each time. This makes it easier to maintain the rather critical surface angles required for best cutting with least wear. Occasional oil-stoning of the cutting edges of a drill or reamer will extend the time between grindings.

The soldering iron can be kept in good condition by keeping the tip well tinned with solder and not allowing it to run at full voltage for long periods when it is not being used. After each period of use, the tip should be removed and cleaned of any scale which may have accumulated. An oxidized tip may be

#### INDISPENSABLE TOOLS

Long-nose pliers, 6-inch.  
Diagonal cutting pliers, 6-inch.  
Screwdriver, 6- to 7-inch,  $\frac{1}{4}$ -inch blade.  
Screwdriver, 4- to 5-inch,  $\frac{1}{8}$ -inch blade.  
Scratch awl or scriber for marking lines.  
Combination square, 12-inch, for laying out work.  
Hand drill,  $\frac{1}{4}$ -inch chuck or larger, 2-speed type preferable.  
Electric soldering iron, 100 watts.  
Hacksaw, 12-inch blades.  
Center punch for marking hole centers.  
Hammer, ball-peen, 1-lb. head.  
Heavy knife.  
Yardstick or other straightedge.  
Carpenter's brace with adjustable hole cutter or socket-hole punches (see text).  
Large, coarse, flat file.  
Large round or rat-tail file,  $\frac{1}{2}$ -inch diameter.  
Three or four small and medium files—flat, round, half-round, triangular.  
Drills, particularly  $\frac{1}{4}$ -inch and Nos. 18, 28, 33, 42 and 50.  
Combination oil stone for sharpening tools.  
Solder and soldering paste (noncorroding).  
Medium-weight machine oil.

#### ADDITIONAL TOOLS

Bench vise, 4-inch jaws.  
Tin shears, 10-inch, for cutting thin sheet metal.  
Taper reamer,  $\frac{1}{2}$ -inch, for enlarging small holes.  
Taper reamer, 1-inch, for enlarging holes.  
Countersink for brace.  
Carpenter's plane, 8- to 12-inch, for woodworking.  
Carpenter's saw, crosscut.  
Motor-driven emery wheel for grinding.  
Long-shank screwdriver with screw-holding clip for tight places.  
Set of "Spintite" socket wrenches for hex nuts.  
Set of small, flat, open-end wrenches for hex nuts.  
Wood chisel,  $\frac{1}{2}$ -inch.  
Cold chisel,  $\frac{1}{2}$ -inch.  
Wing dividers, 8-inch, for scribing circles.  
Set of machine-screw taps and dies.  
Folding rule, 6-foot.  
Dusting brush.



cleaned by dipping it in sal ammoniac while hot and then wiping it clean with a rag. If the tip becomes pitted, it should be filed until smooth and bright, and then tinned by dipping it in solder.

**Useful Materials**

Small stocks of various miscellaneous materials will be required in constructing radio apparatus, most of which are available from hardware or radio-supply stores. A representative list follows:

1/2 x 1/16-inch brass strip for brackets, etc. (half-hard for bending).

1/4-inch-square brass rod or 1/2 x 1/2 x 1/16-inch angle brass for corner joints.

1/4-inch diameter round brass rod for shaft extensions.

Machine screws: Round-head and flat-head, with nuts to fit. Most useful sizes: 4-36, 6-32 and 8-32, in lengths from 1/4 inch to 1 1/2 inches. (Nickel-plated iron will be found satisfactory except in strong r.f. fields, where brass should be used.)

Bakelite and hard-rubber scraps.

Soldering lugs, panel bearings, rubber grommets, terminal-lug wiring strips, varnished-cambrie insulating tubing.

Machine screws, nuts, washers, soldering lugs, etc., are most reasonably purchased in quantities of a gross.

● **CHASSIS WORKING**

With a few essential tools and proper procedure, it will be found that building radio gear on a metal chassis is no more of a chore than building with wood, and a more satisfactory job results.

The placing of components on the chassis is shown quite clearly in the photographs in this *Handbook*. Aside from certain essential dimensions, which usually are given in the text, exact duplication is not necessary.

Much trouble and energy can be saved by spending sufficient time in planning the job. When all details are worked out beforehand the actual construction is greatly simplified.

Cover the top of the chassis with a piece of wrapping paper or, preferably, cross-section

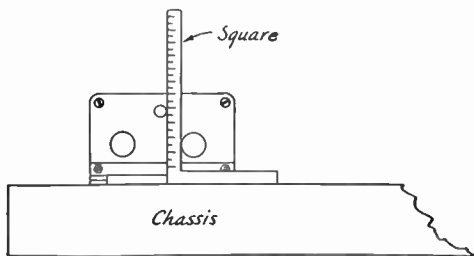


Fig. 18-1 — Method of measuring the heights of condenser shafts, etc. If the square is adjustable, the end of the scale should be set flush with the face of the head.

**TABLE 18-1**  
**Numbered Drill Sizes**

Number	Diameter (mils)	Will Clear Screw	Drilled for Tapping Iron, Steel or Brass*
1	228.0	—	—
2	221.0	12-24	—
3	213.0	—	14-24
4	209.0	12-20	—
5	205.0	—	—
6	204.0	—	—
7	201.0	—	—
8	199.0	—	—
9	196.0	—	—
10	193.5	10-32	—
11	191.0	10-24	—
12	189.0	—	—
13	185.0	—	—
14	182.0	—	—
15	180.0	—	—
16	177.0	—	12-24
17	173.0	—	—
18	169.5	8-32	—
19	166.0	—	12-20
20	161.0	—	—
21	159.0	—	10-32
22	157.0	—	—
23	154.0	—	—
24	152.0	—	—
25	149.5	—	10-24
26	147.0	—	—
27	144.0	—	—
28	140.0	6-32	—
29	136.0	—	8-32
30	128.5	—	—
31	120.0	—	—
32	116.0	—	—
33	113.0	4 36, 1 40	—
34	111.0	—	—
35	110.0	—	6-32
36	106.5	—	—
37	104.0	—	—
38	101.5	—	—
39	99.5	3-48	—
40	98.0	—	—
41	96.0	—	—
42	93.5	—	4-36, 4-40
43	89.0	2-56	—
44	86.0	—	—
45	82.0	—	3-48
46	81.0	—	—
47	78.5	—	—
48	76.0	—	—
49	73.0	—	2-46
50	70.0	—	—
51	67.0	—	—
52	63.5	—	—
53	59.5	—	—
54	55.0	—	—

\*Use one size larger for tapping bakelite and hard rubber.

paper, folding the edges down over the sides of the chassis and fastening with adhesive tape. Then assemble the parts to be mounted on top of the chassis and move them about until a satisfactory arrangement has been found, keeping in mind any parts which are to be mounted underneath, so that interferences in mounting may be avoided. Place condensers and other parts with shafts extending through the panel first, and arrange them so that the controls will form the desired pattern on the panel. Be sure to line up the shafts squarely with the chassis front. Locate any partition shields and panel

brackets next, and then the tube sockets and any other parts, marking the mounting-hole centers of each accurately on the paper. Watch out for condensers whose shafts are off center and do not line up with the mounting holes. Do not forget to mark the centers of socket holes and holes for leads under i.f. transformers, etc., as well as holes for wiring leads.

By means of the square, lines indicating accurately the centers of shafts should be extended to the front of the chassis and marked on the panel at the chassis line, the panel being fastened on temporarily. The hole centers may then be punched in the chassis with the center punch. After drilling, the parts which require mounting underneath may be located and the mounting holes drilled, making sure by trial that no interferences exist with parts mounted on top. Mounting holes along the front edge

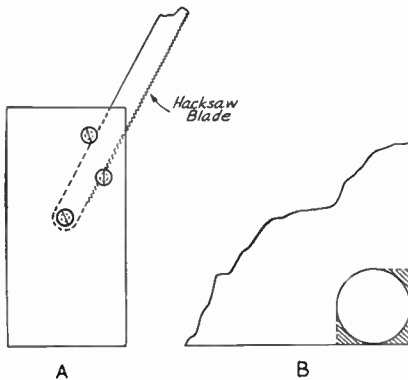


Fig. 18-2—To cut rectangular holes in a chassis corner, holes may be filed out as shown in the shaded portion of B, making it possible to start the hacksaw blade along the cutting line. A shows how a single-ended handle may be constructed for a hacksaw blade.

of the chassis should be transferred to the panel, by once again fastening the panel to the chassis and marking it from the rear.

Next, mount on the chassis the condensers and any other parts with shafts extending to the panel, and measure accurately the height of the center of each shaft above the chassis, as illustrated in Fig. 18-1. The horizontal displacement of shafts having already been marked on the chassis line on the panel, the vertical displacement can be measured from this line. The shaft centers may now be marked on the back of the panel, and the holes drilled. Holes for any other panel equipment coming above the chassis line may then be marked and drilled, and the remainder of the apparatus mounted.

#### Drilling and Cutting Holes

When drilling holes in metal with a hand drill it is important that the centers first be located with a center punch, so that the drill point will not "walk" away from the center when starting the hole. When the drill starts to

break through, special care must be used. Often it is an advantage to shift a two-speed drill to low gear at this point. Holes more than  $\frac{1}{4}$  inch in diameter may be started with a smaller drill and reamed out with the larger drill.

The chuck on the usual type of hand drill is limited to  $\frac{1}{4}$ -inch drills. Although it is rather tedious, the  $\frac{1}{4}$ -inch hole may be filed out to larger diameters with round files. Another method possible with limited tools is to drill a series of small holes with the hand drill along the inside of the diameter of the large hole, placing the holes as close together as possible. The center may then be knocked out with a cold chisel and the edges smoothed up with a file. Taper reamers which fit into the carpenter's brace will make the job easier. A large rat-tail file clamped in the brace makes a very good reamer for holes up to the diameter of the file, if the file is revolved counterclockwise.

For socket holes and other large round holes, an adjustable cutter designed for the purpose may be used in the brace. Occasional application of machine oil in the cutting groove will help. The cutter first should be tried out on a block of wood, to make sure that it is set for the correct diameter. Probably the most convenient device for cutting socket holes is the socket-hole punch. The best type is that which works by turning a take-up screw with a wrench.

#### Rectangular Holes

Square or rectangular holes may be cut out by making a row of small holes as previously described, but is more easily done by drilling a  $\frac{1}{8}$ -inch hole inside each corner, as illustrated in Fig. 18-2, and using these holes for starting and turning the hacksaw. The socket-hole punch also may be of considerable assistance in cutting out large rectangular openings.

The burrs or rough edges which usually result after drilling or cutting holes may be removed with a file, or sometimes more conveniently with a sharp knife or chisel. It is a good idea to keep an old wood chisel sharpened and available for this purpose. A burr reamer will also be useful.

#### CONSTRUCTION NOTES

If a control shaft must be extended or insulated, a flexible shaft coupling with adequate insulation should be used. Satisfactory support for the shaft extension can be provided by means of a metal panel bearing made for the purpose. Never use panel bearings of the non-metal type unless the condenser shaft is grounded. *The metal bearing should be connected to the chassis with a wire or grounding strip.* This prevents any possible danger of shock.

The use of fiber washers between ceramic insulation and metal brackets, screws or nuts will prevent the ceramic parts from breaking.

### Cutting and Bending Sheet Metal

If a sheet of metal is too large to be cut conveniently with a hacksaw, it may be marked with scratches as deep as possible along the line of the cut on both sides of the sheet and then clamped in a vise and worked back and forth until the sheet breaks at the line. Do not carry the bending too far until the break begins to weaken; otherwise the edge of the sheet may become bent. A pair of iron bars or pieces of heavy angle stock, as long or longer than the width of the sheet, to hold it in the vise will make the job easier. "C"-clamps may be used to keep the bars from spreading at the ends. The rough edges may be smoothed up with a file or by placing a large piece of emery cloth or sandpaper on a flat surface and running the edge of the metal back and forth over the sheet.

Bends may be made similarly. The sheet should be scratched on both sides, but not so deeply as to cause it to break.

### Cutting Threads

Brass rod may be threaded, or the damaged threads of a screw repaired, by the use of *dies*. Holes of suitable size (see Table 18-1) may be threaded for screws by means of *taps*. Taps and dies are obtainable in all standard machine-screw sizes. A set usually consists of taps and dies for 4-36, 6-32, 8-32, 10-32 and 14-20 sizes, with a holder suitable for use with either tap or die. Machine oil applied to the tap usually makes cutting easier and sticking less troublesome.

### Wiring

A popular type of wire for receivers and low-power transmitters is that known as "push-back" wire. It comes in sizes No. 16, 18, 20, etc., which are sufficiently large for all power circuits except filament. The insulating covering, which is sufficient for circuits where voltages do not exceed 400 or 500, can be pushed back a few inches at the end, making cutting of the insulation unnecessary when making a connection. Filament wiring should be done with sufficiently large conductors to carry the required current without appreciable voltage drop (see Copper Wire Table, Chapter Twenty-Four). Rubber-covered house-wire sizes No. 14 to No. 10 are suitable for heavy-

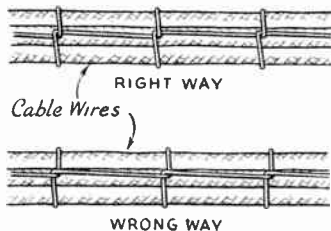


Fig. 18-3 — Right and wrong methods of lacing cable. With the right way the leading line is pinched under each turn and will not loosen if a break occurs in the lacing.

current transmitting tubes, while No. 18 to No. 14 flexible wire is satisfactory for receivers and low-drain transmitting tubes where the total length of the leads is not excessive.

Stiff bare wire, sometimes called **bus wire** or **bus bar**, is most favored for the high r.f.-potential wiring of transmitters and, where practicable, in receivers. It comes in sizes No. 14 and No. 12 and is usually tin-dipped. Soft-drawn antenna wire also may be used. Kinks or bends can be removed by stretching 10 or 15 feet of the wire and then cutting it into small usable lengths.

The insulation covering power wiring which is to carry high transmitter voltages should be appropriate for the voltage involved. Wire with rubber and varnished cambric covering, similar to ignition cable, is available from radio parts dealers.

It is usually advisable to do the power-supply wiring first. The leads should be bunched together as much as possible and kept down close to the surface of the chassis. The lacing of power wiring in cable form not only improves its appearance but also strengthens the wiring. Fig. 18-3 shows the correct way of lacing cabled wires.

Chassis holes for wires should be lined with **rubber grommets** which fit the hole, to prevent chafing of the insulation. In cases where power-supply leads have several branches, it is often convenient to use **fiber terminal strips** as anchorages. These strips also form handy mountings for wire-terminal resistors, etc.

High-voltage wiring should have exposed points kept at a minimum and those which cannot be avoided rendered as inaccessible as possible to accidental contact.

### Soldering

The secret of good soldering is in allowing time for the *joint*, as well as the solder, to attain sufficient temperature. Enough heat should be applied so that the solder will melt when it comes in contact with the wires being joined, without touching the solder to the iron.

Soldering paste, if of the noncorroding type, is extremely helpful when used correctly. In general, it should not be used for radio work except when necessary. The joint should first be warmed slightly and the soldering paste applied with a piece of wire. Only the bit of paste which melts from the warmth of the joint should be used. If the soldering iron is clean it will be possible with one hand to pick up a drop of solder on the tip of the iron which can be applied to the joint, while the other hand is used to hold the connecting wires together. The use of excessive soldering paste causes the paste to spread over the surface of adjacent insulation, causing leakage or breakdown of the insulation. Except where absolutely necessary, solder should never be depended upon for the mechanical strength of the joint; the wire should be wrapped around the terminals or clamped with soldering terminals.

● COMPONENT VALUES

Values of composition resistors and small condensers (mica and ceramic) are specified throughout this *Handbook*, in terms of "preferred values." In the preferred-number system, all values represent (approximately) a constant-percentage increase over the next lower value. The base of the system is the number 10. Only two significant figures are used. Table 18-II shows the preferred values based on tolerance steps of 20, 10 and 5 per cent. All other values are expressed by multiplying or dividing the base figures given in the table by the appropriate power of 10. (For example, resistor values of 33,000 ohms, 6800 ohms, and 150 ohms are obtained by multiplying the base figures by 1000, 100, and 10, respectively.)

"Tolerance" means that a variation of plus or minus the percentage given is considered satisfactory. For example, the actual resistance of a "4700-ohm" 20-per-cent resistor can lie anywhere between 3700 and 5600 ohms, approximately. The permissible variation in the same resistance value with 5-per-cent tolerance would be in the range from 4500 to 4900 ohms, approximately.

Only those values shown in the first column of Table 18-II are available in 20-per-cent tolerance. Additional values, as shown in the second column, are available in 10-per-cent tolerance; still more values can be obtained in 5-per-cent tolerance.

In the component specifications in this *Handbook*, it is to be understood that when no tolerance is specified the *largest* tolerance available in that value will be satisfactory.

TABLE 18-II  
Standard Component Values

20% Tolerance	10% Tolerance	5% Tolerance
10	10	10
		11
	12	12
		13
15	15	15
		16
	18	18
		20
22	22	22
		24
	27	27
		30
33	33	33
		36
	39	39
		43
47	47	47
		51
	56	56
		62
68	68	68
		75
	82	82
		91
100	100	100

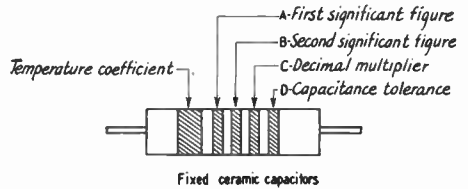
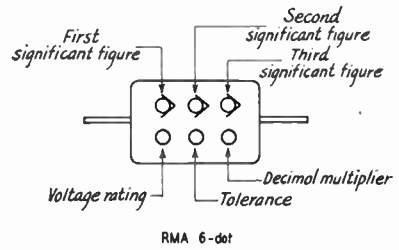
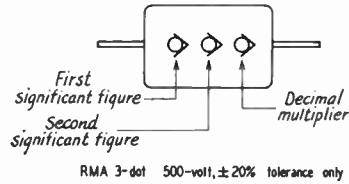
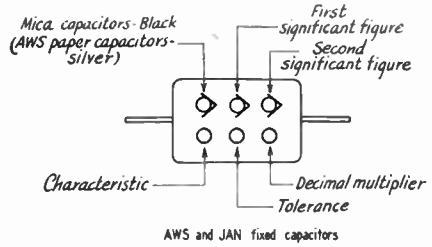


Fig. 18-1—Color coding of fixed mica, molded paper, and tubular ceramic condensers. The color code for mica and molded paper condensers is given in Table 18-III. Table 18-IV gives the color code for tubular ceramic condensers.

Values that do not fit into the preferred-number system (such as 500, 25,000, etc.) easily can be substituted. It is obvious, for example, that a 5000-ohm resistor falls well within the tolerance range of the 4700-ohm 20-per-cent resistor used in the example above. It would not, however, be usable if the tolerance were specified as 5 per cent.

● COLOR CODES

Standardized color codes are used to mark values on small components such as composition resistors and mica condensers, and to identify leads from transformers, etc. The resistor-condenser number color code is given in Table 18-III.

**Fixed Condensers**

The methods of marking "postage-stamp" mica condensers, molded paper condensers, and tubular ceramic condensers are shown in Fig. 18-4. Condensers made to American War Standards or Joint Army-Navy specifications are marked with the 6-dot code shown at the top. Practically all surplus condensers are in this category. The 3-dot RMA code is used for condensers having a rating of 500 volts and  $\pm 20\%$  tolerance only; other ratings and tolerances are covered by the 6-dot RMA code.

Examples: A condenser with a 6-dot code has the following markings: Top row, left to right, black, yellow, violet; bottom row, right to left, brown, silver, red. Since the first color in the top row is black (significant figure zero) this is the AWS code and the condenser has mica dielectric. The significant figures are 4 and 7, the decimal multiplier 10 (brown, at right of second row), so the capacitance is 470  $\mu\text{fd}$ . The tolerance is  $\pm 10\%$ . The final color, the characteristic, deals with temperature coefficients and methods of testing, and may be ignored.

A condenser with a 3-dot code has the following colors, left to right: brown, black, red. The significant figures are 1, 0 (10) and the multiplier is 100. The capacitance is therefore 1000  $\mu\text{fd}$ .

A condenser with a 6-dot code has the following markings: Top row, left to right, brown, black, black; bottom row, right to left, black, gold, blue. Since the first color in the top row is neither black nor silver, this is the RMA code. The significant figures are 1, 0, 0 (100) and the decimal multiplier is 1 (black). The capacitance is therefore 100  $\mu\text{fd}$ . The gold dot shows that the tolerance is  $\pm 5\%$ , and the blue dot indicates 600-volt rating.

**Ceramic Condensers**

Conventional markings for ceramic condensers are shown in the lower drawing of Fig. 18-4. The colors have the meanings indicated in Table 18-IV. In practice, dots may be used instead of the narrow bands indicated in Fig. 18-4.

Example: A ceramic condenser has the following markings: Broad band, violet; narrow bands or dots, green, brown, black, green. The significant figures are 5, 1 (51) and the decimal multiplier is 1, so the capacitance is 51  $\mu\text{fd}$ .

Color	Significant Figure	Decimal Multiplier	Capacitance Tolerance		Temp. Coeff. p.p.m./deg. C.
			More than 10 $\mu\text{fd}$ (in %)	Less than 10 $\mu\text{fd}$ (in $\mu\text{fd}$ )	
Black	0	1	$\pm 20$	2.0	0
Brown	1	10	$\pm 1$		-30
Red	2	100	$\pm 2$		-80
Orange	3	1000			-150
Yellow	4				-220
Green	5		$\pm 5$	0.5	-330
Blue	6				-470
Violet	7				-750
Gray	8	0.01		0.25	30
White	9	0.1	$\pm 10$	1.0	500

Color	Significant Figure	Decimal Multiplier	Tolerance (%)	Voltage Rating*
Black	0	1	—	—
Brown	1	10	1*	100
Red	2	100	2*	200
Orange	3	1000	3*	300
Yellow	4	10,000	4*	400
Green	5	100,000	5*	500
Blue	6	1,000,000	6*	600
Violet	7	10,000,000	7*	700
Gray	8	100,000,000	8*	800
White	9	1,000,000,000	9*	900
Gold	—	0.1	5	1000
Silver	—	0.01	10	2000
No color	—	—	20	500

\* Applies to condensers only.

The temperature coefficient is  $-750$  parts per million per degree C., as given by the broad band, and the capacitance tolerance is  $\pm 5\%$ .

**Fixed Composition Resistors**

Composition resistors (including small wire-wound units molded in cases identical with the composition type) are color-coded as shown in Fig. 18-5. Colored bands are used on resistors having axial leads; on radial-lead resistors the colors are placed as shown in the drawing. When bands are used for color coding the body color has no significance.

Examples: A resistor of the type shown in the lower drawing of Fig. 18-5 has the following color bands: A, red; B, red; C, orange; D, no color. The significant figures are 2, 2 (22) and the decimal multiplier is 1000. The value of resistance is therefore 22,000 ohms and the tolerance is  $\pm 20\%$ .

A resistor of the type shown in the upper drawing has the following colors: body (A), blue; end (B), gray; dot, red; end (D), gold. The significant figures are 6, 8 (68) and the decimal multiplier is 100, so the resistance is 6800 ohms. The tolerance is  $\pm 5\%$ .

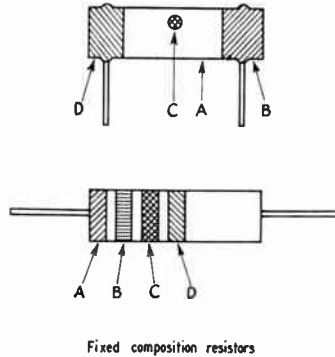


Fig. 18-5 — Color coding of fixed composition resistors. The color code is given in Table 18-III. The colored areas have the following significance:

- A — First significant figure of resistance in ohms.
- B — Second significant figure.
- C — Decimal multiplier.
- D — Resistance tolerance in per cent. If no color is shown, the tolerance is  $\pm 20\%$ .

**I.F. Transformers**

- Blue* — plate lead.
- Red* — “B” + lead.
- Green* — grid (or diode) lead.
- Black* — grid (or diode) return.

NOTE: If the secondary of the i.f.t. is center-tapped, the second diode plate lead is green-and-black striped, and black is used for the center-tap lead.

**A.F. Transformers**

- Blue* — plate (finish) lead of primary.
- Red* — “B” + lead (this applies whether the primary is plain or center-tapped).
- Brown* — plate (start) lead on center-tapped primaries. (Blue may be used for this lead if polarity is not important.)
- Green* — grid (finish) lead to secondary.
- Black* — grid return (this applies whether the secondary is plain or center-tapped).
- Yellow* — grid (start) lead on center-tapped secondaries. (Green may be used for this lead if polarity is not important.)

NOTE: These markings apply also to line-to-grid and tube-to-line transformers.

**Loudspeaker Voice Coils**

- Green* — finish.
- Black* — start.

**Loudspeaker Field Coils**

- Black and Red* — start.
- Yellow and Red* — finish.
- Slate and Red* — tap (if any).

**Power Transformers**

- 1) Primary Leads . . . . . *Black*  
 If tapped:  
     Common . . . . . *Black*  
     Tap . . . . . *Black and Yellow Striped*  
     Finish . . . . . *Black and Red Striped*
- 2) High-Voltage Plate Winding . . . . . *Red*  
     Center-Tap . . . . . *Red and Yellow Striped*
- 3) Rectifier Filament Winding . . . . . *Yellow*  
     Center-Tap . . . . . *Yellow and Blue Striped*
- 4) Filament Winding No. 1 . . . . . *Green*  
     Center-Tap . . . . . *Green and Yellow Striped*
- 5) Filament Winding No. 2 . . . . . *Brown*  
     Center-Tap . . . . . *Brown and Yellow Striped*
- 6) Filament Winding No. 3 . . . . . *Slate*  
     Center-Tap . . . . . *Slate and Yellow Striped*

# Eliminating Broadcast Interference

It is the duty of every amateur to make sure that the operation of his station does not result in annoyance to others in the form of interference with broadcast reception, police and aviation radio, or any other radio service. The nature of this duty is twofold: First, the amateur does not want to jeopardize his own right to be on the air, and second, he does not want to place amateur radio as a whole in an unfavorable light with the public, or with other radio services.

## *FCC Regulations*

The FCC has formulated certain regulations pertaining to interference, as follows:

§12.152. *Restricted operation.* (a) If the operation of an amateur station causes general interference to the reception of transmissions from stations operating in the domestic broadcast service when receivers of good engineering design including adequate selectivity characteristics are used to receive such transmissions and this fact is made known to the amateur station licensee, the amateur station shall not be operated during the hours from 8 o'clock P.M. to 10:30 P.M., local time, and on Sunday for the additional period from 10:30 A.M. until 1 P.M., local time, upon the frequency or frequencies used when the interference is created. (b) In general, such steps as may be necessary to minimize interference to stations operating in other services may be required after investigation by the Commission.

Needless to say, no amateur likes to have his operating hours curtailed by enforced "silent periods," and where interference exists, special efforts are necessary to eliminate the trouble.

Interference with broadcast reception produces more than just a technical problem. There is a definite "public relations" aspect that requires tactful handling on the part of the amateur. Whether the amateur equipment is at fault or not, the broadcast listener is usually unfamiliar with the technical side of radio, and with amateur radio itself, and therefore cannot understand readily that his own receiver may be contributing its share to the trouble. It is only natural that the broadcast listener has a certain amount of pride in his receiver, and often he is not easily convinced without tactful, polite instruction by the amateur. Thus, the amateur who is confronted with BCI usually faces, in addition to the technical problem, a public relations problem that must be solved if he is to live in harmony with his neighbors. Both the public relations problem and the technical problem can be solved if the right approach is used.

## *Public Relations Aspect*

There must be a spirit of coöperation between the amateur and the listener if a satisfactory solution to any BCI problem is to be obtained. The FCC recognizes this fact, and in cases where complaints are received, two letters are written, one to the amateur, the other to the complainant. The amateur is directed to investigate the complaint, and to file a written report of the steps he has taken to eliminate the difficulty. The complainant is informed that the amateur has been requested to investigate, and is asked to coöperate with the amateur in the solution of the problem. The listener is informed that interference is not always the fault of the amateur, but may exist because of deficiencies in his own receiver, and is told what steps he is expected to take in coöperating with the amateur. The FCC offers technical assistance in solving stubborn cases, requesting from the listener a description of the circuits of his receiver. In every instance, both the amateur and the listener are informed that coöperation between them is required. The amateur should never merely assume that the broadcast receiver is at fault, but should first determine that his own station is operating in full compliance with FCC regulations. Once he is certain of this, he should attempt to secure the coöperation of the listener in making whatever adjustments and changes are necessary to eliminate the interference.

## ● SOME "DOS" AND "DON'TS"

Experience has shown that observance of a few simple diplomatic precepts will go a long way toward smoothing the ruffled dispositions that are encountered in BCI difficulties.

### *Prompt Action*

Do something to show the listener that you are concerned for his welfare as soon as a complaint is received. The average person will tolerate a limited amount of interference, but no one can be expected to put up with frequent and extended interruption of his listening pleasures. The sooner you take steps to eliminate the interference, the more agreeable the listener will be; the longer he has to wait for you, the less willing he will be to coöperate.

### Don't Hide Your Identity

If a listener thinks that you are "trying to get away with something" he will not only be unwilling to cooperate, but may be actively hostile. As a general rule, whenever you change location, or mode of transmission, or increase power, or put up a new antenna, check with your neighbors to make sure that they are not



experiencing interference. Announce your presence and conduct occasional tests on the air, requesting anyone whose reception is being spoiled to let you know about it so that you may take steps to eliminate the trouble.

### Check Your Transmitter

Before visiting a complainant check your transmitter thoroughly to make sure that it is free from such things as parasitic oscillations, key clicks, spurious sidebands arising from overmodulation, and other effects that might result in radiation on frequencies not assigned to amateurs. Only when you know your transmitter is "clean" can you approach a complainant with confidence.

Solve the BCI problem in your own home first! It is always convincing if you can say — and demonstrate, if necessary — that you do not interfere with broadcast receivers in your own house.

### Present Your Story Tactfully

Put yourself in the listener's place. He has a right, he believes, to interference-free reception of the broadcast programs he likes. When you interfere, his natural reaction is to assume that you are the one at fault. When you call on him, explain that you do not operate on the frequencies to which he wants to listen, and the real trouble is that you and he happen to be located so close to each other. Explain to him that there are thousands of stations operating simultaneously, all the time, and that the problem of rejecting all but the one he happens to want to hear is one of receiver design. Point out that the average broadcast receiver is made to sell as cheaply as possible, and that features that would prevent interference from near-by stations are left out.

It should be explained to the listener that if it is simply the presence of your strong signal on his receiving antenna that causes the difficulty, the situation can be cleared up by a wavetramp. In other cases the wiring of the receiver itself is picking up your signal, and such cases can be cured only by suppressing this unwanted pick-up in the receiver itself; in other words, some modifications will have to be made in the receiver if he is to expect interference-free reception. Arrange to try a test with a wavetramp, if there is a chance that the type of interference experienced will respond to such treatment.

### Avoid Working on the Receiver

If your tests show that the fault has to be remedied in the receiver itself, *do not offer to work on the receiver*. It is not your fault that the receiver design is defective. Recommend that the work be done by a reliable serviceman, and offer to advise the latter as to the cause and cure if necessary.


It is inadvisable to tackle broadcast receivers, particularly the midget varieties, unless you have had experience working on them. In any event, if you do work on the receiver yourself the chances are that if anything goes wrong later on you'll be blamed for it. Explain that, while you may be technically competent to make the necessary modifications, radio servicing is best left to those who specialize in it, and that you are sure he, the owner, will prefer to have the work done by someone whom he can hold responsible.

If the owner of the receiver obviously prefers to have you make the modifications, do so only with the understanding that it is purely as a favor and because you are anxious to cooperate. Make him understand, with as much tact as possible, that the responsibility for the interference does not lie with you (your transmitter having previously been checked and found O.K.); if the receiver responds to frequencies to which it is not tuned that is a defect in its design. You also have no obligation to pay for having the receiver modified. If you do the work yourself you should not make any charge, of course. In that event, insist that you must take the receiver to your own shop in order to work on it properly; you will be able to tell immediately whether the changes you make effect an improvement and therefore can work more rapidly and conveniently — and without turning the owner's living room into a repair shop. If it is necessary to do some work in the listener's home, *be neat* in the work you do. Remember, the listener's living room cannot be treated in the same manner you would treat your own ham shack!
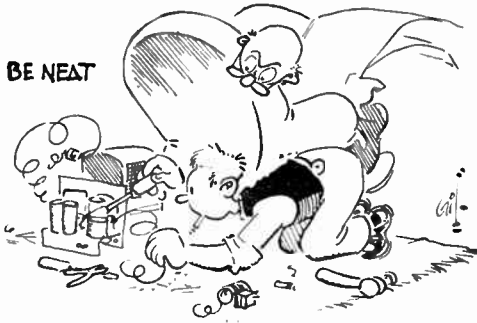
### ● RADIO CLUB BCI COMMITTEES

Organized amateur radio clubs can do a lot to pave the way toward cooperation between individual amateurs and the broadcast listen-





ers. Most clubs maintain an interference committee, charged with handling both the public relations and the technical aspects of BCI. Through such committees, mutual technical assistance is made available to all members of

the club, so that those less qualified can have the benefit of the experience of others. The committee should also maintain contact with the local radio servicemen, supplying them with information and technical assistance whenever possible. Where needed, the committee can maintain valuable contacts with the local newspapers and other authorities to provide the right kind of publicity for the efforts of individuals or groups who are trying to clear up BCI problems.

The Communications Department of the ARRL, as one of its services to affiliated clubs, has prepared material suggesting various ways in which local clubs can form interference committees, and methods by which such groups can function efficiently for the good of all concerned. This material is available to affiliated clubs on request, addressed to ARRL headquarters.

## Technical Aspects of BCI

There are no hard-and-fast rules that can be applied as certain cures for all cases of BCI. The great number of different types of broadcast receivers that have been produced make it necessary for the amateur to apply one remedy for one set, and another for a different set. There are, however, a few generalizations that will be of assistance in most cases. A knowledge of some of the types of interference, and the general methods required to eliminate them, will enable the amateur to avoid much tedious cut-and-try procedure, and will lead to a rapid appraisal of the situation when interference arises.

### Improper Transmitter Operation

An amateur transmitter can create BCI if it is not operating properly. In c.w. transmitters, key clicks and spurious emissions are the usual sources of trouble. In 'phone transmitters overmodulation, parasitic oscillations that occur only under modulation, and low-frequency parasitic oscillations are often the source of trouble. In some instances, an unbalanced antenna system can cause BCI. In any event, the amateur must be certain that none of these faults exists within his own station before he can assume that the "blame" for the interference can be placed on the broadcast set. The methods of determining when improper operating conditions exist are discussed in detail in Chapters Six and Nine.

### Types of Interference

BCI can usually be classified as one of two types. It is either tunable, appearing only at certain spots on the receiver dial, or it is untunable, appearing throughout the entire tuning range. The tunable type is usually encountered only when the transmitter frequency is low enough to permit the amateur signal to

beat against one of the harmonics of the oscillator in the broadcast set. In most cases, this type is encountered only by stations operating in the 3.5- to 4-Mc. band. The untunable type may be encountered by almost any transmitter, regardless of frequency, but is generally restricted to receivers within the immediate area of the transmitter and its antenna. Within these classifications, several variations may be encountered, the general nature of which is described below.

### Blanketing

The interference takes the form of an untunable signal that partially or completely masks all other signals on the broadcast receiver. In the case of a c.w. transmitter, each time the key is pressed, all broadcast signals disappear or are reduced greatly in amplitude. If the transmitter is amplitude-modulated, each time the carrier is turned on, the same "washout" occurs, and the voice modulation is usually severely distorted.

Blanketing is usually encountered only when the transmitting antenna and the receiver are close together. Several things may be done to reduce this form of interference: (1) The receiving antenna may be relocated so that it picks up less energy from the transmitter. If possible, orientate the two wires at right angles to each other. (2) The receiving antenna may be shortened. If it is of such length that it approaches resonance at the transmitter frequency, it will act as a tuned circuit, applying a signal of relatively great amplitude to the receiver. (3) If the receiver is located in a metropolitan area served by several powerful stations, satisfactory reception may be obtained with an indoor antenna a few feet long. (4) Wavetraps tuned to the operating frequency of the transmitter may be installed between the receiver and its antenna.

### *Superheterodyne Interference*

This type of BCI is tunable, appearing only at certain points on the receiver dial. If one of these points happens to fall within audio range of a desired broadcast station, a "birdie" will result. The interference may be noticed at several points on the dial, but these points will usually bear a definite relationship to one another, as they are all the result of the amateur signal beating with a harmonic of the oscillator in the broadcast set to produce a difference-frequency signal that is within the passband of the i.f. stages of the receiver. In rare instances, an amateur signal will beat with the signal from another near-by transmitter, either amateur or commercial, to produce what is called a "phantom" signal. Naturally, the phantom will appear only when both stations are transmitting at the same time. Interference of the superheterodyne type can sometimes be eliminated by wavetraps tuned to the frequency of the interfering signal. In stubborn cases, however, it may be necessary to improve the shielding of the oscillator stage in the receiver, or to change the operating frequency of the transmitter to shift the difference-frequency product away from the points where it interferes with local broadcast stations.

### *Cross-Talk*

In this type of interference, the amateur signal is heard superimposed on each broadcast signal, with no interference noticeable between stations. This type is experienced mainly in older receivers having poorly-shielded input stages. It is seldom experienced in receivers using a variable- $\mu$  tube in the input stage. If it is not possible to install such a tube in the set, shielding the input stage and the wiring associated with it will usually reduce the interference. A wavetraps, tuned to the frequency of the amateur signal, will also be useful in eliminating this type of BCI.

### *Stray Receiver Rectification*

This type is perhaps the most frequently encountered in present-day receivers. It is untunable, with the amateur signal being heard at all settings of the receiver dial. It is caused by rectification of the amateur signal at some point within the receiver, and is found usually in sets located close to a transmitter. The rectification can take place in the second detector, or in the audio system. Its elimination can be accomplished only after determining just where the signal is entering the set, and then finding out which tube, or tubes, are doing the rectification. This can be determined by removing one tube at a time until one is found that eliminates the interference. Details concerning this method are discussed under the heading "Tracking Down Interference" in a later portion of this chapter. Once the offending tube has been located, the r.f. energy may be eliminated by any one of the methods shown under the same heading.

### *Power-Line Pick-Up*

In some cases BCI is caused by r.f. energy entering the broadcast set through the a.c. power lines. In most instances, the r.f. gets into the lines because the transmitting antenna runs close to the a.c. lines, but in some cases, the r.f. may be forced back into the line through the power supply of the transmitter. This is usually caused by unbalance in the transmitting antenna system, and is especially prevalent with Marconi and end-fed Hertz systems. It may also be caused by poorly choked and by-passed supply leads in the r.f. sections of the transmitter. The method of entry into the lines may be determined by operating the transmitter into a dummy load. If the interference disappears when this is done, but is present when the transmitter is operated with its antenna, it is certain that the antenna system is the cause of the trouble, either in being unbalanced, or because it runs close to a.c. lines. Elimination of BCI of this type can be accomplished by redesign or relocation of the antenna system, or by the use of line filters at the receiver power source. Line filters are discussed under a separate heading below.

### *V.H.F. Interference*

Most BCI caused by stations operating at frequencies higher than 28 Mc. is of the type discussed under "Stray Receiver Rectification" above, and is attributable to the fact that the higher-frequency signals are more apt to be picked up by the receiver circuits themselves than are signals from lower-frequency transmitters. Similar methods may be used to eliminate such interference, but in some cases, an a.c. line filter designed for the operating frequency and installed at the power input plug of the receiver is the only cure.

### *Interference with Television Reception*

Severe distortion of the televised image, or even complete blanking of the 'scope screen, can result when a transmitter is operated in the immediate vicinity of a television receiver. Not a great deal of information is available at the present time, but the experience of several amateurs indicates that by far the greatest number of TVI cases is the result of harmonic radiation from the amateur transmitter. A chart showing the harmonic relation of several of the amateur bands to the currently-used television channels is shown in Fig. 19-1. The reduction of harmonic radiation is discussed in Chapter Ten. It is also possible that TVI can be caused by appearance of an amateur signal in the video stages of the television receiver. These stages are comparable to the audio stages of a broadcast set, but with extremely-broad frequency characteristics, because the video stage must be capable of amplifying frequencies all the way through the audio range and up to 3.5 or 4 Mc. Thus, a

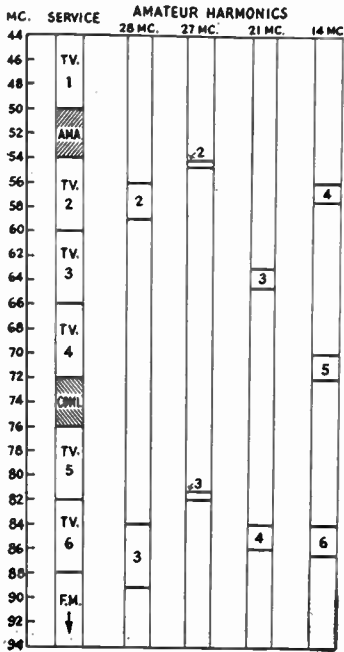


Fig. 19-1 — The relationship of amateur-band harmonics, 14 to 28 Mc., and frequency assignments in the 44-88 megacycle region.

signal from a transmitter operating in the 3.5-Mc. band could easily be amplified if it were to get into the video channel. In such cases, it is probable that the interfering signal is entering through the power lines, or by direct pick-up to the wiring of the video stages. Fortunately, good shielding is required in the video stages of television receivers, so interference of this sort is not apt to be severe, and should be reduced by a.c. line chokes in most cases. No general solution to the TVI problem is known at this writing, but reduction of harmonic radiation seems to be productive of best results. Additional information concerning TVI will be published in *QST* as progress is made.

## TRACKING DOWN AND ELIMINATING INTERFERENCE

A certain amount of cut-and-try is necessary in the tracking down and elimination of BCI, but there are several short-cut procedures that can be used to keep the time required to a minimum. The assistance of another licensed amateur who can operate your transmitter while you conduct tests at the location of the broadcast receiver will save much time and eliminate the misinterpretation that almost always follows when the results of tests are reported to the amateur by someone who is unfamiliar with the "symptoms" and the effects being looked for. The procedure outlined below will save valuable time in getting at the source of the trouble and in satisfactorily eliminating it.

1) Determine whether the interference is tunable or untunable. This will usually indi-

cate the methods required for elimination of the trouble, as it will show which of the general types of interference discussed above is present. In severe cases it is possible that two or more types will be present at the same time, and steps will be necessary to eliminate each type.

2) Disconnect the antenna from the set, turn the volume control up full, and see if the interference disappears. If it does, it is merely necessary to prevent the r.f. appearing on the antenna from entering the set. Wavetraps and low-pass filters should be tried, and if they produce marked reduction in the amplitude of the interfering signal, but some is still present, try relocating the receiving antenna. It should be placed as far as possible from the transmitting antenna, and should run at right angles to it to minimize coupling. If the interference persists even after the antenna is disconnected, the search is narrowed to an investigation of whether the signal is coming in on the power lines, or is being picked up directly on the receiver wiring.

3) Check for power-line interference by using a sensitive wavemeter such as that described in Chapter Sixteen of this *Handbook* to probe along the a.c. cord that connects the set to the power source. Checks should be made at the transmitter frequency, and also at harmonic frequencies. If r.f. is detected in the line, by-pass both sides of the a.c. line to ground with 0.005- $\mu$ f. mica condensers at the point where the line cord enters the set. If this does not completely eliminate the interference, try a line filter designed for the operating frequency.

4) If it is evident that the interference is being picked up on the receiver wiring, explain the situation to the owner and tell him that the exact cause cannot be determined without removing the chassis from the cabinet, and that, in any event, the receiver will have to be modified somewhat if the interference is to be eliminated. As suggested before, recommend that the actual work be done by a radio serviceman. Offer to check into the cause yourself, if he wishes and will allow you to take the set to your shop (with the understanding that you will not make any changes in the receiver

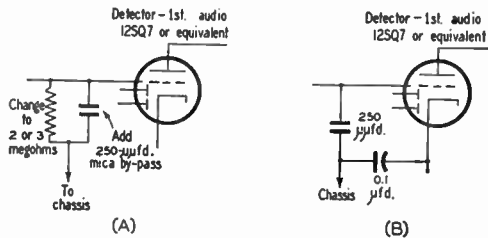


Fig. 19-2 — Two methods of eliminating r.f. from the grid of a combined detector/first-audio stage. At A, the value of the grid leak is reduced to 2 or 3 megohms, and a mica by-pass condenser is added. At B, both grid and cathode are by-passed.

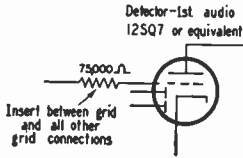


Fig. 19-3 — Using a 75,000-ohm resistor to form a low-pass filter with the tube capacitance. The resistor must be mounted at the tube pin, between the grid and all other grid connections.

without his express permission) so the serviceman can be told what needs to be done.

5) In the event that the owner allows you to take the receiver, set it up near your transmitter and check to see if the amplitude of the interfering signal is changed by various settings of the receiver volume control. If the volume of the interference changes with changes in the volume control, the r.f. is entering the set ahead of the volume control. If it is unaffected by the volume control, it is getting into the audio stages at a point following the volume control.

6) Pin the source down, if it is ahead of the volume control, by removing one tube at a time until one is found that kills the interference when it is removed. In sets using series-connected filaments, this will be possible only if a tube of equal heater rating, and with all but the heater pins clipped off, is substituted for the tube.

7) Determine which element (or elements) of the tube is picking up the interference by touching each tube pin with a test lead about three feet long. The lead, acting as an antenna, will cause the interference to increase when it is placed on a tube pin that is contributing to the interference. Once the sensitive points have been determined, the trouble can be eliminated by shielding the leads connected to the tube element that is affected, and by shielding the tube itself. Grid leads are the principal offenders, especially the long leads that run from a tube cap to a tuning condenser, and it may be necessary to shield thoroughly several parts of the set before the interference is eliminated completely.

8) If the pick-up is found to be in the audio system — as is the case in many sets, especially when the transmitter is operating at 28 Mc. or higher — it can be eliminated by one or another of the methods shown in Fig. 19-2A and

B. Fig. 19-2A is a method that has proved successful with many a.c.-d.c. midget receivers. Both sides of the a.c. line are by-passed to ground with 0.001- $\mu$ f. mica condensers, and the value of the grid leak in the combined detector/first-audio tube (usually a 12SQ7 or its equivalent) is reduced to 2 or 3 megohms. The grid is then by-passed for r.f. with a 250- $\mu$ f. mica condenser. Fig. 19-2B is a similar method. A third method that has worked in a.c.-d.c. receivers requires only that the heater of the detector/first-audio stage be by-passed to ground with a 0.001- $\mu$ f. condenser. The method shown in Fig. 19-3 uses a 75,000-ohm  $\frac{1}{2}$ -watt resistor to form, with the tube capacitance, a low-pass filter. The resistor is connected between the grid pin of the audio stage and all other wires connected to the grid.

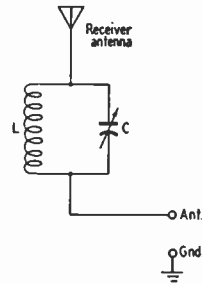


Fig. 19-5 — A simple wavetrapping circuit. *L* and *C* must resonate at the frequency of the interfering signal. Suitable constants are tabulated below.

Band	<i>C</i>		<i>L</i>	
80	140 $\mu$ f. d.	16 $\mu$ h., 32 turns	#22, 1" diam., 1" long	
40	100 $\mu$ f. d.	6 19	#22, 1" 1"	
20	50 $\mu$ f. d.	3.5 14	#18, 1" 1"	
10	25 $\mu$ f. d.	1.5 9½	#18, 1" 1"	

**Interference with T.R.F. Receivers**

Although few t.r.f. receivers are still in use, an occasional set will be found. Interference in these sets is almost always caused by inadequate shielding of the detector stage. Enclosing the tube in a shield, and shielding the wiring to the stage, should eliminate the trouble.

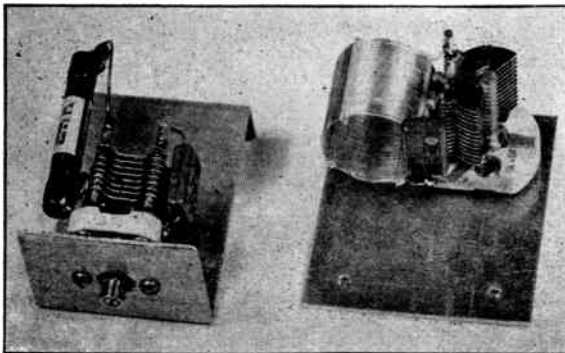
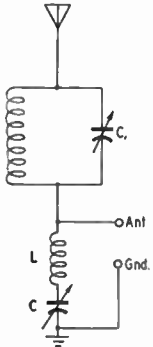


Fig. 19-4 — Two examples of simple wavetraps. In the unit on the left, a 2-meter r.f. choke (Ohmite Z-0) is used with a 50- $\mu$ f. variable condenser shunted by a 22- $\mu$ f. mica condenser to form a trap for the 14-Mc. band. The larger unit on the right uses a 32-turn "Miniductor" (B & W) with a 100- $\mu$ f. variable condenser shunted by a 67- $\mu$ f. mica condenser to cover the 3.5- to 4-Mc. range. Both units are bracket-mounted with provision for mounting within the cabinet of a broadcast receiver. The circuit is shown in Fig. 19-5.

## ● WAVETRAPS

In its simplest form, a wavetraps consists of a parallel-tuned circuit that is connected in series with the broadcast antenna and the antenna post of the receiver. It should be designed to resonate at the frequency of the interfering signal.

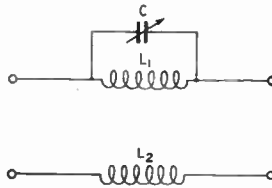


**Fig. 19-6** — Combination of parallel-tuned and series-tuned wavetraps to obtain greater attenuation of the interfering signal. Values for LC are the same as those listed below Fig. 19-5.

interfering signal. The circuit of a simple trap is shown in Fig. 19-5. If multiband operation is necessary, several traps may be connected in series, each tuned to the center of one of the bands in which operation is contemplated. A more elaborate form is illustrated in Fig. 19-6, in which a combination of a parallel-tuned circuit and a series-tuned circuit is used. To adjust the wavetraps, have another licensed amateur operate the transmitter while you tune the trap for maximum attenuation of the interference. The trap should be connected to the broadcast receiver and the normal receiving antenna should be connected in series with the trap, as shown in Figs. 19-5 or 19-6.

## ● A.C. LINE FILTERS

An a.c. line filter usually consists of two r.f. chokes each having an inductance of 10 mh. or so, connected as shown in Fig. 19-7 and by-passed for r.f. The entire trap should be enclosed in a shield can, and the components used should be large enough to carry the full current drawn by the power supply. For traps to be installed in the power lead to a small receiver, No. 16 wire will be adequate but for traps designed to be used ahead of a transmitter power supply, larger wire must be used, in keeping with the current requirements of the supply.



**Fig. 19-7** — An a.c. line filter. A single condenser tunes both  $L_1$  and  $L_2$ , which are unity-coupled, one wound on top of the other. Constants for amateur bands are tabulated below.

Band	C	$L_1 \cdot L_2$
80	140 + 150 (fixed)	25 t. No. 18 insulated, $1\frac{1}{4}$ " dia. $\times$ $2\frac{3}{8}$ " lg.
40	140 $\mu$ fd.	18 t. No. 18 insulated, $1\frac{1}{4}$ " dia. $\times$ $2\frac{3}{8}$ " lg.
20	100 $\mu$ fd.	12 t. No. 18, $1\frac{1}{4}$ " dia. $\times$ $2\frac{3}{8}$ " lg.
10	25 $\mu$ fd.	9 t. No. 18, $1\frac{1}{2}$ " dia. $\times$ $2\frac{3}{8}$ " lg.

Insulated, stranded wire should be used for all coils.

# Operating a Station

The enjoyment of our hobby usually comes from the operation of our station once we have finished its construction. Upon the *station* and its *operation* depend the communication records that are made. We have taken every bit of care that was possible in constructing our transmitter, receiver, frequency-measuring and monitoring equipment, and in erecting a suitable antenna system. Unless we use good judgment and care in operating our stations, we shall fall far short of realizing the utmost in results achieved. More than this, unless we do the right thing, we may interfere with other stations or delay their work, thus acquiring a bad reputation. Occasionally you will pick up an amateur whose method of operating is so clean-cut, so devoid of useless effort, so snappy and systematic, that your respect is gained and it is a pleasure to listen and work with him. One benefits proportionately from what one puts into amateur radio, so make the most of your hobby in the time and opportunities given you.

For best results, the transmitter should be adjusted for stable, satisfactory operation on several amateur frequencies. Known settings for definite frequencies will enable the operator to change frequency quickly at any time. Whenever such a change is made, be sure to check the transmitter frequency accurately. There is absolutely *no excuse* for a station operating off frequency. Any frequency calibrations should be checked often to guard against variations.

The operator and his methods have much to do with limiting the range of the station. The operator must have a good "fist," or good voice procedure. He must have patience and judgment. Some of these qualities in operating will make more station records than many kilowatts of power. Engineering or applied common sense is as essential to the radio operator as to the experimenter. Do not make several changes in the transmitter or receiver hoping for better results. Make one change at a time until the basic trouble or the best adjustment is found.

An operator with a slow, steady, clean-cut method of sending has a big advantage over the poor operator. Good sending is partly a matter of practice but patience and judgment are just as important qualities of an operator as a good "fist." The technique of speaking in connected thoughts and phrases is equally important for the operator who uses voice.

## ● TOLERANCE AND COURTESY

None of us particularly enjoys working through interfering signals. As amateurs we have always had the "interference problem." It's nothing new. We accept it as a part of operation. We have eased the situation to a considerable extent by using VFOs and crystal filters in our receivers. That's part of the solution.

In amateur radio, each amateur may operate on any frequency he chooses in any amateur band, provided he abides by the existing regulations. No amateur or group of amateurs has any *exclusive* claim to any frequency in any band. We must work together, each respecting the rights of the other. QRM is often unavoidable. We occasionally find ourselves on the frequency used by another station. "Who was there first?" or "Whose communication is most important?" doesn't enter the picture. In bona fide emergency communications the station not engaged in emergency work must of course move from the frequency, or QRT. That is in the tradition of amateur radio. FCC in its declarations of emergency requires stations not engaged in bona fide handling of emergency communications to remain silent or go to other than useful emergency frequencies.

Our normal operating interests in amateur radio vary considerably. Some prefer to rag-chew, others handle traffic, others work DX, others concentrate on working certain areas or states, still others get on for an occasional contact to check a new rig or new antenna. "Why do they have to run a traffic net on my frequency?"; "What's the idea of chewing the rag on a traffic-net frequency?"; "Why do these eggs have to use *my* frequency for their contest QSOs?"; etc. We have heard such expressions, and more! Each amateur should be tolerant of the other fellow's interests. He should exercise operating courtesy and common sense.

*Before putting the transmitter on the air, listen on your own frequency.* If you hear a trunk line or traffic net in operation on the frequency you intend to use, or if you hear any stations rag-chewing or conducting any form of communication on that frequency, stand by until you are sure no QRM will be caused by your operations, or shift to another frequency. Remember, those other chaps can cause you as much QRM as you cause them, sometimes more! The majority of amateurs own more than one crystal, many have VFO. It is not always necessary to stick to a single operating frequency.

Spent some time listening on all the frequencies you use for transmitting. You soon will learn what uses other amateurs are making of those spots. If you find, for example, that a net meets on one of the frequencies you use, or someone uses it for a regular schedule, you will soon learn the time that the net or schedule operates, and will be able to cooperate to avoid a conflict. It has become quite general operating procedure these days to work stations on or near your own frequency. This practice will automatically assist in reducing interference.

If we will each do our part to operate with tolerance and consideration, avoiding an attitude of running roughshod over other operators, we will do much to make ham operating more productive and enjoyable for ourselves as well as the other fellow!

## ● C.W. PROCEDURE

Official ARRL stations, both those using voice and c.w., observe the rules regarded as "standard practice" carefully. Any actively-operating c.w. stations will do well to copy these rules, and follow them when operating.

### Calling Stations

1) *Calls:* The calling station shall make the call by transmitting not more than three times the call signal of the station called and the word DE, followed by its own call signal sent not more than three times thus: W6EY W6EY W6EY DE W1AW W1AW W1AW. In amateur practice this procedure may be expanded somewhat. The call signal of the calling station must be inserted at frequent intervals for identification. Repeating the call of the called station five times and signing not more than twice (repeating not more than five times) has proved excellent practice.

*CQ:* The general-inquiry call (CQ) should be sent not more than five times without interspersing one's station identification. The length of repeated calls is carefully limited in intelligent amateur operating. CQ is not to be used when testing or when the sender is not expecting or looking for an answer.

The special abbreviations indicating from what part of the band tuning will start after a CQ are helpful in making your procedure known to the receiving operator.

HM — Will start to listen at *high*-frequency end of band and tune toward *middle* of band.

MH — Will start to listen in the *middle* of the band and tune toward the *high*-frequency end.

LM — Will start to listen at *low*-frequency end of band and tune toward *middle* of band.

ML — Will start to listen in the *middle* of the band and tune toward the *low*-frequency end.

Example: If the procedure will be to tune from the middle of the band to the high end, a CQ call goes: CQ DE W6RBQ MH K.

The directional CQ: To reduce the number of useless answers and lessen QRM, every CQ call should be made informative when possible. Stations desiring communication should fol-

low each CQ by an indication of direction, district, state, or the like.

Examples: A United States station looking for any Hawaiian amateur calls: CQ K6 CQ K6 CQ K6 DE W4IA W4IA W4IA K. A Western station with traffic for the East Coast when looking for an intermediate relay station calls: CQ EAST CQ EAST CQ EAST DE W5IGW W5IGW W5IGW K. A station with messages for points in Massachusetts calls: CQ MASS CQ MASS CQ MASS DE W7CZY W7CZY W7CZY K. In each example indicated it is understood that the combination used is repeated three times.

Hams who do not raise stations readily may find that their sending is poor, their calls ill-timed or judgment in error. When conditions are right to bring in signals from the desired locality, the way to raise stations is to use the appropriate frequency and to call these stations. Reasonably short calls, with appropriate and brief breaks to listen, will raise stations with minimum time and trouble.

2) *Answering a Call:* Call three times (or less); send DE; sign three times (or less); after contact is established decrease the use of the call signals of both stations to *once or twice*. When a station receives a call without being certain that the call is intended for it, QRZ? may be used. It means "By whom am I being called?" QRZ should not be used to replace CQ.

3) *Ending Signals and Sign-Off:* The proper use of AR, K, KN, SK and CL ending signals is as follows:

$\overline{AR}$  — End of transmission. Recommended after call to a specific station before contact has been established.

Example: W6ABC W6ABC W6ABC DE W9LMN W9LMN W9LMN  $\overline{AR}$ . Also at the end of transmission of a radiogram, immediately following the signature, preceding identification.

K — Go ahead (any station). Recommended after CQ and at the end of each transmission during QSO when there is no objection to others breaking in.

Example: CQ CQ CQ DE W1ABC W1ABC W1ABC K or W9XYZ DE W1ABC K.

$\overline{KN}$  — Go ahead (specific station), all others keep out. Recommended at the end of each transmission during a QSO, or after a call, when calls from other stations are not desired and will not be answered.

Example: W4FGH DE XU6GRL  $\overline{KN}$ .

$\overline{SK}$  — End of QSO. Recommended before signing *last* transmission at end of a QSO.

Example: . . .  $\overline{SK}$  W8LMN DE W5BCD.

CL — I am closing station. Recommended when a station is going off the air, to indicate that it will not listen for any further calls.

Example: . . .  $\overline{SK}$  W7HIJ DE W2JKL CL.

4) *Test Signals* used to adjust a transmitter or at the request of another station to permit the latter to adjust receiving equipment usually consist of a series of Vs with the call signal of the transmitting station at frequent intervals.

5) *Receipting* for conversation or traffic: Never send acknowledgment until the transmission has been entirely received. "R" means

"All right, OK, I understand *completely*." Use R *only* when *all* is received correctly.

6) *Repeats*: When most of transmission is lost, a call should be followed by correct abbreviations to ask for repeats. When but a few words are lost the last word received correctly is given after ?AA, meaning that "all after" this should be repeated. ?AB for "all before" a stated word should be used if most of the first part of the copy is missing. ?BN. . . . . and . . . . . (two stated words) asks for a fill "between" certain sections. If only a word or two is lost this is the quickest method of getting it repeated.

Do not send words twice (QSZ) unless it is requested. Send single. Do not fall into the bad habit of sending double *without a request* from fellows you work. Message-handling practices and procedure are discussed in another chapter.

#### General Practices

When a station has receiving trouble, the operator asks the transmitting station to "QSV." The letter "R" is often used in place of a decimal point (e.g., "3R5 Mc.") or the colon in time designation (e.g., "2R30 p.m."). A long dash for "zero" is in common use. Figures are spelled out in texts, for highest accuracy. NFT for "no filing time" is common.

The law concerning superfluous signals should be noted carefully by every amateur. Do not hold the key down for long periods when testing. If you must test, disconnect the antenna system and use an equivalent "dummy" antenna. Send your call frequently when operating. Pick a time for adjusting the station apparatus when few stations will be bothered.

Long calls after communication has been established are unnecessary and inexcusable. The up-to-date amateur station uses "break-in." The best sending speed is a medium speed with the letters quickly formed and sent evenly with proper spacing. The standard-type telegraph key is best for all-round use. Before any freak keys are used, a few months should be spent listening-in and practising. Regular daily practice periods, two or three half-hour periods a day, are best to acquire real familiarity and proficiency with code.

No excuse can be made for a "garbled" text. Operators should copy what is sent and refuse to acknowledge messages until every word has been received correctly. *Good operators never guess*. "Swing" in a fist is *not* the mark of a good operator, is undesirable. Unusual words are sent twice, the word repeated following transmission of "?" If not *sure*, good operators systematically ask for fills or repeats.

Don't say, "QRM" or "QRN" when you mean "QRS."

Don't acknowledge any message until you have received it completely.

Don't CQ unless there is definite reason for so doing. When sending CQ, use judgment. Sign your call frequently, interspersed with calls, and at the end of all transmissions.

#### Speed-Key Adjustment

Manual skill can be acquired only by practice, but no amount of practice will produce accurate sending if the key itself is improperly adjusted. The adjustment of a straight key is discussed in Chapter One and the requirement for proper adjustment is likewise important in using a "bug" or speed-key. Contact points should be carefully cleaned using a burnishing tool or crocus cloth from time to time. If pitted, an initial dressing-off with an oilstone may be necessary.

Make sure that the movable and fixed dot contact points are parallel and have good contact over their entire surface. The pivot bearings should be adjusted so that no play can be felt when finger pressure is applied vertically to the shaft at its outer end.

For the preliminary adjustments, the weights should be at least halfway down the shaft. For a given speed, the exact position will vary considerably with the stiffness of the flat spring.

Back off the horizontal adjusting screw until the end of the shaft is resting against the damper weight. Apply pressure to the thumb paddle moving the shaft slowly toward the dot side, without allowing it to vibrate. If the adjustment is correct, the entire shaft will remain straight as it leaves the stop screw and the damper weight. The stop screw should be backed out as far as possible to allow good damping action by the damper weight without bending the flat spring when the thumb paddle is pressed slowly to the dot side.

Again press the shaft to the dot side without allowing it to vibrate. Vary the left-side stop screw until there is about  $\frac{1}{8}$  inch between the side of the shaft and the damper weight. This determines the total swing of the shaft. The exact amount is a matter of personal preference, but the  $\frac{1}{8}$ -inch separation will be satisfactory to most operators. The swing should not be much greater or less than this figure.

The dash adjustment is made by varying the contact screw until the operating paddle moves the same distance to the *left* of center to make a dash as it moves to the *right* to make dots. If the paddle travel is excessive on the dash side, choppy sending is almost sure to result with spaces too wide between successive dashes. If the travel is too small, the dashes may be insufficiently spaced.

The coil springs should have about the same tension. The spring should return the shaft quickly and positively from the dot side to the rest position against the damper. The dash spring is then adjusted to a corresponding tension. Operators of fixed stations will generally prefer a comparatively light adjustment to minimize arm fatigue. Flight and marine operators like a rather stiff adjustment to compensate for ship motion.

The length of a dot should be equal to the space between dots. If the paddle is held to the dot side, a series of at least 15 to 20 dots will be



made with most "bugs" before there is any noticeable reduction in spacing between dots. If the dot adjustment is screwed in too far, a short series of heavy dots with very little separation will result. If the adjustment is screwed out too far, very light dots with excessive spacing will result. This adjustment is critical.

Many "bugs" are set to make excessively-fast dots. It will be found that most keys having a normal stiffness in the flat spring can be operated at a speed of about 30 w.p.m. with both weights toward the outer end of the shaft. Most operators cannot properly control a "bug" if the dot speed exceeds 11 per second. The rate at which your "bug" is adjusted can be determined by making a string of dots on recorder tape for 3 to 5 seconds, timing with a stop watch, and counting the dots.

The milliammeter method of adjustment involves connecting a battery (or any suitable source of d.e.), rheostat and milliammeter in series with the bug contacts. A typical set-up might use a 22½-volt battery, a 1000-ohm rheostat and a 0-100 milliammeter. With the key contacts closed, adjust the rheostat at the start with all the resistance in the circuit (to avoid burning out the meter!) until the meter reads 100 ma. A string of dots is then produced with the "bug" and the average-current reading on the meter is noted. If the dots are too light, the reading will be less than 50 ma.; if too heavy, more than 50 ma.

There is no point in making dots faster than the operator is able to make dashes to correspond. The purpose of any telegraphic communication is to convey intelligence. Mistakes in sending have no meaning and confuse the receiving operator. The time taken to repeat an incorrectly-transmitted word will result in a net loss in speed of about two words per minute on the average. Set your "bug" for a speed at which you can handle it easily and without an appreciable number of errors.

Beginners with a "bug," and some old hands too, will do well to imitate the 15 w.p.m. transmissions of W1AW or some press station using punched tape at moderate speed. Confine your practice to an audio oscillator until you are able to send correctly for at least two or three minutes at a rate of 20 w.p.m. During the initial practice stages, the dots should be slowed down to not more than 6 per second. Every effort should be made at the start to achieve good control rather than speed.

### ● USING A BREAK-IN SYSTEM

If you aim to have the best, and every ham does, you will have break-in, whether of the push-to-talk or open-the-key variety. If you haven't the ideal installation yet, by all means take every advantage of the other fellow's facilities when break-in is offered! Break-in avoids unnecessarily long calls, prevents QRM, gives you more communication per hour of operating. Brief calls with frequent short

pauses for reply can approach (but not equal) break-in efficiency.

A separate receiving antenna makes it possible to listen to most stations while the transmitting tubes are lighted. It is only necessary with break-in to pause just a moment occasionally when the key is up (or to cut the carrier momentarily and pause in a 'phone conversation) to listen for the other station. The click when the carrier is cut off is as effective as the word "break."

C.w. telegraph break-in is usually simple to arrange. With break-in, ideas and messages to be transmitted can be pulled right through the holes in the QRM. Snappy, effective, efficient, enjoyable amateur work really requires but a simple switching arrangement in your station to cut off the power and switch 'phones from monitor to receiver. If trouble occurs the sending station can "stand by" (QRX), or it can take traffic until the reception conditions at the distant point are again good.

In calling, the transmitting operator sends the letters "BK" at frequent intervals during his call so that stations hearing the call may know that break-in is in use and take advantage of the fact. *He pauses at intervals* during his call, to listen for a moment for a reply from the station being called. If the station being called does not answer, the call can be continued. If the station called answers someone else, he will be heard and the calling can be broken off. With *full* break-in, the transmitter may be remotely-controlled so no receiver switching is necessary. A tap of the key, and the man on the receiving end can interrupt (if a word is missed) since the receiver is monitoring, awaiting just such directions constantly. But it is not necessary that *you* have such complete perfect facilities to take advantage of break-in when the stations you work are break-in-equipped. It is not intelligent handling of a station or coöperation with an operator advertising that he has "break-in" with his calls, to sit idly by minute after minute of a properly-sent call. After the first invitation to break is given and at each subsequent pause, turn on your transmitter and tap your key — and you will find that conversation or business can start immediately.

### ● VOICE OPERATING

Voice work has become increasingly popular over the years. With the availability of new NFM equipment it will make additional progress. The use of proper procedure to get best results is just as important as in using code. In telegraphy words must be spelled out letter by letter. It is therefore but natural that abbreviations and short-cuts should have come into widespread use; they make it possible to convey intelligence faster. In voice work, however, abbreviations are not necessary, and should have no part in our operating procedure when using voice.

The letter "K" has been agreed to in tele-

graphic practice so that the operator will not have to pound out the separate letters that spell the words "go ahead." The voice operator can more readily and understandably say the words "go ahead" or "over," or "come in please."

One laughs on c.w. by spelling out the letters HI. Strangely enough, there are some voice operators who have never thought much about procedure who say HI or "Aitch eye" instead of actually laughing. Use a laugh when one is called for. Be natural as you would with your family and friends.

The matter of reporting *readability* and *strength* is as important to 'phone operators as to those using code. With telegraph nomenclature, it is necessary to spell out words to describe signals or use the abbreviated signal reporting system (RST . . . see Chapter Twenty-Four). Using voice, we have the ability to "say it with words." "Readability four, Strength eight" is the best way to give a quantitative report. Reporting can be done so much more meaningfully with ordinary words: "You are weak but you are in the clear and I can understand you, so go ahead," or "Your signal is strong but you are buried under local interference." Why not say it with words?

#### Voice Equivalents to Code Procedure

Voice	Code	Meaning
Go ahead; over	K	Self-explanatory.
Wait; stand by	AS, QRX	Receipt for a correctly-transcribed message or for "solid" transmission with no missing portions.
Okay	R	Self-explanatory.
Repeat each word twice	QSZ	Repeat everything after . . . . (word).
All after	AA	Repeating a difficult word, phrase or expression.
I will repeat; I say again	IMI	

#### 'Phone-Operating Practice

Efficient voice communication, like good c.w. communication, demands good operating. Adherence to certain points "on getting results" will go a long way toward improving our 'phone-band operating conditions.

*Use push-to-talk technique.* Where possible arrange on-off switches or controls for fast back-and-forth exchanges that emulate the practicality of the wire telephone. This will help reduce the length of transmissions and keep brother amateurs from calling you a "monologist" — a guy who likes to hear himself talk!

*Listen with care.* Carelessness in listening is intolerable. If one has time to operate at all, he should look over his operating practices and "do it right." Noise and other diversions must not be permitted to interfere with the primary objectives in the operating room.

*Interpose your call regularly and at frequent intervals.* Three short calls are better than one long one. In calling CQ, one's call should cer-

#### Voice-Operating Hints

- 1) Listen before calling.
- 2) Make short calls with breaks to listen. Avoid long CQs; do not answer any.
- 3) Use push-to-talk. Give essential data concisely in first transmission.
- 4) Make reports honest. Use definitions of strength and readability for reference. Make your reports informative and useful. Honest reports and *full* word description of signals save amateur operators from FCC trouble.
- 5) Limit QSO length. Two minutes or less will convey much information. When three or more stations converse in round tables, brevity is essential.
- 6) Display sportsmanship and courtesy. Bands are congested . . . make transmissions meaningful . . . give others a break.
- 7) Check transmitter adjustment . . . avoid AM overmodulation and splatter. Do not radiate when moving VFO frequency or checking NFM swing. Use receiver b.f.o. to check stability of signal. Complete testing before busy hours!

tainly appear at least once for every five or six CQs. Calls with frequent breaks to listen will save time and be most productive of results. In identifying, always transmit your *own* call *last*. Don't say "This is W1ABC standing by for W2DEF"; say "W2DEF"; this is W1ABC, over." FCC regulations *require* that the call of the transmitting station be sent *last*.

*Monitor your own frequency.* This helps in timing calls and transmissions. Send when there is a chance of being copied successfully — not when you are merely "more QRM." Timing transmissions is an art to cultivate.

*Speak near the microphone.* Don't let your gaze wander all over the station causing sharply-varying input to your speech amplifier. Keep a proper distance from the microphone, and keep an eye on any modulation indicator used. Change distance or gain only as necessary to insure uniform transmitter performance without overmodulation, splatter or distortion.

*Make connected thoughts and phrases.* Don't mix disconnected subjects. Ask questions consistently. Pause and get answers.

*Have a pad of paper handy.* It is convenient and desirable to jot down questions as they come in the course of discussion in order not to miss any. It will help you to make intelligent to-the-point replies.

*Steer clear of inanities and soap-opera stuff.* Our amateur radio and also our personal reputation as a serious communications worker depend on us.

*Avoid repetition.* Don't repeat back what the

other fellow has just said. Too often we hear a conversation like this: "Okay on your new antenna there, okay on the trouble you're having with your receiver, okay on the company who just came in with some ice cream, okay . . . [etc.]." Just say you received everything OK. Don't try to prove it.

Use phonetics only as required. When clarifying genuinely doubtful expressions and in getting your call identified positively we suggest use of the ARRL Phonetic List. Limit such use to really-necessary clarification.

The speed of radiotelephone transmission (with perfect accuracy) depends almost entirely upon the skill of the two operators involved. One must learn to speak at a rate allowing perfect understanding as well as permitting the receiving operator to copy down the message text, if that is necessary. Because of the similarity of many English speech sounds, the use of alphabetical word lists has been found necessary. All voice-operated stations should use a *standard* list as needed to identify call signals or unfamiliar expressions.

### ARRL Word List for Radiotelephony

ADAM	JOHN	SUSAN
BAKER	KING	THOMAS
CHARLIE	LEWIS	UNION
DAVID	MARY	VICTOR
EDWARD	NANCY	WILLIAM
FRANK	OTTO	X-RAY
GEORGE	PETER	YOUNG
HENRY	QUEEN	ZEBRA
IDA	ROBERT	

Example: W1EH . . . W 1 EDWARD HENRY.

*Round Tables.* One of the most popular kinds of contact on the 'phone bands is the round table, in which several amateurs establish contact with each other and pass the conversation from one to another. The effect is somewhat the same as personal conversation in a group, with one important difference: the person talking cannot be interrupted. The round table has many advantages if run properly. It clears frequencies of interference, especially if all stations involved are on the same frequency, while the enjoyment value remains the same, if not greater. By use of push-to-talk, the conversation can be kept lively and interesting, giving each station ample opportunity to participate without waiting overlong for his turn.

Round tables can become very unpopular if they are not conducted properly. The monologist, off on a long spiel about nothing in particular; cannot be interrupted; *make your transmissions short and to the point.* "Butting in" is discourteous and unsportsmanlike: *don't enter a round table, or any contact between two other amateurs, unless you are invited.* It is bad enough trying to understand voice through prevailing interference without the added difficulty of poor quality: *check your transmitter adjustments frequently.* In general, follow the

precepts as hereinbefore outlined for the most enjoyment in round tables as well as any other form of radiotelephone communication.

## WORKING DX

DX is merely radio shorthand for "distance." Most amateurs at one time or another make "working DX" a major aim. As in every other phase of amateur work, there are right and wrong ways to go about getting best results in working foreign stations, and it is the intention of this section to outline a few of them.

The ham who has trouble raising DX stations readily may find that poor transmitter efficiency is not the reason. He may find that his sending is poor, or his calls ill-timed, or his

### DX ETHICS

Unfortunately, there have been some amateurs specializing in DX work who have not observed proper operating procedures and practices in the methods they are trying to get DX contacts. The points below, if observed by all amateurs interested in DX, will go a long way toward making DX more enjoyable for everybody.

- 1) Call DX only after he calls CQ, QRZ? or signs SK.
- 2) Do *not* call a DX station:
  - a) On the frequency of the station he is working until you are *sure* the QSO is over. This is indicated by the ending signal SK.
  - b) Because you hear someone else calling him.
  - c) When he signs KN, AR or CL.
  - d) Exactly on his frequency.
  - e) After he calls a directional CQ, unless of course you are in the right direction or area.
- 3) Keep within frequency-band limits. Some DX stations operate outside. Perhaps they can get away with it, but you cannot.
- 4) Familiarize yourself with the meanings of ML, LM, HM, MH. DX stations often use these signals.
- 5) Give honest reports. Flattery will get you nowhere. Many foreign stations depend on W reports for adjustment of station and equipment.
- 6) Keep your signal clean. Thumps, clicks, chirps and ripple give you a bad reputation and get you a pink ticket from FCC.
- 7) Listen and call the station you want. Calling CQ DX is not the best assurance that the rare DX will reply.

DATE TIME	STATION CALLED	CALLED BY	MIS FREQ. OR DIAL	MIS SIGNALS RST	MY SIGNALS RST	FREQ. MC.	EMIS. SIGN TYPE	POWER INPUT WATTS	TIME OF ENDING QSO	OTHER DATA
10-20-47										
6:15 PM	W5TQD	x	3.65	589X	569X	25	A-1	250	6:43	<i>Lots of ops! Rec'd 6, sent 10.</i>
7:20	CQ	x				7				
7:21	x	W4TW1	7.24	369	579X				7:32	<i>Too much QRM! Gave it up.</i>
9:32	W3UA	x				3.95	A-3	100		<i>Guess I was snowed under.</i>
10-21-47										
7:05 AM	VK4DY	x	14.03			14	A-1	250		<i>Unanswered a W6</i>
7:07	AC4YN	x	14.02							<i>ND</i>
7:09	VK2ADW	x	14.07	339	559X				7:20	<i>Sydney, Australia. First VK!!</i>
7:31	CQ	x								<i>No luck</i>
7:42	W6RBQ	x	14.05	589	579				8:02	<i>Had to QRT for breakfast nice chat.</i>
8:02		<i>off</i>								

KEEP AN ACCURATE AND COMPLETE STATION LOG AT ALL TIMES! THE F.C.C. REQUIRES IT.

A page from the official ARRL log is shown above, answering every Government requirement in respect to station records. Bound logs made up in accord with the above form can be obtained from Headquarters for a nominal sum or you can prepare your own, in which case we offer this form as a suggestion. The ARRL log has a special wire binding and lies perfectly flat on the table.

judgment in error. When conditions are right to bring in the DX, and the receiver sensitive enough to bring in several stations from the desired locality, the way to work DX is to use the appropriate frequency and timing and call these stations, as against the common practice of calling "CQ DX."

The call CQ DX means slightly different things to amateurs in different bands:

a) On v.h.f., CQ DX is a general call ordinarily used only when the band is open, under favorable "skip" conditions. For v.h.f. work such a call is used for looking for new states and countries, also for distances beyond the customary "line-of-sight" range on most v.h.f. bands.

b) CQ DX on our 7-, 14- and 28-Mc. bands may be taken to mean "General call to any foreign station." The term "foreign station" usually refers to any station in a foreign continent. (*Experienced* amateurs in the U. S. A. and Canada do not use this call, but answer such calls made by foreign stations.)

c) CQ DX used on 3.5 Mc. under winter-night conditions may be used in this same manner. At other times, under average 3.5-Mc. propagation conditions, the call may be used in domestic work when looking for new states or countries in one's own continent, usually applying to stations located over 1000 miles distant from your own.

The way to work DX is not to use a CQ call at all (in our continent). Instead, use your best tuning skill — and listen — and listen — and listen. You have to hear them before you can work them. Hear the desired stations first; time your calls well. Use your utmost skill. A sensitive receiver is often more important than the power input in working foreign stations. Before you can expect to be successful in working any particular foreign country or area, you should be able to hear ten or a dozen stations from that area.

In any band, particularly at line-of-sight frequencies, when directional antennas are used, the directional CQ such as CQ W5, CQ north, etc., is the preferable type of call. Mature amateurs agree that CQ DX is a wishful rather than a practical type of call for most stations in the North Americas looking for contacts in foreign countries. Ordinarily, it is a cause of unnecessary QRM.

Conditions in the transmission medium make all field strengths from a given region more nearly equal at a distance, irrespective of power used. In general, the higher the frequency band, the less important power considerations become.

### ● KEEPING AN AMATEUR STATION LOG

The FCC requires every amateur to keep a complete station operating record. It may also contain records of experimental tests and adjustment data. A stenographer's notebook can be ruled with vertical lines in any form to suit the user. The Federal Communications Commission requirements are that a log be maintained that shows (1) the date and time of each transmission, (2) all calls and transmissions made (whether two-way contacts resulted or not), (3) the input power to the last stage of the transmitter, (4) the frequency band used, (5) the time of ending each QSO and the operator's identifying signature for responsibility for each session of operating. Messages may be written in the log or separate records kept — but record must be made for one year as required by the FCC. For the convenience of amateur station operators ARRL stocks both logbooks and message blanks, and if one uses the official log he is sure to comply fully with the Government requirements if the precautions and suggestions included in the log are followed.

# Message Handling

Amateur traffic handling is highly developed and effective, *if one knows how to use it*. Don't expect that you can get on the air with the message you have written and give it to the first station that comes along and expect miracles to happen. You fellows who get your fun principally from DX, rag-chewing and building equipment should appreciate that you must place the occasional message *you* start and wish to have reach its destination, not in the hands of others like yourselves, but in the hands of one of the many operators who *specializes* in keeping schedules and handling messages, one who gets his fun mainly out of this branch of our hobby, who knows the best current routes and is in a position to use them.

Station owners may originate traffic of *any kind* going to any part of the United States, Hawaii, Puerto Rico and Alaska. Messages with radio amateurs in Canada, Chile and Peru may be handled under certain restrictions. Important traffic in emergencies or messages from expeditions for delivery in Canada must be put on a landwire by the U. S. amateur station handling. International regulations prohibit the handling of third-party messages to the majority of foreign countries. Messages relating to experiments and personal remarks of such unimportance that recourse to the public telegraph service would be out of the question may be handled freely with the amateurs of any country, but third-party messages only under special arrangements between U. S. A. and other governments, and only to the extent agreed upon by the contracting governments.

Messages should be put in as complete form as possible before transmitting them. *Incomplete messages should not be accepted*. As messages are often relayed through several stations before arriving at their destination, *no abbreviations should be used in the text* as mistakes are bound to happen when the text is shortened in this manner. To people not acquainted with radio abbreviations, messages written in shortened form are meaningless. Delivering stations must be careful to see that messages are written out fully.

In handling messages, we are doing something really worth while. We want to start only good worth-while messages from our stations. Our efforts should be directed to making the quality of our message service high. The number of messages we handle is of secondary importance. The *kind of messages* we originate or start from our station, the *speed* with

which the messages pass through our station, and the *reliability or accuracy* with which the messages are handled are the things of paramount importance.

Just as the ultimate aim of amateur radio on all frequency bands is *communication*, so is the relaying of word by radiogram a "natural" when one has something to say to a party beyond immediate reach. Not all hams perhaps appreciate the utility that results from using amateur message service in our ham correspondence. However, no ham, not even a new member of the brotherhood, but feels the satisfaction of having really accomplished something tangible in exchanging a message (recorded communication) with another amateur. Of course, not all beginners develop the advanced operating technique of the finished message handler, but it is within the reach of all who will try. In this chapter we shall discuss basic points to follow in message-handling activities.

The amateur who handles traffic is automatically training himself to do the kind of a job official agencies desire in emergencies, and he becomes a valuable exponent of the whole amateur service.

## Message Form

Each message originated and handled should contain the following component parts in the order given:

- (a) Number
- (b) Station of Origin
- (c) Check
- (d) Place of Origin
- (e) Time Filed
- (f) Date
- (g) Address
- (h) Text
- (i) Signature

A standard form enables one to know just what is coming next, and makes accuracy possible with speed. Start some messages to familiarize yourself with the proper way to write and send traffic in good form. Just as you would be ashamed to admit it if you could not qualify as an experienced amateur by at least "15-w.p.m." code capability, be equally proud of your basic knowledge of how properly to form and send record communications.

- a) Every message transmitted should bear a "number." On the first day of each calendar year, each transmitting station establishes a new series of numbers, beginning at Nr. 1. Keep a sheet with a consecutive list of numbers

handy. File all messages without numbers. When you send the messages, assign numbers to them from the "number sheet," scratching off the numbers on that list as you do so, making a notation on the number sheet of the station to which the message was sent and the date. Such a system is convenient for reference to the number of messages originated each month.

b) The "station of origin" refers to the call of the station at which the message was filed. This should always be included so that a "service" message may be sent back to the originating station if something interferes with the prompt handling or delivery of a message. In the example in (d) below, W1AW is the station of origin, that call being the one assigned the station at the national headquarters of the League.

c) Every word and numeral in the text of a message counts in the check. Full information on checking messages is given later in this chapter.

d) The "place of origin" refers to the name of the city from which the message was sent. If a message is filed at League headquarters by someone in West Hartford, Conn., the preamble reads *Nr 467 W1AW ck 21 West Hartford Conn 8R67 p June 11, etc.*

If a message is sent to your station by mail the preamble shows the place of origin as the town from which the message came. If a message was filed at ARRL headquarters and if it came by mail from Wiscasset, Maine, the preamble would run like this to avoid confusion: *Hr msg nr 467 W1AW ck 21 Wiscasset Maine 8R67 p June 11, etc.*

e) The time filed is the time at which the message is received at the station for transmission. "NFT" in a preamble means no filing time.

f) Every message shall bear a "date" and this date is transmitted by each station handling the message. The date is the "day filed" at the originating station unless otherwise specified by the sender.

g) The "address" refers to the name, street and number, city, state, and telephone number of the party to whom the message is being sent. A *very complete address* should always be given to insure delivery. When accepting messages this point should be stressed. In transmitting the message the address is followed by a double dash or break sign (— . . . —) and it always precedes the text.

h) The "text" consists of the words in the body of the message. No abbreviations should ever be substituted for the words in the text of the message. The text follows the address and is set off from the signature by another break (— . . . —).

i) The "signature" is usually the name of the person sending the message. When no signature is given it is customary to include the words "no sig" at the end of the message to avoid confusion and misunderstanding. When there is a signature, it follows the break; the abbreviation "sig" is not transmitted.

The presence of unnecessary capital letters, periods, commas or other marks of punctuation may alter the meaning of a text. For this reason commercial communication companies use a shiftless typewriter (capitals only). The texts of messages are typed in block letters (all capitals) devoid of punctuation, underlining and paragraphing, *except where expressed in words*. In all communication work accuracy is of first importance. Spell out figures and punctuation.

### Numbering Messages

Use of a "number sheet" or consecutive list of numbers enables any operator to tell quickly just what number is "next." Numbers may be crossed off as the messages are filed for origination. Another method of use consists of filing messages in complete form *except for the number*. Then the list of numbers is consulted and numbers assigned as each message is sent. As the operator you work acknowledges (QSLs) each message, cross off the number used

and note the call of the station and the date opposite this number.

The original number supplied each message by the operator at the originating station is transmitted by each station handling the message. No new numbers are given the message by intermediate stations.

### Checking Traffic—The Landline Check

The ARRL check is the landline or "text-only" count, consisting of the count of only the words in the body or text of the message. It is quicker and easier to count in this fashion than to use the cable count of words in address, text and signature check which is followed in marine-operating work, this simplification being the reason for its adoption. When in the case of a few exceptions to the basic rule in landline checking, certain words in address, signature or preamble are counted, they are known as extra words, and all such are so designated in the check right after the total number of words.

### Counting Words in Messages

The check includes: (1) all words, figures and letters in the body, and (2) the following extra words:

a) Signatures except the first, when there are more than one (a title with signature does not count extra, but an address following a signature does).

b) Words "report delivery" or "rush" in the check.

c) Alternative names and/or street addresses, and such extras as "personal" or "attention -----"

Examples: "Mother, Father, James and Henry" is a family signature, no names counted extra. "John Brown, Second Lieutenant" and "Richard Johnson, Secretary Albany Auto Club" are each one signature with no words counted as extra. An official title or connection is part of one signature, not extra. "Technical Department, Grammer and Mix" as a signature would count two extra words, those italicized after the first name counting as extras. The check of a message with ten words text and two such extras in the signature would be "CK 13 2 extra."

Dictionary words in most languages count as one word irrespective of length of the word. Figures, decimal points, fraction bars, etc., count as one word *each*. It is recommended that, where feasible, words be substituted for figures to reduce the possibility of error in transmission. Detailed examples of word counting are about as difficult in one system of count as in another.

Count as words dictionary words taken from English, German, French, Spanish, Latin, Italian, Dutch and Portuguese languages; initial letters, surnames of persons, names of countries, cities and territorial subdivisions. Abbreviations as a rule should be used only in service messages. Complete spelling of words

is one way to avoid error. Contractions such as "don't" should be changed to "do not." Examples:

Emergency (English dictionary).....	1 word
<i>Nous arriverrons dimanche</i> (French dictionary).....	3 words
DeWitt (surname).....	1 word
E.L.B.D. (initials).....	4 words
United States (country).....	1 word
Prince William Sound.....	3 words
M.S. <i>City of Belgrade</i> (motor ship)....	2 words
<b>EXCEPTIONS</b>	
A.M., P.M.....	1 word
F.O.B. (or fob).....	1 word
O.K.....	1 word
Per cent (or percent).....	1 word

Figures, punctuation marks, bars of division, decimal points—count each separately as one word. The best practice is to spell out all such when it is desired to send them in messages. In groups consisting of letters and figures *each* letter and figure will count as one word. In ordinal numbers, affixes *d*, *nd*, *rd*, *st* and *th* count as one word. Abbreviations of weights and measures in common use count as one word each. Examples:

10 000 000 (figures).....	8 words
Ten millions (dictionary words).....	2 words
5348 (figures).....	4 words
67.98 (figures).....	5 words
64A2.....	4 words
45 1/4 (figures and bar of division).....	5 words
3rd (ordinal number and affix).....	2 words

Groups of letters which are not dictionary words of one of the languages enumerated, or combinations of such words, will count at the rate of five letters or fraction thereof to a word. In the case of combinations each dictionary word so combined will count as a word. In addition, USS, USCG, etc., written and sent as compact letter groups, count as one word. Examples:

Tyffa (artificial 5-letter group) . . . .	1 word
Adecol (artificial 6-letter group).....	2 words
Dothe (improperly combined).....	2 words
alright, alright (improperly combined)	2 words
ARRL.....	1 word

At the request of sender the words "report back delivery," asking for a service showing success or failure in delivering at the terminal station, may be inserted after the check, or "rush" or "get answer" similarly, such words counting as extras in the group or check designation as just covered by example. "Phone" or "don't phone" or other sender's instructions in the address are not counted as extra words. In transmitting street addresses where the words east, west, north or south are part of the address, spell out the words in full. Suffixes "th," "nd," "st," etc., should not be transmitted. Example: Transmit "19 W 9th St" as "19 West 9 St." "F St NE" should be sent "F St Northeast." When figures and a decimal point are to be transmitted, add the words CNT DOT in the check.

Isolated characters each count as one word. Words joined by a hyphen or apostrophe count, as separate words. Such words are sent as two words, without the hyphen. A hyphen or apostrophe each counts as one word. However,

they are seldom transmitted. Two quotation marks or parenthesis signs count as one word. Punctuation is *never* sent in radio messages except at the express command of the sender. *Even then it is spelled out.*

Here is an example of a plain-language message in correct ARRL form, carrying the landline check:

**THE AMERICAN RADIO RELAY LEAGUE**  
**RADIOGRAM**  
VIA AMATEUR RADIO

---

A-1: WAJW      6      WEST HARTFORD CONN      1447      10180      OCT 28

To: ALL RADIO AMATEURS  
 9 BROADWAY ST  
 ANYCITY STATE

ALL AMATEURS ARE REQUESTED TO FOLLOW STANDARD ARRL FORM  
HANDY ARRL

---

RECD: WAJW      WEST HARTFORD CONN      OCT 28, 1947      144700      AL

Very important messages should be checked carefully to insure accuracy. Request originators to *spell out all punctuation marks that must appear in delivered copies. Likewise, never abbreviate in texts, nor use ham abbreviations except in conversations.*

Message handling is one of the major activities that lies in our power as amateurs to do to show our amateur radio in a respected light, rather than from a novelty standpoint. Regardless of experimental, QSL-collecting, friendly rag-chews, and DX objectives, we doubt if the amateur exists who does not want to know how to phrase a message, how to put the preamble in order, how to communicate wisely and well when called upon to do so. Scarcely a month passes but what some of us in some section of our ARRL are called upon to add to the service record of the amateur.

It is important that deliveries be made in businesslike fashion to give the best impression, so that in each instance a new friend and booster for amateur radio may be won. Messages should be typed or neatly copied, preferably on a standard blank, retaining original for the FCC station file. The designation and address of the delivering station should be plainly given so a reply can be made by the same route, if desired.

For those who would disparage some message texts as unimportant, perhaps a reminder is in order that in the last analysis it is not the importance to the ham that handles it that counts, but the importance to the party that sends and the party that receives a message.

The individual handling of traffic in small quantities as well as large is to a very great extent the material that we amateurs use for developing our operating ability, for organizing our relay lines, and for making ourselves such a very valuable asset to the public and our coun-

try in every communications emergency that comes along.

For those "breaking-in" may we say that any ORS, Trunk-liner or experienced ARRL traffic handler will be only too glad to answer your questions and give additional pointers regarding procedure and your station set-up, to help you make your station a really effective communications set-up. Since experience is the only real teacher, newcomers are reminded that becoming highly proficient in any branch of the game is partly just a matter of practice. Start a few messages, to get accustomed to the form. Check some messages to become familiar with the official ARRL (landline) check. You will find increased enjoyment in this side of amateur radio by adding to your ability to perform; by your familiarity with these things the chance of being able to serve your community or country in emergency will be greater. Credit will be reflected on amateur radio as a whole thereby.

#### **Foreign Traffic Restrictions**

Any and all kinds of traffic may be handled between amateur stations in different parts of the United States, Hawaii, Alaska and Puerto Rico. There is no qualification or restriction except that amateur status must be observed and no compensation, direct or indirect, be accepted for station operations or services.

*Internationally* the general regulations attached to the international communications treaty state the limitations to which work between amateur stations in different foreign countries is subject. In practically every nation outside our own country and its possessions, the government owns or controls the public communications systems. Since these systems are maintained as a state monopoly, foreign amateurs have been prohibited by their governments from exchanging traffic which might be regarded as in "competition" with state-owned telegraphs. The international treaty regulations reflect this condition and the domestic traffic restrictions (internal policy) of the majority of foreign countries. Any country ratifying the Madrid (1932) or Cairo (1938) conventions can make its domestic regulations as liberal as it likes; in addition it may conclude special agreements with other governments for amateur communications that are *more liberal* than the quoted terms of the treaty itself. If no specific formal negotiations have been concluded, however, amateurs must observe the following (treaty) regulations in conducting international amateur work:

The exchange of communications between amateur stations and between private experimental stations of different countries shall be forbidden if the Administration of one of the interested countries has given notice of its opposition to this exchange.

When this exchange is permitted the communications must be conducted in plain language and be limited to remarks of a personal nature, for which, by reason of their lack of importance, recourse to the public telegraph service would not be warranted. It shall be absolutely forbidden to

licensees of amateur stations to transmit international communications emanating from third parties. The above provisions may be modified by special arrangements between the interested countries.

Referring to the first paragraph above, in the years since the Washington convention (1927) *no* prohibition on amateur communication (international QSOs) has been filed by *any* country with the Berne Bureau. In some countries, principally European, amateurs are restricted by regulation to privileges much less than made available by international agreement. In the U. S. A. it is the policy, and of course necessary to take care of our greater numbers of amateurs, to give amateurs the fullest frequency allocations and rights possible under international treaty provisions, and to permit free exchange of domestic noncommercial traffic in addition. This policy has justified itself, giving the public amateur radio traffic service and developing highly-skilled operators and technicians who have the ability to keep the U. S. A. in the lead in radio matters.

The second paragraph quoted prohibits *international* handling of third-party traffic, except where two governments have a special arrangement for such exchange. In any event, traffic relating to experimental work, and personal remarks which would not be sent by commercial communications channels, may be sent, when in communication with foreign amateurs.

Previous special arrangements, extending the basic international telecommunications treaty arrangements, have also been effected through ARRL and U. S. A. representations. The special U. S. A.-Canadian agreement will be explained later. Similar arrangements with Chile and Peru permit the handling to those countries of certain types of traffic.

#### **The Canadian Agreement**

The special reciprocal agreement concluded between our country and the Dominion of Canada, at the behest of the ARRL, permits Canadian and U. S. amateurs to exchange messages of importance under certain restrictions. This agreement is an expansion of the international regulations to permit the handling of important traffic.

The authorized traffic is described as follows:

"1. Messages that would not normally be sent by any existing means of electrical communication and on which no tolls must be charged.

"2. Messages from other radio stations in isolated points not connected by any regular means of electrical communications; such messages to be handed to the local office of the telegraph company by the amateur receiving station for transmission to final destination, e.g., messages from expeditions in remote points such as the Arctic, etc.

"3. Messages handled by amateur stations in cases of emergency, e.g., floods, etc., where the regular electrical communication systems



become interrupted; such messages to be handed to the nearest point on the established commercial telegraph system remaining in operation."

The arrangement applies to the United States and its territories and possessions including Alaska, the Hawaiian Islands, Puerto Rico, the Virgin Islands and the Panama Canal Zone. The agreements with Chile and Peru are similar to the above.

#### Originating Traffic

Messages to other amateurs are a natural means of exchanging comment and maintaining friendships. The simplest additional way to get messages is to offer to send a few for friends, reminding them that the message service is free and no one can be held responsible for delay or nondelivery. Wide-awake amateurs have distributed message blanks to tourist camps. Lots of good traffic has been collected through a system of message-collection boxes placed in public buildings and hospitals. A neatly-typed card should be displayed near by explaining the workings of our ARRL traffic organization, and *listing the points to which the best possible service can be given.*

Messages that are not complete in every respect *should not be accepted* for relaying. *Complete address* on every message is important.

To represent amateur radio properly, placards, when used, should avoid any possible confusion with telegraph and cable services. Any posters should refer to *amateur radiograms*, and explain that messages are sent through *amateur radio stations, as a hobby, free, without cost* (since amateurs can't and will not accept compensation). The exact conditions of the service should be stated or explained as completely as possible, including the fact that there is *no guarantee of delivery.* The individual in charge of the station has full powers to refuse any traffic unsuitable for radio transmission, or addressed to points where deliveries cannot be made. Relaying is subject to radio conditions and favorable opportunity for contacting. Better service can be expected on 15-word texts of *apparent importance* than on extremely long messages. Amateur radio traffic should *not be accepted* for "all over the world."

Careful planning and organized schedules are necessary if a *real* job of handling traffic is to be done. Advance schedules are essential to assist in the distribution of messages. It may be possible to schedule stations in cities to which you know quantities of messages will be filed. Distribute messages, in the proper directions, widely enough so that a few outside stations do not become seriously overburdened. Operators must route traffic properly — not merely aim to "clear the hook."

It is better to handle a small or moderate volume of traffic *well* than to attempt to break

records in a manner that results in delayed messages, nondeliveries, and the like which certainly cannot help in creating any public good will for amateur radio.

#### Amateur Stations at Exhibits and Fairs

Whatever type of exhibit is planned, write ARRL in advance, in order to receive sample material to make your amateur booth more complete. A *portable* station can be installed and operated by an already-licensed amateur, subject to FCC notification of location, etc., as provided by regulations. No license coverage is needed if no station is operated, of course.

If the time is short and there is no opportunity for special organization of schedules to insure reliable routing and delivery, quite likely exhibit work, to be most productive of good-will results, had best *not* include message-handling plans — at least not from the booth-station itself where subject to noise, electrical interference, and other handicaps. To handle such traffic as offered with *real efficiency*, it should be distributed for origination with existing schedules of the *several most reliable local amateur stations.* *By dividing the traffic filed with other stations it may be sent more speedily on its way.* Be sure that the operators undertaking to help are qualified and have good schedules for distributing messages.

"Show stations" must avoid origination of "poor traffic" by rigid supervision and elimination of meaningless messages with guessed-at, inaccurate and incomplete addresses *at the source.*

#### General

In successful relaying, *all* factors including "apparent importance" must be taken into account. Incomplete preambles are a common fault. Every station should demand an "office of origin" from stations who have messages, and traffic may be rightly canceled (QTA) on failure to include it. Thus messages will never get on the air without a starting place.

Originating stations should refuse to accept messages to transmit when it is apparent that the address is too meager. A simple logbook, a good filing system, an accurate frequency meter and an equally accurate clock, are sure signs of a well-operated station. The apparatus on the operating table will tell a story without words.

The well-balanced amateur will not only know how to handle a message, but will have extended the principles of neatness and efficiency to his other station activities. The complete amateur station includes attention to traffic matters as part of its regular routine; it is one essential in building a reputation for "reliability" in amateur work. Communication (general) involves an exchange of thoughts. "Traffic" is merely the exchange of thoughts for ourselves or others, using *messages.*

### Relay Procedure

Messages shall be relayed to the station nearest the location of the addressee and over the greatest distance permitting reliable communication.

No abbreviations shall be substituted for the words in the text of a message with the exception of "service messages," to be explained. Delivering stations must be careful that no confusing abbreviations are written into delivered messages.

Sending words twice is a practice to avoid. Use it only when expressly called for by the receiving operator, when receiving conditions are poor.

Messages shall be transmitted as many as three times at the request of the receiving operator. Failing to make a complete copy after three attempts, the receiving operator shall cancel the message (QTA).

Agreement to handle (relay or deliver) a message properly and promptly is always tacitly implied in accepting traffic. When temporarily *not* in a position to so handle, it is a service to amateur radio and your fellow ham to courteously *refuse* a message.

An operator with California traffic does not hear any Western stations so he decides to call a directional "CQ" as per ARRL practice. He calls, *CQ CALIF CQ CALIF DE W1INF W1INF W1INF*, repeating the combination three times.

He listens and hears W9BRD in Chicago calling him, *W1INF W1INF W1INF DE W9BRD W9BRD W9BRD AR*.

Then he answers W9BRD, indicating that he wishes him to take the message. W1INF says, *W9BRD W9BRD DE W1INF R QSP MILL VALLEY CALIF NEAR SF? K*.

After W9BRD has given him the signal to go ahead, the message is transmitted, thus:  
HR MSG NR 78 W1INF CK18 WEST HARTFORD  
CONN NPT (for "no filing time") NOV 18

ALAN D WHITTAKER JR W6SG  
79 ELINOR AVE  
MILL VALLEY CALIF

SUGGEST YOU USE ARRL TRUNK LINE K  
THROUGH W5NW TO HANDLE PROPOSED  
VOLUME TRAFFIC REGARDS

BUBB W1JTD

W9BRD acknowledges the message like this: *W1INF DE W9BRD NR 78 R K*. Not a single *R* should be sent unless the whole message has been correctly received.

Full handling data are placed on the message for permanent record at W1INF. The operator at W9BRD has now taken full responsibility for doing his best in forwarding the message.

### Abbreviated Procedure

Abbreviated procedure deserves a word in the interest of brevity on the air. Abbreviated practices help to cut down unnecessary transmission. However, make it a rule not to abbreviate unnecessarily when working an operator of unknown experience.

*NIL* is shorter than *QRU CU NEXT SKED*. Instead of using the completely spelled-out preamble *HR MSG NR 287 WIGME CK 18 MIDDLEBURY CONN OCTOBER 28 TO*, etc., transmission can be saved by using *287 WIGME 18 MIDDLEBURY CT OCT 28 TO*, etc. One more thing that conserves operating time is the cultivation of the operating practice of writing down "287 W1UE 615P 11/13/37" with the free hand during the sending of the next message.

"Handling" a message always includes the transmission and receipt of radio acknowledgment (QSL) of same, and entry of date, time and station call on *the traffic*, as handled, for purposes of record.

### Getting Fills

If the first part of a message is received but substantially all of the latter portions lost, the request for the missing parts is simply *RPT TXT AND SIG*, meaning "Repeat text and signature." *PBL* and *ADR* may be used similarly for the preamble and address of a message. *RPT AL* or *RPT MSG* should not be sent unless nearly all of the message is lost.

Each abbreviation used after a question mark (. . . — . . .) asks for a repetition of that particular part of a message.

When a few word groups in conversation or message handling have been missed, a selection of one or more of the following abbreviations will enable you to ask for a repeat on the parts in doubt. 'Phone stations, of course, request fills by using the full wording specified, without attempt at abbreviation.

Abbreviation	Meaning
?AA.....	Repeat all after.....
?AB.....	Repeat all before.....
?AL.....	Repeat all that has been sent
?BN...AND.....	Repeat all between...and....
?WA.....	Repeat the word after.....
?WB.....	Repeat the word before.....

The good operator will ask for only what fills are needed, separating different requests for repetition by using the break sign or double dash (— . . . —) between these parts. There is seldom any excuse for repeating a whole message just to get a few lost words.

Another interrogation method is sometimes used, the question signal (. . . — . . .) being sent between the last word received correctly and the first word (or first few words) received after the interruption. *RPT FROM . . . TO . . .* is a long way of asking for message fills.

The figure four (. . . —) is a time-saving abbreviation which deserves popularity with traffic men. It is another of those hybrid abbreviations whose original meaning, "Please start me, where?" has come to us from Morse practice. Of course *?AL* or *RPT AL* will serve the same purpose, where a request for a repetition of parts of a message has been missed.

## Delivering Messages

Provisions of the Communications Act make it a misdemeanor to give out information of any sort to any person except the addressee of a message. It is in no manner unethical to deliver an unofficial copy of a radiogram, if you carefully mark it *duplicate* or *unofficial copy* and do it to improve the speed of handling a message or to insure certain and prompt delivery. Do not forget that there are heavy fines prescribed by Federal laws for divulging the contents of messages to anyone *except* the person addressed in a message.

When it is possible to deliver messages in person, that is usually the most effective way. When the telephone does not prove instrumental in locating the party addressed in the message, it is usually quickest to mail the message.

**FRRL delivery rules:**

Messages received by stations shall be delivered immediately.

Every domestic message shall be relayed within forty-eight (48) hours after receipt, or if it cannot be relayed within this time shall be mailed to the addressee.

Messages for points outside North America must not be held longer than half the length of time required for them to reach their destination by mail.

When a message cannot be delivered, or if it is unduly delayed, a "service" message should be written and started back to the "office of origin."

Each operator who reads these pages is asked to assume *personal responsibility* for accuracy, speed of each message handled, and delivery, that we may approach a 100% delivery figure.

## The Service Message

A service message is a message sent by one station to another station, relating to the service which we are or are not able to give in message handling. The service message may refer to nondeliveries, to delayed transmission, to errors, or to any phase of message-handling activity. It is not proper to abbreviate words in the texts of regular messages, but it is quite desirable and correct to use abbreviations in these station-to-station messages relating to traffic-handling work. Example:

```
HR SVC NR 291 W4IA CK XX ARLINGTON VA NFT
AUG 19
L C MAYBEE W7GE
110 SOUTH SEVENTH AVE
PASCO WASHN — . . . —
UR NR 87 AUG 17 TO CUSHING SIG BOB HELD
HR UNDL D PSE GBA — . . . —
                                     BATTEY W4IA
```

## Counting Messages

To compare the number originated and delivered each month, in order to learn some facts about the "efficiency" of our work in handling messages, a method of counting is used. Each time a message is *handled by radio* it counts one in the total.

A message received in person, by telephone, by telegraph, or by mail, *filed at the station and transmitted by radio* in proper form, counts as *one originated*.

A message *received by radio and delivered* in person, or by telephone, telegraph, or mail, counts as *one delivered*.

A message *received by radio and sent forward by radio* counts as two messages *relayed* (one when received and again one when sent forward).

All messages counted under one of the three classes mentioned must be handled within a 48-hour (maximum) delay period to count as "messages handled." Messages for continents except North America may be held half the length of time it would take them to reach their destination by mail. A "service" message counts the same as any other type of message.

## Extra Delivery Credit

In addition to the basic count of *one* for each time a message is handled by radio, an *extra credit* of one point for each delivery made by mail, telephone, in person, by messenger or other external means *other than use of radio* (which would count as a "relay" of course) will also be allowed. A message received by an operator for himself or his station or a party on the immediate premises counts *only* "one delivered." A message for a third party delivered by *additional means or effort* will receive a point under "extra delivery credits."

The *message total* shall be the *sum* of the messages originated, delivered and relayed, and the "extra" delivery credits. Each station's message file and log shall be used to determine the report submitted by that particular station. Messages with identical texts (so-called rubber-stamp messages) shall count once only for *each* time the complete text, preamble and signature are sent by radio.

In whatever volunteer work it is engaged, a station has an amateur status, and the total is a strictly "amateur" total if handled under ham-band conditions on amateur frequencies.

## Examples of Counting

Let us assume that at the end of the month one operator of a large amateur station receives several messages from another station. (a) Some of these messages are for relaying by radio. (b) Some of them are for local delivery. (c) There are still other messages, the disposal of which cannot be accurately predicted. They are for the immediate neighborhood but either can be mailed or forwarded to another amateur by radio. A short-haul telephone toll call will deliver them but the chances of landing them nearer the destination by radio are pretty good. This operator's "trick" ends at midnight. He must make the report with some messages "on the hook," to be carried over for the next month's report.

a) The messages on the hook that are to be relayed have been received and are to be sent. They count as "1 relayed" in the report that is made out now, and they will also count as "1 relayed" in the next month's report (the month during which they were forwarded by radio).

b) By mailing or phoning the messages at once, they count as "1 delivered" for the current report. By holding them until next day they will count in the *next* report as "1 delivered." Also, they will each have a count of one *extra* delivery credit since they had to be telephoned, mailed, etc.

c) The messages in this class may be carried forward into the next month. If they have to be mailed then they will count in the *next* report as "1 delivered." If they are relayed, we count them as "1 relayed," "1 received" in the preceding month (already reported), and "1 relayed" for the next month, the month in which it was sent forward by radio. If the operator wishes to count this message *at once* as delivered it must be mailed promptly and counted at once.

Some examples of counting:

The operator of Station A gets a message by radio from Station B addressed to himself. This counts as "1 delivered" by himself and by Station A. There is no extra delivery credit possible for no additional delivery effort was needed.

The operator of Station A takes a verbal message from a friend for relaying. He gives it to Station B over the telephone. Operator A does not handle the message by radio. Station B and Operator B count the message as "1 originated." A cannot count the message in *any* manner.

The operator and owner of Station A visits Station B and *while operating* there takes a message for relaying. The operator and owner of B cannot operate for a day or two so the message is carried back to Station A by Operator A who relays it along within a few hours. The traffic report of both Station A and Station B shows "1 relayed" for this work.

*Please note that "handling" a message always includes the transmission and receipt of radio acknowledgment (QSL) of same, and the entry of date, time, and station call on the traffic, as handled, for purposes of record. Only messages promptly handled and with information so recorded shall be counted in ARRL totals.*

#### **"Rubber-Stamp" Messages**

The handling of traffic can be both fun and constructive, interesting work. Because multiple-address (rubber-stamp) messages mean much drudgery and little accomplished, they cannot be handled effectively in a hobby such as amateur radio.

Obviously, a station in handling a rubber-stamp message has to exert only a small amount of effort in receiving the text and signature once. Then by handling the address to different points *en groupe* a large number of messages (?) can be received and transmitted with little time and effort. The League's system for crediting points for messages handled (and except for any *extra* delivery credit) is based on giving one credit each time a *complete* message is handled by amateur radio, i.e., one credit for each originated message, one credit for each delivered message and two credits for each relayed message (one credit for the work in receiving it and one for the work in transmitting it). *Only* every message handled by radio with a *complete* preamble, address, text, and signature shall be counted, except in the case of *deliveries*, each mailed, telephoned or

otherwise delivered message shall count "one delivered" *regardless* of handling in "book" form (with text sent once only).

#### **Reporting**

Whether the principal accomplishments of the station are in traffic handling or other lines, *what you are doing* is always of interest. One part of *QST* is devoted to Station Activities, this written up by your elected section communications manager. His address is given on page 6 of each *QST*. Reports from *all active hams*, sent the SCM at the end of each month and covering the 30 days just previous, are welcomed.

#### **Operating on Schedules**

Traffic-handling work can be most advantageously carried on by arranging and keeping a few schedules. The message "hook" cleared in a few minutes of work on *scrNY* and the station will be free for DX or experimental work. Aim at station appointments if you can do so, and become a member of your ARRL section net. If at the moment you cannot go this far, start out by making some individual schedules, with at least one tie-in to some organized net.

#### **Traffic Handling Develops Skill**

The dispatch of messages makes operators keen and alert. The better the individual operator, the better the whole organization. Proper form in handling traffic, getting fills, and in general operating procedure develops operators who excel in "getting results." Station performance depends 90% on operating ability and 10% on the equipment involved, granting of course that station and operator are always interdependent. Experience in message handling develops a high degree of operating "intelligence."

Message handling leads to organization naturally, through the need for schedules and coöperation between operators. It offers systematic training in "real" operating. It leads to planned, useful, unselfish, constructive work for others at the same time it represents the highest form of operating "skill" and enjoyment to its devotees. Emphasis should be placed on the importance of traffic handling in training operators in the use of procedure — and in general operating reliability. The value of the amateur (as a group), in cases of local or national emergency, depends to a great extent on the *operating ability* of individual operators. This ability is largely developed by message handling.

Practice in handling traffic familiarizes one with detailed time-saving procedure, and develops general skill and accuracy to a higher extent than obtains in "just rag-chewing" or haphazard work.

# Emergency Operation

Public service in emergencies is part of the tradition of amateur radio. It constitutes important justification for the frequency assignments granted by our Government. The public has come to appreciate our emergency work through the consistent performance of amateurs in bridging disaster-created gaps in hundreds of instances, over many years of our radio operation. In view of these emergency-communication values emergency work takes on ever-increasing importance. Handling emergency communications puts across in a striking way that which we most need to have the public appreciate about our ability and willingness to serve. Every licensed amateur owes it to his community to be ready to play a proper part (not necessarily to transmit) in communications emergencies.

This chapter will be dedicated entirely to outlining amateur-service emergency work, plans and policies.

## ● OUR ABILITY TO SERVE

Of all the civilian services licensed by the FCC, amateur stations are most numerous. While the technique of radio use is expanding to embrace new horizons, it is doubtful if the geographical numbers and distribution of amateurs closely in proportion to the urban and suburban population will be challenged in any large way. But new services automatically capable of emergency employment do naturally point to increased competition in this field of potential service.

It remains for the amateur to exercise continuing and increased initiative in the field of emergency organization. Liaison with agencies and officials active in emergencies who are potential users of the amateur service, liaison with other communicators with whom emergency burden will be shared, and the implementation of emergency plans through drills and tests are necessary after local mobilization of equipment and operator facilities by the amateur. Only proper all-out support of emer-

gency plans will permit the amateur to continue to hold the top records for accomplishment in this field.

## ● ADVANCE PLANNING NECESSARY

Individual preparedness and organization of amateurs, community by community, are the most essential elements of a successfully-functioning amateur emergency service. Annual ARRL Field Days supply a tremendous incentive to clubs and individuals to perfect and test emergency-powered equipment. Training in message handling and the principles of working together under unusual circumstances combine in this outing an annual "shake-down" of communications gear afield, to challenge individual and group efforts. But unless each individual in addition to working casually in annual events attaches himself to community organization and the support of local plans, our group effort may sometimes fall short of its organized capabilities of performing a public service.

The chief lesson, from past emergencies, calls for support and membership of every active operator in the ARRL Emergency Corps. By joining, one is supporting organized amateur radio for any and every emergency! The AEC member can enjoy and benefit from *advance* discussions, literature, and participation in exercises covering such matters as procedure, priorities, station dispositions, and other factors. By such alignment with AEC, one justifies his license as "in the public interest." Such support contributes to our emergency-readiness. Emergency-readiness contributions to public welfare as well as our self-training and experimenting characteristics permit FCC to grant amateur licenses as of public value. Once in the AEC you are on the "inside" in any amateur-service plans worked out by your emergency coördinator. Your local ARRL coördinator can provide appropriate blanks for joining the Emergency Corps . . . or write Headquarters.

## The ARRL Emergency Corps

The AEC was first announced in September, 1935. Participation in the Corps is not limited exclusively to members of ARRL or any other group or organization. All amateurs in the U. S. and Canada can belong. The Corps is a challenge to each individual licensee. It pro-

vides a flexible framework of organization with responsibility for local leadership decentralized to a community emergency coördinator. EC appointments are made by section communications managers whose election and broad field-organization administrative duties and

appointments "of, by and for" the amateur are covered in another chapter.

The Emergency Corps in a given city or town consists of the coordinator and all local radio amateurs who have indicated their support and readiness for participation in emergency plans. The mission of the group in providing emergency radio service is accomplished through organization, self-training, and actual operating tests and activities.

The 144-Mc. band is often used for local AEC nets at points where this v.h.f. band has most stations willing to volunteer for coverage of local points in organized fashion. Other frequency bands may be chosen for local organization, where emergency coordinators find insufficient 2-meter activity, or if interference attributable to a volume of 144-Mc. casual activity requires supplementary means.

H.f. band stations will be recruited for long-haul emergency requirements. Stations should be encouraged to participate in ARRL section nets. Preference in AEC work should be given stations having definite regular traffic schedules to outside points.

### ● FULL AND SUPPORTING MEMBERSHIP

Local emergency coordinators will issue ARRL AEC membership cards to individual amateurs whose application forms indicate their availability and willingness to participate in organized emergency assistance to the community in the event of any emergency. Activity and interest are the criteria for continued membership. *Any* amateur licensee is eligible. Assistant ECs and AEC members are not required to hold ARRL membership, though of course most of them do. The cards must be endorsed annually by the emergency coordinator to keep appointments in effect.

Full membership cards will be issued to those amateurs with stations who can be active in regular as well as occasional test periods. Every full member should strive to have *emergency power* and equipment available! Supporting AEC membership cards will be issued to all individuals who otherwise qualify but who must give limited time to this activity and who are seldom able to participate in group radio activity. ECs will issue new cards or transfer AEC members from "supporting" to "full" status or vice versa on application and as appropriate.

Both portable and fixed amateur station equipment working from commercial power and emergency power are needed in the Emergency Corps to fulfill its missions on h.f. and v.h.f. Equipment types or power source will not be used as a criterion for classification of AEC membership; instead, your activity and the contributions to organized community emergency work and tests within the framework of the AEC will decide your classification.

"Joining" the Emergency Corps is on an

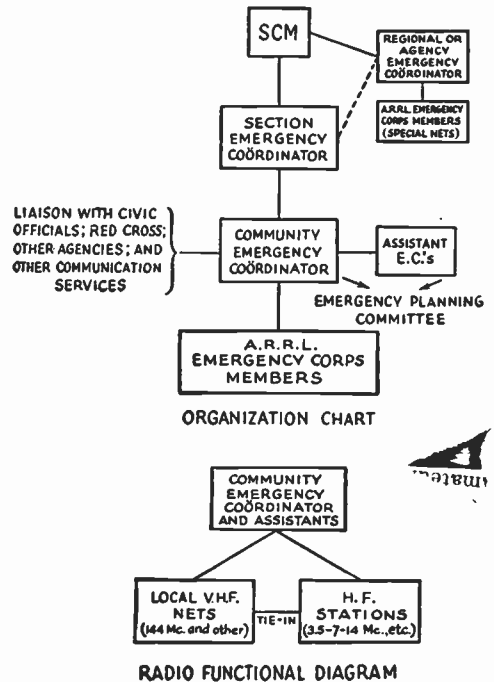


Fig. 22-1 — Chart of AEC organization.

annual basis. The Corps membership cards provide for annual endorsement, at which time ECs should require new station information so that at all times the papers held permit them to know current facts such as the usual operating frequency, telephone number, and available hours for test and operation.

### ● ORGANIZATION

A four-part diagram will best show over-all Emergency Corps organization. The section manager (SCM on Fig. 22-1), is elected under the Constitution and By-Laws of the League to appoint individual member-stations for specific activities in accordance with their qualifications, interest and ability. *Before* emergencies the SCM arranges the most complete local leadership possible through his selection and appointment of qualified men to give exclusive attention to the amateur-service emergency-organizing field.

Section managers (address, p. 6, *QST*) welcome recommendations from emergency-interested amateur groups, radio clubs, and individuals, naming qualified individuals for local emergency leadership. ARRL members who inspire the confidence of community officials, who will act impartially to work out amateur-service plans with amateurs in each local band and mode group, while maintaining friendly contact with agencies served and representatives of other communications facilities, will be appointed by SCMs wherever vacancies exist.

### The Section Emergency Coördinator

A Section Emergency Coördinator (SEC on Fig. 22-1) is appointed by the SCM to promote Emergency Corps organization throughout his entire section. The SEC encourages EC recommendations from local groups, and determines the territory handled by ECs as required. His functions include: (1) Recommendations for EC appointments and endorsements for community coördinators. (2) Promulgation of Emergency Corps membership drives, meetings, activities, tests, procedures, etc., at section levels. The SEC will work through local ECs, or sign AEC member cards for those not in areas covered by a local EC, while trying to secure an EC appointee for such cities. (3) Policy and planning recommendations to the SCM on emergency matters. (4) Consolidation of monthly reports from coördinators for the SCM and ARRL headquarters.

The section emergency coördinator must be an SCM appointee who will devote his full energy and effort to this *one* important emergency-organizing program for amateur radio. His responsibilities require him to act as "Assistant SCM" for emergency-organization matters.

### The Emergency Coördinator

The Emergency Coördinator often has a good station and emergency equipment himself, to set the example, but his *primary* duty is *organization*.

In carrying out his seven-point program, the EC registers (on AEC Form 7A) all available local emergency equipment and operators. His community plan of preparedness will be determined with the assistance of his emergency planning committee (of assistant coördinators) or by otherwise depending on the geography of the area, state of training and past experience in emergency work, and the best assessments that can be made of community needs and available amateur facilities. Points common to every EC program are as follows:

- (1) Organization meetings of all available amateurs . . . explaining objectives, enlisting support of every amateur.
- (2) Designation of assistant ECs for an emergency planning committee.
- (3) General planning for assumed community emergencies.
- (4) Committee meetings and appointments to handle particular responsibilities.
- (5) Liaison with (a) official agencies served, (b) other communications services.
- (6) Designations of (a) exceptional simulated-emergency tests, (b) of regular operational AEC periods.
- (7) Monthly assessment of progress. Reports for ARRL-SCM-QST.

The organizational chart also shows contact the SCM and the SEC with "regional (or

agency) emergency coördinators." Section nets, groups organized by SECs for the Weather Bureau, Engineers, and others often serve as points for reliable "outside" communication in case of an unexpected local emergency. The "regional" ARRL coördinator is SCM-appointed only after policy review with ARRL Hq. to provide and maintain stand-by facilities for specific agencies of a *regional* or community nature. His post will not be explained in detail in these paragraphs except to say that local tie-ins with all such networks should be arranged by emergency coördinators where they may be helpful.

### ● TYPICAL COMMUNITY PLAN

Another diagram (Fig. 22-2) illustrates the key position of the ARRL emergency coördinator as chairman of the amateur-service planning committee. This indicates a "typical" set-up for a town or city, containing practically every element of proper program planning.

Each group plan for utilization of amateur radio should contemplate tying the work of the different groups using different frequencies in emergency instances to an amateur radio control center. In simple wire overloads (minor emergencies) and where only a few amateurs in a locality are concerned, telephone connections between stations or from the coördinator himself to operators in each group, may suffice. As the communities covered are of larger size and the number of amateurs concerned is greater, it is essential that more complete plans for use of telephone, courier, or common v.h.f. channel with stringent circuit discipline be made to facilitate accurate message exchanges and full emergency control. Geographical considerations may require the establishment of relay points within one large community.

A potential list of the agencies served is indicated at the left of Fig. 22-2, showing the organized groups of AEC member-stations (fixed, mobile, and emergency-powered) available in each of the different bands. Liaison is necessary with other communicating services as well as with those officials for whom we handle traffic. At some points airways communications facilities, state police, sheriff's office, state forestry service or military communications facilities may be an important factor, or the local water bureau or public utilities supplying light and power might be served in important ways.

A first important item for the coördinator and his planning committee then is to translate our generalized diagram to a community plan that can be reduced to paper for a specific community. The final "blueprint" should show the names of representatives of agencies and their telephone numbers, the calls of amateurs representative of each frequency band/mode, and if practicable, any assignments of special responsibility under existence of an emergency.

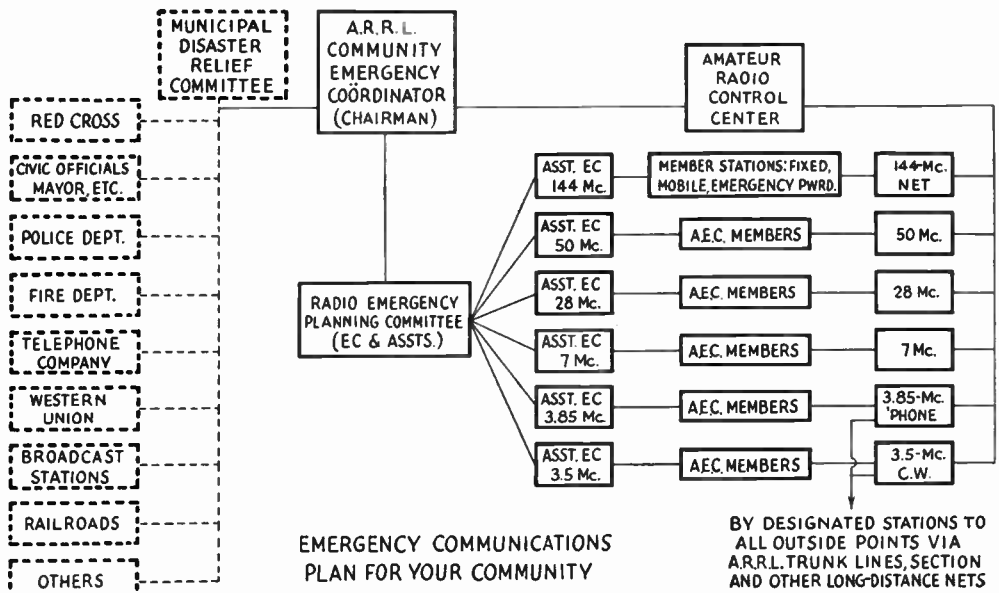


Fig. 22-2 — Block diagram of AEC plan for a typical community.

### Three Phases of Emergency Planning \*

1) There are two types of provisions to be made for emergency radio coverage: (a) that for local short-haul work, (b) that for necessary out-of-the-area or distant coverage. Emergency coordinators have to make plans to cover both cases for implementation, separately or together, depending on the seriousness of the situation.

2) In using radio in the simplest form of emergency work, there is but one objective: to establish contact with an outside point to report difficulties, summon aid, or communicate intelligence of a limited character, when other means fail or are unavailable. *Coverage to some outside point is the thing!*

3) When a populated center has its communications crippled by causes that also disrupt transportation, food and water supply, and other organized public services, the *real emergency* is basically the same, but the effects are greatly magnified by the increased requirements. In addition to communicating considerable distances to get help from outside the paralyzed area, there is a problem of maintaining necessary communications between workers *within the area*.

### Short-Haul Work — Local Nets

Local emergency networks should be established on a regular basis if possible, or on a stand-by basis with monthly tests and simulated drills wherever facilities permit in all the larger cities. Some mobiles and portables usually are assigned to cover points deemed strategically important by city officials for expected emergency use. Ordinarily local nets will use v.h.f. bands. Whether two meters or six meters or ten meters is used will depend on the community and the number of voluntary

amateur workers equipped on a common frequency. In very large cities it may be justifiable to have local emergency nets using more than one amateur frequency band, with proper provision for traffic exchanged through common points. It is suggested that all regularly-operating v.h.f. nets identified with particular communities dedicate themselves to emergency operation in the event of any public need. The responsible net control stations will be glad to assist the appropriate ARRL ECs to permit occasional exceptional tests as well as participation in all major Amateur Emergency Corps exercises.

### H.F. Stations for Outside Contact

Local stations working on lower amateur frequencies should be included in every community plan, for contact to outside points via ARRL trunk lines, section nets, and other h.f. or regional nets. Amateur-service planners should attempt to determine from agencies they expect to serve from what cities or points *outside* the immediate local area supplies, assistance or exchanges of communication would be required in event of possible emergencies. The needs of some agencies may warrant advance designation of a station. Or the setting up of traffic schedules or stand-by c.w. telegraph arrangements between neighboring cities for accurate handling of record communications can be tried on a weekly or other recurrent basis. It is *not* desirable to have too many stations operating on h.f. in haphazard fashion when there is an emergency. In a major catastrophe designated stations should be manned by several shifts of amateurs on 24-hour basis, to avoid overworking one-n set-ups. Create least band congestion & give the best service!



## Policies for Your Emergency Operating

### ● DEFINITION — AGENCIES SERVED

A communications emergency occurs whenever normal facilities are interrupted or overloaded. It may or may not involve general public participation. Public-relief-or-welfare emergencies during floods, tornadoes, hurricanes, blizzards, fires, explosions, or other unexpected conditions are usually accompanied by a communications emergency.

Amateur radio is dedicated to serving any agency that it may help in public interest. The League has long had a cooperative understanding with the National Headquarters of the American Red Cross, the primary agency serving in disasters. Long-term plans for cooperation with relief agencies by ARRL results from careful and deliberate study and consultation over a period of time. Work with the U. S. Weather Bureau, Division of Climatological and Hydrologic Services, and with the Army Engineer Corps, which likewise has certain emergency responsibilities to the public, has developed as important in postwar amateur radio. At the request of the Weather Bureau, the League has asked SCMs to designate liaison men with regional administrative offices of this agency in order that stand-by facilities (amateur nets) may be arranged in as many as practicable of 86 different river courses where emergency radio facilities might be needed. Aside from work with the mentioned agencies, present conditions do not permit the diversion of operator availabilities and station facilities to too great an extent.

### ● ASSIST AS ONE STRONG, INTERCONNECTED FACILITY

In emergencies, the public interest is paramount. Our effectives, who are organized and practiced in handling relief communications, are not so numerous as to permit their services to be devoted closely to assisting all the different private or commercial interests that might like to have an exclusive radio service under emergency conditions. Interconnected nets as diagrammed, one organized group per community, can do the best job. So we say: Join the ARRL Emergency Corps. Build on the principle of *one strong facility*.

Our function as *radio amateurs* is to provide emergency communication. We are not responsible for predicting when dams will fall, estimating lives lost or property damage. There are proper public officials to make technical reports on flood stages, and ask for food or medical supplies. As amateurs we do not wish to take it upon ourselves or be held responsible for making pronouncements in such matters. The standing amateur policy is, therefore, to handle information *only* from official sources and to be sure all information handled is defi-

nately signed or labeled as to its source, with rumors either not transmitted at all or plainly marked as such.

### ● PROVIDING MESSAGE SERVICE

Data on roads should come from the state police or highway department, information on weather and flood conditions from the U. S. Weather Forecaster, data on relief needs and property damage from the Red Cross or mayor's office. Get your inquiries put in the form of messages. Information handled is *not* to be given out to reporters or individuals *by amateurs*. We amateurs are obliged to observe the Communications Act, which imposes heavy penalties for violating the provisions on secrecy of correspondence. Only with express authority from a person or agency addressed may information be released. The message belongs to the addressee and the sender!

#### *Priorities*

Priorities (or precedence) will be determined by the degree of public interest involved in all traffic filed. Highest priority must be given vital first-traffic from officials and responsible agencies from an emergency-stricken area to points outside the affected terrain. Of a wholly secondary nature, *personal-inquiry messages* are commonly referred to as "agony" traffic. They do *not* rate the same "time" importance as official and agency messages which must be handled *first*. In the Texas City disaster in 1947, at least two groups of amateurs rendered special service in the early history of that emergency by "dead-ending and delivering by courier" a large volume of inquiry messages which would have served only to congest already-overloaded emergency radio facilities to no good purpose. In view of the dispersion of "displaced persons" from flood areas and those otherwise devastated, it sometimes takes the appropriate welfare agency ten days to three weeks to locate some of the persons to whom inquiry traffic is directed from "outside," a fact that highlights the secondary nature of such messages.

#### *Address Traffic Correctly*

"Accuracy first" is a slogan constantly before communicators. No operator has a right in emergency or otherwise to *change* the address or text of a message, once it has been filed and is en route. This compounds any chance for error. Service messages and notations should be filed supplementing traffic where absolutely necessary. Originating stations must be especially careful to get correct and complete addresses. There are perhaps a dozen inquiry messages to our ham credit for *each* message from an official. But no message counts for anything but a black mark . . . if it cannot

be delivered. Even though the order of merit may not rate as heavily, the sum total of public appreciation reaches an amazing total for completing the handling of "inquiry" messages. Of course no one files *any* message unless it's with the idea that it will mean something to him or the addressee. Using good message forms, standard operating procedure, phonetic word lists where voice is used, and asking for appropriate fills when necessary, reduces the chance of error. Giving oneself plenty of practice in handling record traffic *before* an emergency comes along is the best precaution to insure accuracy. There are special satisfactions and skill from this type of amateur operation, too.

#### **Authentication and Routing**

The *signed* message is the best identification for the person who receives a message. We recommend that amateurs link emergency stations direct to civil and military authorities, so that all messages derive from reliable sources. Broadcasters and others are often criticized for transmitting hearsay and rumors, even for sending traffic requiring delivery "broadcast" and the like. The more nearly our amateur service can make results conform to the pattern of commercial *communications* and *not* to the field of broadcasting, the higher are our achievements acclaimed by agencies served in emergencies!

#### **QRR**

QRR is the "official ARRL land SOS." It is a distress call for emergency use only, to be used only by a station definitely asking assistance!

Operators *outside* emergency zones, deprived of power in major floods and other disasters, have in the past failed to appreciate adequately the problem of battery- and low-powered stations trying to clear traffic and establish contact to "outside" points. It is *all wrong* for operators having picked up an inquiry message addressed to a point in a devastated area to work themselves up to the point of sending "CQ flood area" or sometimes even "QRR." *Listening* and *cooperating* by keeping quiet are practically always best for "outside stations" until they are called for. It is *also a service* for amateurs to forward inquiry traffic, during the secondary phases of an emergency after all-important first messages have been sent and answers delivered, but the practice of *solicitation* of public traffic of the inquiry type through broadcasting stations or otherwise is rather to be discouraged. All questions of priority and procedure should be decided by evaluation of each particular matter in the light of the degree of public interest involved.

#### **Keeping Channels Clear**

In past emergencies the greatest credit is due those amateurs who have acted as

monitors on frequencies *near* those carrying emergency traffic to keep them clear. Every amateur licensee should quickly *stand by and listen* on request or suspicion that either a near-by or distant communications emergency, large or small, is in progress. Only when convinced that he has every detail that can be learned from listening and can contribute definite constructive effort to the people in the area where the difficulty exists, should a distant station try to communicate with the emergency station. Nine times out of ten such a station in all probability will indicate by its calls the station, city, or direction with which communications are required.

#### **FIXED TEXT MESSAGES — "ARL" CHECK**

In the secondary or personal-inquiry phase of communications emergencies the use of numbered-text messages is recommended. At all times, of course, the recommended phonetic alphabet should be used on those channels employing voice. This will minimize possible chance of error and prevent misunderstandings, as difficult or unusual words occur. The numbered-text message series can be used also to avoid garbled texts. Extra care, repeat-backs and phonetics may be advantageous on addresses and signatures and the text shortened to insure absolute accuracy. The following list of texts was prepared with possible emergency needs and utility in mind. It is a special tool for special occasions. It should be used *only* when stations at each end of a QSO are equipped with lists so that every message delivered or relayed to a station not having a list can be expanded. The device saves a great deal of repeat-transmission time and is, therefore, useful when a large volume of inquiries to be handled can just as well conform to the "numbered-text" plan.

In using the following list the amateur starting the message sends the *number* corresponding to that particular text instead of the text itself. The letters ARL (short for American Radio Relay League numbered-text-to-follow) must be placed before the figures of the check to show that the text is from this particular numbered text list. ARL identifies a communication as a message that has to be expanded for delivery or relaying to a station without such a list. In radio handling, the number designating the text always should be spelled out, for accuracy.

ONE	All safe. Do not be concerned about disaster reports.
TWO	Coming home as soon as possible.
THREE	Am perfectly all right. Don't worry.
FOUR	Everyone safe here. Only slight property damage.
FIVE	All well here. Love to folks.
SIX	Everyone safe, writing soon.
*SEVEN	Reply by amateur radio.
EIGHT	All safe, writing soon, love.
NINE	Come home at once.

TEN	Will be home as soon as conditions permit.
ELEVEN	Cannot get home. Am perfectly all right.
	Will be home as soon as conditions permit.
*TWELVE	Are you safe? Anxious to hear from you.
*THIRTEEN	Is . . . . . safe? Anxious to hear.
*FOURTEEN	Anxious to know if everything is OK. Please advise.
*FIFTEEN	Advise at once if you need help.
*SIXTEEN	Please advise your condition.
*SEVENTEEN	Kindly get in touch with us.
*EIGHTEEN	Please contact me as soon as possible (at . . . . .).

\*Not to be solicited in emergency.

Operators must be alert and careful to insure accurate, useful radio service by whatever method. Sent by itself ARL? means "Do you have the list of ARRL numbered radio-grams and are you ready for such a message?" ARL (reply) gives an affirmative answer to both questions.

Example: NR 1 W1AW CK ARL 1 NEWINGTON, CONNECTICUT MARCH 2  
(address) BT THREE BT JOHN AR.

The principle of effective military communication (and emergency communication requirements are very similar) is to use all channels intelligently without fear or favoritism and as efficiently as possible. Accuracy, speed, and secrecy (avoiding public rumors) are all desirable and important considerations in handling the priority traffic in emergencies. Accurate point-to-point work with messages receipted for properly in two-way handling is preferable to any work patterned after "broadcasting," and c.w. is the preferred method for such work. All amateur stations should endeavor to give officials and agencies written-out messages; our facilities are seldom used for conference exchanges when an emergency arrives. Both voice and c.w. operators should practise handling difficult messages, including same in pre-emergency tests. Traffic should be written on proper forms and delivered just as a telegraph office delivers messages. All traffic should be numbered to show origin and put in standard form to avoid duplications. Voice operators should be brief, talk as fast as good reception permits, repeat or use phonetics as required for accuracy, and should not comment casually about the text of messages.

The important thing is to get the message through and to get it through exactly as it was given to us. The place of origin, date of the message, number of words and signature are all highly important to establish the responsibility for statements made in the message, to permit evaluation of the message as to the conditions at the time it was sent, and to fix the place where it originated so a reply can be made if desired. The "word count" is helpful to make sure no words are added to or dropped from the text.

#### **Traffic Experience Counts; Make Delivery from First Outside Point**

Proper organization and establishment of nets, and tie-in with existing ARRL section

traffic-handling nets which specialize in doing an accurate, speedy job, can expedite service for agencies in any emergency. It is perfectly natural that the networks which dedicate their operating fun to handling some traffic regularly can do a better job as to speed and accuracy than those that are thrown together haphazardly when an emergency presents itself. It is important to the amateur service that every ham participate in radio exercises and message handling in connection with Field Days and tests. This should make it possible to raise the level of skill from that of casual voice operation to that which permits successful, reasonably-accurate written-down work typifying a communications service best fitted to cope with any emergency that comes along.

Once a message is transmitted outside an emergency zone it may be forwarded to its destination by commercial or Government wire service. As long as wires are set up they should carry the load. Wire lines from secondary points greatly reduce radio interference. Where needed, however, amateur radio must do its share and do it effectively with as little noise and heroics as possible. Results are what count.

#### **Further Steps To Reduce Interference**

It is only good common sense to invite the attention of coordinators and amateurs generally to the necessity for complete utilization in emergency of all the frequency bands having appropriate propagation characteristics. Every c.w. frequency is a clear channel compared to the voice bands. Every one of the c.w. channels should be utilized, if possible, by amateurs who are able to put their code to work, before complaint of "congestion" is made. This can be done only by having a sufficient number of trained, skilled operators, familiar with c.w. telegraph message handling, ready and on the job to supplement any voice channels that may be established. No one questions the value of voice work for conferences and fast local liaison, where recorded actionable information is not of prime importance and secrecy is not a consideration. However, many agencies (Red Cross, Western Union, and Weather Bureau) that we expect to serve have stressed from time to time that secrecy from the public is important to prevent leakage of information and the start of rumors, as well as to insure accuracy — always a paramount consideration.

The business of "calling in" to help, as engaged in by some casual operators, should be more and more curtailed in the future. Emergency calls to different points should come from the emergency-area stations. The amateur service should demonstrate "circuit discipline" in emergencies, cooperation in standing by and quickly appointing watchers over the frequencies used by emergency stations, to permit good work to go forward

without calling for official declaration of emergency.

### **Appointing Net Monitors To Reduce Interference**

Both c.w. and voice networks operating in future emergencies should make increased provision for appointing one of their number, *not* actually engaged in handling pertinent traffic, to "stand by." The function of this station should be to operate on an adjacent frequency (not exactly on the net frequency itself) for the purpose of seeing that interference-free operation goes forward. If and whenever stations are observed to come on the frequency for work *not* pertinent to the emergency, the "monitor" opens up in businesslike fashion and in the fewest possible words arranges courteously and tactfully for the troublesome station to move elsewhere or desist from interference.

### ● LOCAL EMERGENCIES

With full advance participation in the AEC and through meetings at suitable intervals, *almost* all amateurs should know what is expected of them in emergency, and where they fit into community plans.

In case of any local trouble, report to the EC and ask for information, advising what you know and what you and your station can do to assist.

*In local emergency*, as many amateurs as possible should be ready to go into action based on their thorough familiarity with the local plans of the emergency coordinator and his committee. If it is a matter of isolation of an individual or small party, or a wire disruption without any public emergency, the station participation will *not* require invoking FCC orders or declaration of a general emergency in most cases. However, all amateurs should follow the rules for orderly standing by and helping with minimum use of the transmitter, nevertheless. If a major area is concerned or FCC has not yet acted, follow the *principles* outlined in this chapter and in the FCC regulations, whether or not yet invoked.

Individual amateurs can assist most materially during an emergency if they will keep the ARRL coordinator fully informed, thus assisting him to fulfill his normal functions creditably. By securing early reports from several amateurs, an EC can assign appropriate h.f. stations to agencies and permit outgoing traffic to flow to points where communications are established to "outside." As amateurs report in, the EC will be able to place numerous volunteer operators in key places where they can help by manning telephones, writing up messages, and setting up delivery systems, to insure proper results and over-all coordination such as are necessary to permit the amateur service to do a creditable job!

### ● THE REMOTE EMERGENCY

*Absolute silence*, for those not in an emergency area, is often the best form of cooperation. Unless and until one logs an emergency station giving a directive call for his very city, it is fitting that one stand by. The glory seeker who itches to be at his rig, whether microphone or key, is not one whit a better citizen than the individual novelty seeker who tries to intercept police calls or tries to beat the fire engine to the fire, congesting the streets and increasing public losses and hazards!

Let the operator working under emergency conditions establish reliable contacts with stations as near to him as possible or at points logical for handling his traffic. Urge *your* locals (and places remote from any emergency) to stand by. Do not make an excuse for getting into a situation someone else can handle better, by reason of his signal (propagation conditions) or location. As a rule it is *not* necessary for stations many hundreds of miles distant to organize themselves into nets for an emergency occasion, since the very nature of emergency makes it a fifty-and-one-hundred-mile proposition. A learning-by-listening attitude permits the actual situation to be handled constructively, keeping interference levels much lower.

### ● RED CROSS WIRE NET

Often a relatively small gap need be bridged by radio before communities with commercial power, wire service, and all modern means of providing aid can be reached. The American Red Cross now has a private wire system which operates coast-to-coast and functions not just for emergencies but for the daily handling of its organizational traffic. In future emergencies three of the points on this wire system, it is understood, will be a "delivery" point for any Red Cross messages. As we write, plans that may result in establishing three special dependable amateur service stations, under control of ARRL-affiliated groups or officials at points like Washington, Chicago, and San Francisco, are under study. The Red Cross will put wire printer loops into all such stations. Follow *QST* for operational plans of such key amateur stations, as established. They will be manned both day and night by radio amateurs to collect your inquiry and additional agency traffic during any major disaster!

The Disaster Service of the American Red Cross recommends that under the above policy, for example, a local 3.5-Mc. station in Delaware with a message from his chapter for Atlanta, Ga., might transmit this directly to the designated special amateur station at Washington, D. C., or a 28-Mc. Delaware amateur with the same message might as readily send it directly to Chicago or San Francisco (if Washington is in his skip zone) where it

will be put on the wire printer system of the Red Cross Telecommunications Service to obviate additional relaying. This set-up should effectively reduce radio-interference levels,

expedite deliveries, and, it is hoped, eliminate duplication in deliveries. Reducing the number of relays may also cut the possibility of garbles and errors.

## Coöperation with The American National Red Cross

An official "understanding" between the Red Cross and amateurs, in effect for many years, has been reviewed and reaffirmed. This appears in the *Disaster Preparedness and Relief Manual* (ARC 209) published by the Red Cross. This manual, for the guidance of Red Cross chapters, assigns the function of providing and maintaining communication services to a subcommittee on transportation and communication. In preparing to meet the needs for communications incident to a disaster relief operation, the subcommittee is charged with surveying all communication resources within a chapter jurisdiction to obtain coöperation and plan necessary coördination and mobilization of appropriate facilities in any emergency situation.

Officials of the ARRL Emergency Corps may be invited to serve on the subcommittee, with other members representing telephone and telegraph companies, radio stations of other services, NCR, AARS, or Air Corps communications agencies, where concerned. Additional "transportation" members serve on subcommittees. Here are pertinent extracts of the ARC 209 information:

Every avenue of communication should be kept open to permit the prompt receipt and dispatch of Red Cross messages. If communications are cut, the subcommittee should establish courier service (by Boy Scouts, motorcycle, etc.), to the nearest communication outlet. Local telephone companies will tag the circuits for authorized Red Cross messages in emergency periods under a coöperative understanding with A. T. & T. The needs of other subcommittees for communications should be determined.

Amateur radio stations and operators, including members of the ARRL, will be contacted to develop a plan for extending priority for emergency communications, and for receiving and transmitting all Red Cross messages, by telephone, telegraph, or radio. Test drills should be held from time to time in coöperation with the Emergency Corps of ARRL. The American Radio Relay League has designated EMERGENCY COÖRDINATORS in many communities to unify the service of amateur radio operators for emergency communications. The Emergency Coördinators or other designated representatives should be asked to assume radio communication responsibilities as part of the subcommittees' plans. Such committee member should designate, and arrange for the services of amateur radio stations and the designation of these facilities, with other radio services, for the American Red Cross.

**THE SENDING OF UNAUTHORIZED MESSAGES, ESPECIALLY APPEALS FOR MEDICAL AND NURSING PERSONNEL, SUPPLIES, AND FUNDS SHOULD BE DISCOURAGED. THE SUBCOMMITTEE SHOULD INFORM ALL COMMUNICATION AGENCIES OF THE PERSONS AUTHORIZED TO SEND RED CROSS MESSAGES.**

**A WRITTEN PLAN FOR "WHEN DISASTER STRIKES" SHOULD BE FORMULATED. PLANS SHOULD BE MADE FOR THE MAINTENANCE OF A MESSAGE CENTER, IN TIME OF DISASTERS, UNDER THE CONTROL OF THE SUBCOMMITTEE, IN COÖPERATION WITH COMMUNICATION AGENCIES.**

Thus the Red Cross provides a special place for ARRL emergency coördinators in its recommended set-up. This place dovetails perfectly with EC functions. It says (1) that amateurs will be taken into consideration, (2) that stations and operators will be lined up, (3) that simulated-emergency tests may be arranged — and (4) that the ARRL emergency coördinator should designate the amateur facilities or station(s) for particular service to the Red Cross — with full coördination with the other types of radio service represented in the subcommittee, of course.

Amateurs may serve many agencies but it is to be noted that ARRL recognizes the Red Cross as the primary disaster relief agency, and therefore entitled to our best possible arrangements. The Communications Department policy is to create and extend effective emergency radio coverage to every possible community and Red Cross chapter jurisdiction, where advance preparedness may pay dividends in the form of service. All amateurs are invited to become members of the Emergency Corps. Drills and other activities help make AEC tests enjoyable, and our ability to serve more effectively! Meetings of SECs and ECs, to plan recruitment, and AEC drills, are highly desirable.

Emergency coördinators will find "Amer Red Cross, chap ofs" in the telephone book. Arrange to contact the appropriate chapter official to discuss these matters informally in person at a mutually convenient time. What are the local prospects for meetings of the Red Cross subcommittee — and who are some of the other communications members? If no written plans involving communication are yet available, perhaps you can be of assistance by making a preliminary examination of the problems as you see them for an informal report to the Red Cross chapter on what could and should be done. If a group has been active, find out how amateur radio is represented in it.

In such contact give the Red Cross folks the idea that you are a communicator, that (without boasting) amateur stations have supplied vital help in many past emergencies of record. The official ARRL-RC "understanding" is detailed in the publication ARC 209 to which reference may be made by Red Cross personnel. You would like the opportunity to assist within the established RC framework, in the advance planning and review of communications plans relative to supply of emergency radio communications. You represent the amateur service and ARRL, of course.

## FCC Amateur-Service Regulations Applicable to Emergencies

All amateurs, insofar as possible, should be familiar with every word of all FCC regulations applicable to amateurs. The numbered sections of the regulations particularly pertinent to emergencies (see §12.156) should be religiously observed.

### **Band Segments for Calling Only**

When FCC "declares" an emergency, the 25-kc. segments on the designated band-edges are reserved by FCC for *emergency calling*. Band segments such as the following are then for *emergency calling* only: 3500-3525 kc., 3975-4000 kc.

### **First Five-Minute Listening Periods Required Hourly**

Every amateur operator using the designated frequency bands for handling relief and emergency traffic must stop and observe the five-minute hourly quiet period (0000-0005) . . . the only exception to that rule, *following a declaration of public emergency by the FCC*, is that a message of utmost priority being handled by an amateur in an emergency zone may be continued, ignoring this quiet-period requirement.

### **Emergency Communications Bands**

Since 25-kc. band-edge segments are specified in the regulations as pertinent to any declaration of a general public-service emergency, the remaining band segments are those that must be used for the purpose of handling all emergency traffic. Such bands are: 3525-3850 kc., 3850-3975 kc.

### **All Casual Operation Prohibited**

The text of the FCC emergency-applicable regulations is quoted specifically below. Note the directness and implication of the language! *Casual* conversation, *incidental* calling, testing, or *working*, *unrelated to the emergency* "shall be prohibited." Remarks *not* pertinent to constructive handling of the communications emergency situation are thus prohibited. The FCC in designating assisting amateur stations (§152.54d) says that these "will report stations failing to comply with any part of the emergency rules."

While there are limitations on the authority of the observer-policing stations, and since they act when possible in an advisory capacity, there is the expressed intention of the Commission to examine fully the reports of the designated operators, taking any necessary disciplinary action after investigation of examples of non-compliance with the Commission's regulations.

## ● F.C.C. REQUIREMENTS SUMMARIZED

The text of the current FCC regulations follows, these having complete force and effect from the time the FCC has "declared" a communications emergency until the Commission declares the emergency ended.

Excerpts of §12.156. *Operations in emergencies.*

In the event of widespread emergency conditions affecting domestic communication facilities, the Commission may confer with representatives of the amateur service and others, and if deemed advisable, declare that a state of general communications emergency exists, designating the area or areas concerned (normally not exceeding 1,000 miles from the center of the affected area), whereupon it shall be incumbent upon each amateur station in such area or areas to observe . . . restrictions for the duration of such emergency: (a) States that transmissions, other than those relating to relief work or other emergency service such as amateur networks can provide shall not be made within designated sub-bands. Incidental calling, testing and working, including casual conversations and remarks not pertinent or necessary to constructive handling of the emergency situation, shall be prohibited.

(b) Frequencies (designated channels) shall be reserved for emergency calling channels, for initial calls from isolated stations of first calls concerning very important emergency relief matters. . . . All stations having occasion to use such channels shall change as quickly as possible to other frequencies for communication.

(c) A five minute listening period for the first five minutes of each hour (during which no traffic of less than the highest priority can be handled) is designated by this section. No replies to calls or resumption of routine traffic shall be made in the five minute (first five minutes of each hour) listening period.

(d) FCC may designate certain amateur stations to assist in promulgating the emergency announcement, to police the bands of frequencies designated and to warn non-complying stations observed to be operating therein. These stations shall report fully to the Commission on any non-compliance, after notice with the pertinent provision. Policing-observer stations shall not enter into discussions with other stations beyond the furnishing of essential facts relative to the emergency.

(e) The special conditions imposed under this section will cease to apply when the Commission terminates the emergency declaration.

## ● TERMINATION OF EMERGENCY DECLARATIONS

The termination of an FCC emergency order should not normally be anticipated at the exact time of restoration of wire facilities. Just as the FCC indicates that it will consult with those primarily interested in making a declaration of public emergency, FCC will similarly examine the conditions "in the public interest" before it terminates any emergency order. At such time as the amateur service and representatives of wire and radio services can indicate to the FCC that communications facilities have been supplemented or restored so that *all communications filed can be handled on a current basis*, the FCC may be expected to issue an order terminating any emergency declaration.

# League Operating Organization

Your ARRL arranges amateur operating activities, promotes preparation and organization for communications emergencies, establishes procedure for efficient operation, encourages good operating, and maintains a strong field organization. The Communications Department of the League is concerned with the practical operation of stations in all branches of amateur activity. Appointments or awards are available for rag-chewer, 'phone operator, traffic enthusiast, experimenter and DX man. It is the League's policy to benefit each group concerned along lines of natural interest. Activities have specific objectives, and widest participation is invited. This insures maximum fun and benefit to all.

Operation must have point and constructive purpose to win public respect. Each individual amateur is the ambassador of the entire fraternity in his public relations and attitude toward his hobby. ARRL field organization adds point and purpose to amateur operating.

Organization of the League is by Divisions and by Sections. Members in each division and Canada elect sixteen Directors. With the President and Vice-President chosen by this group they constitute the governing and policy-making body of the League. Seventy-one ARRL sections, the territory of the several sections within each division determined jointly by the director and the communications manager, form convenient units for field organization and operating administration. Operating affairs in each section are supervised by a Section Communications Manager elected by members in that section for a two-year term of office. Organization appointments are made by the section managers. The election of officials is covered in detail in the League's Constitution and By-Laws. Section communications managers' addresses for all sections are given in full in each issue of *QST*. SCMs welcome monthly activity reports from all amateur stations in their jurisdiction. Full information on appointments may be obtained from SCMs and is also contained in a League booklet, *Operating an Amateur Radio Station*, which will be sent from Headquarters on request (10¢ to nonmembers).

Whether your activity embraces 'phone or telegraphy, or both, there is a place for you in League organization.

## Organization Appointments

The section manager desires representative appointees in each city and town and radio club. He studies geographical distribution and coverage in making leadership and station appointments, and gives consideration to the initiative, experience, tact, ability and other recognized qualifications of candidates, to build the best section organization possible.

## ● LEADERSHIP POSTS

To advance each type of station work and group interest in amateur radio, and to develop practical communications plans with the greatest success, appointments of leaders and organizers in particular single-interest fields are made by SCMs. Each leadership post is important. Each provides activities and assistance for appointee groups and individual members along the lines of natural interest. While some posts further the general ability of amateurs to communicate efficiently at all times, by pointing activity toward networks and round tables, others are aimed specifically at establishment of provisions for organizing the amateur service as a stand-by communications group to serve the public in disaster or emergency of any sort.

### Section Communications Manager

The Section Manager is the section executive or administrator in operating matters. He is the only elected official for the section alone, and the office is open to election each two years, or oftener if a vacancy occurs. Requirements for nomination and the system of mail balloting are covered in the operating booklet. Section managers report on all forms of amateur activity (for *QST*) monthly. Every active amateur licensee is invited to report his station activity to his SCM. Reports are mailed to Hq. by SCMs on or before the 1st of each month, for the reporting month, in mainland U. S. A. and Canada.

### *The Section Emergency Coördinator*

Each SEC is appointed to promote and develop the ARRL Emergency Corps within his section. He endeavors to find qualified local leaders to organize amateur facilities in each and every town or city; he studies the need for regional nets and tie-ins with these cities as well as recommending individual EC territory and plans for grouped communities. The SEC promulgates membership drives, meetings, tests, procedure discussions; takes measures to overcome inertia and avoid jurisdictional conflicts in emergency work. Analysis of reports and monthly progress, and programs to get the fullest support of *all* amateurs, are his responsibility at section level.

### *Emergency Coördinator*

Community organization for emergencies, the building of one strong amateur facility to serve all agencies, liaison with other communications services as well as officials and groups likely to have disaster traffic, the setting up of drill periods and working out simulated-emergency tests in an interesting manner, are all in the directive given this official. The Emergency Coördinator must be a man with initiative and organizing ability who will inspire the coöperation of all classes of amateurs in his locality, attracting the support of active operators who may normally work in any of the bands. To develop broad plans it is recommended that every EC designate Assistant Coördinators, constituting his amateur-service emergency planning committee, and representing each frequency band and geographical or club group for a given area. Emergency coördinators must know and use the principles of teamwork in assuring the successful implementation of tests and planning in advance of the occurrence of actual emergencies.

### *Route Manager*

The Route Manager is the authority on schedules and routes, and his station must be active in traffic and organization work. The route manager's duties include coöperation with all radio amateurs in his territory in organizing and maintaining traffic routes, nets, and schedules. RMs also test candidates for ORS appointment as directed by the SCM. Advice to amateurs wanting schedules or traffic routings via trunk lines, section nets, etc., will be given by RMs on request.

### *Phone Activities Manager*

The 'Phone Activities Manager may sponsor 'phone-operating activities in his territory, in the name of the League. The PAM appointment, while paralleling that of RM in some respects, has to do with the upbuilding of ARRL-section 'phone organization. The 'phone activities manager also tests candidates for OPS when referred by the SCM.

'Phone nets may develop ability to handle traffic or follow objectives divorced from traffic, as worked out with net members by the PAM.

## ● STATION APPOINTMENTS

ARRL's field organization has a place for every active amateur who has a station. The Communications Department organization exists to increase individual enjoyment in amateur radio work, and we extend a cordial invitation to every amateur to participate fully in the activities and to apply to the SCM for ORS, OPS, OES, OBS or OO appointment as soon as sufficiently experienced in amateur radio work.

The section manager makes appointments for specific work in accordance with the qualifications and rules for such appointments. He makes cancellations, likewise, for inactivity, inaptitude or failure to perform adequately the actions contemplated in appointment. All appointment certificates must be returned to SCMs annually for endorsement to keep them in effect — no trouble to this if there is continuing activity. The object is to keep field-organization standards high, and insure a live-functioning organization in each amateur group at all times.

### *Official Relay Station Appointment*

Every radio-telegraphing amateur interested in traffic work and operating activities, who can meet the qualifications, is eligible for ap-



pointment of his station as Official Relay Station. Brass pounders handle traffic because they enjoy such work. The potential value to his community and country of the operator who handles traffic is enhanced by his ability, as well as by the readiness of his station and schedules to function for the community in emergency.

The appointment identifies the holder with high standards of amateur operating, and indicates personal keenness and responsibility. The holder voluntarily agrees to report each month, and with absolute reliability to for-



ward and deliver messages regularly through his station. Secure application forms from your local SCM. See full details on requirements in the booklet *Operating an Amateur Radio Station*.

#### **Official 'Phone Station Appointment**

This appointment is for every qualified ham who uses his microphone more than his key in his amateur station, who takes pride in the manner of signal he puts on the air and who aims to have his station really accomplish worth-while communication work. Official 'Phone Station appointees endeavor to live up to the Amateur's Code. OPS appointment aids 'phone-operating enjoyment by helping to promote good voice-operating practices and readiness for meeting the demands of emergency work.

Cultivation of operating ability that is essential to assure accuracy, conciseness and speed for point-to-point work, in which this desirable technique is altogether different than in broadcasting, is encouraged. OPS technique and operating are designed to encourage fraternalism, facilitate tests between stations of the group, and cultivate by example a precept for excellence looked up to by other voice-operating stations. Official 'Phone Station appointees, like ORS, agree voluntarily in accepting appointment that they will keep active stations and report on activities to the SCM monthly. Application forms are available from your SCM.

#### **Official Experimental Station**

The experimenting amateur also finds in the field organization an appointment designed to assist him in his aims. Official Experimental Station work is dedicated to progress in developing successful communications systems and equipment applications, and in collecting propagation data applicable to the v.h.f., u.h.f. and s.h.f. amateur bands. ARRL makes a special effort to coordinate OES reports on problems of interest to large numbers of amateurs by over-all analysis of data reported. This experimenter appointment is available only to amateurs operating stations on bands above 50 Mc.

The Official Experimental Station appointment is designed to cover our postwar requirements in promoting operating progress, from 50 Mc. through the microwaves, as methods applicable to the use of these for various amateur purposes may be evolved. The broad group aim will be production of data to aid in discussion and knowledge of transmission phenomena peculiar to each of our higher-frequency bands. The correlation of reports and results on the broadest possible scale will assist us in knowing how to use antenna structures, from notation of the pattern of these radiations in different terrain and circumstances, as regards transmitted-wave polarization, absorption, refraction and reflection.

#### **Official Broadcasting Station**

OBS are appointed by section managers, and regularly transmit information specifically addressed to ARRL member-amateurs by code and voice, in all frequency bands. Official and special transmissions, daily except holidays, are made from the Headquarters station, W1AW. OBS appointees receive their information direct from this source and by mail, upward of 500 stations covering all ARRL sections with amateur information of national and local interest, with new information at least once a week. Member-stations must agree to render a good service on regular schedule to receive appointment, and power and signal quality are carefully considered. Many of the stations are so well operated that beginners use their transmissions for code practice. Hours between 6 P.M. and midnight have been chosen for most OBS schedules, for that is the time when most amateurs are listening. Code transmissions are preceded by the call "QST" for four or five minutes to inform amateurs this official information is to be sent.

#### **Official Observers**

To help all amateurs keep on assigned frequencies, and to assist brother amateurs in keeping clear of FCC citations and advisory notices and the penalties for infraction of regulations, ARRL Official Observers are appointed. SCMs require such appointees to have an accurate frequency meter, or other equipment for accurate work of the type in which a specific observer engages. Postal warning forms are provided for different classes of trouble. Reports direct to the amateurs concerned by radio or mail cover improper broadness, a.c. notes, overmodulation, poor speech quality, off-frequency operation, harmonic radiation or other emissions, and technical violations of good practice. If you need a frequency check (or other test) ask the SCM for the address of the OO. Observers not only help amateurs individually, they also protect the privileges of all amateurs and avert official Government restriction invited by the careless. Valuable occupancy and station-distribution surveys have been made several times in the history of the Observing System. The top OO appointment requires qualification at intervals in actual Frequency Measuring Tests. The OO certificate is a badge of high technical proficiency in the measurement field.

#### **Emblem Colors**

Members of the League only may obtain the official League emblem and member stationery. Members wear the emblem with black-enamel background. A red background for an emblem will indicate that the wearer is SCM. SECs, ECs, RMs, PAMs may wear the emblem with green background. Observers and all station appointees are entitled to wear emblems with blue background.

### ● SECTION NETS AND TRUNK LINES

Amateurs can add much experience and pleasure to their own amateur lives, and substance and accomplishment to the credit of all of amateur radio, when organized into effective interconnection of cities and towns.

The successful operation of a net depends a lot on the Net Control Station. This station should be chosen carefully and be one that will not hesitate to enforce each and every net rule and set the example in his own operation on the air.

A progressive net grows, obtaining new members both directly and through other net members. Bulletins may be issued at intervals to keep in direct contact with the members regarding general net business, to keep tab on net procedure and make suggestions for improvement, to keep track of active members and weed out inactive ones. At least, a net manager will obtain and circulate as much information as possible to members.

Official Relay Stations at key points are organized in trunk-line formation, covering fourteen east-west and north-south routes, connecting with numerous section and local networks and feeder systems for the purpose of efficient dispatch of traffic. Speedy and reliable work is carried on, the operation entirely on separate spot frequencies in the 3.5-Mc. amateur band. A station must hold ORS appointment to be considered for a trunk-line post.

### ● RADIO CLUBS AND AFFILIATIONS

It is the policy of the League to grant affiliation to any amateur society having 51 per cent of its licensed amateurs also members of the ARRL. Where a society has common aims and wishes to add strength to that of other club groups to strengthen amateur radio by affiliation with the national amateur organization, a request addressed to the Communications Manager will bring the necessary forms and information to initiate the application for affiliation. Affiliated-club news appears in *QST*, and such clubs receive field-organization bulletins and special information at intervals for posting on club bulletin boards or for relay to their memberships. A travel plan providing communications, technical and secretarial contact from the Headquarters is worked out seasonally to give maximum benefits to as many as possible of the more than four hundred affiliated radio clubs. Papers on club work, suggestions for organizing, for constitutions, for radio courses of study, etc., are available in mimeographed form, free on request.

#### *Club Training Aids*

One section of the ARRL Communications Department devotes its full time to the Training Aids Program. This program is a service

to affiliated clubs. Material is supplied for club programs aimed at education, training and entertainment of club members, to make your club meetings more interesting and consequently better attended.

Training Aids include such items as motion-picture films, film strips, slides, recordings, and lecture outlines. Also, code-proficiency training equipment such as recorders, tape transmitters and tapes will be loaned when such items are available. Training Aids cannot presently be supplied to either nonamateurs or nonaffiliated clubs.

All Training Aids materials are loaned free (except for shipping charges) to ARRL-affiliated clubs. Data on affiliation are available on request and numerous groups use this new ARRL service to good advantage. If your club is affiliated but has not yet taken advantage of this service, you are missing a good chance to add the available features to your meeting programs and general club activities. Watch club bulletins and *QST* or write the ARRL Communications Department for full details.

### ● W1AW

The Maxim Memorial Station, W1AW, is on the air every day, except holidays. Operated by the League headquarters, W1AW is located about four miles south of the Headquarters offices on a seven-acre site. Telegraph and 'phone transmitters are provided for all bands from 3.5 to 144 Mc. The normal frequencies in each band for c.w. and voice transmissions are as follows: 3555, 3950, 7210, 14,150, 14,280, 28,060, 29,150, 52,000 and 146,000



kc. Operating hours and station programs are listed every other month in *QST*.

W1AW is dedicated to fraternity

and service. The available time is divided between different bands and modes.

All amateurs are invited to visit W1AW, as well as to work the station from their own shacks. The station was made possible by the Board of Directors, and established to be a living memorial to Hiram Percy Maxim and carry on the work and traditions of the amateur fraternity.

### ● OPERATING ACTIVITIES

Within the ARRL field organization (in which appointments are open for specified lines of work in ham radio for those with the qualifications) there are several special activities. The first Saturday night each month is set aside for all ARRL officials, officers, and di-

rectors to get together over the air from their own stations. This activity is known to the gang as LO-NITE. Quarterly tests for official relay stations and official phone stations are scheduled to develop operating ability and a spirit of fraternalism. All League members may participate in the Annual ARRL Member Party, usually held in January.

In addition to these special activities for appointees and members, ARRL sponsors various other activities open to all amateurs. The DX-minded amateur may participate in the Annual ARRL International DX Competition scheduled during February and March. This popular contest may bring you the satisfaction of working new countries. Then there is the ever-popular Sweepstakes in November. Of domestic scope, the SS affords the opportunity to work new states for that WAS award. The interests of v.h.f. enthusiasts are also provided for in activities especially planned by ARRL.

As in all our operating, the idea of having a good time is combined in the Annual Field Day, with the more serious thought of preparing ourselves to shoulder the communication load as emergencies turn up and the occasion requires. A premium is placed on the use of equipment without connection to commercial sources of power supply. Clubs and individual groups always have a good time, learn much about the requirements for knockabout conditions afield, and achieve success in testing equipment.

Contest activities are diversified to appeal to all operating interests, and will be found announced in detail in issues of *QST* preceding the different events.

## AWARDS

The League sponsors a variety of operating activities as mentioned above. These have useful objectives and add much enjoyment for members of the fraternity. Point is also added to achievement through recognition in the following:

WAS (Worked All States)  
DX Century Club  
Code Proficiency Award  
Rag Chewers Club  
A-1 Operator Club  
Brass Pounders League  
Old Timers Club

### WAS Award

ARRL certificates are available for those radio amateurs who "work all forty-eight of the United States."

WAS means "Worked All States." This award is available regardless of affiliation or nonaffiliation with any organization. Here are the few simple rules to follow in applying for a WAS Certificate:

1) Two-way communications must be established on the amateur bands with all forty-eight United States; any and



all amateur bands may be used. A card from the District of Columbia may be submitted in lieu of one from Maryland.

2) Contacts with all forty-eight states must be made from the same location. Within a given community one location may be defined as from places no two of which are more than 25 miles apart.

3) Contacts may be made over any period of years, and may have been made any number of years ago, provided only that all contacts are from the same location.

4) Forty-eight QSL cards, or other written communications from stations worked confirming the necessary two-way contacts, must be submitted to ARRL headquarters.

5) Sufficient postage must be sent with the confirmations to finance their return. No correspondence will be returned unless sufficient postage is furnished.

6) The WAS award is available to all amateurs.

7) Address all applications and confirmations to the Communications Department, ARRL, 38 La Salle Road, West Hartford, Conn.

List your missing states and go after QSOs with them. You will find it a very considerable operating achievement. How complete is your coverage? Your certificate awaits you.

### DX Century Club Award

Here are the rules under which the DX Century Club Award will be issued to amateurs who have worked and confirmed contact with 100 countries in the postwar period. If you worked fewer than 100 countries before the war and have since worked and confirmed a sufficient number to make the 100 mark, the DXCC is still available to you under the rules detailed on page 74 of June 1946 *QST*.

1) The Century Club Award Certificate for confirmed contacts with 100 or more countries is available to all amateurs everywhere in the world.

2) Confirmations must be submitted direct to ARRL headquarters for all countries claimed. Claims for a total of 100 countries must be included with first application. Confirmation from foreign contest logs may be requested in the case of the ARRL International DX Competition only, subject to the following conditions:

a) Sufficient confirmations of other types must be submitted so that these, plus the DX Contest confirmations, will total 100. In every case, Contest confirmations must not be requested for any countries from which the applicant has regular confirmations. That is, contest confirmations will be granted only in the case of countries from which applicants have no regular confirmations.

b) Look up the contest results as published in *QST* to see if your man is listed in the foreign scores. If he isn't, he did not send in a log and no confirmation is possible.

c) Give year of contest, date and time of QSO.

d) In future DX Contests, do not request confirmations until after the final results have been published, usually in one of the early fall issues. Requests before this time must be ignored.

3) The ARRL Countries List, printed periodically in *QST*, will be used in determining what constitutes a "country." The Miscellaneous Data chapter of this *Handbook* contains the Postwar Countries List.

4) Confirmations must be accompanied by a list of claimed countries and stations to aid in checking and for future reference.

5) Confirmations from additional countries may be submitted for credit each time ten additional confirmations are available. Endorsements for affixing to certificates and showing the new confirmed total (110, 120, 130, etc.) will be awarded as additional credits are granted. ARRL DX Competition logs from foreign stations may be utilized for these endorsements, subject to conditions stated under (2).

6) All contacts must be made with amateur stations working in the authorized amateur bands or with other stations licensed to work amateurs.

7) In cases of countries where amateurs are licensed in the normal manner, credit may be claimed only for stations using regular government-assigned call letters. No credit may be claimed for contacts with stations in any countries in which amateurs have been temporarily closed down by special government edict where amateur licenses were formerly issued in the normal manner.

8) All stations contacted must be "land stations" . . . contacts with ships, anchored or otherwise, and aircraft, cannot be counted.

9) All stations must be contacted from the same call area, where such areas exist, or from the same country in cases where there are no call areas. One exception is allowed to this rule: where a station is moved from one call area to another, or from one country to another, all contacts must be made from within a radius of 150 miles of the initial location.

10) Contacts may be made over any period of years from November 15, 1945, provided only that all contacts be made under the provisions of Rule 9, and by the same station licensee; contacts may have been made under different call letters in the same area (or country), if the licensee for all was the same.

11) All confirmations must be submitted exactly as received from the stations worked. Any altered or forged confirmations submitted for CC credit will result in disqualification of the applicant. The eligibility of any DXCC applicant who was ever barred from DXCC to reapply, and the conditions for such application, shall be determined by the Awards Committee. Any holder of the Century Club Award submitting forged or altered confirmations must forfeit his right to be considered for further endorsements.

12) **OPERATING ETHICS:** Fair play and good sportsmanship in operating are required of all amateurs working toward the DX Century Club Award. In the event of specific objections relative to continued poor operating ethics an individual may be disqualified from the DXCC by action of the ARRL Awards Committee.

13) Sufficient postage for the return of confirmations must be forwarded with the application. In order to insure the safe return of large batches of confirmations, it is suggested that enough postage be sent to make possible their return by first-class mail, registered.

14) Decisions of the ARRL Awards Committee regarding interpretation of the rules as here printed or later amended shall be final.

15) Address all applications and confirmations to the Communications Department, ARRL, 38 La Salle Road, West Hartford 7, Conn.

### WAC Award

The International Amateur Radio Union issues WAC (Worked All Continents) certificates to all members of member-societies who submit proof of two-way communication with at least one station on each continent. Foreign amateurs submit their proof direct to member-societies in the IARU. A c.w. and a telephony certificate are available. Also, special 28-Mc. endorsement will be placed on certificates upon receipt of request accompanied by proof of this way of having worked all continents.

### Code Proficiency Award

A good many hams can follow the general idea of a contact "by ear" but when pressed to write it down as in real communications work they "muff" the copy. The Code Proficiency Award invites every man to prove himself as a proficient operator, and sets up a progressive system of awards for step-by-step gains in copying proficiency. It enables every radio amateur to check his code proficiency, to better that proficiency, and to receive a certification of his receiving speed.

This program is a whale of a lot of fun. The League will give a certificate to any licensed radio amateur who demonstrates that he can copy perfectly by ear for at least one minute, plain-language Continental code at 15, 20, 25, 30 or 35 words per minute, all of special monthly transmissions from your ARRL station, W1AW, or from WØCO and others mentioned in *QST*.

There are two objectives: (1) To copy by ear, write down by pencil and paper, or better yet, write on a "mill" what is sent, to qualify for a certificate and rating on the best one can now do. (2) To put in a few minutes a day operating our station at the best speeds we can, also listening and copying PX and practice transmissions to train our powers of coordination, in order to win from the League the conspicuous endorsement that will be awarded to go on that first Proficiency Certificate whenever we can boost our speed honestly another 5 w.p.m.!



One of these handsome certificates is yours if you can make one minute's solid copy of the monthly ARRL Code Proficiency qualifying run. The schedules of W1AW and other stations transmitting such runs are announced in each issue of *QST*. Submit your copy to ARRL headquarters for checking. Progress in code proficiency is shown after initial qualification, if below 35 w.p.m., by a separate dated endorsement sticker to be attached to the award as shown. All licensed amateurs are invited to try for the Code Proficiency Certificate and endorsements.

W1AW transmits practice material at speeds from 9 to 35 w.p.m. The tape transmissions are of plain-language material, accompanied by identification of the station, and the speed is briefly indicated.

**Rag Chewers Club**

The Rag Chewers Club is designed to encourage friendly contacts and discourage the "hello-good-by" type of QSO. Its purpose is to bond together operators interested in honest-to-goodness rag-chewing over the air. Membership certificates are available.

**How To Get In:** (1) Chew the rag with a member of the club for at least a solid half hour. This does not mean a half hour spent in trying to get a message over through bad QRM or QRN, but a solid half hour of conversation or message handling. (2) Report the conversation by card to The Rag Chewers Club, ARRL, Communications Department, West Hartford, Conn., and ask the member station you talk with to do the same. When both reports are received you will be sent a membership certificate entitling you to all the privileges of a Rag Chewer.

**How To Stay In:** (1) Be a conversationalist on the air instead of one of those tongue-tied infants who don't know any words except "cuagn" or "cul," or "QRU" or "nil." Talk to the fellows you work with and get to know them. (2) Operate your station in accordance with the radio laws and ARRL practice. (3) Observe rules of courtesy on the air. (4) Sign "RCC" after each call so that others may know you can talk as well as call.

**A-1 Operator Club**

The A-1 Operator Club should include in its ranks every good operator. To become a member, one must be nominated by at least two operators who already belong. General keying or voice technique, procedure, copying ability, judgment and courtesy all count in rating candidates under the club rules detailed at length in *Operating an Amateur Radio Station*. Aim to make yourself a fine operator, and one of these days you will be pleasantly surprised by an invitation to belong to the A-1 Operator Club, which carries a worth-while certificate in its own right.

**Brass Pounders League**

Every individual reporting more than a specified minimum in official monthly traffic

totals is given an honor place in the *QST* listing known as the Brass Pounders League.

The value to amateurs in operator training, and the utility of amateur message handling to the members of the fraternity itself as well as to the general public, make message-handling work of prime importance to the fraternity. Fun, enjoyment, and the feeling of having done something really worth while for one's fellows (in traffic handling) is accentuated by pride in message files, records, and letters from those served.

**Old Timers Club**

The Old Timers Club is open to anyone who holds an amateur call at the present time, and who held an amateur license (operator or station) 20-or-more years ago. Lapses in activity during the intervening years are permitted.

If you can qualify as an "Old Timer," send us a brief chronology of your ham career, being sure to indicate the date of your first amateur license, and your present call. If the evidence submitted proves you eligible for the "Old Timers Club," you will be added to the roster and will receive a membership certificate.


● **INVITATION**

Amateur radio is capable of giving enjoyment, self-training, social, and organization benefits in proportion to what the individual amateur puts into his hobby. All amateurs are invited to become ARRL members, to work toward awards, and to accept the challenge and invitation offered in field-organization appointments. Drop a line for the booklet *Operating an Amateur Radio Station*, which has detailed information on the field-organization appointments and awards. Accept today the invitation to take full part in all ARRL activities and organization work.

# Miscellaneous Data
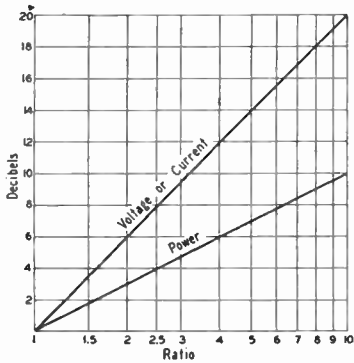
## ● THE DECIBEL

In most radio communication the received signal is converted into sound. This being the case, it is useful to appraise signal strengths in terms of relative loudness as registered by the ear. A peculiarity of the ear is that an increase or decrease in loudness is responsive to the *ratio* of the amounts of power involved, and is practically independent of absolute *value* of the power. For example, if a person estimates that the signal is "twice as loud" when the transmitter power is increased from 10 watts to 40 watts, he will also estimate that a 400-watt signal is twice as loud as a 100-watt signal. In other words, the ear has a *logarithmic* response.



This fact is the basis for the use of the relative-power unit called the decibel. A change of one decibel (abbreviated db.) in the power level is just detectable as a change in loudness under ideal conditions. The power ratio and decibels are related by the following formula:

$$Db. = 10 \log \frac{P_2}{P_1}$$

Common logarithms (base 10) are used.

Note that the decibel is based on *power* ratios. Voltage or current ratios can be used, but *only when the impedance is the same for both values of voltage, or current*. The gain of an amplifier cannot be expressed correctly in db. if it is based on the ratio of the output voltage to the input voltage unless both voltages are measured across the same value of impedance. When the impedance at both points of measurement is the same, the following formula may be used for voltage or current ratios:

$$Db. = 20 \log \frac{V_2}{V_1} \quad \text{or} \quad 20 \log \frac{I_2}{I_1}$$

The two formulas are shown graphically in the accompanying chart for ratios from 1 to 10. Gains (increases) expressed in decibels may be added arithmetically; losses (decreases) may be subtracted. A power decrease is indicated by prefixing the decibel figure with a minus sign. Thus +6 db. means that the power has been multiplied by 4, while -6 db. means that the power has been divided by 4. The chart may be used for other ratios by adding (or subtracting, if a loss) 10 db. each time the ratio scale is multiplied by 10, for power ratios; or by adding (or subtracting) 20 db. each time the scale is multiplied by 10 for voltage or current ratios.

Example: The power input to a transmitter is increased from 75 to 600 watts. Assuming that the efficiency is the same in both cases, the ratio of the new output power to the old is  $600/75 = 8$ . From the chart, the signal will be increased 9 db. Note that increasing the power to 750 watts, a ratio of 10, would increase the signal to 10 db., a barely perceptible increase over 600 watts.

Example: A speech amplifier has an output of 10 watts when excited by 0.02 volt from a crystal microphone. The nominal impedance of the microphone is 50,000 ohms. In a 50,000-ohm load, the voltage developed by the 10 watts would be

$$E = \sqrt{PR} = \sqrt{10 \times 50,000} = \sqrt{500,000} = 707 \text{ volts}$$

The voltage ratio of the amplifier therefore is  $707/0.02 = 35,350$ . This is the same as  $3.5 \times 10,000$ . A voltage ratio of 10,000 ( $10^4$ ) is equal to  $4 \times 20 = 80$  db. From the chart, a voltage ratio of 3.5 = 11 db. Adding the two gives  $11 + 80 = 91$  db. as the gain of the amplifier.

Example: A transmission line is terminated in its characteristic impedance and operates without standing waves. The power put into the line is 150 watts, but the power measured at the output end is 100 watts. The ratio is  $150/100 = 1.5$ . From the chart, this ratio is equal to 1.9 db. The loss in the line is therefore 1.9 db.

### DECIMAL EQUIVALENTS OF FRACTIONS

1/32	.03125	17/32	.53125
1/16	.0625	9/16	.5625
3/32	.09375	19/32	.59375
1/8	.125	5/8	.625
5/32	.15625	21/32	.65625
3/16	.1875	11/16	.6875
7/32	.21875	23/32	.71875
1/4	.25	3/4	.75
9/32	.28125	25/32	.78125
5/16	.3125	13/16	.8125
11/32	.34375	27/32	.84375
3/8	.375	7/8	.875
13/32	.40625	29/32	.90625
7/16	.4375	15/16	.9375
15/32	.46875	31/32	.96875
1/2	.5	1	1.0

**SYMBOLS FOR ELECTRICAL QUANTITIES**

Admittance	$Y, y$
Angular velocity ( $2\pi f$ )	$\omega$
Capacitance	$C$
Conductance	$G, g$
Conductivity	$\gamma$
Current	$I, i$
Difference of potential	$E, e$
Dielectric constant	$K$
Dielectric flux	$\Psi$
Energy	$W$
Frequency	$f$
Impedance	$Z, z$
Inductance	$L$
Magnetic intensity	$H$
Magnetic flux	$\Phi$
Magnetic flux density	$B$
Magnetomotive force	$F$
Mutual inductance	$M$
Number of conductors or turns	$N$
Period	$T$
Permeability	$\mu$
Phase displacement	$\theta$
Power	$P, p$
Quantity of electricity	$Q, q$
Reactance	$X, x$
Reactance, Capacitive	$X_C$
Reactance, Inductive	$X_L$
Reluctivity	$v$
Resistance	$R, r$
Resistivity	$\rho$
Susceptance	$b$
Speed of rotation	$n$
Voltage	$E, e$
Work	$W$

**Pilot-Lamp Data**

Lamp No.	Bead Color	Base (Miniature)	Bulb Type	RATING	
				Volts	Amp.
40	Brown	Screw	T-3 1/4	6-8	0.15
40A <sup>1</sup>	Brown	Bayonet	T-3 1/4	6-8	0.15
41	White	Screw	T-3 1/4	2.5	0.5
42	Green	Screw	T-3 1/4	3.2	**
43	White	Bayonet	T-3 1/4	2.5	0.5
44	Blue	Bayonet	T-3 1/4	6-8	0.25
45	*	Bayonet	T-3 1/4	3.2	**
46 <sup>2</sup>	Blue	Screw	T-3 1/4	6-8	0.25
47 <sup>1</sup>	Brown	Bayonet	T-3 1/4	6-9	0.15
48	Pink	Screw	T-3 1/4	2.0	0.06
49 <sup>3</sup>	Pink	Bayonet	T-3 1/4	2.0	0.06
49A <sup>3*</sup>	White	Screw	T-3 1/4	2.1	0.12
49A <sup>3*</sup>	White	Bayonet	T-3 1/4	2.1	0.12
50	White	Screw	G-3 1/2	6-8	0.2
51 <sup>2</sup>	White	Bayonet	G-3 1/2	6-8	0.2
—	White	Screw	G-4 1/2	6-8	0.4
55	White	Bayonet	G-4 1/2	6-8	0.4
292 <sup>5</sup>	White	Screw	T-3 1/4	2.9	0.17
292A <sup>5</sup>	White	Bayonet	T-3 1/4	2.9	0.17
1455	Brown	Screw	G-5	18.0	0.25
1455A	Brown	Bayonet	G-5	18.0	0.25

\* White in G.E. and Sylvania; green in National Union Raytheon and Tung-Sol.

\*\* 0.35 in G.E. and Sylvania; 0.5 in National Union Raytheon and Tung-Sol.

<sup>1</sup> 40A and 47 are interchangeable.

<sup>2</sup> Have frosted bulb.

<sup>3</sup> 49 and 49A are interchangeable.


<sup>4</sup> Replace with No. 48.

<sup>5</sup> Use in 2.5-volt sets where regular bulb burns out too frequently.


**ABBREVIATIONS FOR ELECTRICAL AND RADIO TERMS**

Alternating current	a.c.	Medium frequency	m.f.
Ampere (amperes)	a.	Megacycles (per second)	Mc.
Amplitude modulation	AM	Megohm	MΩ
Antenna	ant.	Meter	m.
Audio frequency	a.f.	Microfarad	μfd.
Centimeter	cm.	Microhenry	μh.
Continuous waves	c.w.	Micromicrofarad	μμfd.
Cycles per second	c.p.s.	Microvolt	μv.
Decibel	db.	Microvolt per meter	μv/m.
Direct current	d.c.	Microwatt	μw.
Electromotive force	e.m.f.	Milliampere	ma.
Frequency	f.	Millivolt	mv.
Frequency modulation	FM	Milliwatt	mw.
Ground	gnd.	Modulated continuous waves	m.c.w.
Henry	h.	Ohm	Ω
High frequency	h.f.	Power	P
Intermediate frequency	i.f.	Power factor	p.f.
Interrupted continuous waves	i.c.w.	Radio frequency	r.f.
Kilocycles (per second)	kc.	Ultrahigh frequency	u.h.f.
Kilovolt	kv.	Very-high frequency	v.h.f.
Kilowatt	kw.	Volt (volts)	v.
Magnetomotive force	m.m.f.	Watt (watts)	w.

LOW-PASS FILTERS

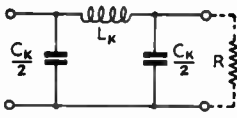


Constant-k pi section

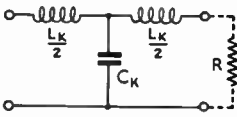


Constant-k T section
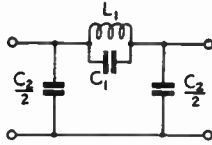
$$L_k = \frac{R}{\pi f_c} \quad C_k = \frac{1}{\pi f_c R}$$




m-derived pi section

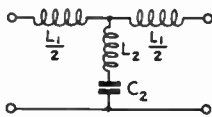


m-derived T section

$$L_1 = mL_k \quad C_1 = \frac{1-m^2}{4m} C_k$$
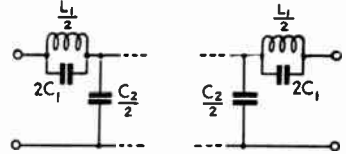
$$L_2 = \frac{1-m^2}{4m} L_k \quad C_2 = m C_k$$



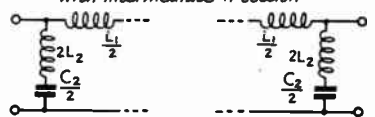m-derived end sections for use with intermediate pi section




m-derived end sections for use with intermediate T section


$$L_1 = mL_k \quad C_1 = \frac{1-m^2}{4m} C_k$$

$$L_2 = \frac{1-m^2}{4m} L_k \quad C_2 = m C_k$$

HIGH-PASS FILTERS

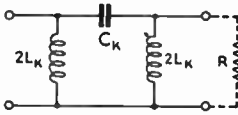


Constant-k pi section

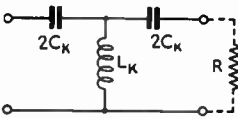


Constant-k T section
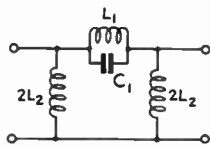
$$L_k = \frac{R}{4\pi f_c} \quad C_k = \frac{1}{4\pi f_c R}$$




m-derived pi section

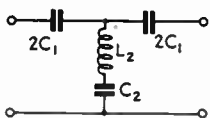


m-derived T section

$$L_1 = \frac{4m}{1-m^2} L_k \quad C_1 = \frac{C_k}{m}$$
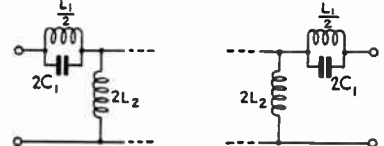
$$L_2 = \frac{L_k}{m} \quad C_2 = \frac{4m}{1-m^2} C_k$$



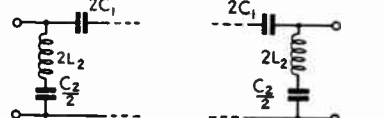m-derived end sections for use with intermediate pi section




m-derived end section for use with intermediate T section


$$L_1 = \frac{4m}{1-m^2} L_k \quad C_1 = \frac{C_k}{m}$$

$$L_2 = \frac{L_k}{m} \quad C_2 = \frac{4m}{1-m^2} C_k$$

BANDPASS FILTERS

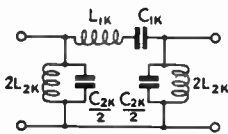


Constant-k pi section

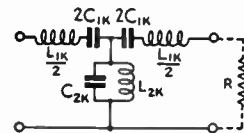


Constant-k T section

$$L_{1k} = \frac{R}{\pi(f_2 - f_1)} \quad C_{1k} = \frac{f_2 - f_1}{4\pi f_1 f_2 R}$$
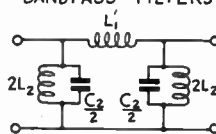
$$L_{2k} = \frac{(f_2 - f_1)R}{4\pi f_1 f_2} \quad C_{2k} = \frac{1}{\pi(f_2 - f_1)R}$$



Three-element pi section

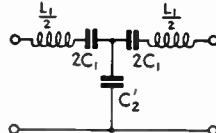


Three-element T section


$$L_1 = L_{1k} \quad L'_1 = \frac{R}{\pi(f_1 + f_2)}$$

$$C_1 = \frac{f_2 - f_1}{4\pi f_1 f_2 R} \quad L_2 = \frac{(f_2 - f_1)R}{4\pi f_1 f_2}$$
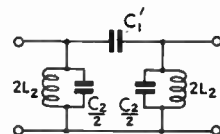
$$C_2 = C_{2k} \quad C'_2 = \frac{1}{\pi(f_1 + f_2)R}$$



Three-element pi section

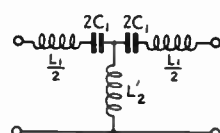

Three-element T section

$$L_1 = \frac{f_1 R}{\pi f_2 (f_2 - f_1)} \quad C_1 = C_{1k}$$

$$C'_1 = \frac{f_1 + f_2}{4\pi f_1 f_2 R} \quad L_2 = L_{2k}$$

$$L'_2 = \frac{(f_1 + f_2)R}{4\pi f_1 f_2} \quad C_2 = \frac{f_1}{\pi f_2 (f_2 - f_1)R}$$



## ● FILTERS

The filter sections shown on the opposite page can be used alone or, if greater attenuation and sharper cut-off are required, several sections can be connected in series. In the low- and high-pass filters,  $f_c$  represents the cut-off frequency, the highest (for the low-pass) or the lowest (for the high-pass) frequency transmitted without attenuation. In the bandpass-filter designs,  $f_1$  is the low-frequency cut-off and  $f_2$  the high-frequency cut-off.

If several low- (or high-) pass sections are to be used, it is advisable to use  $m$ -derived end sections on either side of a constant- $k$  section, although an  $m$ -derived center section can be used. The factor  $m$  relates the ratio of the cut-off frequency and  $f_\infty$ , a frequency of high attenuation. A value of 0.6 is usually used for  $m$ , although a deviation of 10 or 15 per cent from this value is not too serious in amateur work. For a value of  $m = 0.6$ ,  $f_\infty$  will be  $1.25f_c$  for the low-pass filter and  $0.8f_c$  for the high-pass filter. Other values can be found from

$$m = \sqrt{1 - \left(\frac{f_c}{f_\infty}\right)^2} \text{ for the low-pass filter and}$$


$$m = \sqrt{1 - \left(\frac{f_\infty}{f_c}\right)^2} \text{ for the high-pass filter.}$$

The filters shown should be terminated in a resistance =  $R$ , and there should be little or no reactive component in the termination.

Simple audio filters can be made with powdered-iron-core chokes and paper condensers, but above this range mica condensers should be used. The values of the components can vary by  $\pm 5\%$  with little or no reduction in performance. The more sections there are to the filter the greater is the need for accuracy in the components. High resistance in the coils or appreciable leakage in the condensers will also reduce the effectiveness of the filter.
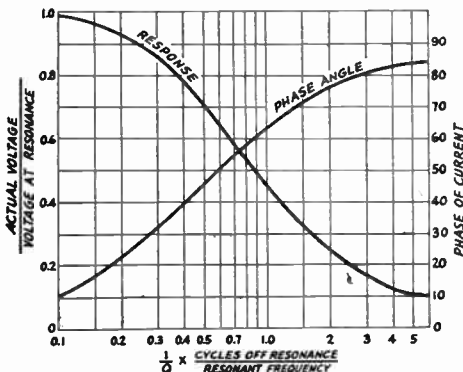
## ● TUNED-CIRCUIT RESPONSE

The graph below gives the response and phase angle of a high- $Q$  parallel-tuned circuit.




Circuit  $Q$  is equal to

$$2\pi fRC \text{ or } \frac{R}{2\pi fL}$$

where  $L$  and  $C$  are the inductance and capacitance at the resonant frequency,  $f$ , and  $R$  is the parallel resistance across the circuit. The curves above become more accurate as the circuit  $Q$  is higher, but the error is not especially great for values as low as  $Q = 10$ .
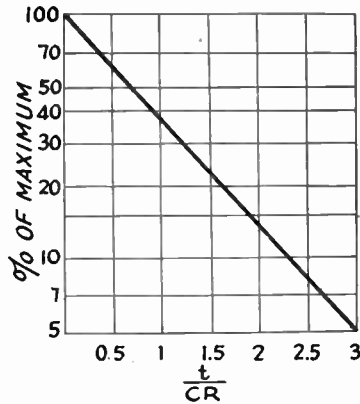
## ● VOLTAGE DECAY IN RC CIRCUITS

The accompanying chart enables calculation of the instantaneous voltage across the terminals of a condenser discharging through a resistance. The voltage is given in terms of percentage of the voltage to which the condenser is initially charged. To obtain the



voltage-decay time in seconds, multiply the factor ( $t/CR$ ) by the time constant of the resistor-condenser circuit.

Example: A  $0.01\text{-}\mu\text{fd.}$  condenser is charged to 150 volts and then allowed to discharge through a  $0.1\text{-megohm}$  resistor. How long will it take the voltage to fall to 10 volts? In percentage,  $10/150 = 6.7\%$ . From the chart, the factor corresponding to  $6.7\%$  is 2.7. The time constant of the circuit is equal to  $CR = 0.01 \times 0.1 = 0.001$ . The time is therefore  $2.7 \times 0.001 = 0.0027$  second, or 2.7 milliseconds.

Example: An  $RC$  circuit is desired in which the voltage will fall to 50% of the initial value in 0.1 second. From the chart,  $t/CR = 0.7$  at the 50%-voltage point. Therefore  $CR = t/0.7 = 0.1/0.7 = 1.43$ . Any combination of resistance and capacitance whose product ( $R$  in megohms and  $C$  in microfarads) is equal to 1.43 can be used; for example,  $C$  could be  $1\text{ }\mu\text{fd.}$  and  $R$  1.43 megohms.

TABLE OF DIELECTRIC CHARACTERISTICS

Dielectric material <sup>1</sup>	Dielectric constant (K)	Power factor					Dielectric strength (puncture voltage) <sup>2</sup>	Volume resistivity <sup>3</sup> (ρ)
		60 cycles	1 kc.	1 Mc.	10 Mc.	100 Mc.		
Air (normal pressure).....	1.0						19.8-22.8	
AlSiMag A196.....	5.7-6.3	2.9		0.21	0.15		240	10 <sup>14</sup>
Aniline formaldehyde.....	3-5	1-6					400	
Asphalts.....	2.7-3.1		2.3				25-30	
Bakelite — See Phenol								
Beeswax.....	2.9-3.2							
Casein plastics <sup>4</sup> .....	6.1-6.4			5.2-6			165	
Castor oil.....	4.3-4.7			7			380	
Celluloid.....	4-16			5-10				
Cellulose acetate <sup>5</sup> .....	6-8	3-6	4-6	4-6	5.5		300-1000	4.5 × 10 <sup>10</sup>
Cellulose nitrate <sup>6</sup> .....	4-7			2.8-5			300-780	2-30 × 10 <sup>10</sup>
Ceresin wax.....	2.5-2.6			0.12-0.21				
Creosol formaldehyde.....	6	10					400	
Dilectene.....	3.57					0.33		
Ethyl cellulose.....	2-2.7	0.7	1.2	1.5			1500	10 <sup>15</sup>
Fiber.....	5-7.5			4.5-5			150-180	5 × 10 <sup>9</sup>
Formica MF-66.....	4.6-4.9		1.5	1.1			450	
Glass:								
Cobalt.....	7.3			0.7				
Common window.....	7.6-8			1.4			200-250	
Crown.....	6.2-7		1	1 <sup>3</sup>			500	
Electrical.....	4-5			0.5			2000	8 × 10 <sup>14</sup>
Flint.....	7-10		0.45	0.4				
Nonex.....	4.2			0.25		0.28		
Photographic.....	7.5			0.8-1				
Plate.....	6.8-7.6			0.6-0.8				
Pyrex.....	4.2-4.9		0.5	0.7		0.54	335	10 <sup>14</sup>
Gutta percha.....	2.5-4.9						200-500	5 × 10 <sup>14</sup> -10 <sup>15</sup>
Lucite <sup>7</sup> .....	2.5-3	7	5	1.5-3	1.9		480-500	
Melamine formaldehyde.....	8	16					300	
Mica.....	2.5-8	0.2	0.3	0.2-6	0.02			2 × 10 <sup>17</sup>
Mica (clear India).....	6.4-7.5	2	2	2	2		600-1500	
Mycalex.....	7.4			0.18			250	10 <sup>13</sup>
Mycalex (British).....	6			0.3			350	
Mykroy.....	6.5-7			0.1-0.2			630	
Nylon.....	3.6			2.2				
Paper.....	2.0-2.6						1250	
Paraffin wax (solid).....	1.9-2.6			0.1-0.3			300	10 <sup>15</sup> -10 <sup>19</sup>
Penque.....	7.21			0.2				
Phenol: <sup>8</sup>								
Pure.....	5			1			400-475	1.5 × 10 <sup>12</sup>
Asbestos base.....	7.5			15			90-150	
Black minkled.....	5-5.5			3.5			400-500	
Fabric base.....	5-6.5			3.5-11			150-500	
Mica-filled.....	5-6			0.8-1			475-600	
Paper base.....	3.8-5.5			2.5-4			650-750	10 <sup>10</sup> -10 <sup>13</sup>
Yellow.....	5.3-5.4			0.36-0.7			500	
Polyethylene.....	2.3-2.4	0.02	0.02	0.02-0.05			1000	10 <sup>17</sup>
Polyindene.....	3	0.04						
Polyisobutylene.....	2.4-2.5	0.04-5	0.05				500	10 <sup>16</sup>
Polystyrene <sup>9</sup> .....	2.4-2.9(2.6)	0.02	0.018	0.02	0.02	0.02	500-2500	10 <sup>20</sup>
Porcelain (dry process).....	6.2-7.5			0.7-15			40-100	5 × 10 <sup>8</sup>
Porcelain (wet process).....	6.5-7			0.6			150	
Pressboard (untreated).....	2.9-4.5						125-300	
Pressboard (oiled).....	5						750	
Quartz (fused).....	3.5-(3-8)	0.01	0.01	0.015-0.03	0.01	0.05	200	10 <sup>14</sup> -10 <sup>18</sup>
Rubber (hard) <sup>10</sup> .....	2-3.5(3)			0.5-1			450	10 <sup>12</sup> -10 <sup>15</sup>
Shellac.....	2.5-4			0.09			900	10 <sup>16</sup>
Steatite: <sup>11</sup>								
"Commercial" grade.....	4.9-6.5	0.02	0.2	0.2	0.4	0.5		
"Low-loss" grade.....	4.4	0.02	0.2	0.2	0.18	0.13	150-315	10 <sup>14</sup> -10 <sup>15</sup>
Titanium dioxide <sup>12</sup> .....	90-170		0.1	0.1				
Urea formaldehyde <sup>13</sup> .....	5-7	3-5	2-3	2-4	4		300-550	10 <sup>12</sup> -10 <sup>13</sup>
Varnished cloth <sup>14</sup> .....	2-2.5			2-3			440-550	
Vinyl resins.....	4			1.4-1.7			400-500	10 <sup>14</sup>
Vitrolex.....	6.4			0.3				
Wood (dry oak).....	2.5-6.8(3)		3.8	4.2				
Wood (paraffined maple).....	4.1						115	

<sup>1</sup> Most data taken at 25° C.

<sup>2</sup> Puncture voltage, in volts per mil. Most data apply to relatively thin sections and cannot be multiplied directly to give breakdown for thicker sections without added safety factor.

<sup>3</sup> In ohm-cm.

<sup>4</sup> Includes such products as Aladdinite, Ameroid, Galalith, Erinoid, Lactoid, etc.

<sup>5</sup> Includes Fibestas, Lumerith, Nixonite, Plastacele, Tenite, etc.

<sup>6</sup> Includes Amerith, Nitron, Nixonoid, Pyralin, etc.

<sup>7</sup> Methylmethacrylate resin.

<sup>8</sup> Phenolaldehyde products include Acrolite, Bakelite,

Catalin, Celeron, Dielecto, Durez, Durite, Formica, Gemstone, Heresite, Indur, Makalot, Marlette, Micarta, Opalon, Prystal, Resinox, Synthane, Textolite, etc. Yellow bakelite is so-called "low-loss" bakelite.

<sup>9</sup> Includes Amphenol 912A, Distrene, Intelin IN 45, Loalin, Lustron, Quartz Q, Rezoglas, Rhodolene M, Ronilla L, Styraflex, Styron, Trolitul, Victron, etc.

<sup>10</sup> Also known as Ebonite.


<sup>11</sup> Soapstone — Alberene, Alsimag, Isolantite, Lava, etc.

<sup>12</sup> Rutile. Used in low temperature-coefficient fixed condensers.

<sup>13</sup> Includes Aldur, Beetle, Plaskon, Pollopas, Prystal, etc.

<sup>14</sup> Includes Empire cloth.

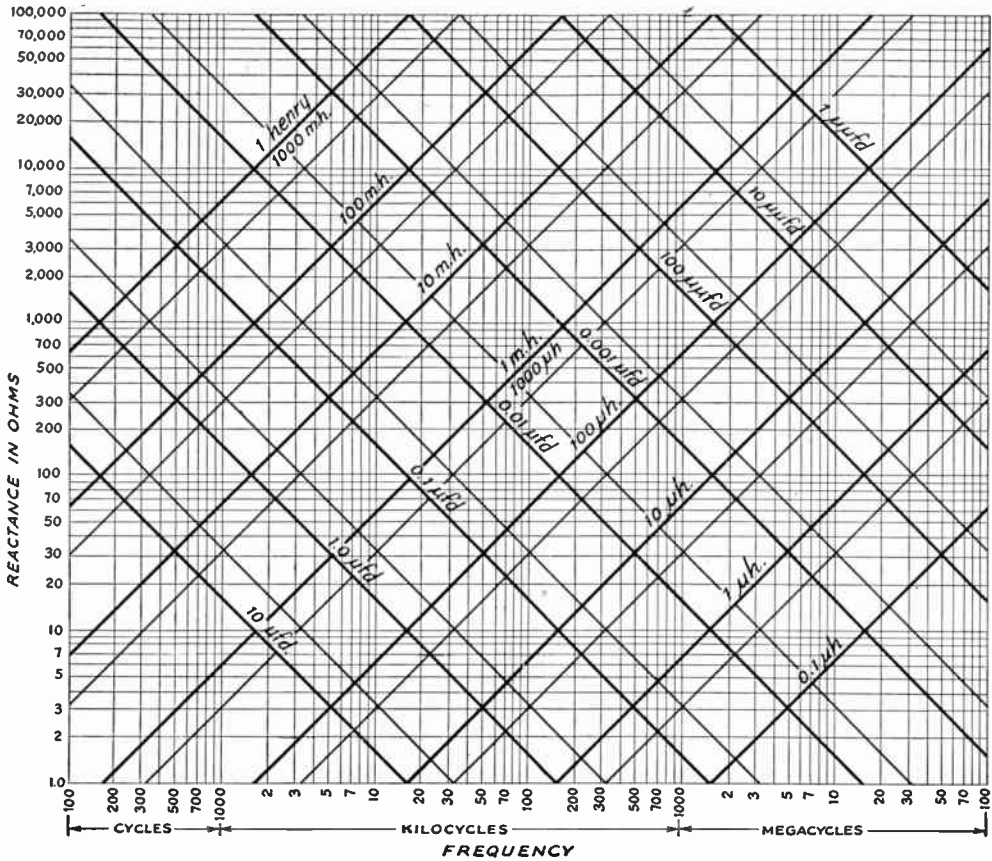INDUCTIVE AND CAPACITIVE REACTANCE VS. FREQUENCY CHART



By use of the chart above, the approximate reactance of any capacitance from 1.0  $\mu\text{fd}$ . to 10  $\mu\text{fd}$ . at any frequency from 100 cycles to 100 megacycles, or the reactance of any inductance from 0.1  $\mu\text{h}$ . to 1.0 henry, can be read directly. Intermediate values can be estimated by interpolation. In making interpolations, remember that the rate of change between lines is logarithmic. Use the frequency or reactance scales as a guide in estimating intermediate values on the capacitance or inductance scales.

This chart also can be used to find the approximate resonance frequencies of LC combinations, or the frequency to which a given coil-and-condenser combination will tune. First locate the respective slanting lines for the capacitance and inductance. The point where they intersect, i.e., where the reactances are equal, is the resonant frequency (projected downward and read on the frequency scale).


ELECTRICAL CONDUCTIVITY OF METALS

	Relative Conductivity <sup>1</sup>	Temp. Coeff. <sup>2</sup> of Resistance		Relative Conductivity <sup>1</sup>	Temp. Coeff. <sup>2</sup> of Resistance
Aluminum (2S; pure) . . . . .	59	0.0049	Lead . . . . .	7	0.0041
Aluminum (alloys):			Manganin . . . . .	3.7	0.00002
Soft-annealed . . . . .	45-50		Mercury . . . . .	1.66	0.00089
Heat-treated . . . . .	30-45		Molybdenum . . . . .	33.2	0.0033
Brass . . . . .	28	0.002-0.007	Monel . . . . .	4	0.0019
Cadmium . . . . .	19		Nichrome . . . . .	1.45	0.00017
Chromium . . . . .	55		Nickel . . . . .	12-16	0.005
Climax . . . . .	1.83		Phosphor Bronze . . . . .	36	0.004
Cobalt . . . . .	16.3		Platinum . . . . .	15	
Constantin . . . . .	3.24	0.00002	Silver . . . . .	106	0.004
Copper (hard drawn) . . . . .	89.5	0.004	Steel . . . . .	3-15	
Copper (annealed) . . . . .	100		Tin . . . . .	13	0.0042
Everdur . . . . .	6		Tungsten . . . . .	28.9	0.0045
German Silver (18%) . . . . .	5.3	0.00019	Zinc . . . . .	28.2	0.0035
Gold . . . . .	65				
Iron (pure) . . . . .	17.7	0.006			
Iron (cast) . . . . .	2-12				
Iron (wrought) . . . . .	11.4				

Approximate relations:  
 An increase of 1 in A. W. G. or B. & S. wire size increases resistance 25%.  
 An increase of 2 increases resistance 60%.  
 An increase of 3 increases resistance 100%.  
 An increase of 10 increases resistance 10 times.

<sup>1</sup> At 20° C., based on copper as 100. <sup>2</sup> Per °C. at 20° C.

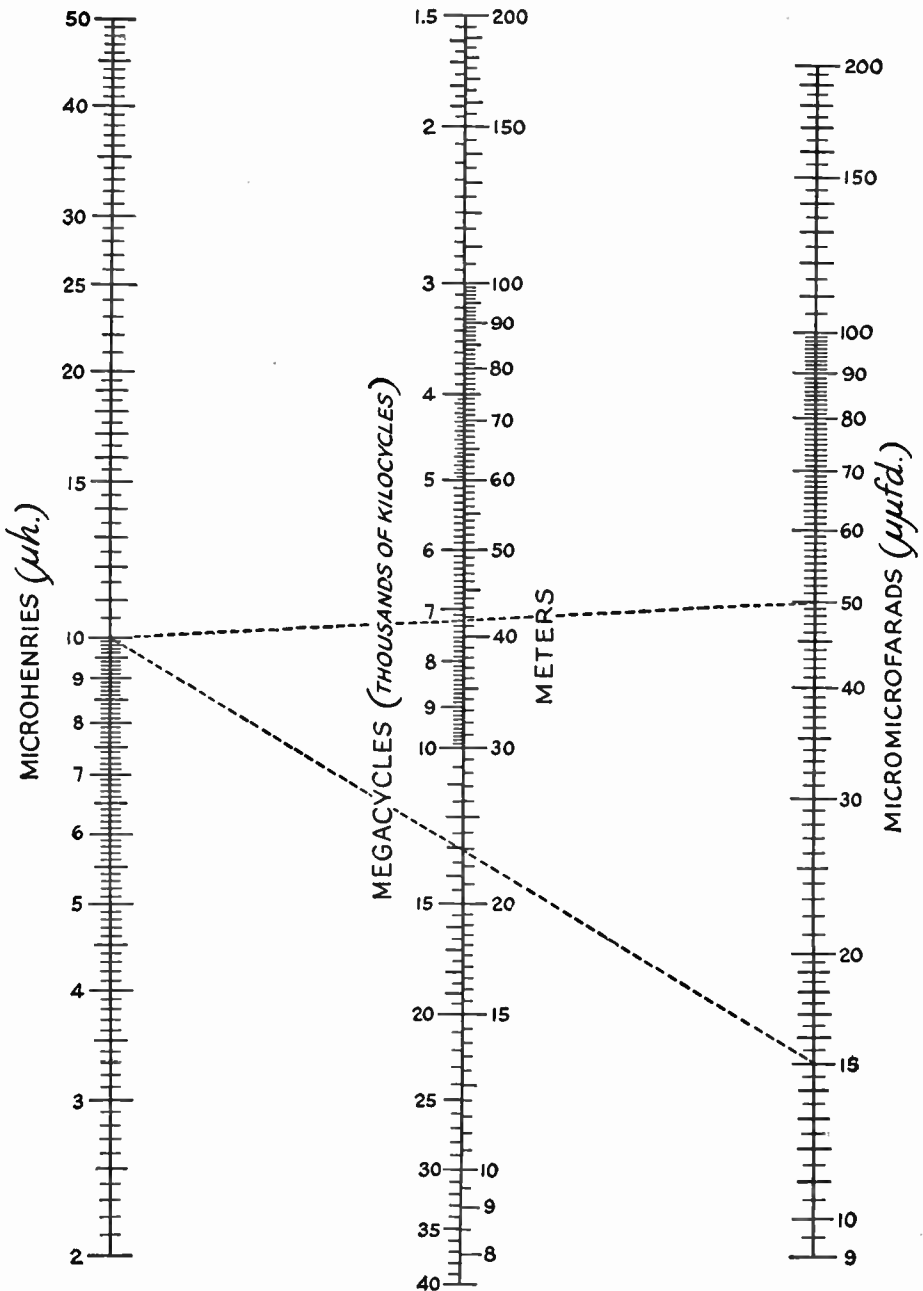INDUCTANCE, CAPACITANCE AND FREQUENCY CHART — 1.5-40 MC.



This chart may be used to find the values of inductance and capacitance required to resonate at any given frequency in the medium- or high-frequency ranges; or, conversely, to find the frequency to which any given coil-condenser combination will tune. In the example shown by the dashed lines, a condenser has a minimum capacitance of 15  $\mu\mu fd.$  and a maximum capacitance of 50  $\mu\mu fd.$  If it is to be used with a coil of 10- $\mu h.$  inductance, what frequency range will be covered? The straightedge is connected between 10 on the left-hand scale and 15 on the right, giving 13 Mc. as the high-frequency limit. Keeping the straightedge at 10 on the left-hand scale, the other end is swung to 50 on the right-hand scale, giving a low-frequency limit of 7.1 Mc. The tuning range would, therefore, be from 7.1 Mc. to 13 Mc., or 7100 kc. to 13,000 kc. The center scale also serves to convert frequency to wavelength.

The range of the chart can be extended by multiplying each of the scales by 0.1 or 10. In the example above, if the capacitances are 150 and 500  $\mu\mu fd.$  and the inductance 100  $\mu h.$ , the range becomes approximately 231 to 422 meters or 0.7 to 1.3 Mc. Alternatively, 1.5 to 5  $\mu\mu fd.$  and 1  $\mu h.$  will give a range of approximately 71 to 130 Mc.

## COPPER-WIRE TABLE

Gauge No. B. & S.	Diam. in Mils <sup>1</sup>	Circular Mil Area	Turns per Linear Inch <sup>2</sup>				Turns per Square Inch <sup>2</sup>			Feet per Lb.		Ohms per 1000 ft. 25° C.	Current Carrying Capacity at 1500 C.M. per Amp. <sup>3</sup>	Diam. in mm.	Nearest British S.W.G. No.
			Enamel	S.C.C.	D.S.C. or S.C.C.	D.C.C.	S.C.C.	Enamel S.C.C.	D.C.C.	Bare	D.C.C.				
1	289.3	83690	—	—	—	—	—	—	—	3.947	—	.1264	55.7	7.348	1
2	257.6	66370	—	—	—	—	—	—	—	4.977	—	.1593	44.1	6.544	3
3	229.4	52640	—	—	—	—	—	—	—	6.276	—	.2009	35.0	5.827	4
4	204.3	41740	—	—	—	—	—	—	—	7.914	—	.2533	27.7	5.189	5
5	181.9	33100	—	—	—	—	—	—	—	9.980	—	.3195	22.0	4.621	7
6	162.0	26250	—	—	—	—	—	—	—	12.58	—	.4028	17.5	4.115	8
7	144.3	20820	—	—	—	—	—	—	—	15.87	—	.5080	13.8	3.665	9
8	128.5	16510	7.6	—	7.4	7.1	—	—	—	20.01	19.6	.6405	11.0	3.264	10
9	114.4	13090	8.6	—	8.2	7.8	—	—	—	25.23	24.6	.8077	8.7	2.906	11
10	101.9	10380	9.6	—	9.3	8.9	87.5	84.8	80.0	31.82	30.9	1.018	6.9	2.588	12
11	90.74	8234	10.7	—	10.3	9.8	110	105	97.5	40.12	38.8	1.284	5.5	2.305	13
12	80.81	6530	12.0	—	11.5	10.9	136	131	121	50.59	48.9	1.619	4.4	2.053	14
13	71.96	5178	13.5	—	12.8	12.0	170	162	150	63.80	61.5	2.042	3.5	1.828	15
14	64.08	4107	15.0	—	14.2	13.8	211	198	183	80.44	77.3	2.575	2.7	1.628	16
15	57.07	3257	16.8	—	15.8	14.7	262	250	223	101.4	97.3	3.247	2.2	1.450	17
16	50.82	2583	18.9	18.9	17.9	16.4	321	306	271	127.9	119	4.094	1.7	1.291	18
17	45.26	2048	21.2	21.2	19.9	18.1	397	372	329	161.3	150	5.163	1.3	1.150	18
18	40.30	1624	23.6	23.6	22.0	19.8	493	454	399	203.4	188	6.510	1.1	1.024	19
19	35.89	1288	26.4	26.4	24.4	21.8	592	553	479	256.5	237	8.210	.86	.9116	20
20	31.96	1022	29.4	29.4	27.0	23.8	775	725	625	323.4	298	10.35	.68	.8118	21
21	28.46	810.1	33.1	32.7	29.8	26.0	940	895	754	407.8	370	13.05	.54	.7230	22
22	25.35	642.4	37.0	36.5	34.1	30.0	1150	1070	910	514.2	461	16.46	.43	.6438	23
23	22.57	509.5	41.3	40.6	37.6	31.6	1400	1300	1080	648.4	584	20.76	.34	.5733	24
24	20.10	404.0	46.3	45.3	41.5	35.6	1700	1570	1260	817.7	745	26.17	.27	.5106	25
25	17.90	320.4	51.7	50.4	45.6	38.6	2060	1910	1510	1031	903	33.00	.21	.4547	26
26	15.94	254.1	58.0	55.6	50.2	41.8	2500	2300	1750	1300	1118	41.62	.17	.4049	27
27	14.20	201.5	64.9	61.5	55.0	45.0	3030	2780	2020	1639	1422	52.48	.13	.3606	29
28	12.64	159.8	72.7	68.6	60.2	48.5	3670	3350	2310	2067	1759	66.17	.11	.3211	30
29	11.26	126.7	81.6	74.8	65.4	51.8	4300	3900	2700	2607	2207	83.44	.084	.2859	31
30	10.03	100.5	90.5	83.3	71.5	55.5	5040	4660	3020	3287	2534	105.2	.067	.2546	33
31	8.928	79.70	101	92.0	77.5	59.2	5920	5280	—	4145	2768	132.7	.053	.2268	34
32	7.950	63.21	113	101	83.6	62.6	7060	6250	—	5227	3137	167.3	.042	.2019	36
33	7.080	50.13	127	110	90.3	66.3	8120	7360	—	6591	4697	211.0	.033	.1798	37
34	6.305	39.75	143	120	97.0	70.0	9600	8310	—	8310	6168	266.0	.026	.1601	38
35	5.615	31.52	158	132	104	73.5	10900	8700	—	10480	6737	335.0	.021	.1426	38-39
36	5.000	25.00	175	143	111	77.0	12200	10700	—	13210	7877	423.0	.017	.1270	39-40
37	4.453	19.83	198	154	118	80.3	—	—	—	16660	9309	533.4	.013	.1131	41
38	3.965	15.72	224	166	126	83.6	—	—	—	21010	10666	672.6	.010	.1007	42
39	3.531	12.47	248	181	133	86.6	—	—	—	26500	11907	848.1	.008	.0897	43
40	3.145	9.88	282	194	140	89.7	—	—	—	33410	14222	1069	.006	.0799	44

<sup>1</sup> A mil is 1/1000 (one-thousandth) of an inch.

<sup>2</sup> The figures given are approximate only, since the thickness of the insulation varies with different manufacturers.

<sup>3</sup> The current-carrying capacity at 1000 C.M. per ampere is equal to the circular-mil area (Column 3) divided by 1000.

STANDARD METAL GAUGES			
Gauge No.	American or B. & S. <sup>1</sup>	U. S. Standard <sup>2</sup>	Birmingham or Stubs <sup>3</sup>
1	.2893	.28125	.300
2	.2576	.265625	.284
3	.2294	.25	.259
4	.2043	.234375	.238
5	.1819	.21875	.220
6	.1620	.203125	.203
7	.1443	.1875	.180
8	.1285	.171875	.165
9	.1144	.15625	.148
10	.1019	.140625	.134
11	.09074	.125	.120
12	.08081	.109375	.109
13	.07196	.09375	.095
14	.06408	.078125	.083
15	.05707	.0703125	.072
16	.05082	.0625	.065
17	.04526	.05625	.058
18	.04030	.05	.049
19	.03589	.04375	.042
20	.03196	.0375	.035
21	.02846	.034375	.032
22	.02535	.03125	.028
23	.02257	.028125	.025
24	.02010	.025	.022
25	.01790	.021875	.020
26	.01594	.01875	.018
27	.01420	.0171875	.016
28	.01264	.015625	.014
29	.01126	.0140625	.013
30	.01003	.0125	.012
31	.008928	.0109375	.010
32	.007950	.01015625	.009
33	.007080	.009375	.008
34	.006350	.00859375	.007
35	.005615	.0078125	.005
36	.005000	.00703125	.004
37	.004453	.006640626	.....
38	.003965	.00625	.....
39	.003531	.....	.....
40	.003145	.....	.....

<sup>1</sup> Used for aluminum, copper, brass and nonferrous alloy sheets, wire and rods.  
<sup>2</sup> Used for iron, steel, nickel and ferrous alloy sheets, wire and rods.  
<sup>3</sup> Used for seamless tubes; also by some manufacturers for copper and brass.

MUSICAL SCALE				
Approximate frequencies of notes of the musical scale, based on A-440.				
(Bottom Octave)				
Note	Frequency		Note	Frequency
A-1	28	Middle C —	C3	262
A#-1	29		C#3	277
B-1	31		D3	294
Co	33		D#3	311
C#o	35		E3	330
Do	37		F3	349
D#o	39		F#3	370
Eo	41		G3	392
Fo	44		G#3	415
F#o	46		A3	440
Go	49		A#3	466
G#o	52		B3	494
Ao	55		C4	523
A#o	58		C#4	554
Bo	62		D4	587
C1	65		D#4	622
C#1	69		E4	659
D1	73		F4	698
D#1	78		F#4	740
E1	82		G4	784
F1	87		G#4	831
F#1	93		A4	880
G1	98		A#4	932
G#1	104		B4	988
A1	110		C5	1047
A#1	117		C#5	1109
B1	123		D5	1175
C2	131		D#5	1245
C#2	139		E5	1319
D2	147		F5	1397
D#2	156		F#5	1480
E2	165		G5	1568
F2	175		G#5	1661
F#2	185		A5	1760
G2	196		A#5	1865
G#2	208		B5	1976
A2	220		C6	2093
A#2	233		C#6	2217
B2	247		D6	2349
			D#6	2489
			E6	2637
			F6	2794
			F#6	2960
			G6	3136
			G#6	3322
			A6	3520
			A#6	3729
			B6	3951
			C7	4186

LETTER SYMBOLS FOR VACUUM-TUBE NOTATION			
Grid potential	$E_g, e_g$	Mutual conductance	$g_m$
Grid current	$I_g, i_g$	Amplification factor	$\mu$
Grid conductance	$g_g$	Filament terminal voltage	$E_f$
Grid resistance	$r_g$	Filament current	$I_f$
Grid bias voltage	$E_c$	Grid-plate capacitance	$C_{gp}$
Plate potential	$E_p, e_p$	Grid-cathode capacitance	$C_{gk}$
Plate current	$I_p, I_p, i_p$	Plate-cathode capacitance	$C_{pk}$
Plate conductance	$g_p$	Grid capacitance (input)	$C_g$
Plate resistance	$r_p$	Plate capacitance (output)	$C_p$
Plate supply voltage	$E_b$		
Cathode current	$I_c$		
Emission current	$I_e$		

NOTE. — Small letters refer to instantaneous values.

GREEK ALPHABET		
Greek Letter	Greek Name	English Equivalent
A α	Alpha	a
B β	Beta	b
Γ γ	Gamma	g
Δ δ	Delta	d
E ε	Epsilon	e
Z ζ	Zeta	z
Η η	Eta	é
Θ θ	Theta	th
I ι	Iota	i
K κ	Kappa	k
Λ λ	Lambda	l
M μ	Mu	m
N ν	Nu	n
Ξ ξ	Xi	x
O ο	Omicron	ō
Π π	Pi	p
P ρ	Rho	r
Σ σ	Sigma	s
T τ	Tau	t
T υ	Upsilon	u
Φ φ	Phi	ph
X χ	Chi	ch
Ψ ψ	Psi	ps
Ω ω	Omega	ō

THE R-S-T SYSTEM
READABILITY
1 — Unreadable.
2 — Barely readable, occasional words distinguishable.
3 — Readable with considerable difficulty.
4 — Readable with practically no difficulty.
5 — Perfectly readable.
SIGNAL STRENGTH
1 — Faint signals, barely perceptible.
2 — Very weak signals.
3 — Weak signals.
4 — Fair signals.
5 — Fairly good signals.
6 — Good signals.
7 — Moderately strong signals.
8 — Strong signals.
9 — Extremely strong signals.
STONE
1 — Extremely rough hissing note.
2 — Very rough a.c. note, no trace of musicality.
3 — Rough low-pitched a.c. note, slightly musical.
4 — Rather rough a.c. note, moderately musical.
5 — Musically-modulated note.
6 — Modulated note, slight trace of whistle.
7 — Near d.c. note, smooth ripple.
8 — Good d.c. note, just a trace of ripple.
9 — Purest d.c. note.
<p>If the signal has the characteristic steadiness of crystal control, add the letter X to the RST report. If there is a chirp, the letter C may be added to so indicate. Similarly for a click, add K. The above reporting system is used on both c.w. and voice, leaving out the "tone" report on voice.</p>

Q SIGNALS

Given below are a number of Q signals whose meanings most often need to be expressed with brevity and clearness in amateur work. (Q abbreviations take the form of questions only when each is sent followed by a question mark.)

- QAV Are you calling me? I am calling. . . .
  - QRG Will you tell me my exact frequency in kilocycles? Your frequency is. . . . kc.
  - QRH Does my frequency vary? Your frequency varies.
  - QRI Is my note good? Your note varies.
  - QRJ Are you receiving me badly? Are my signals weak? I cannot receive you. Your signals are too weak.
  - QRK What is the readability of my signals (1 to 5)? The readability of your signals is. . . (1 to 5).
  - QRL Are you busy? I am busy or busy with ( . . . . . )
  - QRM Are you being interfered with? I am interfered with.
  - QRN Are you troubled by atmospherics? I am being troubled by atmospherics.
  - QRQ Shall I send faster? Send faster ( . . . . . words per min.).
  - QRS Shall I send more slowly? Send more slowly ( . . . . . w.p.m.)
  - QRT Shall I stop sending? Stop sending.
  - QRU Have you anything for me? I have nothing for you.
  - QRV Are you ready? I am ready.
  - QRW Shall I tell . . . . . that you are calling him? Please tell. . . . . that I am calling him.
  - QRX Shall I wait? When will you call me again? Wait (or wait until I have finished with. . . . .). I will call you at. . . . . o'clock (or immediately).
  - QRZ By whom am I being called? You are being called by . . . . .
  - QSA What is the strength of my signals (1 to 5)? The strength of your signals is. . . . . (1 to 5).
  - QSB Does the strength of my signals vary? The strength of your signals varies.
  - QSD Is my keying correct? Are my signals distinct? Your keying is incorrect; your signals are bad.
  - QSG Shall I send. . . . . telegrams (or one) at a time? Send. . . . . telegrams at a time.
  - QSL Can you give me acknowledgment of receipt? I give you acknowledgment of receipt.
  - QSM Shall I repeat the last telegram I sent you? Repeat the last telegram you sent me.
  - QSO Can you communicate with. . . . . direct (or through. . . . .)? I can communicate with . . . . . direct (or through. . . . .).
  - QSP Will you relay to. . . . .? I will relay to. . . . .
  - QSV Shall I send a series of VVV. . . . .? Send a series of VVV.
  - QSW Will you send on. . . . . kc., etc.? I will send on . . . . . kc., etc.
  - QSX Will you listen for. . . . . (call sign) on. . . . . kc.? I am listening for. . . . . on. . . . . kc.
  - QSY Shall I change to. . . . . kilocycles without changing the type of wave? Change to. . . . . kc. without changing type of wave.
  - QSZ Shall I send each word or group twice? Send each word or group twice.
  - QTA Shall I cancel nr. . . . . as if it had not been sent? Cancel nr. . . . . as if it had not been sent.
  - QTB Do you agree with my number of words? I do not agree with your number of words; I will repeat the first letter of each word and the first figure of each number.
  - QTC How many telegrams have you to send? I have. . . . . telegrams for you or for. . . . .
  - QTH What is your position (location)? My location is. . . . . (by any indication.)
  - QTR What is the exact time? The time is. . . . .
- Special abbreviations adopted by ARRL:
- QST General call preceding a message addressed to all amateurs and ARRL members. This is in effect "CQ ARRL."
  - QRR Official ARRL "land SOS." A distress call for emergency use only by a station in an emergency situation.

ABBREVIATIONS FOR C.W. WORK

Abbreviations help to cut down unnecessary transmission. However, make it a rule not to abbreviate unnecessarily when working an operator of unknown experience.

AA	All after	NW	Now; I resume transmission
AB	All before	OB	Old boy
ABT	About	OM	Old man
ADR	Address	OP-OPR	Operator
AGN	Again	OSC	Oscillator
ANT	Antenna	OT	Old timer; old top
BCI	Broadcast interference	PBL	Preamble
BCL	Broadcast listener	PSE-PLS	Please
BK	Break; break me; break in	PWR	Power
BN	All between; been	PX	Press
B4	Before	R	Received solid; all right; OK; are
C	Yes	RAC	Rectified alternating current
CFM	Confirm; I confirm	RCD	Received
CK	Check	REF	Refer to; referring to; reference
CL	I am closing my station; call	RPT	Repeat; I repeat
CLD-CLG	Called; calling	SED	Said
CUD	Could	SEZ	Says
CUL	See you later	SIG	Signature; signal
CUM	Come	SINE	Operator's personal initials or nickname
CW	Continuous wave	SKED	Schedule
DLD-DLVD	Delivered	SRI	Sorry
DX	Distance	SVC	Service; prefix to service message
ECO	Electron-coupled oscillator	TFC	Traffic
FB	Fine business; excellent	TMW	Tomorrow
GA	Go ahead (or resume sending)	TNX-TKS	Thanks
GB	Good-by	TT	That
GBA	Give better address	TU	Thank you
GE	Good evening	TXT	Text
GG	Going	UR-URS	Your; you're; yours
GM	Good morning	VFO	Variable-frequency oscillator
GN	Good night	VY	Very
GND	Ground	WA	Word after
GUD	Good	WB	Word before
HI	The telegraphic laugh; high	WD-WDS	Word; words
HR	Here; hear	WKD-WKG	Worked; working
HV	Have	WL	Well; will
HW	How	WUD	Would
LID	A poor operator	WX	Weather
MILS	Milliamperes	XMTR	Transmitter
MSG	Message; prefix to radiogram	XTAL	Crystal
N	No	YF (XYL)	Wife
ND	Nothing doing	YL	Young lady
NIL	Nothing; I have nothing for you	73	Best regards
NR	Number	88	Love and kisses

W PREFIXES BY STATES

Alabama	W4	Nebraska	W0
Arizona	W7	Nevada	W7
Arkansas	W5	New Hampshire	W1
California	W6	New Jersey	W2
Colorado	W0	New Mexico	W5
Connecticut	W1	New York	W2
Delaware	W3	North Carolina	W4
District of Columbia	W3	North Dakota	W0
Florida	W4	Ohio	W8
Georgia	W4	Oklahoma	W5
Idaho	W7	Oregon	W7
Illinois	W9	Pennsylvania	W3
Indiana	W9	Rhode Island	W1
Iowa	W0	South Carolina	W4
Kansas	W0	South Dakota	W0
Kentucky	W4	Tennessee	W4
Louisiana	W5	Texas	W5
Maine	W1	Utah	W7
Maryland	W3	Vermont	W1
Massachusetts	W1	Virginia	W4
Michigan	W8	Washington	W7
Minnesota	W0	West Virginia	W8
Mississippi	W5	Wisconsin	W9
Missouri	W0	Wyoming	W7
Montana	W7		



## INTERNATIONAL PREFIXES

Below is the list of prefixes assigned to the countries of the world by the 1947 International Radio Conference at Atlantic City. While not yet officially in force, it is reproduced here because it embodies the essentials of the present (Cairo) table as well as contains new assignments which will undoubtedly see use in the future.

AAA-ALZ	United States of America	RAA-RZZ	Union of Soviet Socialist Republics
AMA-AOZ	(Not allocated)	SAA-SMZ	Sweden
APA-ASZ	Pakistan	SNA-SRZ	Poland
ATA-AWZ	India	SSA-SUZ	Egypt
AXA-AXZ	Commonwealth of Australia	SVA-SZZ	Greece
AYA-AZZ	Argentina Republic	TAA-TCZ	Turkey
BAA-BZZ	China	TDA-TDZ	Guatemala
CAA-CEZ	Chile	TEA-TEZ	Costa Rica
CFA-CKZ	Canada	TFA-TFZ	Iceland
CLA-CMZ	Cuba	TGA-TGZ	Guatemala
CNA-CNZ	Morocco	THA-THZ	France and Colonies and Protectorates
COA-COZ	Cuba	TIA-TIZ	Costa Rica
CPA-CPZ	Bolivia	TJA-TZZ	France and Colonies and Protectorates
CQA-CRZ	Portuguese Colonies	UAA-UQZ	Union of Soviet Socialist Republics
CSA-CUZ	Portugal	URA-UTZ	Ukrainian Soviet Socialist Republic
CVA-CXZ	Uruguay	UUA-UZZ	Union of Soviet Socialist Republics
CYA-CZZ	Canada	VAA-VGZ	Canada
DAA-DMZ	Germany	VHA-VNZ	Commonwealth of Australia
DNA-DQZ	Belgian Congo	VOA-VOZ	Newfoundland
DRA-DTZ	Bielorussian Soviet Socialist Republic	VPA-VSZ	British Colonies and Protectorates
DUA-DZZ	Republic of the Philippines	VTA-VWZ	India
EAA-EHZ	Spain	VXA-VYZ	Canada
EIA-EJZ	Ireland	VZA-VZZ	Commonwealth of Australia
EKA-EKZ	Union of Soviet Socialist Republics	WAA-WZZ	United States of America
ELA-ELZ	Republic of Liberia	XAA-XIZ	Mexico
EMA-EOZ	Union of Soviet Socialist Republics	XJA-XOZ	Canada
EPA-EQZ	Iran	XPA-XPZ	Denmark
ERA-ERZ	Union of Soviet Socialist Republics	XQA-XRZ	Chile
ESA-ESZ	Estonia	XSA-XSZ	China
ETA-ETZ	Ethiopia	XTA-XWZ	France and Colonies and Protectorates
EUA-EZZ	Union of Soviet Socialist Republics	XXA-XXZ	Portuguese Colonies
FAA-FZZ	France and Colonies and Protectorates	XYA-XZZ	Burma
GAA-GZZ	Great Britain	YAA-YAZ	Afghanistan
HAA-HAZ	Hungary	YBA-YHZ	Netherlands Indies
HBA-HBZ	Switzerland	YIA-YIZ	Iraq
HCA-HDZ	Ecuador	YJA-YJZ	New Hebrides
HEA-HEZ	Switzerland	YKA-YKZ	Syria
HFA-HFZ	Poland	YLA-YLZ	Latvia
HGA-HGZ	Hungary	YMA-YMZ	Turkey
HHA-HHZ	Republic of Haiti	YNA-YNZ	Nicaragua
HIA-HIZ	Dominican Republic	YOA-YRZ	Rumania
HJA-HKZ	Republic of Colombia	YSA-YSZ	Republic of El Salvador
HLA-HMZ	Korea	YTA-YUZ	Yugoslavia
HNA-HNZ	Iraq	YVA-YYZ	Venezuela
HOA-HPZ	Republic of Panama	YZA-YZZ	Yugoslavia
HQA-HRZ	Republic of Honduras	ZAA-ZAZ	Albania
HSA-HSZ	Siam	ZBA-ZBZ	British Colonies and Protectorates
HTA-HTZ	Nicaragua	ZKA-ZMZ	New Zealand
HUA-HUZ	Republic of El Salvador	ZNA-ZOZ	British Colonies and Protectorates
HVA-HVZ	Vatican City State	ZPA-ZPZ	Paraguay
HWA-HYZ	France and Colonies and Protectorates	ZQA-ZQZ	British Colonies and Protectorates
HZA-HZZ	Kingdom of Saudi Arabia	ZRA-ZUZ	Union of South Africa
IAA-IZZ	Italy and Colonies	ZVA-ZZZ	Brazil
JAA-JSZ	Japan	2AA-2ZZ	Great Britain
JTA-JVZ	Outer Mongolia Peoples Republic	3AA-3AZ	Principality of Monaco
JWA-JXZ	Norway	3BA-3FZ	Canada
JYA-JZZ	(Not allocated)	3GA-3GZ	Chile
KAA-KZZ	United States of America	3HA-3UZ	China
LAA-LNZ	Norway	3VA-3VZ	France and Colonies and Protectorates
LOA-LWZ	Argentina Republic	3WA-3XZ	(Not allocated)
LXA-LXZ	Luxemburg	3YA-3YZ	Norway
LYA-LYZ	Lithuania	3ZA-3ZZ	Poland
LZA-LZZ	Bulgaria	4AA-4CZ	Mexico
MAA-MZZ	Great Britain	4DA-4IZ	Republic of the Philippines
NAA-NZZ	United States of America	4JA-4LZ	Union of Soviet Socialist Republics
OAA-OCZ	Peru	4MA-4MZ	Venezuela
ODA-ODZ	Republic of Lebanon	4NA-4NZ	Yugoslavia
OEA-OEZ	Austria	4PA-4SZ	British Colonies and Protectorates
OFA-OJZ	Finland	4TA-4TZ	Peru
OKA-OMZ	Czechoslovakia	4UA-4UZ	United Nations
ONA-OTZ	Belgium and Colonies	4VA-4VZ	Republic of Haiti
OUA-OZZ	Denmark	4WA-4WZ	Yemen
PAA-PIZ	Netherlands	4XA-4ZZ	(Not allocated)
PJA-PJZ	Curacao	5AA-5ZZ	(Not allocated)
PKA-POZ	Netherlands Indies	6AA-6ZZ	(Not allocated)
PPA-PYZ	Brazil	7AA-7ZZ	(Not allocated)
PZA-PZZ	Surinam	8AA-8ZZ	(Not allocated)
QAA-QZZ	(Service abbreviations)	9AA-9ZZ	(Not allocated)

## A.R.R.L. COUNTRIES LIST

Official List for ARRL DX Contest and the Postwar DXCC

Aden and Socotra Island	VS9	Germany	D	Philippine Islands	KA
Afghanistan	YA	Gibraltar	ZB2	Phoenix Islands (British)	
Alaska	KL7	Gilbert & Ellice Islands and Ocean Island	VR1	Pitcairn Island	VR6
Albania	ZA	Goa (Portuguese India)	CR8	Poland	SP
Aldabra Islands		Gold Coast (and British Togoland)	ZD4	Portugal	CT
Algeria	FA	Greece	SV	Principe and Sao Thome Islands	
Andaman Ids. and Nicobar Ids.		Greenland	OX	Puerto Rico	KP4
Andorra	PX	Guadeloupe	FG8	Rhunion Island	FR8
Anglo-Egyptian Sudan	ST	Guantanamo Bay	NY4	Rhodesia, Northern	VQ2
Angola	CR6	Guatemala	TG	Rhodesia, Southern	ZE
Argentina	LU	Guiana, British	VP3	Rio de Oro	
Ascension Island	ZD8	Guiana, Netherlands (Surinam)	PZ	Roumania	YR
Australia (including Tasmania)	VK	Guiana, French, and Inini	FY8	Ryukyu Islands (e.g., Okinawa)	
Austria	OE	Guinea, Portuguese	CR5	St. Helena	ZD7
Azores Islands	CT2	Guinea, Spanish	HH	Salvador	YS
Bahama Islands	VP7	Haiti	HR	Samoa, American	KS6
Bahrein Island	VU7	Hawaiian Islands	KH6	Samoa, Western	ZM
Baker Island, Howland Island and Am. Phoenix Islands	KB6	Honduras	HR	Sarawak	VS5
Balearic Islands	EA6	Honduras, British	VP1	Sardinia	
Barbados	VP6	Hong Kong	VS6	Saudi Arabia (Hedjaz and Nejd)	HZ
Basutoland	ZS4	Hungary	HA	Scotland	GM
Bechuanaland		Iceland	TF	Seychelles	VQ9
Belgian Congo	OQ	India	VU	Siam	HS
Belgium	ON	Iran	EP-EQ	Sierra Leone	ZD1
Bermuda Islands	VP9	Iraq	YI	Sikkim	(AC3)
Bhutan		Ireland, Northern	GI	Solomon Islands	VR4
Bolivia	CP	Isle of Man	GD	Somaliand, British	VQ6
Bonin Islands and Volcano Islands (e.g., Iwo Jima)	VS4	Italy	I	Somaliand, French	FL8
Borneo, British North	PK5	Jamaica	VP5	Somaliand, Italian	
Borneo, Netherlands	PK4	Jan Mayen Island		South Georgia	VP8
Brazil	PY	Japan	J	South Orkney Islands	VP8
Brunei	VS5	Jarvis Island, Palmyra group (Christmas Island)	KP6	South Sandwich Islands	VP8
Bulgaria	LZ	Java	PK	South Shetland Islands	VP8
Burma	XZ	Johnston Island	KJ6	Southwest Africa	ZS3
Cameroons, French	FE8	Kenya	VQ4	Soviet Union:	
Canada	VE	Kerguelen Islands		European Russian Socialist Federated Soviet Republic	UA1-3-4-6
Canal Zone	KZ5	Korea		Asiatic Russian S.F.S.R.	UA9-0
Canary Islands	EA8	Kuwait		Ukraine	UB5
Cape Verde Islands	CR4	Laccadive Islands	VU4	White Russian Soviet Socialist Republic	UC5
Caroline Islands	VP5	Leeward Islands	VP2	Azerbaijan	UD6
Cayman Islands	VP5	Liberia	EL	Georgia	UD6
Celebes and Molucca Islands	PK6	Libya	(LI)	Armenia	UG6
Ceylon	VS7	Liechtenstein	HE1	Turkoman	UH8
Chagos Islands	VQ8	Little America	KC4	Tadzhik	UI8
Channel Islands	GC	Luxembourg	LX	Kazakh	UJ8
Chile	CE	Macau	CR9	Kirghiz	UL7
China	XU, C	Madagascar	FB8	Karelo-Finnish Republic	UN1
Christmas Island	ZC3	Madeira Islands	CT3	Moldavia	UO5
Clipperton Island		Malaya	VS1, VS2	Lithuania	UP
Cocos Island	TI	Maldive Islands		Latvia	UQ
Cocos Islands	ZC2	Malta	ZB1	Estonia	UR
Colombia	HK	Manchuria		Sumatra	EA
Comoro Islands		Marianas Islands (Guam)	KG6	Svalbard (Spitzbergen)	PK4
Cook Islands	ZK1	Marshall Islands		Swan Island	KS4
Corsica		Martinique	FM8	Swaziland	
Costa Rica	TI	Mauritius	VQ8	Sweden	SM
Crete	SV	Mexico	XE	Switzerland	HB
Cuba	CM-CO	Midway Island	KM6	Syria	(AR)
Cyprus	ZC4	Miquelon and St. Pierre Islands	FP8	Tanganyika Territory	VQ3
Czechoslovakia	OK	Monaco		Tangier Zone	EK
Denmark	OZ	Mongolia		Tannu Tuva	
Dodecanese Islands (e.g., Rhodes)	SV5	Morocco, French	CN	Tibet	AC4
Dominican Republic	HI	Morocco, Spanish	EA9	Timor, Portuguese	CR10
Easter Island		Mozambique	CR7	Togoland, French	FD8
Ecuador	HC	Nepal		Tokelau (Union) Islands	
Egypt	SU	Netherlands	PA	Tonga (Friendly) Islands	VR5
Eire (Irish Free State)	EI	Netherlands West Indies	PJ	Trans-Jordan	ZC1
England	G	New Caledonia	FK8	Trieste	
Eritrea	I6	Newfoundland and Labrador	VO	Trinidad and Tobago	VP4
Ethiopia	ET	New Guinea, Netherlands	PK6	Tristan da Cunha and Gough Island	ZD9
Faeroes, The	OY	New Guinea, Territory of	VK9	Tunisia	FT4
Falkland Islands	VP8	New Hebrides	FU8, YJ	Turkey	TA
Fanning Island (Christmas Island)	VR3	New Zealand	ZL	Turks and Caicos Islands	VP5
Fiji Islands	VR2	Nicaragua	YN	Uganda	VQ5
Finland	OH	Nigeria	ZD2	Union of South Africa	ZS
Formosa (Taiwan)		Niue	ZK2	United States of America	W, K
France	F	Norway	LA	Uruguay	CX
French Equatorial Africa	FO8	Nyasaland	ZD6	Venezuela	YV
French India	FN	Oman		Virgin Islands	KV4
French Indo-China	F18	Palau (Pelew) Islands		Wake Island	KW6
French Oceania (e.g., Tahiti)	FO8	Palestine	ZC6	Wales	GW
French West Africa	FF8	Panama	HP	Windward Islands	VP2
Fridtjof Nansen Land (Franz Josef Land)		Papua Territory	VK4	Wrangel Islands	
Galapagos Islands		Paraguay	ZP	Yemen	
Gambia	ZD3	Peru	OA	Yugoslavia	YT-YU
				Zanzibar	VQ1

INTERNATIONAL AMATEUR PREFIXES

To make possible identification of calls heard on the air, the international telecommunications conferences assign to each nation certain alphabetical blocks, from which all classes of stations are assigned prefixes. The following prefixes are used by amateurs:

AC3	Sikkim	KP6	Palmyra Group, Jarvis Island	VP3	British Guiana
AC4	Tibet	KS0	American Samoa	VP4	Trinidad & Tobago
AR	Syria	KS4	Swan Island	VP5	Jamaica & Cayman Islands
C	China (unofficial)	KV4	Virgin Islands	VP5	Turks & Caicos Islands
CE	Chile	KW6	Wake Island	VP6	Barbados
CM, CO	Cuba	KZ5	Canal Zone	VP7	Bahama Islands
CN	Morocco, French	LA	Norway	VP8	Falkland Islands
CP	Bolivia	LI	Libya	VP8	South Georgia
CR4	Cape Verde Islands	LU	Argentina	VP8	South Orkney Islands
CR5	Guinea, Portuguese	LX	Luxembourg	VP8	South Sandwich Islands
CR6	Angola	LZ	Bulgaria	VP8	South Shetland Islands
CR7	Mozambique	M89	Austria	VP9	Bermuda Islands
CR8	Goa (Portuguese India)	MD1	Cyrenaica	VQ1	Zanzibar
CR9	Macao	MD2	Tripolitania	VQ2	Northern Rhodesia
CR10	Timor, Portuguese	MD3	Eritrea	VQ3	Tanganyika Territory
CT1	Portugal	MD4	Somalia	VQ4	Kenya
CT2	Azores Islands	MD5	Suez Canal Zone	VQ5	Uganda
CT3	Madeira Islands	MD6	Iraq	VQ6	Somaliland, British
CX	Uruguay	MX	Manchukuo (Manchuria)	VQ8	Mauritius & Chagos Islands
D	Germany	NY4	Guantanamo Bay	VQ9	Seychelles
EA	Spain	OA	Peru	VR1	Gilbert & Ellice Islands & Ocean Island
EA6	Balearic Islands	OE	Austria	VR2	Fiji Islands
EA8	Canary Islands	OH	Finland	VR3	Fanning Island (Christmas Island)
EA9	Morocco, Spanish	OK	Czechoslovakia	VR4	Solomon Islands
EL	Eire (Irish Free State)	ON	Belgium	VR5	Tonga (Friendly) Islands
EL	Tangier Zone	OQ	Belgian Congo	VR6	Pitcairn Island
EL	Liberia	OX	Greenland	VS1	Strait Settlements
EP, EQ	Iran (Persia)	OY	Faeroes, The	VS2	Federated Malay States
ET	Ethiopia	OZ	Denmark	VS3	Non-Federated Malay States
FA	France	PJ	Netherlands	VS4	Borneo, British North
FA	Algeria	PJ	Netherlands West Indies	VS5	Sarawak, Brunei
FBS	Madagascar	PK1, 2, 3	Java	VS6	Hong Kong
FD8	Togoland, French	PK4	Sumatra	VS7	Ceylon
FES	Cameroons, French	PK5	Borneo, Netherlands	VS8 (VU7)	Bahrain Islands
F8	French West Africa	PK6	Celebes & Molucca Islands	VS9	Maldiv Islands
FG8	Guadeloupe	PK6	New Guinea, Netherlands	VU	India
F18	French Indo-China	PY	Andorra	VU4	Laccadive Islands
FK8	New Caledonia	PZ	Guiana, Netherlands (e.g., Surinam)	VU7	Bahrein Islands
FL8	Somaliland, French	SM	Sweden	W	United States of America
FM8	Martinique	SP	Poland	XA*	
FN	French India	ST	Anglo-Egyptian Sudan	XE	Mexico
FO8	French Oceania (e.g., Tahiti)	SV	Egypt	XU	China
FR8	St. Pierre & Miquelon Islands	SV	Greece	XZ	Burma
FR8	French Equatorial Africa	SV5	Dodecanese (e.g., Rhodes)	YA	Afghanistan
FT4	Reunion Island	TA	Turkey	YI	Iraq
FU8	Tunisia	TB	Iceland	YN	Nicaragua
FY8	New Hebrides	TG	Guatemala	YR	Roumania
G	Guiana, French & Inini	TI	Costa Rica	YS	Salvador
GC	England	TI	Cocos Island	YT, YU	Yugoslavia
GD	Channel Islands	UA1, 3, 4, 6	European Russian Socialist Federated Soviet Republic	YV	Venezuela
GI	Ile of Man	UA9, Ø	Asiatic Russian S.F.S.R.	ZA	Albania
GM	Ireland, Northern	UB5	Ukraine	ZB1	Malta
GW	Scotland	UC	White Russian Soviet Socialist Republic	ZB2	Gibraltar
HA	Wales	UD6	Azerbaijan	ZC1	Trans-Jordan
HB	Hungary	UF6	Georgia	ZC2	Cocos Islands
HC	Switzerland	UG6	Armenia	ZC3	Christmas Island
HE1	Ecuador	UH8	Turkoman	ZC4	Cyprus
HH	Liechtenstein	UI8	Uzbek	ZC6	Palestine
HI	Haiti	UJ8	Tadzhik	ZD1	Sierra Leone
HK	Dominican Republic	UL7	Kazakh	ZD2	Nigeria
HL	Colombia	UM8	Kirghiz	ZD3	Gambia
HP	Panama	UN1	Karelo-Finnish Republic	ZD4	Togoland, Gold Coast
HR	Honduras	UO5	Moldavia	ZD6	Nyasaland
HS	Siam	UP	Lithuania	ZD7	St. Helena
HZ	Saudi Arabia (Hedjaz & Nejd)	UQ	Latvia	ZD8	Ascension Island
I	Italy	UR	Estonia	ZD9	Tristan da Cunha & Gough Island
I6	Eritrea	VE	Canada	ZE1	Southern Rhodesia
J	Japan	VK	Australia (including Tasmania)	ZK1	Cook Islands
J9	Ryukyu Islands (e.g., Okinawa)	VK4	Papua Territory	ZK2	Niue
K	United States of America	VK9	New Guinea, Territory of	ZL	New Zealand
KA	Philippine Islands	VO	Newfoundland & Labrador	ZM	British Samoa
KB6	Baker, Howland & American Phoenix Islands	VP1	British Honduras	ZP	Paraguay
KC4	Little America	VP2	Leeward & Windward Islands	ZS1, 2, 4, 5, 6	Union of South Africa
KG6	Guam, Saipan, Tinian			ZS3	Southwest Africa
KH6	Hawaiian Islands			ZS4	Basutoland
KJ6	Johnston Islands			ZS6	Bechuanaland
KL7	Alaska				
KM6	Midway Islands				
KP4	Puerto Rico				

\* In addition to call signs starting with the prefixes listed in this tabulation, four-letter calls beginning with the letters XA have been assigned for use in the Mediterranean area by amateurs in the British and American military services.

# Vacuum-Tube Data

For the convenience of the designer, the receiving-type tubes listed in this chapter are grouped by filament voltages and construction types (glass, metal, miniature, etc.). For example, all 6.3-volt metal tubes are listed in Table I, all lock-in base tubes are in Table III, all miniatures are in Table XI, and so on.

Transmitting tubes are divided into triodes and tetrodes-pentodes, then listed according to rated plate dissipation. This permits direct comparison of ratings of tubes in the same power classification.

For quick reference, all tubes are listed in numerical-alphabetical order in the index beginning on the following page.

### Tube Ratings

Vacuum tubes are designed to be operated within definite maximum (and minimum) ratings. These ratings are the maximum safe operating voltages and currents for the electrodes, based on inherent limiting factors such as permissible cathode temperature, emission, and power dissipation in electrodes.

In the transmitting-tube tables, maximum ratings for electrode voltage, current and dissipation are given separately from the typical operating conditions for the recommended classes of operation. In the receiving-tube tables, because of space limitations, ratings and operating data are combined. Where only one set of operating conditions appears, the positive electrode voltages shown (plate, screen,

etc.) are, in general, also the maximum rated voltages for those electrodes.

For certain air-cooled transmitting tubes, there are two sets of maximum values, one designated as CCS (Continuous Commercial Service) ratings, the other ICAS (Intermittent Commercial and Amateur Service) ratings. Continuous Commercial Service is defined as that type of service in which long tube life and reliability of performance under continuous operating conditions are the prime consideration. Intermittent Commercial and Amateur Service is defined to include the many applications where the transmitter design factors of minimum size, light weight, and maximum power output are more important than long tube life. ICAS ratings are considerably higher than CCS ratings. They permit the handling of greater power, and although such use involves some sacrifice in tube life, the period over which tubes will continue to give satisfactory performance in intermittent service can be extremely long.

### Typical Operating Conditions

The typical operating conditions given for transmitting tubes represent, in general, maximum ICAS ratings where such ratings have been given by the manufacturer. They do not represent the *only* possible method of operation of a particular tube type. Other values of plate voltage, plate current, grid bias, etc., may be used so long as the maximum ratings for a particular voltage or current are not exceeded.

### INDEX TO TUBE TABLES

I — 6.3-Volt Metal Receiving Tubes . . .	572	X — Special Receiving Tubes . . . . .	583
II — 6.3-Volt Glass Tubes with Octal Bases	573	XI — Miniature Receiving Tubes . . . . .	585
III — 7-Volt Lock-In Base Tubes . . . . .	575	XII — Control and Regulator Tubes . . .	587
IV — 6.3-Volt Glass Receiving Tubes . . .	576	XIII — Cathode-Ray Tubes and Kine-	
V — 2.5-Volt Receiving Tubes . . . . .	577	scopes . . . . .	588
VI — 2.0-Volt Battery Receiving Tubes .	578	XIV — Rectifiers . . . . .	590
VII — 2.0-Volt Battery Tubes with Octal		XV — Triode Transmitting Tubes . . . . .	592
Bases . . . . .	579	XVI — Tetrode and Pentode Transmit-	
VIII — 1.5-Volt Battery Tubes . . . . .	579	ting Tubes . . . . .	603
IX — High-Voltage Heater Tubes . . . . .	581		

### BASE TYPE DESIGNATIONS

The type of base used on each tube listed in the tables is indicated in the base column by a letter.

The meaning of each letter is

as follows:

- A = Acorn
- B = Glass button miniature
- J = Jumbo
- L = Lock-in

- M = Medium
- N = None or special type
- O = Octal
- S = Small
- W = Wafer

## INDEX TO VACUUM-TUBE TYPES

For convenience in locating data on specific tube types the index below lists all tubes in numerical-alphabetical order, showing the page number where individual tubes may be found in the classified-data section (pages 572-608) and the identifying base-diagram number in the base-diagram section (pages 565-571).

Type	Page	Base	Type	Page	Base	Type	Page	Base	Type	Page	Base			
J-A	583	4D	2E2E	603	7CK	5R4GY	590	5T	6K5GT	574	5U	7K7	576	8BF
I-A	583	4D	2F30	585	7CC	5RPI	588	14F	6K6G	574	7S	7L7	576	8V
A2	587	5BO	2E30	603	7CC	5T4	590	5T	6K7	572	8K	7N7	576	8AC
A3	587	4AJ	2E32	583	—	5T4	588	Fig. 46	6K8	572	8K	7Q8	576	8AL
A4G	587	4AJ	2E36	583	—	5U4G	590	5T	6L5G	574	6Q	7R7	576	8AE
B2	587	5BO	2E42	583	—	5UPI	589	12E	6L6	572	7AC	787	576	8BE
B3	587	4AJ	2G5	578	6R	5V4G	590	5L	6L6	604	7AC	7T7	576	8V
C3	587	4AJ	2G22	583	—	5W4	590	5T	6L6GX	604	7AC	7V7	576	8V
D3	587	4AJ	2K25	608	Fig. 60	5X3	590	4C	6L7	572	7T	7W7	576	8BJ
A4T	587	4BU	2K28	608	Fig. 61	5X4G	590	5Q	6M6G	574	7S	7X16	576	8BZ
Z4	590	4R	2K33	608	Fig. 62	5Y3G	590	5T	6M7G	574	7R	7Y4	590	5AB
Z4A	591	4R	2K34	608	Fig. 58	5Y4G	590	5Q	6M8GT	574	8AU	7Z4	590	5AB
A3	585	4AP	2K35	608	Fig. 58	5Z3	590	4C	6N4	586	7CA	9AP4	589	6AL
A4F	578	4M	2K41	608	Fig. 59	5Z4	590	5L	6N4	592	7CA	9CP4	589	4AF
A4T	578	4K	2K42	608	Fig. 59	6A3	576	4D	6N5	576	6R	9JP1	589	8BR
A5G	579	6X	2K44	608	Fig. 59	6A4	576	5B	6N6G	574	7AU	10T7	584	4D
A6	578	6L	2K43	608	Fig. 59	6A5	576	6T	6N7	572	8B	10HP4	589	Fig. 48
A7G	579	7Z	2K46	608	Fig. 58	6A6	576	7B	6N7	592	8B	10Y	592	4D
AB5	580	5BF	2K47	608	Fig. 58	6A7	576	7C	6P5GT	574	6Q	11/12	584	4F
B3GT	590	3C	2K47	608	Fig. 58	6A8	572	8A	6P7G	574	7U	12A5	581	7F
B4P	578	4M	28/48	577	5D	6A195	576	6R	6P8G	574	8K	12A6	581	7AC
B5	608	6M	2V3G	590	T-4BC	6A196	573	7AU	6Q35G	587	5A	12A7	581	7K
B7G	580	7Z	2V8	590	—	6A197	572	8N	6Q49	574	8Y	12A7	580	7K
B8GT	580	8AW	2X2	590	4AB	6A198	573	6Q	6Q7	572	7V	12A8G	581	8A
B47	587	—	2X2A	590	4AB	6A199	573	7AU	6R6G	574	6AW	12AHTGT	581	8BE
B48	590	—	2Y2	590	4AB	6AC7	572	8N	6R7	572	7V	12AL5	586	6BT
C5G	590	6X	2Z2	590	4B	6AD5G	573	6Q	6S6GT	574	5AK	12AP4	589	6AL
C5G	590	6X	3A4	585	7BB	6AD6G	573	7AH	6S7	572	7E	12AT6	586	7BT
C7G	579	7Z	3A4	585	7BB	6AD7G	574	8AC	6S8GT	573	8CB	12AU6	586	7CC
C21	587	4Y	3A5	592	7BC	6AE5G	573	6Q	6SA7	572	8R	12AU7	586	9A
D5GP	579	5V	3A8GT	583	8AS	6AE6G	573	7AH	6SB7Y	577	8R	12AU7	592	9A
D9GT	579	5R	3AP1	588	7AN	6AE7GT	574	7AX	6SC7	572	8S	12AW7	586	7CM
D7G	579	7Z	3B5GT	583	7AP	6AE8G	576	6Q	6SD7GT	574	8M	12B6M	581	6Y
D8GT	580	8AJ	3B7	580	7BE	6AE9G	576	7AC	6SE7GT	574	8M	12B7	582	8V
E4G	580	5S	3B24	590	T-4A	6A7G	574	8AC	6SF5	572	8AB	12B7ML	581	8V
E5GP	579	5Y	3B25	590	4P	6A7G5	585	7BD	6SH7	572	7AZ	12B8GT	581	8T
E7G	579	8C	3B26	590	Fig. 31	6AG6G	574	7S	6SK7	572	8BK	12B8A6	586	7CC
F4	578	5K	3BP1	588	14A	6AG7	603	8Y	6SH7L	574	Fig. 44	12B8D6	586	7CH
F5G	579	6X	3CGT	583	7AQ	6AH5G	574	6AP	6SJ7	573	8M	12B8E	586	Fig. 37
F8	578	6W	3C6	583	7BW	6AH6GT	573	6Q	6SJ7Y	573	8M	12B8F	586	Fig. 37
F7GV	579	7AD	3C8	590	Fig. 30	6A195	585	7PM	6SK7	573	8N	12CP4	589	4AF
G4G	580	5S	3C23	587	3G	6A17	572	8M	6SL7GT	574	8BD	12DP4	689	5AN
G5G	579	6X	3C24	593	2D	6AK5	585	7BD	6SN7GT	574	8BD	12E5GT	581	6Q
G6G	580	7AB	3C28	593	Fig. 56	6AK6	586	7BK	6SQ7	573	8Q	12F5GT	581	5M
H4G	579	5B	3C34	593	3G	6AK6	603	7BK	6SR7	573	8Q	12G7G	581	7V
H5G	580	5Z	3C37	603	—	6AL7	573	8Q	6ST7	573	8Q	12H6	581	7Q
H6G	579	6AA	3C40	580	6BB	6AL7G	586	6BT	6ST7	573	8Q	12J6GT	581	6Q
J5G	579	6X	3D23	605	Fig. 54	6AL6G	574	6AM	6SU7GT	574	8BD	12J7GT	581	7R
J6G	579	7AB	3D24	605	T-9	6AL7GT	574	8CH	6SV7	573	7AL	12K7GT	581	7R
L4	585	6AR	3DP1	588	Fig. 49	6AN6	586	7BJ	6SZ7	573	8Q	12K8	581	8K
LA4	580	5AD	3DX3	605	Fig. 40	6AQ5	586	7BZ	6T5	577	6R	12L8GT	581	8BU
LA6	580	7AK	3E22	605	8Y	6AQ5	603	7BZ	6T6M	575	6Z	12M7GT	581	7V
LB4	580	6AD	3E29	605	7BP	6AQ6	586	7BT	6T7	573	7V	12SA8GT	581	Fig. 34
LB6	580	8AX	3EP1	588	11A	6AQ7GT	574	8CK	6U5	577	6R	12SA7	581	8R
LC5	580	7AO	3GP1	588	11A	6AR5	586	6CC	6U6GT	575	7AC	12SC7	581	8S
LC6	580	7AK	3JP1	588	14B	6AR6	574	6BQ	6U7G	575	7R	12SF5	581	6AB
LD5	580	6AX	3K21	608	Fig. 58	6AR7GT	574	8CG	6V6G	573	7AC	12SF7	581	7AZ
LE3	580	4AA	3K22	608	Fig. 58	6AS6	586	7C	6V8GT	603	7AC	12SG7	582	8V
LE5	580	5E	3K23	608	Fig. 59	6AT6	586	7BT	6V7G	575	7V	12SH7	582	8BK
LH4	580	5AG	3K27	608	Fig. 59	6AU6	586	7BK	6W5G	590	6S	12SJT	582	8M
LN5	580	7AO	3K30	608	Fig. 58	6AU6	586	7BK	6W8GT	575	7AC	12SK7	582	8M
N5G	580	5Y	3KP1	588	11M	6BA4G	574	5S	6W7G	575	7R	12L7GT	582	8BD
N6G	580	7AM	3LE4	584	6BA	6B5	576	6AN	6X4	590	7CF	12N7GT	582	8BD
P5G	580	5X	3LF4	584	6BB	6B6G	574	7S	6X4	590	6S	12SQ6	582	8V
Q5G	580	6AF	3M2	585	7BA	6B7G	576	7D	6X6G	575	7AL	12SR7	582	8Q
R4	580	4AH	3Q5GT	584	7AP	6B8	572	8E	6Y5	590	6J	12SW7	582	8Q
R5	585	7AT	3S4	585	7BA	6BA6	586	7CC	6Y6G	575	7AC	12SX7	582	8BD
S4	585	7AV	3V4	585	6BX	6BD6	586	7CC	6Y7G	575	8B	12SY7	582	8R
S5	585	6AU	3-25A3	593	3G	6BE6	586	7CH	6Z3	590	4G	12Z3	590	4G
SA6GT	580	8CA	3-25D3	593	2D	6BF6	586	7BT	6Z5	590	6K	12Z5	590	7L
SB6GT	580	6AF	3-50A4	595	3G	6BG6	574	5BT	6Z7G	575	8B	14A4	582	5AC
T4	585	6AR	3-50D4	595	2D	6B6	586	7CM	6ZY5G	590	6S	14A5	582	6AA
T5GT	580	6CB	3-50E2	595	2D	6C4	586	6BG	7A4	575	5A	14A7	582	8V
U4	585	6AR	3-75A2	597	2D	6C4	592	6BG	7A5	575	6AA	14AF7	582	7AC
U5	585	6BW	3-75A3	597	2D	6C6	572	6F	7A6	580	7AJ	14B6	582	8W
V	590	4C	3-100A2	598	2D	6C7	576	7G	7A7	575	8V	14B8	582	8X
Z2	590	7CB	3-100A4	598	2D	6C8G	574	8G	7A8	575	8U	14C5	582	6AA
IA3	577	4D	3X-100A11	599	—	6D4	587	5AY	7AB7	584	Fig. 5	14C7	582	8V
IA4G	587	5S	1-150A2	600	4BC	6D6	576	6F	7AF7	575	8AC	14E6	582	8V
IA5	577	6B	3-150A3	600	—	6D7	576	7H	7AG7	575	Fig. 45	14E7	582	8AE
IA6	577	8C	3-250A2	601	2N	6D8G	574	8A	7AP4	589	5AJ	14F7	582	8AC
IA7	577	7C	3-250A4	601	2N	6E5	576	6R	7B4	587	5AC	14G7	582	8Q
IAP1	580	11D	3-300A2	602	4BC	6E8	576	7B	7B5	575	6AF	14J7	582	8AR
IB6	578	7J	3-300A3	602	4BC	6E7	576	7H	7B6	575	8W	14N7	582	8AC
IB7	578	7D	4A6G3	579	AL	6E8G	574	8O	7B7	575	8V	14Q7	582	8AL
IB25	590	3T	4C32	601	2N	6F4	584	7BR	7B8	575	8X	14R7	582	8AE
IBP1	588	12C	4C34	601	2M	6F4	592	7BR	7BP1	589	5AN	14S7	582	8BL
IC31	587	5AS	4C36	599	Fig. 56	6F5	572	5M	7C4	575	8Y	14T7	582	8G
IC21	592	7BH	4D22	606	Fig. 50	6F6	572	7S	7C5	575	6AA	14W7	582	8BJ
IC22	592	7BH	4D23	607	Fig. 27	6F6	603	7S	7C6	575	8V	14Y4	590	5AB
IC22	573	4AM	4D32	606	Fig. 51	6F7	577	7E	7C7	575	8V	14Z3	590	4G
IC22	592	4AM	4E27	606	7BM	6F8G	574	8G	7CP1	589	6AZ	15	579	5F
IC25	592	4D	4X150A	607	T-9J	6G5	577	6R	7D7	575	8AR	15E	593	3G
IC26A	592	4FB	4-65A	606	Fig. 55	6G6G	574	7S	7D5	584	Fig. 46	17	582	8AF
IC34	592	T-7DC	4-125A	607	—	6H4GT	574	5AF	7E5	588	8BM	18	582	6B
IC35	585	Fig. 38	4-250A	607	Fig. 27	6H5	577	6R	7E6	575	8W	19	579	6C
IC39	599	—	5AP1	588	11A	6H6	572	7Q	7E7	575	8AE	20	584	4D
IC40	592	Fig. 19	5BP1	588	11A									

Type	Page Base	Type	Page Base	Type	Page Base	Type	Page Base	Type	Page Base
25A7G	590 8F	117P7GT	583 8AV	864	584 4D	5556	592 4D	HY114B	592 2T
25A5G	582 6D	117P7GT	591 8AV	865	604 T-4C	5562	606 Fig. 45	HY115	581 5K
2515	582 6D	117Z3	591 4BR	866	591 4P	7000	575 7R	HY123	581 5K
25B6G	582 7A	117Z4	591 5AA	866A	591 4P	7193	592 2AM	HY125	581 5K
25B8GT	582 8T	117Z4GT	591 5AA	867	591 4P	7370	577 6P	HY145	581 5K
25C6G	582 7AC	150T	600 2N	866Br	591 4B	8000	600 2N	HY155	581 5K
25B8GT	582 8AF	152TH	600 4BC	871	591 4P	8001	606 7BM	HY615	592 T-8A(C)
251.6	582 7AC	152TL	600 4BC	872	591 T-3A	8003	599 T-3AB	HY801A	593 4P
25N6G	582 7W	182-B	584 4D	872A	591 T-3A	8005	597 3G	HY866jr	591 5P
258	578 6M	183	584 4D	874	587 4S	8008	591 Fig. 11	HY1231Z	594 T-4
25T	598 3G	203-A	598 4E	876	589 4E	9012	594 T-4BB	HY145	581 5K
25X6GT	590 4Q	203-B	598 T-3AB	878	591 4P	8012	594 T-4BB	HY1148	587 T-8A(C)
25Y4GT	590 5AA	204-A	602 T-1A	879	591 4P	8013-A	591 4P	KY21	587 —
25Y5	590 6E	205D	592 4D	884	587 6Q	8016	591 4AC	KY866	587 Fig. 8
25Z3	590 4G	211	498 4E	885	587 5A	8020	591 4P	M54	585 —
25Z4	590 5AA	212-E	602 T-2A	886	587 —	8025	594 4AQ	M64	585 —
25Z5	590 6E	217A	591 T-3A	902	589 Fig. 1	9001	586 7PM	M74	585 —
25Z6	590 6E	217C	591 T-3A	903	589 6AL	9002	586 NT(35)	NT(35)	585 Fig. 36
26	584 4D	227A	598 T-4B	904	589 Fig. 3	9002	592 7TM	PE340	607 Fig. 27
26A6	586 7BK	241B	602 T-2A	905	589 Fig. 6	9003	586 7PM	QK159	608 Fig. 63
26A7GT	583 8BU	242A	597 4E	906P1	588 7AN	9004	584 4BJ	RK10	593 4D
26C6	586 7BT	242B	598 4E	907	589 Fig. 6	9005	584 Fig. 16	RK11	594 3G
26D6	586 7CH	242C	598 4E	908	589 7AN	9006	586 6BH	RK12	594 3G
26E6	586 7CH	242D	598 4E	908A	589 7AN	9007	586 6BH	RK15	578 4D
28D7	583 8BS	249B	601 Fig. 53	909	589 Fig. 6	9008	590 4J	RK16	578 5A
28Z5	590 5AB	250TH	601 2N	910	589 7AN	9009	590 4J	RK17	578 5F
30	579 4E	250TL	601 2N	911	589 7AN	9010	590 4H	RK18	594 3G
31	579 4D	254A	604 T-4C	912	589 Fig. 8	CE220	590 4P	RK19	591 T-3A
32	579 4K	261A	598 4E	913	589 Fig. 1	CK501	580 —	RK20	605 5J
32L7GT	583 8Z	270A	602 T-1A	914	589 Fig. 12	CK502	580 —	RK20A	605 5J
32L7GT	583 8Z	276A	598 4E	936	596 3C	CK503	580 —	RK21	591 4P
33	579 5K	282A	606 T-4C	938	599 4E	CK504	580 —	RK22	591 T-4AC
34	579 4M	284B	599 T-3AB	950	579 5R	CK505	580 —	RK23	606 T-7C
35/51	578 5E	284D	597 4E	951	578 4M	CK506	580 —	RK24	579 4D
35A5	583 6AA	295A	599 4E	954	584 5BB	CK507	580 —	RK24	592 4D
35B5	586 7BZ	300T	602 2N	955	584 5BC	CK509	581 —	RK25	603 T-7C
35L6G	583 7AC	305A	598 4E	955	584 5BC	CK510	581 —	RK25B	603 T-7C
35M6	583 7AC	304A	602 T-1A	956	584 5BB	CK511	581 —	RK26	607 5J
35T6	595 2D	304B	595 T-1A	957	584 5BD	CK1005	591 T-9F	RK27A	607 5J
35W4	590 5BQ	304TH	602 4BC	958	584 5BD	CK1006	591 4C	RK30	594 2D
35Y4	590 5AL	304TL	602 4BC	958A	584 5BD	CK1007	591 T-9G	RK31	594 3G
35Z3	590 4Z	305A	606 T-4CE	959	592 5BD	CK1009	591 —	RK32	595 2D
35Z4GT	590 5AA	306A	604 T-5CB	959A	584 5BC	CK1010	591 —	RK33	595 2D
35Z5GT	590 5AD	307A	602 T-2A	959B	587 3G	DR-3127	590 4B	RK34	592 T-7DA
35Z6G	590 7Q	308B	602 T-2A	975A	587 T-3A	EF50	584 Fig. 16	RK35	595 2D
36	577 5E	310	593 4D	991	587 —	FI23A	587 Fig. 14	RK36	597 2D
37	577 5A	311	598 4E	1003	591 4R	FI27A	601 Fig. 16	RK37	595 2D
38	577 5F	311CH	599 Fig. 57	1005	591 T-9F	G84	590 2B	RK38	598 2D
39/44	577 5F	312A	606 T-6C	1006	591 4C	GL2C44	584 Fig. 17	RK39	604 T-5BB
40	584 4D	312E	602 T-2AA	1201	584 8BM	GL2C44	592 Fig. 17	RK40	602 T-5BB
40Z5GT	591 6AD	316A	594 —	1203	584 4AH	GL5C24	600 Fig. 16	RK42	581 4D
41	577 6B	327A	598 T-4AD	1204	584 Fig. 5	GL146	599 T-4G	RK43	581 6C
42	577 6B	327B	597 T-4AB	1206	576 8BV	GL152	599 T-4BG	RK44	603 T-7C
43	583 6B	342D	598 4E	1221	577 6F	GL159	601 T-4BG	RK46	605 5J
45	578 4D	356A	596 T-4BD	1223	575 7R	GL169	601 T-4BG	RK47	606 T-5D
45Z5GT	591 6AD	312E	598 4E	1229	575 4K	GL446A	584 Fig. 19	RK48	607 T-5D
46	578 5C	378A	598 4E	1231	576 8V	GL446B	584 Fig. 17	RK48A	607 T-5D
47	578 5B	410R	608 Fig. 58	1232	575 8V	GL446A	584 Fig. 19	RK49	604 T-6B
48	583 6A	482B	684 4D	1265	587 —	GL1559	584 Fig. 18	RK51	596 T-3G
49	579 5C	483	584 4D	1266	587 4AJ	GL592	601 Fig. 52	RK52	596 3G
50	580 4D	485	584 5A	1275	576 8V	GL8012A	594 T-4BR	RK66	603 T-5BB
50A5	583 6AA	487	602 T-4B	1275	581 4C	HD203A	600 T-3AB	RK57	598 T-3AB
50B5	586 7BZ	550	584 Fig. 18	1276	586 2D	HF5	596 2D	RK58	598 T-3AB
50C6GT	583 7AC	705A	591 T-3AA	1284	583 Fig. 4	HF105	597 2D	RK59	593 T-4D
50L6GT	583 7AC	707B	608 Fig. 61	1291	580 7BE	HF100	597 2D	RK60	591 T-4AG
50T	597 2D	715B	605 —	1293	580 Fig. 2	HF120	598 —	RK61	587 —
50X	597 7AJ	717A	575 8BK	1294	580 4AH	HF125	598 —	RK62	587 4D
50Y6GT	591 7Q	723AB	608 Fig. 60	1294	580 6BB	HF130	599 —	RK63	600 2N
50Z6G	591 7Q	756	595 4D	1602	593 4D	HF140	598 —	RK64	603 T-5BB
50Z7G	591 8AN	801	593 4D	1603	577 6F	HF150	599 —	RK64	603 T-5BB
51	578 5E	801A	593 4D	1608	593 4D	HF175	599 —	RK65	607 T-3BC
52	577 Fig. 33	802	603 T-7C	1609	584 5B	HF200	600 2N	RK66	605 5J
53	578 7T	803	607 5J	1610	603 T-5CA	HF250	600 2N	RK75	594 5J
53A	578 T-4B	803A	607 5J	1611	573 7S	HF300	600 2N	RK100	593 T-6B
55	578 6G	805	599 T-3AB	1612	573 7T	HK24	594 3G	RK155A	594 T-3AA
56	578 5A	805	601 2N	1613	603 7A	HK54	594 2D	RK59B	591 —
56AS	577 5A	807	604 T-5BB	1614	604 7AC	HK154	594 2D	RM208	587 —
57	578 6F	808	596 2D	1616	591 4P	HK158	594 2D	RM209	587 —
57AS	577 6F	809	594 3G	1620	573 7R	HK252L	600 T-4BF	T20	593 3G
58	578 6F	810	600 2N	1621	573 7S	HK253	591 T-3A	T21	604 T-6B
58AS	577 6F	811	596 3G	1622	573 7AC	HK254	598 2N	T40	595 3G
59	578 7A	812	596 3G	1623	594 3G	HK257	606 7BM	T55	596 3G
70A7GT	583 8AB	812H	597 3G	1624	605 T-6DC	HK257B	606 7BM	T60	596 2D
70A7GT	591 8AB	813	607 Fig. 28	1625	605 5AZ	HK304L	602 4BC	T100	597 2D
70L7GT	583 8AA	814	606 T-5D	1626	605 6Q	HK354	600 2N	T125	599 2N
70L7GT	591 8AA	815	604 T-8FA	1627	600 2N	HK354B	600 2N	T200	601 2N
71-A	584 4D	816	591 4P	1628	594 T-4BB	HK354D	600 2N	T300	601 T-3AB
72	591 4P	822	601 T-3AB	1629	583 8RA	HK354F	600 2N	T822	601 T-3AB
73	591 4Y	822S	601 2N	1631	583 7AC	HK454H	602 2N	TB35	605 Fig. 54
75	577 6G	826	596 T-9A	1632	583 7AC	HK454L	602 2N	TU F20	593 2T
75TH	597 2D	828	606 5J	1633	583 8BD	HK654	600 2N	TW175	597 2D
75TL	597 2D	829	605 7BP	1634	583 8S	HV10	600 2N	TW150	600 2N
76	577 6F	829A	605 7BP	1635	575 8B	HV2	601 T-3AB	UE220	593 3G
77	577 6F	829B	605 7BP	1641	571 T-4AG	HY615	601 T-3AB	TU30	597 T-3G
78	577 6F	830	595 4D	1642	576 7BH	HY6J5GTX	592 6Q	UE465	597 2D
79	577 6H	830B	596 3G	1644	583 8BU	HY6L6GTX	604 7AC	UE468	600 Fig. 57
80	591 4B	831	602 T-1AA	1654	591 Fig. 41	HY6V6GTX	603 7AC	UE35	596 3G
81	591 4B	832	604 7BP	1800	589 6AL	HY24	592 4A	UH50	595 2D
82	591 4B	832A	604 7BP	1801	589 Fig. 13	HY25	594 3C	UH51	595 2D
83	591 4C	833A	602 7AB	1803P4	589 6AL	HY26	595 T-9B	VR10	595 2D
83-V	591 4AD	834	596 2D	1804P4	589 6AL	HY31Z	594 T-4D	V70A	597 T-3AB
84/GZ4	591 5D	835	598 4E	1805P1	588 11A	HY40	594 3G	V70B	596 3G
85	577 6G	836	591 4P	1806P1	588 11A	HY40Z	595 3G	V70C	597 3G
85AS	577 6G	837	603 T-7C	1809P1	589 8BR	HY51A	596 3G	V70D	597 3G
89	577 4D	838	599 4E	1851	573 7R	HY51B	596 3G	VR75	587 4AJ
95	584 4D	839	602 T-1A	1852	573 7R	HY51Z	596 4B	VR80	587 4AJ
100TH	598 2D	841	593 4D	1853	572 8N	HY62	595 3G	VR105	587 4AJ
100TL	598 2D	841A	596 3G	2001	589 Fig. 2	HY60	603 T-5BB	VR150	587 4AJ
111H	597 2D	841SW	596 3G	2002	589 Fig. 1	HY61	604 T85BB	VT127A	598 T-4B
112-A	584 4D	843	593 5A	2005	589 Fig. 1	HY63	603 T-8DB	WE304A	595 2D
117L7GT	583 8AO	844	604 T-5BB	2050	587 8BA	HY65	603 T-8DB	XXB	585 Fig. 9
117L7GT	591 8AO	845	602 T-1A	2051	587 8BA	HY67	606 T-5DB	XXD	585 8AC
117M7GT	583 8AO	850	607 T-3B	2448H	587 5A	HY75	593 2T	XXE	596 3G
117M7GT	591 8AO	852	599 2D	2523N/128AS	587 5A	HY75	593 2T	XXFM	585 Fig. 10
117N7GT	583 8AV	860	607 T-4C	5514	596 4B	HY75A	593 2T	Z225	591 4P
117N7GT	591 8AV	861	607 T-1B	5516	604 7CLO	HY113	581 5K	Z668	608 —

## VACUUM-TUBE BASE DIAGRAMS

The diagrams on the following pages show standard socket connections corresponding to the base designations given in the column headed "Socket Connections" in the classified tube-data tables. Bottom views are shown throughout. Terminal designations are as follows:


- |                      |                          |                                |                             |                   |
|----------------------|--------------------------|--------------------------------|-----------------------------|-------------------|
| A = Anode            | F = Filament             | IS = Internal Shield           | PBF = Beam-Forming Plates   | S = Shell         |
| B = Beam             | G = Grid                 | K = Cathode                    | RC = Ray-Control Electrode  | TA = Target       |
| BP = Bayonet Pin     | H = Heater               | NC = No Connection             | P = Plate (Anode)           | ● = Gas-Type Tube |
| BS = Base sleeve     | IC = Internal Connection | P <sub>1</sub> = Starter-Anode | Ref = Reflector or repeller | U = Unit          |
| D = Deflecting Plate |                          |                                |                             |                   |

Alphabetical subscripts D, P, T and IX indicate, respectively, diode unit, pentode unit, triode unit or hexode unit in multi unit types. Subscript M, T or CT indicates filament or heater tap.

Generally when the No. 1 pin of a metal-type tube in Table I, with the exception of all triodes, is shown connected to the shell, the No. 1 pin in the glass (G or GT) equivalent is connected to an internal shield.

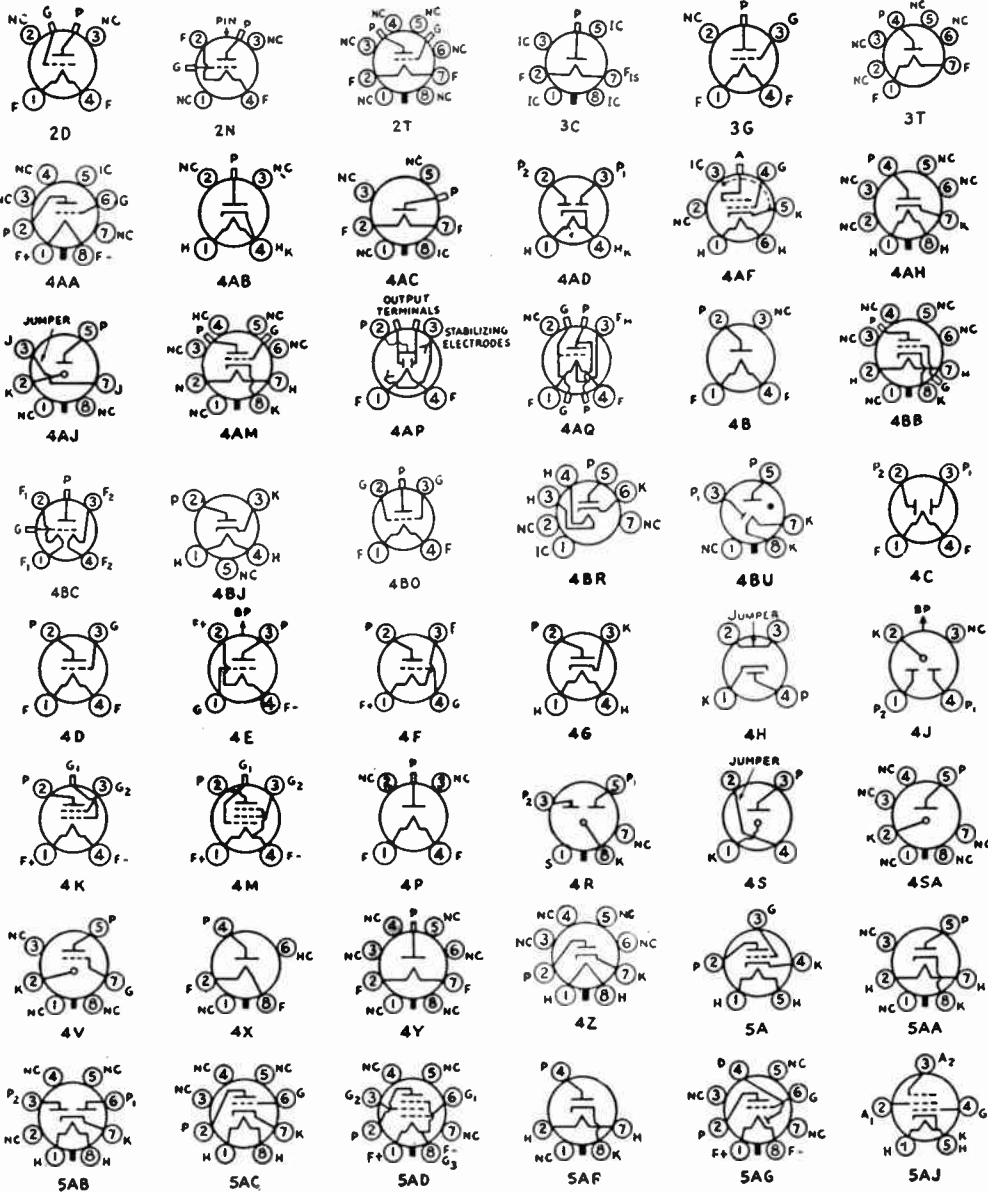
### R.M.A. TUBE BASE DIAGRAMS

Bottom views are shown. Terminal designations on sockets are shown above.



R.M.A. TUBE BASE DIAGRAMS

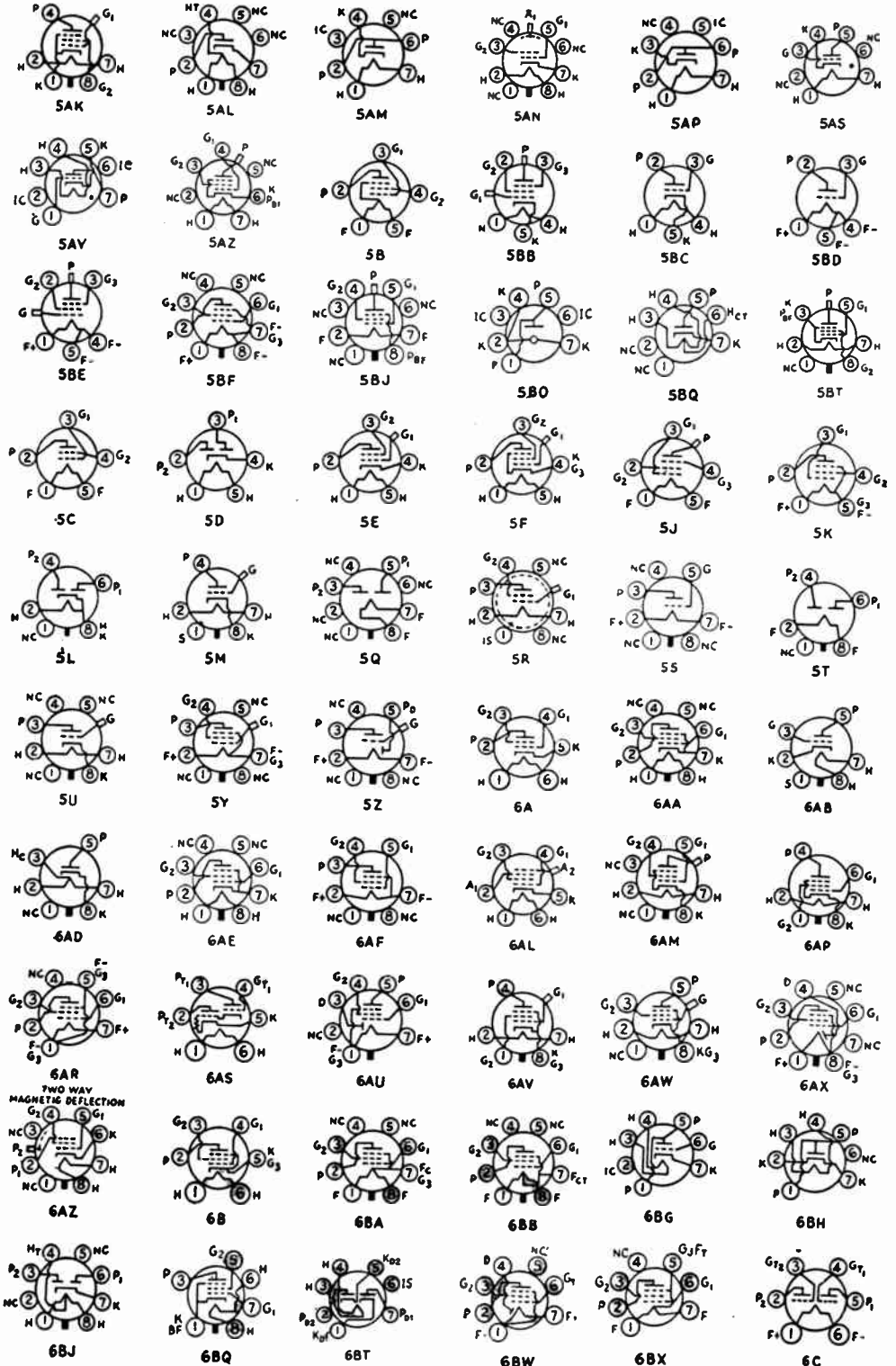
Bottom views are shown. Terminal designations on sockets are given on page 565.





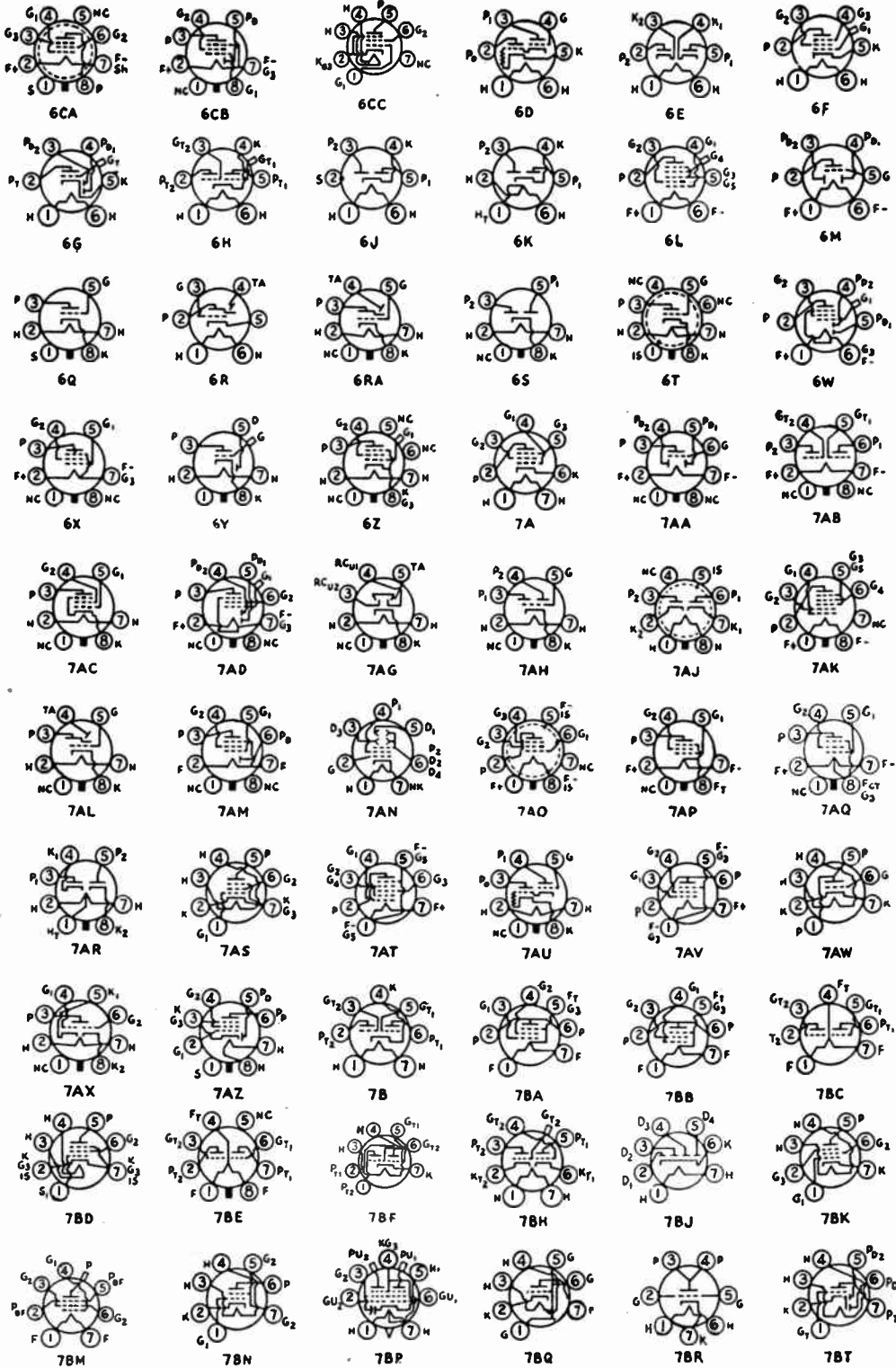
## R.M.A. TUBE BASE DIAGRAMS

Bottom views are shown. Terminal designations on sockets are given on page 565.




R.M.A. TUBE BASE DIAGRAMS

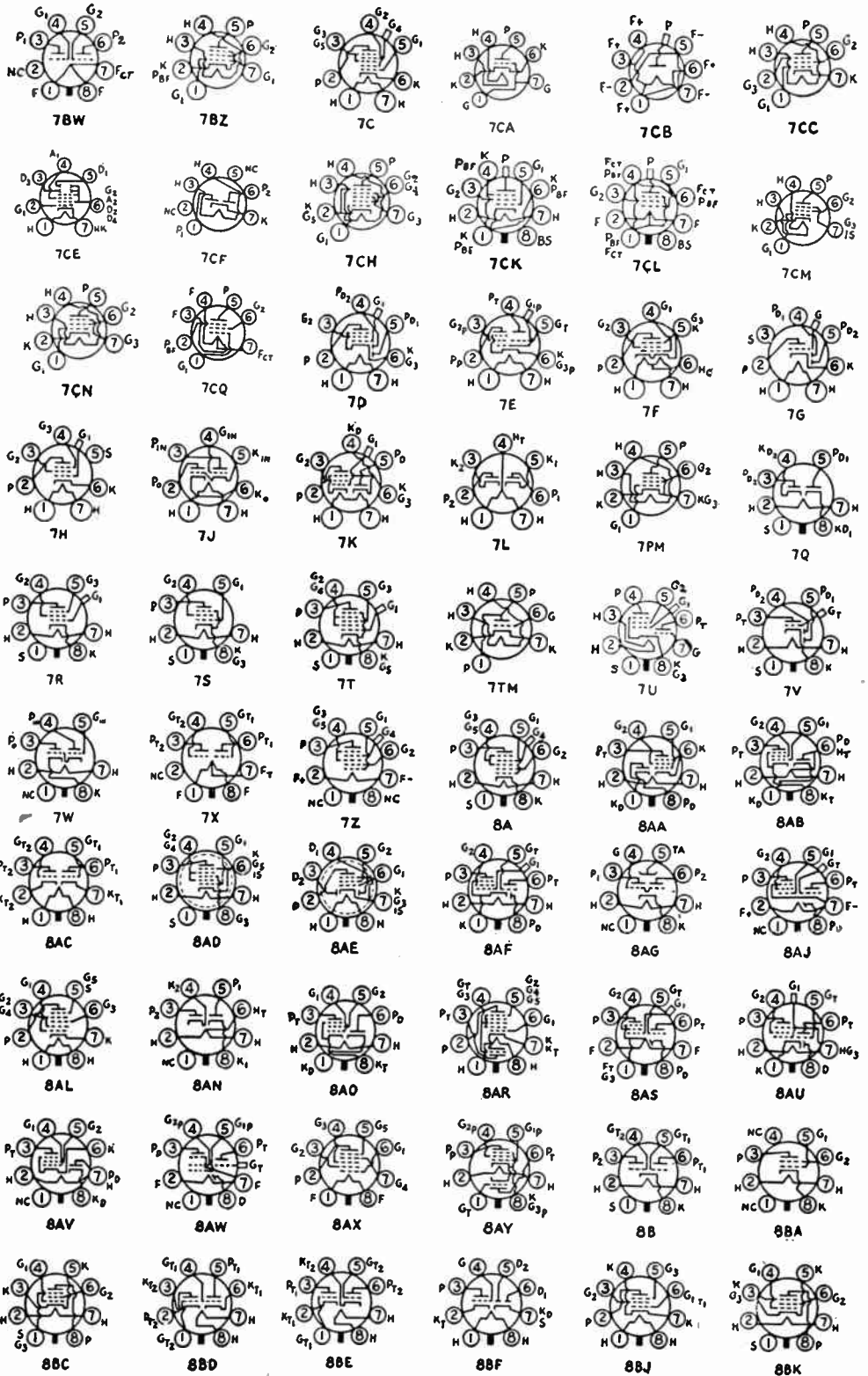Bottom views are shown. Terminal designations on sockets are given on page 565.



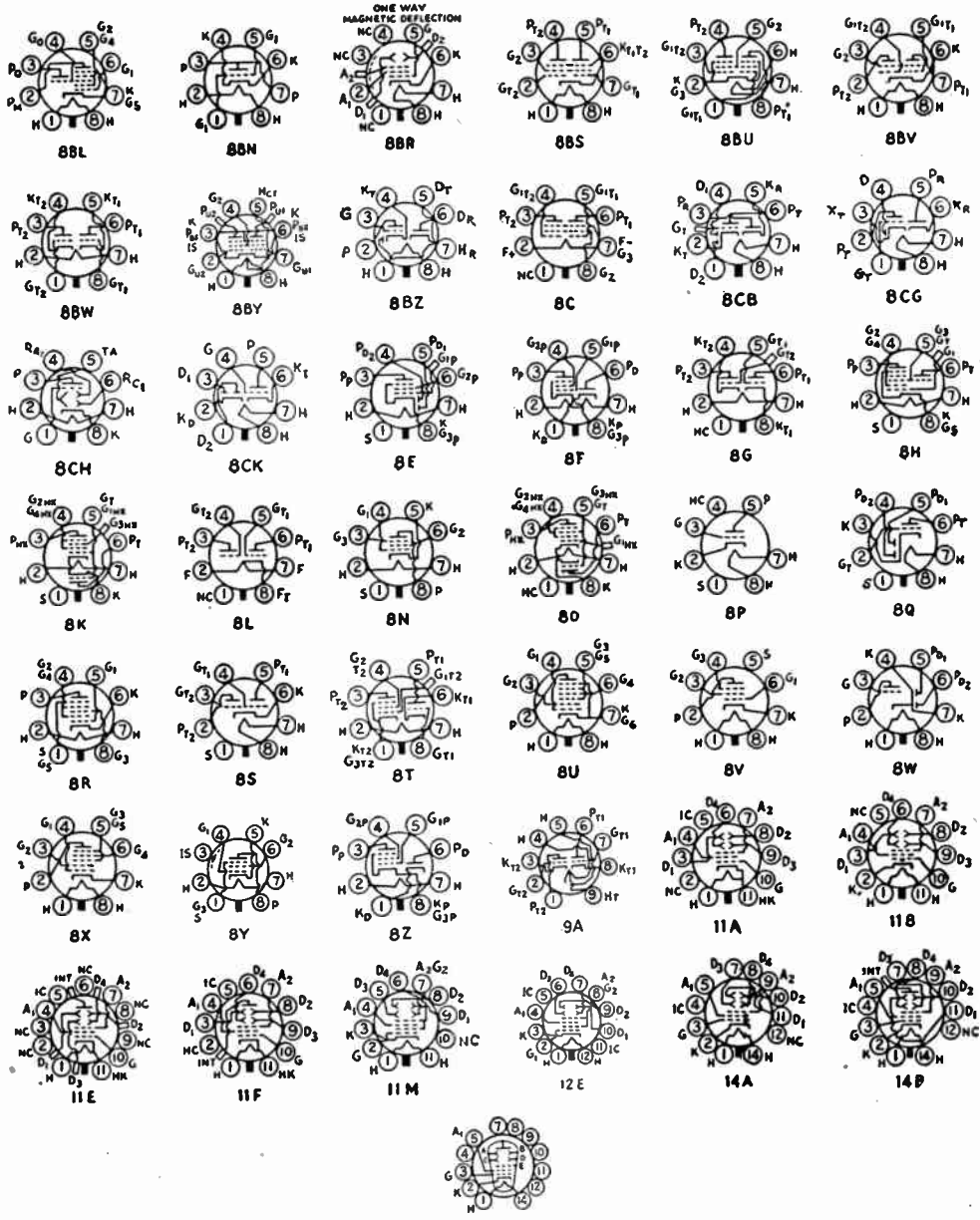
## R.M.A. TUBE BASE DIAGRAMS

Bottom views are shown. Terminal designations on sockets are given on page 565.
















































## SUPPLEMENTARY BASE DIAGRAMS

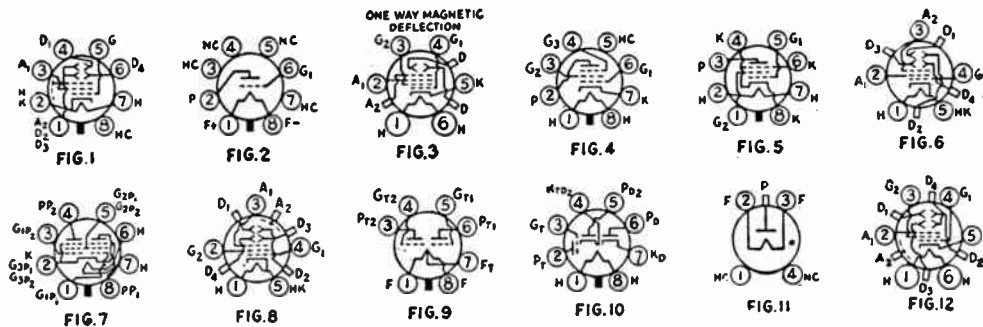

SUPPLEMENTARY BASE DIAGRAMS

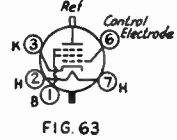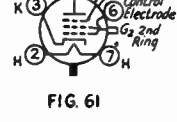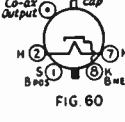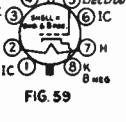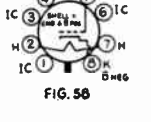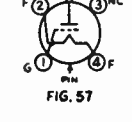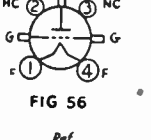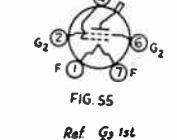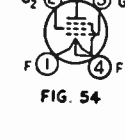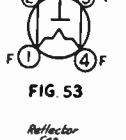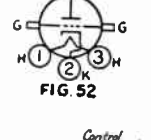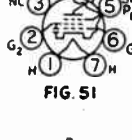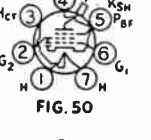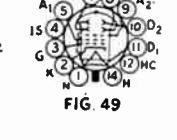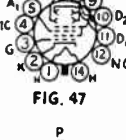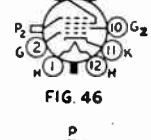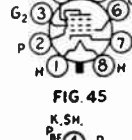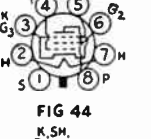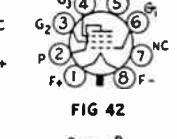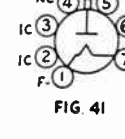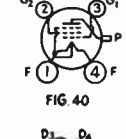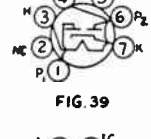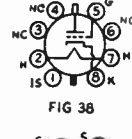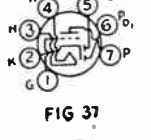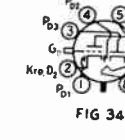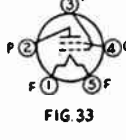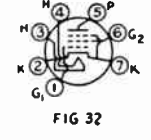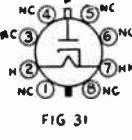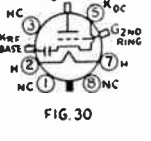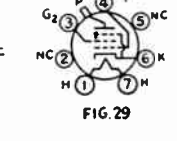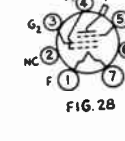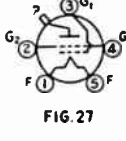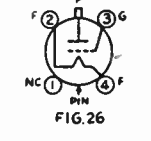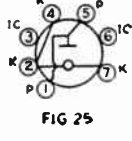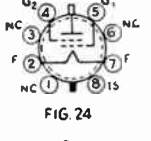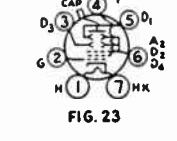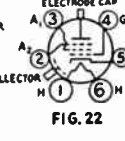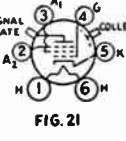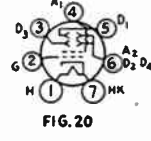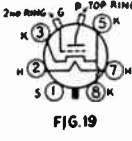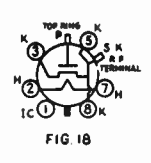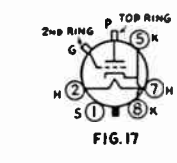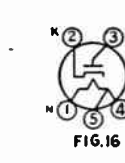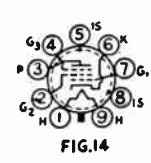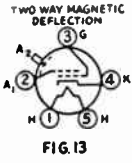Bottom views are shown. Terminal designations on sockets are given on page 365.



## SUPPLEMENTARY "T"-GROUP BASE DIAGRAMS

Bottom views are shown. Terminal designations on sockets are given on page 365.

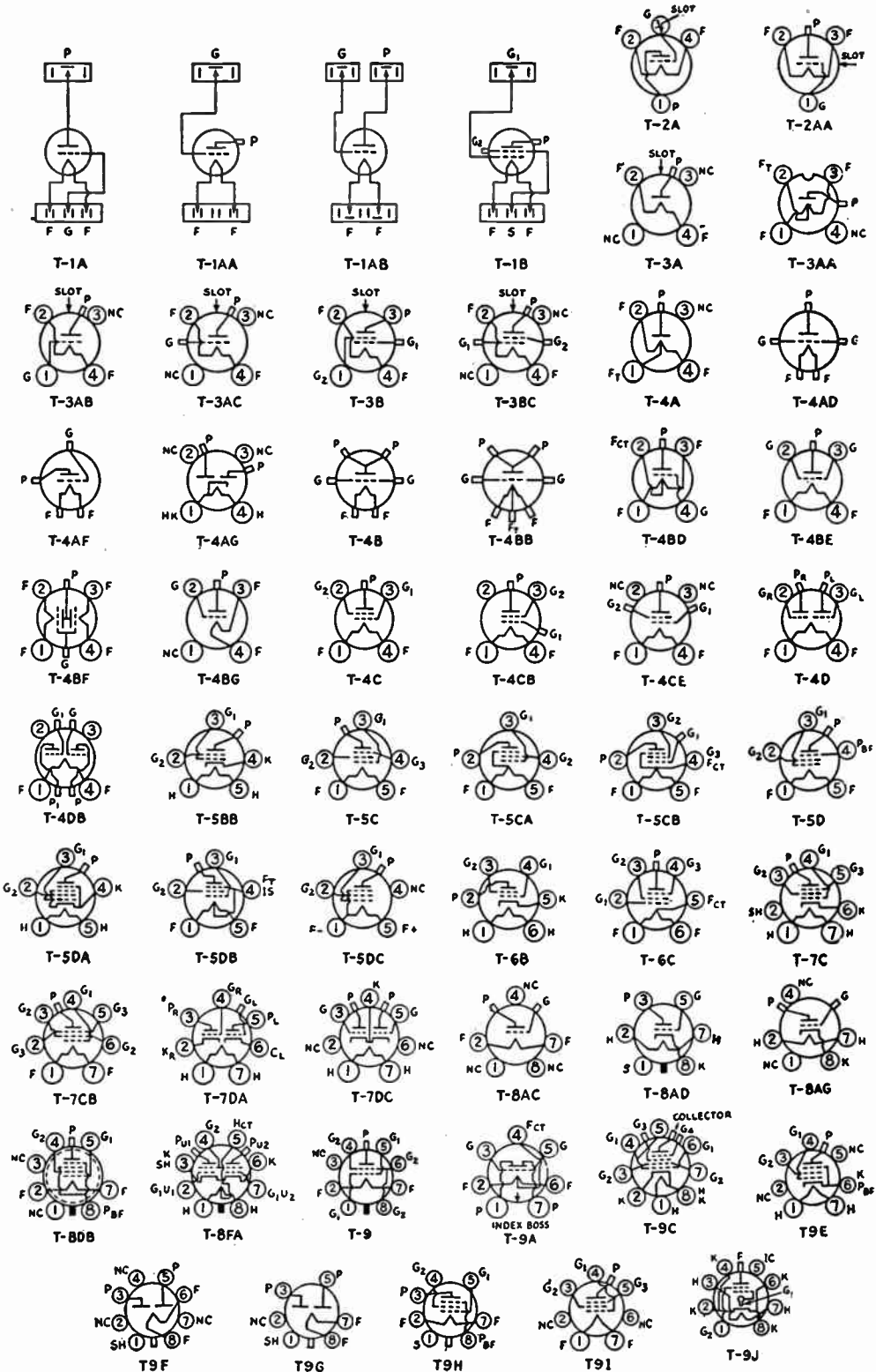


TABLE I—METAL RECEIVING TUBES

Characteristics given in this table apply to all tubes having type numbers shown, including metal tubes, glass tubes with "G" suffix, and bantam tubes with "GT" suffix. For "G" and "GT" tubes not listed (not having metal counterparts), see Tables II, VII, VIII and IX.

Type	Name	Socket Connections	Fil. or Heater		Capacitance $\mu\text{mfd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Mo.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Wats	Type	
			Volts	Amp.	In	Out	Plate-Grid													
6A8	Pentagrid Converter	8A	6.3	0.3	—	—	—	Osc.-Mixer	250	- 3.0	100	3.2	3.3	Anode-grid (No. 2) 250 volts max. thru 20,000 ohms				6A8		
6AB7 1853	Television Amp. Pentode	8N	6.3	0.45	8	5	0.015	Class-A Amp.	300	- 3.0	200	3.2	12.5	700000	5000	3500	—	—	6AB7 1853	
6AC7 1852	Television Amp. Pentode	8N	6.3	0.45	11	5	0.015	Class-A Amp.	300	- 2.0	150	2.5	10	750000	9000	6750	—	—	6AC7 1852	
6AG7	Video Beam Power Amp.	8Y	6.3	0.65	13	7.5	0.06	Class-A <sub>1</sub> Amp.	300	- 3.0	150	7/9	30/30.5	130000	11000	—	10000	3.0	6AG7	
6AJ7	Sharp-Cut-Off Pentode	8N	6.3	0.45	—	—	—	Class-A Amp.	300	160*	300	2.5	10	1000000	9000	—	—	—	6AJ7	
6AK7	Pentode Power Amp.	8Y	6.3	0.65	13	7.5	0.06	Class-A Amp.	300	- 3	150	7	30	130000	11000	—	10000	3.0	6AK7	
6B8	Duplex-Diode Pentode	8E	6.3	0.3	6	9	0.005	Class-A Amp.	250	- 3.0	125	2.3	9.0	650000	1125	730	—	—	6B8	
6C5	Triode Detector, Amplifier	6Q	6.3	0.3	3	11	2	Class-A Amp.	250	- 8.0	—	—	8.0	10000	2000	20	—	—	6C5	
								Bias Detector	250	-17.0	—	—	—	—	—	Plate current adjusted to 0.2 ma. with no signal				
6F5	High- $\mu$ Triode	5M	6.3	0.3	5.5	4	2.3	Class-A Amp.	250	- 1.3	—	0.2	66000	1500	100	—	—	6F5		
								Class-A <sub>1</sub> Pent. <sup>5</sup>	250	-16.5	250	6.5	36 <sup>7</sup>	80000	2500	200	7000		3.2	
6F6	Pentode Power Amplifier	75	6.3	0.7	6.5	13	0.2	Triode Amp. <sup>1</sup>	250	-22.0	—	—	34 <sup>7</sup>	2600	2600	6.8	4000	0.85	6F6	
								Class-AB <sub>1</sub> Amp. <sup>5</sup> Class-AB <sub>2</sub> Amp. <sup>5</sup>	375 350	340* -38.0	250	18 <sup>7</sup>	77 <sup>7</sup>	22.5	Power output for 2 tubes at stated load, plate-to-plate		10000 <sup>8</sup> 6000 <sup>8</sup>	19.0 18.0		
6H6	Twin Diode	7Q	6.3	0.3	—	—	—	Rectifier	Max. a.c. voltage per plate = 100 r.m.s. Max. output current 4.0 ma. d.c.										6H6	
6J5	Detector-Amplifier Triode	6Q	6.3	0.3	3.4	3.6	3.4	Class-A Amp.	250	- 8.0	—	—	9	7700	2600	20	—	—	6J5	
6J7	Triple-Grid Detector, Amp.	7R	6.3	0.3	7	12	0.005	R.F. Amp.	250	- 3.0	100	0.5	2.0	1.5 meg.	1225	1500	—	—	6J7	
								Bias Detector	250	- 4.3	100	Cathode current 0.43 ma.				—	—	0.5 meg.		
6K7	Triple-Grid Variable- $\mu$ Amp.	7R	6.3	0.3	7	12	0.005	R.F. Amp.	250	- 3.0	125	2.6	10.5	600000	1650	990	—	—	6K7	
								Mixer	250	-10.0	100	—	—	—	Oscillator peak volts = 7.0					
6K8	Triode-Hexode Converter	8K	6.3	0.3	—	—	—	Converter	250	- 3.0	100	6	2.5	Triode Plate (No. 2) 100 volts, 3.8 ma.				6K8		
								Single Tube Class A <sub>1</sub>	250	170*	250	5.4/7.2	75/78	—	—	—	2500		6.5	
6L6	Beam Power Amplifier	7AC	6.3	0.9	10	12	0.4	Class A <sub>1</sub>	300	220*	200	3.0/4.6	51/54.5	—	—	—	4500	6.5	6L6	
								Single Tube Class A <sub>1</sub>	250	-14.0	250	5.0/7.3	72/79	22500	6000	—	2500	6.5		
								Class A <sub>1</sub>	350	-18.0	250	2.5/7.0	54/66	33000	5200	—	4200	10.8		
								P.P. Class A <sub>1</sub> <sup>6</sup>	270	125*	270	11/17	134/145	—	—	—	5000 <sup>8</sup>	18.5		
								P.P. Class A <sub>1</sub> <sup>6</sup>	250	-16.0	250	10/16	120/140	24500	5500	—	5000 <sup>8</sup>	14.5		
								P.P. Class A <sub>1</sub> <sup>6</sup>	270	-17.5	270	11/17	134/155	23500	5700	—	5000 <sup>8</sup>	17.5		
								P.P. Class AB <sub>1</sub> <sup>6</sup>	360	250*	270	5/17	88/100	Power output for 2 tubes. Load plate-to-plate				9000 <sup>8</sup>		24.5
								P.P. Class AB <sub>1</sub> <sup>6</sup>	360	-22.5	270	5/15	88/132					6600 <sup>8</sup>		26.5
								P.P. Class AB <sub>2</sub> <sup>6</sup>	360	-18.0	225	3.5/11	78/142					6000 <sup>8</sup>		31.0
								P.P. Class AB <sub>2</sub> <sup>6</sup>	360	-22.5	270	5/16	88/205					3800 <sup>8</sup>		47.0
6L7	Pentagrid Mixer Amplifier	7T	6.3	0.3	—	—	—	R.F. Amp.	250	- 3.0	100	5.5	5.3	800000	1100	—	—	6L7		
								Mixer	250	- 6.0	150	8.3	3.3	Over 1 meg.	Oscillator-grid (No. 3) voltage = -15					
6N7	Twin Triode	8B	6.3	0.8	—	—	—	Class-B Amp.	300	0	—	—	35-70	—	—	8000	10.0	6N7		
6Q7	Duplex-Diode Triode	7V	6.3	0.3	5	3.8	1.4	Triode Amp.	250	- 3.0	—	—	1.1	58000	1200	70	—	—	6Q7	
6R7	Duplex-Diode Triode	7V	6.3	0.3	4.8	3.8	2.4	Triode Amp.	250	- 9.0	—	—	9.5	8500	1900	16	10000	0.28	6R7	
6S7	Triple-Grid Variable- $\mu$	7R	6.3	0.15	6.5	10.5	0.005	Class-A Amp.	250	- 3.0	100	2.0	8.5	1000000	1750	1750	—	—	6S7	
6SA7	Pentagrid Converter	8R <sup>2</sup>	6.3	0.3	—	—	—	Converter	250	0 <sup>3</sup>	100	8.0	3.4	800000	Grid No. 1 resistor 20000 ohms			6SA7		
6SC7	Twin-Triode Amplifier	8S	6.3	0.3	—	—	—	Class-A Amp.	250	- 2.0	—	—	2.0	53000	1325	70	—	—	6SC7	
6SF5	High- $\mu$ Triode	6AB	6.3	0.3	4	3.6	2.4	Class-A Amp.	250	- 2.0	—	—	0.9	66000	1500	100	—	—	6SF5	
6SF7	Diode Variable- $\mu$ Pentode	7AZ	6.3	0.3	5.5	6	0.004	Class-A Amp.	250	- 1.0	100	3.3	12.4	700000	2050	—	—	—	6SF7	
6SG7	Triple-Grid Semivariable- $\mu$	8BK	6.3	0.3	8.5	7	0.003	H.F. Amp.	250	- 2.5	150	3.4	9.2	Over 1 meg.	4000	—	—	—	6SG7	

TABLE I—METAL RECEIVING TUBES—Continued

Type	Name	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
			Volts	Amp.	In	Out	Plate-Grid												
6SH7	Triple-Grid Amplifier	8BK	6.3	0.3	8.5	7	0.003	H.F. Amp.	250	- 1.0	150	4.1	10.8	900000	4900	—	—	—	6SH7
6SJ7 <sup>4</sup>	Triple-Grid Amplifier	8N	6.3	0.3	6	7	0.005	Class-A Amp.	250	- 3.0	100	0.8	3	1500000	1650	2500	—	—	6SJ7
6SK7	Triple-Grid Variable- $\mu$	8N	6.3	0.3	6	7	0.003	Class-A Amp.	250	- 3.0	100	2.4	9.2	800000	2000	1600	—	—	6SK7
6SQ7	Duplex-Diode Triode	8Q	6.3	0.3	3.6	3.2	1.80	Class-A Amp.	250	- 2.0	—	—	0.8	91000	1100	100	—	—	6SQ7
6SR7	Duplex-Diode Triode	8Q	6.3	0.3	3.6	2.8	2.40	Class-A Amp.	250	- 9.0	—	—	9.5	8500	1900	16	—	—	6SR7
6SS7	Triple-Grid Variable- $\mu$	8N	6.3	0.15	5.5	7.0	0.004	Class-A Amp.	250	- 3.0	100	2.0	9.0	1000000	1850	—	—	—	6SS7
6ST7	Duplex-Diode Triode	8Q	6.3	0.15	2.8	3	1.50	Class-A Amp.	250	- 9.0	—	—	9.5	8500	1900	16	—	—	6ST7
6SV7	Diode R.F. Pentode	7AZ	6.3	0.3	6.5	6	0.004	Class-A Amp.	250	- 1	150	2.8	7.5	800000	3400	—	—	—	6SV7
6SZ7	Duplex-Diode Triode	8Q	6.3	0.15	2.6	2.8	1.10	Class-A Amp.	250	- 3	—	—	1.0	58000	1200	70	—	—	6SZ7
6T7	Duplex-Diode Triode	7V	6.3	0.15	1.8	3.1	1.70	Class-A Amp.	250	- 3.0	—	—	1.2	62000	1050	65	—	—	6T7
6V6	Beam Power Amplifier	7AC	6.3	0.45	2.0	7.5	0.7	Class-A <sub>1</sub> Amp. <sup>5</sup>	250	-12.5	250	4.5/7.0	45/47	52000	4100	218	5000	4.5	6V6
								Class-AB <sub>1</sub> Amp. <sup>6</sup>	250	-15.0	250	5/13	70/79	60000	3750	—	10000 <sup>8</sup>	10.0	
									285	-19.0	285	4/13.5	70/92	65000	3600	—	8000 <sup>8</sup>	14.0	
1611	Pentode Power Amplifier	7S	6.3	0.7	—	—	—	Audio Amp.	Characteristics same as 6F6										1611
1612	Pentagrid Amplifier	7T	6.3	0.3	7.5	11	0.001	Class-A Amp.	250	- 3.0	100	6.5	5.3	600000	1100	880	—	—	1612
1620	Triple-Grid Det.-Amp.	7R	6.3	0.3	—	—	—	Class-A Amp.	Characteristics same as 6J7										1620
1621	Power Amplifier Pentode	7S	6.3	0.7	—	—	—	Class-AB <sub>2</sub> Amp. <sup>6</sup>	300	-30.0	300	6.5/13	38/69	—	—	—	4000 <sup>8</sup>	5.0	1621
								Class-A <sub>1</sub> Amp. <sup>6</sup>	330	500*	—	—	—	—	—	—	5000 <sup>8</sup>	2.0	
1622	Beam Power Amplifier	7AC	6.3	0.9	—	—	—	Class-A <sub>1</sub> Amp.	300	-20.0	250	4/10.5	86/125	—	—	—	4000	10.0	1622
1851	Television Amp. Pentode	7R	6.3	0.45	11.5	5.2	0.02	Class-A Amp.	300	- 2.0	150	2.5	10	750000	9000	6750	—	—	1851

\* Cathode resistor—ohms.

<sup>1</sup> Screen tied to plate.

<sup>2</sup> For 6A7GT use base diagram 8AD.

<sup>3</sup> Grid bias—2 volts if separate oscillator excitation is used.

<sup>4</sup> Also Type "6SJ7Y."

<sup>5</sup> Values are for single tube.

<sup>6</sup> Values are for two tubes in push-pull.

<sup>7</sup> Max.-signal value.

<sup>8</sup> Plate-to-plate value.

TABLE II—6.3-VOLT GLASS TUBES WITH OCTAL BASES

(For "G" and "GT"-Type Tubes Not Listed Here, See Equivalent Type in Table I; Characteristics and Connections Will Be Identical)

Type	Name	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
			Volts	Amp.	In	Out	Plate-Grid													
2C22	Triode Amplifier	4AM	6.3	0.3	2.2	0.7	3.60	Class-A Amp.	300	-10.5	—	—	11	6600	3000	20	—	—	2C22	
								Class-A Amp. <sup>4</sup>	250	-45.0	—	—	60	800	—	—	2500	3.75		
6A5G	Triode Power Amplifier	6T	6.3	1.0	—	—	—	P.P. Class AB <sup>5</sup>	325	-68.0	—	—	80	—	5250	—	3000 <sup>8</sup>	15.0	6A5G	
								P.P. Class AB <sup>5</sup>	325	850*	—	—	80	—	—	5000 <sup>8</sup>	10.0			
								Class-A Amp.	250	0	—	—	—	—	—	—	—	—		
6AB6G	Direct-Coupled Amplifier	7AU	6.3	0.5	—	—	—	Class-A Amp.	250	0	—	—	Input	5.0	—	—	—	6AB6G		
									250	0	—	—	Output	34	40000	1800	72		8000	3.5
6AC5G	High- $\mu$ Power-Amplifier Triode	6Q	6.3	0.4	—	—	—	P.P. Class B <sup>5</sup>	250	0	—	—	5.0	36700	3400	125	10000 <sup>8</sup>	8.0	6AC5G	
								Dyn.-Coupled	250	—	—	—	32	—	—	—	7000	3.7		
6AC6G	Direct-Coupled Amplifier	7AU	6.3	1.1	—	—	—	Class-A Amp.	180	0	—	—	Input	7.0	—	3000	54	4000	3.8	6AC6G
									180	0	—	—	Output	45	—	—	—	—		
6AD5G	High- $\mu$ Triode	6Q	6.3	0.3	—	—	—	Class-A Amp.	250	- 2.0	—	—	0.9	—	1500	100	—	—	6AD5G	
6AD6G	Electron-Ray Tube	7AG	6.3	0.15	—	—	—	Indicator	100	—	—	—	0 for 90°; -23 for 135°; 45 for 0°.	—	—	—	—	—	6AD6G	
6AD7G	Triode-Pentode	8AY	6.3	0.85	—	—	—	Triode Amp.	250	-25.0	—	—	4.0	19000	325	6.0	—	—	6AD7G	
								Pentode Amp.	250	-16.5	250	6.5	34	80000	2500	—	7000	3.2		
6AE5G	Triode Amplifier	6Q	6.3	0.3	—	—	—	Class-A Amp.	95	-15.0	—	—	7.0	3500	1200	4.2	—	—	6AE5G	
6AE6G	Twin-Plate Triode with Single Grid	7AH	6.3	0.15	—	—	—	Remote cut-off	250	- 1.5	—	—	6.5	25000	1000	25	—	—	6AE6G	
								Sharp cut-off	250	- 1.5	—	—	4.5	35000	950	33	—	—		

TABLE II—6.3-VOLT GLASS TUBES WITH OCTAL BASES—Continued

Type	Name	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
			Volts	Amp.	In	Out	Plate-Grid													
6AE7GT	Twin-Input Triode	7AX	6.3	0.5	—	—	—	Driver Amplifier	250	-13.5	—	—	5.0	9300	1500	14	—	—	6AE7GT	
6AF5G	Triode Amplifier	6Q	6.3	0.3	—	—	—	Class-A Amplifier	180	-18.0	—	—	7.0	—	1500	7.4	—	—	6AF5G	
6AF7G	Twin Electron Ray	8AG	6.3	0.3	—	—	—	Indicator Tube	—	—	—	—	—	—	—	—	—	—	6AF7G	
6AG6G	Power-Amplifier Pentode	7S	6.3	1.25	—	—	—	Class-A Amplifier	250	-6.0	250	6.0	32	—	10000	—	8500	3.75	6AG6G	
6AH5G	Beam Power Amplifier	6AP	6.3	0.9	—	—	—	Class-A Amplifier	350	-18	250	—	—	33000	5200	—	4200	10.8	6AH5G	
6AH7GT	Twin Triode	8BE	6.3	0.3	—	—	—	Converter & Amp.	250	-9.0	—	—	12 <sup>1</sup>	6600	2400	16	—	—	6AH7GT	
6AL6G	Beam Power Amplifier	6AM	6.3	0.9	—	—	—	Class-A Amplifier	250	-14.0	250	5.0	72	22500	6000	—	2500	6.5	6AL6G	
6AL7GT	Electron-Ray Tube	8CH	6.3	0.15	—	—	—	Indicator	Outer edge of any of the three illuminated areas displaced $\frac{1}{16}$ in. min. outward with +5 volts to its electrode. Similar inward disp. with -5 volts. No pattern with -6 volts grid.										6AL7GT	
6AQ7GT	Duplex Diode Triode	8CK	6.3	0.3	2.3	1.5	2.8	Class-A Amplifier	250	-2.0	—	—	2.3	44000	16000	70	—	—	6AQ7GT	
6AR6	Beam Power Amp.	6BQ	6.3	1.2	11	7	0.55	Class-A Amplifier	250	-22.5	250	5	77	21000	5400	95	—	—	6AR6	
6AR7GT	Diode Triode Rectifier	8CG	6.3	0.3	1.4	1	2	Class-A Amplifier	250	-2	—	—	1.3	66500	1050	70	—	—	6AR7GT	
6AS7G	Low-Mu Twin Triode	8BD	6.3	2.5	—	—	—	D.C. Amplifier	135	250*	—	—	125	280	7500	2.1	—	—	6AS7G	
6B4G	Triode Power Amplifier	5S	6.3	1.0	—	—	—	Power Amplifier	Characteristics same as Type 6A3—Table IV										6B4G	
6B6G	Duplex-Diode High- $\mu$ Triode	7V	6.3	0.3	1.7	3.8	1.7	Detector-Amplifier	Characteristics same as Type 75—Table IV										6B6G	
6BG6	Beam Power Amplifier	5BT	6.3	0.9	11	6.5	0.5	Deflection Amp.	400	-50	350	6.0	70	—	6000	—	—	—	6BG6	
6C8G	Twin Triode	8G	6.3	0.3	—	—	—	Amp. 1 Section	250	-4.5	—	—	3.1	26000	1450	38	—	—	6C8G	
6D8G	Pentagrid Converter	8A	6.3	0.15	—	—	—	Converter	250	-3.0	100	Cathode current 13.0Ma.		Anode grid (No. 2) Volts = 250 <sup>2</sup>					6D8G	
6EBG	Triode-Hexode Converter	8O	6.3	0.3	—	—	—	Osc.-Mixer	250	-2.0	—	Triode Plate 150 volts							6EBG	
6F8G	Twin Triode	8G	6.3	0.6	—	—	—	Amplifier	250	-8.0	—	—	9 <sup>1</sup>	7700	2600	20	—	—	6F8G	
6G6G	Pentode Power Amplifier	7S	6.3	0.15	—	—	—	Class-A Amplifier	180	-9.0	180	2.5	15	175000	2300	400	10000	1.1	—	6G6G
6H4GT	Diode Rectifier	5AF	6.3	0.15	—	—	—	Class-A Amplifier <sup>2</sup>	180	-12.0	—	—	—	4750	2000	9.5	12000	0.25	—	
6H8G	Duo-Diode High- $\mu$ Pentode	8E	6.3	0.3	—	—	—	Detector	100	—	—	—	4.0	—	—	—	—	—	6H4GT	
6J8G	Triode Heptode	8H	6.3	0.3	—	—	—	Class-A Amplifier	250	-2.0	100	—	8.5	650000	2400	—	—	—	6H8G	
6K5GT	High- $\mu$ Triode	5U	6.3	0.3	2.4	3.6	2.0	Converter	250	-3.0	100	2.8	1.2	Anode-grid (No. 2) 250 volts max. <sup>3</sup> 5 ma.					6J8G	
6K6G	Pentode Power Amplifier	7S	6.3	0.4	—	—	—	Class-A Amplifier	250	-3.0	—	—	1.1	50000	1400	70	—	—	6K5GT	
6L5G	Triode Amplifier	6Q	6.3	0.15	—	—	—	Class-A Amplifier	250	-9.0	—	—	8.0	—	1900	17	—	—	6K6G	
6M6G	Power Amplifier Pentode	7S	6.3	1.2	—	—	—	Class-A Amplifier	250	-6.0	250	4.0	36	—	9500	—	7000	4.4	6L5G	
6M7G	Triple-Grid Amplifier	7R	6.3	0.3	—	—	—	R.F. Amplifier	250	-2.5	125	2.8	10.5	900000	3400	—	—	—	6M6G	
6M8GT	Diode Triode Pentode	8AU	6.3	0.6	—	—	—	Triode Amplifier	100	—	—	—	0.5	91000	1100	—	—	—	6M7G	
6N6G	Direct-Coupled Amplifier	7AU	6.3	0.8	—	—	—	Pentode Amplifier	100	-3.0	100	—	8.5	200000	1900	—	—	—	6M8GT	
6P5GT	Triode Amplifier	6Q	6.3	0.3	3.4	5.5	2.6	Power Amplifier	Characteristics same as Type 6B5—Table IV										6N6G	
6P7G	Triode-Pentode	7U	6.3	0.3	—	—	—	Class-A Amplifier	250	-13.5	—	—	5.0	9500	1450	13.8	—	—	6P5GT	
6P8G	Triode-Hexode Converter	8K	6.3	0.8	—	—	—	Class-A Amplifier	Characteristics same as 6F7—Table IV										6P7G	
6Q6G	Diode-Triode	6Y	6.3	0.15	—	—	—	Osc.-Mixer	250	-2.0	75	1.4	1.5	Triode Plate 100 v. 2.2 ma.					6P8G	
6R6G	Pentode Amplifier	6AW	6.3	0.3	—	—	—	Class-A Amplifier	250	-3.0	—	—	1.2	—	1050	65	—	—	6Q6G	
6S6GT	Triple-Grid Variable- $\mu$	5AK	6.3	0.45	—	—	—	Class-A Amplifier	250	-3.0	100	1.7	7.0	—	1450	1160	—	—	6R6G	
6S8GT	Triple Diode Triode	8CB	6.3	0.3	1.2	5	2	R.F. Amplifier	250	-2.0	100	3.0	13	350000	4000	—	—	—	6S6GT	
6SD7GT	Triple-Grid Semi-Variable- $\mu$	8M	6.3	0.3	9	7.5	.0035	Class-A Amplifier	250	-2.0	—	—	0.9	91000	—	100	—	—	6S8GT	
6SE7GT	Triple-Grid Amplifier	8N	6.3	0.3	8	7.5	.005	R.F. Amplifier	250	-1.5	100	1.5	4.5	1100000	3400	3750	—	—	6SD7GT	
6SH7L	Pentode R.F. Amp.	Fig. 44	6.3	0.3	—	—	—	R.F. Amplifier	100	-1.0	100	2.1	5.3	350000	4000	—	—	—	6SE7GT	
6SL7GT	Twin Triode	8BD	6.3	0.3	—	—	—	Class-A Amplifier	250	-1.0	150	1.4	10.8	900000	4900	—	—	—	6SH7L	
6SN7GT	Twin Triode	8BD	6.3	0.6	—	—	—	Amplifier	250	-2.0	—	—	2.3 <sup>1</sup>	44000	1600	70	—	—	6SL7GT	
6SU7GT	Twin Triode	8BD	6.3	0.3	—	—	—	Amplifier	250	-8.0	—	—	9.1	7700	2600	20	—	—	6SN7GT	
6SU7GT	Twin Triode	8BD	6.3	0.3	—	—	—	Class-A Amplifier	250	-2.0	—	—	2.3	44000	1600	70	—	—	6SU7GT	

574



TABLE II—6.3-VOLT GLASS TUBES WITH UCIAL BASES—Continued

Type	Name	Socket Connections	Fil. or Heater		Capacitance $\mu$ fd.			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
			Volts	Amp.	In	Out	Plate-Grid													
6T6GM	Triple-Grid Amplifier	6Z	6.3	0.45	—	—	—	R.F. Amplifier	250	- 1.0	100	2.0	10	1000000	5500	—	—	—	6T6GM	
6U6GT	Beam Power Amplifier	7AC	6.3	0.75	—	—	—	Class-A Amplifier	200	-14.0	135	3.0	56	20000	6200	—	3000	5.5	6U6GT	
6U7G	Triple Grid Variable- $\mu$	7R	6.3	0.3	5	9	.007	R.F. Amplifier	Characteristics same as Type 6D6—Table III										6U7G	
6V7G	Duplex Diode-Triode	7V	6.3	0.3	2	3.5	1.7	Detector-Amplifier	Characteristics same as Type 85—Table III										6V7G	
6W6GT	Beam Power Amplifier	7AC	6.3	1.25	—	—	—	Class-A Amplifier	135	- 9.5	135	12.0	61.0	—	9000	215	2000	3.3	6W6GT	
6W7G	Triple-Grid Det. Amplifier	7R	6.3	0.15	5	8.5	.007	Class-A Amplifier	250	- 3.0	100	2.0	0.5	1500000	1225	1850	—	—	6W7G	
6X6G	Electron-Ray Tube	7AL	6.3	0.3	—	—	—	Indicator Tube	250	0 v. for 300°, 2 ma. - 8 v. for 0°, 0 ma. Vane grid 125 v.										6X6G
6Y6G	Beam Power Amplifier	7AC	6.3	1.25	15	8	0.7	Class-A Amplifier	135	-13.5	135	3.0	60.0	9300	7000	—	2000	3.6	6Y6G	
6Y7G	Twin Triode Amplifier	8B	6.3	0.3	—	—	—	Class-B Amplifier	Characteristics same as Type 79—Table IV										6Y7G	
6Z7G	Twin Triode Amplifier	8B	6.3	0.3	—	—	—	Class-B Amplifier	180	0	—	—	8.4	—	—	—	12000	4.2	6Z7G	
									135	0	—	—	6.0	—	—	—	9000	2.5		
717A	Pentode Amplifier	8BK	6.3	0.175	—	—	—	Class-A Amplifier	120	- 2.0	120	2.5	7.5	390000	4000	—	—	—	717A	
1223	Pentode Amplifier	7R	6.3	0.3	—	—	—	Class-A Amplifier	Characteristics same as 6C6—Table IV										1223	
1635	Twin Triode Amplifier	8B	6.3	0.6	—	—	—	Class-B Amplifier	400	0	—	—	10/63	—	—	—	14000	17	1635	
7000	Low-Noise Amplifier	7R	6.3	0.3	—	—	—	Class-A Amplifier	Characteristics same as Type 6J7—Table I										7000	

\* Cathode resistor-ohms. <sup>1</sup> Per plate. <sup>2</sup> Screen tied to plate. <sup>3</sup> Through 20,000-ohm dropping resistor. <sup>4</sup> Values are for single tube. <sup>5</sup> Values are for two tubes in push-pull. <sup>6</sup> Plate-to-plate value.

TABLE III—7-VOLT LOCK-IN-BASE TUBES  
For other lock-in-base types see Tables VIII, IX, X and XIII

Type	Name	Socket Connections	Heater		Capacitance $\mu$ fd.			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
			Volts	Amp.	In	Out	Plate-Grid												
7A4	Triode Amplifier	5AC	7.0	0.32	3.4	3	4	Class-A Amplifier	250	- 8.0	—	—	9.0	7700	2600	20	—	—	7A4
7A5	Beam Power Amplifier	6AA	7.0	0.75	—	—	—	Class-A <sub>1</sub> Amplifier	125	- 9.0	125	3.2/8	37.5/40	17000	6100	—	2700	1.9	7A5
7A6	Twin Diode	7AJ	7.0	0.16	—	—	—	Rectifier	Max. A.C. volts per plate—150. Max. Output current—10 ma.										7A6
7A7	Remote Cut-off Pentode	8V	7.0	0.32	6	7	.005	R.F. Amplifier	250	- 3.0	100	2.0	8.6	80000	2000	1600	—	—	7A7
7AP	Multigrad Converter	8U	7.0	0.16	—	—	—	Osc.-Mixer	250	- 3.0	100	3.1	3.0	50000	Anode-grid 250 volts max. <sup>1</sup>				7A8
7AF7	Twin Triode	8AC	6.3	0.3	2.2	1.6	2.3	Class-A Amp.	250	-10	—	—	9.0	7600	2100	16	—	—	7AF7
7AG7	Sharp Cut-off Pentode	Fig. 45	7.0	0.16	—	—	—	Class-A <sub>1</sub> Amp.	250	250*	250	2.0	6.0	750000	4200	—	—	—	7AG7
7B4	High- $\mu$ Triode	5AC	7.0	0.32	3.6	3.4	1.6	Class-A Amplifier	250	- 2.0	—	—	0.9	66000	1500	100	—	—	7B4
7B5	Pentode Power Amplifier	6AE	7.0	0.43	—	—	—	Class-A <sub>1</sub> Amplifier	250	-18.0	250	5.5/10	32/33	68000	2300	—	7600	3.4	7B5
7B6	Duo-Diode Triode	8W	7.0	0.32	—	—	—	Class-A Amplifier	250	- 2.0	—	—	1.0	91000	1100	100	—	—	7B6
7B7	Remote Cut-off Pentode	8V	7.0	0.16	5	7	.005	R.F. Amplifier	250	- 3.0	100	2.0	8.5	700000	1700	1200	—	—	7B7
7B8	Pentagrid Converter	8X	7.0	0.32	—	—	—	Osc.-Mixer	250	- 3.0	100	2.7	3.5	360000	Anode-grid 250 volts max. <sup>1</sup>				7B8
7C5	Tetrode Power Amplifier	6AA	7.0	0.48	—	—	—	Class-A <sub>1</sub> Amplifier	250	-12.5	250	4.5/7	45/47	52000	4100	—	5000	4.5	7C5
7C6	Duo-Diode Triode	8W	7.0	0.16	2.4	3	1.4	Class-A Amplifier	250	- 1.0	—	—	1.3	100000	1000	100	—	—	7C6
7C7	Pentode Amplifier	8V	7.0	0.16	5.5	6.5	.007	R.F. Amplifier	250	- 3.0	100	0.5	2.0	2 meg.	1300	—	—	—	7C7
7D7	Triode-Hexode Converter	8AR	7.0	0.48	—	—	—	Osc.-Mixer	250	- 3.0	—	—	—	Triode Plate (No. 3) 150 v. 3.5 ma.				7D7	
7E6	Duo-Diode Triode	8W	7.0	0.32	—	—	—	Class-A Amplifier	250	- 9.0	—	—	9.5	8500	1900	16	—	—	7E6
7E7	Duo-Diode Pentode	8AE	7.0	0.32	4.6	4.6	.005	Class-A Amplifier	250	- 3.0	100	1.6	7.5	700000	1300	—	—	—	7E7
7F7	Twin Triode	8AC	7.0	0.32	—	—	—	Class-A Amplifier <sup>2</sup>	250	- 2.0	—	—	2.3	44000	1600	70	—	—	7F7
7F8	Twin Triode	8BW	6.3	0.30	2.8	1.4	1.2	R.F. Amplifier	250	- 2.5	—	—	10.0	10400	5000	—	—	—	7F8
									180	- 1.0	—	—	12.0	8500	7000	—			
7G7/1232	Triple-Grid Amplifier	8V	7.0	0.48	9	7	.007	Class-A Amplifier	250	- 2.0	100	2.0	6.0	800000	4500	—	—	—	7G7/1232

TABLE III—7-VOLT LOCK-IN-BASE TUBES—Continued

Type	Name	Socket Connections	Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
			Volts	Amp.	In	Out	Plate-Grid													
7G8/1206	Dual Tetrode	8BV	6.3	0.30	3.4	2.6	0.15	R.F. Amplifier <sup>2</sup>	250	- 2.5	100	0.8	4.5	225000	2100	—	—	—	7G8/1206	
7H7	Triple-Grid Semi-Variable- $\mu$	8V	7.0	0.32	8	7	.007	R.F. Amplifier	250	- 2.5	150	2.5	9.0	1000000	3500	—	—	—	7H7	
7J7	Triode-Hexode Converter	8AR	7.0	0.32	—	—	—	Osc.-Mixer	250	- 3.0	100	2.9	1.3	Triode Plate 250 v. Max. <sup>1</sup>			—	—	7J7	
7K7	Duo-Diode High- $\mu$ Triode	8BF	7.0	0.32	—	—	—	Class-A Amplifier	250	- 2.0	—	—	2.3	44000	1600	70	—	—	7K7	
7L7	Triple-Grid Amplifier	8V	7.0	0.32	8	6.5	.01	Class-A Amplifier	250	- 1.5	100	1.5	4.5	100000	3100	Cathode Resistor 250 ohms		—	—	7L7
7N7	Twin Triode	8AC	7.0	0.6	—	—	—	Class-A Amplifier <sup>2</sup>	250	- 8.0	—	—	9.0	7700	2600	20	—	—	7N7	
7Q7	Pentagrid Converter	8AL	7.0	0.32	—	—	—	Osc.-Mixer	250	0	100	8.0	3.4	800000	Grid No. 1 resistor 20000 ohms		—	—	7Q7	
7R7	Duo-Diode Pentode	8AE	7.0	0.32	5.6	5.3	.004	Class-A Amplifier	250	- 1.0	100	1.7	5.7	1000000	3200	—	—	—	7R7	
7S7	Triode Hexode Converter	8BL	7.0	0.32	—	—	—	Osc.-Mixer	250	- 2.0	100	2.2	1.7	2000000	Triode Plate 250 v. Max. <sup>1</sup>			—	—	7S7
7T7	Triple-Grid Amplifier	8V	7.0	0.32	8	7	.005	Class-A Amplifier	250	- 1.0	150	4.1	10.8	900000	4900	—	—	—	—	7T7
7V7	Triple-Grid Amplifier	8V	7.0	0.48	—	—	—	Class-A Amplifier	300	160*	150	3.9	9.6	300000	5800	—	—	—	—	7V7
7W7	Triple-Grid Variable- $\mu$	8BJ	7.0	0.48	—	—	—	Class-A Amplifier	300	- 2.2	150	3.9	10	300000	5800	—	—	—	—	7W7
7X7	Duo-Diode Triode	8BZ	6.3	0.3	—	—	—	Class-A Amplifier	250	- 1.0	—	—	1.9	67000	1500	100	—	—	—	7X7
1231	Pentode Amplifier	8V	6.3	0.45	8.5	6.5	.015	Class-A Amplifier	300	200*	150	2.5	10	700000	5500	3850	—	—	—	1231
1273	Nonmicrophonic Pentode	8V	7.0	0.32	6.0	6.5	.007	Class-A <sub>1</sub> Amplifier	250	- 3.0	100	0.7	2.2	1000000	1575	—	—	—	—	1273
									100	- 1.0	100	1.8	5.7	400000	2275	—	—	—	—	
XXL	Triode Oscillator	5AC	7.0	0.32	—	—	—	Oscillator	250	- 8.0	—	—	8.0	—	2300	20	—	—	—	XXL

\* Cathode resistor—ohms.

<sup>1</sup> Applied through 20000-ohm dropping resistor.

<sup>2</sup> Each section.

TABLE IV—6.3-VOLT GLASS RECEIVING TUBES

Type	Name	Base	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
				Volts	Amp.	In	Out	Plate-Grid													
2C21/1642	Twin-Triode Amplifier	M.	7BH	6.3	0.6	—	—	—	Class-A Amp.	250	- 16.5	—	—	8.3	7600	1375	10.4	—	—	2C21/1642	
									Class-A <sub>1</sub> Amp.	250	- 45	—	—	60	800	5250	4.2	2500	3.5		
6A3	Triode Power Amplifier	M.	4D	6.3	1.0	—	—	—	Class A <sub>1</sub> Amp. <sup>10</sup>	300	- 62	—	—	40	Power output for 2 tubes load plate-to-plate		3000 <sup>11</sup>	15	6A3		
									300	780*	40	40	5000 <sup>11</sup>	10							
6A4	Pentode Power Amplifier	M.	5B	6.3	0.3	—	—	—	Class-A Amp.	180	- 12.0	180	3.9	22	45500	2200	100	8000	1.4	6A4	
6A6	Twin Triode Amplifier	M.	7B	6.3	0.8	—	—	—	Class-B Amp.	250	0	—	—	Power output is for one tube at stated load, plate-to-plate		8300	8.0	6A6			
6A7	Pentagrid Converter	S.	7C	6.3	0.3	—	—	—	Converter	250	- 3.0	100	2.2	3.5	360000	Anode grid (No. 2) 200 volts max.			6A7		
6AB5/6N5	Electron-Ray Tube	S.	6R	6.3	0.15	—	—	—	Indicator Tube	180	Cut-off Grid Bias = - 12 v.		0.5	Target Current 2 ma.			—	6AB5/6N5			
6AF6G	Electron-Ray Tube Twin Indicator Type	S.	7AG	6.3	0.15	—	—	—	Indicator Tube	135	Ray Control Voltage = 81 for 0° Shadow Angle. Target current 1.5 ma.			6AF6G							
									100	Ray Control Voltage = 60 for 0° Shadow Angle. Target current 0.9 ma.											
6B5	Direct-Coupled Power Amplifier	M.	6AS	6.3	0.8	—	—	—	Class-A Amp. <sup>9</sup>	300	0	—	6 <sup>1</sup>	45	241000	2400	58	7000	4.0	6B5	
									400	- 13.0	—	4.5 <sup>1</sup>	40	—	—	10000 <sup>11</sup>	20				
6B7	Duplex-Diode Pentode	S.	7D	6.3	0.3	3.5	9.5	.007	Pentode R.F. Amp.	250	- 3.0	125	2.3	9.0	650000	1125	730	—	—	6B7	
6C6	Triple-Grid Amplifier	S.	6F	6.3	0.3	5	6.5	.007	R.F. Amplifier	250	- 3.0	100	0.5	2.0	1500000	1225	1500	—	—	6C6	
6C7	Duplex Diode Triode	S.	7G	6.3	0.3	—	—	—	Class-A Amp.	250	- 9.0	—	—	4.5	—	20	1250	—	—	6C7	
6D6	Triple-Grid Variable- $\mu$	S.	6F	6.3	0.3	4.7	6.5	.007	R.F. Amplifier	250	- 3.0	100	2.0	8.2	800000	1600	1280	—	—	6D6	
6D7	Triple-Grid Amplifier	S.	7H	6.3	0.3	5.2	6.8	.01	Class-A Amp.	250	- 3.0	100	0.5	2.0	—	1600	1280	—	—	6D7	
6E5	Electron-Ray Tube	S.	6R	6.3	0.3	—	—	—	Indicator Tube	250	0	—	—	0.25	Target Current 4 ma.			—	—	6E5	
6E6	Twin Triode Amplifier	M.	7B	6.3	0.6	—	—	—	Class-A Amp.	250	- 27.5	—	—	Per plate—18.0		3500	1700	6.0	14000	1.6	6E6
6E7	Triple-Grid Variable- $\mu$	S.	7H	6.3	0.3	—	—	—	R.F. Amplifier	Characteristics same as 6U7G—Table II										6E7	

TABLE IV—6.3-VOLT GLASS RECEIVING TUBES—Continued

Type	Name	Base	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type		
				Volts	Amp.	In	Out	Plate-Grid														
6F7	Triode Pentode	S.	7E	6.3	0.3	—	—	—	Triode Unit Amp.	100	— 3.0	—	—	3.5	16000	500	8	—	—	6F7		
						Pentode Unit Amplifier	250	— 3.0	100	1.5	6.5	850000	1100	900	—	—						
6U5/6G5	Electron-Ray Tube	S.	6R	6.3	0.3	—	—	—	Indicator Tube	250	Cut-off Grid Bias = -22 v.		0.24	Target Current 4 ma.						6U5/6G5		
6H5	Electron-Ray Tube	S.	6R	6.3	0.3	—	—	—	Indicator Tube	100	Cut-off Grid Bias = -8 v.		0.19	Target Current 1 ma.						6H5		
						—	—	—	—	—	—	—	—	—	—	—	—	—	—		—	—
6SB7Y	Pentagrid Converter	O.	8R	6.3	0.3	9.6	9.2	—	Converter	100	- 1	100	10.2	3.6	500000	900	—	—	—	6SB7Y		
						—	—	—	—	—	—	—	—	—	—	—	—	—	—		—	—
						—	—	—	—	—	—	—	—	—	—	—	—	—	—		—	—
6T5	Electron-Ray Tube	S.	6R	6.3	0.3	—	—	—	Indicator Tube	250	Cut-off Grid Bias = -12 v.		0.24	Target Current 4 ma.						6T5		
						—	—	—	—	—	—	—	—	—	—	—	—	—	—	—	—	—
36	Tetrode R.F. Amplifier	S.	5E	6.3	0.3	3.8	9	.007	R.F. Amplifier	250	- 3.0	90	1.7	3.2	550000	1080	595	—	—	36		
37	Triode Detector Amplifier	S.	5A	6.3	0.3	3.5	2.9	2	Class-A Amp.	250	-18.0	—	—	7.5	8400	1100	9.2	—	—	37		
38	Pentode Power Amplifier	S.	5F	6.3	0.3	3.5	7.5	0.3	Class-A Amp.	250	-25.0	250	3.8	22.0	100000	1200	120	10000	2.5	38		
39/44	Variable- $\mu$ R.F. Amplifier	S.	5F	6.3	0.3	3.8	10	.007	R.F. Amplifier	250	- 3.0	90	1.4	5.8	1000000	1050	1050	—	—	39/44		
41	Pentode Power Amplifier	S.	6B	6.3	0.4	—	—	—	Class-A Amp.	250	-18.0	250	5.5	32.0	68000	2200	150	7600	3.4	41		
42	Pentode Power Amplifier	M.	6B	6.3	0.7	—	—	—	Class-A Amp.	250	-16.5	250	6.5	34.0	100000	2200	220	7000	3.0	42		
52	2-Grid Triode	M.	Fig. 33	6.3	0.3	—	—	—	Class-A Preamp. <sup>4</sup>	110	0	—	—	43.0	1750	3000	5.2	2000	1.5	52		
						—	—	—	Class-B, 2 tubes <sup>5</sup>	180	0	—	—	3.0	—	—	—	—	—		—	—
56A5	Triode Amplifier	S.	5A	6.3	0.4	—	—	—	Class-A Amp.	Characteristics same as 56										56A5		
57A5	Pentode	S.	6F	6.3	0.4	—	—	—	R.F. Amplifier	Characteristics same as 57										57A5		
58A5	Triode-Grid Variable- $\mu$	S.	6F	6.3	0.4	—	—	—	R.F. Amplifier	Characteristics same as 58										58A5		
75	Duplex-Diode Triode	S.	6G	6.3	0.3	1.7	3.8	1.7	Triode Amplifier	250	- 1.35	—	—	0.4	91000	1100	100	—	—	75		
76	Triode Detector Amplifier	S.	5A	6.3	0.3	3.5	2.5	2.8	Class-A Amp.	250	-13.5	—	—	5.0	9500	1450	13.8	—	—	76		
77	Triple-Grid Detector	S.	6F	6.3	0.3	4.7	11	.007	R.F. Amplifier	250	- 3.0	100	0.5	2.3	1500000	1250	1500	—	—	77		
78	Triple-Grid Variable- $\mu$	S.	6F	6.3	0.3	4.5	11	.007	R.F. Amplifier	250	- 3.0	100	1.7	7.0	800000	1450	1160	—	—	78		
79	Twin Triode Amplifier	S.	6H	6.3	0.6	—	—	—	Class-B Amp.	250	0	—	—	—	Power output is for one tube			14000	8.0	79		
85	Duplex-Diode Triode	S.	6G	6.3	0.3	1.5	4.3	1.5	Class-A Amp.	250	-20.0	—	—	8.0	7500	1100	8.3	20000	0.35	85		
85A5	Duplex-Diode Triode	S.	6G	6.3	0.3	—	—	—	Class-A Amp.	250	- 9.0	—	—	5.5	—	1250	20	—	—	85A5		
						—	—	—	—	—	—	—	—	—	—	—	—	—	—	—	—	
89	Triple-Grid Power Amp.	S.	6F	6.3	0.4	—	—	—	Triode Amp. <sup>2</sup>	250	-31.0	—	—	32.0	2600	1800	4.7	5500	0.9	89		
						—	—	—	—	—	—	—	—	—	—	—	—	—	—		—	—
1221	Pentode R.F. Amplifier	S.	6F	6.3	0.3	—	—	—	Class-A Amp.	Special non-microphonic. Characteristics same as 6C6										1221		
1603 <sup>3</sup>	Triple-Grid Amplifier	M.	6F	6.3	0.3	—	—	—	Class-A Amp.	Characteristics same as 6C6										1603		
7700 <sup>3</sup>	Triple-Grid Amplifier	S.	6F	6.3	0.3	—	—	—	Class-A Amp.	Characteristics same as 6C6										7700		

\* Cathode bias resistor—ohms.

<sup>1</sup> Current to input plate (P<sub>1</sub>).

<sup>2</sup> Grids Nos. 2 and 3 connected to plate.

<sup>3</sup> Low noise, nonmicrophonic tubes.

<sup>4</sup> G<sub>2</sub> tied to plate.

<sup>5</sup> G<sub>1</sub> tied to G<sub>2</sub>.

<sup>6</sup> Osc. grid leak ohms.

<sup>7</sup> Screen dropping resistor ohms.

<sup>8</sup> Grid No. 2, screen; grid No. 3, suppressor.

<sup>9</sup> Values for single tube.

<sup>10</sup> Values for two tubes in push-pull.

<sup>11</sup> Plate-to-plate value.

TABLE V—2.5-VOLT RECEIVING TUBES

Type	Name	Base	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
2S/4S	Duodiode	M.	5D	2.5	1.35	—	—	—	Detector	At 50 d.c. Volts per plate, cathode ma. = 80										2S/4S
2A3	Triode Power Amplifier	M.	4D	2.5	2.5	7.5	5.5	16.5	Class-A Amp.	Characteristics same as Type 6A3, Table IV										2A3
2A5	Pentode Power Amplifier	M.	6B	2.5	1.75	—	—	—	Class-A Amp.	Characteristics same as Type 42, Table IV										2A5
2A6	Duplex-Diode Triode	S.	6G	2.5	0.8	1.7	3.8	1.7	Class-A Amp.	Characteristics same as Type 75, Table IV										2A6
2A7	Pentagrid Converter	S.	7C	2.5	0.8	—	—	—	Osc.-Mixer	Characteristics same as Type 6A7, Table IV										2A7

TABLE V—2.5-VOLT RECEIVING TUBES—Continued

Type	Name	Base	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
2B6	Direct-Coupled Amplifier	M.	7J	2.5	2.25	—	—	—	Amplifier	250	-24.0	—	—	40.0	5150	3500	18.0	5000	4.0	2B6
2B7	Duplex-Diode Pentode	S.	7D	2.5	0.8	3.5	9.5	.007	Pentode Amp.	Characteristics same as Type 6B7—Table IV										2B7
2E5	Electron-Ray Tube	S.	6R	2.5	0.8	—	—	—	Indicator Tube	Characteristics same as Type 6E5—Table IV										2E5
2G5	Electron-Ray Tube	S.	6R	2.5	0.8	—	—	—	Indicator Tube	Characteristics same as 6U5/6G5—Table IV										2G5
24-A	Tetrode R.F. Amplifier	M.	5E	2.5	1.75	5.3	10.5	.007	Screen-Grid R.F. Amplifier	250	-3.0	90	1.7	4.0	600000	1050	630	—	—	24-A
									Bias Detector	250	-5.0	20/45	Plate current adjusted to 0.1 ma. with no signal							
27	Triode Detector-Amplifier	M.	5A	2.5	1.75	3.1	2.3	3.3	Class-A Amp.	250	-21.0	—	—	5.2	9250	975	9.0	—	—	27
									Bias Detector	250	-30.0	—	Plate current adjusted to 0.2 ma. with no signal							
35/51	Variable- $\mu$ Amplifier	M.	5E	2.5	1.75	5.3	10.5	.007	Screen-Grid R.F. Amplifier	250	-3.0	90	2.5	6.5	400000	1050	420	—	—	35/51
45	Triode Power Amplifier	M.	4D	2.5	1.5	4	3	7	Class-A Amp.	275	-56.0	—	—	36.0	1700	2050	3.5	4500	2.00	45
46	Dual-Grid Power Amp.	M.	5C	2.5	1.75	—	—	—	Class-A Amp. <sup>2</sup>	250	-33.0	—	—	22.0	2380	2350	5.6	6400	1.25	46
									Class-B Amp. <sup>3</sup>	400	0	—	Power output for 2 tubes							
47	Pentode Power Amplifier	M.	5B	2.5	1.75	8.6	13	1.2	Class-A Amp.	250	-16.5	250	6.0	31.0	60000	2500	150	7000	2.7	47
53	Twin Triode Amplifier	M.	7B	2.5	2.0	—	—	—	Class-B Amp.	Characteristics same as Type 6A6, Table IV										53
55	Duplex-Diode Triode	S.	6G	2.5	1.0	1.5	4.3	1.5	Class-A Amp.	Characteristics same as Type 85, Table IV										55
56	Triode Amplifier, Detector	S.	5A	2.5	1.0	3.2	2.4	3.2	Class-A Amp.	Characteristics same as Type 76, Table IV										56
57	Triple-Grid Amplifier	S.	6F	2.5	1.0	—	—	—	R.F. Amplifier	250	-3.0	100	0.5	2.0	1500000	1225	1500	—	—	57
58	Triple-Grid Variable- $\mu$	S.	6F	2.5	1.0	4.7	6.3	.007	Screen-Grid R.F. Amplifier	250	-3.0	100	2.0	8.2	800000	1600	1280	—	—	58
									Class-A Triode <sup>4</sup>	250	-28.0	—	—	26.0	2300	2600	6.0	5000	1.25	
59	Triple-Grid Power Amplifier	M.	7A	2.5	2.0	—	—	—	Class-A Pentode <sup>5</sup>	250	-18.0	250	9.0	35.0	40000	2500	100	6000	3.0	59
RK15	Triode Power Amplifier	M.	4D <sup>1</sup>	2.5	1.75	—	—	—	Characteristics same as Type 46 with Class-B connections										RK15	
RK16	Triode Power Amplifier	M.	5A	2.5	2.0	—	—	—	Characteristics same as Type 59 with Class-A triode connections										RK16	
RK17	Pentode Power Amplifier	M.	5F	2.5	2.0	—	—	—	Characteristics same as Type 2A5										RK17	

<sup>1</sup> Grid connection to cap; no connection to No. 3 pin. <sup>2</sup> Grid No. 2 tied to plate. <sup>3</sup> Grids Nos. 1 and 2 tied together. <sup>4</sup> Grids Nos. 2 and 3 connected to plate. <sup>5</sup> Grid No. 2, screen; grid No. 3, suppressor.

TABLE VI—2.0-VOLT BATTERY RECEIVING TUBES

Type	Name	Base	Socket Connections	Filament		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
1A4P	Variable- $\mu$ Pentode	S.	4M	2.0	0.06	5	11	.007	R.F. Amplifier	180	-3.0	67.5	0.8	2.3	1000000	750	750	—	—	1A4P
1A4T	Variable- $\mu$ Tetrode	S.	4K	2.0	0.06	5	11	.007	R.F. Amplifier	180	-3.0	67.5	0.7	2.3	960000	750	720	—	—	1A4T
1A6	Pentagrid Converter	S.	6L	2.0	0.05	—	—	—	Converter	180	-3.0	67.5	2.4	1.3	500000	Anode grid (No. 2) 180 max. volts				1A6
1B4P/951	Pentode R.F. Amplifier	S.	4M	2.0	0.05	5	11	.007	R.F. Amplifier	180	-3.0	67.5	0.6	1.7	1500000	650	1000	—	—	1B4P/951
										90	-3.0	67.5	0.7	1.6	1000000	600	550	—	—	
1B5/255	Duplex-Diode Triode	S.	6M	2.0	0.06	1.6	1.9	3.6	Triode Class-A	135	-3.0	—	—	0.8	35000	575	20	—	—	1B5/255
1C6	Pentagrid Converter	S.	6L	2.0	0.12	10	10	—	Converter	180	-3.0	67.5	2.0	1.5	750000	Anode grid (No. 2) 135 max. volts				1C6
1F4	Pentode Power Amplifier	M.	5K	2.0	0.12	—	—	—	Class-A Amp.	135	-4.5	135	2.6	8.0	200000	1700	340	16000	0.34	1F4
1F6	Duplex-Diode Pentode	S.	6W	2.0	0.06	4	9	.007	R.F. Amplifier	180	-1.5	67.5	0.5	2.0	1000000	650	650	—	—	1F6
									A.F. Amplifier	135	-1.0	135	Plate, 0.25 megohm; screen, 1.0 megohm							

TABLE VI—2.0-VOLT BATTERY RECEIVING TUBES—Continued

Type	Name	Base	Socket Connections	Filament		Capacitance $\mu$ fd.			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
15	R.F. Pentode	S.	5F	2.0	0.22	2.3	7.8	0.01	R.F. Amplifier	135	— 1.5	67.5	0.3	1.85	800000	750	600	—	—	15
19	Twin-Triode Amplifier	S.	6C	2.0	0.26	—	—	—	Class-B Amp.	135	0	—	—	—	Load plate-to-plate	—	10000	2.1	19	
30	Triode Detector Amplifier	S.	4D	2.0	0.06	—	—	—	Class-A Amp.	180	—13.5	—	—	3.1	10300	900	9.3	—	30	
31	Triode Power Amplifier	S.	4D	2.0	0.13	3.5	2.7	5.7	Class-A Amp.	180	—30.0	—	—	12.3	3600	1050	3.8	5700	0.375	31
32	Tetrode R.F. Amplifier	1A.	4K	2.0	0.06	5.3	10.5	.015	R.F. Amplifier	180	— 3.0	67.5	0.4	1.7	1200000	650	780	—	32	
33	Pentode Power Amplifier	1A.	5K	2.0	0.26	8	12	1	Class-A Amp.	180	—18.0	180	5.0	22.0	55000	1700	90	6000	1.4	33
34	Variable- $\mu$ Pentode	M.	4M	2.0	0.06	6	11	.015	R.F. Amplifier	180	— 3.0	67.5	1.0	2.8	1000000	620	620	—	34	
49	Dual-Grid Power Amp.	M.	5C	2.0	0.12	—	—	—	Class-A Amp. <sup>1</sup>	135	—20.0	—	—	6.0	4175	1125	4.7	11000	0.17	49
									Class-B Amp. <sup>2</sup>	180	0	—	—	—	—	—	—	—	—	
840	R.F. Pentode	S.	5J	2.0	0.13	—	—	—	Class-A Amp.	180	— 3.0	67.5	0.7	1.0	1000000	400	400	—	840	
950	Pentode Power Amplifier	M.	5K	2.0	0.12	—	—	—	Class-A Amp.	135	—16.5	135	2.0	7.0	100000	1000	100	13500	0.45	950
RK24	Triode Amplifier	M.	4D	2.0	0.12	—	—	—	Class-A Amp.	180	—13.5	—	—	8.0	5000	1600	8.0	12000	0.25	RK24
1229	Tetrode R.F. Amplifier	M.	4K	2.0	0.06	—	—	—	Class-A Amp.	Special Type 32 for low grid current applications										1229

<sup>1</sup> Grid No. 2 tied to plate.

<sup>2</sup> Grids Nos. 1 and 2 tied together.

TABLE VII—2.0-VOLT BATTERY TUBES WITH OCTAL BASES

Type	Name	Socket Connections	Filament		Capacitance $\mu$ fd.			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
			Volts	Amp.	In	Out	Plate-Grid												
1C7G	Pentagrid Converter	7Z	2.0	0.06	—	—	—	Converter	Characteristics same as Type 1C6—Table VI										1C7G
1D5GP	Variable- $\mu$ R.F. Pentode	5Y	2.0	0.06	5	11	.007	R.F. Amplifier	Characteristics same as Type 1A4P—Table VI										1D5GP
1D5GT	Variable- $\mu$ R.F. Tetrode	5R	2.0	0.06	—	—	—	R.F. Amplifier	180	— 3.0	67.5	0.7	2.2	600000	650	—	—	—	1D5GT
1D7G	Pentagrid Converter	7Z	2.0	0.06	—	—	—	Converter	Characteristics same as Type 1A6—Table VI										1D7G
1E5GP	R.F. Amplifier Pentode	5Y	2.0	0.06	5	11	.007	R.F. Amplifier	Characteristics same as Type 1B4—Table VI										1E5GP
1E7G	Double Pentode Power Amp.	8C	2.0	0.24	—	—	—	Class-A Amplifier	135	— 7.5	135	2.0 <sup>1</sup>	6.5 <sup>1</sup>	220000	1600	350	24000	0.65	1E7G
1F5G	Pentode Power Amplifier	6X	2.0	0.12	—	—	—	Class-A Amplifier	Characteristics same as Type 1F4—Table VI										1F5G
1F7GV <sup>2</sup>	Duplex-Diode Pentode	7AD	2.0	0.06	3.8	9.5	0.01	Detector-Amplifier	Characteristics same as Type 1F6—Table VI										1F7GV
1G5G	Pentode Power Amplifier	6X	2.0	0.12	—	—	—	Class-A Amplifier	135	—13.5	135	2.5	8.7	160000	1550	250	9000	0.55	1G5G
1H4G	Triode Amplifier	5S	2.0	0.06	—	—	—	Detector-Amplifier	Characteristics same as Type 30—Table VI										1H4G
1H6G	Duplex-Diode Triode	7AA	2.0	0.06	1.6	1.9	3.6	Detector-Amplifier	Characteristics same as Type 1B5—Table VI										1H6G
1J5G	Pentode Power Amplifier	6X	2.0	0.12	—	—	—	Class-A Amplifier	135	—16.5	135	2.0	7.0	—	950	100	13500	0.45	1J5G
1J6G	Twin Triode	7AB	2.0	0.24	—	—	—	Class-B Amplifier	Characteristics same as Type 19—Table VI										1J6G
4A6G	Twin Triode	8L	2.0	0.12	—	—	—	Class-A, 1 section	90	— 1.5	—	—	1.1	26600	750	20	—	—	4A6G
			4.0	0.06	—	—	—	Class-B, 2 sections	90	— 1.5	—	—	1.1 <sup>3</sup>	—	—	—	8000	1.0	

<sup>1</sup> Total current for both sections; no signal.

<sup>2</sup> Also Type G or GH.

<sup>3</sup> Max. signal plate current = 10.8 Ma.

TABLE VIII—1.5-VOLT FILAMENT BATTERY TUBES

See also Table X for Special 1.4-volt Tubes

Type	Name	Base	Socket Connections	Filament		Capacitance $\mu$ fd.			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output M-watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
1A5G	Pentode Power Amplifier	O.	6X	1.4	0.05	—	—	—	Class-A <sub>1</sub> Amp.	90	—4.5	90	0.8	4.0	300000	850	240	25000	115	1A5G
1A7G	Pentagrid Converter	O.	7Z	1.4	0.05	—	—	—	Osc.-Mixer	90	0	45	0.6	0.55	600000	Anode-grid volts 90			1A7G	

TABLE VIII—1.5-VOLT FILAMENT BATTERY TUBES—Continued

Type	Name	Base	Socket Connections	Filament		Capacitance $\mu\text{mfd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output M-watts	Type	
				Volts	Amp.	In	Out	Plate-Grid													
1A85	Pentode R.F. Amplifier	O.	5B $\dot{F}$	1.2	0.05	2.8	4.2	0.25	R.F. Amplifier	90	0	90	0.8	3.5	275000	1100	—	—	—	1A85	
1B7G	Pentagrid Converter	O.	7Z	1.4	0.1	—	—	—	Converter	150	-1.5	150	2.0	6.8	125000	1350	—	—	—	1B7G	
1B8GT	Diode Triode Pentode	O.	8AW	1.4	0.1	—	—	—	Triode Amplifier Pentode Amp.	90	0	—	—	0.15	240000	275	—	—	—	1B8GT	
1C5G	Pentode Power Amplifier	O.	6X	1.4	0.1	—	—	—	Class-A <sub>1</sub> Amp.	90	-6.0	90	1.4	6.3	—	11500	14000	210	—	1C5G	
1D8GT	Diode Triode Pentode	O.	8AJ	1.4	0.1	—	—	—	Triode Amp. Pentode Amp.	90	-7.5	90	1.6	7.5	115000	1550	165	8000	240	1D8GT	
1E4G	Triode Amplifier	O.	5S	1.4	0.05	2.4	6	2.40	Class-A Amp.	90	0	—	—	4.5	11000	1325	14.5	—	—	1E4G	
1G4G	Triode Amplifier	O.	5S	1.4	0.05	2.2	3.4	2.80	Class-A Amp.	90	-3.0	—	—	1.5	17000	825	14	—	—	1G4G	
1G6G	Twin Triode	O.	7AB	1.4	0.1	—	—	—	Class-A Amp. Class-B Amp.	90	0	—	—	1.0	45000	675	30	—	—	1G6G	
1H5G	Diode High- $\mu$ Triode	O.	5Z	1.4	0.05	1.1	6	1.00	Class-A Amp.	90	0	—	—	1/7	34 volts input per grid	—	—	12000	675	—	1H5G
1LA4	Pentode Power Amplifier	L.	5AD	1.4	0.05	—	—	—	Class-A Amp.	90	0	—	—	0.14	240000	275	65	—	—	1LA4	
1LA6	Pentagrid Converter	L.	7AK	1.4	0.05	—	—	—	Converter	90	0	45	0.6	0.55	Characteristics same as 1A5G					1LA6	
1LB4	Pentode Power Amplifier	L.	5AD	1.4	0.05	—	—	—	Class-A Amp.	90	-9	90	1.0	5.0	200000	925	—	12000	200	—	1LB4
1LB6	Heptode Converter	L.	8AX	1.4	0.05	—	—	—	Converter	90	0	67.5	2.2	0.4	Grid No. 4—67.5 v., No. 5—0 v.					1LB6	
1LC5	Triple-Grid Variable- $\mu$	L.	7AO	1.4	0.05	3.2	7	.007	R.F. Amplifier	90	0	45	0.2	1.15	1500000	775	—	—	—	—	1LC5
1LC6	Pentagrid Converter	L.	7AK	1.4	0.05	—	—	—	Converter	90	0	35	0.7	0.75	Anode Grid Volts 45					1LC6	
1LD5	Diode Pentode	L.	6AX	1.4	0.05	3.2	6	0.18	Class-A Amp.	90	0	45	0.1	0.6	950000	600	—	—	—	—	1LD5
1LE3	Triode Amplifier	L.	4AA	1.4	0.05	1.7	3	1.70	Class-A Amp.	90	0	—	—	4.5	11200	1300	—	—	—	—	1LE3
1LG5	Pentode R.F. Amp.	L.	Fig. 42	1.4	0.05	—	—	—	Class-A Amp.	90	-3	—	—	1.3	19000	760	14.5	—	—	—	1LG5
1LH4	Diode High- $\mu$ Triode	L.	5AG	1.4	0.05	1.1	6	1.00	Class-A Amp.	90	0	45	0.4	1.7	1000000	800	—	—	—	—	1LH4
1LN5	Triple-Grid Amplifier	L.	7AO	1.4	0.05	3.4	8	.007	Class-A Amp.	90	0	—	—	0.15	240000	275	65	—	—	—	1LN5
1NSG	Pentode R.F. Amplifier	O.	5Y	1.4	0.05	3	10	.007	Class-A Amp.	90	0	90	0.3	1.2	1500000	750	—	—	—	—	1NSG
1N6G	Diode-Power-Pentode	O.	7AM	1.4	0.05	—	—	—	Class-A Amp.	90	-4.5	90	0.6	3.1	300000	800	—	25000	100	—	1N6G
1P5G	Triple-Grid Pentode	O.	5Y	1.4	0.05	3	10	.007	R.F. Amplifier	90	0	90	0.7	2.3	800000	800	640	—	—	—	1P5G
1Q5G	Tetode Power Amplifier	O.	6AF	1.4	0.1	—	—	—	Class-A Amp.	85	-5.0	85	1.2	7.2	700000	1950	—	—	—	—	1Q5G
1R4/1294	U.h.f. Diode	L.	4AH	1.4	0.15	—	—	—	Rectifier	90	-4.5	90	1.6	9.5	75000	2100	—	—	—	—	1R4/1294
1SA6GT	R.F. Pentode	O.	6CA	1.4	0.05	5.2	8.6	0.31	R.F. Amplifier	90	0	67.5	0.68	2.45	800000	970	—	—	—	—	1SA6GT
1SB6GT	Diode Pentode	O.	6CB	1.4	0.05	3.2	3	0.25	Class-A Amp. R.C. Amplifier	90	0	67.5	0.38	1.45	700000	665	—	—	—	—	1SB6GT
1T5GT	Beam Power Amplifier	O.	6AF	1.4	0.05	4.8	8	0.50	Class-A Amp.	90	0	90	—	—	Screen resistor 5 meg., grid 10 meg.			1 meg.	110	—	1T5GT
387/1291	U.h.f. Twin Triode	L.	7BE	1.4	0.22	—	—	—	Class-A Amp.	90	-6.0	90	1.4	6.5	—	1150	—	14000	170	—	387/1291
1293	U.h.f. Triode	L.	Fig. 2	1.4	0.11	—	—	—	Class-A Amp.	90	0	—	—	5.2	11350	1850	21	—	—	—	1293
3D6/1299	U.h.f. Tetode	L.	6BB	2.8	0.11	7.5	6.5	0.30	Class-A Amp.	135	-6	90	0.7	5.7	—	2200	—	13000	500	—	3D6/1299
CK501	Pentode Voltage Amplifier	-1	-7	1.25	0.033	—	—	—	Class-A Amp.	30	0	30	0.06	0.3	1000000	325	—	—	—	—	CK501
CK502	Pentode Output Amplifier	-1	-7	1.25	0.033	—	—	—	Class-A Amp.	45	-1.25	45	0.055	0.28	1500000	300	—	—	—	—	CK502
CK503	Pentode Output Amplifier	-1	-7	1.25	0.033	—	—	—	Class-A Amp.	30	0	30	0.13	0.55	500000	400	—	60000	3	—	CK503
CK504	Pentode Output Amplifier	-1	-7	1.25	0.033	—	—	—	Class-A Amp.	30	0	30	0.33	1.5	150000	600	—	20000	6	—	CK504
CK505	Pentode Voltage Amplifier	-1	-7	0.625	0.33	—	—	—	Class-A Amp.	30	0	30	0.07	0.17	1100000	140	—	—	—	—	CK505
CK506	Pentode Output Amplifier	-1	-7	1.25	0.05	—	—	—	Class-A <sub>1</sub> Amp.	45	-1.25	45	0.08	0.2	2000000	150	—	—	—	—	CK506
CK507	Pentode Output Amplifier	-1	-7	1.25	0.05	—	—	—	Class-A <sub>1</sub> Amp.	45	-4.5	45	0.4	1.25	120000	500	—	30000	25	—	CK507

TABLE IX—HIGH-VOLTAGE HEATER TUBES—Continued

Type	Name	Base	Socket Connections	Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
26A7GT	Twin Beam-Power Audio Amplifier	O.	8BU	26.5	0.6	Each Unit Push-Pull			Class-A Amp. <sup>3</sup>	26.5	- 4.5	26.5	2/5.5	20/20.5	2500	5500	—	1500	0.2	26A7GT
						Class-AB Amo. <sup>3</sup>	26.5	- 7.0	26.5	2/8.5	19/30	—	—	—	2500 <sup>4</sup>	0.5	32L7GT			
32L7GT	Diode-Beam Tetrode	O.	8Z	32.5	0.3	—	—	—	Class-A Amp.	110	- 7.5	110	3	40	15000	6000	—	2500	1.5	32L7GT
35A5	Beam Power Amplifier	L.	6AA	35	0.15	—	—	—	Class-A <sub>1</sub> Amp.	110	- 7.5	110	3/7	40/41	14000	5800	—	2500	1.5	35A5
35L6G	Beam Power Amplifier	O.	7AC	35	0.15	13	9.5	0.80	Class-A <sub>1</sub> Amp.	110	- 7.5	110	3/7	40/41	13800	5800	—	2500	1.5	35L6G
43	Pentode Power Amplifier	M.	6B	25	0.3	8.5	12.5	0.20	Class-A Amp.	95	-15.0	95	4.0	20.0	4500 <sup>3</sup>	2300	90	4500	0.90	43
48	Tetrode Power Amplifier	M.	6A	30	0.4	—	—	—	Class-A Amp.	96	-19.0	96	9.0	52.0	—	3800	—	1500	2.0	48
50A5	Beam Power Amplifier	L.	6AA	50	0.15	—	—	—	Class-A <sub>1</sub> Amp.	110	- 7.5	110	4/11	49/50	10000	8200	—	2000	2.2	50A5
50C6GT	Beam Power Amplifier	O.	7AC	50	0.15	—	—	—	Class-A <sub>1</sub> Amp.	135	-13.5	135	3.5/11.5	58/60	9300	7000	—	2000	3.6	50C6GT
50L6GT	Beam Power Amplifier	O.	7AC	50	0.15	—	—	—	Class-A Amp.	110	- 7.5	110	4/11	49/50	—	8200	82	2000	2.2	50L6GT
70A7GT	Diode-Beam Tetrode	O.	8AB <sup>1</sup>	70	0.15	—	—	—	Class-A Amp.	110	- 7.5	110	3.0	40	—	5800	80	2500	1.5	70A7GT
70L7GT	Diode-Beam Tetrode	O.	8AA	70	0.15	—	—	—	Class-A <sub>1</sub> Amp.	110	- 7.5	110	3/6	40/43	15000	7500	—	2000	1.8	70L7GT
117L7GT/ 117M7GT	Rectifier-Amplifier	O.	8AO	117	0.09	—	—	—	Class-A Amp.	105	- 5.2	105	4/5.5	43	17000	5300	—	4000	0.85	117L7GT/ 117M7GT
117N7GT	Rectifier-Amplifier	O.	8AV	117	0.09	—	—	—	Class-A Amp.	100	- 6.0	100	5.0	51	16000	7000	—	3000	1.2	117N7GT
117P7GT	Rectifier-Amplifier	O.	8AV	117	0.09	—	—	—	Class-A Amp.	105	- 5.2	105	4/5.5	43	17000	5300	—	4000	0.85	117P7GT
1284	U.h.f. Pentode	O.	Fig. 4	12.6	0.15	—	—	—	Class-A Amp.	250	- 3.0	100	2.5	9.0	80000	2000	—	—	—	1284
1629	Electron-Ray Tube	O.	6RA	12.6	0.15	—	—	—	Indicator Tube	Characteristics same as 6E5—Table IV										1629
1631	Beam Power Amplifier	O.	7AC	12.6	0.45	—	—	—	Class-A Amp.	Characteristics same as 6L6—Table I										1631
1632	Beam Power Amplifier	O.	7AC	12.6	0.6	—	—	—	Class-A Amp.	Characteristics same as 25L6										1632
1633	Twin Triode	O.	8BD	25	0.15	—	—	—	Class-A Amp.	Characteristics same as 6SN7GT—Table II										1633
1634	Twin Triode	O.	8S	12.6	0.15	—	—	—	Class-A Amp.	Characteristics same as 6SC7—Table I										1634
1644	Twin Pentode	O.	Fig. 7	12.6	0.15	—	—	—	Class-A Amp.	180	- 9.0	180	2.8/4.6	13	160000	2150	—	10000	1.0	1644
XXD	Twin Triode	L.	8AC	12.6	0.15	—	—	—	Class-A Amp.	250	-10	—	—	9.0	—	2100	16	—	—	XXD
28D7	Double Beam Power Amplifier	L.	8BS	28.0	0.4	—	—	—	Class-A Amp.	390*	28 <sup>2</sup>	0.7 <sup>2</sup>	9.0 <sup>2</sup>	—	—	—	—	—	—	28D7
										180*	28 <sup>3</sup>	1.2 <sup>3</sup>	18.5 <sup>3</sup>	—	—	—	—	—	6000 <sup>4</sup>	0.175 <sup>3</sup>

\* Cathode resistor—ohms.

<sup>1</sup> 6.3-volt pilot lamp must be connected between Pins 6 and 7.  
<sup>2</sup> Per section—resistance-coupled.

<sup>3</sup> P.p. operation—values for both sections, resistance-coupled.  
<sup>4</sup> Plate to plate.

<sup>5</sup> Values are for each unit.  
<sup>6</sup> Values are for single tube.

TABLE X—SPECIAL RECEIVING TUBES

Type	Name	Base	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
				Volts	Amp.	In	Out	Plate-Grid													
00-A	Triode Detector	M.	4D	5.0	0.25	3.2	2.0	8.50	Grid Leak Det.	45	—	—	—	1.5	30000	666	20	—	—	00-A	
01-A	Triode Detector Amplifier	M.	4D	5.0	0.25	—	—	—	Class-A Amp.	135	- 9.0	—	—	3.0	10000	800	8.0	—	—	01-A	
2E32	Sub miniature Pentode	1	—	1.25	0.05	—	—	—	Class-A Amp.	22.5	0	22.5	0.3	0.4	350000	500	—	—	—	2E32	
										22.5	0	22.5	0.07	0.27	220000	385	—	150000	0.0012	2E32	
2E36	Sub miniature Pentode	1	—	1.25	0.03	—	—	—	Class-A <sub>1</sub> Amp.	45	-1.25	45	0.11	0.45	250000	500	—	100000	0.006	2E36	
2E42	Sub miniature Diode Pent.	1	—	1.25	0.03	—	—	—	Detector Amp.	22.5	0	22.5	0.12	0.35	250000	375	—	1 meg.	—	2E42	
2G22	Sub miniature Converter	1	—	1.25	0.05	—	—	—	Converter	22.5	0	22.5	0.3	0.2	500000	60	—	—	—	2G22	
3A8GT	Diode Triode Pentode	O.	8AS	1.4	0.1	—	—	—	Class-A Triode	90	0	—	—	0.15	240000	275	65	—	—	3A8GT	
										90	0	90	0.3	1.2	600000	750	—	—	—		
3B5GT	Beam Power Amplifier	O.	7AP	1.4	0.1	—	—	—	Class-A Amp.	67.5	- 7.0	67.5	0.6	8.0	100000	1650	—	5000	0.2	3B5GT	
3C5GT	Power Output Pentode	O.	7AQ	1.4	0.1	—	—	—	Class-A Amp.	90	- 9.0	90	1.4	6.0	—	1550	1450	—	8000	0.24	3C5GT
3C6	Twin Triode	L.	7BW	1.4	0.1	—	—	—	Class-A Amp.	90	0	—	—	4.5	11200	1300	14.5	—	—	3C6	

TABLE X—SPECIAL RECEIVING TUBES—Continued

Type	Name	Base	Socket Connections	FH. or Heater		Capacitance $\mu$ fd.			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Trans-conductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
3LE4	Power Amplifier Pentode	L.	6BA	2.8	0.05	—	—	—	Class-A Amp.	90	- 9.0	90	1.8	9.0	110000	1600	—	6000	0.30	3LE4
3LF4	Power Amplifier Tetrode	L.	6BB	1.4 2.8	0.1 0.05	—	—	—	Class-A Amp.	90	- 4.5	90	1.3 1.0	9.5 8.0	75000 80000	2200 2000	—	8000 7000	0.27 0.23	3LF4
3Q5GT	Beam Power Amplifier	O.	7AP	1.4 2.8	0.1 0.05	Parallel Filaments Series Filaments			Class-A Amp.	90	- 4.5	90	1.3 1.0	9.5 7.5	—	2100 1800	—	8000	0.27 0.25	3Q5GT
4A6G	Twin Triode Amplifier	O.	8L	4 2	0.06 0.12	Triodes Parallel Both Sections			Class-A Amp. Class-B Amp.	90 90	- 1.5 0	—	—	2.2 4.6	13300 —	1500	20	—	—	4A6G
6F4	Acorn Triode	A.	7BR	6.3	0.225	2.0	0.6	1.90	Class-A Amp.	80	150*	—	—	4.6	—	—	—	8000	1.0	6F4
10	Triode Power Amplifier	M.	4D	7.5	1.25	4.0	3.0	7.00	Class-A Amp.	425	-39.0	—	—	13.0	2700	5800	17	—	—	10
11/12	Triode Detector Amplifier	M.	4F/4D	1.1	0.25	—	—	—	Class-A Amp.	135	-10.5	—	—	18.0	5000	1600	8.0	10200	1.6	11/12
20	Triode Power Amplifier	S.	4D	3.3	0.132	2.0	2.3	4.10	Class-A Amp.	135	-22.5	—	—	3.0	15000	440	6.6	—	—	20
22	Tetrode R.F. Amplifier	M.	4K	3.3	0.132	3.5	10	0.02	Class-A Amp.	135	-1.5	67.5	1.3	3.7	325000	500	160	—	—	22
26	Triode Amplifier	M.	4D	1.5	1.05	2.8	2.5	8.10	Class-A Amp.	180	-14.5	—	—	6.2	7300	1150	8.3	—	—	26
40	Triode Voltage Amplifier	M.	4D	5.0	0.25	2.8	2.2	2.00	Class-A Amp.	180	- 3.0	—	—	0.2	150000	200	30	—	—	40
50	Triode Power Amplifier	M.	4D	7.5	1.25	4.2	3.4	7.10	Class-A Amp.	450	-84.0	—	—	55.0	1800	2100	3.8	4350	4.6	50
71-A	Triode Power Amplifier	M.	4D	5.0	0.25	3.2	2.9	7.50	Class-A Amp.	180	-43.0	—	—	20.0	1750	1700	3.0	4800	0.79	71-A
99 <sup>10</sup>	Triode Detector Amplifier	S.	4D	3.3	0.063	2.5	2.5	3.30	Class-A Amp.	90	- 4.5	—	—	2.5	15500	425	6.6	—	—	99
112A	Triode Detector Amplifier	M.	4D	5.0	0.25	—	—	—	Class-A Amp.	180	-13.5	—	—	7.7	4700	1800	8.5	—	—	112A
182B/482B	Triode Amplifier	M.	4D	5.0	1.25	—	—	—	Class-A Amp.	250	-35.0	—	—	18.0	—	1500	5.0	—	—	182B/482B
183/483	Power Triode	M.	4D	5.0	1.25	—	—	—	Class-A Amp.	250	-60.0	—	—	25.0	18000	1800	3.2	4500	2.0	183/483
485	Triode	S.	5A	3.0	1.3	—	—	—	Class-A Amp.	180	- 9.0	—	—	6.0	9300	1350	12.5	—	—	485
864	Triode Amplifier	S.	4D	1.1	0.25	—	—	—	Class-A Amp.	90	- 4.5	—	—	2.9	13500	610	8.2	—	—	864
954	Pentode Detector, Amplifier	A.	5BB	6.3	0.15	3.4	3.0	0.007	Class-A Amp. Bias Detector	250 250	- 3.0 - 6.0	100 100	0.7	2.0	1.5 meg.	1400	2000	—	—	954
955	Triode Detector, Amplifier, Oscillator	A.	5BC	6.3	0.15	1.0	0.6	1.40	Class-A Amp.	250	- 7.0	—	—	6.3	11400	2200	25	—	—	955
956	Triple-Grid Variable- $\mu$ R.F. Amplifier	A.	5BB	6.3	0.15	3.4	3.0	0.007	Class-A Amp. Mixer	90 250	- 2.5 -10.0	— 100	—	2.5 6.7	14700 700000	1700	25 1440	—	—	956
957	Triode Detector, Amplifier, Oscillator	A.	5BD	1.25	0.05	0.3	0.7	1.20	Class-A Amp.	135	- 5.0	—	—	2.0	20800	650	13.5	—	—	957
958-958-A	Triode A.F. Amplifier, Oscillator	A.	5BD	1.25	0.1	0.6	0.8	2.60	Class-A Amp.	135	- 7.5	—	—	3.0	10000	1200	12	—	—	958-958-A
959	Pentode Detector, Amplifier	A.	5BE	1.25	0.05	1.8	2.5	0.015	Class-A Amp.	145	- 3.0	67.5	0.4	1.7	800000	600	480	—	—	959
7E5/1201	U.h.f. Triode	L.	8BN	6.3	0.15	3.6	2.8	1.50	Class-A Amp.	180	- 3	—	—	5.5	12000	—	36	—	—	7E5/1201
7C4/1203	U.h.f. Diode	L.	4AH	6.3	0.15	—	—	—	Rectifier	—	—	—	—	—	—	—	—	—	—	7C4/1203
7AB7/1204	U.h.f. Pentode	L.	Fig. 5	6.3	0.15	3.5	4.0	0.06	Class-A Amp.	250	- 2	100	0.6	1.75	800000	1200	—	—	—	7AB7/1204
1276	Triode Power Amplifier	M.	4D	4.5	1.14	—	—	—	Class-A Amp.	—	—	—	—	—	—	—	—	—	—	1276
1609	Pentode Amplifier	S.	5B	1.1	0.25	—	—	—	Class-A Amp.	135	- 1.5	—	—	0.65	2.5	400000	725	300	—	1609
9004	U.h.f. Diode	A.	4BJ	6.3	0.15	—	—	—	Detector	—	—	—	—	—	—	—	—	—	—	9004
9005	U.h.f. Diode	A.	5BG	3.6	0.165	—	—	—	Detector	—	—	—	—	—	—	—	—	—	—	9005
EF-50	High-Frequency Pentode Amplifier	L.	Fig. 14	6.3	0.3	8	5	0.007	I.F.-R.F. Amp.	250	150*	250	3.1	10	600000	6300	—	—	—	EF-50
GL-2C44 GL-464A	U.h.f. Triode	O.	Fig. 17	6.3	0.75	—	—	—	Class-A Amp. and Modulator	250	100*	—	—	25.0	—	7000	—	—	—	GL-2C44 GL-464A
GL-446A GL-446B	U.h.f. Triode	O.	Fig. 19	6.3	0.75	—	—	—	Oscillator, Amp. or Converter	250	200*	—	—	15.0	—	4500	45	—	—	GL-446A GL-446B
559 GL-559	U.h.f. Diode	O.	Fig. 18	6.3	0.75	—	—	—	Detector or trans. line switch	5.0	—	—	—	24.0	—	—	—	—	—	559 GL-559



TABLE X—SPECIAL RECEIVING TUBES—Continued

Type	Name	Base	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
				Volts	Amp.	In	Out	Plate-Grid													
NU-2C35	Special Hi-Mu Triode	O.	Fig. 38	6.3	0.3	5.2	2.3	0.62	Shunt Voltage Regulator	8000	-200	—	—	5.0	525000	950	500	—	—	NU-2C35	
M54	Tetrate Power Amplifier	1	—	0.625	0.04	—	—	—	Class-A Amp.	30	0	30	0.06	0.5	130000	200	26	35000	0.005	M54	
M64	Tetrode Voltage Amplifier	1	—	0.625	0.02	—	—	—	Class-A Amp.	30	0	—	—	0.03	200000	110	25	—	—	M64	
M74	Tetrate Voltage Amplifier	1	—	0.625	0.02	—	—	—	Class-A Amp.	30	0	7.0	0.01	0.02	500000	125	70	—	—	M74	
XXB	Twin-Triode Frequency Converter	L.	Fig. 9	2.8/ 1.4 3.24/ 1.6	0.05/ 0.10	—	—	—	Converter <sup>1</sup>	90 <sup>2</sup>	0	—	—	4.5 <sup>3</sup>	11200 <sup>4</sup>	1300 <sup>5</sup>	1300 <sup>5</sup>	14.5 <sup>6</sup>	—	—	XXB
														4.5 <sup>3</sup>	11200 <sup>4</sup>	1300 <sup>5</sup>	1300 <sup>5</sup>	14.5 <sup>6</sup>			
XXFM	Twin-Diode Triode	L.	Fig. 10	6.3	0.3	—	—	—	Special Detector Amplifier	250 <sup>8</sup>	-1	—	—	1.9	6700	1500	100	—	—	XXFM	
										100 <sup>9</sup>	0	—	—	1.2	85000	1000	85	—	—		
										100 <sup>3</sup>	—	—	—	4 <sup>4</sup>	—	—	—	—	—		

<sup>1</sup> Cathode resistor—ohms. <sup>2</sup> No base; tinned wire leads. <sup>3</sup> Diode plates (a.c. max. volts per plate). <sup>4</sup> Section No. 2 recommended for h.f.o. <sup>5</sup> Amplifier plate. <sup>6</sup> Same as X99. Type V99 is same, but socket connections are 4E.  
<sup>7</sup> Both sections. <sup>8</sup> Max. d.c. output. <sup>9</sup> Dry battery operation. <sup>10</sup> Section No. 1. <sup>11</sup> Section No. 2.

TABLE XI—MINIATURE RECEIVING TUBES

Type	Name	Base	Socket Connections	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amp. Factor <sup>1</sup>	Load Resistance Ohms	Power Output Watts	Type	
				Volts	Amp.	In	Out	Plate-Grid													
1A3	H. F. Diode	B.	5AP	1.4	0.15	—	—	—	Detector F.M. Discrim.	—	—	—	—	—	—	—	—	—	—	1A3	
1L4	R.F. Pentode Amplifier	B.	6AR	1.4	0.05	3.6	7.5	.008	Class-A Amp.	90	0	90	2.0	4.5	350000	1025	—	—	—	1L4	
1R5	Pentagrid Converter	D.	7AT	1.4	0.05	—	—	—	Converter	90	0	67.5	3.0	1.7	500000	300	Grid No. 1	100000 ohms	—	1R5	
1S4	Pentagrid Power Amp.	B.	7AV	1.4	0.1	—	—	—	Class-A Amp.	90	-7.0	57.5	1.4	7.4	100000	1575	—	8000	0.270	1S4	
1S5	Diode Pentode	B.	6AU	1.4	0.05	—	—	—	Class-A Amp.	67.5	0	57.5	0.4	1.6	600000	625	—	—	—	—	1S5
									R-Coupled Amp.	90	0	00	—	—	—	—	—	—	—	—	
1T4	Triple-Grid Variable- $\mu$	B.	6AR	1.4	0.05	3.6	7.5	0.01	Class-A Amp.	90	0	45	0.55	2.0	800000	750	—	—	—	1T4	
1U4	Pentode R.F. Amplifier	D.	6AR	1.4	0.05	3.6	7.5	.008	Class-A Amp.	90	0	90	0.45	1.6	1500000	900	—	—	—	1U4	
1U5	Diode Pentode	B.	6EW	1.4	0.05	—	—	—	Class-A Amp.	67.5	0	67.5	0.4	1.6	600000	625	—	—	—	1U5	
2E30	Beam Power Tetrode	B.	7CQ	6.0	0.7	10	4.5	0.5	Class-A <sub>1</sub> Single	250	450 <sup>2</sup>	250	7.4 <sup>3</sup>	44 <sup>4</sup>	—	63000	3700	40 <sup>5</sup>	4500	4.5	2E30
									Class-A <sub>1</sub> Amp. <sup>2</sup>	250	225 <sup>2</sup>	250	14.3 <sup>3</sup>	88 <sup>4</sup>	—	—	—	80 <sup>5</sup>	9000 <sup>6</sup>	9	
									Class-AB <sub>1</sub> Amp. <sup>3</sup>	250	-2.5	250	13.5 <sup>3</sup>	80 <sup>4</sup>	—	—	—	48 <sup>5</sup>	8000 <sup>6</sup>	12.5	
									Class-AB <sub>2</sub> Amp. <sup>3</sup>	250	-30	250	20 <sup>3</sup>	120 <sup>4</sup>	—	—	—	40 <sup>5</sup>	3800 <sup>6</sup>	17	
									Class-A <sub>1</sub> Amp.	135	-7.5	90	2.6	14.9 <sup>2</sup>	—	—	—	—	—	—	
3A4	Power Amplifier Pentode	B.	7BB	1.4 2.8	0.2 0.1	4.8	4.2	0.34	Class-A <sub>1</sub> Amp.	150	-8.4	90	2.2	14.1 <sup>2</sup>	90000	1900	—	8000	0.6 0.7	3A4	
3A5	H.F. Twin Triode	B.	7BC	1.4 2.8	0.22 0.11	0.9	1.0	3.20	Class-A Amp.	90	-2.5	—	—	3.7	8300	1800	15	—	—	3A5	
3Q4	Power Amplifier Pentode	B.	7BA	1.4	0.1	Parallel Filaments			Class-A Amp.	90	-4.5	90	2.1	9.5	100000	2150	—	10000	0.27	3Q4	
				2.8	0.05	Series Filaments							1.7	7.7	120000	2000	—	—	—		—
3S4	Power Amplifier Pentode	B.	7BA	1.4	0.1	Parallel Filaments			Class-A Amp.	90	-7.0	67.5	1.4	7.4	100000	1575	—	8000	0.27	3S4	
				2.8	0.05	Series Filaments							1.1	6.1	—	1425	—	—	—		—
3V4	Power Amplifier Pentode	B.	6BX	1.4	0.1	Parallel Filaments			Class-A Amp.	90	-4.5	90	2.1	9.5	100000	2150	—	10000	0.27	3V4	
				2.8	0.05	Series Filaments							1.7	7.7	120000	2300	—	10000	0.24		
6AG5	Pentode R.F. Amplifier	B.	7BD	6.3	0.3	—	—	—	Class-A Amp.	250	200*	150	2.0	7.0	800000	5000	—	—	—	6AG5	
6AJ5	U.h.f. Pentode	B.	7PM	6.3	0.175	—	—	—	R.F. Amplifier	28	200*	28	1.2	3.0	90000	2750	250	—	—	6AJ5	
									Class-AB Amp.	180	-7.5	75	—	—	—	—	—	—	—		—
6AK5	H.F. Pentode	B.	7BD	6.3	0.175	—	—	—	R.F. Amplifier	180	200*	120	2.4	7.7	690000	5100	3500	—	—	6AK5	
									150	330*	140	2.2	7.0	420000	4300	1800	—	—			
									120	200*	120	2.5	7.5	340000	5000	1700	—	—			

TABLE XI—MINIATURE RECEIVING TUBES—Continued

Type	Name	Base	Socket Connections <sup>1</sup>	Fil. or Heater		Capacitance $\mu\text{fd.}$			Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance Ohms	Transconductance Micramhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amp.	In	Out	Plate-Grid												
6AK6	Power Amplifier Pentode	B.	7BK	6.3	0.15	3.6	4.2	0.12	Class-A Amp.	180	-9.0	180	2.5	15.0	200000	2300	—	10000	1.1	6AK6
6AL5	U.h.f. Twin Diode	B.	6BT	6.3	0.3	—	—	—	Detector	—	—	—	—	—	—	—	—	—	6AL5	
6AN6	Twin Diode	B.	7BJ	6.3	0.2	—	—	—	Detector	R.m.s. voltage per plate = 7.5 volts; d.c. output = 3.5 ma. with 25000 ohms and 8 $\mu\text{fd}$ load; peak current per plate = 10 ma.; peak inverse voltage = 210.										6AN6
6AQ5	Beam Power Tetrode	B.	7BZ	6.3	0.45	7.6	6.0	0.35	Class-A <sub>1</sub> Amp.	190 250	-8.5 -12.5	180 250	4.0 <sup>2</sup> 7.0 <sup>2</sup>	3.0 <sup>2</sup> 4.7 <sup>2</sup>	58000 52000	3700 4100	29 45	5500 3000	2.0 4.5	6AQ5
6AQ6	Duodiode Hi-mu Triode	B.	7BT	6.3	0.15	1.7	1.5	1.80	Class-A Triode	250 100	-3.0 -1.0	—	—	1.0 0.8	58000 61000	1200 1150	70 70	—	—	6AQ6
6AR5	Pentode Power Amp.	B.	6CC	6.3	0.4	—	—	—	Class-A <sub>1</sub> Amp.	250 250	-18 -16.5	250 250	5.5 5.5	33 35	68000 65000	2300 2400	—	7600 7000	3.4 3.2	6AR5
6AS6	Sharp Cut-off Pentode	B.	7CN	6.3	0.175	4.0	3.0	0.02	Class-A Amp.	120	-2	120	3.5	5.5	—	3500	—	—	—	6AS6
6AT6	Duplex Diode Triode	B.	7BT	6.3	0.3	2.3	1.1	2.10	Class-A Amp.	250	-3	—	—	1.0	58000	1200	70	—	—	6AT6
6AU6	Pentode R.F. Amp.	B.	7BK	6.3	0.3	5.5	5.0	.0035	Class-A Amp.	250	-1	150	4.3	10.8	2000000	5200	—	—	—	6AU6
6BA6	Remate Cut-off Pentode	B.	7CC	6.3	0.3	5.5	5.0	.0035	Class-A Amp.	250	68*	100	4.2	11	1500000	4400	—	—	—	6BA6
6BD6	Pentode R.F. Amplifier	B.	7CC	6.3	0.3	—	—	—	Class-A Amp.	100 250	-1 -3	100 100	5 3.5	13 9	120000 700000	2350 2000	—	—	—	6BD6
6BE6	Pentagrid Converter	B.	7CH	6.3	0.3	Osc. Grid 20000 $\Omega$			Converter	250	-1.5	100	7.1	3.0	1000000	475	—	—	—	6BE6
6BF6	Duplex-Diode Triode	B.	7BT	6.3	0.3	1.8	1.1	2.0	Class-A <sub>1</sub> Amp.	250	-9	—	—	9.5	8500	1900	16	10000	—	6BF6
6BJ6	Pentode Remate-Cutoff	B.	7CM	6.3	0.15	4.5	5.0	.0035	Class A <sub>1</sub> Amp.	250	-1	100	3.3	9.2	1300000	3800	—	—	—	6BJ6
6C4	Triode Amplifier	B.	6BG	6.3	0.15	1.8	1.3	1.60	Class-A Amp.	250	-8.5	—	—	10.5	7700	2200	17	—	—	6C4
6J4	U.h.f. Grounded-Grid R.F. Amplifier	B.	7BQ	6.3	0.4	5.5	0.24	4.0	Grounded-Grid Class-A <sub>1</sub> Amp.	150 100	200* 100*	—	—	15.0 10.0	4500 5000	12000 11000	55 55	—	—	6J4
6J6	Twin Triode	B.	7BF	6.3	0.45	2.2	0.4	1.6	Class-A <sub>1</sub> Amp. Mixer, Oscillator	100	50*	—	—	8.5	7100	5300	38	—	—	6J6
6N4	U.h.f. Triode Amplifier	B.	7CA	6.3	0.2	3.0	1.6	1.10	Class-A Amp.	180	-3.5	—	—	12.0	—	6000	32	—	—	6N4
12AL5	Twin Diode	B.	6BT	12.6	0.15	2.5	—	—	Detector	R.m.s. voltage per plate = 117; d.c. output = 9 ma. per plate; peak ma. per plate = 54; peak inverse voltage = 330.										12AL5
12AT6	Duplex Diode Triode	B.	7BT	12.6	0.15	2.3	1.1	2.10	Class-A Amp.	250	-3.0	—	—	1.0	58000	1200	70	—	—	12AT6
12AU6	Sharp Cut-off Pentode	B.	7CC	12.6	0.15	5.5	5.0	.0035	Class-A <sub>1</sub> Amp.	250	-1.0	150	4.3	10.8	1 meg.	5200	—	—	—	12AU6
12AU7	Twin-Triode Amplifier	B.	9A	6.3 12.6	0.3 0.15	1.6 <sup>1</sup> 1.6 <sup>1</sup>	0.5 <sup>1</sup> 0.35 <sup>1</sup>	1.5 <sup>1</sup> 1.5 <sup>1</sup>	Class-A <sub>1</sub> Amp.	250	-8.5	—	—	10.5	7700	2200	17	—	—	12AU7
12AW7	Sharp Cut-off Pentode	B.	7CM	12.6	0.15	6.5	1.5	0.025	Class A <sub>1</sub> Amp.	250	200*	150	2.0	7.0	0.8 meg.	5000	—	—	—	12AW7
12BA6	Remate Cut-off Pentode	B.	7CC	12.6	0.15	5.5	5.0	.0035	Class-A Amp.	250	68*	100	4.2	11.0	1500000	4400	—	—	—	12BA6
12BD6	Pentode Amplifier	B.	7CC	12.6	0.15	4.3	5.0	.004	Class-A Amp.	250	-3	100	3.5	9.0	700000	2000	—	—	—	12BD6
12BE6	Pentagrid Converter	B.	7CH	12.6	0.15	Osc. Grid 20000 $\Omega$			Converter	250	-1.5	100	7.1	3.0	1000000	475	—	—	—	12BE6
12BF6	Duodiode Triode	B.	Fig. 37	12.6	0.15	1.8	1.1	2.00	Class-A Amp.	250	-9	—	—	9.5	8500	1900	16	—	—	12BF6
26A6	Remate cut-off Pentode	B.	7BK	26.5	0.07	6.0	5.0	.0035	Class-A <sub>1</sub> Amp.	250	125*	100	4	10.5	1000000	4000	—	—	—	26A6
26C6	Duplex-Diode Triode	B.	7BT	26.5	0.07	1.8	1.4	2	Class-A <sub>1</sub> Amp.	250	-9	—	—	9.5	8500	1900	16	—	—	26C6
26D6	Pentagrid Converter	B.	7CH	26.5	0.07	Osc. Grid 20000 $\Omega$			Converter	250	-1.5	100	7.8	3.0	1000000	475	—	—	—	26D6
35B5	Beam Power Amplifier	B.	7BZ	35	0.15	11	6.5	0.4	Class-A <sub>1</sub> Amp.	110	-7.5	110	7 <sup>1</sup>	41 <sup>1</sup>	—	5800	40 <sup>1</sup>	2500	1.5	35B5
50B5	Beam Power Amplifier	B.	7BZ	50.0	0.15	13	6.5	0.50	Class-A Amp.	110	-7.5	110	4.0	49.0	14000	7500	—	3000	1.9	50B5
9001	Triple-Grid Detector, Amplifier	B.	7PM	6.3	0.15	3.6	3.0	0.01	Class-A Amp. Mixer	250	-3.0	100	0.7	2.0	1 meg. +	1400	—	—	—	9001
9002	Triode Detector, Amplifier, Oscillator	B.	7TM	6.3	0.15	1.2	1.1	1.40	Class-A Amp.	250 90	-7.0 -2.5	—	—	6.3 2.5	11400 14700	2200 1700	25 25	—	—	9002
9003	Triple-Grid Variable- $\mu$ R.F. Amplifier	B.	7PM	6.3	0.15	3.6	3.0	0.01	Class-A Amp. Mixer	250	-3.0	100	2.7	6.7	700000	1800	—	—	—	9003
9006	U.h.f. Diode	D.	6DH	6.3	0.15	—	—	—	Detector	Max. a.c. voltage—270. Max. d.c. output current—5 ma.										9006

\* Cathode resistor—ohms.

<sup>1</sup> Per Plate.

<sup>2</sup> Maximum-signal current for full-power output.

<sup>3</sup> Values are for two tubes in push-pull.

<sup>4</sup> Also no-signal plate ma. when so indicated.

<sup>5</sup> No-signal plate ma.

<sup>6</sup> Effective plate-to-plate.

<sup>7</sup> Triode No. 1.

<sup>8</sup> Triode No. 2.

TABLE XII—CONTROL AND REGULATOR TUBES

Type	Name	Base	Socket Connections	Cathode	Fil. or Heater		Use	Peak Anode Voltage	Max. Anode Ma.	Minimum Supply Voltage	Operating Voltage	Operating Ma.	Grid Resistor	Tube Voltage Drop	Type
					Volts	Amp.									
0A2	Voltage Regulator	7-pin B.	5B0	Cold	—	—	Voltage Regulator	—	—	185	150	5-30	—	—	0A2
0B2	Voltage Regulator	7-pin B.	5B0	Cold	—	—	Voltage Regulator	—	—	133	108	5-30	—	—	0B2
0A4G	Gas Triode Starter-Anode Type	6-pin O.	4V	Cold	—	—	Cold-Cathode Starter-Anode Relay Tube	With 105-120-volt a.c. anode supply, peak starter-anode a.c. voltage is 70, peak r.f. voltage 55. Peak d.c. ma = 100. Average d.c. ma = 25.						0A4G	
1B47	Voltage Regulator	7-pin B.	—	—	—	—	Voltage Regulator	—	—	225	82	1-2	—	—	1B47
1C21	Gas Triode Glow-Discharge Type	6-pin O.	4V	Cold	—	—	Relay Tube	125-145	—	25	66 <sup>6</sup>	—	—	73	1C21
2A4G	Gas Triode Grid Type	7-pin O.	5S	Fil.	2.5	2.5	Voltage Regulator	—	—	0.1 <sup>6</sup>	180 <sup>1</sup>	—	—	55	2A4G
2E4	Gas Triode Grid Type	8-pin O.	6Q	Htr.	6.3	0.6	Control Tube	200	100	—	—	—	—	15	2E4
6Q5G		5-pin M.	5A	Htr.	2.5	1.4	Sweep Circuit Oscillator	300	300	—	—	1.0	0.1-10 <sup>7</sup>	19	6Q5G
2C4	Gas Triode	7-pin B.	5AS	Fil.	2.5	0.65	Control Tube	Plate volts = 350; Grid volts = -50; Avg. Ma. = 5; Peak Ma. = 20; Voltage drop = 16.						2C4	
2D21	Gas Tetrode	7-pin B.	7BN	Htr.	6.3	0.6	Grid-Controlled Rectifier	650	500	—	650	100	0.1-10 <sup>7</sup>	8	2D21
							Relay Tube	400	—	—	—	1.0 <sup>7</sup>	—		
3C23	Gas and Mercury Vapor Grid Type	4-pin M.	3G	Fil.	2.5	7.0	Grid-Controlled Rectifier	1000	6000	—	500	1500	-4.5 <sup>8</sup>	15	3C23
							Control Tube	—	—	—	100	1500	-2.5 <sup>8</sup>	15	
6D4	Gas Triode	7-pin B.	5AY	Htr.	6.3	0.25	Control Tube	Plate volts = 350; Grid volts = -50; Avg. Ma. = 25; Peak Ma. = 100; Voltage drop = 16.						6D4	
17	Mercury Vapor Triode	4-pin M.	3G	Fil.	2.5	5.0	Grid-Controlled Rectifier	7500 <sup>1</sup>	2000	—	500	200-3000	—	—	17
							Control Tube	2500	—	-5 <sup>3</sup>	1000	250	—	10-24	
874	Voltage Regulator	4-pin M.	4S	—	—	—	Voltage Regulator	—	—	125	90	10-50	—	—	874
876	Current Regulator	Mogul	—	—	—	—	Current Regulator	—	—	—	40-60	1.7	—	—	876
884	Gas Triode Grid Type	6-pin O.	6Q	Htr.	6.3	0.6	Sweep Circuit Oscillator	300	300	—	—	2	25000	—	884
							Grid-Controlled Rectifier	350	300	—	—	75	25000	—	
885	Gas Triode Grid Type	5-pin S.	5A	Htr.	2.5	1.4	Same as Type 884	Characteristics same as Type 884						885	
886	Current Regulator	Mogul	—	—	—	—	Current Regulator	—	—	—	40-60	2.05	—	—	886
967	Mercury Vapor Triode	4-pin M.	3G	Fil.	2.5	5.0	Grid-Controlled Rectifier	2500	500	-5 <sup>3</sup>	—	—	—	10-24	967
991	Voltage Regulator	Bayonet	—	—	—	—	Voltage Regulator	—	—	87	55-60	2.0	—	—	991
1265	Voltage Regulator	6-pin O.	—	—	—	—	Voltage Regulator	—	—	130	90	5-30	—	—	1265
1266	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	—	70	5-40	—	—	1266
1267	Gas Triode	6-pin O.	4V	Cold	—	—	Relay Tube	Characteristics same as 0A4G						1267	
2050	Gas Tetrode	8-pin O.	8BA	Htr.	6.3	0.6	Grid-Controlled Rectifier	650	500	—	—	100	0.1-10 <sup>7</sup>	8	2050
2051	Gas Tetrode	8-pin O.	8BA	Htr.	6.3	0.6	Grid-Controlled Rectifier	350	375	—	—	75	0.1-10 <sup>7</sup>	14	2051
2523N1/ 128AS	Gas Triode Grid Type	5-pin M.	5A	Htr.	2.5	1.75	Relay Tube	400	300	—	—	1.0	300 <sup>7</sup>	13	2523N1/ 128AS
KY21	Gas Triode Grid Type	4-pin M.	—	Fil.	2.5	10.0	Grid-Controlled Rectifier	—	—	—	3000	500	—	—	KY21
RK61	Thyratron	— <sup>9</sup>	—	Fil.	1.4	0.05	Radio-Controlled Relay	45	1.5	30	—	0.5-1.5	3 <sup>7</sup>	30	RK61
RK62	Gas Triode Grid Type	4-pin S.	4D	Fil.	1.4	0.05	Relay Tube	45	1.5	—	30-45	0.1-1.5	—	15	RK62
RM208	Permotron	4-pin M.	—	Fil.	2.5	5.0	Controlled Rectifier <sup>1</sup>	7500 <sup>2</sup>	1000	—	—	—	—	15	RM208
RM209	Permotron	4-pin M.	—	Fil.	5.0	10.0	Controlled Rectifier <sup>1</sup>	7500 <sup>2</sup>	5000	—	—	—	—	15	RM209
0A3/VR75	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	105	75	5-40	—	—	0A3/VR75
0B3/VR90	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	125	90	5-40	—	—	0B3/VR90
0C3/VR105	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	135	105	5-40	—	—	0C3/VR105
0D3/VR150	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	185	150	5-40	—	—	0D3/VR150
KY866	Mercury Vapor Triode	4-pin M.	Fig. 8	Fil.	2.5	5.0	Grid-Controlled Rectifier	10000	1000	0-150	—	—	—	—	KY866

<sup>1</sup> For use as grid-controlled rectifier or with external magnetic control. RM-208 has characteristics of 856, RM-209 of 872.

<sup>2</sup> When under control peak inverse rating is reduced to 2500.  
<sup>3</sup> At 1000 anode volts.

<sup>4</sup> Grid tied to plate.  
<sup>5</sup> Peak inverse voltage.

<sup>6</sup> Grid.  
<sup>7</sup> Megohms.

<sup>8</sup> Grid voltage.  
<sup>9</sup> No base. Tinned wire leads.

TABLE XIII—CATHODE-RAY TUBES AND KINESCOPIES

Type	Name	Socket Connections	Heater		Use	Size	Anode No. 2 Voltage	Anode No. 1 Voltage	Cut-Off Grid Voltage	Grid No. 2 Voltage	Signal-Swing Voltage	Max. Input Voltage <sup>1</sup>	Screen Input Power <sup>2</sup>	Deflection Sensitivity <sup>3</sup>		Anode No. 3 Voltage	Pattern Color	Type
			Volts	Amp.										D <sub>1</sub> D <sub>2</sub>	D <sub>1</sub> D <sub>4</sub>			
2AF1 <sup>7</sup>	Electrostatic Cathode-Ray	11B	6.3	0.6	Oscillograph Television	2"	1000 500	250 125	- 60 - 30	—	—	660	—	0.11 0.22	0.13 0.26	—	Green	2AP1
2BP1-11	Electrostatic Cathode-Ray	12E	6.3	0.6	Oscillograph	2"	2000 1000	300/560 150/280	-135 -67.5	—	—	500 500	—	270 <sup>3</sup> 135 <sup>3</sup>	174 <sup>3</sup> 87 <sup>3</sup>	—	Green	2BP1-11
3AF1/ 906-P1- 4-5-11 <sup>7</sup>	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	1500 1000 600	430 285 170	- 50 - 33 - 20	—	—	550	10	0.22 0.33 0.55	0.23 0.35 0.58	—	Green Blue White	3AP1/ 906-P1- 4-5-11
3BP1-4-11	Electrostatic Cathode-Ray	14A	6.3	0.6	Oscillograph	3"	2000 1500	575 430	- 60 - 45	—	—	550	—	0.13 0.17	0.17 0.23	—	Green	3BP1-4-11
3DF1	Electrostatic Cathode-Ray	Fig. 49	6.3	0.6	Oscillograph	3"	2000 1500	575 430	- 60 - 40	—	—	550	—	200 <sup>3</sup> 150 <sup>3</sup>	148 <sup>3</sup> 111 <sup>3</sup>	—	Green	3DP1
3EP1/ 1806-P1	Electrostatic Cathode-Ray	11A	6.3	0.6	Oscillograph Television	3"	2000 1500	575 430	- 60 - 45	—	—	550	—	0.115 0.153	0.154 0.205	—	Green	3EP1/ 1806-P1
3GP1-4-5-11	Electrostatic Cathode-Ray	11A	6.3	0.6	Oscillograph	3"	1500 1000	350 234	- 50 - 33	—	—	550	—	0.21 0.32	0.24 0.36	—	White Green Blue	3GP1-4-5-11
3JP1-2-4-7-11	Electrostatic Cathode-Ray	14B	6.3	0.6	Oscillograph	3"	2000 1500	575 430	- 60 - 45	—	—	550	—	0.13 0.17	0.17 0.23	4000 3000	Green Blue White	3JP1-2-4-7-11
3KP1	Electrostatic Cathode-Ray	11A	6.3	0.6	Oscillograph	3"	1000 2000	300 600	- 45 - 90	1000 2000	—	500	—	68 <sup>3</sup> 52 <sup>3</sup>	136 <sup>3</sup> 104 <sup>3</sup>	—	Green	3KP1
5AF1/ 1805-P1 5AF4/ 1805-P4 <sup>7</sup>	Electrostatic Picture Tube	11A	6.3	0.6	Oscillograph Television	5"	2000 1500	575 430	- 35 - 27	—	—	500	10	0.17 0.23	0.21 0.28	—	Green White	5AP1/ 1805-P1 5AP4/ 1805-P4
5BP1/ 1802-P1- 2-4-5-11	Electrostatic Picture Tube	11A	6.3	0.6	Oscillograph	5"	2000 1500	450 337	- 40 - 30	—	—	500	10	0.3 0.4	0.33 0.45	—	Green White Blue	5BP1/ 1802-P1- 2-4-5-11
5CP1-2-4-5-11	Electrostatic Cathode-Ray	14B	6.3	0.6	Oscillograph Television	5"	2000 1500 2000	575 430 575	- 60 - 45 - 60	—	—	550	—	0.28 0.37 0.36	0.32 0.43 0.41	4000 3000 2000	White Green Blue	5CP1-2-4-5-11
5FP1-2-4-11 <sup>7</sup>	Electromagnetic Cathode-Ray	5AN	6.3	0.6	Oscillograph Television	5"	7000 4000	250 250	- 45 - 45	—	—	—	—	—	—	—	Green White Blue	5FP1-2-4-11
5HP1 5HP4 <sup>7</sup>	Electrostatic Cathode-Ray	11A	6.3	0.6	Oscillograph	5"	2000 1500	425 310	- 40 - 30	—	—	500	—	0.3 0.4	0.33 0.44	—	Green White	5HP1 5HP4
5JP1-2-4-5-11	Electrostatic Cathode-Ray	11E	6.3	0.6	Oscillograph	5"	2000 1500	520 390	- 75 - 56	—	—	500	—	0.25 0.33	0.28 0.37	4000 3000	White Green Blue	5JP1-2-4-5-11
5LP1-2-4-5-11	Electrostatic Cathode-Ray	11F	6.3	0.6	Oscillograph Television	5"	2000 1500 1000	500 375 250	- 60 - 45 - 30	—	—	500	—	0.25 0.33 0.49	0.28 0.37 0.56	4000 3000 2000	White Green Blue	5LP1-2-4-5-11
5MP1-4-5-11	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	5"	1500 1000	375 250	- 50 - 33	—	—	660	—	0.39 0.58	0.42 0.64	—	White Green Blue	5MP1-4-5-11
5RP1-2-4-11	Electrostatic Cathode-Ray	14F	6.3	0.6	Oscillograph	5"	3000 2000	— 575	- 90 - 60	—	—	1200	—	0.12 0.18	0.12 0.18	15000 10000	Green White Blue	5RP1-2-4-11
5TP4	Projection Kinescope	Fig. 46	6.3	0.6	Television	5"	27000	4900	- 70	200	—	—	—	—	—	—	White	5TP4

88

TABLE XIII—CATHODE-RAY TUBES AND KINESCOPIES—Continued

Type	Name	Socket Connections	Heater		Use	Size	Anode No. 2 Voltage	Anode No. 1 Voltage	Cut-Off Grid Voltage	Grid No. 2 Voltage	Signal-Swing Voltage	Max. Input Voltage <sup>1</sup>	Screen Input Power <sup>2</sup>	Deflection Sensitivity <sup>6</sup>		Anode No. 3 Voltage	Pattern Color	Type			
			Volts	Amp.										D <sub>1</sub> D <sub>2</sub>	D <sub>2</sub> D <sub>4</sub>						
5UP1-7-11	Electrostatic Cathode-Ray	12E	6.3	0.6	Oscillograph	5"	2500	640	- 90	---	---	500	---	38.5 <sup>3</sup>	77 <sup>3</sup>	---	Green Yellow Blue	5UP1-7-11			
							2500	340	- 90	---	---	500	---	20 <sup>3</sup>	56 <sup>3</sup>	---					
							1000	320	- 45	---	---	500	---	31 <sup>3</sup>	62 <sup>3</sup>	---					
							1000	170	- 45	---	---	500	---	23 <sup>3</sup>	46 <sup>3</sup>	---					
7AP	Electromagnetic Picture Tube	5AJ	2.5	2.1	Television	7"	3500	1000	-67.5	---	---	2.5	---	---	White	7AP4					
7BP1-2-4-11	Electromagnetic Cathode-Ray	5AN	6.3	0.6	Oscillograph Television	7"	7000	250	- 45	---	---	---	---	---	---	White Green Blue	7BP1-2-4-11				
							4000	250	- 45	---	---	---	---	---	---						
7CP1/1811-P1	Electromagnetic Cathode-Ray	6AZ	6.3	0.6	Oscillograph	7"	7000	1470	- 45	250	---	---	---	---	---	Green	7CP1/1811-P1				
							4000	840	- 45	250	---	---	---	---	---						
7DP4	Kinescope	Fig. 46	6.3	0.6	Television	7"	6000	1430	- 45	250	---	---	---	---	---	White	7DP4				
7GP4	Electrostatic Kinescope	Fig. 47	6.3	0.6	Television	7"	3000	1200	- 84	3000	---	---	---	123 <sup>3</sup>	102 <sup>3</sup>	---	White	7GP4			
							7000	1425	- 40	---	250	25	---	---	---	---			---		
9AP4/1804-P4	Electromagnetic Picture Tube	6AL	2.5	2.1	Television	9"	6000	1225	- 38	---	---	---	---	---	---	White	9AP4/1804-P4				
9CP4	Electromagnetic Picture Tube	4AF	2.5	2.1	Television	9"	7000	---	-110	---	25	---	10	---	---	White	9CP4				
							5000	1570	- 90	---	---	---	---	0.136	---			---			
9JP1/1809-P1	Electrostatic-Magnetic Cathode-Ray	8BR	2.5	2.1	Oscillograph	9"	2500	785	- 45	---	---	3000	---	---	---	Green	9JP1/1809-P1				
							---	9000	- 45	250	---	---	---	---	---			---			
10BP4	Magnetic Kinescope	Fig. 48	6.3	0.6	Television	10"	---	1460	- 75	250	---	---	---	---	---	---	10BP4				
12AP4/1803-P4	Electromagnetic Picture Tube	6AL	2.5	2.1	Television	12"	7000	1450	- 75	250	25	---	10	---	---	White	12AP4/1803-P4				
							6000	1240	- 75	---	---	---	---	---	---			---			
12CP4	Electromagnetic Picture Tube	4AF	2.5	2.1	Television	12"	7000	---	-110	---	25	---	10	---	---	White	12CP4				
							7000	250	- 45	---	---	---	---	---	---			---			
12DP4	Electromagnetic Cathode-Ray	5AN	6.3	0.6	Television	12"	4000	250	- 45	---	---	---	---	---	---	White	12DP4				
							---	---	---	---	---	---	---	---	---			---			
902 <sup>7</sup>	Electrostatic Cathode-Ray	Fig. 1	6.3	0.6	Oscillograph	2"	600	151	- 60	---	---	300	5	0.19	0.22	---	Green	902			
903 <sup>8</sup>	Electromagnetic Cathode-Ray	6AL	2.5	2.1	Oscillograph	9"	7000	1350	-120	250	---	10	---	---	---	---	Green	903			
904	Electrostatic-Magnetic Cathode-Ray	Fig. 3	2.5	2.1	Oscillograph	5"	4500	970	- 75	200	---	4000	10	0.09	---	---	Green	904			
905 <sup>7</sup>	Electrostatic Cathode-Ray	Fig. 6	2.5	2.1	Oscillograph	5"	2000	450	- 35	---	---	1000	10	0.19	0.23	---	Green	905			
907	Electrostatic Cathode-Ray	Fig. 6	2.5	2.1	Oscillograph	5"	Characteristics same as Type 905										---	---	---	Blue	907
908 <sup>7</sup>	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	Characteristics same as Type 3AP1/906P1										---	---	---	Blue	908
908-A	Electrostatic Cathode-Ray	7CE	2.5	2.1	Oscillograph	3"	1500	430	- 50	---	---	500	---	0.223	0.233	---	Blue	908-A			
							1000	287	- 33	---	---	500	---	0.334	0.348	---					
909 <sup>8</sup>	Electrostatic Cathode-Ray	Fig. 6	2.5	2.1	Oscillograph	5"	Characteristics same as Type 905										---	---	---	Blue	909
910 <sup>8</sup>	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	Characteristics same as Type 3AP1/906P1										---	---	---	Blue	910
911 <sup>8</sup>	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	Characteristics same as Type 3AP1/906P1										---	---	---	Green	911
912	Electrostatic Cathode-Ray	Fig. 8	2.5	2.1	Oscillograph	5"	10000	2000	- 66	250	---	7000	10	0.041	0.051	---	Green	912			
913	Electrostatic Cathode-Ray	Fig. 1	6.3	0.6	Oscillograph	1"	500	100	- 65	---	---	250	5	0.07	0.10	---	Green	913			
914 <sup>7</sup>	Electrostatic Cathode-Ray	Fig. 12	2.5	2.1	Oscillograph	9"	7000	1450	- 50	250	---	3000	10	0.073	0.073	---	Green	914			
1800 <sup>8</sup>	Electromagnetic Kinescope	6AL	2.5	2.1	Television	9"	6000	1250	- 75	250	25	---	10	---	---	---	Yellow	1800			
1801 <sup>8</sup>	Electromagnetic Kinescope	Fig. 13	2.5	2.1	Television	5"	3000	450	- 35	---	20	---	10	---	---	---	Yellow	1801			
2001	Electrostatic Cathode-Ray	Fig. 2	6.3	0.6	Oscillograph	1"	Characteristics essentially same as 913										---	---	---	---	2001
2002	Electrostatic Cathode-Ray	Fig. 1	6.3	0.6	Oscillograph	2"	600	120	---	---	---	---	---	0.16	0.17	---	Green	2002			
2005	Electrostatic Cathode-Ray	Fig. 1	6.3	0.6	Oscillograph	2"	600	120	---	---	---	---	---	0.5	0.56	---	---	2005			
2005	Electrostatic Cathode-Ray	Fig. 1 <sup>1</sup>	2.5	2.1	Television	5"	2000	1000	- 35	200	---	---	---	10	0.5	0.56	---	---			
24-XH	Electrostatic Cathode-Ray	Fig. 1	6.3	0.6	Oscilloscope	2"	600	120	- 60	---	---	---	---	10	0.14	0.16	---	Blue	24-XH		

<sup>1</sup> Between Anode No. 2 and any deflecting plate.  
<sup>2</sup> In mw./sq. cm., max.

<sup>3</sup> 0.c. Volts/in.  
<sup>4</sup> Cathode connected to Pin 7.

<sup>5</sup> Discontinued.  
<sup>6</sup> In mm./volt d.c.

<sup>7</sup> Superseded by same type with letter "A."

TABLE XIV—RECTIFIERS—RECEIVING AND TRANSMITTING

See also Table XII—Control and Regulator Tubes

Type No.	Name	Base	Socket Connections	Cathode	Fil. or Heater		Max. A.C. Voltage Per Plate	D.C. Output Current Ma.	Max. Inverse Peak Voltage	Peak Plate Current Ma.	Type
					Volts	Amp.					
BA	Full-Wave Rectifier	4-pin M.	4J	Cold	—	—	350	350	Tube drop	80 v.	G
BH	Full-Wave Rectifier	4-pin M.	4J	Cold	—	—	350	125	Tube drop	90 v.	G
BR	Half-Wave Rectifier	4-pin M.	4H	Cold	—	—	300	50	Tube drop	60 v.	G
CE-220	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	3.0	—	20	2000	100	HV
OY4	Half-Wave Rectifier	5-pin O.	4BU	Cold	Connect Pins 7 and 8		95	75	300	500	G
OZ4	Full-Wave Rectifier	5-pin O.	4R	Cold	—	—	350	30-75	1250	200	G
1	Half-Wave Rectifier	4-pin S.	4G	Htr.	6.3	0.3	350	50	1000	400	MV
1-V	Half-Wave Rectifier	4-pin S.	4G	Htr.	6.3	0.3	350	50	—	—	HV
1B3GT/801G	Half-Wave Rectifier	6-pin O.	3C	Fil.	1.25	0.2	—	2.0	4000	17	HV
1B48	Half-Wave Rectifier	7-pin B.	—	Cold	—	—	800	6	2700	50	G
1Z2	Half-Wave Rectifier	7-pin B.	7CB	Fil.	1.5	0.3	7800	2	20000	10	HV
2B25	Half-Wave Rectifier	7-pin B.	3T	Fil.	1.4	0.11	1000	1.5	—	9	HV
2V3G	Half-Wave Rectifier	6-pin O.	4AC	Fil.	2.5	5.0	—	2.0	16500	12	HV
2W3	Half-Wave Rectifier	5-pin O.	4X	Fil.	2.5	1.5	350	55	—	—	HV
2X2/879	Half-Wave Rectifier	4-pin S.	4AB	Htr.	2.5	1.75	4500	7.5	—	—	HV
2X2-A	Half-Wave Rectifier	4-pin S.	4AB	Same as 2X2/879 but will withstand severe shock & vibration							
2Y2	Half-Wave Rectifier	4-pin M.	4AB	Fil.	2.5	1.75	4400	5.0	—	—	HV
2Z2/G84	Half-Wave Rectifier	4-pin M.	4B	Fil.	2.5	1.5	350	50	—	—	HV
3B24	Half-Wave Rectifier	4-pin M.	T-4A	Fil.	5.0	3.0	—	60	20000	300	HV
					2.5	3.0	—	30	20000	150	
3B25	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	500	4500	2000	G
3B26	Half-Wave Rectifier	8-pin O.	Fig. 31	Htr.	2.5	4.75	—	20	15000	3000	HV
DR-3B27	Half-Wave Rectifier	4-pin M.	4B	Fil.	2.5	5.0	3000	250	8500	1000	HV
5R4GY	Full-Wave Rectifier	5-pin O.	5T	Fil.	5.0	2.0	900 <sup>4</sup> 950 <sup>7</sup>	150 <sup>4</sup> 175 <sup>7</sup>	2800	650	HV
5T4	Full-Wave Rectifier	5-pin O.	5T	Fil.	5.0	3.0	450	250	1250	800	HV
5U4G	Full-Wave Rectifier	8-pin O.	5T	Fil.	5.0	3.0	—	Same as Type 5Z3			HV
5V4G	Full-Wave Rectifier	8-pin O.	5L	Htr.	5.0	2.0	—	Same as Type 83V			HV
5W4	Full-Wave Rectifier	5-pin O.	5T	Fil.	5.0	1.5	350	110	1000	—	HV
5X3	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	2.0	1275	30	—	—	HV
5X4G	Full-Wave Rectifier	8-pin O.	5Q	Fil.	5.0	3.0	—	Same as 5Z3			HV
5Y3G	Full-Wave Rectifier	5-pin O.	5T	Fil.	5.0	2.0	—	Same as Type 80			HV
5Y4G	Full-Wave Rectifier	8-pin O.	5Q	Fil.	5.0	2.0	—	Same as Type 80			HV
5Z3	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	3.0	500	250	1400	—	HV
5Z4	Full-Wave Rectifier	5-pin O.	5L	Htr.	5.0	2.0	400	125	1100	—	HV
6W5G	Full-Wave Rectifier	6-pin O.	65	Htr.	6.3	0.9	350	100	1250	350	HV
6X4	Full-Wave Rectifier	7-pin B.	7CF	Htr.	6.3	0.6	325	70	1250	210	HV
6X5	Full-Wave Rectifier	6-pin O.	65	Htr.	6.3	0.5	350	75	—	—	HV
6Y5	Full-Wave Rectifier	6-pin S.	6J	Htr.	6.3	0.8	350	50	—	—	HV
6Z3	Half-Wave Rectifier	4-pin M.	4G	Fil.	6.3	0.3	350	50	—	—	HV
6Z5	Full-Wave Rectifier	6-pin S.	6K	Htr.	6.3	0.6	230	60	—	—	HV
6ZY5G	Full-Wave Rectifier	6-pin O.	6S	Htr.	6.3	0.3	350	35	1000	150	HV
7Y4	Full-Wave Rectifier	8-pin L.	5AB	Htr.	6.3	0.5	350	60	—	—	HV
7Z4	Full-Wave Rectifier	8-pin L.	5AB	Htr.	6.3	0.9	450 <sup>1</sup> 325 <sup>4</sup>	100	1250	300	HV
12A7	Rectifier-Pentode	7-pin S.	7K	Htr.	12.6	0.3	125	30	—	—	HV
12Z3	Half-Wave Rectifier	4-pin S.	4G	Htr.	12.6	0.3	250	60	—	—	HV
12Z5	Voltage Doubler	7-pin M.	7L	Htr.	12.6	0.3	225	60	—	—	HV
14Y4	Full-Wave Rectifier	8-pin L.	5AB	Htr.	12.6	0.3	450 <sup>1</sup> 325 <sup>4</sup>	70	1250	210	HV
14Z3	Half-Wave Rectifier	4-pin S.	4G	Htr.	12.6	0.3	250	60	—	—	HV
25A7G	Rectifier-Pentode	8-pin O.	8F	Htr.	25	0.3	125	75	—	—	HV
25X6GT	Voltage Doubler	7-pin O.	7Q	Htr.	25	0.15	125	60	—	—	HV
25Y4GT	Half-Wave Rectifier	6-pin O.	5AA	Htr.	25	0.15	125	75	—	—	HV
25Y5	Voltage Doubler	6-pin S.	6E	Htr.	25	0.3	250	85	—	—	HV
25Z3	Half-Wave Rectifier	4-pin S.	4G	Htr.	25	0.3	250	50	—	—	HV
25Z4	Half-Wave Rectifier	6-pin O.	5AA	Htr.	25	0.3	125	125	—	—	HV
25Z5	Rectifier-Doubler	6-pin S.	6E	Htr.	25	0.3	125	100	—	500	HV
25Z6	Rectifier-Doubler	7-pin O.	7Q	Htr.	25	0.3	125	100	—	500	HV
28Z5	Full-Wave Rectifier	8-pin L.	5AB	Htr.	28	0.24	450 <sup>7</sup> 325 <sup>4</sup>	100	—	300	HV
32L7GT	Rectifier-Tetrode	8-pin O.	8Z	Htr.	32.5	0.3	125	60	—	—	HV
35W4	Half-Wave Rectifier	7-pin B.	5BQ	Htr.	35 <sup>2</sup>	0.15	125	100 <sup>3</sup>	330	600	HV
35Y4	Half-Wave Rectifier	8-pin O.	5AL	Htr.	35 <sup>2</sup>	0.15	235	60 100 <sup>3</sup>	700	600	HV
35Z3	Half-Wave Rectifier	8-pin L.	4Z	Htr.	35	0.15	250 <sup>5</sup>	100	700	600	HV
35Z4GT	Half-Wave Rectifier	6-pin O.	5AA	Htr.	35	0.15	250	100	700	600	HV
35Z5G	Half-Wave Rectifier	6-pin O.	6AD	Htr.	35 <sup>2</sup>	0.15	125	60 100 <sup>3</sup>	—	—	HV
35Z6G	Voltage Doubler	6-pin O.	7Q	Htr.	35	0.3	125	110	—	500	HV

TABLE XIV—RECTIFIERS—RECEIVING AND TRANSMITTING—Continued

See also Table XII—Control and Regulator Tubes

Type No.	Name	Base	Socket Connections	Cathode	Fil or Heater		Max. A.C. Voltage Per Plate	D.C. Output Current Ma.	Max. Inverse Peak Voltage	Peak Plate Current Ma.	Type
					Volts	Amp.					
40Z5GT	Half-Wave Rectifier	6-pin O.	6AD	Htr.	40 <sup>2</sup>	0.15	125	60 100 <sup>8</sup>	—	—	HV
45Z3	Half-Wave Rectifier	7-pin B.	5AM	Htr.	45	0.075	117	65	350	390	HV
45Z5GT	Half-Wave Rectifier	6-pin O.	6AD	Htr.	45 <sup>2</sup>	0.15	125	60 100 <sup>8</sup>	—	—	HV
50X6	Voltage Doubler	8-pin L.	7AJ	Htr.	50	0.15	117	75	700	450	HV
50Y6GT	Full-Wave Rectifier	7-pin O.	7Q	Htr.	50	0.15	125	85	—	—	HV
50Z6G	Voltage Doubler	7-pin O.	7Q	Htr.	50	0.3	125	150	—	—	HV
50Z7G	Voltage Doubler	8-pin O.	8AN	Htr.	50	0.15	117	65	—	—	HV
70A7GT	Rectifier-Tetrad	8-pin O.	8AB	Htr.	70	0.15	125 <sup>5</sup>	60	—	—	HV
70L7GT	Rectifier-Tetrad	8-pin O.	8AA	Htr.	70	0.15	117	70	—	350	HV
72	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	3.0	—	30	20000	150	HV
73	Half-Wave Rectifier	8-pin O.	4Y	Fil.	2.5	4.5	—	20	13000	3000	HV
80	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	2.0	350 <sup>4</sup> 500 <sup>7</sup>	125 125	1400	375	HV
81	Half-Wave Rectifier	4-pin M.	4B	Fil.	7.5	1.25	700	85	—	—	HV
82	Full-Wave Rectifier	4-pin M.	4C	Fil.	2.5	3.0	500	125	1400	400	MV
83	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	3.0	500	250	1400	800	MV
83-V	Full-Wave Rectifier	4-pin M.	4AD	Htr.	5.0	2.0	400	200	1100	—	HV
84/6Z4	Full-Wave Rectifier	5-pin S.	5D	Htr.	6.3	0.5	350	60	1000	—	HV
117L7GT/ 117M7GT	Rectifier-Tetrad	8-pin O.	8AO	Htr.	117	0.09	117	75	—	—	HV
117N7GT	Rectifier-Tetrad	8-pin O.	8AV	Htr.	117	0.09	117	75	350	450	HV
117P7GT	Rectifier-Tetrad	8-pin O.	8AV	Htr.	117	0.09	117	75	350	450	HV
117Z3	Half-Wave Rectifier	7-pin B.	4BR	Htr.	117	0.04	117	90	330	—	HV
117Z4GT	Half-Wave Rectifier	6-pin O.	5AA	Htr.	117	0.04	117	90	350	—	HV
117Z6GT	Voltage Doubler	7-pin O.	7Q	Htr.	117	0.075	235	60	700	350	HV
217-A	Half-Wave Rectifier	4-pin J.	T-3A	Fil.	10	3.25	—	—	3500	600	HV
217-C	Half-Wave Rectifier	4-pin J.	T-3A	Fil.	10	3.25	—	—	7500	600	HV
Z225	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	250	10000	1000	MV
249-B	Half-Wave Rectifier	4-pin M.	Fig. 53	Fil.	2.5	7.5	3180	375	10000	1500	MV
HK253	Half-Wave Rectifier	4-pin J.	T-3A	Fil.	5.0	10	—	350	10000	1500	HV
705A RK-705A	Half-Wave Rectifier	4-pin W.	T-3AA	Fil.	2.5 <sup>9</sup> 5.0	5.0	—	50 100	35000 35000	375 750	HV
816	Half-Wave Rectifier	4-pin S.	4P	Fil.	2.5	2.0	1750	125	5000	500	MV
836	Half-Wave Rectifier	4-pin M.	4P	Htr.	2.5	5.0	—	—	5000	1000	HV
856A/866	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	3500	250	10000	1000	MV
866B	Half-Wave Rectifier	4-pin M.	4P	Fil.	5.0	5.0	—	—	8500	1000	MV
866 Jr.	Half-Wave Rectifier	4-pin M.	4B	Fil.	2.5	2.5	1250	250 <sup>3</sup>	—	—	MV
HY866 Jr.	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	2.5	1750	250 <sup>3</sup>	5000	—	MV
RK866	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	3500	250	10000	1000	MV
871 <sup>10</sup>	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	2.0	1750	250	5000	500	MV
878	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	7100	5	20000	—	HV
879	Half-Wave Rectifier	4-pin S.	4P	Fil.	2.5	1.75	2650	7.5	7500	100	HV
872A/872	Half-Wave Rectifier	4-pin J.	T-3A	Fil.	5.0	7.5	—	1250	10000	5000	MV
975A	Half-Wave Rectifier	4-pin J.	T-3A	Fil.	5.0	10.0	—	1500	15000	6000	MV
OZ4A/ 1003	Full-Wave Rectifier	5-pin O.	4R	Cold	—	—	—	110	880	—	G
1005/ CK1005	Full-Wave Rectifier	8-pin O.	T-9F	Fil.	6.3	0.1	—	70	450	—	G
1006/ CK1006	Full-Wave Rectifier	4-pin M.	4C	Fil.	1.75	2.25	—	200	1600	—	G
CK1007	Full-Wave Rectifier	8-pin O.	T-9G	Fil.	1.0	1.2	—	110	980	—	G
CK1009/BA	Full-Wave Rectifier	4-pin M.	—	Cold	—	—	—	350	1000	—	G
1275	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	1.75	—	—	Same as 523	—	HV
1616	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	130	6000	800	HV
1641/ RK60	Full-Wave Rectifier	4-pin M.	T-4AG	Fil.	5.0	3.0	—	50 250	4500 2500	—	HV
1654	Half-Wave Rectifier	7-pin B.	Fig. 41	Fil.	1.4	0.05	2530	1	7000	6	HV
8008	Half-Wave Rectifier	4-pin <sup>6</sup>	Fig. 11	Fil.	5.0	7.5	—	1250	10000	5000	MV
8013A	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	20	40000	150	HV
8016	Half-Wave Rectifier	6-pin O.	4AC	Fil.	1.25	0.2	—	2.0	10000	7.5	HV
8020	Half-Wave Rectifier	4-pin M.	4P	Fil.	5.0	5.5	10000	100	40000	750	HV
					5.8	6.5	12500	100	40000	750	
RK19	Full-Wave Rectifier	4-pin M.	T-3A	Htr.	7.5	2.5	1250	200 <sup>4</sup>	3500	600	HV
RK21	Half-Wave Rectifier	4-pin M.	4P	Htr.	2.5	4.0	1250	200 <sup>4</sup>	3500	600	HV
RK22	Full-Wave Rectifier	4-pin M.	T-4AG	Htr.	2.5	8.0	1250	200 <sup>4</sup>	3500	600	HV

<sup>1</sup> With input choke of at least 20 henrys.

<sup>2</sup> Tapped for pilot lamps.

<sup>3</sup> Per pair with choke input.

<sup>4</sup> Condenser input.

<sup>5</sup> With 100 ohms min. resistance in series with plate; without series resistor, maximum r.m.s. plate rating is 117 volts.

<sup>6</sup> Same as 872A/872 except for heavy-duty push-type base.

Filament connected to pins 2 and 3, plate to top cap.

<sup>7</sup> Choke input.

<sup>8</sup> Without panel lamp.

<sup>9</sup> Using only one-half of filament.

<sup>10</sup> Discontinued.

TABLE XV—TRIODE TRANSMITTING TUBES

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu\text{fd.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Mo.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts										
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.																					
958-A	0.6	1.25	0.1	135	7	1.0	12	0.6	2.6	0.8	500	A.	5BD	Class-C Amp.-Oscillator	135	- 20	7	1.0	0.035	—	0.6										
RK24	1.5	2.0	0.12	180	20	6.0	8.0	3.5	5.5	3.0	125	S.	4D	Class-C Amp.-Oscillator	180	- 45	16.5	6.0	0.5	—	2.0										
6J6 <sup>2</sup>	1.5	6.3	0.45	300	30	16	32	2.2	1.6	0.4	250	B.	7BF	Class-C Amp. (Telegraphy)	150	- 10	30	16	0.35	—	3.5										
9002	1.6	6.3	0.15	250	8	2.0	25	1.2	1.4	1.1	250	B.	7TM	Class-C Amp.-Oscillator	180	- 35	7	1.5	—	—	0.5										
955	1.6	6.3	0.15	180	8	2.0	25	1.0	1.4	0.6	250	A.	53C	Class-C Amp.-Oscillator	180	- 35	7	1.5	—	—	0.5										
HY114B	1.8	1.4	0.155	180	12	3.0	13	1.0	1.3	1.0	300	O.	2T	Class-C Amp.-Oscillator	180	- 30	12	2.0	0.2	—	1.4 <sup>3</sup>										
														Class-C Amp. (Telephony)	180	- 35	12	2.5	0.3	—	1.4 <sup>3</sup>										
3A5 <sup>2</sup>	2.0	1.4 2.8	0.22 0.11	150	30	5.0	15	0.9	3.2	1.0	40	B.	7BC	Class-C Amp.-Oscillator	150	- 35	30	5.0	0.2	—	2.2										
6F4	2.0	6.3	0.225	150	20	8.0	17	2.0	1.9	0.6	500	A.	7BR	Class-C Amp.-Oscillator	150	- 15	—	—	—	—	—	—									
HY24	2.0	2.0	0.13	180	20	4.5	9.3	2.7	5.4	2.3	60	S.	4D	Class-C Amp. (Telegraphy)	180	- 45	20	4.5	0.2	—	2.7										
														Class-C Amp. (Telephony)	180	- 45	20	4.5	0.3	—	2.5										
RK33 <sup>1, 2</sup>	2.5	2.0	0.12	250	20	6.0	10.5	3-2	3-2	2.5	60	S.	T-7DA	Class-C Amp.-Oscillator	250	- 60	20	6.0	0.54	—	3.5										
12AU7 <sup>2</sup>	2.75 <sup>6</sup>	6.3	0.3	350	12 <sup>4</sup>	3.5 <sup>6</sup>	18	1.5	1.5	0.5	54	B.	9A	Class-C Amp.-Oscillator	350	- 100	24	7	—	—	6.0										
6N4	3.0	6.3	0.2	180	12	—	32	3.1	2.35	0.55	500	B.	7CA	Class-C Amp.-Oscillator	100	—	—	—	—	—	—										
HY6J5GTX	3.5	6.3	0.3	330	20	4.0	20	4.2	3.8	5.0	60	O.	6Q	Class-C Amp.-Oscillator	330	- 30	20	2.0	0.2	—	3.5										
														Class-C Amp. (Telephony)	250	- 30	20	2.5	0.3	—	2.5										
2C22/7193	3.5	6.3	0.3	500	—	—	20	2.2	3.6	0.7	—	O.	4AM	Class-C Amp. (Telegraphy)	—	—	—	—	—	—	—										
HY615 HY-E1148	3.5	6.3	0.175	300	20	4.0	20	1.4	1.6	1.2	300	O.	T-8AG	Class-C Amp.-Oscillator	300	- 35	20	2.0	0.4	—	4.0 <sup>3</sup>										
														Class-C Amp. (Telephony)	300	- 35	20	3.0	0.8	—	3.5 <sup>3</sup>										
GL-446A <sup>1</sup> GL-446B <sup>1</sup>	3.75	6.3	0.75	400	20	—	45	2.2	1.6	0.02	500	O.	Fig. 19	Class-C Amp.-Oscillator	250	—	—	—	—	—	—										
GL-2C44 <sup>1</sup> GL-464A <sup>1</sup>	5.0	6.3	0.75	500	40	—	—	2.7	2.0	0.1	500	O.	Fig. 17	Class-C Amp.-Oscillator	250	—	—	—	—	—	—										
6C4	5.0	6.3	0.15	350	25	8.0	18	1.8	1.6	1.3	54	B.	63G	Class-C Amp.-Oscillator	300	- 27	25	7.0	0.35	—	5.5										
1626	5.0	12.6	0.25	250	25	8.0	5.0	3.2	4.4	3.4	30	O.	6Q	Class-C Amp.-Oscillator	250	- 70	25	5.0	0.5	—	4.0										
2C21/ RK33 <sup>2</sup>	5.0	6.3	0.6	250	40	12	—	1.6	1.6	2.0	—	S.	T-7DA	Class-C Amp.-Oscillator	250	- 60	40	12	1.0	—	7										
6N7 <sup>2</sup>	5.5 <sup>4</sup>	6.3	0.8	350	30 <sup>6</sup>	5.0 <sup>6</sup>	35	—	—	—	10	O.	8B	Class-C Amp. Oscillator	350	- 100	60	10	—	—	14.5										
2C40	6.5	6.3	0.75	500	25	—	36	2.1	1.3	0.05	500	O.	Fig. 19	Class-C Amp.-Oscillator	250	- 5	20	0.3	—	—	0.075										
5556	7.0	4.5	1.1	350	40	10	8.5	4.0	8.3	3.0	6	M.	4D	Class-C Amp. (Telegraphy)	350	- 80	35	2	0.25	—	6										
														Class-C Amp. (Telephony)	300	- 100	30	2	0.3	—	4										
2C43	12	6.3	0.9	500	40	—	48	2.9	1.7	0.05	1250	O.	Fig. 19	Class-C Amp.-Oscillator	470	—	38 <sup>7</sup>	—	—	—	9 <sup>7</sup>										
2C26A	10	6.3	1.10	—	—	—	16.3	2.6	2.8	1.1	250	O.	48B	—	—	—	—	—	—	—	—										
2C34/ RK34 <sup>2</sup>	10	6.3	0.8	300	80	20	13	3.4	2.4	0.5	250	M.	T-7DC	Class-C Amp.-Oscillator	300	- 36	80	20	1.8	—	16										
205D	14	4.5	1.6	400	50	10	7.2	5.2	4.8	3.3	6	M.	4D	Class-C Amp.-Oscillator	400	- 112	45	10	1.5	—	10										
														Class-C Amp. (Telephony)	350	- 144	35	10	1.7	—	7.1										
2C25	15	7.0	1.18	450	60	15	8.0	6.0	8.9	3.0	—	M.	4D	Class-C Amp.-Oscillator	470	- 100	65	15	3.2	—	19										
														Class-C Amp. (Telephony)	350	- 100	50	12	2.2	—	12										
														Class-C Amp. (Telephony)	450	- 100	65	15	3.2	—	19										
10Y	15	7.5	1.25	450	65	15	8	4.1	7.0	3.0	8	M.	4D	Class-C Amp.-Oscillator	450	- 100	65	15	3.2	—	19										
														Class-C Amp. (Telephony)	350	- 100	50	12	2.2	—	12										



TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interletrade Capacitances ( $\mu\text{mfd.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
843	15	2.5	2.5	450	40	7.5	7.7	4.0	4.5	4.0	6	M.	5A	Class-C Amo.-Oscillator	450	-140	30	5.0	1.0	—	7.5
														Class-C Amp. (Telephony)	350	-150	30	7.0	1.6	—	5.0
RK59 <sup>2</sup>	15	6.3	1.0	500	90	25	25	5.0	9.0	1.0	—	M.	T-4D	Class-C Amo.-Oscillator	500	-60	90	14	1.3	—	32
HY75A	15	6.3	2.6	450	90	25	9.6	1.8	2.6	1.0	175	O.	2T	Class-C Amp. (Telegraphy)	450	-140	90	20	5.2	—	26
														Class-C Amp. (Telephony)	400	-140	90	20	5.2	—	21
HY75	15	6.3	2.5	450	80	20	10	1.8	3.8	1.0	60	O.	2T	Class-C Amp.-Oscillator	450	-50	80	12	—	—	21 <sup>1</sup>
														Class-C Amp. (Telephony)	450	-60	80	12	—	—	16 <sup>3</sup>
														Class-C Amo. (Telegraphy)	450	-115	55	15	3.3	—	13
1602	15	7.5	1.25	450	60	15	8.0	4.0	7.0	3.0	6	M.	4D	Class-C Amp. (Telephony)	350	-135	45	15	3.5	—	8.0
														Class-B Amp. Audio <sup>7</sup>	425	-50	110 <sup>8</sup>	260 <sup>9</sup>	2.5 <sup>8</sup>	8000	25
														Class-C Amp. (Telegraphy)	450	-34	50	15	1.8	—	15
841	15	7.5	1.25	450	60	20	30	4.0	7.0	3.0	6	M.	4D	Class-C Amp. (Telephony)	350	-47	50	15	2.0	—	11
														Class-C Amp. (Telegraphy)	450	-100	65	15	3.2	—	19
10 RK10 <sup>1</sup>	15	7.5	1.25	450	65	15	8.0	3.0	8.0	4.0	— 60	M.	4D	Class-C Amo. (Telephony)	350	-100	50	12	2.2	—	12
														Class-B Audio <sup>7</sup>	425	-50	55 <sup>8</sup>	130 <sup>9</sup>	2.5 <sup>8</sup>	8000	25
RK100 <sup>1</sup>	15	6.3	0.9	150	250	100	40	23	19	3.0	—	M.	T-6B	Class-C Oscillator	110	—	80	8.0	—	—	3.5
														Class-C Amplifier	110	—	185	40	2.1	—	12
TUF-20	20	6.3	2.75	750	75	20	10	1.8	3.6	0.095	250	O.	2T	Class-C Amp.-Oscillator	750	-150	75	20	1.5/2.5	—	40
														Class-C Amp. (Telegraphy)	425	-90	95	20	3.0	—	27
1608	20	2.5	2.5	425	95	25	20	8.5	9.0	3.0	45	M.	4D	Class-C Amp. (Telephony)	350	-80	85	20	3.0	—	18
														Class-B Amo. Audio <sup>7</sup>	425	-15	190 <sup>8</sup>	130 <sup>9</sup>	2.2 <sup>8</sup>	4800	50
														Class-C Amp. (Telegraphy)	600	-150	65	15	4.0	—	25
310	20	7.5	1.25	600	70	15	8.0	4.0	7.0	2.2	6	M.	4D	Class-C Amp. (Telephony)	500	-190	55	15	4.5	—	18
														Class-C Amo. (Telegraphy)	600	-150	65	15	4.0	—	25
801-A/001	20	7.5	1.25	600	70	15	8.0	4.5	6.0	1.5	60	M.	4D	Class-C Amp. (Telephony)	500	-190	55	15	4.5	—	18
														Class-B Amp. Audio <sup>7</sup>	600	-75	130	320 <sup>9</sup>	3.0 <sup>8</sup>	10000	45
														Class-C Amp. (Telegraphy)	600	-200	70	15	4.0	—	30
HY801-A	20	7.5	1.25	600	70	15	8.0	4.5	6.0	1.5	60	M.	4D	Class-C Amp. (Telephony)	500	-200	60	15	4.5	—	22
T20	20	7.5	1.75	750	85	25	20	4.9	5.1	0.7	60	M.	3G	Class-C Amp. (Telegraphy)	750	-85	85	18	3.6	—	44
														Class-C Amp. (Telephony)	750	-140	70	15	3.6	—	38
														Class-C Amp. (Telegraphy)	750	-40	85	28	3.75	—	44
TZ20	20	7.5	1.75	750	85	30	62	5.3	5.0	0.6	60	M.	3G	Class-C Amp. (Telephony)	750	-100	70	23	4.8	—	38
														Class-B Amp. Audio <sup>7</sup>	800	0	40/136	160 <sup>9</sup>	1.8 <sup>8</sup>	12000	70
15E	20	5.5	4.2	—	—	—	25	1.4	1.15	0.3	600	N.	T-4AF	—	—	—	—	—	—	—	—
3-25A3 25T	25	6.3	3.0	2000	75	25	24	2.7	1.5	0.3	60	M.	3G	Class-C Amp.-Oscillator	2000	-130	63	18	4.0	—	100
														Class-C Amp. (Telephony)	1500	-95	67	13	2.2	—	75
														Class-C Amp. (Telephony)	1000	-70	72	9	1.3	—	47
														Class-B Amo. Audio <sup>7</sup>	2000	-80	16/80	270 <sup>9</sup>	0.7 <sup>8</sup>	55500	110
3-25D3 3C24 24G	25	6.3	3.0	2000	75	25	23	2.0 1.7	1.6 1.5	0.2 0.3	60	S.	2D	Class-C Amp.-Oscillator	2000	-170	63	17	4.5	—	100
														Class-C Amp. (Telephony)	1500	-110	67	15	3.1	—	75
														Class-C Amp. (Telephony)	1000	-80	72	15	2.6	—	47
														Class-B Audio <sup>7</sup>	2000	-85	16/80	290 <sup>9</sup>	1.1 <sup>8</sup>	55500	110
3C28	25	6.3	3.0	2000	75	25	23	2.1	1.8	0.1	100	S.	Fig. 56	Class-C Amp. Oscillator	Characteristics same as 3C24						
3C34	25	6.3	3.0	2000	75	25	23	2.5	1.7	0.4	60	S.	3G	Class-C Amp. Oscillator	Characteristics same as 3C24						

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu\text{mfd.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
RK11 <sup>1</sup>	25	6.3	3.0	750	105	35	20	7.0	7.0	0.9	60	M.	3G	Class-C Amp. (Telegraphy)	750	-120	105	21	3.2	---	55
														Class-C Amp. (Telephony)	600	-120	85	24	3.7	---	38
RK12	25	6.3	3.0	750	105	40	100	7.0	7.0	0.9	60	M.	3G	Class-C Amp. (Telegraphy)	750	-100	105	35	5.2	---	55
														Class-C Amp. (Telephony)	600	-100	85	27	3.8	---	38
HK24	25	6.3	3.0	2000	75	30	25	2.5	1.7	0.4	60	5.	3G	Class-C Amp. (Telegraphy)	2000	-140	56	18	4.0	---	90
														Class-C Amp. (Telephony)	1500	-145	50	25	5.5	---	60
HY25	25	7.5	2.25	800	75	25	55	4.2	4.6	1.0	60	M.	3G	Class-C Amp. (Telegraphy)	750	-45	75	15	2.0	---	42
														Class-C Amp. (Telephony)	700	-45	75	17	5.0	---	39
8025	30	6.3	1.92	1000	65	---	18	2.7	2.8	0.35	500	M.	4AQ	Class-C Amp. (Grid. Mod.)	1000	-135	50	4	3.5	---	20
	20				65	20								800	-105	40	10.5	1.4	---	22	
	30				80	20								1000	-90	50	14	1.6	---	35	
HY30Z <sup>1</sup>	30	6.3	2.25	850	90	25	87	6.0	4.9	1.0	60	M.	4B0	Class-C Amp.-Oscillator	850	-75	90	25	2.5	---	58
														Class-C Amp. (Telephony)	700	-75	90	25	3.5	---	47
HY31Z <sup>2</sup> HY1231Z <sup>2</sup>	30	6.3	3.5	500	150	30	45	5.0	5.5	1.9	60	M.	T-4D	Class-C Amp. (Telegraphy)	500	-45	150	25	2.5	---	56
		12.6	1.7											400	-100	150	30	3.5	---	45	
316A	30	2.0	3.65	450	80	12	6.5	1.2	1.6	0.8	500	N.	---	Class-C Amp. (Telegraphy)	450	---	80	12	---	---	7.5
														Class-C Amp. (Telephony)	400	---	80	12	---	---	6.5
809	30	6.3	2.5	1000	125	---	50	5.7	6.7	0.9	60	M.	3G	Class-C Amp. (Telegraphy)	1000	-75	100	25	3.8	---	75
														Class-C Amp. (Telephony)	750	-60	100	32	4.3	---	55
														Class-B Amp. Audio <sup>7</sup>	1000	-9	40/200	155 <sup>9</sup>	2.7 <sup>8</sup>	11600	145
1623	30	6.3	2.5	1000	100	25	20	5.7	6.7	0.9	60	M.	3G	Class-C Amp.-Oscillator	1000	-90	100	20	3.1	---	75
														Class-C Amp. (Telephony)	750	-125	100	20	4.0	---	55
														Class-B Amp. Audio <sup>7</sup>	1000	-40	30/200	230 <sup>9</sup>	4.2 <sup>8</sup>	12000	145
53A	35	5.0	12.5	15000	---	---	35	3.6	1.9	0.4	---	N.	T-4B	Oscillator at 300 Mc.	Approximately 50 watts output						
RK30 <sup>1</sup>	35	7.5	3.25	1250	80	25	15	2.75	2.5	2.75	60	M.	2D	Class-C Amp. (Telegraphy)	1250	-180	90	18	5.2	---	85
														Class-C Amp. (Telephony)	1000	-200	80	15	4.5	---	60
800	35	7.5	3.25	1250	80	25	15	2.75	2.5	2.75	60	M.	2D	Class-C Amp. (Telegraphy)	1250	-175	70	15	4.0	---	65
														Class-C Amp. (Telephony)	1000	-200	70	15	4.0	---	50
														Class-B Amp. Audio <sup>7</sup>	1250	-70	30/130	300 <sup>9</sup>	3.4 <sup>8</sup>	21000	106
1628 <sup>1</sup>	40	3.5	3.25	1000	60	15	23	2.0	2.0	0.4	500	N.	T-4BB	Class-C Amp.-Oscillator	1000	-65	50	15	1.7	---	35
														Class-C Amp. (Telephony)	800	-100	40	11	1.6	---	22
														Grid-Modulated Amp.	1000	-120	50	3.5	5.0	---	20
8012 GL-0012-A	40	6.3	2.0	1000	80	20	18	2.7	2.8	0.35	500	N.	T-4BB	Class-C Amp.-Oscillator	1000	-90	50	14	1.6	---	35
								2.7	2.5	0.4				Class-C Amp. (Telephony)	800	-105	40	10.5	1.4	---	22
								Grid-Modulated Amp.	1000	-135				50	4.0	3.5	---	20			
RK18 <sup>1</sup>	40	7.5	3.0	1250	100	40	10	6.0	4.8	1.8	60	M.	3G	Class-C Amp. (Telegraphy)	1250	-160	100	12	2.8	---	95
														Class-C Amp. (Telephony)	1000	-160	80	13	3.1	---	64
RK31	40	7.5	3.0	1250	100	35	170	7.0	1.0	2.0	30	M.	3G	Class-C Amp. (Telegraphy)	1250	-80	100	30	3.0	---	90
														Class-C Amp. (Telephony)	1000	-80	100	28	3.5	---	70
HY40 <sup>1</sup>	40	7.5	2.25	1000	125	25	25	6.1	5.6	1.0	60	M.	3G	Class-C Amp. (Telegraphy)	1000	-90	125	20	5.0	---	94
														Class-C Amp. (Telephony)	850	-90	125	25	5.0	---	92
														Grid-Modulated Amp.	1000	---	125	---	---	---	20

100

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D. C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances (μmfd.)			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D. C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
HY40Z <sup>1</sup>	40	7.5	2.6	1000	125	30	80	6.2	6.3	0.8	60	M.	3G	Class-C Amp. (Telegraphy)	1000	- 27	125	25	5.0	—	94
														Class-C Amp. (Telephony)	1000	- 30	100	30	7.0	—	82
														Grid-Modulated Amp.	1000	—	60	—	—	—	20
T40	40	7.5	2.5	1500	150	40	25	4.5	4.8	0.8	60	M.	3G	Class-C Amp.-Oscillator	1500	-140	150	28	9.0	—	158
														Class-C Amp. (Telephony)	1250	-115	115	20	5.25	—	104
														Class-C Amp.-Oscillator	1500	- 90	150	38	10	—	165
TZ40	40	7.5	2.5	1500	150	45	62	4.8	5.0	0.8	60	M.	3G	Class-C Amp. (Telephony)	1250	-100	125	30	7.5	—	116
														Class-B Amp. Audio <sup>7</sup>	1500	- 9	250 <sup>3</sup>	285 <sup>3</sup>	6.0 <sup>3</sup>	12000	250
														Class-C Amp. (Telegraphy)	850	- 48	110	15	2.5	—	70
HY57	40	6.3	2.25	850	110	25	50	4.9	5.1	1.7	60	M.	3G	Class-C Amp. (Telephony)	700	- 45	90	17	5.0	—	47
														Grid-Modulated Amp.	850	—	70	—	—	—	20
														Class-C Amplifier	850	—	110	25	—	—	—
756 <sup>1</sup>	40	7.5	2.0	850	110	25	8.0	3.0	7.0	2.7	—	M.	4D	Class-C Amplifier	750	-180	110	18	7.0	—	55
830 <sup>1</sup>	40	10	2.15	750	110	18	8.0	4.9	9.9	2.2	15	M.	4D	Grid-Modulated Amp.	1000	-200	50	2.0	3.0	—	15
3-50A4 35T 3-50D4 35TG	50	5.0	4.0	2000	150	50	39	4.1	1.8	0.3	100	M.	3G	Class-C Amp. (Telegraphy)	2000	-135	125	45	13	—	200
														Class-C Amp. (Telephony)	1500	-120	100	30	5.0	—	120
														Class-B Amp. Audio <sup>7</sup>	2000	- 40	34/167	255 <sup>3</sup>	4.0 <sup>3</sup>	27500	235
8010-R	50	6.3	2.4	1350	150	20	30	2.3	1.5	0.07	350	N.	—	Class-C Amplifier	—	—	—	—	—	—	—
														Class-C Amp. (Telegraphy)	1250	-225	100	14	4.8	—	90
														Class-C Amp. (Telephony)	1000	-310	100	21	8.7	—	70
RK32 <sup>1</sup>	50	7.5	3.25	1250	130	25	11	2.5	3.4	0.7	100	M.	2D	Class-C Amp. (Telegraphy)	1500	-250	115	15	5.0	—	120
														Class-C Amp. (Telephony)	1250	-250	100	14	4.6	—	93
														Grid-Modulated Amp.	1500	-180	37	—	2.0	—	25
RK37	50	7.5	4.0	1500	125	25	23	3.5	3.2	0.2	60	M.	2D	Class-C Amp. (Telegraphy)	1500	-130	115	30	7.0	—	122
														Class-C Amp. (Telephony)	1250	-150	100	23	5.6	—	90
														Grid-Modulated Amp.	1500	- 50	50	—	2.4	—	26
3-50G2 UH50	50	7.5	3.25	1250	125	25	10.6	2.2	2.6	0.3	60	M.	2D	Class-C Amp. (Telegraphy)	1250	-225	125	20	7.5	—	115
														Class-C Amp. (Telephony)	1250	-325	125	20	10	—	115
														Grid-Modulated Amp.	1250	-200	60	2.0	3.0	—	25
UH51 <sup>1</sup>	50	5.0	6.5	2000	175	25	10.6	2.2	2.3	0.3	60	M.	2D	Class-C Amp. (Telegraphy)	2000	-500	150	20	15	—	225
														Class-C Amp. (Telephony)	1500	-400	165	20	15	—	200
														Grid-Modulated Amp.	1500	-400	85	2.0	8.0	—	65
HK54	50	5.0	5.0	3000	150	30	27	1.9	1.9	0.2	100	M.	2D	Class-C Amp. (Telegraphy)	3000	-290	100	25	10	—	250
														Class-C Amp. (Telephony)	2500	-250	100	20	8.0	—	210
														Class-B Amp. Audio <sup>7</sup>	2500	- 85	20/150	350 <sup>3</sup>	5.0	40000	275
HK134 <sup>1</sup>	50	5.0	6.5	1500	175	30	6.7	4.3	5.9	1.1	60	M.	2D	Class-C Amp. (Telegraphy)	1500	-590	167	20	15	—	200
														Class-C Amp. (Telephony)	1250	-460	170	20	12	—	162
														Grid-Modulated Amp.	1500	-450	52	—	5.0	—	28
HK134B	50	12.6	2.5	2000	200	40	25	4.7	4.6	1.0	60	M.	2D	Class-C Amp.-Oscillator	2000	-150	125	25	6.0	—	200
														Class-C Amp. (Telephony)	2000	-140	105	25	5.0	—	170
														Class-C Amp. (Telegraphy)	1250	-200	100	—	—	—	85
WE304A <sup>1</sup> 304B	50	7.5	3.25	1250	100	25	11	2.0	2.5	0.7	100	M.	2D	Class-C Amp. (Telephony)	1000	-180	100	—	—	—	65

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu\text{mf.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
355A	50	5.0	5.0	1500	120	35	50	2.25	2.75	1.0	60	N.	T-4BD	Class-C Amp. (Telegraphy)	1500	- 60	100	—	—	—	100
														Class-C Amp. (Telephony)	1250	- 100	100	35	—	—	85
608	50	7.5	4.0	1500	150	35	47	5.3	2.8	0.15	30	M.	2D	Class-C Amp. (Telegraphy)	1500	- 200	125	30	9.5	—	140
														Class-C Amp. (Telephony)	1250	- 225	100	32	10.5	—	105
														Class-B Amp. Audio <sup>7</sup>	1500	- 25	30/190	220 <sup>9</sup>	4.8 <sup>8</sup>	18300	185
834	50	7.5	3.1	1250	100	20	10.5	2.2	2.6	0.6	100	M.	2D	Class-C Amp. (Telegraphy)	1250	- 225	90	15	4.5	—	75
														Class-C Amp. (Telephony)	1000	- 310	90	17.5	6.5	—	58
641A <sup>1</sup>	50	10	2.0	1250	150	30	14.6	3.5	9.0	2.5	—	M.	3G	Class-C Amplifier	—	—	—	—	—	—	85
641SW	50	10	2.0	1000	150	30	14.6	—	9.0	—	—	M.	3G	Class-C Amplifier	—	—	—	—	—	—	—
T55	55	7.5	3.0	1500	150	40	20	5.0	3.9	1.2	60	M.	3G	Class-C Amp. (Telegraphy)	1500	- 170	150	18	6.0	—	170
														Class-C Amp. (Telephony)	1500	- 195	125	15	5.0	—	145
811	55	6.3	4.0	1500	150	50	160	5.5	5.5	0.6	60	M.	3G	Class-C Amp. (Telegraphy)	1500	- 113	150	35	8.0	—	170
														Class-C Amp. (Telephony)	1250	- 125	125	50	11	—	120
														Class-B Amp. Audio <sup>7</sup>	1500	- 9	20/200	150 <sup>9</sup>	3.0 <sup>8</sup>	17600	220
														Class-C Amp. (Telegraphy)	1500	- 175	150	25	6.5	—	170
812	55	6.3	4.0	1500	150	35	29	5.3	5.3	0.8	60	M.	3G	Class-C Amp. (Telephony)	1250	- 125	125	25	6.0	—	120
														Class-B Amp. Audio <sup>7</sup>	1500	- 45	50/200	232 <sup>9</sup>	4.7 <sup>8</sup>	18000	225
														Class-C Amp. (Telegraphy)	1500	- 250	150	31	10	—	170
														Class-C Amp. (Telephony)	1250	- 200	105	17	4.5	—	96
RK51	60	7.5	3.75	1500	150	40	20	6.0	6.0	2.5	60	M.	3G	Grid-Modulated Amp.	1500	- 130	60	0.4	2.3	—	128
														Class-C Amp. (Telegraphy)	1500	- 120	130	40	7.0	—	135
														Class-C Amp. (Telephony)	1250	- 120	115	47	8.5	—	102
														Class-B Amp. Audio <sup>7</sup>	1250	0	40/300	180 <sup>9</sup>	7.5 <sup>8</sup>	10000	250
T-60 HF60	60	10	2.5	1600	150	50	20	5.5	5.2	2.5	60 30	M.	2D	Class-C Amp.-Oscillator	1500	- 150	150	50	9.0	—	100
														Class-C Amp.-Oscillator	1000	- 70	125	35	5.8	—	86
826	60	7.5	4.0	1000	125	40	31	3.7	2.9	1.4	250	N.	T-9A	Class-C Amp. (Telephony)	800	- 98	94	35	6.2	—	53
														Grid-Modulated Amp.	1000	- 125	65	9.5	8.2	—	25
														Class-C Amp.-Oscillator	1000	- 110	140	30	7.0	—	90
														Class-C Amp. (Telephony)	800	- 150	95	20	5.0	—	50
830B 930B	60	10	2.0	1000	150	30	25	5.0	11	1.0	15	M.	3G	Class-B Amp. Audio <sup>7</sup>	1000	- 35	20/280	270 <sup>9</sup>	6.0 <sup>8</sup>	7600	175
														Class-C Amp. (Telegraphy)	1000	- 75	175	20	7.5	—	131
														Class-C Amp. (Telephony)	1000	- 67.5	130	15	7.5	—	104
HY51A <sup>1</sup> HY51B <sup>1</sup>	65	7.5 10	3.5 2.25	1000	175	25	25	6.5	7.0	1.1	60	M.	3G	Grid-Modulated Amp.	1000	—	100	—	—	—	33
														Class-C Amp. (Telegraphy)	1000	- 22.5	175	35	10	—	131
														Class-C Amp. (Telephony)	1000	- 30	150	35	10	—	104
HY51Z <sup>1</sup>	65	7.5	3.5	1000	175	35	05	7.0	7.2	0.9	60	M.	4B0	Grid-Modulated Amp.	1000	—	100	—	—	—	33
														Class-C Amp. (Telegraphy)	1500	- 106	175	60	12	—	200
														Class-C Amp. (Telephony)	1250	- 84	142	60	10	—	135
5514	65	7.5	3.0	1500	175	60	145	7.0	7.9	1.0	60	M.	4B0	Class-B Audio <sup>7</sup>	1500	- 4.5	350 <sup>8</sup>	88 <sup>8</sup>	6.5 <sup>8</sup>	10500	400
														Class-C Amp. (Telegraphy)	1500	- 170	150	30	7.0	—	170
														Class-C Amp. (Telephony)	1500	- 120	100	30	5.0	—	120
UH35 <sup>1</sup>	70	5.0	4.0	1500	150	35	30	1.4	1.6	0.2	60	M.	3G	Class-C Amp. (Telegraphy)	1500	- 215	130	6.0	3.0	—	140
														Class-C Amp. (Telephony)	1250	- 250	130	6.0	3.0	—	120
V70 V70B	70	10	2.5	1500	140	25	14	5.0	9.0	2.3	—	J. M.	T-3AB 3G	Class-C Amp. (Telegraphy)	1500	- 215	130	6.0	3.0	—	140
														Class-C Amp. (Telephony)	1250	- 250	130	6.0	3.0	—	120

969

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu\mu\text{fd.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
V70A V70C	70	10	2.5	1500	140	20	25	5.0	9.5	2.0	—	J. M.	T-3AB 3G	Class-C Amp. (Telegraphy)	1000	-110	140	30	7.0	—	90
50T <sup>1</sup>	75	5.0	6.0	3000	100	30	12	2.0	2.0	0.4	—	M.	2D	Class-C Amp. (Telephony)	800	-150	95	20	5.0	—	50
3-75A3 75TH	75	5.0	6.25	3000	225	40	20	2.7	2.3	0.3	40	M.	2D	Class-C Amplifier	3000	-600	100	25	—	—	250
3-75A2 75TL						35	12	2.6	2.4	0.4				Class-C Amp. (Telegraphy)	2000	-200	150	32	10	—	—
HF75	75	10	3.25	2000	120	—	12.5	—	2.0	—	75	M.	2D	Class-B Amp. Audio <sup>7</sup>	2000	-90	50/225	350 <sup>9</sup>	3 <sup>9</sup>	19300	300
TW75	75	7.5	4.15	2000	175	60	20	3.35	1.5	0.7	60	M.	2D	Class-C Amp. (Telegraphy)	2000	-300	150	21	8	—	225
T-100 HF100	75	10	2.0	1500	150	30	23	3.5	4.5	1.4	30	M.	2D	Class-B Amp. Audio <sup>7</sup>	2000	-160	50/250	535 <sup>9</sup>	5 <sup>9</sup>	18000	350
														Class-C Oscillator-Amp.	2000	—	120	—	—	—	150
														Class-C Amp.-Oscillator	2000	-175	150	37	12.7	—	225
														Class-C Amp. (Telephony)	2000	-260	125	32	13.2	—	198
UE-100	75	10	2.5	1750	150	30	23	3.5	4.5	1.4	30	M.	2D	Class-C Amp. (Telephony)	1500	-200	150	18	6.0	—	170
														Class-C Amp. (Telephony)	1250	-250	110	21	8.0	—	105
														Grid-Modulated Amp.	1500	-280	72	1.5	6.0	—	42
														Class-B Amp. Audio <sup>7</sup>	1750	-62	40/270	324 <sup>9</sup>	9.0 <sup>9</sup>	16000	350
111H	75	10	2.25	1500	160	—	23	—	4.6	—	25	M.	2D	Class-C Amp. (Telephony)	1500	-200	150	18	6.0	—	170
														Class-C Amp. (Telephony)	1250	-250	120	21	8.0	—	105
ZB120	75	10	2.0	1250	160	40	90	5.3	5.2	3.2	30	J.	4E	Class-B Audio <sup>7</sup>	1750	-62	540 <sup>8</sup>	—	9.0	16000	350
327D	75	10.5	10.6	—	—	—	30	3.4	2.45	0.3	—	N.	T-4AD	Class-C Osc.-Amp.	1500	—	160	—	—	—	175
242A	85	10	3.25	1250	150	50	12.5	6.5	13	4.0	6	J.	4E	Class-C Amp. (Telegraphy)	1250	-135	160	23	5.5	—	145
284D	85	10	3.25	1250	150	100	4.8	6.0	8.3	5.6	—	J.	4E	Class-C Amp. (Telephony)	1000	-150	120	21	5.0	—	95
														Grid-Modulated Amp.	1250	—	95	8.0	1.5	—	45
812-H	85	6.3	4.0	1750	200	45	—	5.3	5.3	0.8	30	M.	3G	Class-B Amp. Audio <sup>7</sup>	1500	-9	60/296	196 <sup>9</sup>	5.0 <sup>9</sup>	11200	300
														Class-C Amp. (Telegraphy)	1750	-175	170	26	6.5	—	225
														Class-C Amp. (Telephony)	1250	-125	125	25	5.0	—	116
														Class-C Amp. (Telephony)	1500	-125	165	21	6.0	—	180
8005	85	10	3.25	1500	200	45	20	6.4	5.0	1.0	60	M.	3G	Class-C Amp. (Telephony)	1250	-125	125	25	6.0	—	120
														Class-C Amp. (Telephony)	1250	-125	125	25	6.0	—	120
														Class-C Amp.-Oscillator	1500	-46	42/200	—	—	18000	225
														Class-C Amp. (Telephony)	1500	-130	200	32	7.5	—	220
V-70-D	85	7.5	3.25	1750	200	45	—	4.5	4.5	1.7	30	M.	3G	Class-C Amp. (Telephony)	1250	-195	190	28	9.0	—	170
														Class-B Amp. Audio <sup>7</sup>	1500	-70	40/310	310 <sup>9</sup>	4.0 <sup>9</sup>	10000	300
														Class-C Amp. (Telegraphy)	1750	-100	170	19	3.9	—	225
														Class-C Amp. (Telephony)	1500	-90	165	19	3.9	—	195
RK36 <sup>1</sup>	100	5.0	8.0	3000	165	35	14	4.5	5.0	1.0	60	M.	2D	Class-C Amp. (Telephony)	1500	-90	165	19	3.7	—	185
														Class-C Amp. (Telephony)	1250	-72	127	16	2.6	—	122
														Class-C Amp. (Telegraphy)	2000	-360	150	30	15	—	200
														Class-C Amp. (Telephony)	2000	-360	150	30	15	—	200
														Grid-Modulated Amp.	2000	-270	72	1.0	3.5	—	42

507

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu\text{mf.d.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
RK38 <sup>1</sup>	100	5.0	8.0	3000	165	40	—	4.6	4.3	0.9	60	M.	2D	Class-C Amp. (Telegraphy)	2000	-200	160	30	10	—	225
														Class-C Amp. (Telephony)	2000	-200	160	30	10	—	225
														Grid-Modulated Amp.	2000	-150	80	2.0	5.5	—	60
3-100A4 100TH	100	5.0	6.3	3000	225	60	40	2.9	2.0	0.4	40	M.	2D	Class-C Amp. (Telegraphy)	3000	-200	165	51	18	—	400
														Class-C Amp. (Telephony)	3000	-210	167	45	18	—	400
														Grid-Modulated Amp.	3000	-400	70	3.0	7.0	—	100
														Class-B Amp. (Audio) <sup>7</sup>	3000	-65	40/215	335 <sup>9</sup>	5.0 <sup>8</sup>	31000	650
3-100A2 100TL	100	5.0	6.3	3000	225	50	14	2.3	2.0	0.4	40	M.	2D	Class-C Amp. (Telegraphy)	3000	-400	165	30	20	—	400
														Class-C Amp. (Telephony)	3000	-600	167	35	18	—	400
														Grid-Modulated Amp.	3000	-560	60	2.0	7.0	—	90
														Class-B Amp. (Audio) <sup>7</sup>	3000	-185	43/215	640 <sup>9</sup>	6.0 <sup>8</sup>	30000	450
VT127A	100	5.0	10.4	3000	—	30	15.5	2.7	2.3	0.35	150	N.	T-4B	Class-C Amp.-Oscillator	Characteristics similar to 100TL						
227A	100	10.5	10.7	—	—	—	31	3.0	2.2	0.30	—	N.	T-4B	Oscillator at 200 Mc.	—	—	—	—	—	—	
327A	100	10.5	10.7	—	—	—	31	3.4	2.3	0.35	—	N.	T-4AD	Oscillator at 200 Mc.	—	—	—	—	—	—	
HK254	100	5.0	7.5	4000	200	40	25	3.3	3.4	1.1	50	J.	2N	Class-C Amp. (Telegraphy)	4000	-380	120	35	20	—	475
														Class-C Amp. (Telephony)	3000	-290	135	40	23	—	320
														Grid-Modulated Amp.	3000	—	51	3.0	4.0	—	58
														Class-B Amp. (Audio) <sup>7</sup>	3000	-100	40/240	456 <sup>9</sup>	7.0 <sup>8</sup>	30000	520
RK58	100	10	3.25	1250	175	70	—	8.5	6.5	10.5	—	J.	T-3AB	Class-C Amp. (Telegraphy)	1250	-90	150	30	6.0	—	130
														Class-C Amp. (Telephony)	1000	-135	150	50	16	—	100
HF120	100	10	3.25	1250	175	—	12	—	10.5	—	20	J.	—	Class-C Amp.-Oscillator	1250	—	175	—	—	—	150
HF125	100	10	3.25	1500	175	—	25	—	11.5	—	30	J.	—	Class-C Amp.-Oscillator	1500	—	175	—	—	—	200
HF140	100	10	3.25	1250	175	—	12	—	12.5	—	15	J.	—	Class-C Amp.-Oscillator	1250	—	175	—	—	—	150
203A 303A	100	10	3.25	1250	175	60	25	6.5	14.5	5.5	15	J.	4E	Class-C Amp. (Telegraphy)	1250	-125	150	25	7.0	—	130
														Class-C Amp. (Telephony)	1000	-135	150	50	14	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	-45	26/320	330 <sup>9</sup>	11 <sup>8</sup>	9000	260
203H	100	10	3.25	1500	175	60	25	6.5	11.5	1.5	15	J.	T-3AB	Class-C Amp. (Telegraphy)	1500	-200	170	12	3.8	—	200
														Class-C Amp. (Telephony)	1250	-160	167	19	5.0	—	160
														Class-B Amp. (Audio) <sup>7</sup>	1500	-52	30/320	304 <sup>9</sup>	5.5 <sup>8</sup>	11000	340
211 311 835 <sup>1</sup>	100	10	3.25	1250	175	50	12	6.0	14.5	5.5	15	J.	4E	Class-C Amp. (Telegraphy)	1250	-225	150	18	7.0	—	130
														Class-C Amp. (Telephony)	1000	-260	150	35	14	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	-100	20/320	410 <sup>9</sup>	8.0 <sup>8</sup>	9000	260
														Class-C Amp. (Telegraphy)	1250	-175	150	—	—	—	130
242B 342B	100	10	3.25	1250	150	50	12.5	7.0	13.6	6.0	6	J.	4E	Class-C Amp. (Telegraphy)	1000	-160	150	50	—	—	100
														Class-C Amp. (Telephony)	1250	-175	150	—	—	—	130
														Class-B Amp. (Audio) <sup>7</sup>	1250	-80	25/150	—	25 <sup>8</sup>	7600	200
242C	100	10	3.25	1250	150	50	12.5	6.1	13.0	4.7	6	J.	4E	Class-C Amp. (Telegraphy)	1250	-175	150	—	—	—	100
														Class-C Amp. (Telephony)	1000	-160	150	50	—	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	-80	25/150	—	25 <sup>8</sup>	7200	200
														Class-C Amp. (Telegraphy)	1250	-175	125	—	—	—	100
261A 361A	100	10	3.25	1250	150	50	12	6.5	9.0	4.0	30	J.	4E	Class-C Amp. (Telegraphy)	1000	-160	150	50	—	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	-90	20/150	—	25 <sup>8</sup>	7200	200
														Class-C Amp. (Telephony)	1250	-175	125	—	—	—	100
276A 376A	100	10	3.0	1250	125	50	12	6.0	9.0	4.0	30	J.	4E	Class-C Amp. (Telegraphy)	1000	-160	125	50	—	—	85
														Class-C Amp. (Telephony)	1250	-90	20/125	—	25 <sup>8</sup>	9000	175
														Class-B Amp. (Audio) <sup>7</sup>	1250	-90	20/125	—	25 <sup>8</sup>	9000	175

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu\text{mfd.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
284B	100	10	3.25	1250	150	100	5.0	4.2	7.4	5.3	—	J.	T-3AB	Class-C Amp. (Telegraphy)	1250	-500	150	—	—	—	125
														Class-C Amp. (Telephony)	1000	-430	150	50	—	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	-245	15/130	—	10 <sup>8</sup>	7200	200
295A	100	10	3.25	1250	175	50	25	6.5	14.5	5.5	—	J.	4E	Class-C Amp. (Telegraphy)	1250	-125	150	—	—	—	125
														Class-C Amp. (Telephony)	1000	-125	150	50	—	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	-40	12/160	—	20 <sup>8</sup>	9000	250
838 938	100	10	3.25	1250	175	70	—	6.5	8.0	5.0	30	J.	4E	Class-C Amp. (Telegraphy)	1250	-90	150	30	6.0	—	130
														Class-C Amp. (Telephony)	1000	-135	150	60	16	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	0	148/320	200 <sup>9</sup>	7.5 <sup>8</sup>	9000	260
852	100	10	3.25	3000	150	40	12	1.9	2.6	1.0	30	M.	2D	Class-C Amp. (Telegraphy)	3000	-600	85	15	12	—	165
														Class-C Amp. (Telephony)	2000	-500	67	30	23	—	75
														Class-B Amp. (Audio) <sup>7</sup>	3000	-250	14/160	780 <sup>9</sup>	3.5 <sup>8</sup>	10250	320
8003	100	10	3.25	1500	250	50	12	5.8	11.7	3.4	30	J.	T-3AB	Class-C Amp.-Oscillator	1350	-180	245	35	11	—	250
														Class-C Amp. (Telephony)	1100	-260	200	40	15	—	167
														Class-B Amp. (Audio) <sup>7</sup>	1350	-100	40/490	480 <sup>9</sup>	10.5 <sup>8</sup>	6000	460
3X100A11 2C39	100	6.3	1.1	1000	60	40	100	6.5	1.95	0.03	500	N.	—	"Grid Isolation" Circuit	600	-35	60	40	5.0	—	20
311-CH	125	10	3.25	1750	200	50	12	5.5	8.0	4.5	30	J.	Fig. 57	Class-C Amp. (Telegraphy)	1750	-200	200	20	4.5	—	260
														Class-C Amp. (Telephony)	1250	-200	166	8	3.5	—	148
														Class-B (Audio) <sup>7</sup>	1500	-110	400 <sup>8</sup>	—	—	8200	400
3C22	125	6.3	2.0	1000	150	70	40	4.9	2.4	0.05	500	O.	Fig. 30	Class-C Amp.-Oscillator	1000	-200	150	70	—	—	65
4C36	125	5	7.5	4000	—	—	29	3.2	3.0	0.4	60	J.	Fig. 56	Class-C Amp.-Oscillator	—	—	—	—	18	—	480
F-123-A DR-123C	125	10	4.0	2000	300	75	14.5	6.5	8.5	3.3	—	J.	Fig. 26	Class-C Amp. (Telegraphy)	1500	-250	250	30	11	—	300
														Class-C Amp. (Telephony)	1500	-290	160	25	10	—	200
														Class-B Amp. (Audio) <sup>7</sup>	2000	-130	30/175	217 <sup>9</sup>	3.4 <sup>8</sup>	13800	522
RK57/805	125	10	3.25	1500	210	70	—	6.5	8.0	5.0	30	J.	T-3AB	Class-C Amp. (Telegraphy)	1500	-105	200	40	8.5	—	215
														Class-C Amp. (Telephony)	1250	-160	160	60	16	—	140
														Class-B Amp. (Audio) <sup>7</sup>	1500	-16	84/400	280 <sup>9</sup>	7.0 <sup>8</sup>	8200	370
T125	125	10	4.5	2500	250	60	25	6.3	6.0	1.3	60	J.	2N	Class-C Amp. (Telegraphy)	2500	-200	240	31	11	—	475
HF130	125	10	3.25	1250	210	—	12.5	—	9.0	—	20	J.	—	Class-C Amp. (Telephony)	2000	-215	200	28	10	—	320
HF150	125	10	3.25	1500	210	—	12.5	—	7.2	—	30	J.	—	Class-C Amp.-Oscillator	1250	-210	—	—	—	—	170
HF175	125	10	4.0	2000	250	—	18	—	6.3	—	25	J.	—	Class-C Amp.-Oscillator	1500	—	210	—	—	—	200
GL146	125	10	3.25	1500	200	60	75	7.2	9.2	3.9	15	J.	T-4BG	Class-C Amp.-Oscillator	2000	—	250	—	—	—	300
														Class-C Amp. (Telephony)	1250	-150	180	30	—	—	150
														Class-B Amp. (Audio) <sup>7</sup>	1500	-160	160	60	16	—	140
GL152	125	10	3.25	1500	200	60	25	7.0	8.8	4.0	15	J.	T-4BG	Class-C Amp. (Telephony)	1000	-200	160	40	—	—	100
														Class-B Amp. (Audio) <sup>7</sup>	1250	0	34/320	—	—	8400	250
														Class-C Amp.-Oscillator	1250	-150	180	30	—	—	150
805	125	10	3.25	1500	210	70	40/60	8.5	6.5	10.5	30	J.	T-3AB	Class-C Amp. (Telephony)	1000	-200	160	40	—	—	100
														Class-C Amp. (Telephony)	1250	-160	160	60	16	—	140
														Class-B Amp. (Audio) <sup>7</sup>	1500	-16	84/400	280 <sup>9</sup>	7.0 <sup>8</sup>	8200	370

r11g

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances (μmfd.)			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts				
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.															
3X150A3 3C37	150	6.3	2.5	1000	—	—	23	4.2	3.5	0.6	500	N.	—	—	—	—	—	—	—	—	—				
150T <sup>1</sup>	150	5.0	10	3000	200	50	13	3.0	3.5	0.5	—	J.	2N	Class-C Amp. (Telegraphy)	3000	-600	200	35	—	—	—	450			
3-150A3 152TH	150	5/10	12.51/ 6.25	3000	450	85	20	5.7	4.5	0.8	40	J.	4BC	Class-C Amp. (Telegraphy)	3000	-300	250	70	27	—	—	—	600		
3-150A2 152TL						75	12	4.5	4.4	0.7				4BC	Class-B Amp. (Audio) <sup>7</sup>	3000	-150	67/335	430 <sup>9</sup>	3.0 <sup>8</sup>	20300	700			
														3000	-400	250	40	20	—	—	—	600			
														3000	-260	65/335	675 <sup>9</sup>	3.0 <sup>8</sup>	20400	—	—	700			
TW150	150	10	4.1	3000	200	60	35	3.9	2.0	0.8	—	J.	2N	Class-C Amp.-Oscillator	3000	-170	200	45	17	—	—	—	470		
														3000	-260	165	40	17	—	—	—	400			
HK252-L	150	5/10	13/6.5	3000	500	75	10	7.0	5.0	0.4	125	N.	4BC	Class-C Amp.-Oscillator	3000	-400	250	30	15	—	—	—	610		
														2500	-350	250	35	16	—	—	—	500			
HF200 HV1B	150	10-11	3.4	2500	200	50	18	5.2	5.8	1.2	20	J.	2N	Class-C Amp. (Telegraphy)	2500	-300	200	18	8.0	—	—	—	380		
														2000	-350	160	20	9.0	—	—	—	250			
														2500	-130	60/360	460 <sup>9</sup>	8.0 <sup>8</sup>	16000	—	—	600			
HD203A	150	10	4.0	2000	250	60	25	—	12	—	15	J.	T-3AB	Class-C Amplifier	—	—	—	—	—	—	—	—	375		
HF250	150	10.5	4.0	2500	200	—	18	—	5.8	—	20	J.	2N	Class-C Amp.-Oscillator	2500	—	200	—	—	—	—	—	—	375	
														4000	-690	245	50	48	—	—	—	—	830		
6X0 HK354 HK354C	150	5.0	10	4000	300	50	14	4.5	3.0	1.1	30	J.	2N	Class-C Amp. (Telephony)	3000	-550	210	50	35	—	—	—	—	525	
														Grid-Modulated Amp.	3000	-400	78	3.0	12	—	—	—	—	—	85
														3000	-205	65/313	630 <sup>9</sup>	2.0 <sup>8</sup>	22000	—	—	—	665		
														3500	-490	240	50	38	—	—	—	—	690		
														3500	-425	210	55	36	—	—	—	—	525		
														3500	-448	240	60	45	—	—	—	—	690		
														3000	-437	210	60	45	—	—	—	—	525		
														3500	-368	250	75	50	—	—	—	—	720		
														3000	-312	210	75	45	—	—	—	—	525		
														2500	-300	200	18	8.0	—	—	—	—	380		
UE-468	150	10	4.05	2500	200	60	18	0.8	7.0	1.25	30	J.	Fig. 57	Class-C Amp. (Telephony)	2000	-350	160	20	9.0	—	—	—	—	250	
														2500	-130	320 <sup>8</sup>	410 <sup>9</sup>	2.5	16000	—	—	—	—	500	
														2500	-180	300	60	19	—	—	—	—	—	575	
810 1627 <sup>1</sup>	175	10	4.5	2500	300	75	36	0.7	4.0	12	30	J.	2N	Class-C Amp. (Telephony)	2000	-350	250	70	35	—	—	—	—	—	380
		5.0	9.0											Grid-Modulated Amp.	2250	-140	100	2.0	4.0	—	—	—	—	75	
														2250	-60	70/450	380 <sup>9</sup>	13 <sup>8</sup>	11600	—	—	—	—	725	
														2500	-240	300	40	18	—	—	—	—	—	575	
														2000	-370	250	37	20	—	—	—	—	—	380	
														2250	-265	100	0	2.5	—	—	—	—	—	75	
														2250	-130	65/450	550 <sup>9</sup>	7.9 <sup>8</sup>	12000	—	—	—	—	725	
GL-5C24	150	10	5.2	1750	107	—	0	5.6	8.8	3.3	—	N.	Fig. 26	Class-A Amp. (Audio)	1500	-155	107	—	—	—	—	—	—	8200 <sup>5</sup>	55
														1750	-200	320 <sup>8</sup>	390 <sup>9</sup>	—	—	—	—	—	—	8000	240
RK63 RK63A	200	5.0	10	3000	250	60	37	2.7	3.3	1.1	—	J.	2N	Class-C Amp. (Telegraphy)	3000	-200	233	45	17	—	—	—	—	—	525
		6.3	14											Class-C Amp. (Telephony)	2500	-200	205	50	19	—	—	—	—	405	
														3000	-250	100	7.0	12.5	—	—	—	—	—	100	



TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu$ fd.)			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
T200	200	10	5.75	2500	350	80	16	9.5	7.9	1.6	30	J.	2N	Class-C Amp. (Telegraphy)	2500	-280	350	54	25	—	685
F-127-A	200	10	4.0	3000	325	70	38	13	4	13	—	J.	Fig. 26	Class-C Amp. (Telephony)	2000	-260	300	54	23	—	460
														Class-C Amp. (Telegraphy)	3000	-250	250	47	18	—	600
														Class-C Amp. (Telephony)	2500	-300	200	58	25.2	—	420
822 822S	200	10	4.0	2500	300	60	30	8.5	13.5	2.1	20 30	J.	T-3AB 2N	Class-B Amp. (Audio) <sup>7</sup>	2800	-75	20/400	175 <sup>9</sup>	6.65 <sup>8</sup>	16600	820
														Class-C Amp. (Telegraphy)	2500	-190	300	51	17	—	600
														Class-C Amp. (Telephony)	2000	-75	250	43	13.7	—	405
4C32	200	10	4.5	3000	300	60	30	5.5	5.8	1.1	60	J.	2N	Class-B Amp. (Audio) <sup>7</sup>	3000	-80	450 <sup>8</sup>	362 <sup>9</sup>	8.0 <sup>8</sup>	16000	1000
														Class-C Amp.-Oscillator	2000	-165	275	20	10	—	400
														Class-C Amp. (Telephony)	2000	-200	250	20	15	—	375
GL-592	200	10	5.0	3500	250	50	24	3.6	3.3	0.41	110	N.	Fig. 52	Class-C Amp.-Oscillator	2600	-240	250	45	18	—	425
														Class-C Amp. (Telephony)	2000	-500	250	50	—	—	
														Class-C Amp. (Telegraphy)	3000	-400	250	28	16	—	600
4C34 HF300	200	11-12	4.0	3000	275	60	23	6.0	6.5	1.4	60 20	J.	2N	Class-C Amp. (Telephony)	2000	-300	250	36	17	—	385
														Class-B Amp. (Audio) <sup>7</sup>	3000	-115	60/360	450 <sup>9</sup>	13 <sup>8</sup>	20000	780
														Class-C Amp. (Telegraphy)	2500	-240	300	30	10	—	575
T814 HV12	200	10	4.0	2500	200	60	12	8.5	12.8	1.7	30	J	T-3AB	Class-C Amp. (Telephony)	2000	-370	300	40	20	—	485
														Class-B Amp. (Audio) <sup>7</sup>	2000	-160	50/275	350 <sup>9</sup>	7.0 <sup>8</sup>	14400	400
														Class-C Amp. (Telegraphy)	2500	-175	300	50	15	—	585
T822 HV27	200	10	4.0	2500	300	60	27	8.5	13.5	2.1	30	J.	T-3AB	Class-C Amp. (Telephony)	2000	-195	250	45	15	—	400
														Class-C Amp. (Telegraphy)	3000	-400	250	28	20	—	600
														Class-C Amp. (Telephony)	2000	-300	250	36	17	—	385
T-300	200	11	6.0	3000	300	—	23	6.0	7.0	1.4	—	—	—	Class-B (Audio) <sup>7</sup>	2500	-100	60/450	—	7 $\frac{1}{2}$ <sup>8</sup>	—	750
														Class-C Amp. (Telegraphy)	3300	-600	300	40	34	—	780
														Class-C Amp. (Telephony)	3300	-670	195	27	24	—	460
806	225	5.0	10	3300	300	50	12.6	6.1	4.2	1.1	30	J.	2N	Class-B Amp. (Audio) <sup>7</sup>	3300	-240	80/475	930 <sup>9</sup>	35 <sup>8</sup>	16000	1120
														Class-C Amp. (Telegraphy)	2000	-120	350	100	34	—	500
														Class-C Amp. (Telephony)	3000	-210	330	75	42	—	750
3-250A4 250TH	250	5.0	10.5	4000	350	100	37	5.0	2.9	0.7	40	J.	2N	Grid-Modulated Amp.	3000	-160	125	4.5	20	—	125
														Class-B Amp. (Audio) <sup>7</sup>	3000	-65	100/560	460 <sup>9</sup>	24 <sup>8</sup>	12250	1150
														Class-C Amp. (Telegraphy)	3000	-350	335	45	29	—	750
3-250A2 250TL	250	5.0	10.5	4000	350	50	14	3.7	3.1	0.7	40	J.	2N	Class-C Amp. (Telephony)	3000	-350	335	45	29	—	750
														Grid-Modulated Amp.	3000	-450	125	2.0	15	—	125
														Class-B Amp. (Audio) <sup>7</sup>	3000	-175	100/500	840 <sup>9</sup>	17 <sup>8</sup>	13000	1000
GL159	250	10	9.6	2000	400	100	20	11	17.6	5.0	15	J.	T-4BG	Class-C Amp.-Oscillator	2000	-200	400	17	6.0	—	620
														Class-C Amp. (Telephony)	1500	-240	400	23	9.0	—	450
														Class-B Amp. (Audio) <sup>7</sup>	2000	-100	30/660	400 <sup>9</sup>	4.0 <sup>8</sup>	6880	900
GL169	250	10	9.6	2000	400	100	25	11.5	19	4.7	15	J.	T-4BG	Class-C Amp.-Oscillator	2000	-100	400	42	10	—	620
														Class-C Amp. (Telephony)	1500	-100	400	45	10	—	450
														Class-B Amp. (Audio) <sup>7</sup>	2000	-18	30/650	220 <sup>9</sup>	6.0 <sup>8</sup>	7000	900

108

TABLE XV—TRIODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ( $\mu\text{mfd.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.					Grid to Fil.	Grid to Plate	Plate to Fil.											
204A 304A	250	11	3.05	2500	275	80	23	12.5	15	2.3	3	N.	T-1A	Class-C Amp. (Telegraphy)	2500	-200	250	30	15	—	450
														Class-C Amp. (Telephony)	2000	-250	250	35	20	—	350
														Class-B Amp. (Audio) <sup>7</sup>	3000	-100	80/372	500 <sup>9</sup>	18 <sup>8</sup>	20000	700
308B	250	14	4.0	2250	325	75	8.0	13.6	17.4	9.3	1.5	N.	T-2A	Class-C Amp. (Telegraphy)	1750	-345	300	—	—	—	350
														Class-B Amp. (Audio) <sup>7</sup>	1500	-300	300	—	—	—	300
														Class-C Amp. (Telephony)	3500	-275	270	60	28	—	760
HK454H	250	5.0	11	5000	375	85	30	4.6	3.4	1.4	100	J.	2N	Class-C Amp. (Telephony)	3500	-450	270	45	30	—	760
HK454-L	250	5.0	11	5000	375	60	12	4.6	3.4	1.4	100	J.	2N	Class-C Amp. (Telephony)	3500	-450	270	45	30	—	760
212E 241B 312E	275	14	4.0	3000	350	75	16	14.9	18.8	8.6	1.5	N.	T-2A T-2AA	Class-C Amp. (Telegraphy)	3500	-275	270	60	28	—	760
														Class-C Amp. (Telephony)	3500	-450	270	45	30	—	760
														Class-B Amp. (Audio) <sup>7</sup>	2000	-105	40/300	—	50 <sup>8</sup>	8000	650
300T <sup>1</sup>	300	8.0	11.5	3500	350	75	16	4.0	4.0	0.6	—	J.	2N	Class-C Amp. (Telegraphy)	2000	-225	300	—	—	—	400
HK304-L	300	5/10	26/13	3000	1000	150	10	12	9.0	0.8	—	N.	4BC	Class-C Amp. (Telephony)	1500	-200	300	75	—	—	300
527	300	5.5	135.0	—	—	—	38	19.0	12.0	1.4	200	N.	T-4B	Oscillator at 200 Mc.	Approximately 250 watts output						
HK654	300	7.5	15	4000	600	100	22	6.2	5.5	1.5	20	J.	2N	Class-C Amp. (Telegraphy)	2000	-380	500	75	57	—	720
														Class-C Amp. (Telephony)	2000	-365	450	110	70	—	655
														Grid-Modulated Amp.	3500	-210	150	15	15	—	210
3-300A3 304TH	300	5/10	25/12.5	3000	900	170	20	13.5	10.2	0.7	40	N.	4BC	Class-C Amplifier	1500	-125	667	115	25	—	700
														Class-B Amp. (Audio) <sup>7</sup>	3000	-150	134/667	420 <sup>9</sup>	6.0 <sup>8</sup>	10200	1400
														Class-C Amplifier	1500	-250	665	90	33	—	700
3-300A2 304TL	300	5/10	25/12.5	3000	900	150	12	8.5	9.1	0.6	40	N.	4BC	Class-B Amp. (Audio) <sup>7</sup>	3000	-260	130/667	650 <sup>9</sup>	6.0 <sup>8</sup>	10200	1400
														Class-C Amp. (Telegraphy)	2000	-200	475	65	25	—	740
833A	300	10	10	3000	500	100	35	12.3	6.3	8.5	30	N.	T-1AB	Class-C Amp. (Telephony)	2500	-300	335	75	30	—	635
270A	350	10	4.0	3000	375	75	16	18	21	2.0	7.5	N.	T-1A	Class-C Amp. (Telegraphy)	3000	-375	350	—	—	—	700
														Class-C Amp. (Telephony)	2250	-300	300	80	—	—	450
849 <sup>1</sup>	400	11	5.0	2500	350	125	19	17	33.5	3.0	3	N.	T-1A	Class-C Amp. (Telephony)	2500	-250	300	20	8.0	—	560
														Class-C Amp. (Telegraphy)	2000	-300	300	30	14	—	425
831 <sup>1</sup>	400	11	10	3500	350	75	14.5	3.8	4.0	1.4	—	N.	T-1AA	Class-C Amp. (Telephony)	3500	-400	275	40	30	—	590
														Class-C Amp. (Telephony)	3000	-500	200	60	50	—	360

\* Cathode resistor in ohms.

<sup>1</sup> Discontinued.

<sup>2</sup> Twin triode. Values, except interelement capacities, are for both sections in push-pull.

<sup>3</sup> Output at 112 Mc.

<sup>4</sup> Grid-leak resistor in ohms.

<sup>5</sup> Max. peak volts, plate pulsed.

<sup>6</sup> Per section.

<sup>7</sup> Values are for two tubes in push-pull.

<sup>8</sup> Max. signal value.

<sup>9</sup> Peak a.f. grid-to-grid volts.

<sup>10</sup> For single tube.

TABLE XVI—TETRODE AND PENTODE TRANSMITTING TUBES

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Screen Voltage	Max. Screen Dissipation Watts	Interelectrode Capacitances (μmfd.)			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Screen Resistor Ohms	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.				Grid to Fil.	Grid to Plate	Plate to Fil.															
3A4	2.0	1.4 2.8	0.2 0.1	150	135	0.9	4.8	0.2	4.2	10	B.	7BB	Class-C Amp.-Oscillator	150	135	0	-26	18.3	6.5	0.13	2300	—	—	1.2
HY63 <sup>1</sup>	3.0	2.5 1.25	0.1125 0.225	200	100	0.6	8.0	0.1	8.0	60	O.	T-8DB	Class-C Amp.-Osc.	200	100	—	-22.5	20	4.0	2.0	—	0.1	—	3.0
													Class-C Amp. (Telephony)	180	100	—	-35	15	3.0	2.0	—	0.2	—	2.0
6AK6	3.5	6.3	0.15	375	250	1.0	3.6	0.12	4.2	54	B.	7BK	Class-C Amp.-Oscillator	375	250	—	-100	15	4.0	3.0	—	—	—	4.0
6AQ5	8.0	6.3	0.45	350	250	2.0	7.6	0.35	6.0	54	B.	7BZ	Class-C Amp.-Oscillator	350	250	—	-100	47	7.0	5.0	—	—	—	11
6V6GT	8.0	6.3	0.45	350	250	2.0	9.5	0.7	7.5	10	O.	7AC	Class-C Amp.-Oscillator	350	250	—	-100	47	7.0	5.0	—	—	—	11
6AG7	9.0	6.3	0.65	375	250	1.5	13	0.06	7.5	10	O.	8Y	Class-C Amp.-Oscillator	375	250	—	-75	30	9.0	5.0	—	—	—	7.5
RK64 <sup>1</sup>	6.0	6.3	0.5	400	100	3.0	10	0.4	9.0	60	M.	T-5BB	Class-C Amp. (Telegraphy)	400	100	30	-30	35	10	3.0	—	0.18	—	10
													Class-C Amp. (Telephony)	300	—	30	-30	26	8.0	4.0	30000	0.2	—	6.0
1610	6.0	2.5	1.75	400	200	2.0	8.6	1.2	13	20	M.	T-5CA	Class-C Amp.-Oscillator	400	150	—	-50	22.5	7.0	1.5	—	—	—	5.0
RK56	8.0	6.3	0.55	300	300	4.5	10	0.2	9.0	60	M.	T-5BB	Class-C Amp. (Telegraphy)	400	300	—	-40	62	12	1.6	—	0.1	—	12.5
													Class-C Amp. (Telephony)	250	200	—	-40	50	10	1.6	2800	0.28	—	8.5
RK23 <sup>1</sup> RK25 RK25B <sup>1</sup>	10	2.5 6.3	2.0 0.9	500	250	8	10	0.2	10	—	M.	T-7C	Class-C Amp. (Telegraphy)	500	200	45	-90	55	38	4.0	—	0.5	—	22
													Class-C Amp. (Telephony)	400	150	0	-90	43	30	6.0	8300	0.8	—	13.5
1613	10	6.3	0.7	350	275	2.5	8.5	0.5	11.5	45	O.	7S	Class-C Amp. (Telegraphy)	350	200	—	-35	50	10	3.5	20000	0.22	—	9
													Class-C Amp. (Telephony)	275	200	—	-35	42	10	2.8	10000	0.16	—	6.0
2E30	10	6.0	0.7	250	250	2.5	10	0.5	4.5	160	B.	7CQ	Class-C Amp.-Oscillator	250	200	—	-50	50	10	2.5	—	0.2	—	7.5
													Class-AB <sub>2</sub> Amp. (Audio) <sup>6</sup>	250	250	—	-30	40/120	4/20	2.3 <sup>7</sup>	87 <sup>8</sup>	0.2	3800	17
6F6 6F6G	12.5	6.3	0.7	400	275	3.0	6.5	0.2	13	10	O.	7AC	Class-C Amp.-Oscillator	400	275	—	-100	50	11	5.0	—	—	—	14
							8.0	0.5	6.5				Class-C Amp. (Telephony)	275	200	—	-35	42	10	2.8	—	0.16	—	6.0
837 RK44 <sup>1</sup>	12	12.6	0.7	500	300	8	16	0.2	10	20	M.	T-7C	Class-C Amp. (Telegraphy)	500	200	40	-70	80	15	4.0	20000	0.4	—	28
													Class-C Amp. (Telephony)	400	140	40	-40	45	20	5.0	13000	0.3	—	11
2E24	9.0 13.5	6.3 <sup>5</sup>	0.65	500	200	2.3	8.5	0.11	6.5	125	O.	7CL	Suppressor-Modulated Amp.	500	—	-65	-20	30	23	3.5	14000	0.1	—	5.0
				600	200	2.5							Class-C Amp. (Telephony)	400	180	—	-45	50	8.0	2.5	27500	0.15	—	13.5
2E26	13.5 9.0	6.3	0.8	500	200	2.3	13	0.2	7.0	125	O.	7CK	Class-C Amp. (Telephony)	500	180	—	-50	54	8.0	2.5	40000	0.16	—	18.0
				600	200	2.5							Class-C Amp. (Telegraphy)	400	200	—	-45	75	10.0	3.0	20000	0.19	—	20
802	13	6.3	0.9	600	250	6.0	12	0.15	8.5	30	M.	T-7C	Class-C Amp. (Telephony)	600	185	—	-50	66	10	3.0	40500	0.21	—	27
													Class-AB <sub>2</sub> Amp. (Audio) <sup>6</sup>	500	125	—	-15	22/150	32 <sup>7</sup>	—	60 <sup>8</sup>	0.36 <sup>7</sup>	8000	54
HY6V6-GTX	13	6.3	0.5	350	225	2.5	9.5	0.7	9.5	60	O.	7AC	Class-C Amp. (Telephony)	600	250	40	-120	55	16	2.4	22000	0.30	—	23
													Class-C Amp.-Oscillator	300	200	—	-45	60	7.5	2.5	—	0.3	—	12
HY60	15	6.3	0.5	425	225	2.5	10	0.2	8.5	60	M.	T-5BB	Class-C Amp. (Telephony)	500	245	40	-40	40	15	1.5	16300	0.10	—	12
													Class-C Amp. (Telephony)	425	200	—	-62.5	60	8.5	3.0	—	0.3	—	18
HY65 <sup>1</sup>	15	6.3	0.85	450	250	4.0	9.1	0.18	7.2	60	O.	T-8DB	Class-C Amp. (Telephony)	600	250	-45	-100	30	24	5.0	14500	0.6	—	6.3
													Class-C Amp.-Oscillator	300	200	—	-45	60	7.5	2.5	—	0.3	—	12
HY65 <sup>1</sup>	15	6.3	0.85	450	250	4.0	9.1	0.18	7.2	60	O.	T-8DB	Class-C Amp. (Telephony)	425	200	—	-45	60	7.0	2.5	—	0.2	—	14
													Class-C Amp.-Oscillator	450	250	—	-45	75	15	3.0	—	0.5	—	24
													Class-C Amp. (Telephony)	350	200	—	-45	63	12	3.0	—	0.5	—	16

TABLE XVI—TETRODE AND PENTODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Screen Voltage	Max. Screen Dissipation Watts	Interelectrode Capacitances (μmfd.)			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Screen Resistor Ohms	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.				Grid to Fil.	Grid to Plate	Plate to Fil.															
2E25	15	6.0	0.8	450	250	4.0	8.5	0.15	6.7	125	O.	5BJ	Class-C Amp.—Oscillator	450	250	—	-45	75	15	3.0	—	0.4	—	24
													Class-C Amp. (Telephony)	400	200	—	-45	60	12	3.0	—	0.4	—	16
													Class-AB <sub>1</sub> Amp. (Audio) <sup>6</sup>	450	250	—	-30	44/150	10/40	3.0	142 <sup>8</sup>	0.9 <sup>7</sup>	6000	40
306A	15	2.75	2.0	300	300	6.0	13	0.35	13	—	M.	1-5CB	Class-C Amp. (Telephony)	300	180	—	-50	36	15	3.0	3000	—	—	7.0
307A RK-75	15	5.5	1.0	500	250	6.0	15	0.55	12	—	M.	T-5C	Class-C Amp. (Telephony)	500	250	0	-35	60	13	1.4	23000	—	—	20
													Suppressor-Modulated Amp.	500	200	-50	-35	40	20	1.5	14000	—	—	6.0
832 <sup>3</sup>	15	6.3	1.6	500	250	5.0	7.5	0.05	3.8	200	N.	7BP	Class-C Amp. (Telephony)	500	200	—	-65	72	14	2.6	21000	0.18	—	26
		12.6	0.8										425	200	—	-60	52	16	2.4	14000	0.15	—	16	
832A <sup>3</sup>	15	6.3	1.6	750	250	5.0	7.5	0.05	3.8	200	N.	7BP	Class-C Amp. (Telephony)	750	200	—	-65	48	15	2.8	36500	0.19	—	26
		12.6	0.8										600	200	—	-65	35	16	2.6	25000	0.16	—	17	
		Class-C Amp. (Telegraph)	500										175	—	-125	25	—	5.0	—	—	—	9.0		
844 <sup>1</sup>	15	2.5	2.5	500	180	3.0	9.5	0.15	7.5	—	M.	T-5BB	Class-C Amp. (Telegraph)	500	150	—	-100	20	—	—	—	—	—	4.0
													Class-C Amp. (Telephony)	750	125	—	-80	40	—	5.5	—	1.0	—	15
865	15	7.5	2.0	750	175	3.0	8.5	0.1	8.0	15	M.	T-4C	Class-C Amp. (Telephony)	500	125	—	-120	40	—	9.0	—	2.5	—	10
													Class-C Amp. (Telegraph)	400	300	—	-55	75	10.5	5.0	9500	0.36	—	17.5
1619	15	2.5	2.0	400	300	3.5	10.5	0.35	12.5	45	O.	7AC	Class-C Amp. (Telephony)	325	285	—	-50	62	7.5	2.8	5000	0.18	—	13
													Class-AB <sub>1</sub> Amp. (Audio) <sup>6</sup>	400	300	0	-16.5	75/150	6.5/11.5	—	77 <sup>8</sup>	0.4 <sup>7</sup>	6000	35
													Class-C Amp. (Telegraph)	600	250	—	-60	75	15	5.0	—	0.5	—	32
5516	15	6.0	0.7	600	250	5.0	8.5	0.12	6.5	80	O.	7CL	Class-C Amp. (Telephony)	475	250	—	-90	63	10	4.0	22500	0.5	—	22
													Class-AB <sub>1</sub> (Audio) <sup>6</sup>	600	250	—	-25	36/140	1/24	4 <sup>7</sup>	80 <sup>8</sup>	0.16	10500	67
													Class-C Amplifier	750	175	—	-90	60	—	—	—	—	—	25
254A	20	5.0	3.25	750	175	5.0	4.6	0.1	9.4	—	M.	1-4C	Class-C Amp.—Oscillator	400	300	—	-125	100	12	5.0	—	—	28	
6L6	21	6.3	0.9	400	300	3.5	10	0.4	12	10	O.	7AC	Class-C Amp. (Telephony)	325	250	—	-70	65	—	9.0	—	0.8	—	11
6L6G							11.5	0.9	9.5				Class-C Amp. (Telegraph)	500	250	—	-50	90	9.0	2.0	—	0.25	—	30
6L6GX	21	6.3	0.9	500	300	3.5	11	1.5	7.0	—	O.	7AC	Class-C Amp. (Telephony)	325	225	—	-45	90	9.0	3.0	—	0.25	—	20
													Class-C Amp.—Oscillator	500	250	—	-50	90	9.0	2.0	—	0.5	—	30
													Class-C Amp. (Telephony)	400	225	—	-45	90	9.0	3.0	16000	0.8	—	20
HY6L6- GTX	21	6.3	0.9	500	300	3.5	11	0.5	7.0	60	O.	7AC	Class-C Amp. (Telephony)	400	250	—	-50	90	8.0	3.0	—	0.2	—	25
													Class-C Amp. (Telephony)	350	200	—	-45	65	17	5.0	—	0.35	—	14
T21	21	6.3	0.9	400	300	3.5	13	0.7	12	30	M.	T-5B	Class-C Amp. (Telegraph)	400	250	—	-50	95	8.0	3.0	—	0.2	—	25
													Class-C Amp. (Telephony)	400	250	—	-45	60	15	5.0	6700	0.34	—	12
													Class-C Amp. (Telegraph)	400	250	—	-50	95	8.0	3.0	—	0.2	—	25
RK49	21	6.3	0.9	400	300	3.5	11.5	1.4	10.6	—	M.	1-6B	Class-C Amp. (Telephony)	450	250	—	-45	100	8	2.0	12500	0.15	—	81
													Class-C Amp. (Telegraph)	400	250	—	-50	95	8.0	3.0	—	0.2	—	25
													Class-C Amp. (Telephony)	300	200	—	-45	60	15	5.0	6700	0.34	—	12
1614	25	6.3	0.9	450	300	3.5	10	0.4	12.5	80	O.	7AC	Class-C Amp. (Telephony)	375	250	—	-50	90	2.0	2.0	10000	0.15	—	21.5
													Class-AB <sub>1</sub> Amp. (Audio) <sup>6</sup>	530	340	—	-36	60/160	20 <sup>7</sup>	—	72 <sup>8</sup>	—	7200	50
													Class-C Amp. (Telegraph)	600	250	—	-90	90	10	3.0	—	0.38	—	36
RK41 <sup>1</sup> RK39	25	2.5	2.4	600	300	3.5	13	0.2	10	30	M.	T-5BB	Class-C Amp. (Telephony)	475	250	—	-50	85	9.0	2.5	25000	0.2	—	26
		6.3	0.9										600	300	—	-50	85	9.0	4.0	30000	0.4	—	40	
		Class-C Amp. (Telegraph)	600										250	—	-50	100	9.0	3.5	25000	0.2	—	27		
HY61/ 807	25	6.3	0.9	600	300	3.5	11	0.2	7.0	60	M.	T-5BB	Class-AB <sub>1</sub> Amp. (Audio) <sup>6</sup>	600	300	—	-30	200 <sup>7</sup>	10 <sup>7</sup>	—	—	0.1 <sup>7</sup>	—	80
													Class-C Amp.—Oscillator	500	200	—	-45	150	17	2.5	—	0.13	—	56
													Class-C Amp. (Telephony)	400	175	—	-45	150	15	3.0	—	0.16	—	45
815 <sup>3</sup>	25	12.6	0.8	500	200	4.0	13.3	0.2	8.5	125	O.	T-8FA <sup>4</sup>	Class-C Amp. (Telephony)	400	175	—	-15	22/150	32 <sup>7</sup>	—	60 <sup>8</sup>	0.35 <sup>7</sup>	2000	54
		6.3	1.6										Class-AB <sub>1</sub> Amp. (Audio) <sup>3</sup>	500	125	—	-15	22/150	32 <sup>7</sup>	—	60 <sup>8</sup>	0.35 <sup>7</sup>	2000	54

409

TABLE XVI—TETRODE AND PENTODE TRANSMITTING TUBES—Continued

TABLE XVI—TETRODE AND PENTODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Screen Voltage	Max. Screen Dissipation Watts	Interelectrode Capacitances ( $\mu\text{mfd.}$ )			Max. Freq. Mc. Full Ratings	Base	Socket Connections	Typical Operation	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Screen Resistor Ohms	Approx. Grid Driving Power Watts	Class B P-to-P Load Res. Ohms	Approx. Output Power Watts
		Volts	Amp.				Grid to Fil.	Grid to Plate	Plate to Fil.															
254B	25	7.5	3.25	750	150	5.0	11.2	0.085	5.4	—	M.	T-4C	Class-C Amplifier	750	150	—	-135	75	—	—	—	—	—	30
1624	25	2.5	2.0	600	300	3.5	11	0.25	7.5	60	M.	T-5DC	Class-C Amo. (Telegraphy)	600	300	—	-60	90	10	5.0	30000	0.4	—	35
													Class-C Amo. (Telephony)	500	275	—	-40	75	9.3	3.3	25000	0.25	—	24
													Class-AB <sub>2</sub> Amp. (Audio) <sup>6</sup>	600	300	—	-25	42/180	5/15	1.36 <sup>5</sup>	—	1.2 <sup>7</sup>	7500	72
3DX3	25	6.3	3.0	1500	220	—	—	—	—	250	S.	Fig. 4C	Class-C Amp. (Telegraphy)	1000	200	—	-155	75	—	2.8	—	0.57	—	50
3E22 <sup>3</sup>	30	12.6	0.8	560	225	6.0	14	0.22	8.5	—	O.	8BY	Class-C Amo. (Telegraphy) <sup>3</sup>	600	200	—	-55	160	20	7.0	20000	0.45	—	72
													Class-C Amp. (Telephony) <sup>3</sup>	560	200	—	-50	160	20	6.5	18000	0.4	—	67
													Class-C Amp.-Oscillator	600	300	—	-60	90	11	5.0	—	0.5	—	40
RK66	30	6.3	1.5	600	300	3.5	12	0.25	10.5	60	M.	T-5C	Class-C Amp. (Telephony)	500	—	—	-50	75	8.0	3.2	25000	0.23	—	25
													Class-C Amp. (Telegraphy)	750	250	—	-45	100	6	3.5	85000	0.22	—	50
													Class-C Amo. (Telephony)	600	275	—	-90	100	6.5	4.0	50000	0.4	—	42.5
807 1625	30	6.3	0.9	750	300	3.5	11	0.2	7.0	60	M.	T-5BB 5AZ	Class-AB <sub>2</sub> Amp. (Audio) <sup>6</sup>	750	300	—	-32	50/240	5/10	92 <sup>8</sup>	—	0.2 <sup>7</sup>	6950	120
													Class-C Amp.-Oscillator	500	250	22.5	-60	100	16	6.0	15000	0.55	—	34
													Class-C Amp.-Oscillator	750	250	22.5	-60	100	16	6.0	30000	0.55	—	53
2E22	30	6.3	1.5	750	250	10	13	0.2	8.0	—	M.	5J	Suppressor-Modulated Amp.	750	250	-90	-65	55	29	6.5	17000	0.6	—	16.5
													Class-C Amp. (Telegraphy)	1500	375	—	-300	110	22	15	—	4.5	—	130
													Class-C Amp. (Telephony)	1000	300	—	-200	85	14	10	—	2.0	—	60
3D23 TB-35	35	6.3	3.0	—	—	—	6.5	0.2	1.8	250	M.	Fig. 54	Class-C Amp. (Telegraphy)	1250	300	45	-100	92	35	11.5	—	1.6	—	84
													Class-C Amp. (Telephony)	1000	300	0	-100	75	30	10	23000	1.3	—	52
													Suppressor-Modulated Amp.	1250	300	-45	-100	48	44	11.5	—	1.5	—	21
RK20 <sup>1</sup> RK20A RK46 <sup>1</sup>	40	7.5	3.0	1250	300	15	14	0.01	12	—	M.	T-5C	Grid-Modulated Amp.	1250	300	45	-142	40	7.0	1.8	—	1.5	—	20
													Class-C Amp.-Oscillator	600	250	—	-60	100	12.5	4.0	30000	0.25	—	42
													Class-C Amp. (Telephony)	600	250	—	-60	100	12.5	5.0	30000	0.35	—	42
HY69	40	6.3	1.5	600	300	5.0	15.4	0.23	6.5	60	M.	T-5D	Modulated Doubler	600	200	—	-300	90	11.5	6.0	35000	2.8	—	27
													Class-AB <sub>2</sub> Amp. (Audio) <sup>6</sup>	600	300	—	-35	200 <sup>7</sup>	18 <sup>7</sup>	5.0 <sup>7</sup>	—	0.3 <sup>7</sup>	—	80
													Class-C Amp. (Telegraphy)	500	200	—	-45	240	32	12	9300	0.7	—	83
829 <sup>1,3</sup>	40	6.3	2.25	500	225	40	14.5	0.1	7.0	200	N.	7BP	Class-C Amp. (Telephony)	425	200	—	-60	212	35	11	6400	0.8	—	63
													Grid-Modulated Amp.	500	200	—	-38	120	10	2.0	—	0.5	—	23
													Class-C Amp.-Oscillator	750	200	—	-55	160	30	12	18300	0.8	—	87
829A <sup>1,3</sup>	40	6.3	2.25	750	240	7.0	14.4	0.1	7.0	200	N.	7BP	Class-C Amp. (Telephony)	600	200	—	-70	150	30	12	13300	0.9	—	70
													Grid-Modulated Amp.	750	200	—	-55	80	5.0	0	—	0.7	—	24
													Class-C Amp. (Grid Mod.)	500	200	—	-38	120	10	2	—	0.5	—	23
829B <sup>3</sup> 3E29 <sup>3</sup>	30	12.6	1.125	600	225	6	14.5	0.12	7.0	200	N.	7BP	Class-C Amp. (Telephony)	425	200	—	-60	212	35	11.0	6400	0.8	—	63
													Class-C Amp. (Telegraphy)	500	200	—	-45	240	32	12.0	9300	0.7	—	83
													Class-C Amp.-Oscillator	750	300	—	-70	120	15	4	—	0.25	—	63
HY1269	40	6.3	3.5	750	300	5.0	16.0	0.25	7.5	6	M.	T-5DB	Class-C Amp. (Telephony)	600	250	—	-70	100	12.5	5	35000	0.5	—	42
													Grid-Modulated Amp.	750	300	—	—	80	—	—	—	—	—	20
													Class-AB <sub>2</sub> Amp. (Audio) <sup>6</sup>	600	300	—	-35	200 <sup>7</sup>	—	—	—	0.3	—	80
3D24	45	6.3	3.0	2000	400	10	6.5	0.2	2.4	125	L.	T-9J	Class-C Amp.-Oscillator	2000	375	—	-300	90	20	10	—	4.0	—	140
													Class-C Amp. (Telegraphy)	1500	375	—	-300	90	22	10	—	4.0	—	105
715-B	50	25/28	—	—	—	—	—	—	—	—	—	—	Class-C Amp. (Telegraphy)	1500	300	—	—	125	—	—	—	—	—	

TABLE XVII—KLYSTRONS

Type	Freq. Range-Mc.	Cathode		Base Con- nec- tions	Typical Operation	Beam Volts	Beam Ma. (Max.)	Beam Watts (Max.)	Control- Electrode Volts	Reflector Volts	Cathode Ma.	R.F. Driving Power Watts <sup>4</sup>	Output Watts
		Volts	Amp.										
2K25/ 723A-B	8702-9548	6.3	0.44	Fig. 60	Reflex Oscillator	300	32	—	—	-130/-185	25	—	0.033
2K-28 <sup>5</sup>	1200-3750	6.3	0.65	Fig. 61	Reflex Oscillator	300 <sup>7</sup>	45	—	300	-155/-290	30	—	0.140
2K33	23500-24500	6.3	0.65	Fig. 62	Reflex Oscillator	1800 <sup>7</sup>	—	—	-20/-100	-80/-220	6	—	0.04
2K34	2730-3330	6.3	1.6	Fig. 58	Oscillator-Buffer *	1900	150	450	-45	—	75	—	10-14
2K35	2730-3330	6.3	1.6	Fig. 58	Cascade Amplifier *	1500	150	450	0	—	75	0.005	5
2K41	2650-3310	6.3	1.3	Fig. 59	Reflex Oscillator <sup>8</sup>	1000	60	75	+24	-510	60	—	0.75
2K42 <sup>3</sup>	3300-4200	6.3	1.3	Fig. 59	Reflex Oscillator *	1000	60	75	0	-650	45	—	0.75
2K43 <sup>3</sup>	4200-5700	6.3	1.3	Fig. 59	Reflex Oscillator *	1000	60	75	0	-320	40	—	0.8
2K44 <sup>3</sup>	5700-7500	6.3	1.3	Fig. 59	Reflex Oscillator *	1000	60	75	0	-700	43	—	0.9
2K39 <sup>3</sup>	7500-10300	6.3	1.3	Fig. 59	Reflex Oscillator *	1000	60	75	0	-660	30	—	0.46
2K46	2730-3330 <sup>1</sup> 8190-10000 <sup>2</sup>	6.3	1.3	Fig. 58	Frequency Multiplier *	1500	60	60	-90	—	30	0.01/0.07	0.01-0.07
2K47	250-280 <sup>1</sup> 2250-3360 <sup>2</sup>	6.3	1.3	Fig. 58	Frequency Multiplier *	1000	60	60	-35	—	50	3.5	0.15
3K21 <sup>3</sup>	2300-2725	6.3	1.6	Fig. 58	Oscillator-Amplifier *	2000	150	450	0	—	125	1-3	10-20
3K22 <sup>3</sup>	3320-4000	6.3	1.6	Fig. 58	Oscillator-Amplifier *	2000	150	450	0	—	125	1-3	10-20
3K23 <sup>3</sup>	950-1150	6.3	1.6	Fig. 59	Reflex Oscillator *	1000	90	80	0	-300	70	—	1-2
3K27 <sup>3</sup>	750-960	6.3	1.6	Fig. 59	Reflex Oscillator *	1000	90	80	0	-300	70	—	1-2
3K30 (410R) <sup>3</sup>	2700-3300	6.3	1.6	Fig. 58	Oscillator-Amplifier *	2000	150	450	0	—	125	1-3	10-20
707B <sup>5</sup>	1200-3750	6.3	0.65	Fig. 61	Reflex Oscillator	300 <sup>7</sup>	45	—	300	-155/-290	30	—	0.140
OK159	2950-3275	6.3	0.65	Fig. 63	Reflex Oscillator	300	45	—	300	-100/-175	20	—	0.150
Z-668	21900-26100	—	—	—	Reflex Oscillator *	1700	—	15	—	-1700/-2300	—	—	0.02

<sup>1</sup> Input frequency.  
<sup>2</sup> Output frequency.

<sup>3</sup> Tuner required.  
<sup>4</sup> At max. ratings.

<sup>5</sup> Has demountable tuning cavity.  
<sup>6</sup> Cathode current specified on each tube.

<sup>7</sup> G2 and G3 voltage.  
<sup>8</sup> Forced-air cooling required.

# Index

	PAGE		PAGE
<b>Charts and Tables</b>		Vibrator Power Supplies (Types and Data)	258
Abbreviations for Electrical and Radio Terms	549	WWV Schedules	473
Abbreviations, Radiotelegraph	517, 558	Wave-Guide Dimensions	467
Alphabet, Greek	557	Wire Table	555
Amateur Emergency Corps Organization Chart	16	Word Lists for Accurate Transmission	521
Amateur Frequency Bands	362		
Antenna and Feeder Lengths	366, 367, 371	<b>Formulas</b>	
Antenna Gain	104	A. C. Average, Effective and Peak Values	20
Bandwidth, Typical I.F.	260	Antenna Length	356, 360, 367, 368
Battery Service Hours	558	Capacitance of Condenser	27
Call Areas	281	Capacitive Reactance	38
Cathode-Modulation Performance Curves	328, 336-337	Capacitance of Condenser	27
Characteristic Impedance	97	Cathode Bias	37, 72
Circuit and Operating Values for Converter Tubes	451	Characteristic Impedance	337, 369
Coaxial Antennas	484	Coupling-Transformer Turns Ratio	302
Coil Data for Test Oscillator	508	Critical Inductance	237
Color Code for Radio Parts	507	Decibels, Gain in	548
Condenser Color Code	21, 553	Delta-Matching Transformer Design	359
Conductivity of Metals	13	Efficiency, Power	25
Continental Code	23	Energy, Electrical	26
Conversion of Fractional and Multiple Units	555	Feeder Length	337
Copper-Wire Table	560	Filter Design	276
Country List, ARRL	548	Folded Dipole, Driven-Element Length	447
Decimal Equivalents of Fractions	552	Frequency, Resonant	47
Dielectric characteristics	26	Frequency-Wavelength Conversion	20
Dielectric Constants	503	Grid-Leak Bias	161
Drill Sizes	162	Grid-Leak Detectors	89
Driving-Power-Plate-Circuit-Efficiency Curve	254	High-Pass Filter	551
Dynamotors (Types and Data)	241	Impedance	40, 41
Filter-Choke Design	536-537	Impedance Matching	45, 46
Fixed-Text Messages	366, 367, 371	Impedance Ratios	45, 333
Gain of Directive Antennas	259	Impedance, Resistive at Resonance	49
Gas-Driven Generators (Types and Data)	376	Inductance Calculation	30
Impedance Step-Up in Folded Dipoles	237	Inductance Measurement	484
Inductance and Capacitance for Ripple Reduction	554	Inductive Reactance	38
Inductance, Capacitance and Frequency Charts	559	LC Constant	51
International Amateur Prefixes	34	Lecher Wires	477
L-R Time Constant	523	Low-Pass Filter	551
Message Form	21	LR Time Constant	35
Metals, Relative Resistivity of	276	Lumped-Constant Circuit Elements	456
Modulator Characteristic Chart	556	Modulation Impedance	281
Musical Scale	20	Modulation Index	317
Nomenclature of Frequencies	304	Modulation Percentage	310
Output Voltage Regulation of Beam-Tetrode Driver with Negative Feed-Back	521	Modulator Transformers, Turns Ratio	306
Phonetic Code	549	Multiplier, Meter	480
Pilot-Lamp Data	162	Ohm's Law (A.C.)	39, 41
Plate-Circuit-Efficiency-Driving-Power Curve	26	Ohm's Law (D.C.)	22-23, 25
Puncture Voltages, Dielectric	557	Output Voltage	238, 239
R-S-T System	355	Parallel Impedance	49
Radiation Angles	361	Parallel Resonance	49, 50
Radiation Patterns	355, 360	Peak Output Voltage at Driver-Transformer Primary	301
Radiation Resistance	553	Phasing-Line Length	367, 368
Reactance Chart	563-564	Pot-Tank Design	460
Receiving-Tube Classification Table	248	Power	25
Regulation and Output Voltage for Voltage-Multiplication Chart	513	Power-Supply Output Voltage	239
Relationship of Amateur-Band Harmonics	287	Power-Supply Transformer Voltage	239
Resistance-Coupled Voltage-Amplifier Data	21	Q	48, 50
Resistivity of Metals, Relative	507	"Q" Antenna	369
Resistor Color Code	364	RC Time Constant	34
Rhombic Antenna Design	557	Reactance	39
Schematic Symbols	Frontispiece	Resistance Measured by Voltmeter	481
Signal-Strength, Readability and Tone Scales	557	Resonance	47
Standard Component Values	506	Resonant Frequency	47
Standing-Wave Ratio	339, 497	Rhombic Antenna	364
Stub Position and Length	370	Ripple	235, 236
Surge Impedance	337	Series, Parallel, and Series-Parallel Capacitances	28, 29
Tank-Circuit Capacitance	156	Series, Parallel, and Series-Parallel Inductances	32
Tap Sizes	503	Series, Parallel, and Series-Parallel Resistances	23, 25
Time, Condenser Charge and Discharge	34	Shunts, Meter	480
Time Constant, L-R Circuit	34	Standing-Wave Ratio	334, 496, 497
Tools	502	Surge Impedance	337, 369
Transformer Design	240	Time Constant	34
Transmission Lines, Spacing	337	Transformer Current	44
V-Antenna Design Chart	363	Transformer Efficiency	44
Vacuum-Tube Characteristics	562-608	Transformer Turns, Primary	240
Vacuum-Tube Classification Chart, Receiving	572-586	Transformer Voltage	44
Vacuum-Tube Index	563-564	Transformer Volt-Ampere Rating	239
Vacuum-Tube Socket Diagrams	565-571	Transmission-Line Length	337
Velocity Factor and Attenuation of Transmission Lines	338	Transmission-Line Output Impedance	333
		Turns Ratio	44, 302, 306
		Voltage Dividers	242
		Voltage-Dropping Series Resistor	242

	PAGE
Voltage Regulation	236
Voltage-Regulator Limiting Resistor	243
Wavelength	20
Wavelength-Frequency Conversion	20
<b>Text</b>	
"A" Battery	60
A.C.	19, 35-43
A.C.-D.C. Converters	254
A.C.-D.C. Power Supplies	246, 247
A.C. Line Filters	515
Absorption Frequency Meters	474, 476
Alignment, Receiver	136-138
Alternating Current	19, 35-43
Amateur Bands	16
Amateur Emergency Corps	531, 540
Amateur Operator and Station Licenses	13
Amateur Regulations	509
American Radio Relay League:	
Headquarters	12-13
Hiram Percy Maxim Memorial Station	12, 544
Joining the League	547
Ammeters	342, 479
Ampere	20
Amplification Factor	63
Amplifier, Class-A	67
Amplifier Classifications	284-285
Amplifiers (see basic classifications, e.g., "Receivers," "Transmitters," and "Radiotelephony")	
Amplitude Modulation	273, 274-315
Angle of Radiation	82, 354, 355
Anode	60
Antenna Length	356
Atoms	18
Atmospheric Bending	81, 391, 392
Audio-Amplifier Classifications	284-285
Audio Frequencies	20
Audio-Frequency Amplifiers	92-94
Audio Image	115
Audio Limiting	107
Audio Oscillators	482-484
Auroral Reflection	81-82
Autodyne Reception	85
Automatic Volume Control	105-107
Autotransformer	46
Average Current Value	20
"B" Battery	60
Back-Wave	262
Band-Pass Filters	550-551
Bandspreading	95
Bandwidth	86
Battery Service Hours (Table)	260
Beam Antennas	363-376
Beat Frequencies	57
Beat-Note	85
Beat Oscillator	105
Bias	64-65, 159-161, 307
Bias, Cathode	72-73
Bias Modulation	276, 278, 281
Bias Supplies	248-249
"Birdies"	181, 187, 203, 206, 217, 228
Bleeder	228
Blocked-Grid Keying	265
Blocking, Condenser	55
Break-In	263, 271-272, 499-500, 519
Bridge Rectifiers	233
Bridge-Type Standing-Wave Indicators	491-494
Broadcast Interference, Elimination of	509-515
Buffer Amplifier	155-156, 275
Buffer Condenser	255
Butterfly Circuits	456-457
Buzzer Code-Practice Set	14
By-Passing	55-56
C (Capacitance)	26
"C" Battery	63
C-L Ratios	50-51
C-R and R-L Time Constants	34-35
Cable Lacing	505
Canadian General Manager	12
Capacitance and Condensers	26-29
Capacitance Measurement	488-489
Capacitive Coupling	51-52, 154-155
Capacitive Reactance	37-38
Capacitance, Distributed	56
Capacitance, Feed-Back	75
Capacitance, Inductance, and Frequency Charts	554
Capacitance, Interelectrode	68-69, 162
Capacitance-Resistance Time Constant	34
Capacitance, Specific Inductive	27
Carbon Microphone	282-283
Carrier	273
Cathode	59, 60
Cathode-Bias Calculation	72-73
Cathode Circuits	71-73
Cathode Follower	71
Cathode Keying	265-266

	PAGE
Cathode Modulation	276, 281-282
Cathode-Ray Oscilloscopes	485-490
Cathode Resistor	72
Cavity Resonators	467-468
Center-Tap, Filament	72
Center-Tap Full-Wave Rectifier	232-233
Center-Tap Keying	265-266
Characteristic Curves	62
Characteristic Impedance	328, 336-337
Characteristics, Dynamic	63
Characteristics of Radio Waves	79-80
Charges, Electrical	18
Chassis Layout	503-504
Chirp, Keying	143, 262, 263, 269
Choke Coil	239-242
Choke-Coupled Modulator	278
Choke, Filter	237
Choke-Input Filter	235-238
Choke, Swinging	237
Circuit Tracking	95
Circuits:	
Balanced	57
Butterfly	456-457
Coaxial-Line	454-456
Colpitts	75, 141, 142
Converter	98
Coupled	51-54
Electrical	17-58
Hartley	75, 141, 142
High-Frequency Oscillator	99
High-G	456
Lag	266-267
Lumped-Constant	456
Nonlinear	57
Parallel	41-42
Parallel-Resonant	49-50
Pot Tank	456
Power-Amplifier	65
Radio-Frequency Power-Amplifier	147-150
Receiver (see "Receivers")	
Resonant	47-51
Resonant-Line	454-456
Resonator	456
Series	40-41
Single-ended	57
Sweep	493
Transmitter (see "Transmitters")	
Tuned-Plate Tuned-Grid	75
Ultraudion	141-142
Voltage Multiplying	246-248
Class-A, -AB and -B Amplifiers	284-285
Class-B Modulators	305-309
Clicks, Keying	262-263, 266-267, 269
Clipper Circuit	293-297
Coaxial Antennas	451
Coaxial-Line Circuits	459-460
Coaxial Transmission Lines	336
Code (Continental) and Code Practice	13-16
Coefficient of Coupling	32
Coefficient, Temperature	21-22
Coil (see "Inductance")	
Coil, Field	94
Coil, Voice	94
Cold-Cathode Rectifiers	233
Collinear Arrays	365-366
Color Codes, RMA	506-508
Colpitts Circuit	75, 141, 142
Combined A.C. and D.C.	54-58
Combination Arrays	366, 376
Compact Antennas	362-363
Complex Input Impedance	340
Complex Waves	43
Component Values	506
Condenser	26
Condenser, Band-Setting	95
Condenser, Blocking	55, 158
Condenser Color Code	507
Condenser Coupling	51-52
Condenser-Input Filter	238-239
Condenser Microphones	284
Condenser Series and Parallel Connections	28-29
Condensers, Bandspread	95
Condensers, Buffer	255
Condensers, By-Pass	55, 158
Condensers, Electrolytic	27
Condensers, Filter	237-239
Condensers, Fixed	27
Condensers, Neutralizing	164-165
Condensers, Variable	27
Conductance	22
Conductance, Mutual	63
Conduction, Thermionic	59-60
Conductivity	21-22
Conductor Size, Antennas	357
Conductors	18
Constants, LC	51
Construction, Antenna	377-388



	PAGE		PAGE
Construction Practice	502-508	Directivity, Antenna	354
Continental Code	13-16	Director, Antenna	371
Control Circuits, Station	252-253, 496	Directors, ARRL	12
Control Grid	62	Discriminator	416-417
Controlled-Rectifier Keying	265	Dissipation, Plate and screen	161-162
Conversion Efficiency	97	Distortion, Harmonic	64-65
Converters, A.C.-D.C.	254	Distributed Capacitance and Inductance	56
Converters, Frequency	96	Dividers, Voltage	242-243
Converters, V.H.F.	399-404, 406-414	Divisions, ARRL	12
Copper-Wire Table	555	Door-Knob Tube	457
Cores	43	Doubler, Frequency	150-153
Corner-Reflector Antenna	452-453	Doublet, Folded	358
Coupled Circuits	51-54	Double Resonance	166
Coupling	32, 126-127	Double-Section Filter	236
Coupling, Antenna to Receiver	376-377	Double Superheterodyne	97
Coupling, Antenna to Transmitter	339-353	Drift, Frequency	76, 143
Coupling, Capacitive	51-52, 154-155	Drill Sizes (Table)	503
Coupling, Choke	65	Driven Elements	305
Coupling, Critical	52	Driver	153
Coupling, Impedance	65	Driver Power	161, 284, 301-302
Coupling, Inductive	52, 153-154	Driving-Power/Plate-Circuit-Efficiency Curve	162
Coupling, Link	53-54, 153-154, 345	Duplex-Diode Triodes and Pentodes	74
Coupling, Resistance	65, 286	Duplex Power Supplies	246-248
Coupling to Transmission Lines	339-353	Dynamic Characteristics	63
Coupling to Wave Guides and Cavity Resonators	468-469	Dynamic Instability	76
Critical Angle	82	Dynamic Inversion	391
Critical Coupling	52	Dynamic Loudspeakers	94
Critical Frequency	80	Dynamic Microphones	283-284
Critical Inductance	237	Dynamotors	253-254
Cross-Modulation	117-118	Dynatron Oscillator	77, 459
Cross-Talk	512	E (Voltage)	22
Crystals, Piezoelectric	54	E Layer	81
Crystal-Controlled Transmitter Construction (see "Transmitters" and "Very-High Frequencies")		Eddy Current	31
Crystal Filters	116-117	Effective Current Value	20
Crystal Frequency Calibrator	476-478	Efficiency, Amplifier	162
Crystal Grinding	146-147	Efficiency, Transformer	44
Crystal Headphones	93-94	Electrical Laws and Circuits	17-58
Crystal Microphones	283	Electrical Length	356
Crystal Oscillators	145-146	Electrode	60
Current, Alternating	19	Electrolytic Condensers	27
Current, Antenna	354, 359	Electrolytic Conduction	18
Current, Direct	19	Electromagnetic Deflection	486
Current Feed for Antennas	343	Electromagnetic Field	17
Current-Intensity Modulation	457-458	Electromagnetic Waves	17
Current Lag and Lead	35	Electromotive Force (E.M.F.)	18
Current Line	328-329, 342-343	Electron-Coupled Oscillator	151, 197-220
Current Loop	330, 354	Electron Lens	485
Current Magnetizing	44	Electronic Conduction	18
Current Measurement	479-481	Electronic Keys	272
Current Node	330, 354	Electronic Switching	74
Current, Pulsating	54	Electron Transit Time	457
Current Values	20	Electronic Voltage Regulation	244-245
Currents, Eddy	31	Electrons	17
Curves, Tube-Characteristic	62	Electrostatic Coupling	51-52
Cut-Off Frequency	551	Electrostatic Deflection	486
Cut-off, Plate-Current	62	Electrostatic Field	17
Cycle	19	Electrostatic Shield	348-349
Cyclic Variations	81	Element Spacing, Antenna	372
Cylindrical Antennas	451-452	Emergency Coordinator	533, 544
D Layer	80	Emergency Power Supply	253-261
D.C.	19	Emission, Electron	59-60
D.C. Instruments	483-486	Emission, Grid	166
Dead Spots	91	Emission, Secondary	89
Decibel	548	Emission, Thermionic	59-60
Decoupling	286	End Effect	356
Deflection Plates	486	End-Fire Arrays	366-367
Degeneration	67-68	Energy	25-26
Degenerative Oscillator	76-77	Energy Relationships	44
Delayed A.V.C.	106	Excitation	161
Delivering Messages	529	Excitation, Grid	75
Delta Matching Transformer	359, 445	Exciter Units (see "Transmitters")	368
Demodulation	87-92	Extended Double-Zepp Antenna	81, 389-390
Density, Flux	17	F-Layers	83
Detection	85, 87-92	Fading	27
Detectors:		Farad	348-349
Crystal	87	Faraday Shield	55
Diode	87-89	Feed, Series and Parallel	67-68, 135-136, 315
Grid-Leak	89	Feed-Back	327, 353
Infinite-Impedance	90	Feeders and Feed Systems	372, 373
Plate	89-90	Feeding Close-Spaced Antenna Arrays	357-359
Regenerative	90-92	Feeding Half-Wave Antennas	87, 103, 282
Deviation Ratio	318	Fidelity	17
Diagrams, Schematic Symbols for	<i>Frontispiece</i>	Fields	482-484, 490-491
Diamond Antenna	364-365	Field-Strength Meters	59
Dielectrics	27	Filament	72
Dies	505	Filament Center-Tap	249-250
Difference of Potential	23-24	Filament Supply	528-529
Diffraction	79	Fills and Repeats	116
Diode Detectors	87-89	Filter, Crystal	238
Diodes	60	Filter Resonance	235-239, 550-551
Dipole, Folded	358, 446	Filters	266-267
Direct Coupling	51	Filters, Keying	266
Direct Current	19	Filters, R. F.	96
Direct Feed for Antennas	357-358	First Detector	17
Directive Antennas	363-377	Flux Density, Magnetic	45
		Flux, Leakage	17
		Flux, Lines of	17

	PAGE		PAGE
Fly-Back	486	Impedance, Antenna	354-357, 360-361
Focusing Electrode	485	Impedance-Coupled Amplifiers	65
Folded Dipole	358, 446	Impedance Matching	46, 306, 445-446
Force, Electromotive	18	Impedance Ratio, Transformer	45-46
Force, Lines of	17	Impedance, Transmission-Line	336-337
Frequency	19	Impedance, Surge	328, 336-337
Frequency Allocations, Amateur	16	Impedance Transformer	33, 339-340
Frequency, Audio	20	Indicators, Tuning	114-115
Frequency, Critical	80	Inductance	29-33
Frequency Deviation	316	Inductance, Capacitance, and Frequency Chart	554
Frequency Doublers	150-153	Inductance, Critical	237
Frequency Drift	76	Inductance, Distributed	56
Frequency Inductance and Capacitance Chart	554	Inductance, Leakage	45
Frequency Measurement:		Inductance Measurement	488-489
Absorption Frequency Meters	474-476	Inductance, Mutual	32-33
Frequency Standards	471	Inductances in Series and Parallel	32
Heterodyne Frequency Meters	471-474	Inductive Capacitance, Specific	28
Lecher Wires	476-478	Inductive Coupling	52, 153-154
V.H.F. Wavemeter	475-476	Inductive Neutralization	150
WWV Schedules	473	Inductive Reactance	38-39
Frequency Modulation:		Infinite Impedance Detector	90
Constructional:		Input Choke	237
Frequency-Control and FM Modulator Unit	321-322	Insulators	18
Narrow-Band PM Exciter Unit	323-324	Inter-electrode Capacitances	68-69, 162
Deviation Ratio	318	Intermediate Frequency	96
Discriminator	416-417	Intermediate-Frequency Amplifier	102-107, 115-117
Limiter	415-416	Intermediate-Frequency Bandwidths, Table	104
Index	317	Intermediate-Frequency Noise Silencer	109
Principles	316-319, 415	Intermediate-Frequency Transformers	104
Reactance Modulator	320	International Amateur Radio Union	10
Reception	138-139, 415-417	Interruption Frequency	365
Frequency Multipliers	150-153	Interstage Coupling	153-156
Frequency, Radio	20	Inverse Peak Voltage	234
Frequency, Resonant	47	Inversion, Dynamic	391
Frequency Response	282, 286	Inversion, Nocturnal	391
Frequency Response, Restriction of	293-294, 306-307	Inversion, Phase	288
Frequency Spectrum	20-21	Inversion, Temperature	391
Frequency-Wavelength Conversion	20	Ionization	80-83, 389-392
Gaseous Conduction	18	Ionosphere	79-81
Gaseous Regulator Tubes	243-244	Ions	18
Gasoline-Engine-Driven Generators	259-261	Isolating Amplifiers	155-156
Genmotors	254	"J" Antenna	445
Grid	61-62	Key Chirps	263, 269
Grid Bias	64-65, 159-161	Key, How To Use	15
Grid-Bias Modulation	276, 278-281	Keying:	
Grid-Cathode Capacitance	68-69	Back-Wave	262
Grid Condenser	74	Break-In	263, 271-272
Grid-Control Rectifiers	74	Electronic Keys	272
Grid-Controlled Rectifier Keying	265	Key-Click Reduction	266-267
Grid Current	62	Methods:	
Grid-Dip Meter	482-484	Blocked Grid	265
Grid Emission	166	Cathode or Center-Tap	265-266
Grid Excitation	75	Grid-Controlled Rectifier	264
Grid Keying	265	Plate	263, 264
Grid Leak	74	Power Supply	264
Grid-Leak Calculation	161	Primary	264-265
Grid-Leak Detectors	89	Screen Grid	263-264
Grid Neutralization	149-150	Suppressor Grid	265
Grid-Plate Capacitance	68-69	Tube Keyer	267
Grid-Plate Oscillator	152-153	Monitoring	270-271, 478
Grid-Plate Transconductance	63	Oscillator Keying	269-270
Grid, Suppressor	70	Parasitic Clicks	165-166
Grid Voltage	63	Relays	266
Ground	56	Kilocycle	20
Ground Effect	354-356	Kilohm	23
Ground Waves	79-80	Kilovolt	23
Grounded-Grid Amplifier	71	Kilowatt	23
Grounded-Plate Amplifier	358-459	Kilowatt Hour	26
Guys, Antenna	380-381	Kinescopes (Table)	588-589
Half-Wave Antenna	356-359	Klystrons	458-459
Half-Wave Rectifiers	232	L (Inductance)	30
Halyards, Antenna	381	LC Constants	51
Harmonic	19	L/C Ratios	50-51
Harmonic Distortion	64-65	L-R Time Constant	35
Harmonic Generation	151-153	"L"-Section Filters	550-551
Harmonic Operation of Antennas	359-363	Lag Circuits	266
Harmonic Suppression	166, 306-307	Lag, Current	35
Hartley Circuit	75, 141, 142	Laminations	31
Headphones	93-94	Laws Concerning Amateur Operations	13, 509, 540
Heater	60	Laws, Electrical	17-58
Henry	29	Lazy-H Antenna	367
Hertz Antenna	356	Learning the Radiotelegraph Code	14
Heterodyne Reception	85	Lecher Wires	476-478
High-C Circuit	50	License Manual, The Radio Amateur's	13
High-Frequencies	20	Licenses, Amateur	13
High-Frequency Receivers	85-139	Lighthouse Tubes	457
High-Pass Filters	551	Lightning Protection	382
High-Q Circuits	50	Limiter, FM	415-416
High-Vacuum Rectifiers	233-234	Line Filters	515
Hiram Percy Maxim Memorial Station	12, 544	Line-of-Sight Transmission	389
History of Amateur Radio	9-16	Line-Voltage Adjustment	250
Hum	91-92, 136, 314-315	Linear Amplifiers	492-493
Hysteresis	31	Linear Antenna Transformers	369-371
I (Current)	22	Linear Sweep	486, 488-489
Image, A.F.	115	Lines, Flux	17
Image, R.F.	96	Lines of Force	17
Impedance	40-43, 277	Lines, Non-resonant, Resonant, Two-Conductor	334-335

	PAGE		PAGE
Link Coupling	53-54, 153-154	Narrow-Band Frequency Modulation	318-319
Link Neutralization	149-150	Negative Feed-Back	67-68, 303-305
Load	46, 51	Negative Resistance	77
Load Impedance	277	Negative-Resistance Oscillators	76-77, 459
Load Resistor	61	Neutralization	148-150, 164-165
Long-Wire Antennas	359-361, 450	Nodes	330
Loops	330	Noise	86, 107, 314-315
Losses, Hysteresis	31-32	Noise Reduction	107-109, 256, 261
Loudspeakers	93-94	Nonconductors	18
Low-C Circuit	50	Nonresonant Lines	334-335
Low Frequencies	20	Ohm	21
Low-Level Modulators	321-324, 418-421	Ohm's Law	22-23, 25, 167
Low-Pass Filters	550-551	Ohm's Law for A.C.	39, 41, 42
Lumped-Constant Circuits	456	Ohmmeters	480-482
Magnetizing Current	44	Open-Wire Line	336
Magnetrons	459-460	Operating Bias	159-161
Masts	378-380	Operator's License, Amateur	13
Maximum Usable Frequency	80	Oscillation	68
Maxwell-Bridge Standing-Wave Indicator	492	Oscillator Keying	269-270
Measurements:		Oscillators, Negative-Resistance	76-77, 459
Antenna	490-494	Oscillators, Test	482-484
Capacitance	488-489	Oscilloscope Amplifiers	488-490
Current	483-486	Oscilloscope Patterns	312, 417, 486
Frequency	471-478	Oscilloscopes	485-490
Inductance	488-489	Output Capacitance, Tube	69
Modulation	482-483, 491-494	Output Limiting	292-293
Power	483-486	Output Power	66, 145, 161
Resistance	483-486	Output Voltage	238, 239
Standing-Wave Ratio	491-494	Oxide-Coated Cathode	60
Voltage	483-486	Overexcitation	308
Measuring Instruments	471-494	Overmodulation	275
Megacycle	20	Overmodulation Indicators	315, 478-479, 485-490
Megatrons	457	P (Power)	25
Megohm	21	Padding Condenser	95
Mercury-Vapor Rectifiers	74, 234	Parabolic Reflectors	456
Message Handling	521-530	Parallel Amplifiers	67
Meteor Trails	83, 391	Parallel Antenna Tuning	343-345
Meter Switching	167	Parallel Capacitances	28-29
Mho	22	Parallel Circuits	23-25, 28-29, 32
Microampere	21	Parallel-Conductor Line	336
Microfarad and Micromicrofarad	26	Parallel Feed	55
Microhenry	30	Parallel Impedance	41-42
"Micro-Match"	371, 491-492	Parallel Inductances	32
Microphones	282-284	Parallel-Line Oscillators	32
Microwaves (See also "Very-High Frequencies")	454-470	Parallel Resistances	23-25
Milliammeters	60, 484-485	Parallel Resonance	49-50
Milliampere	20	Parallel Tuning	343-345
Millihenry	30	Parasitic Elements	371
Millivolt	21	Parasitic Oscillations	165-166
Milliwatt	21	Patterns, Oscilloscope	312, 417, 486
Mixers	96	Patterns, Radiation	357, 360, 361
Mobile Antennas	450-451	Peak-Current Value	20
Mobile, Receiving Equipment for 2, 6 and 10 Meters	406-415	Peak Voltage Rating	234
Modes of Propagation	467	Pentagrid Converters	98
Modulation:		Pentode Amplifiers	70
Adjustments and Testing	308-315	Pentode Crystal Oscillators	145
Amplitude Modulation	273, 274-315	Pentodes	69-71
Cathode Modulation	276, 281-282	Percentage of Modulation	274-275
Characteristic	276	Per Cent Ripple	235
Choke-Coupled Modulation	278	Permeability	31
Depth	317	Phase	35-36
Envelope	311-312	Phase Inversion	288
Frequency Modulation	273, 316-326	Phase Modulation	273, 317-326
Grid-Bias Modulation	276, 278-281	Phase-Modulation Reception	139
Heising Modulation	278	Phase Relations, Amplifiers	64
Impedance	277, 281	Phased Antennas	367
Index	317-318	"Phone Reception	134-135
Linearity	276, 277	Phonetic Alphabet	521
Methods	273	Pi-Section Filters	550-551
Monitoring	478-479	Pierce Oscillator	145, 153, 170-173, 184-187
Narrow-Band Frequency Modulation	318-319	Piezoelectric Crystals	54
Percentage	274-275	Piezoelectric Microphone	283
Phase Modulation	273, 317-326	Plane-Reflector Antennas	452
Plate Modulation	276-278	Plate	60
Power	275	Plate-Cathode Capacitance	68
Suppressor Modulation	280-281	Plate-Circuit-Efficiency-Driving-Power Curve	162
Test Equipment	315, 487-488	Plate-Current Shift	313-314
Velocity	457-458	Plate Detectors	89-90
Waveforms	311-312	Plate Dissipation	161-162
Modulators	305-308	Plate Efficiency	162
Monitors	268, 270-271, 478-479	Plate Modulation	276-278
Motorboating	138	Plate Neutralization	148-149
Mu ( $\mu$ )	63	Plate Resistance	63
Mu, Variable	70-71	Plate Supply	307-308
Multiband Antennas	361-363	Plate Transformer	239-242
Multielement Tubes	74	Plate Tuning, Power-Amplifier	163
Multihop Transmission	83	Plates, Deflection	486
Multimeters	480-482	Polarization	79, 354-356, 488
Multipliers, Voltage	246-248	Portable Antennas	450-451
Multipurpose Tubes	74	Positive Feed-Back	68
Multipliers, Frequency	480-482	Pot Tank Circuits	456
Multipliers, Voltmeter	479-480	Potential Difference	23-25
Multirange Meters	484-486	Power	25
Mutual Conductance	63	Power Amplification	65-67
Mutual Inductance	32	Power Amplifier	42
NBFM Reception	138-139	Power Factor	354, 360-361
NBS-ARRL 28-Mc. Observing Project	78, 84	Power Gain, Antenna	61
		Power Input	61

	PAGE		PAGE
Power Measurement	25, 479-482	Reactance, Inductive	38-39
Power Output	44, 66, 161	Reactance, Leakage	45
Power, Reactive	39	Reactance Modulation	320
Power Sensitivity	67	Reactance, Transmission-Line	333
Power-Supply Keying	264-265	Reactive Power	39
Power-Supply Construction Data	251	Readability Scale	557
Power Supplies:		Receivers, High-Frequency:	
A.C.-D.C.	246-248	Antennas for	376-377
A.C.-D.C. Converters	254	Constructional:	
Bias Supplies	248-249	1-Tube Converter for 10 and 11 Meters	128-130
Combination A.C.-Storage Battery Supplies	256-258	2-Tube Superheterodyne (6K8-6SN7)	100-102
Constructional (See also Chapters Five and Six):		3-Tube Converter for 28 to 50 Mc.	406-411
250-Volt 35 Ma. Receiver Supply	243-244	6-Tube General-Coverage and Bandspread Super-	
1000/400-Volt 125/150-Ma. Dual Supply	247	heterodyne	110-114
Heavy-Duty Regulated Power Supply	245	8-Tube Regenerative S.S. Superheterodyne	119-123
Dry Batteries	261	Antenna Coupling Unit for Receiving	126-127
Dynamotors	253-254	Audio Noise Limiter	107-108
Emergency Power Supply	253-261	Bandpass Converter for 14, 28 and 50 Mc. (see	
Filament Supply	249-250	also "Very-High Frequencies Receivers")	130-134
Generators	254	Signal-Strength Indicator	114-115
Generators, Gas-Driven (Table)	259	Triode Preamplifier	124-126
Noise Elimination	256-261	Rectification	61
Plate Supply	232	Rectifiers	74, 233, 235
Principles	232	Rectifiers, Grid-Control	74
Vibrators	235	Rectifiers, Mercury-Vapor	74, 234
Vibrator Supplies (Table)	258	Reflected Impedance	46
Preferred Values, Component	506	Reflected Waves	330
Preselectors	117	Reflection of Radio Waves	79
Primary Coil	43	Reflection from Meteor Trails	391
Primary Keying	264-265	Reflection, Ground	354-356
Propagation, Ionospheric	80-84	Reflector	371
Propagation Modes	467	Reflector Electrode	458
Protective Bias	159-161	Refraction of Radio Waves	79
Pulling	97	Regeneration	90
Pulsating Current	54	Regenerative Detectors	90-92
Puncture Voltage	28	Regenerative I.F.	115-116
Push-Pull Amplifiers	67	Regulation, Voltage	243-245
Push-Pull Multiplier	150	Principles, Design and Construction	85-139
Push-Pull Neutralization	149	Receivers, V.H.F. (See "Very-High Frequencies")	
Push-to-Talk	500	Selectivity	86
Q	48	Sensitivity	123-124
"Q" Antenna	369	Servicing	136-138
Q-Loaded Circuits	50	Tuning	134-135
"Q"-Section Transformer	369, 445	Regulations, Amateur	13, 509, 540
QST	12	Regulator Tubes	243-244
Quarter Wave	368	Regulator, Voltage	244
Quench Frequency	395	Relaxation Oscillator	77, 459
R (Resistance)	22	Resistance	21-26
R.F.	20	Resistance-Bridge Standing-Wave Indicator	497-498
R.M.S. Current Value	22	Resistance-Capacitance Filter	550, 551
Radiation	335	Resistance-Capacitance Time Constant	34
Radiation Angle	82, 354, 355	Resistance-Coupled Amplifier Data (Chart)	287
Radiation Characteristics	357	Resistance Coupling	65, 286
Radiation Patterns	356-357, 360, 361	Resistance Measurement	480-482
Radiation Resistance	376-377	Resistance, Negative	77
Radio Frequency	20	Resistance, Radiation	376, 377
Radio-Frequency Ammeters	342-343	Resistance, Temperature Effects	22
Radio-Frequency Amplification	147-150	Resistance, Transmission-Line	332-333
Radio-Frequency Amplifiers (receivers)	117	Resistance, Wires	21-22
Radio-Frequency Choke Coil	55	Resistances in Series and Parallel	23-25
Radio-Frequency Feed-Back	315	Resistor	22
Radio-Frequency Power-Amplifier Circuits	147-150	Resistor Color Code	507
Radiotelegraph Operating Procedure	517-519	Resonance	47-50, 238
Radiotelephony:		Resonance Curve	47-50, 86
Adjustments and Testing	310-315	Resonance, Sharpness of	47-48, 373-376
Audio-Harmonic Suppression	306-307	Resonant Cavity	463-464
Class-B Modulators	305-309	Resonant-Line Circuits	454-456
Checking FM and PM Transmitters	324-326	Resonant Transmission Lines	334-335
Constructional:		Resonator, Cavity	467-468
6-Watt P.P. 2A3 Speech Amplifier and Driver with		Response Frequency	282
Volume Compression	292-293	Restricted-Space Antennas	362-363
8-Watt Speech Amplifier, Push-Pull Triodes	290-291	Restriction of Frequency Response	293-294
100-Watt 807 Speech Amplifier/Modulator	299-301	Rhombic Antenna	364-365
350-Watt Phone-C.W. Transmitter	321-320	Rhubarbtrons	458-459
Frequency-Control and FM-Modulator Unit	321-322	Ripple Frequency and Voltage	235
High-Power Modulators	307	Rochelle Salts Crystals	54
Narrow-Band PM Exciter Unit	323-324	Rotary Antennas	37
Measurements	310-315	Rotary-Beam Construction	382-388
Microphones	282-284	S-Meter Circuits	109-110
Modulation	273-282	S-Meters	114-115
Modulator Plate Supply	307-308	S Scale	557
Monitors	478-479	Saturation Point	61
Output Limiting	292-293	Sawtooth Sweep	488-489
Overmodulation Indicators	315	Scatter	82
Principles	273	Screen By-Pass Condenser	73
Reception	138-139	Screen Dissipation	161-162
Resistance-Coupled Speech-Amplifier Data	287	Screen-Dropping Resistor	73
Speech Amplifiers	282-305	Screen-Grid Amplifiers	162-164, 277-278
Volume Compression	292-293	Screen-Grid Keying	263-264
Radio Waves, Characteristics of	78-80	Screen-Grid Tubes	69-71
Range, V.H.F.	389	Second Detector	96, 105
Ratio, Impedance	45	Secondary Coil	43
Ratio, Turns	43	Secondary Emission	69
Ratio, Power-Amplification	67	Selectivity	53
Ratio, Voltage-Amplification	64	Selectivity Control	104
Ratio, L/C	50-51, 156-158	Selectivity, Receiver	85, 86
Reactance, Capacitive	37	Selenium Rectifiers	234

	PAGE		PAGE
Self-Bias	159-161	Tetrodes, Beam	73-74
Self-Controlled Oscillators	141-145	Thermal-Agitation Noise	86
Self-Inductance	29	Thermionic Emission	59-60
Self-Oscillation	74	Thoriated-Tungsten Cathodes	60
Self-Quenching	306	Thyratrons	74
Sensitivity, Receiver	85-86, 123-124	Time Base	486
Series Antenna Tuning	343-345	Time Constant	33-35
Series Capacitances	28-29	Tone Control	93
Series Circuits	23-25, 28-29, 32	Trace, Cathode-Ray	486
Series Feed	55	Tracking	118
Series Inductances	32	Transceivers	443
Series Resistances	23	Transconductance, Grid-Plate	63
Series Resonance	47	Transformer Color Codes	508
Series Voltage-Dropping Resistor	242	Transformer Coupling	65, 286-288
Service Message	529	Transformer, Delta-Matching	359, 445
Sharp Cut-Off Tubes	62	Transformer Design	239-242
Shielding	57-58	Transformer Efficiency	44
Shields	58	Transformer, "Q"-Section	369, 445
Shields, Electrostatic	348-349	Transformerless Power Supplies	246
Shot Noise	107	Transformers, I.F.	104
Shunts, Meter	483-484	Transformers, Linear-Circuit	369-370
Sidebands	273-274	Transformers, Plate	239-242
Signal Generators	482-484	Transformers, Triple-Tuned	104
Signal-Handling Capability	87	Transitron	77
Signal-to-Image Ratio	96	Transit Time	457
Signal Monitor	268, 270-271, 478-479	Transmission Lines	327-339, 358-359, 466-467
Signal-Strength Indicators	109-110	Transmission Lines as Circuit Elements	454-458
Signal-Strength Scale	557	Transmission-Line Coupling	339-353
Silencers, Noise	107-109, 256, 261	Transmitters:	
Sine Wave	19	Constructional:	
Single-Ended Circuits	57	Complete Transmitter Assemblies:	
Single-Signal Reception	115	60-Watt 3-Band Transmitter, 807 Output	173-178
Skip Distance	82-83	60-Watt Transmitter for 14, 28 and 50 Mc.	424-427
Skirt Selectivity	86	100-Watt Output Bandswitching Transmitter	
Skywave	79-80	or Exciter	200-204
Smoothing Choke	237	150-Watt Transmitter with Plug-In Stages	178-184
Socket Connections (Diagrams)	565-571	250-Watt Three-Stage Transmitter	184-187
Solar Cycle	389	350-Watt Phone-C.W. Transmitter	221-229
Soldering	505	900-Watt Two-Stage Transmitter	187-191
Space Charge	59	A Simple Single-Tube Transmitter	168-170
Space Wave	80	An Inexpensive Two-Tube Transmitter	170-173
Spectrum Frequency	21-22	Enclosed 1-Kw. Transmitter	191-197
Speech Amplifiers	284-305	Exciters or Low-Power Transmitters:	
Speech Clipping and Filtering	293-297	Variable-Frequency Exciters	197-200
Speech Equipment	282-309	60-Watt Output 6V6GT-807 Plug-In-Coil	173-178
Speech Intelligibility	274	Power Amplifiers:	
Speech Waves	275	200-500-Watt Input Push-Pull	212-214
Sporadic-E Layer Ionization	82, 390	450-Watt Input Push-Pull	214-217
Spurious Responses	97, 135	450-Watt Bandswitching Push-Pull	204-207
Spurious Sidebands	275	500-Watt Beam-Tube Single-Ended	207-211
Squeezing	99	1-Kw. Push-Pull	217-220
Stability, Receiver	87	Control Circuits	252-253
Stacked Arrays	447-448	Line-Voltage Adjustment	250
Stage Gain	286	Metering	167
Stagger-Tuning	53	Principles and Design	140-231
Standard Component Values	506	Rack Construction	229-231
Standards, Frequency	470	Transverse Electric and Magnetic Mode	467
Standing Waves	329-335, 359, 491	Trapezoidal Pattern	310, 312
Standing-Wave Ratio	334, 371, 491-494	Trimmer Condenser	95
Static Characteristics	62	Triodes	61-63
Station Control Circuits	252-253, 496	Triode Amplifiers	148-149, 164-165
Straight Amplifier	147	Triode Crystal Oscillators	145
Stray Coupling	347-349	Triple-Detection Superheterodyne	117
Stray Receiver Rectification	512	Tri-Tet Oscillator	151-152, 168-170, 173-178
Striking Voltage	488		187-191, 200-204, 221-229
Stubs, Antenna-Matching	369-371	Troposphere Propagation	83
Subsidence Inversion	391-392	Tropospheric Bending	391-392
Sunspot Cycle	389	Tropospheric Waves	79-80
Superheterodyne	96-139, 394-395	Trouble Shooting (Receivers)	136-138
Superhigh Frequencies	20	Tube Keyer	267
(see also "Very-High Frequencies")		Tube Noise	86
Superegeneration	395-399	Tuned-Grid Tuned-Plate Circuit	75, 141-142
Suppressor Grid	70	Tuned Transmission Lines	335
Suppressor-Grid Keying	265	Tuners, Antenna, Construction of:	
Suppressor-Grid Modulation	280-281	Bandswitching Universal Coupler	351-352
Suppressor, Noise	109	Low-Power Rack-Mounted Antenna Coupler	350-351
Surge Impedance	328	Receiver Coupler	126-127
Sweep Circuits	489	Series-Parallel Coupler for Wall Mounting	350
Sweep Waveforms	489	Wide-Range Antenna Coupler	352-353
Swing, Grid	62	Tuning Indicators	109-110
Swinging Choke	237	Tuning Receivers	92-96
Swinging Link	343	Turns Ratio	43
Switching, Antenna	377	Twin-Lamp Standing-Wave Indicator	493-494
Switching, Control-System	252-253	Two-Conductor Lines	327-339, 358-359, 466-467
Switching, Meter	167	Ultrahigh Frequencies (see also "Very-High Frequencies")	36
Synchronous Vibrators	255	Ultraudion Circuit	141, 142
"T" Match to Antennas	445-446	Unbalance in Transmission Lines	338-339, 371
"T" Section Filters	350-351	Universal Antenna Coupler	345-346
Tank-Circuit Q	50	Untuned Transmission Lines	334-335
Tank Constants	156	Upward Modulation	313-314
Temperature Effects	21-22	"V" Antennas	363-364
Temperature Inversion	391	Vacuum-Tube Principles	59-77
Termination, Line	332-334	Vane Tuning	96
Tertiary Winding	104	Variable-Frequency Oscillators	141-145, 197-200
Tetrode	69	Variable- $\mu$ Tubes	70-71
Tetrode Amplifiers	147-148	Variable Selectivity	116-117
Tetrode Crystal Oscillators	145		

	PAGE		PAGE
Velocity-Modulated Tubes	458-460	Vibrator Power Supplies	255-261
Velocity Modulation	457-458	Virtual Height	80-81
Velocity of Radio Waves	20	Volt	19
Vertical Amplifiers	489	Volt-Amperes	42
Very-High Frequencies:		Voltage Amplification	66-67, 284-288
Antenna Systems:		Voltage Dividers	242, 243
Coaxial Antenna	451	Voltage Distribution, Antenna	359
Corner-Reflector Antenna	452-453	Voltage Drop	23-24
Cylindrical Antennas	455-456	Voltage Feed for Antennas	343
Delta Match	445	Voltage Gain	66, 286
Design Factors	444	Voltage Loop	331
Directive Arrays	446-453	Voltage-Multiplier Circuits	246-248
Folded Dipole	446	Voltage Node	331
"J" Antenna	445	Voltage Ratio, Transformer	43-44
Long-Wire Antennas	450	Voltage Regulation	236, 243-245
Mobile Antennas	450-451	Voltage Ripple	235
Parabolic Reflectors	453	Voltage-Stabilized Power Supplies	243-246
Plane-Sheet Reflectors	452	Voltmeters	483-486
"Q" Section	445	Volume Compression	292-293
Stacked Antennas	447-448	WIAW	12, 544
"T"-Match	445-446	WAC Certificates	546
Constructional:		Watt	25, 26
Receivers:		Wave Angles, Optimum	82-84
6-, 10- and 11-Meter Mobile Converter	412-415	Wave-Envelope Pattern	311
50-Mc. Two-Tube Converter	399-401	Wave Guides	466-467
50- and 28-Mc. Three-Tube Converter	406-411	Wave, Ground	79-80
144-Mc. Crystal-Controlled Converter	401-402	Wave Propagation	80-84, 389-392
144-Mc. Mobile Converter	411	Wave, Sine	19
144-Mc. One-Tube Converter	402-404	Wave, Sky	79-80
144-Mc. T.R.F. Superregenerative	396-399	Wavetraps	515
235-Mc. Converter	462-463	Waveform	19
420-Mc. Superregenerative Receiver	465-466	Wavelength	20-21
Superregenerative I.F. and Audio Unit	406	Wavelength-Frequency Conversion	20-21
Transmitters:		Wavelength Performance	78-79
14-, 28- and 50-Mc. Transmitter	424-427	Wavelengths, Amateur	16
50-144-Mc. Driver-Amplifier	421-424	Wavemeter (see "Frequency Meters")	
144-Mc. Crystal-Controlled Mobile Trans-	438-441	Waves, Complex	43
mitter	404-406	Waves, Electromagnetic	17
144-Mc. Grounded-Grid R.F. Amplifier	461-462	Wide-Band Antennas	451-452
235-Mc. 10-Watt Transmitter	463-465	Wide-Band FM Reception	415-417
420-Mc. Transmitter	418-421	Wire Table	555
AM-FM 50-Mc. Transmitter	429-431	Wiring Diagrams, Symbols for	<i>Frontispiece</i>
Double Beam-Tetrode Amplifier	431-434	Word Lists for Accurate Transmission	521
Low-Cost 2-Meter Transmitter	441-443	Workshop Practice	502-508
Low-Power 50-Mc. Transmitter	427-429	WWV Schedules	473
MOPA Transmitter for 144-Mc.	434-438	X (Reactance)	36-39
Mobile Transmitter for 50 and 28 Mc.	392-393	Z (Impedance)	40-43
Techniques	443	Zero Beat	92
Transceivers		Zepp Feed for Antennas	358



# The Catalog Section



In the following pages is a catalog-file of products of the principal manufacturers who serve the short-wave field. Appearance in these pages is by invitation—space has been sold only to those dependable firms whose established integrity and whose products have met with the approval of the American Radio Relay League.



# INDEX OF ADVERTISERS

## ★ CATALOG SECTION ★

### *The Radio Amateur's Handbook*

	Page		Page
Advance Electric & Relay Co. . . . .	99	Marion Electrical Instrument Co. . . . .	75
Allied Radio Corporation . . . . .	97	McElroy Manufacturing Co. . . . .	130-133
American Lava Corporation . . . . .	66	Measurements Corporation . . . . .	51
American Phenolic Corporation . . . . .	49	Merit Coil & Transformer Corp. . . . .	122
American Radio Relay League, Inc. 1, 2, 129, 135-143, 144		Micro-Switch Corporation . . . . .	33
Amperex Electronic Corporation . . . . .	40	Millen Mfg. Co., Inc., James . . . . .	34-39
Arrow Electronics, Inc. . . . .	121	National Co., Inc. . . . .	3-14
Ashe Radio Company, Walter . . . . .	114	Newark Electric Co. . . . .	91
Astatic Corporation, The . . . . .	50	Ohmite Manufacturing Co. . . . .	56, 57
Audel & Co., Theo. . . . .	126	Par-Metal Products Corp. . . . .	54
Barker & Williamson . . . . .	82-84	Petersen Radio Co., Inc. . . . .	67
Birnbach Radio Company . . . . .	113	Premax Products Company . . . . .	79
Bliley Electric Company . . . . .	32	Radio Corporation of America . . . . .	30, 31
Boland & Boyce . . . . .	90	Radio Manufacturing Engineers . . . . .	100, 101
Brach Mfg. Corp., L. S. . . . .	80	Radio Shack Corporation . . . . .	95
Browning Laboratories, Inc. . . . .	78	Raytheon Manufacturing Co. . . . .	15
Burgess Battery Company . . . . .	17	Rider Publishers, Inc., John F. . . . .	105
Cameradio Company . . . . .	108	Sangamo Electric Company . . . . .	48
Candler System Company . . . . .	98	Shure Brothers, Inc. . . . .	81
Centralab . . . . .	62, 63	Silver Co., Inc., McMurdo . . . . .	70, 71
Collins Radio Company . . . . .	41-44	SNC Manufacturing Co., Inc. . . . .	85
Commercial Radio Institute . . . . .	134	Sola Electric Company . . . . .	29
Cornell-Dubilier Elec. Corp. . . . .	52, 53	Solar Capacitor Sales Corp. . . . .	112
Eitel-McCullough, Inc. . . . .	60, 61	Sonar Radio Corporation . . . . .	106, 107
Electric Soldering Iron Co. . . . .	116	Sprague Products Company . . . . .	74
Electro-Voice, Inc. . . . .	64	Standard Transformer Corp. . . . .	110
General Electric Company . . . . .	65	Superior Instrument Company . . . . .	109
Hallicrafters Co., Inc., The . . . . .	18-28	Supreme Transmitter Corporation . . . . .	120
Hammarlund Mfg. Co., Inc., The . . . . .	45-47	Sylvania Electric Products Co. . . . .	58, 59
Harvey Radio Company . . . . .	111	Terminal Radio Corporation . . . . .	104
Heintz & Kaufman, Ltd. . . . .	103	Thermador Elec. Mfg. Company . . . . .	92, 93
Henry Radio Stores . . . . .	102	Triplett Elec. Instrument Co. . . . .	118
Hewlett-Packard Co. . . . .	68, 69	Turner Co., The . . . . .	119
Hytron Radio & Electronics Corp. . . . .	73	United Transformer Corporation . . . . .	16
Instructograph Co., The . . . . .	124	Universal Microphone Co. . . . .	117
International Resistance Co. . . . .	86-89	Volpey Crystal Corp. . . . .	94
Johnson Co., E. F. . . . .	76, 77	Vibroplex Co., Inc., The . . . . .	115
Knights Company, The James . . . . .	96	Word Leonard Electric Co. . . . .	55
Macmillan Co., The . . . . .	127	Wile, Eugene G. . . . .	128
Mallory & Co., P. R. . . . .	72	Workshop Associates . . . . .	123
		World Radio Laboratories . . . . .	125





# **National**

**RADIO PRODUCTS**

# **1948**



**NATIONAL COMPANY, INC.**  
**MALDEN, MASSACHUSETTS, U.S.A.**

# 4 Modern Communications Receivers

by

**National**  
EST. 1914

Building communications receivers to the standards set by our experienced engineering department for over two decades, National has prided itself on the performance of its receivers in the specialized markets for which they have been designed.

National post-war receivers incorporate the newest circuit techniques and offer the operator the maximum value per dollar spent.

National standards are upheld in the 1948 receivers shown on these pages.

Your National distributor will have these modern receivers on display at your favorite radio store.

*The Finest*

NEW  
HRO-7

Known and used by hams the world over for 13 years, the old HRO now has a new successor — the HRO-7 — incorporating every one of its strong points and adding a number of modern refinements. Still present is excellent signal noise ratio and image rejection.


Brand new features include: automatic adjustable-threshold noise limiter; stabilized voltage supply for new high frequency oscillator; tone switch; accessory connector socket; and radio-phonograph switch.

Special improvements have been added, such as slide-rule type calibration on coil

sets and lever-type handles to facilitate coil changing. The HRO-7 is housed in a streamlined gray cabinet with matching speaker.

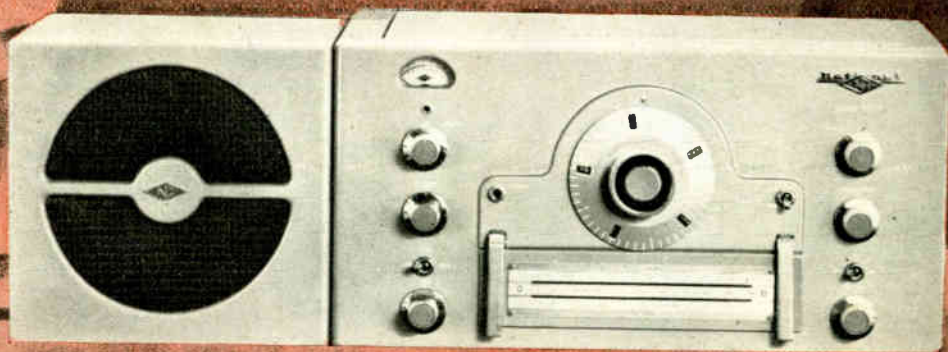
#### FEATURES:

- Frequency Range of 50 to 430 and 480 to 30,000 KC.
- AM phone and code reception with maximum bandwidth spread.
- Accessory Connector Socket.
- New automatic noise limiter with variable threshold.
- 5 position wide range crystal filter with phasing control.



HRO-7 complete with standard coils for 1.7 to 30 MC. coverage, power supply and 8" speaker... Amateur Net \$311.36.

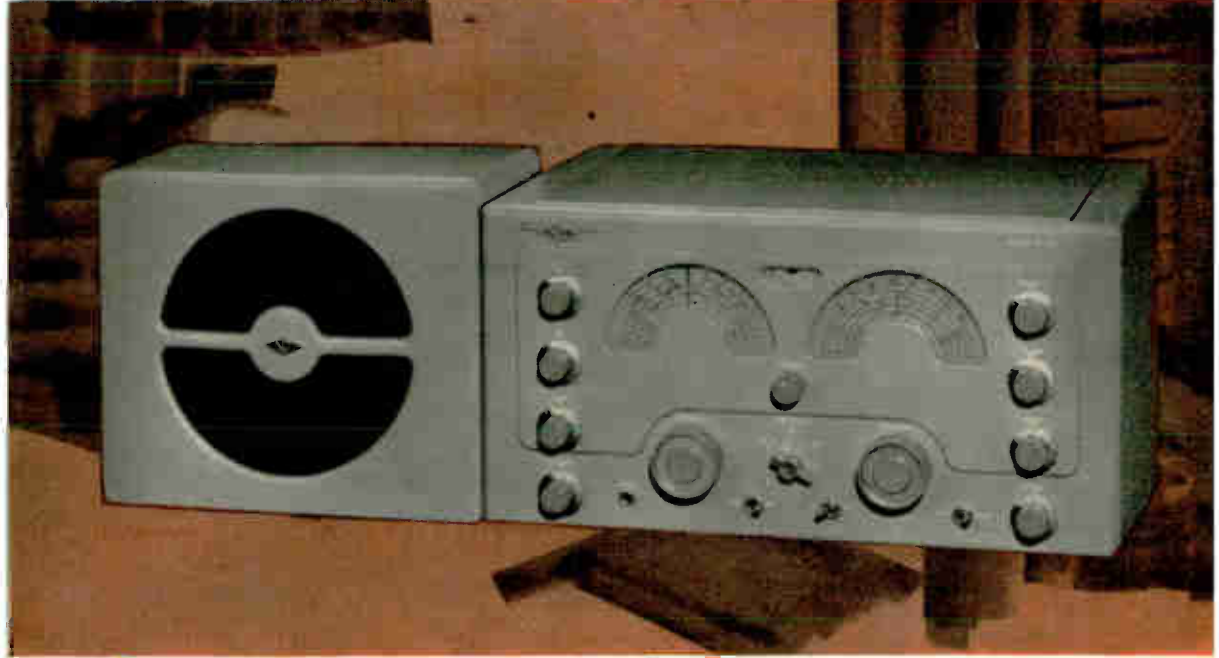HRO-7C Deluxe Receiver Combination, Black Wrinkle Finish, Mounted in Table Rack 29 inches high. Amateur Net... \$358.50



**NC-183**

Newest in National's line of communications receivers is the band-switching NC-183, covering 0.54 to 31 Mc. plus the 6 meter band. Two r.f. amplifier stages provide excellent image rejection. National's latest crystal filter and automatic adjustable threshold double-diode noise limiter circuits are incorporated in the NC-183.

Adjustable sensitivity control for "S" meter operation on either c.w. or 'phone is a feature of this receiver. Stabilized voltage regulator circuits make the NC-183 an excellent performer on the highest frequencies. A push-pull audio output stage with separate 10" speaker allows excellent fidelity of output. These, plus other features, combine to make the NC-183 a really "hot" receiver. It will become a favorite with those stations that specialize in digging DX out of the background.

Supplied for 115 volts 50/60 cycle AC operation — easily adapted to 230 volts.

Amateur Net Price (complete with 10" speaker) . . \$269.00

**HFS**


An up-to-date successor to the famous National 1-10, the HFS is a new v.h.f. superheterodyne receiver with a super-regenerative second detector. The frequency range of the HFS is 27 to 250 mc., continuous coverage with six sets of coils.

The model HFS is capable of receiving CW and AM or FM signals, and is readily adaptable to portable or mobile operation. An antenna trimmer control is conveniently located on the front panel.

The HFS is extremely versatile in v.h.f. operation for an i.f. output jack is incorporated, permitting it to be used as a converter in conjunction with any conventional superhet receiver which tunes 10.7 mc. As a converter, the HFS and superhet combination results in dual conversion type superheterodyne operation with all its advantages, including excellent image rejection at all frequencies from 27 to 250 mc.

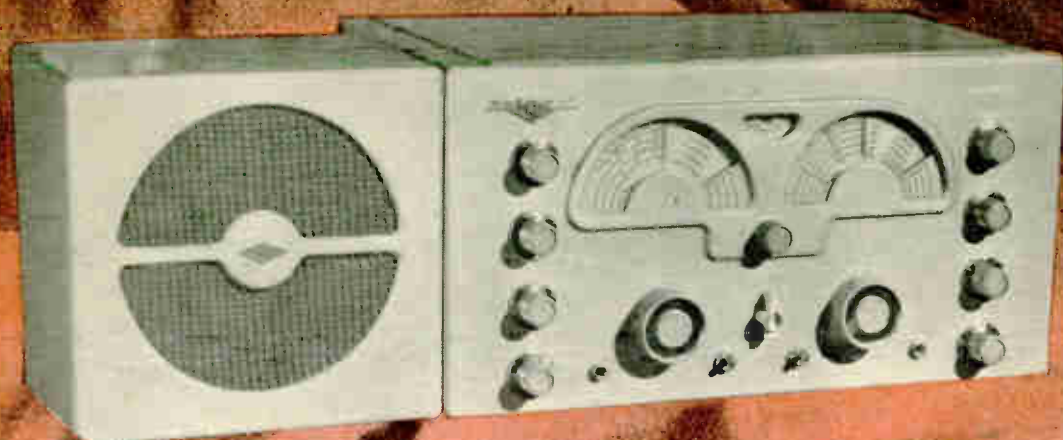See your National Distributor for Amateur Net Price.





**National  
NC-173**

A new and versatile receiver, popularly priced, the new NC-173 has received favorable comment on the ham bands from operators who have found it stepped up their percentage of successful QSO's.

The sensitivity and stability of the NC-173 will not only increase your traffic, but will add much to your operating pleasure.

**OUTSTANDING FEATURES:**

- Frequency Coverage from 540 KC. to 31 MC. plus 48-56 MC.
- Calibrated Amateur Bandsread on 6, 10-11, 20, 40 and 80 meter bands.
- 5 Position Wide Range Crystal Filter.
- Double-Diode Automatic Noise Limiter for Both Phone and C.W. Reception.
- A.V.C. for both Phone and C.W. Reception.
- S Meter with Adjustable Sensitivity for Phone and C.W.
- A.C. Powered — 110/120 or 220/240 volts, 50/60 Cycle. Amateur Net (with speaker)..... **\$189.50**

**The New  
NC-57**


To meet the needs of the many hams who have asked for a sensitive, first-rate bandswitching receiver in the lower price bracket, complete with speaker and power supply in one cabinet, the National Company has developed the brand new NC-57.

Although moderate in price, this little receiver incorporates features usually found in the more expensive models. Excellent tone quality, sensitivity, selectivity and high signal-to-noise ratio afford a level of performance which will be appreciated by any operator. A superb receiver for the beginner, the NC-57 will be found ideal as a standby in any amateur station.

**FEATURES:**

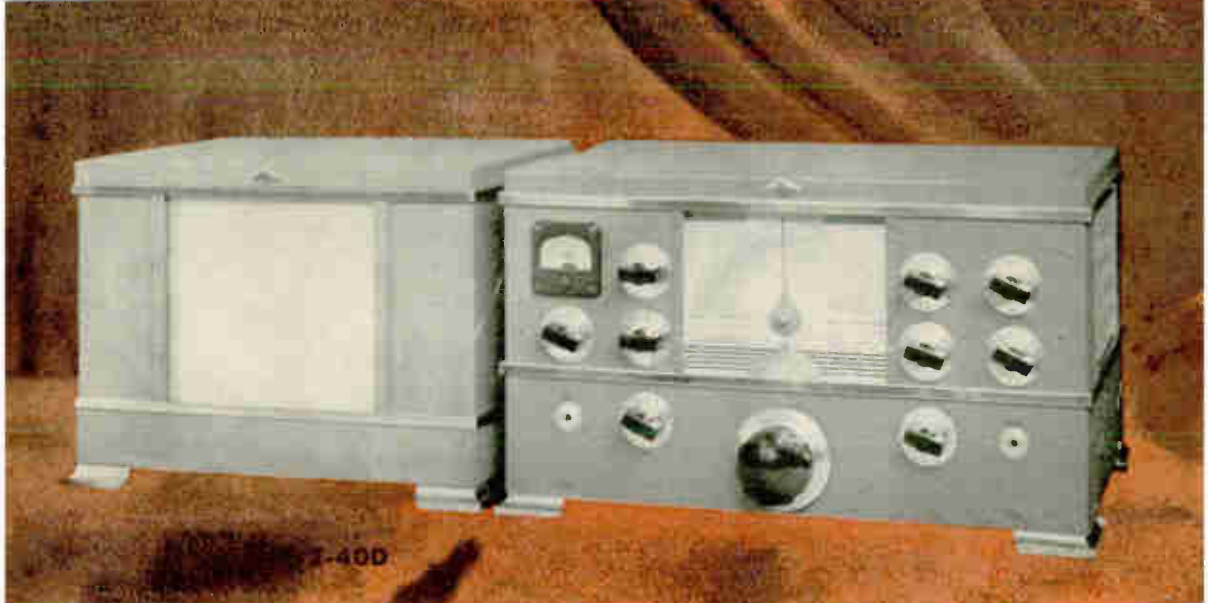1. Continuous frequency coverage from 550 kc to 55 mc. Bandswitching in 5 ranges. Bandsread tuning at any frequency.
2. Seven tube superheterodyne (plus rectifier and voltage regulator).
3. Automatic Noise Limiter.
4. Built-in loudspeaker and A.C. power supply.
5. R. F. stage with panel controlled antenna trimmer.
6. Operates from 105-130 volts, 50-60 cycles A.C. (Provision for battery operation.)
7. Housed in a streamlined gray cabinet. Amateur Net..... **\$89.50**





**The NC-2-40D**

For hams who appreciate engineering, the NC-2-40D will be a thoroughly satisfying possession. Used by airlines and communications companies throughout the world, the NC-2-40D has become famous for its ability to pick up weak signals, and its fine stability.

A 10" speaker and a hi-fidelity push-pull audio system afford tone quality that will please the most critical operator. A series valve noise limiter minimizes noise pulses.

This is a receiver for the ham who demands superb performance.

**FEATURES:**

- Frequency Coverage from 490 to 30,000 kc. Four Amateur Bands (10-11, 20, 40 and 80 meters) with uniform band-spread.
- 8 Watts of undistorted audio.
- 5 Position wide range Crystal Filter.
- Single control for band changing and tuning.
- Temperature Compensation.
- Amateur Net (with 10" speaker) . . . . . \$241.44

**National NC-46**

The National NC-46 is a communication-type A.C.-D.C. receiver of exceptional performance and unique design. Hams and SWLs hoving only D.C. available have found the NC-46 a most capable performer.

Many vessels of the Boston and Gloucester fishing fleets have this receiver aboard for entertainment while at sea, and as a supplement to their ship-to-shore radiotelephones.

In the lower price brackets the NC-46 is the foremost "quality" receiver on the market today.

The loudspeaker is housed in a separate matching cabinet.

**FEATURES:**

- Continuous frequency coverage from 540 Kc to 30 mc. Band-spread tuning at any frequency.
- Nine tube superheterodyne (plus rectifier).
- Automatic Noise Limiter.
- Operates from 105-130 Volts A.C. or D.C.
- Push-pull audio stage delivers 4 watts to speaker.
- Easy to read, slide-rule type dial.
- Amateur Net (with speaker) . . . . . \$107.40



# Modern Radio Components

by



National radio components have been standardized in radio circuits for many years. They have been voted the favorite brand by thousands of amateurs and the National NC signature has become a guarantee of quality.

Listed in these few pages are typical National products. National's 1948 complete catalog of


radio products, available soon, will feature new items, designed for present-day applications. In addition, hundreds of components will be listed and recognized as repeat performers by the designer or builder of radio equipment.

Get your copy of the new National catalog from distributor or write direct to factory.

## NEW NATIONAL MULTI-BAND TANK
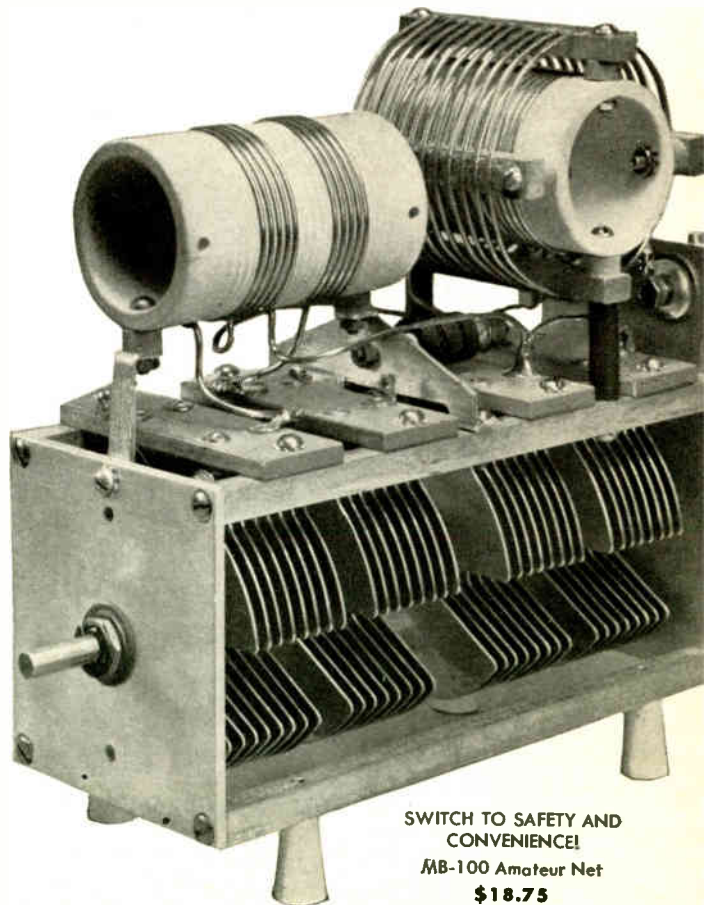
### FEATURES:

- Tunes amateur bands from 80 to 10 meters with single 180° rotation of capacitor from front-of-panel.
- Link pick-up coil matches impedances up to 600 ohms.
- Split-stator capacitor rated at 1500 volts peak.
- Input 100 watts for push-pull or balanced single-ended operation.
- Dimensions 7½" long—7" high—3" wide.
- Rugged construction with ceramic insulation.



SWITCH TO SAFETY AND  
CONVENIENCE!

MB-100 Amateur Net

\$18.75

# NATIONAL


## DIRECT CALIBRATION DIALS

Supplementing National's Famous ACN Dial — A Whole New Line of Dials Designed for Every Amateur's Requirements. Each one incorporates the noted Velvet-Vernier Mechanism, providing smooth action and no backlash.

ACN Amateur Net.....\$3.30


With the introduction of the ICN, SCN and MCN dials, National has recognized and met the requirements of the amateur for a versatile line of dials for every size and shape of rig. All of these dials embody the same 5:1 drive ratio Velvet-Vernier mechanism that has made the ACN dial the standard of comparison among constructors everywhere. No other line of dials is so complete or permits such precision tuning.

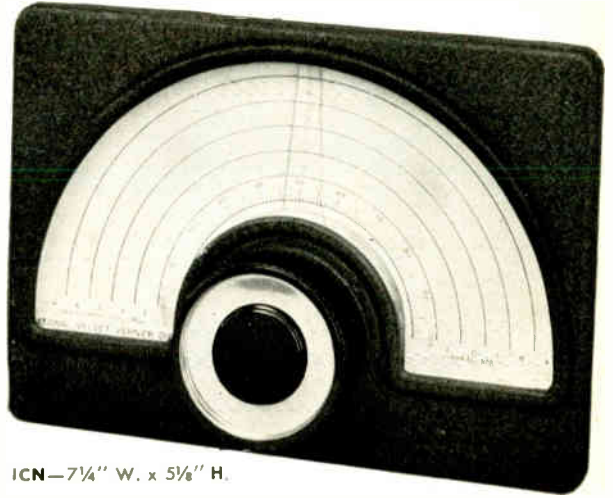For complete line see National 1948 catalog




ICN—7¼" W. x 5½" H.

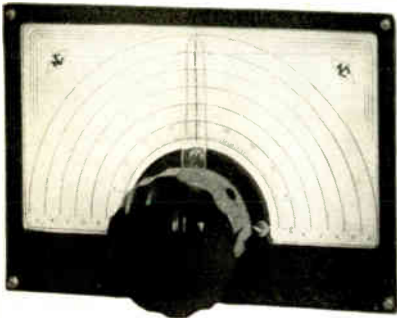The ICN dial meets those hundreds of requests from amateurs the world over for an illuminated ACN dial. Two dial light brackets are mounted on the top rear corners of the dial and provide efficient and even illumination on all bands. The dial scale has been blanked out in semi-circular shape to prevent shadow casting. Dial scales are the same as those on ACN dial. Amateur Net.....\$6.00




ACN  
7¼" W.  
5" H.

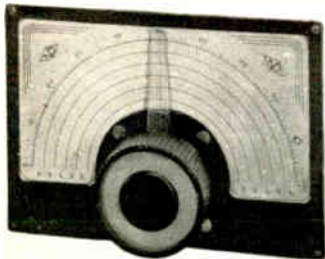The SCN dial provides the same dial scales as the ACN dial but in a reduced size. It is used where economy of panel-mounting space is desirable and where a smaller dial would be out of proportion with the size of the panel. A truly professional appearance can now be given your rig. Amateur Net. ....\$3.00



SCN  
6¼" W.  
4¾" H.

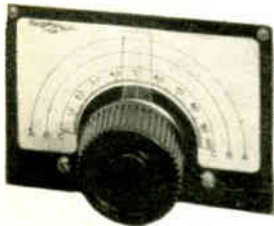The MCN dial has been scaled down to lend itself ideally to mobile installations and small converters and tuners. It may also be mounted on the standard 3-7/32" rack panel where such mounting may be desirable. The dial provides three calibrating scales and a 0-100 logging scale. On the rear side of the dial, (rear of panel) the mechanism extends ¼" below the dial frame. Amateur Net.....\$2.70




MCN  
3¾" W.  
2¼" H.

See this complete line of dials and other precision National parts at your nearest National distributor. Write to us direct for any information you may desire.





Type N

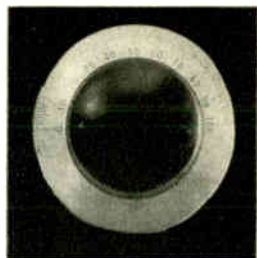

Type AM

# NATIONAL VELVET VERNIER DIALS




Type B

The four-inch N and AD Dials have engine divided and die stamped scales respectively. The N Dial has a decimal vernier; the AD Dial employs a pointer. The planetary drive has a ratio of 5 to 1, and is contained within the body of the dial. 2, 3, 4 or 5 scale. Fits 1/4" shaft. Specify scale.

N Dial . . . . . \$4.50 Amateur Net  
AD Dial . . . . . \$2.84 Amateur Net

The original "Velvet Vernier" mechanism is now available in a metal skirted dial 3" in diameter. The planetary drive has a ratio of 5 to 1. It is available with 2, 3, 4, 5 or 6 scale and fits 1/4" shaft.

AM Dial . . . . . \$2.25 Amateur Net

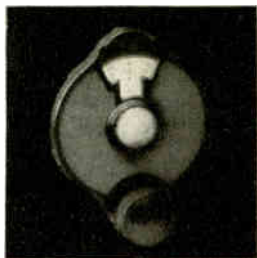

Type BM

## "VELVET VERNIER" DIAL, TYPE B


has a compact variable ratio 6 to 1 minimum, 20 to 1 maximum drive that is smooth and trouble free. The case is black bakelite. 1 or 5 scale. 4" diam. Fits 1/4" shaft.

B Dial . . . . . \$2.70 Amateur Net  
BM Dial, 3" diam. . . . . \$2.10 Amateur Net

DIAL SCALES			
SCALE	DIVISIONS	ROTATION	DIRECTION OF CONDENSER ROTATION FOR INCREASE OF DIAL READING
1	0-100-0	180°	Either Counter Clockwise Clockwise Clockwise Clockwise Counter Clockwise
2	0-100	180°	
3	100-0	180°	
4	150-0	270°	
5	200-0	360°	
6	0-150	270°	

SPECIFY DIAL SCALE WHEN ORDERING

## NON-VERNIER DIALS

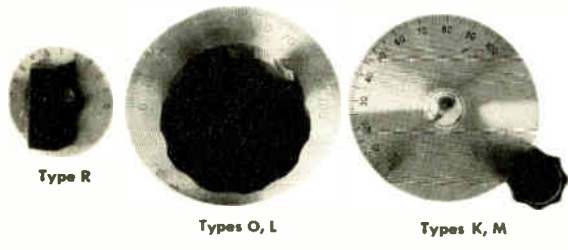

Type R

Types O, L

Types K, M

TYPE O \$1.00 3 1/2" diameter	TYPE L \$1.95 5" diameter
	TYPE M \$2.25 5" diameter
TYPE R \$.51 1 3/8" diameter	TYPE K \$1.50 3 1/2" diameter

R Dial scale 3 only but marked 10-0; O, K, L, M, scale 2. All fit 1/4" shafts.

## KNOBS



HRK

HRP-P

HRP

HRK (Fits 1/4" shaft) . . . . . \$ .57  
Black bakelite knob 2 3/8" diam.

HRP-P (Fits 1/4" shaft) . . . . . \$ .24  
Black bakelite knob 1 1/4" long and 1/2" wide. Equipped with pointer.

HRP . . . . . \$ .18  
The type HRP knob has no pointer, but is otherwise the same as the knob above.

The HRT is a new plastic tuning knob with a chrome plated appearance circle. The HRT knob fits a 1/4" dia. shaft and is 2 1/8 in. dia. Black or Gray.

HRT Knob . . . . . Amateur Net \$ .75  
The HRS Knobs are a new plastic knob with a 1 3/8" dia. chrome plated skirt. HRS Knobs fit 1/4" dia. shafts. Three types are available as follows: Black or Gray.

HRS-1 Knob ON-OFF through 30° rotation . . . . . \$ .51

HRS-2 Knob 5-0-5 through 180° rotation . . . . . \$ .51

HRS-3 Knob 0-10 through 300° rotation . . . . . \$ .51



HRT

## ACCESSORIES

ODL . . . . . \$ .33

A locking device which clamps the rim of O, K, L and M Dials. Brass, nickel plated.

ODD . . . . . \$ .42

Vernier drive for O, L, or other plain dials.

SB (Fits 1/4" shaft) . . . . . \$ .18

A nickel plated brass bushing 1/2" in diam.

RSL (Fits 1/4" shaft) . . . . . \$ .57

Rotor Shaft Lock for TMA, TMC and similar condensers.



ODL

ODD

RSL

SB




HRS-1

HRS 2

HRS-3




# NATIONAL TRANSMITTING CONDENSERS

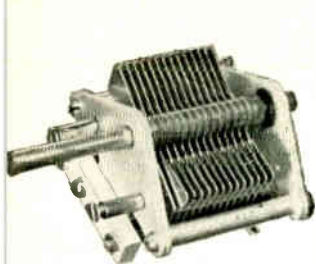

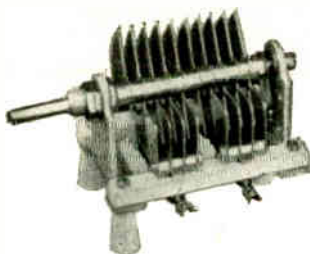**TMS**

Maximum capacities of TMS series range from 35 mmfd. to 300 mmfd. Split-stator models available.



**TMH**

Maximum capacities of TMH series range from 35 mmfd. to 100 mmfd. Split-stator models available.



**TMK**

Maximum capacities of TMK series range from 35 mmfd. to 250 mmfd. Split-stator models available.

Series	Maximum Capacity	Minimum Capacity	Length	Air Gap	Peak Voltage	No. of Plates	Catalog Symbol	Net Price
<b>TMS</b>	See Catalog	See Catalog	3"	.026" .065"	1000v. 2000v.	See Catalog	See Catalog	See Catalog
<b>TMH</b>	See Catalog	See Catalog	3 3/4" 5 1/8"	.085" .180"	3500v. 6500v.	See Catalog	See Catalog	See Catalog
<b>TMK</b>	See Catalog	See Catalog	2 3/8" 4 1/8"	.047"	1500v.	See Catalog	See Catalog	See Catalog
<b>TMC</b>	See Catalog	See Catalog	3" 6 3/4"	.077"	3000v.	See Catalog	See Catalog	See Catalog
<b>TMA</b>	See Catalog	See Catalog	4 9/16" 12 7/8"	.171" .359"	6000v. 12,000v.	See Catalog	See Catalog	See Catalog
<b>TML</b>	See Catalog	See Catalog	8 5/16" 18 1/16"	.469" .719"	15,000v. 20,000v.	See Catalog	See Catalog	See Catalog




**TMC**

Maximum capacities of TMC series range from 50 mmfd. to 300 mmfd. Split-stator models available.



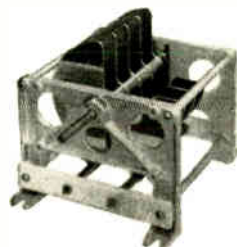**TMA**

Maximum capacities of TMA series range from 50 mmfd. to 300 mmfd. Split-stator models available.



**TML**

Maximum capacities of TML series range from 50 mmfd. to 500 mmfd. Split-stator models available.

# NATIONAL NEUTRALIZING CONDENSERS



**NC-800A**


**NC-800A** — The NC-800A disk-type neutralizing condenser is suitable for the RCA-800, 809, 35TG, HK-54, 5514 and similar tubes. It is equipped with a clamp to lock its setting. See Catalog for capacity and air gap for different settings.

**NC-75** — For 811, 812 etc.

**NC-150** — For HK354, 250TH etc.


**NC-500** — For WE-251, 450TH, 450TL, 750TL etc.

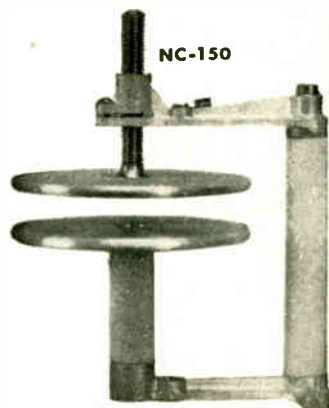*Disks are aluminum, insulation steatite.*



**NC-150**

# NATIONAL I.F. TRANSFORMERS

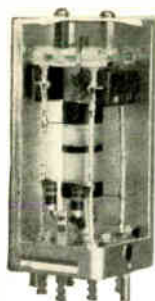


**IFL, IFM, IFN** and **IFO** transformers operate at 10.7 Mc. and are designed for use in AM or FM Superheterodyne receivers. The transformer cans are 1 3/8" square and stand 3 1/8" above the chassis.

Two 6-32 spade bolts are provided for mounting.

The **IFO** transformer is a 10.7 Mc. FM discriminator transformer of the ratio type and is linear over a band of  $\pm$  100 kc.

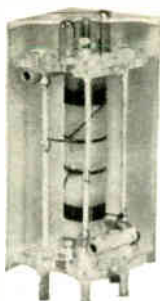- IFL FM Discriminator.....\$6.90 Net
- IFM IF Transformer.....\$6.45 Net
- IFN IF Transformer.....\$6.45 Net
- IFO FM Ratio Discriminator...\$6.98 Net



The **IFN** transformer is a 10.7 Mc. i.f. transformer with a 100 Kc. pass band at 1.5 db attenuation. Approximate stage gain of 30 is obtained with IFN transformer and 6SG7 tube.

The **IFL** transformer is a 10.7 Mc. FM discriminator transformer suitable for use in conventional FM receiver discriminator circuit and is linear over a band of  $\pm$  100 Kc.

The **IFM** transformer is a 10.7 Mc. i.f. transformer with a 150 Kc. bandwidth at 1.5 db. attenuation. Approximate stage gain of 30 is obtained with IFM Transformer and 6SG7 tube.



15 Mc. i.f. transformers suitable for ultra high frequency superheterodynes. They are made in two models with and without variable coupling. Approximate stage gain of 10 is obtained with **IFJ**


or **IFK** transformer and 6AB7 tube.

**IFJ**, with variable coupling.....\$8.25  
Amateur Net

**IFK**, with fixed coupling.....\$7.25  
Amateur Net

**N.B.F.M.** Transformer — Type SA4842, as described in Nov. 47 QST. Amateur Net.....\$4.50

## NATIONAL SMALL PARTS

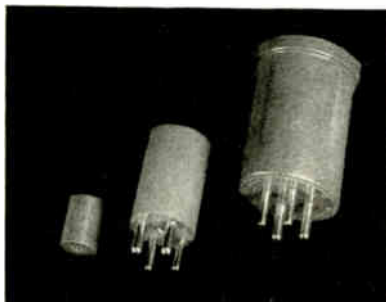

### COIL FORMS

**XR-1**, Four prong .....\$33

**XR-2**, without prongs .....\$24

Molded of R-39, permitting them to be grooved and drilled. Coil form diameter 1", length 1 1/2".

**XR-3**, molded of R-39. Diameter 3/8", length 3/4". Without prongs \$21


**XR-4**, Four prong..\$.51    **XR-5**, Five prong..\$.51    **XR-6**, Six prong..\$.60

Molded of R-39, permitting them to be grooved and drilled. Coil form diameter 1 1/2", length 2 1/4". A special socket is required for the six-prong form.

### ADJUSTABLE MICA CONDENSER →

**M-30** — Type **M-30** is a small adjustable mica condenser with a maximum capacity of 30 mmf. Dimensions 1 1/16" x 1/16" x 1/2". Isolantite base. This condenser has found many uses in innumerable electronic circuits.....Amateur Net \$2.22

### GRID & PLATE GRIPS

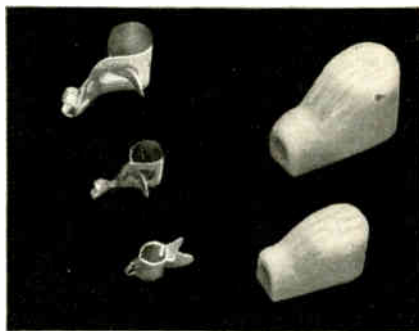

National Safety Grid and Plate Caps have a ceramic body which offers protection against accidental

contact with high voltage caps on tubes.

National Grid and Plate Grips provide a secure and positive contact with the tube cap and yet are released easily by a slight pressure on the ear.

Type 12, for 9/16" Caps.....\$0.06

Type 24, for 3/8" Caps.....\$0.03


Type 8, for 1/4" Caps.....\$0.03

**SPP-9**—Ceramic insulation. Fits 9/16" diameter \$2.27


**SPP-3**—Ceramic insulation. Fits 3/8" diameter \$2.21
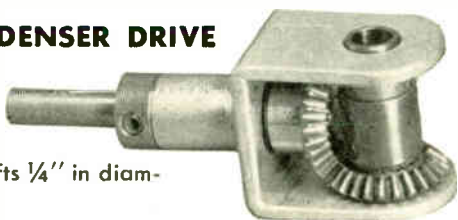
### ANGLE CONDENSER DRIVE

This sturdy angle drive has many uses and will drive single or dual shafts 1/4" in diameter.



**ACD-1** Amateur Net...\$3.75

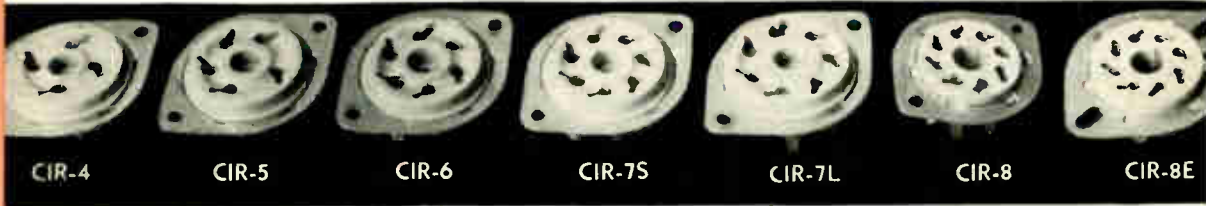


**Type CIR Sockets** feature low-loss steatite insulation, a contact that grips the tube prong for its entire length, and a metal ring for six position

mounting.  
 CIR 4, 5, 6, 7S, 8, 8E..... Amateur Net \$ .27  
 CIR 7L..... Amateur Net \$ .33
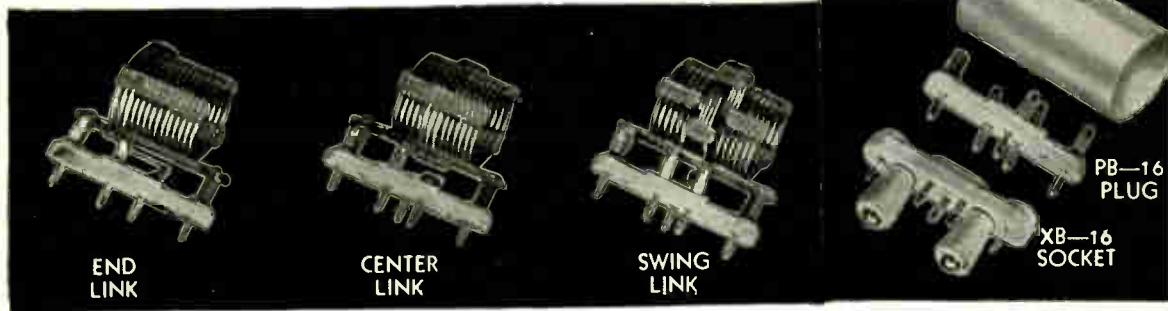
## EXCITER COILS AND FORMS

**AR-16**, Coils — Any type (see table). Include **PB-16** Plug as illustrated....\$1.25  
**SMH**, Swivel mounting hardware Amateur Net..... \$ .10



### TYPE AR-16 (Air Spaced)


These air-spaced coils are suitable for use in stages where the plate input does not exceed 50 watts and are available in the sizes tabulated. Capacities listed will resonate the coils at the low frequency end of the band and include all stray circuit capacities. All have separate link coupling coils and all fit the XB-16 Socket.

The XR-16 Coil Form also fits the PB-16 Plug and XB-16 Socket. It has a winding diameter of 1 1/4" and a winding length of 1 3/4".

Band	End Link	Cap Mmf	Center Link	Cap Mmf	Swinging Link	Cap Mmf
6 meter	AR16-6E	25	AR16-6C	25		
10 meter	AR16-10E	20	AR16-10C	20	AR16-10S	25
20 meter	AR16-20E	26	AR16-20C	26	AR16-20S	40
40 meter	AR16-40E	33	AR16-40C	33	AR16-40S	55
80 meter	AR16-80E	37	AR16-80C	37	AR16-80S	60

**XR-16**, Coil Form only . . . \$ .42  
**PB-16**, Plug-in Base Only . . \$ .45  
**XB-16**, Plug-in Socket only. \$ .45

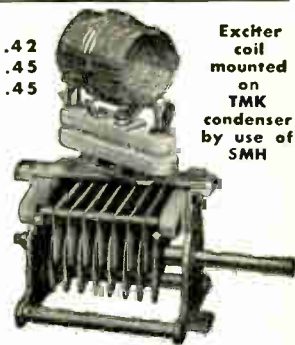
Exciter coil mounted on TMK condenser by use of SMH


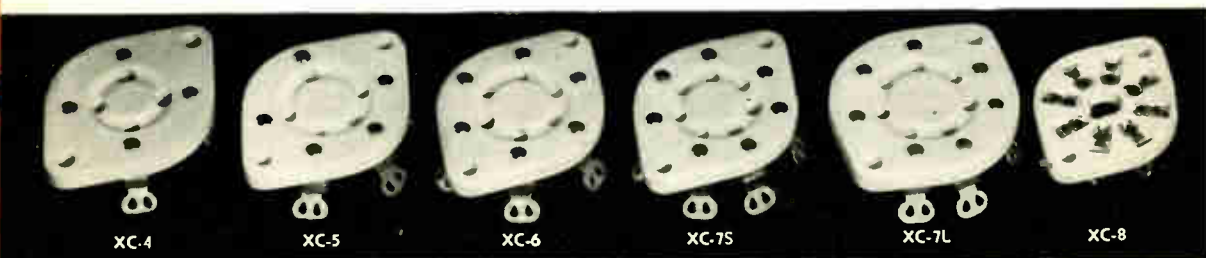
## XC SERIES SOCKETS

National wafer sockets have exceptionally good contacts with high current capacity together with low loss steatite insulation. All types have a locating groove to make tube or coil form insertion easy. These sockets are ideal in experimental layouts where coil or tube sockets are called for.

**XC-4**..... Amateur Net \$ .36  
**XC-5**..... Amateur Net \$ .39  
**XC-6**..... Amateur Net \$ .42  
**XC-7S**..... Amateur Net \$ .45  
**XC-7L**..... Amateur Net \$ .45  
**XC-8**..... Amateur Net \$ .39



# TRANSFORMERS FOR EVERY APPLICATION

**LINEAR  
STANDARD**



**HYPERM  
ALLOY**



**ULTRA  
COMPACT**



**COMMERCIAL  
GRADE**



**OUNCER**




**SUB  
OUNCER**



**SPECIAL  
SERIES**



**VARIABLE  
INDUCTOR**

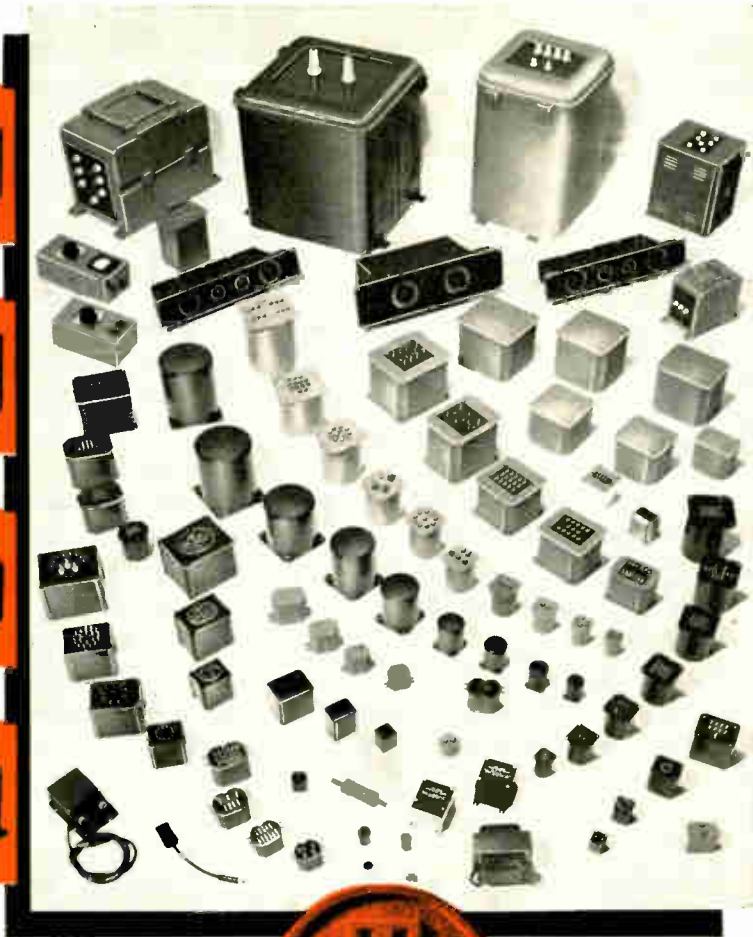

*Foremost Manufacturers of Transformers to the Electronic Industry*

*United Transformer Corp.*

150 VARICK STREET

NEW YORK 13, N. Y.

EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y.

CABLES: "ARLAB"



**LISTEN, HAM OPERATORS—  
2 OUT OF 3 ELECTRONIC  
ENGINEERS PREFER AND USE  
**BURGESS  
BATTERIES****

**Use the Brand the Experts Choose—See  
Your Local Distributor—Buy Burgess!**

Illustrated on this page are only a few of the many battery types popular with amateur radio operators. Your local Burgess distributor has fresh stocks for all your needs.



**No. 10308.** 45 volts. Popular heavy-duty type. Taps at —, +22½, +45. With spring clips or 3-hole socket. Size 8½" x 4½" x 7¼".



**No. Z30.** Popular small size 45 volt "B" battery. Top quality for long economical service. Plug-in socket. Size 3½" x 2½" x 4½".



**No. 4F.** Most popular economy size 1½ volt "A" battery. Plug-in socket. Gives long dependable service. Rated 40 watt hours. Size 2¼" x 2¼" x 4¾".



**No. 2308.** 45 volt "B" battery in smaller size. Taps at —, +22½, +45. Spring clip or plug-in terminals. Long service life. Size 8½" x 2½" x 7¾".



**No. F4PI.** Popular 6 volt plug-in "A" battery. Universal type. Gives dependable, economical service. Size 2½" x 2½" x 4¼".



**No. 4156.** 22½ volt "B" battery. Equipped with screw terminals. Small and compact with long service life. Size 3½" x 2¼" x 2½".

### **New Honors for Burgess Quality**

Burgess quality is recognized by the recent award of the Certificate of Merit for 1947 by the New York Museum of Science and Industry in recognition of outstanding achievements in the development of improved dry batteries for a wide range of applications. Burgess is the only dry battery manufacturer to receive this honor.

Burgess Batteries were important equip-

ment on Operation Highjump in the Antarctica; and Burgess Batteries left at Little America seven years before operated perfectly in service on this last expedition.

The same careful engineering and laboratory-controlled manufacture in Burgess Batteries for amateur radio assures ham operators of long, dependable service.


**BURGESS BATTERY COMPANY**  
DEPT. RAH-8  
FREPORT, ILLINOIS



# Perfection

**COVERAGE**

**Mc. AM • FM • CW**

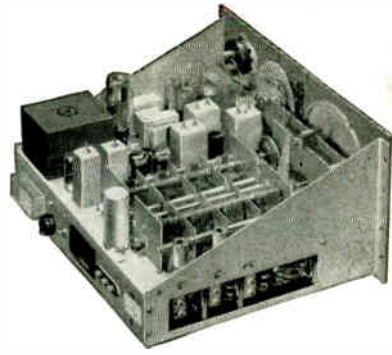

operation. MAIN TUNING and BAND-SPREAD knobs are mounted coaxially, focusing the tuning functions in a single precision-built unit. BAND-SWITCH and VOLUME are located at either side of the main dial. Auxiliary controls such as CRYSTAL PHASING, SENSITIVITY, etc., are logically placed so that those most frequently used are in the most accessible positions. Hallicrafters new system of color coding makes it possible for the entire family to enjoy this fine receiver. The normal control positions for standard broadcast reception are indicated by tiny red dots while FM adjustments are in green.

The main tuning knob is provided with a precision vernier scale which is separately illuminated through a small window in the one-piece Lucite main dial housing. The main tuning dial is calibrated in megacycles and is marked with channel numbers in the new FM band of 88 to 108 megacycles. The bandspread dial is calibrated for the amateur 3.5, 7, 14, 28, and 50 megacycle bands. An additional logging scale is provided on this dial for use in other ranges. The small locking knob mounted coaxially with the main and bandspread tuning knobs permits either to be rotated freely while holding the other firmly in position.

## AMATEURS SAY: "Unsurpassed CW performance"

IN ADDITION to its many new features the SX-42 continues all of the time-tried advantages characteristic of Hallicrafters top models. Freedom from drift and maximum stability are provided by temperature compensation and the use of a type VR-150 voltage regulator tube. A crystal filter circuit combined with variable intermediate frequency channel width offers six different degrees of selectivity on the four lower bands (to 30 megacycles). CRYSTAL

PHASING, CW PITCH, SENSITIVITY, and four-position TONE control for LOW, MED, HI FI, and BASS are all conveniently placed on the front panel as are RECEIVE/STANDBY, NOISE LIMITER, and AVC switches.

The beauty and modern functional styling of this new receiver are self evident. Without in any way detracting from the "precision instrument" appearance which characterizes fine communications equipment, Hallicrafters designers have succeeded in creating a receiver which is not out of place in the most luxurious surroundings. The rich deep gray of the panel, satin chrome "airdized" top, and light gray lettering with touches of red and green combine with the precision-tooled controls and light translucent green of the illuminated dials and meter in a harmoniously integrated whole.

### R-42 SPEAKER

This is the first speaker of its size to offer the splendid advantages of the bass reflex principle. Heretofore the famous Jensen-originated bass reflex reproduction has been available only in large cabinet speakers. Now in this sleek, highly functional design, matching the new line of Hallicrafters receivers, the bass reflex feature is available in a compact speaker that offers a new high quality of reproduction. The R-42 was designed as a companion

piece to the SX-42 receiver but it may be used with any other receivers such as the SX-28 and the SX-43. The speaker size is 8 inches. Two-position switch on front panel for communications or high fidelity reception. Terminals on rear for 500-ohm line. R-42 size: 12½ in. deep, 11¾ in. high, 17 in. wide.



R-42 SPEAKER . . . . . \$29.50

**DIMENSIONS:** Model SX-42. Cabinet only, 20 inches wide by 9¾ inches high by 16 inches deep. Overall, 20 inches wide by 10¼ inches high by 18 inches deep.

**WEIGHT:** Model SX-42. Receiver only, approximately 52 pounds. Packed for shipment, approximately 65 pounds. Model B-42, adjustable base, packed for shipment, approximately 5 pounds.

**hallicrafters RADIO**

THE

SX-43

OFFERS SIX BANDS:

All the essential amateur  
frequencies from 540 kc. to 108 Mc.



**\$169.50**

Amateur Net


**T**HE Model SX-43 is designed for the discriminating amateur who demands excellent performance and wide frequency range at a medium price. This new member of the Hallicrafters line offers continuous coverage from 540 kilocycles to 55 megacycles and has an additional band from 88 to 108 megacycles. AM reception is provided on all bands except band 6, CW on the 4 lower bands and FM on frequencies above 44 Mc. In the band of 44 to 55 Mc., wide band FM or narrow band AM just right for narrow band FM reception is provided.

One stage of high gain tuned RF and a type 7F8 dual triode converter assure an exceptionally good signal-to-noise ratio. Image ratio on the AM channel on band 5 (44 to 55 Mc.) is excellent as the receiver is used as a double superheterodyne on this band. The new Hallicrafters dual IF transformers provide a 455 kilocycle IF channel for operating frequencies below 44 megacycles and a 10.7 megacycle IF channel for the VHF

bands. Two IF stages are used on the 4 lower bands and a third stage is added above 44 megacycles. Switching of IF frequencies is automatic. The separate electrical band-spread dial is calibrated for the amateur 3.5, 7, 14, and 28 megacycle bands and in addition is used to tune the 44 to 55 and 88 to 108 Mc. VHF bands, the main tuning gang being disconnected on these frequencies.

Every important feature for excellent communications receiver performance is included in the SX-43. The crystal filter and expanding IF channel provide four variations of selectivity on the lower frequency bands. Temperature compensation for freedom from drift, series type noise limiter, permeability-adjusted "microset" inductances in the RF circuits, separate RF and AF gain controls, color coding for simplified operation by the entire family, beautiful styling, all destine this new Hallicrafters receiver for top place in the moderate price field.



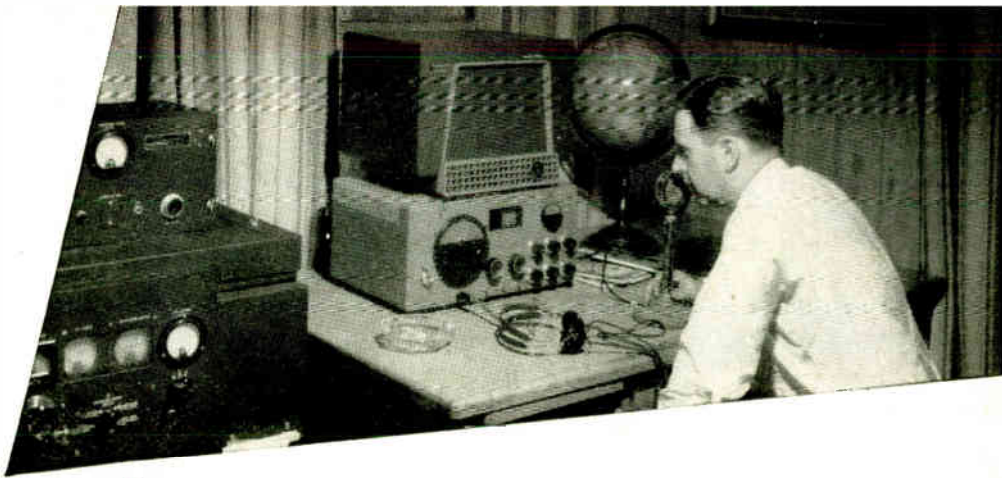

# Everything **THE HAM ASKS FOR** in a medium price receiver

**OUTSTANDING FEATURE:** Wide band FM, AM or narrow band FM on 44-55 megacycles.

**CONTROLS:** BAND SELECTOR, TUNING, BANDSPREAD, TONE, RECEIVE/STANDBY, NOISE LIMITER, CRYSTAL PHASING, SELECTIVITY, SENSITIVITY, VOLUME AND POWER OFF, RECEPTION, CW PITCH.

**EXTERNAL CONNECTIONS:** Antenna connections for doublet or single wire. Input impedance matches 300-ohm line except on broadcast band which is designed for single wire antenna. Speaker terminals for 500 or 5000 ohms. Phone jack on front panel. Phonograph input connector on rear of chassis. Socket for use with external power supply. Remote standby control connections in power socket. Power cord, plug.

**PHYSICAL CHARACTERISTICS:** The cabinet of the Model SX-43 is styled in the new Hallicrafters pattern and is finished in rich satin gray. Panel and chassis may be removed as a unit for servicing without disturbing any con-

## R-44 SPEAKER

Offers for the first time in a professional style cabinet, the advantages of an oval speaker.

The large oval size plus ample baffling give excellent low frequency response. The cabinet proportions and finish provide a perfect match with any communications receivers. Especially designed as a companion unit to the SX-43, but it may also be used with the SX-25, SX-28, and SX-42. The speaker size is 6 x 9 inches. Two-position switch on front panel for communications on high fidelity reception. Terminals on rear for 500 ohm line.

R-44 size: 18½ in. wide by 8½ in. high by 9¾ in. deep . . . . . \$19.50



trols. "Airodized" steel top swings open on full length piano hinge for maximum accessibility. Panel lettering is in light gray with incidental red and green markings for standard and FM broadcast reception. Dials are indirectly illuminated and are a light translucent green.

**TUBES:** 1—6BA6 RF amplifier; 1—7F8 converter-oscillator; 1—6SG7 1st IF amplifier; 1—6SH7 2nd IF amplifier and second converter, band 5 AM; 1—6SH7 3rd IF amplifier (10.7 Mc.); 1—6H6 AM detector and noise limiter; 1—6AL5 FM detector; 1—6SQ7 1st AF amplifier; 1—6J5 beat frequency oscillator or second converter oscillator, band 5; 1—6V6 audio output tube; 1—5Y3 rectifier.

**OPERATING DATA:** The standard Model SX-43 is designed for operating on 105-125 volts, 50/60 cycle alternating current. The universal Model SX-43U may be operated on 110, 130, 150, 220, or 250 volts, 25 to 60 cycles, alternating current. The standard model draws 90 watts at 117 volts. When operated from external batteries the heaters require 3.8 amperes at 6 volts and the plate circuit draws 105 milliamperes at 270 volts.

**DIMENSIONS:** Model SX-43. Cabinet only, 18½ inches wide by 8½ inches high by 12 inches deep. Overall 18½ inches wide by 8¾ inches high by 13 inches deep.

**WEIGHT:** Model SX-43. Receiver only, approximately 35 pounds. Packed for shipment, approximately 45 pounds.

**hallicrafters RADIO**



# S-40A

*—it covers from  
40 kc. to 43 Mc.  
and is called by hams*

**\$89<sup>50</sup>**

**“ONE OF THE GREATEST RECEIVER  
VALUES AVAILABLE”**

**T**HE sensational new S-40A with the finest performance ever presented in the popular price field is housed in a cabinet of true functional design—a completely new conception of receiver beauty and styling.

The Model S-40A incorporates many circuit refinements and features never before available in this price class. The RF section uses permeability adjusted “micro-set” inductances, identical with those in the most expensive Hallicrafters receivers. Automatic noise limiter, temperature compensated RF oscillator, beat frequency oscillator, separate RF and AF gain controls, three-position tone control, separate electrical bandspread, with inertia flywheel tuning, and many other features make this beautiful new receiver an outstanding value.

Overall frequency range—540 kilocycles to 43 megacycles in 4 bands:

- Band 1—540 to 1700 kilocycles
- Band 2—1.7 to 5.35 megacycles
- Band 3—5.35 to 15.7 megacycles
- Band 4—15.7 to 43 megacycles.

Adequate overlap is provided at the ends of all bands.

**CONTROLS:** SENSITIVITY (including “S” meter on/off switch), BAND SELECTOR, VOLUME, TUNING, BANDSPREAD, AVC ON/OFF, CW/AM, NOISE LIMITER ON/OFF, TONE AND AC ON/OFF, PITCH CONTROL, STAND-BY/RECEIVE.

**DIMENSIONS:** Model S-40A. Cabinet only, 18½ inches wide by 8½ inches high by 9½ inches deep. Overall, 18½ inches wide by 9 inches high by 11 inches deep. Model SM-40 Meter. Overall, 5¾ inches wide by 4 inches high by 4½ inches deep.

**WEIGHT:** Model S-40A. Receiver only, approximately 28 pounds. Packed for shipment, approximately 33 pounds. Model SM-40. Meter only, approximately 1¾ pounds. Packed for shipment approximately 3 pounds.

#### MODEL SM-10 “S” METER

This new external “S” meter is available as an accessory and can be easily connected through a special socket on the rear of the receiver chassis. May also be used with other Hallicrafters models such as the S-20R, S-18, etc.






☆ For land - sea - air ☆ communications

**S-51**

## NEW RECEIVER

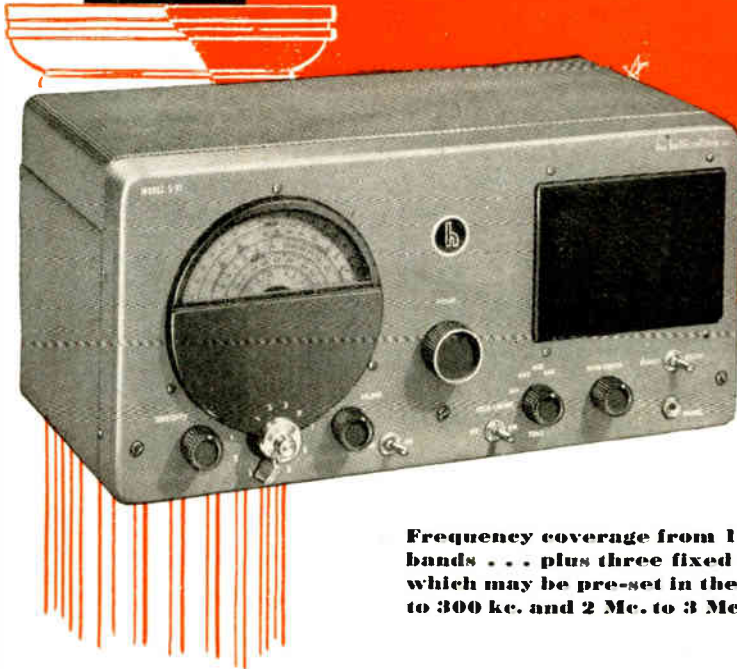

- Low price
- Highly
- ☆ dependable

*Prices on Request*

**Frequency coverage from 132 kc. to 13 Mc. in 4 bands . . . plus three fixed frequency channels which may be pre-set in the range between 200 to 300 kc. and 2 Mc. to 3 Mc.**

**Y**ACHTSMEN, mariners, pilots and all who depend on specialized communications equipment for safe land, sea and air operations will find in the S-51 just what they have been looking for. Covering from 132 kc. to 13 Mc., the S-51 provides reception on all important channels—airport towers, Coast Guard stations, weather stations and other vital communications outlets. Maximum convenience is assured through the use of a directly calibrated main tuning dial and the division of bands so that calling and working frequencies lie in the same band.

Styled to match the balance of the highly functional Hallicrafters line, the S-51 is especially rugged. Precautions have been taken to protect the model against the hazards of salt sea atmosphere. Trimmer condensers are treated to maintain their adjustment, transformers are impregnated and the chassis is heavy cadmium plated to resist the roughest sort of treatment. Temperature compensation for freedom from drift and permeability adjusted "microset" inductances in RF circuits add to the receiver's stability and high quality. Iron cores are used with silver mica capacitors for high stability.

*Two outstanding features set the S-51 well above average:*


**1. VERSATILITY.** The S-51 can be used practically anywhere. Equipped for 110 volt AC/DC operation, provision is made for the addition of power supply combinations permitting operation from either 6, 12 or 32 volt batteries.

**2. FIXED FREQUENCIES.** Besides the four tuning ranges covered by regular tuning controls there are three fixed frequency channels which can be pre-set to be brought in with a flick of the switch. Provision is made for pre-setting on one fixed frequency between 200 to 300 kc. and on two frequencies between 2 Mc. and 3 Mc. Private pilots, who from home or airport want to keep constantly tuned to a certain weather station, sailors and yachtsmen who must keep in regular touch with certain Coast Guard stations and others who depend on fast, regular communications over fixed frequencies, will find the S-51 invaluable in this regard.

In addition to other features the S-51 has a beat frequency oscillator with pitch variable from the front panel; combined a.v.c. and b.f.o. switch; separate r.f. and a.f. gain controls; inertia flywheel tuning and a PM speaker with internal rubber shock mounting.

Ten Tubes Including  
Cathode Ray Tube  
**\$49.50** Amateur  
Net

## SEE WHAT YOU'RE LOOKING FOR

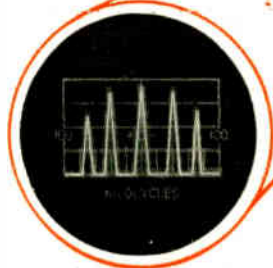

**LOTS MORE QSL'S**  
with the Skyrider Panoramic


**SP-44**

**H**ALLICRAFTERS Skyrider Panoramic, Model SP-44 is actually a "third hand" to help you reach for new horizons in ham radio. You get lots more QSL's with the Hallicrafters Panoramic because you can "see" and "feel" your way over a wide stretch of the radio spectrum. The Panoramic shows not only the received signal but every signal 100 kc. on either side of the received signal . . . provided visual sweepwidth is set at maximum. By making a wide range of radio signals visible a new dimension is added to the field of radio operating. Listed opposite are a few of the things Panoramic enables you to do:

1. Spot frequency modulation or parasitics on an amplitude modulated signal.
2. Measure percentage of modulation and the quality of the signal being transmitted under all conditions.
3. Read signal strength instantaneously, aiding in quickly adjusting the output stages of the transmitter or the field pattern of directional antennas.
4. Check other frequencies against known standards or the receiver calibrations. Any frequency drift can be spotted immediately.
5. Show where and how much to shift frequency to avoid interference once a QSL is under way.

## Precision instruments for VERY HIGH FREQUENCY WORK

**S-37**

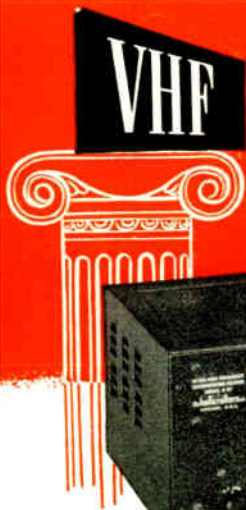

provides sensitivity and selectivity in the range from 130 to 210 Mc. that is in every way comparable to the performance of fine communications receivers on the standard frequencies.

A new pre-loaded gear drive with separate bandsread dial provides ease of tuning, and the entire range of the receiver is covered without band-switching. Two RF stages are used and in conjunction with an intermediate frequency of 16 Mc. assure an amazingly high ratio of image rejection. Hermetically sealed transformers and capacitors make the Model S-37 suitable for use in any climate.


This new receiver again emphasizes Hallicrafters pre-eminence in the commercial production of VHF equipment.

**\$591.75**

Amateur Net

**T**HE Model S-37 has been designed to fill the need for very high frequency equipment with the performance characteristics of Hallicrafters top communications receivers, and a frequency range extending above 200 Mc. Basically similar to the Model S-36A this new receiver incorporates the latest developments in VHF circuit design and

**hallicrafters RADIO**

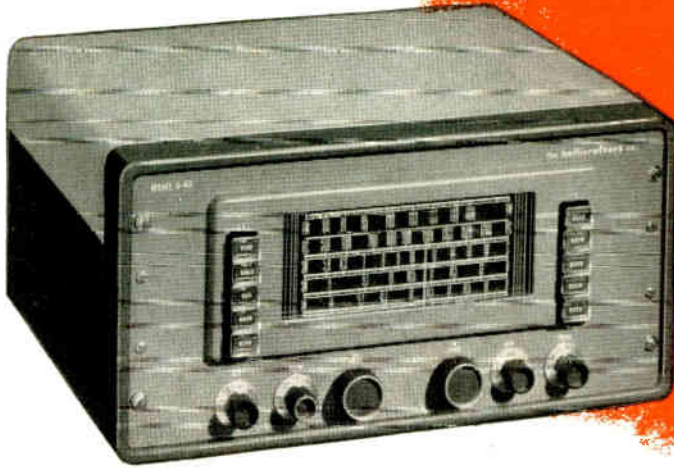

**S-47**

## AM-FM RECEIVER FOR SPECIALIZED INSTALLATIONS

### A superb radio chassis with push button tuning

**H**ERE is a brand new kind of receiving instrument, designed by Hallicrafters to fill a long felt need. It is a 14 tube (plus rectifier) AM and FM receiver with an overall frequency range of 535 kc. to 108 Mc. in three bands with five positions on the band switch. A new development is the addition of push button controls for FM tuning. There are push button controls for the AM tuning also. This is a high precision, fine quality receiver that will have numerous applications in homes, schools or public institutions or in any location where a good specialized

radio installation is needed. Styled to match the new Hallicrafters line, the S-47 receiver lends itself perfectly to "custom" installations of your own choosing—such as in specially designed cabinets in bookcases or built-in sound systems for fine homes. Here is radio that is all radio, made simple to operate with the push button controls and the wide, easily read dial.


**CONTROLS:** BAND SELECTOR AND PHONO SWITCH, AM TUNING, FM TUNING, FIVE AM PUSH BUTTONS, FIVE FM PUSH BUTTONS, VOLUME, TREBLE TONE AND AM SELECTIVITY, BASS TONE AND POWER ON/OFF.

**EXTERNAL CONNECTIONS:** Antenna connections for single wire or doublet AM antenna and doublet FM antenna. AC power cord. Power outlet for phono motor connection. Phono input socket. 500 ohm speaker terminals.

**OPERATING DATA:** The Model S-47 receiver is designed for operation on 105-125 volts 50/60 cycle alternating current. The power drain is 100 watts. It may be used with any speaker having 500/600 ohm input.

**OVERALL DIMENSIONS:** S-47 (with steel cabinet) 8-11/16 in. high, 16½ in. deep, 20 in. wide . . . . . **\$200<sup>00</sup>**

Amateur Net

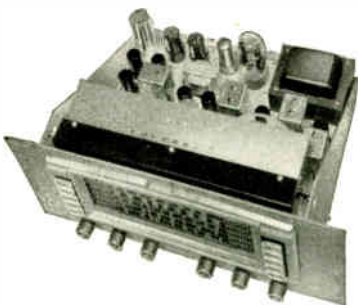

#### S-47 C CHASSIS ONLY

Same chassis, available without the steel cabinet. Overall dimensions: 8-11/16 in. high, **\$189<sup>50</sup>**  
16 in. deep, 18-15/16 in. wide . . . . .

# Modernize YOUR OLD TRANSMITTER



## New Variable Master Oscillator

... the Model

# HT-18



**H**ERE is the hottest transmitter item available today! Narrow band FM and calibrated 5-band V.F.O. complete in one compact cabinet with all coils and power supply built in. These outstanding features have never before been available in one low-priced unit, including low frequency drift, low FM distortion, low hum and noise level, excellent keying, voltage regulators, and low impedance output circuit.

This is the unit you have been waiting for to modernize your old transmitter, whether it is a 50-watt or a one-kilowatt station.

The HT-18 is also a valuable tool for antenna tuning on all ham bands. Run a quick response curve of the antenna to find the best operating frequency.

Do you have B.C.I. trouble? Simple; just add an HT-18 on narrow band FM and watch the neighbors smile and say "Hello" again.

- ★ **Directly calibrated for easy operation**
- ★ **Incorporates narrow band FM**
- ★ **As easy to tune as a modern receiver**
- ★ **Excellent stability**
- ★ **Good clean keying**

**\$110.00**

Amateur Net

**hallicrafters RADIO**



## Choose the HT-9 TRANSMITTER

For power . . . 100 watts

For price . . . \$35000

Amateur Net  
(Less coils  
and crystals)

**H**ALLICRAFTERS Model HT-9 is an ideal medium power transmitter. Designed for maximum flexibility and convenience, it is completely self-contained, requiring only a microphone or key, antenna, and source of AC power to go on the air.

Five individual plug-in tuning units and crystals may be accommodated in the exciter section simultaneously. Band switching is easily accomplished by changing one coil in the final amplifier and selecting the desired exciter frequency

by means of a panel switch. Exciter units are pre-tuned and the only additional operation needed is a slight adjustment of the final tank tuning capacitor.

Separate meters are provided for the power amplifier plate and grid circuits and a third meter may be switched into either the exciter or modulator cathode circuits. All controls are conveniently arranged on the panel and a safety interlock switch is provided for protection against accidental shock when cabinet is opened.



. . . a low power, high quality,  
low price TRANSMITTER




## HT-17

\$6950 (Less coils  
and crystals)  
Amateur Net

**T**HE Model HT-17 offers real Hallicrafters transmitter performance with maximum convenience and economy. No larger than a small receiver and styled to match the postwar Hallicrafters line, this new transmitter provides an honest 10 to 20 watts of crystal-controlled CW output on the amateur 3.5, 7, 14, 21, and 28 megacycle bands.

A pi-section matching network is an integral part of the plate circuit and, together with an adjustable link, provides coupling to any type of antenna or permits the HT-17 to be used as an exciter for a high power final amplifier. The

oscillator stage uses a type 6V6-GT tube and is automatically switched to a Tritet circuit when coils for the three higher bands are plugged in. Full output on the 14, 21, and 28 megacycle bands is obtained with 7 megacycle crystals. A type 807 tube is used in the final amplifier, and the self-contained power supply, for 105-120 volt AC operation, employs a 5Y3-GT rectifier. Connections are provided for an external modulator. The "Airodized" steel top opens on a full length piano hinge for maximum accessibility and ease in changing coils and crystals. A pilot lamp is provided on front panel for tuning. Coil sets extra.

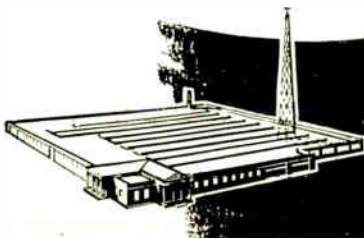

# hallicrafters RADIO

THE HALLICRAFTERS CO., MANUFACTURERS OF RADIO  
AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.

Sole Hallicrafters Representatives in Canada:  
Rogers Majestic Limited, Toronto-Montreal






TYPE 11

## SMALL, LOW-COST, SOLA CONSTANT VOLTAGE TRANSFORMERS FOR CHASSIS MOUNTING

Reliable communications equipment must have stabilized voltage—and the right place to provide for it is in the equipment itself. These three types of SOLA Constant Voltage Transformers have been specifically designed for “built-in” applications. They are low in cost and their use will often permit the elimination of other components. For complete information consult Bulletin 34CV-102, available on request.

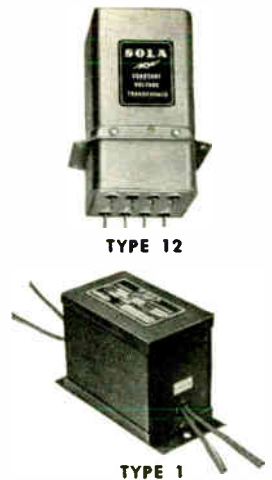

TYPE 12

TYPE 1

TYPE 1

TYPE 11

TYPE 12

Catalog Number	Output Capacity in VA	Input Volts	Output Volts	Dimensions in Inches					Approx. Shipping Weight	List Price Each
				A	B	C	E	F		
30488	15	95-125	6.0	5 11/16	2 3/8	3 7/8	5 1/2		6	\$15.00
30492	15	95-125	6.3	5 11/16	2 5/8	3 7/8	5 1/2		6	15.00
30498	15	95-125	115.0	5 11/16	2 5/8	3 7/8	5 1/2		6	15.00
30785	17	95-125	6.3	5 13/16	3 1/4	2 1/2	3	2	5 1/2	20.00
30955	17	95-125	115.0	5 13/16	3 1/4	2 1/2	3	2	5 1/2	20.00
301002	15	95-125	6.3	5 5/8	3 1/4	2 1/4	3	1 1/2	2 1/2	18.50
301003	15	95-125	115.0	5 5/8	3 1/4	2 1/4	3	1 1/2	2 1/2	18.50

\*Condenser supplied as separate unit.

### DIMENSIONS:

- A: Overall Length
  - B: Overall Width
  - C: Overall Height
  - E & F: Mounting Dimensions
- Prices subject to change without notice.

VOLTAGE FLUCTUATIONS UP TO 30%

STABILIZED WITHIN ± 1% OF RATED VALUE



TYPE 2

## FOR COMMUNICATIONS EQUIPMENT NOW IN SERVICE

Where provision for constant voltage protection has not been made within the equipment itself, these standard SOLA Constant Voltage Transformers can be easily installed. They require no supervision or maintenance, are instantaneous in operation and they protect both themselves and the equipment against short-circuit. Other capacities ranging from 10VA to 15KVA fully described in Bulletin 34CV-102, available on request.



TYPE 3

TYPE 2

TYPE 3

Catalog Number	Output Capacity in VA	Input Volts	Output Volts	Dimensions in Inches					Approx. Shipping Weight	List Price Each
				A	B	C	E	F		
30804	30	95-125	115.0	8 3/8	4 3/8	4 3/8	7 1/2	2 3/8	12	\$17.00
30805	60	95-125	115.0	8 1/2	4 3/8	4 3/8	8 1/2	2 3/8	13	24.00
30806	120	95-125	115.0	9 1/2	4 3/8	4 3/8	8 1/2	2 3/8	17	32.00
30807	250	95-125	115.0	11 5/8	6 1/2	5 5/8	3 1/4	6 1/2	30	52.00
30M807	250	190-250	115.0	11 5/8	6 1/2	5 5/8	3 1/4	6 1/2	30	52.00
30808	500	95-125	115.0	14 1/2	6 1/2	5 5/8	5	6 1/2	40	75.00
30M808	500	190-250	115.0	14 1/2	6 1/2	5 5/8	5	6 1/2	40	75.00

# Constant Voltage SOLA Transformers

SOLA ELECTRIC COMPANY, 4633 WEST 16TH STREET, CHICAGO 50, ILLINOIS

THERE'S AN

RCA

TUBE

## RCA Power Tube Chart for Amateur Transmitters

CW, FM, AND PHONE TO 30 Mc.

This table has been set up to give suitable choice of tubes for the final and for a preceding stage to drive the final. A choice of buffer, doubler or oscillator driver stage is

provided. The tubes shown have been chosen conservatively to provide ample driving power at 30 Mc even in circuits having higher than usual losses.

Final Amplifier		Tube Types for Driving Final Amplifier (CW, FM and Phone)			Class B Modulator	
Input Power Watts CW & FM	Tube Type	As Buffer	As Doubler	As Oscillator	Tube Type	
		Phone				
40	27	1-2E26	2E26 6AK6 6AG7 6F6	2E26 6N7 6AG7 6V6GT 6F6	2E26 6F6 6AG7 6V6GT	2-6L6 (AB <sub>1</sub> ) 2-6F6 (AB <sub>2</sub> )
75	54	2-2E26	2E26 802	2E26 6L6	2E26 6L6	2-2E26
75	60	1-815	6AG7 807	6AG7 802	6AG7 802	1-815
75	60	1-807	6F6	6F6 807	6F6 807	2-807
150	120	2-807	2E26 802 6F6 807	2E26 6N7 6F6 802 6L6 807	2E26 6V6GT 6F6 802 6L6 807	2-807 2-811
225	150	1-812	2E26 807 802	2E26 802 6L6 807	2E26 802 6L6 807	2-807 2-811
225	150	1-811	2E26 807 802	807 811 809 814	807 814	2-807 2-811
300	240	1-8005	2E26 807	807 811	807 814	2-811
300	200	1-808	802	809 814		2-808 2-8005
450	300	2-812	2E26 809 802 812 807 815	807 814 809 815 811	807 815 814	2-811 2-808 2-8005
450	300	2-811	2-2E26 809 2-802 812 807 815	2-807 811 809 814	2-807 1-828 1-814	2-811 2-808 2-8005
500	375	1-4-125A/ 4D-21	2E26 802	2E26 6L6 802	2E26 802 6L6 807	2-811 4-807 2-8005
500	400	1-813	807	807		
600	400	2-808	2-2E26 811	2-807	2-807 814	2-811
600	480	2-8005	807 812 809 815	809 812 811 814		2-808 2-8005
750	500	1-8000	807 811 809 812 814	807 811 809 814	807 814	4-811 2-8005
750	500	1-810	809 812	808 814	not recommended	4-811
1000	600	1-806	811 814	811 828		2-8005
1000	750	2-4-125A/ 4D21	2E26 807 802 815	2E26 802 2-6L6 807 815	2E26 802 2-6L6 807 815	2-810 2-8000 4-8005
1000	800	2-813				
1000	835	1-833A	808 812 809 814 811 8005	808 814 811 828	not recommended	2-810 2-8000 4-8005
1000	1000	2-8000	2-807 811 2-809 812 814	808 811 2-809 814	not recommended	2-810 2-8000 4-8005
1000	1000	2-810	808 812 2-809 814 811 8005	808 813 811 828	not recommended	2-810 2-8000 4-8005

# FOR EVERY AMATEUR SERVICE



## RCA POWER TRIODES

806	1000 watts input* at 30 Mc.
808	300 watts input* at 30 Mc.
810	750 watts input* at 30 Mc.
811	225 watts input* at 60 Mc.
812	225 watts input* at 60 Mc.
833-A	1000 watts input* at 30 Mc.
8005	300 watts input* at 60 Mc.



## RCA BEAM POWER TUBES

2E26	33 watts input* at 150 Mc.
807	75 watts input* at 60 Mc.
813	500 watts input* at 30 Mc.
815	68 watts input* at 150 Mc.
829-B	120 watts input* at 200 Mc.



## RCA RECTIFIERS AND THYATRONS

5R4-GY	Full-wave, vacuum type. With choke input, 175 ma. at 750 volts.
816	Half-wave, mercury-vapor type. Two tubes in full-wave, 250 ma. up to 2380 volts.
866-A	Half-wave, mercury-vapor type. Two tubes in full-wave, 500 ma. up to 3180 volts.
2050	Gas thyatron. Up to 200 ma. at 400 volts in grid-controlled full-wave circuit.
5957	Mercury-vapor thyatron. Up to 1 amp. at 1500 volts in full-wave choke-input circuit.



## RCA UHF AND VHF TUBES

2C43	20 watts input* at 1500 Mc.
4-125A/4D21	500 watts input* at 125 Mc.
6C24	1000 watts input* at 160 Mc.
826	130 watts input* at 250 Mc.
8025-A	50 watts input* at 500 Mc.

\*Maximum value, class C telegraphy service.

● RCA has a popular tube for every amateur service, every power and every active band. A few of the best-known types in each classification are listed.

In addition, there are special-application types, such as *voltage regulators, phototubes, acorns, kinescopes, iconoscopes*, and the well-known *receiving types* in metal, glass, and miniature.

Your local RCA Tube Distributor has complete technical data on all RCA tube types. Contact him for further information, or write RCA, Commercial Engineering, Section M-67, Harrison, New Jersey.

## Free—RCA Headliners for Hams

... 4-page folder, gives power tube voltages, currents, driving power, dissipations, etc. for each tube service. Indispensable to every Amateur who builds transmitting equipment. Ask your RCA Tube Distributor for a copy of Headliners, or write RCA, Commercial Engineering, Section M-35, Harrison, New Jersey.



THE FOUNTAINHEAD OF MODERN TUBE DEVELOPMENT IS RCA




TUBE DEPARTMENT

**RADIO CORPORATION of AMERICA**

HARRISON, N. J.

# Bliley
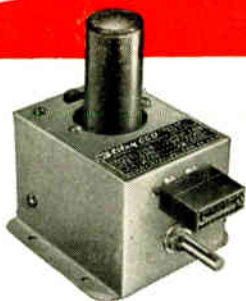
## CRYSTALS AND CRYSTAL CONTROLLED OSCILLATOR



### CCO — CRYSTAL CONTROLLED OSCILLATOR — MODEL 2A

For 2-6-10-11 Meters

With this basic oscillator, employing a 6AG7 tube, the advantages of VHF crystal control are easily achieved. Has direct output on 6-10-11 meters and ample output to drive tripler stage on 2 meters. Single tuning control, bandswitch and crystal socket are mounted on outside of painted metal subchassis with power and output

terminals at back. Uses Bliley AX2 2 meter crystals for output on 10 and meters, new Bliley AX3 crystals for 6 a 2 meter operation. Ideal as nucleus for new construction or conversion of existing equipment.

Supplied less tube and crystal ..... \$9.

## AMATEUR FREQUENCY CRYSTALS

### TYPE AX2

These high stability advanced design crystals are plated to insure long term precision and reliability. Calibrated to  $\pm 0.002\%$  with drift less than  $.0002\%$  per degree Centigrade. Holder pins spaced on .486" centers.

Supplied	Range	Price
$\pm 2$ Kc	3500—4000 Kc	\$2.80
$\pm 2$ Kc	7000—7425 Kc	2.80
$\pm 30$ Kc	12500—13500 Kc	3.95
$\pm 30$ Kc	13580—13714 Kc	3.95
$\pm 30$ Kc	14000—14850 Kc	3.95



### TYPE AX3

A new third overtone crystal unit produced for use in the Bliley CCO-2A. Has exceptionally high activity at operating frequency. Calibration accurate to  $\pm 0.003\%$  in CCO-2A with drift less than  $.0002\%$  per degree Centigrade. Plated crystal is mounted in gasket sealed holder with pins spaced .486" centers.

Supplied	Range	Price
$\pm 5$ Kc	24000—24333 Kc	\$3.95
$\pm 5$ Kc	25000—25500 Kc	3.95



### TYPE CF6 455 Kc

Single signal filter crystal unit. Exceptionally low holder capacity permits sharp signal discrimination in filter network of general communications receivers. Frequency 455 Kc free from spurious responses within  $\pm 7$  Kc.

Price \$4.50



### TYPE CF3 455 Kc

Single signal filter crystal unit. Frequency 455 Kc,  $\pm 5$  Kc—free from spurious responses within  $\pm 7$  Kc of fundamental. Designed for intermediate frequency filter in general communications receivers.

Price \$5.00



### TYPE MC9 3105 Kc

This unit is suggested for use in private aircraft transmitters operating at 3105 Kc. The crystal is guaranteed to be within  $\pm 0.02\%$  of 3105 Kc any temperature between  $0^{\circ}\text{C}$  and  $50^{\circ}\text{C}$  and is factory tested for performance over this temperature range. Plug-in type holder is gasket sealed against moisture and humidity.

Price \$5.50



### TYPE VX2 3105 Kc

Designed for applications where space is at a premium, this unit is recommended for private aircraft communication at 3105 Kc. Guaranteed to maintain frequency within  $\pm 0.02\%$  at any temperature between  $0^{\circ}\text{C}$  and  $50^{\circ}\text{C}$ . Solder lug connections permit mounting under chassis and assembly is gasket sealed against moisture and humidity.

Price \$5.00



### TYPE KV3 100 Kc

A precision crystal designed for use in secondary standards. Crystal silver plated and mounted between wire supports which are soldered to the plated surfaces. Exceptionally low drift crystal is adjustable to exactly 100 Kc at  $25^{\circ}\text{C}$  when used in recommended oscillator circuit.

Price \$6.95



### TYPE SMC100 100-1000 Kc

Dual frequency crystal providing either 100 Kc or 1000 Kc frequency source. When used in recommended oscillator circuit 1000 Kc frequency is within  $\pm 0.05\%$  at  $25^{\circ}\text{C}$  and 1 Kc frequency can be adjusted zero beat at  $25^{\circ}\text{C}$ . Suggested for signal generators used in alignment radio receivers.

Price \$8.75



For complete dimensional information consult Bulletin 35 available at any Bliley distributor.



# Bliley CCO

CRYSTAL CONTROLLED OSCILLATOR

For instant channel selection and frequency accuracy, radio service technicians use this Bliley test instrument.

It provides direct crystal control for alignment. Write for descriptive Bulletin 32.

Complete with 7 Bliley crystals, tubes and concentric output cable..... \$69.50

BLILEY ELECTRIC COMPANY • UNION STATION BUILDING • ERIE, PENNSYLVANIA

WorldRadioHistory

# MICRO <sup>TRADE</sup> MS <sup>MARK</sup> SWITCH

A DIVISION OF FIRST INDUSTRIAL CORPORATION

Freeport, Illinois

## Branch Offices

CHICAGO 6...308 W. Washington Street  
 NEW YORK 17.....101 Park Avenue  
 CLEVELAND 3.....4900 Euclid Avenue  
 LOS ANGELES 14...1709 West 8th Street  
 BOSTON 16.....126 Newbury Street

## The Precise, Small Lightweight, Sensitive Switch for Radio Applications

Micro Switch precision snap-action switches have proved invaluable for applications that call for switching substantial amounts of power by a unit operating in a small space. Micro Switch products are important electrical switching units for electrical mechanisms that make change, package products, control temperatures, heat water, bottle fluids, limit machine tools, record airplane flights, control electronic tubes and perform thousands of other diversified electrical control functions.

### MICRO SWITCH Products Meet These Requirements

**Small Size** . . . No larger than your thumb, the basic, plastic enclosed switch measures 11/16" x 27/32" x 1 15/16".


**Light Weight** . . . With pin-type plunger, the plastic enclosed switch weighs less than one ounce.

**Long Life** . . . Patented three-bladed beryllium copper spring gives millions of accurate repeat operations.

**Small Operating Force** . . . Force required to operate the switch may be as little as one ounce . . . or as much as 60 ounces.

**Small Operating Movement** . . . Movement of the operating plunger may be as little as .0004".

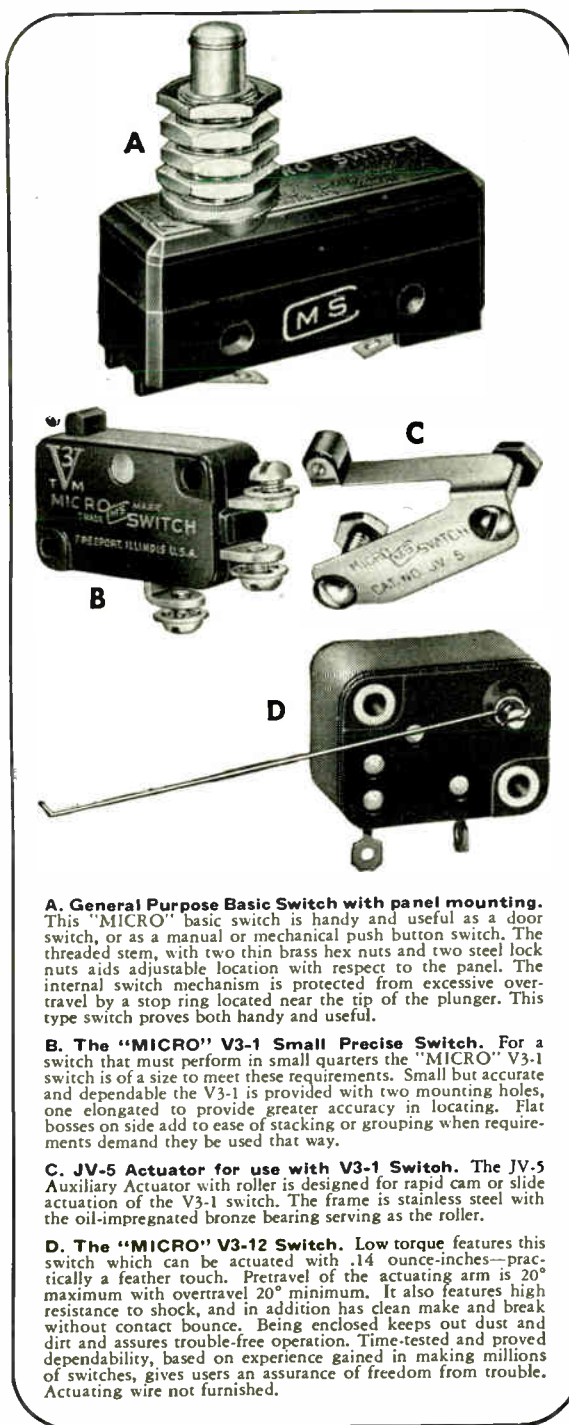**Good Electrical Capacity** . . . Switch is Underwriters' listed and rated at 1200 V.A. at 125 to 460 volts a.c.



**A. General Purpose Basic Switch with panel mounting.** This "MICRO" basic switch is handy and useful as a door switch, or as a manual or mechanical push button switch. The threaded stem, with two thin brass hex nuts and two steel lock nuts aids adjustable location with respect to the panel. The internal switch mechanism is protected from excessive overtravel by a stop ring located near the tip of the plunger. This type switch proves both handy and useful.


**B. The "MICRO" V3-1 Small Precise Switch.** For a switch that must perform in small quarters the "MICRO" V3-1 switch is of a size to meet these requirements. Small but accurate and dependable the V3-1 is provided with two mounting holes, one elongated to provide greater accuracy in locating. Flat bosses on side add to ease of stacking or grouping when requirements demand they be used that way.

**C. JV-5 Actuator for use with V3-1 Switch.** The JV-5 Auxiliary Actuator with roller is designed for rapid cam or slide actuation of the V3-1 switch. The frame is stainless steel with the oil-impregnated bronze bearing serving as the roller.


**D. The "MICRO" V3-12 Switch.** Low torque features this switch which can be actuated with .14 ounce-inches—practically a feather touch. Pretravel of the actuating arm is 20° maximum with overtravel 20° minimum. It also features high resistance to shock, and in addition has clean make and break without contact bounce. Being enclosed keeps out dust and dirt and assures trouble-free operation. Time-tested and proved dependability, based on experience gained in making millions of switches, gives users an assurance of freedom from trouble. Actuating wire not furnished.

# JAMES M. MILLEN

MALDEN · MASSACHUSETTS

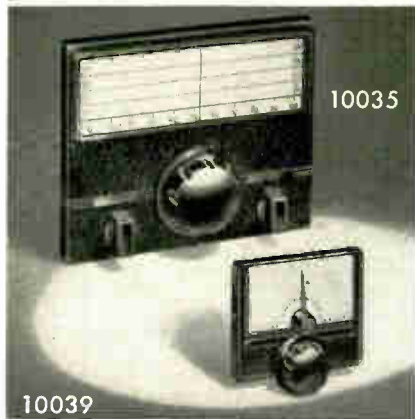

10039

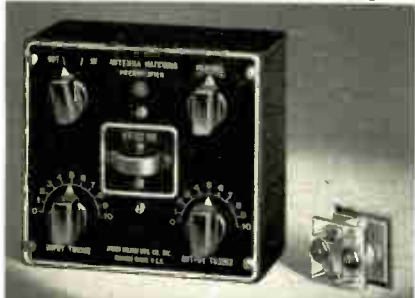

92101



90810



15011

## INSTRUMENT DIALS

The No. 10030 is an extremely sturdy instrument type indicator. Control shaft has 1 to 1 ratio. Veeder type counter is direct reading in 99 revolutions and vernier scale permits readings to 1 part in 100 of a single revolution. Has built-in dial lock and  $\frac{1}{4}$ " drive shaft coupling. May be used with multi-revolution transmitter controls, etc., or through gear reduction mechanism for control of fractional revolution capacitors, etc., in receivers or laboratory instruments.

The No. 10035 illuminated panel dial has 12 to 1 ratio; size,  $8\frac{1}{2}$ " x  $6\frac{1}{4}$ ". Small No. 10039 has 8 to 1 ratio; size, 4" x  $3\frac{1}{4}$ ". Both are of compact mechanical design, easy to mount and have totally self-contained mechanism, thus eliminating back of panel interference. Provision for mounting and marking auxiliary controls, such as switches, potentiometers, etc., provided on the No. 10035. Standard finish, either size, flat black art metal.

No. 10039 ..... \$ 2.70  
 No. 10030 ..... 25.00  
 No. 10035 ..... 6.00

## PANEL MARKING TRANSFERS

The panel marking transfers have  $\frac{1}{16}$ " black letters. Special solution furnished. Must not be used with water. Equally satisfactory on smooth or wrinkle finished panels or chassis. Ample supply of every conceivable word or marking required for amateur or commercial equipment.

No. 59001, white letters ..... \$1.25  
 No. 59002, black letters ..... 1.25

## R9'er MATCHING PREAMPLIFIER

The Millen 92101 is an electronic impedance matching device and a broad-band preamplifier combined into a single unit, designed primarily for operation on 6 and 10 meters. Coils for 20 meter band also available.

No. 92101, less tubes ..... \$24.75

## HIGH FREQUENCY TRANSMITTER

The No. 90810 crystal control transmitter provides 75 watt output (higher output may be obtained by the use of forced cooling) on the 10-11, 6 and 2 meter amateur bands. Provisions are made for quick band shift by means of the new 48000 series high frequency plug-in coils.

No. 90810, less tubes and crystals ..... \$69.75

## HIGH VOLTAGE POWER SUPPLY

The No. 90281 high voltage power supply has a d.c. output of 700 volts, with maximum current of 250 ma. In addition, a.c. filament power of 6.3 volts at 4 amperes is also available so that this power supply is an ideal unit for use with transmitters, such as the Millen No. 90800, as well as general laboratory purposes. The power supply uses two No. 816 rectifiers and has a two section pi filter with 10 henry General Electric chokes and a 2-2-10 mfd. bank of 1000 volt General Electric Pyralon capacitors. The panel is standard  $8\frac{1}{2}$ " x 19" rack mounting.

No. 90281, less tubes ..... \$84.50

## NEUTRALIZING CAPACITOR



Designed originally for use in our own No. 90881 Power Amplifier, the No. 15011 disc neutralizing capacitor has such unique features as rigid channel frame, horizontal or vertical mounting, fine thread over-size lead screw with stop to prevent shorting and rotor lock. Heavy rounded-edged polished aluminum plates are 2" diameter. Glazed Steatite insulation.

No. 15011 ..... \$3.15
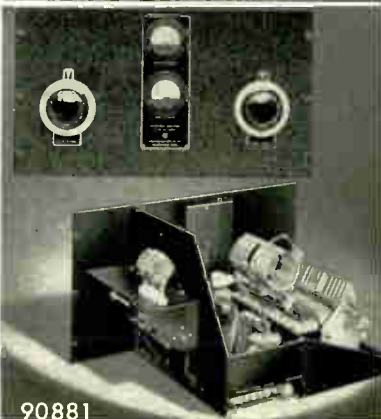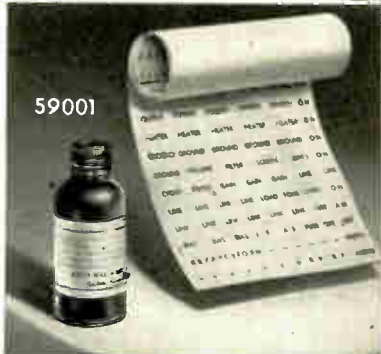
## RF POWER AMPLIFIER


This 500 watt amplifier may be used as the basis of a high power amateur transmitter or as a means for increasing the power output of an existing transmitter. As shipped from the factory, the No. 90881 RF power amplifier is wired for use with the popular RCA or G.E. "812" type tubes, but adequate instructions are furnished for readjusting for operation with such other popular amateur style transmitting tubes as Taylor T240, Eimac 35T, etc. The amplifier is of unusually sturdy mechanical construction, on a  $10\frac{1}{2}$ " relay rack panel. Plug-in inductors are furnished for operation on 10, 20, 40 or 80 meter amateur bands. The standard Millen No. 90800 exciter unit is an ideal driver for the new No. 90881 RF power amplifier.

No. 90881, with one set of coils, but less tubes ..... \$89.50



# JAMES MILLER

MALDEN · MASSACHUSETTS

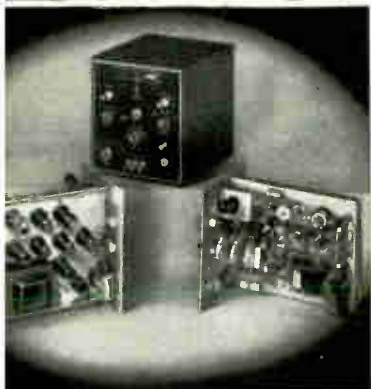

90902



90700

## SECONDARY FREQUENCY STANDARD

A precision frequency standard for both laboratory and production uses, adjustable output, provided at intervals of 10, 25, 100 and 1000 kc, with magnitude useful to 50 mc. Harmonic amplifier with tuned plate circuit and panel range switch, 800 cycle modulator with panel control switch. In addition to oscillators, multivibrators, modulators and amplifiers, a built-in detector with phone jack and gain control is incorporated. Self-contained power supply.  
Model 90505, with tubes . . . . . \$155.00

## ABSORPTION WAVEMETERS

The 90600 series of absorption wavemeters are available in several styles and many different ranges. Most popular is kit of four units, covering range of 3.0 to 140 mc.  
Model 90600 . . . . . \$18.00

## FREQUENCY CALIBRATORS

The cavity type frequency calibrator covers a range of 200 to 700 mc., with a maximum error of not over 0.25%. This range is covered by two plug-in cavity type tuning units, which may be easily interchanged. The calibrator consists of an accurately calibrated cavity-type tuning unit, a crystal detector, a two-stage video amplifier and a peak reading VT voltmeter.  
Model 90630, with tubes . . . . . \$375.00

## SYNCHROSCOPES

The 5" synchroscopes are available with and without detector-video strips.  
Model P-4, with tubes . . . . . \$300.00  
Model P-4E, with tubes . . . . . 395.00

## OSCILLOSCOPES

The basic type 2" oscilloscope is complete with power supply, focusing and centering controls and 60 cycle sweep, for use in normal form for transmitter monitoring or as basic unit for addition of specially designed external sweeps, amplifiers, etc., for specialized applications.  
Model 90902, less tubes . . . . . \$42.50

## REGULATED POWER SUPPLIES

A compact, uncased, regulated power supply, either for table use in the laboratory or for incorporation as an integral part of larger equipments. 50 watts, with regulated voltage from 0 to 200 volts.  
Model 90201, less tubes . . . . . \$100.00

## FREQUENCY SHIFTER

A favorite frequency shifter, plugs in, in place of crystal, for instant finger-tip control of carrier frequency. Low drift, chirpless keying, vibration immune, big band spread, accurate calibration.  
Model 90700, with tubes . . . . . \$42.50

## 50 WATT TRANSMITTER

Based on an original Handbook design, this flexible unit is ideal for either low power amateur band transmitter use or as an exciter for high power PA stages.  
Model 90800, less tubes . . . . . \$42.50



90201



90600

# JAMES MILLEN


MALDEN · MASSACHUSETTS



### SHAFT LOCKS

In addition to the original No. 10060 and No. 10061 "DESIGNED FOR AFFLICTION" shaft locks, we can also furnish such variations as the No. 10062 and No. 10063 for easy thumb operation as illustrated above. The No. 10061 instantly converts any plain "1/4" shaft" volume control, condenser, etc. from "plain" to "shaft locked" type. Each to mount in place of regular mounting nut.

No. 10060.....	\$ .36
No. 10061.....	.36
No. 10062.....	.45
No. 10063.....	.45

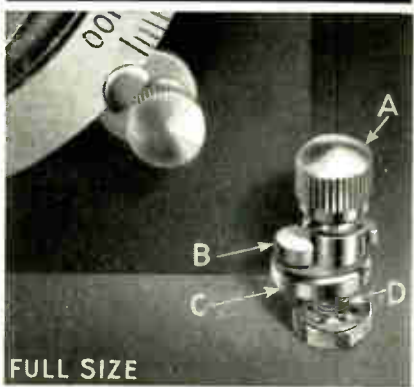

### DIAL LOCK

Compact, easy to mount, positive in action, does not alter dial setting in operation! Rotation of knob "A" depresses finger "B" and "C" without imparting any rotary motion to Dial. Single hole mounted.  
No. 10050..... \$ .45

### RIGHT ANGLE DRIVE

Extremely compact, with provisions for many methods of mounting. Ideal for operating potentiometers, switches, etc., that must be located, for short leads, in remote parts of chassis.  
No. 32150..... \$3.75

### THRU-BUSHING

Efficient, compact, easy to use and neat appearing. Fits 1/4" hole in chassis. Held in place with a drop of solder or a "wick" from a cleaning tool.  
No. 32150..... \$ .05

### FLEXIBLE COUPLINGS

The No. 39000 series of Millen "Designed for Application" flexible coupling units include, in addition to improved versions of the conventional types, also such exclusive original designs as the No. 39001 insulated universal joint and the No. 39006 "slide-action" coupling (in both steatite and bakelite insulation).

The No. 39006 "slide-action" coupling permits longitudinal shaft motion, eccentric shaft motion and out-of-line operation, as well as angular drive without backlash.

The No. 39005 is similar to the No. 39001, but is not insulated and is designed for applications where relatively high torque is required. The steatite insulated No. 39001 has a special anti-backlash ball and socket grip feature, which, however, limits its serviceable operation to torques of six inch-pounds, or less. All of the above illustrated units are for 1/4" shaft and are standard production type units.

No. 39001.....	\$ .36
No. 39002.....	.36
No. 39003.....	.21
No. 39005.....	.36
No. 39006.....	.36




### CATHODE RAY TUBE SHIELDS

For many years we have specialized in the design and manufacture of magnetic metal shields of nicoloi and mumetal for cathode ray tubes in our own complete equipment, as well as for applications of all other principal complete equipment manufacturers. Stock types as well as special designs to customers' specifications promptly available.

### BEZELS FOR CATHODE RAY TUBES

Bezel of cast aluminum with black wrinkle finish. Complete with neoprene cushion, green lucite filter scale and four "behind the panel" thumb screws for quick detachment from panel when inserting tube.

No. 80075—5".....	\$7.50
No. 80073—3".....	3.90
No. 80072—2".....	1.25

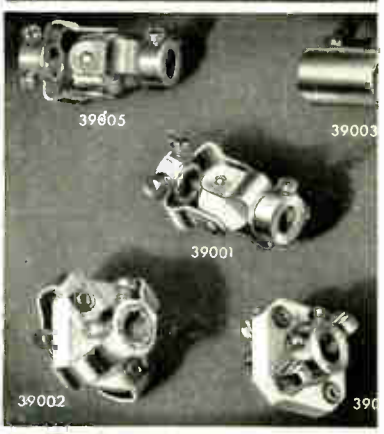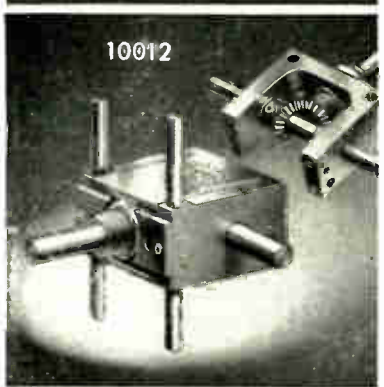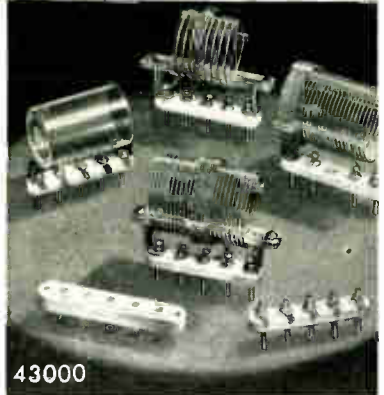



# JAMES M MILLEN

MALDEN · MASSACHUSETTS





## 04000 and 11000 SERIES TRANSMITTING CONDENSERS

A new member of the "Designed for Application" series of transmitting variable air capacitors is the 04000 series with peak voltage ratings of 3000, 6000, and 9000 volts. Right angle drive, 1-1 ratio. Adjustable drive shaft angle for either vertical or sloping panels. Sturdy construction, thick, rounded, polished aluminum plates with 1 3/4" radius. Constant impedance, heavy current, multiple finger rotor contactor of new design. Available in all normal capacities.

The 11000 series has 16/1 ratio center drive and fixed angle drive shaft.



Code	Volts	Capacity	Price
11035	3000	35	\$ 6.90
11050	3000	50	7.14
11070	3000	70	7.80
04050	6000	50	16.00
04060	9000	60	18.00
04100	6000	90	18.00
04200	3000	205	20.00

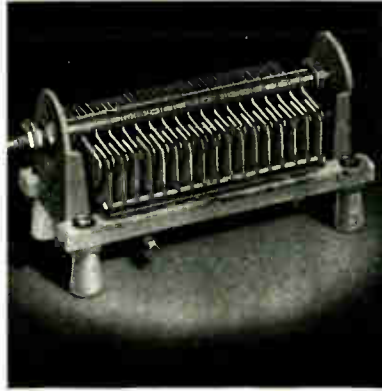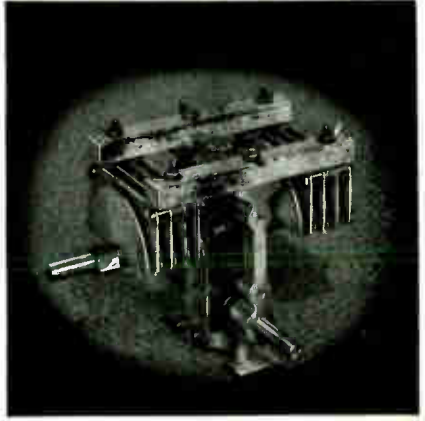
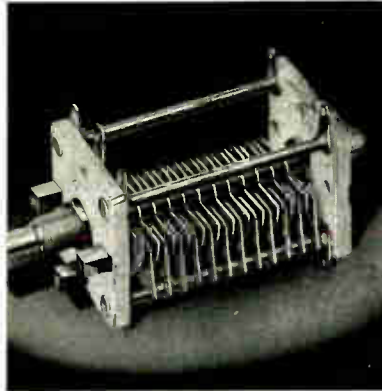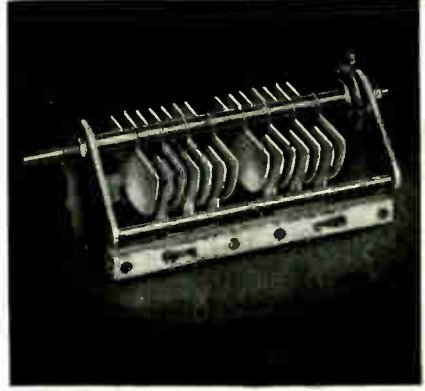
## 12000 and 16000 SERIES TRANSMITTING CONDENSERS



Rigid heavy channeled aluminum end plates. Isolantite insulation, polished or plain edges. One piece rotor contact spring and connection lug. Compact, easy to mount with connector lugs in convenient locations. Same plate sizes as 11000 series above.

The 16000 series has same plate sizes as 04000 series. Also has constant impedance, heavy current, multiple finger rotor contactor of new design. Both 12000 and 16000 series available in single and double sections and many capacities and plate spacing.


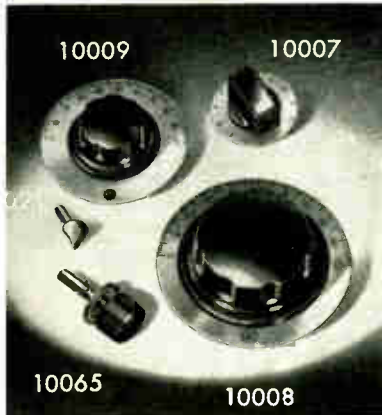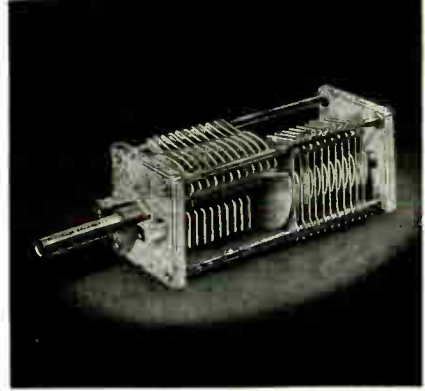
## THE 28000-29000 SERIES VARIABLE AIR CAPACITORS

"Designed for Application," double bearings, steatite end plates, cadmium or silver plated brass plates. Single or double section .022" or .066" air gap. End plate size: 19 1/16" x 11 1/16". Rotor plate radius: 3/4". Shaft lock, rear shaft extension, special mounting brackets, etc., to meet your requirements. The 28000 series has semi-circular rotor plate shape. The 2900 series has approximately straight frequency line rotor plate shape. Prices quoted on request. Many stock sizes.




## DIALS

Just a few of the many stock types of small dials and knobs are illustrated herewith. 10007 is 1 3/4" diameter, 10009 is 2 1/2" and 10008 is 3 1/2".

No. 10007	.....	\$ .60
No. 10008	.....	1.00
No. 10009	.....	.85
No. 10021	.....	.15
No. 10065	.....	.36



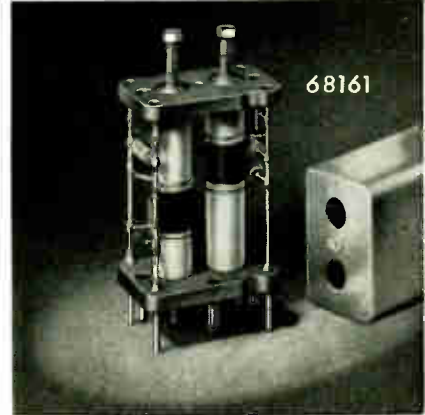
## I.F. TRANSFORMERS

The Millen "Designed for Application" line of I.F. transformers includes air condenser tuned, mica condenser tuned and permeability tuned types for all applications. Standard stock units are for 465, 1600 and 5000 kc. B.F.O. and Crystal Filter units also available.



# JAMES M MILLEN

MALDEN · MASSACHUSETTS

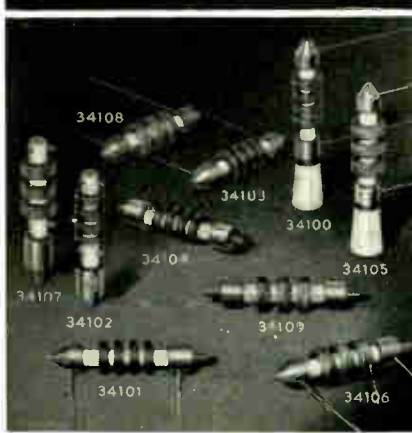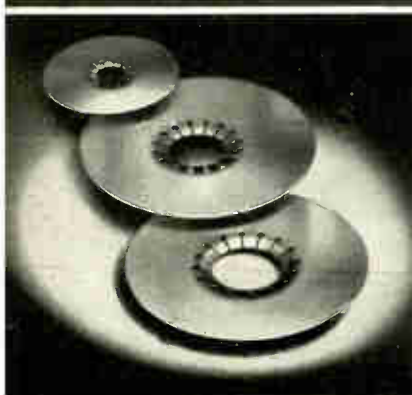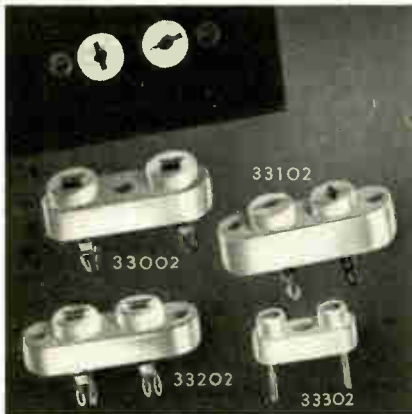

## TUBE SOCKETS DESIGNED FOR APPLICATION

**MODERN SOCKETS FOR MODERN TUBES!**  
Long Flashover path to chassis permits use with transmitting tubes, 866 rectifiers, etc. Long leakage path between contacts. Contacts are type proven by hundreds of millions already in government, commercial and broadcast service, to be extremely dependable. Sockets may be mounted either with or without metal flange. Mounts in standard size chassis hole. All types have barrier between contacts and chassis. All but octal and crystal sockets also have barriers between individual contacts in addition.

The No. 33888 shield is for use with the 33008 octal socket. By its use, the electrostatic isolation of the grid and plate circuits of single-ended metal tubes can be increased to secure greater stability and gain.

The 33087 tube clamp is easy to use, easy to install, effective in function. Available in special sizes for all types of tubes. Single hole mounting. Spring steel, cadmium plated.

Cavity Socket Contact Discs, 33446 are for use with the "Lighthouse" ultra high frequency tube. This set consists of three different size unhardened beryllium copper multi-finger contact discs. Heat treating instructions forwarded with each kit for hardening after spinning or forming to frequency requirements.

Voltage regulator dual contact bayonet socket, 33991 black Bakelite insulation and 33992 with low loss high leakage mica filled Bakelite insulation.


No. 33004.....	\$ .27
No. 33005.....	.27
No. 33006.....	.27
No. 33007.....	.34
No. 33008.....	.27
No. 33888.....	.18
No. 33087.....	.30
No. 33002.....	.25
No. 33102.....	.25
No. 33202.....	.25
No. 33302.....	.21
No. 33446.....	5.00
No. 33991.....	.45
No. 33992.....	.55

## RF CHOKES

Many have copied, few have equalled, and none have surpassed the genuine original design Millen Designed for Application series of midget RF Chokes. The more popular styles now in constant production are illustrated herewith. Special styles and variations to meet unusual requirements quickly furnished on high priority.

**General Specifications:** 2.5 mH, 250 mA for types 34100, 34101, 34102, 34103, 34104, and 1mH, 300 mA for types 34105, 34106, 34107, 34108, 34109.

No. 34100.....	\$ .36
No. 34101.....	.30
No. 34102.....	.36
No. 34103.....	.30
No. 34104.....	.36

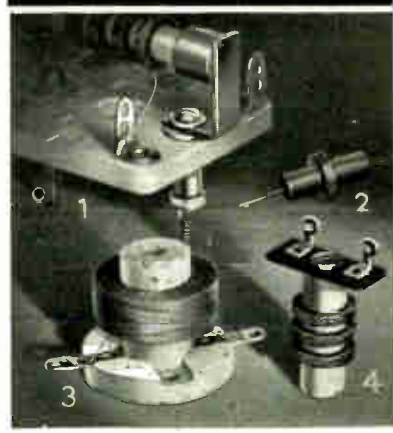

# JAMES MILLEN

MALDEN • MASSACHUSETTS



## CERAMIC PLATE OR GRID CAPS

Soldering lug and contact one-piece. Lug ears annealed and solder dipped to facilitate easy combination "mechanical plus soldered" connection of cable.

No. 36001—9/16"..... \$.21  
 No. 36002—3/4"..... .21  
 No. 36004—1/4"..... .21

## SNAP LOCK PLATE CAP

For Mobile, Industrial and other applications where tighter than normal grip with multiple finger 360° low resistance contact is required. Contact self-locking when cap is pressed into position. Insulated snap button at top releases contact grip for easy removal without damage to tube.

No. 36011—9 16"..... \$.60

## SAFETY TERMINAL

Combination high voltage terminal and thru-bushing. Tapered contact pin fits firmly into conical socket providing large area, low resistance connection. Pin is swivel mounted in cap to prevent twisting of lead wire.

No. 37001, Black or Red..... \$.40  
 No. 37501, Low loss..... .55

## TERMINAL STRIP

A sturdy four-terminal strip of molded black Textolite. Barriers between contacts. "Non turning" studs, threaded 8/32 each end.

No. 37104..... \$.60



## POSTS, PLATES and PLUGS

Designed for Application! Compact, easy to use. Made in black and red regular bakelite as well as low loss brown mica filled bakelite for R.F. uses. Posts have captive head.

No. 37202 Plates..... \$.30  
 No. 37212 Plugs..... .70  
 No. 37222 Posts..... .40

## STEATITE TERMINAL STRIPS

Terminal and lug are one piece. Lugs are Navy turret type and are free floating so as not to strain steatite during wide temperature variations. Easy to mount with series of round holes for integral chassis bushings.

No. 37302..... \$.60  
 No. 37303..... .70  
 No. 37304..... .80  
 No. 37305..... .90  
 No. 37306..... 1.00

## MIDGET COIL FORMS






Made of low loss mica filled brown bakelite. Guide funnel makes for easy threading of leads through pins.

No. 45000..... \$.45  
 No. 45004..... .45  
 No. 45005..... .35
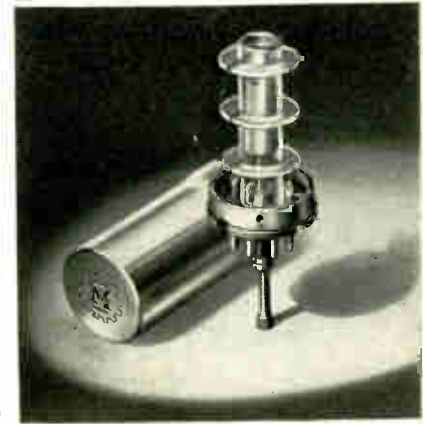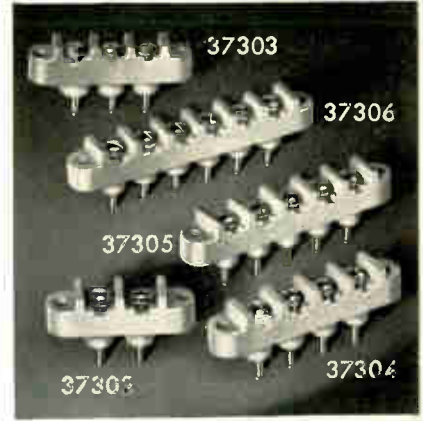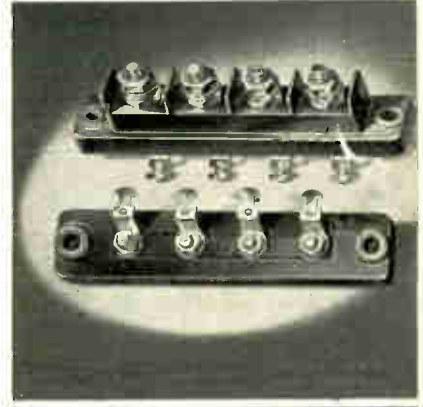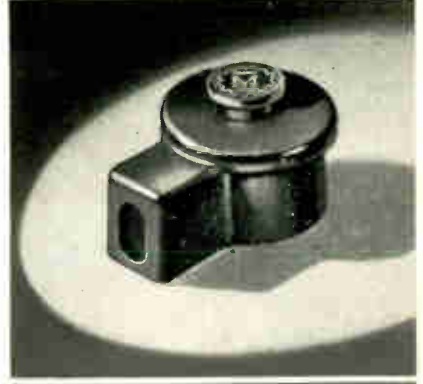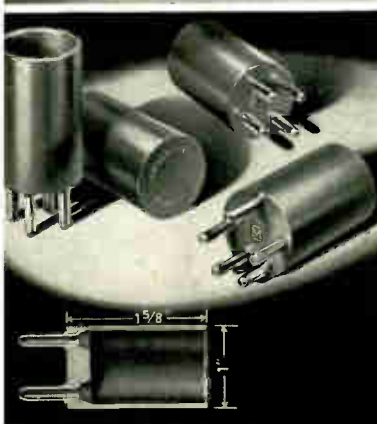
## TUNABLE COIL FORM

Standard octal base of low loss mica-filled bakelite, polystyrene 1/2" diameter coil form, heavy aluminum shield, iron tuning slug of high frequency type, suitable for use up to 35 mc. Adjusting screw protrudes through center hole of standard octal socket.

No. 74001, with iron core..... \$1.85  
 No. 74002, less iron core..... 1.50



We know that our brazing techniques are as good as can be . . . but we also know that you can't always be sure of perfect heat conduction through the brazed metals.

For that reason, we've developed a method of cutting our radiators for the 8002-R out of a solid chunk of metal; giving us a perfect heat conducting path between the core and its fins. This prevents "spot heating" of the tube's copper anode.

It's quite a trick to slice those cooling fins so that they radiate equally from the center and do not vary in thickness. But we mastered it!


And we have hundreds of other "little differences" in the design and construction of the many, many types of transmitting, rectifying and special purpose tubes that comprise the extensive Amperex line.

It's these little differences that combine to make the BIG difference when you

**re-tube with Amperex**

make the  
**BIG**  
difference

the **LITTLE**  
differences

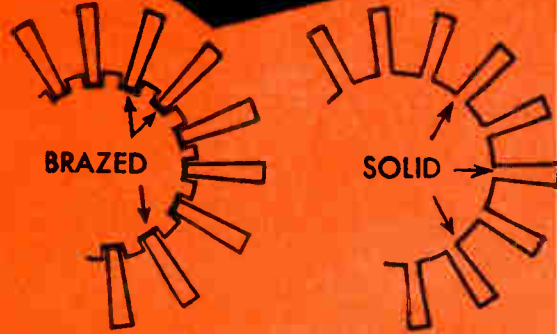

**AMPEREX ELECTRONIC CORP.**

25 WASHINGTON STREET, BROOKLYN 1, N. Y.

In Canada and Newfoundland: Rogers Majestic Limited

11-19 Brentcliffe Road, Leaside, Toronto, Ontario, Canada



# Collins

## transmitters, exciters, receiver and variable frequency oscillator for Amateurs

The Collins ham gear illustrated and described on the following three pages is all of completely new postwar design. It is engineered specifically for amateurs, and reflects a long, successful experience in developing the most advanced types of radio communication equipment for amateur, commercial and military uses.

Collins engineering is evident in every detail of this equipment, from input to output. Cabinets, chassis units, and critical components such as variable pitch machine-wound coils (for precise linear tuning) are Collins-made. Purchased components are made to

Collins specifications and must meet those specifications under searching tests before acceptance. Assembly, wiring, sub-assembly and assembly tests, final tests and adjustments, are held to wartime standards.

It is our intention to furnish the serious amateur with equipment that will give him the best performance that can be had, at reasonable cost. Users of this new equipment are expressing enthusiastic satisfaction.

Write to any of our offices, below, for illustrated bulletins fully describing the Collins amateur equipment in which you are interested.

For best results in amateur radio, it's . . .



**COLLINS RADIO COMPANY, Cedar Rapids, Iowa**

**11 West 42nd Street, New York 18, N. Y. • 458 South Spring Street, Los Angeles 13, Cal.**



## 30K-1 TRANSMITTER

**500 watts CW, 375 watts phone input**

The Collins 30K-1 is a versatile, reliable bandswitching transmitter for the 80, 40, 20, 15, 11 and 10 meter bands. It has an audio peak clipping circuit which permits running the audio gain at a high level, thus maintaining a high level of modulation. With the circuit set to become operative at 90% modulation, the carrier will not be overmodulated, and the increased audio power in the carrier side bands strengthens the signal and improves intelligibility.

Bandswitching eliminates coil changing with the exception of the antenna tuning network, in which an antenna impedance matching circuit is incorporated. Two separate plug-in coils are supplied for this position, one covering 80 and 40 meters, the other covering 20, 15, 11 and 10 meters. This circuit efficiently couples the 30K-1 to any antenna or transmission lines approximating an integral number of  $\frac{1}{4}$  or  $\frac{1}{2}$  wave lengths.

**TUBE LINE-UP:**

- 1—4-125A r-f power amplifier
- 1—6SJ7 speech amplifier
- 1—6SN7 audio amplifier
- 1—6H6 speech clipper
- 1—6B4G modulator driver
- 2—75TH Class B modulators
- 1—5R4GY bias rectifier
- 1—5R4GY low voltage rectifier
- 2—866A high voltage rectifiers

**Dimensions:** 22" wide, 16 $\frac{1}{2}$ " deep, 66 $\frac{1}{2}$ " high.

**Power source:** 115 volts a-c, 60 cps, single phase.

**Net price** (complete with tubes), including 310A-1 Exciter Unit (complete with tubes), Microphone Cord, R.F. Cable, Power Cable and Instruction Book, F.O.B. Cedar Rapids, Iowa . . . . \$1,450.00

## 310A EXCITER UNIT

The bandswitching 310A exciter unit for the 30K-1 has a highly stable permeability tuned oscillator. All circuits are ganged together and controlled by a single tuning knob. The band-lighted dial is calibrated directly in frequency and is adjusted at the factory to an accuracy of better than one dial division on 40 meters. Accuracy on the other bands is directly proportional to the harmonic utilized. The output circuit is also adjusted at the factory for proper excitation of the 30K-1.

**Dimensions:** 17 $\frac{1}{4}$ " wide, 12 $\frac{1}{2}$ " deep, 10 $\frac{1}{2}$ " high.

**Power source:** 115 volts a-c, 60 cps, single phase.



**TUBE LINE-UP:**

- 1—6SJ7 PTO
- 1—6AG7 buffer amplifier
- 1—6AG7 doubler
- 1—807 multiplier
- 1—807 output
- 2—VR105 voltage regulators
- 1—5R4GY rectifier
- 1—6x5 bias rectifier

# FINEST COLLINS EVER MADE



## 75A RECEIVER

### 80, 40, 20, 15, 11 and 10 meter bands

Double conversion and crystal filter controls, with a high frequency first i-f and a low frequency second i-f, provide approximately 50 db image rejection, even on 10 meters, and a band width that is variable in 5 steps from 4 kc to 200 cycles at 2X down. A 2 microvolt r-f signal across the antenna terminals gives normal output with approximately 6 db signal to noise ratio. Precision quartz crystals in the first conversion circuit, the inherent accuracy and stability of the Collins v.f.o. in the second conversion circuit, and linearity and lack of backlash in the tuning mechanism, all contribute to extreme accuracy and stability. Visual tuning is adjusted at the factory to better than 1 division of the band-lighted dial, which reads directly in frequency. Line voltage fluctuations from 90 to 120 volts cause the pitch of a code signal to change less than 100 cycles at 21,500,000 cycles (no voltage regulator tube used).

**Dimensions:** 21 $\frac{1}{8}$ " wide, 12 $\frac{1}{4}$ " high, 13 $\frac{3}{8}$ " deep.

**Power source:** 115 volts a-c, 60 cps, single phase.

**Net price,** complete with 14 tubes (including rectifier), Speaker and Cabinet assembly, and Instruction Book, F.O.B. Cedar Rapids, Iowa . . . \$375.00

## 32V TRANSMITTER

### 150 watts CW, 120 watts phone

A receiver-type cabinet houses the complete band-switching transmitter—r-f (v.f.o. controlled), audio, power supply, and a network for antenna tuning and impedance matching. The v.f.o. is more accurate and stable than most crystals used by amateurs. All stages except the final are permeability tuned. The 32V can be visually tuned with a high degree of accuracy directly in frequency on the band-lighted dial. Audio distortion is less than 8% at 90% modulation with 1000 cps input. The frequency response is within 2 db from 200-3000 cps. Frequency coverage: 80, 40, 20, 15, 11 and 10 meter bands. The 32V may be used for either permanent or portable installations. The only requirements are a simple antenna, a 115 volt a-c power source, and a key or microphone. It may also be used to drive a kilowatt final r-f stage and modulator.

**Net price,** complete with tubes and Instruction Book, F.O.B. Cedar Rapids, Iowa . . . . . \$475.00



#### TUBE LINE-UP:

- 1—6SJ7 oscillator
- 1—6AK6 class A r-f buffer
- 1—6AG7 harmonic amplifier
- 1—7C5 buffer doubler
- 1—7C5 buffer doubler
- 1—4D32 r-f power amplifier
- 1—6SL7 audio amplifier
- 1—6SN7 audio amplifier
- 2—807 modulators
- 1—5Z4 L. V. rectifier
- 2—5R4GY H. V. rectifiers
- 1—OA3/VR75 bias regulator

# FINEST COLLINS EVER MADE


## COLLINS PTO EXCITER UNITS

The Collins 310B-1 and 310C-2 excitors provide not only the flexibility and convenience of variable frequency, but also the accurate calibration and high stability inherent in the Collins 70E-8 permeability tuned oscillator. Frequency is read directly from the dial with precision comparable to that of crystals. There are no reference charts or curves to interpolate. Like all Collins equipment shown on these pages, the 310B-1 and 310C-2 are engineered for extreme frequency stability in spite of line voltage fluctuations.

Both of these excitors have self-contained power supplies. A third, the 310C-1, is similar to the 310C-2, minus power supply.

Net prices, complete with tubes and Instruction Book, F.O.B. Cedar Rapids, Iowa.

<b>310B-1 Exciter Unit</b> .....	<b>\$190.00</b>
<b>310C-1 Exciter Unit</b> .....	<b>85.00</b>
<b>310C-2 Exciter Unit</b> .....	<b>100.00</b>

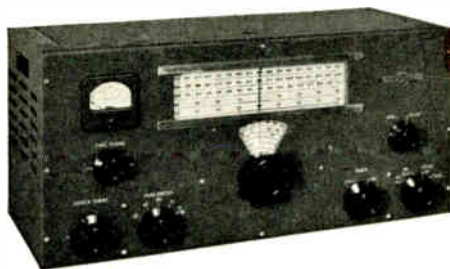


### 310B-1


The 310B-1 is a versatile bandswitching exciter unit, conservatively rated at 15 watts output on all amateur bands under 32 megacycles, and can be used as a complete low power cw transmitter. It has ample drive for a kilowatt final utilizing the new pentode tubes available. With additional multiplication it makes an excellent frequency control for amateur bands in the VHF and UHF regions.
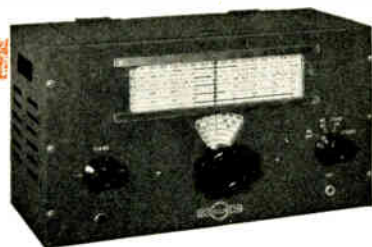
### 310C-2

The 310C-2 consists of a 70E-8 PTO and a multiplier, with an r-f output of approximately 80 volts rms across 40,000 ohms. Its frequency range is from 3.2 mc to 4.0 mc. Its output can be plugged into the crystal socket, or applied to the grid of an 807 buffer stage, thus providing a versatility far greater than any number of crystals, while at the same time maintaining crystal accuracy and stability.



## 70E-8 VARIABLE FREQUENCY OSCILLATOR

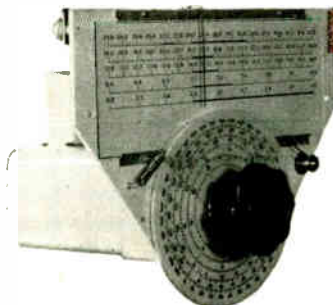

The Collins 70E-8 v.f.o., which is incorporated in the 310B-1, 310C-1 and 310C-2 excitors above, may be purchased separately as illustrated. It is permeability tuned, and has a linear range of 1600 kc-2000 kc. Its overall accuracy and stability are of a very high degree. A secondary frequency standard, continually checked against WWV, is used in the factory calibration of the 70E-8. A special corrector mechanism in the oscillator produces the linear calibration curve. Sixteen turns of the vernier dial are required to cover the 400 kc range. This v.f.o. may be used in an exciter, or in many types of measuring instruments such as heterodyne frequency meters and band-edge spotters.

Net price, complete with tube, Collins type 305H-2 Dial Assembly and Instruction Book, F.O.B. Cedar Rapids, Iowa..... \$40.00





# HAMMARLUND

SINCE 1910



45

## You're Looking at the Finest—



## —a complete Hammarlund station

The "HQ-129-X" RECEIVER is designed to meet the demands of the most critical amateurs. Its design includes every feature essential to finest performance.

The "HQ-129-X" has a continuous range from .54 to 31 megacycles in six separately calibrated bands with continuous bandspread on the four higher bands. In addition, the bandspread dial is calibrated for each of the four most important amateur bands—3.5-4 mc, 7-7.3 mc, 14-14.4 mc and 28-30 mc.

The "HQ-129-X" has the Hammarlund patented variable wide-band crystal filter which works exceptionally well on phone or short wave broadcast signals. There are many other features: Variable antenna compensator, beat oscillator, voltage regulator, series noise limiter, send-recv switch, automatic volume control, calibrated "S" meter, audio gain control, sensitivity control—plus all that goes into a receiver built by engineers who have spent a lifetime designing commercial communication equipment.

The "HQ-129-X" is available complete in a two-tone gray finish including tubes and a 10 inch P. M. dynamic speaker.

"HQ-129-X" with speaker.....Net Price \$189.15

Send for twenty-page technical booklet

The "FOUR-20" TRANSMITTER is a complete crystal controlled CW unit with a full 20 watts output at the antenna terminals on all amateur bands from 80 through 10 meters. The oscillator and multiplier stages are controlled by MONO-SEQUENCE tuning, a Hammarlund development which tunes four circuits to four different, but harmonically related frequencies, by means of one control.

All stages except the final can be switched to any band by means of the band change switch. The final stage uses plug-in coils. Stability is assured by means of an improved oscillator circuit. A tap on the output coil assures a match between the output of the transmitter and any transmission line from 50 to 600 ohms.

FOUR-20 with 10 meter coil.....	Net Price \$120.00
20 meter coil.....	Net Price 2.70
40 meter coil.....	Net Price 2.70
80 meter coil.....	Net Price 2.70

The "FOUR-11" MODULATOR is designed for use with the Four-20 when phone operation is desired. A complete audio system with built-in power supply the Four-11 will produce more than enough power to modulate the 807 final of the transmitter.

FOUR-11 with 8000 ohm output.....	Net Price \$72.50
FOUR-11 with 600 ohm output.....	Net Price 73.50

Send for technical booklet

HAMMARLUND MANUFACTURING CO., INC., 460 West 34th Street, New York 1, N. Y.



### "MC" MIDGET CAPACITORS

Split type rear bearings and noiseless wiping contact. Isalantite insulation. All contacts riveted or soldered. Vibration proof. Nickel plated soldered brass plates.

Code	Capacity	Net
MC-20-S	20 mmf.	\$1.80
MC-35-S	35 mmf.	1.86
MC-50-S	50 mmf.	1.92
MC-50-M	50 mmf.	1.92
MC-75-S	80 mmf.	2.04
MC-75-M	80 mmf.	2.04
MC-100-S	100 mmf.	2.16
MC-100-M	100 mmf.	2.16
MC-140-S	140 mmf.	2.34
MC-140-M	140 mmf.	2.34
MC-200-M	200 mmf.	2.58
MC-250-M	260 mmf.	2.70
MC-325-M	320 mmf.	2.94

"M"—Midline Plates.

"S"—Straight Line Cap. Plates.

### MIDGET "APC" CAPACITORS

This new midget variety of the well known APC condenser is designed for use where space is limited. Size of 100 mmf,  $1\frac{1}{16}'' \times 2\frac{1}{2}'' \times 1\frac{3}{16}''$ . Mounting holes  $1\frac{1}{32}''$  apart. Ideal for H.F. circuits. Isalantite insulation. Nickel plated soldered brass plates.



Code	Capacity	Net
MAPC-15	15	\$ .99
MAPC-25	25	1.02
MAPC-35	35	1.08
MAPC-50	50	1.14
MAPC-75	75	1.26
MAPC-100	100	1.38

### "APC" MICRO CAPACITORS

Far H.F. and very H.F. For I.F. tuning, trimming R.F. Coils or gang capacitors, general padding, etc. Constant capacity under any condition of temperature or vibration. Size 100 mmf.  $1\frac{1}{32}'' \times 1\frac{1}{16}'' \times 1\frac{1}{32}''$ . Isalantite base. Nickel plated soldered brass plates.



Code	Capacity	Net
APC-25	25 mmf.	\$1.02
APC-50	50 mmf.	1.14
APC-75	75 mmf.	1.26
APC-100	100 mmf.	1.38
APC-140	140 mmf.	1.62



### "MTC" TRANSMITTING CAPACITORS

Isalantite insulation. Base or panel mounting. "B" models have rounded plate edges, "C" types have plain plate edges.

Code	Capacity	Net
MTC-20-B	20 mmf.	\$4.05
MTC-100-B	100 mmf.	5.25
MTC-150-C	150 mmf.	5.85
MTC-250-C	260 mmf.	4.65
MTC-350-C	365 mmf.	4.80

### BUTTERFLY CAPACITOR

Designed for use in VHF and UHF applications where the butterfly design is indispensable. Can be used as a single series unit or as a split stator with grounded rotor. Low-loss ceramic end panel, approximately  $1\frac{1}{8}''$  square.



Code	MMF. Cap.		Series Cap.		Net
	Max.	Min.	Max.	Min.	
BFC-12	14.5	3.5	7.9	2.2	\$1.50
BFC-25	27.5	5.0	14.5	3.0	1.68
BFC-38	40.5	6.3	21.0	3.7	1.98

### "FS-135-C" FREQUENCY STANDARD




The FS-135-C is a compact frequency standard which can be built into almost any receiver. A special 100 KC crystal generates marker signals ever 100 KC throughout the entire range of the receiver. The crystal frequency can be adjusted to zero beat with WWV and once this adjustment has been made the accuracy of the unit equals that of a costly frequency standard.

Code	Net
FS-135-C	\$14.25
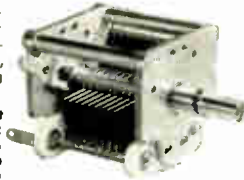
### "RMC" CAPACITOR

Sturdy frame consists of  $\frac{3}{16}''$  aluminum end plates reinforced by three horizontal bars which hold the assembly absolutely rigid. Brackets are provided for mounting either side down, or to a front panel with spacing pillars.



Code	Capacity	Net
RMC-50-S	50 mmf.	\$2.22
RMC-100-S	105 mmf.	2.55
RMC-140-S	143.5 mmf.	2.70
RMC-325-S	327 mmf.	3.39

### FLEXIBLE COUPLINGS



Designed for both insulated and non-insulated applications. The FC-46-S is insulated for 5000 volts with silicone treated ceramic. Overall depth  $1\frac{1}{16}''$ , diameter  $1\frac{1}{4}''$ . The FNC-46-S is a non-insulated coupling. Overall depth  $2\frac{3}{32}''$ , diameter  $1\frac{1}{4}''$ .

Code	Net
FC-46-S—Insulated	\$ .66
FNC-46-S—Non-insulated	.66

### "NZ-10" NEUTRALIZING CAPACITOR

The improved design of the NZ-10 features smooth micrometer capacity adjustment and positive locking. Aluminum plates are smoothly rounded to prevent flashover. Low loss glazed steatite insulators. Aluminum base. Horizontal adjustment.

Dimensions:  $2\frac{1}{8}''$  high x  $1\frac{11}{16}''$  deep.

Code	Capacity	Net
NZ-10	2.3—10 mmf.	\$3.15



PRICES AND ITEMS SUBJECT TO CHANGE WITHOUT NOTICE. WRITE FOR COMPLETE CATALOG.

HAMMARLUND MANUFACTURING CO., INC., 460 West 34th Street, New York 1, N. Y.



# HAMMARLUND

SINCE 1910



47



## SERIES 600 "SUPER-PRO"

### DESCRIPTION

Cheers from the experts—The new Series 600 SUPER-PRO is the finest communications receiver that money can buy. No "warmed over" model, the Series 600 is entirely new in electrical concept and mechanical design—truly "years ahead" of present day receivers. When you check this entirely new SUPER-PRO for such things as image rejection, stability, calibration accuracy, etc. . . . you will find performance that you would not have thought possible. You'll find that "years ahead" in design mean "years ahead" in performance.

Band changing in the new SUPER-PRO is accomplished by means of an ingeniously designed rotary turret which places the coil assemblies of the two R.F., Mixer and Oscillator stages directly adjacent to their respective sections of the four gang tuning condenser where they are electrically most efficient.

By means of the mechanical system used in the SUPER-PRO 600-X both the main and band spread dials are tuned simultaneously with one control and the need for first setting the main dial is eliminated. The dial drive mechanism is entirely gear coupled to the main tuning condenser, producing the kind of calibration accuracy usually associated only with costly laboratory standards.

A double conversion circuit affords two advantages—the high frequency I.F. channel produces so great a degree of image suppression that image response in the receiver is negligible even at the highest frequencies—the low frequency (455 KC) I.F. channel makes possible a receiver of extreme selectivity. The 455 KC I.F. channel has the famous SUPER-PRO crystal filter.

### RANGE

- Band 1 • 540 Kc—1.35 MC
- 2 • 1.35 MC—3.5 MC
- 3 • 3.5 MC—7.0 MC
- 4 • 7.0 MC—14.4 MC
- 5 • 14.4 MC—29.7 MC
- 6 • 29.7 MC—54 MC

### CALIBRATED BAND SPREAD

80, 40, 20, 10 and 6 meter amateur bands.

### TUBES

17 tubes (plus 5U4G rectifier and VR150 voltage regulator) as follows:

- |              |             |
|--------------|-------------|
| Three—6BA6's | One—6SN7GT  |
| Two—6BE6's   | Two—6H6     |
| Two—6C4's    | One—6J5     |
| Four—6SG7's  | Two—6V6GT's |

### SELECTIVITY

Variable in 6 steps, three with crystal out and three with crystal in. From wide band high fidelity to razor sharp single signal reception.

### SENSITIVITY

The sensitivity is better than 2 microvolts throughout the entire frequency range of the receiver, based on a 10 DB signal plus noise to noise ratio.

### PRICE

SPC-600-X receiver (Table Model) with PM Speaker and Speaker Cabinet \$395.00 Net.

*Write For Technical Booklet*

PRICES SUBJECT TO CHANGE WITHOUT NOTICE, SLIGHTLY HIGHER ON WEST COAST

**HAMMARLUND MANUFACTURING CO., INC., 460 West 34th Street, New York 1, N. Y.**



# “Particular People--

those folk at Sangamo! They know that top-notch rigs need precise, stable capacitors to stay on the air—and they have been making just such dependable capacitors for a quarter of a century.”

Old-time hams recognize Sangamo Quality . . . Get acquainted with the Sangamo line today. Your jobber can supply you.



**Type 71  
Diaclor  
Impregnated  
Capacitors**  
600 to 6000 W. V. D. C.



**Type H Mica Capacitors**  
600 to 2500 W. V. D. C.



**Type A Mica Capacitors**  
600 to 2500 W. V. D. C.



**Type E Mica Capacitors**  
Specifically Designed for Hams

**SANGAMO**  
CAPACITORS  
MICA  
PAPER  
SILVER

**SANGAMO**  
ELECTRIC COMPANY  
SPRINGFIELD • ILLINOIS

5C472

# AMPHENOL ROTARY BEAM

## SIGNAL SQUIRTER

### The DX "Champ" on 10 and 20 Meters

- ▶ Unlimited rotation either direction
- ▶ Inductostub matched coupling
- ▶ Two band operation
- ▶ Deluxe rotator
- ▶ Positive position lock
- ▶ High forward directivity
- ▶ High front-to-back ratio
- ▶ Rigid low-loss elements
- ▶ Easily tuned
- ▶ Durable and efficient
- ▶ Non-resonant transmission line

Extremely effective for reception as well as transmission, the Deluxe Dual-Three Signal Squirter is the first rotary beam offering full performance on both 10 and 20 meters.

Each of the two three-element arrays is coupled to the line with a separate Inductostub inductive coupling. Match between antenna and line is so simplified that the Signal Squirter can be assembled, installed and operated without tedious, complicated adjustments.

The strong Deluxe Rotator weighs only 56 pounds.

Base and top diameters only 15 inches. Rotator delivers ample torque through precision reducing gears actuated by non-interfering motor.

The selsyn indicator is synchronized with the array.

Signal Squirter Kit includes Rotator with mounted Inductostub assembly, direction indicator, center section, elements and insulators with all hardware ready for installation.

See your Jobber, or write today for complete details.

*Manufactured under Mims patent number 2,292,791.*



Deluxe Rotator



Direction Indicator

To assure top performance, thousands of alert amateurs also depend on Amphenol for: Twin-lead transmission line, plastic window pane, Silicone compound, stand-off and screw eye insulators, line spreaders, and a complete line of communications components!

**AMERICAN PHENOLIC CORPORATION**  
1830 S. 54th AVE., CHICAGO 50, ILLINOIS

COAXIAL CABLES AND CONNECTORS • INDUSTRIAL CONNECTORS, FITTINGS AND CONDUIT • ANTENNAS • RADIO COMPONENTS • PLASTICS FOR ELECTRONICS

# ASTATIC

## CRYSTAL AND DYNAMIC MICROPHONES


*Preferred and  
Used by Many  
Radio  
Hams*



JT  
SERIES



N  
SERIES

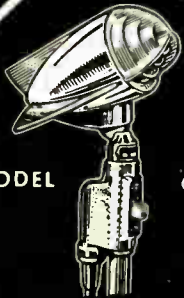

MODEL 600-S



MODEL DN-HZ-S



Grip-  
to-Talk  
Stand



MODEL D-104



Grip-  
to-Talk  
Stand



JT  
SERIES



MODEL 600-S

ON  
STAND

"CONNEAUT"



MODEL  
T-3



DN  
SERIES

THE *Astatic*  
ASTATIC CORPORATION  
CONNEAUT OHIO  
IN CANADA CANADIAN ASTATIC LTD TORONTO ONTARIO

Astatic Crystal Devices Manufactured  
under Brush Development Co. patents

*"Known the World Over!"*

# RADIO'S NEWEST MULTI-PURPOSE INSTRUMENT

## MEASUREMENTS

Model 59

## MEGACYCLE METER

The Model 59 consists of a compact oscillator connected by a flexible cord to its power supply. The instrument is a variable frequency oscillator, an absorption wave-meter, an oscillating detector and a tuned circuit absorption detector. The engineer, technician, service man or amateur will find the Model 59 a most versatile instrument suitable for many applications.

### SPECIFICATIONS:

#### FREQUENCY:

2.2 Mc. to 400 Mc.; seven plug-in coils.

#### MODULATION:


CW or 120 cycles; or external.

#### DIMENSIONS:

Power Unit, 5 $\frac{1}{8}$ " wide; 6 $\frac{1}{8}$ " high; 7 $\frac{1}{2}$ " deep. Oscillator Unit, 3 $\frac{3}{4}$ " diameter; 2" deep.

#### POWER SUPPLY:

110-120 volts, 50-60 cycles; 20 watts.

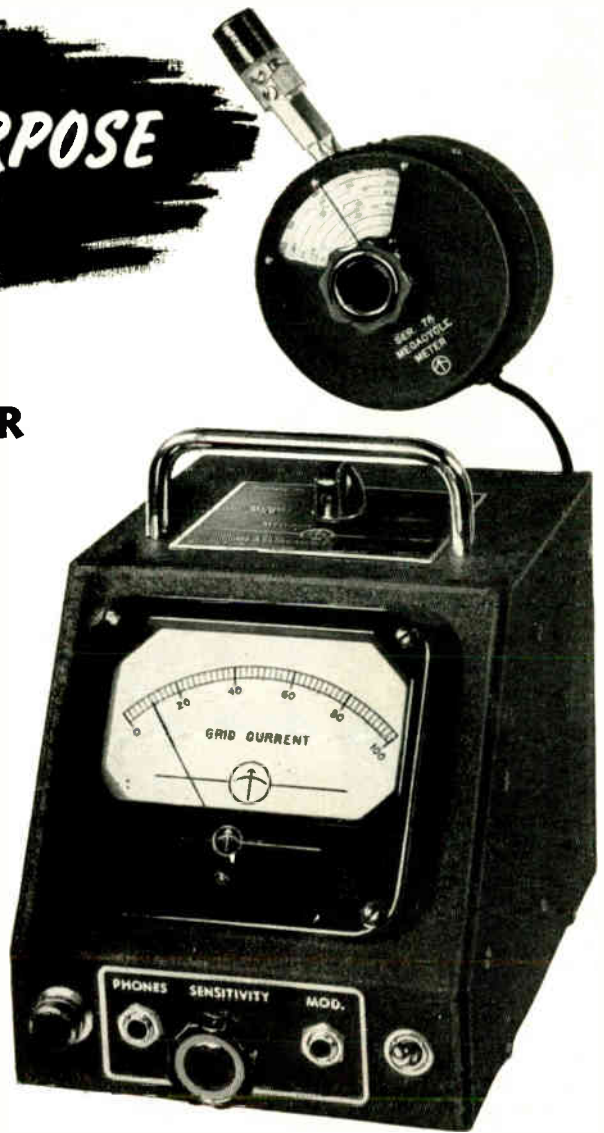

### MODEL 59 APPLICATIONS:

- For the determination of the resonant frequency of tuned circuits, antennas, transmission lines, by-pass condensers, chokes or any resonant circuit.
- For measuring capacitance, inductance, Q, mutual inductance.
- For preliminary tracking and alignment of receivers.
- As an auxiliary signal generator; modulated or unmodulated.
- For antenna tuning and transmitter neutralizing, power off.
- For locating parasitic circuits and spurious resonances.
- As a low sensitivity receiver for signal tracing.

*Descriptive Circular on Request*

**MANUFACTURERS OF**  
Standard Signal Generators  
Pulse Generators  
FM Signal Generators  
Square Wave Generators  
Vacuum Tube Voltmeters  
UHF Radio Noise & Field  
Strength Meters  
Capacity Bridges  
Megohm Meters  
Phase Sequence Indicators  
Television and FM Test  
Equipment

**MEASUREMENTS CORPORATION**  
BOONTON  NEW JERSEY

# There's a **C-D** capacitor



## CORNELL-DUBILIER CAPACITORS

have long been noted for their extra measure of dependability and stability of electrical characteristics. Today — as radio digs deeper and deeper into V-H-F and U-H-F — this C-D “extra” gives hams complete assurance of accurate tuning, frequency stability, and uninterrupted operation.

Cornell-Dubilier Electric Corporation, Dept. AH8, South Plainfield, N. J. Other plants at New Bedford, Worcester and Brookline, Massachusetts, and Providence, Rhode Island.

## KEEP YOUR RIG ON THE AIR — ON YOUR FREQUENCY WITH THESE C-D CAPACITORS

### TYPE TJU

Dykonol transmitter filter copocitor — compact, safety-roted, supplied with universal mounting clamp and heavily-insulated terminals. Hermetically sealed against all climatic conditions. Housed in sturdy steel container, aluminum-pointed non-corrosive finish. Can be mounted in any position. Extra high dielectric strength. Conservative D-C rating — triple tested. Wide range of capacity and voltage values available.

### TYPE 59

Mico transmitter copocitor — extremely adaptable, dependable under the most severe operating conditions. In low-loss, white glazed ceramic case. Low-resistance, wide-pitch terminals. Can be mounted individually or stocked in groups for series or parallel combinations. For grid and plate blocking, coupling, tank and by-pass applications in hi-power hom transmitters.

### TYPE 6

Mica transmitter copocitor for medium power rigs — designed for R-F applications where size and weight must be kept of minimum. Exclusive C-D patented series-stock mico construction. Impregnated for low loss, high insulation, prevention of air voids. Suited for grid, plate, coupling, tank and by-pass uses.


### TYPE 1R

C-D “Silver-Mike” Silvered Mica Copocitors are for use in high Q electronic circuits where frequency stability and minimum loss must be maintained. They are ideally suited for use in circuits where the LC product must be maintained constant. All units are rated at 500 V.D.C. and tested at 1,000 V.D.C.

M I C A • P A P E R • D Y K A N O L



53  
*for every ham application*

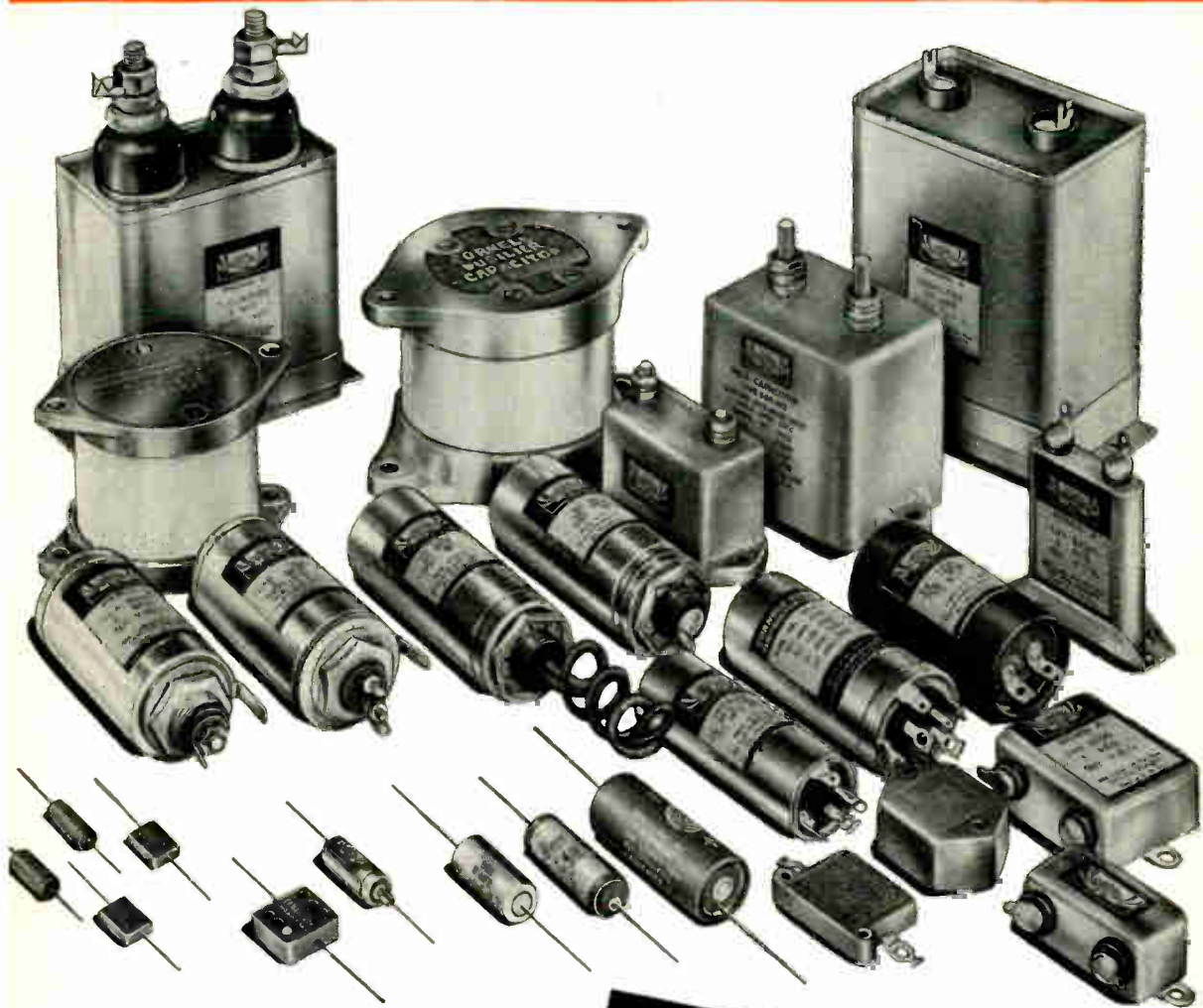

WRITE FOR YOUR  
FREE COPY OF  
CATALOG NO. 200

Gives helpful information and data  
on C-D's complete line of Capacitors  
for every ham application.

**CORNELL-DUBILIER**  
WORLD'S LARGEST MANUFACTURER OF  
**CAPACITORS**



E L E C T R O L Y T I C

# PAR-METAL *Standard* RACKS, CABINETS CHASSIS, PANELS

ADAPTABLE FOR EVERY REQUIREMENT



**Par-Metal Housings for Electronic Apparatus**, offer new features, including beautiful streamlined design, rugged construction, and adaptability. Eliminate need for Special Made-to-Order units on many jobs. Par-Metal offers standard ready-to-use housings for every type of transmitting or receiving apparatus.

Par-Metal offers all the essential equipment needed to build up any sort of a job—from a Small Receiver to a DeLuxe Broadcasting System.



**WRITE FOR  
CATALOG!**




## PAR-METAL PRODUCTS CORPORATION

32-62 49th Street, Long Island City 3, N. Y.

EXPORT DEPT.: ROCKE INT. CORP., 13 E. 40th St., New York 16, N. Y.

your  
basic  
**3R's**  
for correct  
current control

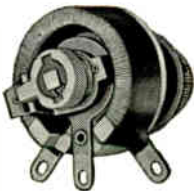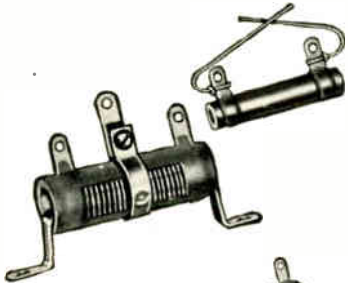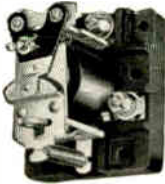↑  
Ward Leonard  
**RELAYS**  
✌  
Ward Leonard  
**RESISTORS**  
✋  
Ward Leonard  
**RHEOSTATS**



**RELAYS**—provide convenient circuit control, protection, and greater operating efficiency . . . help reduce length of connecting leads. Amateur Relays available from stock: Antenna Change-Over, Antenna Grounding, Keying, Band Switching, RF Break-In, Safety, Overload, Underload, Latch-In, Remote Control, Sensitive, Time Delay. Also Industrial and General-Purpose Relays.

**RESISTORS**—exclusive features of VITROHM wire-wound resistors insure that *extra* performance needed in critical circuits. Fixed type in 8 stock sizes from 5 to 200 watts. Adjustable type in 7 stock sizes from 10 to 200 watts. Wide range of resistance values. Stripohm, Discohm, and Plaque types also available.

**RHEOSTATS**—for fixed or variable close control. Protected by tough, acid resistant, crazeless vitreous enamel. Sizes: 25, 50, 100, and 150 watts, in wide range of resistances.

*Authorized Distributors Everywhere*

**WARD LEONARD ELECTRIC COMPANY**  
Radio and Electronic Distributor Division  
53-K West Jackson Blvd., Chicago 4, U. S. A.



**SEND FOR  
FREE CATALOGS**

Write for Amateur Relay Catalog No. D-111, and for Resistor-Rheostat Catalog No. D-2.

**WARD LEONARD**  
**RELAYS • RESISTORS • RHEOSTATS**

Electric control  devices since 1892



# Be Right with OHMITE

## BROWN DEVIL RESISTORS



Small, extra sturdy, wire wound, vitreous enameled resistors for voltage dropping, bias units, bleeders, etc. Proved right in vital installations the world over. In 5, 10 and 20-watt sizes in values to 100,000 ohms.

## DUMMY ANTENNA RESISTORS



To check r.f. power, determine transmission line losses, check line to antenna impedance match. Helps tune up to peak efficiency. Noninductive, non-capacitive, constant in resistance. 100 and 250-watt, in various resistances.

## CENTER TAPPED RESISTORS



For use across tube filaments to provide an electrical center for the grid and plate returns. Center tap accurate to plus or minus 1%. Wirewatt (1 watt) and Brown Devil (10 watt) units, in resistances from 10 to 200 ohms.

## NEW HIGH FREQUENCY CHOKES



Single layer wound on low power factor steatite or bakelite cores, with moisture-proof coating. Seven stock sizes for all frequencies from 2 to 520 mc. Two units rated 600 ma, all others are rated 1000 ma.

## ADJUSTABLE DIVIDOHMS



You can quickly adjust these handy vitreous enameled Dividohm resistors to the exact resistance you want, or put on one or more taps whenever needed for multi-tap-resistors and voltage dividers. In 7 sizes from 10 to 200 watts. Resistances to 100,000 ohms.

## PARASITIC SUPPRESSOR



Small, light, compact noninductive resistor and choke in parallel, designed to prevent u.h.f. parasitic oscillations which occur in the plate and grid leads of push-pull and parallel tube circuits. Only 1 3/4" long over-all and 5/8" in diameter.

## FIXED RESISTORS



Resistance wire is wound over a ceramic core, permanently locked in place, insulated and protected by Ohmite vitreous enamel. Terminated by lugs. 25, 50, 100, 160 and 200-watt stock sizes, in resistances from 1 to 250,000 ohms.

## R. F. POWER LINE CHOKES



Keep r. f. currents from going out over the power line and causing interference with radio receivers. Also used at receivers to stop incoming r. f. interference. Wound on a ceramic core and has a moistureproof coating. Three stock sizes, rated 5, 10, and 20 amp.

**RHEOSTATS...RESISTORS...CHOKES...**

**POTENTIOMETERS...SWITCHES**

*Accurate \* Dependable \* Long-lived*



**CLOSE-CONTROL RHEOSTATS**

Insure permanently smooth, close control in communication, electronic and electrical devices. Widely used in industry. All ceramic, vitreous enameled. 25, 50, 75, 100, 150, 225, 300, 500, 750 and 1000-watt sizes.




**HIGH-CURRENT TAP SWITCHES**

Compact, all ceramic, multi-point rotary selectors for A.C. use. Silver to silver contacts. Rated at 10, 15, 25, 50 and 100 amperes, with any number of taps up to 11, 12, 12, 12, and 8 respectively. Single or tandem.



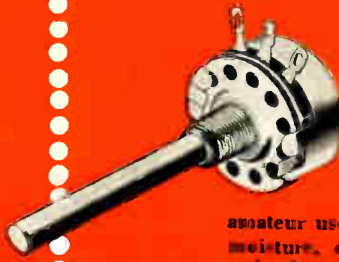**RB-2 DIRECTION INDICATOR POTENTIOMETER**

A compact, low cost unit used in a simple potentiometer circuit as a transmitting element to indicate, remotely, the position of a rotary-beam antenna. Used with a 0-1 millimeter and 6v. battery.



**MOLDED COMPOSITION POTENTIOMETER**


A high quality 2-watt unit with a good margin of safety, for industrial and amateur use. Unaffected by heat, cold, moisture, or length of service. Sold only through Ohmite distributors.



**LITTLE DEVIL INDIVIDUALLY MARKED INSULATED COMPOSITION RESISTORS**

New, tiny, molded fixed resistors each marked with resistance and wattage rating. 1/2 Watt, 1 watt, and 2 watt sizes, ±10% tolerance. Also ±5% in 1/2 and 1-watt sizes. 10 Ohms to 22 megohms. Sold only through Ohmite distributors.

**HANDY OHM'S LAW CALCULATOR**

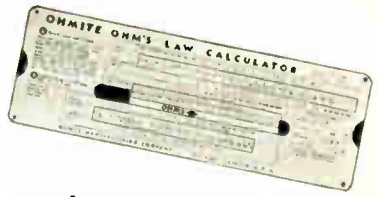

Figures ohms, watts, volts, amperes—quickly, easily. Solves any Ohm's Law problem with one setting of the slide. New pocket size—9"x3" has all computing scales on one side. Resistor color code on back. Send 25¢ in coin to cover handling cost.

**OHMITE**

**OHMITE MANUFACTURING COMPANY**

**4840 Flournoy Street, Chicago, U. S. A. Cable "Ohmiteco"**



**SEND FOR FREE CATALOG**

Stock catalog lists hundreds of units, gives helpful information.

# IT'S SYLVANIA

## RADIO TUBES—CRYSTAL DIODES—



Lock-In  
Tube



Germanium Crystal  
Diode 1N34



... and Duo-Diode 1N35

It can never be a hit or miss proposition when it comes to radio tubes manufactured by Sylvania Electric. Experiments for new and better materials for further improving Sylvania Radio Tubes are carried on constantly.

The famous Lock-In Tube, for example, is so mechanically rugged, so efficient electrically, that it can handle high and ultra-high frequency circuits with ease.

These diodes are well adapted for use as second detectors and d-c restorers in television receivers; frequency discriminators in FM circuits; first detectors; modulators and demodulators.

Supplied in tiny cartridges, they require no heater supply or adjustment and may be wired directly into circuits by means of tinned copper leads.

## ELECTRONIC DEVICES



3-inch Cathode Ray  
Tube Oscilloscope,  
Type 131

This instrument is especially useful in rapid receiver alignment and trouble-shooting. Controls are easily accessible. Hood shades face of cathode ray tube permitting use of instrument in well-lighted room. This 3-inch cathode ray tube is shock-mounted and shielded against stray fields.

Cabinet is steel construction, ventilated with louvers, and finished in attractive pearl-gray baked enamel. Easily carried; weighs only 18 pounds. Eight-foot power cord provided for quick installation.



# SYLVANIA

MAKERS OF RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES;

# FOR...

## TRANSMITTING TUBES— SPECIAL ELECTRONIC TUBES—



3D24



GG-304



GB-302

First of Sylvania's new line of transmitting tubes, the 3D24 is a four-electrode amplifier and oscillator with 45 watt anode dissipation. An outstanding development is the electronic graphite anode, which allows high plate dissipation for small area and maintains constant inter-electrode relationship and uniform tube characteristics.

For the first time, counter tubes with *stable, uniform characteristics* are now available for practical use in the field of radioactivity. The GB-302 beta-ray tube will be very valuable in tracer techniques in industry, research and medicine, especially in medical diagnosis and therapy. Sylvania Type GG-304, the gamma-ray counting companion to the GB-302, is useful in radiological safety surveys and other applications where gamma radiation must be efficiently measured. In addition, the GG-304 can be used for cosmic ray studies, particularly in coincidence work.

**T**hese quality products of Sylvania Electric indicate the scope of manufacturing facilities constantly serving all phases of the radio industry.


*Sylvania Electric Products Inc., Radio Tube Division, Emporium, Pa.*

# ELECTRIC



FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; ELECTRIC LIGHT BULBS

59

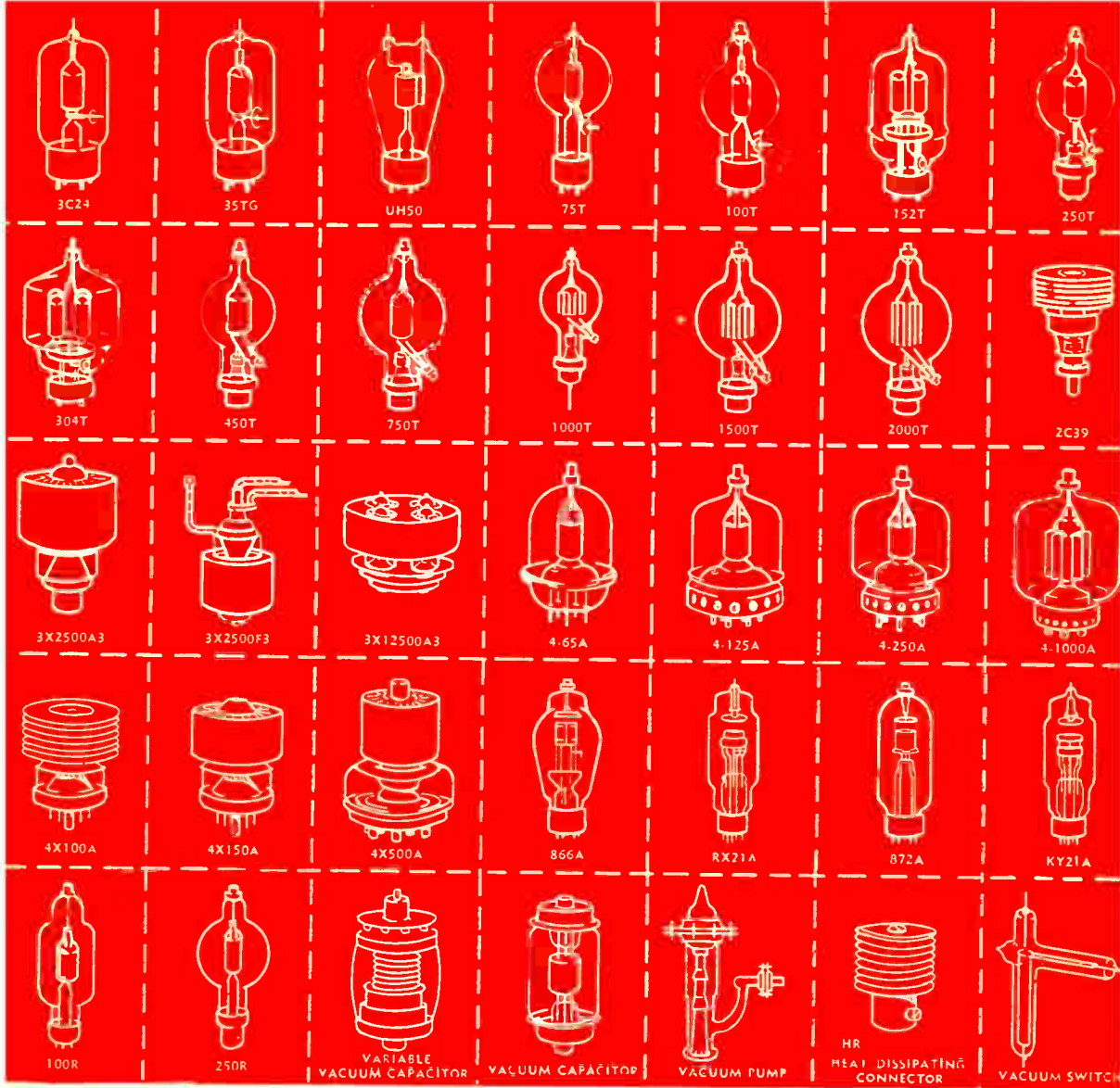

Listed on these pages are Eimac tubes, "proven in service" for more than a decade in the most outstanding electronic equipment in operation. When you invest in a product trade marked "Eimac" you are assured of the utmost in performance and dependability . . . backed by the reputation of America's foremost manufacturer of high-frequency transmitting tubes.

Further data and application notes are available, write direct, or see your dealer.

EITEL-McCULLOUGH, INC., 184 San Mateo Avenue, San Bruno, California

**Eimac**  
REG. U.S. PAT. OFF.  
**TUBES**



# EIMAC TUBES

EIMAC TUBE TYPES	ELECTRICAL							MECHANICAL				MAX. RATINGS				RECOMMENDED HR HEAT DISSIPATING CONNECTORS						
	FIL. VOLTS	FIL. AMPS.	AMP. FACTOR	GRID-PLATE, UUF	INPUT UUF	OUTPUT UUF	TRANSCONDUCTANCE UMHOS	BASE	BASING	MAX LENGTH, INCHES	MAX DIAMETER INCHES	PL. VOLTAGE	PL. CURRENT, MA.	SCREEN VOLTAGE	SCREEN DISSIPATION WATTS	GRID DISSIPATION WATTS	PL. DISSIPATION WATTS	TUBE PRICE	PLATE	GRID		
TRIODES	25T	6.3	3.0	29	1.6	2.4	0.4	2500	M8-071	3G	4.38	1.43	2000	75	...	7	25	6.00	HR-1	...		
	3C24	6.3	3.0	25	1.6	1.8	0.2	2500	M8-071	3G	4.38	1.43	2000	75	...	8	25	6.00	HR-1	HR-1		
	35T	5.0	4.0	30	1.9	4.0	0.2	2850	M8-078	3G	5.5	1.81	2000	150	...	15	50	7.00	HR-3	...		
	35TG	5.0	4.0	30	1.9	1.9	0.2	2850	M8-078	2M	5.75	1.81	2000	150	...	15	50	8.00	HR-3	HR-3		
	UH50	7.5	3.25	13	2.4	2.2	0.4	...	M8-078	2M	7.0	2.69	1250	125	...	13	50	15.00	HR-2	HR-2		
	75TH	5.0	6.5	20	2.3	3.5	0.25	4150	M8-078	2M	7.25	2.81	3000	225	...	16	75	10.50	HR-3	HR-2		
	75TL	5.0	6.5	11	2.3	2.2	0.4	3350	M8-078	2M	7.25	2.81	3000	225	...	13	75	10.50	HR-3	HR-2		
	2C39*	6.3	1.1	...	1.95	6.5	0.30	21,000	...	...	2.75	1.26	1000	100	...	3	100	30.00	...	...		
	100TH	5.0	6.2	40	2.0	2.9	0.4	5500	M8-078	2M	7.75	3.19	3000	225	...	20	100	15.00	HR-6	HR-2		
	100TL	5.0	6.5	12	2.3	2.0	0.4	2300	M8-078	2M	7.75	3.19	3000	225	...	15	100	15.00	HR-6	HR-2		
	152TH	5 or 10	13 or 6.5	20	4.7	7.0	0.5	8300	5000B	4BC	7.63	2.56	3000	450	...	30	150	24.00	HR-5	HR-6		
	152TL	5 or 10	13 or 6.5	11	5.0	4.8	0.8	7150	5000B	4BC	7.63	2.56	3000	500	...	25	150	24.00	HR-5	HR-6		
	3C37*	6.3	2.4	...	3.50	4.25	0.60	8000	...	...	3.10	1.50	1000	...	...	...	...	45.00	...	...		
	250TH	5.0	10.5	37	2.9	5.0	0.7	6650	5001B	2N	10.13	3.81	4000	350	...	40	250	27.50	HR-6	HR-3		
	250TL	5.0	10.5	13	3.5	3.0	0.5	2650	5001B	2N	10.13	3.81	4000	350	...	35	250	27.50	HR-6	HR-3		
	304TH	5 or 10	26 or 13	20	9.4	14.0	1.0	16,700	5000B	4BC	7.63	3.56	3000	900	...	60	300	50.00	HR-7	HR-6		
	304TL	5 or 10	26 or 13	11	10.0	10.0	1.5	16,700	5000B	4BC	7.63	3.56	3000	1000	...	50	300	50.00	HR-7	HR-6		
	450TH	7.5	12.0	38	4.7	8.1	0.8	6650	5002B	4AQ	12.63	5.13	6000	500	...	80	450	70.00	HR-8	HR-8		
	450TL	7.5	12.0	19	5.0	6.6	0.9	6060	5002B	4AQ	12.63	5.13	6000	500	...	65	450	70.00	HR-8	HR-8		
	750TL	7.5	21.0	15	4.5	6.0	0.8	3500	5003B	4B0	17.0	7.13	6000	1000	...	100	750	150.00	HR-8	HR-8		
	1000T	7.5	16.0	30	4.0	6.0	0.6	9050	5004B	4AQ	12.63	5.13	6000	750	...	80	1000	125.00	HR-9	HR-9		
	1500T	7.5	26.0	24	7.0	9.0	1.3	10,000	5005B	4B0	17.0	7.13	6000	1250	...	125	1500	200.00	HR-8	HR-8		
	2000T	10.0	26.0	20	9.0	13.0	1.5	11,000	5006B	4B0	17.75	8.13	6000	1750	...	150	2000	250.00	HR-8	HR-9		
	3X2500A3*	7.5	48	20	20	48	1.2	20,000	...	...	9.0	4.25	5000	2000	...	125	2500	165.00	...	...		
	3X2500F3*	7.5	192	20	95	240	5.	30,000	...	...	9.5	11.1	5000	800	...	600	12,500	700.00	...	...		
	3X12500A3*	7.5	192	20	95	240	5.	30,000	...	...	9.5	11.1	5000	800	...	600	12,500	700.00	...	...		
	TETRODES	4-05 A	6.	3.5	5	08	8.	2.1	4000	...	...	4.25	2.31	1000	150	400	10	5	65	14.50	HR-6	...
		4X100A*	6.	2.8	4.5	.02	14.1	4.7	12,000	...	...	2.56	1.62	1000	250	300	15	4	100	28.00	...	...
		4-125A	5.0	6.2	6.2	0.03	10.3	3.0	2450	5008B	...	5.69	2.72	3000	225	400	3	5	125	25.00	HR-6	...
		4X150A*	6.	2.8	4.5	.02	14.1	4.7	12,000	...	...	2.5	1.75	1000	250	300	15	4	150	31.00	...	...
4-250A		5.0	14.5	...	0.06	12.7	4.5	4000	5008B	...	6.38	3.56	4000	350	600	50	5	250	36.00	HR-6	...	
4X500A*		5.0	12.2	...	0.05	11.1	3.75	5200	...	...	4.32	2.57	4000	300	450	30	5	500	85.00	...	...	
4-1000A	7.5	21	7.2	24	27.2	7.8	10,000	...	...	9.25	5.	6000	700	1000	75	25	1000	108.00	HR-8	...		

\* Extra. Anode insulator (included) is required. Cathode Current.

## EIMAC RECTIFIERS

\* E. J. Johnson, Inc., 151-247 St. 22, N. Y. C.

	MERCURY VAPOR RECTIFIERS				HIGH VACUUM RECTIFIERS			
	866A	RX21A	872A	KY21A	100-R	2-150A	2-150B	250-R
1. Filament Voltage	2.5	2.5	5.0	2.5	5.0	5.0	5.0	5.0
2. Filament Current	5.0 amperes	10 amperes	7.5 amperes	10 amperes	6.5	13.0	13.0	10.5
3. Peak Inverse Voltage	10,000	11,000	10,000	11,000	40,000	30,000	30,000	60,000
4. Peak Plate Current	1.0 amperes	3 amperes	5.0 amperes	3 amperes	...	...	...	...
5. Average Plate Current	.25 amperes	.75 amperes	1.25 amperes	.75 amperes	.100 amperes	.150 amperes	150 amperes	.250 amperes
Price	\$1.75	\$8.00	\$7.50	\$10.00	\$13.50	\$15.00	\$15.00	\$20.00

## EIMAC VACUUM CAPACITORS

Type	VC6-20	VC12-20	VC25-20	VC50-20	VC6-32	VC12-32	VC25-32	VC50-32
Capacity	6-mmfid	12-mmfid	25-mmfid	50-mmfid	6-mmfid	12-mmfid	25-mmfid	50-mmfid
Rating	20-KV	20-KV	20-KV	20-KV	32-KV	32-KV	32-KV	32-KV
RF Peak	...	...	...	...	...	...	...	...
Price	\$12.00	\$13.50	\$16.50	\$20.00	\$14.00	\$16.00	\$19.00	\$22.50

## HEAT DISSIPATING CONNECTORS

Type	Hole Dia.	Price	HR-5	.125	\$ .80
HR-1	.052	\$.60	HR-6	.360	.80
HR-2	.0625	.60	HR-7	.125	1.60
HR-3	.070	.60	HR-8	.570	1.60
HR-4	.1015	.80	HR-9	.570	3.00

## EIMAC DIFFUSION PUMP


HV-1 Diffusion Pump	PRICE ON APPLICATION
An air-cooled vacuum pump of the oil-diffusion type. Capable of reaching an ultimate vacuum of $4 \times 10^{-7}$ mm. of mercury when used with a suitable mechanical forepump. Speed without baffle approximately 67 liters/second at $4 \times 10^{-7}$ to $4 \times 10^{-6}$ mm.	
Eimac Pump Oil	

## EIMAC VACUUM SWITCHES

TYPE	GENERAL DATA	PRICE
VS-2	Single pole double throw switch within a high vacuum adaptable for high voltage switching. Contact spacing .015". Switch will handle R-F potentials as high as 20 Kv. In DC-switching will handle approximately 1.5 Amps at 5 Kv.	\$12.00
VS-1...	Same as above except for slightly smaller glass tubulation.	\$12.00


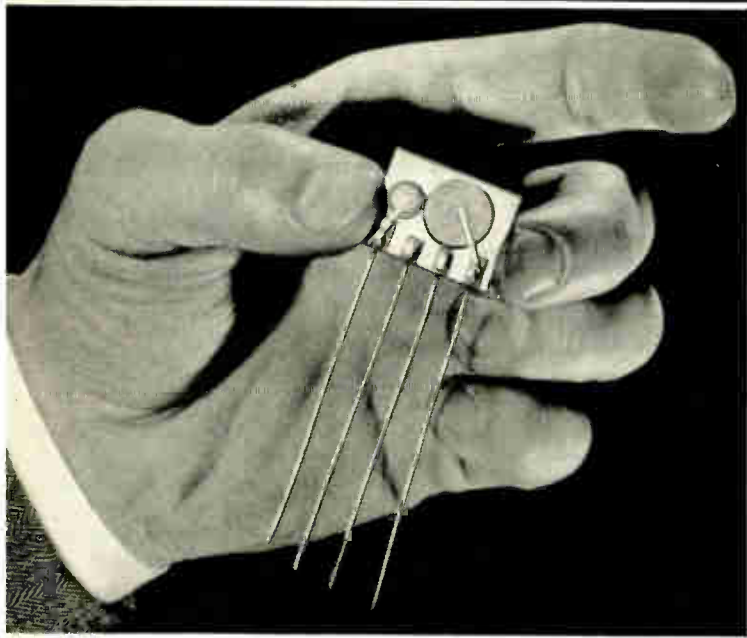
# LOOK TO **Centralab**

First in component research that means lower costs for the electronic industry.



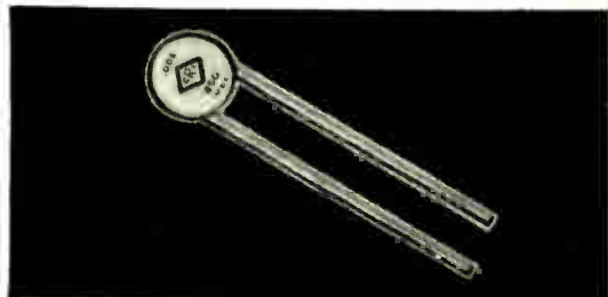
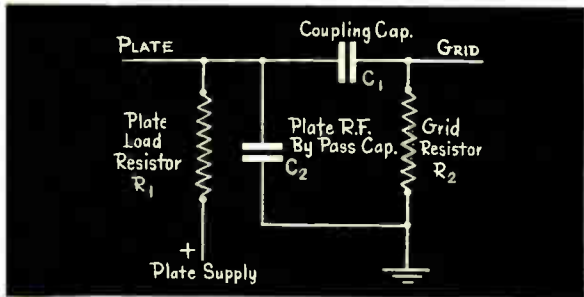
## Here are Exclusive New **CENTRALAB** Developments

**N**EW Multi-Unit "Couplate" assures fast, precision wiring on interstage couplings. First commercial application of the "printed circuit", the *Couplate* is a complete interstage coupling circuit which combines into one compact unit the plate load resistor, the grid resistor, the plate by-pass capacitor and the coupling capacitor.



Each Couplate is an integral assembly of "Hi-Kap" capacitors and resistors closely bonded to a ceramic plate and mutually connected by metallic silver paths "printed" on the base plate.

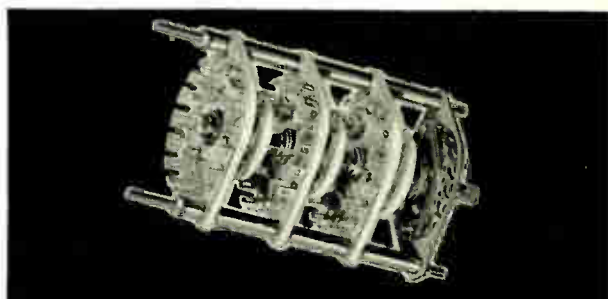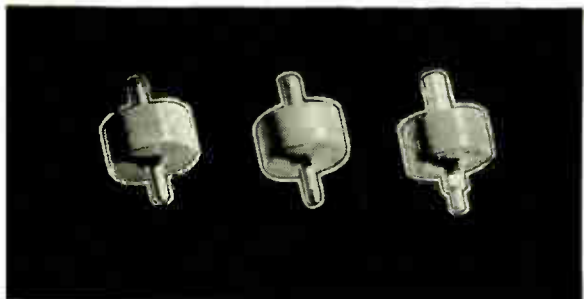In addition, Centralab has just announced a sensational new quality line of miniature ceramic disc capacitors. Permanent Ceramic-X stability of Hi-Kaps assures utmost reliability in small physical size and low mass weight.



For television units, "Hi-Vo-Kaps" offer high voltage, small size... as filter and by-pass capacitors in video amplifiers for high DC voltages with small component AC voltages. Choice of three terminal types.


Specially designed for transmitters, power supply converters, X-ray equipment, etc., CRL medium-duty Power Switch gives efficient performance up to 20 megacycles. Minimum life operation of 25,000 cycles without failure.

# BUY FROM **Centralab**

Makers of a complete line of components for the electronic industry.


**SWITCHES**... complete line featuring high quality, rugged construction for every type of electronic and industrial application.

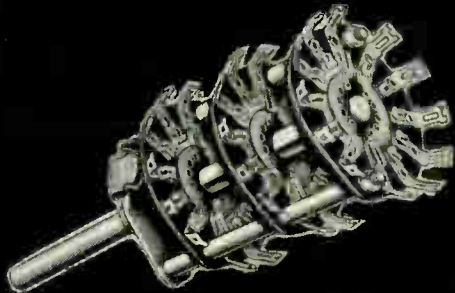- 1) "H" Index: (at right) primarily for band change and general tap switch applications. Spring and ball mechanism. Life test — 5 positions — 10,000 cycles.
- 2) Tone Switch: 3-4-6-8-9 or 10 clips available in tone switch group. All rated at 6 watts. Contact resistance less than  $2\frac{3}{4}$  milliohms.
- 3) Lever Switch: features coil spring mechanism with index spring replaceable without removal of switch from chassis. Life test — 50,000 cycles.
- 4) Power Switch: designed for special industrial and electronic uses. Efficient performance up to 20 megacycles. Life test — 25,000 cycles.



**CONTROLS**... full line featuring dependable performance, long life, low noise level and wide range of possible variations.

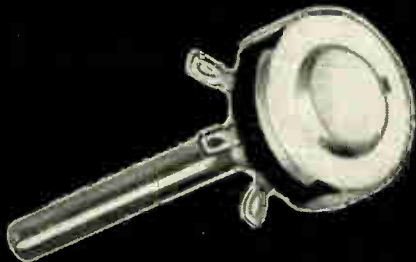- 1) "R" Radiohms: two types — wire wound rated at 3 watts, composition rated at 1 watt. Both types can 1/2 twinned.
- 2) "E" Radiohms: Composition type. Rubbing, contact. 6 different resistance tapers. Rated at 1/4 watt.
- 3) "M" Radiohms: most versatile control of all. Composition type. Rated at 1/2 watt. Many variations possible.
- 4) "I" Radiohms: no bigger than a dime, for miniature receivers, amplifiers. Rating 1/10 watt. Low noise level.
- 5) Switch Covers: five types for "R" Radiohms, 4 types for "M" Radiohms, 1 type for "E" Radiohms. Rated at 3 amp. 125 volts, 1 amp. 250 volts.
- 6) Rheostats: for small motor speed controls, charging rate adjusters, etc. Two sizes available: 25 and 50 watt.



**CAPACITORS**... made with Centralab's high dielectric constant Ceramic X, combining economy, size, and dependability.

- 1) TC Tubulars: stable, no change with aging, humidity or temperature. 4 sizes from 860 to 1 mmf., rated at 500 WVDC.
- 2) BC Tubulars: for use where temperature compensation is unimportant. 4 tube sizes, .000010 to .01 mfd., 500 WVDC.
- 3) High Accuracy: for rigid frequency control applications. Capacity tolerance,  $\pm 5\%$ . Working voltage 500 volts DC.
- 4) High Voltage: Capacity tolerance  $\pm 10\%$ . 5 sizes from 5000 to 15,000 WVDC. Flash test 10,000 to 30,000 VDC.
- 5) Disc: miniature disc capacitors combining reliability with small size, low weight. Dia.  $\frac{3}{8}$ ". Thickness  $\frac{5}{32}$ ".
- 6) Trimmers: four basic types. 500 WVDC. Flash test 1100 VDC. Power factor, less than 0.2% at 1 megacycle.



**CERAMICS**... engineered for special applications requiring specific properties of hardness, coefficient of expansion, porosity. Available to manufacturers only.

- 1) Steatite: Uniform white, high dielectric strength, high mechanical strength, low dielectric loss at high frequencies. Impervious to moisture and common acids, will withstand high temperature and its characteristics remain stable with age.
- 2) Cordierite: For use where low thermal expansion and high resistance to heat shock is desired. Composed chiefly of Cordierite, a magnesium aluminum silicate crystalline material. Low in porosity. Variations available.
- 3) Zirconite: Has low coefficient of expansion and good thermal shock properties plus high strength characteristics. For extruded or wet-pressed shapes. Variations available.



**Speak out...  
and be Heard!**

*Overcome Room  
Reverberation...  
Cut through QRM*

**THE CARDAX**  
CARDIOID CRYSTAL MICROPHONE

**The Only High Level Cardioid Crystal  
Microphone with Dual Frequency Response**

You can sit back and relax . . . when you call with the CARDAX. E-V Mechanophase\* unidirectivity overcomes room reverberation, permits working at greater distance from microphone. Dual Frequency Response gives you high fidelity for clear channel or rising characteristic for *extra crisp* speech signals that cut through QRM. Brings *more* and *better* QSO's. For DX or Rag-Chewing, there's nothing like it! Smart looking, too! CARDAX, Model 950, lists at \$39.50.

*Authorized Distributors Everywhere*



NO FINER CHOICE THAN

**Electro-Voice**

**ELECTRO-VOICE, INC., BUCHANAN, MICH.** Export Division: 13 East 40th St., New York 16, N. Y. Cables: Arlab



"Cardyne" Cardioid Dynamic  
Models 731 and 726



Crystal—Model 910  
Dynamic—Model 610



High Fidelity Dynamic  
Model 830



"Comet" Crystal Model 902  
Dynamic—Model 601



Send for Catalog 101  
Get valuable data on  
today's most complete  
microphone line.

\*Patent Pending. Crystal Microphones Licensed under Brush Patents



# PLUS VALUES...

**THEY MEAN YOUR DOLLARS BUY MORE WHEN  
YOU CHOOSE GENERAL ELECTRIC TUBES!**



**+1** There's a G-E tube distributor near you, ready and glad to consult with you on selecting the right tube for any application. He deals with scores of other amateurs, and based on their experience and preferences, can help make sure your dollars are shrewdly invested. His stocks are substantial; his service of a high standard that fully warrants the statement "Your G-E tube distributor is local ham-tube headquarters."



**+2** Lighthouse Larry — G.E.'s up-to-the-minute home-office ham who lives, breathes, and sleeps amateur radio — likes nothing better than to hear from you and discuss your technical problems. The answers you get from him are especially helpful because Larry has at hand the research, engineering, and test facilities of the General Electric Company which is actively engaged in all phases of the radio industry. Lighthouse Larry will be glad to guide you personally in every step of your progress as a ham.

948 by  
eral Elec-  
Company

**+3** G.E.'s Ham News — 8 fact-filled pages of timely hints for alert amateurs — keeps you abreast of latest circuit developments. You owe it to yourself to see your G-E tube distributor regularly for the newest bi-monthly edition. The R-9 Pre-amplifier, the new Guillotine Converter — these are two of the important designs already announced in *Ham News*, with full instructions on how to build. Don't miss a copy!



**PLUSSES** like these are cartoned with every G-E ham tube. The General Electric monogram signifies not just a product, but the full, helpful service that goes with that product. And, most important of all, you can count on G-E tube quality, dependability, advanced design, as solid foundation stones for the efficient performance of your rig! *Electronics Department, General Electric Company, Schenectady 5, New York.*

—and other popular G-E ham types (a complete line) as listed with ratings and prices in Booklet ETX-19. Ask your G-E tube distributor for your free copy.

ELECTRONIC TUBES OF ALL TYPES FOR THE RADIO AMATEUR

# GENERAL ELECTRIC



CUSTOM MADE

TECHNICAL CERAMICS

FOR ELECTRONIC AND ELECTRICAL USES (SOLD ONLY TO MANUFACTURERS)

**ALSIMAG**

TRADE MARK

**AMERICAN LAVA CORPORATION**

46TH YEAR OF CERAMIC LEADERSHIP

CHATTANOOGA 5, TENNESSEE



# ACCURACY — STABILITY ACTIVITY — HIGH OUTPUT DEPENDABILITY *at Low Cost*

For years PR Precision Crystals have set performance standards in all types of service . . . amateur, commercial, marine, broadcast, mobile, police, aircraft. PRs are the foremost choice of amateurs . . . the most critical users of crystals today. PR Crystals have earned this reputation by LOW DRIFT characteristics, less than 2 cycles per MC per degree Centigrade . . . HIGH OUTPUT AND DEPENDABILITY even at highest permissible crystal currents . . . ACCURACY within .01 per cent of specified frequency . . . HIGH ACTIVITY especially desirable for break-in CW operation . . . X-ray orientation . . . CONTAMINATION AND MOISTURE-PROOF through permanent gasket seal . . . 1/2-inch pin spacing. Every PR is UNCONDITIONALLY GUARANTEED. Your EXACT FREQUENCY (Integral Kilocycle) WITHIN AMATEUR BANDS, AT NO EXTRA COST. See your jobber for PRs. His stock is complete for ALL BANDS. Accept no substitute. — Petersen Radio Company, Inc., 2800 West Broadway, Council Bluffs, Iowa. (Telephone 2760)

## COMMERCIAL PR Type Z-1

## 80 and 40 METERS PR Type Z-2

## 20 METERS PR Type Z-3

## 10 METERS PR Type Z-5

Frequency range 1.5 to 10.5 MC. Designed for rigors of all types of commercial service. Calibrated .005 per cent of specified frequency. Weight less than 3/4 ounce. Sealed against moisture and contamination. Meets FCC requirements for all types of service.

Rugged. Low drift fundamental oscillators. High activity and power output. Stands up under maximum crystal currents. Stable, long-lasting, permanently sealed. . . . \$2.75 Net

Harmonic oscillator. Low drift. High activity. Can be keyed in most circuits. Stable as fundamental oscillators. Fine for doubling to 10 and 11 meters or "straight through" 20 meter operation. \$3.75 Net

Harmonic oscillator for "straight through" mobile operation and for frequency multiplying to VHF. Heavy output in our special circuit. . . . \$5.00 Net



Z-1



Z-2



Z-3



Z-5

# PR Precision CRYSTALS

**hp** ...for all important  
electronic measurements



hp-200C Resistance-Tuned Audio Oscillator



hp-330B Noise and Distortion Analyzer



hp-400A Vacuum Tube Voltmeter



hp-430A Amplifier

-hp- precision instruments combine in one compact unit, the essential qualities of speed, accuracy and versatility. They are ideal for use anywhere...in laboratory, broadcasting, production or amateur radio.

**AUDIO OSCILLATORS**

**AUDIO SIGNAL GENERATORS**

**LOW FREQUENCY STANDARD SQUARE WAVE GENERATOR WAVE ANALYZER**

**DISTORTION ANALYZERS**

**ATTENUATOR**

**VACUUM TUBE VOLTMETERS**

**AMPLIFIER ELECTRONIC FREQUENCY METER**

**ELECTRONIC TACHOMETER**

**UHF SIGNAL GENERATORS**

**REGULATED POWER SUPPLY**

INSTRUMENT	FREQUENCY	CALIBRATION
<b>200A</b>	35 cps to 35 kc	Dial Scale—25-350 cps Calibration Points—Ranges—3 (1, 10, 100 times dial calibration)
<b>200B</b>	20 cps to 20 kc	Dial Scale—20-200 cps Calibration Points—Ranges—3 (1, 10, 100 times dial calibration)
<b>200C</b>	20 cps to 200 kc	Dial Scale—20-200 cps Calibration Points—Ranges—4 (1, 10, 100, 1000 times dial calibration)
<b>200D</b>	7 cps to 70 kc	Dial Scale—7-70 cps Calibration Points—7 Ranges—4 (1, 10, 100, 1000 times dial calibration)
<b>202D</b>	2 cps to 70 kc	Dial Scale—7-70 cps Calibration Points—7 Ranges—4 (1, 10, 100, 1000 times dial calibration) Dial Scale A—2-50 cps Calibration Points
<b>200I</b>	6 cps to 6 kc	Dial Scale A—6-20 cps Calibration Points—1 Ranges—3 (1, 10, 100 times dial calibration) Dial Scale B—20-60 cps Calibration Points—1 Ranges—3 (1, 10, 100 times dial calibration)
<b>201B</b>	20 cps to 20 kc	Dial Scale—20-200 cps Calibration Points—95 Ranges—3 (1, 10, 100 times dial calibration)
<b>205A</b>	20 cps to 20 kc	Dial Scale—20-200 cps Calibration Points—80 Ranges—3 (1, 10, 100 times dial calibration)
<b>205AG</b>	20 cps to 20 kc	Dial Scale—20-200 cps Calibration Points—80 Ranges—3 (1, 10, 100 times dial calibration)
<b>205AH</b>	1 kc to 100 kc	Dial Scale—1-10 kc Calibration Points—130 Ranges—2 (1, 10 times dial calibration)

FUNCTION	INSTRUMENT	FREQUENCY	ACCURACY
<b>LOW FREQUENCY STANDARD SQUARE WAVE GENERATOR WAVE ANALYZER</b>	<b>100A</b>	Output—100 kc, 10 kc, 1 kc, 100 cps	±0.01% over room temperature variation of 33° C
	<b>100B</b>	Output—100 kc, 10 kc, 1 kc, 100 cps	±0.001% from -10° C to +50° C
	<b>210A</b>	Input—20 cps to 100 kc	Square within ±1% from 20 cps to 10 kc
	<b>300A</b>	Measurement Range—30 cps to 16 kc	Frequency—±3% Voltage overall—±5%
	<b>320A</b>	Measures at—400 cps and 5 kc	Less than ±5% (at distortions of 30% or less)
<b>DISTORTION ANALYZERS</b>	<b>320B</b>	Measures at—50 cps, 100 cps, 400 cps, 1 kc, 5 kc and 7.5 kc	Less than ±5% (at distortions of 30% or less)
	<b>325B</b>	Measures at—30 cps, 50 cps, 100 cps, 400 cps, 1 kc, 5 kc, 7.5 kc, 15 kc	Voltmeter overall—±3% Distortion—Less than ±5% (at distortion of 30% or less)
	<b>330B</b>	Measurement Range—20 cps to 70 kc	Voltmeter overall—±3% Distortion—±3% for distortion levels as low as
<b>ATTENUATOR</b>	<b>350A</b>	Max. input—100 kc	Each Resistor—±0.5% Response—Accumulative Error at 100 kc approx. 1 db in 50 db
<b>VACUUM TUBE VOLTMETERS</b>	<b>400A</b>	Measurement Range—10 cps to 1 mc	10 cps to 100 kc—±3% 100 kc to 1 mc—±5%
	<b>410A</b>	Measurement Range—20 cps to 700 mc	±3% AC and DC Frequency Response flat within 1 decibel 20 cps to 700 mc
<b>AMPLIFIER ELECTRONIC FREQUENCY METER</b>	<b>450A</b>	10 cps to 10,000,000 flat within ±1% db	40 or 20 db gain ±1% db
<b>ELECTRONIC TACHOMETER</b>	<b>500A</b>	Measurement Range—5 cps to 50 kc in 10 ranges	±2% of full scale
<b>UHF SIGNAL GENERATORS</b>	<b>505A</b>	An Electronic Frequency Meter and a Tachometer Assembly calibrated to measure speeds up to 7,000,000 RPM	
	<b>610A</b>	500 to 1350 mc	±1 db over entire range
	<b>616A</b>	1800 to 4000 mc	±1 db over entire range
<b>REGULATED POWER SUPPLY</b>	<b>710A</b>		



hp-616A UHF Signal Generator



FREQUENCY RESPONSE	STABILITY	ACCURACY OF CALIBRATION	POWER OUTPUT INTO RATED LOAD	LOAD IMPEDANCE	DISTORTION AT RATED OUTPUT	HUM LEVEL BELOW RATED OUTPUT
#1 decibel, 20 cps to 15 kc	±2%	±2%	1 watt	500 ohms	less than 1%	60 db
#1 decibel, 20 cps to 15 kc	±2%	±2%	1 watt	500 ohms	less than 1%	60 db
#1 decibel, 20 cps to 150 kc	±2%	±2%	100 milliwatts	1000 ohms	less than 1% 20 cps to 20 kc	60 db
#1 decibel, 7 cps to 70 kc	±2%	±2%	100 milliwatts	1000 ohms	less than 1% 10 cps to 20 kc	60 db
#1 decibel, 7 cps to 70 kc #2 decibels, 7 cps to 7 cps	±2%	±2%	100 milliwatts	1000 ohms	less than 2% 7 cps to 70 kc	60 db
#1 decibel, 6 cps to 6 kc	±2% or ±1% with Standardization	±2%	100 milliwatts	1000 ohms	less than 1% 10 cps to 6 kc	60 db
#1 decibel, 20 cps to 20 kc	±2% or ±1% with Standardization	±2%	3 watts	600 ohms	less than 1% at 3 watts (less than 1/2% at 1 watt)	60 db
Down 2.0 decibels at 20 cps Down 1.0 decibel at 20 kc at full output	±2% or ±1% with Standardization	±2%	5 watts	50, 200, 500, 5000 ohms (all ct)	less than 1% 30 cps to 20 kc at rated output	60 db below output or 90 db below zero level whichever is larger
Generator—down 2.0 db at 20 cps Down 1.0 db at 2.0 kc at full output Voltmeter—within ±0.2 db of 400 cps ref. from 20 cps to 20 kc	±2% or ±1% with Standardization	±2%	5 watts	Generator—50, 200, 500, 5000 ohms (all ct) Voltmeter—5000 ohms input impedance	less than 1% 30 cps to 20 kc at rated output	60 db below output or 90 db below zero level whichever is larger
±1 db from 10 kc ref. 1 kc to 100 kc at full output	±1% after 1 1/2 hour warm-up	±2%	5 watts	50, 200, 500, 5000 ohms (all ct)	less than 1% at 1 watt 3% at 5 watts	65 db below output or 65 db below zero level whichever is larger

VOLTAGE	IMPEDANCE	MISCELLANEOUS CHARACTERISTICS
Output—5 volts into 1000 ohms	Load—Not less than 1000 ohms	Wave Shape—Sinusoidal— total distortion not more than 4% on open circuit
Output—5 volts into 1000 ohms	Load—Not less than 1000 ohms	Wave Shape—Sinusoidal— total distortion not more than 4% on open circuit
Input—min. 2; max. 200 Output—60 v peak to peak on open circuit	Input—25,000 ohms Internal—Each side, 500 ohms to ground	Wave Shape—Square (1 microsecond to 90% of maximum) Attenuator—20 db in 5 db steps
Input—1 mv to 500 v	Input—200,000 ohms	Variable Selectivity at 40 db down from resonance: max. selectivity is 30 cps; min. selectivity is 145 cps; Dial Calibration Points—62
Max. Input—100 v	Analyzer Input—20,000 ohms Detector Input—Should be not less than 100,000 ohms	Max. Attenuation: Fundamental—more than 60 db (1%). Second and higher harmonics—less than 5%. Filters—Tuned to nominal frequencies within ±5% (non-adjustable). Attenuator—70 db in 1 db steps.
Max. Input—100 v	Analyzer Input—20,000 ohms Detector Input—Should be not less than 100,000 ohms	Max. Attenuation: Fundamental—more than 60 db (1%). Second and higher harmonics—less than 5%. Filters—Tuned to nominal frequencies within ±5% (non-adjustable). Attenuator—70 db in 1 db steps.
Voltmeter Measurement Range—.01 v to 300 v in 9 ranges Distortion—min. input 1 v for .1% distortion Noise—min. input .003 volts for full scale	Amplifier Input— 200,500 ohms shunted by approx. 24 mmd Voltmeter Input— 1 megohm (min.) shunted by approx. 32 mmd	Max. Attenuation: Fundamental—more than 60 db (1%). Second and higher harmonics—less than 5%. Filters—Tuned to nominal frequencies within ±5% (adjustable—1%). Voltmeter—Average Reading (calibrated in rms volts and in db above a 1 mw, 600 ohm level).
Voltmeter measurements— .01 v to 300 v in 9 ranges Distortion—min. input 1 v for .1% distortion Noise—minimum input—0.0003 v for full scale	Amplifier Input—200,000 ohms shunted by approx. 24 mmd Voltmeter Input—1 megohm (min.) shunted by approx. 32 mmd	Max. Attenuation: Fundamental—more than 60 db (0.1%). Second and higher harmonics—less than 10%. Voltmeter—Average reading (calibrated in rms volts and db above a 1 mw, 600 ohm level)
Maximum Input—50 v	Input—500 ohms—one side grounded Output—500 ohms—one side grounded	Attenuation—110 db in 1 db steps
Measurement Range— .03 v to 300 v in 9 ranges	Input— 1 megohm (min.) shunted by approx. 16 mmd	Voltmeter—Average Reading (calibrated in rms volts and in db above a 1 mw, 600 ohm level)
Measurement Range— 1 to 300 VAC in 6 ranges 1 to 1000 VDC in 7 ranges	Input—AC—8 megohms in parallel with 1.3 mmd at frequencies below 10 mc Input—DC—100 Megohms	AC Voltmeter—Peak reading instrument will indicate voltage to 3000 mc Ohmmeter: 0.2 ohms to 500 megohms in 7 ranges
Output 10 volts 1% distortion	Input—1 megohm Output—3000 ohms or more	Increases sensitivity of 400A, 100 times
Input—0.5 v to 200 v	Input—50,000 ohms	Separate External Attachments—1. Photocell Input (jack provided), 2. Esterline-Angus 1 mil, 1400 ohm Automatic Recorder (jack provided)
Output 0.1 microvolts to 0.1 volts	50 ohm line coaxial type N connector	Internal pulse modulation. External pulse and amplitude modulation.
Output 0.1 microvolts to 0.1 volts	50 ohm line coaxial type N connector	Internal pulse and FM modulation. External pulse modulation.
180 to 360 VDC (regulated) 6.3 VAC ct (unregulated)		Output constant within approx. 1% for loads from 0 to 75 ma and for line- voltage variations of ±0%. Noise and hum less than 0.005 v.

Brief specifications of these nationally known instruments are shown here. Full details are available in the new **-hp-** catalog. Write for your free copy, today.

Hewlett-Packard Company · 1450 Page Mill Road · Palo Alto, Calif.

**hp** laboratory instruments  
FOR SPEED AND ACCURACY



410A Vacuum Tube Voltmeter



**LCETI**

*Laboratory Caliber Electronic Test Instruments*

**5 WORDS** that assure **ACCURACY, DEPENDABILITY** and **VALUE**  
in all **SILVER** test instruments

You . . . and every serious service technician . . . have long dreamed of your shop equipped with the same caliber of laboratory instruments found in the factories making the radios you must service. Today's complex AM, FM and Television receivers can't be efficiently serviced by anything less.

Under war pressure McMurdo Silver devised new techniques to lift the manufacture of laboratory-type instruments out of the costly model-shop. He discovered how to put them on the low-cost, high-volume production line. The result is instruments of laboratory precision, accuracy, dependability . . . at prices far below what you'd expect to pay. These are the same identical Laboratory Caliber Electronic Test Instruments the big manufacturers, universities and the government select.

Can you afford less than the best — when the best costs you less?

**MODEL 906 FM/AM SIGNAL GENERATOR:** 8 ranges calibrated  $\pm 1\%$  accurate, 90 kc. thru 210 mc. 0-100% variable 400 $\sim$ AM; 0-500 kc. variable FM sweep built-in. Metered microvolts; variable 0-1 volt. Strays lower than \$500 laboratory generators. Only \$99.50 net.

**"VOMAX" UNIVERSAL V.T.V.M.:** The overwhelming choice of experts. 51 ranges, d.c., a.c., a.f., i.f., r.f., current, db., and resistance. Visual signal tracing to 500 mc. New 5" pencil-thin flexible r.f. probe. Only \$59.85 net.

**MODEL 904 CONDENSER/RESISTANCE TESTER:** Measures accurately  $\frac{1}{4}$  mmfd. thru 1,000 mfd.;  $\frac{1}{4}$  thru 1,000 meg $\Omega$ . Internal 0-500 V. variable d.c. polarizing voltage. Measures condensers with rated d.c. volts applied. Only \$49.90 net.

**MODEL 905 "SPARX" SIGNAL TRACER:** Visual and audible tracing; also tests phono pickups, microphones, speakers, PA amplifiers. Is your shop test-speaker, too. 20 $\sim$  thru 200 mc.; PM speaker; mains-insulated transformer power supply. Only \$39.90 net.

OVER 36 YEARS OF RADIO ENGINEERING ACHIEVEMENT  
*McMurdo Silver Co., Inc.*  
EXECUTIVE OFFICES: 1240 MAIN ST., HARTFORD 3, CONN.  
FACTORY OFFICE: 1249 MAIN ST., HARTFORD 3, CONN.

SEND FOR COMPLETE CATALOG. See these and Silver communication transmitters, receivers, "Micro match," Xtal-controlled VFO, pre-tuned freq. multiplier at your jobber.

# SILVER

## SPELLS TOP VALUE AT LOWEST COST

Exactly as SILVER is known the world over for producing Laboratory Caliber Electronic Test Instruments — LCETI — for critical users at unbelievably low prices, so you'll find that your dollars will buy you the most in amateur equipment when you select SILVER. Examine the instruments here illustrated and highlighted. Compare — and you'll see why more and more amateurs turn to SILVER.



908



800



700



701



801

**MODEL 908 MICROMATCH** standing wave ratio and r.f. wattmeter will let you put more power into your antenna — from your present transmitter — for only **\$29.90**.

**MODEL 800 U.H.F. RECEIVER** is E. P. Tilton's A.R.R.L. HANDBOOK, "T.R.F. Superregenerative Receiver" — the sweetest performing 2½ and 1¼ meter, non-radiating receiver we've seen — in finished commercial form for only **\$39.75** less tubes and power supply.

**MODEL 700 U.H.F. TRANSMITTER** is xtal controlled for maximum signaling effectiveness in 2½ and 1¼ meter bands, yet costs you only **\$36.95** less tubes and power supply.

**MODEL 701 TRANSMITTER** goes into more amateur stations to produce more CW and phone DX than anything else, it seems. A 6AQ5 Tritet drives an 807 to 75 watts CW, 30 watts phone, input, 80 through 6 meters. Modulator is built-in. Less coils (3 per band at \$.50 ea.), power supply, 4 tubes and crystal, it's the outstanding transmitter "buy" at **\$36.95**.

**MODEL 801 RECEIVER** covers 450 kc. through 60 mc., consisting of r.f. stage, regenerative detector, two a.f. stages and built-in speaker, it's the old reliable standby — just the thing for portable, emergency, test — and serious ham reception. **\$29.95** for 6.3 volt operation; **\$28.95** for 1.5 volt dry battery tubes; coils, **\$1.00** per pair.

**MODEL 703** is new — a pre-tuned bandpass freq. multiplier. Driven by any VFO or xtal, it puts you in any band 80 through 6 meters, on selected freq. as fast as you can turn two knobs. Its 807 gives 40 watts max. output and instant control of every band. Price **\$49.90**.

**MODEL 802 SUPER-HETERODYNE RECEIVER** is an amateur-band-only receiver using i.f. regeneration to give variable phone up to single-signal CW selectivity. Following A.R.R.L. HANDBOOK teachings, it provides more than usual 8-tube results, over 7 feet of band spread on 80, 40, 20, 16, 11, 10 and 6 meter bands, all for only **\$38.95** less tubes, power supply and coils at **\$1.00** per pair.

**MODEL 903 ABSORPTION WAVEMETER** is close to the most useful instrument in any shack. Thousands in use attest its prime necessity. Price is but **\$3.30** net, plus **\$.65** ea. for plug-in coils covering 1600 kc. up to 500 mc.

**MODEL 702 VFO** includes NFM. Covering 3,000 through 4,000 kc., its 3-watt output may be multiplied 80 through 2½ meters. It's something brand new — a crystal controlled VFO including and using a 5 mc. xtal frequency standard to give complete break-in operation, superbly clean keying — the VFO you've dreamed would come. Only **\$49.90** less tubes, including power supply.

**TYPE 619 AIR TRIMMER CAPACITORS** are high Q, low-loss, good up beyond 500 mc. for tuning, trimming, coupling, etc. 3 mmfd. to 30 mmfd. spread out over 3 complete revolutions for easy adjustment. Like all SILVER instruments, price is more than right — only **\$.30** ea., net.



703



802



903



702



619

OVER 36 YEARS OF RADIO ENGINEERING ACHIEVEMENT

*McMurdo Silver Co., Inc.*

EXECUTIVE OFFICES: 1240 MAIN ST., HARTFORD 3, CONN.

FACTORY OFFICE: 1249 MAIN ST., HARTFORD 3, CONN.

See these new, top-value-and-performance instruments at your favorite jobber. Send for complete catalog including SILVER Laboratory Caliber Electronic Test Instruments.

**PREMIUM QUALITY**  
*at no extra cost*



PAPER, MICA AND  
FP CAPACITORS



TRANSMITTING  
CAPACITORS



FIXED AND ADJUSTABLE  
RESISTORS



VIBRATORS AND  
VIBRAPACKS\*



POTENTIOMETERS  
AND RHEOSTATS



"HAMBAND" SWITCHES



NOISE FILTERS

When you go to the time and expense of building a new rig, it doesn't pay to take chances on unknown components. Protect your work with **APPROVED PRECISION PARTS**: make it Mallory and make sure.

Mallory was first to introduce many components to the radio

\*Reg. U. S. Pat. Off.

field—first, too, to standardize and simplify their manufacture. The very name Mallory means **PREMIUM QUALITY**. It's a guarantee of performance for which you pay no more.

Expect more from Mallory: you're certain to get it. See your Mallory Distributor.

**P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA**



# TO HELP YOU PICK THE BEST


Here are a few facts to help you choose the best: In approximately 90% of the new commercial mobile transmitter designs, you will find Hytron instant-heating tubes. Over 2,500,000 Hytron gaseous voltage regulators speak for themselves. Ratings of Hytron vhf tubes are CCS and based on actual equipment performance which you can duplicate. No other transmitting triode can touch the new all-purpose 5514 for economical versatility. Famed for transmitting tubes, Hytron also originated the popular "GT", and is the oldest manufacturer specializing in receiving tubes. You pick the best when you pick Hytron.

## HYTRON TRANSMITTING AND SPECIAL PURPOSE TUBES CONTINUOUS COMMERCIAL SERVICE RATINGS

Description	Type No.	Filament Ratings		Type	Max Plate Volts	Max Plate Ma	Max Plate Dis	Amateur Net Price
		Volts	Amps					
LOW AND MEDIUM MU TRIODES	10Y	7.5	1.25	Thor	450	65	15	\$1.60
	HY24	2	0.13	Oxide	180	20	2	1.50
	801A/801	7.5	1.25	Thor	600	70	20	3.00
	864	1.1	0.25	Oxide	135	5	—	1.20
	1626	12.6	0.25	Cath	250	25	5	1.60
HIGH-MU TRIODES	HY312 §	6	2.55	Thor	500	150*	30*	3.95
	HY1231Z §	6	3.2	Thor	500	150*	30*	4.50
		12	1.6	Thor	500	150*	30*	4.50
	5514*	7.5	3	Thor	1500	175	65	3.95
VHF TRIODES	2C26A	6.3	1.15	Cath	3500	NOTE	10	7.75
	HY75A* §	6.3	2.6	Thor	450	90	15	3.95
	HY114B §	1.4	0.155	Oxide	180	12	1.8	2.25
	HY615	6.3	0.175	Cath	300	20	3.5	2.25
	955	6.3	0.15	Cath	200	8	1.8	3.10
	9002	6.3	0.15	Cath	200	8	1.8	2.15
BEAM PENTODES AND PENTODES	2E25* §	6	0.8	Thor	450	75	15	3.95
	2E30 §	6	0.65	Oxide	250	60	10	2.25
	3D21A	6.3	1.7	Cath	3500	NOTE	15	7.50
	HY69 §	6	1.6	Thor	600	100	30	3.95
	807	6.3	0.9	Cath	600	120	25	2.30
	837	12.6	0.7	Cath	500	80	12	4.15
ACORNS MINIATURES		6	3.2	Thor	750	120	30	4.50
	1625	12.6	0.45	Cath	600	120	25	2.30
	5516 §	6	0.7	Oxide	600	90	15	5.95
	954	6.3	0.15	Cath	Sharp cutoff pentode			4.90
9001	6.3	0.15	Cath	Sharp cutoff pentode			2.70	
RECTIFIERS	Type No.	Filament Volts	Ratings Amps	Type Rect	Peak Plate Ma	Max D-C Ma†	Inv Peak Pot.	Amateur Net Price
	816	2.5	2.0	Mer	500	250	5000	\$1.25
	866A/866	2.5	5.0	Mer	1000	500	10000	1.75
	1616	2.5	5.0	Vac	800	260	6000	7.50
GASEOUS VOLTAGE REGULATORS	Type No.	Average Operating Voltage	Operating Ma	Min	Max	Av Volts Reg	Min Starting Voltage	Amateur Net Price
	OA2	150	5	5	30	2	185	\$2.30
	OB2	108	5	5	30	1	133	2.30
	OC3/VR105	108	5	5	40	2	133	1.20
	OD3/VR150	150	5	5	40	3.5	185	1.20

\*Both sections of twin triode. NOTE: Special pulse tube, not recommended for c-w, consult Hytron Commercial Engineering Dept. for data. †5514 supplants the HY30Z, HY40, HY40Z, HY51A, HY51B, and HY51Z, the HY75A the HY75, and the 2E25 the HY65. ‡Current for full wave. §Instant-heating.

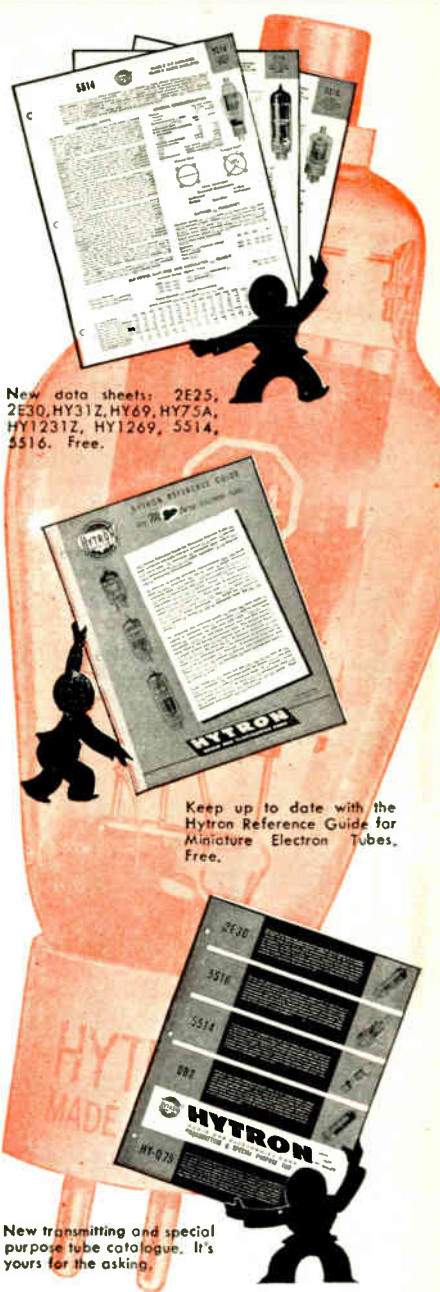
For better reception, it's also Hytron — GT, G, lock-in, or miniature.



New data sheets: 2E25, 2E30, HY31Z, HY69, HY75A, HY1231Z, HY1269, 5514, 5516. Free.

Keep up to date with the Hytron Reference Guide for Miniature Electron Tubes. Free.

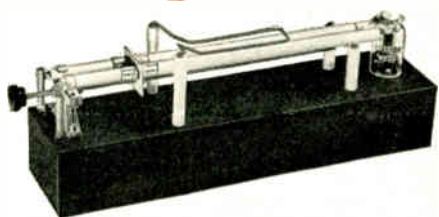New transmitting and special purpose tube catalogue. It's yours for the asking.




Simple, sure-fire vfo for 1 1/4 or 2 meters. HY-Q 75 kit: unassembled, \$9.95; assembled, \$11.95.

# HYTRON RADIO & ELECTRONICS CORP. SALEM, MASSACHUSETTS
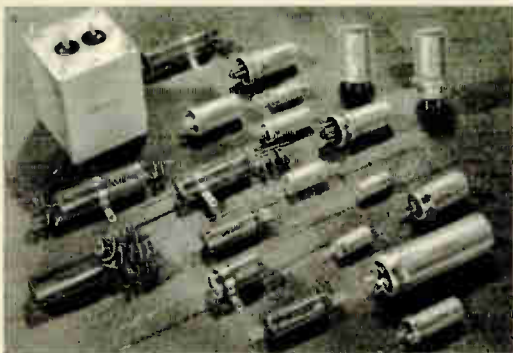
# Here's Capacitor Dependability!


Shown here are a few of more than 9675 capacitor and \*Koolohm resistor types that Sprague produces every year. Many of these are for critical industrial applications, others for national defense and ultra-exacting scientific needs.

From this vast array come the capacitors that are carefully selected for amateur radio uses—types that mean more for your money because they're better engineered, built more dependably. Catalog on request.


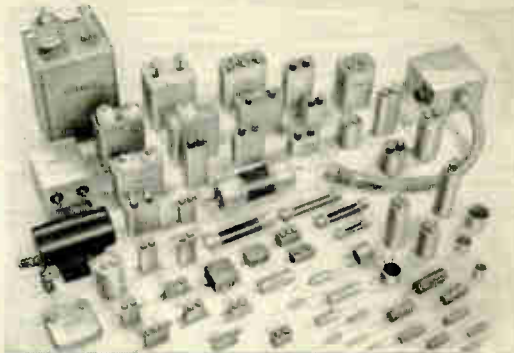
## DRY ELECTROLYTICS

Sprague offers the most diversified dry electrolytic capacitor line ever presented for standard distributor stock. Tiny "Atom" midgels; self-mounting multi-section units; high-capacity, low-voltage tubulars; rectangular and cylindrical shapes; lug, bracket and self-mounting types; terminals and lead connections and many others!



## PAPER DIELECTRICS

Standard Sprague paper dielectric capacitors for amateur use include 15 types and over 250 items. Chief among them are three small, popularly priced transmitting types that are both filled and impregnated with \*KVO, the exclusive Sprague dielectric. And don't forget the TC Tubular By-pass types— "Not a failure in a million!"



## MICA DIELECTRICS

Sprague distributors carry complete stocks of popular mica capacitors including all needed capacities and voltage ratings—in sizes from "postage stamp" silvered micas to high-voltage ceramic-jacketed units. All provide maximum quality for R-F applications where low power factor and high insulation resistance at high frequencies are essential.



## \*KOOLOHM RESISTORS

Sprague Koolohm Resistors are wound with wire insulated before winding with a flexible ceramic coating that is impervious to heat as high as 1000° C. Doubly protected by glazed ceramic shells and moisture resistant seals. Insulated for 10,000 volts resistance breakdown to ground. Larger, sturdier wire sizes in smaller resistors. Use Koolohms at full wattage ratings—anywhere!

\*Trademarks Reg. U. S. Pat. Off.

# SPRAGUE

PIONEERS OF ELECTRONIC AND ELECTRICAL PROGRESS  
SPRAGUE PRODUCTS COMPANY, NORTH ADAMS, MASS.

Jobbing distributing organization for products of Sprague Electric Co.

# TRULY HERMETICALLY SEALED... FOR POST-WAR PERFORMANCE

100% GUARANTEED

## SEALED LIKE A VACUUM TUBE







Marion Glass-To-Metal Truly Hermetically Sealed Electrical Indicating Instruments are guaranteed for six months. You get top performance... critical accuracy... at a cost no more than that of most competitive unsealed instruments.

Additional economy is offered in Marion's special replacement offer. After the initial six-month guarantee expires, any 2½" and 3¼" type, ranging from 200 micro-amperes upward, will be replaced, regardless of whether the instrument has been overloaded, burned out, or mistreated... provided the seal has not been broken, for a flat fee of \$1.50. Instruments with sensitivity greater than 200 microamperes will be replaced for \$2.50.

### MARION "4 FOR 1" FEATURE

Interchangeable Round and Square Colored Flanges... one instrument can thus fill four different needs:

1. ROUND 
2. ROUND FOR STEEL PANEL 
3. RECTANGULAR 
4. RECTANGULAR FOR STEEL PANEL 

Stop in at your nearest radio supply shop today and see the best in electrical indicating instruments... the Marion line.

### MORE EXTRAS WITH MARION "HERMETICS"

#### DURABLE

... Unaffected by extremes of heat or cold... permanently protected against dust, dirt, moisture... instrument malfunctioning eliminated.

#### SHIELDED

... Heavy steel case gives magnetic and electrostatic shielding so important in modern high frequency equipment.

#### INTERCHANGEABLE

... The Marion case, with its high conductivity plating, eliminates the need for separate shielding and permits interchangeability on any type of panel without affecting calibration.

#### DRESSY!

... Marion "hermetics" are supplied with either round or square flanges in black... or any one of 12 iridescent colors at no extra cost.



MARION ELECTRICAL INSTRUMENT CO.

MANCHESTER, NEW HAMPSHIRE

Export Division

458 Broadway

New York 13, U. S. A.

Cables: MORHANEX

THE NAME "MARION" MEANS  
THE "MOST" IN METERS


IN CANADA: THE ASTRAL ELECTRIC COMPANY, SCARBORO BLUFFS, ONTARIO

# ROTOMATIC BEAM
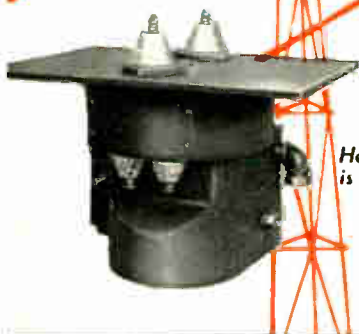
## LATEST ADDITION TO FAMOUS JOHNSON LINE

The solution to QRM on the crowded DX bands is the new JOHNSON Rotomatic Antenna Array. It's strong, light, has broad band characteristics, and provides tremendous increase in signal strength. Two band operation is possible with the Deluxe model. Two 3-element arrays can be matched and fed with the same efficient open wire transmission line. On ten, as many as four elements can be used.

The drive unit is really **heavy-duty** — providing rotation through 360° at 1½ RPM. May be purchased without motor for hand drive. The combined direction indicator, with great circle map and beam control is a marvel of operating efficiency — where speed counts as never before.




Heavy-duty drive unit is self-lubricating and fully enclosed.



New direction indicator and beam control is Selsyn motor operated.

## INSULATORS

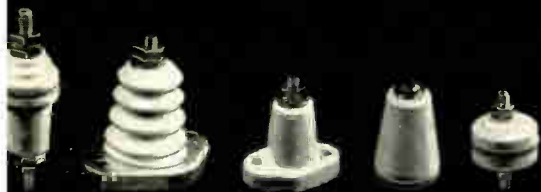

JOHNSON Insulators are specifically designed to handle high RF with low loss. They possess, in addition, logical proportions, clean-cut accurate molding, and high grade nickel plated brass hardware with milled — not stamped — nuts. The Johnson line includes stand-off, cone, thru-panel, antenna, feeder and strain insulators.

## SPEED X TRANSMITTING KEYS




The Speed X line, long a leader in its field, is now manufactured by JOHNSON. It includes everything from buzzers to high speed semi-automatic keys. Pictured are the hand key, Model 326, and beautiful chrome finish, new and improved Model 501 semi-automatic. Model 501, Amateur Model 515 and Junior 510 also available in left hand models.

## PILOT LIGHTS



To round out its line, JOHNSON recently purchased the entire Gothard line of fine pilot lights. The Gothard line is a complete line and will be maintained to provide a wide choice and permit selection of a light which will more exactly meet your needs. All metal parts are brass with the exception of hex nuts. Parts are heavily plated and jewel holders are polished chrome or nickel.

## TUBE SOCKETS

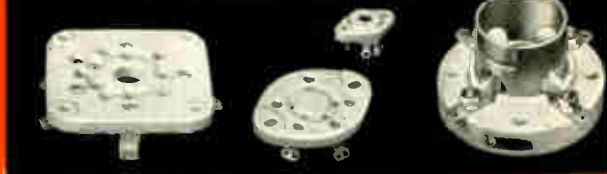

JOHNSON Tube Sockets have consistently led the way to better design for better results. Present day demands for ever better radio-electronic circuits and equipment are more than adequately met with JOHNSON Tube Sockets. Superior in mechanical and electrical design, JOHNSON Tube Sockets are available in both standard and "special" sizes.






## NEW CABINETS, RADIO PANELS AND CHASSIS

The skill of JOHNSON in building cabinets for its Phasing and Antenna Coupling Equipment is now directed to mass production of cabinets, racks, panels and chassis. They are professional in appearance, characteristically reasonable in price. A unique feature is the ventilation system which permits units to be placed flush side-by-side. Chassis have a new type flush joint which eliminates sharp and protruding edges.

## NEW, FINER TRANSMITTER COILS

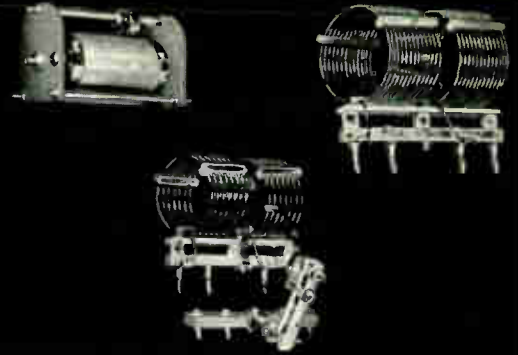

JOHNSON is the first to offer the amateur a complete line of transmitting inductors with commercial efficiency. New plug-in link pick-up coils make possible efficient impedance matching to the transmission line. Correct LC ratio with either high or low voltage tubes, can be secured by the purchase of only one additional coil in the series for operation from 6 to 80 meters. Also pictured is the JOHNSON Rotary Inductor.

## CONDENSERS



Dependable performance is the yardstick by which quality of condensers is measured. Every JOHNSON condenser is precision engineered not only for superlative performance but for durability as well. The exacting requirements of amateur, commercial broadcast and industrial operation are rigidly met for your

complete satisfaction. What's more, JOHNSON makes a condenser for every stage of the amateur transmitter from oscillator through the final amplifier. Whatever your requirements, the choice of JOHNSON condensers is complete.

## PLUGS, JACKS AND HARDWARE



Constant attention to detail plus pride in manufacture make JOHNSON hardware a perfect compliment to your "dream station". The quality is there, yet the price is modest. Included in the JOHNSON Hard-

ware line are couplings, tube caps, plugs and jacks, inductor clips, soldering terminals, tube locking clamps, panel bearings, flexible shafts, fuse clips, handle indicators and cable connectors.



JOHNSON products can be obtained from radio-electronic parts jobbers, or write directly for further information. You'll be glad you did!

SEND FOR LATEST JOHNSON CATALOG

# JOHNSON . . . a famous name in Radio

E. F. JOHNSON CO. WASECA, MINNESOTA

## MOST ACCURATE HAM BAND FREQ. METER

CHECKS XMTR FREQ. IN ANY  
HAM BAND FROM 3.5 TO 148  
MC. ON FM OR AM

This latest Browning unit designed especially for hams — the Model MJ-9 Frequency Meter — is a high sensitivity job that checks your operating frequencies accurately. If you place it near your xmtr, you may not even need a pickup wire for usable signals! Can be used for measuring frequency of remote transmitters and for calibration of receivers within ham bands or ham band harmonics. Truly a necessity for every modern shack.




### MODEL MJ-9 FREQ. METER

- Direct, frequency-reading dial on seven ham bands.
- .05% accuracy at all frequencies.
- Audio detection of zero beat.
- Low power consumption.
- All operating controls on front panel.

**PLUS MANY OTHER FEATURES.  
WRITE US FOR LITERATURE.**
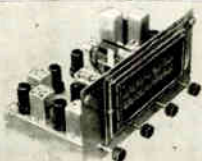
## MOST WIDELY USED FM-AM TUNER IN THE WORLD



### MODEL RJ-12 FM-AM TUNER

- Separate RF and IF systems on both bands.
- One antenna serves both FM and AM.
- Tuning eye shows correct tuning.
- 2-stage cascade limiting on FM.
- Phono position on channel selector switch; phono input connector in back.
- Armstrong circuit employed on FM.

**PLUS MANY OTHER FEATURES.  
WRITE US FOR LITERATURE.**

### FOR HI-FI RECEPTION IN THE NEW FM BAND AND IN STANDARD BC. BAND

Ask any old-timer about the Browning-Drake tuner, and he'll warm right up with a recitation of how much that unit meant to him. Now put an RJ-12 in your house, and the xyl and all the neighbors will decide that you, after all, are the king pin of radio in your community! For here's a hi-fi, hi-sensitivity unit which provides distortion-free reception. Put it in special cabinet, desk drawer, shelf — wherever it will look best. Or for use with rack-mounted amplifier. Diagram of HI-FI AMPLIFIER included with every unit.



**BROWNING LABORATORIES, INC.**  
**WINCHESTER, MASS.**

CANADIAN REPRESENTATIVES: MEASUREMENT ENGINEERING 61 DUKE STREET, TORONTO, CANADA

# REMAX

# VERTICAL ANTENNAS--ELEMENTS AND MOUNTING ACCESSORIES

Premax Tubular Vertical Antennas are fully collapsing and adjustable, yet give exceptionally efficient, dependable performance under most severe conditions. Will withstand ordinary stresses, but should be supported by guys or standoff insulators against abnormal winds. In 6 to 35-foot heights, in monel, aluminum or steel.

## Weather Resistant Steel Antennas

No.	Description	Extended Length	Collapsed Length	Base O.D.	Base I.D.	Weight Each
112-M	2-sec. telescoping	11'8"	6'1"	.656"	.556"	4 lbs.
318-M	3-sec. telescoping	17'3"	6'2"	.875"	.775"	7 lbs.
224-M	4-sec. telescoping	22'9"	6'3"	1.063"	.963"	11 lbs.
130-M	5-sec. telescoping	28'3"	6'4"	1.250"	1.150"	15 lbs.
136-M	6-sec. telescoping	33'9"	6'5"	1.500"	1.400"	20 lbs.

## Light-Weight Aluminum Antennas

No.	Description	Extended Length	Collapsed Length	Base O.D.	Base I.D.	Weight Each
AL-106	1-pc. tapered rod	6'3"	6'3"	.313"	...	1½ lb.
AL-312	2-sec. telescoping	12'4"	6'4"	.500"	.334"	1½ lbs.
AL-518	3-sec. telescoping	18'5"	6'4"	.750"	.584"	3 lbs.
AL-324	4-sec. telescoping	24'4"	6'4"	1.000"	.834"	5 lbs.
AL-530	5-sec. telescoping	30'0"	6'5"	1.250"	1.084"	7 lbs.
AL-535	6-sec. telescoping	35'8"	6'5"	1.500"	1.310"	12 lbs.

## Heavy-Duty Aluminum Masts

No.	Description	Extended Length	Collapsed Length	Base O.D.	Base I.D.	Weight Each
AM-017	1-pc. tapered tube	17'9"	17'9"	.969"	.889"	5½ lbs.
AM-035	2-sec. tapered	35'0"	17'9"	2.000"	1.732"	19 lbs.

## Long-Enduring Monel Antennas

No.	Description	Extended Length	Collapsed Length	Base O.D.	Base I.D.	Weight Each
MM-313	2-sec. telescoping	appx. 13'	6'9"	.615"	.545"	2½ lbs.
MM-419	3-sec. telescoping	appx. 19'	6'9"	.747"	.667"	5 lbs.
MM-425	4-sec. telescoping	appx. 25'	6'9"	.893"	.799"	8 lbs.
MM-430	5-sec. telescoping	appx. 30'	6'9"	1.065"	.945"	13 lbs.
MM-435	5-sec. telescoping	appx. 35'	7'8"	1.065"	.945"	15 lbs.

Ask your Radio Jobber for new Premax Antenna Catalog. He also can supply the Premax Radio Antenna Manual of Vertical and Horizontal installations.

Alum'n Monel

## RULITE ELEMENTS for Beam Arrays



remax Corulite Elements meet the need for light-weight but sturdy elements for horizontal arrays and similar applications. Exceptionally light weight yet they provide the needed strength and rigidity so essential in horizontal installations — and at extremely low cost. The special steel tubing used in these elements is a Premax development to insure unusual stiffness and strength. Heavily electroplated to insure corrosion resistance and high electrical conductivity. Fully adjustable to any desired length. A special locking clamp secures rigid joints and positive electrical contact. A "hairpin" tuning bar provides ease of adjustment.

No.	Description	Extended Length	Collapsed Length	Base O.D.	Recommended For	Weight Per Pr.
105-M	1-section	5'0"	5'0"	.625"	6-meter	1 lb.
108-M	2-section	8'2"	4'7"	.750"	10-meter	2 lbs.
113-M	3-section	12'4"	4'8"	.875"	20-meter	3½ lbs.
618-M	4-section	17'0"	5'3"	1.000"	20-meter	5½ lbs.

(Sold only in pairs, complete with Premax "Hairpin" Tuning Bar)

1-Element Corulite for 10 or 20 meters, mounting clamps detailed drawings sliding wood frame support.

Four-Element Corulite Kits for 10 or 20 meters, with mounting clamps and detailed drawings for building wood frame and support.

Rotary Beam Kit RB-6309 for 6, 10 and 20 meters, includes frame, 3 pr. Elements, hardware, T-Match accessories. Weight 30 lbs.

Base Insulator, Type 1: Heavy-duty type with compression rating up to 10,000 lbs. In galvanized malleable iron or bronze to fit ¾" to 1 9/32" I.D.



Base Insulator Type 2: Light design for masts up to 18' or higher if guyed or supported by standoff insulators. ¾" top post is standard but with use of adapters will fit other sizes.

Type 1



Type 2

Base Insulator Type 6: For tower platform, rooftops or marine. Lead-thru construction permits antenna connections below roof or deck. Available for ¾" to 1 9/32" I.D. tubular masts.




Type 6

Type 3 Standoff Insulator for supporting verticals or for use in pairs as complete antenna or element mountings. Galvanized iron or bronze with porcelain body. Styles to fit ½" to 1½" O.D. elements.



Type 3

Type 8-C Insulated Mounting Clamp for horizontal arrays, verticals, etc. Galvanized iron with porcelain split bushing. For 5/8" to 1" O.D. masts.

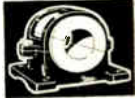

Type 8-C

Type 9-C Insulated Mounting Clamp for horizontal elements, verticals, etc. Galvanized iron with porcelain split bushing. Fits 5/8", ¾", 7/8" or 1" O.D. elements.



Type 9-C

Type 10-C Insulated Mounting Clamp. Electroplated stamped steel with porcelain split bushing; light-weight for rotary and dipole installations. For 5/8" to 1" elements.



Type 10-C

Type 10-S Insulated Mounting Clamp. Chrome-plated bronze base and head-caps, porcelain insulator. Fits 5/8" to 1½" O.D. elements.



Deck Bushing of brown glazed porcelain with galvanized malleable flange which bolts thru rubber gasket to roof or deck. I.D. ¾", 1¼" or 1¾".



Bushing

Bronze Mounting Clip for horizontal elements, vertical antennas or for feed and transmission connections. For ¾", 7/8" or 1" O.D.



Mounting Clip

Wall Bracket of heavy steel for mounting vertical antennas on side walls, parapets, etc. Drilled to fit Types 1 and 2 Base Insulators.



Wall Bracket

# PREMAX PRODUCTS

A DIVISION OF CHISHOLM-RYDER CO., INC. • 4821 HIGHLAND AVE. • NIAGARA FALLS, N. Y.

**BRACH****FM & TV ANTENNAS**

for the  
**PEAK OF  
RECEPTION**

**ANTENNA  
SYSTEMS**

manufactured under

**PRIVATE LABELS  
and TRADE MARKS**


for

**AUTOMOBILES**


and

**RESIDENTIAL  
AM • FM • TV**

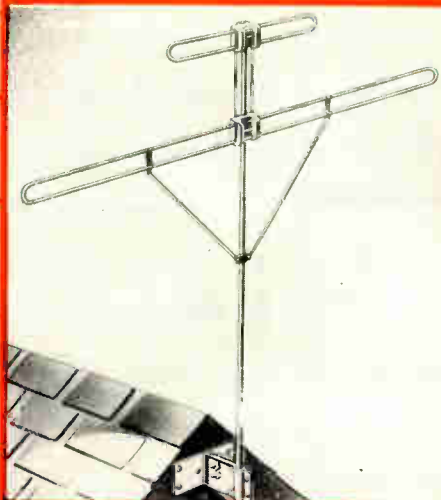Our engineers will cooperate in designing collapsible and transmitting antennas for every purpose, for quantity production.



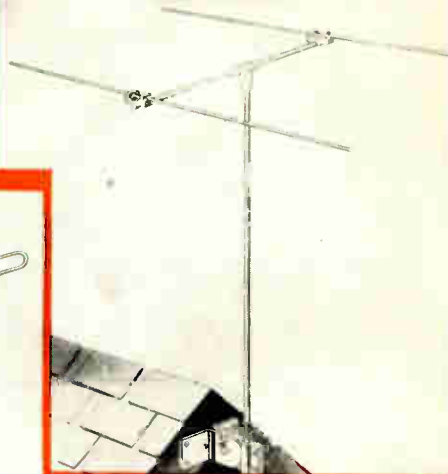**BROAD - BAND FM & TV ANTENNA  
No. 338**



**STRAIGHT DIPOLE & REFLECTOR  
FM ANTENNA No. 339**

**WRITE FOR  
SPECIFICATION SHEETS**

**SOME OF THE OTHER BRACH PRODUCTS**


Puratone Signal Booster for noise-free store demonstrations—carries AM, FM and Television Antennas all on the same mast • Lightning Protective Devices • Junction Boxes • Pot Heads • Gas Relays • Arrester Housings • Protective Panels • Solderall • Terminals and Housings • High Tension Detectors • Test-O-Lite for Circuits 100-550 AC or DC.

**L.S. BRACH  
MFG. CORP.**


ESTABLISHED 1906

**200 CENTRAL AVENUE  
NEWARK 4, N. J.**

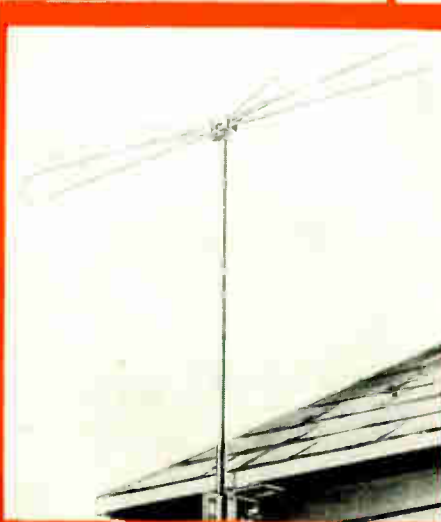WORLD'S OLDEST AND LARGEST  
MANUFACTURERS OF RADIO ANTENNAS  
AND ACCESSORIES.



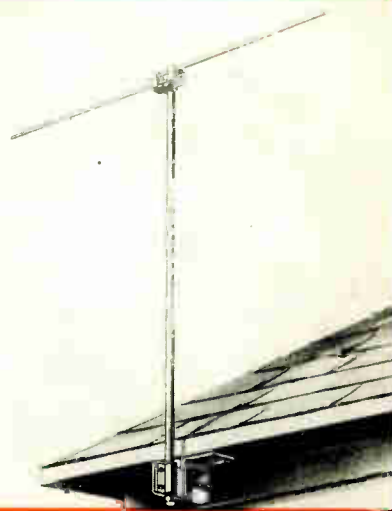**MULTI - BAND FM & TV ANTENNA  
No. 344**



**STRAIGHT DIPOLE  
FM ANTENNA No. 334**

**EASILY AND QUICKLY INSTALLED  
WITH THE**



**BRACH UNIVERSAL BASE MOUNT**

# 6 NEW SHURE PRODUCTS FOR AMATEURS



Model "718A"

The "VERSATEX," versatile Crystal microphone, features high-output, maximum speech response, moisture proof Crystal, shock proof Plastic case, R-F Filter. Eliminates mechanical noise pickup. Ideal for Ham communications. Also fine for recording and low cost P. A. systems.

The "MONOPLEX," the only super-cardioid crystal microphone. Has high-output, wide-range frequency response. Perfect for Hams who want the extra "push" that insures a "strong" voice. Features high-quality performance at low cost.



Model "737A"



Model "51"

The "SONODYNE," high-output dynamic microphone with wide-range frequency response. Has moving coil unit. Features a Multi-Impedance switch. A rugged unit with high sensitivity, yet perfect for Hams in high temperature and high humidity locations.

The "ECONODYNE," an economical high-output dynamic microphone with wide-range frequency response. Ideal for Hams who require good performance at low cost. An outstanding buy for any Ham.



Model "52"



Model "55"

Multi-Impedance "UNIDYNE." A high quality super-cardioid dynamic microphone for Hams whose rigs are rigged for dependable performance, even under difficult conditions. Has same mechanical properties as Model 556, except for vibration isolation unit.

Multi-Impedance "BROADCAST" dynamic microphone. The perfect microphone for the veteran, experienced topflight Ham who wants only the best in communications equipment. Features a vibration-isolation unit. Eliminates feedback. Random noise reduced 73%.



Model "556"

Other SHURE Microphones and Phonograph Pickups are illustrated in the new SHURE Catalogs. Write for catalogs No. 157 and 158.

*Patented by Shure Brothers and licensed under the Patents of the Brush Development Company*



## SHURE BROTHERS, INC.

Microphones and Acoustic Devices


225 W. Huron St., Chicago 10, Ill.

Cable Address: SHUREMICRO




# B & W AIR INDUCTORS


## AND VARIABLE AIR CONDENSERS

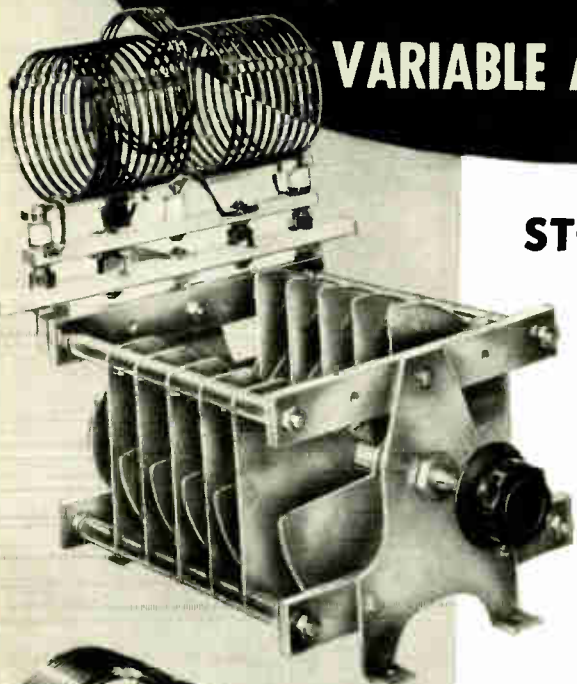


**CX-49A**

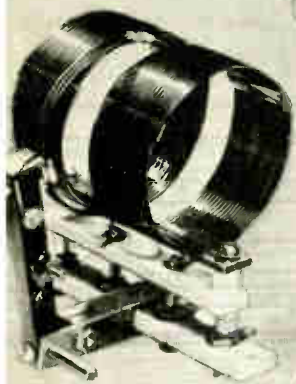


**BVL**

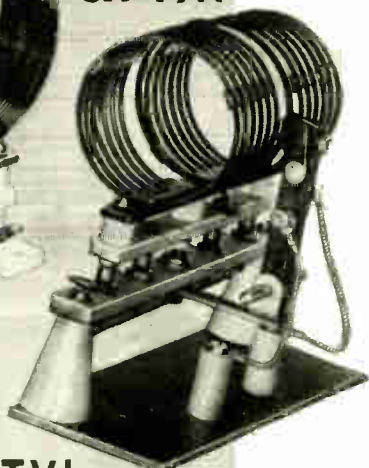

**TVL**

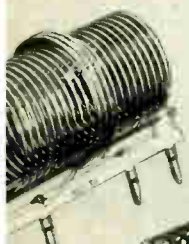

**40-TA**

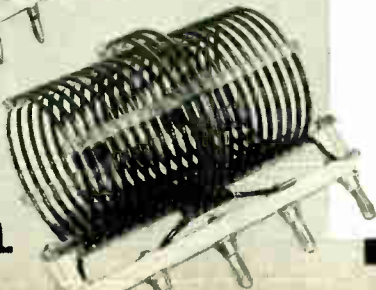

**HDCL**

## STOP TANK CIRCUIT LEAKS

... with this complete B & W Coil  
and Capacitor assembly

B & W Type CX Variable Capacitors provide for direct mounting of B & W Air Inductors. Wiring is eliminated. Circuit lead lengths are reduced to an absolute minimum. Opposed stator sections in the capacitors provide short r-f path. Butterfly rotor construction permits grounding rotor at the center r-f voltage point with respect to stators. Built-in neutralizing capacitors can be mounted on end plate. Standard types rated at 500, 750 and 1,000 watts. Treat your new rig to real tank circuit efficiency! Write for catalog.

*Neutralizing Plates Available in 4 Types*

## B & W B, T AND HD INDUCTORS

100-WATT, 500-WATT AND 1 KW TYPES

- MINIMUM DIELECTRIC IN THE FIELD OF THE COIL
- EXTREMELY LOW LOSSES — RUGGED CONSTRUCTION
- EXCELLENT APPEARANCE — LOW COST

Type "B" inductor is for use on oscillator and buffer-doubler stages developing up to 100 watts. Available in center tapped models without link; end link; center link; center tapped; and variable link—center tapped. For 5, 10, 15, 20, 40 and 80 meter bands.

Type "T" is specially suited for high powered neutralized buffer and final tank stages where powers of 500 watts are developed. Available in center tapped models without link; center linked with center tap and variable linked with center tap. Made for 10, 15, 20, 40 and 80 meter bands.

Type "HD" is for maximum power and handles a kilowatt with ease. Available in center tapped models without link; center linked with center tap and variable linked with center tap. Made for 10, 15, 20, 40 and 80 meter bands.

## B & W TVH INDUCTORS

for powers up to 500-watts input

Here is a special group of units designed for greater flexibility through use of an eight plug jack bar. With these inductors it is possible to connect automatically, a fixed padding capacitor when using the low frequency coil. Available for 10, 15, 20, 40 and 80 meter bands.

SEE B & W PRODUCTS AT YOUR JOBBER'S

Write for Complete Amateur Catalog

## 2 A "BAND HOPPERS"



### B & W TURRET ASSEMBLIES

Fast, positive band switching for your rig! Moderate in cost — easy to install — adaptable to 30, 40, 20, 15 and 10 meter bands. These turrets eliminate absorption effects through use of a unique switching assembly which shorts unused coils.

**B & W — 75-Watt 2A "BAND HOPPERS"** — A compact and panel controlled unit which may be used for inter-stage coupling between two beam power tubes or between beam power tubes and triodes.

**B & W 75-WATT TURRETS** — for link coupling single ended or push-pull low power stages. Mounted on a positive action switch arranged for panel mounting through a single  $\frac{3}{8}$ " hole.

*Type JTCL* — Center linked, center tapped coils.

*Type JTEL* — End linked, untapped coils.

**B & W 150-WATT TURRETS** — for single- and double-ended circuits. These mount the same as 75-watt turrets and are used with tubes operating at voltages up to 1000 volts.

*Type BCL* — Center linked, center tapped coils.

*Type BEL* — End linked, untapped coils.

### B & W BABY TURRETS — 35-WATTS

Rated at 35 watts, these compact, 5-band switching units cover amateur bands from 10 to 80 meters. They are suitable for all services with any of the 50 mmfd. midget condensers. Sturdy construction and unusual design assures permanent coil alignment and maximum efficiency with the minimum number of tubes. Available in four types: BTM straight untapped; BTCT — center tapped; BTCL — end linked; and BTCL — center linked. All provide vastly improved band switching efficiency in low power transmitters and exciter stages.

### ANTENNA INDUCTORS TA AND HDA

These coils are wound with tinned copper wire for ease in tapping feeders and have fixed center links for coupling to either fixed or variable linked final tank circuits through low impedance line. Available for 10, 15, 20, 40 and 80 meter bands. Type TA for power input up to 500 watts and Type HDA for power inputs of one kilowatt.


### B & W 3400 SERIES INDUCTORS

Presenting the utmost in sturdy construction and electrical flexibility, these coils are built with an individual internal center coupling, adjustable over 360° — permitting precise impedance matching up to 600 ohms. For powers up to 500 watts. Available for 10, 15, 20, 40 and 80 meter bands.
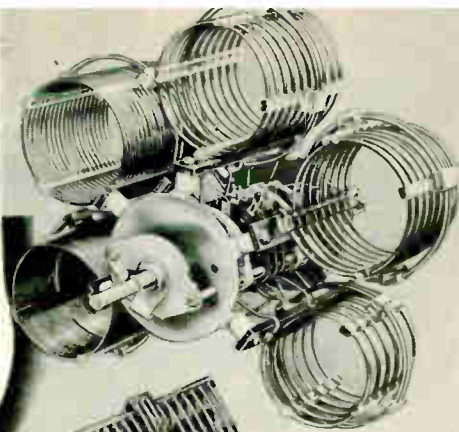
### THE MIDGET R-F COILS of dozens of uses


Goodbye to homemade high-frequency coils! B & W Midget coils cost little, are beautifully constructed — and do the job right. Every day, amateurs, experimenters and equipment manufacturers tell us of new applications where Midget coils have replaced homemade coils with a big boost of efficiency. Use them for receivers, transmitters and test equipment — in tank circuits as r-f chokes, high-frequency i-f transformers and loading coils and for dozens of other purposes.

B & W "Air Wound" construction permits small but sturdy supports with the absolute minimum of insulating material in the electrical field. Q factor is amazingly high. Standard Midgetor diameters are  $\frac{1}{2}$ ",  $\frac{5}{8}$ ",  $\frac{3}{4}$ " and 1", each available in four different winding pitches. Ask your jobber. He can supply these coils, individually packaged, in standard 2" or 3" lengths.



BCL

JCL

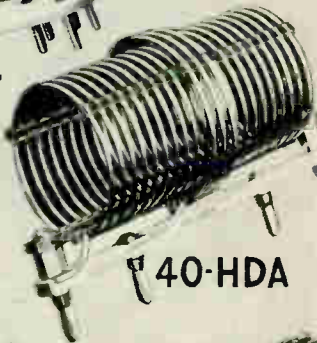

40-HDA

3400



TCL



**NEW! B & W TEST EQUIPMENT ON FOLLOWING PAGE**  
**BARKER & WILLIAMSON, Inc.**

# 6 New B & W Products

## 1—MIDGET "BUTTERFLY" CAPACITORS

With only 25% frontal area of the heavier CX Variable Capacitors, these new B&W JCN units are ideal for general uses — especially for medium-powered triode or tetrode stage plate circuits. Coils can be mounted directly on the capacitors.

## 2—VFO EXCITER

Stability of the highest order.

This new Model 500 B&W VFO Exciter is both a low-powered transmitter and a deluxe exciter for the amateur who demands an exceptionally high degree of mechanical and thermal stability. The ideal Exciter for those who want ultimate VFO control at moderate cost.

The Model 502 VFO complete with dial assembly and full instructions may be obtained separately.

## 3—AUDIO OSCILLATOR

For any application where an extremely stable, accurately calibrated source of frequencies between 30 and 30,000 cycles is required.

Small size, light weight, ease of operation and outstanding performance make this B&W Model 200 Audio Oscillator unsurpassed for distortion or frequency measurements.

## 4—AUDIO FREQUENCY METER

For direct measurement of audio frequencies up to 30,000 cycles.

A compact, light weight, highly efficient instrument for routine checking of audio oscillators and tone generators or for direct measurements of unknown audio frequencies. Six ranges cover from 0-100; 300; 1,000; 3,000; 10,000 and 30,000 cycles.

## 5—DISTORTION METER

An ideal meter for frequency analysis.

Designed for measuring low-level audio voltages and determining their noise and harmonic content, the B&W Model 400 Distortion Meter is a highly satisfactory instrument for either field or laboratory use. It is also well suited for measuring frequency and gain characteristics of audio amplifiers where a vacuum tube voltmeter is required in the audio range.

## 6—SINE WAVE CLIPPER

The B&W Model 250 Sine Wave Clipper is a device for generating a test signal that is particularly useful for examining the performance characteristics of audio frequency circuits. Small size, 5 3/8" x 3 3/8" x 2 1/8". Light weight coupled with low price make this entirely new instrument of great value to the discriminating amateur or technician who wishes peak performance in audio equipment.

**B & W COILS** — Including Famous "Air Wound" types  
FOR ALMOST EVERY ELECTRONIC APPLICATION

See Previous Pages



### COAXIAL CONNECTOR "CC-50"

For Efficient, Watertight Coaxial  
Cable Connections



FEATURED BY LEADING DISTRIBUTORS. DATA  
BULLETIN COVERING ALL TYPES ON REQUEST

# BARKER & WILLIAMSON, Inc.

237 FAIRFIELD AVENUE, UPPER DARBY, PA.

EXPORT: ROYAL NATIONAL CO., INC. • 75 WEST ST., NEW YORK, N. Y.





Skilful engineering, latest production techniques and highest quality materials . . . backed by careful workmanship, exacting step-by-step inspection and rigorous final testing . . . are your assurance that SNC Transformers are a quality product—built for outstanding performance.



A partial list of SNC transformers of particular interest to Hams is outlined below. For full information concerning the entire SNC line, write for FREE catalog . . . your records are not complete without it!

**CHOKES**

Type Number	Inductance at Rated D C	D C Mils	D C Res.	Mtg.	Volt Inhiul.	Wt.	Dimensions				
							A	B	C	D	E
2P147	8 HY	200	125	G	2000	5-1/2	3-1/2	2-27/32	3-1/8	2-1/4	2
2P148	3-15 HY	200-20	125	G	2000	5-1/2	3-1/2	2-27/32	3-1/8	2-1/4	2
2P151	8 HY	300	90	G	3500	10	4-17/32	3-25/32	3-7/8	3	2-13/16
2P152	3-15 HY	300-30	90	G	3500	10	4-17/32	3-25/32	3-7/8	3	2-13/16
2P155	8 HY	500	65	H	3500	25	5-1/2	5-15/16	4-3/8	4-13/16	7-1/8
2P156	3-15 HY	500-50	65	H	3500	25	5-1/2	5-15/16	4-3/8	4-13/16	7-1/8

**DRIVER TRANSFORMERS**

Type Number	Primary Impedance	Watts	Ratio Pri to 1/2 Sec. or Sec. Z	Pri Mils	Wt.	Mtg.	Dimensions				
							A	B	C	D	E
3P323	6,000 to 10,000	15	6.5 5.5 5.1	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P329	3,000 to 5,000	15	6.5 5.5 5.1	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P334	6,000 to 10,000	15	4.5 4.3 5.1	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P338	3,000 to 5,000	15	4.5 4.3 5.1	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P342	6,000 to 10,000	15	3.2 1.1	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P347	3,000 to 5,000	15	3.2 1.1	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P353	6,000 to 10,000	15	500 Ohms	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P358	3,000 to 5,000	15	500 Ohms	60	3	G	3-1/32	2-17/32	2-5/8	2	1-11/16
3P363	10,000	5	2 4 1	10	3/4	B	1-7/8	2-3/8	1-3/8	2	

**FILAMENT TRANSFORMERS**

Type Number	Primary Voltage	Secondary Voltage	Secondary Current	Volt Inhiul.	Wt.	Mtg.	Dimensions				
							A	B	C	D	E
4P226	120	2 5 C T	10 Amps	7,500	2-1/2	B	2-5/8	3-5/16	1-7/8	2-13/16	
4P242	120	5 0 C T	20 Amps	10,000	6-1/2	Bs	4-1/8	3-7/16	2-3/4	2-3/4	2-1/8

**UNIVERSAL MODULATION TRANSFORMERS**

Type Number	Primary Impedance	Power Watts	Primary Current Mils	Secondary Characteristics				Wt.	Mtg.	Dimensions				
				Series Sec.		Parallel Sec.				A	B	C	D	E
				Z Ohms	Ma	Z Ohms	Ma.							
5P341	3K-8K	15	60	3K-8K	50	1K-5K	100	2-1/4	D	2-5/8	3-1/8	1-7/8	2-13/16	
5P346	3K-15K	50	80	2K-18K	75	500-4.5K	150	5-1/2	G	3-15/16	3-1/8	3-3/8	2-1/2	2-3/16
5P352	3K-15K	100	120	2K-18K	100	500-4.5K	200	10	G	4-5/8	3-3/4	4-5/8	3	3-9/16
5P354	3K-15K	200	200	2K-18K	150	500-4.5K	300	27	J	5-1/2	5-15/16	4-3/8	4-13/16	7-1/8
5P355										5-1/2	5-15/16	4-3/8	4-13/16	7-1/8
5P357	3K-15K	300	250	2K-18K	250	500-4.5K	500	34	J	6-1/2	7-1/4	5-3/8	6-1/8	7-1/8
5P358										6-1/2	7-1/4	5-3/8	6-1/8	7-1/8
5P363	3K-15K	500	300	2K-18K	300	500-4.5K	600	51	J	6-1/2	7-1/4	5-3/8	6-1/8	10-3/4
5P364										6-1/2	7-1/4	5-3/8	6-1/8	10-3/4

**PLATE TRANSFORMERS**

Type Number	Primary Voltage	Pri. V.A.	Secondary Voltage	D C Voltage	D C Current	Wt.	Mtg.	Dimensions					
									A	B	C	D	E
7P530	115-230	220	920-0-920 740-0-740	750 600	200MA	12	G	4-21/32	3-25/32	5-1/8	3	4-1/16	
7P535	115-230	300	940-0-940	750	300	23	J	5-1/2	5-15/16	4-3/8	4-13/16	7-1/8	
7P536			760-0-760	600									
7P542	115-230	500	1430-0-1430	1250	300	28	H	6-1/2	7-1/4	5-3/8	6-1/8	7-1/8	
7P543			1180-0-1180	1000									
7P551	115-230	750	2100-0-2100	1750	300	35	H	6-1/2	7-1/4	5-3/8	6-1/8	7-1/8	
7P552			1830-0-1830	1500									
7P557	115-230	1100	2950-0-2950	2500	300	50	H	6-1/2	7-1/4	5-3/8	6-1/8	10-3/4	
7P558			2350-0-2350	2000									
7P563	115-230	1900	2950-0-2950	2500	500	77	H	7-3/4	7-1/4	6-5/8	6-1/8	10-3/4	
7P564			2350-0-2350	2000									

**POWER TRANSFORMERS**

Type Number	Pri. Volts	R M S Rect. Plate Sec.	D.C. Ma.	R.M.S. Rect Fil. Volts	R M S Heater Volts	Wt.	Mtg.	Dimensions					
									A	B	C	D	E
8P202	120	450-0-450	200	5V. @ 3A.	6.3V. CT @ 8 A.	7	F	4-17/32	3-25/32	4-3/4	3-3/4	3	
8P205	120	450-0-450	325	5V. @ 6A.	6.3V. CT @ 8 A.	15	H	5-1/2	5-15/16	4-3/8	4-13/16	7-1/8	
8P208	120	550-0-550	275	5V. @ 6A.	6.3V. CT @ 6 A.	15	H	5-1/2	5-15/16	4-3/8	4-13/16	7-1/8	

\* Available in G mounting on order at same price.

# WHEREVER THE CIRCUIT SAYS




## INSULATED COMPOSITION AND WIRE WOUND RESISTORS


Type BT Insulated Composition Resistors— $\frac{1}{2}$ ,  $\frac{1}{2}$ , 1 & 2 watt. Utilize patented IRC filament principle. Low operating temperature; excellent wattage dissipation. 330 ohms to 22 meg. in RMA ranges.

Type BW Insulated Wire Wound Resistors— $\frac{1}{4}$ ,  $\frac{1}{2}$ , 1 & 2 watt. Exceptionally stable resistor for low range requirements. 0.24 ohms to 8,200 ohms in RMA ranges.

(Fully described in IRC Catalog #3.)

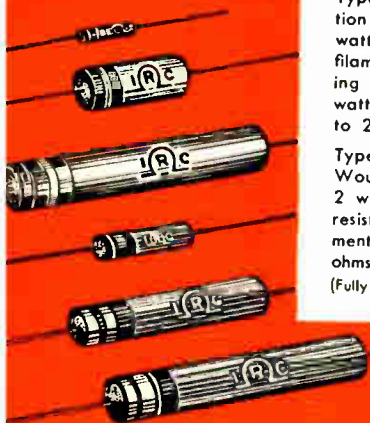

## VOLUME CONTROLS

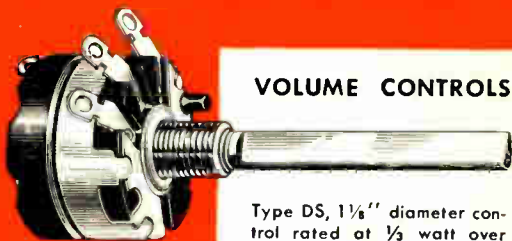

Type DS,  $1\frac{1}{8}$ " diameter control rated at  $\frac{1}{2}$  watt over entire element.

Type D all-purpose control with IRC Tap-In Shaft. Accommodates any one of 11 shafts. Both types feature exclusive Spiral Spring Connector and Five Finger Contactor.

(Fully described in IRC Catalog A-3.)



## POWER WIRE WOUNDS

Available in full range of sizes, types and terminals. Two types of special cement coating to meet varied types of service requirements. Uniformly wound with highest grade alloy wire on tough non-hygroscopic tubes. Rugged terminals securely attached.

(Fully described in IRC Catalog C-2.)




## FLAT POWER WIRE WOUNDS

Designed for vertical or horizontal mounting, singly or in stacks. Higher space-power ratio than standard tubular wire wounds. Lightweight construction with extreme mechanical strength. Fixed and adjustable types.

(Fully described in IRC Catalog C-1.)

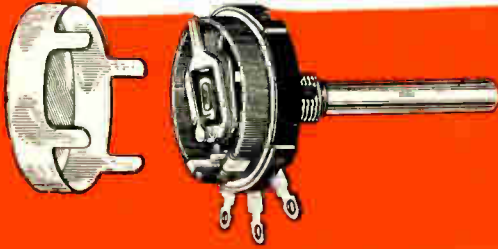
## 2 WATT WIRE WOUND POTENTIOMETER

A fully dependable wire wound control providing maximum adaptability to most rheostat and potentiometer applications within its power rating. 1 1/4" diameter featuring IRC Spiral Spring Connector, long wearing alloy contactor and welded terminals between resistance element and terminals.  
(Fully described in IRC Catalog A-2.)



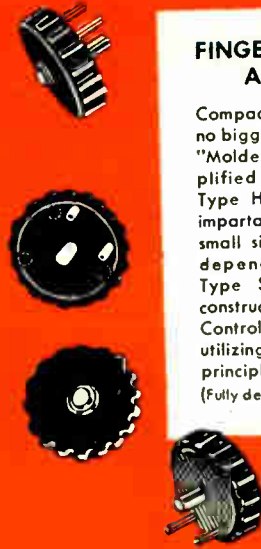
## FINGER-TIP CONTROL AND SWITCH

Compact, wafer-thin control, no bigger 'round than a nickel. "Molded-In" element and simplified construction enable Type H Control to fill many important applications where small size must combine with dependable performance. Type SH Switch, similar in construction to the Fingertip Control, is a four point switch utilizing the rotating cover principle.  
(Fully described in IRC Catalog A-1.)


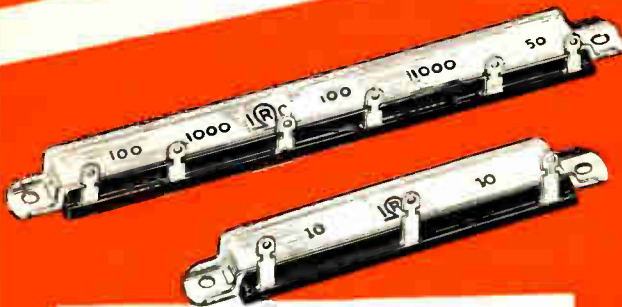
## PRECISION RESISTORS

A scientifically designed resistor combining highest quality materials with maximum in accuracy and dependability. Used extensively by leading instrument makers. 1% accuracy is standard; closer tolerances available at slightly increased cost.  
(Described in IRC Catalog D-1.)



## WIRE WOUND RESISTORS

Type MW is a flat wire wound resistor of radically different design. Completely insulated and protected. Offers many opportunities in cost reduction by low initial cost, lower mounting cost, flexibility in providing taps of low cost, and saving in space. Multi-section feature permits exceptional flexibility for voltage dividing applications.  
(Fully described in IRC Catalog B-2.)



other products in IRC's complete resistor line are described on the following pages.

# INTERNATIONAL RESISTANCE COMPANY

401 N. Broad Street

Philadelphia 8, Pa.

In Canada: International Resistance Co., Ltd., Toronto, Licensee

World Radio History


# WHEREVER THE CIRCUIT SAYS



## HIGH FREQUENCY RESISTORS

Type MP for frequencies above those of conventional resistors.  $\frac{1}{4}$  watt to 90 watts. Thin film of resistance material is bonded on ceramic form to provide a stable resistor with low inherent inductance and capacity. Broad range of terminal types.

(Fully described in IRC Catalog F-1.)

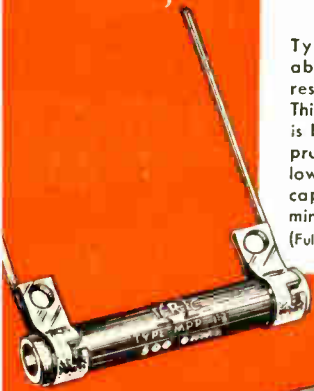

## HIGH VOLTAGE RESISTORS


Type MV resistors are designed for high voltage applications where high resistance and power are required. Unique application of filament resistance coating in helical turns on ceramic tube provides conducting path of long effective length. 2 watts to 90 watts. Variety of terminal types. (Fully described in IRC Catalog G-1.)



## POWER RHEOSTAT

Type PR 25 and 50 watt. All-metal construction, Heat dissipating qualities of aluminum fully utilized. Operate at full rating at approximately half the temperature rise of equivalent units. Can be operated at full power in as low as 25% of rotation without appreciable difference in temperature rise.


(Fully described in IRC Catalog E-2.)

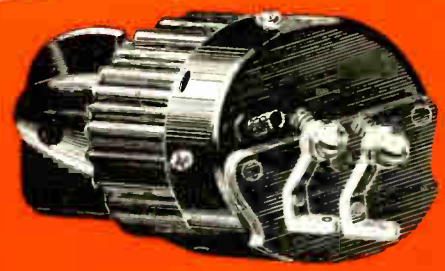


## RHEOSTAT AN3155

Type PRT 25 and 50 watt. Developed to meet rigid Army-Navy specifications. Totally enclosed for protection against dirt and damage. All-metal construction. Can be operated down to 25% of full rotation with only minor increase in temperature rise.

(Fully described in IRC Catalog E 1.)

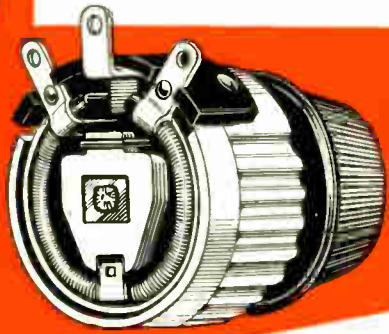

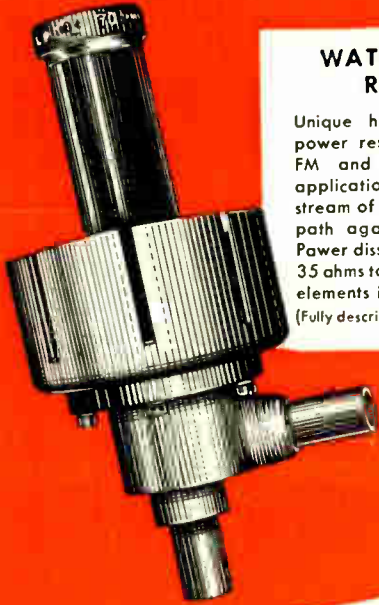Other products in IRC's complete resistor line are described on the preceding pages



### WATER-COOLED RESISTOR

Unique high frequency-high power resistor for television, FM and dielectric heating applications. High velocity stream of water flows in spiral path against resistance film. Power dissipation up to 5 K.W. 35 ohms to 1500 ohms. Resistor elements interchangeable.  
(Fully described in IRC Catalog F-2.)



### VOLTMETER MULTIPLIERS

Type MF consists of a number of IRC Precisions interconnected and encased in a glazed ceramic tube. Tube is hermetically sealed. Completely impervious to humidity. Maximum current: 1.0 M.A.; 0.5 megohms to 6 megohms.  
(Fully described in IRC Catalog D-2.)



### MATCHED PAIR RESISTORS


Two resistors matched in series or parallel to as close as 1% initial accuracy. Dependable low cost solution to close tolerance requirements. Both IRC Type BT and BW resistors are available in Matched Pairs.  
(Fully described in IRC Catalog B-3.)


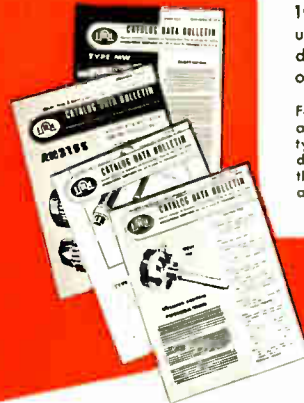
### IRC RESIST-O-GUIDE

New aid in resistor range identification. Turn three wheels to correspond with color code and standard RMA Range is automatically indicated. 10¢ at all IRC Distributors. When ordering direct send stamps or coin.

For detailed information on any of IRC's many resistor types write for catalog data bulletins specifying the product in which you are interested.



All standard IRC resistors are readily available in nominal quantities right from distributors' well-stocked shelves. These stock units are listed in Catalog 50... write for your copy and the name of your nearest IRC distributor.


# INTERNATIONAL RESISTANCE COMPANY

401 N. Broad Street

Philadelphia 8, Pa.

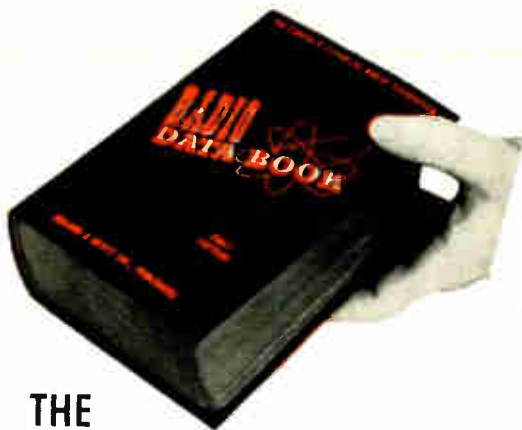In Canada: International Resistance Co., Ltd., Toronto, Licensee





## THE RADIO DATA BOOK

All data and basic knowledge in radio and electronics digested into 12 sections . . . over 1000 pages in a complete, quick to find, easy to read, handbook form.

Plan every operation in radio and electronics with the RADIO DATA BOOK. This new radio bible will be your lifelong tool . . . you will use it every day, on the board, at the bench, in the field. Use it for construction, troubleshooting and testing. The RADIO DATA BOOK will be your invaluable aid in design, experiment and in layout. It will help make your production better, faster and easier. In any and every operation in radio and electronics, you will use the RADIO DATA BOOK.

The RADIO DATA BOOK is a work of complete authority, prepared by engineers with many years of practical experience. They have been assisted by the Boland & Boyce staff of editors skilled in preparing electronics manuals for the U. S. Signal Corps for many years. These men have worked for several years gathering material for this book . . . all the knowledge of radio principles and operation . . . all the statistics . . . all the newest developments in electronics . . . every possible angle and detail. Eighteen months were spent digesting this material into the most concise, the clearest, and the most readable form. The result is this invaluable manual . . . The RADIO DATA BOOK. Whether you use this book for general reference, for scientific instruction, or for education, one thing is certain—the practical help, the daily usefulness you will derive from it will prove to be worth many, many times its astonishingly low price.

Advanced Sale . . . first printing. Only 10,000 available. . . To make sure to get your RADIO DATA BOOK, mail your order NOW.

12 sections . . . 1000 pages . . . Completely illustrated

- Section 1. THE 150 BASIC CIRCUITS IN RADIO.
- Section 2. COMPLETE TEST EQUIPMENT DATA.
- Section 3. TESTING, MEASURING AND ALIGNMENT.
- Section 4. ALL ABOUT ANTENNAS.
- Section 5. SOUND SYSTEMS.
- Section 6. ELECTRICAL AND PHYSICAL CHARACTERISTICS OF RADIO COMPONENTS.
- Section 7. COMPLETE TUBE MANUAL.
- Section 8. CHARTS, GRAPHS AND CURVES.
- Section 9. CODES, SYMBOLS AND STANDARDS.
- Section 10. 50 TESTED CIRCUITS DESIGNED FOR OPTIMUM PERFORMANCE.
- Section 11. DICTIONARY OF RADIO AND ELECTRONIC TERMS.
- Section 12. RADIO BOOK BIBLIOGRAPHY.

12 complete books in one, only \$5.00

Handsomely bound in red and gold

Less than 42¢ per book

Send in your order TODAY — \$5.00 for either book — or \$9.00 for BOTH



## THE VIDEO HANDBOOK

Everything in Television in one Complete Textbook. Over 500 pages completely illustrated.

This new handbook will be invaluable to everyone concerned with technical Television. Everything in basic theory of television through the design, construction and production of receivers to final installation, operation and maintenance is covered. This is a completely new book that includes all of the latest developments in the field—the components discussed are of the newest design . . . the practical maintenance described is a result of intensive study and operation of equipment during the last two years.

There are five completely illustrated sections in the VIDEO HANDBOOK, each over a hundred pages long. Each section completely covers one phase of television. They can be referred to constantly in any type of work dealing with this rapidly expanding field. Television transmission is thoroughly explained in order to broaden the understanding of Video reception. The techniques of receiver design are analyzed technically and from a standpoint of economics. The problems of installation of receivers and antennas are clarified, and all instructions are presented in detail. How to operate equipment for optimum satisfaction is thoroughly explained and complete maintenance of all existing components is clearly and carefully outlined—stage by stage—part by part.

No matter what your interest or position in the world of Radio and Television is—you will want the VIDEO HANDBOOK for your reference. You will want to read it for its vital, monumental story of a great new industry. And you will want it for it can help YOU make Television even greater! Send in your order today, it's an investment that will pay off day after day for years to come!

Advanced Sale, first printing. . . In order to get your Video Handbook, send in your order NOW

- The Video Handbook
- Section 1 • Theory
  - Section 2 • Design
  - Section 3 • Installation
  - Section 4 • Operation
  - Section 5 • Maintenance

500 completely illustrated pages  
handsomely bound in red and gold  
only \$5.00

**BOLAND & BOYCE INC., PUBLISHERS**

460 BLOOMFIELD AVE.

MONTCLAIR 11, N. J.

# What Every Radio Amateur Knows . .

# "NEWARK" means DEPENDABLE SERVICE

More and more, every day, Amateurs are learning to "DEPEND on NEWARK" for Service — for Values! And here are some of the reasons why:

- **Huge Stocks.** Our inventories of Standard Brand merchandise are among the largest in the country.
- **Fast Service.** Our organization is geared to speed your order through to shipment within 24 hours after receipt!
- **Values in Surplus.** As authorized agents of War Assets Administration, we're first to offer you the best in surplus material and equipment.
- **"Ham" Personnel.** We'll give

you order the kind of attention you want—because we're Hams too!

- **Three Large Stores** in New York and Chicago, with tremendous stocks and competent courteous personnel to make a great event of your shopping trip.

- **Periodic Bulletins,** keep you posted on what's new in standard equipment and bargains. To get on our mailing list, simply send your name and address on postcard.

and remember — when ordering, don't ask if we've got the item you want — just name it, that's all! We'll fill your order promptly! That's NEWARK's DEPENDABLE SERVICE.

Choose What You Need NOW  
Take ONE YEAR to Pay  
20% DOWN • 12 MONTHLY PAYMENTS

Now you can buy all the wonderful new equipment you want—  
 Receivers . . . Transmitters . . . Test Equipment . . . Sound Systems  
 . . . Parts . . . and hundreds of other items . . . for only a Small  
 Down Payment! Yes, take ONE YEAR TO PAY the Balance on our  
 convenient low Cost Plan. The only carrying charge, is 6% of the  
 unpaid balance. No More!  
 Here's how the plan works: Choose any equipment totalling \$75 or  
 more from our tremendous stock of standard lines . . . Pay only  
 20% down . . . The balance in 12 Easy Monthly Installments.  
 LIBERAL TRADE-IN ALLOWANCE



N. Y. Store  
UPTOWN



N. Y. Store  
DOWNTOWN



Chicago Store



N. Y.  
Warehouse

NEW YORK  
Offices & Warehouse  
242 W. 55th St., N.Y. 19

**NEWARK**  
ELECTRIC COMPANY, INC

CHICAGO  
323 W. Madison St.  
Chicago 6, Ill.

New York City Stores: 115-17 W. 45th St. & 212 Fulton St.

# THERMADOR


## *America's Finest*

### RADIO TRANSFORMERS


The Thermador transformer models listed have been engineered to cover the widest range of application for use in receivers, amplifiers and small transmitters. Both the L Case Type and the A Case Type are attractively finished in durable baked grey enamel. High silicon content core materials, with low current and flux densities, contribute to the engineering superiority which results in small physical size and low temperature rise of Thermador power transformers. All power transformers have static shields which are grounded to the case and core. Thermador transformers are Thermitate treated, an exclusive process which gives them resistance to withstand extreme conditions of humidity and heat.

*Thermador Transformers Are Guaranteed for One Year*

### POWER COMPONENTS

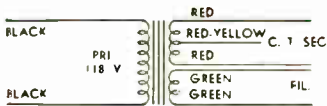

### POWER TRANSFORMERS

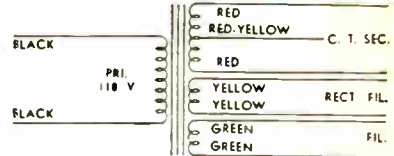


TYPE	CASE	SEC.	SEC. CUR.	RECT. FIL.	FIL.	OUTSIDE DIM.			MOUNTING CENTERS		WEIGHT	LIST PRICE
						H.	W.	D.	W.	D.		
5A4056	A	205-0-205	50 Mo.		6.3 @ 2.5A	2 <sup>3</sup> / <sub>4</sub>	2 <sup>3</sup> / <sub>8</sub>	3 <sup>1</sup> / <sub>8</sub>	1 <sup>3</sup> / <sub>4</sub>	2-13/16	2 # 5 Oz.	\$4.80
5A5066	A	270-0-270	60 Mo.	5V 2A	6.3 @ 2A	3 <sup>1</sup> / <sub>4</sub>	2 <sup>3</sup> / <sub>4</sub>	3 <sup>1</sup> / <sub>4</sub>	2	2-7/16	3 # 6 Oz.	\$5.90
5A6076	A	300-0-300	65 Mo.		6.3 @ 2.7A	3 <sup>1</sup> / <sub>4</sub>	2 <sup>3</sup> / <sub>4</sub>	3 <sup>1</sup> / <sub>4</sub>	2	2-7/16	3 #	\$5.35
5A6066	A	300-0-300	65 Mo.	5V 2A	6.3 @ 2.1A	3 <sup>1</sup> / <sub>4</sub>	2 <sup>3</sup> / <sub>4</sub>	3 <sup>1</sup> / <sub>4</sub>	2	2-7/16	3 # 6 Oz.	\$6.50
5A6086	A	300-0-300	75 Mo.	5V 2A	6.3 @ 2.85A	3 <sup>1</sup> / <sub>2</sub>	5-3/16	3-7/16	2 <sup>1</sup> / <sub>4</sub>	2-9/16	4 # 1 Oz.	\$6.80
5A6096	A	275-0-275	90 Mo.	5V 2A	6.3 Ct. 3.15A	3 <sup>1</sup> / <sub>2</sub>	3-3/16	3-5/16	2 <sup>1</sup> / <sub>4</sub>	1-15/16	3 # 11 Oz.	\$7.35
5A6116	A	310-0-310	110 Mo.	5V 3A	6.3 Ct. 5A	4 <sup>1</sup> / <sub>8</sub>	3 <sup>5</sup> / <sub>8</sub>	3-5/16	2 <sup>3</sup> / <sub>4</sub>	2	5 #	\$7.10
5A6146	A	300-0-300	135 Mo.	5V 3A	6.3 Ct. 3.3A	4 <sup>1</sup> / <sub>8</sub>	3 <sup>5</sup> / <sub>8</sub>	3 <sup>3</sup> / <sub>4</sub>	2 <sup>3</sup> / <sub>4</sub>	2 <sup>1</sup> / <sub>4</sub>	5 # 13 Oz.	\$8.10
5A6196	A	320-0-320	185 Mo.	5V 3A	6.3 Ct. 6A	4 <sup>1</sup> / <sub>8</sub>	3 <sup>5</sup> / <sub>8</sub>	4	2 <sup>3</sup> / <sub>4</sub>	2-11/16	7 # 8 Oz.	\$10.25

### CHOKES



TYPE	CASE	IND.	CURRENT	RESIS.	OUTSIDE DIM.			MOUNTING CENTERS		WEIGHT	LIST PRICE
					H.	W.	D.	W.	D.		
7L1005	L	10 Hy.	50 Mo.	450 Ohms	1 <sup>5</sup> / <sub>8</sub>	2 <sup>3</sup> / <sub>4</sub>	1 <sup>3</sup> / <sub>8</sub>	2 <sup>1</sup> / <sub>4</sub>		9 Oz.	\$2.45
7L1008	L	10 Hy.	75 Mo.	380 Ohms	2	3 <sup>1</sup> / <sub>8</sub>	1 <sup>1</sup> / <sub>2</sub>	1 <sup>3</sup> / <sub>4</sub>		8 Oz.	\$2.90
7A1809	A	18 Hy.	90 Mo.	600 Ohms	2 <sup>7</sup> / <sub>8</sub>	2 <sup>3</sup> / <sub>8</sub>	2-13/16	1 <sup>3</sup> / <sub>4</sub>	1-15/16	1 # 14 Oz.	\$4.85
7A1414	A	14 Hy.	135 Mo.	260 Ohms	3 <sup>1</sup> / <sub>4</sub>	3 <sup>3</sup> / <sub>4</sub>	3	2	2-3/16	2 # 12 Oz.	\$5.00
7A0819	A	8 Hy. Ct.	185 Mo.	212 Ohms	3-3/16	2-11/16	3 <sup>3</sup> / <sub>8</sub>	2 x 2 <sup>1</sup> / <sub>2</sub>		3 # 8 Oz.	\$5.15

### FILAMENT TRANSFORMERS

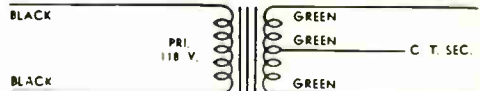

TYPE	CASE	FIL.	CURRENT	TEST	OUTSIDE DIM.			MOUNTING CENTERS		WEIGHT	LIST PRICE
					H.	W.	D.	W.	D.		
6L6022	L	6.3 Ct.	2.25 A	2000	2	3 <sup>1</sup> / <sub>8</sub>	1 <sup>7</sup> / <sub>8</sub>	2 <sup>3</sup> / <sub>4</sub>		1 # 8 Oz.	\$3.00
6A6042	A	6.3 Ct.	4.0 A	2000	2 <sup>3</sup> / <sub>4</sub>	2 <sup>3</sup> / <sub>8</sub>	3-3/16	1 <sup>3</sup> / <sub>4</sub>	2 <sup>1</sup> / <sub>4</sub>	2 # 5 Oz.	\$4.80

Cose "A" is on Enclosed Underwriters' approved cose Upright Mounted, leads through bottom of cose.  
 Cose "L" is on Open Bracket Strop Mounted type with Leads and Lugs.

All prices subject to change without notice.

Prices subject to usual trade discounts.


F.O.B. Factory. Freight allowed on shipments in U.S.A. \$100.00 net or over

**MANUFACTURED BY THERMADOR ELECTRICAL**






SEVEN LEAGUES AHEAD

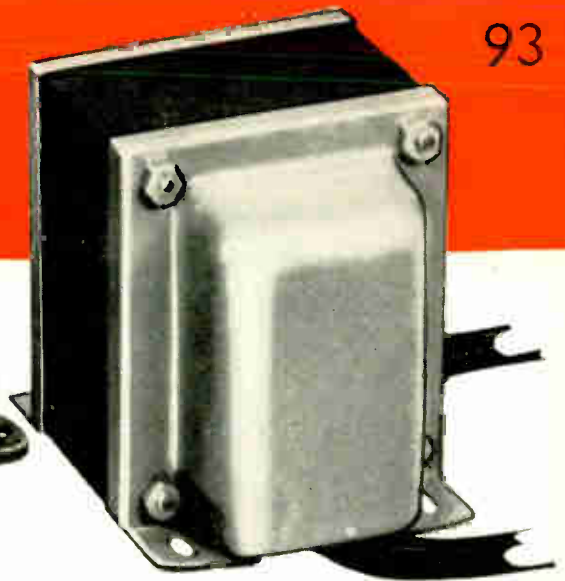

**AUDIO COMPONENTS**

**TRANSCEIVER TRANSFORMERS**

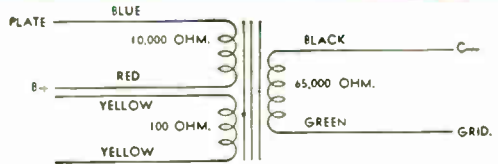


TYPE NO.	CASE TYPE	PRI.	SEC.	RATIO	OUTSIDE DIM.			MOUNTING CENTERS		WEIGHT	LIST PRICE
					H.	W.	D.	W.	D.		
2L1726	L	100-10,000	65,000	1.0:25.5	1-5/16	1-13/16	1	1 1/2	3 Oz.	\$3.65	



**INTERSTAGE TRANSFORMERS**

TYPE	CASE	PRI.	SEC.	TURN RATIO	OUTSIDE DIM.			MOUNTING CENTERS		WEIGHT	LIST PRICE	
					H.	W.	D.	W.	D.			
3A2602	A	20,000 P.P.	55,000 P.P.	1:1.73	2 7/8	2 3/8	2 3/8	1 3/4	2	1 #	13 Oz.	\$6.10
3L1103	L	10,000 Sngl.	100,000 P.P.	1:3.16	1 5/8	2 3/4	1 5/8	2 1/4			8 Oz.	\$2.95

**OUTPUT TRANSFORMERS**

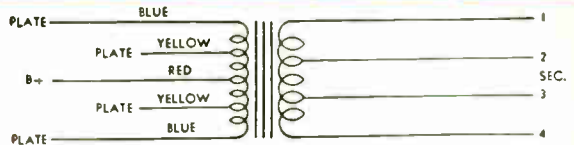

TYPE	CASE	PRI.	SEC.	WATTS	MA.	PRI.	OUTSIDE DIM.			MOUNTING CENTERS		WEIGHT	LIST PRICE	
							H.	W.	D.	W.	D.			
4L1026	L	5K, 7K, 10K, Sngl.	2-6 Ohms	2	15	15	1-5/16	1-13/16	1 1/8	1 1/2		3 Oz.	\$2.70	
4L1048	L	3.5K, 5K, 8K, 10K, Sngl. & P.P.	2-8 Ohms	5	40	40	1-7/16	2-7/16	1 1/2	2		5 Oz.	\$3.10	
4L4066	L	2K, 2.5K, 3K, 4K, Sngl.	2-6 Ohms	5	55	55	1 1/2	2 3/8	1 1/2	2		5 Oz.	\$3.00	
4L1051	L	4K, 5K, 8K, 10K, P.P.	2-12 Ohms	10	50	50	2 3/8	3	1 7/8	2 1/2	1 #	5 Oz.	\$3.55	
4L1046	L	2K, 2.5K, 3.5K, 5K, 7K, 10K, Sngl.; 3K, 5K, 7K, 10K, P.P.	1-6 Ohms	7.5	45	45	1-9/16	2 3/4	1 1/2	2-5/16		8 Oz.	\$3.25	
4AB105	A	5 & 8K C.T. P.P.	4-8-500 Ohms	15	95	95	2 3/4	2 3/8	2 7/8	1 3/4	x 1-15/16	1 #	12 Oz.	\$6.00
4A7145	A	5 & 6.6K C.T. P.P.	3-4-6-8-16-500 Ohms	26	140	140	3 1/2	2-15/16	3 1/2	2 1/4	x 2-9/16	4 #	8 Oz.	\$9.50

OTHER MODELS WILL BE AVAILABLE SOON—WRITE FOR INFORMATION

**MANUFACTURING COMPANY • LOS ANGELES 22, CALIF.**

# INVARIABLY IT'S VALPEY



VR6



VS1



VR1



A1



VS5



CBC



VT1



CF1



XL-100



XLS



VM2



VD5



VD8




CBC-O



VP3



VDO

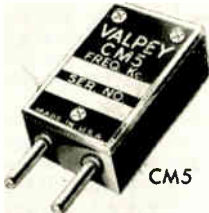

CM5



CM1

TYPE	FREQUENCY RANGE	PINS	DESCRIPTION	USE
CBC-O	60-10000KC	Standard 5-Pin Mount	6, 8, 10 Volt Oven Variable Air Gap $\pm 1/2^{\circ}$ C. Accuracy	Broadcast, Fixed Stations and Freq. Standards.
CBC	60-10000KC	Special	Micrometer Adjust. Variable Air Gap	Broadcast, Fixed Stations and Freq. Standards.
VDO	1000-10000KC	Standard 5-Pin Mount	Single or Dual 6 Volt Oven Gasket Sealed $\pm 1/2^{\circ}$ C. Accuracy	Fixed and Mobile for Transceiver Equipment, Railroad Communications.
VS5	1000-4000KC	.125 Dia. Pins $3/4"$ Spacing	Variable Air Gap Horizontal Mount	Police and Fixed Stations.
VS1	1000-4000KC	.125 Dia. Pins $3/4"$ Spacing	Fixed Air Gap Pressure Clamped Horizontal Mount	Police and Fixed Stations.
VD5	1000-6000KC	Special 3-Pin Mount $5/32"$ Dia.	Single or Dual Crystals Gasket Sealed	Marine, Aircraft or Police.
VD8	1000-6000KC	Octal 1, 8-4, 5 Xtal A—Xtal B	Single or Dual Crystals Gasket Sealed	Marine, Aircraft or Police.
XLS	80-1000KC	.125 Dia. Pins $3/4"$ Spacing	Clamped Crystal Mount. Hermetically Sealed	Radar and Fixed Stations in the Low Frequency Range.
XL-100	100KC	.125 Dia. Pins $3/4"$ Spacing	Clamped Crystal Mount. Hermetically Sealed	Frequency Standards.
VT1	1000-10000KC	Octal 2, 3-7, 8	Vacuum Sealed Metal Tube Type Unit	Frequency Meters, Standards and General Applications.
VM2	1000-4000KC	.125 Dia. Pins $3/4"$ Spacing	Fixed Air Gap Horizontal Mount Gasket Sealed	Fixed and Mobile Applications.
VP3	2000-60000KC	.125 Dia. Pins $3/4"$ Spacing	Fixed Air Gap Horizontal Mount Gasket Sealed	Marine, Police Amateur, Fixed and Mobile Stations.
CM1	1000-4000KC	.125 Dia. Pins and G.R. Pins $3/8"$ , $5/8"$ , $7/8"$ , .850 Spacing	Gasket Sealed Fixed Air Gap Vertical Mount	Marine, Police, Aircraft and General Applications.
CM5	2000-60000KC	.094 Dia. Pins .486" Spacing	Gasket Sealed Fixed Air Gap Vertical Mount	Marine, Police, Amateur, Fixed and Mobile Stations.
A1	1000-4000KC	Solder Lugs	Flat Compact Gasket Sealed	Aircraft
VR1	2000-10000KC	.125 Dia. Pins .486" Spacing	Fixed Air Gap Vertical Mount Gasket Sealed	Marine, Police, Aircraft.
CF1	455, 456, 465 KC	Solder Lugs	Small, Flat, Compact	Filter Applications.
VR6	4000-60000KC	.050 Dia. Pins .486" Spacing	Vacuum Sealed Metal Case	Mobile, Fixed Stations, VHF, Experimental.

For every crystal application, VALPEY invariably gives outstanding performance. Select your VALPEY unit from the above chart, or send your specific crystal requirements to VALPEY. In every field where accurate crystal control is the aim — invariably it's VALPEY.

**Valpey**  
CRYSTALS

HOLLISTON, MASS.

Craftsmanship in Crystals Since 1931

Hallicrafters  
 Guardian  
 Cardwell  
 Eimac  
 Hickok  
 Burgess  
 Audiodiscs  
 IRC  
 Jensen  
 Meissner  
 Ohmite  
 National  
 Raytheon  
 Patter & Brumfield  
 Ohmite  
 Universal  
 Taylor  
 Sangamo  
 Ward Leonard  
 Mallory  
 H & H  
 Belden  
 Hammarlund  
 General Electric  
 Cornell-Dubilier  
 Brush  
 Astatic  
 Hytron  
 Johnson  
 Millen  
 RCA  
 Shure  
 Thordarson  
 UTC  
 Clarostat  
 Browning  
 Mueller  
 Rider  
 Simpson  
 Tobe  
 Bogen  
 Bliley  
 Amphenol  
 Barker-Williamson  
 Amperite  
 Mu-Switch  
 Aerovox  
 Advance  
 Stancor  
 Abbott  
 Struthers-Dunn  
 Triplett  
 Centralab  
 Gammatron  
 ESICO  
 DUNCO  
 Dumont  
 Dialco  
 Coto  
 Cetron  
 Cannon-ball  
 Brandes  
 Birnbach  
 ATR  
 Arrow  
 Heintz and Koufman  
 Kato  
 Lenk  
 Pyrex  
 Recordisc  
 Sigma  
 Trimm  
 Turner  
 Kwikheat  
 Kester

**The RADIO SHACK**  
 167 WASHINGTON ST.  
 BOSTON, MASS., U.S.A. ★

## Reliable Service

FOR AMATEURS ALL OVER THE WORLD

WHY do hams in Casablanca, Buenos Aires, Athens, Shanghai, and Helsinki seek out "The Shack" — by mail, cable, and sometimes in person? BECAUSE since 1924 RADIO SHACK has meant RELIABLE SERVICE to amateurs in the far corners of the world . . . Service made possible by our real understanding of the problems of the amateur and by an enormous stock of the products of all the world-famous manufacturers.

The service that has made Radio Shack customers in Cavite and Constantinople was established for you — the amateurs of America. Use it to build your better, bigger "Ham Shack" — faster, for less cost.

You'll find our Catalog H-48 a handy aid. Write today — it's free.

# What you should know about POST WAR CRYSTALS



**B**ECAUSE of the lack of accurate information supplied the ham fraternity, more than ordinary trouble is being experienced in getting post-war crystals to operate properly. Regardless of make, many amateurs are having difficulty with frequency drift and with chirps when the oscillator is keyed. Because hams are a curious group, who want the facts, here they are!

Good post-war crystals are definitely superior to pre-war types — in applications for which they were intended.

The new post-war crystals are nearly all AT or BT cuts, with a temperature coefficient of less than 2 parts per million per degree Centigrade, compared to old pre-war X or Y cuts with 23 to 100 parts per million.

About 1940, equipment manufacturers and the Armed Forces wanted better crystals — and realized that to have them, crystals were to be used for frequency control not for the handling of huge amounts of power. Thus smaller crystals were satisfactory, and with drift but 10% of what it used to be, the use of a huge plate to dissipate heat was no longer necessary. These crystals

met the military demands for they also possessed excellent activity.


Prior to the war, acid etching was almost unknown. Crystals were finished with abrasive. This led to "aging" — a gradual increase in frequency as small chips broken loose by the abrasive came off the surface of the crystal — and reduced activity. By acid etching as it is done at the James Knights plant, crystals are "stabilized" so these effects were eliminated and increased activity was achieved. Ham equipment was usually designed to use the pre-war, less active, unetched crystals. Unless precautions are taken, the new crystal when plugged into old type equipment frequently results in excessive heat and fracturing due to violent activity.

The solution is simple — reduce crystal current and see what fine performers these new crystals really are!

A word about some of the surplus variety: many are quickly lapped into a ham band without etching.

For the convenience of amateurs, James Knights manufactures a complete line of crystals in both the  $\frac{1}{2}$ " and  $\frac{3}{4}$ " pin spacing.

## Crystals for the Critical

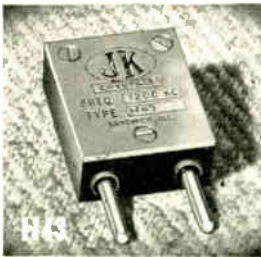

$\frac{3}{4}$ " pin spacing in a frequency range of 2,000 to 20,000KC.




H173

### NEW 10 METER CRYSTAL

No special circuit required. Third mode crystals, 27 to 29.7 MC hermetically sealed, with standard  $\frac{1}{2}$ " pin spacing. Also available in 25 MC for doubling to 6 meters.

Price - - - - \$4.95.

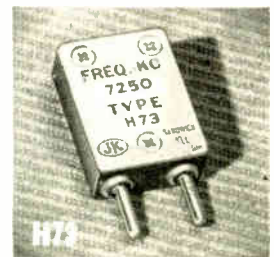

$\frac{1}{2}$ " pin spacing, frequency range 2,000 to 20,000 KC.

**The JAMES KNIGHTS Co.**  
SANDWICH, ILLINOIS

Manufacturers of a Complete Line of Industrial, Broadcast, Communication and Amateur Crystals.  
**WRITE FOR ILLUS. CATALOGS**

# Knock at Any Ham Shack Door...

Knock at a thousand ham shack doors—*anywhere*—and the chances are you'll find ALLIED-supplied station equipment and a file of well-thumbed ALLIED Catalogs in *most* of them. . . .

Amateurs everywhere—for more than 25 years—have looked *first* to ALLIED as their most dependable supply source. "*Equipped by ALLIED*" has become a popular phrase, descriptive of thousands of fine amateur stations all over the country and abroad.

Our large staff of hams, who share your interest in Amateur radio, see to it year-in and year-out that ALLIED has ready for immediate shipment at the lowest prices, the world's largest stocks of quality station equipment. Try us. Count on us. We'll deliver the goods to your shack door—and stay right with you on any and all of your problems. . . .



WRITE FOR YOUR COPY OF THE  
LATEST ALLIED CATALOG

IN AMATEUR RADIO  
**ALLIED RADIO**  
FOR OVER 25 YEARS

833 W. JACKSON BLVD., DEPT. 10-8  
CHICAGO 7, ILLINOIS

97



**A**lways First with the Latest  
**L**argest Stocks in the World  
**L**owest Prevailing Prices  
**I**mmEDIATE Shipment  
**E**asiest Time Payments  
**D**ependable Ham Service




WHEN

*Code Speed*

MAKES YOUR HEAD WHIRL

*take it easy!*

**THIS FREE BOOK  
TELLS YOU HOW..**

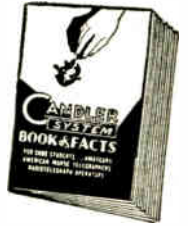

EVERY OPERATOR (COMMERCIAL or AMATEUR)  
SHOULD HAVE A COPY OF THIS BOOK . . .

Are you wasting your time because you neglect or overlook increasing your speed and efficiency? Then the Candler System Book of Facts is just the thing for you. It tells you in clear, easy-to-read terms which are scientific and distinctive, how to learn code or improve your code proficiency to meet any requirements.

Many operators face the handicaps of nervous tension. If you are one, the Candler system will relieve you of this insecurity and build up self-confidence in your own ability. In this way you will be able to apply your talents to top speed and maximum proficiency.

Thousands of operators today learned the Candler Champion way. Many of the foremost

operators in the business today are included among Candler's former students. You have the same opportunity to better your own speed and efficiency now. Perhaps you want to become a Commercial Operator. Or maybe you just want the thrill of being an expert Amateur Operator. In either case the technique of fast, accurate telegraphing and the ability to meet all requirements is necessary. The Candler System offers you all these.

Develop your skill now. Improve your speed. Expert operators are always in demand so it is very wise to prepare yourself for the top bracket among operators. That's what the Candler System is designed for — and at a price so reasonable that *anyone* interested in developing skill and speed can afford.

## THE *Candler* WAY IS THE *Champion* WAY

### NO EXPENSIVE EQUIPMENT NEEDED

TED McElroy is the Official Champion Radio Operator, Speed 75.2 w.p.m., won at Asheville Code



Tournament, July 2, 1939. Here is what World Champion McElroy has to say: "My skill and speed are the result of the exclusive, scientific training Walter Candler gave me. Practice is necessary, but without proper training to develop Concentration, Co-ordination and a keen Perceptive Sense, practice is of little value. One likely will practice the wrong way."

Special training is the prime requisite in learning code or in developing skill and speed. CANDLER, from wide experience in training high-speed operators, offers a System designed to make you an expert in a simple, thorough and interesting way — to help you get ahead faster and go further. Much valuable time is saved when you know the CANDLER SYSTEM, and apply the laws and fundamentals governing speed and accuracy. The CANDLER SYSTEM offers you SPEED, SKILL and TELEGRAPHING PROFICIENCY.

#### For BEGINNERS and OPERATORS

The *SCIENTIFIC CODE COURSE*, especially designed for the beginner. Teaches the basic principles of code operation scientifically.

The *HIGH SPEED TELEGRAPHING COURSE*, intended for the operator who wishes code speed and skill, to become a good operator or a better one faster.

The *HIGH SPEED TYPEWRITING COURSE*, designed for those who desire typewriting proficiency and speed. Especially designed for copying messages and press with typewriter.

**SEND FOR YOUR BOOK NOW — YOU'LL NEVER REGRET IT**

**CANDLER SYSTEM COMPANY**

P. O. Box 928, Dept. 10, Denver 1, Colo., U. S. A.  
and at 121 Kingsway, London, W.C. 2, England




101-K (AC) 201-K (DC)



Series 900




Series 300

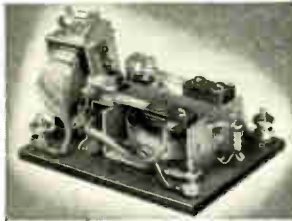

Series 600



Series 1000

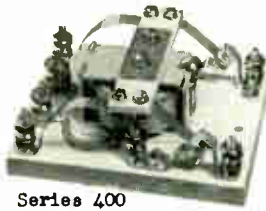

Series 400



Types  
8200 (DC)  
7200 (AC)




Hermetically  
sealed



Type 750



Type 800

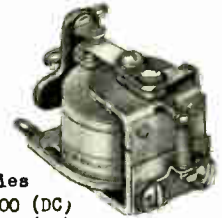

Series  
K1600 (DC)  
K1500 (AC)



Series 950



Type 1200



Series  
5200 (AC)  
6200 (DC)

TYPE	USE	CONTACTS	COIL VOLTS	SIZE
101-K (AC) 201-K (DC)	Keying	1/8" Silver DPST P.O.	1 - 440 V.A.C. 1 - 220 V.D.C.	2 x 3 x 1 9/16
Series 300	Time delay	1/8" Silver SPST - DPST NO or NC	1 - 440 V.A.C. 1 - 220 V.D.C.	3 1/4 x 2 5/8 x 1 1/2
Series 400	Antenna relay	1/8" Silver DPST	1 - 440 V.A.C. 1 - 220 V.D.C.	3 9/16 x 2 13/16 x 1 5/8
Series 600	Lock-up Elect. reset	1/8" - 3/8" DPST, DPST P.O., DPST P.C.	1 - 440 V.A.C. 1 - 220 V.D.C.	3 7/16 x 2 1/2 x 2 3/8
Type 750	Overload Elect. reset	1/8" Silver DPST	Type A 250-500 Ma, Type B 500-1000 Ma.	4 x 2 13/16 x 2 5/16
Type 800	Underload	1/8" Silver DPST	Type A 150-300 Ma, Type B 300-500 Ma.	3 x 3 x 1 7/8
Series 900	Impulse	DPST, DPST 1/8", 3/16", 1/4"	1 - 440 V.A.C. 1 - 220 V.D.C.	3 1/4 x 2 1/4 x 2
Series 1000	Hidget ceramic insulated rel.	1/8" Silver DPST or DPDT	1 - 440 V.A.C. 1 - 220 V.D.C.	2 1/4 x 1 1/2 x 1 5/16
Series K1600 (DC) Series K1500 (AC)	Hidget	1/8" or 1/16" up to 3PDT	1 - 220 V.A.C. 1 - 110 V.D.C.	1 1/4 x 1 1/16 x 1 1/8
Type 1200	Ultra-sensitive DC relay	1 amp 110 V.A.C.	1 - 30,000 Ohms	2 9/16 x 2 x 1 1/2
Type 8200 (DC) Type 7200 (AC)	52 or 75 Ohm Coaxial rel.	1/8" Silver with DPST Auxil. contacts	1 - 440 V.A.C. 1 - 220 V.D.C.	3 1/4 x 2 7/8 x 1 3/4
Series 950	Industrial Control	1/8" - 3/8" SPST - DPST	1 - 440 V.A.C. 1 - 220 V.D.C.	2 21/32 x 1 1/2 x 1 1/2
Series 5200 (AC) Series 6200 (DC)	Hidget Telephons	1/8" or 3/16" SPST - DPST	1 - 440 V.A.C. 1 - 220 V.D.C.	1 1/2 x 1 1/8 x 1 5/16

Hermetically  
sealed

This is a sealed unit available for use with  
most hidget and standard sized relays.

## A few BEST SELLERS in the ADVANCE LINE

Conservatively rated . . . carefully  
engineered . . . and sold by leading  
jobbers throughout the U.S.A. and  
abroad . . . Advance relays continue  
to enjoy ever increasing preference  
among "hams" and design engi-  
neers alike.

**FREE catalog**

shows prices and complete details of  
entire line.

**WRITE  
TODAY!**

  
**Advance Relays**

**ADVANCE ELECTRIC & RELAY CO.**  
1262 West 2nd Street, Los Angeles, California • Phone Michigan 9331

# matched in appearance..



DB 22A  
STANDARD

RME 45B

VHF 152A  
STANDARD

## THE RME 45 RECEIVER

The RME 45 communications receiver provides peak performance on both the high and low frequencies. It's accomplished by the use of loctal tubes — shorter leads — reduced distributed capacity and temperature compensating padders.

Especially desirable are two additional refinements — Cal-O-Matic two speed tuning and calibrated bandspread. Two speed tuning tunes fast to cover the band, tunes slowly to find the station. It provides the maximum in mechanical and electrical efficiency. Other features include:

- Streamlined two-toned cabinet that matches the Standard DB 22 A and VHF 152 A in size and appearance
- Six Bands, 550 to 33,000 KC
- Automatic Noise Limiter
- Variable Crystal Filter
- Signal Level Meter

## DB 22 A PRESELECTOR

The new DB 22 A has been completely redesigned for greater efficiency and higher signal to noise ratio. It uses two of the new efficient 6BA6 miniature tubes. The DB 22 A provides tremendous increase in both gain and selectivity when used with a good communications receiver. Average overall gain is 30 DB achieved throughout the tuning range of .54 to 44 MC. Image rejection is phenomenal — better than 50 DB with a communications receiver having a single stage of RF. The DB 22 A has its own power supply — is entirely self contained — entirely in a class by itself! This preselector also comes in two models to match in size and appearance either the RME 45 or the RME 84 receivers. The larger cabinet of the DB 22 A matches the RME 45, the DB 22 A "Type S" matches the smaller RME 84. The price is the same. Both are identical except for cabinet size.

## *Just Announced*

### THE HF 10-20 CONVERTER FOR 10-11-15 and 20 METERS

Because of the double conversion system, the HF 10-20 provides outstanding and imageless reception on the above frequencies. And it's an especially vital adjunct to those receivers that tune only to 18 MC. Features include provision for four separate antennas, self contained power supply, planetary tuning mechanism and many others.





# Unmatched in performance!



VHF 152A  
TYPE S

RME 84

DB 22A  
TYPE S

## THE VERSATILE RME 84

The RME 84 is versatile because it can be used for home, portable or mobile operation. It operates off 110 AC or a 6 volt power pack with cable attached. Optional equipment for the RME 84 is the RME VP2 — power pack and the carrier level "S" meter, CM-1, both with cord and plug.

It's an all band coverage receiver for phone or CW — RME's first entry into the lower priced communications field, and built to RME's rigid specifications of quality components and quality workmanship. Other features include:

- Excellent over-all sensitivity
- All gear and planetary tuning mechanism
- New "loctal" tubes
- Four tuning ranges: .54 to 44 MC
- One preselector stage
- Automatic noise limiter
- Self contained shock mounted PM speaker
- Seven tube superheterodyne circuit, excluding rectifier.

## THE VHF 152

Utilizing the extremely effective double conversion system, the VHF 152 Converter provides peak performance on 2, 6, 10 and 11 meters when used with any communications receiver. Wide bandspread on each band is obtained through 180 degree travel over a 7" diameter scale with accurate calibration.

## ANTENNA CONNECTIONS

Provision is made for the use of four separate antenna connections. Thus each band has its own especially designed antenna input circuit. Other features include an individual power supply, shielded output cable, calibrated dial, all-gear planetary tuning mechanism, voltage regulator, VHF oscillator circuits that are temperature stabilized and new high gain miniature tubes.

*Illustrated Folder Available For Each RME Product*




# RME

FINE COMMUNICATIONS EQUIPMENT

## RADIO MFG. ENGINEERS, INC.

*Provia 6, Illinois U. S. A.*

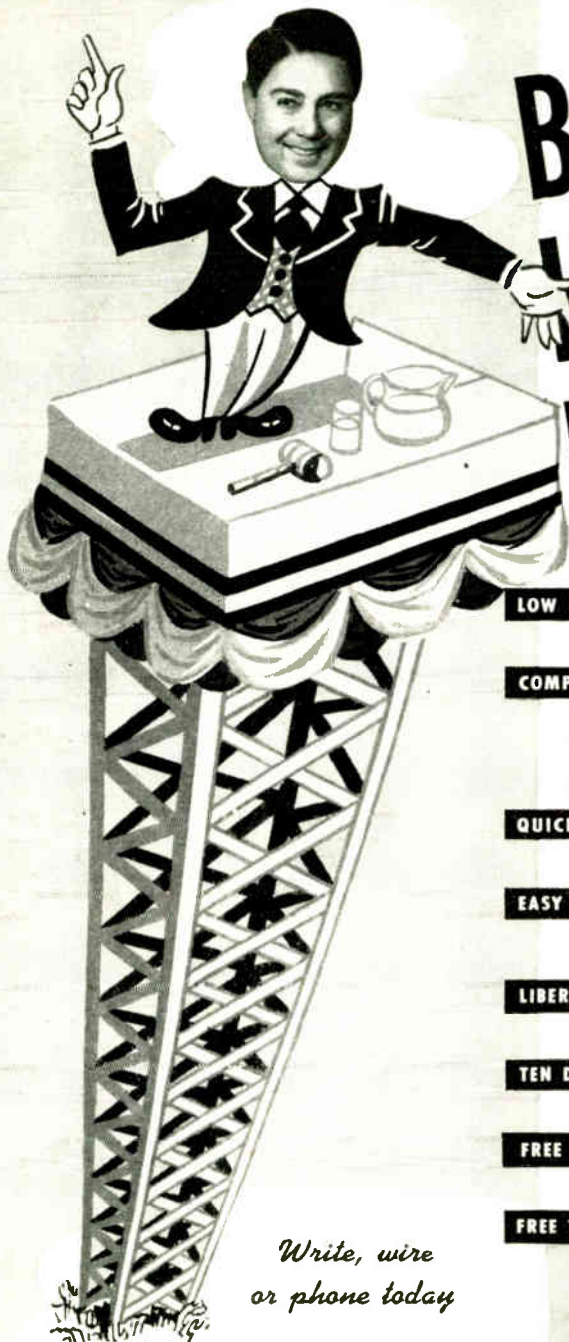

# BOB HENRY'S PLATFORM

## LOW PRICES

I guarantee to sell to you as cheap as you can buy anywhere.

## COMPLETE STOCKS

Hallicrafters, National, Hammarlund, Collins, Millen, RME, Pierson, Temco, Meissner, Supreme Transmitters, Meck, Gordon, Ampheno-Mims, RCA, Vibroplex, Sonar, all other amateur receivers, transmitters, beams, parts, etc. If it is amateur or communications equipment—I can supply it.

## QUICK DELIVERY

Mail, phone, or wire your order. *Shipment within four hours.*

## EASY TERMS

I have the world's best time sale plan because I finance the terms myself. I save you time and money. I cooperate with you. Write for details.

## LIBERAL TRADE-IN ALLOWANCE

Other jobbers say I allow too much. Tell me what you have to trade and what you want.

## TEN DAY FREE TRIAL

Try any receiver ten days, return it for full refund if not satisfied.

## FREE NINETY DAY SERVICE

I service everything I sell free for 90 days. At a reasonable price after 90 days.

## FREE TECHNICAL ADVICE

and personal attention and help on your inquiries and problems.

*Write, wire  
or phone today*


*Orders from outside continental  
U.S.A. also welcomed*

Butler, Missouri
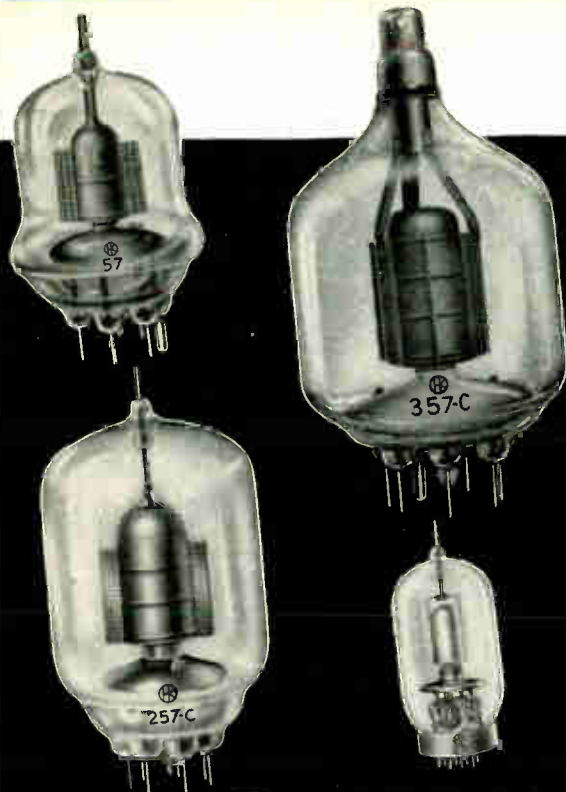
# HENRY RADIO STORES

Los Angeles 25, Calif.

"WORLD'S LARGEST DISTRIBUTORS OF SHORT WAVE RECEIVERS"



## Four new HK pentodes with higher wattage, higher frequency ratings

Four new Gammatron pentodes, with power output ratings from 25 to 750 watts, and maximum frequency ratings from 100 to 200 Mc. are the most recent additions to the HK line.

The HK-27 is a small radiation cooled instant-heating pentode ideal for mobile installations, operating efficiently throughout the VHF band. The HK-257C is similar to the widely used 257B, but has a higher maximum frequency, and lower interelectrode capacitances. The two other new Gammatron pentodes are the HK-57 and 357C.

You can rely on the electrical and mechanical ruggedness of Gammatron tubes. Their reputation for endurance and long life is based on 20 years of amateur, emergency and government communication service.

... SEND FOR DATA SHEET ON ANY OF THESE TUBES

# Gammatrons



Gammatron Tube Division  
**HEINTZ AND KAUFMAN LTD.**  
 South San Francisco · California  
 Communications Equipment Division · 50 Drumm Street  
 San Francisco · California

TYPE NO.	24	24G	27*	54	57*	254	257B*	257C*	304L	304H	354C	354E	357C*	454L	454H	654	854L	854H	1054L
MAX. POWER OUTPUT: Class 'C' R.F. ....	90	90	50	250	250	500	400	400	1220	1220	615	615	750	900	900	1400	1800	1820	3000
PLATE DISSIPATION: Watts .....	25	25	25	50	75† 50‡	100	125 † 100 ‡	125† 100‡	300	300	150	150	250	250	250	300	450	450	750
Ave. AMPLIFICATION FACTOR .....	25	25	-	27	-	25	-	-	10	19	14	35	-	14	30	22	14	30	13.5
MAX. RATINGS: Plate Volts .....	2000	2000	1000	3000	3000	4000	4000	4000	3000	3000	4000	4000	5000	5000	5000	4000	6000	6000	6000
Plate M.A. ....	75	75	10.0	150	150	225	225	225	1000	1000	300	300	375	375	375	600	600	600	1000
Grid M.A. ....	25	25	10	30	15	40	25	25	150	150	60	70	20	60	85	100	80	110	125
MAX. FREQUENCY, Mc.: Power Amplifier ..	200	300	200	200	200	175	200	125	175	175	50	50	150	150	150	50	125	125	100
INTERELECTRODE CAP: C <sub>g-p</sub> u.u.f. ....	1.7	1.6	0.035	1.8	0.05	3.6	0.08	0.04	9	10.5	3.8	3.8	0.08	3.4	3.4	5.5	5	4	5
C <sub>g-f</sub> u.u.f. ....	2.5	1.8	5.7‡	2.1	7.29‡	3.3	10.5‡	6.2‡	12	14	4.5	4.5	11.9‡	4.6	4.6	6.2	6	8	8
C <sub>p-f</sub> u.u.f. ....	0.4	0.2	2.9*	0.5	3.13*	1.0	4.7*	4.5*	0.8	1.0	1.1	1.1	4.6*	1.4	1.4	1.5	0.5	0.5	0.8
FILAMENT: Volts .....	6.3	6.3	6.3	5.0	5.0	5.0	5.0	5.0	5.10	5.10	5	5	5.0	5	5	7.5	7.5	7.5	7.5
Amperes .....	3	3	3.0	5	5.0	7.5	7.5	7.5	26.13	26.13	10	10	10.0	11	11	15	12	12	21
PHYSICAL: Length, Inches .....	4 1/4	4 1/4	4	5 7/16	4 1/8	7	6 3/8	5 1/8	7 3/8	7 3/8	9	9	6 1/2	10	10	10 3/8	12 3/8	12 3/8	16 3/8
Diameter, Inches ..	1 1/8	1 3/8	1 1/8	2	2 3/8	2 3/8	2 1/2	3 1/8	3 3/8	3 3/8	3 3/8	3 3/8	3 1/2	3 3/8	3 3/8	3 3/8	3 3/8	3 3/8	3 3/8
Weight, Oz. ....	1 1/2	1 1/2	1 1/2	2 1/2	2 1/2	2 1/2	3 1/2	3 1/2	9	9	6 1/2	6 1/2	7	7	7	14	14	14	42
Base .....	Small UX	Small UX	Small Octal	Std. UX	#247 Johnson	Std. 50 Wott	7 Pin	#247 Johnson	John-son #213	John-son #213	Std. 50 Wott	Std. 50 Wott	Special	Std. 50 Wott	Std. 50 Wott	Std. 50 Wott	Std. 50 Wott	Std. 50 Wott	John-son #214

\* Beam pentode    † Input    • Output    ‡ Intermittent telegraph rating    § Constant key down rating

# NEW TUBES ARE NO LUXURY!

INCREASED EFFICIENCY WITH NEW RATINGS! LONGER LIFE!

**T**HERE'S A DIFFERENCE, in YOUR favor when you specify the new, improved RCA Power Tubes. Tubes account for but a small fraction of the cost of your rig, yet their efficiency and stamina determine your operating results! **NEW TUBES ARE YOUR BEST BUY!**

Newly developed materials and manufacturing technique contribute greatly to RCA's success in making fine vacuum tubes.

The Terminal Radio Corporation is proud, as one of RCA's tube distributors, to offer these improved RCA tubes for amateur radio and commercial applications.

Each and every NEW RCA tube is accompanied with the full written warranty of the Radio Corporation of America guaranteeing its faithful high performance.

## Check These ADVANTAGES!

You get them **ONLY** when you buy **NEW** tubes (now in stock at **TERMINAL**).

- ✓ Latest design improvements
- ✓ Newest post-war materials
- ✓ Highly uniform characteristics
- ✓ Increased power ratings for many types
- ✓ Manufacturer's liberal warranty
- ✓ Confidence in Quality — No uncertainty about this!



## NEW, IMPROVED RCA POWER TUBES — IN STOCK



TRIODES		BEAM POWER TUBES AND PENTODES		VOLTAGE REGULATORS		RECTIFIERS Vacuum Types	
800	\$10.00	2E24	\$ 4.60	OA2	\$ 2.00	2X2/879	\$ 1.80
805	11.75	2E26	3.50	OA3/VR75	1.20	2X2-A	1.80
809	3.50	3E22	6.85	OC3/VR105	1.20	2V3-G	2.75
810	12.50	4E27/8001	27.50	OD3/VR150	1.20	5R4-GY	1.30
811	3.50	802	4.25			579-B	12.00
812	3.50	803	21.00	<b>RECTIFIERS</b>			
826	9.25	804	15.00	Mercury Vapor			
830-B	10.00	807	2.30	Types			
8000	13.25	813	14.50	575-A	\$28.00	1616	7.50
8003	11.25	814	12.50	816	1.25	8013-A	9.00
8005	7.00	815	6.25	866-A/866	1.75	8020	20.00
8012-A	14.00	828	12.50	872-A/872	7.50	<b>TETRODES</b>	
8025-A	9.25	829-B	14.75	5558	12.00	4-125A/4D21	\$25.00
		832-A	10.60	5561	33.00	860	30.00
		837	4.15	8008	7.50	865	10.00

We are also distributors for AMPEREX, EIMAC, GENERAL ELECTRIC, H-K GAMMATRONS, HYTRON, RAULAND VISITRONS, RAYTHEON, SYLVANIA, TAYLOR and UNITED tubes. WRITE TO US FOR COMPLETE PRICE LISTS AND NEW OPERATING DATA, FREE ON REQUEST.

Ask us for Newest Listing of RCA Radiotron Receiving Tubes — *We Have Them!* WE PAY FOR SHIPPING AND INSURANCE on all tube orders over \$5.00 when accompanied with remittance in full.

# TERMINAL

## RADIO CORPORATION

Distributors of Radio & Electronic Equipment

85 CORTLANDT STREET, NEW YORK 7, N. Y.

PHONE: WOrth 2-4415



# RIDER Radio Publications

## UNDERSTANDING MICROWAVES

BY VICTOR J. YOUNG. For those who have not previously considered radio waves shorter than 10 centimeters. Provides foundation for understanding various microwave developments of past five years.

**CHAPTER HEADS:** The Ultra High Frequency Concept; Stationary Charge and Its Field; Magnetostatics; Alternating Current and Lumped Constants; Transmission Lines; Poynting's Vector and Maxwell's Equations; Wave-guides; Resonant Cavities; Antennas and Microwave Oscillators; Radar and Communication. Section Two is devoted to descriptions of Microwave Terms, Ideas and Theorems. Index. 400 Pages—Price \$6.00.

## A-C CALCULATION CHARTS

BY R. LORENZEN. Students and engineers will find this book invaluable. Simplifies and speeds work involving AC calculations. Contains 146 charts. Covers AC calculations from 10 cycles to 1000 megacycles. 160 Pages—Price \$7.50.

## INSIDE THE VACUUM TUBE

BY JOHN F. RIDER. A new approach and technique that makes its message easy to understand. Here is a solid, elementary concept of the theory and operation of the basic types of vacuum tubes based on the electro static field theory. Throughout the entire book, which covers diodes, triodes, tetrodes, and pentodes, the aim is to present a clear physical picture of exactly what is happening in a vacuum tube, inclusive of the development of characteristic curves of all kinds, and associated load lines.

A goldmine for the student; a must for the libraries of servicemen, amateurs and engineers. 425 Pages—Price \$4.50.

## THE CATHODE-RAY TUBE AT WORK

BY JOHN F. RIDER. This book presents a complete explanation of the various types of cathode-ray tubes and what role each element within the device plays in making voltages and currents visible. The only book of its kind!

This volume offers a complete and elaborate, easy to understand explanation of the theory of the tube. It is this information, with many hundreds of typical oscillograms illustrating practical applications, which makes this book so valuable. 338 Pages. 450 Illustrations—Price \$4.00.

## RIDER MANUALS—FOR RADIO TROUBLE SHOOTING

Unchallenged authority in the field of radio servicing reference books. Containing receiver schematics, voltage data, alignment data, resistance values, chassis layouts and wiring and trimmer connection material they aid in quick location of faults in ailing receivers. Sixteen volumes cover all important American made receivers issued from 1920 to early months of 1947 inclusive.

VOLUME XVI (including "HOW IT WORKS" Book) ..... \$ 6.60  
 VOLUME XV (including 181 pg. "HOW IT WORKS" Book) 18.00  
 VOLUME XIV to VII. Each volume ..... 15.00  
 VOLUME VI ..... 11.00  
 ABRIDGED VOLUMES I to V (II volume) ..... 17.50  
 RECORD CHANGERS and RECORDERS ..... 9.00

## AN HOUR A DAY WITH RIDER SERIES

**D.C. VOLTAGE DISTRIBUTION IN RADIO RECEIVERS**—The applications of Ohm's law, practically interpreted in terms of how circuits are employed in radio receivers.

**ALTERNATING CURRENTS IN RADIO RECEIVERS**—An exposition on fundamentals of alternating currents and voltages and where they appear in receiving system.

**RESONANCE AND ALIGNMENT**—The importance of the subject in relation to all communication systems, and the clarity of this text, have produced a sale of over 50,000 of this title.

**AUTOMATIC VOLUME CONTROL**—An easy to understand explanation of how AVC is utilized in radio receivers.

96 PAGES EACH (ILLUSTRATED) — \$1.25 EACH

## FOR PUBLICATION

### IN WINTER OF 1947-48

F-M Transmission and Reception

Broadcast Operator's Handbook

The Signal Generator at Work

R-F and I-F Selectivity

Understanding Low Power Transmitters

Adjusting Transmitters with Oscilloscope

Installing and Servicing Low-Power P-A Systems

Understanding Vectors and Phase in Radio Work

Watch for Publication Dates

## FREQUENCY MODULATION

One of the most talked-of developments in radio field; details of F-M receiver maintenance and how it differs from A-M. 136 Pages—81 Illustrations—\$2.00.

## SERVICING BY SIGNAL TRACING

Explains approved system of diagnosing faults in radio receivers and all kinds of communication systems. The method was introduced by the author of the book, John F. Rider. The system has won endorsement by individuals and associations the world over as well as technical branches of our government. 360 Pages—188 Illustrations—\$4.00. Spanish edition—\$4.00.

## VACUUM TUBE VOLTMETERS

Explains the theory upon which the functioning of the different types of v-t voltmeters is based, and also the practical applications of these instruments. Includes a bibliography consisting of 145 international references. 180 Pages—111 Illustrations—\$2.50.

## THE METER AT WORK

How each type of meter works and how each is used in the field to best advantage. Covers whichever phase of the subject the reader is interested in. 152 Pages—138 Illustrations—\$2.00.

## THE OSCILLATOR AT WORK

Shows how various oscillator circuits function and methods to improve their performance. Also describes the r-f and a-f oscillators used as signal sources. Covers laboratory test methods, and other related tests. 256 Pages—167 Illustrations—\$2.50.

## SERVICING RECEIVERS BY MEANS OF RESISTANCE MEASUREMENT

Discusses series and parallel combinations of resistances and the distribution of currents and voltages, providing the basis underlying the circuit arrangements used in various types of radio receivers. Also discusses application of resistance measurement to radio servicing. 203 Pages—94 Illustrations—\$2.00.

## AUTOMATIC FREQUENCY CONTROL SYSTEMS

The basic operation of the discriminator and Automatic Frequency control circuits is explained in great detail in the first part of the book. Descriptions of systems used in commercial receivers are fully described in the second part. 144 Pages—102 Illustrations—\$1.75.

## ALIGNING PHILCO RECEIVERS

I-F peaks—adjustment frequencies—trimmer and podder locations—complete and detailed information for aligning every Philco model from 1929 to 1941. Covers 7,000,000 Receivers.  
 VOL. I—1929 to 1936—176 Pages ..... \$2.00  
 VOL. II—1937 to 1941—200 Pages ..... 2.00

## RADAR

A non-technical explanation of the operating principles of Radar. 72 Pages—Unique Illustrations—\$1.00.

# JOHN F. RIDER PUBLISHER, INC.

404 FOURTH AVENUE, NEW YORK 16, N. Y.

EXPORT AGENT: ROCKE-INTERNATIONAL CORP., 13 East 40th Street, New York 16, N. Y. Cable ARLAB  
 Publishers Exclusively for the Radio and Electronic Industry

SEND FOR  
 LATEST CATALOG

# SONAR ORIGINATORS OF NBFM



# NBFM

## USING THE EXCLUSIVE SONAR PHASE MODULATION†

32 years of unsurpassed achievements in designing, engineering, manufacturing and mass production of radio equipment. This is the heredity of Sonar Radio Corp., and the development of the exclusive Sonar Phase Modulation circuit, used in all Sonar equipment was the result of this heredity. Being the first to discover the many potentialities of NBFM for ham use (eliminating shock excitation BCI, the most common when using AM) Sonar has put its experience to work, not only in developing the NBFM units but in keeping the price of the product within the range of all.

Sonar has also made it possible for the radio amateur in this expensive post war era, to modulate a KW rig for the same small price that it costs to modulate a 100 watt rig.

Stability is the essence of any ham rig and Sonar has made frequency stability the keynote in their units, making it as excellent as the xtal or VFO used because the phase modulation is completely independent of the oscillator. For vital data on phase modulation versus reactance modulation read page 21 in the July issue of QST, 1947.

Sonar has pioneered the field of NBFM and will continue to do so, announcing their new achievements in their monthly advertisements. For quality, price and craftsmanship to keep your station modern insist and get SONAR — the leader.

## \*NOW ON ALL BANDS

Model is as shown required in USA on frequency band 3600 to 3800 Kc. 14250 to 14255 Kc. 28.5 to 29.7 Mc. 57.0 to 58.0 Mc. in Canada on 27.975 to 27.985 Mc. 27.5 to 27.7 Mc.

Sole Representatives in Canada—Frank's Agencies, Ltd., Toronto.  
Sole Representatives in U.S.A.—Massachusetts Engineering, Ltd., Toronto.

**SEE THEM AT YOUR DEALERS**

SEE  
YOUR  
DEALER  
OR  
WRITE US  
DIRECT



**SONAR**  
*Radio*

SONAR  
RADIO  
CORP  
384465  
MAYN L.  
NEW YORK

**HARROW BAND FM**

# EQUIPMENT FOR THE HAM SONAR

**THE XE-10**, first of the SONAR products, was designed to give the Ham a modulation unit for his complete AM rig. The XE-10 will convert any CW rig (regardless of power) to NBFM. Your VFO can be used to regulate the frequency input to the XE-10 or the xtal can be inserted directly into the XE-10.

**THE VFX 680** was designed to meet the demands for a stable VFO-xtal exciter and also incorporates the exclusive SONAR NBFM circuit giving a complete 4 to 6 watt all band exciter, with NBFM phone and/or straight CW. The VFX 680 also has VFX (rubberizes any cut xtal) giving xtal stability with a variable signal. An ideal "pre-stage" for that new rig.

**THE MB-611** is another SONAR product incorporating NBFM, designed for mobile or fixed operation, on 6 to 11 mtrs—40 watts input with a pi-network to match any antenna. Further details on this xmitter and other new SONAR developments will be found in future advertisements. The engineering staff at SONAR has many new designs including low, medium, and high power xmitters.

**THE C.F.C.** Sonar's new Calibrated Frequency Control has a Direct All-Band, calibrated VFO; a finger-tip controlled 5" dial plainly marked for all bands 80, 40, 20, 15, 11, 10; a built-in 1000 kc frequency standard; calibrated against WWV; CW keying and built-in CW monitor with 5 watt output; provisions for remote control, the C.F.C. can be linked to any type xmitter. The C.F.C. is furnished complete with tubes, regulated power supply and a 1000 kc crystal.

**THE SRT 75** is a new complete allband xmitter for NBFM and CW operation. This xmitter will deliver a minimum output of 50 watts to any type antenna or load impedance. The SRT 75 employs the VFX 680 link coupled to the new AMP 50 amplifier which uses a 2E22 in the final. The SRT 75 is designed for table top use as a final or to push the HP final. The AMP 50 and the PS 50 (power supply for AMP 50) are available separately for the present users of the VFX 680 at your dealers








# The New Model 670

# SUPER-METER

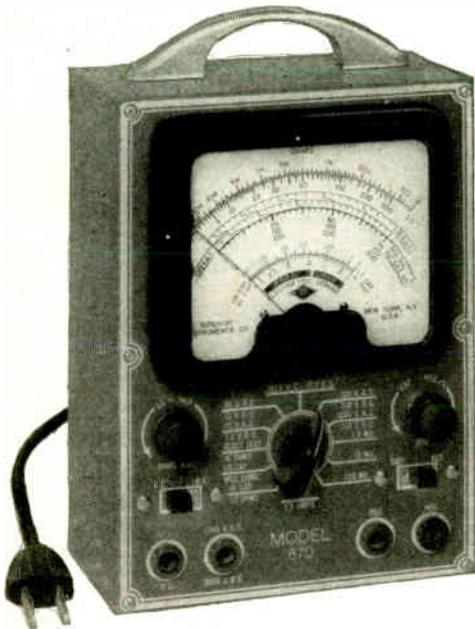

*A Combination*

**VOLT-OHM MILLIAMMETER  
plus CAPACITY REACTANCE  
INDUCTANCE and  
DECIBEL MEASUREMENTS**

*Added Feature*

The Model 670 includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

## *Specifications*

**D.C. VOLTS:** 0 to 7.5/15/75/150/750/1,500/7,500 Volts  
**A.C. VOLTS:** 0 to 15/30/150/300/1,500/3,000 Volts  
**OUTPUT VOLTS:** 0 to 15/30/150/300/1,500/3,000 Volts  
**D.C. CURRENT:** 0 to 1.5/15/150 Ma. 0 to 1.5 Amperes  
**RESISTANCE:** 0 to 500/100,000 ohms 0 to 10 Megohms  
**CAPACITY:** .001 to .2 Mfd. .1 to 4 Mfd. (Quality test for electrolytics)  
**REACTANCE:** 700 to 27,000 Ohms 13,000 Ohms to 3 Megohms  
**INDUCTANCE:** 1.75 to 70 Henries 35 to 8,000 Henries  
**DECIBELS:** -10 to +18 +10 to +38 +30 to +58

*The Model 670 comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 5½" x 7½" x 3".*

**\$ 2840**  
NET

# SUPERIOR INSTRUMENTS CO.

Dept. H \* 227 FULTON STREET \* NEW YORK 7, N. Y.

PLEASE PLACE YOUR ORDER WITH YOUR REGULAR RADIO PARTS JOBBER. IF YOUR JOBBER DOES NOT HANDLE OUR LINE PLEASE SEND YOUR ORDER DIRECT TO US

109

NOW AVAILABLE *for Amateurs*

# STANCOR'S

## ST-202-A *Transmitter Kit*



*Here is a Versatile Transmitter that was Definitely Designed to Please the Amateur*

**L**ISTED at the right are some of the more salient features embodied in the ST-202-A. For complete details see your Stancor distributor or write direct for a descriptive bulletin.

Amateur net price of ST-202-A Complete Transmitter Kit, less accessories . . . \$92<sup>80</sup>

### STANCOR QUALITY TRANSFORMERS

The amateurs' acceptance of Stancor transformers results from the consistent maintenance of high standards of engineering, quality materials and precision manufacturing. Be familiar with our complete line of transformers and reactors by having a Stancor catalog for reference.



SEE YOUR STANCOR DISTRIBUTOR OR WRITE DIRECT FOR A COMPLETE CATALOG

*featuring . . .*

- 100-125 WATTS INPUT TO FINAL AMPLIFIER.
- COVERS ALL AMATEUR BANDS BETWEEN 3.5 AND 30 MCS.
- THREE STAGE R. F. CIRCUIT.
- BAND SWITCHING OF EXCITER STAGES.
- ONLY TWO TUNING CONTROLS (EXCITER AND AMPLIFIER).
- SELECTION OF SIX CRYSTAL POSITIONS.
- ADJUSTABLE LINK OUTPUT CIRCUIT.
- TWO SEPARATE POWER SUPPLIES INCLUDED.
- EASE OF CONSTRUCTION (CABLED WIRING HARNESS SUPPLIED).
- SMALL SIZE — APPROXIMATELY 14" x 13" x 9".
- PROVISIONS FOR USE WITH AM OR FM MODULATOR.
- PRICED RIGHT.

## STANDARD TRANSFORMER CORPORATION

ELSTON, KEDZIE AND ADDISON

CHICAGO 18, ILLINOIS



# HARVEY'S *is ham* headquarters

Sonny got started right. Dad has been a Harvey customer since 1927, though he lives miles from New York. When Sonny got his ticket Dad told him to get his gear from Harvey's because he'd get the best, the quickest service, and friendly help and advice on his problems. Dad knows that Harvey's staff is made up of hams who know the ham's problems and can usually come up with a solution. If you live in or near New York, this friendly service is more direct but it can't be more personal.



## HARVEY'S HIT OF THE MONTH

Watch this space in our QST ad each month. In it you'll find bargains in items you can really use.

## HARVEY'S HAMFESTIVAL OF VALUES

You'll find Harvey's ad each month in QST and in this space you'll see offerings of unusual value in addition to the staples of ham radio. Harvey carries large stocks of components including meters, crystals, transmitting tubes and test equipment along with the complete units including all the popular receivers, transmitters, frequency meters and other things that add up to a complete ham station.

Harvey's reputation for reliability has been growing ever since 1927 and you can be sure of the same prompt, courteous attention if you order by mail, wire, or phone as if you could call and place your order in person. By the way, if you get near Times Square, we're only a block away, so drop in and see us.

W2DIO  
W2FXB  
W2IJJ  
W2KQY  
W2LJA

Telephone:  Longacre 3-1800

**HARVEY**  
RADIO COMPANY INC.

103 West 43rd St., New York 18, N. Y.

Get your name on our mailing list. Send us a postcard or letter, stating whether you are amateur, serviceman or engineer. We'll keep you posted on merchandise available, new equipment and special Harvey bargains.


**LARGE**

or

**SMALL**

**SOLAR CAPACITORS TYPIFY**

**"QUALITY ABOVE ALL"**

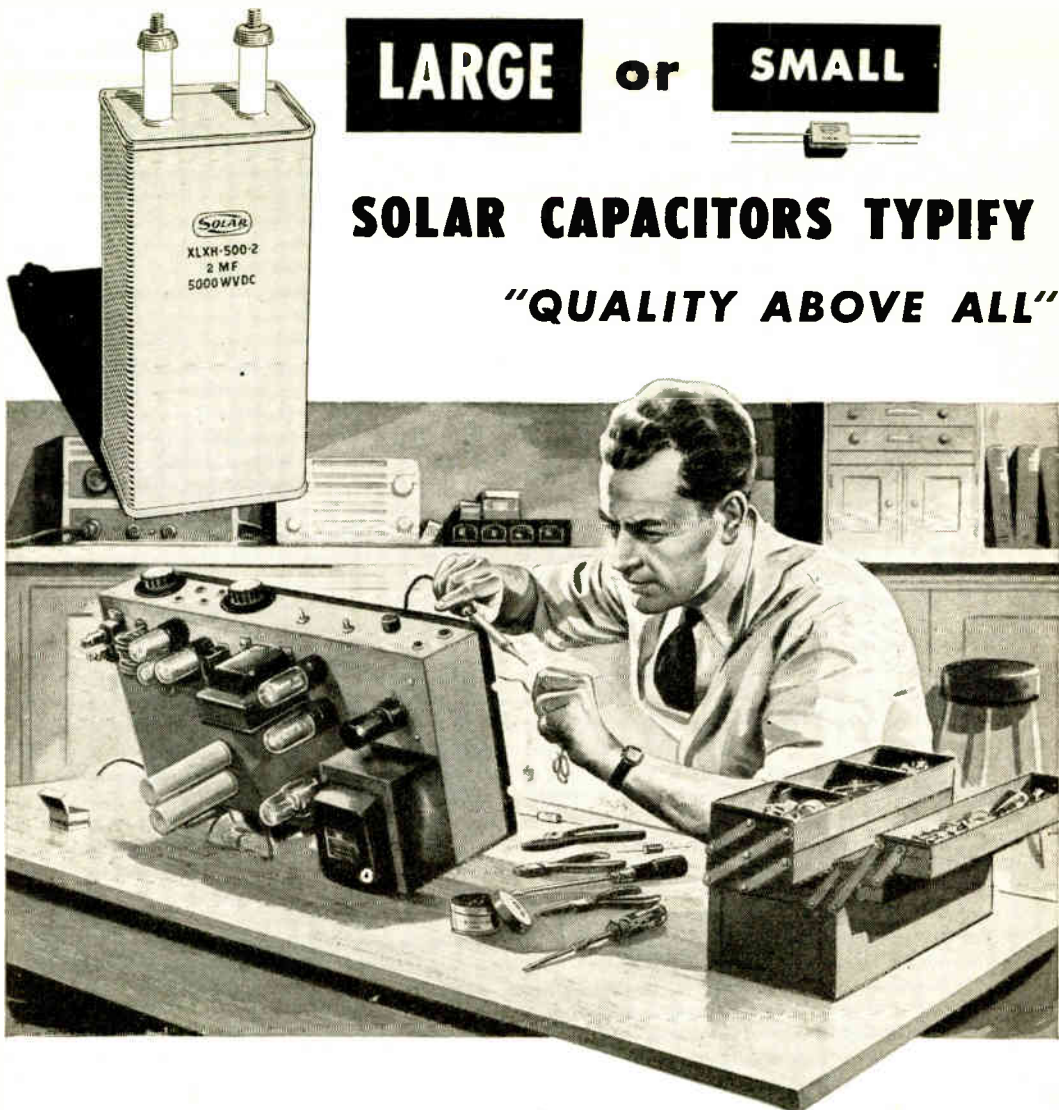

Whether you need mica, paper or electrolytic capacitors  
for the rig you're building or for replacement in present  
equipment, Solar's complete line is tops to choose from.

Built to rigid specifications, and to stand-up under  
the most severe service and operating conditions,  
Solar capacitors are the obvious choice for dependability.

Get the Solar catalog for your shack today.



**CAPACITOR SALES CORP.**

1445 HUDSON BLVD.

• NORTH BERGEN, N. J.



**DEPENDABLY ENGINEERED**

**RADIO HARDWARE  
WIRES AND CABLES**

*Since 1923 — pioneers in the design and manufacture of Wires—Cables —Plastic and Push-back Hook-up Wires—Radio Hardware—Shielded Microphone Cable and S. J. Cable —also Ceramics, Porcelain and Steatite Insulators—Antennas, etc.*

*Specify and use "BIRNBACH" Products — an old, reliable name in the Radio-Electronic Industry. Complete stock at your Dealer.*

**BIRNBACH RADIO CO., Inc.**  
145 HUDSON ST.      NEW YORK, 13, N. Y.



# THE NEWS IS SPREADING FAST!

IT'S WALTER ASHE FOR ALL THE LATEST AND THE BEST IN RADIO AND ELECTRONICS

## ALL THE BIG NAME BRANDS OF AMATEUR SHORT WAVE RECEIVERS and TRANSMITTERS

Choose your favorite new receiver, transmitter or related apparatus from Walter Ashe's ample and varied stocks. Prices are right. Deliveries are prompt.

## "SURPRISE" TRADE-IN ALLOWANCES . . .

Your receiver may be worth far more than you think! Yes, the "Surprise" trade-in allowances offered by Walter Ashe on your used equipment are truly the sensation of the industry. Act now. Get your trade-in deal working today. Simply write wire or phone us what you have to trade. We'll take it from there.

SEE WALTER ASHE BEFORE YOU MAKE THAT TRADE!

## "Ahead of the Parade" . . . SERVICE . . . FACILITIES . . . VALUES.

Walter Ashe Radio Co. has long been recognized as the reliable source for a complete line of dependable radio and electronics equipment for every conceivable purpose. Amateurs in this country and abroad have learned to depend on Walter Ashe for prompt and efficient handling of their every requirement.

## A COMPLETE STOCK OF UP-TO-THE-MINUTE EQUIPMENT and COMPONENT PARTS

Our really complete stock of parts is our pride and joy. However, you'll never find us making wild unfounded claims that we stock every last part that was ever manufactured. Long ago we cast out obsolete items to make way for the kind of merchandise your orders indicate you want. Of this you can be sure . . . if you see the item in our catalog you'll find it in our stock. And that's a promise.

### HASH IT OVER WITH ASHE

Perplexed about what power or modulation transformer to use . . . what bleeder resistor you need? Hash over your problems with Walter Ashe. Your fellow amateurs here have been carefully trained and are thoroughly qualified to assist you. You can send your order right on in to us with full assurance that sound judgment born of our 25 years' experience will provide the practical solution.

INTERNATIONAL DISTRIBUTORS OF A COMPLETE LINE OF HAM GEAR . . . TEST EQUIPMENT . . . COMPONENTS . . . SUPPLIES

Established 1922

*Coming!*

A new, bigger, better Walter Ashe Catalog will be available soon! For priority delivery of your free copy get your name on our mailing list now.

REMEMBER . . . Your Trade-In's Worth More at The Walter Ashe Store

WØJWD • WØULH • WØWTM • W9NRF • WØIYD • WØPGI • WØQDF

**Walter Ashe** RADIO CO.  
1125 PINE ST. • ST. LOUIS, MO.

THE FAVORITE KEY OF GOOD OPERATORS THE WORLD OVER

THE EASIEST WAY  
OF SENDING  
EVER DEvised


GENUINE EASY-WORKING

# VIBROPLEX


Reg. Trade Marks: Vibroplex, Lightning Bug, Bug

**"ORIGINAL"  
DELUXE MODEL  
WITH PATENTED  
JEWEL MOVEMENT**

Represents the greatest improvement in keys since the advent of the BUG type key. Eliminates tiresome hand-sending. Transmits strong, clear signals at all speeds. Beautifully built. Polished chromium parts and base. DIE CUT contacts and main spring, JEWEL movement. Colorful red switch knob, finger and thumb piece. 3/16th contacts. Circuit closer, cord and wedge. \$19.50. Standard finish with polished chromium parts and black base, \$15.95.

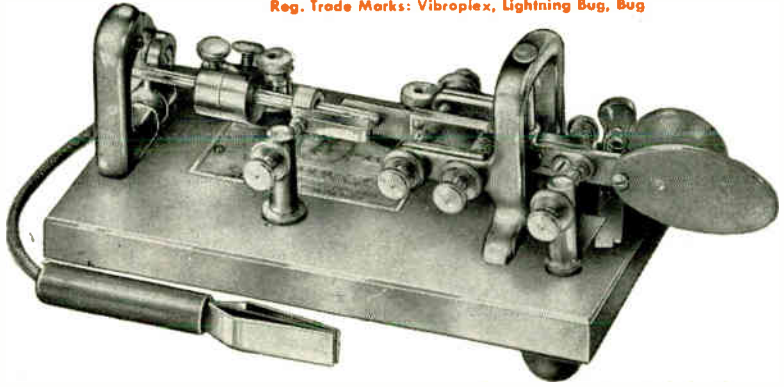

VIBROPLEX is the favorite key of good operators the world over, because it is best suited to all operating conditions, dependable and so easy to use. These built-in Vibroplex qualities are all-important wherever good sending is essential, and are equally valuable in the development of a good sending 'fist.' No special skill required. No tiresome effort is involved. **SIMPLY PRESS LEVER — VIBROPLEX DOES THE REST.**

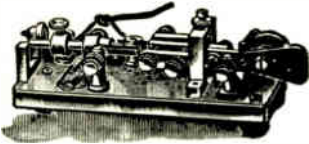

**"BLUE RACER" VIBROPLEX** is a smaller model patterned after the "Original" and with the same sending efficiency for which that key is internationally famous. Standard finish with polished chromium parts and black base, \$15.95. Also available in deluxe finish with the same deluxe features described above, \$19.50.

**"CHAMPION" VIBROPLEX**

is a full size, efficient key for radio use only. Similar to the "Lightning Bug" model and an ideal key for the beginner. Chrome finished parts and black base, \$9.95



Every Vibroplex key is scientifically designed, precision machined and improved in every possible detail. No matter which Vibroplex key you choose you can be assured of the utmost in ease of operation and all around sending satisfaction. Remit by money order or registered mail. **FREE** illustrated catalog.



**"LIGHTNING BUG" VIBROPLEX** has many advanced and exclusive features which add greatly to its sending efficiency and ease of operation. Widely used on land, sea and in the air. Standard finish with polished chromium parts and black base, \$13.95. Also available in deluxe finish with the same deluxe features as the "Original" model, \$17.50.

**VIBROPLEX CARRYING CASE**

Plush-lined, finished in handsome simulated black morocco. Reinforced corners. Flexible leather handle. Lock and key. Protects key from dust, dirt and moisture. Insures safe keeping when not in use. \$5.50.



The "BUG" Trade Mark identifies the Genuine Vibroplex key.



It's your guaranty of complete satisfaction. Accept no substitute.

**THE VIBROPLEX CO., Inc.**

833 Broadway • New York 3, N. Y.

W. W. Albright, President

# ESICO

REG. U. S. PAT. OFF.

## THERE ARE THREE GRADES OF IRONS

### GREEN LABEL

For intermittent duty use. Fill all of the requirements of the amateur and the home craftsman.

No. 415.....List \$1.95



3/8" tip 55 watts

No. 416.....List \$2.95



1/4" tip 60 watts

No. 417.....List \$3.95



3/8" tip 100 watts

No. 418.....List \$4.95



1/2" tip 130 watts

### Thermostatic temperature control stand



No. 5 to 1" dia. tip.

No. 6 to 1 3/4" dia.

List price \$6.50

### ORANGE LABEL

For the professional mechanic. For light or heavy soldering where an iron must withstand operation for eight hour periods or more, on frequent occasions.

No. 62.....List \$3.95



1/4" tip 60 watts

No. 63.....List \$4.95



3/8" tip 100 watts

No. 64.....List \$5.95



1/2" tip 130 watts

No. 65.....List \$6.95



5/8" tip 200 watts

No. 67.....List \$7.95



7/8" tip 300 watts

No. 69.....List \$8.95



1 1/8" tip 500 watts

### RED LABEL

For production line continuous operation. These irons are of the most rugged construction.

No. 38.....List \$5.95



3/8" tip 100 watts

No. 58.....List \$7.95



5/8" tip 200 watts

No. 78.....List \$8.95



7/8" tip 300 watts

No. 98.....List \$9.95



1 1/8" tip 550 watts

### SOLDER POTS



No. 12—1 1/2" D.....\$4.50

No. 36—2 1/2" D.....\$5.50

No. 60—3 1/2" D.....\$6.50

## ELECTRIC SOLDERING IRON CO., INC.



# UNIVERSAL MICROPHONES

ready to help you pin the meter!

As America's oldest independent manufacturer of microphones, the Universal Microphone Company has always been at the service of radio amateurs everywhere. You

were our first customers "away back when," and we are ready, now and in the future, to help you make your rig pin the meter with a Universal Microphone!



## NEW D20 SERIES DYNAMIC MICROPHONES

This postwar model is especially suited for recording, public address, transmitters, or wherever a full-ranged dynamic microphone is desired. It combines modern appearance and rugged stability. The built-in cable connection is easily accessible without interference with the microphone, and "stand and cord" noises are minimized because the internal element is mechanically isolated. The D20 Dynamic Microphone is designed for indoor and outdoor use with a frequency range of 50 to 8000 cycles. Its special "Micro-Adjust Swivel" assures smooth, easy adjustment and steady, positive positioning anywhere throughout a 60° angle. Finished in satin chrome. Complete with 25' low loss cable and detachable connector. Available in models of 50, 200, 500, and 40,000 Ohms. An exceptional value at only \$32.50.

## A HOME RECORDING HEAD OF PROFESSIONAL QUALITY!

Universal's design and engineering skill, long experienced in the manufacture of precision studio recorders, has produced this superior home recording head. It outperforms similar recording heads of magnetic design since it purposely accentuates the high frequency range in amount and degree to compensate for high frequency losses common to home recording records and phonograph circuits. This assures a "sparkling" tone quality. Its sensitivity and impedance are keyed to match standard home recorders, thus eliminating special adjustments. Finished in deep brown enamel. Complete with solder terminals, spring tempered phosphor bronze knife edge, steel attachment plate, mounting screws and long styli set screw. Only \$11.50.



A132 RECORDING HEAD



## "KD" DYNAMIC MICROPHONE

This popular low-cost microphone now is available in a new and improved design. Excellent for home recording, amateur applications. Complete with 10 ft. rubber covered cable. Impedance 40,000 Ohms. Only \$17.75.

## D61 CONSTANT VELOCITY FREQUENCY RECORD

Here's a handy tool for direct checking of response characteristics of phonograph pick-ups. Also for indirect checking of recording heads,



loud speakers, loud speaker installations, theater sound equipment, public address equipment and audio frequency equipment. Complete with data sheet. Only \$3.00 each.

OTHER UNIVERSAL MODELS ARE AVAILABLE, including dynamic, velocity, and carbon in standard, hand, communications and cartridge types. For a complete catalog on these as well as Universal Recording Components, see your radio parts distributor or write direct to us.

YOUR LOCAL RADIO PARTS DISTRIBUTOR CARRIES UNIVERSAL PRODUCTS



## UNIVERSAL MICROPHONE CO.

Inglewood, California



**MAKE THE MOST OF YOUR *Station Power***


**VOLT-OHM-MILLIAMMETER  
MODEL 666-HH**

A precision-made marvel of compactness that provides a complete miniature laboratory for voltage, resistance, and direct current analyses.

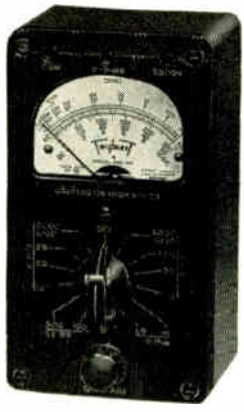**RANGES**


- D.C. Volts: 0-10-50-250-1000-5000 at 1000 ohms-Volt.
- A.C. Volts: 0-10-50-250-1000-5000 at 1000 ohms-Volt.
- D.C. Milliamperes: 0-10-100-500 at 250 Millivolts.
- OHMS: 0-2000-400,000.

In a new, streamlined milled case, completely insulated, Model 666-HH is the tester of a thousand uses.



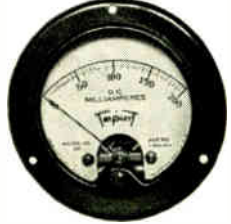**A COMPLETE LINE OF METERS**

Triplet panel and portable meters are available in more than 26 case styles—round, square, and fan—2" to 7" sizes. Included are voltmeters, ammeters, milliammeters, millivoltmeters, microammeters, thermammeters, DB meters, VU meters and electrodynamometer type instruments.



**... WITH MODEL 3296**

With Model 3296 you can modulate to the fullest, for top power output, yet you know at once when you are over-modulating. Four separate circuits measure amplitude modulation—(1) percent modulation, average; (2) peak flash percent modulation; (3) carrier shift; and (4) audio output for headphones. These may be used separately, all at once, or in any combination. Peak indicator can be pre-set for any percent of modulation from 20 to 120, to flash when pre-determined modulation is reached.



**ABSORPTION FREQUENCY  
METER • Model 3256**

A band-switching, tuned absorption type frequency meter that covers five amateur bands. Has new germanium crystal and a DC Milliammeter indicator for greater sensitivity. Direct calibration on panel—no coils to change. Switching permits instantaneous band change. Audio jack provides for monitoring of phone signals—another new feature. Fully shielded. Calibration is in megacycles in following bands: 3.5-4 MC; 7-7.3 MC; 14-14.4 MC; 20-21.5 MC; 28-30 MC.



Address all inquiries to Dept. AHB47

**ELECTRICAL INSTRUMENT COMPANY  
BLUFFTON, OHIO**

**Triplet**

# TURN TO MICROPHONES BY TURNER

## for SOUND PERFORMANCE

### FAMOUS TURNER 22X—

Engineered for smooth response to both voice and music pickups. Output sharp and clear. **22X Crystal** has built-in wind-gag permitting outdoor operation. Crystal protected against humidity and changes in barometric pressure. Level: 52db below 1 volt/dyne/sq.cm. Response:  $\pm 5$ db from 50-9000 c.p.s. **22D Dynamic** has high level dynamic circuit. Dependable indoors or out. Level: 54db below 1 volt/dyne/sq.cm. at high impedance. Response:  $\pm 5$ db from 50-9000 c.p.s. Available in 50, 200, 500 ohms or high impedance. 22X and 22D are equipped with 90° tilting head and 7 ft. removable cable set. Satin chrome finish.

Models 22X, 22D, 33X, 33D, and 20X available with slide, on-off switch at extra cost



### MODEL 211 Dynamic

The ultimate in dynamic microphone performance. Engineered for highest quality recording, public address, sound system and amateur work. Utilizes new type magnet structure and acoustic network. Specially designed diaphragm results in unusually low harmonic and phase distortion. High effective output level: 54db below 1 volt/dyne/sq.cm. at high impedance. Response:  $\pm 5$ db from 30-10,000 c.p.s. Available in all standard impedances with 90° tilting head and 20 ft. 2-conductor removable cable set.



### TURNER 99 Dynamic

The most rugged microphone in the entire Turner line. Engineered and built for the discriminating user who wants top efficiency and dependability. Withstands severest climate and temperature changes. Semi- or non-directional operation. Professional gun-metal finish. Level: 52 db below 1 volt/dyne/sq.cm. at high impedance. Response:  $\pm 5$ db from 40-9000 c.p.s. In 50, 200, 500 ohms, or high impedance. Complete with 20 ft. removable cable set. Also available as model 999 with Balanced Line features for critical applications.



### Rugged TURNER 33X—33D

An all-purpose unit combining high output with smooth response over a wide frequency range. Full satin chrome finished case adds distinction to any rig. Equipped with 90° tilting head and 20 ft. removable cable set. **33X Crystal** has high quality humidity protected crystal. Level: 52db below 1 volt/dyne/sq.cm. Response:  $\pm 5$ db from 50-9000 c.p.s. **33D Dynamic** has heavy duty dynamic cartridge. Takes rougher handling and bad climatic conditions. Level: 54db below 1 volt/dyne/sq.cm. at high impedance. Response:  $\pm 5$ db from 30-9000 c.p.s. Available in 50, 200, 500 ohms, or high impedance.



### MODEL VT-73

CRYSTAL DESK MICROPHONE. A world wide favorite with amateurs for crisp clear reports. Highest quality moisture sealed crystal is used in a specially engineered circuit. Rising curvature of response between 500-4000 c.p.s. increases intelligibility at effective voice frequencies without over-modulation. Head is adjustable through 60°. Finished in rich black crinkle and chrome. Complete with ball swivel head, stand, and 7 ft. attached cable. Level: 52db below 1 volt/dyne/sq.cm. Response:  $\pm 5$ db from 50-7000 c.p.s.



### NEW MODEL 20X Crystal Hand Mike

High in performance, low in cost—this new hand microphone offers unusual response characteristics. The Turner 20X features a Metalseal crystal which withstands humidity conditions not tolerated by the ordinary crystal. Circuit design results in high effective output and ideal response for amateur communications. Light in weight—natural to hold and use. Finished in rich baked brown enamel. Level: 54db below 1 volt/dyne/sq.cm. Response:  $\pm 5$ db from 50-7000 c.p.s.



Licensed under U. S. patents of the American Telephone and Telegraph Company, and Western Electric Company Incorporated. Crystals licensed under patents of the Brush Development Co.

**THE TURNER CO.**  
CEDAR RAPIDS, IOWA


Write for Complete Catalog

# CQ

means

*Commercial  
Quality*

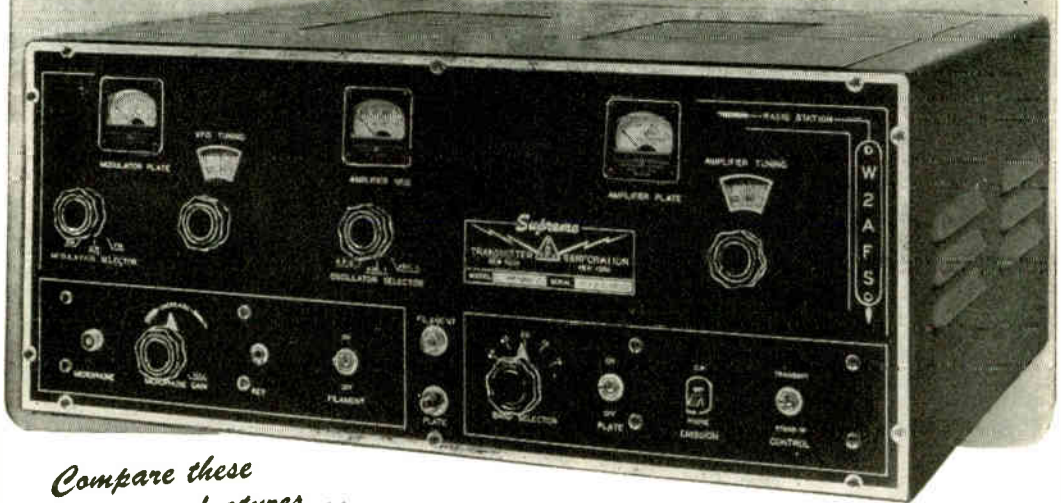in the *Supreme* Model AF-100  
Transmitter



*Compare these  
features...*

Simplest "rig" to install and operate. Efficient with either balanced or unbalanced transmission line of 50 to 600 ohm characteristic surge impedance.

Highly stable Variable Frequency Oscillator followed by slug-tuned buffer and doubler stages ganged to oscillator dial. Simplifies working through severe QRM. Readily establishes and holds QSOs.

A six-band job — 10, 11, 15, 20, 40 and 80 meters, for CW, ICW, AM and FM Phone.

Narrow, medium or wide-band FM transmission obtained by adjusting same volume control that controls level for amplitude modulation!

Because of ICW feature, it maintains OSOs under severest conditions of QRM and QRN! Peak power for ICW approximately four times average carrier level ICW output fully 200 watts!

Each AF-100 subjected to four-hour locked key square-wave 100% modulated heat run before leaving plant. Same life test as for U. S. Signal Corp. equipment!

Complete with all tubes and coils, \$550.00.



**This six-band 100-watt desk-type transmitter is one of the most versatile "ham rigs" yet offered. Embodies everything the "ham" has sought and longed for. Also, it's the first transmitter offered to amateurs which has the very latest feature of Frequency Modulation in the 80, 20, 11 and 10 meter bands. Continuously tunable throughout each amateur band! Definitely, it's built for the present and the future.**

**Typically "Supreme", embodying superlative engineering and craftsmanship which are also available in AF and FM broadcast, in television, in police, marine, aircraft, remote-relay and other types of Supreme commercial quality transmitters.**

**★ Specify "Supreme!"** Whatever you want — "ham" or "professional", insist on a "Supreme" job. Standard types available for many functions. Unusual needs met with special designs and built-to-order equipment. Let us quote on your requirements.



## *Supreme*

### TRANSMITTER CORPORATION

Manufacturers of Communications Equipment  
280 Ninth Avenue • New York City 1, N. Y. • Wisconsin 7-6413  
Export Division: The Radelma Company, 53 Park Place, N. Y. C.

# COMPLETELY STOCKED

TO SUPPLY • HAMS • SERVICEMEN • ENGINEERS



NATIONAL HRO-7



NATIONAL NC 173



SONAR CFC



RME VHF 152A



RME DB 22 R



MILLEN R-9cr

15 YEARS OF UNPARALLELED SERVICE TO THE INDIVIDUAL RADIOMAN. PARTS SUPPLIES INFORMATION, OUR HAM DEPARTMENT IS EVER READY TO SERVE YOU PROMPTLY, COMPLETELY, COURTEOUSLY, WITH ANY OF THE FOLLOWING.

- |                   |                |
|-------------------|----------------|
| ADVANCE           | MALLORY        |
| AEROVOX           | MARION         |
| ALTEC-LANSING     | MEISSNER       |
| AMPHENOL          | MILLEN         |
| ASTATIC           | MILLER         |
| ATR               | MUELLER        |
| B & W             | NATIONAL       |
| BIRNBACH          | OHMITE         |
| BLILEY            | PRECISION      |
| BROWNING          | PREMAX         |
| BRUSH             | RADIART        |
| BUD               | RCA            |
| BURGESS           | RME            |
| CARDWELL          | SANGAMO        |
| CINAUDAGRAPH      | SHURE          |
| CORNELL-DUBILIER  | SIMPSON        |
| DRAKE             | SONAR          |
| DUMONT            | STANCOR        |
| EIMAC             | SPEED-X        |
| ELECTRO VOICE     | SUPREME        |
| HALLICRAFTERS     | TAYLOR         |
| HAMMARLUND        | THORDARSON     |
| HEINTZ & KAUFMANN | TRIMM          |
| HYTRON            | TRIPLETT       |
| ICA               | TURNER         |
| IRC               | UNITED ELECT.  |
| JACKSON           | UTC            |
| JENSON            | UTAH           |
| JOHNSON           | VIBROPLEX      |
| JONES             | WARD-LEONARD   |
| KENYON            | WORKSHOP ASSO. |



HAMMARLUND HQ 129X



HAMMARLUND FOUR 20



NATIONAL NC 2-40D



NATIONAL NC 46



SONAR VFX 680



MILLEN HF XMTR.

W2JRF W2MEI W2MY Y W2PBM

VISIT THEM  
AT

WRITE FOR OUR LIBERAL  
TRADE-IN ALLOWANCE  
AND EASY PAYMENT PLAN

MAIL ORDERS  
FILLED IN  
FOUR HOURS

# ARROW ELECTRONICS, INC.

HAM DEPT., 82 CORTLANDT ST., N.Y. 7, N.Y.



Learn how you can cut costs at every step with Merit Transformers. Built specifically to meet your needs for practical as well as technical engineering. You can depend on top quality in every Merit product. Ask your dealer.

New complete catalogs will be available early in 1948. Send this coupon now to reserve your free copy.

*Mail  
Coupon!*



## MERIT COIL & TRANSFORMER CORP.

TELEPHONE

4427 North Clark St. Long Beach 6311 CHICAGO 40, ILL.

Please reserve my free copy of the  
MERIT 1948 CATALOG.

Name .....

Address .....



# WORKSHOP BROAD-BAND ANTENNAS and ACCESSORY EQUIPMENT

Available at Your Dealer

## 2-METER BEAM ANTENNA — Model #146AB

A highly efficient 6-element array with two driven elements. The power gain is 6 (7.8 db.) The antenna is matched to give maximum efficiency when coupled with 50 ohm coaxial line. Price.....\$21.50.

## 6-METER BEAM ANTENNA — Model #52AB

A high-gain, 3-element, directional antenna to be used with Workshop rotating mast equipment. All necessary bolts, connector assembly, and fittings are supplied. Price.....\$9.00.

## 10-METER DIPOLE ANTENNA — Model #29AD

This Workshop antenna is designed to cover the spectrum from 27 mc. to 30 mc. The construction is heavy enough to withstand high winds. Standard low-loss coaxial cable such as RG-8U, RG-11U, and others in this series, is recommended. Price.....\$8.00.

## 10-METER DIPOLE-TO-BEAM CONVERSION KIT — Model #29B

This kit of accessories converts the 10-Meter Dipole Model #29AD to a 3-element 10-meter beam antenna. Price.....\$31.50.

## 10-METER COMPLETE 3-ELEMENT BEAM ANTENNA — Model #29

The elements are made of adjustable duraluminum sleeves which telescope together. Spacing between elements is also adjustable. Designed for strength and durability to withstand high winds and ice. Impedance of 68 ohms matches 72 ohm line. Price.....\$39.50.

## NEW 6-ELEMENT "DUAL-TEN" BEAM ANTENNA—Model #29X

This new "Dual-Ten" is for those who want the ultimate in a high-gain 10-meter beam. It consists of two complete 10-meter beams vertically polarized and spaced one-half wavelength apart.

- Actual power gain of 6 (7.8 db.).
- Rugged 1½" standard pipe used for the supporting structure.
- Can be bolted directly to the Workshop Rotator.
- Broad band characteristics.

Complete "Dual-Ten" Antenna with instructions. Price.....\$100.

## 20-METER 3-ELEMENT BEAM ANTENNA — Model #14

This big 36-foot beam incorporates all of the refinements of design — both electrical and mechanical — which distinguish the other Workshop beams. The large span demands both light weight and rigidity for smooth rotation and the ability to withstand high winds and ice loading. This is provided by two rugged duraluminum 2-inch diameter booms which make up the supporting structure. The elements are carefully designed for a minimum of sag and taper from 1¼" diameter down to ½" diameter. Price.....\$120.

## ANTENNA MAST AND MOUNT — Model #AM

This rugged tubular steel mast is made in two 4-foot sections which, when joined together, provide an overall length of 7½ feet. The complete kit contains all the bolts and brackets necessary for installation. Price.....\$8.25.

## MODEL #AM1

Extra 4-foot sections of mast to heighten Model -AM. Price...\$1.30.

## WORKSHOP ROTATOR


Low loss coaxial line unbroken from transmitter to antenna, eliminates costly, troublesome impedance matching relays, coupling devices, rotating joints, etc. Rotation automatically stops at North so that the breaking or twisting of coax lines is impossible.

- Full 360 rotation at 1 RPM. Reverses instantly from any point.
- Single switch on Indicator controls rotation.
- Sturdy base plate mounted on ball thrust bearing handles 500-pound load with ease. (All other bearings are oil-less.)
- Heavy-duty motor, 110V-AC, with high gear ratio.
- Rotator housed in weathertight aluminum casting, 9" x 9" x 6" — weight, 27 pounds. Price..\$157.50.
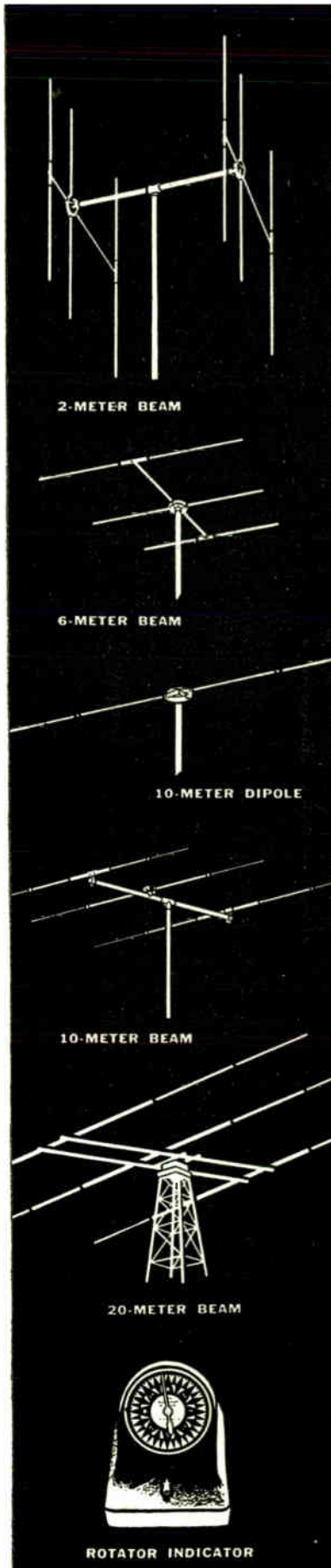
## THE WORKSHOP ASSOCIATES, INC.

Specialists in High Frequency Antennas

66 Needham Street . Newton Highlands 61, Mass.



2-METER BEAM

6-METER BEAM

10-METER DIPOLE

10-METER BEAM

20-METER BEAM

ROTATOR INDICATOR

# Learn Code the EASY Way

*Beginners, Amateurs and Experts alike recommend the INSTRUCTOGRAPH, to learn code and increase speed.*

Learning the INSTRUCTOGRAPH way will give you a decided advantage in qualifying for Amateur or Commercial examinations, and to increase your words per minute to the standard of an expert. The Government uses a machine in giving examinations.

Motor with adjustable speed and spacing of characters on tapes permit a speed range of from 3 to 40 words per minute. A large variety of tapes are available — elementary, words, messages, plain language and coded groups. Also an "Airways" series for those interested in Aviation.

## MAY BE PURCHASED OR RENTED

The INSTRUCTOGRAPH is made in several models to suit your purse and all may be purchased on convenient monthly payments if desired. These machines may also be rented on very reasonable terms and if when renting should you decide to buy the equipment the first three months rental may be applied in full on the purchase price.

## ACQUIRING THE CODE

It is a well-known fact that practice and practice alone constitutes ninety per cent of the entire effort necessary to "Acquire the Code," or, in other words, learn telegraphy either wire or wireless. The Instructograph supplies this ninety per cent. It takes the place of an expert operator in teaching the student. It will send slowly at first, and gradually faster and faster, until one is just naturally copying the fastest sending without conscious effort.

## BOOK OF INSTRUCTIONS

Other than the practice afforded by the Instructograph, all that is required is well directed practice instruction, and that is just what the Instructograph's "Book of Instructions" does. It supplies the remaining ten per cent necessary to acquire the code. It directs one how to practice to the best advantage, and how to take advantage of the few "short cuts" known to experienced operators, that so materially assists in acquiring the code in the quickest possible time. Therefore, the Instructograph, the tapes, and the book of instructions is everything needed to acquire the code as well as it is possible to acquire it.

## MACHINES FOR RENT OR SALE



## The Instructograph

ACCOMPLISHES THESE PURPOSES:

- FIRST:** *It teaches you to receive telegraph symbols, words and messages.*
- SECOND:** *It teaches you to send perfectly.*
- THIRD:** *It increases your speed of sending and receiving after you have learned the code.*

With the Instructograph it is not necessary to impose on your friends. It is always ready and waiting for you. You are also free from Q.R.M. experienced in listening through your receiver. This machine is just as valuable to the licensed amateur for increasing his speed as to the beginner who wishes to obtain his amateur license.

*Postal Card* WILL BRING FULL PARTICULARS IMMEDIATELY

## THE INSTRUCTOGRAPH CO.

4707 SHERIDAN ROAD

CHICAGO 40, ILLINOIS

Representative for Canada—Canadian Marconi Co., P.O. Box 1690, Montreal, Quebec



# Amateurs 'Round the World . . .



Leo, W8GFQ at the new 275 Watt Globe King Kit

## SAVE WITH WRL

**THE NEW WRL 275 WATT XMTR KIT.** A versatile, advanced design transmitter kit that will give you top performance on 6, 10, 20, 40 and 80 meter bands on CW and fone. Has *RF exciter* section capable of 40 watts input on all bands including 6 meters; *RF Final: Speech Amplifier and Modulator* capable of modulating inputs from 300 to 350 watts; and a *Dual Power Supply*. Comes in gray streamlined gray crackle finish steel cabinet, 28 $\frac{3}{4}$ " high x 22" wide x 14 $\frac{3}{4}$ " deep. Send today for complete descriptive literature.

Includes, complete set tubes, meters, coils and cabinet.

KIT FORM	WIRED	AS LOW AS
<b>\$356.45</b>	<b>\$376.45</b>	<b>\$70 DOWN</b>

## WRL EQUIPMENT GUARANTEED OR YOUR MONEY BACK

### A PROVEN 1947 SUCCESS WRL GLOBE TROTTER XMTR KIT

Hams everywhere say it's the hottest transmitter kit on the market. You will, too, once you've used it. It's a 40 watt input kit including all parts, power supplies, chassis, panel and streamlined cabinet. Write for export prices.

**KIT FORM, \$69.95 WIRED, \$79.50** As low as **\$13.99**  
(1 set coils, tubes, meters \$17.15 extra) **DOWN**



### Leo offers you more . . .

Hams all over the world are enjoying our personal service, fast delivery, liberal trade-ins and Easy Payment Plan. We make it easy to buy and easy to pay for equipment you want. If you would like a new transmitter or receiver just write and tell us what you want, the make and model you now have, and I'll answer your inquiry the same day giving you your trade-in allowance. Many times it will serve as a down payment on new gear. Dollar for dollar you will get MORE at WRL. Write me for anything you want. We can fill your needs.

*Sincerely,*  
**Leo & Meyerson**  
W8GFQ

### Get Acquainted Offer

#### GIANT RADIO REFERENCE MAP

Just right for your control room wall. Approximately 4' x 3'. Contains major networks, time zones, amateur zones, leading shortwave stations, standard broadcast stations, monitoring stations, etc.



MAIL COUPON TODAY and 25¢



## NO RED TAPE — WE FINANCE OUR OWN PAPER. USE LEO'S EASY PAY PLAN

Item	Liberal Trade-ins	
	Cash Price	Down Payment
Halicrafters S38	\$ 47.50	\$ 9.50
Halicrafters S40A	85.50	17.90
Halicrafters SP44	49.50	9.90
Halicrafters SX42	275.00	55.00
Halicrafters SX43	169.50	33.90
Halicrafters HT-17 Transmitter	79.50	15.90
Halicrafters HT-18 Transmitter and ECO	110.00	22.00
Halicrafters HT-9 Transmitter	350.00	70.00
RME VH-F-152	86.60	17.35
RME DB-22 Presolector	66.00	13.20
RME-84	98.70	19.74
RME-45	198.70	39.74
RME HF 10-20 Converter	77.00	15.40
Hammarlund HQ 129X with speaker	189.15	37.83
Hammarlund SPC400X with speaker	398.25	79.65
Stancor ST-282A Transmitter Kit	92.80	18.56
New National NC-57	85.50	17.90
National NC46	97.50	19.50
National 1-10A	67.50	13.50
National NC173	179.50	35.90
National NC240FT or NC240D R	225.00	45.00
National HRO-7 Complete	311.36	62.27
National NC183 with speaker	269.00	53.80
Gen-Set Converters	39.95	7.99
Collins 70E-8	40.00	8.00
Bud VFO-21	52.50	10.50
Meissner Signal Shifter	99.50	19.90
New Micro-Match Unit	29.50	5.90
Millen R-9er	24.75	4.95
BB-27 10 meter converter F.B. for 348	27.50	5.50
Sonar Mobile MB-611 transmitter	72.45	14.49
WRL exciter unit wired	23.95	4.79
Millen 90800 exciter	42.50	8.50
Sonar XE-10 transmitter	39.45	7.89
Sonar VFX-680	87.45	17.49
Workshop 28 megacycle beam 3 element	39.50	7.90
Workshop 26 element 28 megacycle type	100.00	20.00
Workshop 20 meter beam 3 element	120.00	24.00
Gordon Rotary Beam	225.00	45.00
Direct-O-Beam	117.00	23.40
New Beach ECO	32.50	7.50

**FREE**

**WORLD RADIO LABORATORIES**  
Department H48  
44 West Broadway  
Council Bluffs, Iowa

Send Latest FREE Flyer  
 Send data on WRL 275 Watt Xmt'r  
 Send more data on Globe Trotter  
Here's 25¢. Send Map at once

Send more data on \_\_\_\_\_

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Call Letters \_\_\_\_\_  
Zone \_\_\_\_\_ State \_\_\_\_\_

**AUDELS REFRIGERATION & AIR CONDITIONING GUIDE.....\$4**

New from Cover to Cover—1280 Pages, Fully Illus. Covering basic principles, servicing, operation & repair of household, commercial & industrial refrigeration & air conditioning. A gold mine of essential important facts for engineers, servicemen, users.

**AUDELS CARPENTERS & BUILDERS GUIDES—4 Vols. .... \$6**

A practical illustrated trade assistant on modern construction for carpenters, joiners, builders, mechanics and all woodworkers. 4 vols., 1600 pages, 3700 illustrations, flexible covers. Pocket size. Each volume sold separately \$1.50 a vol.

**AUDELS AUTOMOBILE GUIDE.....\$4**

A practical quick ready reference book for auto mechanics, service men, operators & owners. Explains theory, construction & servicing of modern motor cars, trucks, buses & auto type Diesel engines. 1700 pages, fully illustrated. 55 chapters. Indexed. A standard book for mechanics. New fluid drive covered.

**AUDELS DIESEL ENGINE MANUAL..\$2**

A practical, concise treatise with questions and answers on the theory, operation and maintenance of modern diesel engines including General Motors 2 cycle Diesels, 633 pages, fully illus., flexible binding, pocket size. All details plainly brought out, this book is of extreme value to engineers, operators & students.

**AUDELS WIRING DIAGRAMS.....\$1**

210 Pages. Illustrated. Gives practical facts on wiring of electrical apparatus. It shows clearly how to wire apparatus for practically all fields of electricity. Each diagram is complete & self-explanatory. Highly Endorsed Pocket Companion.

**AUDELS PLUMBERS & STEAMFITTERS GUIDES—4 Vols. .... \$6**

A Practical Trade Assistant & Ready Reference. Explains in plain language & by clear illustrations, diagrams, charts, graphs, pictures principles of modern plumbing practice including Marine Pipe Fitting and Air Conditioning. 4 Vols.—1670 Pages—3642 Diagrams. Pocket size. Each Vol. Sold Separately \$1.50 a Vol.

**AUDELS SHEETMETAL WORKERS HANDY BOOK.....\$1**

Practical inside information. Fundamentals of Sheet Metal Work. 388 pages. Illustrated. 21 sections. Clear writing. Essential & important facts, figures, pointers in everyday language. Ref. Index.

**AUDELS SHEETMETAL PATTERN LAYOUTS.....\$4**

Developed by Experts for Sheet Metal Workers, Layout Men & Mechanics. A Practical Encyclopedia in 10 Sections, size 7 x 10 x 2—1125 Pages—350 Layouts—1600 Illustrations. 1001 Key Facts. Fully indexed for ready reference in answering your layout problems. Covers all phases of sheet metal work including Pattern Cutting, Pattern Development & Shop Procedure.

**AUDELS ANSWERS ON BLUE PRINT READING.....\$2**

For Mechanics & Builders. Covers all types of blue print reading including ship & airplane. 416 pages, fully illustrated.

**AUDELS NEW MACHINIST & TOOLMAKERS HANDY BOOK.....\$4**

Covers modern machine shop practice in all its branches. 5 practical books in 1. New from cover to cover. Tells how to set up & operate lathes, screw and milling machines, shapers, drill presses and all other machine tools. 1600 pages, fully illustrated, 5 x 6 1/2 x 2. Indexed. 5 sections. 1—Modern Machine Shop Practice. 2—Blue Print Reading & How to Draw. 3—Calculations & Mathematics for Machinists. 4—Shop Physics. 5—How to Use the Slide Rule. 60 chapters. Easy to read and understand. A shop companion that answers your questions.

**AUDELS MATHEMATICS & CALCULATIONS FOR MECHANICS \$2**

Mathematics for home study or reference. 700 pages, 550 illus. Practical mathematics from beginning. How to figure correctly. Easy, correct methods covering complete review. Illus. & Indexed.

**AUDELS HANDY BOOK OF PRACTICAL ELECTRICITY.....\$4**

For maintenance engineers, electricians & all electrical workers. 1440 Pages, 2600 Illus. Covers important electrical information in handy form—including Marine Wiring, Radio Principles, Welding. Indexed. A Key to a practical understanding of electricity.

**AUDELS RADIOMANS GUIDE.....\$4**

A key to the practical understanding of radio including Frequency Modulation, Television, etc. Aircraft & Marine Radio. For radio engineers, servicemen, amateurs. 914 Pages, 633 Illustrations & Diagrams. Photos. Review Questions & Answers, Reference Index. Authentic, clear, concise.


**AUDELS ELECTRONIC DEVICES.....\$2**

Tells What You Want to Know About Electric Eye. Easily Understood. Covers photo-electric cells & their applications. Amplifiers, illumination, frequencies, voltage, photocells, tubes, Ohm's Law, wiring diagrams, etc.

**AUDELS WELDERS GUIDE.....\$1**

A concise, practical text on operation & maintenance of all welding machines for all mechanics. Over 400 pages, illustrated. Covers all methods of electric and acetylene welding including airplane work.

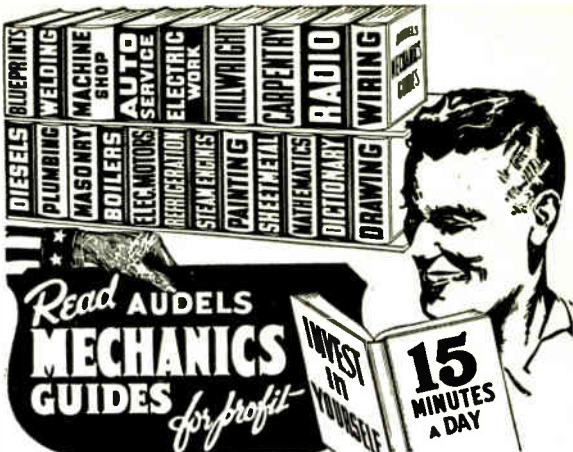**AUDEL, Publishers, 49 W. 23 St., N. Y. 10**



**AN AUDEL GUIDE IS A GOOD FRIEND!**

Step Up Your Own Skill with the Practical Facts and Figures of Your Trade. Save time and money with right methods, short cuts, labor saving ideas. CHECK NOW! You can look over any Audel Guide in your home. Start the Easy Payments if satisfied.

**CUT HERE MAIL ORDER**

**THEO. AUDEL & CO., 49 W. 23 St., New York 10, N. Y.**

Please mail me for 7 days' free examination the books marked (X) below. I agree to mail \$1 in 7 days on each book or set ordered, and to further mail \$1 a month on each book or set ordered until I have paid purchase price.

If I am not satisfied with Guides I will return them.

- Audels ELECTRIC MOTOR GUIDE . . . . . \$4.
- Audels OIL BURNER GUIDE . . . . . 1.
- Audels REFRIGERATION & Air Conditioning Guide . . . . . 4.
- Audels POWER PLANT ENGINEERS GUIDE . . . . . 4.
- Audels PUMPS, HYDRAULICS & AIR COMPRESSORS 4.
- Audels WELDERS GUIDE . . . . . 1.
- Audels BLUE PRINT READING . . . . . 2.
- Audels SHEET METAL WORKERS Handy Book . . . . . 1.
- Audels SHEET METAL PATTERN LAYOUTS . . . . . 4.
- Audels AIRCRAFT WORKER . . . . . 1.
- Audels MATHEMATICS AND CALCULATIONS . . . . . 2.
- Audels MACHINISTS & TOOLMAKERS Handy Book 4.
- Audels MECHANICAL Dictionary . . . . . 4.
- Audels AUTOMOBILE GUIDE . . . . . 4.
- Audels DIESEL ENGINE MANUAL . . . . . 2.
- Audels MARINE ENGINEERS Handy Book . . . . . 4.
- Audels MECHANICAL DRAWING GUIDE . . . . . 1.
- Rogers MECHANICAL DRAWING and DESIGN . . . . . 2.
- Audels MILLWRIGHTS and Mechanics Guide . . . . . 4.
- Audels CARPENTERS and Builders Guides (4 vols.) . . . . . 6.
- Audels PLUMBERS and Steamfitters Guides (4 vols.) . . . . . 6.
- Audels MASONS and Builders Guides (4 vols.) . . . . . 6.
- Master PAINTER and DECORATOR . . . . . 2.
- Audels GARDENERS & GROWERS GUIDES (4 vols.) . . . . . 6.
- Audels ENGINEERS & FIREMANS EXAMINATIONS 1.
- Audels ENGINEERS and Mechanics Guides . . . . . 12.
- Nos. 1, 2, 3, 4, 5, 6, 7 and 8 complete . . . . . 12.
- Audels Answers on Practical ENGINEERING . . . . . 1.
- Audels ELECTRICIANS EXAMINATIONS . . . . . 1.
- Audels WIRING DIAGRAMS . . . . . 1.
- Audels Handy Book of PRACTICAL ELECTRICITY . . . . . 4.
- Audels ELECTRICAL POWER CALCULATIONS . . . . . 2.
- Audels ELECTRONIC DEVICES . . . . . 2.
- Audels ELECTRIC Dictionary . . . . . 2.
- Audels RADIOMANS GUIDE . . . . . 4.
- Audels NEW ELECTRIC LIBRARY at \$1.50 a Volume . . . . . 4.

Name.....  
 Address.....  
 Occupation.....  
 Employed by..... Q.S.T.

# USEFUL BOOKS

*Basic essentials for license exams; for reference by technicians, operators, servicemen; for apprentice training.*

## Introduction to Practical Radio

*By D. J. Tucker. 322 pp. 160 ill. \$3*

Based on extensive practical and teaching experience, this book explains in the clearest, most practical terms *everything* the beginner needs to know about the theory, construction and operation of radio apparatus. The necessary math is reviewed at the points where it is used. The author is owner and operator of W5VU (since 1921), and Chief Engineer of WRR, KVP, KVPA, Dallas.

## Principles of Radio for Operators

*By Ralph Atherton. 344 pp. 470 ill. \$4*

Using methods found so successful in training radio personnel for war service, this book teaches the operating principles of each radio part, including antennas. Hundreds of illustrations, simple graphic explanations, demonstrations make learning easy. Much useful reference information in the appendix.

## Shop Job Sheets in Radio

*By R. N. Auble*

**Bk. 1—Fundamentals \$1.90**

**Bk. 2—Service Problems \$1.90**

In these workbooks large, clear working drawings accompanied by worksheets provide practice in wiring and connections, use of measuring instruments, operation of basic parts, and construction of power supplies, amplifiers, the superheterodyne receiver and transmitters. In each "job" the objective is clearly stated, the fundamental theory outlined, and the job itself developed in a practical what-to-do manner. Excellent for vocational and apprentice training.

**Engineering handbooks and references**

## An Introduction to Electronics

*By R. G. Hudson. 97 pp. 37 plates. 72 ill. \$3.30*

An expert provides the non-specialist with a working knowledge of the principles, current applications and future possibilities of this miracle-working science. The explanation of theory and of all basic devices is exceptionally clear, easy-to-understand and at the same time exact.

## Ultra-High-Frequency Radio Engineering

*By W. L. Emery. 295 pp. 131 ill. \$3.75*

A brief, practical text covering all essential theory with many examples of how to apply it in the design, construction and testing of circuit elements and the prediction of circuit performance. Illustrative experiments and reference tables are given at the end of the book.

## Fundamental Electronics and Vacuum Tubes

*By A. L. Albert. 546 pp. 300 ill. \$5.50*

A new edition of a standard text, incorporating the new developments of the past 5 years. Gives a very thorough treatment of theory and examples of both power and communications applications. (Price tentative).

**A most useful reference for ALL who work in radio and electronics**

## Practical Radio Mathematics

*A Handbook of Problems and Solutions*

*By Bernhard Fischer*

This book shows how to set up and solve over 350 typical problems encountered in radio and electronics. Arranged for convenience under electronic topics. Thus, if a solution to a problem of cathode-follower output impedance in television is sought, it will be found under that heading. All calculations from those involving circuit components to those concerned with specialized elements in modern control apparatus are covered. All solutions are given in simple, logical steps with NO omissions. Also includes all electronic formulas, all useful tables, and a review of basic math. *To be published in March, 1948.*

*Send for our latest catalog of technical and engineering books.*

*We shall be happy to send you a copy of any of the above books on 10-days' approval. For on-approval copies, write to Dept. R.*

**THE MACMILLAN COMPANY** 60 Fifth Avenue  
New York 11, N. Y.

COMPLETE OUTFITTERS

*for the HAM . . .*

COMMUNICATIONS

AND

ELECTRONIC

ENGINEERS



**EUGENE G. WILE**

10 South 10th Street

Philadelphia 7, Pa.

*Distributors of*

Nationally Advertised Lines of

RADIO, TELEVISION and ELECTRONIC Parts

# Atlantic City Documents!

AT THE REQUEST of the General Secretariat of the International Telecommunication Union, this society is acting as the distribution agency for the public sale in the Western Hemisphere of the Final Acts of the Atlantic City International Telecommunication and International Radio Conferences. The League is performing this work on a nonprofit basis as a public service to the telecommunication interests of the American Region, to make the documents available sooner and more conveniently than if orders had to be sent to Switzerland.

These Final Acts comprise the new International Telecommunication Convention, the International Radio Regulations, and all of their respective Appendices, Annexes, Protocols, Resolutions and Recommendations, including their illustrations. They are the source material on which the regulation of international radio communication will be based for some years. Of indispensable reference value to all those concerned with the administration and control of communications, the amateur and general student will also find them of interest and assistance in understanding world communication problems.

The price, set by I.T.U., is \$1.20, postpaid, to governments and government agencies, \$1.50 to all others (such as private operating agencies and individuals). Remittances should be made payable to the undersigned society and must yield the appropriate amount net in U. S. funds. Remittance must accompany order — except that in the case of government agencies of the American Region which find themselves unable, through their internal regulations, to send remittance in advance, the League will honor the order and advise the General Secretariat of the Union at Bern to bill the government agency direct. Page size  $5\frac{7}{8} \times 8\frac{1}{4}$  inches, white paper, heavy paper covers. *Now available in two editions; specify which is desired:*

**French-English Texts:** The official texts of the conferences, facing pages in parallel in the two languages, set in type, letterpress-printed, about 1100 pages.

**Spanish Text:** A limited quantity is available of a Spanish translation prepared by the Conference Secretariat. Produced by planograph lithography from typewriter text copy but including all illustrations and charts; about 530 pages.

## The American Radio Relay League, Inc.

38 La Salle Road • West Hartford 7, Connecticut, U. S. A.

# McELROY TRAINING AIDS



## MEMO

TO: All who are active in the Reserve Training Program

FROM: T. R. McElroy

SUBJECT: The BEST electronic and radio-telegraphic TRAINING AIDS in the world.

Ted McElroy has developed and built more apparatus for training radio operators than any one else in the world. His widely imitated phototube keyer was the foundation for training operators of all the United Nations. Employing an inked slip and a photo tube scanner, this device was developed by Ted twenty-five years ago.

With three brothers radio operators in the Navy, and his son a midshipman, it is natural that Ted's first thought is the training of our Naval Reserve. But all other branches of the Armed Forces have equally important jobs in training their reserves. The need is urgent for such training in a sound, well-planned Reserve program.

We show here some of the equipment we produce for this job. We welcome the opportunity to discuss the project with you in detail, and will send you descriptive material promptly on request.

Yours,

*Ted*

T. R. McElroy.


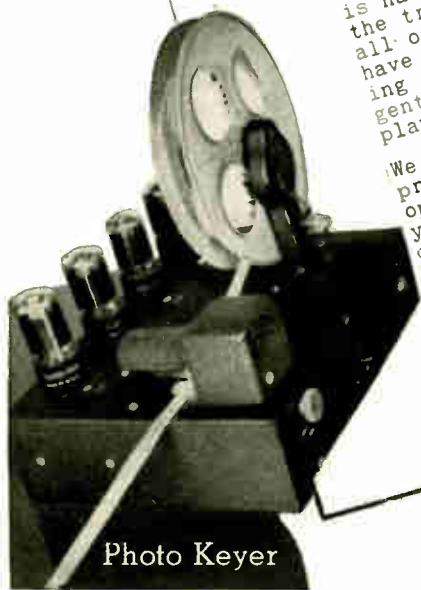


Photo Keyer

# for RADIO TELEGRAPHY and ELECTRONICS

*Now  
available!*

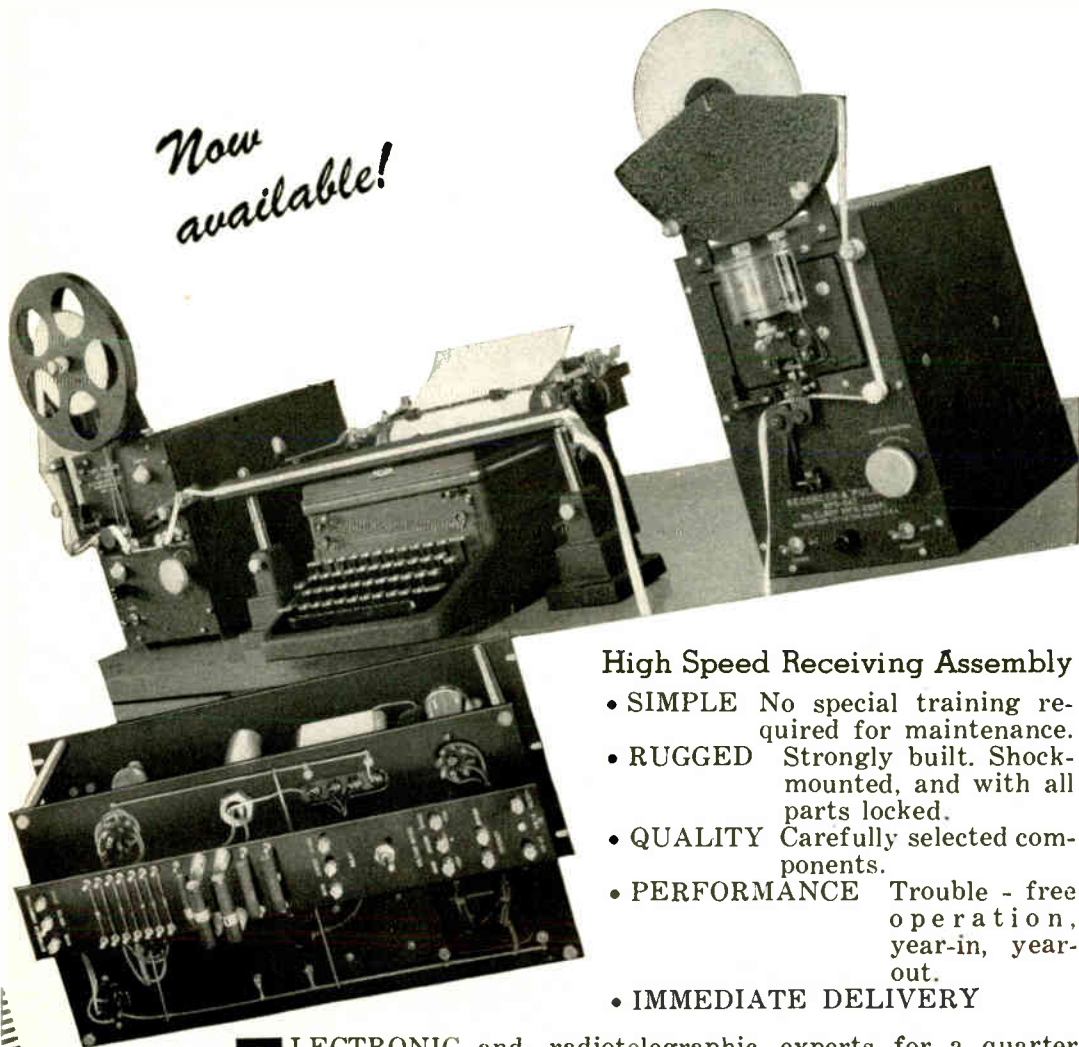

Relay and  
Voltage Keyer

## High Speed Receiving Assembly


- **SIMPLE** No special training required for maintenance.
- **RUGGED** Strongly built. Shock-mounted, and with all parts locked.
- **QUALITY** Carefully selected components.
- **PERFORMANCE** Trouble - free operation, year-in, year-out.
- **IMMEDIATE DELIVERY**

**E**LECTRONIC and radiotelegraphic experts for a quarter century, McElroy engineers and production men have the knowledge and experience to provide you with outstanding equipment for communications and for training radio operators. The speed, accuracy, simplicity, ease of maintenance and *extra rugged* construction of McElroy training equipment make it especially suitable for use in the new Reserve Training Program.

Executive offices at Littleton, Mass. Call Littleton 250.

**McELROY MANUFACTURING CORPORATION**  
**BOSTON AND LITTLETON, MASS.**

131

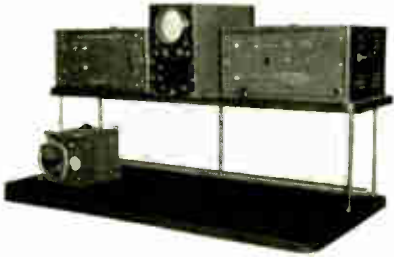

HIGH SPEED TRANSMITTING ASSEMBLY

The fastest and most accurate communication means in existence! The simplest and easiest to maintain!



AUTO HEAD AND DRIVE AHD-54

The uniform speed drive, accurately controlled in words per minute, has a plug-in connection to the auto head, for easy maintenance.

## TRANSMITTING



HIGH SPEED RECEIVING ASSEMBLY

All the operator does is concentrate on copying the signals as they run across the tape bridge.



RECORDER AND PULLER RPC-547

Continuously adjustable speed is provided by the precision tape drive. *Square signals at any speed!* The only recorder with a built-in drive!

## RECEIVING

**SPEED!** The McElroy undulator ink recorder can surpass the highest speeds of existing transmitters! Allowing a wide margin for development of faster transmitters in the future, this equipment will function long and effortlessly at the highest present-day operating speeds.

The McElroy automatic transmitter, simplest and most rugged in radiotelegraph service, operates with precision at 600 words per minute. No other mechanical contacting transmitter approaches this performance. Only complicated photoscanning keyers can match it.

Prompt delivery on all items, including Kleinschmidt and McElroy Wheatstone perforators and McElroy photo tube keyers.



## **DEPENDABLE High Speed Communication**

---




**AUTO HEAD HED-547**

Three speed ranges allow operation from 1 to 600 words per minute. The non-fatigue springs measure up to the hardest service, year after year.



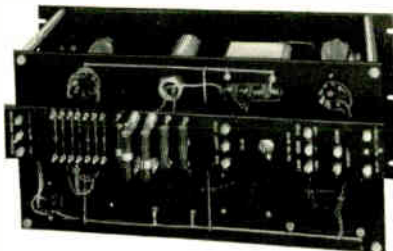**RELAY AND VOLTAGE KEYS RVK-547**


This wholly new circuit application provides keying of the largest transmitters without relays. Electronic switching allows either on-off or frequency shift keying. The RVK-547 is constructed for rack and panel mounting. Tubes are horizontally placed for easy performance test during operation.



---

## **By SKILLED Communications Engineers**

---

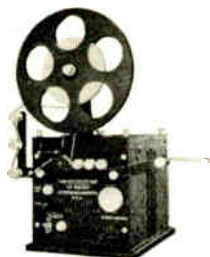


**TAPE PULLER CTP-547**

A principle new to automatic radiotelegraphy results in a long life tape-drive mechanism which maintains unvarying speed at any setting.



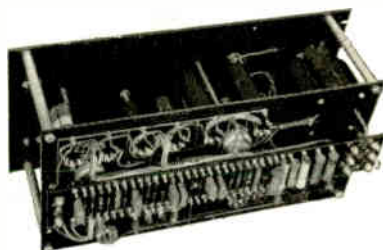**DIFFERENTIATING AMPLIFIER RDA-946**


Two simple controls maintain sharp, clear signals no matter what the speed of reception. Circuits compensate for fading and poor transmission. All parts are readily accessible for voltage and resistance readings, making preventive maintenance easy and routine.



---

## **of long EXPERIENCE and INTEGRITY**
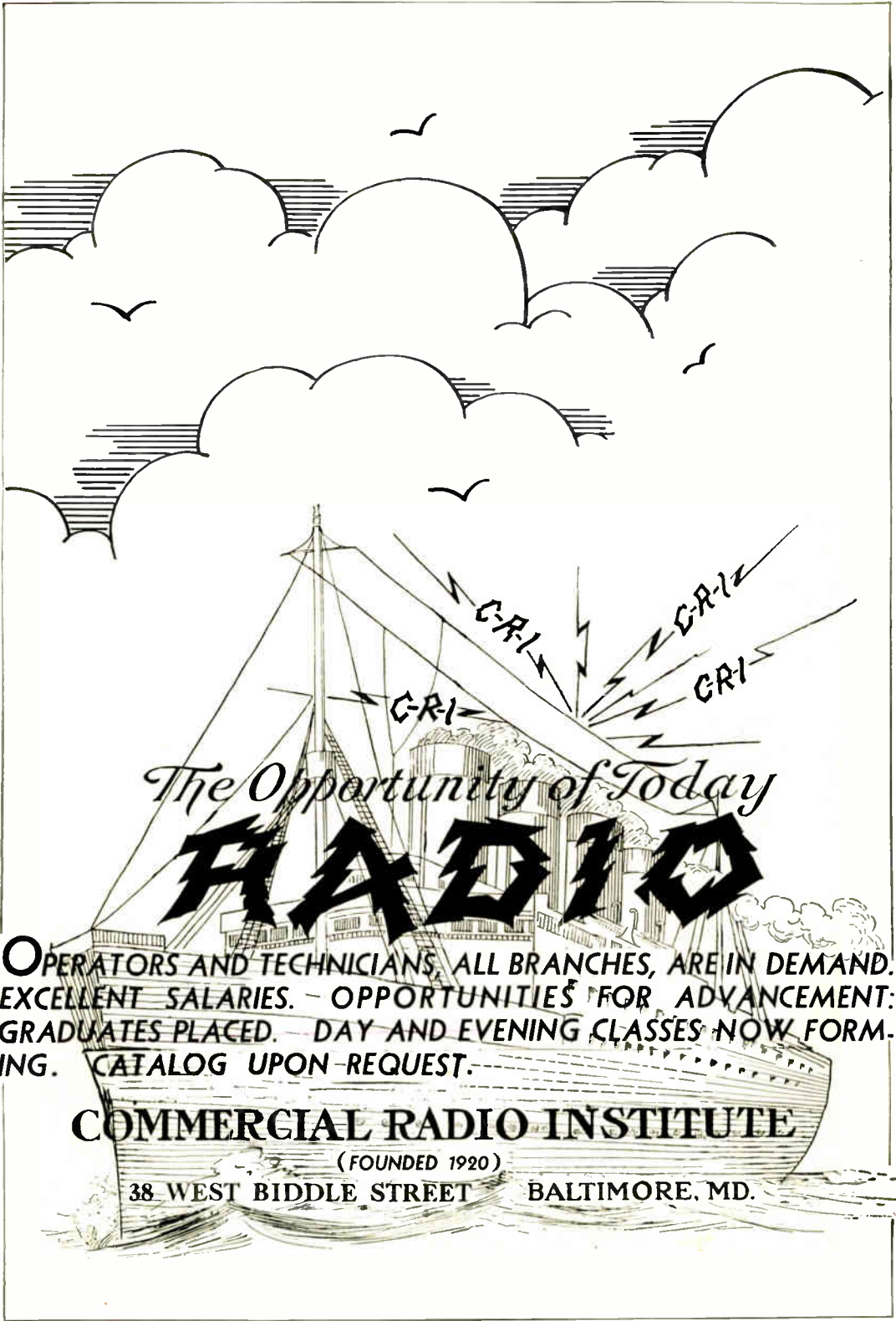
# **McELROY** MANUFACTURING CORPORATION BOSTON AND LITTLETON, MASS.



*The Opportunity of Today*

# **RADIO**


**O**PERATORS AND TECHNICIANS, ALL BRANCHES, ARE IN DEMAND. EXCELLENT SALARIES. - OPPORTUNITIES FOR ADVANCEMENT: GRADUATES PLACED. - DAY AND EVENING CLASSES NOW FORMING. CATALOG UPON REQUEST.

**COMMERCIAL RADIO INSTITUTE**

(FOUNDED 1920)

38 WEST BIDDLE STREET

BALTIMORE, MD.

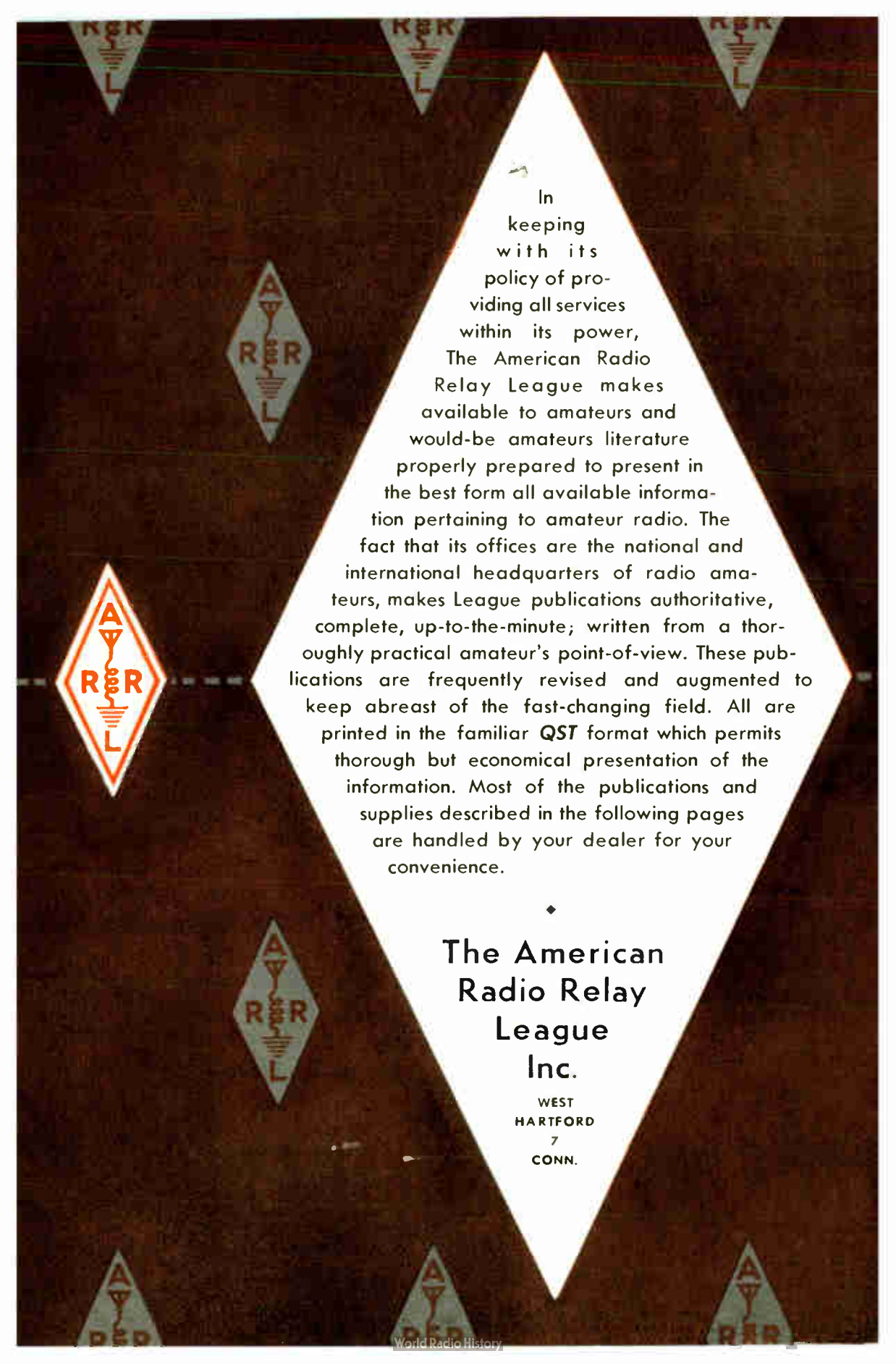
The background is a dark brown color with several ARRL logos scattered across it. At the top, there are three inverted triangles containing the letters 'ARRL'. In the center, there is a large white diamond shape that contains the main text. To the left of the diamond, there is a single ARRL logo. Below the diamond, there are more ARRL logos, including one in the center and two at the bottom corners. The text inside the diamond is arranged in a paragraph, with a small diamond symbol centered below it.

In keeping with its policy of providing all services within its power, The American Radio Relay League makes available to amateurs and would-be amateurs literature properly prepared to present in the best form all available information pertaining to amateur radio. The fact that its offices are the national and international headquarters of radio amateurs, makes League publications authoritative, complete, up-to-the-minute; written from a thoroughly practical amateur's point-of-view. These publications are frequently revised and augmented to keep abreast of the fast-changing field. All are printed in the familiar **QST** format which permits thorough but economical presentation of the information. Most of the publications and supplies described in the following pages are handled by your dealer for your convenience.

◆

## The American Radio Relay League Inc.

WEST  
HARTFORD  
7  
CONN.

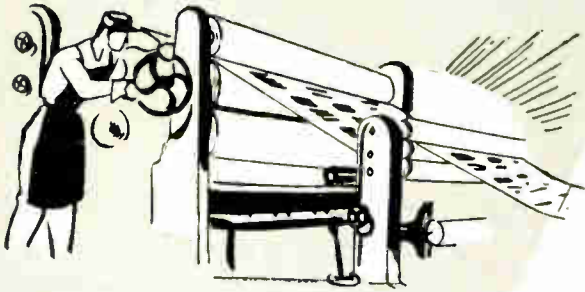

**THE  
OFFICIAL  
MAGAZINE  
OF THE  
AMERICAN  
RADIO RELAY  
LEAGUE**

*QST* faithfully and adequately reports each month the rapid development which makes Amateur Radio so intriguing. Edited in the sole interests of the members of The American Radio Relay League, who are its owners, *QST* treats of equipment and practices and construction and design, and the romance which is part of Amateur Radio, in a direct and analytical style which has made *QST* famous all over the world. It is essential to the well-being of any radio amateur. *QST* goes to every member of The American Radio Relay League and membership costs \$3.00 in the United States and Possessions, \$3.50 in the Dominion of Canada, \$4.00 in all other countries. Elsewhere in this book will be found an application blank for A.R.R.L. membership.



For thirty-three years (and thereby the oldest American radio magazine) *QST* has been the "bible" of Amateur Radio.



# QST BINDERS


Price \$2.00 each, postpaid

*Available only in U. S. and Possessions*

Those who take pride in the appearance of their bookshelf and wish to keep their reference file of *QST*'s in a presentable manner, appreciate the *QST* binder. It is stiff-covered, finished in beautiful and practical fabrikoid. Cleverly designed to take each issue as received and hold it firmly without mutilation, it permits removal of any desired issue without disturbing the rest of the file. It accommodates 12 copies of *QST*. Opens flat at any page of any issue.

With each Binder is furnished a sheet of gold and black gummed labels for years 1929 through 1949. The proper one can be cut from the sheet and pasted in the space provided for it on the back of the binder. The back copies of *QST* contain the record of development of modern amateur technique. They are invaluable as technical references. Some back copies are available—list will be sent upon request.



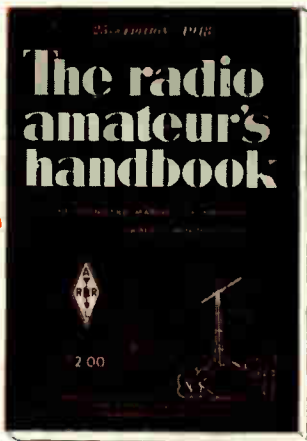

The  
*Handbook*  
 tells the things  
 which are needed for a  
 comprehensive understanding  
 of Amateur Radio. From the story  
 of how Amateur Radio started through  
 an outline of its wide scope of the present—  
 from suggestions on how to learn the code  
 through explanations of traffic-handling  
 procedure and good operating practices—from  
 electrical and radio fundamentals through the  
 design, construction, and operation of amateur  
 equipment—this book covers the subject  
 thoroughly. It includes the latest and the  
 best information on everything in  
 Amateur Radio.

**\$2.00**

*U.S., Its Possessions and Canada*

\$2.50 Elsewhere

Buckram Bound

\$3.00



The  
 standard  
 elementary  
 guide for the pro-  
 spective amateur. Features  
 equipment which, although simple  
 in construction, conforms in  
 every detail to present practices.  
 The apparatus is of a thoroughly practical  
 type capable of giving long and  
 satisfactory service—while at the same time  
 it can be built at a minimum of expense. The  
 design is such that a high degree of flexibility  
 is secured, making the various units fit into  
 the more elaborate station layouts which  
 inevitably result as the amateur progresses.


Complete operating instructions and  
 references to sources of detailed  
 information on licensing procedure  
 are given.

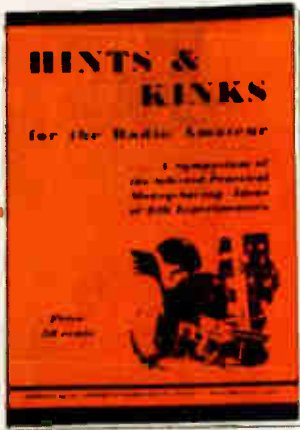**25c**

Postpaid  
 Anywhere



Amateurs are noted for their ingenuity in overcoming by clever means the minor and major obstacles they meet in their pursuit of their chosen hobby. An amateur must be resourceful and a good tinkerer. He must be able to make a small amount of money do a great deal for him. He must frequently be able to utilize the contents of the junk box rather than buy new equipment. Hints and Kinks is a compilation of hundreds of good ideas which amateurs have found helpful. It will return its cost many times in money savings — and it will save hours of time.



**50c**

Postpaid



A comprehensive manual of antenna design and construction, by the headquarters staff of the American Radio Relay League. Eighteen chapters, profusely illustrated. Both the theory and the practice of all types of antennas used by the amateur, from simple doublets to multi-element rotaries, including long wires, rhomboids, vees, phased systems, v.h.f systems, etc. Feed systems and their adjustment. Construction of masts, lines and rotating mechanisms. The most comprehensive and reliable information ever published on the subject.




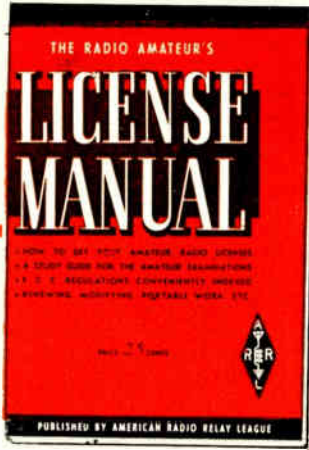**50c**

Postpaid




To obtain an amateur operator's license you must pass a government examination. The License Manual tells how to do that —tells what you must do and how to do it. It makes a simple and comparatively easy task of what otherwise might seem difficult. In addition to a large amount of general information, it contains questions and answers such as are asked in the government examinations. If you know the answers to the questions in this book, you can pass the examination without trouble.



**25c**

Postpaid

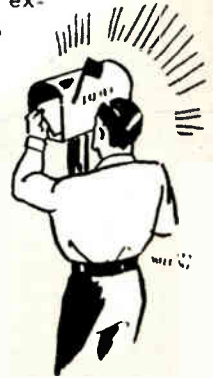


This booklet is designed to train students to handle code skillfully and with precision, both in sending and in receiving. Employing a novel system of code-learning based on the accepted method of sound conception, it is particularly excellent for the student who does not have the continuous help of an experienced operator or access to a code machine. It is similarly helpful home-study material for members of code classes. Adequate practice material is included for classwork as well as for home-study.

There are also helpful data on high-speed operation, typewriter copy, general operating information—and an entire chapter on tone sources for code practice, including the description of a complete code instruction table with practice oscillator.

**25c**

Postpaid

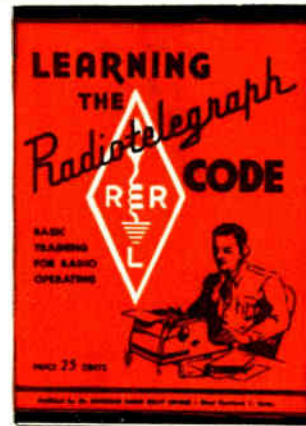





## TYPE A

### Radio Calculator

This calculator is useful for the problems that confront the amateur every time he builds a new rig or rebuilds an old one or winds a coil or designs a circuit. It has two scales for physical dimensions of coils from one-half inch to five and one-half inches in diameter and from one-quarter to ten inches in length; a frequency scale from 400 kilocycles through 150 megacycles; a wavelength scale from two to 600 meters; a capacity scale from 3 to 1,000 micro-microfarads; two inductance scales with a range of from one microhenry through 1,500; a turns-per-inch scale to cover enameled or single silk covered wire from 12 to 35 gauge, double silk or cotton covered from 0 to 36 and double cotton covered from 2 to 36. Using these scales in the simple manner outlined in the instructions on the back of the calculator, it is possible to solve problems involving frequency in kilocycles, wavelength in meters, inductance in microhenrys and capacity in microfarads, for practically all problems that the amateur will have in designing—from high-powered transmitters down to simple receivers. Gives the direct reading answers for these problems with accuracy well within the tolerances of practical construction. **\$1.00 Postpaid.**

## Lightning Calculators

Aware of the practical bent of the average amateur and knowing of his limited time, the League, under license of the designer, W. P. Koechel, has made available these calculators to obviate the tedious and sometimes difficult mathematical work involved in the design and construction of radio equipment. The lightning calculators are ingenious devices for rapid, certain and simple solution of the various mathematical problems which arise in radio and allied work. They make it possible to read direct answers without struggling with formulas and computations. They are tremendous time-savers for amateurs, engineers, servicemen and experimenters. Their accuracy is more than adequate for the solution of practical problems, and is well within the limits of measurement by ordinary means. Each calculator has on its reverse side detailed instructions for its use; the greatest mathematical ability required is that of dividing or multiplying simple numbers. They are printed in several colors. You will find lightning calculators the most useful gadgets you ever owned.

## TYPE B

### Ohm's Law Calculator


This calculator has four scales: a power scale from 10 microwatts through 10 kilowatts, a resistance scale from .01 ohm through 100 megohms, a current scale from 1 microampere through 100 amperes, a voltage scale from 10 microvolts through 10 kilovolts.

With this concentrated collection of scales, calculations may be made involving voltage, current, and resistance, and can be made with a single setting of a dial. The power or voltage or current or resistance in any circuit can be found easily if any two are known. This is a newly-designed Type B Calculator which is more accurate and simpler to use than the justly-famous original model. It will be found useful for many calculations which must be made frequently but which are often confusing if done by ordinary methods. All answers will be accurate within the tolerances of commercial equipment. **\$1.00 Postpaid.**



# lies

## MEMBERSHIP

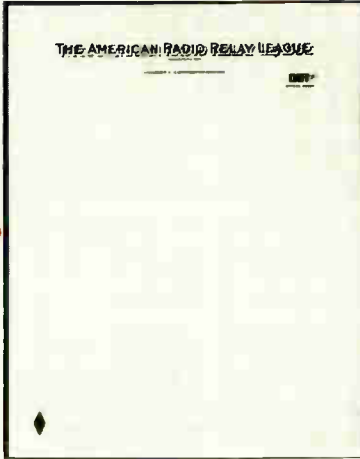

### Members' Stationery

Members' stationery is lithographed on standard 8½ x 11 bond paper which every member should be proud to use for his radio correspondence.

100 Sheets, **\$1.00** 250 Sheets, **\$1.50**  
 500 Sheets  
**\$2.50**  
*postpaid*

In the January, 1920 issue of **QST** there appeared an editorial requesting suggestions for the design of an A.R.R.L. emblem—a device whereby every amateur could know his brother amateur when they met. In the July, 1920 issue the design was announced—the familiar diamond that greets you everywhere in Ham Radio. For years it has been the unchallenged emblem of amateur radio.

**The League Emblem**, with gold border and lettering, and with black enamel background, is available in either pin (with safety clasp) or screw-back type. In addition, there are special colors for Communications Department appointees. • Red enameled background for the SCM. • Blue enameled background for the ORS or OPS.

**50c** each *postpaid*

**The Emblem Cut.** A mounted printing electrotype, ⅝" high, for use by members on amateur printed matter, letterheads, cards, etc.

**\$1.00**  
 each  
*postpaid*



## ***To Manufacturers of Products Used in Short-Wave Radio Communication***

THE RADIO AMATEUR'S HANDBOOK is the world's standard reference on the technique of high-frequency radio communication. Now in its twenty-fifth annual edition, it is used universally by radio engineers and technicians as well as the thousands of amateurs and experimenters. Year after year, it has sold more widely, until the Handbook now has a world-wide annual distribution greater than any other technical handbook in any field of human activity. To manufacturers whose integrity is established and whose products meet the approval of the American Radio Relay League technical staff, we offer use of space in the Handbook's Catalog-Advertising Section. Testimony to its effectiveness is the large volume of advertising which the Handbook carries each year. It is truly the standard guide for amateur, commercial and government buyers of short-wave radio equipment. Particularly valuable as a medium through which complete data on products can be made easily available to the whole radio engineering and experimenting field, it offers a surprisingly inexpensive method of producing and distributing a creditable catalog, accomplishes its production in the easiest possible manner, and provides adequate distribution and permanent availability impossible to attain by any other means. We solicit inquiries from qualified manufacturers who wish full data for their examination when catalog and advertising plans are under consideration.

**ADVERTISING DEPARTMENT . . .**

**American Radio Relay League**

**WEST HARTFORD 7, CONNECTICUT**



the 1930s, the 1940s, and the 1950s. The 1960s and 1970s were the most difficult years for the station, and the 1980s and 1990s were the most successful. The station's success was due to its commitment to quality programming and its dedication to its audience.

The station's programming was a mix of news, music, and entertainment. It was known for its news coverage, which was both timely and accurate. The station's music programming was also highly regarded, and it was a major force in the development of the rock and roll genre.

The station's success was also due to its dedication to its audience. It was always willing to listen to its audience's feedback and make changes accordingly. This commitment to its audience helped the station build a loyal following over the years.

The station's success was also due to its commitment to quality programming. It always strived to provide the best possible programming to its audience, and this commitment helped it stand out from its competitors.

The station's success was also due to its dedication to its community. It was always willing to help those in need, and this dedication helped it build a strong relationship with its community.

The station's success was also due to its commitment to innovation. It was always willing to try new things, and this commitment helped it stay ahead of the competition.

The station's success was also due to its dedication to its staff. It was always willing to invest in its staff, and this dedication helped it build a strong team.

The station's success was also due to its commitment to its history. It was always proud of its long history, and this commitment helped it maintain its identity over the years.

The station's success was also due to its dedication to its future. It was always willing to invest in its future, and this dedication helped it stay relevant in a constantly changing world.