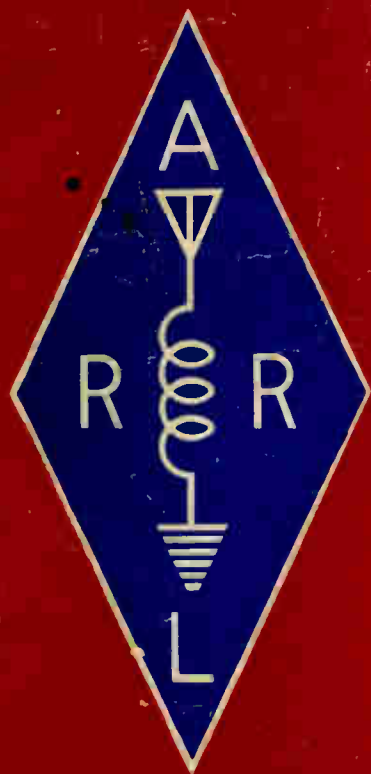


Ned H. Hockensmith

The radio amateur's handbook

THE STANDARD MANUAL OF AMATEUR
RADIO COMMUNICATION



1946
EDITION

\$1 IN CONTINEN-
TAL U.S.A.

PUBLISHED BY

THE AMERICAN RADIO RELAY LEAGUE


Ned H. Hockensmith

Ned Hockensmith

The Radio Amateur's Handbook

Ned H. Hockensmith

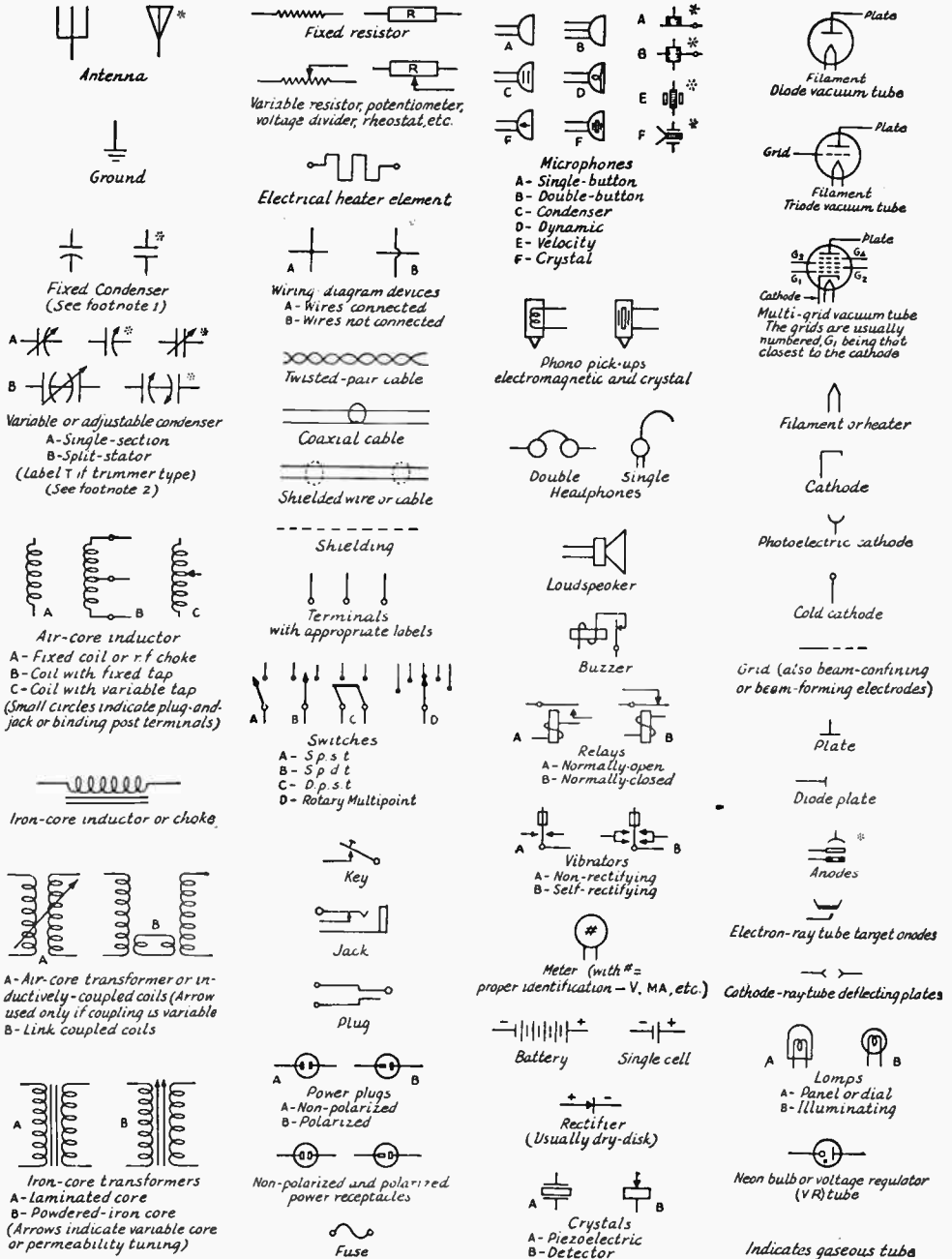STANDARD SCHEMATIC SYMBOLS USED IN CIRCUIT DIAGRAMS



For convenience and simplicity, schematic wiring diagrams employing conventionalized symbols which represent various components, as shown above, are used to show the circuit connections in assemblies of radio apparatus. The symbols used in this Handbook follow the standardized forms adopted by the radio industry under the ASA standardization program in 1944. Alternative symbols marked with an asterisk are conventional forms used prior to mid-1944, included for reference where the original symbol has undergone appreciable change.

¹ Where it is necessary or desirable to identify the electrodes, the curved element represents the *outside* electrode (marked "outside foil," "ground," etc.) in fixed paper- and ceramic-dielectric condensers, and the *negative* electrode in electrolytic condensers.

² In the modern symbol, the curved line indicates the moving element (rotor plates) in variable and adjustable air- or mica-dielectric condensers. To distinguish trimmers, the letter "T" should appear adjacent to the symbol.

In the case of switches, jacks, relays, etc., only the basic combinations are shown. Any combination of these symbols may be assembled as required, following the elementary forms shown.

TWENTY-THIRD EDITION
NINETEEN FORTY-SIX

THE RADIO AMATEUR'S HANDBOOK

BY THE HEADQUARTERS STAFF OF
THE AMERICAN RADIO RELAY LEAGUE



PUBLISHED BY
THE AMERICAN RADIO RELAY LEAGUE, INC.
WEST HARTFORD 7, CONNECTICUT, U. S. A.

COPYRIGHT 1946 BY
THE AMERICAN RADIO RELAY LEAGUE, INC.

Copyright secured under the Pan-American Convention

This work is Publication No. 6 of The Radio Amateur's Library, published by the League. All rights reserved. No part of this work may be reproduced in any form except by written permission of the publisher. All rights of translation are reserved. Printed in U. S. A.

Twenty-Third Edition

First Printing, November, 1945, 75,000 copies

(Of the previous twenty-two editions, 1,398,250 copies were published in forty-six printings.)

This book is produced in full compliance with government regulations for conservation of paper and all other essential materials.

THE RUMFORD PRESS
CONCORD, NEW HAMPSHIRE

Foreword

TWENTY years ago — in 1926 — the first edition of *The Radio Amateur's Handbook* was presented to the amateur world. Produced by the amateur's own organization, the American Radio Relay League, and written with the needs of the practical amateur constantly in mind, its publication was eagerly greeted by the radio enthusiasts of that day. Subsequent editions have earned ever-increasing acceptance not only by amateurs but by all segments of the radio world, from students to engineers, servicemen to operators.

This wide dependence on the *Handbook*, evidenced by a total printing of nearly a million and a half copies, primarily is founded on its practical utility, its treatment of radio communication problems in terms of how-to-do-it rather than by abstract discussion and abstruse formulas.

But there is another factor as well: dealing with a fast-moving and progressive science, sweeping and virtually continuous modification has been a feature of the *Handbook* — always with the objective of presenting the soundest and best aspects of current practice rather than the merely new and novel. Its annual rewriting is a major task of the headquarters group of the League, participated in by skilled and experienced amateurs well acquainted with the practical problems in the art.

In contrast to most publications of a comparable nature, the *Handbook* is printed in the format of the League's monthly magazine, *QST*. This, together with extensive and usefully-appropriate catalog advertising by manufacturers producing equipment for the radio amateur, makes it possible to distribute for a very modest charge a work which in volume of subject matter and profuseness of illustration surpasses most available radio texts selling for several times its price.

When war came to this nation it was discovered by the military and other agencies that the *Handbook* was precisely what was needed to help make practical radiomen for the Army and Navy and to help those who were training themselves for wartime radio work. Not only was the *Handbook* used as a text or reference in many training programs, but it also provided source data for many service-written special courses. During the war years the training aspects have been given increasing emphasis — not, however, to the detriment of other long-established features, but rather by increasing the size and scope of the book.

The United States was still at war when work on the present edition was begun. With most forecasters placing the probable end of the conflict in the summer of 1946, it seemed wise to carry the wartime structure of the *Handbook* through this edition. August, 1945, found most of the revision completed and a great deal of the book actually printed. But with V-J Day bringing the imminent prospect of resumption of amateur operation, part of it in newly-assigned bands calling for revamping or complete redesigning of prewar equipment, it was apparent that to maintain the high standard of practical usefulness set by previous editions a new treatment of the v.h.f. section of the book was urgently needed. Although it meant re-doing much of the work and delaying the appearance of the *Handbook* beyond the anticipated publication date, this revision has been completed. In the Principles and Design section, which already had been through the presses, the occasional reference to prewar v.h.f. assignments should be read in the light of the new frequencies; revised formulas and charts for the new bands appear on the back of this page, together with references to the *Handbook* page and (where applicable) figure number they replace.

A word about the reference system: It will be noted that each chapter is divided into sections and that these are numbered serially within each chapter. The number takes the form of two digits or groups separated by a hyphen. The first figure is the chapter number, the second the section number within the chapter. Cross-references in the text take such a form as (§ 4-7), for example, which means that the subject referred to will be found discussed in Chapter Four, Section 7. Throughout the book, illustrations are serially numbered within each chapter. Thus Fig. 1107 can be readily identified as the seventh illustration in Chapter Eleven. There is a carefully-prepared index at the rear of the book.

To a long-established reputation of indispensability in the amateur station of prewar days the *Handbook* now has added a proud record of participation in the national war effort. With the coming of a new peace and the opening of a new era in amateur communication, we earnestly hope that the present edition will succeed in bringing as much assistance and inspiration to amateurs and would-be amateurs as have its predecessors.

KENNETH B. WARNER
Managing Secretary, A.R.R.L.


WEST HARTFORD, CONN.
November, 1945

Frequency Changes

Occasional references will be found in Chapters 2 to 10, inclusive, to the 56- and 112-Mc. bands. These bands are now 50-54 Mc. and 144-148 Mc., respectively, and the new figures should be substituted wherever encountered.

On page 194, formulas (3) and (4) can be used without change for computing antenna lengths in the 50-Mc. band.

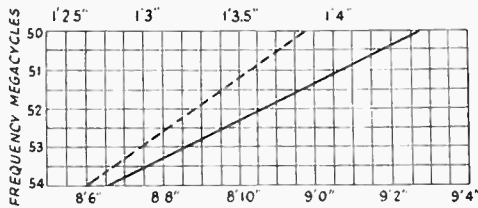On page 205, the following chart should be substituted for the lowermost one in Fig. 1016:



The table below should be substituted for Table V, page 226, giving dimensions for square-corner reflectors:

TABLE V					
Frequency Band	Length of Side	Length of Reflector Elements	Number of Reflector Elements	Spacing of Reflector Elements	Spacing of Driven Dipole to Vertex
220-225 Mc. (1½ meters)	4' 2"	2' 8"	20	5"	2' 3"
144-148 Mc. (2 meters)	6' 8"	3' 11"	20	8"	3' 4"
144-148 Mc.* (2 meters)	5' 4"	3' 11"	16	8"	2' 6"
50-54 Mc. (6 meters)	18' 4"	11' 4"	20	1' 10"	9' 6"
50-54 Mc.* (6 meters)	14' 8"	11' 4"	16	1' 10"	7' 7"

Dimensions of square-corner reflector for the 220-, 144-, and 50-Mc. bands. Alternative designs are listed for the 144- and 50-Mc. bands. These designs, marked (*), have fewer reflector elements and shorter sides, but the effectiveness is only slightly reduced. There is no reflector element at the vertex in any of the designs.

TABLE OF CONTENTS

INTRODUCTION	{	<i>Frontispiece</i>	2
		<i>The Amateur—His Code of Ethics</i>	8
		<i>Chapter I . . . Amateur Radio</i>	9
PRINCIPLES AND DESIGN	{	<i>Chapter II . . . Electrical and Radio Fundamentals</i>	13
		<i>Chapter III . . . Vacuum Tubes</i>	60
		<i>Chapter IV . . . Radio-Frequency Power Generation</i>	94
		<i>Chapter V . . . Radiotelephony</i>	117
		<i>Chapter VI . . . Keying</i>	137
		<i>Chapter VII . . . Receiver Principles and Design</i>	142
		<i>Chapter VIII . . . Power Supply</i>	175
		<i>Chapter IX . . . Wave Propagation</i>	188
		<i>Chapter X . . . Antenna Systems</i>	194
		EQUIPMENT CONSTRUCTION	{
<i>Chapter XII . . . Receiver Construction</i>	234		
<i>Chapter XIII . . . Transmitter Construction</i>	256		
<i>Chapter XIV . . . Modulation Equipment</i>	305		
<i>Chapter XV . . . V.H.F. Receivers</i>	316		
<i>Chapter XVI . . . V.H.F. Transmitters</i>	337		
<i>Chapter XVII . . . Antenna Construction</i>	375		
<i>Chapter XVIII . . . Emergency and Portable</i>	385		
<i>Chapter XIX . . . Measurements and Measuring Equipment</i>	395		
GENERAL	{	<i>Chapter XX . . . Tube Characteristics and Miscellaneous Data</i>	413
		<i>Chapter XXI . . . Radio Operating</i>	460
		<i>Index</i>	469

The Amateur's Code



1. *The Amateur is Gentlemanly*

He never knowingly uses the air for his own amusement in such a way as to lessen the pleasure of others. He abides by the pledges given by the ARRL in his behalf to the public and the Government.

2. *The Amateur is Loyal*

He owes his amateur radio to the American Radio Relay League, and he offers it his unswerving loyalty.

3. *The Amateur is Progressive*

He keeps his station abreast of science. It is built well and efficiently. His operating practice is clean and regular.

4. *The Amateur is Friendly*


Slow and patient sending when requested, friendly advice and counsel to the beginner, kindly assistance and coöperation for the broadcast listener; these are marks of the amateur spirit.

5. *The Amateur is Balanced*

Radio is his hobby. He never allows it to interfere with any of the duties he owes to his home, his job, his school, or his community.

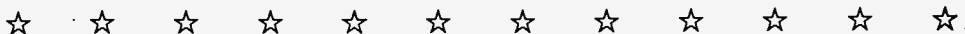6. *The Amateur is Patriotic*

His knowledge and his station are always ready for the service of his country and his community.



Amateur Radio

COUNTLESS thousands of persons all over the world have enjoyed the thrills and pleasures of amateur radio. This is a brief account of how it grew into the magnificently-useful institution it is today.

Amateur radio is as old as the art itself. There were amateurs before the present century. Shortly after the late Marconi astounded the world with his experiments proving that wireless telegraph messages actually could be sent, "amateurs" were attempting to duplicate his results. But amateur radio actually began when private citizens discovered this means for personal communication with others, and set about learning enough about "wireless" to build home-made stations. Its subsequent development may be divided into two phases, the period before 1917 and the years between that war and December 7, 1941. Plus, of course, the new phase now opening.

Amateur radio of pre-World War I bore little resemblance to radio as we know it today, except in principle. Transmitting and receiving equipment was of a type now long obsolete. No U. S. amateur had ever heard a foreign one nor had any foreigner ever reported an American signal. The oceans were an impenetrable wall. Cross-country communication could be accomplished only by relays. "Short waves" meant 200 meters; the entire spectrum below that was a vast silence undisturbed by any signals. By 1912, however, there were numerous Government and commercial stations and hundreds of amateurs; regulation was needed; and laws, licenses and wavelength specifications for the various services appeared.

"Amateurs? . . . Oh, yes. . . . Well, stick 'em on 200 meters and below; they'll never get out of their backyards with that."

But as the years rolled on, amateurs found out how, and DX jumped from local to 500-mile and even occasional 1,000-mile two-way contacts. Because all long-distance messages had to be relayed, relaying developed into a fine art — an ability that was to prove invaluable when the Government suddenly called hundreds of skilled amateurs into war service in 1917. Meanwhile U. S. amateurs began to wonder if there were amateurs in other countries across the seas and if, some day, we might not span the Atlantic on 200 meters.

Most important of all, this period witnessed the birth of the American Radio Relay League, the amateur radio organization whose name was to be virtually synonymous with subsequent amateur progress and short-wave development. Conceived and formed by the famous inventor, the late Hiram Percy Maxim, ARRL was formally launched in early 1914. It

had just begun to exert its full force in amateur activities when the United States declared war in 1917, and by that act sounded the knell for amateur radio for the next two and a half years. There were then over 6,000 amateurs. Over 4,000 of them served in the armed forces during that war.

Today, few amateurs realize that World War I not only marked the close of the first phase of amateur development but came very near marking its end for all time. The fate of amateur radio was in the balance in the days immediately following the signing of the Armistice. The Government, having had a taste of supreme authority over communications in wartime, was more than half inclined to keep it. The war had not been ended a month before Congress was considering legislation that would have made it impossible for the amateur radio of old ever to be resumed. ARRL's President Maxim rushed to Washington, pleaded, argued, and the bill was defeated. But there was still no amateur radio; the war ban continued. Repeated representations to Washington met only with silence. . . . The League's offices had been closed for a year and a half, its records stored away. Most of the former amateurs had gone into service; many of them would never come back. Would those returning be interested in such things as amateur radio? Mr. Maxim, determined to find out, called a meeting of the old board of directors. The situation was discouraging: amateur radio still banned by law, former members scattered, no organization, no membership, no funds. But those few determined men financed the publication of a notice to all the former amateurs that could be located, hired Kenneth B. Warner as the League's first paid secretary, floated a bond issue among old League members to obtain money for immediate running expenses, bought the magazine *QST* to be the League's official organ, started activities, and dunned officialdom until the wartime ban was lifted and amateur radio resumed again, on October 1, 1919. There was a headlong rush to get back on the air.

From the start, amateur radio took on new aspects. Wartime needs had stimulated technical development. Vacuum tubes were being used both for receiving and transmitting. Amateurs immediately adapted the new gear to 200-meter work. Ranges promptly increased and it became possible to bridge the continent with but one intermediate relay.

As DX became 1,000, then 1,500 and then 2,000 miles, amateurs began to dream of trans-Atlantic work. Could they get across? In December, 1921, in what has been called the

greatest sporting event of all time, ARRL sent abroad an expert amateur, Paul F. Godley, 2ZE, with the best receiving equipment available. Tests were run, and thirty American stations were heard in Europe. In 1922 another trans-Atlantic test was carried out and 315 American calls were logged by European amateurs and one French and two British stations were heard on this side.

Everything now was centered on one objective: two-way amateur communication across the Atlantic! It must be possible — but somehow it couldn't quite be done. More power? Many already were using the legal maximum. Better receivers? They had superheterodynes. Another wavelength? What about those undisturbed wavelengths below 200 meters? The engineering world thought they were worthless — but they had said that about 200 meters. So, in 1922, tests between Hartford and Boston were made on 130 meters with encouraging results. Early in 1923, ARRL-sponsored tests on wavelengths down to 90 meters were successful. Reports indicated that *as the wavelength dropped the results were better*. A growing excitement began to spread through amateur ranks.

Finally, in November, 1923, after some months of careful preparation, two-way amateur trans-Atlantic communication was accomplished, when Schnell, 1MO, and Reinartz, 1XAM (now W9UZ and W3IBZ, respectively) worked for several hours with Deloy, 8AB, in France, with all three stations on 110 meters! Additional stations dropped down to 100 meters and found that they, too, could easily work two-way across the Atlantic. The exodus from the 200-meter region had started. The "short-wave" era had begun!

By 1924 dozens of commercial companies had rushed stations into the 100-meter region. Chaos threatened, until the first of a series of national and international radio conferences partitioned off various bands of frequencies for the different services. Although thought still centered around 100 meters, League officials at the first of these conferences, in 1924, wisely obtained amateur bands not only at 80 meters but at 40, 20, 10 and even 5 meters.

Eighty meters proved so successful that "forty" was given a try, and QSOs with Australia, New Zealand and South Africa soon became commonplace. Then how about 20 meters? This new band revealed entirely unexpected possibilities when 1XAM worked 6TS on the West Coast, direct, at high noon. The dream of amateur radio — daylight DX! — was finally true.

From then until "Pearl Harbor," when U. S. amateurs were again closed down "for the duration," amateur radio thrilled with a series of unparalleled accomplishments. Countries all over the world came on the air, and the world total of amateurs passed the 100,000 mark. . . . ARRL representatives deliberated with the representatives of twenty-two other

nations in Paris in 1925 where, on April 17th, the International Amateur Radio Union was formed — a federation of national amateur radio societies. . . . The League began issuing certificates to those who could prove they had worked all six continents. By 1941 over five thousand WAC certificates had been issued!

Amateur radio is a grand and glorious hobby but this fact alone would hardly merit such wholehearted support as was given it by our Government at international conferences. There are other reasons. One of these is a thorough appreciation by the Army and Navy of the value of the amateur as a source of skilled radio personnel in time of war. Another asset is best described as "public service."

About 4,000 amateurs had contributed their skill and ability in '17-'18. After the war it was only natural that cordial relations should prevail between the Army and Navy and the amateur. These relations strengthened in the next few years and, in gradual steps, grew into cooperative activities which resulted, in 1925, in the establishment of the Naval Communications Reserve and the Army-Amateur Radio System. In World War II thousands of amateurs in the Naval Reserve were called to active duty, where they served with distinction, while many other thousands served in the Army, Air Forces, Coast Guard and Marine Corps. Altogether, more than 25,000 radio amateurs served in the armed forces of the United States. Other thousands were engaged in vital civilian electronic research, development and manufacturing.

The "public service" record of the amateur is a brilliant tribute to his work. These activities can be roughly divided into two classes, expeditions and emergencies. Amateur cooperation with expeditions began in '23 when a League member, Don Mix, 1TS, of Bristol, Conn. (now assistant technical editor of *QST*), accompanied MacMillan to the Arctic on the schooner *Bowdoin* with an amateur station. Amateurs in Canada and the United States provided the home contacts. The success of this venture was such that other explorers followed suit. During subsequent years a total of perhaps two hundred voyages and expeditions were assisted by amateur radio, and for many years no expedition has taken the field without such plans.

Since 1913 amateur radio has been the principal, and in many cases the only, means of outside communication in several hundred storm, flood and earthquake emergencies in this country. The 1936 eastern states flood, the 1937 Ohio River Valley flood, and the Southern California flood and Long Island-New England hurricane disaster in '38 called for the amateur's greatest emergency effort. In these disasters and many others — tornadoes, sleet storms, forest fires, blizzards — amateurs played a major rôle in the relief work and earned wide commendation for their resource-

fulness in effecting communication where all other means had failed. During 1938 ARRL inaugurated a new emergency-preparedness program, registering personnel and equipment in its Emergency Corps and putting into effect a comprehensive program of cooperation with the Red Cross.

Throughout these many years the amateur was careful not to slight experimental development in the enthusiasm incident to international DX. The experimenter was constantly at work on ever-higher frequencies, devising improved apparatus, and learning how to cram several stations where previously there was room for only one! In particular, the amateur pressed on to the development of the very high frequencies and his experience with five meters is especially representative of his initiative and resourcefulness and his ability to make the most of what is at hand. In 1924, first amateur experiments in the vicinity of 56 Mc. indicated that band to be practically worthless for DX. Nonetheless, great "short-haul" activity eventually came about in the band and new gear was developed to meet its special problems. Beginning in 1934 a series of investigations by the brilliant experimenter, Ross Hull (later *QST*'s editor), developed the theory of v.h.f. wave-bending in the lower atmosphere and led amateurs to the attainment of better distances; while occasional manifestations of ionospheric propagation, with still greater distances, gave the band uniquely-erratic performance. By Pearl Harbor thousands of amateurs were spending much of their time on this and the next higher band, many having worked hundreds of stations at distances up to several thousand miles — transcontinental 5-meter DX had been accomplished! It is a tribute to these indefatigable amateurs that today's concept of v.h.f. propagation was developed largely through amateur research.

The amateur is constantly in the forefront of technical progress. Many amateur developments have come to represent valuable contributions to the art. The complete record would fill a book! From the ARRL's own laboratory in 1932 came James Lamb's "single-signal" superheterodyne — the world's most advanced high-frequency radiotelegraph receiver — and, in 1936, the "noise-silencer" circuit for superheterodynes. During the war, thousands of skilled amateurs contributed their knowledge to the development of secret radio devices, both in Government and private laboratories. Equally as important, the prewar technical progress by amateurs provided the keystone for the development of modern military communications equipment.

Emergency relief, expedition contact, experimental work and countless instances of other forms of public service — rendered, as they always have been and always will be, without hope or expectation of material reward — made amateur radio an integral part of our peacetime national life. The importance

of amateur participation in the armed forces and in other aspects of national defense have emphasized more strongly than ever that amateur radio is vital to our national existence.

¶ The American Radio Relay League

The ARRL is today not only the spokesman for amateur radio in this country but it is the largest amateur organization in the world. It is strictly of, by and for amateurs, is noncommercial and has no stockholders. The members of the League are the owners of the ARRL and *QST*.

The League is organized to represent the amateur in legislative matters. It is pledged to promote interest in two-way amateur communication and experimentation. It is interested in the relaying of messages by amateur radio. It is concerned with the advancement of the radio art. It stands for the maintenance of fraternalism and a high standard of conduct. One of its principal purposes is to keep amateur activities so well conducted that the amateur will continue to justify his existence.

The operating territory of ARRL is divided into fourteen U. S. and six Canadian divisions. The affairs of the League are managed by a Board of Directors. One director is elected every two years by the membership of each U. S. division, and a Canadian General Manager is elected every two years by the Canadian membership. These directors then choose the president and vice-president, who are also members of the Board. The managing secretary, treasurer and communications manager are appointed by the Board.

ARRL owns and publishes the monthly magazine, *QST*. Acting as a bulletin of the League's organized activities, *QST* also serves as a medium for the exchange of ideas and fosters amateur spirit. Its technical articles are renowned. It has grown to be the "amateur's bible," as well as one of the foremost radio magazines in the world. Membership dues include a subscription to *QST*.

ARRL maintains a model headquarters amateur station, known as the Hiram Percy Maxim Memorial Station, in Newington, Conn. Its call is W1AW, the call held by Mr. Maxim until his death and later transferred to the ARRL station by a special FCC action. Separate transmitters of maximum legal power on each amateur band have permitted the station to be heard regularly all over the world.

Among its other activities the League maintains, at its headquarters offices in West Hartford, Conn., a Communications Department concerned with the operating activities of League members. A large field organization is headed by a Section Communications Manager in each of the country's seventy-one sections. There are appointments for qualified members as Official Relay Station or Official Phone Station for traffic-handling; as Official Observer for monitoring frequencies and the quality of signals; as Route Manager and

'Phone Activities Manager for the establishment of trunk lines and networks; as Emergency Coördinator for the promotion of amateur preparedness to cope with natural disasters. Mimeographed bulletins keep appointees informed of the latest developments. Special activities and contests promote operating skill and thereby add to the ability of amateur radio to function "in the public interest, convenience and necessity." A special section is reserved each month in *QST* for amateur news from every section of the country.

☐ Amateur Licensing in the United States

The Communications Act lodges in the Federal Communications Commission authority to classify and license radio stations and to prescribe regulations for their operation. Pursuant to the law, FCC has issued detailed regulations for the amateur service.

A radio amateur is a duly authorized person interested in radio technique solely with a personal aim and without pecuniary interest. Amateur operator licenses are given to U. S. citizens who pass an examination on operation and apparatus and on the provisions of law and regulations affecting amateurs, and who demonstrate ability to send and receive code at 13 words per minute. Station licenses are granted only to licensed operators and permit communication between such stations for amateur purposes, i. e., for personal noncommercial aims flowing from an interest in radio technique. An amateur station may not be used for material compensation of any sort nor for broadcasting. Narrow bands of frequencies are allocated exclusively for use by amateur stations. Transmissions may be on any frequency within the assigned bands. All the frequencies may be used for c. w. telegraphy and some are available for radio-telephony by any amateur, while others are reserved for radiotelephone use by persons having at least a year's experience and who pass the examination for a Class A license. The input to the final stage of amateur stations is limited to 1,000 watts and on frequencies below 60 Mc. must be adequately filtered direct current. Emissions must be free from spurious radiations. The licensee must provide for measurement of the transmitter frequency and establish a procedure for checking it regularly. A complete log of station operation must be maintained, with specified data. The station license also authorizes the holder to operate portable and portable-mobile stations on certain frequencies, subject to further regulations. An amateur station may be operated only by an amateur operator licensee, but any licensed amateur operator may operate any amateur station. All radio licensees are subject to penalties for violation of regulations.

Amateur licenses are issued entirely free of charge. They can be issued only to citizens but that is the only limitation, and they are given without regard to age or physical condition to

anyone who successfully completes the examination. When you are able to copy 13 words per minute, have studied basic transmitter theory and are familiar with the law and amateur regulations, you are ready to give serious thought to securing the Government amateur licenses which are issued you, after examination at a local district office, through FCC at Washington. A complete up-to-the-minute discussion of license requirements, and a study guide for those preparing for the examination, are to be found in an ARRL publication, *The Radio Amateur's License Manual*, available from the American Radio Relay League, West Hartford 7, Conn., for 25¢, postpaid.

☐ The Amateur Bands

During May, 1945, FCC announced its final determination of postwar frequency allocations above 25 Mc. in which certain alterations and additions to prewar amateur frequencies were made. Similarly, the Commission announced proposed changes below 25 Mc. and these changes are still under consideration as this is being written in October, 1945. The Commission's final recommendations for the region below 25 Mc. are then subject to further consideration at the next international conference. Since further changes may be instituted, it is suggested that the reader consult subsequent issues of *QST* or write ARRL for the latest information.

As of our press date, the prospective postwar amateur bands are the following:

3,500-4,000 kc.	50-54 Mc.	2,300-2,450 Mc.
7,000-7,300 "	144-148 "	5,250-5,650 "
14,000-14,400 "	220-225 "	10,000-10,500 "
21,000-21,500 "	420-450 "	21,000-22,000 "
28,000-29,700 "	1,215-1,295 "	

In addition it is expected that the amateur, along with other services, will be given non-exclusive rights to operate in the frequencies 1750-1800 kc. solely for the maintenance of emergency networks and the necessary tests and drills incident thereto; and the right to make such use as is possible of the frequencies 27,185-27,455 kc., assigned to scientific, industrial and medical uses.

It must be understood that the proposed 21-Mc. band is not likely to be made available until after the agreement of the next worldwide conference, possibly effective in 1947.

Finally, it should be carefully noted that, as of this writing, the position of amateur radio is that of being gradually released from wartime restrictions, band by band. These are the amateur bands, but our rights to operate on them are being restored band by band, as our frequencies are released to us by the military services. Also, certain portions of these bands are normally open to 'phone operation and the portions so allocated are customarily varied from time to time in accordance with changes in amateur operational habits. Hence each amateur must keep himself currently informed on what bands are authorized.

Electrical and Radio Fundamentals

2-1 FUNDAMENTALS OF A RADIO SYSTEM

THE BASIS of radio communication is the transmission of electromagnetic waves through space. The production of suitable waves constitutes radio transmission, and their detection, or conversion at a distant point into the intelligence put into them at the originating point, is radio reception. There are several distinct processes involved in the complete chain. At the transmitting point, it is necessary first to generate power in such form that when it is applied to an appropriate radiator, called the *antenna*, it will be sent off into space in electromagnetic waves. The message to be conveyed must be superimposed on that power by suitable means, a process called *modulation*.

As the waves spread outward from the transmitter they rapidly become weaker, so at the receiving point an antenna is again used to abstract as much energy as possible from them as they pass. The wave energy is transformed into an electric current which is then amplified, or increased in amplitude, to a suitable value. Then the modulation is changed back into the form it originally had at the transmitter. Thus the message becomes intelligible.

Since all these processes are performed by electrical means, a knowledge of the basic principles of electricity is necessary to understand them. These essential principles are the subject of the present chapter.

2-2 THE NATURE OF ELECTRICITY

Electrons — All matter — solids, liquids and gases — is made up of fundamental units called *molecules*. The molecule, the smallest subdivision of a substance retaining all its characteristic properties, is constructed of *atoms* of the elements comprising the substance.

Atoms in turn are made up of particles, or charges, of electricity, and atoms differ from each other chiefly in the number and arrangement of these charges. The atom has a nucleus containing both "positive" and "negative" charges, with the positive predominating so that the nature of the nucleus is positive. The charges in the nucleus are closely bound together. Exterior to the nucleus are negative charges — *electrons* — some of which are not so closely bound and can be made to leave the vicinity of the nucleus without too much urging. These electrons whirl around the nucleus like the planets around the sun, and their orbits are not random paths but geometrically-regular ones determined by the charges on the

nucleus and the number of electrons. Ordinarily the atom is electrically neutral, the outer negative electrons balancing the positive nucleus, but when something disturbs this balance electrical activity becomes evident, and it is the study of what happens in this unbalanced condition that makes up electrical theory.

Electrons are exceedingly small particles — so small that many billions of them must act together before measurable electrical effects are observed.

Insulators and Conductors — Materials which will readily give up an electron are called *conductors*, while those in which all the electrons are firmly bound in the atom are called *insulators*. Most metals are good conductors, as are also acid or salt solutions. Among the insulators are such substances as wood, hard rubber, bakelite, quartz, glass, porcelain, textiles, and many other non-metallic materials.

Resistance — No substance is a perfect conductor — a "perfect" conductor would be one in which an electron could be detached from the atom without the expenditure of energy — and there is also no such thing as a perfect insulator. The measure of the difficulty in moving an electron by electrical means is called *resistance*. Good conductors have low resistance, good insulators very high resistance. Between the two are materials which are neither good conductors nor good insulators, but they are nonetheless useful since there is often need for intermediate values of resistance in electrical circuits.

Conduction — Under the influence of a suitable force — that is, an electric *field* — electrons tend to move. If the substance is one in which electrons can be detached from atoms as explained above, these electrons will move through the substance. This is the process of *conduction*, and the moving electrons constitute an electric *current*. The intensity of the current depends upon the amount of force exerted on the electrons, and also upon the resistance of the material through which they are moving.

Strictly speaking, this description applies only to conduction through solid substances. However, conduction in liquids and gases, although different in detail, is similar in principle. These cases are treated later in chapter.

Circuits — A circuit is simply a complete path along which electrons can transmit their charges. There will normally be a source of energy (a battery, for instance) and a *load* or portion of the circuit where the current is made to do work. There must be an unbroken path

through which the electrons can move, with the source of energy acting as an electron pump and sending them around the circuit. The circuit is said to be *open* when no charges can move, because of a break in the path. It is *closed* when no break exists — when switches are closed and all connections are made.

2-3 Static Electricity

The electric charge — Many materials that have a high resistance can be made to acquire a charge (surplus or deficiency of electrons) by mechanical means, such as friction. The familiar crackling when a hard-rubber comb is run through hair on a dry winter day is an example of an electric charge generated by friction. Objects can have either a surplus or a deficiency of electrons — a surplus of electrons is called a *negative* charge; a lack of them is called a *positive* charge. The kind of charge is called its *polarity*. A negatively charged object is frequently called a *negative pole*, while a positively charged object similarly is called a *positive pole*.

Attraction and repulsion — Unlike charges (one positive, one negative) exert an attraction on each other. This can be demonstrated by giving charges of opposite polarity to two very light, well-insulated conductors, such as bits of metal foil suspended from dry thread (Fig. 201). Pith balls covered with foil frequently are used in this experiment.

When the two charged objects are brought close together, it will be observed that they will be attracted to each other. If the charges are equal and the charged bodies are permitted to touch, the surplus electrons on the negatively charged object will transfer to the positively charged object (i.e., the one deficient in electrons) and the two charges will neutralize,

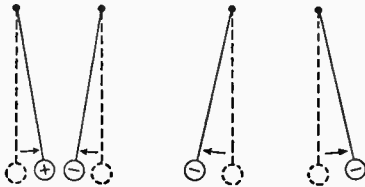


Fig. 201 — Attraction and repulsion of charged objects, as demonstrated by the familiar pith-ball experiment.

leaving both bodies uncharged. If the charges are not equal, the weaker charge neutralizes an equal amount of the stronger when the two bodies touch, upon which the excess of the stronger charge distributes itself over both. Both bodies then have charges of the same polarity, and a force of repulsion is exercised between them. Consequently, the bits of foil tend to spring away from each other. *Unlike charges attract, like charges repel.*

Electrostatic field — From the foregoing it is evident that an electric charge can exert a force through the space surrounding the charged object. The region in which this force is exerted is considered to be pervaded by an

electrostatic field, this concept of a field being adopted to explain the "action at a distance" of the charge. The field is pictured as consisting of *lines of force* originating on the charge and

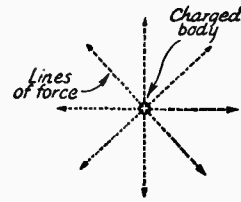


Fig. 202 — Lines of force from a charged object extend outward radially. Although only two dimensions are shown, the field extends in all directions from the charge, and should be visualized in three dimensions.

spreading in all directions, finally terminating on other charges of opposite polarity. These other charges may be a very large distance away. The number of lines of force per unit area is, however, a measure of the intensity of the field.

The general picture of a charged object in isolated space is shown in Fig. 202. This is an idealized situation, since in practice the charged object could not be completely isolated. The presence of other charges, or simply of insulators or conductors, in the vicinity will greatly change the configuration of the field. The direction of the field, as indicated by the arrowheads, is away from a positively charged object; if the charge were negative, the direction would be toward the charge.

It should be understood that the field picture as represented above is merely a convenient method of explaining observed effects, and is not to be taken too literally. The electric force does not consist of separate lines like strings or rods; instead, it completely pervades the medium through which the force is exerted. With this understanding in mind, it is *convenient* to talk of lines of force and to measure the field intensity in terms of number of lines per unit area.

The intensity of the field dies away with distance from the charged object in a manner determined by its shape and the circumstances of its surroundings. In the case of an isolated charge at a point (an infinitesimally small object), the field strength is inversely proportional to the square of the distance. However, this relationship is not true in many other cases; in some important practical applications the field intensity is inversely proportional to the distance involved, and not to its square.

Electrostatic induction — If a piece of conducting material is brought near a charged object, the field will exert a force on the electrons of the metal so that those free to move will do so. If the object is positively charged, as indicated in Fig. 203, the free electrons will move toward the end of the conductor nearest the charged body, leaving a deficiency of electrons at the other end. Hence, one end of the

conductor becomes negatively charged while the other end has an equal positive charge. The lines of force from the charged body terminate on the conductor, where sufficient electrons accumulate to provide an electric intensity equal and opposite to that of the field at that point. Because of this effect, the electrostatic field inside the conductor is completely neutralized by the induced charge; in other words, the field does not penetrate the conductor. In radio work this principle provides the means by which electrostatic fields may be excluded from regions where they are not wanted.

Charges induced in a conductor as shown in Fig. 203-A are held in existence by the field from the charged object. On taking the conductor out of the field the electrons will redistribute themselves so that the charges disappear. However, if the conductor is connected to the earth through a wire while under the influence of the field, as shown in Fig. 203-B, the induced positive charge will tend to move as far as possible from the source of the field (that is, electrons will flow from the earth to the conductor). If the grounding wire is then removed, the conductor will be left with an excess of electrons and will have acquired a "permanent" charge — permanent, that is, so long as the conductor is well enough insulated to prevent the charge from escaping to earth or to other objects. The polarity of the induced charge always is opposite to the polarity of the charge which set up the original field.

Energy in the electrostatic field — The expenditure of energy is necessary to place an electrical charge upon an object and thus establish an electrostatic field. Once the field is established and is constant, no further expenditure of energy is required. The energy supplied to establish the field is stored in the field; thus the field represents *potential* energy (that is, energy available for use). The potential energy is acquired in the same way that potential energy is given any object (a 10-pound weight, for instance) when it is lifted against the gravitational pull of the earth. If

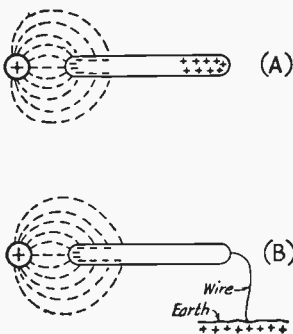


Fig. 203 — Electrostatic induction. The field from the positively charged body attracts electrons, which accumulate to form a negative charge. The opposite end of the conductor consequently acquires a positive charge. This charge may be "drained off" to earth as shown at B.

the weight is allowed to drop, its potential energy is changed into the energy of motion. Similarly, if the electrostatic field is made to disappear its potential energy is transformed into a movement of electrons; in other words, into an electric current.

The potential energy of the lifted weight is measured by its weight and the distance it is lifted; that is, by the work done in lifting it. Similarly, the potential energy (called simply *potential*) of the electrostatic field at any point is measured by the work done in moving a charge of specified value to that point, against the repulsion of the field. In practice, absolute potential is of less interest than the *difference of potential* between two points in the field.

Potential difference — If two objects are charged differently, a potential difference exists between them. Potential difference is measured by an electrical unit called the *volt*. The greater the potential difference, the higher (numerically) the voltage. This voltage exerts an electrical pressure or *force* as explained above, and is often called *electromotive force* or, simply, *e.m.f.* It is not necessary to have unlike charges in order to have a difference of potential; both, for instance, may be negative, so long as one charge is more intense than the other. From the viewpoint of the stronger charge, the weaker one appears to be positive in such a case, since it has a smaller number of excess electrons; in other words, its *relative polarity* is positive. The greater the potential difference, the more intense is the electrostatic field between the two charged objects.

Capacity — More work must be done in moving a given charge against the repulsion of a strong field than against a weak one; hence, potential is proportional to the strength of the field. In turn, field strength is proportional to the charge or quantity of electricity on the charged object, so that potential also is proportional to charge. By inserting a suitable constant, the proportionality can be changed to an equality:

$$Q = CE$$

where Q is the quantity of charge, E is the potential, and C is a constant depending upon the charged object (usually a conductor) and its surroundings and is called the *capacity* of the object. Capacity is the ratio of quantity of charge to the potential resulting from it, or

$$C = \frac{Q}{E}$$

When Q is in coulombs and E in volts, C is measured in *farads*. A conductor has a capacity of one farad when the addition of one coulomb to its charge raises its potential by one volt.

The farad is much too large a unit for practical purposes. In radio work, the *microfarad* (one millionth of a farad) and the *micro-microfarad* (one millionth of a microfarad) are the units most frequently used. They are abbreviated $\mu fd.$ and $\mu\mu fd.$, respectively.

The capacity of a conductor in air depends upon its size and shape. A given charge on a small conductor results in a more intense electrostatic field in its vicinity than the same charge on a larger conductor. This is because the charge distributes itself over the surface, hence its density (the quantity of electricity per unit area) is smaller on the larger conductor. Consequently, the potential of the larger conductor is smaller, for the same amount of charge. In other words, its capacity is greater because a greater charge is required to raise its potential by the same amount.

Condensers — If a grounded conductor, *A* (Fig. 204), is brought near a second conductor, *B*, which is charged, the former will acquire a charge by electrostatic induction. Since the charge on *A* is opposite in polarity to that on *B*, the field set up by the induced charge on *A* will oppose the original field set up by the charge on *B*, hence the potential of *B* will be lowered. Because of this, more charge must be placed on *B* to raise its potential to its original value; in other words, its capacity has been increased by the presence of the second conductor. The combination of the two conductors separated by a dielectric is called a *condenser*.

The capacity of a condenser depends upon the areas of the conductors, as before, and also becomes greater as the distance between the conductors is decreased, since, with a fixed amount of charge, the potential difference between them decreases as they are moved closer together.

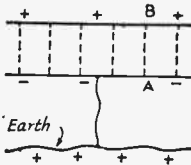


Fig. 204 — The principle of the condenser.

If insulating or dielectric material other than air is inserted between the conductors, it is found that the potential difference is lowered still more — that is, there is a further increase in capacity. This lowering of the potential difference is considered to be the result of *polarization* of the dielectric. By this it is meant that the molecules of the substance tend to be distorted under the influence of the electrostatic field in such a way that the negative charges within the molecule are drawn toward the positively charged conductor, leaving the other end of the molecule with a positive charge facing the negatively charged conductor. Since the electrons are firmly bound in the atoms of the dielectric, there is no flow of current and the total charge on each atom is still zero, but there is a *tendency* toward separation which causes a reaction on the electrostatic field. The dielectric of a charged condenser thus is under mechanical stress, and if the potential difference between the plates of the condenser is

great enough the dielectric may break down mechanically and electrically.

The ratio of the capacity of a condenser with a given dielectric material between its plates to the capacity of the same condenser with air as a dielectric is called the *specific inductive capacity* of the dielectric, or, probably more commonly, the *dielectric constant*. Strictly speaking, the comparison should be made to empty space (i.e., a vacuum) rather than to air, but the dielectric constant of air is so nearly that of a vacuum that the practical difference is negligible. A table of dielectric constants is given in Chapter Twenty.

Condensers have many uses in electrical and radio circuits, all based on their ability to store energy in the electric field when a potential difference or voltage is caused to exist between the plates — energy which later can be released to perform useful functions.

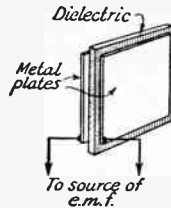


Fig. 205 — A simple condenser, consisting of two metal plates separated by dielectric material.

§ 2-4 The Electric Current

Conduction in metals — When a difference of potential is maintained between the ends of a metallic conductor, there is a continuous drift of electrons through the conductor toward the end having a positive potential (relative polarity positive). This electron drift constitutes an electric current through the metal (§ 2-2). The speed with which the electron movement is established is very nearly the speed of light (300,000,000 meters, or approximately 186,000 miles, per second), so that the current is said to travel at nearly the speed of light. By this it is meant that the time interval between the application of the electromotive force and the flow of current in all parts of a circuit, even one extending over hundreds of miles, is negligible. However, the individual electrons do not move at anything approaching such a speed. The situation is similar to that existing when a mechanical force is transmitted by means of a rigid rod. A force applied to one end of the rod is transmitted practically instantaneously to the other end, even though the rod itself moves relatively slowly or not at all.

The magnitude of the electric current is the rate at which electricity is moved past a point in the circuit. If the rate is constant, then the current is equal to the quantity of electricity moved past a given point in some selected time interval. That is,

$$I = \frac{Q}{t}$$

where I is the intensity or magnitude of the current, Q is the quantity of electricity, and t is the time. If Q is in coulombs and t in seconds, the unit for I is called the *ampere*. One ampere of current is equal to one coulomb of electricity moving or "flowing" past a given point in a circuit in one second.

The currents used by different electrical devices vary greatly in magnitude. The current which flows in an ordinary 60-watt lamp, for instance, is about one-half ampere, the current in an electric iron is about 5 amperes, and that in a radio tube may be as low as 0.001 ampere.

When a current flows through a metallic conductor there is no visible or chemical effect on the conductor. The only physical effect is the heat developed (§ 2-2) as the result of energy loss in the conductor. Under normal conditions the rate at which heat is generated and that at which it is radiated by the conductor will quickly reach equilibrium. However, if the heat is developed at a more rapid rate than it can be radiated, the temperature will continue to rise until the conductor burns or melts.

Experimental measurements have shown that the current which flows in a given metallic conductor is directly proportional to the applied e.m.f., so long as the temperature of the conductor is held constant. There is no e.m.f. so small but that some current will flow as a result of its application to a metallic conductor.

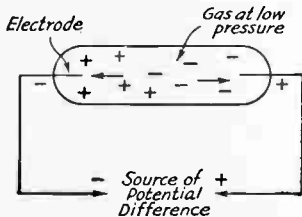


Fig. 266 — Illustrating conduction through a gas at low pressure. Positive ions are attracted to the negative electrode, while electrons are attracted to the positive electrode. This takes place only after the gas is ionized.

Caseous conduction — In any gas or mixture of gases (such as air, for example) there are always some free electrons — that is, electrons not attached to an atom — and also some atoms lacking an electron. Thus there are both positively and negatively charged particles in the gas, as well as many neutral atoms. An atom lacking an electron is called a *positive ion*, while the free electron is called a *negative ion*. The term *ion* is, in fact, applied to any elemental particle which has an electric charge.

If the gas is in an electric field, the free electrons will be attracted toward the source of positive potential and the positive ions will be attracted toward the source of negative potential. If the gas is at atmospheric pressure neither particle can travel very far before meeting an ion of the opposite kind, when the two combine to form a neutral atom. Since a neutral atom is not affected by the electric field, there is no flow of current through the gas.

However, if the gas is enclosed in a glass container in which two separate metal pieces called *electrodes* are sealed, and the gas pressure is then reduced by pumping out most of the gas, a different set of conditions results. At low pressure there is a comparatively large distance between each atom, and when an electric field is established by applying a difference of potential to the electrodes the ions can travel a considerable distance before meeting another ion or atom. The farther the ion travels the greater the velocity it acquires, since the effect of the field is to accelerate its motion. If the field is strong enough the ions will acquire such velocity that when one happens to collide with a neutral atom the force of the collision will knock an electron out of the atom, so that this atom also becomes *ionized*. The process is cumulative, and the freed electrons are attracted to the positive electrode while the positive ions are attracted to the negative electrode. This movement of charged particles constitutes an electric current through the gas.

Since an ion must acquire a certain velocity before it can knock an electron out of a neutral atom, a definite field strength is required before conduction can take place in a gas. That is, a certain value of potential difference, called the *ionizing potential*, must be applied to the electrodes. If less voltage is applied, the gas does not ionize and the current is negligible. On the other hand, once the gas is ionized an increase in potential does not have much effect on the current, since the ions already have sufficient velocity to maintain the ionization. The ionizing potential required depends upon the kind of gas and the pressure. Ionization is usually accompanied by a colored glow, different gases having different characteristic colors.

Current flow in liquids — A very large number of chemical compounds have the peculiar characteristic that, when they are put into solution, the component parts become ionized. For example, common table salt (sodium chloride), each molecule of which is made up of one atom of sodium and one of chlorine, will, when put into water, break down into a sodium ion (positive, with one electron deficient) and a chlorine ion (negative, with one excess electron). This can only occur so long as the salt is in solution — take away the

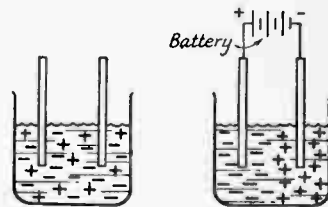


Fig. 207 — Electrolytic conduction. When an e.m.f. is applied to the electrodes, negative ions are attracted to the positively charged plate and positive ions to the negatively charged plate. The battery, which is the source of the e.m.f., is indicated by its customary symbol.

water and the ions are recombined into the neutral sodium chloride. This spontaneous *dissociation* in solution is another form of ionization. If two wires with a difference of potential between them are placed in the solution, the negative wire will attract the positive sodium ions while the positive wire will attract the negative chlorine ions and an electric current will flow through the solution. When the ions reach the wires the electron surplus or deficiency will be remedied, and a neutral atom will be formed.

In this process, the water is decomposed into its gaseous constituents, hydrogen and oxygen. The energy used up in decomposing the water and in moving the ions is supplied by the source of potential difference. The energy used in decomposing the water is equivalent to an opposing e.m.f., of the order of a volt or two. If this constant "back voltage" is subtracted from the applied voltage, it is found that the current flowing through a given solution, or *electrolyte*, is proportional to the difference between the two voltages.

Current flow in vacuum — If a suitable metallic conductor is heated to a high temperature in a vacuum, electrons will be emitted from the surface. The electrons are freed from this *filament* or *cathode* because it has been

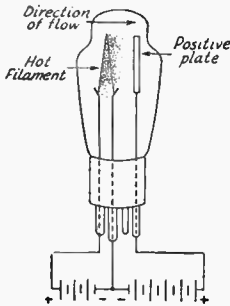


Fig. 208 — Conduction by thermionic emission in a vacuum tube. One battery is used only to heat the filament to a temperature where it will emit electrons. The other battery places a potential on the plate which is positive with respect to the filament, and as a result the electrons are attracted to the plate. The electron flow from filament to plate completes the circuit.

heated to a temperature that gives them sufficient energy of motion to allow them to break away from the surface. The process is called *thermionic electron emission*. Now, if a metal plate is placed in the vacuum and given a positive charge with respect to the cathode, this plate or *anode* will attract a number of the electrons that surround the cathode. The passage of the electrons from cathode to anode constitutes an electric current. All thermionic vacuum tubes depend for their operation on the emission of electrons from a hot cathode.

Since the electrons emitted from the hot cathode are negatively charged, it is evident that they will be attracted to the plate only when the latter is at a positive potential with respect to the cathode. If the plate is negatively charged with respect to the cathode the electrons will be repelled back to the cathode, hence no current will flow through the vacuum. Consequently, a thermionic vacuum tube conducts current *in one direction only*. When the plate is positive, it is found that (if the poten-

tial is not too large) the current increases with an increase in potential difference between the plate and cathode. However, the relationship between current and applied voltage is not a simple one. If the voltage is made large enough all the electrons emitted by the cathode will be drawn to the plate, and a further increase in voltage therefore cannot cause a further increase in current. The number of electrons emitted by the cathode depends upon the temperature of the cathode and the material of which it is constructed.

Direction of current flow — Use was being made of electricity for a long time before its electronic nature was understood. While it is now clear that current flow is a drift of negative electrical charges or electrons toward a source of positive potential, in the era preceding the electron theory it was *assumed* that the current flowed from the point of higher positive potential to a point of lower (i.e., less positive or more negative) potential. While this assumption turned out to be wholly wrong, it is still customary to speak of current as flowing "from positive to negative" in many applications. The practice often causes confusion, but this distinction between "current" flow and "electron" flow often must be taken into account. If electron flow is specifically mentioned there can be, of course, no doubt as to the meaning; but when the direction of *current* flow is specified, it may be taken, by convention, as being opposite to the direction of electron movement.

Primary cells — If two electrodes of dissimilar metals are immersed in an electrolyte, it is found that a small difference of potential exists between the electrodes. Such a combination is called a *cell*. If the two electrodes are connected together by a conductor external to the cell, an electric current will flow between them. In such a cell, chemical energy is converted into electrical energy. The difference of potential arises as a result of the fact that material from one or both of the electrodes goes into solution in the electrolyte, and in the process ions are formed in the vicinity of the electrodes. The electrodes acquire charges because of the electric field associated with the charged ions. The difference of potential between the electrodes is principally a function of the metals used, and is more or less independent of the kind of electrolyte or the size of the cell.

When current is supplied to an external circuit, two principal effects occur within the cell. The negative electrode (negative as viewed from outside the cell) loses weight as its material is used up in furnishing energy, and hydrogen bubbles form on the positive electrode. Since the gas bubbles are non-conducting, their accumulation tends to reduce the effective area of the positive electrode, and consequently reduces the current. The effect is cumulative, and eventually the electrode will be completely covered and no further current can flow. This effect is called *polarization*. If the bubbles are

removed, or prevented from forming by chemical means, polarization is reduced and current can flow as long as there is material in the negative electrode to furnish the energy. A chemical which prevents the formation of hydrogen bubbles in a cell is called a *depolarizer*.

In addition to polarization effects, a cell has a certain amount of *internal resistance* because of the resistance of the electrodes and the electrolyte and the contact resistance between the electrodes and electrolyte. The internal resistance depends upon the materials used and the size and electrode spacing of the cell. Large cells with the electrodes close together will have smaller internal resistance than small cells made of the same materials.

A collection of cells connected together is called a *battery*. The term battery also is applied (although incorrectly) to a single cell.

Dry cells—The most familiar form of primary cell is the *dry cell*. Like the elementary type of cell just described, it has a liquid electrolyte, but the liquid is mixed with other materials to form a paste. The cell therefore can be used in any position and handled as though it actually were dry.

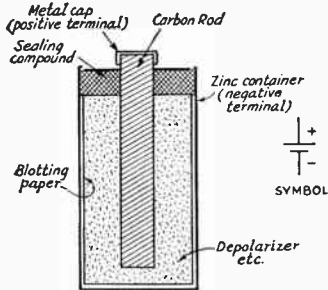


Fig. 209 — Construction of a dry cell.

The construction of an ordinary dry cell is shown in Fig. 209. The container is the negative electrode and is made of zinc. Next to it is a section of blotting material saturated with the electrolyte, a solution of sal ammoniac. The positive electrode is a carbon rod, and the space between it and the blotting paper is filled with a mixture of carbon, manganese dioxide (the depolarizer) and the electrolyte. The top is filled with sealing compound to prevent evaporation, since the cell will not work when the electrolyte dries out. The e.m.f. of a dry cell is about 1.5 volts.

Dry cells are made in various sizes, depending upon the current which they will be called upon to furnish. The construction frequently varies from that shown in Fig. 209, although in general the basic materials are the same in all dry cells. Batteries of small cells are assembled together as a unit for furnishing plate current for the vacuum tubes used in portable receiving sets; such "B" batteries, as they are called, can supply a current of a few hundredths of an ampere continuously. Larger cells, such as the common "No. 6" cell, can deliver currents of a fraction of an ampere con-

tinuously, or currents of several amperes for very short periods of time. The total amount of energy delivered by a dry cell is larger when the cell is used only intermittently, as compared with continuous use. The cell will deteriorate even without use, and should be put into service within a year or so from the time it is manufactured. The period during which it is usable (without having been put in service) is known as the "shelf life" of the cell or battery.

Secondary cells—The types of cells just described are known as *primary cells*, because the electrical energy is obtained directly from chemical energy. In some types of cells the chemical actions are reversible; that is, forcing a current through the cell, in the opposite direction to the current flow when the cell is delivering electrical energy, causes just the reverse chemical action. This tends to restore the cell to its original condition, and electrical energy is transformed into chemical energy. The process is called *charging* the cell. A cell which must first be charged before it can deliver electrical energy is called a *secondary cell*.

A simple form of secondary cell can be made by immersing two lead electrodes in a dilute solution of sulphuric acid. If a current is forced through the cell, the surface of the electrode which is connected to the positive terminal of the charging e.m.f. will be changed to lead peroxide and the surface of the electrode connected to the negative terminal will be changed to spongy lead. After a period of charging the charging source can be disconnected, and the cell will be found to have an e.m.f. of about 2.1 volts. It will furnish a small current to an external circuit for a period of time. This *discharge* of electrical energy is accompanied by chemical action which forms lead sulphate on both electrodes. When the lead peroxide and spongy lead are converted to lead sulphate there is no longer a difference of potential, since both electrodes are now the same material, and the cell is completely discharged.

The lead storage battery—The most common form of secondary cell is the lead storage cell. The common storage battery for automobile starting consists of three such cells connected together electrically and assembled in a single container. The principle of operation is similar to that just described, but the construction of the cell is considerably more complicated. To obtain large currents it is necessary to use electrodes having a great deal of surface area and to put them as close together as possible. The electrodes are made in the form of rectangular flat plates, consisting of a latticework or grid of lead or an alloy of lead. The interstices of the latticework are filled with a paste of lead oxide. The electrolyte is a solution of sulphuric acid in water. When the cell is charged, the lead oxide in the positive plate is converted to lead peroxide and that in the negative plate to spongy lead. To obtain high current capacity, a cell consists of a number of positive plates, all connected together,

If a bar magnet is cut in half, as in Fig. 213-B, it is found that the cut ends also are poles, of opposite kind to the original poles on the same piece. Such cutting can be continued indefinitely, and, no matter how small the pieces are made, there are always two opposite poles associated with each piece. In other words, a single magnetic pole cannot exist alone; it must always be associated with a pole of the opposite kind.

To explain this property of a magnet, it is considered that each molecule of a magnetic substance is itself a miniature magnet. If the material is not magnetized, the molecules are in random positions and the total magnetic effect is zero since there are just as many molecules tending to set up a magnetic field in one direction as there are others tending to set up a field in the opposite direction. When the substance becomes magnetized, however, the molecules are aligned so that most or all of the *N* poles of the molecular magnets are turned toward one end of the material while the *S* poles point toward the other end.

Magnetic induction — When an unmagnetized piece of iron is brought into the field of a magnet, its molecules tend to align themselves as described in the preceding paragraph. If one end of the iron is near the *N* pole of the magnet, the *S* poles of the molecules will turn toward that end and an *S* pole is said to be *induced* in the iron. An *N* pole will appear at the opposite end. Because of the attraction between opposite poles, the iron will be drawn toward the magnet. Since the iron has become a magnet under the influence of the field, it also possesses the property of attracting other pieces of iron.

When the magnetic field is removed, the molecules may or may not resume their random positions. If the material is soft iron the magnetism disappears quite rapidly when the field is removed, but in some types of steel the molecules are slow to resume their random positions and such materials will retain magnetism for a long time. A magnet which loses its magnetism quickly when there is no external magnetizing force is called a *temporary magnet*, while one which retains its magnetism for a long time is called a *permanent magnet*. The tendency to retain magnetism is called *retentivity*. The process of destroying magnetism can be hastened by heating, which increases the motion of the molecules within the substance, as well as by mechanical shock, which also tends to disturb the molecular alignment.

Electric current and the magnetic field — Experiment shows that a moving electron generates a magnetic field of exactly the same nature as that existing about a permanent magnet. Since a moving electron, or group of electrons moving together, constitutes an electric current, it follows that the flow of current is accompanied by the creation of a magnetic field. When the conductor is a wire the magnetic lines of force are in the form of concentric

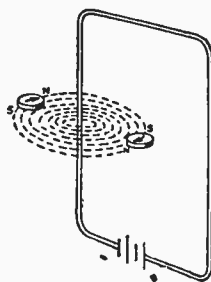


Fig. 214 — Whenever electric current passes through a wire, magnetic lines of force are set up, in the form of concentric circles, at right angles to the wire, and a magnetic field is said to exist around the wire. The direction of this field is controlled by the direction of current flow, and can be traced by means of a small compass.

circles around it and lie in planes at right angles to it, as shown in Fig. 214. The direction of this field is controlled by the direction of current flow.

There is an easily remembered method for finding the relative directions of the current and of the magnetic field it sets up. Imagine the fingers of the right hand curled about the wire, with the thumb extended along the wire in the direction of current flow (the conventional direction, from positive to negative, not the direction of electron movement). Then the fingers will be found to point in the direction of the magnetic field; that is, from *N* to *S*.

Magnetomotive force — The force which causes the magnetic field is called *magnetomotive force*, abbreviated *m.m.f.* It corresponds to electromotive force or e.m.f. in the electric circuit. The greater the magnetomotive force, the stronger the magnetic field; that is, the larger the number of magnetic lines per unit area. Magnetomotive force is proportional to the current flowing. When the wire carrying the current is formed into a coil so that the magnetic flux will be concentrated instead of being spread over a large area, the *m.m.f.* also is proportional to the number of turns in the coil. Consequently magnetomotive force can be expressed in terms of the product of current and turns, and the *ampere-turn*, as this product is called, is in fact the common unit of magnetomotive force. The same magnetizing effect can be secured with a great many turns and a weak current or with a few turns and a strong current. For example, if 10 amperes flow in one turn of wire, the magnetizing effect is 10 ampere-turns. If there is one ampere flowing in 10 turns of wire, the magnetomotive force also is 10 ampere-turns.

The magnetic circuit — Since magnetic lines of force are always closed upon themselves, it is possible to draw an analogy between the magnetic circuit and the ordinary electrical circuit. The electrical circuit also must be closed so that a complete path is provided around which the electrons or current can flow. However, there is no insulator for the magnetic field, so that the magnetic circuit is always complete even though no magnetic material (such as iron) may be present.

The number of lines of magnetic force, or *flux*, is equivalent in the magnetic circuit to current in the electric circuit. However, it is

removed, or prevented from forming by chemical means, polarization is reduced and current can flow as long as there is material in the negative electrode to furnish the energy. A chemical which prevents the formation of hydrogen bubbles in a cell is called a *depolarizer*.

In addition to polarization effects, a cell has a certain amount of *internal resistance* because of the resistance of the electrodes and the electrolyte and the contact resistance between the electrodes and electrolyte. The internal resistance depends upon the materials used and the size and electrode spacing of the cell. Large cells with the electrodes close together will have smaller internal resistance than small cells made of the same materials.

A collection of cells connected together is called a *battery*. The term battery also is applied (although incorrectly) to a single cell.

Dry cells—The most familiar form of primary cell is the *dry cell*. Like the elementary type of cell just described, it has a liquid electrolyte, but the liquid is mixed with other materials to form a paste. The cell therefore can be used in any position and handled as though it actually were dry.

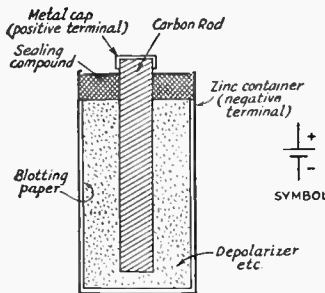


Fig. 209—Construction of a dry cell.

The construction of an ordinary dry cell is shown in Fig. 209. The container is the negative electrode and is made of zinc. Next to it is a section of blotting material saturated with the electrolyte, a solution of sal ammoniac. The positive electrode is a carbon rod, and the space between it and the blotting paper is filled with a mixture of carbon, manganese dioxide (the depolarizer) and the electrolyte. The top is filled with sealing compound to prevent evaporation, since the cell will not work when the electrolyte dries out. The e.m.f. of a dry cell is about 1.5 volts.

Dry cells are made in various sizes, depending upon the current which they will be called upon to furnish. The construction frequently varies from that shown in Fig. 209, although in general the basic materials are the same in all dry cells. Batteries of small cells are assembled together as a unit for furnishing plate current for the vacuum tubes used in portable receiving sets; such "B" batteries, as they are called, can supply a current of a few hundredths of an ampere continuously. Larger cells, such as the common "No. 6" cell, can deliver currents of a fraction of an ampere con-

tinuously, or currents of several amperes for very short periods of time. The total amount of energy delivered by a dry cell is larger when the cell is used only intermittently, as compared with continuous use. The cell will deteriorate even without use, and should be put into service within a year or so from the time it is manufactured. The period during which it is usable (without having been put in service) is known as the "shelf life" of the cell or battery.

Secondary cells—The types of cells just described are known as *primary cells*, because the electrical energy is obtained directly from chemical energy. In some types of cells the chemical actions are reversible; that is, forcing a current through the cell, in the opposite direction to the current flow when the cell is delivering electrical energy, causes just the reverse chemical action. This tends to restore the cell to its original condition, and electrical energy is transformed into chemical energy. The process is called *charging* the cell. A cell which must first be charged before it can deliver electrical energy is called a *secondary cell*.

A simple form of secondary cell can be made by immersing two lead electrodes in a dilute solution of sulphuric acid. If a current is forced through the cell, the surface of the electrode which is connected to the positive terminal of the charging e.m.f. will be changed to lead peroxide and the surface of the electrode connected to the negative terminal will be changed to spongy lead. After a period of charging the charging source can be disconnected, and the cell will be found to have an e.m.f. of about 2.1 volts. It will furnish a small current to an external circuit for a period of time. This *discharge* of electrical energy is accompanied by chemical action which forms lead sulphate on both electrodes. When the lead peroxide and spongy lead are converted to lead sulphate there is no longer a difference of potential, since both electrodes are now the same material, and the cell is completely discharged.

The lead storage battery—The most common form of secondary cell is the lead storage cell. The common storage battery for automobile starting consists of three such cells connected together electrically and assembled in a single container. The principle of operation is similar to that just described, but the construction of the cell is considerably more complicated. To obtain large currents it is necessary to use electrodes having a great deal of surface area and to put them as close together as possible. The electrodes are made in the form of rectangular flat plates, consisting of a latticework or grid of lead or an alloy of lead. The interstices of the latticework are filled with a paste of lead oxide. The electrolyte is a solution of sulphuric acid in water. When the cell is charged, the lead oxide in the positive plate is converted to lead peroxide and that in the negative plate to spongy lead. To obtain high current capacity, a cell consists of a number of positive plates, all connected together,

and a number of negative plates likewise connected together. They are arranged as shown in Fig. 210, with alternate negative and positive plates kept from touching by means of thin *separators* of insulating material, generally treated wood or perforated hard rubber. The separators preferably should be porous, so that the electrolyte can pass through them freely; thus they do not impede the passage of current from one plate to the next. There is always one extra negative plate in such an assembly, because the active material in the positive plate expands when the cell is being charged and if all the expansion took place on one side the plate would be distorted out of shape.

The e.m.f. of a fully charged storage cell is about 2.1 volts. When the e.m.f. drops to about 1.75 volts on discharge, the cell is considered to be completely discharged. Discharge beyond this limit may result in the formation of so much lead sulphate on the plates that the cell cannot be recharged, since lead sulphate is an insulator. During the charging process water in the electrolyte is used up, with the result that the sulphuric acid solution becomes more concentrated. The higher concentration increases the specific gravity of the solution, so that the specific gravity may be used to indicate the state of the battery with respect to charge. In the ordinary lead storage cell the solution is such that a specific gravity of 1.285 to 1.300 indicates a fully charged cell, while a discharged cell is indicated by a specific gravity of 1.150 to 1.175. The specific gravity can be measured by means of a *hydrometer*, shown in Fig. 211. For use with portable batteries, the hydrometer usually consists of a glass tube fitted with a syringe so that some of the electrolyte can be drawn from the cell into the tube. The hydrometer float is a smaller glass tube, air-tight and partly filled with shot to make it sink into the solution. The lower the specific gravity of the solution, the farther the float sinks into it. A graduated scale on the float shows the specific gravity directly, being read at the level of the solution.

Storage cells are rated in *ampere-hour capacity*, based on the number of amperes which can be furnished continuously for a stated period of time. For example, the cell may have a rating of 100 ampere-hours at an 8-hour discharge

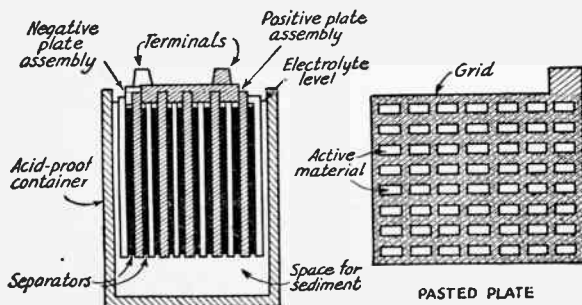


Fig. 210—Details of typical lead storage-battery construction.

rate. This means that the cell will deliver 100/8 or 12.5 amperes continuously for 8 hours after having been fully charged. The ampere-hour capacity of a cell will vary with the discharge rate, becoming smaller as the rated time of discharge is made shorter. It also depends upon the size of the plates and their number. In automobile-type batteries the dimensions of the plates are fairly well standardized, so that the ampere-hour capacity is chiefly determined by the number of plates in a cell. It is, therefore, common practice to speak of "11-plate," "15-plate," etc., batteries as an indication of the battery capacity.

Lead storage batteries must be kept fully charged if they are to stay in good condition. If a discharged battery is left standing idle,

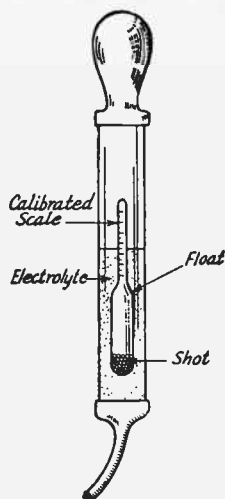


Fig. 211—The hydrometer, a device with a calibrated scale for measuring the specific gravity of the electrolyte, used to determine the state of charge of a lead storage battery.

lead sulphate will form on the plates and eventually the battery will be useless. When the battery is being charged, hydrogen bubbles are given off by the electrolyte which, in bursting at the surface, throw out fine drops of the electrolyte. This is called "gassing." The sulphuric-acid solution spray from gassing will attack many materials, and consequently care must be used to see that it is not permitted to fall on near-by objects. It should also be wiped off the battery itself.

A lead battery may be charged at its nominal discharge rate; i.e., a 100-ampere-hour battery, 8-hour rating, can be charged at 100/8,

or 12.5 amperes. The charging voltage required is slightly more than the output voltage of the cell. The preferred method is to charge at the full rate until the cells start to "gas" freely, after which the charging rate should be dropped to about half its initial value until the battery is fully charged, as indicated by the hydrometer reading. Alternatively, the battery may be charged from a constant-potential source (about 2.3 volts per cell), when the rise of terminal voltage of the battery as it accumulates a charge will automatically "taper" the charging rate.

The solution in a lead storage battery will freeze at a temperature of about zero degrees Fahrenheit when the battery is discharged, but a fully charged battery will not freeze until the temperature reaches about 90 degrees below zero. Keeping the battery

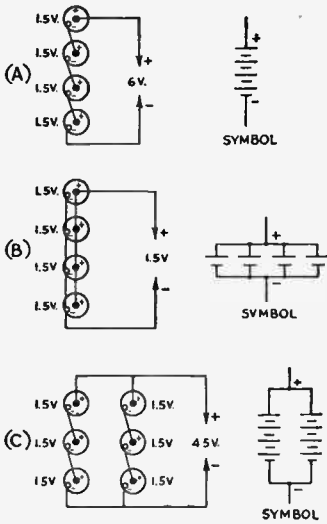


Fig. 212 — Series, parallel, and series-parallel connection of cells. Series connection increases the total voltage without changing current capacity; parallel connection increases current capacity without increasing voltage.

charged therefore is the best way to insure against damage by freezing.

Cells in series and parallel — For proper operation, many electrical devices require higher voltage or current than can be obtained from a single cell. If greater voltage is needed, cells may be connected in *series*, as shown in Fig. 212-A. The negative terminal of one cell is connected to the positive terminal of the next, so that the total e.m.f. of the battery is equal to the sum of the e.m.f.s of the individual cells. For radio purposes, batteries of 45 and 90 volts or more are built up in this way from 1.5-volt dry cells. An automobile storage battery consists of three lead storage cells in series, totaling 6.3 volts — or, in round figures, 6 volts. The current which may be taken safely from a battery composed of cells in series is the same as that which may be taken safely from one cell alone; since the same current flows through all cells, the current capacity is unchanged.

When the device or load to which the battery is to be connected requires more current than can be taken safely from a single cell, the cells may be connected in parallel, as shown in Fig. 212-B. In this case the total current is the sum of the currents contributed by the individual cells, each contributing the same amount if the cells are all alike. When cells are connected in parallel it is essential that the e.m.f.s all be the same, since if one cell generated a larger voltage than the others it would force current through the other cells in the reverse direction and thus would take most, if not all, of the load. Also, if one cell has a lower terminal voltage than the others it will take current from the others rather than carrying its fair share.

Cells may be connected in series-parallel, as in Fig. 212-C, to increase both the voltage and the current-carrying capacity of the battery.

2-5 Electromagnetism

The magnetic field — Everyone is familiar with the fact that a bar or horseshoe magnet will attract small pieces of iron. Just as in the case of electrostatic attraction (§ 2-3) the concept of a *field*, in this case a field of *magnetic force*, is adopted to explain the magnetic action. The field is visualized as being made up of *lines of magnetic force*, the number of which per unit area determines the field strength. As in the case of the electrostatic field, the lines of force do not have physical existence but simply represent a convenient way of describing the properties of the force.

Magnetic attraction and repulsion — The forces exerted by the magnetic field are analogous to electrostatic forces. Corresponding to positive and negative electric charges, it is found that there are two kinds of magnetic *poles*. Instead of being called “positive” and “negative,” however, the magnetic poles are called “north” (N) and “south” (S) poles. These names arise from the fact that, when a magnetized steel rod is freely suspended, it will turn into such a position that one end points toward the north. The end which points north is called the “north-seeking,” or simply the “north,” pole.

Unlike electric lines of force, which terminate on charges of opposite polarity (§ 2-3), magnetic lines of force are *closed upon themselves*. This is illustrated by the field about a bar magnet, as shown in Fig. 213-A. The lines extend through the magnet, the direction being taken from S to N inside the magnet and from N to S outside the magnet. If similar poles of two magnets are brought near each other, there is a force of repulsion between them, while dissimilar poles are attracted when brought close together. As in the case of electric charges, like poles repel, unlike poles attract.

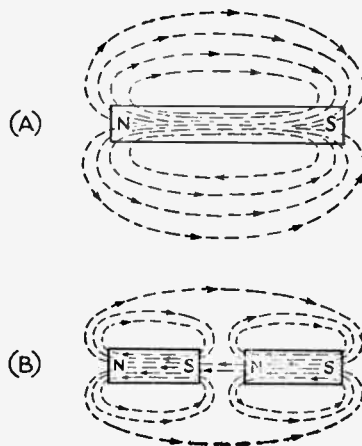


Fig. 213 — (A) The field about a bar magnet. The magnetic lines of force are continuous, part of the path being inside the magnet and part outside. (B) Cutting a magnet produces two magnets, each complete with N and S poles. With the magnets in the positions shown, some of the lines of force are common to both magnets.

If a bar magnet is cut in half, as in Fig. 213-B, it is found that the cut ends also are poles, of opposite kind to the original poles on the same piece. Such cutting can be continued indefinitely, and, no matter how small the pieces are made, there are always two opposite poles associated with each piece. In other words, a single magnetic pole cannot exist alone; it must always be associated with a pole of the opposite kind.

To explain this property of a magnet, it is considered that each molecule of a magnetic substance is itself a miniature magnet. If the material is not magnetized, the molecules are in random positions and the total magnetic effect is zero since there are just as many molecules tending to set up a magnetic field in one direction as there are others tending to set up a field in the opposite direction. When the substance becomes magnetized, however, the molecules are aligned so that most or all of the *N* poles of the molecular magnets are turned toward one end of the material while the *S* poles point toward the other end.

Magnetic induction — When an unmagnetized piece of iron is brought into the field of a magnet, its molecules tend to align themselves as described in the preceding paragraph. If one end of the iron is near the *N* pole of the magnet, the *S* poles of the molecules will turn toward that end and an *S* pole is said to be *induced* in the iron. An *N* pole will appear at the opposite end. Because of the attraction between opposite poles, the iron will be drawn toward the magnet. Since the iron has become a magnet under the influence of the field, it also possesses the property of attracting other pieces of iron.

When the magnetic field is removed, the molecules may or may not resume their random positions. If the material is soft iron the magnetism disappears quite rapidly when the field is removed, but in some types of steel the molecules are slow to resume their random positions and such materials will retain magnetism for a long time. A magnet which loses its magnetism quickly when there is no external magnetizing force is called a *temporary magnet*, while one which retains its magnetism for a long time is called a *permanent magnet*. The tendency to retain magnetism is called *retentivity*. The process of destroying magnetism can be hastened by heating, which increases the motion of the molecules within the substance, as well as by mechanical shock, which also tends to disturb the molecular alignment.

Electric current and the magnetic field — Experiment shows that a moving electron generates a magnetic field of exactly the same nature as that existing about a permanent magnet. Since a moving electron, or group of electrons moving together, constitutes an electric current, it follows that the flow of current is accompanied by the creation of a magnetic field. When the conductor is a wire the magnetic lines of force are in the form of concentric

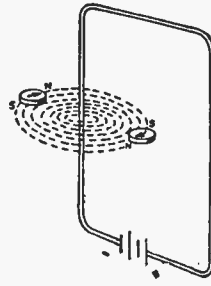


Fig. 214 — Whenever electric current passes through a wire, magnetic lines of force are set up, in the form of concentric circles, at right angles to the wire, and a magnetic field is said to exist around the wire. The direction of this field is controlled by the direction of current flow, and can be traced by means of a small compass.

circles around it and lie in planes at right angles to it, as shown in Fig. 214. The direction of this field is controlled by the direction of current flow.

There is an easily remembered method for finding the relative directions of the current and of the magnetic field it sets up. Imagine the fingers of the right hand curled about the wire, with the thumb extended along the wire in the direction of current flow (the conventional direction, from positive to negative, not the direction of electron movement). Then the fingers will be found to point in the direction of the magnetic field; that is, from *N* to *S*.

Magnetomotive force — The force which causes the magnetic field is called *magnetomotive force*, abbreviated *m.m.f.* It corresponds to electromotive force or e.m.f. in the electric circuit. The greater the magnetomotive force, the stronger the magnetic field; that is, the larger the number of magnetic lines per unit area. Magnetomotive force is proportional to the current flowing. When the wire carrying the current is formed into a coil so that the magnetic flux will be concentrated instead of being spread over a large area, the *m.m.f.* also is proportional to the number of turns in the coil. Consequently magnetomotive force can be expressed in terms of the product of current and turns, and the *ampere-turn*, as this product is called, is in fact the common unit of magnetomotive force. The same magnetizing effect can be secured with a great many turns and a weak current or with a few turns and a strong current. For example, if 10 amperes flow in one turn of wire, the magnetizing effect is 10 ampere-turns. If there is one ampere flowing in 10 turns of wire, the magnetomotive force also is 10 ampere-turns.

The magnetic circuit — Since magnetic lines of force are always closed upon themselves, it is possible to draw an analogy between the magnetic circuit and the ordinary electrical circuit. The electrical circuit also must be closed so that a complete path is provided around which the electrons or current can flow. However, there is no insulator for the magnetic field, so that the magnetic circuit is always complete even though no magnetic material (such as iron) may be present.

The number of lines of magnetic force, or *flux*, is equivalent in the magnetic circuit to current in the electric circuit. However, it is

usual practice to express the strength of the field in terms of the number of lines per unit area, or *flux density*. The unit of flux density is the *gauss*, which is equal to one line per square centimeter, but the terms "lines per square centimeter" or "lines per square inch" are commonly used instead.

Corresponding to resistance in the electric circuit is the tendency to obstruct the passage of magnetic flux, which is called *reluctance*. The reluctance of good magnetic materials, such as iron and steel, is quite low.

The *permeability* of a material is the ratio of the flux which would be set up in a closed magnetic path or circuit of the material to the flux that would exist in a path of the same dimensions in air, the same m.m.f. being used in both cases. The permeability of air is assigned the value 1. The permeability of steels of various types varies from about 50 to several thousand, depending upon the materials alloyed with the steel. Very high permeabilities are attained in certain special magnetic materials, such as "permalloy," which is an alloy of iron and nickel.

The permeability of magnetic materials depends upon the density of magnetic flux in the material. At very high flux densities the permeability is less than its value at low or moderate flux densities. This is because the flux in magnetic materials is proportional to the applied m.m.f. only over a limited range. As the m.m.f. increases more and more of the molecular magnets within the material become aligned, until eventually a point is reached where a very great increase in m.m.f. is required to cause a relatively small increase in flux. This is called *magnetic saturation*. In this region of saturation the permeability decreases, since the *ratio* between the number of lines in the material and the number in air, for the same m.m.f., is smaller than when the flux density is below the saturation point.

Energy in the magnetic field — Like the electrostatic field (§ 2-3), the magnetic field represents potential energy. Consequently the expenditure of energy is necessary to set up a magnetic field, but once the field has been established and remains constant no further energy is consumed in maintaining it. If by some means the field is caused to disappear, the stored-up magnetic energy is converted to energy in some other form. In other words the energy undergoes a transformation when the magnetic field is *changing*, being stored in the field when the field strength is increasing and being released from the field when the field strength is decreasing.

When a magnetic field is set up by a current flowing in a wire or coil, a certain amount of energy is used initially in bringing the field into existence. Thereafter the current must continue to flow, if the field is to be maintained at steady strength, but no expenditure of energy is required for this purpose. (There will be a steady energy loss in the circuit, but only

because of the resistance of the wire.) If the current stops the energy of the field is transformed back into electrical energy, tending to keep the current flowing. The amount of energy stored and subsequently released depends upon the strength of the field, which in turn depends upon the intensity of the current and the circuit conditions; i.e., it depends upon the relationship between field strength and current in the circuit.

Induced voltage — Since a magnetic field is set up by an electric current, it is not surprising to find that, in turn, a magnetic field can cause a current to flow in a closed electrical circuit. That is, an e.m.f. can be *induced* in a wire in a magnetic field. However, since a *change* in the field is required for energy transformation, an e.m.f. will be induced only when there is a change in the field with respect to the wire.

This change may be an actual change in the field strength or may be caused by relative motion of the field and wire; e.g., a moving field and a stationary wire, or a moving wire and a stationary field. It is convenient to consider this induced e.m.f. as resulting from the wire's "cutting through" the lines of force of the field. The strength of the e.m.f. so induced is proportional to the *rate* of cutting of the lines of force.

If the conductor is moving parallel with the lines of force in a field, no voltage is induced since no lines are cut. Maximum cutting results when the conductor moves through the field in such a way that both its longer dimension and direction of motion are perpendicular to the lines of force, as shown in Fig. 215. When the conductor is stationary and the field strength varies, the induced voltage results from the alternate increase and decrease in the number of lines of force cutting the wire as the m.m.f. varies in intensity.

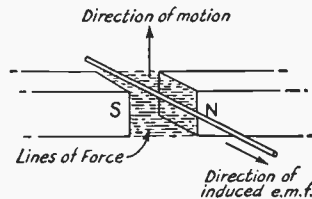


Fig. 215 — Showing how e.m.f. is induced in a conductor moving through a stationary magnetic field, cutting the lines of force. Conversely, a current sent through the conductor in the same direction by means of an external e.m.f. will cause the conductor to move downward.

Lenz's Law — When a voltage is induced and current flows in a conductor moving in a magnetic field, energy of motion is transformed into electrical energy. That is, mechanical *work* is done in moving the conductor when an induced current flows in it. If this were not so the induced voltage would be creating electrical energy, in violation of the fundamental principle of physics that energy can neither be created nor destroyed but only transformed.

It is found, therefore, that the flow of current creates an opposing magnetic force tending to stop the movement of the wire. The statement of this principle is known as Lenz's Law: "In all cases of electromagnetic induction, the induced currents have such a direction that their reaction tends to stop the motion which produces them."

Motor principle — The fact that current flowing in a conductor moving through a magnetic field tends to oppose the motion indicates that current sent through a *stationary* conductor in a magnetic field would tend to *set the conductor in motion*. Such is the case. If moving the conductor through the field in the direction indicated in Fig. 215 causes a current to flow as shown, then, if the conductor is stationary and an e.m.f. is applied to send a current through the conductor in the same direction, the conductor will tend to move across the field in the *opposite* direction.

This principle is used in the electric motor. The same rotating machine frequently may be used either as a generator or motor; as a generator it is turned mechanically to cause an induced e.m.f., and as a motor electric current through it causes mechanical motion.

Self-induction — When an e.m.f. is applied to a wire or coil, current begins to flow and a magnetic field is created. Just before closing the circuit there was no field; just after closing it the field exists. Consequently, at the instant of closing the circuit the *rate of change* of the field is very rapid. Since the wire or coil carrying the current is a conductor in a changing field, an e.m.f. will be induced in the wire. This induced voltage is the *e.m.f. of self-induction*, so called because it results from the current flowing in the wire itself.

By the principle of conservation of energy (and Lenz's Law), the polarity of the induced voltage must be such as to oppose the applied voltage; that is, the induced voltage must tend to send current through the circuit in the direction opposite to that of the current caused by the applied voltage. At the instant of closing the circuit the field changes at such a rate that the induced voltage equals the applied voltage (it cannot exceed the applied voltage, because

then it would be supplying energy to the source of applied e.m.f.), but after a short interval the rate of change of the field no longer is so rapid and the induced voltage decreases. Thus the current flowing is very small at first when the applied and induced e.m.f.s are about equal, but rises as the induced voltage becomes smaller. The process is cumulative, the current eventually reaching a final value determined only by the resistance in the circuit.

In forcing current through the circuit against the pressure of the induced or "back" voltage, work is done. The total amount of work done during the time that the current is rising to its final value is equal to the amount of energy stored in the magnetic field, neglecting heat losses in the wire itself. As explained before, no further energy is put into the field once the current becomes steady. However, if the circuit is opened and current flow caused by the applied e.m.f. ceases, the field collapses. The rate of change of field strength is very great in this case, and a voltage is again induced in the coil or wire. This voltage causes a current flow in the *same* direction as that of the applied e.m.f., since energy is now being restored to the circuit. The energy usually is dissipated in the spark which occurs when such a circuit is opened. Since the field collapses very rapidly when the switch is opened, the induced e.m.f. at such a time can be extremely high.

Inductance — As explained above, the strength of the self-induced voltage is proportional to the rate of change of the field. However, it is also apparent from the foregoing that the voltage also depends upon the properties of the circuit, since, if a number of similar conductors are in the same varying field, the same voltage will be induced in each. By combining the conductors properly, the total induced voltage in such a case will be the sum of the voltages induced in each wire. Also, the rate of change of field strength depends upon the strength of the field set up by a given amount of current flowing in the wire or coil, and this in turn depends upon the ampere-turns, permeability, length and cross-section of the magnetic path, etc.

For a given circuit, however, the field strength will be determined by the current, and the rate of change of the field consequently will be determined by the rate of change of current. Hence, it is possible to group all of these other factors into one quantity, a property of the circuit. This property is called *inductance*. When this is done, the equation giving the value of the induced voltage becomes:

$$\begin{aligned} \text{Induced voltage} \\ = L \times \text{rate of change of current} \end{aligned}$$

where L is the value of inductance in the circuit.

Inductance is a property associated with all circuits, although in many cases it may be so small in comparison to other circuit properties (such as resistance) that no error results from neglecting it. The inductance of a straight wire

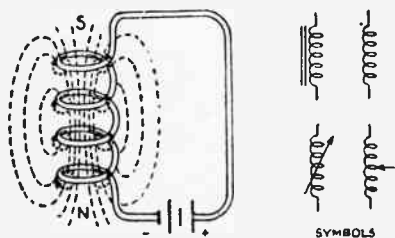


Fig. 216 — When the conducting wire is coiled, the individual magnetic fields of each turn are in such a direction as to produce a field similar to that of a bar magnet. The schematic symbols for inductance are shown at the right. The symbol at the left in the top row indicates an iron-core inductance; at the right, air core. Variable inductances are shown in the bottom row.

increases with the length of the wire and decreases with increasing wire diameter. The inductance of such a wire is small, however. For a given length of wire, much greater inductance can be secured by winding the wire into a coil so that the total flux from the wire is concentrated into a small space and the flux density correspondingly increased. The unit of inductance is the *henry*. A circuit or coil has an inductance of one henry if an e.m.f. of one volt is induced when the current changes at the rate of one ampere per second. In radio work it is frequently convenient to use smaller units; those commonly used are the *millihenry* (one thousandth of a henry) and the *microhenry* (one millionth of a henry).

It will be recognized that the relationship between inductance and the magnetic field is similar to that between capacity and the electrostatic field. The greater the inductance, the greater the amount of energy stored in the magnetic field for a given amount of current; the greater the capacity, the greater the amount of energy stored in the electrostatic field for a given voltage.

The inductance of a coil of wire depends upon the number of turns, the cross-sectional dimensions of the coil, and the length of the winding. It also depends upon the permeability of the material on which the coil is wound, or *core*. Formulas for computing the inductance of air-core coils of the type commonly used in radio work, are given in Chapter Twenty.


Mutual inductance — If two coils are arranged with their axes coinciding, as shown in Fig. 217, a current sent through Coil 1 will cause a magnetic field which cuts Coil 2. Consequently, an e.m.f. will be induced in Coil 2 whenever the field strength is changing. This induced e.m.f. is similar to the e.m.f. of self-induction; that is,

$$\begin{aligned} \text{Induced e.m.f.} \\ = M \times \text{rate of change of current} \end{aligned}$$

where M is a quantity called the *mutual inductance* of the two coils. The mutual inductance may be large or small, depending upon the self-inductances of the coils and the proportion of the total flux set up by one coil which cuts the turns of the other coil. If all the flux set up by one coil cuts all the turns of the other coil the mutual inductance has its maximum possible value, while if only a small part of the flux set up by one coil cuts the turns of the other the mutual inductance may be relatively small. Two coils having mutual inductance are said to be *coupled*.

The *degree of coupling* expresses the ratio of actual mutual inductance to the maximum possible value. Coils which have nearly the maximum possible mutual inductance are said to be *closely*, or *tightly*, coupled, while if the mutual inductance is relatively small the coils are said to be *loosely* coupled. The degree of coupling depends upon the physical spacing between the coils and how they are placed with

Fig. 217 — Mutual inductance. When the switch, S, is closed current flows through coil No. 1, setting up a magnetic field which induces an e.m.f. in the turns of coil No. 2.

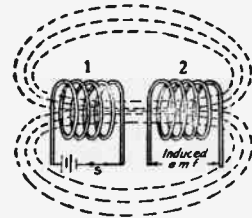

respect to each other. Maximum coupling exists when they have a common axis, as shown in Fig. 217, and are as close together as possible.

If two coils having mutual inductance are connected in the same circuit, the directions of the respective magnetic fields may be such as to add or oppose. In the former case the mutual inductance is said to be "positive"; in the latter case, "negative." Positive mutual inductance in such a circuit means that the total inductance is greater than the sum of the two individual inductances, while negative inductance means that the total inductance is less than the sum of the two individual inductances. The mutual inductance may be made either positive or negative simply by reversing the connections to one of the coils.

2-6 Fundamental Relations

Direct current — A current which always flows in the same direction through a circuit is called a *direct current*, frequently abbreviated *d.c.* Current flow caused by batteries, for example, is direct current. One terminal of each cell is always positive and the other always negative, hence electrons are attracted only in the one direction around the circuit. To make the current change direction, the connections to the battery terminals must be reversed.

Work, energy and power — When a quantity of electricity is moved from a point of one potential to a point at a second potential, work is done. The work done is the product of the quantity of electricity and the difference of potential through which it is moved; that is,

$$W = QE$$

In the practical system of units, with Q in coulombs and E in volts, the unit of work is called the *joule*. Energy, which is the capacity for doing work, is measured in the same units.

Since $I = Q/t$ when the current is constant (§ 2-1), $Q = It$. Substituting for Q in the equation above gives

$$W = EIt$$

where E is in volts, I in amperes, and t in seconds. One ampere flowing through a difference of potential of one volt for one second does one joule of work. *Power* is the time rate at which work is done, so that, if the work is done at a uniform rate, dividing the equation by t will give the electrical power:

$$P = EI$$

The unit of electrical power is the *watt*.

In practical work, the term "joule" is seldom used for the unit of work or energy. The more common name is *watt-second* (one joule is equal to one watt applied for one second). The watt-second is a relatively small unit; a larger one, the *watt-hour* (one watt of power applied for one hour) is more frequently used. Again, for some purposes the watt is too small a unit, and the *kilowatt* (1000 watts) is used instead. A still larger energy unit is the *kilowatt-hour*, the meaning of which is easily interpreted.

Fractional and multiple units — As illustrated by the examples in the preceding paragraph, it is frequently convenient to change the value of a unit so that it will not be necessary to use very large or very small numbers. As applied to electrical units, the practice is to add a prefix to the name of the fundamental unit to indicate whether the modified unit is larger or smaller. The common prefixes are *micro* (one millionth), *milli* (one thousandth), *kilo* (one thousand) and *mega* (one million). Thus, a microvolt is one millionth of a volt, a milliamperere is one thousandth of an ampere, a kilovolt is one thousand volts, and so on.

Unless there is some indication to the contrary, it should be assumed that, whenever a formula is given in terms of unprefix letters (*E*, *I*, *P*, *R*, etc.), the fundamental units are meant. If the quantities to be substituted in the equation are given in fractional or multiple units, conversion to the fundamental units is necessary before the equation can be used.

Ohm's Law — In any metallic conductor, the current which flows is directly proportional to the applied electromotive force. This relationship, known as *Ohm's Law*, can be written

$$E = RI$$

where *E* is the e.m.f., *I* is the current, and *R* is a constant, depending on the conductor, called the *resistance* of the conductor. By definition, a conductor has one unit of resistance when an applied e.m.f. of one volt causes a current of one ampere to flow. The unit of resistance is called the *ohm*.

Ohm's Law does not apply to all types of conduction, particularly to conduction through gases and in a vacuum. The law is of very great importance, however, because practically all electrical circuits use metallic conduction.

By transposing the equation, the following equally useful forms are obtained:

$$R = \frac{E}{I} \quad I = \frac{E}{R}$$

The three equations state that, in a circuit to which Ohm's Law applies, the voltage across the circuit is equal to the current multiplied by the resistance; the resistance of the circuit is equal to the voltage divided by the current; and the current in the circuit is equal to the voltage divided by the resistance.

Resistance and resistivity — The resistance of a conductor is determined by the material of which it is made and its temperature, and is

directly proportional to the length of the conductor (that is, the length of the path of the current through the conductor) and inversely proportional to the area through which the current flows. If the temperature is constant,

$$R = k \frac{L}{A}$$

where *R* is the resistance, *k* is a constant depending upon the material of which the conductor is made, *L* is the length and *A* the area. For the purpose of giving a specific value to *k*, *L* is taken as one centimeter and *A* as one square centimeter (a cube of the material measuring one centimeter on a side); *k* is then the resistance in ohms of such a cube at a specified temperature. It is called the *specific resistance* or *resistivity* of the material. If the resistivity is known, the resistance of any conductor of known length and uniform cross-section readily can be determined by the formula above. The length must be in centimeters and the area in square centimeters.

The relationships given above are true only for unidirectional (direct) currents and low-frequency alternating currents. Modifications must be made when the current reverses its direction many times each second (§ 2-8).

Conductance and conductivity — The reciprocal of resistance is called *conductance*, and has the opposite properties to resistance. The lower the resistance of a circuit, the higher is the conductance, and vice versa. The symbol of conductance is *G*, and the relationship to resistance is

$$G = \frac{1}{R} \quad R = \frac{1}{G}$$

The unit of conductance is called the *mho*. A circuit or conductor which has a resistance of one ohm has a conductance of one mho. By substituting $1/G$ for *R* in Ohm's Law,

$$G = \frac{I}{E} \quad I = EG \quad E = \frac{I}{G}$$

The reciprocal of resistivity is called the *specific conductance* or *conductivity* of a material, and is measured in mhos per centimeter cube. It is frequently useful to know the *relative* conductivity of different materials. This is usually expressed in *per cent conductivity*, the conductivity of annealed copper being taken as 100 per cent. A table of per cent conductivities is given in Chapter Twenty.

Power used in resistance — If two conductors of different resistances have the same current flowing through them, then by Ohm's Law the conductor with the larger resistance will have a greater difference of potential across its terminals. Consequently, more energy is supplied to the larger resistance, since in a given period of time the same amount of electricity is moved through a greater potential difference. The energy appears in the form of heat in the conductor. With a steady current, the heat will raise the temperature of the con-

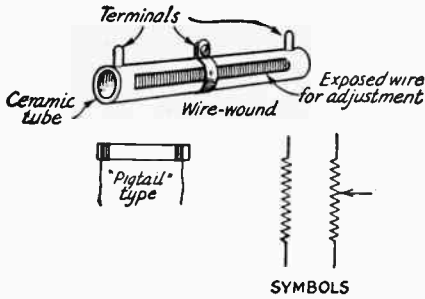


Fig. 218 — Two common types of fixed resistors. The wire-wound type is used for dissipating power of the order of 5 watts or more. "Pigtail" resistors, usually made of carbon or other resistance material in the form of a molded rod or as a thin coating on an insulating tube, rather than being wound with wire, are small in size but do not safely dissipate much power. Schematic symbols for fixed and variable resistors are shown at lower right.

ductor until a balance is reached between the heat generated and that radiated to the surrounding air or otherwise carried away.

Since $P = EI$, substituting for E the appropriate form of Ohm's Law ($E = IR$) gives

$$P = I^2R$$

and making a similar substitution for I gives

$$P = \frac{E^2}{R}$$

That is, the power used in heating a resistance (or dissipated in the resistance) is proportional to the square of the voltage applied or to the square of the current flowing. In these formulas P is in watts, E in volts and I in amperes.

Further transposition of the equations gives the following forms, useful when the resistance and power are known:

$$E = \sqrt{PR} \quad I = \sqrt{\frac{P}{R}}$$

Unless the circuit containing the resistance is being used for the specific purpose of generating heat, the power used in heating a resistance is generally considered as a loss. However, there are very many applications in radio circuits where, despite the loss of power, a useful purpose is served by introducing resistance deliberately. Resistances made to specified values and provided with connecting terminals are called *resistors*. They are frequently wound on ceramic or other heat-resisting tubing with wire having high resistivity.

Temperature coefficient of resistance — The resistance of most pure metals increases with an increase in temperature. The resistance of a wire at any temperature is given by

$$R = R_0 (1 + at)$$

where R is the required resistance, R_0 the resistance at 0°C . (temperature of melting ice), t is the temperature (Centigrade), and a is the *temperature coefficient of resistance*. For copper, a is about 0.004; that is, starting at 0°C ., the resistance increases 0.4 per cent per degree above zero.

Temperature coefficient of resistance becomes of importance when conductors operate at high temperatures. In the case of resistors used in electrical and radio circuits, the heat developed by current flow may raise the temperature of the resistance wire to several hundred degrees F. Thus the resistance at operating temperatures can be very much higher than the resistance at room temperature. Consequently such resistors are wound with wire which has a low temperature coefficient of resistance, so that the resistance will be more nearly constant under all conditions.

Resistances in series — When two or more resistances are connected so that the same current flows through each in turn, as shown in Fig. 219, they are said to be connected *in series*. Then, by Ohm's Law,

$$\begin{aligned} E_1 &= IR_1 \\ E_2 &= IR_2 \\ E_3 &= IR_3 \end{aligned}$$

etc., where the subscripts 1, 2, 3 indicate the first, second and third resistor, and the voltages E_1 , E_2 and E_3 are the voltages appearing across the terminals of the respective resistors. Adding the three voltages gives the total voltage across the three resistors:

$$E = E_1 + E_2 + E_3 = IR_1 + IR_2 + IR_3 = I(R_1 + R_2 + R_3) = IR$$

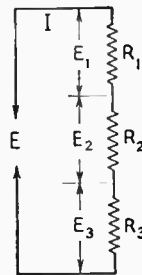


Fig. 219 — Resistances in series.

That is, the voltage across the resistors in series is equal to the current multiplied by the sum of the individual resistances. In the above equation, R , which denotes this sum, may be called the *equivalent resistance* or *total resistance*. The equivalent resistance of a number of resistors connected in series is, therefore, equal to the sum of the values of the individual resistors.

Resistances in parallel — When a number of resistances are connected so that the same voltage is applied to all, as shown in Fig. 220,

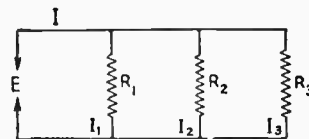


Fig. 220 — Resistances in parallel.

they are said to be connected *in parallel*. By Ohm's Law,

$$I_1 = \frac{E}{R_1} \quad I_2 = \frac{E}{R_2} \quad I_3 = \frac{E}{R_3}$$

so that the total current, I , which is the sum

of the currents in the individual resistors, is

$$I = I_1 + I_2 + I_3 = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3} = E \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = E \frac{1}{R}$$

where R is the equivalent resistance — i.e., the resistance through which the same total current would flow if such a resistance were substituted for the three shown. Therefore,

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

That is, the reciprocal of the equivalent resistance of a number of resistances in parallel is equal to the sum of the reciprocals of the individual resistances. Since the reciprocal of resistance is conductance,

$$G = G_1 + G_2 + G_3$$

where G is the total conductance and G_1, G_2, G_3 , etc., are the individual conductances in parallel.

To obtain R instead of its reciprocal the equation above may be inverted, so that

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

The number of terms in the denominator of this equation will, of course, be equal to the actual number of resistors in parallel.

For the special case of only two resistances in parallel, the equation reduces to

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

Series-parallel connection of resistors is shown in Fig. 221. When circuits of this type are encountered the equivalent or total resistance can be found by first adding the series resistances in each group, then treating each group as a single resistor so that the formula for resistors in parallel can be used.

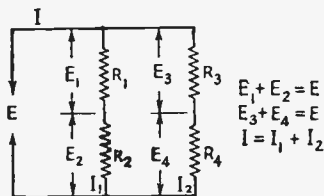


Fig. 221 — Series-parallel connection of resistances. Voltage and current relationships are given at the right.

Voltage dividers and potentiometers — Since the same current flows through resistors connected in series, it follows from Ohm's Law that the voltage (termed *voltage drop*) across each resistor of a series-connected group is proportional to its resistance. Thus, in Fig. 222-A, the voltage E_1 across R_1 is equal to the applied voltage, E , multiplied by the ratio of

R_1 to the total resistance, or

$$E_1 = \frac{R_1}{R_1 + R_2 + R_3} \cdot E$$

Similarly, the voltage, E_2 , is equal to

$$\frac{R_1 + R_2}{R_1 + R_2 + R_3} \cdot E$$

Such an arrangement is called a *voltage divider*, since it provides a means for obtaining smaller voltages from a source of fixed voltage. When current is drawn from the divider at the various tap points the above relations are no longer strictly true, for then the same current does not flow in all parts of the divider. Design data for such cases are given in § 8-10.

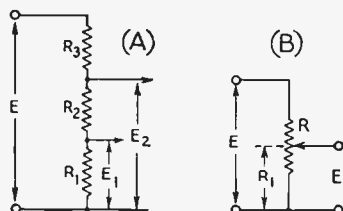


Fig. 222 — Voltage divider (A) and potentiometer (B).

A similar arrangement is shown in Fig. 222-B, where the resistor, R , is equipped with a sliding tap for fine adjustment. Such a variable resistor is frequently called a *potentiometer*.

Inductances in series and parallel — As explained in § 2-5, inductance determines the voltage induced when the current changes at a given rate. That is, $E = L \times$ rate of change of current. This resembles Ohm's Law, if L corresponds to R and the rate of change of current to I . Thus, by reasoning similar to that used in the case of resistors, it can be shown that, for inductances in series,

$$L = L_1 + L_2 + L_3$$

and for inductances in parallel,

$$L = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$

where the number of terms in either equation is determined by the actual number of inductances connected in series or parallel.

These equations do not hold if there is mutual inductance (§ 2-5) between the coils.

Condensers in series and parallel — When a number of condensers are in parallel, as in Fig. 223-A, the same e.m.f. is applied to all. Consequently, the quantity of electricity stored in each is in proportion to its capacity. The total quantity stored is the sum of the quantities in the individual condensers:

$$Q = Q_1 + Q_2 + Q_3 = C_1 E + C_2 E + C_3 E = (C_1 + C_2 + C_3) E = CE$$

where C is the equivalent capacity. The equivalent capacity of condensers in parallel is equal to the sum of the individual capacities.

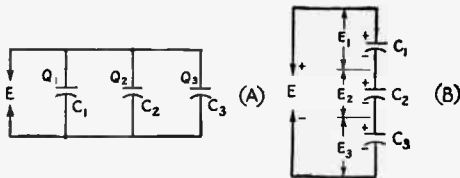


Fig. 223 — Condensers in parallel (A) and in series (B).

When condensers are connected in series, as in Fig. 223-B, the application of an e.m.f. to the circuit causes a certain quantity of electricity to accumulate on the top plate of \$C_1\$. By electrostatic induction, an equal charge of opposite polarity (negative in the illustration) appears on the bottom plate of \$C_1\$, and, since the lower plate of \$C_1\$ and the upper plate of \$C_2\$ are connected together, this must leave an equal positive charge on the upper plate of \$C_2\$. This, in turn, causes the lower plate of \$C_2\$ to assume an equal negative charge, and so on down to the plate connected to the negative terminal of the source of e.m.f. In other words the same quantity of electricity is placed on each condenser, and this is equal to the total quantity stored. The voltage across each condenser will depend upon its capacity, and the sum of these voltages must equal the applied voltage. Thus,

$$E = E_1 + E_2 + E_3 = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) = \frac{Q}{C}$$

where \$C\$ is the equivalent capacity. This leads to an expression similar to that for resistances in parallel:

$$C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

where the number of terms in the denominator should be the same as the actual number of condensers in series.

Time constant — When a condenser and resistor are connected in series with a source of e.m.f., such as a battery, the initial flow of current into the condenser is limited by the resistance, so that a longer period of time is required to complete the charging of the con-

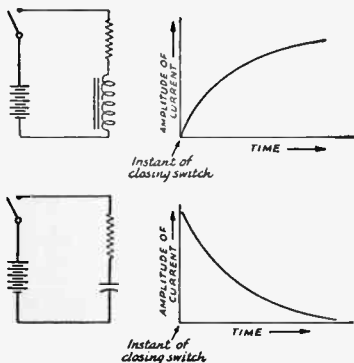


Fig. 224 — The RC and LC circuits at the left, together with the curves of current amplitude vs. time, show how the current in a circuit combining resistance with inductance or capacity takes a finite period of time to reach steady-state value.

denser than would be the case without the resistor. Likewise, when the condenser is discharged through a resistor a measurable period of time is taken for the current flow to reach a negligible value. In the case of either charge or discharge the time required is proportional to the capacity and resistance, the product of which is called the *time constant* of the circuit. If \$C\$ is in farads and \$R\$ in ohms, or \$C\$ in microfarads and \$R\$ in megohms, the product gives the time in seconds required for the voltage across a discharging condenser to drop to \$1/e\$, or approximately 37 per cent of its original value. (The constant \$e\$ is the base of the natural series of logarithms.)

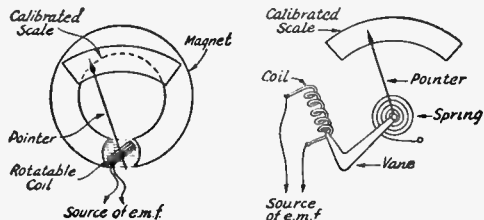


Fig. 225 — Left — The d'Arsonval or moving-coil meter for d.c. current measurement. Current flowing through the rotatable coil in the field of the permanent magnet causes a force to act on the coil, tending to turn it. The turning tendency is counteracted by springs (not shown) so that the amount of movement is proportional to the value of the current in the coil. Right — In the simpler moving-iron-vane type, a light-weight soft-iron plunger is attracted by current flowing in a fixed coil. As the plunger moves the pointer to which it is linked also moves, until the magnetic force in the coil is balanced by the spiral spring restraining the plunger movement.

In a circuit containing inductance and resistance in series, the effect of the resistance is to *shorten* the period required for the current to reach its final value (§ 2-5) after an e.m.f. is applied to the circuit. The time constant of such a circuit is equal to \$L/R\$, where \$L\$ is in henrys and \$R\$ in ohms. It gives the time in seconds required for the current to reach \$1-1/e\$, or approximately 63 per cent of its final steady value when a constant voltage is applied.

By proper application to associated circuits and devices such as vacuum tubes, it is possible by suitable selection of time constant to create almost any desired wave or pulse shape. This is of practical importance in many circuit applications in amateur transmission and reception, as in electronic keyers, automatic volume control, resistance-capacity filters and remote control. Apart from these applications, many of the techniques employed in television and specialized electronic devices are based on this principle.

Measuring instruments — Instruments for measuring d.c. current and voltage make use of the force acting on a coil carrying current in a magnetic field (§ 2-5), produced by a permanent magnet, to move a pointer along a calibrated scale. The magnetic field may be produced by a permanent magnet acting upon a moving coil, or by a fixed coil acting upon a moving iron vane or plunger.

The first type of instrument, based on what is known as the d'Arsonval moving-coil movement, is shown at the left in Fig. 225. The moving-iron vane instrument shown at the right is less accurate and requires higher energizing current, making it relatively insensitive as compared to the moving-coil type. Only the cheaper measuring instruments available to amateurs are based on this principle.

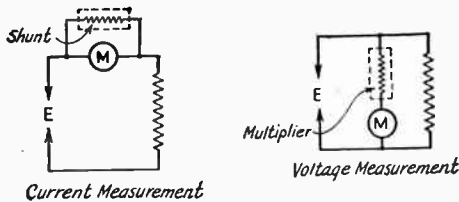


Fig. 226 — Circuit connections for measuring current and voltage. The shunt resistor is used for increasing the value of the current which the instrument can measure, by providing an alternate path through which some of the current can flow. The series multiplier limits the current when the instrument is used to measure voltage.

In such instruments the current required for full-scale deflection of the pointer varies from several milliamperes to a few microamperes, according to the sensitivity required. If the instrument is to read high currents, it is *shunted* (paralleled) by a low resistance through which most of the current flows, leaving only enough flowing through the instrument to give a full-scale deflection corresponding to the total current flowing through both meter and shunt. An instrument which reads microamperes is called a *microammeter* or *galvanometer*; one calibrated in milliamperes is called a *milliammeter*; one calibrated in amperes is an *ammeter*. A *voltmeter* is simply a milliammeter with a high resistance in series so that the current will be limited to a suitable value when the instrument is connected across a voltage source; it is calibrated in terms of the voltage which must appear across the terminals to cause a given value of current to flow. The series resistance is called a *multiplier*. A *wattmeter* is a combination voltmeter and ammeter in which the pointer deflection is proportional to the power in the circuit.

An ammeter or milliammeter is connected in series with the circuit in which current is being measured, so that the current flows through the instrument. A voltmeter is connected in parallel with the circuit.

2-7 Alternating Current

Description — An alternating current is one which periodically reverses its direction of flow. In addition to this alternate change in direction, usually the amount or *amplitude* of the current also varies continually during the period when the current is flowing in one direction. These variations are accompanied by corresponding variations in the magnetic field set up by the current, and it is this feature which makes the alternating current so useful. By means of the varying field, energy may be

continually transferred (by induction) from one circuit to another without direct connection, and the voltage may be changed in the process. Neither of these is possible with direct current because, except for brief periods when the circuit is closed or opened, the field accompanying a steady direct current is unchanging, and hence there is no way of inducing an e.m.f. except by moving a conductor through the field (§ 2-5).

Alternating currents may be generated in several ways. Rotating electrical machines (*a.c. generators* or *alternators*) are used for developing large amounts of power when the rate of reversal is relatively slow. However, such machines are not suitable for producing currents which reverse direction thousands or millions of times each second. The thermionic vacuum tube is used for this purpose, as described in Chapter Three.

The simplest form of alternating current (or voltage) is shown graphically in Fig. 227. This chart shows that the current starts at zero value, builds up to a maximum in one direction, comes back down to zero, builds up to a maximum in the opposite direction and comes back to zero. The curve follows the sine law and is known as a *sine wave*, because of the wavelike nature of the curve which results when sine values are plotted on rectangular coordinates as a function of angle or time.

Frequency — The complete wave shown in Fig. 227 is called a *cycle*, and the length of time required to complete one cycle is called the *period*. Each half of the cycle, during which the current is flowing in one direction, although its strength is varying, is known as an *alteration*. The number of cycles the wave goes through each second of time is called the *frequency*. In radio work, where frequencies are extremely large, it is convenient to use two other units, *kilocycles* per second (cycles per second \div 1000) and *megacycles* per second (cycles per second \div 1,000,000). These are usually abbreviated ke. and Me., respectively. Occasionally these abbreviations are written kes. and Mes. to indicate "kilocycles per second" and "megacycles per second" rather than simply "kilocycles" and "megacycles," but it is understood that "per second" is meant when the shorter forms are used.

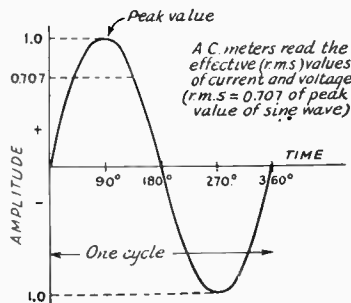


Fig. 227 — Sine wave of alternating current or voltage.

Electrical degrees — If we take a fixed point on the periphery of a revolving wheel, we find that at the end of each revolution, or cycle, the point has come back to its original starting place. Its position at any instant can be expressed in terms of the angle between two lines, one drawn from the center of the wheel to the point at the instant of time considered, the other drawn from the wheel center to the starting point. In making one complete revolution the point has travelled through 360 degrees, a half revolution 180 degrees, a quarter revolution 90 degrees, and so on. The periodic wave of alternating current may be treated similarly, one complete cycle equalling one revolution or 360 degrees, one alternation (half cycle) 180 degrees, and so on. With the cycle divided up in this way, the sine curve simply means that the value of current at any instant is proportional to the sine of the angle which corresponds to the particular fraction of the cycle considered.

The concept of angle is universally used in alternating currents. Generally, it is expressed in the fundamental form, using the radian rather than the degree as a unit, whence a cycle is equal to 2π radians, or a half cycle to π radians. The expression $2\pi f$, for which the symbol ω is often used, simply means electrical degrees per cycle times frequency, and is called the *angular velocity*. It gives the total number of electrical radians passed through by a current of given frequency in one second.

Peak, instantaneous, effective and average values — The highest value of current or voltage during the time when the current is flowing in one direction is called the *maximum* or *peak* value. For the sine wave, the peak has the same absolute value on both the positive and negative halves of the cycle. This is not necessarily true of waves having shapes other than the true sine form.

The value of current or voltage existing at any particular point of time in the cycle is called the *instantaneous* value. The instant for which a particular value is to be found can be specified in terms of time (fraction of the period) or of angle.

Since both the voltage and current are swinging continuously between their positive maximum and negative maximum values, it might be wondered how one can speak of so many amperes of alternating current when the value is changing continuously. The problem is simplified in practical work by considering that an alternating current has an effective value of one ampere when it produces heat, in flowing through a given resistance, at the same average rate as one ampere of continuous direct current flowing through the same resistance. This effective value is the square root of the mean of all of the instantaneous current values squared. In the case of the sine-wave form,

$$E_{\text{eff}} = \sqrt{\frac{1}{2}E_{\text{max}}^2}$$

For this reason, the effective value of an alter-

nating current or voltage is also known as the *root-mean-square*, or *r.m.s.*, value. Hence, the effective value is the square root of $\frac{1}{2}$, or 0.707, times the maximum value.

In a purely a.c. circuit the average current over a whole cycle must be zero, because if the average current on, say, the positive half of the cycle were greater than the average on the negative half, there would be a net current flow in the positive direction. This would correspond to a direct (although intermittent) current, and hence must be excluded because a purely alternating current was assumed. The "average" value of an alternating current is defined as the average current during the part of the cycle when the current is flowing in one direction only. It is of particular importance when alternating current is changed to direct current by the methods considered in later chapters. For a sine wave, the average value is equal to 0.636 of the peak value.

In the sine wave the three voltage values, peak, effective and average, are related to each other as follows:

$$\begin{aligned} E_{\text{max}} &= E_{\text{eff}} \times 1.414 = E_{\text{ave}} \times 1.57 \\ E_{\text{eff}} &= E_{\text{max}} \times 0.707 = E_{\text{ave}} \times 1.11 \\ E_{\text{ave}} &= E_{\text{max}} \times 0.636 = E_{\text{eff}} \times 0.9 \end{aligned}$$

The relationships for current are equivalent to those given above for voltage.

Phase — As the next few paragraphs will show, the current and voltage in an alternating-current circuit may not pass through their maximum and minimum values at the same time, even though both are sine waves of the same frequency. The time at which a particular part of the cycle (such as the positive peak) occurs is called the *phase* of the wave. If two waves are not exactly in step there is a *phase difference* between them. The phase difference can be expressed in terms of the actual difference in time between the two instants at which the two waves reach corresponding parts of their cycles, but it is generally more convenient to measure it in angular units. A phase difference of 90 degrees, for example, means that one wave reaches its maximum value one-quarter cycle before the other wave reaches its maximum value in the same direction.

The phase relationships between two currents (or two voltages) of the same frequency are defined in the same way. When two such currents are combined the resultant is a single current of the same frequency, but having an instantaneous amplitude equal to the algebraic sum of the amplitudes of the two components at the same instant. The amplitude of the resultant current hence is determined by the phase relationship between the two currents before combination. Thus if the two currents are exactly in phase, the maximum value of the resultant will be the numerical sum of the maximum values of the individual currents; if they are 180 degrees out of phase, one reaches its positive maximum at the instant the other reaches its negative maximum, hence the resultant current is the difference between the

two. In the latter case, if the two currents have the same amplitude the resultant current is zero.

Current, voltage and power in an inductance—When alternating current flows through an inductance, the continually varying magnetic field causes the continuous generation of an e.m.f. of self-induction (§ 2-5). The induced voltage at any instant is proportional to the rate at which the current is changing at that instant. If the current is a sine wave, it can be shown that the rate of change is greatest when the current is passing through zero and least when the current is maximum. For this reason, the induced voltage is maximum when the current is zero and zero when the current is maximum. The direction or polarity of the induced voltage is such as to tend to sustain the current flow when the current is decreasing and to prevent it from flowing when the current is increasing (§ 2-5). As a result, the induced voltage in an inductance lags 90 degrees behind the current.

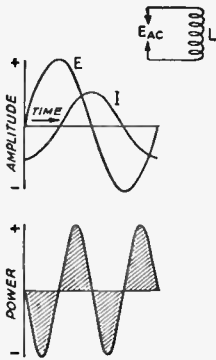


Fig. 228 — Voltage, current and power relations in an alternating-current circuit consisting of inductance only.

By Lenz's Law, the induced voltage must always oppose the applied voltage; that is, the induced and applied voltages must be in phase opposition, or 180 degrees out of phase. Consequently, the applied voltage leads the current by 90 degrees. Or, using the voltage as a reference, the current in an inductance lags 90 degrees, or one-quarter cycle, behind the voltage. These relationships are shown in Fig. 228.

When the current is increasing in either direction, energy is being stored in the magnetic field. At such times the voltage has the same polarity as the current, so that the product of the two, which gives the instantaneous power fed to the inductance, is positive. When the current is decreasing energy is being restored to the circuit and the applied voltage has the opposite polarity, so that the product of current and voltage is negative. This is also shown in Fig. 228. Positive power means power taken from the source (i.e., the source of the applied e.m.f.), while negative power means power returned to the source. Power is alternately taken and given back in each quarter cycle, and, since the amount given back is the same as that taken, the average power in an inductance is zero when considering a whole cycle. In a practical inductance the wire will have some resistance, so that some of the power supplied will be consumed in heating the wire, but if the resistance of the circuit is small compared to the inductance the power

consumption is very small compared to the power which is alternately stored and returned.

Current, voltage and power in a condenser—When an alternating voltage is applied to a condenser, the condenser acquires a charge while the voltage is rising and loses its charge while the voltage is decreasing. The quantity of electricity stored in the condenser at any instant is proportional to the voltage across its terminals at that instant ($Q = CE$). Since current is the rate of transfer of quantity of electricity, the current flowing into the condenser (when it is being charged) or out of it (when it is discharging) consequently will be proportional to the rate of change of the applied voltage. If the voltage is a sine wave, its rate of change will be greatest when passing through zero and least when the voltage is maximum. As a result, the current flowing into or out of the condenser is greatest when the voltage is passing through zero and least when the voltage reaches its peak value.

This relationship is shown in Fig. 229. Whenever the voltage is rising (in either direction) the current flow is in the same direction as the applied voltage. When the voltage is decreasing and the condenser is discharging, the current flows in the opposite direction. The energy stored in the condenser on the charging part of the cycle is restored to the circuit on the discharge part, and the total energy consumed in a whole cycle therefore is zero. A condenser operating on a.c. takes no average power from the source, except for such actual energy losses as may occur as the result of heating of the dielectric (§ 2-3). The energy loss in air condensers used in radio circuits is negligibly small except at extremely high frequencies.

As shown by Fig. 229, the phase relationship between current flow and applied voltage is such that the current leads the voltage by 90 degrees. This is just the opposite to the inductance case.

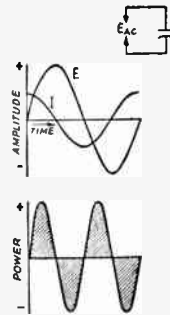


Fig. 229 — Voltage, current and power relations in an alternating-current circuit consisting of capacity only.

Current, voltage and power in resistance—In a circuit containing resistance only there are no energy storage effects, and consequently the current and voltage are in phase. The current therefore always flows in the same direction as the applied voltage, and, since the power is always positive, there is continual power

dissipation in the resistance. The relationships are shown in Fig. 230.

Strictly speaking, no circuit can have resistance only, because the flow of current always is accompanied by the creation of a magnetic field and every conductor also has a certain amount of capacity. Whether or not such residual inductance and capacity are large enough to require consideration is determined by the frequency at which the circuit is to operate.

The a.c. spectrum — Alternating currents of different frequencies have different properties and are useful in a variety of ways. For the transmission of power to light homes, run motors and perform familiar everyday tasks by electrical means, low frequencies are most suitable. Frequencies of 25, 50 and 60 cycles are in common use, the latter being most widely used in this country. The range of frequencies between about 15 and 15,000 cycles is known as the *audio-frequency* range, because when frequencies of this order are converted from a.c. into air vibrations, as by a loud-speaker or telephone receiver, they are distinguishable as sounds having a tone pitch proportional to the frequency.

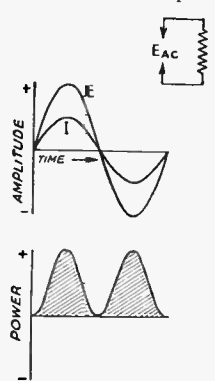


Fig. 230 — Voltage, current and power relations in an alternating-current circuit consisting of resistance only.

Frequencies above 15,000 cycles (15 kilocycles) are used for radio communication, because at frequencies of this order it is possible to convert electrical energy into radio waves which can be radiated over long distances.

For convenience in reference, the following classifications for radio frequencies have been recommended by an international technical conference and are now increasingly in use:

10 to 30 kilocycles	Very-low frequencies
30 to 300 kilocycles	Low frequencies
300 to 3000 kilocycles	Medium frequencies
3 to 30 megacycles	High frequencies
30 to 300 megacycles	Very-high frequencies
300 to 3000 megacycles	Ultrahigh frequencies
3000 to 30,000 megacycles	Super-high frequencies

Until recently, other terminology was used; for example, the region above 30 megacycles formerly was considered the "ultrahigh" frequencies.

Waveform, harmonics — The sine wave is not only the simplest but for many purposes is the most desirable waveform. Many other waveforms are met in practice, however, and they may differ considerably from the simple sine case. It is possible to show by analysis that any such waveform can be resolved into a number of components of differing frequencies and amplitudes, but related in frequency in such a way that all are integer multiples of

the lowest frequency present. The lowest frequency is called the *fundamental*, and the multiple frequencies are called *harmonics*. Thus a wave may consist of fundamental, 3rd, 5th, and 7th harmonics, meaning, if the fundamental frequency is say 100 cycles, that frequencies of 300, 500 and 700 cycles also are present in the wave.

Fig. 231 shows how a fundamental and a second harmonic might combine to form a non-sinusoidal wave. An infinite number of waveforms could be obtained from the combination of two such waves, since the shape of the combined wave will depend upon the amplitude and phase of the two component waves.

The square wave, also shown in Fig. 231, consists of a fundamental and an infinite number of harmonics. This type of wave is useful in a variety of applications.

2-8 Ohm's Law for Alternating Currents

Resistance — Since current and voltage are always in phase through a resistance, the instantaneous relations for a.c. are equivalent to those in d.c. circuits. By definition, the effective units of current and voltage for a.c. are made equal to those for d.c. in resistive circuits (§ 2-7). Therefore the various formulas expressing Ohm's Law for d.c. circuits apply without any change to a.c. circuits containing resistance only, or for purely resistive parts of complex a.c. circuits. See § 2-6.

In applying the formulas, it must be remembered that consistent units must be used. For example, if the instantaneous value of current is used in finding voltage or power, the voltage found will be the instantaneous voltage and the power will be the instantaneous power. Likewise, if the effective value is used for one quantity in the formula, the unknown will be expressed in effective value. Unless otherwise indicated, the effective value of current or voltage is always understood to be meant when reference is made to "current" or "voltage."

Reactance — In the preceding section it was shown that energy-storage effects in inductance and capacitance cause a phase difference to exist between the applied voltage and the cur-

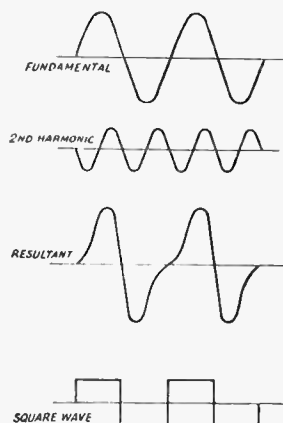


Fig. 231 — Combination of a fundamental and second harmonic with the amplitude and phase relationships shown gives the non-sinusoidal resultant. The square wave, below, contains an infinite number of harmonics.

rent that flows as a result. Because of this, Ohm's Law cannot be applied in its entirety to a.c. circuits containing inductance and/or capacitance, particularly for the calculation of power consumed. However, the amplitude of the current that flows in such circuits is directly proportional to the voltage applied, just as it is in purely resistive circuits. In other words, both inductance and capacity offer opposition to current flow, and this opposition can be measured in ohms just as it is in the case of resistance. But the opposition is called *reactance* to indicate that it does not consume power and thereby distinguish it from resistance.

Ohm's Law formulas extended to include reactance are quite similar to the formulas for resistive circuits:

$$I = \frac{E}{X} \quad E = XI \quad X = \frac{E}{I}$$

where X is the symbol for reactance.

Reactance differs from resistance in another respect - its value, for a given amount of inductance or capacity, varies with the frequency of the current flowing, whereas resistance is not inherently affected by frequency. However, the reactance of a given inductance or capacity is constant for all values of applied voltage so long as the frequency is constant.

Inductive reactance - When alternating current flows through an inductance it must take just the right value to make the induced voltage equal the applied voltage (§ 2-7). Since the induced voltage is equal to the inductance multiplied by the rate of change of the current, it is evident that the larger the value of inductance considered, the smaller the rate of current change required to induce a given voltage. If the frequency is fixed, the rate at which the alternating current changes is simply proportional to the amplitude of the current. Hence a small current will suffice if the inductance is large, while a large current will be required if the inductance is small, assuming that the applied voltage is the same in both cases. In other words, the reactance of an inductance is directly proportional to the value of the inductance, at a fixed frequency.

However, the rate of change of current is proportional to *frequency* as well as to amplitude, because the greater the number of cycles per second the more rapidly the current goes through its regular variations. Consequently, increasing the frequency will have the same effect as increasing the amplitude of the current insofar as the induced voltage is concerned; or, to put it another way, if the frequency is increased the amplitude may be decreased in the same proportion to maintain the same induced voltage in a given inductance. Smaller current amplitude through a fixed value of inductance means that the reactance is higher, so it is apparent that the reactance of an inductance increases with increasing frequency.

Thus three factors, inductance, current amplitude, and frequency (angular velocity) de-

termine the induced voltage. Combining them, we have, for sine-wave current,

$$E = 2\pi fLI, \text{ or } \frac{E}{I} = 2\pi fL$$

Since $X = E/I$, then

$$X_L = 2\pi fL$$

where the subscript L indicates that the reactance is inductive.

The fundamental units (ohms, cycles, henrys) must be used in the above equation, or appropriate factors inserted if other units are employed. If inductance is in millihenrys, the frequency should be stated in kilocycles; if inductance is in microhenrys, the frequency should be given in megacycles, to bring the answer in ohms.

Capacitive reactance - The quantity of electricity stored in a condenser depends upon the capacity and the applied voltage ($Q = CE$), and if losses are negligible the same quantity of electricity is taken out of the condenser on discharge. Current must flow into the condenser to charge it, and must flow out of it to discharge it; the value of the current is the rate at which the quantity of electricity is put into the condenser or taken out (§ 2-4). When an a.c. voltage is applied to a condenser the alternate movement of a quantity of electricity to charge and discharge it as the applied voltage rises and falls and reverses polarity, constitutes current flow "through" the condenser.

The amplitude of the current at any instant is proportional to the rate of change of the voltage at that instant; the greater the rate of change the faster the given quantity of electricity is moved. The amplitude is also proportional to the capacitance of the condenser, since a larger capacitance will take a larger quantity of electricity at a given voltage. Since the rate of change of voltage is proportional to the amplitude of the voltage and its frequency, then for a sine-wave voltage

$$I = 2\pi fCE, \text{ or } \frac{E}{I} = \frac{1}{2\pi fC}$$

Since $X = E/I$, then

$$X_C = \frac{1}{2\pi fC}$$

where the subscript C indicates that the reactance is capacitive. Capacitive reactance is *inversely* proportional to capacity and to the applied frequency. For a given value of capacity, the reactance decreases as the frequency increases.

Fundamental units (farads, cycles per second) must be used in the right-hand side of the equation to obtain the reactance in ohms. Conversion factors must be used if the frequency and capacity are in units other than cycles and farads. If C is in microfarads and f in megacycles, the conversion factors cancel.

Impedance - In any series circuit the same current flows through all parts of the circuit. If a resistance and inductance are connected in series to form an a.c. circuit they both carry

the same current, but the voltage across the resistance is in phase with the current while the voltage across the inductance leads the current by 90 degrees. In a d.c. circuit with resistances in series, the applied voltage is equal to the sum of the voltages across the individual resistances (§ 2-6). This is also true of the a.c. circuit with resistance and inductance in series if the *instantaneous* voltages are added algebraically to find the instantaneous value of applied voltage. But, because of the phase difference between the two voltages, the maximum value of the applied voltage will not be the sum of the maximum values of the two voltages, so that the effective values cannot be added directly. The same considerations hold in the case of resistance and capacity in series.

In either case the total voltage is given by the following expressions:

$$E = E^2_X + E^2_R, \text{ or } E = \sqrt{E^2_R + E^2_X}$$

where E_X indicates the voltage across the reactance, which may be either inductive or capacitive, and E_R is the voltage across the resistance.

Since $E_R = IR$ and $E_X = IX$, substitution gives

$$E = I \sqrt{R^2 + X^2}, \text{ or } \frac{E}{I} = \sqrt{R^2 + X^2}$$

E/I is called the *impedance* of the circuit and is designated by the letter Z . Hence,

$$Z = \sqrt{R^2 + X^2}$$

The impedance determines the voltage which must be applied to the circuit to cause a given current to flow. The unit of impedance is, therefore, the ohm, just as in the case of resistance and reactance, which also determine the ratio of voltage to current. Ohm's Law for alternating current circuits then becomes

$$I = \frac{E}{Z}; Z = \frac{E}{I}; E = IZ$$

It should be noted that the equivalent Ohm's Law relationship for *power* in a d.c. circuit does not apply directly in the case of an a.c. circuit, where Z replaces R . As will be explained, the power factor of the circuit must be taken into consideration.

In summary, impedance is a generalized quantity applying to a.c. or d.c. circuits, simple or complex. In a d.c. circuit or in an a.c. circuit containing resistance only, the phase angle is zero (current and voltage are in phase) and the impedance is equal to the resistance.

In an a.c. circuit containing reactance only the phase angle is 90 degrees, with current lagging the voltage if the reactance is inductive and current leading the voltage if the reactance is capacitive. In either case, the impedance is equal to the reactance.

In an a.c. circuit containing both resistance and reactance the phase angle may have any

value between zero and 90 degrees, with the current lagging the voltage if the reactance is inductive and leading the voltage if the reactance is capacitive. The value of impedance, in ohms, may be found from the equation given above.

Power is consumed in a circuit only when the current flow produced by the applied voltage is less than 90 degrees out of phase with that voltage. Power consumption decreases from maximum with in-phase conditions to zero at a 90-degree phase difference.

Series circuits with L, C and R—When inductance, capacity and resistance all are in series in an a.c. circuit, the voltage relations are a combination of the separate cases just considered. The voltage across each element will be proportional to the resistance or reactance of that element, since the current is the same through all. The voltages across the inductance and capacity are 180 degrees out of phase, since one leads the current by 90 degrees and the other lags the current by 90 degrees. This means that the two voltages tend to cancel; in fact, if the voltage across only the inductance and capacity in series is considered (leaving out the resistance), the total voltage is the *difference* between the two voltages.

The *total* reactance in a series circuit is, therefore, the difference between the individual inductive and capacitive reactances; or

$$X = X_L - X_C$$

If more than one inductance element is present in the circuit, the total inductive reactance is the sum of the individual reactances; similarly, the same is true for capacitive reactances. Inductive reactance is conventionally taken as "positive" (+) in sign and capacitive reactance as "negative" (-). With this convention, algebraic addition of all the reactances in a series circuit gives the total reactance of the circuit.

Parallel circuits with L, C and R—The equivalent resistance of a number of resistances in parallel in an a.c. circuit is found by the same rules as in the case of d.c. circuits (§ 2-6). Parallel reactances of the same kind have an equivalent reactance given by a similar rule:

$$\frac{1}{X} = \frac{1}{X_1} + \frac{1}{X_2} + \frac{1}{X_3} + \dots$$

This formula applies to reactances of the same sign; it cannot be used if both inductive and capacitive reactance are in parallel.

When both resistance and reactance are in parallel the same voltage is applied to both, but the current in the resistance branch will not be in phase with the current in the reactive branch. The phase difference will be 90 degrees if each branch contains *only* resistance or *only* reactance, so that the total current may be found by a rule similar to that used for finding

the total voltage in a series circuit. That is,

$$I = \sqrt{I_R^2 + I_X^2}$$

The impedance of the circuit is equal to E/I , so

$$Z = \frac{E}{\sqrt{I_R^2 + I_X^2}}$$

By assuming some convenient value for the applied voltage and then solving for the currents in the resistance and reactance, the values so found may be substituted in this equation to find the impedance of the circuit.

The formulas above may be used for either inductive or capacitive reactance. When inductive reactance and capacitive reactance are in parallel, the current through the inductance is 180 degrees out of phase with the current through the condenser, hence the total current is the *difference* between the two currents. This difference may be substituted for I_X in the above equations.

It is of interest to note that, since the total current flowing in a circuit containing inductive and capacitive reactance in parallel is the difference between the currents in the two branches, the impedance of such a parallel combination always is larger than the reactance of either branch alone. Any resistance which also may be in parallel is unaffected, since the current taken by the resistance is determined solely by the applied voltage.

With series-parallel circuits the solution becomes considerably more complicated, since the phase relationships in any parallel branch may not be either 90 degrees or zero. However, the majority of parallel circuits used in radio work can be solved by the rather simple approximate methods described in § 2-10.

Power factor—The power dissipated in an a.c. circuit containing both resistance and reactance is consumed entirely in the resistance, hence is equal to I^2R . However, the reactance is also effective in determining the current or voltage in the circuit, even though it consumes no energy. Hence the product of volts times amperes (which gives the power consumed in d.c. circuits) for the whole circuit may be several times the actual power used up. The ratio of power dissipated (watts) to the *volt-ampere* product is called the power factor of the circuit, or

$$\text{Power factor} = \frac{\text{Watts}}{\text{Volt-amperes}}$$

Distributed capacity and inductance—It should not be thought that the reactance of coils becomes infinitely high as the frequency is increased to a high value and, likewise, that the reactance of condensers becomes infinitely low at high frequencies. All coils have some capacity between turns, and the reactance of this capacity can become low enough at some high frequencies to tend to cancel the high reactance of the coil. Likewise, the leads and plates of condensers will have considerable inductance at very high frequencies, which will

tend to offset the capacitive reactance of the condenser itself. For these reasons, coils constructed for high-frequency use must be designed to have low "distributed" capacity. Similarly, condensers must be made with short, heavy leads so that they will have low self-inductance.

Units and instruments—The units used in a.c. circuits may be divided or multiplied to give convenient numerical values to different orders of magnitude, just as in d.c. circuits (§ 2-6). Because the rapidly reversing current is accompanied by similar reversals in the magnetic field, instruments used for measurement of d.c. (§ 2-6) will not operate on a.c.

At low frequencies suitable instruments can be constructed by making the current produce both magnetic fields, one by means of a fixed coil and the other by the moving coil. Instruments having movements of this kind are variously known as *dynamometer*, *electrodynamometer* and *electrodynamic* types.

Another type of instrument suitable for measuring alternating current is less expensive in construction and therefore more widely used. This is the *repulsion-type* moving-iron ammeter shown in Fig. 232. Fundamentally, the movement is based on the same principle as the inexpensive moving-iron-vane meter for d.c. shown in Fig. 225. In the repulsion-type instrument current flowing through the stationary coil magnetizes two iron vanes, one

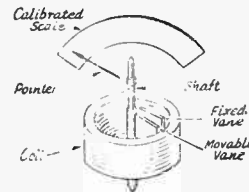


Fig. 232 — Ammeter based on a repulsion-type moving-iron movement used for a.c. measurements.

fixed and the other attached to the moving pointer shaft. Inasmuch as the two vanes are in the same plane and magnetized by the same source, the magnetic effect upon them by the current through the coil will be identical regardless of its polarity. When the two vanes are magnetized they repel each other (§ 2-2) and the movable vane moves away from the fixed vane, causing the pointer to travel along the scale. The degree of travel is controlled by a spring which brings the pointer to rest at a point where the electrical and mechanical forces balance, and returns the pointer to zero on the scale when current flow ceases.

Such instruments are used for measurement of either current or voltage. However, when employed for voltage measurement by the use of high-resistance series multipliers, the minimum current drain required by such instruments because of their inherent insensitivity is so great that excessive load is placed upon the measurement source. For this reason, in radio work it is more common practice to convert the a.c. voltage to d.c. by means of a

copper-oxide or vacuum-tube rectifier and then measure the resulting indication on a d.c. instrument, as described in § 2-6.

At radio frequencies instruments of the type described above are inaccurate because of distributed capacity and other effects, and the only reliable type of direct-reading instrument is the *thermocouple* ammeter or milliammeter. This is a power-operated device consisting of a resistance wire heated by the flow of r.f. current through it, to which is attached a thermocouple or pair of wires of dissimilar metals joined together and possessing the property of developing a small d.c. voltage between the terminals when heated. This voltage, which is proportional to the heat applied to the couple, is used to operate a d.c. instrument of ordinary design.

2-9 The Transformer

Principles—It has been shown in the preceding sections that, when an alternating voltage is applied to an inductance, the flow of alternating current through the coil causes an induced e.m.f. which is opposed to the applied e.m.f. The induced e.m.f. results from the varying magnetic field accompanying the flow of alternating current. If a second coil is brought into the same field, a similar e.m.f. likewise will be induced in this coil. This induced e.m.f. may be used to force a current through a wire, resistance or other electrical device connected to the terminals of the second coil.

Two coils operating in this way are said to be *coupled*, and the pair of coils constitutes a *transformer*. The coil connected to the source of energy is called the *primary* coil, and the other is called the *secondary* coil. Energy may be taken from the secondary, being transferred from the primary through the medium of the varying magnetic field.

Types of transformers—The usefulness of the transformer lies in the fact that energy can be transferred from one circuit to another without direct connection, and in the process can be readily changed from one voltage level to another. Thus, if a device to be operated requires, for example, 120 volts and only a 440-volt source is available, a transformer can be used to change the source voltage to that required. The transformer, of course, can be used only on a.c., since no voltage will be induced in the secondary if the magnetic field is not changing. If d.c. is applied to the primary of a transformer, a voltage will be induced in the secondary only at the instant of closing or opening the primary circuit, since it is only at these times that the field is changing.

As shown in Fig. 233, the primary and secondary coils of a transformer may be wound on a *core* of magnetic material. This increases the inductance of the coils so that a relatively small number of turns may be used to induce a given value of voltage with a small current. A *closed* core (one having a continuous magnetic path) such as that shown in Fig. 233

also tends to insure that practically all of the field set up by the current in the primary coil will cut the turns of the secondary coil. However, the core introduces a power loss because of *hysteresis*, an effect which occurs because the iron tends to retain its magnetism, and hence requires the expenditure of energy to overcome this *residual* magnetism every time the alternating current reverses in direction, and because of *eddy currents*, or currents induced in the core by the varying magnetic field.

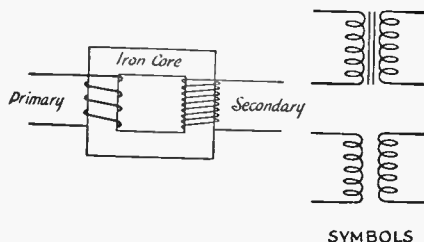


Fig. 233 — The transformer. Power is transferred from the primary coil to the secondary by means of the magnetic field. The upper symbol at right indicates an iron-core transformer, the lower one an air-core transformer.

Core losses increase with frequency to such an extent that they become excessive at radio frequencies if a transformer is wound on the type of core used for power and audio frequencies. Transformers for use at radio frequencies either are wound on non-magnetic material ("air core") or on special cores made of powdered iron particles held in an insulating binder. In the latter case the core is not used as a means of carrying the magnetic field from the primary to the secondary, but simply to give a larger inductance with a fixed number of turns. In radio-frequency transformers relatively little of the magnetic flux set up by the primary cuts the turns of the secondary. The discussion in this section is confined to low-frequency iron-core transformers, where practically all of the primary flux cuts the secondary. Radio-frequency transformers are considered in § 2-10.

Voltage and turns ratio—For a given varying magnetic field, the voltage induced in a coil in the field will be proportional to the number of turns on the coil. If the two coils of a transformer are in the same field, it follows that the induced voltages will be proportional to the number of turns on each coil. In the case of the primary, or coil connected to the source of power, the induced voltage is practically equal to, and opposes, the applied voltage. Hence, for all practical purposes,

$$E_s = \frac{n_s}{n_p} E_p$$

where E_s is the secondary voltage, E_p is the primary voltage, and n_s and n_p are the number of turns on the secondary and primary, respectively. The ratio n_s/n_p is called the *turns ratio* of the transformer.

This relationship is true *only* when all the flux set up by the primary current cuts all the turns of the secondary. If some of the magnetic flux follows a path which does not make it cut the secondary turns then the secondary voltage is less than given by this formula, since this reduces the number of lines of force (and thus reduces the effective strength of the magnetic field affecting the secondary) by causing the rate of change of flux to be less in the secondary than in the primary. In general, the equation can be used only when both coils are wound on a closed core of high permeability, so that practically all of the flux can be confined to definite paths.

Effect of secondary current — The primary current which has been discussed above is usually called the *magnetizing current* of the transformer. Like the current in any inductance, it lags the applied voltage by 90 degrees, neglecting the small energy losses in the resistance of the primary coil and in the iron core.

When current is drawn from the secondary winding, the secondary current sets up a magnetic field of its own in the core. The phase relationship between this field and that caused by the magnetizing current will depend upon the phase relationship between current and voltage in the secondary circuit. In every case there will be an effect upon the original field. To maintain the induced primary voltage equal to the applied voltage, however, the original field *must* be maintained. Consequently, the primary current must change in such a way that the effect of the field set up by the secondary current is completely canceled. This is accomplished when the primary draws additional current that sets up a field exactly equal to the field set up by the secondary current, but which opposes the secondary field. The additional primary current is thus 180 degrees out of phase with the secondary current.

In rough calculations on transformers it is convenient to neglect the magnetizing current and to assume that the primary current is caused entirely by the secondary load. This is justifiable, because in any well-designed transformer the magnetizing current is quite small in comparison to the load current when the latter is near the rated value.

For the fields set up by the primary and secondary load currents to be equal, the number of ampere turns in the primary must equal the number of ampere turns in the secondary. That is,

$$n_s I_s = n_p I_p$$

Hence,

$$I_p = \frac{n_s}{n_p} I_s$$

The load current in the primary for a given load current in the secondary is proportional to the turns ratio, secondary to primary. This is the opposite of the voltage relationships.

If the magnetizing current is neglected, the phase relationship between current and voltage

in the primary circuit will be identical with that existing between the secondary current and voltage. This is because the applied voltage and induced voltage are 180 degrees out of phase, and the primary current and secondary current likewise are 180 degrees out of phase.

Energy relationships: efficiency — A transformer cannot create energy; it can only transfer and transform it. Hence, the power taken from the secondary cannot exceed that taken by the primary from the source of applied e.m.f. Since there is always some power loss in the resistance of the coils and in the iron core, the power taken from the source always will exceed that taken from the secondary. Thus,

$$P_o = n P_i$$

where P_o is the power taken from the secondary, P_i is the power input to the primary, and n is a factor which always is less than 1. It is called the *efficiency* of the transformer and is usually expressed as a percentage. The efficiency of small power transformers such as are used in radio receivers and transmitters may vary between about 60 per cent and 90 per cent, depending upon the size and design.

Leakage reactance — In a practical transformer not all of the magnetic flux is common to both windings, although in well-designed transformers the amount of flux which cuts one coil and not the other is only a small percentage of the total flux. This *leakage flux* acts in the same way as flux about any coil which is not coupled to another coil; that is, it gives rise to self-induction. Consequently, there is a small amount of *leakage inductance* associated with both windings of the transformer, but not common to them. Leakage inductance acts in exactly the same way as an equivalent amount of ordinary inductance inserted in series with the circuit. It has, therefore, a certain reactance, depending upon the amount of inductance and the frequency. This reactance is called *leakage reactance*.

In the primary the practical effect of leakage reactance is equivalent to a reduction in applied voltage, since the primary current flowing through the leakage reactance causes a voltage drop. This voltage drop increases with increasing primary current, hence it increases as more current is drawn from the secondary. The induced voltage consequently decreases, since the applied voltage (which the induced voltage must equal in the primary) has been effectively reduced. The secondary induced voltage also decreases proportionately. When current flows in the secondary circuit the secondary leakage reactance causes an additional voltage drop, which results in a further reduction in the voltage available from the secondary terminals. Thus, the greater the secondary current, the smaller the secondary terminal voltage becomes. The resistance of the primary and secondary windings of the transformer also causes voltage drops when current is flowing, and, although these voltage

drops are not in phase with those caused by leakage reactance, together they result in a lower secondary voltage under load than is indicated by the turns ratio of the transformer.

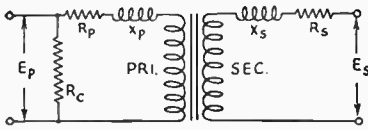


Fig. 234—The equivalent circuit of a transformer includes the effects of leakage inductance and resistance of both primary and secondary windings. The resistance R_c is an equivalent resistance representing the constant core losses. Since these are comparatively small, their effect may be neglected in many approximate calculations.

At power frequencies (60 cycles) the voltage at the secondary, with a reasonably well-designed transformer, should not drop more than about 10 per cent under load. The drop in voltage may be considerably more than this in a transformer operating at audio frequencies, however, since the leakage reactance in a transformer increases directly with the frequency.

Impedance ratio—In an ideal transformer having no losses or leakage reactance, the primary and secondary volt-amperes are equal; that is,

$$E_p I_p = E_s I_s$$

On this assumption, and by making use of the relationships between voltage, current and turns ratio previously given, it can be shown that

$$\frac{E_p}{I_p} = \frac{E_s}{I_s} \left(\frac{n_p}{n_s} \right)^2$$

Since $Z = E/I$, E_s/I_s is the impedance of the load on the secondary circuit, and E_p/I_p is the impedance of the loaded transformer as viewed from the line. The equation states that the impedance presented by the primary of the transformer to the line, or source of power, is equal to the secondary load impedance multiplied by the square of the primary-to-secondary turns ratio. This primary impedance is called the *reflected impedance* or *reflected load*. The reflected impedance will have the same phase angle as the secondary load impedance, as previously explained. If the secondary load is resistive only, then the input terminals of the transformer primary will appear to the source of e.m.f. as a pure resistance.

In practice there is always some leakage reactance and power loss in the transformer, so that the relationship above does not hold exactly. However, it gives results which are adequate for many practical cases. The *impedance ratio* of the transformer consequently is considered to be equal to the square of the turns ratio, both ratios being taken from the same winding to the other.

Impedance matching—Many devices require a specific value of load resistance (or impedance) for optimum operation. The re-

sistance of the actual load which is to dissipate the power may differ widely from this value, hence the transformer, with its impedance-transforming properties, is frequently called upon to change the actual load to the desired value. This is called *impedance matching*. From the preceding paragraph,

$$\frac{n_s}{n_p} = \sqrt{\frac{Z_s}{Z_p}}$$

where n_s/n_p is the required secondary-to-primary turns ratio, Z_s is the impedance of the actual load, and Z_p is the impedance required for optimum operation of the device delivering the power.

Transformer construction—Transformers are generally built so that flux leakage is minimized insofar as possible. The magnetic path is laid out so that it is as short as possible, since this reduces its reluctance and hence the number of ampere-turns required for a given flux density, and also tends to minimize flux leakage. Two core shapes are in common use, as shown in Fig. 235. In the shell type both windings are placed on the inner leg, while in the core type the primary and secondary windings may be placed on separate legs, if desired. This is sometimes done when it is necessary to minimize capacity effects between the primary and secondary, or when there is a large difference of potential between primary and secondary.

Core material for small transformers is usually silicon steel, called "transformer iron." The core is built up of thin sheets, called *laminations*, insulated from each other (by a thin coating of shellac, for example) to prevent the flow of *eddy currents* which are induced in the iron at right angles to the direction of the field. If allowed to flow, these eddy currents would cause considerable loss of energy in overcoming the resistance of the core material. The separate laminations are overlapped, to make the magnetic path as continuous as possible and thus reduce leakage.

The number of turns required on the primary for a given applied e.m.f. is determined by the maximum permissible flux density in the

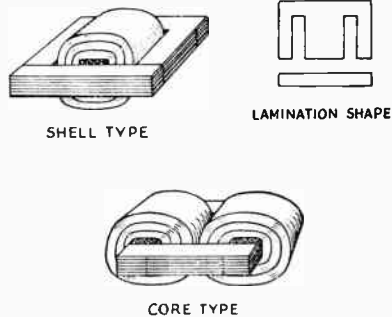


Fig. 235—Two common types of transformer construction. Core pieces are interleaved to provide a continuous magnetic path with as low reluctance as possible.

type of core material used, the frequency, and the magnetomotive force required to force the flux through the iron. As a rough indication, windings of small power transformers frequently have about two turns per volt for a core of 1 square inch cross-section and a magnetic path 10 or 12 inches in length. A longer path or smaller cross section would require more turns per volt, and vice versa.

In most transformers the coils are wound in layers, with a thin sheet of paper insulation between each layer. Thicker insulation is used between separate coils and between the coils and the core.

In power transformers distributed capacity in the windings is of little consequence, but in audio-frequency transformers it may cause undesired resonance effects (see § 2-10 for a discussion of resonance). High-grade audio transformers often have special types of windings designed to minimize distributed capacity.

The autotransformer—The transformer principle can be utilized with only one winding instead of two, as shown in Fig. 236; the principles just discussed apply equally well. The autotransformer has the advantage that, since

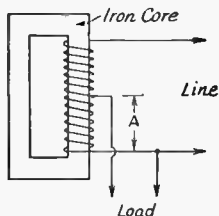


Fig. 236—The auto-transformer is based on the transformer principle, but uses only one winding. The line and load currents in the common winding (A) flow in opposite directions, so that the resultant current is the difference between them. The voltage across A is proportional to the turns ratio.

the line and load currents are out of phase, the section of the winding common to both circuits carries less current than the remainder of the coil. This advantage is not very marked unless the primary and secondary voltages do not differ very greatly, while it is frequently disadvantageous to have a direct connection between primary and secondary circuits. For these reasons, application of the autotransformer is usually limited to boosting or reducing the line voltage by a relatively small amount for purposes of voltage correction.

2-10 Resonant Circuits

Principle of resonance—It has been shown (§ 2-8) that the inductive reactance of a coil and the capacitive reactance of a condenser are oppositely affected by frequency. In any series combination of inductance and capacitance, therefore, there is one particular frequency for which the inductive and capacitive reactances are equal. Since these two reactances cancel each other, the net reactance in the circuit becomes zero, leaving only the resistance to impede the flow of current. The frequency at which this occurs is known as the *resonant frequency* of the circuit and the circuit is said to be *in resonance* at that frequency, or *tuned* to that frequency.

Series circuits—The frequency at which a series circuit is resonant is that for which $X_L = X_C$. Substituting the formulas for inductive and capacitive reactance (§ 2-8) gives

$$2\pi fL = \frac{1}{2\pi fC}$$

Solving this equation for frequency gives

$$f = \frac{1}{2\pi\sqrt{LC}}$$

This equation is in the fundamental units—cycles per second, henrys and farads—and so, if fractional or multiple units are used, the appropriate factors must be inserted to change them to the fundamental units. A formula in units commonly used in radio circuits is

$$f = \frac{1}{2\pi\sqrt{LC}} \times 10^6$$

where f is the frequency in kilocycles per second, 2π is 6.28, L is the inductance in microhenrys (μ h.), and C is the capacitance in micro-microfarads ($\mu\mu$ f.).

The resistance that may be present does not enter into the formula for resonant frequency.

When a constant a.c. voltage of variable frequency is applied, as shown in Fig. 237-A, the current flowing through such a circuit will be maximum at the resonant frequency. The magnitude of the current at resonance will be determined by the resistance in the circuit. The curves of Fig. 237 illustrate this, curve *a* being for low resistance and curves *b* and *c* being for increasingly greater resistances.

In the circuits used at radio frequencies the reactance of either the coil or condenser at resonance is usually several times as large as the resistance of the circuit, although the *net* reactance is zero. As the applied frequency departs from resonance, say on the low-frequency side, the reactance of the condenser increases and that of the inductance decreases, so that the net reactance (which is the difference between the two) increases rather rapidly. When it becomes several times as high as the resistance, it becomes the chief factor in determining the amount of current flowing. Hence, for circuits having the same values of inductance and capacity but varying amounts of resistance, the resonance curves tend to coincide at fre-

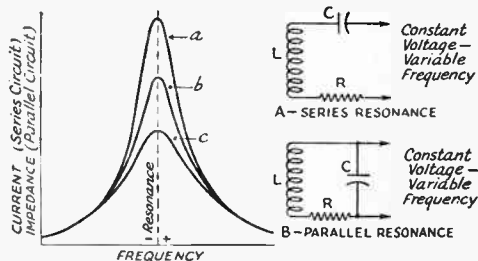


Fig. 237—Characteristics of series-resonant and parallel-resonant circuits with variations in resistance, R.

quencies somewhat removed from resonance. The three curves in the figure show this tendency.

Parallel circuits—The parallel-resonant circuit is illustrated in Fig. 237-B. This circuit also contains inductance, capacitance and resistance in series, but the voltage is applied in parallel with the combination instead of in series with it as in A. As explained in connection with parallel inductance and capacity (§ 2-8), the total current through such a combination is less than the current flowing in the branch having the smaller reactance. If the currents through the inductive and capacitive branches are equal in amplitude and exactly 180 degrees out of phase, the total current, called the *line current*, will be zero no matter how large the individual branch currents may be. The impedance ($Z = E/I$) of such a circuit, viewed from its parallel terminals, would be infinite. In practice the two currents will not be exactly 180 degrees out of phase, because there is always some resistance in one or both branches. This resistance makes the phase relationship between current and voltage less than 90 degrees in the branch containing it, hence the phase difference between the currents in the two branches is less than 180 degrees and the two currents will not cancel completely. However, the line current may be very small if the resistance is small compared to the reactance, and thus the parallel impedance at resonance may be very high.

As the applied frequency is increased or decreased from the resonant frequency, the reactance of one branch decreases and that of the other branch increases. The branch with the smaller reactance takes a larger current, if the applied voltage is constant, and that with the larger reactance takes a smaller current. As a result, the difference between the two currents becomes larger as the frequency is moved farther from resonance. Since the line current is the difference between the two currents, the current increases when the frequency moves away from resonance; in other words, the parallel impedance of the circuit decreases.

The variation of parallel impedance of a parallel-resonant circuit with frequency is illustrated by the same curves of Fig. 237 that show the variation in current with frequency for the series-resonant circuit. The parallel impedance at resonance increases as the series resistance is made smaller.

In the case of parallel circuits, resonance may be defined in three ways: the condition which gives maximum impedance, that which gives a power factor of 1 (impedance purely resistive), or (as in series circuits) when the inductive and capacitive reactances are equal. If the resistance is low, the resonant frequencies obtained on the three bases are practically identical. This condition usually is satisfied in radio work, so that the resonant frequency of a parallel circuit is generally computed by the series-resonance formula given above.

Resistance at high frequencies—When current flows in a conductor a magnetic field is set up inside the conductor as well as externally. When the current is alternating, the internal magnetic field induces a voltage inside the conductor which opposes the applied voltage and becomes larger as the center of the conductor is approached. As a result, the current is forced to distribute itself so that the greater proportion flows near the surface and less near the center. This is known as *skin effect*.

Skin effect is negligible at low frequencies, but increases with increasing frequency to such an extent that at radio frequencies the major portion of the current flows near the surface. In the u.h.f. range, all the current may be concentrated within one or two thousandths of an inch of the surface, so that for all practical purposes the current flows entirely on the surface.

Since little current flows in the interior of a conductor at radio frequencies, the effect is the same as though the current were flowing in a thin conducting tube. This is the same as reducing the cross-sectional area of the conductor, which increases its resistance. Consequently skin effect increases the resistance of a solid conductor as compared to its value for d.c. and low-frequency a.c.

Low resistance at radio frequencies can be achieved by using conductors with large surface area. Since the inner part of the conductor does not carry current, thin-walled tubing may be used for coils equally as well as solid wire of the same diameter.

In the case of inductance coils, the magnetic field close to the wire causes the current to tend to concentrate in the part of the conductor where the field is weakest, again causing an effective decrease in the conductor size and raising the resistance. These effects, plus the effects of stray currents flowing through the distributed capacity (§ 2-8) between turns, raise the effective resistance of a coil at radio frequencies to many times the d.c. resistance of the wire.

Sharpness of resonance—As the internal series resistance is increased the resonance curves become "flatter" for frequencies near the resonance frequency, as shown in Fig. 237. The relative sharpness of the resonance curve near resonance frequency is a measure of the *sharpness of tuning* or *selectivity* (ability to discriminate between voltages of different frequencies) in such circuits. This is an important consideration in tuned circuits for radio work.

Flywheel effect; Q—A resonant circuit may be compared to a flywheel in its behavior. Just as such a wheel will continue to revolve after it is no longer driven, so also will oscillations of electrical energy continue in a resonant circuit after the source of power is removed. The flywheel continues to revolve because of its stored mechanical energy; current flow continues in a resonant circuit by virtue of the energy stored in the magnetic field of the coil and the electric field of the condenser. When

the applied power is shut off the energy surges back and forth between the coil and condenser, being first stored in the field of one, then released in the form of current flow, and then re-stored in the field of the other. Since there is always resistance present some of the energy is lost as heat in the resistance during each of these *oscillations* of energy, and eventually all the energy is so dissipated. The length of time the oscillations will continue is proportional to the ratio of the energy stored to that dissipated in each cycle of the oscillation. This ratio is called the Q (quality factor) of the circuit.

Since energy is stored by either the inductance or capacity and may be dissipated in either the inductive or capacitive branch of the circuit, a Q can be established for either the inductance or capacity alone as well as for the entire circuit. It can be shown that the energy stored is proportional to the reactance and that the energy dissipated is proportional to the resistance, so that, for either inductance or capacity associated with resistance,

$$Q = \frac{X}{R}$$

This relationship is useful in a variety of circuit problems.

In resonant circuits at frequencies below about 28 Mc. the internal resistance is almost wholly in the coil; the condenser resistance may be neglected. Consequently, the Q of the circuit as a whole is determined by the Q of the coil. Coils for use at frequencies below the very-high-frequency region may have Q s ranging from 100 to several hundred, depending upon their size and construction.

The sharpness of resonance of a tuned circuit is directly proportional to the Q of the circuit. As an indication of the effect of Q , the current in a series circuit drops to a little less than half its resonance value when the applied frequency is changed by an amount equal to $1/Q$ times the resonant frequency. The parallel impedance of a parallel circuit similarly decreases with change in frequency. For example, in a circuit having a Q of 100, changing the applied frequency by $1/100$ th of the resonant frequency will decrease the parallel impedance to less than half its value at resonance.

Damping, decrement — The rate at which current dies down in amplitude in a resonant circuit after the source of power has been removed is called the *decrement* or *damping* of the circuit. A circuit with high decrement (low Q) is said to be highly damped; one with low decrement (high Q) is lightly damped.

Voltage rise — When a voltage of the resonant frequency is inserted in series in a resonant circuit, the voltage which appears across either the coil or condenser is considerably higher than the applied voltage. This is because the current in the circuit is limited only by the actual resistance of the coil-condenser combination in the circuit, and hence may have a relatively high value; however, the same

current flows through the high reactances of the coil and condenser, and consequently causes large voltage drops (§ 2-8). As explained above, the reactances are of opposite types and hence the voltages are opposite in phase, so that the net voltage around the circuit is only that which is applied. The ratio of the reactive voltage to the applied voltage is proportional to the ratio of reactance to resistance, which is the Q of the circuit. Hence, the voltage across either the coil or condenser is equal to Q times the voltage inserted in series with the circuit.

If, for example, the inductive reactance of a circuit is 200 ohms, the capacitive reactance is 200 ohms, the resistance 5 ohms, and the applied voltage is 50, the two reactances cancel and there will be but the 5 ohms of pure resistance to limit the current flow. Thus the current will be $50/5$, or 10 amperes. The voltage developed across either the coil or the condenser will be equal to its reactance times the current, or $200 \times 10 = 2000$ volts.

The ratio of reactive voltage to applied voltage is equal to the ratio of the reactance of the coil or the condenser to the resistance. Since the latter ratio equals the Q of the circuit, the reactive voltage equals the applied voltage times the Q ($200/5$ or $40 \times 50 = 2000$ volts).

Parallel-resonant circuit impedance — The parallel-resonant circuit offers pure resistance (its *resonant impedance*) between its terminals because the line current is practically in phase with the applied voltage. At frequencies off resonance the current increases through the branch having the lower reactance (and vice versa) so that the circuit becomes reactive, and the resistive component of the impedance decreases as shown in Fig. 238.

If the circuit Q is 10 or more, the parallel impedance at resonance is given by the formula

$$Z_r = X^2/R = XQ$$

where X is the reactance of either the coil or the condenser and R is the internal resistance.

Q of loaded circuits — In many applications, particularly in receiving, the only power dissipated is that lost in the resistance of the resonant circuit itself. Hence the coil should be designed to have as high Q as possible. Since, within limits, increasing the number of turns raises the reactance faster than it raises the

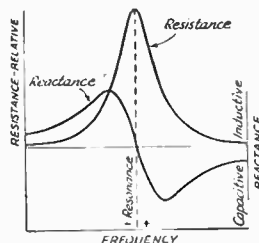


Fig. 238 — The impedance of a parallel-resonant circuit is shown here separated into its reactance and resistance components. The parallel resistance of the circuit is equal to the parallel impedance at resonance.

resistance, coils for such purposes are made with relatively large inductance for the frequency under consideration.

On the other hand, when the circuit delivers energy to a load, as in the case of the resonant circuits used in transmitters, the energy consumed in the circuit itself is usually negligible compared with that consumed by the load. The equivalent of such a circuit can be represented as shown in Fig. 239-A, where the parallel resistor represents the load to which power is delivered. If the power dissipated in the load is greater by 10 times or more than the power lost in the coil and condenser, the parallel impedance of the resonant circuit alone will be so high compared to the resistance of the load that the latter may be considered to determine the impedance of the combined circuit. (The parallel impedance of the tuned circuit alone is resistive at resonance, so that the impedance of the combined circuit may be calculated from



Fig. 239 — The equivalent circuit of a resonant circuit delivering power to a load. The resistor *R* represents the load resistance. At (B) the load is tapped across part of *L*, which by transformer action is equivalent to using a higher load resistance across the whole circuit.

the formula for resistances in parallel. If one of two resistances in parallel has 10 times the resistance of the other, the resultant resistance is practically equal to the smaller resistance.) The error will be small, therefore, if the losses in the tuned circuit alone are neglected. Then, since $Z = XQ$, the *Q* of a circuit loaded with a resistive impedance is

$$Q = \frac{Z}{X}$$

where *Z* is the load resistance connected across the circuit and *X* is the reactance of either the coil or condenser. Hence, for a given parallel impedance, the effective *Q* of the circuit including the load is inversely proportional to the reactance of either the coil or the condenser. A circuit loaded with a relatively low resistance (a few thousand ohms) must therefore have a large capacity and relatively small inductance to have reasonably high *Q*.

From the above it is evident that connecting a resistance in parallel with a resonant circuit decreases the impedance of the circuit. However, the reactances in the circuit are unchanged, hence the reduction in impedance is equivalent to a reduction in the *Q* of the circuit. The same reduction in impedance also could be brought about by increasing the series resistance of the circuit. The equivalent series resistance introduced in a resonant circuit by an actual resistance connected in parallel is that value of resistance which, if added in series with the coil and condenser, would decrease the circuit *Q* to the same value it has when the parallel resistance is connected.

When the resistance of the resonant circuit alone can be neglected, the equivalent resistance is

$$R = \frac{X^2}{Z}$$

the symbols having the same meaning as in the formula above.

The effect of a load of given resistance on the *Q* of the circuit can be changed by connecting the load across only part of the circuit. The most common method of accomplishing this is by tapping the load across part of the coil, as shown in Fig. 239-B. The smaller the portion of the coil across which the load is tapped, the less the loading on the circuit; in other words, tapping the load "down" is equivalent to connecting a higher value of load resistance across the whole circuit. This is similar in principle to impedance transformation with an iron-core transformer (§ 2-9). However, in the high-frequency resonant circuit the impedance ratio does not vary exactly as the square of the turn ratio, because all the magnetic flux lines do not cut every turn of the coil. A desired reflected impedance usually must be obtained by experimental adjustment.

L/C ratio — The formula for resonant frequency of a circuit shows that the same frequency always will be obtained so long as the product of *L* and *C* is constant. Within this limitation, it is evident that *L* can be large and *C* small, *L* small and *C* large, etc. The relation between the two for a fixed frequency is called the *L/C ratio*. A *high-C* circuit is one which has more capacity than "normal" for the frequency; a *low-C* circuit one which has less than normal capacity. These terms depend to a considerable extent upon the particular application considered, and have no exact numerical meaning.

LC constants — As pointed out in the preceding paragraph, the product of inductance and capacity is constant for any given frequency. It is frequently convenient to use the numerical value of the *LC constant* when a number of calculations have to be made involving different *L, C* ratios for the same frequency. The constant for any frequency is given by the following equation:

$$LC = \frac{25330}{f^2}$$

where *L* is in microhenrys, *C* in micromicrofarads, and *f* is in megacycles.

2-11 Coupled Circuits

Energy transfer; loading -- Two circuits are said to be *coupled* when energy can be transferred from one to the other. The circuit delivering energy is called the primary circuit; that receiving energy is called the secondary circuit. The energy may be practically all dissipated in the secondary circuit itself, as in receiver circuits, or the secondary may simply act as a medium through which the energy is transferred to a load resistance where it does

work. In the latter case, the coupled circuits may act as a radio-frequency impedance-matching device (§ 2-9) where the matching can be accomplished by adjusting the loading on the secondary (§ 2-10) and by varying the coupling between the primary and secondary.

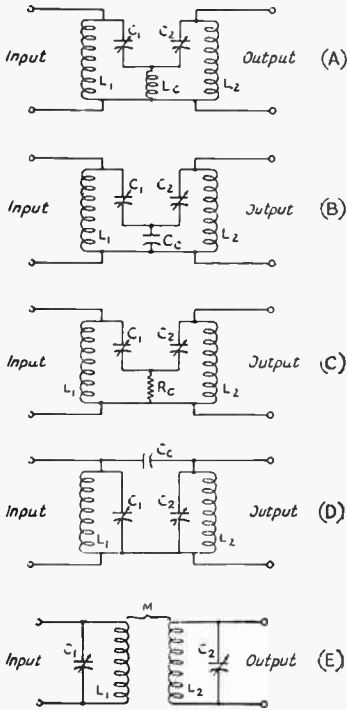


Fig. 240 — Basic methods of circuit coupling.

Coupling by a common circuit element — One method of coupling between two resonant circuits is to have some type of circuit element common to both circuits. The three variations of this type of coupling (often called *direct coupling*) shown at A, B and C of Fig. 240, utilize a common inductance, capacity and resistance, respectively. Current circulating in one LC branch flows through the common element (L_c , C_c , or R_c) and the voltage developed across this element causes current to flow in the other LC branch. The degree of coupling between the two circuits becomes greater as the reactance (or resistance) of the common element is increased in comparison to the remaining reactances in the two branches.

If both circuits are resonant to the same frequency, as is usually the case, the common impedance — reactance or resistance — required for maximum energy transfer is generally quite small compared to the other reactances in the circuits.

Capacity coupling — The circuit at D shows electrostatic coupling between two resonant circuits. The coupling increases as the capacity of C_c is made greater (reactance of C_c is decreased). When two resonant circuits are coupled by this means, the capacity required

for maximum energy transfer is quite small if the Q of the secondary circuit is at all high. For example, if the parallel impedance of the secondary circuit is 100,000 ohms, the reactance of the coupling condenser need not be lower than 10,000 ohms or so for ample coupling. The corresponding capacity required is only a few micromicrofarads at high frequencies.

Inductive coupling — Fig. 240-E illustrates inductive coupling, or coupling by means of the magnetic field. A circuit of this type resembles the iron-core transformer (§ 2-9) but, because only a small percentage of the flux lines set up by one coil cut the turns of the other coil, the simple relationships between turns ratio, voltage ratio and impedance ratio in the iron-core transformer do not hold. To determine the operation of such circuits, it is necessary to take account of the mutual inductance (§ 2-5) between the coils.

Link coupling — A variation of inductive coupling, called *link coupling*, is shown in Fig. 241. This gives the effect of inductive coupling between two coils which may be so separated that they have no mutual inductance; the link may be considered simply as a means of providing the mutual inductance. Because mutual inductance between coil and link is involved at each end of the link, the total mutual inductance between two link-coupled circuits cannot be made as great as when normal inductive coupling is used. In practice, however, this ordinarily is not disadvantageous. Link coupling frequently is convenient in the design of equipment where inductive coupling would be impracticable for constructional reasons.

The link coils generally have few turns compared to the resonant-circuit coils, since the coefficient of coupling is relatively independent of the number of turns on either coil.

Coefficient of coupling — The degree of coupling between two coils is a function of their mutual inductance and self-inductances:

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

where k is called the *coefficient of coupling*. It is often expressed as a percentage. The coefficient of coupling cannot be greater than 1, and generally is much smaller in resonant circuits.

Inductively coupled circuits — Three types of circuits with inductive coupling are in general use. As shown in Fig. 242, one type has a tuned-secondary circuit with an untuned-primary coil, the second a tuned-primary circuit and untuned-secondary coil, and the third uses tuned circuits in both the primary and

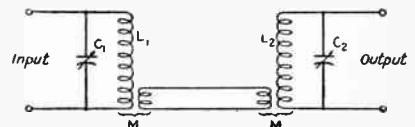


Fig. 241 — Link coupling. The mutual inductances at both ends of the link are equivalent to mutual inductance between the tuned circuits, and serve the same purpose.

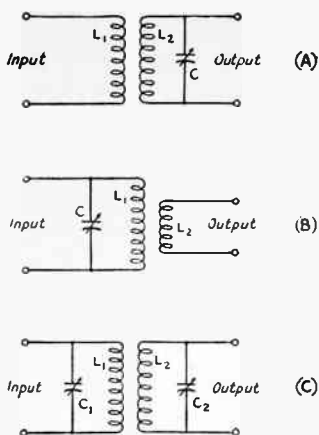


Fig. 242 — Types of inductively coupled circuits. In A and B one circuit is tuned, the other untuned. C shows the method of coupling between two tuned circuits.

secondary. The circuit at A is frequently used in receivers for coupling between amplifier tubes when the tuning of the circuit must be varied to respond to signals of different frequencies. Circuit B is used principally in transmitters, for coupling a radio-frequency amplifier to a resistive load. Circuit C is used for fixed-frequency amplification in receivers. The same circuit also is used in transmitters for transferring power to a load which has both reactance and resistance.

If the coupling between the primary and secondary is "tight" (coefficient of coupling large), the effect of inductive coupling in circuits A and B, Fig. 242, is much the same as though the circuit having the untuned coil were tapped on the tuned circuit (§ 2-10). Thus any resistance in the circuit to which the untuned coil is connected is coupled into the tuned circuit in proportion to the mutual inductance. This is equivalent to an increase in the series resistance of the tuned circuit, and its Q and selectivity are reduced (§ 2-10). The higher the coefficient of coupling, the lower the Q for a given value of resistance in the coupled circuit. These circuits may be used for impedance matching by adjustment of the coupling and of the number of turns in the untuned coil.

If the circuit to which the untuned coil is connected has reactance, a certain amount of reactance will be "coupled in" to the tuned circuit depending upon the amount of reactance present and the degree of coupling. The chief effect of this coupled reactance is to require readjustment of the tuning when the coupling is increased, if the tuned circuit has first been adjusted to resonance under conditions of very loose coupling.

Coupled resonant circuits— The effect of a tuned-secondary circuit on a tuned primary is somewhat more complicated than in the simpler circuits just described. When the secondary is tuned to resonance with the applied frequency, its impedance is resistive only. If the primary also is tuned to resonance, the current

flowing in the secondary circuit (caused by the induced voltage) will, in turn, induce a voltage in the primary which is opposite in phase to the voltage acting in series in the primary circuit. This opposing voltage reduces the effective primary voltage, and thus causes a reduction in primary current. Since the actual voltage applied in the primary circuit has not changed, the reduction in current can be looked upon as being caused by an increase in the resistance of the primary circuit. That is, the effect of coupling a resonant secondary to the primary is to increase the primary resistance. The resistance under consideration is the series resistance of the primary circuit, not the parallel impedance or resistance. The parallel resistance decreases, since the increase in series resistance reduces the Q of the primary circuit.

If the secondary circuit is not tuned to resonance, the voltage induced back in the primary by the secondary current will not be exactly out of phase with the voltage acting in the primary; in effect, reactance is coupled into the primary circuit. If the applied frequency is fixed and the secondary circuit tuning is being varied, this means that the primary circuit will have to be retuned to resonance each time the secondary tuning is changed.

If the two circuits are initially tuned to resonance at a given frequency and then the applied frequency is varied, both circuits become reactive at all frequencies off resonance. Under these conditions, the reactance coupled into the primary by the secondary retunes the primary circuit to a new resonant frequency. Thus, at some frequency off resonance, the primary current will be maximum, while at the actual resonant frequency the current will be smaller because of the resistance coupled in from the secondary at resonance. There is a point of maximum primary current both above and below the true resonant frequency.

These effects are almost negligible with very "loose" coupling (coefficient of coupling very small), but increase rapidly as the coupling increases. Because of them, the selectivity of a pair of coupled resonant circuits can be varied over a considerable range simply by changing the coupling between them. Typical curves showing the variation of selectivity are shown in Fig. 243, lettered in order of increasing co-

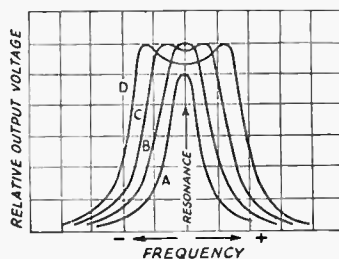


Fig. 243 — Showing the effect on the output voltage from the secondary circuit of changing the coefficient of coupling between two resonant circuits independently tuned to the same frequency. The input voltage is held constant in amplitude while the frequency is varied.

efficient of coupling. At loose coupling, A, the voltage across the secondary circuit (induced voltage multiplied by the Q of the secondary circuit) is less than the maximum possible because the induced voltage is small with loose coupling. As the coupling increases the secondary voltage also increases, until critical coupling, B, is reached. At still closer coupling the effect of the primary current "humps" causes the secondary voltage to show somewhat similar humps, while when the coupling is further increased the frequency separation of the humps becomes greater. Resonance curves such as those at C and D are called "flat-topped," because the output voltage is substantially constant over an appreciable frequency range.

Critical coupling — It will be observed that maximum secondary voltage is obtained in the curve at B in Fig. 243. With tighter coupling the resonance curve tends to be double-peaked, but in no case is such a peak higher than that shown for curve B. The coupling at which the secondary voltage is maximum is known as *critical coupling*. With this coupling the resistance coupled into the primary circuit is equal to the resistance of the primary itself, corresponding to the condition of matched impedances. Hence, the energy transfer is maximum at critical coupling. The over-all selectivity of the coupled circuits at critical coupling is intermediate between that obtainable with loose coupling and tight coupling. At very loose coupling, the selectivity of the system is very nearly equal to the product of the selectivities of the two circuits taken separately; that is, the effective Q of the circuit is equal to the product of the Q s of the primary and secondary.

Effect of circuit Q — Critical coupling is a function of the Q s of the two circuits taken independently. A higher coefficient of coupling is required to reach critical coupling when the Q s are low; if the Q s are high, as in receiving applications, a coupling coefficient of a few per cent may give critical coupling.

With loaded circuits it is not impossible for the Q to reach such low values that critical coupling cannot be obtained even with the highest practicable coefficient of coupling (coils as close physically as possible). In such case the only way to secure sufficient coupling is to increase the Q of one or both of the coupled circuits. This can be done either by decreasing the L/C ratio or by tapping the load down on the secondary coil (§ 2-10). One or the other of these methods often must be used with link coupling, because the maximum coefficient of coupling between two coils seldom runs higher than 50 or 60 per cent and the net coefficient is approximately equal to the products of the coefficients at each end of the link. If the load resistance is known beforehand, the circuits may be designed for a Q in the vicinity of 10 or so with assurance that sufficient coupling will be available; if unknown, the proper Q s can be determined by experiment.

Shielding — Frequently it is necessary to prevent coupling between two circuits which, for constructional reasons, must be physically near each other. Capacitive coupling may readily be prevented by enclosing one or both of the circuits in grounded low-resistance metallic containers, called *shields*. The electrostatic field from the circuit components does not penetrate the shield, because the lines of force are short-circuited (§ 2-3). A metallic plate called a *baffle shield*, inserted between two components, may suffice to prevent electrostatic coupling between them, since very little of the field tends to bend around such a shield if it is large enough to make the components invisible to each other.

Similar metallic shielding is used at radio frequencies to prevent magnetic coupling. In this case the magnetic field induces a current (*eddy current*) in the shield, which in turn sets up its own magnetic field opposing the original field (§ 2-5). The induced current is proportional to the frequency and also to the conductivity of the shield, hence the shielding effect increases with frequency and with the conductivity and thickness of the shielding material. A closed shield is required for good magnetic shielding; in some cases separate shields, one about each coil, may be required. The baffle shield is rather ineffective for magnetic shielding, although it will give partial shielding if placed at right angles to the axes of, as well as between, the two coils to be shielded from each other.

Cancellation of part of the field of the coil reduces its inductance, and, since some energy is dissipated in the shield, the effective resistance of the coil is raised as well. Hence the Q of the coil is reduced. The effect of shielding on coil Q and inductance becomes less as the distance between the coil and shield is increased. The losses also decrease with an increase in the conductivity of the shield material. Copper and aluminum are satisfactory materials. The Q and inductance will not be greatly reduced if the spacing between the sides of the coil and the shield is at least half the coil diameter, and is not less than the coil diameter at the ends of the coil.

At audio frequencies the shielding container should be made of magnetic material, preferably of high permeability (§ 2-5), to provide a low-reluctance path for the external flux about the coil to be shielded. A nonmagnetic shield is quite ineffectual at these low frequencies since the induced current is small.

Filters — By suitable choice of circuit elements a coupling system may be designed to pass, without undue attenuation, all frequencies below and reject all frequencies above a certain value, called the *cut-off frequency*. Such a coupling system is called a *filter*, and in the above case is known as a *low-pass filter*.

If frequencies above the cut-off frequency are passed and those below attenuated, the filter is a *high-pass filter*. Simple filter circuits of both

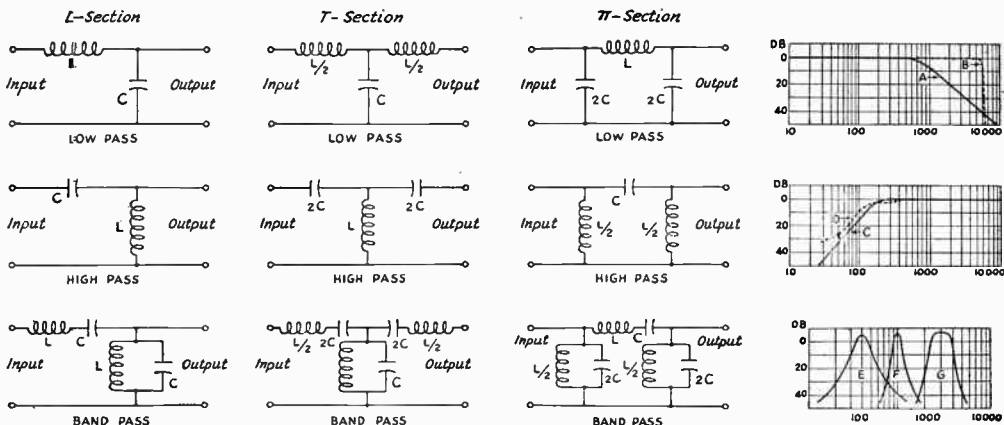


Fig. 244 — Basic forms of filter networks. Typical frequency response curves for each type are shown at the right.

types are shown in Fig. 244, along with typical frequency-response curves. The fundamental circuit, from which more complex filters are constructed, is the *L-section*. Fig. 244 also shows *π-section* and *T-section* filters, both constructed from the basic *L-section*.

A *band-pass* filter, also shown in Fig. 244, is a combination of high- and low-pass filter elements designed to pass without attenuation all frequencies between two selected cut-off frequencies, and to attenuate all frequencies outside these limits. The group of frequencies which is passed by the filter is called the *pass-band*. Two resonant circuits with greater than critical coupling represent a common form of band-pass filter.

In curves of Fig. 244, A shows the attenuation at high frequencies of a single-section low-pass filter with high-*Q* components; B illustrates the extremely sharp cut-off obtainable with a more elaborate three-section filter. Curve C is that of a high-pass section having high *Q*, comparable to A. D shows the attenuation by a less-efficient section having some resistance in the inductance branch. Curves E, F and G illustrate various band-pass characteristics, E being a low-*Q* narrow-band filter, F a high-*Q* narrow-band, and G a wide-band high-*Q* two-section filter.

Filter circuits are frequently encountered both in low-frequency and r.f. applications. The proportions of *L* and *C* for proper operation depend upon the load resistance connected across the output terminals, *L* being larger and *C* smaller as the load resistance is increased. The type of section does not affect the attenuation curve, provided the input and output resistances are correct. In a symmetrical filter the input and output impedances must be equal to the impedance for which the filter is designed. Assuming these relationships, the

following design equations apply to the sections illustrated in Fig. 244.

Low-pass filter:

$$L = \frac{R}{\pi f_c} \quad C = \frac{1}{\pi f_c R}$$

$$R = \frac{\sqrt{L_1}}{C_2} \quad f_c = \frac{1}{\pi \sqrt{L_1 C_2}}$$

High-pass filter:

$$L = \frac{R}{4\pi f_c} \quad C = \frac{1}{4\pi f_c R}$$

$$R = \frac{\sqrt{L_2}}{C_1} \quad f_c = \frac{1}{4\pi \sqrt{L_2 C_1}}$$

Band-pass filter:

$$L_1 = \frac{R}{\pi(f_2 - f_1)} \quad C_1 = \frac{f_2 - f_1}{4\pi f_1 f_2 R}$$

$$L_2 = \frac{(f_2 - f_1)R}{4\pi f_1 f_2} \quad C_2 = \frac{1}{\pi(f_2 - f_1)R}$$

$$R = \frac{\sqrt{L_1}}{C_2} = \frac{\sqrt{L_2}}{C_1} \quad f_M = \sqrt{f_1 f_2}$$

$$f_M = \frac{1}{2\pi \sqrt{L_1 C_1}} = \frac{1}{2\pi \sqrt{L_2 C_2}}$$

In these formulas, *R* is the terminal impedance and *f_c* the design cut-off frequency for low-pass and high-pass filters. For band-pass filters, *f₁* and *f₂* are the pass-band limits and *f_M* the middle frequency. *L₂* (*C₂*) the parallel shunt elements.

The *resistance-capacity filter*, shown in Fig. 245, is used where both d.c. and a.c. are flowing through a circuit and greater attenuation is desired for the a.c. than for d.c. It is usually employed where the direct current is small so that d.c. voltage drop is not excessive, or

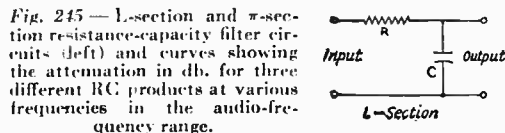


Fig. 245 — *L-section* and *π-section* resistance-capacity filter circuits (left) and curves showing the attenuation in db. for three different RC products at various frequencies in the audio-frequency range.

when a voltage drop actually is required. The time constant, RC , (§ 2-6) must be large compared to the time of one cycle of the lowest frequency to be attenuated. In determining the time constant, the resistance of the load must be included as well as that in the filter itself.

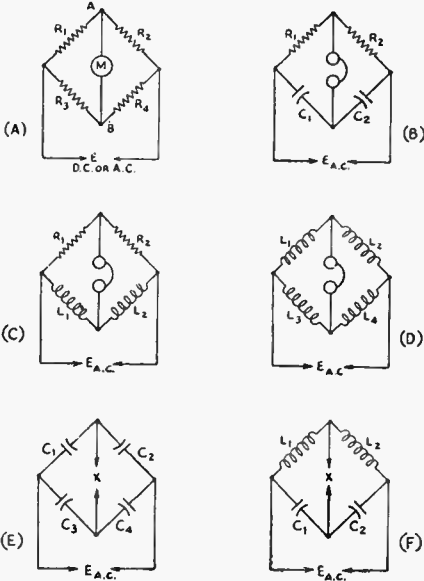


Fig. 246 — Bridge circuits utilizing resistance, inductance and capacity arms, both alone and in combination.

Bridge circuits — A bridge circuit is a device primarily used in making measurements of resistance, reactance or impedance (§ 2-8), and frequency, although bridges also have other applications in radio circuits.

The fundamental form is shown in Fig. 246-A. It consists of four resistances (called *arms*) connected in series-parallel to a source of voltage, E , with a sensitive galvanometer, M , connected between the junctions of the series-connected pairs. When the equation

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

is satisfied there is no potential difference between points A and B , since the drop across R_2 equals that across R_4 and the drop across R_1 equals that across R_3 . Under these conditions the bridge is said to be *balanced*, and no current flows through M . If R_3 is an unknown resistance and R_4 is a variable known resistance, R_3 can be found from the following equation after R_4 has been adjusted to balance the bridge (*null* indication on M):

$$R_3 = \frac{R_1}{R_2} R_4$$

R_1 and R_2 are known as the *ratio arms* of the bridge; the ratio of their resistances is usually adjustable (frequently in steps of 1, 10, 100, etc.), so that a single variable resistor, R_4 , can serve as a standard for measuring widely different values of unknown resistance.

Bridges similarly can be formed with arms containing capacity or inductance, and with combinations of either with resistance. Typical simple arrangements are shown in Fig. 246. For measurements involving alternating current the bridge must not introduce phase shifts which will destroy the balance, hence similar impedances should be used in each branch, as shown in Fig. 246, and the Q s of the coils and condensers should be the same. When bridges are used at audio frequencies, a telephone headset is a suitable null indicator. The bridges at E and F are commonly used in r.f. neutralizing circuits (§ 4-7); the voltage from the source, E_{ac} , is balanced out at X .

¶ 2-12-A Linear Circuits

Standing waves — If an electrical impulse is started along a wire, it will travel at approximately the speed of light until it reaches the end. If the end of the wire is open circuited, the impulse will be *reflected* at this point and will travel back again. When a high-frequency alternating voltage is applied to the wire a current will flow toward the open end, and reflection will occur continuously. If the wire is long enough so that time comparable to a half cycle or more is required for current to travel to the open end, the phase relations between the reflected current and outgoing current will vary along the wire. At one point the two currents will be 180° out of phase and at another in phase, with intermediate values between. Assuming negligible losses, the resultant current along the wire, as measured by a current-indicating instrument such as a thermo-couple ammeter, will vary in amplitude from zero to a maximum value. Such a variation is called a *standing wave*. The voltage along the wire also goes through standing waves, reaching its maximum value where the current is minimum and vice versa.

When the wire is cut to such a length that the current traverses it in one direction in exactly the time of one-half cycle, a single standing wave will occur along the wire and the wire is said to be resonant to the applied frequency. Although the inductance and capacity are distributed along the wire rather than being concentrated in a coil and condenser, such a wire is in many ways equivalent to an ordinary resonant circuit.

Frequency and wavelength — It is possible to describe the constants of such line circuits in terms of inductance and capacitance, but it is more convenient to give them simply in terms of fundamental resonant frequency or of length. Since the velocity at which the current travels is 300,000 kilometers (186,000 miles) per second, the *wavelength*, or distance the current will travel in the time of one cycle, is

$$\lambda = \frac{300,000}{f_{kc}}$$

where λ is the wavelength in meters and f_{kc} is the frequency in kilocycles.

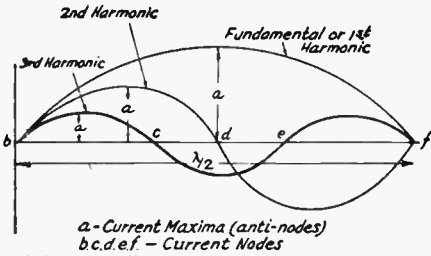


Fig. 247 — Standing-wave current distribution on a wire operating as an oscillatory circuit, at the fundamental, second harmonic and third harmonic frequencies.

Harmonic resonance — Although a coil-condenser combination having lumped constants (capacitance and inductance) resonates only at one frequency, circuits such as antennas which contain distributed constants resonate readily at frequencies which are very nearly integral multiples of the fundamental frequency. These frequencies are, therefore, in *harmonic* relationship to the fundamental frequency, and hence are referred to as *harmonics* (§ 2-7). In radio practice the fundamental itself is called the *first harmonic*, the frequency twice the fundamental is called the *second harmonic*, and so on.

Fig. 247 illustrates the distribution of current on a wire for fundamental, second and third harmonic excitation. There is one point of maximum current with fundamental operation, two when operation is at the second harmonic, and three at the third harmonic; the number of current maxima corresponds to the order of the harmonic and the number of standing waves on the wire. As noted in the figure, the points of maximum current are called *anti-nodes* (also known as “loops”) and the points of zero current are called *nodes*.

In the case of the harmonic current curves, the half-wave curves are drawn alternately above and below the reference line to indicate that the phase of the current reverses in each half wavelength. In other words, if current in one half-wave section is flowing to the right, for example, the current in the adjacent half-wave section will be flowing to the left. However, when the current is measured with an r.f. ammeter there will simply be a maximum indication at the center of each half-wave section, since the ammeter cannot indicate phase.

Radiation resistance — Since a line circuit has distributed inductance and capacity, cur-

rent flow causes storage of energy in magnetic and electrostatic fields (§ 2-3, 2-5). As the fields travel outward from the wire at the speed of light, some of the energy escapes from the circuit in the form of electromagnetic waves; that is, energy is *radiated* from the wire. Such a wire is, in fact, an antenna. Since the energy radiated by the line or antenna represents a loss, insofar as the line is concerned, the loss of energy can be considered to take place in an *equivalent resistance*. The value of the equivalent resistance is found from the ordinary Ohm's Law formula, $R = P/I^2$, where P is the power radiated and I is the current in the wire. R , the equivalent resistance, is called *radiation resistance*.

Two-conductor lines — The effective resistance of a resonant straight wire is fairly high, because a large proportion of the power supplied to such a wire is radiated. In many cases it is necessary to transfer power from one point to another with the least possible loss — for example, from a transmitter to a radiating antenna which may be located some distance away. If the line is folded so that there are two conductors instead of one, as shown in Fig. 248, the currents in adjacent sections of the two wires are flowing in opposite directions, consequently the fields set up by the two oppose each other and there is very little radiation.

The quarter-wave folded line in Fig. 248 has a *total* length of one-half wavelength, hence is resonant to the frequency corresponding to its length. Since the current is large and the voltage is low at the closed end, the impedance at this point is quite low. On the other hand, the

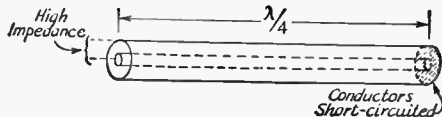


Fig. 249 — A quarter-wave coaxial-line resonant circuit.

voltage is high and the current is very low at the open end, so at this point the impedance is high. These properties of a quarter-wave two-conductor line have applications to be described later.

A folded line also may be constructed in the form of two coaxial or concentric conductors, as shown in Fig. 249. In effect, this line is directly comparable with the parallel conductor line, except that one conductor may be said to have been rotated around the other in a complete circle. The *coaxial line* has even lower radiation resistance than the folded-wire line, since the outer conductor acts as a shield. Standing waves exist but are confined to the outside of the inner conductor and the inside of the outer conductor, since skin effect prevents the currents from penetrating to the other sides. Thus such a line will have no radio-frequency potentials on its exposed surfaces, and no radiation can occur. Because of the low radiation resistance and the relatively large

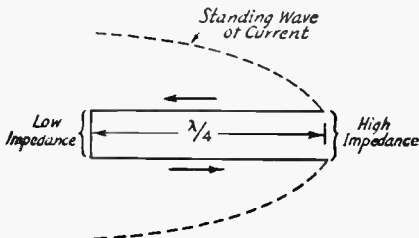


Fig. 248 — Standing wave and instantaneous current (shown by the arrows) in a folded resonant-line circuit.

conducting surfaces, such self-enclosed resonant lines can be made to have much higher *Q*s than are attainable with coils and condensers. They are most applicable at very high frequencies (very short wavelengths) (§ 2-7), where the dimensions are small.

A modified form of construction for coaxial lines is the "trough" line in which a tubular inner conductor is enclosed within a rectangular sheet-metal box or trough, usually left open on one side to facilitate tapping or other adjustments. The absence of shielding on one side does not affect the performance materially, and the simplicity of construction is an advantage.

The term *transmission line* is generally applied to all lines whether they are actually used as a means for transferring radio-frequency power between two points or whether they are used as replacements for coil-and-condenser resonant circuits. The lines shown in Figs. 248 and 249 are "short" lines of the type frequently used for the latter purpose. For transferring power the line may be many wavelengths long, depending upon the distance over which the power is to be transmitted. Furthermore, a line used for this purpose is not necessarily resonant; in fact, it may be desirable to avoid resonance effects entirely.

If a transmission line could be made infinitely long, power would simply travel along it until it was entirely dissipated in the resistance of the line: there would be nothing to reflect it and standing waves would not exist. Such a line would present a constant impedance in the form of a pure resistance to an input at *any* frequency, and hence would show no resonance

effects. Practically, the characteristics of an infinitely-long line can be simulated by terminating a line of finite length in a load resistance equal to the *characteristic impedance* of the line. This and other general properties of transmission lines are discussed in the following paragraphs.

Characteristic impedance — The *characteristic impedance* of a transmission line, also known as the *surge impedance*, is defined as that impedance which a long line would present to an electrical impulse induced in the line. In an ideal line having no resistance it is equal to the square root of the ratio of inductance to capacity per unit length of the line.

The characteristic impedance of air-insulated transmission lines may be calculated from the following formulas:

Parallel-conductor line:

$$Z = 276 \log \frac{b}{a} \tag{5}$$

where *Z* is the surge impedance, *b* the spacing, center to center, and *a* the radius of the conductor. The quantities *b* and *a* must be measured in the same units (inches, cm., etc.).

Coaxial or concentric line:

$$Z = 138 \log \frac{b}{a} \tag{6}$$

where *Z* again is the surge impedance. In this case, *b* is the *inside diameter* (not radius) of the outer conductor and *a* is the *outside diameter* of the inner conductor. The formula is true for lines having air as the dielectric, and approximately so with ceramic insulators so spaced that the major part of the insulation is air.

The surge impedance for both parallel and coaxial lines using various sizes of conductors is given in chart form in Fig. 250.

When a solid insulating material is used between the conductors, the increase in line capacity causes the impedance to decrease by the factor $1/\sqrt{K}$, where *K* is the dielectric constant of the insulating material.

Although two-conductor lines have lower radiation, a single-conductor line can be used for transferring power if it is terminated in its characteristic impedance. Under such circumstances the current in the line will be small, and since radiation is proportional to current the radiation also will be small. The characteristic impedance of a single-wire transmission line varies with conductor size, height above ground, and orientation with respect to ground. An average figure is about 500 ohms.

Standing-wave ratio — The lengths of transmission lines used at radio frequencies are of the same order as the operating wavelengths, and therefore standing waves of current and voltage may appear on the line. The ratio of current (or voltage) at a loop to the value at a node (*standing-wave ratio*) depends upon the ratio of the resistance of the load connected to the output end of the line (its *termination*) to the characteristic imped-

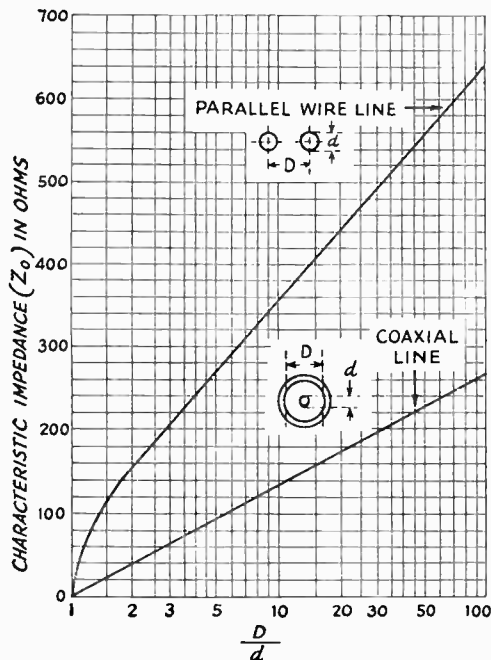


Fig. 250 — Characteristic impedance of uniform lines.

ance of the line itself. That is,

$$\text{Standing-wave ratio} = \frac{Z_s}{Z_i} \text{ or } \frac{Z_i}{Z_s} \quad (7)$$

where Z_s is the characteristic impedance of the line and Z_i is the terminating resistance. Z_i is generally called an impedance, although it must be non-reactive and therefore must correspond to a pure resistance for the line to operate as described. For example, this means that if the load or termination is an antenna, it must be resonant at the operating frequency.

The formula is given in two ways because it is customary to put the larger number in the numerator, so that the ratio will not be fractional. As an example, a 600-ohm line terminated in a resistance of 70 ohms will have a standing wave ratio of 600/70, or 8.57. The ratio on a 70-ohm line terminated in a resistance of 600 ohms would be the same. Thus, if the current as measured at a node is 0.1 ampere, the current at a loop will be 0.857 ampere.

A line terminated in a resistance equal to its characteristic impedance is equivalent to an infinitely long line; consequently there is no reflection, and no standing waves will appear. The standing wave ratio therefore is 1. The input end of such a line appears as a pure resistance of a value equal to the characteristic impedance of the line.

Electrical length — The electrical length of a line is not exactly the same as its physical length for reasons corresponding to the end effects in antennas (§ 10-2). Spacers used to separate the conductors have dielectric constants larger than that of air, so that the waves do not travel quite as fast along a line as they would in air. The lengths of electrical quarter waves of various types of lines can be calculated from the formula

$$\text{Length (feet)} = \frac{246 \times V}{\text{Freq. (Mc.)}}$$

where V depends upon the type of line. For lines of ordinary construction, V is as follows:

Parallel wire line	$V = 0.975$
Parallel tubing line	$V = 0.95$
Concentric line (air-insulated)	$V = 0.85$
Concentric line (rubber-insulated)	$V = 0.56 \text{ } 0.65$
Twisted pair	

Reactance, resistance, impedance — The input end of a line may show reactance as well as resistance, and the values of these quantities will depend upon the nature of the load at the output end, the electrical length of the line, and the line characteristic impedance. The reactance and resistance are important in determining the method of coupling to the source of power. Assuming that the load at the output end of the line is purely resistive, a line less than a quarter wavelength long electrically will show inductive reactance at its input terminals when the output termination is less than the characteristic impedance, and capaci-

Characteristics of Line Sections LESS THAN A QUARTER WAVELENGTH With Definite Source-Resistance			Characteristics of Line Sections BETWEEN ONE-QUARTER AND ONE-HALF WAVELENGTH With Definite Source-Resistance		
Relative Lengths of Line Sections	Relative Values of Input Resistance (R_i) and Line Impedance	Open End Looks Like	Relative Lengths of Line Sections	Relative Values of Input Resistance (R_i) and Line Impedance	Open End Looks Like
	$R = Z$			$R = Z$	
	$R > Z$			$R > Z$	
	$R < Z$			$R < Z$	

Fig. 251 — Input reactive characteristics of resistance-terminated transmission lines as a function of line length.

tive reactance when the termination is higher than the characteristic impedance. If the line is more than a quarter wave but less than a half wave long, the reverse conditions exist. These properties are shown in Fig. 251. With still longer lengths, the reactance characteristics reverse in each succeeding quarter wavelength. The input impedance is purely resistive if the line is an exact multiple of a quarter wave in length. The reactance at intermediate lengths is higher the greater the standing-wave ratio, being zero for a ratio of 1.

Whether lines are classified as *resonant* or *nonresonant* depends upon the standing-wave ratio. If the ratio is near 1, the line is said to be nonresonant, and reactive effects will be small even when the line length is not an exact multiple of a quarter wavelength. If the standing-wave ratio is large, the input reactance must be canceled or "tuned out" unless the line is resonant — i.e., a multiple of a quarter wavelength.

Impedance transformation — Regardless of the standing-wave ratio, the input impedance of a line a half-wave long electrically will be equal to the impedance connected at its output end; the same thing is true of a line any integral multiple of a half-wave in length. Such a line can be considered to be a one-to-one transformer. However, if the line is a quarter-wave (or an odd multiple of a quarter-wave) long, the input impedance will be equal to

$$Z_i = \frac{Z_s^2}{Z_o}$$

where Z_s is the characteristic impedance of the line and Z_o the impedance connected to the output end. That is, a quarter-wave section of line will match two impedances, Z_i and Z_o , provided its characteristic impedance, Z_s , is equal to the geometric mean of the two impedances. A quarter-wave line may, therefore, be used as an *impedance transformer*. By suitable selection of constants, a wide range of impedance-matching values can be obtained.

Since the impedance measured between the two conductors anywhere along the line will vary between the two end values, a quarter-wave line short-circuited at the output end can be used as a *linear transformer* with an adjustable impedance ratio. For best operation,

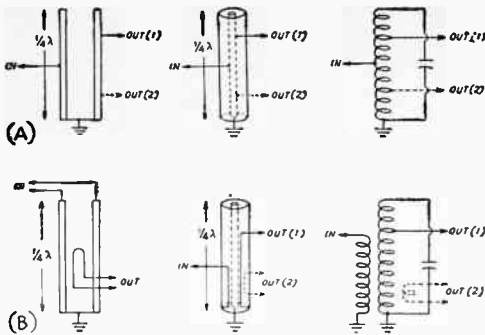


Fig. 252 — Equivalent coupling circuits for parallel-line, coaxial-line and conventional resonant circuits.

the two terminating impedances must be of the same order of magnitude. However, a series of quarter-wave sections can be used to obtain a step-by-step match of two terminal impedances efficiently if they are widely different.

Impedance-matching or transformation with transmission-line sections may also be effected by taps on quarter-wave resonant lines employed as coupling circuits in the same manner as conventional coil-condenser circuits. The equivalent relationships between parallel-line, coaxial-line and coil-and-condenser circuits for this purpose are shown in Fig. 252.

Other impedance-matching arrangements employ the use of matching stubs or equivalent sections so arranged so as to balance out the reactive component introduced by the coupled circuit. These are employed primarily in connection with antenna feed systems and are described in detail in § 10-8.

Transmission lines as circuit elements — Sections of transmission lines, together with combinations of such sections, can be used to simulate practically any electrical circuit property. Transmission lines can be used as resistance, inductance and capacity, as well as for resonant circuits, impedance-matching transformers, filters, and even as insulators.

When a short-circuited quarter-wavelength line is connected between a "hot" circuit and ground, the input end offers an extremely high resistive impedance. In other words, the transmission line is virtually an insulator. Insulating lines of this sort are commonly employed in ultrahigh frequency work. Such insulators can be used to provide a d.c. path between the r.f. conductor and chassis, and at the same time effectively block the flow of r.f. current.

A transmission line terminated in its characteristic impedance affords a pure resistance at high frequencies, and so may be used as a non-reactive resistor. Unterminated lines afford a variety of reactive properties. Lengths of short-circuited line less than a quarter wavelength represent pure inductive reactance, while open-circuited lines have pure capacitive reactance.

Thus the former can be used in lieu of r.f. chokes, while the latter can serve as by-pass condensers.

The reactive characteristics of open- and closed-end lines are summarized in Fig. 253.

Resonant lines as tuned circuits — In resonant circuits as employed at the lower frequencies it is possible to consider each of the reactance components as a separate entity. A coil is used to provide the required inductance and a condenser is connected across it to provide the necessary capacity. The fact that the coil has a certain amount of self-capacity of its own, as well as some resistance, while the condenser also possesses a small self-inductance, can usually be disregarded.

At the very-high and ultrahigh frequencies, however, it is no longer possible to separate these components. The connecting leads which, at lower frequencies, would serve merely to join the condenser to the coil now may have more inductance than the coil itself. The required inductance coil may be no more than a single turn of wire, yet even this single turn may have dimensions comparable to a wavelength at the operating frequency. Thus the energy in the field surrounding the "coil," may in part be radiated. At a sufficiently high frequency the loss by radiation may represent a major portion of the total energy in the circuit. Since energy which cannot be utilized as intended is wasted, regardless of whether it is consumed as heat by the resistance of the wire or simply radiated into space, the effect is as though the resistance of the tuned circuit were greatly increased and its *Q* greatly reduced.

For this reason, it is common practice to utilize resonant sections of transmission line as tuned circuits at frequencies above 100 Mc. A quarter-wavelength line, or any odd multiple thereof, shorted at one end and open at the other, exhibits large standing waves. When a voltage of the frequency at which such a line is resonant is applied to the open end, the response is very similar to that of a parallel resonant circuit; it will have very high input impedance at resonance and a large current flowing at the short-circuited end.

Characteristics of OPEN LINE SECTIONS			Characteristics of SHORTED LINE SECTIONS		
Relative Lengths of Line Sections	Output End Looks Like	Reactance Curve for Each Section	Relative Lengths of Line Sections	Output End Looks Like	Reactance Curve for Each Section
$\frac{1}{4}\lambda$	--- 		$\frac{1}{4}\lambda$	--- 	
$\frac{1}{2}\lambda$	--- 		$\frac{1}{2}\lambda$	--- 	
$\frac{3}{4}\lambda$	--- 		$\frac{3}{4}\lambda$	--- 	
λ	--- 		λ	--- 	
$\frac{5}{4}\lambda$	--- 		$\frac{5}{4}\lambda$	--- 	
$\frac{3}{2}\lambda$	--- 		$\frac{3}{2}\lambda$	--- 	
$\frac{7}{4}\lambda$	--- 		$\frac{7}{4}\lambda$	--- 	
2λ	--- 		2λ	--- 	

Fig. 253 — Open and closed transmission lines as circuit elements.

The action of a resonant quarter-wavelength line can be compared with that of a coil-and-condenser combination whose constants have been adjusted to resonance at a corresponding frequency. Around the point of resonance, in fact, the line will display very nearly the same characteristics as those of the tuned circuit. The equivalent relationships are shown in Fig. 253. At frequencies off resonance the line displays qualities comparable to the inductive and capacitive reactances of the coil and condenser circuit, although the exact relationships involved are somewhat different. For all practical purposes, however, sections of resonant wire or transmission line can be used in much the same manner as coils or condensers.

In v.h.f. circuits operating above 300 Mc., the spacing between conductors becomes an appreciable fraction of a wavelength. To keep the radiation loss as small as possible the parallel conductors should not be spaced farther apart than 10 per cent of the wavelength, center to center. On the other hand, the spacing of large-diameter conductors should not be reduced to much less than twice the diameter because of what is known as the *proximity effect*, whereby another form of loss is introduced through eddy currents set up by the adjacent fields. Because the cancellation is no longer complete, radiation from an open line becomes so great that the *Q* is greatly reduced. Consequently, at these frequencies coaxial lines must be used. The coaxial line is advantageous at the lower frequencies, as well, but because it is more complicated to construct and adjustments are more difficult the open type of line is generally favored at these frequencies.

Transmission-line filter networks — The same general equations can be applied to any type of electrical network whether it be an actual section of transmission line, a combination of lumped-circuit elements, or a combination of transmission-line elements. Ordinary electric filters (§ 2-11) at lower frequencies use combinations of coils and condensers, but conventional circuit elements cannot be used at extremely high frequencies. However, combinations of transmission-line sections or combinations of transmission lines and parallel-plate condensers may be used for the elements of very-high-frequency filter networks, instead.

Construction — Practical information concerning the construction of transmission lines for such specific uses as feeding antennas and as resonant circuits in radio transmitters will be found in the constructional chapters of this *Handbook*. Certain basic considerations applicable in general to resonant lines used as circuit elements may be considered here, however.

While either parallel-line or coaxial sections may be used, the latter are preferred for higher-frequency operation. Representative methods for adjusting the length of such lines to resonance are shown in Fig. 254. At the left, a sliding shorting disc is used to reduce the effective length of the line by altering the position of

the short circuit. In the center, the same effect is accomplished by using a telescoping tube in the end of the inner conductor to vary its length and thereby the effective length of the

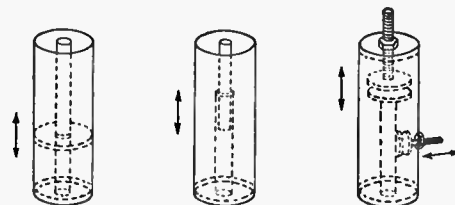


Fig. 254 — Methods of tuning coaxial resonant lines.

line. At the right, two possible methods of mounting parallel plate condensers, used to tune a "foreshortened" line to resonance, are illustrated. The arrangement with the loading capacity at the open end of the line has the greatest tuning effect per unit of capacity; the alternative method, which is equivalent to "tapping" the condenser down on the line, has less effect on the *Q* of the circuit. Lines with capacity "loading" of the sort illustrated will be shorter, physically, than an unloaded line resonant at the same frequency.

The short-circuiting disc at the end of the line must be designed to make perfect electrical contact. The voltage is a minimum at this end of the line; therefore, it will not break down some of the thinnest insulating films. Usually a soldered connection or a tight clamp is used to secure good contact. When the length of line must be readily adjustable, the shorting plug is provided with spring collars which make contact on the inner and outer conductors at some distance away from the shorting plug at a point where the voltage is sufficient to break down the film between the collar and conductor.

Two methods of tuning parallel-conductor lines are shown in Fig. 255. The sliding short-circuiting strap can be tightened by means of screws and nuts to make good electrical contact. The parallel-plate condenser in the second drawing may be placed anywhere along the line, the tuning effect becoming less as the condenser is located nearer the shorted end


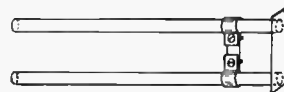


Fig. 255 — Methods of tuning parallel-type resonant lines.

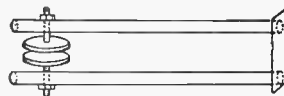

of the line. Although a low-capacity variable condenser of ordinary construction can be used, the circular-plate type shown is symmetrical and thus does not unbalance the line. It also has the further advantage that no insulating material is required.

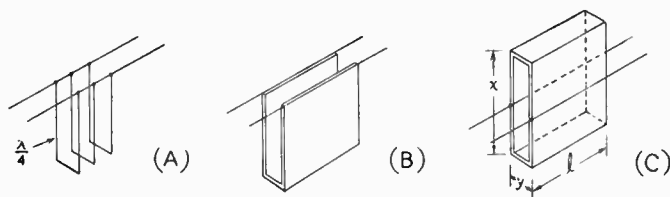


Fig. 256 — Evolution of a wave guide from a two-wire transmission line.

□ 2-12-B Wave Guides and Cavity Resonators

Hollow wave guides — A wave guide is a conducting tube through which energy is transmitted in the form of electromagnetic waves. The tube is not considered as carrying a current in the same sense that the wires of a two-conductor line do, but rather as a *boundary* which confines the waves in the enclosed space. Skin effect prevents any electromagnetic effects from being evident outside the guide. The v.h.f. energy is injected at one end, either through capacitive or inductive coupling or by radiation, and is received at the other end. The wave guide then merely confines the energy of the fields, which are propagated through it to the receiving end by means of reflections against its inner walls.

The difficulty of visualizing energy transfer without the usual closed circuit can be relieved somewhat by considering the guide as being evolved from an ordinary two-conductor line.

In Fig. 256-A, several closed quarter-wave stubs are shown connected in parallel across a two-wire transmission line. Since the open end of each stub is equivalent to an open circuit, the line impedance is not affected by their presence. Enough stubs may be added to form a U-shaped rectangular tube with solid walls, as at B, and another identical U-shaped tube may be added edge-to-edge to form the rectangular pipe shown in Fig. 256-C. As before, the line impedance still will not be affected. But now, instead of a two-wire transmission line, the energy is being conducted within a hollow rectangular tube.

This analogy to wave-guide operation is not exact, and therefore should not be taken too literally. In the evolution from the two-wire line to the closed tube the electric and magnetic field configurations undergo considerable change, with the result that the guide does not actually operate like a two-conductor line shunted by an infinite number of quarter-wave stubs. If it did, only waves of the proper length to correspond to the stubs would be propagated through the tube, but the fact is that such waves do *not* pass through the guide. Only waves of shorter length — that is, higher frequency — can go through. The distance x represents half the *cut-off wavelength*, or the shortest wavelength which is unable to go through the guide. Or, to put it another way, waves of length equal to or greater than $2x$ cannot be propagated in the guide.

A second point of difference is that the apparent length of a wave along the direction of propagation through a guide always is greater than that of a wave of the same frequency in free space, whereas the wavelength along a two-conductor transmission line

is the same as the free-space wave-length (when the insulation between the wires is air).

Operating principles of wave guides —

Analysis of wave-guide operation is based on the assumption that the guide material is a perfect conductor of electricity. Typical distributions of electric and magnetic fields in a rectangular guide are shown in Fig. 257. It will be observed that the intensity of the electric field is greatest at the center along the x dimension, diminishing to zero at the end walls. The latter is a necessary condition, since any electric field parallel to the walls at the surface would cause an infinite current to flow in a perfect conductor. This represents an impossible situation.

Zero electric field at the end walls will result if the wave is considered to consist of two separate waves moving in zig-zag fashion down the guide, reflected back and forth from the end walls as shown in Fig. 258. Just at the walls, the positive crest of one wave meets the negative crest of the other, giving complete cancellation of the electric fields. The angle of reflection at which this cancellation occurs depends upon the width x of the guide and the length of the waves; Fig. 258-A illustrates the

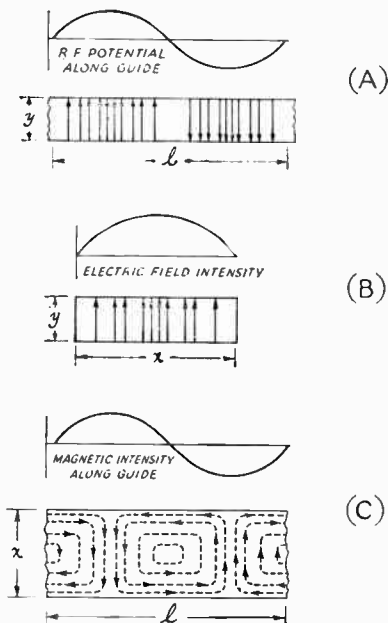


Fig. 257 — Field distribution in a rectangular wave guide. The TE_{10} mode of propagation is depicted.

case of a wave considerably shorter than the cut-off wavelength, while B shows a longer wave. When the wavelength equals the cut-off value, the two waves simply bounce back and forth between the walls and no energy is transmitted through the guide.

The two waves travel with the speed of light, but since they do not travel in a straight line the energy does not travel through the guide as rapidly as it does in space. A further conse-

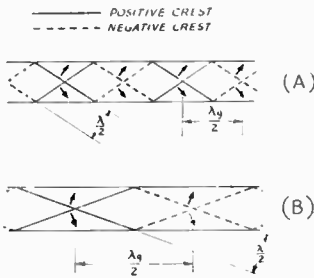


Fig. 258 — Reflection of two component waves in a rectangular guide. λ = wavelength in space, λ_g = wavelength in guide. Direction of wave motion is perpendicular to the wave front (crests) as shown by the arrows.

quence of the repeated reflections is that the points of maximum intensity or wave crests are separated more along the line of propagation in the guide than they are in the two separate waves. In other words, the wavelength in the guide is greater than the free-space wavelength. This is also shown in Fig. 258.

Modes of propagation — Fig. 257 represents a relatively simple distribution of the electric and magnetic fields. There is in general an infinite number of ways in which the fields can arrange themselves in a guide so long as there is no upper limit to the frequency to be transmitted. Each field configuration is called a *mode*. All modes may be separated into two general groups. One group, designated *TM* (*transverse magnetic*), has the magnetic field entirely transverse to the direction of propagation, but has a component of electric field in that direction. The other type, designated *TE* (*transverse electric*) has the electric field entirely transverse, but has a component of magnetic field in the direction of propagation. TM waves are sometimes called *E* waves, and TE waves are sometimes called *H* waves, but the TM and TE designations are preferred.

The particular mode of transmission is identified by the group letters followed by two subscript numerals, for example, $TE_{1,0}$, $TM_{1,1}$, etc. The number of possible modes increases with frequency for a given size of guide. There is only one possible mode (called the *dominant mode*) for the lowest frequency that can be transmitted. The dominant mode is the one generally used in practical work.

Wave-guide dimensions — In the rectangular guide the critical dimension is x in Fig. 256; this dimension must be more than $\frac{1}{2}$ wavelength at the lowest frequency to be transmitted. In practice, the y dimension usu-

ally is made about equal to $\frac{1}{2}x$ to avoid the possibility of operation at other than the dominant mode.

Other cross-sectional shapes than the rectangle can be used, the most important being the circular pipe. Much the same considerations apply as in the rectangular case.

Wavelength formulas for rectangular and circular guides are given in the following table, where x is the width of a rectangular guide and r is the radius of a circular guide. All figures are in terms of the dominant mode.

	Rectangular	Circular
Cut-off wavelength	$2x$	$3.41r$
Longest wavelength transmitted with little attenuation	$1.6x$	$3.2r$
Shortest wavelength before next mode becomes possible	$1.1x$	$2.8r$

Cavity resonators — At low and medium radio frequencies resonant circuits usually are composed of "lumped" constants of L and C ; that is, the inductance is concentrated in a coil and the capacity concentrated in a condenser. However, as the frequency is increased coils and condensers must be reduced to impractically small physical dimensions. Up to a certain point this difficulty may be overcome by using linear circuits (§ 2-12-B) but even these fail at extremely high frequencies. Another kind of circuit particularly applicable at wavelengths of the order of centimeters is the *cavity resonator*, which may be looked upon as a section of a wave guide with the dimensions chosen so that waves of a given length can be maintained inside.

The derivation of one type of cavity resonator from an ordinary LC circuit is shown in Fig. 259. As in the case of the wave-guide derivation, this picture must be accepted with some reservations, and for the same reasons.

Considering that even a straight piece of wire has appreciable inductance at very-high frequencies, it may be seen in Fig. 259-A and -B that a direct short across a two-plate condenser with air dielectric is the equivalent of a tuned circuit with a typical coiled inductance. With two wires between the plates, as shown in Fig. 259-C, the circuit may be thought of as

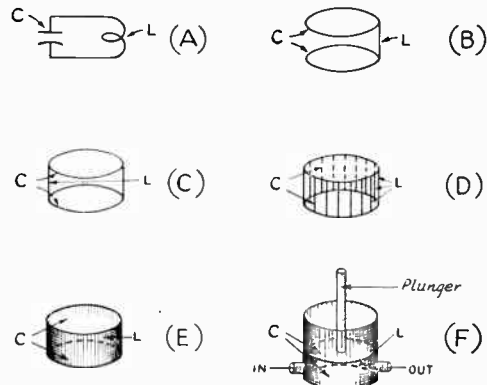


Fig. 259 — Steps in the derivation of a cavity resonator from a conventional coil-and-condenser tuned circuit.

a resonant-line section. For d.c. or even low frequency r.f., this line would appear as a short across the two condenser plates. At the ultra-high frequencies, however, as shown in Fig. 252, such a section of line a quarter-wavelength long would appear as an open circuit when viewed from one of the plates with respect to the other end of the section.

Increasing the number of parallel wires between the plates of the condenser would have no effect on the equivalent circuit, as shown at D. Eventually, the closed figure at E will be developed. Since each wire which is added in D is like connecting inductances in parallel, the total inductance across the condenser becomes increasingly smaller as the solid form is approached, and the resonant frequency of the figure therefore becomes higher.

If energy from some v.h.f. source now is introduced into the cavity in a manner such as that shown at F, the circuit will respond like any equivalent coil-condenser tank circuit at its resonant frequency. A cavity resonator may therefore be used as a u.h.f. tuning element, along with a vacuum tube of suitable design, to form the main components of an oscillator circuit which will be capable of functioning at frequencies considerably beyond the maximum limits possible when conventional tubes, coils and condensers are employed.

in such a mode. Other tuning methods include placing adjustable tuning paddles or "slugs" inside the cavity so that the standing-wave pattern of the electric and magnetic fields can be varied.

A form of cavity resonator in wide practical use is the re-entrant cylindrical type shown in Fig. 261. It is useful in connection with vac-

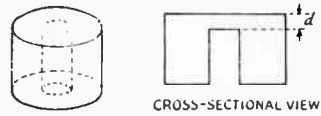


Fig. 261 - Re-entrant cylindrical cavity resonator.

uum-tube oscillators of the types described for u.h.f. use in Chapter Three. In construction it resembles a concentric line closed at both ends with capacity loading at the top, but the actual mode of oscillation may differ considerably from that occurring in coaxial lines. The resonant frequency of such a cavity depends upon the diameters of the two cylinders and the distance d between the ends of the inner and outer cylinders.

Compared to ordinary resonant circuits, cavity resonators have extremely high Q . A value of Q of the order of 1000 or more is readily obtainable, and Q values of several thousand can readily be secured with good design and construction.

Coupling to wave guides and cavity resonators—Energy may be introduced into or abstracted from a wave guide or resonator by means of either the electric or magnetic field. The energy transfer frequently is through a coaxial line, two methods for coupling to which are shown in Fig. 262. The probe shown at A is simply a short extension of the inner conductor of the coaxial line, so oriented that it is parallel to the electric lines of force. The loop shown at B is arranged so that it encloses some of the magnetic lines of force. The point at which maximum coupling will be secured depends upon the particular mode of propagation in the guide or cavity; the coupling will be maximum when the coupling device is in the most intense field.

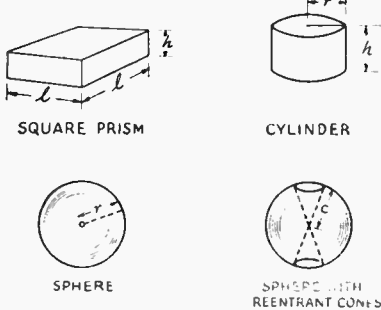


Fig. 260 - Forms of cavity resonators.

Other shapes than the cylinder may be used as resonators, among them the rectangular box, the sphere, and the sphere with re-entrant cones, as shown in Fig. 260. The resonant frequency depends upon the dimensions of the cavity and the mode of oscillation of the waves (comparable to the transmission modes in a wave guide). For the lowest modes the resonant wavelengths are as follows:

Cylinder.....	$2.61r$
Square box.....	$1.41l$
Sphere.....	$2.28r$
Sphere with re-entrant cones.....	$4r$

The resonant wavelengths of the cylinder and square box are independent of the height when the height is less than a half wavelength. In other modes of oscillation the height must be a multiple of a half wavelength as measured inside the cavity. Fig. 259-F shows how a cylindrical cavity can be tuned when operating

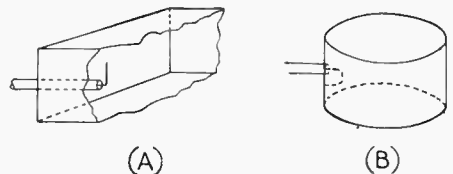


Fig. 262 - Coupling to wave guides and resonators.

Coupling can be varied by turning either the probe or loop through a 90-degree angle. When the probe is perpendicular to the electric lines the coupling will be minimum; similarly, when the plane of the loop is parallel to the magnetic lines the coupling will have its least possible value.

2-12-C Lumped-Constant Circuits


V.h.f. resonator circuits—At the very-high frequencies the low values of L and C required make ordinary coils and condensers impracticable, while linear circuits offer mechanical difficulties in making tuning adjustments over a wide-frequency range.

To overcome these difficulties, special high- Q lumped-constant circuits have been developed in which connections from the “condenser” to the “coil” are an inherent part of the structure. Integral design minimizes both resistance and inductance and increases the C/L ratio.

The simplest of these circuits is based on the use of discs combining half-turn inductance loops with semi-circular condenser plates. By connecting several of these half-turn coils in parallel, the effective inductance is reduced to a value appreciably below that for a single turn. Tuning is accomplished by interleaving grounded rotor plates between the turns. Both by shielding action and short-circuited-turn effect, these further reduce the inductance.

Another type of high- C circuit is a single-turn toroid, commonly termed the “hat” resonator. Two copper shells with wide, flat “brims” are mounted facing each other on an axially aligned copper rod. The capacity in the circuit is that between the wide shells, while the central rod comprises the inductance.

Fig. 263—Concentric-cylinder or “pot”-type tank for v.h.f. The equivalent circuit diagram is also shown. Connections are made to the terminals marked T. For maximum Q the ratio of b to c should be between 3 and 5.

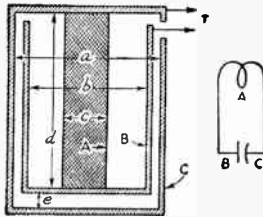

“Pot”-type tank circuits—The lumped-constant concentric-element tank in Fig. 263, commonly referred to as the “pot” circuit, is equivalent to a very short coaxial line (no linear dimension should exceed 1/20th wavelength), loaded by a large integral capacity.

The inductance is supplied by the copper rod, A . The capacity is provided by the concentric cylinders, B and C , plus the capacity between the plates at the bottoms of the cylinders.

Approximate values of capacity and inductance for tank circuits of the “pot” type can be determined by the following:

$$L = 0.0117 \log \frac{b}{c} \mu h.$$

$$C = \left(\frac{0.6225 d}{\log \frac{a}{b}} \right) + \left(\frac{0.1775 b^2}{e} \right) \mu \text{fd.}$$

where the symbols are as indicated in Fig. 263, and all dimensions are in inches. The left-hand term for capacity applies to the concentric cylinders, B and C , while the second term gives the capacity between the bottom plates.

“Butterfly” circuits—The tank circuits described in the preceding section are primarily fixed-frequency devices. The “butterfly” circuits shown in Fig. 264 are capable of being tuned over an exceptionally wide range,

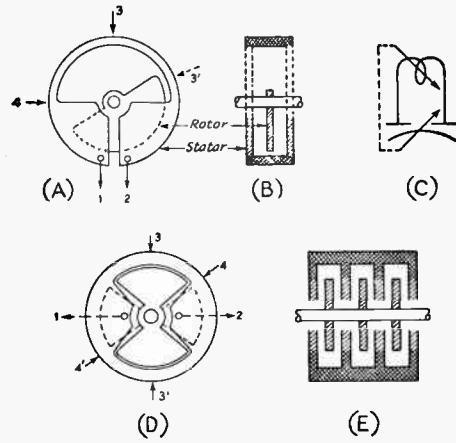


Fig. 264—“Butterfly” tank circuits for v.h.f., showing front and cross-section views and the equivalent circuit.

while still having high Q and reasonable physical dimensions. The circuit at A is derived from a conventional balanced-type variable condenser. The inductance is in the wide circular band connecting the stator plates. At its minimum setting the rotor plate fills the opening of the loop, reducing the inductance to a minimum. Connections are made to points 1 and 2. This basic structure eliminates all connecting leads and avoids all sliding or wiping electrical contacts to a rotating member. A disadvantage is that the electrical midpoint shifts from point 3 to point 3' as the rotor is turned. Constant magnetic coupling may be obtained by a coupling loop located at point 4, however.

In the modification shown at D , two sectoral stators are spaced 180 degrees, thereby achieving the electrical symmetry required to permit tapping for balanced operation. Connections to the circuit should be made at points 1 and 2 and it may be tapped at points 3 and 3', which are the electrical midpoints. Where magnetic coupling is employed, points 4 and 4' are suitable locations for coupling links.

The capacity of any butterfly circuit may be computed by the standard formula for parallel-plate condensers given in Chapter 20. The maximum inductance can be obtained approximately by finding the inductance of a full ring of the same diameter and multiplying the result by a factor of 0.17. The ratio of minimum to maximum inductance varies between 1.5 and 4 with usual construction.

Any number of butterfly sections may be connected in parallel. In practice, units of four to eight plates prove most satisfactory. The ring and stator may either be made in one piece or with separate sectoral stator plates and spacing rings assembled with machine screws.

2-12-D Piezoelectric Crystals

Piezoelectricity — Properly ground plates or bars of quartz and certain other crystalline materials, such as Rochelle salts, show a mechanical strain when subjected to an electric charge and, conversely, a difference in potential between two faces when subjected to mechanical stress. The relationship between mechanical force and electrical stress under such conditions is known as the *piezoelectric effect*. The charges appearing on the crystal as a result of mechanical force applied to the crystal, or of mechanical vibration of the crystal itself, are termed *piezoelectricity*.

Piezoelectric crystals may be employed as devices either for changing mechanical energy to electrical energy or for changing electrical energy to mechanical energy. In the former category are such devices as crystal microphones and phonograph pickups; in the latter, crystal headphones, crystal loud-speakers and crystal recording heads.

A properly cut crystal is a mechanical vibrator electrically equivalent to a series-resonant circuit of very high Q , and so can be also used for many of the purposes for which ordinary resonant circuits are used. The resonant frequency depends upon shape, thickness, length and cut.

Natural quartz crystals are usually in the form of a hexagonal prism terminated at one or both ends by a six-sided pyramid. Joining the vertices of these pyramidal ends, and perpendicular to the plane of the hexagonal cross section, is the optical or Z axis. The three electrical or X axes lie in a plane perpendicular to the optical axis and passing through opposite corners of the hexagon. The three mechanical or Y axes lie in the same plane but perpendicularly to the sides of the hexagon.

Active plates cut from a raw crystal at various angles to its optical, electrical and mechanical axes have differing characteristics as to thickness, frequency-temperature coefficient, power-handling capabilities, etc. The basic cuts are designated X and Y after their respective axes, but a variety of specialized cuts, such as the AT , are in more common use.

Frequency-thickness ratio — At frequencies above about 500 kc., the thickness of the crystal is the principal frequency-determining factor, the other dimensions being of relatively minor importance. Thickness and frequency are related by a constant, K , such that

$$f = \frac{K}{t}$$

where f is the frequency in megacycles and t the thickness of the crystal in mils. For the X -cut, $K = 112.6$; Y -cut, $K = 77.0$; AT -cut, $K = 66.2$; BT -cut, $K = 97.3$.

At frequencies above about 10 Mc., the crystal becomes very thin and correspondingly fragile, so that crystals seldom are manufactured for fundamental operation above this

frequency. Direct crystal control on 14 and 28 Mc. is secured by use of "harmonic" crystals, which are ground to be active oscillators when excited at a harmonic (usually the third).

Temperature coefficient of frequency — The resonant frequency of a crystal varies with temperature, the variation depending upon the type of cut. The frequency change is usually expressed as a coefficient relating the number of cycles of frequency change per megacycle per °C. It may be either positive (increasing frequency with increasing temperature) or negative (decreasing frequency with increasing temperature). X -cut crystals have a negative coefficient of 15 to 25 cycles/Mc./°C. The coefficient of Y -cut crystals may vary from -20 cycles/Mc./°C. to +100 cycles/Mc./°C.

Variations in frequency caused by temperature changes can be minimized by proper cutting of the plate. By orienting the plate through various angles in relation to its optical, electrical and mechanical axes, a compensatory relationship can be derived between the dimensions of the plate, its density, and its elastic constants — the components responsible for the temperature coefficient.

The AT cut is the type perhaps most extensively used for transmitter frequency control. This plate can be ground to almost any frequency between 300 and 5000 kc. Its complement, the BT cut, is used for frequencies within the range 1500 to 10,000 kc.

For frequencies below 500 kc., CT and DT shear-type cuts have been developed which depend not upon thickness but on length and width for determining frequency. Plates of the CT and DT type vibrating at a harmonic mode are designated ET or FT cuts.

The low-drift types described above show a zero temperature coefficient through only a few degrees of change. Another type of cut, the GT , will drift less than 1 cycle/Mc./°C. over a temperature change of 100° C. In this plate a face shear vibration is changed into two longitudinal vibrations coupled together. At a certain ratio of length to width one mode

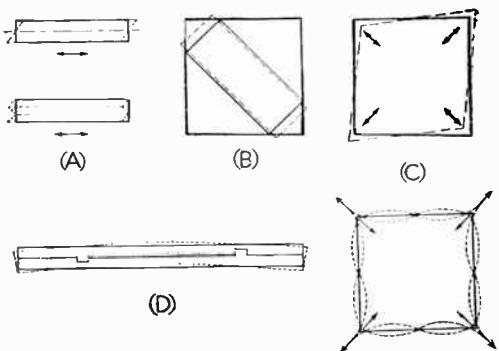


Fig. 265 — Modes of vibration for various crystal cuts. A — Fundamental (above) and harmonic (below) of the AT and BT cuts. B — The GT cut. C — CT and DT cuts (above) and ET and FT cuts (below). D — NT cut.

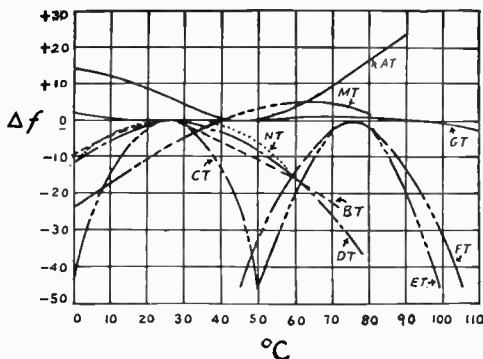


Fig. 266 — Frequency change in parts per million vs. variation in temperature in °C. for various crystal cuts.

has a zero temperature coefficient, making it especially useful as a frequency standard. The MT cut, which also vibrates longitudinally, can be used from 50 to 100 ke. The NT crystal is a flexurally vibrating cut having a low temperature coefficient in the range from 4 to 50 ke. MT and NT cuts are useful for phase-modulated f.m. transmitters.

¶ 2-13 Miscellaneous Circuit Details

Combined a.c. and d.c. — There are many practical instances of simultaneous flow of alternating and direct currents in a circuit. When this occurs there is a *pulsating* current, and it is said that an alternating current is *superimposed* on a direct current. As shown in Fig. 267, the maximum value is equal to the d.c. value plus the a.c. maximum, while the minimum value (on the negative a.c. peak) is the difference between the d.c. and the maximum a.c. values. The average value (§ 2-7) of the current is simply equal to the direct-current component alone. The effective value (§ 2-7) of the combination is equal to the square root of the sum of the effective a.c. squared and the d.c. squared:

$$I = \sqrt{I_{ac}^2 + I_{dc}^2}$$

where I_{ac} is the effective value of the a.c. component, I is the effective value of the combination, and I_{dc} is the average (d.c.) value of the combination.

Beats — If two or more alternating currents of different frequencies are present in a normal circuit they will have no particular effect upon one another and can be separated again by the proper selective circuits. However, if two (or more) alternating currents of different frequencies are present in an element having unilateral or one-way current flow properties, not only will the two original frequencies be present in the output but also currents having frequencies equal to the sum, and difference, of the original frequencies. These sum and difference frequencies are called the *beat* frequencies. For example, if frequencies of 2000 and 3000 ke. are present in a normal circuit only those two frequencies exist, but if they are passed through a

unilateral element there will be present in the output not only the two original frequencies of 2000 and 3000 ke. but also currents of 1000 (3000 - 2000) and 5000 (3000 + 2000) ke. Suitable circuits can be used to select the desired beat frequency. The human ear has unilateral characteristics and is, therefore, capable of hearing audible beat frequencies. Electronic devices of this nature are called mixers, converters, and detectors.

By-passing — In combined circuits, it is frequently necessary to provide a low-impedance path for a.c. around, for instance, a source of d.c. voltage. This can be done by using a *by-pass condenser*, which will not pass direct current but will readily permit the flow of alternating current. The capacity of the condenser should be of such value that its reactance is low (of the order of 1/10th or less) compared to the a.c. impedance of the device being by-passed. The lower the reactance, the more effectively will the alternating current be confined to the desired path.

Similarly, alternating current can be prevented from flowing through a direct-current circuit to which it may be connected by inserting an inductance of high reactance (called a *choke coil*) between the two circuits. This will permit the direct current to flow without hindrance, since the resistance of the choke coil may be made quite low, but will effectively prevent the alternating current from flowing where it is not wanted.

If both r.f. and low-frequency (audio or power) currents are present in a circuit, they may be confined to desired paths by similar means, since an inductance of high reactance for radio frequencies will have negligible reactance at low frequencies, while a condenser of low reactance at radio frequencies will have high reactance at low frequencies.

Grounds — The term "ground" is frequently encountered in discussions of circuits. Normally it means the voltage reference point

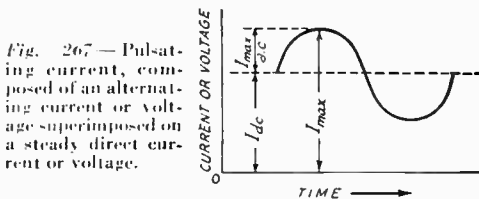


Fig. 267 — Pulsating current, composed of an alternating current or voltage superimposed on a steady direct current or voltage.

in the circuit. There may or may not be an actual connection to earth, but it is understood that a point in the circuit said to be at *ground potential* could be connected to earth without disturbing the operation of the circuit in any way. In direct-current circuits, the negative side generally is grounded. The ground symbol in circuit diagrams is used for convenience in indicating common connections between various parts of the circuit, as through a metal chassis, and, with respect to actual ground, usually has the meaning indicated above.

Vacuum Tubes

3-1 Diodes

Rectification — Practically all of the vacuum tubes used in radio work depend upon thermionic conduction (§ 2-4) for their operation. The simplest type of vacuum tube is that shown in Fig. 301. It has two elements, a cathode and a plate, and is called a *diode*. When heated by the "A" battery the cathode emits electrons, which are attracted to the plate if the plate is at a positive potential with respect to the cathode.

Because of the nature of thermionic conduction, the tube is a conductor in one direction only. If a source of alternating voltage is connected between the cathode and plate, then electrons will flow only on the positive half-cycles of alternating voltage; there will be no electron flow during the half cycle when the plate is negative with respect to the cathode. Thus the tube can be used as a *rectifier*, to change alternating current to pulsating direct current. This alternating current can be anything from the 60-cycle kind to the highest radio frequencies.

Rectification finds its chief applications in detecting radio signals and in power supplies. These are treated in Chapters Seven and Eight, respectively.

Characteristic curves — The performance of the tube can be reduced to easily understood terms by making use of tube *characteristic curves*. A typical characteristic curve for a diode is shown at the right, in Fig. 301. It shows the current flowing between plate and cathode with different d.c. voltages applied between the elements. The curve of Fig. 301 shows that, with fixed cathode temperature, the plate current increases as the voltage between cathode and plate is raised. For an actual tube the values of plate current and plate voltage would be plotted along their respective axes.

The power consumed in the tube is the product of the plate voltage multiplied by the plate current, just as in any d.c. circuit. In a vacuum tube this power is dissipated in heat developed in the plate and radiated to the bulb.

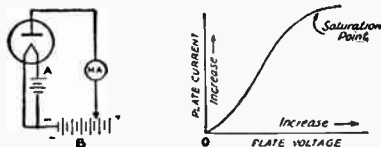


Fig. 301 — The diode or two-element tube and a typical characteristic curve showing plate current vs. voltage.

Space charge — With the cathode temperature fixed the total number of electrons emitted is always the same, regardless of the plate voltage. Fig. 301 shows, however, that less plate current will flow at low plate voltages than when the plate voltage is large. With low plate voltage, only those electrons nearest the plate are attracted to the plate. The electrons in the space near the cathode, being themselves negatively charged, tend to repel the similarly charged electrons leaving the cathode surface and cause them to fall back on the cathode. This is called the *space-charge* effect. As the plate voltage is raised more and more electrons are attracted to the plate, until finally the space charge effect is completely overcome. When this occurs all the electrons emitted by the cathode are attracted to the plate, and a further increase in plate voltage can cause no further increase in plate current. This condition is called *saturation*.


3-2 Triodes

Grid control — If a third element, called the *control grid*, or simply the *grid*, is inserted between the cathode and plate of the diode, the space-charge effect can be controlled. The tube then becomes a *triode* (three-element tube) and is useful for more things than rectification. The grid is usually in the form of an open spiral or mesh of fine wire. If the grid is connected externally to the cathode so that it is at the same potential as the cathode, and a steady voltage from a d.c. supply is then applied between the cathode and plate (the positive of the "B" supply is always connected to the plate), there will be a constant flow of electrons from cathode to plate through the openings of the grid, much as in the diode. However, if the grid is given a positive potential with respect to the cathode, the space charge will be partially neutralized and there will be an increase in plate current. If the grid is made negative with respect to the cathode, the space charge will be reinforced and the current will decrease.

This effect of grid voltage can be shown by curves in which plate current is plotted against grid voltage. At any given value of grid voltage the plate current will still depend upon the plate voltage, so if complete information about the tube is to be secured it is necessary to plot a *series* of curves taken with various values of plate voltage. Such a set of grid voltage vs. plate current curves, typical of a small receiving triode, is shown in Fig. 303.

So long as the grid has a negative potential with respect to the cathode, electrons emitted

Fig. 302 — Illustrating the construction of an elementary triode vacuum tube, showing the filament, grid (with an end view of the grid wires) and plate. The relative density of the space charge is indicated roughly by the dot density. Battery symbols follow those of the usual schematic diagrams, while the schematic tube symbol is shown at the right.

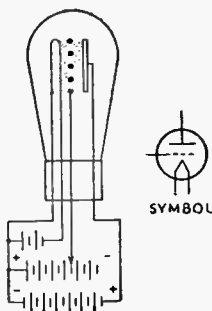

by the cathode are repelled (§ 2-3) from the grid, with the result that no current flows to the grid. Hence, under these conditions, the grid consumes no power. However, when the grid becomes positive with respect to the cathode, electrons are attracted to it, and a current flows to the grid; when this *grid current* flows, power is dissipated in the grid circuit.

In addition to the set of curves showing the relationship between grid voltage and plate current at various fixed values of plate voltage, two other sets of curves may be plotted to show the characteristics of a triode. These are the plate voltage vs. plate current characteristic, which shows the relationship between plate voltage and plate current for various fixed values of grid voltage, and the constant-current characteristic, which shows the relationship between plate voltage and grid voltage for various fixed values of plate current.

Amplification — The grid evidently acts as a valve to control the flow of plate current, and it is found that it has a much greater effect on plate current flow than does the plate voltage; that is, a small change in grid voltage is just as effective in bringing about a given change in plate current as is a large change in plate voltage.

The fact that a small voltage acting on the grid is equivalent to a large voltage acting on the plate indicates the possibility of *amplification* with the triode tube; that is, the generation of a large voltage by a small one, or the generation of a relatively large amount of power from a small amount. The many uses of the electronic tube nearly all are based upon this amplifying feature. The amplified power or voltage output from the tube is obtained, not from the tube itself, but from the source of e.m.f. connected between its plate and cathode. The tube simply *controls* the power from this source, changing it to the desired form.

To utilize the controlled power, a device for consuming it, or for transferring it to another circuit, must be connected in the plate circuit, since no particularly useful purpose would be served in having the current merely flow through the tube and the source of e.m.f. Such a device is called the *load*, and may be either a resistance or an impedance. The term "impedance" is frequently used even though the load may be purely resistive.

Amplification factor — The relative effect of the grid and plate voltages on the plate current is measured by the *amplification factor* of the tube, usually represented by the Greek letter μ . Amplification factor is defined as the ratio of the change in plate voltage required to produce a given change in plate current to the change in grid voltage required to produce the same plate-current change. Strictly speaking, very small changes in both grid and plate voltage must be used in determining the amplification factor, because the curves showing the relationship between plate voltage and plate current, and between grid voltage and plate current, are not perfectly straight, especially if the plate current is nearly zero. This indicates that the amplification factor varies at different points along the curves, and different values will be obtained as larger or smaller voltage differences are taken for the purpose of calculating it. The expression for amplification factor can be written:

$$\mu = \frac{\Delta E_p}{\Delta E_g}$$

where ΔE_p indicates a very small change in plate voltage and ΔE_g is the change in grid voltage producing the same plate current change. The symbol Δ (the Greek letter *delta*) indicates a small increment, or small change.

The amplification factor is simply a ratio, and has no unit.

Plate resistance — Since only a limited amount of plate current flows when a given voltage is applied between plate and cathode, it is evident that the plate-cathode circuit of the tube has resistance. However, there is no simple relationship between plate voltage and plate current, so that in general the plate circuit of the tube does not follow Ohm's Law. Under a given set of conditions the application of a given plate voltage will cause a certain plate current to flow, and if the plate voltage is divided by the plate current a "resistance" value will be obtained which frequently is called the "d.c. resistance" of the tube. This "d.c. resistance" will be different for every value of plate voltage and also for different values of grid voltage, since the plate current also depends upon the grid voltage when the plate voltage is fixed.

In applications of the vacuum tube, it is more

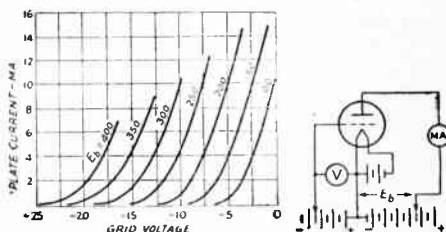


Fig. 303 — Grid voltage vs. plate current curves at various fixed values of plate voltage (E_b) for a typical small triode. Characteristic curves of this type can be taken by varying the battery voltages in the circuit at the right.

important to know how the plate current changes with a change in plate voltage than it is to know the relationship between the actual values of plate current and plate voltage. The relationship between plate-current change and plate-voltage change determines the *a.c. plate resistance* of the tube. This resistance, which usually is designated r_p , is significant when there is an a.c. component in the plate current. It can be found from the plate voltage vs. plate current characteristic curves. That is,

$$r_p = \frac{\Delta E_p}{\Delta I_p}$$

where ΔE_p is a small change in plate voltage and ΔI_p the corresponding small change in plate current, the grid voltage being fixed.

Plate resistance is expressed in ohms, since it is the ratio of voltage to current. The value of plate resistance will, in general, change with the particular voltages applied to the plate and grid. It depends as well upon the structure of the tube; low- μ tubes have relatively low plate resistance and high- μ tubes have high plate resistance.

Transconductance — The effect of grid voltage upon plate current is expressed by the *grid-plate transconductance* of the tube. Transconductance is a general term giving the relationship between the voltage applied to one electrode and the current which flows, as a result, in a second electrode. As in the previous two cases, it is defined as the *change* in current through the second electrode caused by a change in voltage on the first. Thus the grid-plate transconductance, commonly called the *mutual conductance*, is

$$g_m = \frac{\Delta I_p}{\Delta E_g}$$

where g_m is the mutual conductance, ΔI_p the change in plate current, and ΔE_g the change in grid voltage, the plate voltage being fixed. As before, the sign Δ indicates that the changes must be small. Transconductance is measured in mhos, since it is the ratio of current to voltage. The unit usually employed in connection with vacuum tubes is the *micromho* (one millionth of a mho), because the conductances are small. By combining with the two preceding formulas, it can be shown that $g_m = \mu r_p$.

The mutual conductance of a tube is a rough indication of its merit as an amplifier, since it

includes the effects of both amplification factor and plate resistance. Its value varies with the voltages applied to the plate and grid. With the plate voltage fixed, the mutual conductance decreases when the grid is made increasingly negative with respect to the cathode. This characteristic frequently can be used to advantage in the control of amplification, since the amount of amplification can be varied over wide limits simply by adjusting the value of a steady voltage applied to the grid.

Static and dynamic curves — Curves of the type shown in Figs. 301 and 303 are called *static* curves. They show the current which flows when various voltages are applied directly to the tube electrodes. Another useful set of static curves is the "plate family," or plate voltage vs. plate current characteristic. A typical set of curves of this type is shown in Fig. 304.

A curve showing the relationship between grid voltage and plate current when a load resistance is connected in the plate circuit is called a *dynamic* characteristic curve. Such a curve includes the effect of the load resistance, and hence is more indicative of the performance of the tube as an amplifier. With a fixed value of plate-supply voltage the actual value of voltage between the plate and cathode of the tube will depend upon the amount of plate current flowing, since the plate current also flows through the load resistance and therefore results in a voltage drop which must be subtracted from the plate-supply voltage. The dynamic curve includes the effect of this voltage drop. Consequently, the plate current always is lower, for a given value of grid bias and plate-supply voltage, with the load resistance in the circuit than it is without it.

Representative dynamic characteristics are shown in Fig. 305. These were taken with the same type of tube whose static curves are shown in Fig. 303. Different curves would be obtained with different values of plate-supply voltage, E_b ; this set is for a plate-supply voltage of 300 volts. Note that increasing the value of the load resistance reduces the plate current at a given bias voltage, and also that the curves are straighter with the higher values of load resistance. Zero plate current always occurs at the same value of negative grid bias, since at zero plate current there is no voltage drop in the load resistance and the full supply voltage is applied to the plate.

Fig. 306 shows how the plate current responds to an alternating voltage (*signal*) applied to the grid. If the plate current is to have the same waveshape as that of the signal, it is necessary to confine the operation to the straight section of the curve. To do this, it is necessary to select an *operating point* near the middle of the straight portion; this operating point is determined by the fixed voltage (*bias*) applied to the grid. The alternating signal voltage then adds to or subtracts from the grid bias, depending upon whether the instantaneous

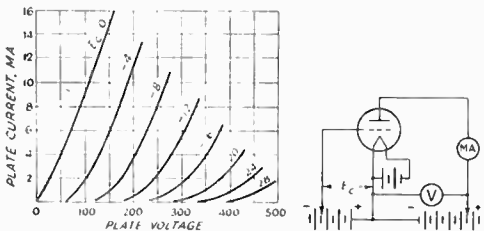


Fig. 304 — Plate voltage vs. plate current curves at various fixed values of negative grid voltage for the same triode as that used to obtain the curves in Fig. 303.

ous signal voltage is negative or positive with respect to the cathode, and causes a corresponding variation in plate current. The maximum departure of instantaneous grid voltage or plate current from the operating point is called the *swing*. The varying plate current flows through the load resistance, causing a varying voltage drop which constitutes the useful output voltage of the tube.

The point at which the plate current is reduced to zero is called the *cut-off point*. The value of negative grid voltage at which cut-off occurs depends upon the amplification factor of the tube and the plate voltage. It is approximately equal to the plate-supply voltage divided by the amplification factor.

Interelectrode capacities — Any pair of elements in a tube forms a miniature condenser (§ 2-3), and, although the capacities of these condensers may be only a few micromicrofarads or less, they must frequently be taken into account in vacuum-tube circuits. The capacity from grid to plate (*grid-plate capacity*) has an important effect in many applications. In triodes, the other capacities are the *grid-cathode* and *plate-cathode*. In multi-element tubes (§ 3-6), similar capacities exist between these and other electrodes. With screen-grid tubes, the terms "input" and "output" capacity mean, respectively, the capacity measured from grid to all other elements connected together and from plate to all other elements connected together. The same terms are used with triodes but are not so easily defined, since the effective capacities existing depend upon the operating conditions (§ 3-3).

Tube ratings — Specifications of suitable operating voltages and currents are called *tube ratings*. Ratings include proper values for filament or heater voltage and current, plate voltage and current, and similar operating specifications for other elements. An important rating in power tubes is the *maximum safe plate dissipation*, or the maximum power that can be dissipated continuously in heat on the plate (§ 3-1).

3-3 Amplification

Principles — The operation of a simple amplifier, which was described briefly in the preceding section, is shown in more detail in Fig. 307. The load in the plate circuit is the resistor, R_p . For the sake of example, it is assumed that the plate-supply voltage is 300 volts, the negative grid bias is 5 volts, and the plate current at this bias when R_p is 50,000 ohms is 2 milliamperes (0.002 ampere). If no signal is applied to the grid circuit, the voltage drop in the load resistor is $50,000 \times 0.002$, or 100 volts, leaving 200 volts between the plate and cathode.

If a sine-wave signal having a peak value of 2 volts is applied in series with the bias voltage in the grid circuit, the instantaneous voltage at the grid will swing to -3 volts at the instant the signal reaches its positive peak and to -7 volts at the instant the signal reaches its negative peak. The maximum plate current

will occur at the instant the grid voltage is -3 volts and, as shown by the graph, will have a value of 2.65 milliamperes. The minimum plate current occurs at the instant the grid voltage is -7 volts, and has a value of 1.35

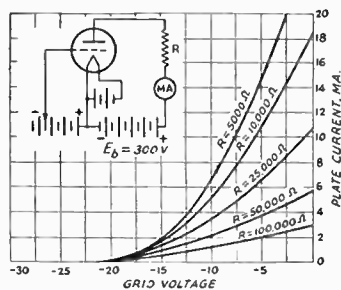


Fig. 305 — Dynamic characteristics of a small triode with various load resistances from 5,000 to 100,000 ohms.

ma. At intermediate values of grid voltage, intermediate plate-current values will occur. The instantaneous voltage between the plate and cathode of the tube also is shown on the graph. When the plate current is maximum the instantaneous voltage drop in R_p is $50,000 \times 0.00265$ or 132.5 volts, and when the plate current is minimum the instantaneous voltage drop in R_p is $50,000 \times 0.00135$ or 67.5 volts. The actual voltage between plate and cathode is therefore the difference between the plate-supply voltage, 300 volts, and these voltage drops in the load resistance, or 167.5 and 232.5 volts, respectively.

The varying plate voltage is an a.c. voltage superimposed (§ 2-13) on the steady plate-cathode voltage of 200 volts, which was previously determined for no-signal conditions. The peak value of this a.c. output voltage is the difference between either the maximum or minimum plate-cathode voltage and the no-signal value of 200 volts. In the illustration this difference is $232.5 - 200$ or $200 - 167.5$, or 32.5 volts. Since the grid signal voltage has a peak value of 2 volts, the voltage amplification ratio of the amplifier is $32.5/2$ or 16.25. That is, approximately 16 times as much volt-

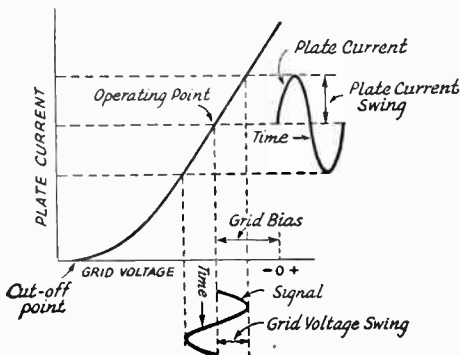


Fig. 306 — Behavior of the plate current of a vacuum tube in response to an alternating signal voltage superimposed on a steady negative grid voltage or bias.

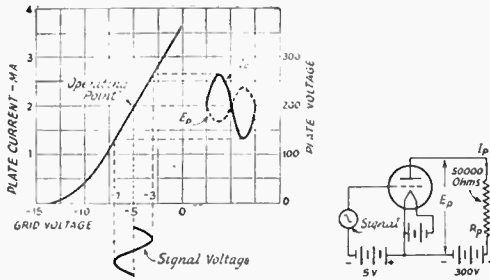


Fig. 307 — Amplifier operation. When the plate current varies in response to the signal applied to the grid, a varying voltage drop appears across the load, R_p , as shown by the dashed curve. E_p , I_p is the plate current.

age will be obtained from the plate circuit as is applied to the grid circuit.

It will be observed that only the alternating plate and grid voltages enter into the calculation of the amplification ratio. The d.c. plate and grid voltages are of course essential to the operation of the tube, since they set the operating point, but otherwise their presence may be ignored. This being the case, it is possible to show that the tube can be replaced by an equivalent generator which has an internal resistance equal to the a.c. plate resistance of the tube (§ 3-2) at the operating point chosen and which generates a voltage equal to the amplification factor of the tube multiplied by the signal voltage applied to the grid. The equivalent generator, together with the load resistance, R_p , is shown in Fig. 308. This simplification enables ready calculation of the amplification. If the generated voltage is μE_g , then the same current flows through r_p and R_p , and hence the voltage drop across R_p , which is the useful output voltage, is

$$E_o = \mu E_g \frac{R_p}{r_p + R_p}$$

since R_p and r_p together constitute a voltage divider (§ 2-6). The voltage-amplification ratio is given by the output voltage divided by the input voltage, hence dividing the above expression by E_g gives the following formula for the amplification of the tube:

$$\text{Amplification} = \frac{\mu R_p}{r_p + R_p}$$

This expression shows that, to obtain a large voltage-amplification ratio, it is necessary to make the plate load resistance, R_p , large compared to the plate resistance, r_p , of the tube. The maximum possible amplification, obtained when R_p is infinitely larger than r_p , is equal to the μ of the tube. A tube with a large value of μ will, in general, give more voltage amplification than one with a medium or low value. However, the advantage of the high μ is less than might be expected; because a high- μ tube usually also has a correspondingly high value of r_p , so that a high value of load resistance must be used to realize an appreciable part of

the possible amplification. This in turn not only requires the use of high values of plate-supply voltage, but has some further disadvantages to be described later.

Amplifiers in which the voltage output, rather than the power output, is the primary consideration are called *voltage amplifiers*.

Power in grid circuit — In the operation depicted in Fig. 306, the grid is always negative with respect to the cathode. If the peak signal voltage is larger than the bias voltage, the grid will be positive with respect to the cathode during part of the signal cycle. Grid current will flow during this time, and the signal source will be called upon to furnish power during the period while grid current is flowing. In many cases the signal source is not capable of furnishing appreciable power, so that care must be taken to avoid "driving the grid positive."

When dealing with small signals the source of signal voltage frequently has high internal resistance, so that a considerable voltage drop occurs in the source itself whenever it is called upon to furnish grid current. Since this voltage drop occurs only during part of the cycle, the voltage applied to the grid undergoes a change in waveshape because of the current flow. This is shown in Fig. 309, where a sine-wave signal is generated but, because of the internal resistance of the source, is *distorted* at the grid of the tube during the time when grid current flows.

If the internal resistance of the signal source is low, so that the internal voltage drop is negligible when current flows, this distortion does not occur. With such a source, it is possible to operate over a greater portion of the amplifier characteristic.

Harmonic distortion — If the operation of the tube is not confined to a straight or linear portion of the dynamic characteristic, the waveshape of the output voltage will not be exactly the same as that of the signal voltage. This is shown in Fig. 310, where the operating point is selected so that the signal voltage swings into the curved part of the characteristic. While the upper half-cycle of plate current reproduces the sine-wave shape of the positive half-cycle of signal voltage, the lower half-cycle of plate current is considerably distorted and bears little resemblance to the upper half-cycle of plate current.

As explained in § 2-7, a non-sinusoidal waveshape can be resolved into a number of sine-wave components or harmonics which are integral multiples of the lowest frequency present. Consequently, this type of distortion is known as *harmonic distortion*. Distortion re-

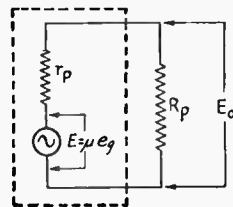


Fig. 308 — Equivalent circuit of the vacuum-tube amplifier. The tube is replaced by an equivalent generator having an internal resistance equal to the a.c. plate resistance of the vacuum tube.

sulting from grid-current flow, described in the preceding paragraph, also is harmonic distortion. Harmonic distortion from either or both causes may arise in the same amplifier.

Harmonic distortion may or may not be tolerable in an amplifier. At audio frequencies it is desirable to keep harmonic distortion to a minimum, but radio-frequency amplifiers are frequently operated in such a way that the r. f. wave is greatly distorted.

Frequency distortion — Another type of distortion, known as *frequency distortion*, occurs when the amplification varies with the frequency of the a.c. voltage applied to the grid circuit of the amplifier. It is not necessarily accompanied by harmonic distortion. It can be shown by a *frequency-response curve* or graph in which the relative amplification is plotted against frequency over the frequency range of interest.

Resistance-coupled amplifiers — An amplifier with a resistance load is known as a "resistance-coupled" amplifier. This type of amplifier is widely used for amplification at audio frequencies. A simplified circuit is shown in Fig. 311, where the amplifier is coupled to a following tube. Since all the power output of a resistance-coupled amplifier is consumed in the load resistor such amplifiers are used almost wholly for voltage amplification, usually working into still another amplifier.

A single amplifier is called a *stage* of amplification, and a number of amplifier stages in succession are said to be in *cascade*.

The purpose of the coupling condenser, C_c , is to transfer to the grid of the following tube the a.c. voltage developed across R_p , and to prevent the d.c. plate voltage on tube A from being applied to the grid of tube B. The grid resistor, R_g , transfers the bias voltage to the grid of tube B and prevents short-circuiting the a.c. voltage through the bias battery. Since no grid current flows, there is no d.c. voltage drop in R_g ; consequently the full bias voltage is applied to the grid. In order to obtain the maxi-

Fig. 309 — Distortion of applied signal because of grid-current flow. With the operating point at 3 volts negative bias, grid current will flow as shown by the curve whenever the applied signal voltage is more than 3 volts positive. If there is appreciable internal resistance, as indicated in the second drawing, there will be a voltage drop in the resistance whenever current is flowing but not during the period when no current flows. The signal will reach the grid unchanged so long as the instantaneous voltage is less than 3 volts positive, but the voltage at the grid will be less than the instantaneous voltage when the latter is above this figure. The shape of the negative half-cycle is unaltered.

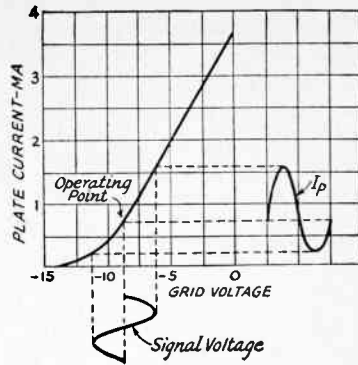
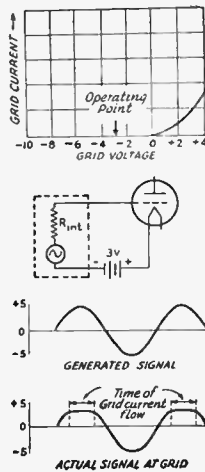


Fig. 310 — Harmonic distortion resulting from choice of an operating point on the curved part of the tube characteristic. The lower half-cycle of plate current does not have the same shape as the grid voltage causing it.

imum a.c. voltage at the grid of tube B the reactance of the coupling condenser must be small compared to the resistance of R_g , so that most of the voltage will appear across R_g rather than across C_c . Also, the resistance of R_g must be large compared to R_p , because, so far as the a.c. voltage developed in R_p is concerned, R_g is in parallel with R_p and therefore is just as much a part of R_p as though it were connected directly in parallel with it. (The impedance of the plate-supply battery is assumed to be negligible, so that there is no a.e. voltage drop between the lower end of R_p and the common connection between the two tubes.) In practice the maximum usable value of R_p is limited to from 0.5 to about 2 megohms, depending upon the characteristics of the tube with which it is associated. If the value is made too high, stray electrons collecting on the grid may not "leak off" back to the cathode rapidly enough to prevent the accumulation of a negative charge on the grid. This is equivalent to an increase in the negative grid bias, and hence to a shift in the operating point.

The equivalent circuit of the amplifier now includes C_c , R_g , and a shunt capacity, C_s , which represents the input capacity of tube B and the plate-cathode capacity of tube A, together with such stray capacity as exists in the circuit. The reactance of C_s will depend upon the frequency of the voltage being amplified, and, since C_s is in parallel with R_p and R_g , it also becomes part of the load impedance for the amplifier. At low frequencies — below 1000 cycles or so — the reactance of C_s usually is so high that it has practically no effect on the amplification, but, since the reactance decreases at higher frequencies, it is found that the amplification drops off rapidly when the reactance of C_s becomes comparable to the resistance of R_p and R_g in parallel. To maintain the amplification at high frequencies, it is necessary that R_p be relatively small if C_s is large, or that C_s be small if R_p is large.

Under the best conditions, in practice C_s will be of the order of 15 μfd . or more, while it is

possible for it to reach values as high as a few hundred $\mu\mu\text{fd}$. The larger values are encountered when tube *B* is a high- μ triode, as described in a later paragraph. Even with a low value of shunt capacity, the shunt reactance

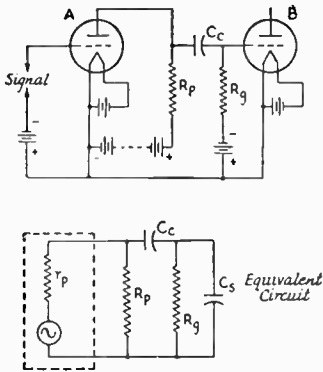


Fig. 311 — Typical resistance-coupled amplifier circuits.

will decrease to a comparatively low value at the upper limit of the audio-frequency range: a shunting capacity of 20 $\mu\mu\text{fd}$., for example, represents a reactance of about 0.5 megohm at 15,000 cycles, and hence is of the same order as R_p for the type of tubes with which such a low value of capacity would be associated. In order to secure the same amplification at high as at low frequencies, therefore, it is necessary to sacrifice low-frequency amplification by reducing the value of R_p to the point where the reactance of C_s at the highest frequency of interest is considerably larger than R_p .

At radio frequencies the reactance of C_s becomes so low that the amount of amplification it is possible to realize is negligible compared to that which can be obtained in the audio-frequency range. The resistance-coupled amplifier, therefore, is used principally for audio-frequency work.

Impedance-coupled amplifiers — If either the plate resistor or grid resistor (or both) in the amplifier described in the preceding paragraph is replaced by an inductance, the amplifier is said to be *impedance-coupled*. The inductance or impedance is commonly substituted for the plate load resistor, so that the usual circuit for such an amplifier is as given in Fig. 312.

Considering the operation of the tube from the standpoint of the equivalent circuit of Fig. 308, it is evident that a voltage drop would exist across a reactance of suitable value substituted for the indicated load resistance, R_p , so long as the output of the generator is alternating current. From the physical standpoint, any change in the current flowing through the inductance in Fig. 312 would cause a self-induced e.m.f. having a value proportional to the rate of change of current and to the inductance of the coil. Consequently, if an a.c. signal voltage is applied to the grid of the tube, the resultant variations in plate current cause a corresponding a.c. voltage to appear across

the coil terminals. This induced voltage is the useful output voltage of the tube.

The amplitude of the output voltage can be calculated, knowing the μ and plate resistance of the tube and the impedance of the load, in much the same way as in the case of resistance coupling, except that the equation must be modified to take account of the fact that the phase relationship between current and voltage is not the same in an impedance as it is in a resistance. In practice, the plate load inductance is shunted by the tube and stray distributed capacity. Since the greatest amplification will be secured when the load impedance is as high as possible, the coil usually is made to have sufficient inductance so that, in combination with these shunting capacities, the circuit as a whole will be parallel-resonant at some frequency near the middle of the audio-frequency range. Under these conditions the load impedance has its highest possible value, and is approximately resistive rather than reactive.

The equation for amplification with resistance coupling shows that, when R_p is several times the plate resistance, r_p , a further increase in R_p results in comparatively little increase in amplification. The load circuit of an impedance-coupled amplifier usually has an impedance value quite high in comparison to the plate resistance of the tube with which it is used, so that the load impedance can vary over a considerable range without much effect on the amplification. This gives the impedance-coupled amplifier an amplification vs. frequency characteristic which is fairly "flat" — that is, the amplification is practically constant with changes in frequency — over a considerable portion of the audio-frequency range. However, the performance of the impedance-coupled amplifier is not as good in this respect as that of a well-designed resistance-coupled amplifier.

If the impedance of the load circuit is high compared to the plate resistance of the tube, which will be the case if the tube is a low- μ triode and normal inductance values (a few hundred henrys) are used in the plate circuit,

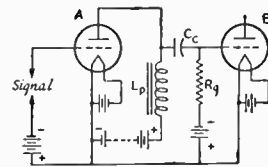


Fig. 312 — Impedance-coupled amplifier.

the amplification in the optimum frequency range will be practically equal to the μ of the tube. At lower frequencies the impedance decreases because of the decreasing reactance of the coil, while at higher frequencies the impedance again decreases because of the decreasing reactance of the shunt capacities. Thus the amplification drops off at both ends of the range, usually more rapidly than with resistance coupling.

The frequency-response characteristic of the impedance-coupled amplifier depends considerably upon the plate resistance of the tube. If impedance coupling is used with tubes of very high plate resistance, the response will be markedly greater at the resonant frequency than at frequencies either higher or lower.

Impedance coupling can be used at radio frequencies, since the inductance can be adjusted to resonate with the shunt capacities at practically any desired frequency.

Transformer-coupled amplifiers — The coupling impedance in Fig. 312 may be replaced by a transformer, connected as shown in Fig. 313. A.c. voltage is developed across the primary of the transformer in the same way as in the case of impedance coupling. The secondary of the transformer serves as a means for transferring the voltage to the grid of the following tube, and if the secondary has more turns than the primary the voltage across the secondary terminals will, in general, be larger than the voltage across the primary terminals.

As in the case of impedance coupling, the effective capacity shunting the primary of an audio-frequency transformer usually causes the primary circuit to be parallel-resonant at some frequency in the middle of the audio-frequency range. At the medium audio frequencies, therefore, the voltage across the primary is practically equal to the applied grid voltage multiplied by the μ of the tube. The voltage across the secondary will be the primary voltage multiplied by the secondary-to-primary turns ratio of the transformer, so that the total voltage amplification is μ times the turns ratio. The amplification at low frequencies depends upon the ratio of the primary reactance to the plate resistance of the tube, as in the case of impedance-coupled amplifiers.

At some high frequency, usually in the range 5000–10,000 cycles with ordinary transformers, the leakage inductance (§ 2-9) of the secondary becomes series resonant with the effective capacity shunting the secondary. At and near this resonant frequency the resonant rise in voltage may increase the amplification considerably, giving rise to a "peak" in the frequency-response curve of the amplifier. At frequencies above this resonance point amplification decreases rapidly, because as the reactance of the shunting capacity decreases it tends to act more and more as a short circuit across the secondary of the transformer. The relative height of the high-frequency peak depends principally upon the effective resistance of the secondary circuit. This effective resistance includes the actual resistance of the secondary coil and the "reflected" (§ 2-9) plate resistance of the tube, this resistance being in parallel with the primary of the transformer. Consequently, the height of the peak is affected by the tube with which the transformer is used. The peak can be reduced by connecting a 0.25 to 1 megohm resistor across the transformer secondary. While this helps to flatten the fre-

quency response curve, it also reduces the amplification at medium and low frequencies.

Transformer coupling is most suitable for triodes of low or medium μ and having medium values of plate resistance. This is because the primary inductance required for good amplification at low frequencies is proportional to the plate resistance of the tube with which the transformer is to be used, and in practice it is difficult to obtain high primary inductance, a large secondary-to-primary turns ratio ("step-up ratio"), and low distributed capacity in the windings all at the same time. Increasing the primary inductance usually means that the turns ratio must be reduced, because the increase in distributed capacity as the coils are made larger tends to bring the resonant peak down to a relatively low frequency unless the secondary inductance is decreased to compensate for the increase in capacity. The step-up ratio seldom is more than 3 to 1 in transformers designed for good frequency response.

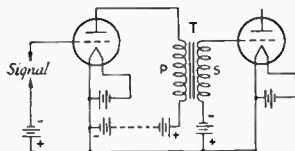


Fig. 313 — Transformer-coupled amplifier.

Transformer coupling can be used at radio frequencies if the transformers are properly designed for the purpose. In such transformers either the primary or secondary (or both) is made resonant at the frequency to be used, so that maximum amplification will be secured.

Phase relations in plate and grid circuits

— When the exciting voltage on the grid has its maximum positive instantaneous value, the plate current also is maximum (§ 3-2), so that the voltage drop across the resistance connected in the plate circuit of a resistance-coupled amplifier likewise has its greatest value. The actual instantaneous voltage between plate and cathode is therefore minimum at the same instant, because it is equal to the d.c. supply voltage (which is unvarying) minus the voltage drop across the load resistance. When the signal voltage is at its negative peak the plate current has its least value, with the result that the voltage drop in the load resistance is less than at any other part of the cycle. At this instant, therefore, the voltage between plate and cathode is maximum.

These variations in plate-cathode voltage constitute the a.c. output of the tube, superimposed on the mean or no-signal plate-cathode voltage. Since the alternating plate-cathode voltage is decreasing when the instantaneous grid voltage is increasing (becoming more positive with respect to the cathode), the output voltage is less than the mean value, or negative, when the signal voltage is positive. Likewise, when the signal voltage is negative the output voltage is positive, or greater than

the mean value. In other words, the alternating plate voltage is 180 degrees out of phase with the alternating grid voltage. Thus there is a *phase reversal* through the amplifier. The relationships should become clear from the behavior of the signal voltage and E_p in Fig. 307.

The same phase relationship between signal and output voltages holds when the amplifier is impedance- or transformer-coupled, in the frequency region where the load acts like a parallel-resonant circuit. However, if the load is reactive the phase relationship is not exactly 180 degrees but depends upon the kind of reactance present and the relative amounts of reactance and resistance. (This is true also of the resistance-coupled amplifier at low frequencies where the reactance of the coupling condenser affects the amplification, or at high frequencies where the reactance of the shunting capacities becomes important.) Since the reactance varies with the applied signal frequency, the phase relationship between signal voltage and output voltage depends upon the frequency in such cases.

Input capacity and resistance — When an alternating voltage is applied between the grid and cathode of an amplifier tube, an alternating current flows through the small condenser formed by these elements (§ 3-2) just as it would in any other condenser. Similarly, an alternating current also flows in the condenser formed by the grid and plate, since there is an alternating difference of potential between these elements. When the tube is amplifying, the alternating plate voltage and signal voltage are effectively applied in series across the grid-plate condenser, as indicated in Fig. 314. As described in the preceding paragraph, in the resistance-coupled amplifier the two voltages are out of phase with respect to the cathode, but inspection of the circuit shows that they are in phase so far as the grid-plate condenser is concerned. Consequently, the voltage applied to the grid-plate capacity is the sum of the alternating grid and plate voltages, or $E_g + E_p$. Since E_p is equal to $A \times E_g$, where A is the voltage amplification of the tube and circuit, the a.c. voltage between the grid and plate is $E_g (1 + A)$. The current, I , flowing in the grid-plate capacity is $E_g (1 + A)$ divided by the reactance of the grid-plate condenser, and thus is proportional to the grid-plate capacity.

The signal voltage must help in causing this relatively large current to flow, and, since the reactance as viewed from the input circuit

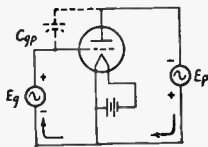


Fig. 314—The a.c. voltage appearing between the grid and plate of the amplifier is the sum of the signal voltage and the output voltage, as shown by this simplified circuit. Instantaneous polarities are indicated.

is $X_p = E_g/I$, the input reactance becomes smaller as the current becomes larger. That is, the *effective* input capacity of the amplifier is increased when the tube is amplifying. From the above, the increase in input capacity is approximately proportional to the voltage amplification of the circuit and to the grid-plate capacity of the tube. The total input capacity is the sum of the grid-cathode capacity and this additional effective capacity. The total input capacity of an amplifier may reach values ranging from 50 to a few hundred micromicrofarads, if the voltage amplification is high and the grid-plate capacity relatively large. Both usually are true in a high- μ triode.

When the load is reactive the a.c. grid and plate voltages still act in series across the grid-plate condenser, but since they are not exactly 180 degrees out of phase with respect to the cathode they are not exactly in phase with respect to the grid-plate capacity. The lack of exact phase relationship indicates that resistance as well as capacity is introduced into the input circuit. Analysis shows that, when the reactance of the load circuit is capacitive, the resistance component is positive — that is, it represents a loss of power in the input circuit — and that when the load circuit has inductive reactance the resistance component is negative. Negative resistance indicates that power is being supplied to the grid circuit from the plate.

Feed-back — If some of the amplified energy in the plate circuit of an amplifier is coupled back into the grid circuit, the amplifier is said to have *feed-back*. If the voltage fed from the plate circuit to the grid circuit is in such phase that, when it is added to the signal voltage already existing, the sum of the two voltages is larger than the original signal voltage, the feed-back is said to be *positive*. Positive feed-back usually is called *regeneration*. If regeneration exists in a circuit the total amplification is increased because the feed-back increases the amplitude of the signal at the grid and this larger signal is amplified in the same ratio, giving a greater output voltage than would exist if the signal voltage alone were present in the grid circuit. Many types of circuits can be used to secure positive feed-back. A simple one is shown in Fig. 315. The feed-back coil, L , a third winding on the grid-circuit transformer, is connected in series with the primary of the transformer in the plate circuit, so that some of the amplified voltage appears across its terminals. This induces a voltage in the secondary, S , of the grid-circuit transformer which, if the winding directions of the two coils are correct, will increase the value of signal voltage applied to the grid.

Positive feed-back is accompanied by a tendency to give maximum amplification at only one frequency, since the feed-back voltage will tend to be highest at the frequency at which the original amplification is greatest. It therefore increases the selectivity of the amplifier, and hence is used chiefly where high gain

and sharpness of resonance both are wanted.

If the phase of the voltage fed back to the grid circuit is such that the sum of the feed-back voltage and the original signal voltage is less than the latter alone, the feed-back is said to be *negative*. Negative feed-back frequently is called *degeneration*. In this case the total amplification is decreased, since the grid signal has been made smaller, and hence the amplified output voltage is smaller for a given original signal than it would be without feed-back.

The amount of voltage fed back will depend upon the actual amplification of the tube and circuit, and if the amplification ratio tends to change, as it may at the extreme high or low frequencies in the audio-frequency range, the feed-back voltage will be reduced when the amplification decreases. For example, suppose that an amplifier has a voltage gain of 20 and that it is delivering an output voltage of 50 volts. Without feed-back, the grid signal voltage required to produce 50 volts output is $50/20$ or 2.5 volts. But suppose that 10 per cent of the output voltage (5 volts) is fed back to the grid circuit in opposite phase to the applied grid voltage. Then, since it is still necessary to have a 2.5-volt signal to produce 50 volts output, the applied voltage must be $2.5 + 5$ or 7.5 volts. Now suppose that at some other frequency the voltage gain drops to 10. Then for the same 50-volt output a 5-volt signal is required, but since the feed-back voltage is still 5 volts the total required signal is now 10 volts. With feed-back the gain in the first case was 50/7.5 volts or 6.66 and in the second case 50/10 or 5, the gain in the second case being 75 per cent as high as in the first. Without feed-back the gain in the second case was 50 per cent as high as in the first. The effect of feed-back therefore is to make the resultant gain more uniform, despite the tendency of the amplifier itself to discriminate against certain frequencies.

Negative feed-back also tends to decrease harmonic distortion arising in the plate circuit of the amplifier. This distortion is present in the amplified output voltage, but not in the original signal voltage applied to the grid. The voltage fed back to the grid circuit contains the distortion but in opposite phase to the distortion components in the plate circuit, hence the two tend to cancel each other. For similar reasons, the over-all amplification is less dependent upon the value of load impedance used in the plate circuit; in fact, if a large amount of negative feed-back is used in an amplifier it is even possible to substitute tubes of rather widely different characteristics without much effect on the over-all performance.

Both positive and negative feed-back may be applied over several stages of an amplifier, rather than being applied directly from the plate circuit to the grid circuit of a single stage.

Power amplification — In the types of amplifiers previously described, the chief consideration was that of securing as much voltage

gain as possible within the permissible limits of harmonic distortion and frequency response characteristic. Such amplifiers are principally used to furnish an amplified signal voltage, which in turn can be supplied to a succeeding amplifier. If the succeeding amplifier is operated in such a way that its grid is never driven positive with respect to its cathode, grid current does not flow, and hence the power requirements are negligibly small. However, if an amplifier is used to actuate some power-consuming device, such as a loudspeaker or a succeeding amplifier in which it is permissible to drive the grid into the positive region, the primary consideration is that of obtaining the maximum power output consistent with the permissible distortion. In such a case the voltage at which the power is secured is of little consequence, since a transformer may be used to change the voltage to any desired value, within reasonable limits. Hence, the voltage gain of a power amplifier is of little importance.

In power-amplifier operation the grid may or may not be driven into the positive region, depending upon the particular application. The present discussion will be confined to the triode amplifier operating without grid current; other types are considered in § 3-4. The principles upon which such a power amplifier operates are practically identical with those already described. The chief differences between a voltage amplifier and a power amplifier lie in the selection of tubes and in the choice of the value of load resistance. As previously described, if voltage gain is the primary consideration the load resistance should be as large as possible in comparison to the plate resistance of the tube. It can be shown that, in any electrical circuit, maximum *power* output is secured when the resistance of the load is made equal to the internal resistance of the source of power. This is true whether the power source is a battery, a generator or a vacuum tube. In the case of the vacuum tube the internal resistance is the plate resistance of the tube, so that for maximum power output the load resistance should be made equal to the plate resistance. However, when the tube is operated with so low a value of load resistance there is considerable harmonic distortion, and *optimum* power output, representing an acceptable compromise between distortion and the power obtainable, is secured when the load resistance is approximately twice the plate resistance.

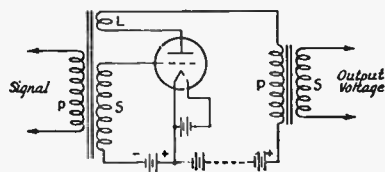


Fig. 315 — An elementary form of feed-back circuit. The feed-back may be either positive or negative, depending upon how the coil *L* is connected in the circuit. This type of circuit illustrates the principle of feed-back, but it is not practical for use in an actual audio-frequency amplifier.

Power-amplifier circuits — The plate or output circuit of a power amplifier almost invariably is transformer-coupled to the power-consuming device or load with which it is associated. This is because the impedance of the desired load seldom is the proper value for obtaining optimum power output from the amplifier. Consequently, the load impedance must be changed to a value suitable for the plate circuit of the amplifier tube. This can be done by the use of transformers, as described in § 2-9.

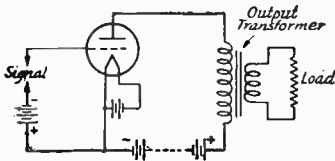


Fig. 316 — An elementary power-amplifier circuit in which the power-consuming load is coupled to the plate circuit through an impedance-matching transformer.

A basic power-amplifier circuit is shown in Fig. 316. So long as the amplifier is operated entirely in the negative-grid region and no grid current flows, any of the previously described types of coupling may be used between the grid of the power amplifier and the preceding amplifier. If there is no preceding amplifier, the method of coupling will depend principally on the characteristics of the source of the signal.

In Fig. 316 the load is represented as a resistance. An actual load may have a reactance as well as a resistance component, but only the resistance will consume power (§ 2-8).

Power amplification ratio — The ratio of a.c. output power to the a.c. power consumed in the grid circuit (*driving power*) is called the *power amplification ratio* or simply *power amplification* of the amplifier. If the amplifier operates without grid current the a.c. power consumed in the grid circuit is negligibly small, so that the power amplification ratio of such an amplifier is extremely large. With other types of operation the power amplification ratio may be relatively small, as described in § 3-4.

Plate efficiency — The ratio of a.c. output power to the d.c. power supplied to the plate circuit is called the *plate efficiency* of the amplifier. It is expressed as a percentage:

$$\% \text{ plate efficiency} = \frac{P_o}{EI} \times 100$$

where P_o is the a.c. output power, E the plate voltage and I the plate current, the latter two being d.c. values.

The plate efficiency of amplifiers designed for minimum distortion and a high power amplification ratio (operation without grid current) is relatively low — of the order of 15 to 30 per cent. For minimum distortion the operation must be confined to the region where the waveshape of the alternating plate current is substantially identical with that of the signal on the grid, and, as previously explained, this requirement can be met only by limiting the

plate-current variations (that is, the alternating component of plate current) to the straight portion of the dynamic grid voltage vs. plate current characteristic. Since with a given load resistance the power output is proportional to the square of the alternating component of plate current, it follows that limiting the plate-current variation also limits the power output in comparison to the d.c. plate power input.

Higher plate efficiency can be secured by increasing the alternating component of plate current, but this is accompanied by increased distortion. Special types of amplifiers have been devised to compensate for this distortion, as described in the next section. In some applications, as in r.f. power amplification, the fact that the signal applied to the grid is greatly distorted is of no consequence, so that such amplifiers can have high plate efficiency.

Power sensitivity — The ratio of a.c. power output to alternating grid voltage is called the *power sensitivity* of an amplifier. It provides a convenient measure for comparing power tubes, especially those designed for audio-frequency amplification where the operation is to be without grid current, since it expresses the relationship between power output and the amount of signal voltage required to produce the power.

The term power sensitivity also is used in connection with radio-frequency power amplifiers, in which case it has the same meaning as power amplification ratio. A tube which delivers its rated output power with a relatively small amount of power consumed in the grid circuit is said to have high power sensitivity.

Parallel operation — When it is necessary to obtain more power output than one tube is capable of giving, two or more tubes may be connected in *parallel*. In this case the similar elements in all tubes are connected together. This method is shown in Fig. 317 for a transformer-coupled amplifier. The power output of a parallel stage will be in proportion to the number of tubes used; the exciting voltage required, however, is the same as for one tube.

If the amplifier operates in such a way as to consume power in the grid circuit, the grid power required also is in proportion to the number of tubes used.

Push-pull operation — An increase in power output can be secured by connecting two tubes in *push-pull*, the grids and plates of the two tubes being connected to opposite ends of the circuit as shown in Fig. 317. A "balanced" circuit, in which the cathode returns are made to the midpoint of the input and output devices, is necessary with push-pull operation. At any instant the ends of the secondary winding of the input transformer, T_1 , will be at opposite potentials with respect to the cathode connection, so that the grid of one tube is swung positive at the same instant that the grid of the other is swung negative. Hence, in any push-pull-connected stage the voltages and currents of one tube are out of phase with those of the other tube. The

plate current of one tube is rising while the plate current of the other is falling, hence the name "push-pull." In push-pull operation the even-harmonic (second, fourth, etc.) distortion is cancelled in the symmetrical plate circuit, so that for the same power output the distortion will be less than with parallel operation.

The exciting voltage measured between the two grids must be twice that required for one tube. If the grids consume power, the driving power for the push-pull stage is twice that taken by either tube alone.

The decibel — The ratio of the power levels at two points in a circuit such as an amplifier can be expressed in terms of a unit called the *decibel*, abbreviated *db*. The number of decibels is 10 times the logarithm of the power ratio, or

$$\text{db.} = 10 \log \frac{P_1}{P_2}$$

The decibel is a particularly useful unit because it is logarithmic, and thus corresponds to the response of the human ear to sounds of varying loudness. One decibel is approximately the power ratio required to make a just noticeable difference in sound intensity. Within wide limits, changing the power by a given ratio produces the same apparent change in loudness regardless of the power level; thus if the power is doubled the increase is 3 db., or three steps of intensity; if it is doubled again the increase is again 3 db., or three further distinguishable steps. Successive amplifications expressed in decibels can be added to obtain the over-all amplification.

A power loss also can be expressed in decibels. A decrease in power is indicated by a minus sign (e.g., - 7 db.), and an increase in power by a plus sign (e.g., + 4 db.). Negative and positive quantities can be added numerically. Zero db. indicates the reference power level, or a power ratio of 1.

Applications of amplification — The major uses of vacuum-tube amplifiers in radio work are for amplifying at audio and radio frequencies (§ 2-7). The audio-frequency amplifier generally is used to amplify without dis-

crimination at all frequencies in a wide range (say from 100 to 3000 cycles for voice communication), and therefore is associated with non-resonant or untuned circuits which offer a uniform load over the desired range. The radio-frequency amplifier, on the other hand, generally is used to amplify selectively at a single radio frequency, or over a small band of frequencies at most, and therefore is associated with resonant circuits tunable to the desired frequency.

An audio-frequency amplifier may be considered a *broad-band amplifier*: most radio-frequency amplifiers are designed to have relatively narrow bandwidths.

In audio circuits the power tube or output tube in the last stage usually is designed to deliver a considerable amount of audio power, while requiring but negligible power from the input or exciting signal. To get the alternating voltage (*grid swing*) required for the grid of such a tube, voltage amplifiers are used employing high- μ tubes which greatly increase the voltage amplitude of the signal. Voltage amplifiers are used in the radio-frequency stages of receivers as well as in audio amplifiers; power amplifiers are used in the radio-frequency stages of transmitters.

§ 3-4 Classes of Amplifiers

Reason for classification — It is convenient to divide amplifiers into groups according to the work they are intended to perform, as related to the operating conditions necessary to accomplish the purpose. This makes identification easy and obviates the necessity for giving a detailed description of the operation when *specific* operating data are not required.

Class A — An amplifier operated as shown in Fig. 306 or 307, in which the output waveshape is a faithful reproduction of the input waveshape, is known as a *Class-A* amplifier.

As generally used, the grid of a Class-A amplifier never is driven positive with respect to the cathode by the exciting signal, and never is driven so far negative that plate-current cut-off is reached. The plate current is constant both with and without grid excitation. The chief characteristics of the Class-A amplifier are low distortion, relatively low power output for a given size of tube, and a high power-amplification ratio. The plate efficiency is relatively low (§ 3-3).

Class-A power amplifiers find application as output amplifiers in audio systems and as drivers for Class-B power amplifiers. Class-A voltage amplifiers are found in the stages preceding the power stage or stages in such applications, and as r.f. amplifiers in receivers.

Class B — The *Class-B* amplifier is primarily one in which the output current, or alternating component of the plate current, is proportional to the amplitude of the exciting grid voltage. Since power is proportional to the square of the current, the power output of a Class-B amplifier is proportional to the square of the exciting grid voltage.

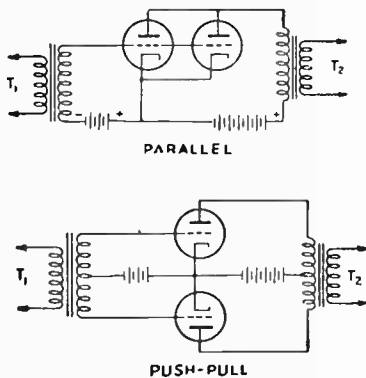


Fig. 317 — Parallel and push-pull a.f. amplifier circuits.

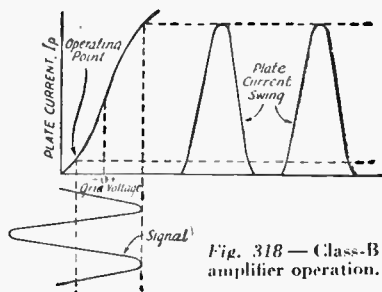


Fig. 318 — Class-B amplifier operation.

In Class-B service the grid bias is set so that the plate current is relatively low without grid excitation; the exciting signal amplitude is made such that the entire linear portion of the characteristic is used. Fig. 318 illustrates operation with the tube biased practically to cut-off. In this condition plate current flows only during the positive half-cycle of excitation. No plate current flows during the negative half-cycle. The shape of the plate current pulse is essentially the same as that of the positive swing of the signal voltage. Since the plate current is driven up toward the saturation point, it is usually necessary for the grid to be driven positive with respect to the cathode during part of the grid swing. Grid current flows, therefore, and the driving source must furnish power to supply the grid losses.

Class-B amplifiers are characterized by medium power output, medium plate efficiency (50 to 60 per cent at maximum signal), and a moderate ratio of power amplification. At radio frequencies they are used as *linear amplifiers* to raise the output power level in radio-telephone transmitters after modulation.

For Class-B audio-frequency amplification two tubes must be used, the second tube working alternately with the first so that both halves of the cycle will be present in the output. A typical method of achieving this is shown in Fig. 319. The signal is fed to a transformer, T_1 , whose secondary is divided into two equal parts, with the tube grids connected to the outer terminals and the grid bias fed in at the center. A transformer, T_2 , with a similarly divided primary, is connected to the plates of the tubes. When the signal voltage in the upper half of T_1 is positive with respect to the center

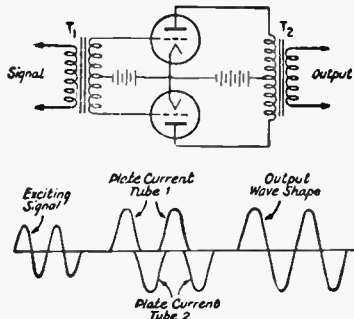


Fig. 319 — Showing how the outputs of the two tubes in push-pull are combined in the Class-B audio amplifier.

connection (*center tap*), the upper tube draws plate current while the lower tube is idle; when the lower half of T_1 becomes positive, the lower tube draws plate current while the upper tube is idle. The voltages induced in the primary of T_2 combine in the secondary to produce an amplified reproduction of the signal.

Class AB — The similarity between the *Class-A B* amplifier, Fig. 319, and the ordinary push-pull circuit (Fig. 317) will be noted. Actually, the only difference lies in the method of operation. If the bias is adjusted so that the tubes draw a moderate value of plate current with no signal, the amplifier will operate Class A at low signal voltages and more nearly Class B at high signal voltages. This method gives low distortion at moderate signal levels and high plate efficiency at high signal levels, making possible the use of relatively small tubes in audio power amplifiers.

A further distinction can be made between amplifiers which draw grid current and those which do not. The *Class-AB₁* amplifier draws no grid current and thus consumes no power from the driving source. The *Class-AB₂* amplifier draws grid current at higher signal levels, and power must be supplied to its grid circuit.

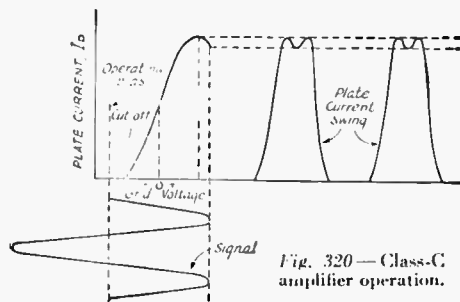


Fig. 320 — Class-C amplifier operation.

Class C — The *Class-C* amplifier is one operated so that the alternating component of the plate current is directly proportional to the plate voltage. The output power is therefore proportional to the square of the plate voltage. Other characteristics inherent to Class-C operation are high plate efficiency, high power output, and relatively low power amplification.

The grid bias is set at a value at least twice that required for plate-current cut-off without excitation. Thus plate current flows during only a fraction of the positive excitation cycle. The exciting signal should be of sufficient amplitude to drive the plate current to the saturation point, as shown in Fig. 320. Since the grid must be driven far into the positive region to cause saturation, considerable numbers of electrons are attracted to the grid at the peak of the cycle, robbing the plate of some that it would normally attract. This causes the droop at the upper bend of the characteristic, and also may cause the plate-current pulse to be indented at the top. The output wave-form is badly distorted, but at radio frequencies the distortion is largely eliminated by the flywheel effect of the tuned output circuit.

3-5 Cathodes; Grid Bias

Types of cathodes — There are two general types of cathodes, known as *directly heated* and *indirectly heated*. In the former the heating current is passed directly through the electron-emitting material, usually a fine wire or filament. In the latter the electrons are emitted from a sleeve or thimble raised to the proper temperature by an electrically-separate heating element as shown in Fig. 321.

Directly-heated or filament-type cathodes may be of pure tungsten, tungsten having a small amount of thorium dissolved in it, or tungsten coated with rare earths (*oxide-coated type*). The latter give the largest amount of electron emission per watt of heating power. Thoriated tungsten filaments are intermediate in electron-emitting efficiency, and are used universally in small and medium-power transmitting tubes. Indirectly-heated cathodes are invariably of the oxide-coated type.

When directly-heated cathodes are operated on alternating current, the cyclic variation of current causes the plate current of the tube to vary at the supply-frequency rate, producing hum in the output. Hum from this source is eliminated in the indirectly heated cathode. This type is also known as the *equi-potential* cathode since all of it is at the same potential, in contrast to the directly heated filament where a voltage drop occurs along the wire.

The source of filament power for a directly heated cathode — battery or transformer — necessarily is directly connected to the tube circuit. With an indirectly heated cathode the source of heating power can be entirely independent of the tube circuit.

The operating temperature of a thoriated tungsten filament is fairly critical, and the specified filament voltage should be maintained within a few per cent. These filaments, as well as oxide-coated cathodes, eventually "lose emission"; that is, the emission efficiency of the cathode decreases until sufficient electron emission for satisfactory tube operation cannot be obtained without raising the cathode temperature to an unsafe value.

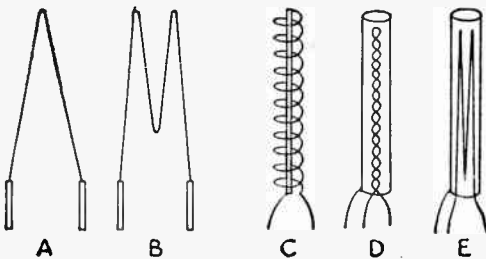


Fig. 321 — Types of cathode construction. Directly heated cathodes or filaments are shown at A, B, and C. The inverted V filament is used in small receiving tubes, the M in both receiving and transmitting tubes. The spiral filament is a transmitting-tube type. The indirectly heated cathodes at D and E show two types of heater construction, one a twisted loop and the other bunched heater wires. Both types tend to cancel the magnetic fields set up by the current through the heater.

Cathode circuits; filament center tap — When a filament-type cathode is heated by a.c., hum can be minimized by making the two ends of the filament have equal and opposite potentials with respect to a center point, usually grounded (§ 2-13), to which the grid and

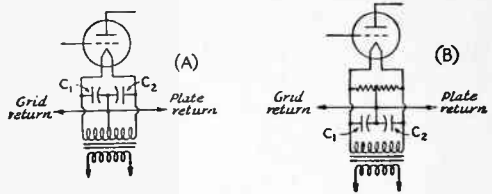


Fig. 322 — Filament transformer center-tap connections.

plate return circuits are connected. The filament transformer winding may be *center-tapped* for this purpose, as shown in Fig. 322-A. With an untapped winding, a center-tapped resistor of 10 to 50 ohms is used, as at B. The by-pass condensers, C_1 and C_2 , are used in r.f. circuits to avoid having the r.f. current flow through the transformer or resistor.

The heater supply for tubes with indirectly heated cathodes sometimes is center-tapped for the same purpose; more frequently, however, one side of the heater is grounded.

Methods of obtaining grid bias — Grid bias may be obtained from a source of voltage especially provided for that purpose, such as a battery or other type of d.c. power supply. This is indicated in Fig. 323-A. A second method, utilizing a *cathode resistor*, is shown at B; d.c. plate current flowing through the resistor causes a voltage drop which, with the connections shown, has the right polarity to bias the grid negatively with respect to the cathode. The value of the resistor is determined by the bias required and the plate current which flows at that value of bias, as found from the tube characteristic curves; with the voltage and current known, the resistance can be determined by Ohm's Law (§ 2-6):

$$R_c = \frac{E \times 1000}{I_c}$$

where R_c = cathode bias resistor in ohms

E = desired bias voltage

I_c = total d.c. cathode current in milliamperes.

If the tube is a multi-element type, the screen- and suppressor-grid currents should be added to the plate current to obtain the total cathode current. The control-grid current also should be included if the control grid is driven positive.

The a.c. component of plate current flowing through the cathode resistor will cause an a.c. voltage drop which gives negative feedback (§ 3-3) into the grid circuit, and thus reduces the amplification. To prevent this, the resistor usually is by-passed (§ 2-13), C_c being the *cathode by-pass condenser*. To be effective, the reactance of the by-pass condenser must be small compared to R_c at the frequency being

amplified. This condition generally is satisfied if the reactance is 10 percent or less of the cathode resistance. In audio-frequency amplifiers, the *lowest* frequency at which full amplification must be secured should be used in calculating the required capacity.

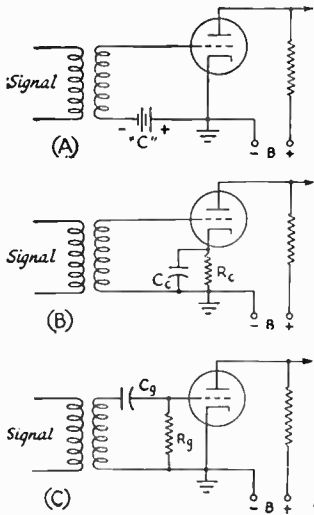


Fig. 323—The three basic methods of obtaining grid bias. A, fixed bias; B, cathode bias; C, grid-leak bias.

A third biasing method is by use of a *grid leak*, R_g in Fig. 323-C. This requires that the exciting voltage be positive with respect to the cathode during part of the cycle, so that grid current will flow. The flow of grid current through the grid leak causes a voltage drop across the resistor, which gives the grid a negative bias. The time constant (§ 2-6) of the grid leak and grid condenser should be large in comparison to the time of one cycle of the exciting voltage, so that the grid bias will be substantially constant and will not follow the variations in a.c. grid voltage. For grid-leak bias,

$$R_g = \frac{E \times 1000}{I_g}$$

where R_g is the grid-leak resistance in ohms, E the desired bias voltage and I_g the d.c. grid current in ma.

For two tubes operated in push-pull or parallel with a common cathode- or grid-leak resistor, the required resistance becomes one-half that for a single tube. In push-pull Class-A circuits operating at audio frequencies, it is unnecessary to by-pass the cathode resistor. In this case the a.c. component of cathode current in one tube is out of phase with the a.c. component in the other, so that the two cancel each other.

The choice of a biasing method depends upon the type of operation. Fixed bias usually is required where the d.c. plate current of the amplifier varies in operation, as in Class-B audio-frequency amplifiers; if cathode bias is used the bias voltage would vary with the

plate current. Since the plate current of a Class-A amplifier is constant with or without signal, such amplifiers almost invariably have cathode bias. Grid-leak bias cannot be used with amplifiers operated so that the grid is always negative with respect to the cathode, since in such a case there is no grid current and hence no voltage drop in the grid leak. Grid-leak bias is chiefly used for r.f. power amplifiers and for certain types of detectors. In power amplifiers, a combination of two or even all three types of bias may be used on one tube.

§ 3-6-A Multi-Grid Tubes

Radio-frequency amplification — As described in § 3-1, the reactances of the grid-to-cathode and plate-to-cathode capacities (together with unavoidable stray capacities) in a vacuum tube become very low at frequencies higher than the audio-frequency range. As a result, ordinary resistance, impedance or transformer coupling cannot be used at radio frequencies because these capacities act as low-reactance by-passes across the input and output circuits. Hence the total impedance in either the plate or the grid circuit is too low for appreciable voltage to be developed.

This situation can be overcome by using resonant circuits as impedances for radio-frequency amplification. As described in § 2-10, the parallel impedance of a resonant circuit can reach quite high values when the Q is high. Values of parallel-resonant impedance suitable for effective amplification are readily obtainable with reasonably well-designed circuits. The tube and stray capacities become part of the tuning capacity and thus are made to serve a useful purpose. However, the circuits have maximum impedance at the resonant frequency only, hence the amplification will decrease at frequencies somewhat removed from resonance. Thus a radio-frequency amplifier must be designed for a specific frequency.

An elementary circuit illustrating the principles of r.f. amplification is shown in Fig. 324. The grid circuit, L_1C_1 , and the plate circuit, L_2C_2 , must be tuned to the same frequency for maximum amplification. But if the plate circuit is tuned slightly to the high-frequency side of resonance it will show inductive reactance, and as described in § 3-3 energy will be transferred from the plate circuit to the grid circuit under such conditions. If enough energy is transferred the tube will generate a self-sustaining r.f. current, in which case it is said to be *oscillating*. When oscillation commences the circuit ceases to amplify incoming signals, since it is generating a signal of its

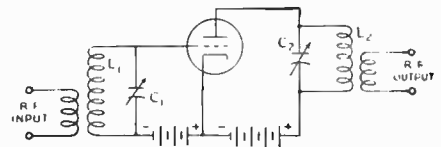


Fig. 324—Elementary radio-frequency amplifier.

own. Unfortunately, it is almost impossible to prevent such oscillation in a simple triode amplifier such as is shown in Fig. 324.

Special "neutralizing" circuits (§ 4-7) have been devised to prevent oscillation with triode amplifiers, but most of these are more suitable for use in transmitting applications, where the amplifier does not have to be tunable over a wide range of frequencies, than in receivers. However, oscillation can be avoided by using a circuit in which the feed-back is negative rather than positive, as indicated in the next paragraph.

Grounded-grid amplifier — In the circuit of Fig. 325 the grid of the tube is connected to ground and the cathode is connected to the

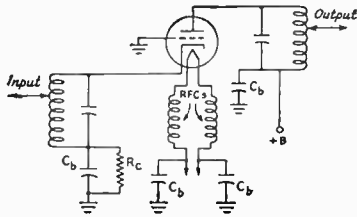


Fig. 325 — Grounded-grid amplifier circuit.

high-potential side of the input resonant circuit, reversing the usual connections. The output circuit is connected in the customary way between plate and ground. Since the alternating component of plate current must flow through the tuned input circuit to return to the cathode there is feed-back from the plate to the grid circuit, but it is negative rather than positive feed-back. Hence this coupling between the two circuits will not cause oscillation.

However, it is still possible for the circuit to oscillate if there is capacity coupling between the plate and cathode. The grounded grid prevents this coupling by acting as a shield between the other two elements (§ 2-11). The circuit is most successful with tubes having very low plate-to-cathode capacity. It is used principally at ultra-high frequencies (where the screen-grid tubes described in the next paragraph become ineffective as amplifiers) with tubes designed especially for the purpose.

The r.f. chokes in the cathode circuit are used to isolate the heater from ground and thus eliminate the effect of the capacity between cathode and heater. This capacity tends to short-circuit the tuned input circuit and thus prevents the amplifier from operating properly.

Screen-grid tubes — The grid-plate capacity can be eliminated, or at least reduced to a negligible value, by inserting a second grid between the control grid and the plate as indicated in Fig. 326. The second grid, called the *screen grid* or *shield grid*, acts as an electrostatic shield (§ 2-11) between the control grid and plate. It is made in the form of a grid or coarse screen rather than as a solid metal sheet, so that electrons can pass through it to the

plate; a solid shield would entirely prevent the flow of plate current. The screen grid is connected to the cathode through a by-pass condenser, which has low impedance at the radio frequency being amplified. The electric lines of force from the plate terminate on the screen grid, very little of the field getting through to the control grid; similarly, the field set up by the control grid does not penetrate past the screen grid. Thus there is no common field between the control grid and plate; hence no capacity between these two tube elements.

Since the electric field from the plate does not penetrate into the region occupied by the control grid, which is the region in which most of the space charge is concentrated, the plate is unable to exert an attraction upon the electrons in this region. Consequently, the plate voltage cannot control the flow of plate current as it does in a triode. In order to get electrons to the plate, it is necessary to apply a positive potential (with respect to the cathode) to the screen. The screen then attracts electrons much as does the plate in a triode tube. In traveling toward the screen the electrons acquire velocity, so that most of them shoot between the screen wires into the field from the plate. Those that pass through and are attracted to the plate constitute the plate current of the tube. A certain proportion do strike the screen, however, with the result that some current also flows to the screen grid. The screen current will be low compared to the plate current in a *tetrode*, or four-element tube, however.

Secondary emission — When an electron traveling at appreciable velocity through a tube strikes the plate it dislodges other electrons. These "splash" from the plate into the

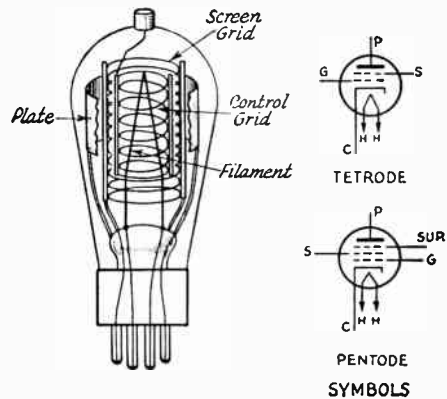


Fig. 326 — Representative arrangement of elements in a screen-grid tube, with front part of plate and screen-grid cut away. The screen grid usually is made longer than either the control grid or plate, so that the shielding will be as effective as possible. In this drawing the control grid connection is made through a cap on the top of the tube, thus eliminating the capacity which would exist between the plate and grid lead wires if both passed through the base. Some modern tubes which have both leads going through the base use special shielding and construction to eliminate capacity. Symbols for pentode and tetrode tubes: H, heater; C, cathode; G, control grid; P, plate; S, screen grid; Sup., suppressor grid.

interelement space, a phenomenon called *secondary emission*. In a triode ordinarily operated with the grid negative with respect to cathode, secondary electrons are repelled back into the plate and cause no disturbance. In the screen-grid tube, however, the positively charged screen attracts the secondary electrons, causing a reverse current to flow between screen and plate. The effect is particularly marked when the plate and screen potentials are nearly equal, which may be the case during the part of the a.c. cycle when the instantaneous plate current is large and the plate voltage low (§ 3-3).

Pentode tubes — To overcome the effects of secondary emission, a third grid, called the *suppressor grid*, may be inserted between the screen and plate. This grid, which is connected directly to the cathode, repels the relatively low-velocity secondary electrons. They are driven back to the plate without appreciably obstructing the regular plate-current flow.

Although the screen grid in either the tetrode or pentode greatly reduces the influence of the plate upon plate-current flow, it is quite obvious that the control grid still can control the plate current in essentially the same way that it does in a triode, since the control grid is still in the space-charge region. Consequently, the grid-plate transconductance (or mutual conductance) of a tetrode or pentode will be of the same order of value as in a triode of corresponding structure. On the other hand, since the plate voltage has very little effect on the plate-current flow, both the amplification factor and plate resistance of a pentode or tetrode are very high, as is apparent from the definitions of these constants (§ 3-2). In small receiving pentodes the amplification factor is of the order of 1000 or higher, while the plate resistance may be from 0.5 to 1 or more megohms. Because of the high plate resistance, the actual voltage amplification possible with a pentode is very much less than the large amplification factor might indicate. In resistance-coupled audio-frequency amplifiers, voltage amplification or gain of 100 to 200 is typical.

A typical set of characteristic curves for a small pentode is shown in Fig. 327. That the plate voltage has little effect on the plate current is indicated by the fact that the curves are practically horizontal once the plate voltage is

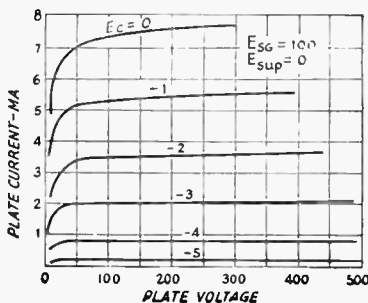


Fig. 327 — Plate voltage vs. plate current curves for a small receiving pentode. Screen-grid voltage, E_{sg} , is 100 volts and suppressor-grid voltage, E_{sup} , is zero.

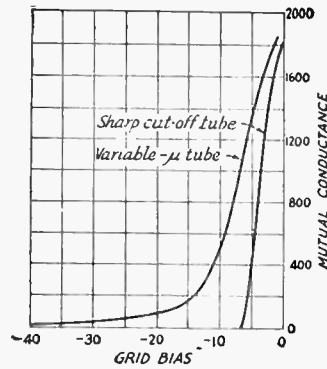


Fig. 328 — Curves showing the relationship between mutual conductance vs. negative grid bias for two small receiving pentodes, one being a sharp cut-off type and the other a variable- μ type.

high enough to prevent the electrons in the space between the screen grid and the plate from being attracted back to the screen. The plate potential at which this occurs is less than the screen potential, because the electrons entering the space have considerable velocity and hence tend to move away from the screen despite the fact that it has a positive charge.

In addition to their applications as radio-frequency amplifiers, pentode or tetrode screen grid tubes also can be constructed for audio-frequency power amplification. In tubes designed for this purpose the shielding effect of the screen grid is not so important: the chief function of the screen is to serve as an accelerator of the electrons, so that large values of plate current can be drawn at relatively low plate voltages. Such tubes have quite high power sensitivity (§ 3-4) compared to triodes of the same power output, because the amplification factor of an equivalent triode has to be made quite low in order to secure the same plate current at the same plate voltage. Because of the low μ , the triode requires a relatively large signal voltage for full output, hence has low power sensitivity. The harmonic distortion is somewhat greater with pentodes and tetrodes than with triodes, however.

Variable- μ and sharp cut-off tubes — Receiving screen-grid tetrodes and pentodes for radio-frequency voltage amplification are made in two types, known as *sharp cut-off* and *variable- μ* or "super-control" types. In the sharp cut-off type the amplification factor is practically constant regardless of grid bias, while in the variable- μ type the amplification factor decreases as the negative bias is increased. The purpose of this design is to permit the tube to handle large signal voltages without distortion in circuits in which grid-bias control is used to vary the mutual conductance, and hence the amplification.

The way in which mutual conductance varies with grid bias in two typical small receiving pentodes, similar except in that one is a sharp cut-off type and the other a variable- μ type, is shown in Fig. 328. Obviously, the variable- μ type can handle a much larger signal voltage without swinging beyond either the point of zero grid bias or of plate-current cut-

off (zero mutual conductance), if the bias is properly chosen.

Beam tubes — A "beam"-type tube is a tetrode with grids so constructed as to form the electrons traveling to the plate into concentrated beams, resulting in higher plate efficiency and power sensitivity. Suitable design also overcomes the effects of secondary emission without the necessity for a suppressor grid. Tubes constructed on the beam principle are used in receivers as both r.f. and audio amplifiers, and are built in larger sizes for transmitting circuits.

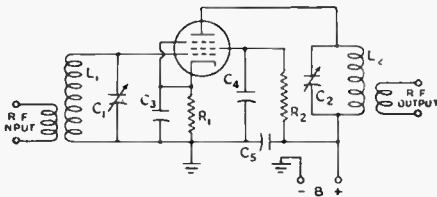


Fig. 329 — Pentode r.f. amplifier circuit. L_1C_1 and L_2C_2 are tuned to the same frequency. R_1 is the cathode resistor, by-passed for r.f. by C_3 . R_2 is the screen voltage-dropping resistor, by-passed by C_4 . C_5 is the plate by-pass.

3-6-B Pentode Amplifiers

R.F. amplification — A fundamental circuit for radio-frequency amplification with a pentode tube is shown in Fig. 329. The grid and plate circuits may be tuned to the same frequency, thus obtaining maximum amplification, without danger of oscillation provided there is no feed-back coupling between the tuned circuits themselves. Practical variations of this circuit and their application to receivers are discussed in § 7-6 and § 7-11.

A.F. amplification — Receiving-type pentodes frequently are used as voltage amplifiers for audio frequencies, using the circuit shown in basic form in Fig. 330. In this application they are capable of much higher voltage gain than can be obtained from triodes, and have the advantage that since there is no coupling from plate to grid there is no increase in input capacity with amplification (§ 3-3). For the latter reason it is possible to obtain high gain, in resistance-coupled amplifiers, at considerably higher frequencies than is possible with a triode.

The discussion of amplification in § 3-3 applies equally to pentodes and triodes, with the exception that the plate resistance of a pentode is so high that the amplification is

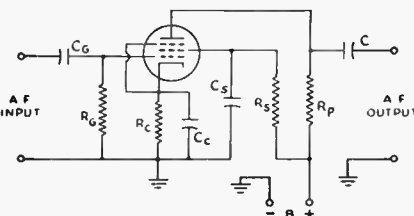


Fig. 330 — Typical pentode audio-frequency amplifier.

usually considered to be proportional to the plate load resistance alone. For maximum voltage gain, R_p should have as high resistance as possible without causing too great a voltage drop. Values range from 0.1 to 0.5 megohm. The value of R_c depends upon R_p , which principally determines the plate current. Values for the screen resistor, R_s , may vary from 0.25 to 2 megohms. A screen by-pass condenser (C_s) of 0.1 μ f. will be adequate in most cases.

Table I in Chapter Fourteen shows suitable values for the more popular types of amplifier tubes. The calculated stage gain and peak undistorted output voltage also are given.

Plate and screen voltage — Since the d.c. plate current flows through any resistance placed in the plate circuit of a tube as a load or coupling medium (§ 3-3), the actual voltage at the plate is less than the supply voltage by the voltage drop across the total resistance.

With transformer coupling this effect is not ordinarily of great importance, because the inductance of the transformer primary provides a high-impedance load at audio frequencies, while the d.c. resistance of the winding causes only a small drop in d.c. plate voltage.

In a resistance-coupled or parallel-fed stage the operating voltage is less than the supply voltage by the drop through the load resistor, R_p . Thus, in Fig. 331-A, $E_p = E_b - (I_p \times R_p)$.

Screen voltage is determined in the same way, using the screen current, I_s , to calculate the drop across the screen dropping resistor, R_s .

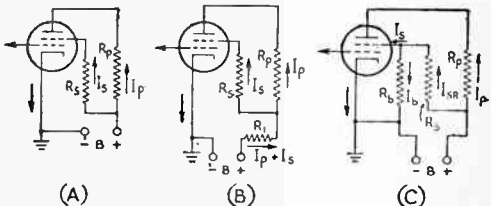


Fig. 331 — Calculation of plate and screen voltages.

In Fig. 331-B both plate and screen current flows through a common filter resistor, so that both currents must be added in calculating the voltage drop across it. Thus

$$E_p = E_b - (I_p + I_s)(R_1) - I_p R_p$$

$$E_s = E_b - (I_p + I_s)(R_1) - I_s R_s$$

In Fig. 331-C, the screen voltage, E_s , is obtained from a tap on a voltage divider consisting of R_s and R_b . The screen voltage, E_s , is equal to the voltage drop across R_b . First assigning a value of bleeder current, I_b (§ 8-4), this value is added to I_s to obtain I_{sr} . Then $R_s = E_s/I_{sr}$. The voltage across R_b is the difference between the screen voltage and the supply voltage, or $E_s = E_b - E_s/I_{sr}$. E_p is determined as above.

The resistance-capacity filter (§ 2-11) in Fig. 332, $C_f R_f$, is a decoupling circuit which isolates the stage from the power supply, to eliminate unwanted coupling between stages through the common impedance of the power

supply. Although shown in connection with a triode amplifier in the diagram, the same type of filter is used with pentodes.

Wide-band amplifiers — Amplification of audio frequencies, which extend from about 50 to 15,000 cycles, presents no particularly difficult problems so long as the design points discussed in § 3-3 are observed. However, for amplifying signals such as television signals or pulses having a time duration of only a few millionths of a second it is necessary to extend the frequency response of the amplifier well beyond the audio frequency range — and even well into the medium radio-frequency range. At the same time it is frequently necessary to extend the lower frequency limit of the amplifier as well. This extension of range is made possible by the use of *compensating* circuits.

Low-frequency compensation — While the amplitude response of a resistance-coupled amplifier usually is satisfactory at low frequencies, the phase angle introduced by the output coupling condenser and the next-stage grid resistor is sufficient to prevent proper reproduction of low-frequency square waves unless very large values are employed. Yet such

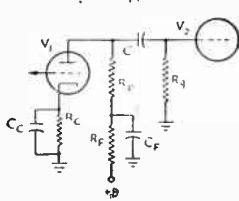


Fig. 332 — Decoupling in a resistance-coupled amplifier.

large values increase the time constant of the circuit, introduce grid-current difficulties in the following stage, and may even induce relaxation oscillations (motor-boating).

The effect of the time constant of the $C_{G2}R_{G2}$, Fig. 333, may be compensated for by proper design of the amplifier plate circuit. The design equation is $C_F R_P = C_{G2} R_{G2}$ provided the resistance of the decoupling resistor, R_P , is at least 10 times the reactance of C_F at the lowest frequency to be amplified.

High-frequency compensation — It was brought out in § 3-3 that the capacities shunting the plate load resistor are responsible for loss of amplification at the high frequencies in a resistance-coupled amplifier. If the plate load resistor is made low enough in value, the effect of the shunting capacities will be minimized and the upper frequency range will be extended, but at the expense of gain at the lower frequencies. Reducing the plate load resistance to a value low enough to extend the range of uniform amplification to a few megacycles would be impractical with ordinary tubes, since there would be little or no voltage gain, but it is quite practicable with special high-transconductance pentodes such as the 6AC7 and 6AG5. These tubes will give voltage gains of 10 to 15 with plate load resistances as low as a few thousand ohms.

A further extension of high frequency response can be secured by special compensating circuits. The most widely-used method is the *shunt-peaking* circuit, with a resonating (peak-

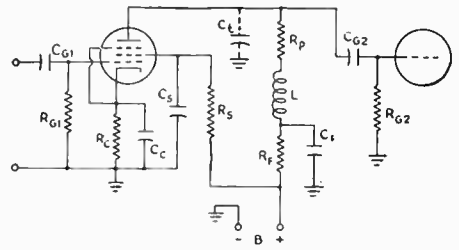


Fig. 333 — Wide-band frequency-compensated amplifier.

ing) inductance in parallel with the circuit capacity, as shown in Fig. 333. By resonance effects this raises the impedance to an extent and over a frequency range determined by the Q of the circuit consisting of L , R_P and C_t . Since R_P is relatively large for a resonant circuit, the Q is fairly low and the resonance curve is quite broad. This is desirable for an amplifier intended for wide-band applications. The design values of L and R_P are based on the shunt capacity, C_t , and the maximum required frequency, f_{max} . C_t can be estimated by adding 3 to 5 $\mu\mu\text{fd}$. (for socket and wiring) to the sum of the tube input and output capacities.

The reactance of L is made one-half the reactance of C_t at f_{max} . This is equivalent to making the resonant frequency between L and C_t equal to 1.41 times f_{max} .

Simplified design equations for shunt peaking compensation are as follows:

$$R_P = \frac{1}{2\pi f_{max} C_t}$$

$$L = 0.5 C_t R_P^2$$

Typical values of R_P are from 2000 to 10,000 ohms; of L , from 25 to 100 μh .

Cathode follower — The *cathode-coupler* or *cathode follower* shown in Fig. 334, differs from a conventional amplifier in that output is taken from the cathode circuit rather than from the plate. The circuit is applicable wherever matching to a low value of load impedance (fifty to several hundred ohms) is required and the use of a transformer is impracticable, as in wide-band amplifiers. Because the cathode follower is inherently degenerative, it is particularly useful wherever equalized frequency response and minimum phase shift are important. Power amplification comparable to that of an equivalent plate-coupled stage may be secured, but the voltage gain is always less than unity.

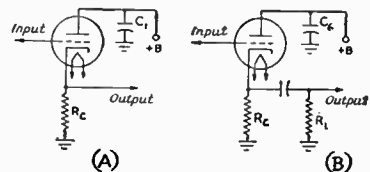


Fig. 334 — Cathode follower or inverted amplifier circuits. A, direct-coupled output; C, resistance-capacity coupling to load. R_k is the usual cathode-bias resistor.

¶ 3-6-C Special-Purpose Tubes

Multi-purpose types — A number of combination types of tubes have been constructed to perform multiple functions, particularly in receiver circuits. For the most part these are multi-unit tubes made up of individual tube element structures, combined in a single bulb for compactness and economy. Among the simplest are full-wave rectifiers, combining two diodes in one envelope, and twin triodes, consisting of two triodes in one bulb for Class-B audio amplification. More complex types include duplex-diode triodes, duplex-diode pentodes, converters and mixers (for superheterodyne receivers), combination power tubes and rectifiers, and so on. In many cases the nature can be identified by the name.

Mercury-vapor rectifiers — For a given value of plate current, the power lost in a diode rectifier (§ 3-1) will be lessened if it is possible to decrease the plate-cathode voltage at which the current is obtained. If a small amount of mercury is put in the tube, the mercury will vaporize when the cathode is heated, and, further, will ionize (§ 2-4) when plate voltage is applied. The positive ions neutralize the space charge and reduce the plate-cathode voltage drop to a practically constant value of about 15 volts, regardless of the value of plate current. Since this voltage drop is smaller than can be attained with purely thermionic conduction, there is less power loss in the rectifier. Voltage drop is constant despite variations in load current. Mercury-vapor tubes are widely used in rectifiers built to deliver large power outputs.

Grid-control rectifiers — If a grid is inserted in a mercury-vapor rectifier it is found that with sufficient negative grid bias it is possible to prevent plate current from flowing, but only if the bias is present before plate voltage is applied. If the bias is lowered to the point where plate current can flow, the mercury vapor will ionize and the grid will lose control of plate current, since the space charge disappears when ionization occurs. It can assume control again only after the plate voltage is reduced below the ionizing potential. The same phenomenon also occurs in triodes filled with other gases which ionize at low pressure. Grid-control rectifiers or thyratrons find considerable application in "electronic switching."

¶ 3-7-A Oscillators

Self-oscillation — An amplifier tube can be made to generate a sustained radio-frequency current (§ 3-6-A) because more energy is developed in the plate circuit than is required in the grid circuit. If enough energy is fed back from the plate to the grid, the feed-back process becomes independent of any applied signal voltage. The tube supplies its own grid excitation and continuous oscillations are generated. The actual energy required to overcome the grid losses is, in the end, taken from the d.c. plate supply.

The process of oscillation may also be considered from the standpoint of *negative resistance*. As previously described (§ 3-3), positive feed-back is equivalent to shunting a negative resistance across the input circuit of the tube. When the value of negative resistance becomes lower than the positive resistance of the circuit (if the circuit is parallel resonant the positive resistance will be the resonant impedance of the circuit) the net resistance is negative, indicating that the circuit can be looked upon as a *source of energy*. Such a source is capable of maintaining a constant voltage which can be amplified by the tube. The actual energy, of course, comes from the plate circuit of the tube, so that the two viewpoints are equivalent.

A circuit having the property of generating continuous oscillations is called an *oscillator*. It is not necessary to apply external excitation to such a circuit, since any random variation in current will be amplified to cause oscillation. The frequency of oscillation will be that at which the feed-back voltage has the proper phase and amplitude. Where resonant circuits are associated with oscillators, the oscillation frequency is very nearly that of the tuned circuit.

Excitation and bias — The excitation voltage required depends upon the characteristics of the tube and the losses in the grid circuit. In practically all oscillators the grid is driven positive during part of the cycle, so that power is consumed in the grid circuit (§ 3-2). This power must be supplied from the plate circuit. With insufficient excitation, the tube will not oscillate; with over-excitation, the *grid losses* (power consumed in the grid circuit) will be excessive.

Oscillators customarily are grid-leak biased (§ 3-5). This takes advantage of the grid-current flow and gives better operation, the bias adjusting itself to the excitation voltage.

Tank circuit — The resonant circuit associated with the oscillator is commonly called the *tank circuit*, a name derived from the storage of energy associated with a resonant circuit (§ 2-10). The term is applied to any resonant circuit in transmitting applications, whether in an oscillator or in an amplifier.

Plate efficiency — The *plate efficiency* (§ 3-3) of an oscillator depends upon the load resistance, excitation and other operating factors. Usually it is around 50 per cent. It is not as high as in an amplifier, since the oscillator must supply its own grid losses. These may represent 10 to 20 per cent of the output power.

Power output — The *power output* of an oscillator is the useful a.c. power consumed in any load connected to the oscillator. The load may be coupled as described in § 2-11.

Frequency stability — The frequency stability of an oscillator is its ability to maintain constant frequency. The more important factors which may cause a change in frequency are (1) temperature, (2) plate voltage, (3) loading, (4) mechanical variations of circuit elements. Temperature changes will cause vacuum-tube

elements to expand or contract slightly, thus causing variations in the interelectrode capacities (§ 3-2). Since these are unavoidably part of the tuned circuit, the frequency will change correspondingly. Temperature changes in the coil or condenser will alter their inductance or capacity slightly, again causing a shift in the resonant frequency. These effects are relatively slow in operation, and the frequency change caused by them is called *drift*.

Load variations act in much the same way as plate voltage variations. A temperature change in the load may also result in drift.

Plate-voltage variations will cause a corresponding instantaneous shift in frequency; this type of frequency shift is called *dynamic instability*. Dynamic instability can be reduced by using a tuned circuit of high effective Q . Since the tube and load represent a relatively low resistance in parallel with the circuit, this means that a low L/C ratio ("high- C ") must be used (§ 2-10) and that the circuit should be lightly loaded. Dynamic stability also can be improved by using a high value of grid leak, which gives high grid bias and raises the effective resistance of the tube as seen by the tank circuit, and by using relatively high plate voltage and low plate current. Drift can be minimized by keeping the d.c. input low for the size of tube, by using coils of large wire to prevent undue temperature rise, and by providing good ventilation to carry off heat rapidly. A low L/C ratio in the tank circuit is desirable, because the interelectrode capacity variations have proportionately less effect on the frequency when shunted by a large condenser.

Mechanical variations, usually caused by vibration, cause changes in inductance and/or capacity which in turn cause the frequency to "wobble" in step with the vibration.

Mechanical instability can be minimized by using well-designed components and by insulating the oscillator from mechanical vibration.

3-7-B Feed-Back Oscillators

Magnetic feed-back — One form of feed-back is by electromagnetic coupling between plate (output) and grid (input) circuits. Two representative circuits of this type are shown in Fig. 335. That at A is called the *tickler* circuit. The amplified current flowing in the "tickler," L_2 , induces a voltage in L_1 in the proper phase when both coils are wound in the same direction and connected as shown in the

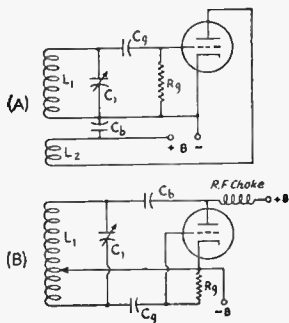


Fig. 335 — Two types of oscillator circuits with magnetic feed-back. A, grid tickler; B, Hartley.

diagram. The feed-back can be adjusted by adjusting the coupling between L_1 and L_2 .

The *Hartley* circuit, B, is similar in principle. There is only one coil, but it is divided so that part of it is in the plate circuit and part in the grid circuit. The magnetic coupling between the two sections provides the feed-back, which can be adjusted by moving the tap on the coil.

Capacity feed-back — The feed-back can also be obtained through capacity coupling, as shown in Fig. 336. In A, the *Colpitts* circuit, the voltage across the resonant circuit is divided, by means of the series condensers, into two parts. The instantaneous voltages at the ends of the circuit are opposite in polarity with respect to the cathode, hence in the right phase to sustain oscillation. The tuned-grid tuned-plate circuit at B utilizes the grid-plate capacity of the tube to provide feed-back coupling. There should be no magnetic coupling

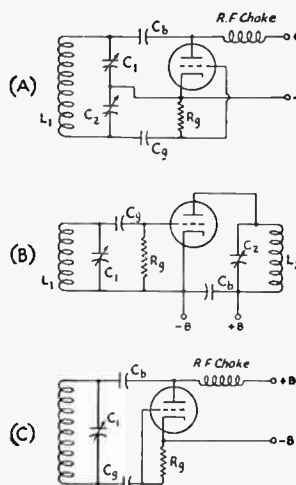


Fig. 336 — Capacity feed-back oscillators. A, Colpitts; B, tuned-grid; C, ultraudion.

between the two tuned-circuit coils. Feed-back can be adjusted by varying the tuning of either the grid or plate circuit. The circuit with the higher Q (§ 2-10) determines the frequency of oscillation. The plate circuit must be tuned to a slightly higher frequency than the grid circuit, so that it will have inductive reactance and hence give positive feed-back (§ 3-3). The amount of detuning is so small it is customary to assume that the circuits are tuned to the same frequency.

The *ultraudion* circuit at C is equivalent to the *Colpitts*, with the voltage division for oscillation brought about through the grid-to-filament and plate-to-filament capacities of the tube. In this and in the *Colpitts* circuit, the feed-back can be controlled by varying the ratio of the two capacities. In the *ultraudion* circuit, this can be done by connecting a small variable condenser between grid and cathode. Feed-back decreases with increasing capacity.

The electron-coupled oscillator — The effects of loading and coupling to the next stage can be greatly reduced by use of the *electron-coupled* circuit, in which a screen-grid tube (§ 3-5) is so connected that its screen grid is used as a plate, in conjunction with the control grid and cathode, in an ordinary triode oscillator circuit. The screen is operated

at ground r. f. potential (§2-13) to act as a shield between the actual plate and the cathode and control grid; the latter two elements therefore must be above ground potential. The out-

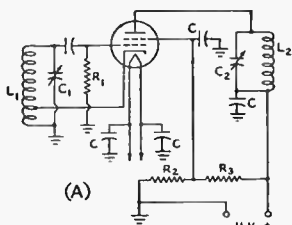


Fig. 337 — Electron-coupled oscillator circuit.

put is taken from the plate circuit. Under these conditions the capacity coupling (§ 2-11) between the plate and other ungrounded tube elements is quite small, hence the output power is secured almost entirely by variations in the plate current caused by the varying potentials on the grid and cathode. Since in a screen-grid tube the plate voltage has a relatively small effect on the plate current, the reaction on the oscillator frequency for different conditions of loading is small.

A Hartley circuit is used in the frequency-determining portion of the oscillator shown in Fig. 337, where L_1C_1 is the oscillator tank circuit. The screen is grounded for r.f. through a by-pass condenser (§ 2-13), but has the usual d.c. potential. The cathode connection is made to a tap on the tank coil to provide feed-back. The resonant plate circuit, L_2C_2 , is tuned either to the oscillation frequency or to a harmonic. Untuned output coupling also may be used; the output voltage and power are considerably lower, but better isolation between oscillator and amplifier is secured.

If the oscillator tube is a pentode having an external suppressor connection the suppressor grid should be grounded. This provides additional internal shielding and further isolates the plate from the frequency-determining circuit.

Franklin oscillator — The Franklin oscillator circuit of Fig. 338, popular abroad, has characteristics similar to the c.c.o. A high-gain feed-back amplifier is very loosely coupled to a tank circuit, LC , via two condensers, C_1 and C_2 , of extremely small capacity. So weak is the coupling that the tube circuit has negligible effect upon the frequency-controlling tank.

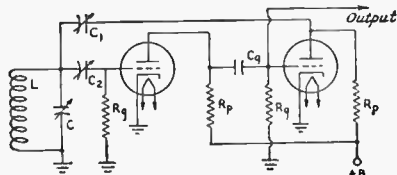


Fig. 338 — Franklin master-oscillator circuit.

C_1, C_2 — Approximately 1 to 2- μ fd. (adjustable).
 C_c — 0.001- μ fd. R_g, R_p — 50,000 ohms.

Crystal oscillators — Since a properly cut quartz crystal is equivalent to a high-Q tuned circuit (§ 2-10), it may be substituted for a conventional tuned circuit in an oscillator to control the frequency of oscillation. A simple crystal oscillator circuit is shown in Fig. 339. It is similar to the tuned-plate tuned-grid circuit except that a crystal is substituted for the resonant grid circuit. Detailed information on crystal oscillators is given in Chapter Four.

Series and parallel feed — A circuit such as the tickler circuit of Fig. 335-A is said to be *series fed* because the source of plate voltage and the r.f. plate circuit (the tickler coil) are connected in series; hence the d.c. plate current flows through the coil to the plate. A by-pass (§ 2-13) condenser, C_b , is connected across the plate supply to shunt the r.f. current around the power source. Other examples of series plate feed are shown in Figs. 336-B and 337.

In some cases the source of plate power must be connected in parallel with the tuned circuit to provide a direct-current path to the plate. This is illustrated in Fig. 335-B, where it would be impossible to feed the plate current through the coil because there is a direct connection between the coil and cathode. Hence the voltage is applied to the plate through a radio-frequency choke, which prevents the r.f. current

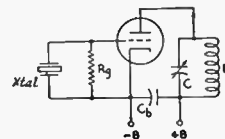


Fig. 339 — Simple crystal oscillator circuit. Many variations of this basic circuit are used in practice.

from flowing to the plate supply and thus short-circuiting the oscillator. The blocking condenser, C_b , provides a low-impedance path for radio-frequency current flow but is an open circuit for direct current (§ 2-13). Other examples of parallel feed are shown in Figs. 336-A and 336-C.

Values for the r.f. chokes, by-pass and blocking condensers shown will be determined by the considerations outlined in § 2-13.

¶ 3-7-C Negative Resistance Oscillators.

Negative-resistance oscillations — In addition to its ability to simulate negative resistance by feed-back (§ 3-7-A), a vacuum tube can in itself be made to show negative resistance by a number of arrangements of electrode potentials. When a tube so operated is connected to a parallel-resonant circuit, oscillation will be established if the negative resistance is less than the parallel impedance of the resonant circuit. Typical oscillator circuits are shown in Fig. 340.

The circuit of Fig. 340-A is that of the *dynatron* oscillator, which functions because of the secondary emission from the plate occurring in certain types of screen-grid tetrodes. The simplest but also the least stable of the negative-resistance or two-terminal oscillators,

it makes use of the fact that the plate current of a screen-grid tetrode decreases when the plate voltage is increased at certain values of screen voltage, giving a negative plate-resistance characteristic.

In the negative-transconductance or *transitron* circuit shown in Fig. 340-B,

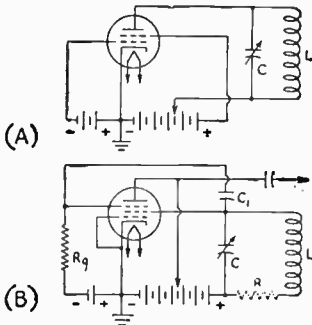


Fig. 340 — Negative-resistance oscillator circuits. A, dynatron; B, transitron.

negative resistance is produced by virtue of the fact that, if the suppressor grid of a pentode is given negative bias, electrons which normally would pass through to the plate are turned back to the screen, thus increasing the

screen current and reversing normal tube action (§ 3-2). The negative resistance produced between the screen and suppressor grids is sufficiently low so that ordinary tuned circuits will oscillate readily up to 15 Mc. or so.

3-7-D Other Types of Oscillators

Resistance-capacity tuning — It is possible to replace the *LC* resonant circuit in an oscillator by a resistance-capacity combination having an appropriate time constant, in which case $f = 1/2\pi RC$. Moreover, by varying either *R* or *C* the circuit can be tuned over a wide range in the same manner as an *LC* circuit.

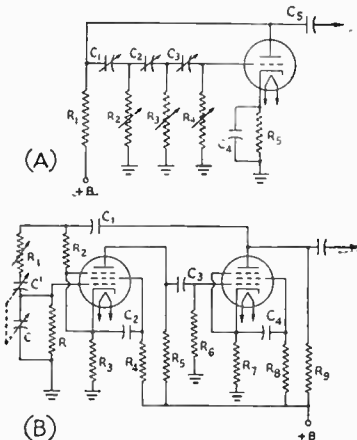


Fig. 341 — Resistance-capacity oscillators. A, phase-shift. B, negative feedback.

connected between output and input, so arranged that just enough signal is fed back 180° out of phase at the desired frequency to sustain oscillation. By careful feed-back adjustment, excellent sine-wave form with good frequency stability may be obtained.

The two-tube *RC*-tuned circuit at B is derived from a two-stage cascade resistance-coupled amplifier with pentode tubes, the second tube constituting the phase-shifting element supplying a regenerative signal to the adjustable *C*, *C*₁ and *R*₁ combination at the desired frequency, while at all other frequencies the circuit is degenerative.

Phase-shift oscillators are most useful at audio frequencies, although they can be made to operate up to about 50 kc.

Relaxation oscillators — There is another basic category of oscillators, the *relaxation* type, in which the oscillation frequency is controlled not by a resonant circuit but by the reciprocating change of a current or voltage through the charging or discharging of a condenser when a certain critical value is reached. Relaxation oscillation requires, first, a means for charging a condenser (or other reactive element) at a uniform rate and, second, means for rapidly discharging this condenser once a pre-determined voltage has been built up across it. The action is characterized by a period of rapid change or instability followed by a period of relative quiescence or stability during which the stored-up energy transferred or otherwise dissipated in the circuit.

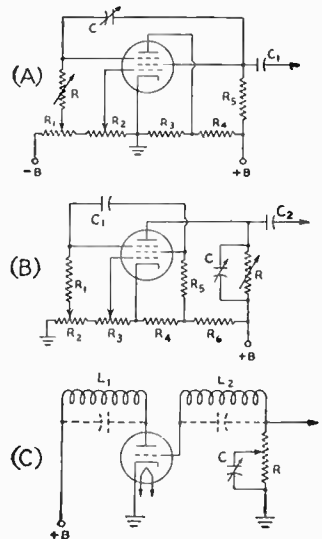


Fig. 342 — Typical relaxation oscillators. A, "dynatron"-type pentode circuit. B, high-frequency pentode circuit. C, squegging oscillator.

Relaxation oscillators have high harmonic content (nonsinusoidal output) and are inherently unstable, permitting ready synchronization with an external controlling voltage.

In the circuit of Fig. 342-A, the operation is based on the reversed screen-current or dynatron characteristic of a pentode tube, the frequency being determined by the rate at which the feed-back condenser, *C*, discharges through the tube. Apart from the frequency-controlling mechanism, this circuit resembles that of the transitron oscillator (Fig. 340-B).

The alternative pentode circuit at B has the frequency-controlling elements, *C* and *R*, in the plate circuit. It is capable of operation at frequencies up to several hundred kilocycles, and affords greater control of wave form.

Operation of the squегging oscillator at C is based on the tendency of any oscillator with excessive feed-back to produce relatively low-frequency intermittent oscillations, controlled by the rate of charge and discharge of L_2 , C and R through the tube grid resistance, if the time constant of the combination is large compared to the normal period of oscillation.

The most versatile relaxation oscillator circuit of all, shown in Fig. 313, is known as the *multivibrator*. Two tubes are used with resistance coupling, the output of one tube being fed to the input circuit of the other. The frequency of the resulting oscillation is determined by the time constants (§ 2-6) of the resistance-capacity combinations. The principle of oscillation is that of alternately switching conduction from one tube to the other, with one grid at cut-off and the other at zero bias, so that continuous oscillation is maintained, the second tube being necessary to obtain the proper phase relationship (§ 3-3) for oscillation when the energy is fed back.

Although the multivibrator is a very unstable oscillator, its frequency can be controlled readily by a small signal of steady frequency introduced into the circuit. This phenomenon is called *locking* or *synchronization*. The output waveshape of the multivibrator is highly distorted, hence has high harmonic content (§ 2-7). A useful feature is that the multivibrator can be locked at its fundamental frequency by a frequency corresponding to one of its higher harmonics (the tenth harmonic is frequently used), and thus the circuit can be used as a *frequency divider*.

3-8 Cathode-Ray Tubes

Principles — The cathode-ray tube is a vacuum tube in which the electrons emitted from a hot cathode are first accelerated to give them considerable velocity, then formed into a beam, and finally allowed to strike a special translucent screen which *fluoresces*, or gives off light at the point where the beam strikes. A narrow beam of moving electrons is analogous to a wire carrying current (§ 2-4) and, as in the wire, is accompanied by electrostatic and electromagnetic fields. Hence the beam can be moved laterally, or deflected, by electric or

magnetic fields. Such fields exert a force on the beam in much the same way as on charged bodies or on wires carrying current (§ 2-3, 2-5).

Since the cathode-ray beam consists only of moving electrons, its weight and inertia are negligibly small. For this reason, it can be made to follow instantly the variations in periodically changing fields even at radio frequencies.

Electron gun — The electrode arrangement which forms the electrons into a beam is called the *electron gun*. In the simple tube structure shown in Fig. 314, the gun

consists of the cathode, grid, and anodes Nos. 1 and 2. The intensity of the electron beam is regulated by the grid in the same way as in an ordinary tube (§ 3-2). Anode No. 1 is operated at a positive potential with respect to the cathode, thus accelerating the electrons which pass through the grid, and is provided with

small apertures through which the electron stream passes. On emerging from the apertures the electrons are traveling in practically parallel straight-line paths. The electrostatic fields set up by the potentials on anode No. 1 and anode No. 2 form an *electron lens* system, comparable to an optical lens, which makes the electron paths converge to a point at the fluorescent screen in much the same way that a glass lens takes parallel rays of light and brings them to a point focus. Focusing of the electron beam is accomplished by varying the potentials on the anodes, the potential in turn determining the strength of the field. The potential on anode No. 2 is usually fixed, while that on anode No. 1 is varied to bring the beam into focus. Anode No. 1 is, therefore, called the *focusing electrode*.

Sharpest focus is obtained when the electrons of the beam have high velocity, so that relatively high d.c. potentials are common with cathode-ray tubes. However, the current required is small, so that the power consumption is negligible. A second grid may be placed between the control grid and anode No. 1, for additional acceleration of the electrons.

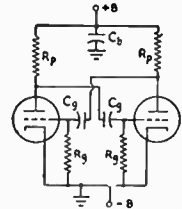


Fig. 313 — The multivibrator, or relaxation oscillator.

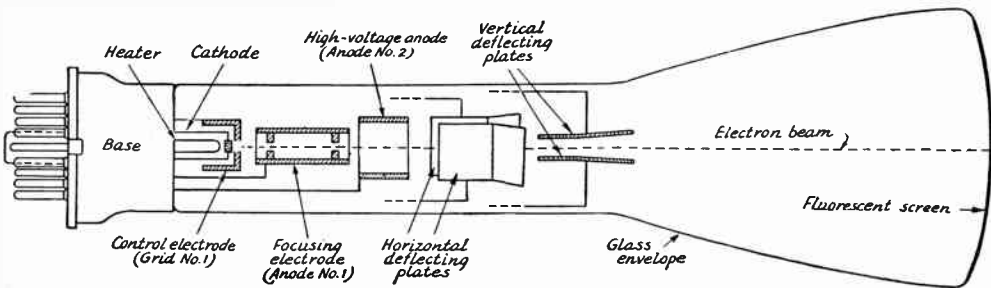


Fig. 314 — Typical construction for a modern cathode-ray tube of the electrostatic-deflection type. The envelope is made of glass, with the fluorescent screen at one end. Leads for the high-voltage anode, the deflection plates, and other electrodes are insulated low-capacity conductors carried inside the envelope to the base.

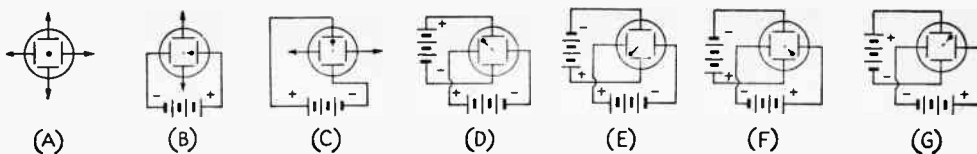


Fig. 345 — Spot diagrams showing the position of the cathode-ray beam on the fluorescent screen for different deflector potentials. A — Both deflectors at zero potential. B — Positive potential on right horizontal deflector. C — Positive potential on upper vertical deflector. D, E, F, G — Equal positive potentials on adjacent plates.

Methods of deflection — When focused, the beam from the gun produces only a small spot on the screen, as described above. However, if after leaving the gun the beam is deflected by either magnetic or electrostatic fields, the spot will move across the screen in accordance with the force exerted on the beam. If the motion is rapid, the path of the spot (*trace*) appears as a continuous line.

Electrostatic deflection, the type generally used in the smaller tubes, is produced by *deflecting plates*. Two sets of plates are placed at right angles to each other, as indicated in Fig. 344. The fields are created by applying suitable voltages between the two plates of each pair. Usually one plate of each pair is connected to anode No. 2, to establish the polarities (§ 2-3) of the vertical and horizontal fields with respect to the beam and to each other.

Tubes for magnetic deflection use the same type of electron gun, but have no deflection plates. Instead, the deflecting fields are set up by means of coils corresponding to the plates used in tubes having electrostatic deflection. The coils are external to the tube, as shown in Fig. 346, but are mounted close to the glass envelope in the relative positions occupied by electrostatic deflection plates. Coils A_1 and A_2 are connected so their fields aid and their axes are on the same line through the tube. Coils B_1 and B_2 likewise are connected with fields aiding and are aligned along the same axis through the tube, but perpendicularly to the A_1A_2 axis.

Fluorescent screens — The fluorescent screen materials used have varying characteristics, according to the type of work for which the tube is intended. The spot color is green, white, yellow or blue, depending upon the screen material. The *persistence* of the screen is the time duration of the after-glow which exists when the excitation of the electron beam is removed. Screens are classified as long-

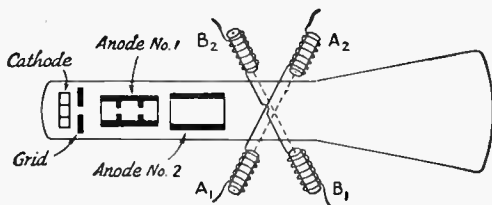


Fig. 346 — A cathode-ray tube with magnetic deflection. The gun is the same as in the electrostatic-deflection tube shown in Fig. 344, but the beam is deflected by magnetic instead of electric fields. Actual deflection coils fit closely to the neck of the tube, so that the field will be as strong as possible for a given coil current.

medium- and short-persistence types. Small tubes for oscilloscope use usually have medium-persistence screens of greenish fluorescence.

Tube circuits — A representative cathode-ray tube circuit with electrostatic deflection is shown in Fig. 347. One plate of each pair of deflecting plates is connected to anode No. 2. Since the voltages required normally are rather high, the positive terminal of the supply is usually grounded (§ 2-13) so that the common deflection plates will be at ground potential. This places the cathode and other elements at high potentials above ground, hence these elements must be well insulated. The various electrode voltages are obtained from a voltage divider (§ 2-6) across the high-voltage d.c. supply. R_3 is a variable divider or "potentiometer" for adjusting the negative bias on the control grid and thereby varying the beam current; it is called the *intensity* or *brightness* control. The *focus*, or sharpness of the luminous spot formed on the screen by the beam, is controlled by R_2 , which changes the ratio of the anode No. 2 and anode No. 1 voltages. The focusing and intensity controls interlock to some extent, and the sharpest focus is obtained by keeping the beam current low.

Deflecting voltages for the plates are applied to the terminals marked "vertical" and "horizontal." R_4 and R_5 drain off any accumulation of charge on the deflecting plates. Usually some provision is made to place an adjustable d.c. voltage on each set of plates, so that the spot can be "centered" when stray electrostatic or magnetic fields are present; the adjustable d.c. voltage neutralizes the effect of such fields.

The tube is mounted so that one set of plates produces a horizontal line when a varying voltage is applied to it, while the other set of plates produces a vertical line under similar conditions. They are called, respectively, the "horizontal" and "vertical" plates, but which set of actual plates produces which line is simply a matter of how the tube is mounted. It is usually necessary to provide a mounting which can be rotated to some extent, so that the lines will actually be horizontal and vertical.

Power supply — The d.c. voltage required for operation of the tube may vary from 500 volts for the miniature type (1-inch diameter screen) to several thousand volts for the larger tubes. The current, however, is very small, so that the power required likewise is small. Because of the low current drain, a power supply with half-wave rectification (§ 8-3) and a single 0.5- to 2- μ fd. filter condenser is satisfactory.

3-9 The Oscilloscope

Description — An oscilloscope is essentially a cathode-ray tube in the basic circuit of Fig. 347, but with provision for supplying a suitable deflection voltage on one set of plates (ordinarily those giving horizontal deflection). The deflection voltage is the *time base* or *sweep*. Oscilloscopes frequently are also equipped with vacuum-tube amplifiers for increasing the amplitude of small a.c. voltages to values suitable for application to the deflecting plates. These amplifiers ordinarily are limited to operation in the audio- or video-frequency range.

Formation of patterns — When periodically varying voltages are applied to the two sets of deflecting plates, the path traced by the fluorescent spot forms a *pattern* which is stationary so long as the amplitude and phase relationships of the voltages remain unchanged. Fig. 348 shows how such patterns are formed. The horizontal sweep voltage is assumed to have the "sawtooth" waveshape indicated; with no voltage applied to the vertical plates the trace simply sweeps from left to right across the screen along the horizontal axis $X-X'$ until the instant H is reached, when it reverses direction and returns to the starting point. The sine-wave voltage applied to the vertical plates similarly would trace a line along the axis $Y-Y'$ in the absence of any deflecting voltage on the horizontal plates. However, when both voltages are present the position of the spot at any instant depends upon the voltages on both sets of plates at that instant. Thus at time B the horizontal voltage has moved the spot a short distance to the right and the vertical voltage has similarly moved it upward, so that it reaches the actual position B' on the screen. The resulting trace is easily followed from the other indicated positions, which are taken at equal time intervals.

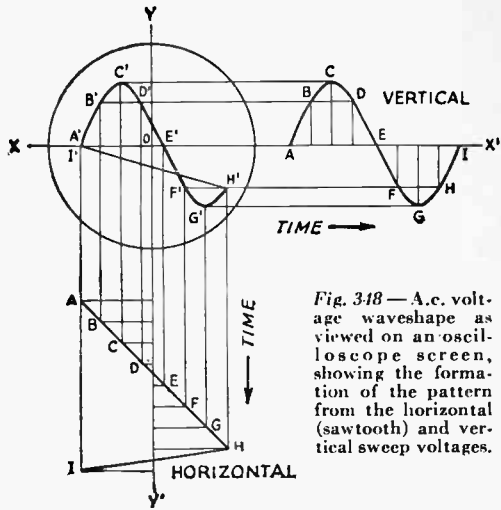


Fig. 348 — A.c. voltage waveshape as viewed on an oscilloscope screen, showing the formation of the pattern from the horizontal (sawtooth) and vertical sweep voltages.

Types of sweeps — A sawtooth sweep-voltage waveshape, such as is shown in Figs. 348 and 350 is called a *linear sweep*, because the deflection in the horizontal direction is directly proportional to the time. If the sweep were perfect the "fly-back" time, or time taken for the spot to return from the end (II) to the beginning (I or A) of the horizontal trace, would be zero, so that the line III would be perpendicular to the axis $Y-Y'$. Although the fly-back time cannot be made zero in practicable sweep-voltage generators it can be made quite small in comparison to the time of the desired trace AI , at least at most frequencies within the audio range. The fly-back time is somewhat exaggerated in Fig. 345, to show its effect on the pattern. The line $H'I'$ is called the *return trace*; with a linear sweep it is less brilliant than the pattern, because the spot is moving much more rapidly during the fly-back time than during the time of the main trace. If the fly-back time is short enough, the return trace will be invisible.

The linear sweep has the advantage that it shows the shape of the wave applied to the vertical plates in the same way in which it is usually represented graphically (§ 2-7). If the time of one cycle of the a.c. voltage applied to the vertical plates is a fraction of the time taken to sweep horizontally across the screen, several cycles of the vertical or signal voltage will appear in the pattern. The shape of only the last cycle (or the last few cycles, depending upon the number in the pattern and the characteristics of the sweep) to appear will be affected by the fly-back in such a case.

Although the linear sweep generally is most useful, other sweep waveshapes may be desirable for certain purposes. The shape of the pattern obtained, with a given signal waveshape on the vertical plates, obviously will depend upon the shape of the horizontal sweep voltage. If the horizontal sweep is sinusoidal, the main and return sweeps each occupy the same time and the spot moves faster horizontally in the

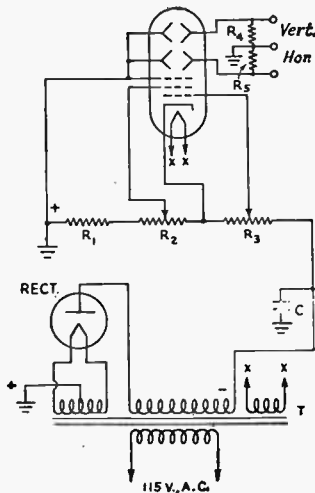


Fig. 347 — Cathode-ray tube circuit. Typical values for a 3-inch (screen-diameter) tube such as the 3AP1/906: R_4, R_5 — 1 to 10 megohms. R_2 — 0.2 megohm. R_3 — 20,000 ohms. R_1 — 0.5 megohm.

center of the pattern than it does at the ends. If two sinusoidal voltages of the same frequency are applied simultaneously to both sets of plates, the resulting pattern may be a straight line, an ellipse or a circle, depending upon the

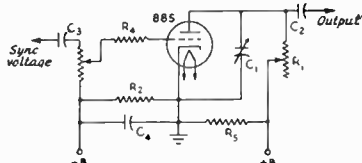


Fig. 349 - A linear-sweep oscillator using a gas triode.
 C_1 - 0.001 to 0.25 μ f.
 C_2 - 0.5 μ f.
 R_1 - 0.3 to 1.5 megohms.
 R_2 - 2000 ohms.
 R_3 - 0.25 megohm.
 The "B" supply should deliver 300 volts. C_1 and R_1 are proportioned to give a suitable sweep frequency; the higher the time constant (§ 2-6), the lower the frequency. R_4 limits grid-current flow during the deionizing period, when positive ions are attracted to the negative grid.

amplitude and phase relationships. If the frequencies are harmonically related (§ 2-7) a stationary pattern will result, but if one frequency is not an exact harmonic of the other the pattern will show continuous motion. This is also the case when a linear sweep circuit is used; the sweep frequency and the frequency under observation must be harmonically related or the pattern will not be stationary.

The sweep generator does not ordinarily function as a self-controlled oscillator but rather as an externally controlled or synchronized oscillator which supplies voltage of the required waveform at the same frequency as the signal under study, or a sub-multiple thereof.

Sweep circuits - A sinusoidal sweep is easiest to obtain, since it is possible to apply a.c. voltage from the power line, either directly or through a suitable transformer, to the horizontal plates. A variable voltage divider or potentiometer may be used to regulate the width of the horizontal trace.

A typical circuit for a linear sweep generator is shown in Fig. 349. The tube is a *gas triode* or grid-control rectifier (§ 3-6-C). The *striking* or breakdown voltage, which is the plate voltage at which the tube ionizes or *fires* and starts conducting, is determined by the grid bias.

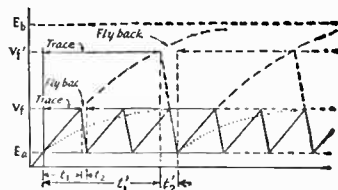


Fig. 350 - Condenser charging curves showing how a sawtooth wave is produced by a gaseous-tube linear sweep oscillator.

When plate voltage, E_b , is applied, the condenser, C_1 , acquires a charge through R_1 . As shown in Fig. 350, the charging voltage rises relatively slowly, as shown by the solid line, until the breakdown or flashing point, V_f , is


reached. Then the condenser discharges rapidly through the comparatively low plate-cathode resistance of the tube. When the voltage drops to a value too low to maintain plate-current flow, E_b , the ionization is extinguished and C_1 once more charges through R_1 . If R_1 is large enough, the voltage across C_1 rises linearly with time, t_1 , up to the breakdown point. This linear voltage change is used for the sweep, being applied to the cathode-ray tube plates through C_2 . The fly-back time, t_2 , is the time required for discharge through the tube; to keep this time small, the resistance during discharge must be low.

To obtain a stationary pattern, the "sawtooth" rate is controlled by varying C_1 and R_1 and synchronized by introducing some of the voltage being observed on the vertical plates into the grid circuit of the 884 tube. This voltage "triggers" the tube into operation in synchronism with the signal frequency. Synchronization will occur so long as the signal frequency is nearly the same as, or a multiple of, the sweep frequency, provided the circuit constants and the amplitude of the synchronizing voltage are properly adjusted.

The upper frequency limit of gaseous-tube sweep oscillators is in the vicinity of 50,000 cycles, even with the most careful design, because of the fly-back time limitations imposed by the gaseous content of the tube.

Fig. 351 - Pentode-tube high-speed sweep generator.
 C - 0.001 to 0.1 μ f.

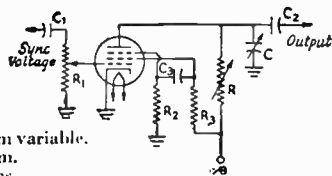- C_1, C_2 - 0.1 μ f.
- C_3 - 1.0 μ f.
- R - 25,000 ohms to 5 megohms.
- R_1 - 0.5 megohm variable.
- R_2 - 0.1 megohm.
- R_3 - 25,000 ohms.



To attain a higher-frequency sweep, a "hard"-tube oscillator such as that shown in Fig. 351 must be used. This circuit may be recognized as being similar to that of the pentode relaxation oscillator of Fig. 342-B. With suitable constants it is capable of an upper frequency limit of 100 to 200 kc. or more. If a tube is used which has a high ratio of plate current to screen current, the screen voltage will rise to a very high value during the plate discharge and thus aid in reducing the fly-back time.

A variety of waveshapes may be obtained from this circuit, ranging from the sawtooth or triangular waves which occur at the plate to the rectangular waveform of the screen-grid voltage. The plate-circuit waveforms are those most often employed for oscilloscope work.

The sweep rate is controlled by R and C , but it is influenced also by the value of R_2, R_3 determines the output waveshape by regulating the ratio of charge to discharge time, thus determining the part of the cycle occupied by the rectangular-shaped screen-voltage wave.

The *blocking-tube oscillator* in Fig. 352 is also capable of high-frequency operation,

chiefly because the oscillator portion generates a very short, sharp pulse which charges C almost instantaneously. Because of its superiority in this respect, this circuit has received considerable application in television work. Its operation is distinguished from that of the squegging oscillator (Fig. 342-C) in that the intermittent high-frequency oscillations are almost instantly blocked as the bias built up by the grid-leak and condenser, C and R , goes far beyond cut-off. With suitable constants, the build-up time for this blocking bias can be limited to a single high-frequency cycle, resulting in a very short, abrupt pulse of plate current (I_p). Because of the large time constant of C and R , the discharge time is very much slower. Until the charge again leaks off through R , the circuit is paralyzed. When C is discharged, the cycle repeats.

I_1 and I_2 are tightly coupled and designed to be self-resonant at perhaps ten times the maximum sweep frequency.

In the practical form, shown in Fig. 352, the blocking oscillator itself is the left-hand section of the dual triode. The second triode section is used as a discharge tube, the rate of discharge being controlled by the C_2R_1 combination. By giving this combination the proper time constant, the output wave can be made to have almost any desired form. R exercises limited control over the frequency range, while the value of R_1 determines the output amplitude.

Vacuum-tube switching circuits — In contrast to time-base circuits which deliver recurrent output impulses, certain applications in oscilloscope and other electronic work call for what are termed *vacuum-tube* or *electronic* switching circuits.

A *keying* circuit is a non-locking electronic switch which closes (or opens) a circuit when a control voltage is applied and returns the circuit to normal when the control voltage is removed. The keying voltage is usually applied as control-grid bias, although screen- and suppressor-grid voltage also are employed.

A *trigger circuit*, also called a *flip-flop* circuit, may also be operated in this manner, but more strictly it is a type of locking or holding electronic switch, wherein a second impulse is required to restore the circuit. After the

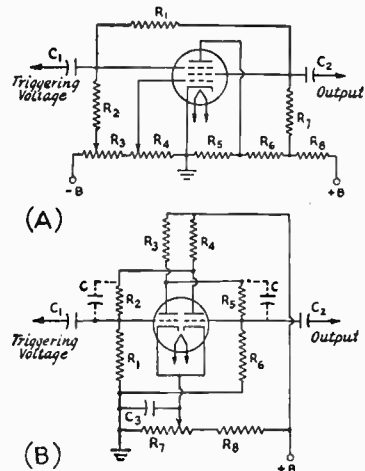


Fig. 353 — Typical vacuum-tube trigger circuits.

initiating control pulse the circuit remains closed, despite removal of the control voltage, until a second releasing impulse is received. Circuits in which values of current or voltage change abruptly from one stable condition to another at some critical value of voltage or resistance, and then change back abruptly at a different critical value of the controlling voltage or resistance, are used for this purpose.

Fig. 353-A shows the basic pentode form of trigger circuit. In this circuit d.c. coupling between the screen and suppressor grids causes the suppressor voltage to change with screen voltage. With a high value of resistance in series with the screen, abrupt changes in these currents occur when the supply voltages or the screen-circuit resistance are varied. For example, by proper choice of voltage and circuit constants the plate current corresponding to a given value of screen current may be made zero. Triggering impulses may be introduced in series with any of the electrodes, but the control grid is the most sensitive. The values of the supply voltages are not critical, but the proper relation must be maintained between them.

In the two-tube trigger circuit of Fig. 353-B, a positive impulse applied to the grid of the first tube will increase its plate current. This causes an increased voltage drop across R_3 , which in turn makes the bias on the second tube more negative. Consequently the plate current of the second tube decreases, decreasing the voltage drop across R_4 . This makes the grid bias on the first tube more positive, causing a further increase in the plate current of this tube and a resultant further decrease in the plate current of the second tube. The process continues until the second tube is cut off, when only the first tube takes current. This condition will continue until a negative pulse is applied to the first grid, or a positive pulse to the second grid, when the action will be reversed. The initial operating point is established by the variable tap on the cathode resistor, R_7 .

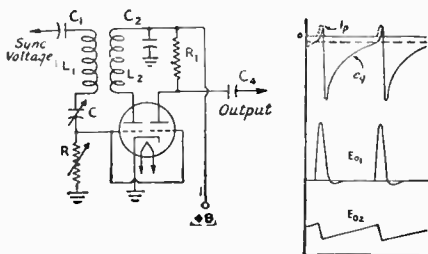


Fig. 352 — Dual-triode blocking-tube oscillator and discharge tube, with characteristic waveforms at the right.

C — 0.001–0.01- μ fd. mica. R — 0.25 megohm variable.
 C_1, C_3 — 0.005–0.5 μ fd. R_1 — 0.1–2 megohm.
 C_2 — 0.1 μ fd. L_1, L_2 — See text.

3-10 Pulse Technique

In pulse transmission and reception (§ 1-4), specialized means are employed to generate and shape characteristic pulses on the transmitting end and to recreate and interpret these pulses on the receiving end. One is a process of waveshaping and injection; the other of separation and selection. Certain basic circuit elements are common to both; elementary examples of such circuits will be discussed in this section.

Waveshaping — The primary waveforms employed in pulse transmission, apart from the basic sine wave, are the rectangular wave (from narrow pulse to square wave), trapezoidal wave, triangular wave (from isosceles to right-angle sawtooth), exponential and sawtooth waves.

The nonsinusoidal waveforms obtainable from certain oscillators, particularly those of the relaxation type, approximate the general shapes required. To trim such waves to the ideal form required, auxiliary waveshaping cir-

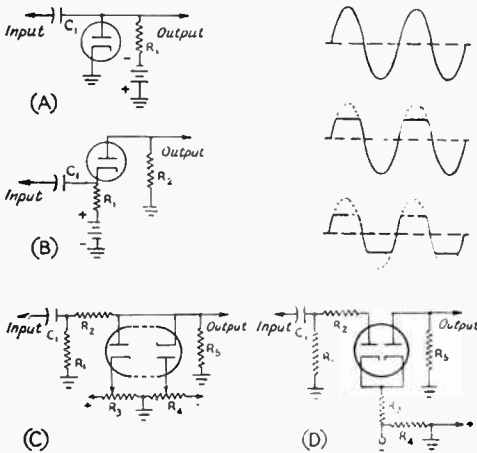


Fig. 351 — Shaping of sine wave to square wave by diode clipping action. The waveforms at the upper right illustrate, progressively, the sinusoidal input wave, the positive peak clipped by the diode parallel limiter (A), and the negative peak clipped by the diode series limiter (B). These are performed jointly in the double-diode parallel limiter (C) and double-diode series limiter (D).

cuits are employed. The basic categories are (1) limiter circuits, which utilize the voltage-limiting action of vacuum tubes, and (2) peaking circuits, which employ RC (or LC) time-constant circuits.

Fig. 354 shows the use of biased-diode limiters in clipping a sine wave to create a square or trapezoidal waveshape by limiting action.

The diode parallel limiter at A does not limit the output until the input voltage attains a value more positive than that of the negative biasing voltage applied in series

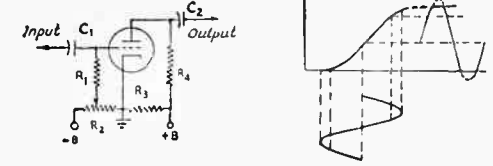


Fig. 355 — Triode limiter action in generating square or trapezoidal wave by clipping peaks of a sinusoidal wave.

with R_1 . In the diode series limiter at B, conduction can occur only when the input is more positive than the biasing voltage inserted in series with R_1 . Thus there can be no increase in output during the most negative period of the cycle. The series limiter produces a more squarely clipped wave than the parallel type. The operation of either type can be reversed by reversing the diode connections and the polarity of the biasing voltage.

In the double-diode parallel limiter at C, the left-hand diode removes positive peaks while that at the right clips the negative. The degree of limiting is adjusted by varying the fixed bias by means of R_3 and R_4 . The double series limiter at D functions in a similar manner but is more critical of adjustment.

Triode limiters may be operated at cut-off or at saturation. In Fig. 355, the tube is biased near the center of its characteristic. When the signal voltage goes negative, at cut-off plate current ceases to flow and the bottom of the sine wave is clipped. On the positive peak the plate current is limited by saturation and the top of the sine curve is squared off. The input signal should be 20 or 30 times the grid bias for the sine wave to be squared off sharply.

Limiter circuits may also be employed for generating other types of pulses. If the tube in Fig. 355 is biased beyond cut-off and a condenser is connected between plate and ground, a positive rectangular pulse applied to the grid will produce a sawtooth wave. During the interval between pulses the condenser is charged in a relatively slow linear rate through R_4 . The sharp front of the positive pulse on the grid causes plate current to flow, and the condenser discharges rapidly through the tube. A triangular waveshape can be obtained by reducing the bias to zero and applying negative pulses to the grid. Between pulses plate current

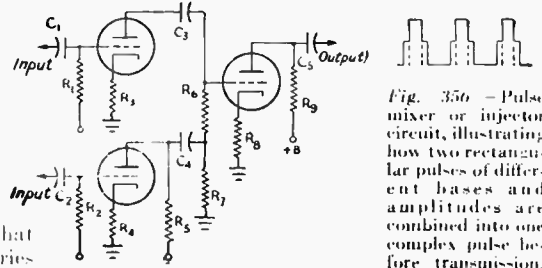


Fig. 356 — Pulse mixer or injector circuit, illustrating how two rectangular pulses of different bases and amplitudes are combined into one complex pulse before transmission.

will flow, but each negative pulse biases the tube beyond cut-off, making it nonconducting. The condenser charges through R_4 for the duration of the pulse, then discharges through R_4 . The result is a symmetrical triangular pulse.

Pulse selection — Pulse selectivity is based on the following characteristics: (1) polarity; (2) amplitude; (3) shape; and (4) duration (including both "mark" and "space" intervals).

The diode separator functions much like the diode limiters of Fig. 354, except that the action is reversed. Selection by polarity is based on the unilateral conductivity of the diode rectifier, and requires only that the diode be so con-

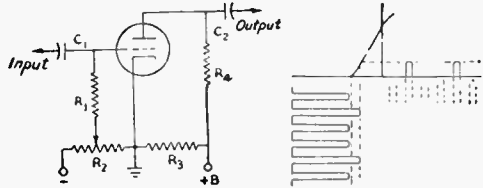


Fig. 357 — Cut-off biased triode amplitude separator. C_1 — 0.1 μ fd. R_1 — 1 megohm. R_3 — 50,000 ohms. C_2 — 0.5 μ fd. R_2 — 2000 ohms. R_4 — 25,000 ohms.

nected as to pass positive or negative pulses, as desired. For amplitude separation the diode is so biased that only pulses having an amplitude exceeding the bias voltage will be passed.

The same resemblance applies in the case of triode amplitude separators. In the cut-off separator of Fig. 357, the grid normally is biased beyond cut-off. When a positive voltage of sufficient amplitude is applied, plate current flows. There will be no response to voltages of lesser amplitude, or to negative pulses.

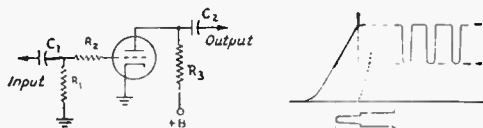


Fig. 358 — Zero-bias or positive-grid limiter separator. C_1 — 0.1 μ fd. C_2 — 0.5 μ fd. R_1, R_2 — 1 megohm. R_3 — 0.1 megohm.

The positive-grid or blocked-grid separator, Fig. 358, operates at saturation and is characterized by a series resistor in the grid circuit. Positive pulses drive the tube into the positive-grid region, where grid-current flow increases bias and limits plate-current to a steady value regardless of signal level. Since this circuit passes only negative pulses, it is selective as to polarity.

Differentiation and integration — If the front of a rectangular wave is applied to an RC circuit with series capacity and shunt resistance, as in Fig. 359, the voltage across the load resistor will equal the applied voltage at the instant of application. Then, as the condenser acquires charge the voltage across the resistor will decrease exponentially (§ 2-6). If the time

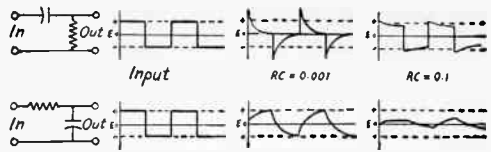


Fig. 359 — With square wave input, the voltage wave-shapes across R and C respectively in an RC circuit have the shapes shown. Note the variation in waveshapes for different time constants. (Time constant values given are in terms of fractions of the period of the input wave.)

constant of the circuit is very small, the charging period will be very short. Thus the voltage across the resistor will have the shape of a short pulse, sharply peaked at the front.

Following this initial pulse, no current flows through the resistor because the condenser is charged to the maximum voltage of the applied square wave. Hence the voltage across the resistor is zero so long as the input voltage is unchanging. At the trailing edge of the input wave the process is repeated, except that the resultant pulse has the opposite polarity since the condenser is now discharging.

By altering the steepness of either the ascending or descending slopes of the input wave the amplitude of the output pulse can be controlled. This is the principle upon which pulse selection by waveshape is based, as illustrated in Fig. 360. A steep front produces a sharp pulse having an amplitude equal to the applied voltage, while a sloping front produces a pulse of correspondingly greater length and lesser amplitude. For sharp pulses the time constant must be considerably shorter than one-half cycle of the input wave. With a longer time constant the charging period becomes correspondingly longer, while retaining a logarithmic shape, and approaches the duration and form of the wave. Such a network is called a *differentiating circuit*.

In a circuit with the resistor in series and the condenser in shunt, also shown in Fig. 359, the action is such that with a very short time constant the output wave resembles that of the input except for a slight curvature at the beginning because of the exponential charging characteristic. The amplitude is, however, greatly reduced because of the voltage divider effect of the reactance-resistance combination. Increasing the time constant to a value comparable to the duration of the constant-amplitude portion of the input wave increases the amplitude but accentuates also both the ascending and descending slopes of the wave.

Increasing the time constant to a value very long compared with the base of the input wave, results in what is called an *integrating circuit*. In this circuit discrimination or selection is

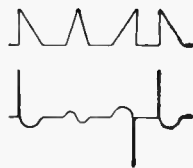


Fig. 360 — Pulse selection based on the discriminating action of a differentiating circuit with inputs of different wavefront shapes. Typical input waves are shown above and the resulting output pulses below.

based on the duration or frequency of the input wave. For example, if a series of short pulses is applied, the energy stored in the condenser by each individual pulse will be small and will be discharged before the next pulse arrives. If, however, a series of pulses with longer bases and shorter intervals is applied, only a portion of the energy from

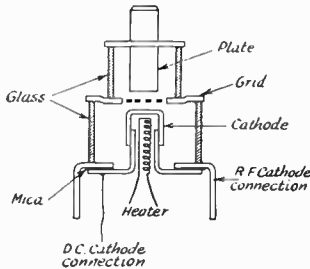


Fig. 361—Sectional view of the "lighthouse" tube's construction. Close electrode spacing reduces transit time while the disc electrode connections reduce lead inductance.

each pulse will be discharged before the next begins charging. Energy is therefore accumulated on the condenser until a predetermined amplitude is established. Thus long-base pulses can be separated from shorter pulses.

3-11 V.H.F. and U.H.F. Tubes

Negative-grid tubes—At very high frequencies, interelectrode capacities and the inductance of internal leads determine the highest possible frequency to which a vacuum tube can be tuned. The tube usually will not oscillate up to this limit, however, because of dielectric losses, grid emission, and "transit-time" effects. In low-frequency operation, the actual time of flight of electrons between the cathode and the anode is negligible in relation to the duration of the cycle. At 1000 kc., for example, transit time of 0.001 microsecond, which is typical of conventional tubes, is only 1/1000 cycle. But at 100 Mc., this same transit time represents 1/10 of a cycle, and a full cycle at 1000 Mc. These limiting factors establish about 3000 Mc. as the upper frequency limit for negative-grid tubes.

With tubes of ordinary construction, the upper limit of oscillation is about 150 Mc. For higher frequencies, v.h.f. tubes of special construction are used.

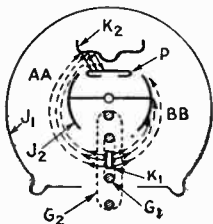


Fig. 362—Schematic cross-section of the orbital-beam secondary-electron multiplier tube.

Very low interelectrode capacities and lead inductance have been achieved in the newer tubes of modified construction. In multiple-

lead types the electrodes are provided with up to three separate leads which, when connected in parallel, have considerably reduced effective inductance. In double-lead types the plate and grid elements are supported by heavy single wires which run entirely through the envelope, providing terminals at either end of the bulb. When a resonant circuit is connected to each pair of leads, the shunting capacity divides between the two circuits. With linear circuits the leads become a part of the line and have distributed rather than lumped constants. Radiation loss is minimized and the effect of the transit time is reduced. In "lighthouse" tubes or *megatrons* the plate, grid and cathode are assembled in parallel planes, as shown in Fig. 361, instead of coaxially. The uniform coplanar electrode design and disc-seal terminals permit very low interelectrode capacities.

In the orbital-beam tube, Fig. 362, a small electrode structure is used in combination with a secondary-electron emitter to raise the effective transconductance. Electrons emitted from the cathode, K_1 , are accelerated through the control grid, G_1 , by a positive grid, G_2 , and

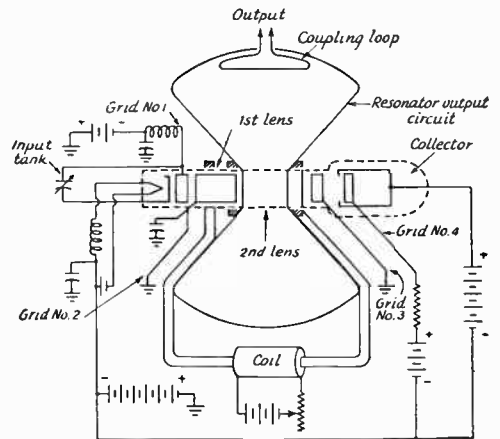


Fig. 363—Schematic of the inductive output amplifier.

enter a radial electrostatic field established by the cylindrical electrodes, J_1 and J_2 , causing the electrons to move in a circular path and driving them against the secondary-emitter electrode, K_2 . About ten secondary electrons are emitted for each primary electron; thus the ultimate electron flow to the plate, P , is considerably greater than the original current emitted. As a result, high over-all transconductance (15,000 at 500 Mc. in an experimental tube) is obtained without increasing transit-time losses or internal capacities.

Inductive output amplifier—In the inductive-output tube shown in Fig. 363 a high-velocity electron beam is intensity-modulated by the control grid (grid No. 1). After being accelerated and focused by the combined action of the first and second lenses in the magnetic circuit and the sleeve electrodes (grids

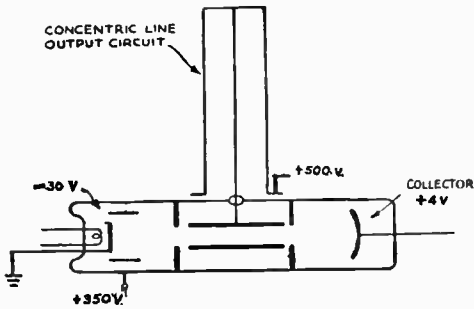


Fig. 364 — Simple form of cylindrical-grid velocity-modulated tube with retarding-field collector and coaxial-line output circuit, used as a superheterodyne high-frequency oscillator or as a superregenerative detector. Similar tubes can also be used as r.f. amplifiers and frequency converters in the 5-50-cm. region.

No. 2 and 3), the beam moves past a small aperture in the "dimpled sphere" cavity resonator. The potential difference across this gap slows down the electrons and thereby causes the resonant cavity to absorb power from the beam. Electrons passing through the structure are decelerated by a suppressor electrode (grid No. 4) before reaching the final anode or collector. The control-grid structure gives sharp cut-off and large transconductance, while the high accelerating potentials and small apertures result in very short transit time and consequently low input conductance. The inductive-output tube is useful for wide-band operation above 500 Mc., giving efficiencies of 25 per cent or better.

Velocity modulation — In negative-grid operation the potential on the grid tends to reduce the electron velocity during the more negative half of the oscillation cycle, while on the other half cycle the positive potential on the grid serves to accelerate them. Thus the electrons tend to separate into groups, those leaving the cathode during the negative half cycle being collectively slowed down, while those leaving on the positive half are accelerated. After passing into the grid-plate space only a part of the electron stream follows the original form of the oscillation cycle, the remainder traveling to the plate at differing velocities. Since these contribute nothing to the power output at the operating frequency, the efficiency is reduced in proportion to the variation in velocity, the output becoming zero when the transit time approaches a half cycle.

This effect, such a disadvantage in conventional tubes, is an advantage in velocity-modulated tubes in that the input signal voltage on the grid is used to change the velocity of the electrons in a constant-current electron beam, rather than to vary the intensity of a constant velocity current flow as in ordinary tubes.

A simple form of velocity-modulation oscillator tube is shown in Fig. 364. Electrons emitted from the cathode are accelerated through a negatively biased cylindrical grid by a constant positive voltage applied to a

sleeve electrode, shown in heavy lines. This electrode, which is the velocity-modulation control grid, consists of two hollow tubes, with a small space at each end between the inner tube, through which the electron beam passes, and the discs at the ends of the larger tube portion. With r.f. voltage applied across these gaps, which are small compared to the distance traveled by the electrons in one half cycle, electrons entering the tube will be accelerated on positive half cycles and decelerated on the negative half cycles. The length of the tube is made equal to the distance covered by the electrons in one-half cycle, so that the electrons will be further accelerated or decelerated as they leave the tube.

As the beam approaches the collector electrode, which is at nearly zero potential, the electrons are retarded, brought to rest, and ultimately turned back by the attraction of the positive sleeve electrode. The collector electrode is, therefore, also termed a *reflector*. The point at which electrons are returned depends on their velocity. Thus the velocity modulation is again translated into current modulation.

Velocity-modulated tubes operate satisfactorily up to 6000 Mc. (5 cm.) and higher, with outputs of 100 watts or more.

The klystron — In the *klystron* velocity-modulated tube, the electrons emitted by the cathode are accelerated or retarded during their passage through an electric field established by two grids in a cavity resonator, or *rhumbatron*, called the "buncher." The high-frequency electric field between the grids is parallel to the electron stream. This field accelerates the electrons at one moment and retards them at another, in accordance with the variations of the r.f. voltage applied.

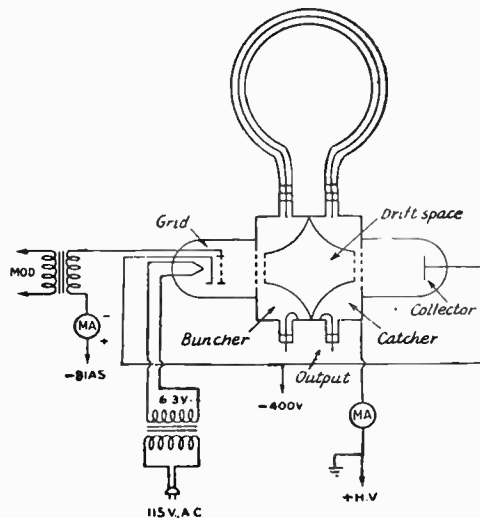


Fig. 365 — Circuit diagram of the klystron oscillator, showing the feed-back loop coupling the frequency-controlling rhumbatrons and the output loop in the catcher.

The resulting velocity-modulated beam travels through a field-free "drift space," where the slowly moving electrons are gradually overtaken by the faster ones. The electrons emerg-

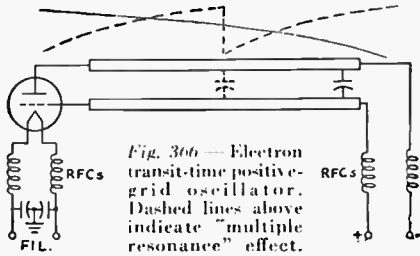


Fig. 366 — Electron transit-time positive-grid oscillator. Dashed lines above indicate "multiple resonance" effect.

ing from the pair of grids therefore are separated into groups or bunched along the direction of motion. The velocity-modulated electron stream is passed to a "catcher" rhumbatron. Again the beam passes through two parallel grids, the r.f. current created by the bunching of the electron beam induces an r.f. voltage between the grids. The catcher cavity is made resonant at the frequency of the velocity-modulated electron beam, so that an oscillating field is set up within it by the passage of the electron bunches through the grid aperture.

If a feed-back loop is provided between the two rhumbatrons, as shown in Fig. 365, oscillations will occur. The resonant frequency depends on the electrode voltages and on the shape of the cavities, and may be adjusted by varying the supply voltage and altering the dimensions of the rhumbatrons. The bunched beam current is rich in harmonics, but the output waveform is remarkably pure because the high *Q* of the catcher rhumbatron suppresses the unwanted harmonics.

Positive-grid electron oscillators — A triode in which the grid rather than the plate is positive with respect to the cathode will oscillate at frequencies higher than those at which transit-time effects cause the tube to be inoperative as a normal negative-grid oscillator. Oscillators of the positive-grid type are known as "brakefield" or "electron transit-time" oscillators. Successful performance is most readily achieved with tube structures having cylindrical grids and plates.

This type of operation makes use of the transit time of electrons from the cathode to the grid and plate regions. Electrons emitted by the cathode are accelerated toward the positive grid, some striking it and some passing through. Those that pass through are repelled by the negative plate and turn around, passing between the grid wires once more. In the process, the electrons induce a.c. voltages in the grid at a frequency depending upon the transit time. Some electrons may pass back and forth between the grid wires several times, while others may strike the grid after a single round trip. Those which remain free in the tube for several oscillations lose energy, but those which make only one trip gain energy. However, since

the former are free for a longer time there is a net transfer of energy which can be used to maintain oscillations.

In this type of oscillator, shown in Fig. 366, the frequency is controlled primarily by the grid voltage and the tube element spacing. The resonant circuit must be tuned to approximately the oscillation frequency for maximum output.

Positive-grid oscillators can be operated at frequencies up to 10,000 Mc. (3 cm.), but the efficiency is usually only 2 or 3 per cent. Since most of the power is dissipated in the grid, the tube is not capable of delivering much power.

Magnetrons — A magnetron is fundamentally a diode with cylindrical electrodes placed in a uniform magnetic field with the lines of electromagnetic force parallel to the elements. The simple cylindrical magnetron consists of a filamentary cathode surrounded by a concentric cylindrical anode. In the more efficient split-anode magnetron the cylinder is divided longitudinally.

Magnetron oscillators are operated in two different ways. Electrically the circuits are similar, the difference being in the relation between electron transit time and the frequency of oscillation.

In the negative-resistance or dynatron type of magnetron oscillator, the element dimensions and anode voltage are such that the transit time is short compared with the period of the oscillation frequency. Electrons emitted from the cathode are driven towards both halves of the anode. If the potentials of the two halves are unequal, the effect of the magnetic field is such that the majority of the electrons travel to that half of the anode which is at the lower potential. In other words, a decrease in the potential of either half of the anode results in an increase in the electron current flowing to that half. The magnetron consequently exhibits negative-resistance characteristics (§ 3-7). Negative-resistance magnetron oscillators are useful between 100 and 1000 Mc. Under the best operating conditions efficiencies of 20 to 25 per cent may be obtained. Since the power loss in the tube appears as heat in the anode, where it is readily dissipated, relatively large power-handling capacity can be obtained.

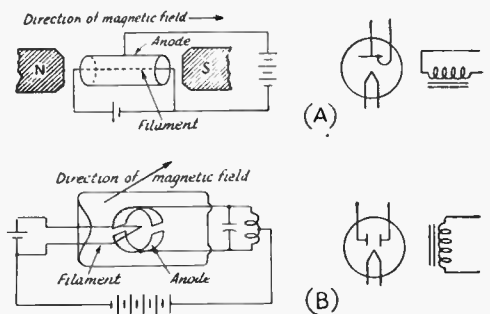


Fig. 367 — Conventional magnetrons, with equivalent schematic symbols at the right. A, simple cylindrical magnetron. B, split-anode negative-resistance magnetron.

In the transit-time magnetron the frequency is determined primarily by its dimensions and by the electric and magnetic field intensities rather than by the tuning of the tank circuits. The efficiency is much better than that of a positive-grid oscillator and good power output can be obtained even on the superhighs.

In a nonoscillating magnetron with a weak magnetic field, electrons traveling from the cathode to the anode move almost radially, their trajectories being bent only slightly by the magnetic field. With increased magnetic field the electrons tend to spiral around the filament, their radial component of velocity being much smaller than the angular component. Under critical conditions of magnetic field strength, a cloud of electrons rotates about the filament. It extends up to the anode but does not actually reach it.

The nature of these electron trajectories is shown in Fig. 368. Cases A, B, and C correspond to the non-oscillating condition. For a

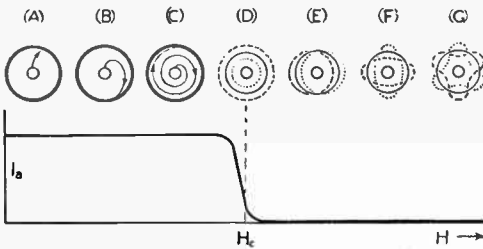


Fig. 368 — Electron trajectories for increasing values of magnetic field strength, H . Below is shown the corresponding curve of plate current, I_b . Oscillations commence when H reaches a critical value, H_c ; progressively higher order modes of oscillation occur beyond this point.

small magnetic field (A) the trajectory is bent slightly near the anode. This bending increases for a higher magnetic field (B) and the electron moves through quite a large angle near the anode before reaching it, signifying a large increase of space charge near the anode. For a strong magnetic field (C) electrons start radially from the cathode but are soon bent and curl about the filament in the form of a long spiral before reaching the anode. This means a very long transit time and a very large space charge in the whole region where the spiraling takes place. Under critical conditions (D), no current flows to the anode and no electron is able to move from cathode to anode, but a large space charge still exists between the cathode and anode. The spiraling becomes a set of concentric circles, and the entire space-charge distribution rotates about the filament.

Figs. 368-E, -F and -G depict higher order (harmonic-type) modes of operation in which the space charge oscillates not only symmetrically but in transverse directions contrasting to the vibrations of the fundamental.

In a transit-time magnetron oscillator the intensity of the magnetic field is adjusted so that, under static conditions, electrons leaving the cathode move in curved paths which just


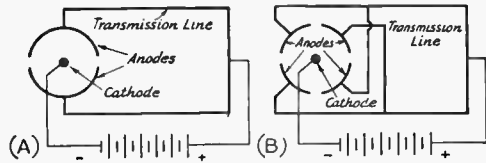
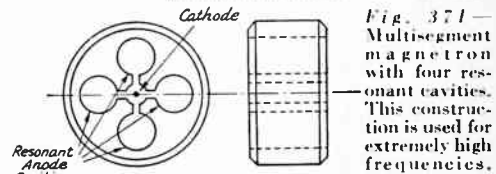


Fig. 369 — U.h.f. magnetron circuits, A, split-anode type, B, four-anode type with opposite electrodes paralleled.

fail to reach the anode. All electrons are therefore deflected back to the cathode, and the anode current is zero. When an alternating voltage is applied between the two halves of the anode, causing the potentials of these halves to vary about their average positive values, the conditions in the tube become analogous to those in a positive-grid oscillator. If the period of the alternating voltage is made equal to the time required for an electron to make one complete rotation in the magnetic field, the a.c. component of the anode voltage reverses direction twice with each electron rotation. Some electrons will lose energy to the electric field, with the result that they are unable to reach the cathode and continue to rotate about it. Meanwhile other electrons gain energy from the field and are returned to the cathode. Since those electrons which lose energy remain in the interelectrode space longer than those which gain energy, the net effect is a transfer of energy from the electrons to the electric field. This energy can be applied to sustain oscillations in a resonant transmission line connected between the two halves of the anode.

Split-anode magnetrons for u.h.f. are constructed with a cavity resonator built into the tube structure, as illustrated in Fig. 370. The assembly is a solid block of copper which assists in heat dissipation. At extremely high frequencies operation is improved by subdividing the anode structure into from 4 to 16 or more segments, the resonant cavities for each anode coupled by slots of critical dimensions to the common cathode region, as in Fig. 371.

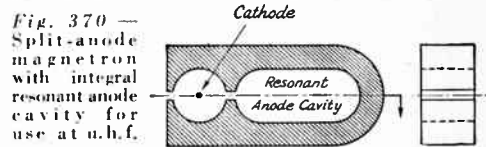

The efficiency of multi-segment magnetrons reaches 65 or 70 per cent. Slotted-anode magnetrons with four segments function up to 30,000 Mc. (1 cm.) delivering up to 100 watts at efficiencies greater than 50 per cent. Using larger multiples of anodes and higher-order modes, performance can be attained at 0.2 cm.

R.-F. Power Generation

4-1 Transmitter Requirements

General requirements — To minimize interference when a large number of stations must work in one frequency band, the power output of a transmitter must be as stable in frequency and as free from spurious radiations as the state of the art permits. The steady r.f. output, called the *carrier* (§ 5-1), must be free from amplitude variations attributable to ripple from the plate power supply (§ 8-4) or other causes, its frequency should be unaffected by variations in supply voltages or inadvertent changes in circuit constants, and there should be no radiation on other than the intended frequency. The degree to which these requirements can be met depends upon the operating frequency.

Design principles — The design of the transmitter depends on the output frequency, the required power output and the type of operation (c.w. telegraphy or 'phone). For c.w. operation at low power on medium-high frequencies (up to 7 Mc. or so), a simple crystal oscillator circuit can meet the requirements satisfactorily. However, the stable power output which can be taken from an oscillator is limited, so that for higher power the oscillator is used simply as a frequency-controlling element, the power being raised to the desired level by means of amplifiers. The requisite frequency stability can be obtained only when the oscillator is operated on relatively low frequencies, so that for output frequencies up to about 60 Mc. it is necessary to increase the oscillator frequency by multiplication (harmonic generation — § 3-3), which usually is done at fairly low power levels and before the final amplification. An amplifier which delivers power on the frequency applied to its grid circuit is known as a *straight amplifier*; one which gives harmonic output is known as a *frequency multiplier*. An amplifier used principally to isolate the frequency-controlling oscillator from the effects of changes in load or other variations in following amplifier stages is called a *buffer amplifier*. A complete transmitter therefore may consist of an oscillator followed by one or more buffer amplifiers, frequency multipliers and straight amplifiers, the number being determined by the output frequency and power in relation to the oscillator frequency and power. The last amplifier is called the *final amplifier*, and the stages up to the last comprise the *exciter*. Transmitters usually are designed to work in a number of frequency bands so that means for changing frequency in har-

monic steps usually is provided, generally by means of plug-in inductances.

The general method of designing a transmitter is to decide upon the power output and the highest output frequency required, and also the number of bands in which the transmitter is to operate. The latter usually will determine the oscillator frequency, since it is general practice to set the oscillator on the lowest frequency band to be used. The oscillator frequency seldom is higher than 7 Mc. except in some portable installations where tubes and power must be conserved. A suitable tube (or pair of tubes) should be selected for the final amplifier, and the required grid driving power determined from the tube manufacturer's data. This sets the power required from the preceding stage. From this point the same process is followed back to the oscillator, including frequency multiplication wherever necessary. The selection of a suitable tube complement requires a knowledge of the operating characteristics of the various types of amplifiers and oscillators. These are discussed in the following sections.

Above 100 Mc. and higher frequencies these methods of transmitter design tend to become rather cumbersome, because of the necessity for a large number of frequency multiplier stages. However, in this frequency region less severe stability requirements are imposed because the transmission range is limited (§ 9-5) and the possibility of interference to other communication is reduced. Simple oscillator transmitters, without frequency multiplication or buffer amplifiers, are widely used.

Vacuum tubes — The type of tube used in the transmitter has an important effect on the circuit design. Tubes of high power sensitivity (§ 3-3) such as pentodes and beam tetrodes give larger power amplification ratios per stage than do triodes, hence fewer tubes and stages may be used to obtain the same output power. On the other hand triodes have certain operating advantages, such as simpler power supply circuits and relatively simpler adjustment for modulation (§ 5-3), and in addition are considerably less expensive for the same power output rating. Consequently it is usually more economical to use triodes as output amplifiers, even though an extra low-power amplifier stage may be necessary.

At frequencies in the region of 50 Mc. and above it is necessary to select tubes designed particularly for operation at very-high frequencies, since tubes built primarily for lower frequencies may work poorly or not at all.


¶ 4-2 Self-Controlled Oscillators

Advantages and disadvantages — The chief advantage of a self-controlled oscillator is that the frequency of oscillation is determined by the constants of the tuned circuit, and hence readily can be set to any desired value. However, extreme care in design and adjustment are essential to secure satisfactory frequency stability (§ 3-7). Since frequency stability is generally poorer as the load on the oscillator is increased, the self-controlled oscillator should be used purely to control frequency and not for the purpose of obtaining appreciable power output in transmitters intended for working below 60 Mc.

Oscillator circuits — The inherent stability of all of the oscillator circuits described in § 3-7 is about the same, since stability is more a function of choice of proper circuit values and of adjustment than of the method by which feed-back is obtained. However, some circuits are more convenient to use than others, particularly from the standpoint of feed-back adjustment, mechanical considerations (whether the tuning condenser rotor plates can be grounded or not, etc.), and uniform output over a considerable frequency range. In all simple circuits the power output must be taken from the frequency-determining tank circuit, which means that, aside from the effect of loading on frequency stability, the following amplifier stage can react on the oscillator and cause a change in the frequency.

Factors influencing stability — The causes of frequency instability and the necessary remedial steps have been discussed in § 3-7. These apply to all oscillators. In the case of the electron-coupled oscillator the ratio of plate to screen voltage has marked effect on the stability with changes in supply voltage; the optimum ratio is generally of the order of 3:1, but should be determined experimentally for each case. Since the cathode is above ground potential, means should be taken to reduce the effects of heater-to-cathode capacitance or leakage which, by allowing a small a.c. voltage from the heater supply to develop between cathode and ground, may cause modulation (§ 5-1) at the supply frequency.


Fig. 401 — Electron-coupled oscillator circuit. R_1 should be 100,000 ohms or more, the grid condenser 100 μfd . and the other fixed condensers 0.002 to 0.1 μfd .

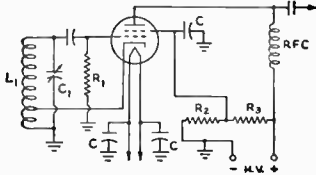

This effect, which is usually appreciable only at 14 Mc. and higher, may be reduced by by-passing the heater as in Fig. 401 or by operating the heater at the same r.f. potential as the cathode. The latter may be accomplished by the wiring arrangement shown in Fig. 402.

Tank-circuit Q — The most important single factor in determining frequency stability is the Q of the oscillator tank circuit. The effective Q must be as high as possible for best stability. Since oscillation is accompanied by grid-current flow the grid-cathode circuit

Fig. 402 — Method of operating the heater at cathode r.f. potential in an electron-coupled oscillator. L_2 should have the same number of turns as the cathode section of L_1 and should be closely coupled (preferably interwound). Condenser C may be 0.01 to 0.1 μfd .

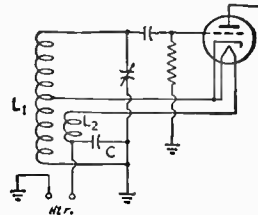

constitutes a resistance load of appreciable proportions, the effective resistance being low enough to be the determining factor in establishing the effective parallel impedance of the tank circuit. Consequently, if the ends of the tank are connected to plate and grid, as is usual, a high effective Q can be obtained only by decreasing the L/C ratio and making the inherent resistance in the tank as low as possible. The tank resistance can be decreased by using low-loss insulation and by winding the coil with large wire. With ordinary construction, the optimum tank capacity is of the order of 500 to 1000 μfd . at a frequency of 3.5 Mc.

The effective circuit Q can be raised by increasing the resistance of the grid circuit and thus decreasing the loading. This can be accomplished through reducing the oscillator grid current, which may be accomplished by using minimum feed-back for stable oscillation, plus a high value of grid-leak resistance.

A high- Q tank circuit can also be obtained with a higher L/C ratio by "tapping down" the tube connections on the tank (§ 2-10). This is advantageous in that a coil with higher inherent Q can be used; also, the circulating r.f. current in the tank circuit is reduced so that drift from coil heating is decreased. However, under some conditions parasitic oscillations may be set up (§ 4-10).

Plate supply — Since the oscillator frequency will be affected to some extent by changes in plate-supply voltage, it is necessary that the latter be free from ripple (§ 8-4) which would cause frequency variations at the ripple-frequency rate (*frequency modulation*). It is advantageous to use a voltage-stabilized power supply (§ 8-8). Since the oscillator usually is operated at low voltage and current, VR-type gaseous regulator tubes are quite suitable.

Power level — The self-controlled oscillator should be designed purely for frequency control and not to give appreciable power output, hence small tubes of the receiving type may be used. The power input ordinarily is not more than a watt or two, subsequent buffer amplifiers being used to increase the power to the desired level. The use of receiving tubes is advantageous mechanically, since the small elements are less susceptible to vibration and

usually are securely braced to the envelope of the tube.

Oscillator adjustment — The adjustment of an oscillator consists principally in observing the design principles outlined in the preceding paragraphs. Frequency stability should be checked with the aid of a stable receiver. An auxiliary crystal oscillator may be used as a standard for checking dynamic stability and drift, the self-controlled oscillator being adjusted to approximately the same frequency so that an audio-frequency beat (§ 2-13) can be obtained. If it is possible to vary the oscillator plate voltage (an adjustable resistor of 50,000 or 100,000 ohms in series with the plate supply lead will give considerable variation), the change in frequency with change in plate voltage may be observed and the operating conditions varied until minimum frequency shift results. The principal factors affecting dynamic stability will be the tank circuit L/C ratio, the grid-leak resistance, and the amount of feed-back. In the electron-coupled circuit the latter may be adjusted by changing the cathode tap on the tank coil; critical adjustment is required for optimum stability.

Drift may be checked by allowing the oscillator to operate continuously from a cold start, the frequency change being observed at regular intervals. Drift may be minimized by using less than the rated power input to the plate of the tube, by construction which prevents tube heat from reaching the tank circuit elements, and by use of large wire in the tank coil to reduce temperature rise from internal heating.

In the electron-coupled oscillator having a tuned plate circuit (Fig. 334), resonance at the fundamental and harmonic frequencies of the oscillator portion of the tube will be indicated by a decrease in plate current as the plate tank condenser is varied. This "dip" is less marked at the fundamental than on harmonics.

4-3 Crystal Control

Characteristics — Piezoelectric crystals (§ 2-12-D) are widely used for controlling the frequency of transmitting oscillators, because the extremely high Q of the crystal and the necessarily loose coupling between it and the

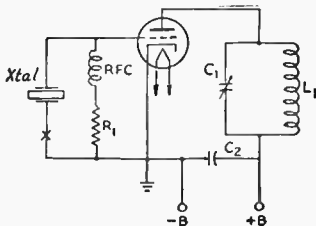


Fig. 403 — Triode crystal oscillator. The tank condenser, C_1 , may be a 100- μ fd. variable, with L_1 proportioned so that the tank will tune to the crystal frequency. C_2 should be 0.001 μ fd. or larger. The grid leak, R_1 , will vary with the type of tube; high- μ tubes take values of 2500 to 10,000 ohms, while medium and low- μ types take values of 10,000 to 25,000 ohms. A small flashlight bulb or r.f. milliammeter (§ 4-3) may be inserted at X.

oscillator tube make the frequency stability of a crystal-controlled oscillator very high.

The ability to adhere closely to a known frequency is the outstanding characteristic of a crystal oscillator. This also is a disadvantage, in that a different crystal is required for each frequency on which the transmitter is to operate.

Power limitations — The temperature of a crystal depends not only on the temperature of its surroundings but also on the power it must dissipate while oscillating, since power dissipation causes heating (§ 2-6, 2-8). Consequently, the crystal temperature in operation may be considerably above that of the surrounding air. To minimize heating and frequency drift (§ 3-7), the power dissipated must be kept to a minimum.

If the crystal is made to oscillate too strongly, as when it is used in an oscillator circuit with high plate voltage and excessive feed-back, the amplitude of the mechanical vibration will become great enough to crack or puncture the quartz. An indication of the vibration amplitude (and power dissipated) can be obtained by connecting an r.f. current-indicating device of suitable range in series with the crystal. Safe r.f. crystal currents range from 50 to 200 milliamperes, depending upon the type of crystal cut. A flashlight bulb or dial light of equivalent current rating makes a good current indicator. By choosing a bulb of lower rating than the current specified by the manufacturer as safe for the particular type of crystal used, the bulb will serve as a fuse, burning out before a current dangerous to the crystal is reached. The 60-ma. and 100-ma. bulbs may be used for this purpose.

Crystal mountings — To make use of the crystal, it must be mounted between two metal electrodes. There are two types of mountings, one having a small air-gap between the top plate and the crystal and the other maintaining both plates in contact with the crystal. It is essential that the surfaces of the metal plates in contact with the crystal be perfectly flat. In the air-gap type of holder, the frequency of oscillation depends to some extent upon the size of the gap. By using a holder having a top plate with closely adjustable spacing, a controllable frequency variation can be obtained. A suitable 3.5-Mc. crystal will oscillate without great variation in power output over a range of about 5 kc. X- and Y-cut crystals are not generally suitable for this type of operation; they have a tendency to "jump" in frequency with different air gaps.

A holder having a heavy metal bottom plate with a large surface exposed to the air is advantageous in that it radiates quickly the heat generated in the crystal, thereby reducing temperature effects. Different plate sizes, pressures, etc., will cause slight changes in frequency, so that if a crystal is being ground to an exact frequency it should be tested in the same holder and in the same oscillator circuit with which it will be used in the transmitter.

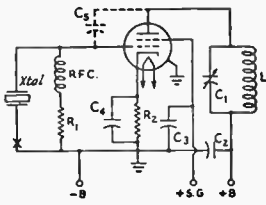


Fig. 404 — Tetrode or pentode crystal oscillator. Typical values: C_1 , 100 $\mu\text{fd.}$, with L wound to suit frequency; C_2 , C_3 , 0.001 $\mu\text{fd.}$ or larger; C_4 , 0.01 $\mu\text{fd.}$; R_1 , 10,000 to 50,000 ohms (value determined by trial); R_2 , 250 to 400 ohms.

4-4 Crystal Oscillators

Triode oscillators — The triode crystal oscillator circuit (§ 3-7) is shown in Fig. 403. The limit of plate voltage that can be used without endangering the crystal is about 250 volts. With the r.f. crystal current limited to a safe value of about 100 ma., the power output obtainable is about 5 watts. The oscillation frequency is dependent to some extent on the plate tank tuning, because of the change in input capacity with changes in effective amplification (§ 3-3).

Tetrode and pentode oscillators — Since the power output of a crystal oscillator is limited by the permissible r.f. crystal current (§ 4-3), it is advantageous to use an oscillator tube of high power sensitivity (§ 3-3) such as a pentode or beam tetrode (§ 3-5). Thus for a given crystal voltage or current more power output may be obtained than with the triode oscillator, or for a given output the crystal voltage will be lower, thereby reducing crystal heating. In addition, tank-circuit tuning and loading react less on the crystal frequency because of the lower grid-plate capacity (§ 3-3).

Fig. 404 shows a typical pentode or tetrode oscillator circuit. Pentode and tetrode tubes originally designed for audio power work are excellent crystal-oscillator tubes. The screen voltage is generally of the order of half the plate voltage for optimum operation. Small tubes rated at 250 volts for audio work may be operated with 300 volts on the plate and 100-125 on the screen as crystal oscillators. The screen is at ground potential for r.f. and has no part in the operation of the circuit other than to set the operating characteristics of the tube. The larger beam tubes may be operated at 400 to 500 volts on the plate and 250 on the screen for maximum output.

Pentode oscillators operating at 250 to 300 volts will give 4 or 5 watts output under normal conditions. Beam-type tubes such as the 6L6 and 807 will give 15 watts or more at maximum plate voltage.

The grid-plate capacity may be too low to give sufficient feed-back, particularly at the lower frequencies, in which case a feed-back condenser, C_5 , may be required. Its capacity should be the lowest value which will give stable oscillation; 1 or 2 $\mu\text{fd.}$ is generally sufficient. R_2 and C_4 may be omitted, connecting the cathode directly to ground, if plate voltage is limited to 250 volts. C_5 (if needed) may be formed by two metal plates $\frac{1}{2}$ -inch square spaced $\frac{1}{4}$ inch. If the tube has a suppressor

grid, it should be grounded. X indicates where a flashlight bulb may be inserted (§ 4-3).

Circuit constants — Typical values for grid-leak resistances and by-pass condensers are given in Figs. 403 and 404. Since the crystal is the frequency-determining element, the Q of the plate tank circuit has a relatively minor effect on the oscillator frequency. A Q of 12 (§ 4-8) is satisfactory for average conditions, but some departure from this figure will not greatly affect the performance of the oscillator.

Adjustment of crystal oscillators — The tuning characteristics and procedure to be followed in tuning are essentially the same for triode, tetrode or pentode crystal oscillators. Using a plate milliammeter as an indicator of oscillation (a 0-100 ma. d.c. meter will have ample range for all low-power oscillators), the plate current will be found to be steady when the circuit is in the non-oscillating state, but will dip when the plate condenser is tuned through resonance at the crystal frequency. Fig. 405 is typical of the behavior of plate current as the tank condenser capacity is varied. An r.f. indicator, such as a small neon bulb touched to the plate end of the tank coil, will show a maximum indication at point A. However, when the oscillator is delivering power to a load it is best to operate in the region B-C since the oscillator will be more stable and there is less likelihood that a slight change in loading will throw the circuit out of oscillation, which is likely to happen when operation is too near the critical point, A. The crystal current also is lower in the B-C region.

When power is taken from the oscillator the dip in plate current is less pronounced, as indicated by the dotted curve. The greater the power output, the smaller the dip in plate current. If the load is made too great, oscillations will not start. Loading is adjusted by varying the coupling to the load circuit (§ 2-11).

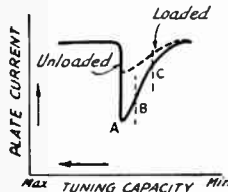


Fig. 405 — Curves showing d.c. plate current vs. plate-circuit tuning in a crystal oscillator, both with and without load. These curves apply equally to the triode, tetrode or pentode crystal oscillator.

The greater the loading, the smaller the voltage fed back to the grid circuit for excitation purposes. This means that the r.f. voltage across the crystal also will be reduced under load, hence there is less crystal heating when the oscillator is delivering power than when it is unloaded.

Failure of a crystal circuit to oscillate may be caused by any of the following:

- 1) Dirty, chipped or fractured crystal.
- 2) Imperfect or unclean holder surfaces.
- 3) Too tight coupling to load.
- 4) Plate tank circuit not tuning correctly.
- 5) Insufficient feed-back capacity.

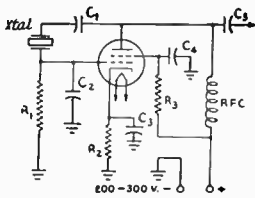


Fig. 406 — Pierce oscillator circuit. R_1 is 25,000 to 50,000 ohms. R_2 is 1000 ohms; R_3 , 75,000 ohms for a 6F6; C_1 , 0.001 to 0.01 $\mu\text{fd.}$; C_3 and C_4 , 0.01 $\mu\text{fd.}$ For values of C_2 and C_5 , see text.

Pierce oscillator — This circuit, Fig. 406, is equivalent to the ultraudion circuit (§3-7), with the crystal replacing the tuned circuit. Although the output is small, it has the advantage that no tuning controls are required. The circuit requires capacitive coupling to a following stage. The amount of feed-back is determined by the condenser, C_2 ; its capacity must be determined by experiment, usual values being between 50 and 150 $\mu\text{fd.}$ To sustain oscillation, the net reactance (§2-8) of the plate-cathode circuit must be capacitive; this condition is met so long as the inductance of the r.f. choke, together with the inductance of any coils associated with the input circuit of the following stage and the tube and stray capacities, forms a circuit tuned to a lower frequency than that of the crystal.

Tubes such as the triode 6C5 and pentode 6F6 are suitable for use in this circuit. (When a triode is used the screen-voltage dropping resistor, R_3 , and by-pass condenser, C_4 , in Fig. 406 should, of course, be omitted.) The applied plate voltage should not exceed 300, to prevent crystal fracture. The capacity of the output-coupling condenser, C_5 , should be adjusted by experiment so that the oscillator is not overloaded; usually 100 $\mu\text{fd.}$ is a satisfactory value.

4-5 Harmonic-Generating Crystal Oscillators

Tri-tet oscillator — The Tri-tet oscillator circuit is shown in Fig. 407. In this circuit the screen grid is operated at ground potential and the cathode at an r.f. potential above ground. The screen-grid acts as the anode of a triode crystal oscillator, while the plate or output circuit is tuned to the oscillator frequency or, for harmonic output, to a multiple of it.

Besides giving harmonic output, the Tri-tet circuit has the "buffering" feature of electron-coupling between crystal and output circuits (§4-2). This makes the crystal frequency less susceptible to changes in loading or tuning, and hence improves the stability.

If the output circuit is to be tuned to the same frequency as the crystal, a tube having low grid-plate capacity (§3-2, 3-5) must be used. Otherwise there may be excessive feed-back with consequent danger of fracturing the crystal. The cathode tank circuit, $L_1 C_1$, is not tuned to the frequency of the crystal, but to a considerably higher frequency. Recommended values for L_1 are given under the diagram. C_1 should be set to as near minimum capacity as is consistent with good output. This reduces the crystal voltage.

With pentode-type tubes having separate suppressor connections, the suppressor may be either connected directly to ground or operated at about 50 volts positive. The latter method will give somewhat higher output.

With transmitting pentodes or beam tubes operated at 500 volts on the plate an output of 15 watts can be obtained on the fundamental and nearly as much on the second harmonic.

Grid-plate oscillator — In the grid-plate oscillator, Fig. 408, the crystal is connected between grid and ground and the cathode tuned circuit, C_2 and RFC, is tuned to a frequency lower than that of the crystal. This circuit gives high output on the fundamental crystal frequency with low crystal current. The output on even harmonics (2nd, 4th, etc.) is not so great as that obtainable with the Tri-tet, but on odd harmonics (3rd, 5th, etc.) the output is appreciably better.

If harmonic output is not needed, C_2 may be a fixed capacity of 100 $\mu\text{fd.}$ The cathode coil, RFC, may be a 2.5-mh. choke, since the inductance is not critical.

Output power of 15 to 20 watts at the crystal fundamental may be obtained with a tube such as the 6L6G at plate and screen voltages of 400 and 250, respectively.

Tuning and adjustment — The tuning procedure for the Tri-tet oscillator is as follows: With the cathode tank condenser at about three-quarters scale turn the plate tank condenser until there is a sharp dip in plate cur-

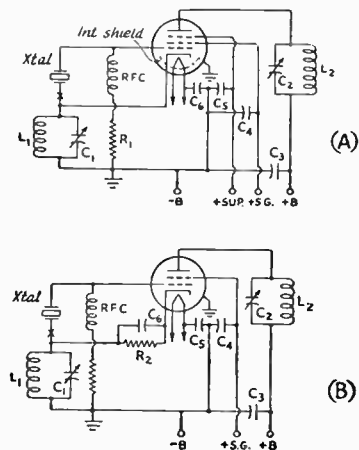


Fig. 407 — Tri-tet oscillator circuit, using pentodes (A) or beam tetrodes (B). C_1 and C_2 are 200- $\mu\text{fd.}$ variable condensers. C_3 , C_4 , C_5 , C_6 may be 0.001 to 0.01 $\mu\text{fd.}$; their values are not critical. R_1 , 20,000 to 100,000 ohms. R_2 should be 400 ohms for 400- or 500-volt operation. The following specifications for the cathode coils, L_1 , are based on a diameter of 1½ inches and a length of 1 inch; turns should be spaced evenly to fill the required length: for 1.75-Mc. crystal, 32 turns; 3.5 Mc., 10 turns; 7 Mc., 6 turns. The screen should be operated at 250 volts or less. Audio beam tetrodes such as the 6L6 and 6L6G should be used only for second-harmonic output. A flash-light bulb may be inserted at the point marked X (§4-3). The L/C ratio in the plate tank, $L_2 C_2$, should be such that the capacity in use is 75 to 100 $\mu\text{fd.}$ for fundamental output and about 25 $\mu\text{fd.}$ for second-harmonic output.

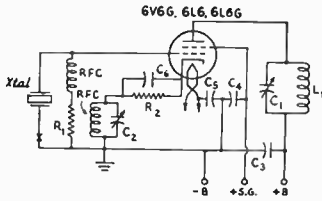


Fig. 408 — Grid-plate crystal oscillator circuit. In the cathode circuit, RFC is a 2.5-mh. r.f. choke. Other constants are the same as in Fig. 407. A crystal-current indicator may be inserted at the point marked X (§ 4-3).

rent, indicating that the plate circuit is in resonance. The crystal should be oscillating continuously, regardless of the setting of the plate condenser. Set the plate condenser so that plate current is minimum. The load circuit may then be coupled and adjusted so that the oscillator delivers power. The minimum plate current will rise; it may be necessary to retune the plate condenser when the load is coupled to bring the plate current to a new minimum. Fig. 409 shows the typical behavior of plate current with plate-condenser tuning.


After the plate circuit is adjusted and the oscillator is delivering power, the cathode condenser should be readjusted to obtain optimum power output. The setting should be as far toward the low-capacity end of the scale as is consistent with good output; it may, in fact, be desirable to sacrifice a little output if so doing lowers the current through the crystal and thus reduces heating.

For harmonic output the plate tank circuit is tuned to the harmonic instead of the fundamental of the crystal frequency. A plate-current dip will occur at the harmonic. If the cathode condenser is adjusted for maximum output at the harmonic, this adjustment will usually serve for the fundamental as well. The crystal should be checked for excessive heating,

the most effective remedy being to lower plate and/or screen voltage or to reduce the loading. Maximum r.f. voltage across the crystal is developed at maximum load, so heating should be checked with the load coupled.

When a fixed cathode condenser is used in the grid-plate oscillator the plate tank circuit is simply resonated, as indicated by the plate-current dip, to the fundamental or a harmonic of the output frequency, loading being adjusted to give optimum power output. If the variable cathode condenser is used, it should be set to give, by observation, the maximum power output consistent with safe crystal current. The variable condenser is useful chiefly in increasing the output on the third and higher harmonics; for fundamental operation, the cathode capacity is not critical and the fixed condenser may be used.

Fig. 409 — Curves showing d.c. plate current vs. plate-condenser tuning, both with and without load, for the Tri-tet oscillator. The setting for minimum plate current may shift with loading.

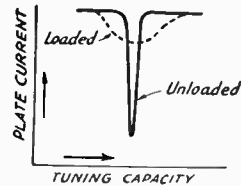

4-6 Interstage Coupling

Requirements — The purpose of the interstage coupling system is to transfer, with as little energy loss as possible, the power developed in the plate circuit of one tube (the driver) to the grid circuit of the following amplifier tube or frequency multiplier. The circuits in practical use are based on the fundamental coupling arrangements described in § 2-11. In the process of power transfer, impedance transformation (§ 2-9) frequently is necessary so that the proper exciting voltage and current will be available at the grid of the driven tube.

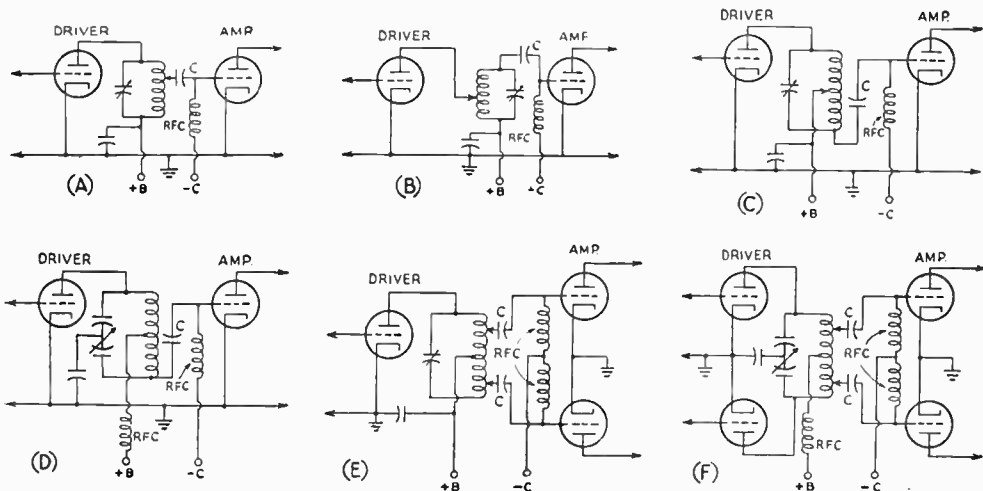


Fig. 410 — Direct- or capacity-coupled driver and amplifier stages. The coupling capacity may be from 50 $\mu\text{fd.}$ to 0.002 $\mu\text{fd.}$; it is not critical except where tapping the coils for control of excitation is not possible. Parallel plate feed to the driver and series grid feed to the amplifier may be substituted in any of these circuits (§ 3-7).

Capacity coupling — Fig. 410 shows several types of capacitive coupling. In each case, C is the coupling condenser. The coupling condenser serves also as a blocking condenser (§ 2-13) to isolate the d.c. plate voltage of the driver from the grid of the amplifier. The circuits of C and D are preferable when a balanced circuit is used in the output of the driver; instead of both tubes being in parallel across one side, the output capacity of the driver tube and the input capacity of the amplifier are across opposite sides of the tank circuit, thereby preserving a better circuit balance. The circuits of E and F are designed for coupling to a push-pull stage.

In A, B, E and F, excitation is adjusted by moving the tap on the coil to provide an optimum impedance match. In E and F, the two grid taps should be maintained equidistant from the center-tap on the coil.

While capacitive coupling is simplest from the viewpoint of construction, it has certain disadvantages. The input capacity of the amplifier is shunted across at least a portion of the driver tank coil. When added to the output capacity of the driver tube, this additional capacity may be sufficient, in many cases, to prevent use of a desirable L/C ratio in circuits for frequencies above about 7 Mc.

Link coupling — At the higher frequencies it is advantageous in reducing the effects of tube capacities on the L/C ratio to use separate tank circuits for the driver plate and amplifier grid, coupling the two circuits by means of a link (§ 2-11). This method of coupling also has some constructional advantages, in that separate parts of the transmitter may be constructed as separate units without the necessity for running long leads at high r.f. potential.

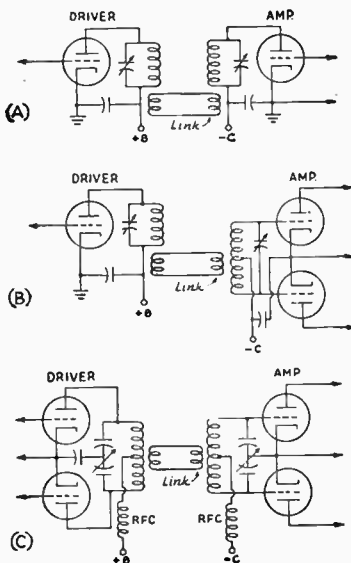


Fig. 411 — Link coupling between driver and amplifier.

Circuits for link coupling are shown in Fig. 411. The coupling ordinarily is by a turn or two of wire closely coupled to the tank inductance at a point of low r.f. potential, such as the center of the coil of a balanced tank circuit or the "ground" end of the coil in a single-ended circuit. The link line usually consists of two closely spaced parallel wires; occasionally the wires are twisted together, but this usually causes undue losses at high frequencies.

It is advisable to have some means of varying the coupling between link and tank coils. The link coil may be arranged to be swung in relation to the tank coil or, when it consists of a large turn around the outside of the tank coil, may be split into two parts which can be pulled apart or closed somewhat in the fashion of a pair of calipers. If the tank coils are wound on forms, the link may be wound close to the main coil.

With fixed coils, some adjustment of coupling usually can be obtained by varying the number of turns on the link. In general, the proper number of turns for the link must be found by experiment.

4-7 R.F. Power-Amplifier Circuits

Tetrode and pentode amplifiers — When the input and output circuits of an r.f. amplifier tube are tuned to the same frequency it will oscillate as a tuned-grid tuned-plate oscillator, unless some means is provided to eliminate the effects of feed-back through the plate-to-grid capacity of the tube (§ 3-5). In all transmitting r.f. tetrodes and pentodes, this capacity is reduced to a satisfactory degree by the internal shielding between grid and plate provided by the screen. Tetrodes and pentodes designed for audio use (such as the 6L6, 6V6, 6F6, etc.) are not sufficiently well screened for use as r.f. amplifiers without employing suitable means for nullifying the effect of the grid-plate capacity.

Typical circuits of tetrode and pentode r.f. amplifiers are shown in Fig. 412. The high power sensitivity (§ 3-3) of pentodes and tetrodes, makes them prone to self-oscillate with very small values of feed-back voltage, however, so that particular care must be used to prevent feed-back by means external to the tube itself. This calls for adequate isolation of plate and grid tank circuits to prevent undesired magnetic or capacity coupling between them. The requisite isolation can be secured either by keeping the circuits well separated and mounting the coils so that magnetic coupling is minimized, or by the use of interstage shielding (§ 2-11).

Triode amplifiers — The feed-back through the grid-plate capacity of a triode cannot be eliminated, and therefore special circuit means called *neutralization* must be used to prevent oscillation. A properly neutralized triode amplifier then behaves as though it were operating at very low frequencies, where the grid-plate capacity feed-back is negligible (§ 3-3).

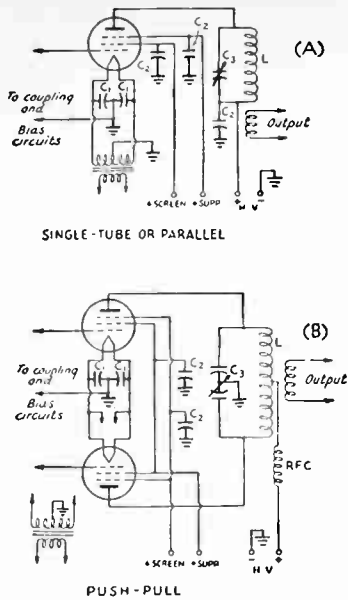


Fig. 412 — Typical tetrode-pentode r.f. amplifier circuits. $C_1 = 0.01 \mu\text{fd}$. $C_2 = 0.001 \mu\text{fd}$. $C_3 - L$ — See § 4-8. In circuits for tetrodes, the suppressor-grid connection and its associated by-pass condenser are omitted.

Neutralization — Neutralization amounts to taking some of the radio-frequency current from the output or input circuit of the amplifier and introducing it into the other circuit in such a way that it effectively cancels the current flowing through the grid-plate capacity of the tube, thus rendering it impossible for the tube to supply its own excitation. For complete neutralization of the amplifier, the two currents must be opposite in phase (§ 2-7) and equal in amplitude.

The out-of-phase current (or voltage) can be obtained quite readily by using a balanced tank circuit for either grid or plate, taking the neutralizing voltage from the end of the tank opposite that to which the grid or plate is connected. The amplitude of the neutralizing voltage can be regulated by means of a small condenser, the *neutralizing condenser*, having the same order of capacity as the grid-plate capacity of the tube. Circuits in which the neutralizing voltage is obtained from a balanced grid tank and fed to the plate through the neutralizing condenser are *grid-neutralized* circuits, while if the neutralizing voltage is obtained from a balanced plate tank and fed to the grid the circuit is *plate-neutralized*.

Plate-neutralized circuits — The circuits for plate neutralization are shown in Fig. 413 at A, B and C. In A, voltage induced in the extension of the tank coil is fed back to the grid through the neutralizing condenser, C_n , to balance the voltage appearing between grid and plate. In this circuit, the capacity required at C_n increases as the tank coil extension is made smaller; in general, neutralization is satisfactory over only a small range of frequencies since the coupling between the two sections of the tank coil will vary with the amount of capacity in use at C .

In B the tank coil is center-tapped to give equal voltages on either side of the center tap, the tank condenser being across the whole coil. The neutralizing capacity is approximately equal to the grid-plate capacity of the tube, in this case. A disadvantage of the circuit, when used with the single tank condenser shown, is that the rotor of the condenser is above ground potential, and hence small capacity changes caused by bringing the hand near the tuning control (*hand capacity*) cause detuning. In general, neutralization is complete at only one

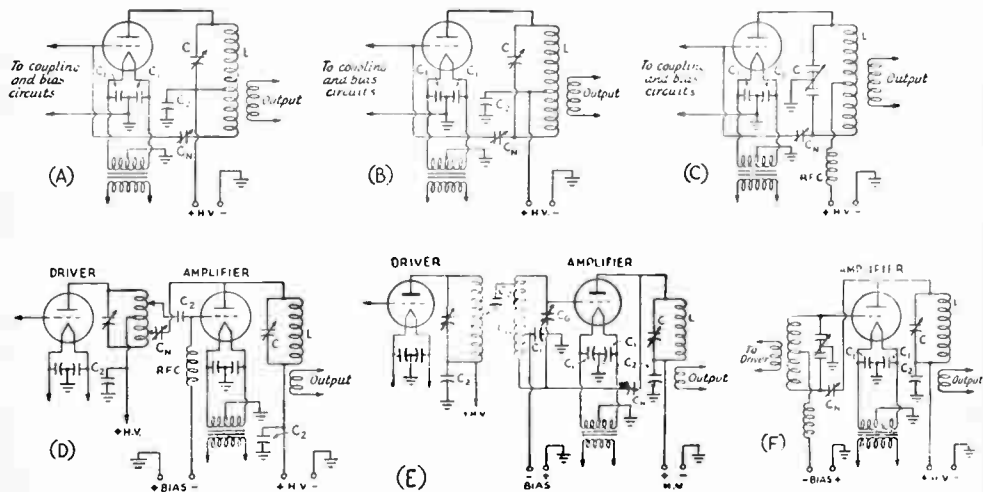


Fig. 413 — Neutralized triode amplifier circuits. Plate neutralization is shown in A, B and C, while D, E and F show types of grid neutralization. Either capacitive or link coupling may be used with the circuits of A, B or C. $C - L$ — See § 4-8. $C_0 - L_0$ — Grid tank circuit. C_n — Neutralizing condensers. $C_1 = 0.01 \mu\text{fd}$. $C_2 = 0.001 \mu\text{fd}$.

frequency since the plate-cathode capacity of the tube is across only half the tank coil; also, it is difficult to secure an exact center-tap. Both of these factors cause unbalance, which in turn causes the voltages across the two halves of the coil to differ when the frequency is changed.

The circuit of C also uses a center-tapped tank circuit, the voltage division being secured by use of a balanced (split-stator) tank condenser, the two condenser sections being identical. C_n is approximately equal to the grid-plate capacity of the tube. In this circuit the upper section of the tank condenser is in parallel with the output capacity of the tube, hence the circuit can be completely neutralized at only one setting of the tank condenser unless a

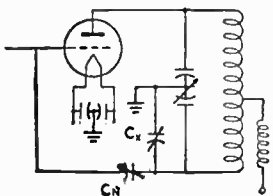


Fig. 414 — Compensating for unbalance in the single-tube neutralizing circuit. C_n , the balancing condenser, has a maximum capacity somewhat larger than the output capacity of the tube.

compensating capacity (Fig. 414) is connected across the lower section. It is adjusted so the neutralizing condenser need not be changed when frequency is shifted. In practice, if the capacity in use in the tank circuit is large compared to the plate-cathode capacity the unbalancing effect is not serious.

Grid-neutralized circuits — Typical circuits employing grid neutralization are shown in Fig. 413 at D, E and F. The principle of balancing out the feed-back voltage is the same as in plate neutralization. However, in these circuits the neutralizing voltage may be either in phase or out of phase with the excitation voltage on the grid side of the input tank circuit depending upon whether the tank is divided by means of a balanced condenser or a tapped coil. Circuits such as those at D and E, neutralized by ordinary procedure (described below), will be regenerative when the plate voltage is applied; the circuit at F will be degenerative. In addition the normal unbalancing effects previously described are present, so that grid neutralizing is less satisfactory than the plate method.

Inductive neutralization — With this type of neutralization, inductive coupling between the grid and plate circuits is provided in such a

way that the voltage induced in the grid coil by magnetic coupling from the plate coil opposes the voltage fed back through the grid-plate capacity of the tube. A representative circuit arrangement, using a coupling link to provide the mutual inductance (§ 2-11), is shown in Fig. 415-A. The link coils are of one or two turns coupled to the grounded ends of the tank coils. Neutralization is adjusted by moving the link coils in relation to the tank coils. Reversal of connections to one coil may be required for proper phasing. Ordinary inductive coupling between the two coils also could be used, but it is less convenient. Inductive neutralization is complete only at one frequency since the effective mutual inductance changes to some extent with tuning, but is useful in cases where the grid-plate capacity of the tube is very small and suitable circuit balance cannot be obtained by using neutralizing condensers.

Another form of neutralization, known as "coil" or "shunt" neutralization, is shown at B. Its operation is based on making the inductance of L_n such that, together with the grid-plate capacity of the tube, it resonates at the operating frequency. C_2 is merely a plate-voltage blocking condenser. If the Q of the coil is sufficiently high, the parallel resonant impedance between grid and plate is much higher than the grid-cathode circuit impedance. Because the system is difficult to adjust and functions satisfactorily only at one frequency, it is used chiefly in fixed-frequency transmitters. The variation in Fig. 414-C is useful for v.h.f. In this arrangement the coil is replaced by a parallel line, the effective length of which is adjusted until it is resonant when loaded by the grid-plate capacity.

Push-pull neutralization — With push-pull circuits two neutralizing condensers are used, as shown in Fig. 416. In these circuits, the grid-plate capacities of the tubes and the neutralizing capacities form a capacity bridge (§ 2-11) which is independent of the grid and plate tank circuits. The neutralizing capacities are approximately the same as the tube grid-plate capacities. With electrically similar tubes and symmetrical construction (stray capacities to ground equal on both sides of the circuit), the neutralization is complete and independent of frequency. A circuit using a balanced condenser, as at B, is preferred, since it is an aid in obtaining good circuit balance.

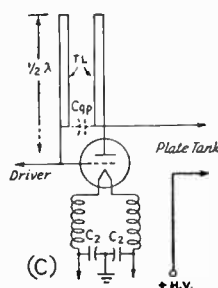
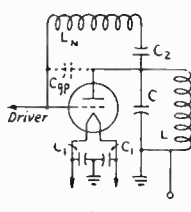
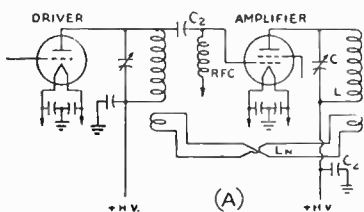


Fig. 415 — Inductive neutralization circuits. A, link neutralization. B, "coil" or shunt neutralization. C, modified shunt neutralizing circuit for v.h.f. using a half-wave line.

Frequency effects — The effects of slight dissymmetry in a neutralized circuit become more important as the frequency is raised, and may be sufficient at the very-high frequencies (or even lower) to prevent good neutralization. At these frequencies the inductances and stray capacities of even short leads become important elements in the circuit, while input loading effects (§ 7-6) may make it impossible to get proper phasing, particularly in single-tube circuits. In such cases the use of a push-pull amplifier, with its general freedom from the effects of dissymmetry, is not only much to be preferred but may be the only type of circuit which can be satisfactorily neutralized.

Neutralizing condensers — In most cases the neutralizing voltage will be equal to the r.f. voltage between the plate and grid of the

When two or more tubes are connected in parallel, the neutralizing capacity required will be in proportion to the number of tubes.

The voltage rating of neutralizing condensers must at least equal the r.f. voltage across the condenser plus the sum of the d.c. plate voltage and the grid-bias voltage.

Neutralizing procedure — The procedure in neutralizing is essentially the same for all tubes and circuits. The filament of the tube should be lighted and excitation from the preceding stage fed to the grid circuit. There should be no plate voltage on the amplifier.

The grid-circuit milliammeter makes a good neutralizing indicator. If the circuit is not completely neutralized, tuning of the plate tank circuit through resonance will change the tuning of the grid circuit and affect its loading, causing a change in the rectified d.c. grid current. The setting of the neutralizing condenser which leaves the grid current unaffected as the plate tank is tuned through resonance is the correct one. If the circuit is out of neutralization, the grid current will drop perceptibly as the plate tank is tuned through resonance. As the point of neutralization is approached, by adjusting the neutralizing capacity in small steps the dip in grid current as the plate condenser is swung through resonance will become less and less pronounced, until, at exact neutralization, there will be no dip at all. Further change of the neutralizing capacity in the same direction will bring the grid-current dip back. The neutralizing condenser should always be adjusted with a screwdriver of insulating material to avoid hand-capacity effects.

Adjustment of the neutralizing condenser may affect the tuning of the grid tank or driver plate tank, so both circuits should be retuned each time a change is made in neutralizing capacity. In neutralizing a push-pull amplifier the neutralizing condensers should be adjusted together, step by step, keeping their capacities as equal as possible.

With single-ended circuits having split-stator neutralizing, the behavior of the grid meter will depend somewhat upon the type of tube used. If the tube output capacity is not great enough to upset the balance, the action of the meter will be the same as in other circuits. With high-capacity tubes, however, the meter usually will show a gradual rise and fall as the plate tank is tuned through resonance, reaching a maximum right at resonance when the circuit is properly neutralized.

When an amplifier is not neutralized a neon bulb touched to the plate of the amplifier tube or to the plate side of the tuning condenser will glow when the tank circuit is tuned through resonance, providing the driver has sufficient power. The glow will disappear when the amplifier is neutralized. However, touching the neon bulb to such an ungrounded point in the circuit may introduce enough stray capacity to unbalance the circuit slightly, thus upsetting the neutralizing.

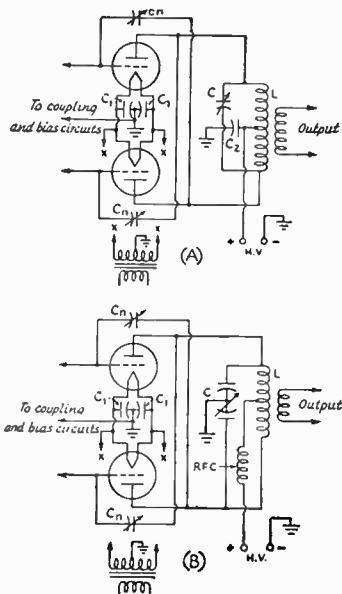


Fig. 416 — "Cross-neutralized" push-pull r.f. amplifier circuits. Either capacitive or link coupling may be used. C-L — See § 4-3. C_n — Neutralizing condensers. C₁ — 0.01 μfd. C₂ — 0.001 μfd. or larger.

tube, so that for perfect balance the capacity required in the neutralizing condenser theoretically will be equal to the grid-plate capacity. If, in the circuits having tapped tank coils, the tap is more than half the total number of turns from the plate end of the coil, the required neutralizing capacity will increase approximately in proportion to the relative number of turns in the two sections of the coil.

With tubes having grid and plate connections brought out through the bulb, a condenser having at about half-scale or less a capacity equal to the grid-plate capacity of the tube should be chosen. If the grid and plate leads are brought through a common base the capacity needed is greater, because the tube socket and its associated wiring adds some capacity to the actual interelement capacities.

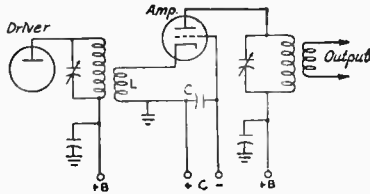


Fig. 417 — Inverted amplifier. The number of turns at *L* should be adjusted by experiment to give optimum grid excitation. By-pass condenser *C* is 0.001 μ fd. or larger.

A flashlight bulb connected in series with a single-turn loop of wire 2½ or 3 inches in diameter, with the loop coupled to the tank coil, also will serve as a neutralizing indicator. Capacitive unbalance can be avoided by coupling the loop to the low-potential part of the tank coil.

Incomplete neutralization — If a setting of the neutralizing condenser can be found which gives minimum r.f. current in the plate tank circuit without completely eliminating it, there may be magnetic or capacity coupling between the input and output circuits external to the tube itself. Short leads in neutralizing circuits are highly desirable, and the input and output inductances should be so placed with respect to each other that magnetic coupling is minimized. Usually this requires that the axes of the coils must be at right angles to each other. In some cases it may be necessary to shield the input and output circuits from each other. Magnetic coupling can be detected by disconnecting the plate tank from the remainder of the circuit and testing for r.f. in it (by means of the flashlight lamp and loop) as the tank condenser is tuned through resonance. The driver stage must be operating while this is done, of course.

With single-ended amplifiers there are many stray capacities left uncompensated for in the neutralizing process. With large tubes, especially those having relatively high interelectrode capacities, these commonly neglected stray capacities can prevent perfect neutralization. Symmetrical arrangement of a push-pull stage is about the only way to obtain practically perfect balance throughout the amplifier.

The neutralization of tubes with extremely low grid-plate capacity, such as the 6L6, is often difficult, since it frequently happens that the wiring itself will introduce sufficient capacity between the right points to "over-neutralize" the grid-plate capacity. The use of a neutralizing condenser only aggravates the condition. Inductive or link neutralization, as shown in Fig. 415, has been used successfully with such tubes.

The inverted amplifier — The circuit of Fig. 417 avoids the necessity for neutralization by operating the control grid of the tube at ground potential, thus making it serve as a shield between the input and output circuits. It is particularly useful with tubes of low grid-plate capacity, which are difficult to neutralize by ordinary methods. Excitation is ap-

plied between grid and cathode through the coupling coil, *L*; since this coil is common to both the plate and grid circuits the amplifier is degenerative with the circuit constants normally used, hence more excitation voltage and power are required for a given output than is the case with a neutralized amplifier. The tube used must have low plate-cathode capacity (of the order of 1 μ fd. or less) since larger values will give sufficient feed-back to permit it to oscillate, the circuit then becoming the ultraudion (§ 3-7). Tubes having sufficiently low plate-cathode capacity (audio pentodes, for example) can be used without danger of oscillation at frequencies up to perhaps 30 Mc. or so.

4-8 Power Amplifier Operation

Efficiency — An r.f. power amplifier is usually operated Class-C' (§ 3-4) to obtain a reasonably high value of plate efficiency (§ 3-3). The higher the plate efficiency the higher the power input that can be applied to the tube without exceeding the plate dissipation rating (§ 3-2), up to the limits of other tube ratings (plate voltage and plate current). Plate efficiencies of the order of 75 per cent are readily obtainable at frequencies up to the 30-50-Mc. region. The *over-all* efficiency of the amplifier will be lower by the power lost in the tank and coupling circuits, so that the actual efficiency is less than the plate efficiency.

Operating angle — The operating angle is the proportionate part of the exciting grid-voltage cycle (§ 2-7) during which plate current flows, as shown in Fig. 418. For Class-C operation, it is usually in the vicinity of 120-150 degrees. With other operating considerations, this angle results in an optimum relationship between plate efficiency and grid driving power.

Load impedance — The load impedance (§ 3-3) for an r.f. power amplifier is adjusted, by tuning the plate tank circuit to resonance, to represent a pure resistance at the operating frequency (§ 2-10). Its value, which usually is in the neighborhood of a few thousand ohms, is

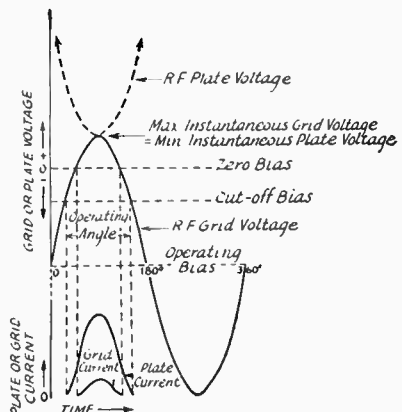


Fig. 418 — Instantaneous voltages and currents in a Class-C amplifier operating under optimum conditions.

adjusted by varying the loading on the tank circuit, closer coupling to the load giving lower values of load resistance and vice versa (§ 2-11). The load may be either the grid circuit of a following stage or the antenna circuit.

For highest efficiency the value of load resistance should be relatively high, but if only limited excitation voltage is available greater power output will be secured by using a lower value of load resistance. The latter adjustment is accompanied by a decrease in plate efficiency. The optimum load resistance is that which, for the maximum permissible peak plate current, causes the minimum instantaneous plate voltage (Fig. 418) to be equal to the maximum instantaneous grid voltage required to cause the peak plate current to flow; this gives the optimum ratio of plate efficiency to required grid driving power.

Rf. grid voltage and grid bias — For most tubes optimum operating conditions result when the minimum instantaneous plate voltage is 10 to 20 per cent of the d.c. plate voltage, so that the maximum instantaneous positive grid voltage must be approximately the same figure. Since plate current starts flowing when the instantaneous voltage reaches the cut-off value (§ 3-2), the d.c. grid voltage must be considerably higher than cut-off to confine the operating angle to 150 degrees or less (with grid bias at cut-off, the angle would be 180 degrees). For an angle of 120 degrees, the r.f. grid voltage must reach 50 per cent of its peak value (§ 2-7) at the cut-off point. The corresponding figure for an angle of 150 degrees is 25 per cent. Hence, the operating bias required is the cut-off value plus 25 to 50 per cent of the peak r.f. grid voltage. These relations are shown in Fig. 418. The grid bias should be at least twice cut-off if the amplifier is to be plate modulated, so that the operating angle will be not less than 180 degrees when the plate voltage rises to twice the steady d.c. value (§ 5-3). Because of their relatively high amplification factors, with most modern tubes Class-C operation requires considerably more than twice cut-off bias to make the operating angle fall in the region mentioned above. Suitable operating conditions are usually given in the data accompanying the type of tube used.

Grid bias may be secured either from a bias source (*fixed bias*), a grid leak (§ 3-6) of suitable value, or from a combination of both. When a bias supply is used, its voltage regulation should be taken into consideration (§ 8-9).

Driving power — As indicated in Fig. 418, grid current flows only during a small portion of the peak of the r.f. grid voltage cycle. The power consumed in the grid circuit therefore is approximately equal to the peak r.f. grid voltage multiplied by the average rectified grid current as read by a d.c. milliammeter. The peak r.f. grid voltage, if not included in the tube manufacturer's operating data, can be estimated roughly by adding 10 to 20 per cent of the plate voltage to the operating grid bias,

assuming the operating conditions are as described above.

At frequencies up to 30 Mc. or so, the grid losses are practically entirely those resulting from grid-current flow. At the very-high frequencies, however, dielectric losses in the glass envelope and base materials become appreciable, together with losses caused by transit-time effects (§ 7-6), and may necessitate supplying several times the driving power indicated above. At any frequency, the driving stage should be capable of a power output two to three times the power it is expected the grid circuit of the amplifier will consume. This is necessary because losses in the tank and coupling circuits must also be supplied, and also to provide reasonably good regulation of the r.f. grid voltage. Good voltage regulation (see § 8-1 for general definition) insures that the waveform of the excitation voltage will not be distorted because of the changing load on the driver during the r.f. cycle.

Grid impedance — During most of the r.f. grid-voltage cycle no grid current is flowing, as

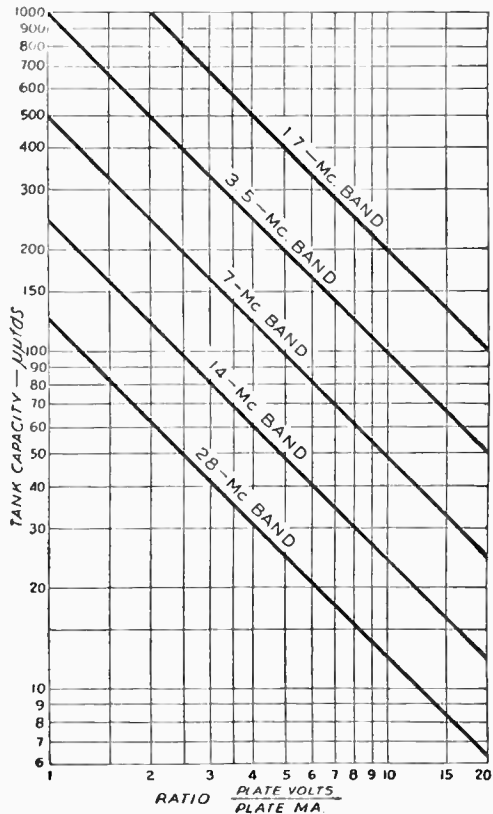


Fig. 419 — Chart showing tank capacities required for a Q of 12 with various ratios of plate voltage to plate current, for various frequencies. In circuits F, G, H (Fig. 420), the capacities shown in the graph may be divided by four. In circuits C, D, E, I, J and K, the capacity of each section of the split-stator condenser may be one-half that shown by the graph. The values given by the graph should be used for circuits A and B.

indicated in Fig. 418, hence the grid impedance is infinite. During the peak of the cycle, however, the impedance may drop to very low values (of the order of 1000 ohms), depending upon the type of tube. Both the minimum and average values of grid impedance depend to a considerable extent on the amplification factor of the tube, being lower with tubes having large amplification factors.

The average grid impedance is equal to E^2/P , where E is the r.m.s. (§ 2-7) value of r.f. grid voltage and P is the grid driving power. Under optimum operating conditions, values of average grid impedance ranging from 2000 ohms for high- μ tubes to four or five times as much for low- μ types are representative. Values in the vicinity of 4000 to 5000 ohms are typical of modern triodes with amplification factors of 20 to 30.

Because of the large change in impedance during the cycle, it is necessary that the tank circuit associated with the amplifier grid have fairly high Q . This is essential to provide sufficient storage capacity so that the voltage regulation over the cycle will be good. The requisite Q may be obtained by adjusting the L/C ratio or by tapping the grid circuit across only part of the tank (§ 4-6).

Tank-circuit Q — Besides serving as a means for transforming the actual load resistance to the required value of plate load impedance for the tube, the plate tank circuit also should suppress the harmonics present in the tube output as a result of the non-sinusoidal plate current (§ 2-7, 3-3). For satisfactory harmonic suppression, a Q of 12 or more (with the circuit fully loaded) is desirable. A Q of this order also is helpful from the standpoint of securing adequate coupling to the load or antenna circuit (§ 2-11). The proper Q can be obtained by suitable selection of L/C ratio in relation to the optimum plate load resistance for the tube (§ 2-10).

For a Class-C amplifier operated under optimum conditions as described above, the plate load impedance is approximately proportional to the ratio of d.c. plate voltage to d.c. plate current. For a given effective Q the tank capacity required at a given frequency will be inversely proportional to the parallel resistance (§ 2-10), so that it will also be inversely proportional to the plate-voltage/plate-current ratio.

The tank capacity required on various amateur bands for a Q of 12 is shown in Fig. 419 as a function of this ratio. The capacity given is for single-ended tank circuits, as shown in Fig. 420 at A and B. When a balanced tank circuit is used the total tank capacity required is reduced to one-fourth this value, because the tube is connected across only half the circuit (§ 2-9). Thus, if the plate-voltage/plate-current ratio calls for a capacity of 200 $\mu\text{fd.}$ in a single-ended circuit at the desired frequency, only 50 $\mu\text{fd.}$ would be needed in a balanced circuit. If a split-stator or balanced tank condenser is used each section should have a capacity of 100 $\mu\text{fd.}$, the total capacity of the two in series being 50 $\mu\text{fd.}$ These are "in use" capacities; not simply the rated maximum capacity of the condenser. Larger values may be used with an increase in the effective Q .

To reduce energy loss in the tank circuit, the inherent Q of the coil and condenser should be high. Since transmitting coils usually have Q s ranging from 100 to several hundred, the tank transfer efficiency generally is 90 per cent or more. An unduly large C/L ratio is not advisable since it will result in large circulating r.f. tank current and hence relatively large losses in the tank, with a consequent reduction in the power available for the load.

Tank constants— When the capacity necessary for a Q of 12 has been determined from Fig. 419, the inductance required to resonate at the given frequency can be found by means

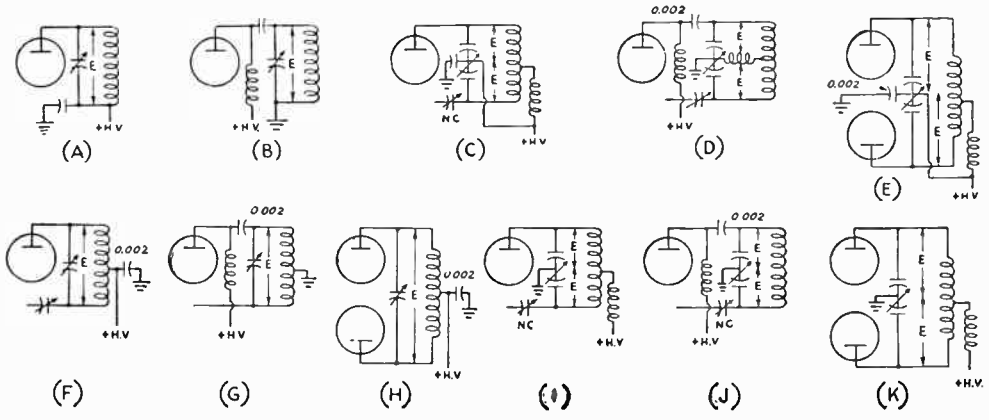


Fig. 420 — In circuits A, B, C, D and E, the peak voltage E will be approximately equal to the d.c. plate voltage applied for c.w. or twice this value for 'phone. In circuits F, G, H, I, J and K, E will be twice the d.c. plate voltage for c.w. or four times the plate voltage for 'phone. The circuit is assumed to be fully loaded. Tubes in parallel in any of the circuits will not affect the peak voltage. Circuits A, C, E, F, G and H require that the tank condenser be insulated from chassis or ground and that it be provided with a suitably insulated shaft coupling for tuning.

of the formula in § 2-10. Alternatively, the required number of turns on coils of various construction can be found from the charts of Figs. 421 and 422.

Fig. 421 is for coils wound on receiving-type forms having a diameter of $1\frac{1}{2}$ inches and ceramic forms having a diameter of $1\frac{3}{4}$ inches and winding length of 3 inches. Such coils would be suitable for oscillator and buffer stages where the power is not over 50 watts. In all cases, the number of turns given must be wound to fit the length indicated and the turns should be evenly spaced.

Fig. 422 gives data on coils wound on transmitting-type ceramic forms. In the case of the smallest form, extra curves are given for double spacing (winding turns in alternate grooves). This is sometimes advisable in the case of 14- and 28-Mc. coils when only a few turns are required. In all other cases, the specified number of turns should be wound in the grooves without any additional spacing.

Ratings of components — The peak voltage to be expected between the plates of a tank condenser depends upon the arrangement of the tank circuit as well as the d.c. plate voltage. Peak voltage may be determined from Fig. 420, which shows all of the commonly used tank-circuit arrangements. These estimates assume that the amplifier is fully loaded; the voltage will rise considerably should the amplifier be

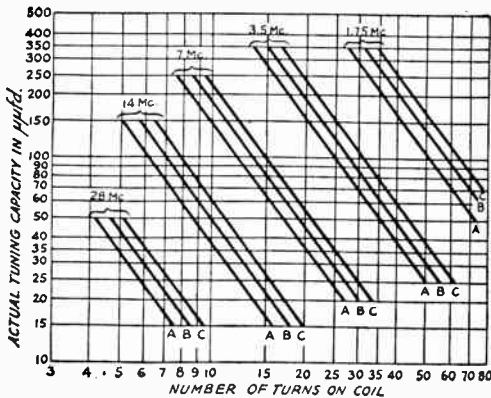


Fig. 421 — Coil-winding data for receiving-type forms, diameter $1\frac{1}{2}$ inches. Curve A — winding length, 1 inch; Curve B — winding length, $1\frac{1}{2}$ inches; Curve C — winding length, 2 inches. Curve C is also suitable for coils wound on $1\frac{3}{4}$ -inch diameter transmitting-type ceramic forms with 3 inches of winding length.

operated without load. The figures include a reasonable factor of safety.

The condenser plate spacing required to withstand any particular voltage will vary with the construction. Most manufacturers specify peak-voltage ratings in describing their condensers.

Plate or screen by-pass condensers of 0.001 μ fd. should be satisfactory for frequencies as low as 1.7 Mc. Cathode-resistor and filament by-passes in r.f. circuits should be not less than 0.01 μ fd. Fixed condensers used for these pur-

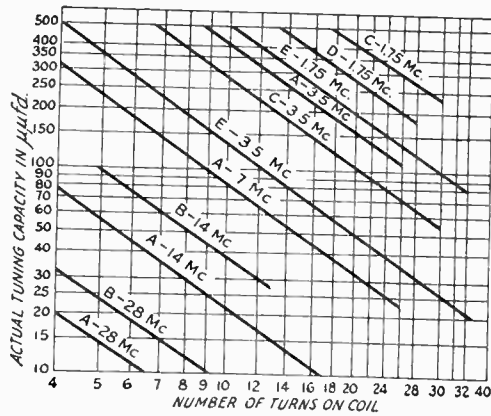


Fig. 422 — Coil-winding data for ceramic transmitting-type forms. Curve A — ceramic form $2\frac{1}{2}$ -inch effective diameter, 26 grooves, 7 per inch; Curve B — same as A, but with turns wound in alternate grooves; Curve C — ceramic form $2\frac{7}{8}$ -inch effective diameter, 32 grooves, 7.1 turns per inch, approximately; Curve D — ceramic form 4-inch effective diameter, 28 grooves, 5.85 turns per inch, approximately; Curve E — ceramic form 5-inch effective diameter, 26 grooves, 7 per inch. Coils may be wound with either No. 12 or No. 14 wire.

poses should have voltage ratings 25 to 50 per cent greater than the maximum d.c. or a.c. voltage across them.

Interstage coupling condensers should have voltage ratings 50 to 100 per cent greater than the sum of the driver plate and amplifier grid-biasing voltages.

4-9 Adjustment of Power Amplifiers

Excitation — The effectiveness of adjustments to the coupling between the driver plate and amplifier grid circuits can be gauged by the relative values of amplifier rectified grid current and driver plate current, the object being to obtain maximum grid current with minimum driver loading. The amplifier grid circuit represents the load on the driver stage, and the average grid impedance must therefore be transformed to the value for optimum driver operation (§ 4-8).

With capacity coupling, either the driver plate or amplifier grid must be tapped down on the driver tank coil, as shown in Fig. 410 at A and B, unless the grid impedance is approximately the right value for the driver plate load, when it will be satisfactory to connect both elements to the end of the tank. If the grid impedance is lower than the required driver plate load, Fig. 410-A is used; if higher, Fig. 410-B. In either case, the coupling which gives the desired grid current with minimum driver loading should be determined experimentally by moving the tap. Should both plate and grid be connected to the end of the circuit it is sometimes possible to control the loading, when the grid impedance is low, by varying the capacity of the coupling condenser, C_1 , but this method is not altogether satisfactory since it is simply an expedient to prevent driver overloading without giving suitable impedance matching.

In push-pull circuits the method of adjustment is similar, except that the taps should be kept symmetrically located with respect to the center of the tank circuit.

With link coupling, Fig. 411, the object of adjustment is the same. The two tanks are first tuned to resonance, as indicated by maximum grid current, and the coupling adjusted by means of the links (§ 4-6) to give maximum grid current with minimum driver plate current. This usually will suffice to load the driver to its rated output, provided the driver plate and amplifier grid tank circuits have reasonable values of Q . If the Q of one or both of the circuits is too low, it may not be possible to load the driver fully with any adjustment of link turns or coupling at either tank. In such a case, the Q s of the tank circuits must be increased to the point where adequate coupling is secured. If the driver plate tank is designed to have a Q of 12, the difficulty almost invariably is in the amplifier grid tank. The Q can be increased to a suitable value either by adjustment of the L/C ratio or by tapping the load across part of the coil (§ 2-10).

Whatever the type of coupling, a preliminary adjustment should be made with the proper bias voltage and/or grid leak, but with the amplifier plate voltage off; then the amplifier should be carefully neutralized. After neutralization the driver-amplifier coupling should be readjusted for optimum power transfer, after which plate voltage may be applied and the amplifier plate circuit adjusted to resonance and coupled to its load. Under actual operating conditions the grid current decreases below the value obtained without plate voltage on the amplifier and the effective grid impedance rises, hence the final adjustment is to re-check the coupling to take care of this shift.

With recommended bias, the grid current obtained before plate voltage is applied to the amplifier should be 25 to 30 per cent higher than the value required for operating conditions. If this value is not obtained, and the driver plate input is up to rated value, the reason may be either improper matching of the amplifier grid to the driver plate or simply insufficient power output from the driver to take care of all losses. Driver operating voltages should be checked to assure they are up to rated values. If batteries are used for bias and are not strictly fresh, they should be replaced, since batteries which have been in use for some time often develop high internal resistance which effectively acts as additional grid-leak resistance. If a rectified a.c. bias supply is used, the bleeder or voltage-divider resistances should be checked to make certain that low grid current is not caused by greater grid-circuit resistance than is recommended. In this connection it is helpful to measure the actual bias when grid current is flowing, by means of a high-resistance d.c. voltmeter. There is also the possibility of loss of filament emission of the amplifier tube, either from prolonged serv-

ice or from operating the filament under or over the rated voltage.

Plate tuning — In preliminary tuning, it is desirable to use low plate voltage to avoid possible damage to the tube. With excitation and plate voltage applied, rotate the plate tank condenser until the plate current dips. Then set the condenser at the minimum plate-current point (resonance). When the resonance point has been found, the plate voltage may be increased to its normal value.

With adequate excitation, the off-resonance plate current of a triode amplifier may be two or more times the normal operating value. With screen-grid tubes the off-resonance plate current may not be much higher than the normal operating value, since the plate current is principally determined by the screen rather than the plate voltage.

Under reasonably efficient operating conditions the minimum plate current with the amplifier unloaded will be a small fraction of the rated plate current for the tube (usually a fifth or less), since with no load the parallel impedance of the tank circuit is high. If the excitation is low the "dip" will not be very marked, but with adequate excitation the plate current at resonance without loading will be just high enough so that the d.c. plate power input supplies all the losses in the tube and circuit. As an indication of probable efficiency, the minimum plate current value should not be taken too seriously, because

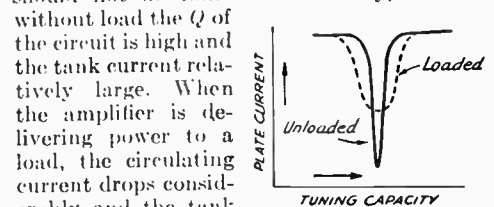


Fig. 423 — Typical behavior of d.c. plate current vs. tuning capacity in the plate circuit of an amplifier.

without load the Q of the circuit is high and the tank current relatively large. When the amplifier is delivering power to a load, the circulating current drops considerably and the tank losses correspondingly decrease. High minimum unloaded plate current is chiefly encountered at 28 Mc. and above, where tank losses are higher and the tank L/C ratio is usually lower than normal because of irreducible tube capacities. The effect is particularly noticeable with screen-grid tubes, which have relatively high output capacity. Because of the decrease in tank r.f. current with loading, however, the actual efficiency under load is reasonably good.

With the load (antenna or following amplifier grid circuit) connected, the coupling between plate tank and load should be adjusted to make the tube take rated plate current, keeping the tank always tuned to resonance. As the output coupling is increased the minimum plate current also will increase, about as shown in Fig. 423. Simultaneously the tuning becomes less sharp, because of the increase in effective resistance of the tank. If the load circuit simulates a resistance, the resonance setting of the

tank condenser will be practically unchanged with loading; this is generally the case, since the load circuit usually is also tuned to resonance. A reactive load (such as an antenna or feeder system not tuned exactly to resonance) may cause the tank condenser setting to change with loading, since reactance as well as resistance is coupled into the tank (§ 2-11).

Power output — As a check on the operation of an amplifier, its power output may be measured by the use of a load of known resistance, coupled to the amplifier output as shown in Fig. 424. At A a thermoammeter, M , and a noninductive (ordinary wire-wound resistors are not satisfactory) resistance, R , are connected across a coil of a few turns coupled to the amplifier tank coil. The higher the resistance of R , the greater the number of turns required in the coupling coil. A resistor used in this way is generally called a "dummy antenna," since its use permits the transmitter to be adjusted without actually radiating power. The loading may readily be adjusted by varying the coupling between the two coils, so that the amplifier draws rated plate current when tuned to resonance. The power output is then calculated from Ohm's Law:

$$P \text{ (watts)} = I^2 R$$

where I is the current indicated by the thermoammeter and R is the resistance of the non-inductive resistor. Special resistance units are available for this purpose, ranging from 73 to 600 ohms (simulating antenna and transmission-line impedances) at power ratings up to 100 watts. For higher powers, the units may be connected in series-parallel. The meter scale required for any expected value of power output may also be determined from Ohm's Law:

$$I = \sqrt{\frac{P}{R}}$$

Incandescent light bulbs can be used to replace the special resistor and thermoammeter. The lamp should be equipped with a pair of leads, preferably soldered to the terminals on the lamp base. The coupling should be varied until the greatest brilliancy is obtained for a given plate input. In using lamps as dummy antennas a size corresponding to the expected power output should be selected, so that the lamp will operate near its normal brilliancy. Then, when the adjustments have been completed, an approximation of the power output can be obtained by comparing the brightness of the lamp with the brightness of one of similar power rating in a 115-volt socket.

The circuit of Fig. 424-B is for resistors or lamps of relatively high resistance. In using this circuit, care should be taken to avoid accidental contact with the plate tank when the power is on. This danger is avoided by circuit C, in which a separate tank circuit, LC , tuned to the operating frequency, is coupled to the plate tank circuit. The loading is adjusted by varying the number of turns across which the

dummy antenna is connected on L and by changing the coupling between the two coils. With push-pull amplifiers, the dummy antenna should be tapped equally on either side of the center of the tank when the circuit of Fig. 424-B is used.

Harmonic suppression — The most important step in the elimination of harmonic radiation (§ 4-8, 2-12) is to use an output tank circuit having a Q of 12 or more. Beyond this it is desirable to avoid any considerable amount of over-excitation of a Class-C amplifier, since excitation in excess of that required for normal Class-C operation further distorts the plate-current pulse and increases the harmonic content in the output of the amplifier even though the proper tank Q is used. If the antenna system in use will accept harmonic frequencies they will be radiated when distortion is present, and consequently the antenna coupling system preferably should be selected with harmonic transfer in mind (§ 10-6).

Harmonic content can be reduced to some extent by preventing distortion of the r.f. grid-voltage waveshape. This can be done by using a grid tank circuit with high effective Q . Link coupling between the driver and final amplifier are helpful, since the two tank circuits provide more attenuation than one at the harmonic frequencies. However, the advantages of link coupling in this respect may be nullified unless the Q of the grid tank is high enough to give good voltage regulation, which minimizes harmonic transfer and thus prevents distortion in the grid circuit.

The stray capacity between the antenna coupling coil and the tank coil may be sufficient to couple harmonic energy into the antenna system. This coupling may be eliminated by the use of electrostatic shielding (*Paraday shield*) between the two coils. Fig. 425 shows the construction of such a shield, while Fig. 426 illustrates the manner in which it is installed. The construction shown in Fig. 425 prevents current flow in the shield, which would occur if the wires formed closed circuits since the shield is in the magnetic field of the tank coil.

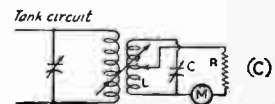
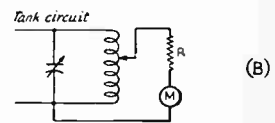
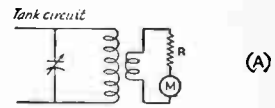


Fig. 424 — "Dummy antenna" circuits for checking power output and making operating adjustments under load without applying power to the actual antenna.

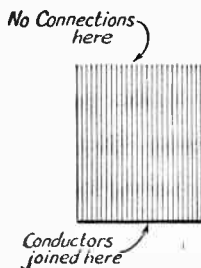


Fig. 425 — The Faraday electrostatic shield for eliminating capacitive transfer of harmonic energy. It is made of parallel conductors, insulated from each other except at one end where all are joined. Stiff wire or small diameter rod may be used, spaced about the diameter of the wire or rod. The shield should be larger than the diameter of the coil.

Should this occur, there would be magnetic shielding as well as electrostatic; in addition, there would be a power loss in the shield.

Improper operation — Inexact neutralization or stray coupling between plate and grid circuits may result in regeneration. This effect is most evident with low excitation, when the amplifier will show a sudden increase in output when the plate tank circuit is tuned slightly to the high-frequency side of resonance. It is accompanied by a pronounced increase in grid current.

Self-oscillation is apt to occur with tubes of high power sensitivity, such as the r.f. pentodes and tetrodes. In event of either regeneration or oscillation, circuit components should be arranged so that those in the plate circuit are well isolated from those of the grid circuit. Plate and grid leads should be made as short as possible and the screen should be by-passed as close to the socket terminal as possible. A cylindrical shield surrounding the lower portion of the tube up to the lower edge of the plate is sometimes required.

"Double resonance," or two tuning spots on the plate-tank condenser, one giving minimum plate current and the other maximum power output, may occur when the tank circuit Q is too low (§ 2-10). A similar effect also occurs at times with screen-grid amplifiers when the screen-voltage regulation (§ 8-1) is poor, as when the screen is supplied through a dropping resistor. The screen voltage decreases with a decrease in plate current, because the screen current increases under the same conditions. Thus the minimum plate-current point causes the screen voltage, and hence the power output, to be less than when a slightly higher plate current is drawn.

A phenomenon known as "grid emission" may occur when the amplifier tube is operated at higher than rated power dissipation on either the plate or grid. It is particularly likely to occur with tubes having oxide-coated cathodes, such as the indirectly heated types. It is caused by the grid reaching a temperature high enough to cause electron emission (§ 2-4). The electrons so emitted are attracted to the plate, further increasing the power input and heating, so that grid emission is characterized by gradually increasing plate current and heat which eventually will ruin the tube if the power is not removed. Grid emission can be prevented by operating the tube within its ratings.

4-10 Parasitic Oscillations

Description — If the circuit conditions in an oscillator or amplifier are such that self-oscillation exists at some frequency other than that desired, the spurious oscillation is termed *parasitic*. The energy required to maintain a parasitic oscillation is wasted insofar as useful output is concerned, hence an oscillator or amplifier having parasites will operate at reduced efficiency. In addition, its behavior at the operating frequency often will be erratic. Parasitic oscillations may be either higher or lower in frequency than the operating frequency.

The parasitic oscillation usually starts the instant plate voltage is applied, or, when the amplifier is biased beyond cut-off, at the instant excitation is applied. In the latter case, the oscillation frequently will be self-sustaining after the excitation has been removed. At other times the oscillation may not be self-sustaining, becoming active only in the presence of excitation. It may be apparent only by the production of abnormal key clicks (§ 6-1) over a wide frequency range, or by the presence of spurious side-bands (§ 5-2) with 'phone modulation.

Low-frequency parasites — Parasitic oscillations at low frequencies (usually 500 kc. or less) are of the tuned-plate tuned-grid type, the tuned circuits being formed by r.f. chokes and associated by-pass and coupling condensers, with the regular tank tuning condensers having only a minor effect on the oscillation. The operating-frequency tank coil has negligible inductance for such low frequencies and may be short-circuited without affecting the oscillations. The oscillations do not occur when no r.f. chokes are used, hence whenever possible in series-fed circuits such chokes should be omitted. With single-ended amplifiers, it is usually possible to arrange the circuit so that either the grid or plate circuit needs no choke. In push-pull stages having chokes in both plate and grid circuits, it is helpful to connect an unby-passed grid leak from the choke to the bias supply or ground, thus placing the resistance in the parasitic circuit and tending to prevent oscillation. When the driver plate circuit has parallel feed and the amplifier grid circuit series feed (§ 3-7) this type of oscillation cannot occur if no choke is used in the series grid circuit, since the grid is grounded through the tank coil for the parasitic frequency.

Parasitics near operating frequency — In circuits utilizing a tap on the plate tank coil to establish a ground for a balanced neutralizing circuit, such as Fig. 413-B, a parasitic oscillation may be set up if the amplifier grid is tapped down on the grid (or driver plate) tank circuit for adjustment of driver-amplifier coupling (§ 4-6). In this case the turns between grid and ground and between plate and ground form, with the stray and other capacities present, a t.p.t.g. circuit (§ 3-7) which oscillates at a frequency somewhat higher than the nominal operating frequency. Such an oscillation can

be prevented by dispensing with the taps in either the plate or grid circuit. Balancing the plate circuit by means of a split-stator condenser (Fig. 413-C) is recommended.

Very-high-frequency parasitics — Parasitics in the v.h.f. region are likely to occur with any amplifier having a balanced tank circuit, particularly when associated with neutralizing connections. The parasitic resonant circuit, formed by the leads connecting the various components, may be of either the t.p.t.g. or the ultradion type.

The frequency of such oscillations may be determined by connecting a tuned circuit in series with the grid lead to the tube. A variable condenser (50 or 100 $\mu\text{mfd.}$) may be used, in conjunction with three or four self-supporting turns of heavy wire wound into a coil an inch or so in diameter. With the amplifier oscillating at the parasitic frequency, the condenser is slowly tuned through its range until oscillations cease. If this point is not found on the first trial, the turns of the coil may be spread apart or a turn removed and the process repeated. The use of such a tuned circuit as a trap is an almost certain remedy if the frequency can be determined, and introduces little if any loss at the operating frequency.

An alternative cure, which is feasible when the oscillation is of the t.p.t.g. type, is to detune the parasitic circuit in either the plate or grid circuit. Since this type of oscillation occurs most frequently with push-pull amplifiers, it may often be cured by making the grid and plate leads to their respective tank circuits of considerably different length. Similar considerations apply to neutralizing connections in push-pull circuits. The extra wire length may be coiled up in the form of a so-called "choke," which in this case is simply additional inductance for detuning the parasitic circuit.

Testing for parasitic oscillations — An amplifier always should be tested for parasitic oscillations before being considered ready for service. The preferable method is first to neutralize the amplifier, then apply sufficient fixed bias to permit a moderate value of plate current to flow without excitation. (The plate current should not be large enough to cause the power input to exceed the rated plate dissipation of the tube.) If the amplifier is free from self-starting parasitics, the plate current will remain steady as the tank condensers are varied; also, there will be no grid current and a neon bulb touched either to the plate or grid will show no glow. Extreme care must be

used not to let the hand come into contact with any metal parts of the transmitter when using the neon bulb.

If any of these effects are present, the frequency of the parasitic must first be determined. If r.f. chokes are used in both the plate

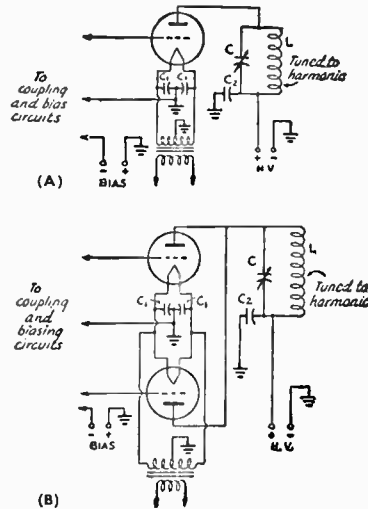


Fig. 427 — Frequency-multiplying circuits. A is for triodes, used either singly or in parallel. The push-push doubler is shown at B. Any type of coupling may be used between the grid circuit and the driver. C_1 should be 0.01 $\mu\text{fd.}$ or larger; C_2 , 0.001 $\mu\text{fd.}$ or larger.

and grid circuits, one of them should be short-circuited to determine if the oscillation is at a low frequency; if so, it may be eliminated by the methods outlined above. If the test indicates that the parasitic is not a low-frequency oscillation, the grid trap described above should be tried for the v.h.f. type. The type which occurs near the operating frequency will not exist unless the plate and grid tank coils are both tapped, hence may be eliminated from consideration if this is not the case in the circuit used. When such an oscillation is present its existence can be detected by moving the grid tap to include the whole tank circuit, whereupon the oscillation will cease.

Some indication of the frequency of the parasitic can be obtained from the color of the glow in the neon bulb. Usually it will be yellowish with low-frequency oscillations and violet with v.h.f. oscillations.

If the amplifier is stable under the conditions described above, excitation should be applied and then removed to ascertain if a self-sustaining oscillation is set up with excitation. If the plate current does not return to the previous value when the excitation is cut off, the same tests should be applied to determine the parasitic frequency.

As a final test, the transmitter should be put on the air and a near-by receiver tuned over as wide a frequency range as possible, to locate

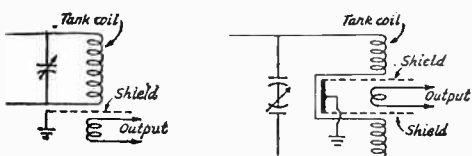


Fig. 426 — Methods of using Faraday shields. Two are required with a push-pull or balanced tank circuit.

any off-frequency signals associated with the radiation. Parasitics usually can be recognized by their poor stability as contrasted to the normal harmonics of the signal, which will have the same stability as the fundamental signal as well as the usual harmonic relationship. Harmonics should be quite weak compared to the output at the fundamental frequency, whereas parasitic oscillations may have considerable strength.

4-11 Frequency Multiplication

Circuits — A frequency multiplier is an amplifier having its plate tank circuit tuned to a multiple (harmonic) of the frequency applied to its grid. The difference between a straight amplifier (§ 4-1) and a frequency multiplier is in the way in which it is operated, rather than in the circuit. However, since the grid and plate tank circuits are tuned to different frequencies a triode frequency multiplier will not self-oscillate, hence does not need neutralization. A typical circuit arrangement is shown in Fig. 427-A. For screen-grid multipliers, the circuit is the same as in Fig. 412-A. Under usual conditions the plate efficiency of a frequency multiplier drops off rapidly with an increase in the number of times the frequency is multiplied. For this reason most multipliers are used as *frequency doublers*, giving second harmonic output.

A special circuit for frequency doubling ("push-push" doubler) is shown in Fig. 427-B. The grids of the tubes are in push-pull and the plates in parallel, thus the plate tank receives two pulses of plate current for each cycle of excitation frequency. The circuit is similar to that of a full-wave rectifier (§ 8-3), where the output ripple frequency is twice the applied frequency.

Push-pull amplifiers are suitable for frequency multiplication at odd harmonics, particularly the third, but they are unsuited to even-harmonic multiplication because the even harmonics are largely balanced out in the push-pull tank circuit (§ 3-3).

Operating conditions and circuit constants — To obtain good efficiency the operating angle at the harmonic frequency must be 180 degrees or less, preferably in the vicinity of 150-120 degrees (§ 4-8). In a doubler, this means that plate current should flow during only half this angle of fundamental frequency. Consequently the r.f. grid voltage, operating bias, and grid driving power must be increased considerably beyond the values obtaining for normal Class-C amplification. For comparable plate efficiency the bias will ordinarily be four to five times the normal Class-C bias, and the r.f. grid voltage must be considerably larger to drive the tube to the same peak plate current. Since the plate and grid current pulses under these conditions have the same peak amplitudes but only half the time duration as in a straight amplifier, the average d.c. values should be one-half those for normal Class-C

operation. That is, a tube operated in this way will have the same plate efficiency as a Class-C amplifier but can be operated at only half the plate input, so that the output power also is halved. The driving power required usually is about twice that necessary with straight-through amplification to obtain the same plate efficiency.

Greater output can be secured by using a larger operating angle (lower grid bias) or a lower plate load resistance, to increase the plate current; but this is accompanied by a decrease in efficiency. Since operation of the tube as described in the preceding paragraph is below its maximum plate dissipation rating, the decreased efficiency usually can be tolerated in the interests of securing more power output. In practice, an efficiency of 40 to 50 per cent is about average.

The tank circuit should have reasonably high Q (12 is satisfactory) to give good output voltage regulation (§ 4-9), since a plate-current pulse occurs only once for every two cycles of the output frequency. A low- Q circuit (high L/C ratio) is helpful chiefly when the operating angle is greater than 180 degrees at the second harmonic. Such a tank circuit will have relatively high impedance to the fundamental-frequency component of plate current which is present with large operating angles, and thus will aid in reducing the average d.c. plate current.

The grid impedance of a frequency multiplier is considerably higher than that of a straight-through amplifier, because of the high bias voltage. The average impedance can be calculated as previously described (§ 4-8). The L/C ratio of the grid tank circuit may be higher, therefore, for a given Q . Often it is advantageous to use a fairly high ratio, since a large r.f. voltage must be developed between grid and cathode. However, it must not be made too high (Q too low) to permit adequate coupling between the grid tank circuit and the preceding driver stage.

It may prove necessary to step up the driver output voltage to obtain sufficient r.f. grid voltage for the doubler; this can be done by tapping the driver plate on its tank circuit, when capacity coupling is used, or by similar tapping down or the use of a higher C/L ratio in the driver plate tank when the stages are link-coupled (§ 4-6).

Tubes for frequency multiplication — There is no essential difference between tubes of various characteristics in their performance as frequency doublers. Tubes having high amplification factors will require somewhat less bias for equivalent operation but the grid driving power needed is almost independent of the μ , assuming tubes of otherwise similar construction and characteristics. Pentodes and tetrodes will, as in normal amplifier operation, require less driving power than triodes for efficient doubling, although more power will be needed than for straight amplification.

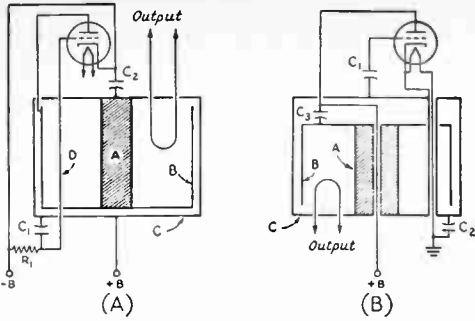


Fig. 428 — High- Q "pot"-type lumped-constant tank circuit as used in v.h.f. oscillators. The tank, shown in cross-section, is made of concentric closed cylinders.

4-12 Very-High-Frequency Oscillators

High- Q circuits with lumped constants — To obtain reasonably high effective Q when a low resistance is connected across the tank circuit, it is necessary to use a high C/L ratio and a tank of inherently high Q (§ 2-10). At low frequencies the inherent Q of any well-designed circuit will be high enough so that it may be neglected in comparison to the effective Q when loaded, so that no special precautions have to be taken with respect to the resistance of coils and condensers. At the very-high frequencies these internal resistances are too large to be ignored, however.

Reduction of the L/C ratio will not increase the effective Q unless the internal resistance of the tank can be made very small. This resistance can be reduced by use of large conducting surfaces and elimination of radiation. In such cases special lumped-constant tank circuits (§ 2-12) are used. The oscillator shown in Fig. 428-A uses a "pot"-type tank in the tickler circuit (§ 3-7), with the feed-back coil in the grid circuit: this inductance is the wire D in the diagram. Output is taken from the tank by means of a hairpin coupling loop.

Fig. 428-B corresponds to the shunt-fed Hartley circuit. Such a tank also may be used in the ultradion circuit. A variable condenser may be connected across the tank for tuning, although the Q may be reduced if a considerable portion of the tank r.f. current flows through it.

Linear Circuits — A quarter-wave or half-wave line, either of the parallel-conductor open type or of the coaxial type, is equivalent to a resonant circuit (§ 2-12) and can be used as the tank circuit (§ 3-7) in an oscillator.

The resonant line is usually constructed of thin-walled copper tubing, rather than wire, since this reduces resistance and provides a mechanically stable circuit, particularly at the lower frequencies. At frequencies above 100 Mc. flat copper strip conductor of equivalent cross-section may be used for parallel-line circuits with comparable efficiency. Frequency can be changed by moving a shorting bar or condenser to change the effective line length,

or by reducing its length and loading it to resonance by connecting a low-capacity variable condenser across the open end of the line. The added capacity makes it necessary to shorten the line considerably for a given frequency. This, together with the additional loss in the condenser, causes a decrease in Q . These effects will be less if the condenser is connected down on the line. Tapping down also gives greater bandwidth effect (§ 7-7).

At very high frequencies an adequate ground connection for the cathode circuit becomes a problem because of the inductance of the cathode lead. Special tubes are available

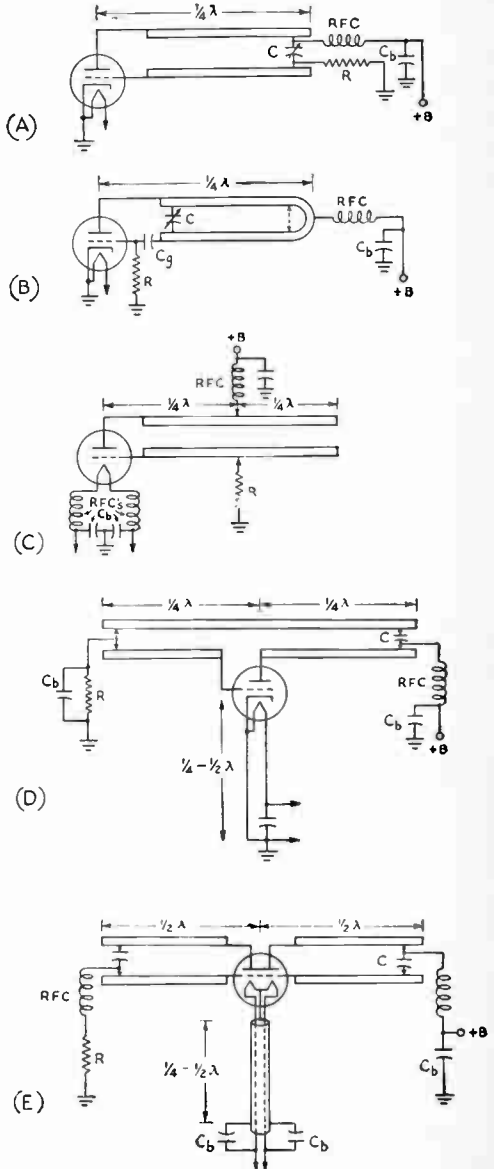


Fig. 429 — Typical single-tube parallel-line oscillators. Constants and applications are discussed in the text.

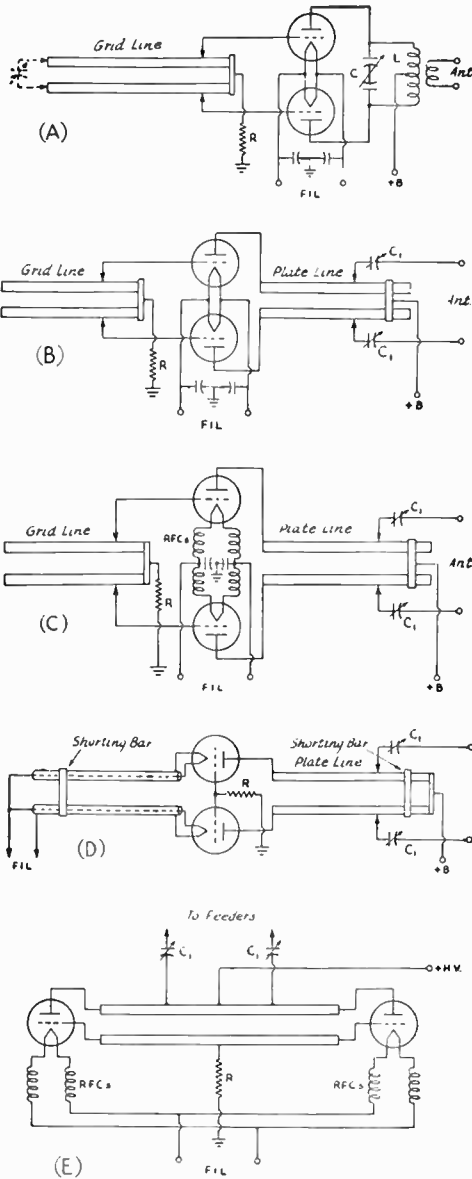


Fig. 430 - Push-pull parallel-line oscillator circuits.

with two or three cathode leads (§ 3-6) connected in parallel, these reduce the effective inductance. With ordinary tubes, coils may be inserted in the filament circuit to compensate for the effects of the internal inductance. The effective length of the filament circuit should be one-half wavelength, to bring the cathode filament to the same potential as the shorted ends of the tank lines. The added inductance required must be determined by experiment, the coils being adjusted for optimum stability and power output.

Another method is to use a tuned line in the filament circuit, adjusting its length so that the electrical length of the line plus that of the

filament is one-half wavelength. A convenient arrangement is the use of a coaxial (or trough) line with an initial length of about $\frac{3}{4}$ wavelength. A shorting disc in the form of a movable plunger equipped with an extension handle may be provided for ease of adjustment. With filament-type tubes one such line will be required for each filament lead. In the case of cathode-type tubes only one line is necessary, the cathode and one side of the filament being connected to the outer conductor and the other filament connection being made by an insulated lead running through a hollow-tubing inner conductor. The return lead should be by-passed where it emerges from the line.

The antenna or other load may be connected through blocking condensers direct to the line (the correct point being determined experimentally). Alternatively, a hair-pin coupling link or, in the case of an oscillator-amplifier system, direct inductive coupling to the grid line of the amplifier may be used.

For highest-frequency operation separate lines must be used for each electrode — grid, plate and cathode. This places all of the interelectrode capacities in series, reducing the loading effect. Still higher frequencies can be reached by using double-lead tubes (Fig. 429-E), in which case the leads form an integral part of the line and the interelectrode capacities are divided between the two quarter-wave sections.

Parallel-line oscillators — Typical parallel-line oscillator circuits are shown in Fig. 429. In A, a shunting condenser (which may be either a fixed blocking condenser or a small variable which will provide a limited tuning range) is used to bridge the line at the voltage node; the frequency can also be changed by sliding the shunting condenser along the line.

The circuit at B eliminates the need for a blocking condenser at the voltage node, where the r.f. current reaches its maximum value. An r.f. choke may be inserted between the grid and the associated grid resistor, *R*. This circuit also can be resonated either by a variable condenser, *C*, or by a sliding bar as indicated by the dashed line.

Fig. 429-C uses a half-wave open-ended line. The grid and plate feed connections are made at nodal points on the line. As indicated on the diagram, these do not occur at the physical center of the line because of the loading effect of the tube. In practice, the position of the taps, as well as the over-all length of the line, are adjusted to obtain maximum grid current. Using this circuit, a 955 acorn or a 9002 can be made to oscillate up to 600 or 700 Mc.

Fig. 429-D is a variation of the above preferable for use with tubes having grid and plate terminals at opposite ends of the envelope. The circuit of Fig. 429-E is most useful with double-lead tubes. To attain high output at the maximum operating frequency, the desirable arrangement is to use two or more double-lead tubes, each in a circuit such as this, with the lines connected end to end.

Push-pull parallel-line oscillators — It is often advantageous to use push-pull oscillator circuits at the very-high frequencies, not only as a means to secure more power output but also for better circuit symmetry. In addition, the interelectrode capacities of the push-pull tubes are in series across the point of connection to the tank circuit, hence have less capacity-loading effect than is experienced with a single tube.

Fig. 430 shows typical push-pull circuits of this type. Figs. 430-A, -B and -C all employ the same circuit — the t.p.t.g. type (§ 3-7). The grid line is usually operated as the frequency-controlling circuit, since it is not associated with the load and hence its Q can be kept high. The same adjustment considerations apply as in the case of single-tube oscillators. Grid taps in particular should be tapped down as far as possible, to improve the frequency stability.

In Fig. 430-A, a conventional coil-and-condenser tank is used in the plate circuit where the lower Q does not have so great an effect on frequency stability. For maximum efficiency the use of a linear output circuit is desirable at the higher frequencies, however. This is shown at B, and at C with isolating r.f. chokes in the filament circuit.

Fig. 430-D shows a push-pull oscillator having tuned plate and cathode lines, the cathode circuit being tuned with a quarter-wave line which controls excitation and, to some extent, tuning. The grids are connected together and grounded through the grid leak, R_1 ; ordinarily no by-pass condenser is needed across R_1 . This circuit gives good power output at very-high frequencies, but is not especially stable unless the plates are tapped down on the plate tank circuit to avoid too great a reduction in Q . Tapping on the cathode line is not feasible for mechanical reasons. With ordinary tubes this oscillator is capable of higher-frequency operation than the conventional t.g.t.p. type, and it has been found particularly useful on 224 Mc.

The symmetrical circuit at E is preferable above 200 Mc. Coaxial or equivalent lines may be used instead of r.f. chokes in the filament circuits for ultrahigh-frequency operation. With this modification, and (assuming the use of double-lead tubes) by the addition of quarter-wave sections at each end, this circuit may be considered equivalent to the center section of a double linear oscillator as discussed in connection with Fig. 429-E.

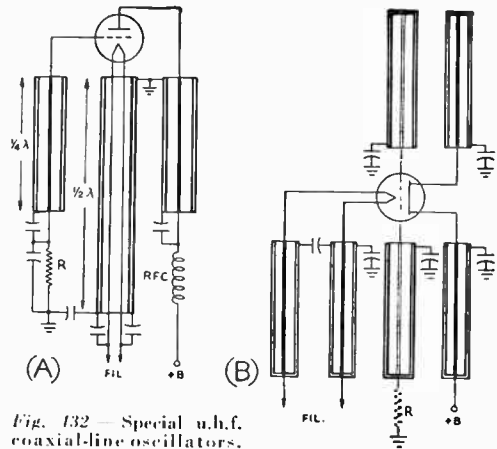


Fig. 432 — Special u.h.f. coaxial-line oscillators.

Coaxial-line circuits — At frequencies in the neighborhood of 300 Mc. the radiation loss (§ 2-12) from open lines greatly reduces the Q , because the conductor spacing unavoidably becomes an appreciable fraction of a wavelength. Consequently, these frequencies and higher coaxial lines, in which the field is confined inside the line so that radiation is negligible, are used. A further advantage is that the outside of the line is "cold"; that is, no r.f. potentials develop between points on the outer surface. While the coaxial line is also advantageous at lower frequencies, it is more complicated to construct and adjust than parallel lines.

For ease of construction, the coaxial line sometimes is modified into a "trough," in which the cross-section of the outer conductor is in the shape of a square U, one side being left open for tapping and adjustment of the inner conductor. Some radiation takes place with this type of construction, although not so much as with open lines.

The conventional coaxial-line oscillator circuits shown in Fig. 431 illustrate the application of two basic circuits — the Hartley and the t.g.t.p. — to both cathode-type and filamentary tubes. The tube loads the line, as previously described; hence the actual length is always shorter than a quarter wavelength. The length can be adjusted by a short-circuiting sliding plunger, a close-fitting low-resistance contact being necessary to avoid losses. The inner conductor may also have a short tight-


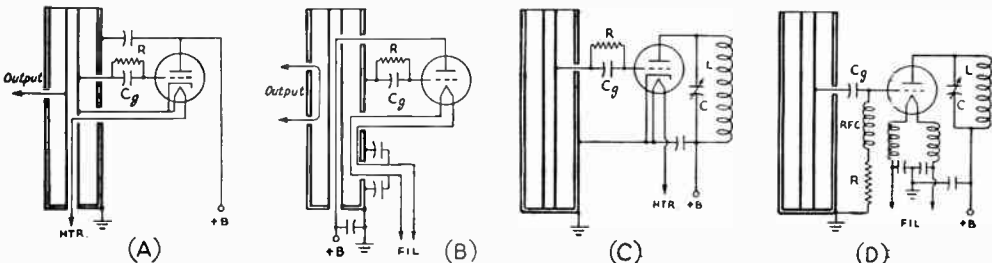


Fig. 431 — Single-tube v.h.f. coaxial-line oscillators. A and B use Hartley circuits; C and D are t.g.t.p. equivalents.

Fig. 433 — Push-pull coaxial-line oscillators.

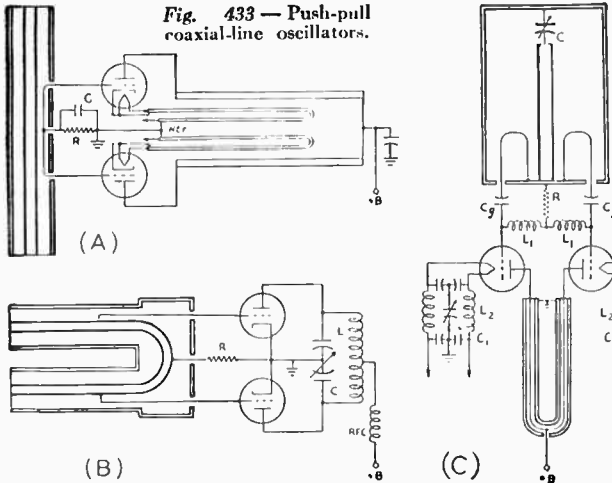

the ends of the outer conductor in each line constitute one plate of the condenser; a grounded metal sheet serves as the other plate.

Push-pull coaxial-line oscillators—The push-pull circuits of Fig. 433 employ the same basic elements as the arrangements previously described.

At A, a half-wave open-ended line is used in the grid circuit, the grids of the tubes being "tapped" down on the line by coupling them inductively through a small balanced loop running inside the outer conductor. A conventional parallel line is used in the plate circuit, with the cathodes balanced to ground by means of closed half-wave lines.

fitting extension tube which is slid in or out to change the effective conductor length.

The t.g.t.p. circuits are somewhat easier to adjust and load as well as to construct, but are not as satisfactory from the standpoint of frequency stability because of reaction on the frequency-controlling grid line by the tuning of the output circuit. The grid tap should be as far down on the line as will permit reliable oscillation under load. Under some conditions the addition of a small adjustable feed-back capacity between grid and plate not only permits a lower tap location but also increases the upper frequency limit obtainable by advancing the phase of the grid excitation to compensate partially for transit-time lag in the tube.

In the Hartley circuit at A, an output tap is provided on the inner conductor. At B inductive output coupling by means of a half-turn "hairpin" is shown; loading can be changed to some extent by varying its position.

Fig. 432 shows two types of coaxial-line oscillator circuits designed particularly for operation near the upper frequency limits for negative-grid tubes. The circuit at A, with quarter-wave grid and plate lines and a half-wave filament line, is convenient for use with single-lead tubes such as the 955 and 316-A. With the three lines arranged in the form of a triangle, so that their inner conductors attach directly to the tube terminals for minimum lead length, this oscillator will function satisfactorily up to 700-800 Mc.

The circuit of Fig. 432-B is designed to take maximum advantage of the u.h.f. capabilities of double-lead and ring-electrode tube types. Interelectrode capacities are divided between each pair of grid and plate lines, and separate parallel-resonant filament lines complete the isolation. Frequencies as high as 1500-1700 Mc. have been attained with this arrangement.

The by-pass condensers shown in the two circuits of Fig. 432 are made of copper plates insulated by sheet mica. Flanges soldered to

The cathode lines may be small-diameter copper tubing, folded to conserve space, through which rubber-insulated wire is run for the return circuit. These lines may be shielded from the plate line by running them underneath the chassis or separated by a shielding partition.

A folded half-wave grid line is used at B. The copper-tubing inner conductor is bent into the shape of a U. The outer conductor may be either a square-section double trough of sheet copper or two short sections of pipe soldered to a rectangular box of sheet copper which forms the "closed" end. Where even more compact construction is required, the dimensions of the grid line may be still further reduced by using sections of folded coaxial line (§ 2-12). A conventional coil-and-condenser output circuit is shown; at the comparatively low frequencies where this type of construction would be advantageous in the interest of compactness, such an output circuit should be satisfactory.

The arrangement at C has certain modifications which make it particularly suitable for use with higher-powered tubes. The quarter-wave capacity-loaded coaxial line in the grid circuit is of relatively large dimensions and consequently has high Q. Coupling to the tube grids, which is made very loose to preserve the Q of the line, is by means of twin hairpin loops. The inductance of the shunt choke coils, L_1 , is adjusted for maximum grid current.

To minimize radiation loss and preserve circuit symmetry, a coaxial line is used in the plate tank circuit. If desired this line may be tuned by a balanced split-stator condenser of the type which has the rotor connection at the center, connected across the plate terminals.

Parallel resonant circuits in the filament leads, tuned to resonance at the operating frequency by the variable condensers, C_1 , isolate the filament from ground. The fixed by-pass condensers must have low reactance at the operating frequency. The filament coils, which are in parallel for r.f., are of copper tubing.

Radiotelephony

5-1 Modulation

The carrier — The steady radio-frequency power generated by transmitting circuits cannot alone result in the transmission of an intelligible message to a receiving point. The continuous wave from the transmitter itself serves only as a "carrier" for the message; the intelligence is conveyed by *modulation* (a change) of the carrier. In radiotelephony, this modulation reproduces electrically the sounds it is intended to convey in a form which can be correctly interpreted or demodulated at the receiving end.

Sound and alternating currents — Sounds are caused by vibrations of air particles. The pitch of the sound depends upon the rate of vibration; the more rapid the vibration, the higher the pitch. Most sounds consist of complex combinations of vibrations of differing rates or frequencies; the human voice, for instance, generates frequencies from about 100 cycles per second to several thousand per second. The problem of transmitting speech by radio, therefore, is one of varying the r.f. carrier in a way which corresponds to the air-particle vibrations. The first step in doing this is to change the sound vibrations into alternating electrical currents of the same frequency and relative intensity; the electromechanical device which achieves this translation is the *microphone*. These audio-frequency currents then may be amplified and used to vary or modulate the normally steady r.f. output of the transmitter.

Methods of modulation — The carrier may be made to vary in accordance with the speech current by using the current to change the phase (§ 2-7), frequency or amplitude of the carrier. *Amplitude modulation* of a constant-frequency carrier is by far the most common system, and is used exclusively on all frequencies below the very-high-frequency region (§ 2-7). *Frequency modulation* of a constant-amplitude carrier, which has special characteristics which make its use desirable under certain conditions, is used to a considerable extent on the very-high frequencies. *Phase modulation*, which is closely related to frequency modulation, has had little or no direct application in practical communication.

Other specialized varieties of modulation, developed for other applications of radio transmission, have been proposed for voice communication. Thus far none of these has achieved practical utilization, however.

5-2 Amplitude Modulation

Carrier requirements — For proper amplitude modulation, the carrier should be completely free from inherent amplitude variations such as might be caused by insufficient filtering of a rectified-a.c. power supply (§ 8-4). It is also essential that the carrier frequency be entirely unaffected by the application of modulation. If modulating the amplitude of the carrier also causes a change in the carrier frequency the signal wobbles back and forth with the modulation, introducing distortion and widening the channel taken by the signal. This causes unnecessary interference to other transmissions. In practice, this undesirable frequency modulation is prevented by applying the modulation to an r.f. amplifier stage which is isolated from the frequency-controlling oscillator by a "buffer" amplifier. Amplitude modulation of an oscillator almost always is accompanied by frequency modulation. Under existing regulations it is permitted, therefore, only on frequencies above 112 Mc., because the

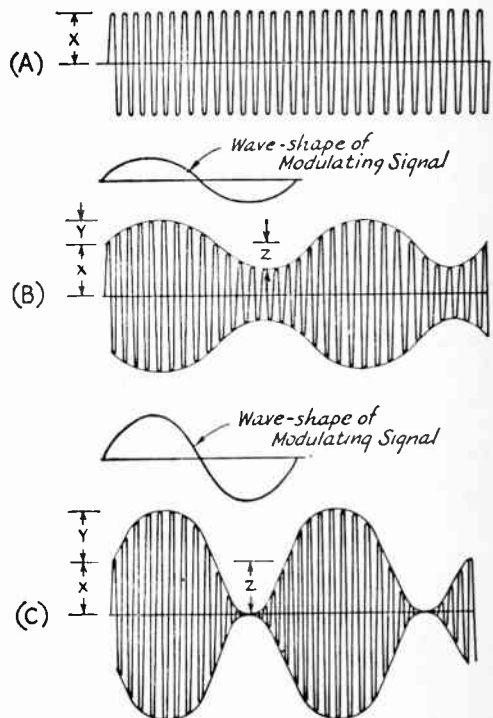


Fig. 501 — Graphical representation of (A) carrier unmodulated, (B) modulated 50%, (C) modulated 100%.

problem of interference is less acute in this region than on lower frequencies.

Percentage of modulation — In the amplitude-modulation system the audible output at the receiver depends entirely upon the amount of variation — termed *depth of modulation* — in the carrier wave, and not upon the strength of the carrier alone. It is desirable therefore to obtain the largest permissible variations in the carrier wave. This condition is reached when the carrier amplitude during modulation is at times reduced to zero and at other times increased to twice its unmodulated value. Such a wave is said to be *fully modulated*, or *100 per cent modulated*. Any desired degree of modulation can be expressed as a percentage, using the unmodulated carrier as a base. Fig. 501 shows, at A, an unmodulated carrier wave; at B, the same wave modulated 50 per cent, and at C, the wave with 100 per cent modulation, using a sine-wave (§ 2-7) modulating signal. The outline of the modulated r.f. wave is called the *modulation envelope*.

The percentage modulation can be found by dividing either *Y* or *Z* by *X* and multiplying the result by 100. If the modulating signal is not symmetrical, the larger of the two (*Y* or *Z*) should be used.

Power in modulated wave — The amplitude values correspond to current or voltage, so that the drawings may be taken to represent instantaneous values of either. Since power varies as the square of either the current or voltage (so long as the resistance in the circuit is unchanged), at the peak of the modulation up-swing the instantaneous power in the wave of Fig. 501-C is four times the unmodulated carrier power. At the peak of the down-swing the power is zero, since the amplitude is zero. With a sine-wave modulating signal, the *average* power in a 100 per cent modulated wave is one and one-half times the unmodulated carrier power; that is, the power output of the transmitter increases 50 per cent with 100 per cent modulation.

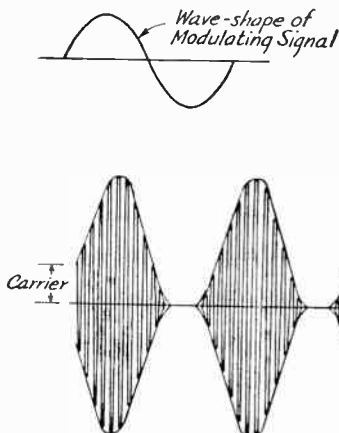


Fig. 502 — An overmodulated r.f. carrier wave.

Linearity — Up to the limit of 100 per cent modulation, the amplitude of the carrier should follow faithfully the amplitude variations of the modulating signal. When the modulated r.f. amplifier is incapable of meeting this condition, it is said to be *non-linear*. The amplifier may not, for instance, be capable of quadrupling its power output at the peak of 100 per cent modulation. A non-linear modulated amplifier causes distortion of the modulation envelope.

Modulation characteristic — A graph showing the relationship between r.f. amplitude and instantaneous modulating voltage is called the *modulation characteristic* of the modulated amplifier. This graph should be a straight line (linear) between the limits of zero and twice carrier amplitude. Curvature of the line between these limits indicates non-linearity in the amplifier.

Modulation capability — The *modulation capability* of the transmitter is the maximum percentage of modulation that is possible without objectionable distortion from non-linearity. The maximum capability is, of course, 100 per cent. The modulation capability should be as high as possible, so that the most effective signal can be transmitted for a given carrier power.

Overmodulation — If the carrier is modulated more than 100 per cent, a condition such as is shown in Fig. 502 occurs. Not only does the peak amplitude exceed twice the carrier amplitude, but actually there may be a considerable period during which the output is entirely cut off. The modulated wave is therefore distorted (§ 3-3), with the result that harmonics of the audio modulating frequency appear. The carrier should never be modulated more than 100 per cent.

Sidebands — The combining of the audio frequency with the r.f. carrier is essentially a heterodyne process, and therefore gives rise to beat frequencies equal to the sum and difference of the a.f. and r.f. frequencies involved (§ 2-13). Therefore, for each audio frequency appearing in the modulating signal, two new radio frequencies appear, one equal to the carrier frequency plus the audio frequency, the other equal to the carrier minus the audio frequency. These new frequencies are called *side frequencies*, since they appear on each side of the carrier, and the groups of side frequencies representing a band or group of modulation frequencies are called *sidebands*. Hence a modulated signal occupies a group of radio frequencies, or *channel*, rather than a single frequency as in the case of the unmodulated carrier. The *channel width* is twice the highest modulation frequency.

To accommodate the largest number of transmitters in a given part of the r.f. spectrum it is apparent that the channel width should be as small as possible. On the other hand it is necessary, for speech transmission of reasonably good quality, to use modulating

frequencies up to a minimum of about 3000 or 4000 cycles. This calls for a channel width of 6 to 8 kilocycles.

Spurious sidebands — Besides the normal sidebands required by speech frequencies, unwanted sidebands may be generated by the transmitter. These usually lie outside the normally required channel, and hence cause it to be wider without increasing the useful modulation. By increasing the channel width, these spurious sidebands cause unnecessary interference to other transmitters. The quality of transmission also is adversely affected when spurious sidebands are generated.

The chief causes of spurious sidebands are harmonic distortion in the audio system, over-modulation, unnecessary frequency modulation, and lack of linearity in the modulated r.f. system.

Types of amplitude modulation — The most widely used type of amplitude-modulation system is that in which the modulating signal is applied in the plate circuit of a radio-frequency power amplifier (*plate modulation*). In a second type the audio signal is applied to a control-grid (*grid-bias modulation*). A third system, involving variation of both plate and grid voltages, is called *cathode modulation*.

5-3 Plate Modulation

Transformer coupling — In Fig. 503 is shown the most widely used system of plate modulation. A balanced (push-pull Class-A, Class-AB or Class-B) modulator is transformer-coupled to the plate circuit of the modulated r.f. amplifier. The audio-frequency power generated in the modulator plate circuit is combined with the d.c. power in the modulated-amplifier plate circuit by transfer through the coupling transformer, *T*. For 100 per cent modulation the audio-frequency output of the modulator and the turns ratio of the coupling transformer must be such that the voltage at the plate of the modulated amplifier varies between zero and twice the d.c. operating plate voltage, thus causing corresponding variations in the amplitude of the r.f. output.

Modulator power — The average power output of the modulated stage must increase 50 per cent for 100 per cent modulation (§ 5-2), so that the modulator must supply to the modulated r.f. stage audio power equal to 50 per cent of the d.c. plate input. For example, if the d.c. plate power input to the r.f. stage is 100 watts, the sine-wave audio power output of the modulator must be 50 watts.

Modulating impedance; linearity — The *modulating impedance*, or load resistance presented to the modulator by the modulated r.f. amplifier, is equal to

$$\frac{E_b}{I_p} \times 1000$$

where E_b is the d.c. plate voltage and I_p the d.c. plate current in milliamperes, both measured without modulation.

Since the power output of the r.f. amplifier must vary as the square of the plate voltage (the r.f. voltage must be proportional to the applied plate voltage) in order for the modulation to be linear, the amplifier must operate under Class-C conditions (§ 3-4). The linearity then depends upon having sufficient grid excitation and proper bias, and upon the adjustment of circuit constants to the proper values (§ 4-8).

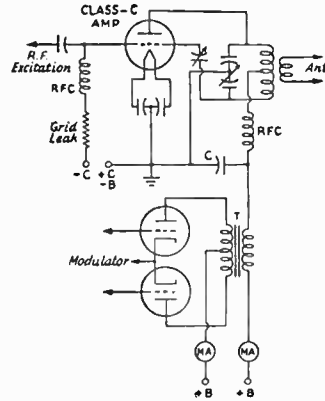


Fig. 503 — Plate modulation of a Class-C r.f. amplifier. The r.f. plate by-pass condenser, *C*, in the amplifier stage should have high reactance at audio frequencies. A capacity of 0.002 μfd. or less usually is satisfactory.

Power in speech waves — The complex waveform of a speech sound translated into alternating current does not contain as much power, on the average, as there is in a pure tone or sine wave of the same peak (§ 2-7) amplitude. That is, with speech waveforms the ratio of peak to average amplitude is higher than in the sine wave. For this reason, the previous statement that the power output of the transmitter increases 50 per cent with 100 per cent modulation, while true for tone modulation, is not true for speech. On the average, speech waveforms will contain only about half as much power as a sine wave, both having the same peak amplitude. The average power output of the transmitter therefore increases only about 25 per cent with 100 per cent speech modulation. However, the *instantaneous* power output must quadruple on the peak of 100 per cent modulation (§ 5-2) regardless of the modulating waveform. Therefore, the peak output power capacity of the transmitter must be the same for any type of modulating signal.

Adjustment of plate-modulated amplifiers — The general operating conditions for Class-C operation have been described (§ 3-4, 4-8). The grid bias and grid current required for plate modulation usually are given in the operating data supplied by the tube manufacturer; in general, the bias should be such as to give an operating angle (§ 4-8) of about 120 degrees at carrier plate voltage, and the excitation should be sufficient to maintain the plate efficiency constant when the plate volt-

age is varied over the range from zero to twice the d.c. plate voltage applied to the amplifier. For best linearity, the grid bias should be obtained partly from a fixed source of about the cut-off value, supplemented by grid-leak bias to supply the remainder of the required operating bias.

The maximum permissible d.c. plate power input for 100 per cent modulation is twice the sine-wave audio-frequency power output of the modulator. This input is obtained by varying the loading on the amplifier (keeping its tank circuit tuned to resonance) until the product of d.c. plate voltage and plate current is the desired power. The modulating impedance under these conditions will be the proper value for the modulator, if the proper output-transformer turns ratio (§ 2-9) is used.

Neutralization, when triodes are used, should be as nearly perfect as possible, since regeneration may cause non-linearity. The amplifier also should be free from parasitic oscillations (§ 4-10).

Although the *effective* value (§ 2-7) of power input increases with modulation, as described above, the *average* plate input to a plate-modulated amplifier does not change, since each increase in plate voltage and plate current is balanced by an equivalent decrease in voltage and current. Consequently, the d.c. plate current to a properly modulated amplifier is always constant, with or without modulation.

Screen-grid amplifiers — Screen-grid tubes of the pentode or beam tetrode type can be used as Class-C plate-modulated amplifiers provided the modulation is applied to both the plate and screen grid. The method of feeding the screen grid with the necessary d.c. and modulation voltage is shown in Fig. 504. The dropping resistor, *R*, should be of the proper value to apply normal d.c. voltage to the screen under steady carrier conditions. Its value can be calculated by taking the difference between plate and screen voltages and dividing it by the rated screen current.

The modulating impedance is found by dividing the d.c. plate voltage by the sum of the plate and screen currents. The plate voltage

multiplied by the sum of the two currents is the power-input figure which is used as the basis for determining the audio power required from the modulator.

Choke coupling — In Fig. 505 is shown the circuit of the choke-coupled system of plate modulation. The plate power for the modulator tube and modulated amplifier is furnished from a common source through the modulation choke, *L*, which has high impedance for audio frequencies. The modulator operates as a power amplifier with the plate circuit of the r.f. amplifier as its load, the audio output of the modulator being superimposed on the d.c. power supplied to the amplifier. For 100 per cent modulation, the audio voltage applied to the r.f. amplifier plate circuit across the choke, *L*, must have a peak value equal to the d.c. voltage on the modulated amplifier. To obtain this without distortion the r.f. amplifier must be operated at a d.c. plate voltage less than the

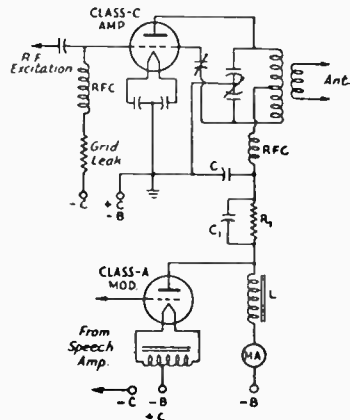


Fig. 505 — Choke-coupled plate modulation.

modulator plate voltage, the extent of the voltage difference being determined by the type of modulator tube used. The necessary drop in voltage is provided by the resistor, *R*₁, which is by-passed for audio frequencies by the by-pass condenser, *C*₁.

This type of modulation seldom is used except in very low-power portable sets, because a single-tube Class-A (§ 3-4) modulator is required. The output of a Class-A modulator is very low compared to that obtainable from a pair of tubes of the same size operated Class B, hence only a small amount of r.f. power can be modulated.

Absorption modulation — Absorption or "loss" modulation, in its basic form the oldest and simplest method of all, recently has been revived for wide-band modulation (such as television) at ultrahigh frequencies. In the system shown in Fig. 506, the modulating tubes are connected to the antenna feed line through a quarter-wave stub line, located a quarter-wavelength from the transmitter tank circuit. With no modulation (i.e., no conduc-

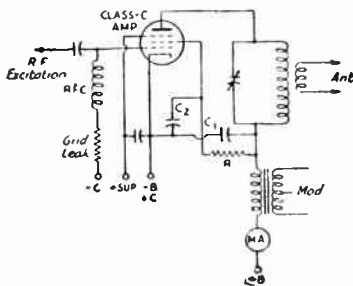


Fig. 504 — Plate and screen modulation of a Class-C r.f. amplifier using a pentode tube. The plate and screen r.f. by-pass condensers, *C*₁ and *C*₂, should have high reactance at all audio frequencies (0.002 μ fd. or less).

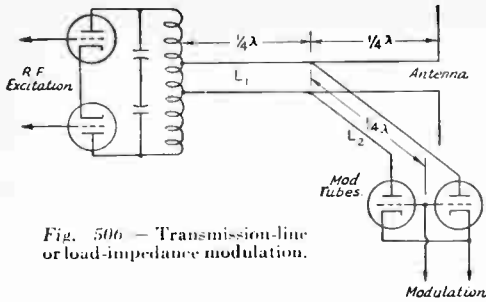


Fig. 506 — Transmission-line or load-impedance modulation.

tion through the modulating tubes) the stub appears as a short circuit across the line and little or no power reaches the antenna. When modulating voltage is applied to the grids of the modulator tubes, however, their conductance serves to increase the effective impedance of the quarter-wave shunt, permitting a proportionate amount of energy to reach the antenna. At maximum modulation the stub approaches an open circuit, allowing maximum r.f. output to the antenna.

§ 5-4 Grid-Bias Modulation

Circuit — Fig. 507 is the diagram of a typical arrangement for grid-bias modulation. In this system, the secondary of an audio-frequency output transformer, the primary of which is connected in the plate circuit of the modulator tube, is connected in series with the grid-bias supply for the modulated amplifier. The audio voltage thus introduced varies the grid bias, and thus the power output of the r.f. stage, when suitable operating conditions are chosen. The r.f. stage is operated as a Class-C amplifier, with the d.c. grid bias considerably beyond cut-off.

Operating principles — In this system the plate voltage is constant, and the increase in power output with modulation is obtained by making the plate current and plate efficiency vary with the modulating signal. For 100 per cent modulation, both plate current and efficiency must, at the peak of the modulation upswing, be twice their carrier values, so that the peak power will be four times the carrier power. Since the peak efficiency in practicable circuits is of the order of 70 to 80 per cent, the carrier efficiency ordinarily cannot exceed about 35 to 40 per cent. For a given r.f. tube, the carrier output is about one-fourth the power obtainable from the same tube plate-modulated. Grid bias, r.f. excitation, plate loading and the audio voltage in series with the grid must be adjusted to give a linear modulation characteristic.

Modulator power — Since the increase in average carrier power with modulation is secured by varying the plate efficiency and d.c. plate input of the amplifier, the modulator need supply only such power losses as may be occasioned by connecting it in the grid circuit. These are quite small, hence a modulator capable of only a few watts output will

suffice for transmitters of considerable power. Since the load on the modulator varies over the a.f. cycle as the rectified grid current of the modulated amplifier changes, the modulator should have good voltage regulation (§ 5-6).

Grid-bias source — The change in bias voltage with modulation causes the rectified grid current of the amplifier also to vary, the r.f. excitation being fixed. If the bias source has appreciable resistance, the change in grid current also will cause a change in bias in a direction opposite to that caused by the modulation. It is necessary, therefore, to use a grid-bias source having low resistance, so that these bias variations will be negligible. Battery bias is satisfactory. If a rectified a.c. bias supply is used, the type having regulated output (§ 8-9) should be chosen. Grid-leak bias for a grid-modulated amplifier is unsatisfactory, and its use should not be attempted.

Driver regulation — The load on the driving stage varies with modulation, and a linear modulation characteristic may not be obtained if the r.f. voltage from the driver does not stay constant with changes in load. Driver regulation (ability to maintain constant output voltage with changes in load) may be improved by using a driving stage having two or three times the power output necessary for excitation of the amplifier (this is somewhat less than the power required for ordinary Class-C operation), and by dissipating the extra power in a constant load such as a resistor. The load variations are thereby reduced in proportion to the total load.

Adjustment of grid-bias modulated amplifiers — This type of amplifier should be adjusted with the aid of an oscilloscope, to obtain optimum operating conditions. The oscilloscope should be connected as described in § 5-10, the wedge pattern being preferable. A tone source for modulating the transmitter will be convenient. The fixed grid bias should be two or three times the cut-off value (§ 3-2). The d.c. input to the amplifier, assuming 33

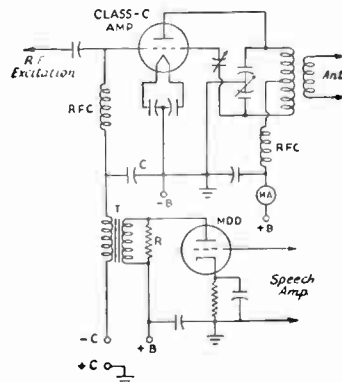


Fig. 507 — Grid-bias modulation of a Class-C amplifier. The r.f. grid by-pass condenser, C, should have high reactance at audio frequencies (0.002 μ f. or less).

per cent carrier efficiency, will be $1\frac{1}{2}$ times the plate dissipation rating of the tube or tubes used in the modulated stage. The plate current for this input (in milliamperes, $1000 P/E$, where P is the power and E the d.c. plate voltage) must be determined. Apply r.f. excitation

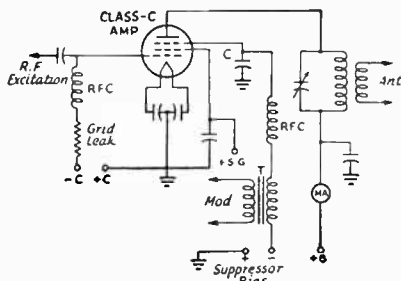


Fig. 508 — Suppressor-grid modulation of an r.f. amplifier using a pentode-type tube. The suppressor-grid r.f. by-pass condenser, C , should be $0.002 \mu\text{fd.}$ or less.

and, without modulation, adjust the plate loading to give the required plate current (keeping the plate tank circuit tuned to resonance). Next, apply modulation and increase the modulating signal until the modulation characteristic shows curvature (§ 5-10). This probably will occur well below 100 per cent modulation, indicating that the plate efficiency is too high. Increase the plate loading and reduce the excitation to maintain the same plate current; then apply modulation and check the characteristic again. Continue this process until the characteristic is linear from the axis to twice the carrier amplitude. It is advantageous to use the maximum permissible plate voltage on the tube, since it is usually easier to obtain a more linear characteristic with high plate voltage and low current (carrier conditions) than with relatively low plate voltage and high plate current.

The amplifier can be adjusted without an oscilloscope by determining the plate current as described above, then setting the bias to the cut-off value (or slightly beyond) for the d.c. plate voltage used and applying maximum excitation. Adjust the plate loading, keeping the tank circuit at resonance, until the amplifier draws twice the carrier plate current, and note the antenna current. Decrease the excitation until the output and plate current just start to drop. Then increase the bias, leaving the excitation and plate loading unchanged, until the plate current drops to the proper carrier value. The antenna current should be just half the previous value; if it is larger, try somewhat more loading and less excitation; if smaller, less loading and more excitation. Repeat until the antenna current drops to half its maximum value when the plate current is biased down to the carrier value. Under these conditions the amplifier should modulate properly, provided the plate supply has good voltage regulation (§ 8-1) so that the

plate voltage is practically the same at both values of plate current during the initial testing. The d.c. plate current should be substantially constant with or without modulation (§ 5-3).

Suppressor modulation — The circuit arrangement for suppressor-grid modulation of a pentode tube is shown in Fig. 508. The operating principles are the same as for grid-bias modulation. However, the r.f. excitation and modulating signals are applied to separate grids, which gives the system a simpler operating technique since best adjustment for proper excitation requirements and proper modulating circuit requirements are more or less independent. The carrier plate efficiency is approximately the same as for grid-bias modulation, and the modulator power requirements are similarly small. With tubes having suitable suppressor-grid characteristics, linear modulation up to practically 100 per cent can be obtained with negligible distortion.

The method of adjustment is essentially the same as that described in the preceding paragraph. Apply normal excitation and bias to the control grid and, with the suppressor bias at zero or the positive value recommended for c.w. telegraph operation with the particular tube used, adjust the plate loading to obtain twice the carrier plate current (on the basis of 33 per cent carrier efficiency). Then apply sufficient negative bias to the suppressor to bring the plate current to the carrier value, leaving the loading unchanged. Simultaneously, the antenna current also should drop to half its maximum value. The amplifier is then ready for modulation. Should the plate current not follow the antenna current in the same proportion when the suppressor bias is made negative, the loading and excitation should be readjusted to make them coincide.

§ 5-5 Cathode Modulation

Circuit — The fundamental circuit for cathode or "center-tap" modulation is shown in Fig. 509. This type of modulation is a com-

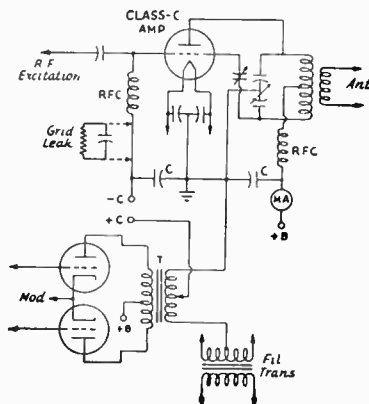


Fig. 509 — Cathode modulation of a Class-C r.f. amplifier. The grid and plate r.f. by-pass condensers, C , should be $0.002 \mu\text{fd.}$ or less (for high a.f. reactance).

bination of the plate and grid-bias methods, and permits a carrier efficiency midway between the two. The audio power is introduced in the cathode circuit, and both grid bias and plate voltage vary during modulation.

The cathode circuit of the modulated stage must be independent of other stages in the transmitter; that is, when filament-type tubes are modulated they must be supplied from a separate filament transformer. The filament by-pass condensers should not be larger than about 0.002 μ d., to avoid by-passing the audio-frequency modulation.

Operating principles — Because part of the modulation is by the grid-bias method, the plate efficiency of the modulated amplifier must vary during modulation. The carrier efficiency therefore must be lower than the efficiency at the modulation peak. The required reduction in carrier efficiency depends upon the proportion of grid modulation to plate modulation; the higher the percentage of plate modulation, the higher the permissible carrier efficiency, and vice versa. The audio power required from the modulator also varies with the percentage of plate modulation, being greater as this percentage is increased.

The way in which the various quantities vary is illustrated by the curves of Fig. 510. In these curves the performance of the cathode-modulated r.f. amplifier is plotted in terms of the tube ratings for plate-modulated telephony, with the percentage of plate modulation as a base. As the percentage of plate modulation is decreased, it is assumed that the grid-bias modulation is increased to make the over-all percentage of modulation reach 100 per cent. The limiting condition, 100 per cent plate modulation and no grid-bias modulation, is at the right (A); pure grid-bias modulation is represented by the left-hand ordinate (B and C).

As an example, assume that 40 per cent plate modulation is to be used. Then the modulated r.f. amplifier must be adjusted for a carrier plate efficiency of 56 per cent, the permissible plate input will be 65 per cent of the ratings of the same tube with pure plate modulation, the power output will be 48 per cent of the rated output of the tube with plate modulation, and the audio power required from the modulator will be 20 per cent of the d.c. input to the modulated amplifier.

Modulating impedance — The modulating impedance of a cathode-modulated amplifier is approximately equal to

$$m \frac{E_b}{I_b}$$

where m is the percentage of plate modulation expressed as a decimal, E_b is the plate voltage and I_b the plate current of the modulated r.f. amplifier. This figure for the modulating impedance is used in the same way as the corresponding figure for pure plate modulation, in

determining the proper modulator operating conditions (§ 5-6).

Conditions for linearity — R.f. excitation requirements for the cathode-modulated amplifier are midway between those for plate modulation and grid-bias modulation. More excitation is required as the percentage of plate modulation is increased. Grid bias should be considerably beyond cut-off; fixed bias from a supply having good voltage regulation (§ 8-9) is preferred, especially when the percentage of plate modulation is small and the amplifier is operating more nearly like a grid-bias modulated stage. At the higher percentages of plate modulation a combination of fixed and grid-leak bias can be used, since the variation in rectified grid current is smaller. The grid leak should be by-passed for audio frequencies. The percentage of grid modulation may be regulated by choice of a suitable tap on the modulation transformer secondary.

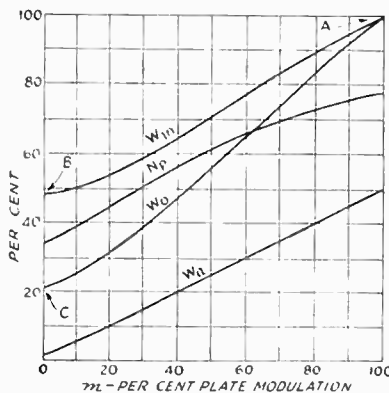


Fig. 510 — Cathode-modulation performance curves, in terms of percentage of plate modulation plotted against percentage of Class-C telephony tube ratings. W_{in} — D.c. plate input watts in terms of percentage of plate-modulation rating. W_o — Carrier output watts in per cent of plate-modulation rating (based on plate efficiency of 77.5%). W_a — Audio power in per cent of d.c. watts input. N_p — Plate efficiency of the amplifier in percentage.

Adjustment of cathode-modulated amplifiers — In most respects, the adjustment procedure is similar to that for grid-bias modulation (§ 5-4). The critical adjustments are those of antenna loading, grid bias, and excitation. The proportion of grid-bias to plate modulation will determine the operating conditions.

Adjustments should be made with the aid of an oscilloscope (§ 5-10). With proper antenna loading and excitation, the normal wedge-shaped pattern will be obtained at 100 per cent modulation. As in the case of grid-bias modulation, too-light antenna loading will cause flattening of the upward-peaks of modulation (indicating downward modulation), as also will too-high excitation (§ 5-10). The cathode current will be practically constant with or without modulation when the proper operating conditions have been established (§ 5-3).

§ 5-6 Class-B Modulators

Modulator tubes — In the case of plate modulation, the relatively large audio power needed (§ 5-3) practically dictates the use of a Class-B (§ 3-4) modulator, since the power can be obtained most economically with this type of amplifier. A typical circuit is given in Fig. 511. A pair of tubes must be chosen which is capable of delivering sine-wave audio power equal to half the d.c. input to the modulated Class-C amplifier. It is sometimes convenient to use tubes which will operate at the same plate voltage as that applied to the Class-C stage, since one power supply of adequate current capacity may then suffice for both stages. Available components do not always permit this, however, and better over-all performance and economy may result from the use of separate power supplies.

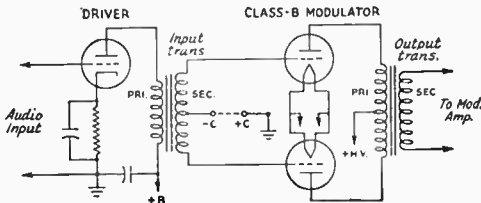


Fig. 511 — Class-B audio modulator and driver circuit.

Matching to load — In giving Class-B ratings on power tubes, manufacturers specify the plate-to-plate load impedance (§ 3-3) into which the tubes must operate to deliver the rated audio power output. This load impedance seldom is the same as the modulating impedance (§ 5-3) of the Class-C r.f. stage, so that a match must be brought about by adjusting the turns ratio of the coupling transformer. The required turns ratio, primary to secondary, is

$$\sqrt{\frac{Z_p}{Z_m}}$$

where Z_m is the Class-C modulating impedance and Z_p is the plate-to-plate load impedance specified for the Class-B tubes.

Commercial Class-B output transformers usually are rated to work between specified primary and secondary impedances and are designed for specific Class-B tubes. In such a case, the turns ratio can be found by substituting the given impedances in the formula above. Many transformers are provided with primary and secondary taps, so that various turns ratios can be obtained to meet the requirements of various tube combinations.

Driving power — Class-B amplifiers are driven into the grid-current region, so that power is consumed in the grid circuit (§ 3-3). The preceding stage (*driver*) must be capable of supplying this power at the required peak audio-frequency grid-to-grid voltage. Both of these quantities are given in the manufactur-

er's tube ratings. The grids of the Class-B tubes represent a variable load resistance over the audio-frequency cycle, since the grid current does not increase directly with the grid voltage. To prevent distortion, therefore, it is necessary to have a driving source which has good *regulation* — that is, which will maintain the waveform of the signal without distortion even though the load varies. This can be brought about by using a driver capable of delivering two or three times the actual power consumed by the Class-B grids, and by using an input coupling transformer having a turns ratio giving the largest step-down in the voltage between the driver plate or plates and the Class-B grids that will permit obtaining the specified grid-to-grid a.f. voltage.

Driver coupling — A Class-A or Class-AB (§ 3-4) driver is used to excite a Class-B stage. Tubes for the driver preferably should be triodes having low plate resistance, since these will have the best regulation. Having chosen a tube or tubes capable of ample power output from tube data sheets, the peak output voltage will be, approximately,

$$E_o = 1.4 \sqrt{PR}$$

where P is the power output and R the load resistance. The input transformer ratio, primary to secondary, will be

$$\frac{E_o}{E_g}$$

where E_o is as given above and E_g is the peak grid-to-grid voltage required by the modulator tubes.

Commercial transformers normally are designed for specific driver-modulator combinations, and usually are adjusted to give as good driver regulation as the conditions will permit.

Grid bias — Modern Class-B audio tubes are intended for operation without fixed bias. This lessens the variable grid-circuit loading effect and eliminates the need for a grid-bias supply.

When a grid-bias supply is required, it must have low internal resistance so that the flow of grid current with excitation of the Class-B tubes does not cause a continual shift in the actual grid bias and thus cause distortion. Batteries or a regulated bias supply (§ 8-9) should be used.

Plate supply — The plate supply for a Class-B modulator should be sufficiently well filtered (§ 8-3) to prevent hum modulation of the r.f. stage (§ 5-2). An additional requirement is that the output condenser of the supply should have low reactance (§ 2-8) at 100 cycles or less compared to the load into which each tube is working, which is one-fourth the plate-to-plate load resistance. A 1- μ fd. output condenser with a 1000-volt supply, or a 2- μ fd. condenser with a 2000-volt supply, usually will be satisfactory. With other plate voltages, condenser values should be in inverse proportion to the plate voltage.

Overexcitation — When a Class-B amplifier is overdriven in an attempt to secure more than the rated power, distortion in the output waveshape increases rapidly. The high-frequency harmonics which result from the distortion (§ 3-3) modulate the transmitter, producing spurious sidebands (§ 5-2) which readily can cause serious interference over a band of frequencies several times the channel width required for speech. This may happen even though the transmitter is not being overmodulated, as in the case where the modulator is incapable of delivering the power required to modulate the transmitter fully, or when the Class-C amplifier is not adjusted to give the proper modulating impedance (§ 5-3).

The tubes used in the Class-B modulator should be capable of somewhat more than the power output nominally required (50 per cent of the d.c. input to the modulated amplifier) to take care of losses in the output transformer. These usually run from 10 per cent to 20 per cent of the tube output. In addition, the Class-C amplifier should be adjusted to give the proper modulating impedance and the correct output transformer turns ratio should be used. Such high-frequency harmonics as may be generated in these circumstances can be reduced by connecting condensers across the primary and secondary of the output transformer (about 0.002 μ fd. in the average case), to form, with the transformer leakage inductance (§ 2-9) a low-pass filter (§ 2-11) which cuts off just above the maximum audio frequency required for speech transmission (about 4000 cycles). The condenser voltage ratings should be adequate for the peak a.f. voltages appearing across them.

Operation without load — Excitation should never be applied to a Class-B modulator until after the Class-C amplifier is turned on and is drawing the value of plate current required to present the rated load to the modulator. With no load to absorb the power, the primary impedance of the transformer rises to a high value and excessive audio voltages are developed across it — frequently high enough to break down the transformer insulation. If the modulator is to be tested separately from the transmitter, a load resistance of the same value as the modulating impedance, and capable of dissipating the full power output of the modulator, should be connected across the transformer secondary.

¶ 5-7 Low-Level Modulators

Selection of tubes — Modulators for grid-bias and suppressor modulation can be small audio power tubes, since the audio power required usually is small. A triode such as the 2A3 is preferable because of its low plate resistance, but pentodes will work satisfactorily.

Matching to load — Since the ordinary Class-A receiving power tube will develop about 200 to 250 peak volts in its plate circuit, which is ample for most low-level modulator

applications, a 1:1 coupling transformer is generally used. If more voltage is required, a step-up ratio must be provided in the transformer. It is usual practice to load the primary of the output-coupling transformer with a resistance equal to or slightly higher than the rated load resistance of the tube, to stabilize the voltage output and thus improve the regulation. This is indicated in Fig. 507.

¶ 5-8 Microphones

Sensitivity — The level of a microphone is its electrical output for a given speech intensity input. Level varies greatly with microphones of different basic types, and also varies between different models of the same type. The output is also greatly dependent on the character of the individual voice (that is, the audio frequencies present in the voice) and the distance of the speaker's lips from the microphone, decreasing approximately as the square of the distance. Hence, only approximate values based on averages of "normal" speaking voices can be attempted. The values given in the following paragraphs are based on close talking; that is, with the microphone less than an inch from the speaker's lips.

Frequency response — The frequency response or fidelity of a microphone is its relative ability to convert sounds of different frequencies into alternating current. With fixed sound intensity at the microphone, the electrical output may vary considerably as the sound frequency is varied. For understandable speech transmission only a limited frequency range is necessary, and natural-sounding speech can be obtained if the output of the microphone does not vary more than a few decibels (§ 3-3) at any frequency within a range of about 200 cycles to 4000 cycles. When the variation expressed in terms of decibels is small between two frequency limits, the microphone is said to be flat between those limits.

Carbon microphones — Fig. 512-A and B show connections for single- and double-button carbon microphones, with a rheostat included in each circuit for adjusting the button current to the correct value as specified with each microphone. The single-button microphone consists of a metal diaphragm placed against an insulating cup containing loosely packed carbon granules (*microphone button*). Current from a battery flows through the granules, the diaphragm being one connection and the metal back-plate the other. The primary of a transformer is connected in series with the battery and microphone. As the diaphragm vibrates its pressure on the granules alternately increases and decreases, causing a corresponding increase and decrease of current flow through the circuit, since the pressure changes the resistance of the mass of granules. The resulting change in the current flowing through the transformer primary causes an alternating voltage, of corresponding frequency and intensity, to be set up in the transformer sec-

ondary (§2-9). The double-button type is similar, but with two buttons in push-pull.

Good quality single-button carbon microphones give outputs ranging from 0.1 to 0.3 volt across 50 to 100 ohms; that is, across the primary winding of the microphone transformer. With the step-up of the transformer, a peak voltage of between 3 and 10 volts across 100,000 ohms or so can be assumed available at the grid of the first tube. The usual button current is 50 to 100 ma.

The level of good-quality double-button microphones is considerably less, ranging from 0.02 volt to 0.07 volt across 200 ohms. With this type of microphone and the usual push-pull input transformer, a peak voltage of 0.4 to 0.5 across 100,000 ohms or so can be assumed available at the first speech-amplifier grid. The button current with this type of microphone ranges from 5 to 50 ma. per button.

Crystal microphones—The input circuit for a piezoelectric or crystal type of microphone is shown in Fig. 512-F. The element in this type consists of a pair of Rochelle salts crystals cemented together, with plated electrodes. In the more sensitive types, the crystal is mechanically coupled to a diaphragm. Sound waves actuating the diaphragm cause the crystal to vibrate mechanically and, by piezoelectric action (§2-10), to generate a corresponding alternating voltage between the electrodes, which are connected to the grid circuit of a vacuum-tube amplifier, as shown. The crystal type requires no separate source of current or voltage.

Although the level of crystal microphones varies with different models, an output of 0.01 to 0.03 volt is representative for communication types. The level is affected by the length of the cable connecting the microphone to the first amplifier stage; the above figure is for lengths of 6 or 7 feet. The frequency characteristic is unaffected by the cable, but the load resistance (amplifier grid resistor) does affect it, the lower frequencies being attenuated as the shunt resistance becomes less. A

grid-resistor value of 1 megohm or more should be used for reasonably flat response, 5 megohms being a customary figure.

Condenser microphones—The condenser microphone of Fig. 512-C consists of a two-plate capacity, with one plate stationary. The other, which is separated from the first by about a thousandth of an inch, is a thin metal membrane serving as a diaphragm. This condenser is connected in series with a resistor and a d.c. voltage source. When the diaphragm vibrates, the change in capacity causes a small charging current to flow through the circuit. The resulting audio voltage which appears across the resistor is fed to the grid of the tube through the coupling condenser.

The output of condenser microphones varies with different models, the high-quality type being about one-hundredth to one-fiftieth as sensitive as the double-button carbon microphone. The first speech-amplifier stage must be built into the microphone, since the capacity of a connecting cable would impair both output and frequency range.

Velocity and dynamic microphones—In a velocity or "ribbon" microphone, the element acted upon by the sound waves is a thin corrugated metallic ribbon suspended between the poles of a magnet. When vibrating, the ribbon cuts the lines of force between the poles, first in one direction and then the other, thus generating an alternating voltage. The movement of the ribbon is proportional to the velocity of the sound-energized air particles. Velocity microphones are built in two types, high impedance and low impedance, the former being used in most applications. A high-impedance microphone can be directly connected to the grid of an amplifier tube, shunted by a resistance of 0.5 to 5 megohms (Fig. 512-E). Low-impedance microphones are used when a long connecting cable (75 feet or more) must be employed. In such a case the output of the microphone is coupled to the first amplifier stage through a suitable step-up transformer, as shown in Fig. 512-D).

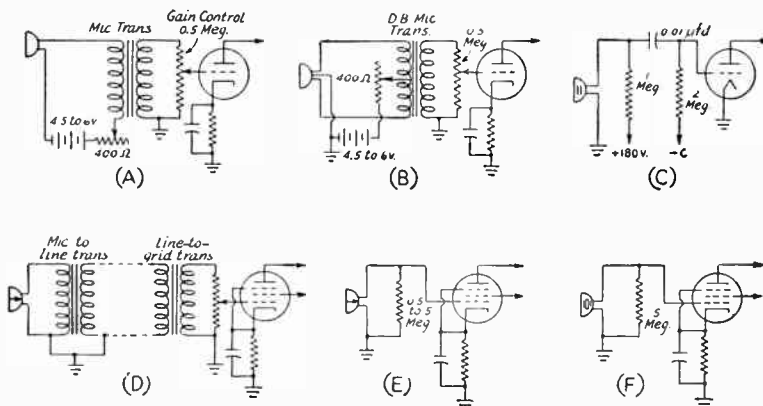


Fig. 512 — Speech input circuits of five commonly used types of microphones. A, single-button carbon; B, double-button carbon; C, condenser; D, low-impedance velocity; E, high-impedance velocity; F, crystal.

The level of the velocity microphone is about 0.03 to 0.05 volt. This figure applies directly to the high-impedance type, and to the low-impedance type when the voltage is measured across the coupling transformer secondary.

The dynamic microphone somewhat resembles a dynamic loud speaker in principle. A light-weight voice coil is rigidly attached to a diaphragm, the coil being placed between the poles of a permanent magnet. Sound causes the diaphragm to vibrate, thus moving the coil back and forth between the magnet poles and generating an alternating voltage the frequency of which is proportional to the frequency of the impinging sound and the amplitude proportional to the sound pressure. The dynamic microphone usually is built with high-impedance output, suitable for working directly into the grid of an amplifier tube. If the connecting cable must be unusually long a low-impedance type should be used, with a step-up transformer at the end of the cable. A small permanent-magnet speaker can be used as a dynamic microphone, although the fidelity is not as good as is obtainable with a properly designed microphone.

§ 5-9 The Speech Amplifier

Description — The function of the speech amplifier is to build up the weak microphone voltage to a value sufficient to excite the modulator to the required output. It may have from one to several stages. The last stage nearly always must deliver a certain amount of audio power, especially when it is used to excite a Class-B modulator. Speech amplifiers for grid-bias modulation usually end in a power stage which also functions as the modulator.

The speech amplifier frequently is built as a unit separate from the modulator, and in such a case may be provided with a step-down transformer designed to work into a low impedance, such as 200 or 500 ohms (tube-to-line transformer). When this is done, a step-up input transformer intended to work between the same impedance and the modulator grids (line-to-grid transformer) is provided in the modulator circuit. The line which connects the two transformers may be made of any convenient length.

General design considerations — The last stage of the speech amplifier must be selected on the basis of the power output required from it; for instance, the power necessary to drive a Class-B modulator (§ 5-6). It may be either single-ended or push-pull (§ 3-3), the latter generally being preferable because of the higher power output and lower harmonic distortion. Push-pull amplifiers may be either Class A, Class AB₁ or Class AB₂ (§ 3-4), as the power requirements dictate. If a Class-A or AB₁ amplifier is used, the preceding stages all may be voltage amplifiers, but when a Class-AB₂ amplifier is used the stage immediately preceding it must be capable of furnishing the power consumed by its grids at full output.

The requirements in this case are much the same as those which must be met by a driver for a Class-B stage (§ 5-6), but the actual power needed is considerably smaller and usually can be supplied by one or two small receiving triodes. All lower-level speech amplifier stages invariably are worked purely as voltage amplifiers.

The minimum amplification which must be provided ahead of the last stage is equal to the peak audio-frequency grid voltage required by the last stage for full output (peak grid-to-grid voltage in the case of a push-pull stage), divided by the output voltage of the microphone or secondary of the microphone transformer if one is used (§ 5-8). The peak a.f. grid voltage required by the output tube or tubes is equal to the d.c. grid bias in the case of a single-tube Class-A amplifier, and approximately twice the grid bias for a push-pull Class-A stage. The requisite information for Class-AB₁ and AB₂ amplifiers can be obtained from the manufacturer's data on the type considered. If the gain is not obtainable in one stage, several stages must be used in cascade. When the output stage is operated Class AB₂, due allowance must be made for the fact that the next-to-the-last stage must deliver power as well as voltage. In such cases, suitable driver combinations usually are recommended by manufacturers of tubes and inter-stage transformers. The coupling transformer must be designed especially for the purpose.

The total gain provided by a multi-stage amplifier is equal to the product of the individual stage gains. For example, when three stages are used, the first having a gain of 100, the second 20 and the third 15, the total gain is $100 \times 20 \times 15$, or 30,000. It is good practice to provide two or three times the minimum required gain in designing the speech amplifier. This will insure having ample gain available to cope with varying conditions.

When the gain must be fairly high, as when a crystal microphone is used, the speech amplifier frequently has four stages, including the power output stage. The first generally is a pentode, because of the high gain attainable with this type of tube. The second and third stages usually are triodes, the third frequently having two tubes in push-pull when it drives a Class-AB₂ output stage. Two pentode stages seldom are used consecutively, because of the difficulty of getting stable operation when the gain per stage is very high. With carbon microphones less amplification is needed and hence the pentode first stage usually is omitted, one or two triode stages being ample to obtain full output from the power stage.

Stage gain and voltage output — In voltage amplifiers, the *stage gain* is the ratio of a.c. output voltage to a.c. voltage applied to the grid. It will vary with the applied audio frequency, but for speech the variation should be small over the range of 100–4000 cycles. This condition is easily met in practice.

The output voltage is the maximum value which can be taken from the plate circuit without distortion. It is usually expressed in terms of the peak value of the a.c. wave (§ 2-7), since this value is independent of the waveform. The peak output voltage usually is of interest only when the stage drives a power amplifier, since only in this case is the stage called upon to work near its maximum capabilities. Low-level stages very seldom are worked near their full capacity, hence harmonic distortion is negligible and the voltage gain of the stage is the primary consideration.

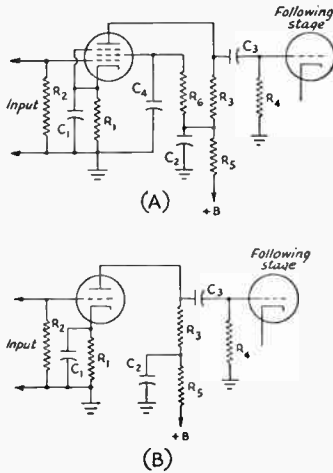


Fig. 513 — Resistance-coupled voltage amplifier circuits. A, pentode; B, triode. Designations are as follows: C₁ — Cathode by-pass condenser. C₂ — Plate by-pass condenser. C₃ — Output coupling condenser (blocking condenser). C₄ — Screen by-pass condenser. R₁ — Cathode resistor. R₂ — Grid resistor. R₃ — Plate resistor. R₄ — Next-stage grid resistor. R₅ — Plate decoupling resistor. R₆ — Screen resistor. Values for suitable tubes are given in Chapter Fourteen.

Resistance coupling — Resistance coupling generally is used in voltage amplifier stages. It is relatively inexpensive, good frequency response can be secured, and there is little danger of hum pick-up from stray magnetic fields associated with heater wiring. It is the only type of coupling suitable for the output circuits of pentodes and high- μ triodes, since with transformers a sufficiently high load impedance (§3-3) cannot be obtained without considerable frequency distortion. Typical circuits are given in Fig. 513 and design data in § 3-6.

Transformer coupling — Transformer coupling between stages ordinarily is used only when power is to be transferred (in such a case resistance coupling is very inefficient), or when it is necessary to couple between a single-ended and a push-pull stage. Triodes having an amplification factor of 20 or less are used in transformer-coupled voltage amplifiers.

Representative circuits for coupling single-ended to push-pull stages are shown in Fig. 514. That at A uses a combination of resistance and transformer coupling, and may be used for exciting the grids of a Class-A or AB₁ following stage. The resistance coupling is used to keep the d.c. plate current from flowing through the transformer primary, thereby preventing a reduction in primary inductance below its no-current value (§ 8-4). This improves the low-frequency response. With low- μ triodes (6C5, 6J5, etc.), the gain is equal to that with resistance coupling multiplied by the secondary-to-primary turns ratio of the transformer.

In B the transformer primary is in series with the plate of the tube, and thus must carry the tube plate current. When the following amplifier operates without grid current, the voltage gain of the stage is practically equal to the μ of the tube multiplied by the transformer ratio. This circuit also is suitable for transferring power (within the capabilities of the tube) as in the case of a following Class-AB₂ stage used as a driver for a Class-B modulator.

Gain control — The over-all gain of the amplifier may be changed to suit the output level of the microphone, which will vary with voice intensity and distance of the speaker from the microphone, by varying the proportion of a.c. voltage applied to the grid of one of the stages.

The gain-control potentiometer should be near the input end of the amplifier, so that there will be no danger of overloading the stages ahead of the gain control. With carbon microphones the gain control may be placed directly across the microphone transformer secondary, but with other types the gain control usually will affect the frequency response of the microphone when connected directly across it. The control therefore usually is placed in the grid circuit of the second stage.

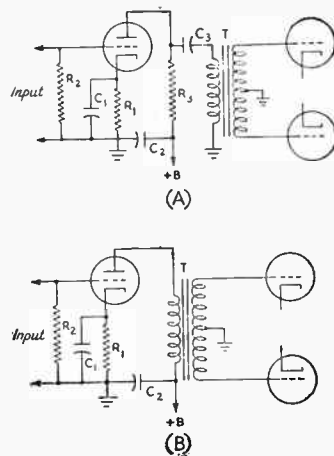


Fig. 514 — Transformer-coupled amplifier circuits for driving a push-pull amplifier. A is for resistance-transformer coupling; B, for transformer coupling. Designations correspond to those in Fig. 513. In A, values can be taken from Table I. In B, the cathode resistor is calculated from the rated plate current and grid bias as given for the particular type of tube used (§ 3-6).

§ 5-10 Checking 'Phone Transmitter Operation

Modulation percentage—The most reliable method of determining percentage of modulation is by means of the cathode-ray oscilloscope (§ 3-9). The oscilloscope gives a direct picture of the modulated output of the transmitter, and by its use the waveform errors inherent in other types of measurements are eliminated.

Two types of oscilloscope patterns may be obtained, known as the "wave envelope" and "trapezoid." The former shows the shape of the modulation envelope (§ 5-2) directly, while the latter in effect plots the modulation characteristic (§ 5-2) of the modulated stage on the cathode-ray tube screen. To obtain the wave-envelope pattern, the oscilloscope must have a horizontal sweep circuit. The trapezoidal pattern requires only the oscilloscope, the sweep circuit being supplied by the transmitter itself. Fig. 517 shows methods of connecting the oscilloscope to the transmitter for both types of patterns. The oscilloscope connections for the wave-envelope pattern, Fig. 517-A, are usually simpler than those for the trapezoidal figure. The vertical-deflection plates are coupled to the amplifier tank coil or an antenna coil by means of a pick-up coil of a few turns connected to the oscilloscope through a twisted-pair line. The position of the pick-up coil is varied until a carrier pattern, Fig. 518-B, of suitable height is obtained. The sweep voltage should be adjusted to make the width of the pattern somewhat more than half the diameter of the screen. It is frequently helpful in eliminating r.f. harmonics from the pattern to connect a resonant circuit, tuned to the operating frequency, between the vertical deflection plates, using link coupling between this and the transmitter tank circuit.

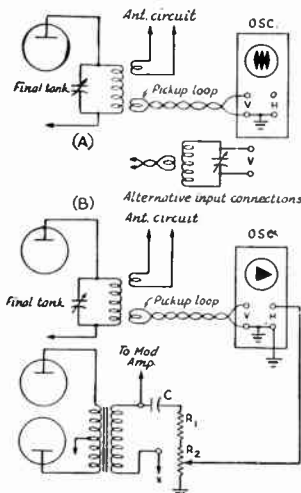


Fig. 517 — Methods of connecting an oscilloscope to the modulated r.f. amplifier for checking modulation.

With the application of voice modulation, a rapidly changing pattern of varying height will be obtained. When the maximum height of this pattern is just twice that of the carrier alone, the wave is being modulated 100 per cent (§ 5-2). This is illustrated by Fig. 518-D, where the point X represents the sweep line (reference line) alone, YZ is the carrier height, and PQ is the maximum height of the modulated wave. If the height is greater than the distance PQ, as illustrated in E, the wave is overmodulated in the upward direction. Overmodulation in the downward direction is indicated by a gap in the pattern at the reference axis, where a single bright line appears on the screen. Overmodulation in either direction may take place even when the modulation in the other direction is less than 100 per cent. Assuming that the modulation is symmetrical, however, any modulation percentage can be measured directly from the screen by measuring the maximum height with modulation and the height of the carrier alone; calling these two heights h_1 and h_2 respectively, the modulation percentage is

$$\frac{h_1 - h_2}{h_2} \times 100$$

Connections for the trapezoidal pattern are shown in Fig. 517-B. The vertical plates are similarly coupled to the transmitter tank circuit through a pick-up loop; the tuned input circuit to the oscilloscope may also be used. The horizontal plates are coupled to the output of the modulator through a voltage divider (§ 2-6). R_1R_2 , the resistance of R_2 being variable to permit adjustment of the audio voltage to a suitable value to give a satisfactory horizontal sweep on the screen. R_2 may be a 0.25-megohm volume control resistor. The value of R_1 will depend upon the audio output voltage of the modulator. This voltage is equal to \sqrt{PR} , where P is the audio power output of the modulator and K is the modulating impedance of the modulated r.f. amplifier. In the case of grid-bias modulation with a 1:1 output transformer, it will be satisfactory to assume that the a.c. output voltage of the modulator is equal to $0.7E$ for a single tube or $1.4E$ for a push-pull stage, where E is the d.c. plate voltage on the modulator. If the transformer ratio is other than 1:1, the voltage so calculated should be multiplied by the actual secondary-to-primary turns ratio.

The total resistance of R_1 and R_2 in series should be 0.25 megohm for every 150 volts of modulator output; for example, if the modulator output voltage is 600, the total resistance should be four (600/150) times 0.25 megohm, or 1 megohm. Then, with 0.25 megohm at R_2 , R_1 should be 0.75 megohm. The blocking condenser, C , should be 0.1 μ fd or more, and its voltage rating should be greater than the maximum voltage in the circuit. With plate modulation, this is twice the d.c. voltage applied to the plate of the modulated amplifier.

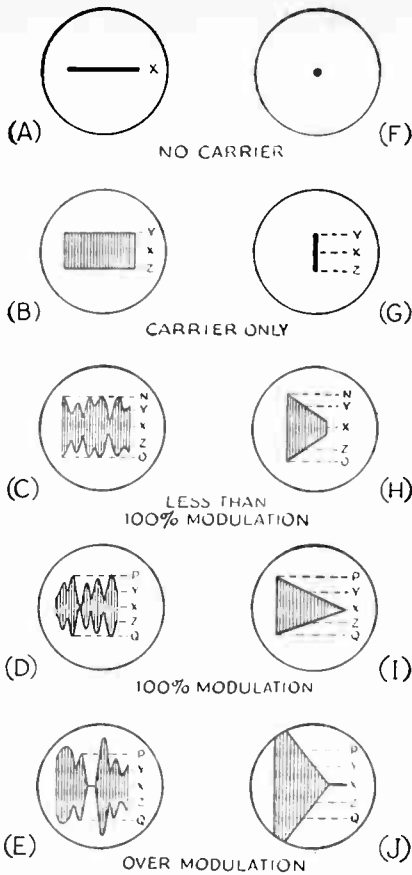


Fig. 518 — Wave-envelope and trapezoidal patterns encountered under different conditions of modulation.

The trapezoidal patterns are shown in Fig. 518 at F to J, each alongside the corresponding wave-envelope pattern. With no signal, only the cathode-ray spot appears on the screen. When the unmodulated carrier is applied, a vertical line appears; the length of the line should be adjusted, by means of the pick-up coil coupling, to a convenient value. When the carrier is modulated, the wedge-shaped pattern appears; the higher the modulation percentage, the wider and more pointed the wedge becomes. At 100 per cent modulation it just makes a point on the axis, X, at one end, and the height, PQ, at the other end is equal to twice the carrier height, YZ. Overmodulation in the upward direction is indicated by increased height over PQ, and in the downward direction by an extension along the axis X at the pointed end. The modulation percentage may be found by measuring the modulated and unmodulated carrier heights, in the same way as with the wave-envelope pattern.

Non-symmetrical waveforms — In voice waveforms the average maximum amplitude in one direction from the axis frequently is greater than in the other direction, although

the average energy on both sides is the same. For this reason the percentage of modulation in the "up" direction frequently differs from that in the "down" direction. With a given voice and microphone, this difference in modulation percentage is usually always in the same direction. Since overmodulation in the downward direction causes more out-of-channel interference than overmodulation upward because of the steeper wavefront (§ 6-1), it is advisable to "phase" the modulation so that the side of the voice waveform having the larger excursions causes the instantaneous carrier power to increase and the smaller excursions to cause a power decrease. This reduces the likelihood of overmodulation on the "down" peak. The direction of the larger excursions can readily be found by careful observation of the oscilloscope pattern. The phase can be reversed by reversing the connections of one winding of any transformer in the speech amplifier or modulator.

Modulation monitoring — While it is desirable to modulate as fully as possible, 100 per cent modulation should not be exceeded, particularly in the downward direction, because harmonic distortion will be introduced and the channel width increased (§ 5-2), thus causing unnecessary interference to other stations. The oscilloscope may be used to provide a continuous check on the modulation, but simpler indicators may be used for the purpose, once calibrated. A convenient indicator, when a Class-B modulator (§ 5-6) is used, is the plate milliammeter in the Class-B stage, since plate current fluctuates with the voice intensity. Using the oscilloscope, determine the gain-control setting and voice intensity which gives 100 per cent modulation on voice peaks, and simultaneously observe the maximum Class-B plate-milliammeter reading on the peaks. When this maximum reading is obtained, it will suffice in regular operation to adjust the gain so that it is not exceeded.

A sensitive rectifier-type voltmeter (copper-oxide type) also can be used for modulation monitoring. It should be connected across the output circuit of an audio driver stage where the power level is a few watts, and similarly calibrated against the oscilloscope to determine the reading which represents 100 per cent modulation.

The plate milliammeter of the modulated r.f. stage may also be used as an indicator of overmodulation. Since the average plate current is constant (§ 5-3, 5-4, 5-5) when the amplifier is linear, the reading will be the same with or without modulation. When the amplifier is overmodulated, especially in the downward direction, the operation is no longer linear and the average plate current will change. A flicker of the pointer may therefore be taken as an indication of overmodulation or non-linearity. However, it is possible that the average plate current will remain constant with considerable overmodulation

under some operating conditions, so that an indicator of this type is not wholly reliable unless it has been checked previously against an oscilloscope.

Linearity — The linearity (§ 5-2) of a modulated amplifier may readily be checked with the oscilloscope. The trapezoidal pattern is more easily interpreted than the wave envelope pattern, and less auxiliary equipment is required. The connections are the same as for measuring modulation percentage (Fig. 517). If the amplifier is perfectly linear, the sloping sides of the trapezoid will be perfectly straight from the point at the axis up to at least 100 per cent modulation in the upward direction. Non-linearity will be shown by curvature of the sides. Curvature near the point, extending the point farther along the axis than would occur with straight sides, indicates that the output power does not decrease rapidly enough in this region; it may also be caused by imperfect neutralization (a push-pull amplifier is recommended because better neutralization is possible than with single-ended amplifiers) or by r.f. leakage from the exciter through the final stage. The latter condition can be checked by removing the plate voltage from the modulated stage, when the carrier should disappear, leaving only the beam spot remaining on the screen (Fig. 518-F). If a small vertical line remains, the amplifier should be re-neutralized; if this does not eliminate the line, it is an indication that r.f. is being picked up from lower-power stages, either by coupling through the final tank or via the oscilloscope pick-up loop.

Inward curvature at the large end of the pattern is caused by improper operating conditions of the modulated amplifier, usually improper bias or insufficient excitation, or both, with plate modulation. In grid-bias and

cathode-modulated systems, the bias, excitation and plate loading are not correctly proportioned when such curvature occurs, usually because the amplifier has been adjusted to have too-high carrier efficiency without modulation (§ 5-4, 5-5).

For the wave-envelope pattern, it is necessary to have a linear horizontal-sweep circuit in the oscilloscope and a source of sine-wave audio signal voltage (such as an audio oscillator or signal generator) which can be synchronized with the sweep circuit. The linearity can be judged by comparing the wave envelope with a true sine wave. Distortion in the audio circuits will affect the pattern in this case (such distortion has no effect on the trapezoidal pattern, which shows the modulation characteristic of the r.f. amplifier alone), and it is also readily possible to misjudge the shape of the modulation envelope, so that the wave envelope is less useful than the trapezoid for checking linearity of the modulated amplifier.

Fig. 519 shows typical patterns of both types. The cause of the distortion is indicated for grid-bias and suppressor modulation. The patterns at A, although not truly linear, are representative of properly operated grid-bias modulation systems. Better linearity can be obtained with plate modulation of a Class-C amplifier.

Faulty patterns — The drawings of Figs. 518 and 519 show what is normally to be expected in the way of pattern shapes when the oscilloscope is used to check modulation. If the actual patterns differ considerably from those shown, it is probable that the pattern is faulty rather than the transmitter. It is important that only r.f. from the modulated stage be coupled to the oscilloscope, and then only to the vertical plates. The effect of stray r.f. from other stages in the transmitter has been mentioned in the preceding paragraph. If r.f. is present also on the horizontal plates, the pattern will lean to one side instead of being upright. If the oscilloscope cannot be moved to a spot where the unwanted pick-up disappears, a small by-pass condenser (10 $\mu\text{f.d.}$) should be connected across the horizontal plates as close to the cathode-ray tube as possible. An r.f. choke (2.5 mh. or smaller) may also be connected in series with the ungrounded horizontal plate.

"Folded" trapezoidal patterns occur when the audio sweep voltage is taken from some point in the audio system other than that where the a.f. power is applied to the modulated stage. Such patterns are caused by a phase difference between the sweep voltage and the modulating voltage. The connections should always be as shown in Fig. 517-B.

Plate-current shift — As mentioned above, the d.c. plate current of a modulated amplifier will be the same with and without modulation so long as the amplifier operation is perfectly linear and other conditions remain unchanged. This also assumes that the modulator is work-

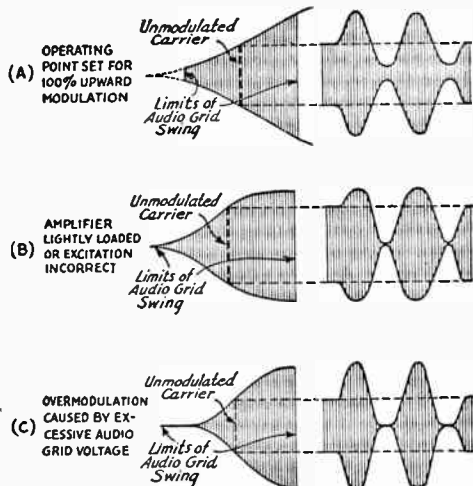


Fig. 519 — Oscilloscope patterns representing proper and improper adjustments for grid-bias or cathode modulation. The pattern obtained with a correctly adjusted amplifier is shown at A. The other drawings indicate non-linear modulation from typical causes.

ing within its capabilities. Because there is usually some curvature of the modulation characteristic with grid-bias modulation there is normally a slight upward change in plate current of a stage so modulated, but this occurs only at high modulation percentages and is barely detectable under the usual conditions of voice modulation.

With plate modulation, a downward shift in plate current may indicate one or more of the following:

- 1) Insufficient excitation to the modulated r.f. amplifier.
- 2) Insufficient grid bias on the modulated stage.
- 3) Wrong load resistance for the Class-C r.f. amplifier.
- 4) Insufficient output capacity in the filter of the modulated-amplifier plate supply.
- 5) Heavy overloading of the Class-C r.f. amplifier tube or tubes.

Any of the following may cause an upward shift in plate current:

- 1) Overmodulation (excessive audio power, audio gain too great).
- 2) Incomplete neutralization of the modulated amplifier.
- 3) Parasitic oscillation in the modulated amplifier.

When a common plate supply is used for both a Class-B (or Class-AB) modulator and a modulated r.f. amplifier, the plate current of the latter may "kick" downward because of poor power-supply voltage regulation (§ 8-1) with the varying additional load of the modulator on the supply. The same effect may occur with high-power transmitters because of poor regulation of the a.c. supply mains, even when a separate power-supply unit is used for the Class-B modulator. Either condition may be detected by measuring the plate voltage applied to the modulated stage; in addition, poor line regulation also may be detected by observing if there is any downward shift in filament or line voltage.

With grid-bias modulation, any of the following may be the cause of a plate current shift greater than the normal mentioned above:

Downward kick: Too much r.f. excitation; insufficient operating bias; distortion in modulator or speech amplifier; too-high resistance in bias supply; insufficient output capacity in plate-supply filter to modulated amplifier; amplifier plate circuit not loaded heavily enough; plate-circuit efficiency too high under carrier conditions.

Upward kick: Overmodulation (excessive audio voltage); distortion in audio system; regeneration because of incomplete neutralization; operating grid bias too high.

A downward kick in plate current will accompany an oscilloscope pattern like that of Fig. 519-B; the pattern with an upward kick will look like Fig. 519-A, with the shaded

portion extending farther to the right and above the carrier, for the "wedge" pattern.

Noise and hum on carrier — These may be detected by listening to the signal on a receiver sufficiently removed from the transmitter to avoid overloading. The hum level should be low compared to the voice at 100 per cent modulation. Hum may come either from the speech amplifier and modulator or from the r.f. section of the transmitter. Hum from the r.f. section can be detected by completely shutting off the modulator; if hum remains when this is done, the power-supply filters for one or more of the r.f. stages have insufficient smoothing (§ 8-4). With a hum-free carrier, hum introduced by the modulator can be checked by turning on the modulator but leaving the speech amplifier off; power-supply filtering is the likely source of such hum. If carrier and modulator are both clean, connect the speech amplifier and observe the increase in hum level. If the hum disappears with the gain control at minimum, the hum is being introduced in the stage or stages preceding the gain control. The microphone also may pick up hum, a condition which can be checked by removing the microphone from the circuit but leaving the first speech-amplifier grid circuit otherwise unchanged. A good ground on the microphone and speech system usually is essential to hum-free operation.

Hum can be checked with the oscilloscope, where it appears as modulation on the carrier in the same way as the normal modulation. While the percentage usually is rather small, if the carrier shows modulation with no speech input hum is the likely cause. The various parts of the transmitter may be checked through as described above.

Spurious sidebands — A superheterodyne receiver having a crystal filter (§ 7-8, 7-11) is needed for checking spurious sidebands outside the normal communication channel (§ 5-2). The r.f. input to the receiver must be kept low enough, by removing the antenna or by adequate separation from the transmitter, to avoid overloading and consequent spurious receiver responses (§ 7-8). With the crystal filter in its sharpest position and the beat oscillator turned on, tune through the region outside the normal channel limits (3 to 4 kilocycles each side of the carrier) while another person talks into the microphone. Spurious sidebands will be observed as intermittent beat notes coinciding with voice peaks, or, in bad cases of distortion or overmodulation, as "clicks" or crackles well away from the carrier frequency. Sidebands more than 4 kilocycles from the carrier should be of negligible strength in a properly modulated 'phone transmitter. The causes are overmodulation or non-linear operation (§ 5-3).

R.f. in speech amplifier — A small amount of r.f. current in the speech amplifier — particularly in the first stage, which is most susceptible to such r.f. pick-up — will cause over-

loading and distortion in the low-level stages. Frequently also there is a regenerative effect which causes an audio-frequency oscillation or "howl" to be set up in the audio system. In such cases the gain control cannot be advanced very far before the howl builds up, even though the amplifier may be perfectly stable when the r.f. section of the transmitter is not turned on.

Complete shielding of the microphone, microphone cord, and speech amplifier are necessary to prevent r.f. pick-up, and a ground connection separate from that to which the transmitter is connected is advisable. Unsymmetrical or capacity coupling to the antenna (single-wire feed, feeders tapped on final tank circuit, etc.) may be responsible in that these systems sometimes cause the transmitter chassis to take an r.f. potential above ground. Inductive coupling to a two-wire transmission line is advisable. This antenna effect can be checked by disconnecting the antenna and dissipating the power in a dummy antenna (§ 4-9), when it usually will be found that the r.f. feed-back disappears. If it does not, the speech amplifier and microphone shielding are at fault.

§ 5-11 Frequency Modulation

Principles — In frequency modulation the carrier amplitude is constant and the output frequency of the transmitter is made to vary about the carrier or mean frequency at a rate corresponding to the audio frequencies of the speech currents. The extent to which the frequency changes in one direction from the unmodulated or carrier frequency is called the *frequency deviation*. It corresponds to the change of carrier amplitude in the amplitude-modulation system (§ 5-2). Deviation is usually expressed in kilocycles, and is equal to the difference between the carrier frequency and either the highest or lowest frequency reached by the carrier in its excursions with modulation. There is no modulation percentage, in the usual sense; with suitable circuit design the deviation may be made as large as desired without encountering any effect equivalent to overmodulation in the amplitude-modulated system.

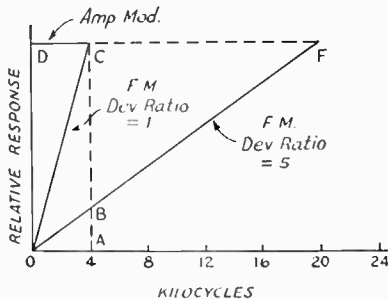


Fig. 520 — Triangular spectrum showing the noise response in an f.m. receiver compared with amplitude modulation. Deviation ratios of 1 and 5 are shown.

Deviation ratio — The ratio of the maximum frequency deviation to the audio frequency of the modulation is called the *deviation ratio*. It also is called the modulation index. Unless otherwise specified, it is taken as the ratio of the maximum frequency deviation to the *highest* audio frequency to be transmitted.

Advantages of f.m. — The chief advantage of frequency modulation over amplitude modulation is noise reduction at the receiver. All electrical noises in the radio spectrum, including those originating in the receiver, are r.f. oscillations which vary in amplitude, this variation causing the noise response in amplitude-modulation receivers. If the receiver does not respond to amplitude variations but only to frequency changes, noise can affect it only by causing a phase shift which appears as frequency modulation on the signal. The effect of such frequency modulation by the noise can be made small by making the frequency change (deviation) in the signal large.

A second advantage is that the power required for modulation is inconsequential, since there is no power variation in the modulated output of the transmitter.

Triangular spectrum — The way in which noise is reduced by a large deviation ratio is illustrated by Fig. 520. In this figure the noise is assumed to be evenly distributed over the channel used, an assumption which is almost always true. It is also assumed that audio frequencies above 4000 cycles (4 kc.) are not necessary to voice communication, and that the audio system in the receiver has no response above this frequency. Then, if an amplitude modulation receiver is used and its selectivity is such that there is no attenuation of sidebands (§ 5-2) below 4000 cycles, the noise components of all frequencies within the channel will produce equal response when they beat with a carrier centered in the channel. The response under these conditions is shown by the line *DC*.

In the f.m. receiver the output amplitude is proportional to the frequency deviation, and noise components in the channel can be considered to frequency-modulate the steady carrier with a deviation proportional to the difference between the actual frequency of the component and the frequency of the carrier, and also to give an audio-frequency beat of the same frequency difference. This leads to a rising response characteristic, such as the line *OC'*, where the noise amplitude is proportional to the audio beat frequency. The average noise power output is proportional to the square root of the sum of the squares of all the amplitude values (§ 2-7), so that the noise power with frequency modulation having a deviation ratio of 1 is only one-third that with amplitude modulation, or an improvement of 4.75 db.

If the deviation ratio is increased to 5, the noise response is represented by the line *OF*. Since only frequencies up to 4000 cycles are reproduced in the output, however, the audible

noise is confined to the triangle *OAB*. These relations hold only when the carrier is strong compared to the noise. For reception of stations with weak signal strength, the signal-to-noise ratio is better with a deviation ratio of 1.

Linearity — A transmitter in which frequency deviation is directly proportional to the amplitude of the modulating signal is said to be *linear*. It is essential also that the carrier amplitude remain constant under modulation, which in turn requires that the transmitter tuned circuits, as well as the antenna, have broad enough response to handle without discrimination the entire range of audio frequencies transmitted. This requirement is easily met under ordinary conditions.

Sidebands — In frequency modulation there is a series of sidebands on either side of the carrier frequency for each audio-frequency component in the modulation. In addition to the usual sum and difference frequencies (§ 5-2) there are also beats at harmonics of the fundamental modulating frequency, even though the latter may be a pure tone. This occurs because of the necessity for maintaining the proper phase relationships between the carrier and sidebands to keep the power output constant. Hence, a frequency-modulated signal inherently occupies a wider channel than an amplitude-modulated signal. Because of the necessity for conserving space in the usual communication spectrum, the use of f.m. by amateurs is confined to the very-high frequencies in the region above 28 Mc.

The number of sidebands for a single modulating frequency increases with the frequency deviation. When the deviation ratio is of the order of 5 the sidebands beyond the maximum frequency deviation are usually negligible, so that the channel required is approximately twice the frequency deviation.

5-12 Methods of Frequency Modulation

Requirements and methods — At present there are no fixed standards of frequency deviation in amateur work. Since a deviation ratio of 5 is considered high enough in any case, the maximum deviation necessary is 15 to 20 kc. for an upper audio-frequency limit of 3000 or 4000 cycles (§ 5-2), or a channel width of 30 to 40 kc. The permissible deviation is determined by the receiver (§ 7-18), since deviation beyond the limits of the receiver pass-band causes distortion. If the transmitter is designed to be linear (§ 5-11) with a deviation of about 15 kc., it can be used at a lower deviation ratio simply by reducing the gain in the speech amplifier. Thereby it can be made to conform to the requirements of the receiver in use.

The several possible methods of frequency modulation include mechanical modulation (for instance, varying condenser plate spacing in accordance with voice vibrations), initial phase-shift modulation which later is transformed into frequency modulation, and direct

frequency modulation of an oscillator by electronic means. The latter, in the form of the *reactance-tube modulator*, is the simplest system.

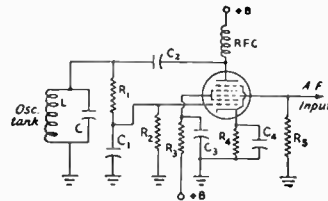


Fig. 521 — Reactance modulator circuit using a 6L7 tube. C — Tank capacity. C_1 — 3-10 μfd . C_2 — 250 μfd . C_3 — 8- μfd , electrolytic (a.f. by-pass) in parallel with 0.01- μfd . paper (r.f. by-pass). C_4 — 0.01 μfd . L — Oscillator tank inductance. R_1 — 50,000 ohms. R_2 , R_5 — 0.5 megohm. R_3 — 30,000 ohms. R_4 — 300 ohms.

The reactance modulator — The reactance modulator consists of a vacuum tube connected to the r.f. tank circuit of an oscillator in such a way as to act as a variable inductance or capacity, of a value dependent upon the instantaneous a.f. voltage applied to its grid. Fig. 521 is a representative circuit. The control grid circuit of the 6L7 tube is connected across the small capacity, C_1 , which is in series with the resistor, R_1 , across the oscillator tank circuit. Any type of oscillator circuit (§ 3-7) may be used. R_1 is large compared to the reactance (§ 2-8) of C_1 , so the r.f. current through R_1C_1 will be practically in phase (§ 2-7) with the r.f. voltage appearing at the terminals of the tank circuit. However, the voltage across C_1 will lag the current by 90 degrees (§ 2-8). The r.f. current in the plate circuit of the 6L7 will be in phase with the grid voltage (§ 3-3), and consequently is 90 degrees behind the current through C_1 , or 90 degrees behind the r.f. tank voltage. This lagging current is drawn through the oscillator tank, giving the same effect as though an inductance were connected across the tank (in an inductance the current lags the voltage by 90 degrees — § 2-8). The frequency increases in proportion to the lagging plate current of the modulator, as determined by the a.f. voltage applied to the No. 3 grid of the 6L7; hence the oscillator frequency varies with the audio signal voltage.

If, on the other hand, C_1 and R_1 are reversed and the reactance of C_1 is made large compared to the resistance of R_1 the r.f. current in the 6L7 plate circuit will lead the oscillator tank r.f. voltage, making the reactance capacitive rather than inductive.

Other circuit arrangements to produce the same effect may be employed. It is convenient to use a tube (such as the 6L7) in which the r.f. and a.f. voltages can be applied to separate control grids; however, both voltages may be applied to the same grid provided precautions are taken to prevent r.f. from flowing in the external audio circuit, and vice versa (§ 2-13).

The modulated oscillator usually is operated on a relatively low frequency, so that a high

order of carrier stability can be secured. Frequency multipliers are used to raise the frequency to the final frequency desired. The frequency deviation increases with the number of times the initial frequency is multiplied; for instance, if the oscillator is operated on 7 Mc. and the output frequency is to be 112 Mc., an oscillator frequency deviation of 1000 cycles will be raised to 16,000 cycles at the output frequency.

Design considerations — The sensitivity of the modulator (frequency change per unit change in grid voltage) increases when C_1 is made smaller, for a fixed value of R_1 , and also increases with an increase in L_1/C_1 ratio in the oscillator tank circuit. Since the carrier stability of the oscillator depends on the L_1/C_1 ratio (§ 3-7), it is desirable to use the highest tank capacity which will permit the desired deviation to be secured while keeping within the limits of linear operation. When the circuit of Fig. 521 is used in connection with a 7-Mc. oscillator, a linear deviation of 2000 cycles above and below the carrier frequency can be secured when the oscillator tank capacity is approximately 200 μfd . A peak a.f. input of two volts is required for full deviation. At 56 Mc. the maximum deviation would be 8×2000 , or 16 ke.

Since a change in any of the voltages on the modulator tube will cause a change in r.f. plate current, and consequently a frequency change, it is advisable to use a regulated plate power supply for both modulator and oscillator. At the low voltages used (250 volts), the required stabilization can be secured by means of gaseous regulator tubes (§ 8-8).

Speech amplification — The speech amplifier preceding the modulator follows ordinary design (§ 5-9), except that no power is required from it and the a.f. voltage taken by the modulator grid usually is small — not more than 10 or 15 volts, even with large modulator tubes. Because of these modest requirements, only a few speech-amplifier stages are needed; a two-stage amplifier consisting of a pentode followed by a triode, both resistance-coupled, will suffice for crystal microphones (§ 5-8).

R.f. amplifier stages — The frequency multiplier and output stages following the modulated oscillator may be designed and adjusted in accordance with ordinary principles. No special excitation requirements are imposed, since the amplitude of the output is constant. Enough frequency multiplication must be used to give the desired maximum deviation at the final frequency; this depends upon the maximum linear deviation available from the modulator-oscillator. All stages in the transmitter should be tuned to resonance, and careful neutralization (§ 4-7) of any straight amplifier stages is necessary to prevent r.f. phase shifts which might cause distortion.

Checking operation — The two quantities to be checked in the f.m. transmitter are linearity and frequency deviation. With a modulator

of the type shown in Fig. 521, both the r.f. and a.f. voltages are small enough to make the operation Class A (§ 3-4), so that the plate current of the modulator is constant so long as operation is over the linear portions of the No. 1 and No. 3 grid characteristics. Hence, non-linearity will be indicated by a change in plate current as the a.f. modulating voltage is increased. The distortion will be within acceptable limits, with the tube and constants given in Fig. 521, when the plate current does not change more than 5 per cent with signal.

Non-linearity is accompanied by a shift in the carrier frequency, so it also can be checked by means of a selective receiver such as one with a crystal filter (§ 7-11). A tone source is convenient for the test. Set the receiver for high selectivity, switch on the beat oscillator, and tune to the oscillator carrier frequency. (The check does not need to be made at the output frequency and the oscillator frequency usually is more convenient, since it will fall within the tuning range of a communications receiver.) Increase the modulating signal until a definite shift in carrier frequency is observed; this indicates the point at which non-linearity starts. The modulating signal should be kept below the level at which carrier shift is observed, for minimum distortion.

A selective receiver also can be used to check frequency deviation, again at the oscillator frequency. A source of tone of known frequency is required, preferably a continuously variable calibrated audio oscillator or signal generator. Tune in the carrier as described above, using the beat oscillator and high selectivity, and adjust the modulating signal to the maximum level at which linear operation is secured. Starting with the lowest frequency available, slowly raise the tone frequency while listening closely to the carrier beat note. As the tone frequency is raised the beat note first will decrease in intensity, then disappear entirely at a definite frequency, and finally come back and increase in intensity as the tone frequency is raised still more. The frequency at which the beat note disappears, multiplied by 2.4, is the frequency deviation at that level of modulating signal; for example, if the beat note disappears with an 800-cycle tone, the deviation is 2.4×800 , or 1920 cycles. The deviation at the output frequency is the oscillator deviation multiplied by the number of times the frequency is multiplied; in this example, if the oscillator is on 7 Mc. and the output on 56 Mc., the final deviation is 1920×8 , or 15.36 ke.

The output of the transmitter can be checked for amplitude modulation by observing the antenna current. It should not change from the unmodulated carrier value when the transmitter is modulated. Where there is no antenna ammeter in the transmitter, a flashlight lamp and loop can be coupled to the final tank coil to serve as a current indicator. If the carrier amplitude is constant, the lamp brilliance will not change with modulation.

Keying

6-1 Keying Principles and Characteristics

Requirements — The keying of a transmitter can be considered satisfactory if the method employed reduces the power output to zero when the key is open, or “up,” and permits full power to reach the antenna when the key is closed, or “down.” Furthermore, the keying system should accomplish this without producing keying transients or “clicks,” which cause interference with other amateur stations and with local broadcast reception, and the keying process should not affect the frequency of the emitted wave.

Back-wave — From various causes, some energy may get through to the antenna during keying spaces. The effect then is as though the dots and dashes were only louder portions of a continuous carrier; in some cases, in fact, the *back-wave*, or signal heard during the keying spaces, may seem to be almost as loud as the keyed signal. Under these conditions the keying is hard to read. A pronounced back-wave often results when the amplifier stage feeding the antenna is keyed; it may be present because of incomplete neutralization (§ 4-7) of the final stage, allowing some energy to get to the antenna through the grid-plate capacity of the tube, or because of magnetic coupling between antenna coupling coils and one of the low-power stages.

A back-wave also may be radiated if the keying system does not reduce the input to the keyed stage to zero during keying spaces. This trouble will not occur in keying systems which cut off the plate voltage when the key is open, but may be present in grid-blocking systems (§ 6-3) if the blocking voltage is not great enough and in power-supply primary keying systems (§ 6-3) if only the final-stage power-supply primary is keyed.

Keying waveform and sidebands — A keyed c.w. signal can be considered equivalent to a modulated signal (§ 5-1), except that, in-

stead of being modulated by sinusoidal waves and their harmonics, it is modulated by a rectangular wave, as in Fig. 601-A. If it were modulated by a sinusoidal wave of single frequency, as in Fig. 601-B, the only sidebands would be those equal to the carrier frequency plus and minus the modulation frequency (§ 5-2). A keying speed of 50 words per minute, sending sinusoidal dots, would give sidebands only 20 cycles either side of the carrier. However, when harmonics are present in the modulation the sidebands will extend out on both sides of the signal as far as the frequency of the highest harmonic. The rectangular wave form contains an infinite number of harmonics of the keying frequency, so a carrier modulated by truly rectangular dots would have sidebands covering the entire spectrum. Actually, the high-order harmonics are eliminated because of the selectivity of the tuned circuits (§ 2-10) in the transmitter, but there still is enough energy in the lower harmonics to extend the sidebands considerably. Considered from another viewpoint, whenever a pulse of current has a steep front (or back) high frequencies are certain to be present. If the pulse can be slowed down, or caused to *lag*, through a suitable filter circuit, the highest-order harmonics are filtered out.

Key clicks — Because the high-order harmonics exist only during the brief interval when the keying character is started or ended (when the amplitude of the keying wave is building up or dying down), their effects outside the normal communication channel are observed as pulses of very short duration. These pulses are called *key clicks*.

Tests have shown that practically all operators prefer to copy a signal which is “solid” on the “make” end of each dot or dash; i.e., one that does not build up too slowly but just slowly enough to have a slight click when the key is closed. The same tests indicate that the most pleasing and least difficult signal to copy, particularly at high speeds, is one that has a fairly soft “break” characteristic; i.e., one that has practically no click as the key is opened. A signal with heavy clicks on both make and break is difficult to copy at high speeds (and also causes considerable interference), but if it is too “soft” the dots and dashes will tend to run together. It is relatively simple to adjust the keying of a transmitter so that for all normal hand speeds (15 to 40 w.p.m.) the readability will be satisfactory while the keying still will not cause interference to reception of other signals near the frequency of the transmitter.

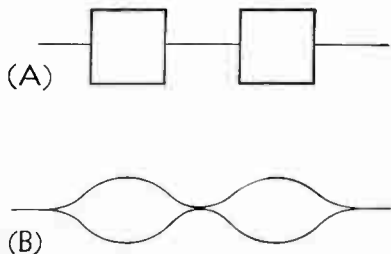


Fig. 601 — Extremes of possible keying waveshapes. A, rectangular characters; B, sine-wave characters.

Break-in keying — In code transmission, there are definite intervals, between dots and dashes and between words, when no power is being radiated by the transmitter. It is possible, therefore, to allow the receiver to operate continuously and thus be capable of receiving incoming signals during the keying intervals.

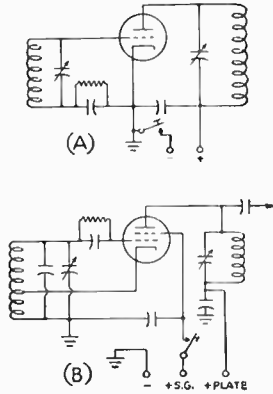


Fig. 602 A, shows plate keying; B, screen grid keying. Oscillator circuits are shown in both cases, but the same keying methods can be used with amplifier circuits.

This practice facilitates communication, because the receiving operator can signal the transmitting operator, by holding down the key of his transmitter, whenever he has failed to copy part of the message, and thus obtain a repetition of the part that is missing without waiting until the end of the message. This is called *break-in* operation.

Frequency stability — Keying should have no effect upon the output frequency of a properly designed and adjusted transmitter. However, in many instances keying will cause a "chirp," or small frequency change, at the instant of closing or opening the key, which makes the signal difficult to read. Multistage transmitters keyed in a stage subsequent to the oscillator usually are free from this condition, unless the keying causes line-voltage changes which in turn affect the frequency of the oscillator. When the oscillator is keyed for break-in operation, special care must be taken to insure that the signal does not have keying chirps.

Selecting the stage to key — It is advantageous from an operating standpoint to design the c.w. transmitter for break-in operation. In ordinary cases this dictates that the oscillator be keyed, since a continuously running oscillator will create interference in the receiver and thus prevent break-in operation on or near the transmitter frequency. On the other hand, it is easier to avoid a chirpy signal by keying a buffer or amplifier stage. In either case, the tubes following the keyed stage must be provided with sufficient fixed bias to limit the plate currents to safe values when the key is up and the tubes are not being excited (§ 8-9). Complete cut-off reduces the possibility of a back-wave if a stage other than the oscillator is keyed, but the keying waveform is not as well preserved and some clicks can be introduced even though the keyed stage itself produces

no clicks. It is a good general rule to bias the tubes so that they draw a key-up plate current equal to about 5 per cent of the normal key-down value.

Keyed power — The power broken by the key is an important consideration, both from the standpoint of safety for the operator and that of arcing at the key contacts. Keying the oscillator or a low-power stage is favorable in both respects. The use of a keying relay is highly recommended when a high-power circuit is keyed.

¶ 6-2 Keying Circuits

Plate-circuit keying — Any stage of the transmitter can be keyed by opening and closing the plate power circuit. Two methods are shown in Fig. 602. In A the key is in series with the negative lead from the plate power supply to the keyed stage. It could also be placed in the positive lead, although this is to be avoided whenever possible because the key is necessarily at the plate voltage above ground, and there is danger of shock unless a keying relay is used.

Fig. 602-B shows the key in the screen-supply lead of an electron-coupled oscillator. This can be considered to be a variation of plate keying.

Both the plate and screen-grid keying circuits, A and B of Fig. 602, respond well to the use of key-click filters, and are particularly suitable for use with crystal and self-controlled oscillators which are operated at low plate voltage and power input.

Power-supply keying — A variation of plate keying, in which the keying is introduced in the power-supply system itself, rather than in

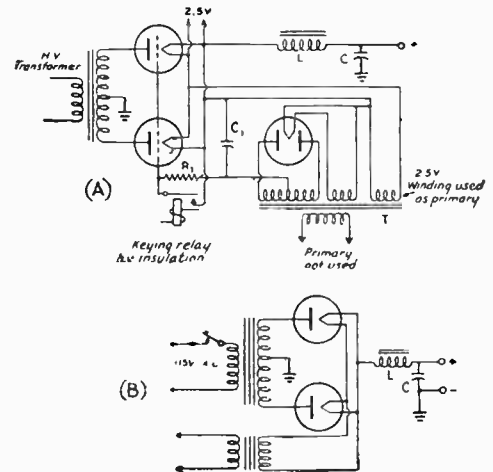


Fig. 603 — Power-supply keying. Grid-control rectifiers are used in A. Transformer T is a small multiple-secondary unit of the type used in receiver power supplies, and is used in conjunction with the full-wave rectifier tube to develop bias voltage for the grids of the high-voltage rectifiers. R₁ limits the load on the bias supply when the keying relay is closed; 50,000 ohms is a suitable value. C₁ may be 0.1 μfd. or larger. L and C constitute the smoothing filter for the high-voltage supply in both circuits. B shows direct keying of the transformer primary.

the connections between the power supply and transmitter, is illustrated by the diagrams in Fig. 603.

Fig. 603-A shows the use of grid-controlled rectifier tubes (§ 3-5) in the power supply. Keying is accomplished by applying suitable bias to the grids to cut off plate current flow when the key is open, and by removing the bias when the key is closed. Since in practice this circuit is used only with high-powered high-voltage supplies, a well-insulated keying relay is a necessity.

Direct keying of the primary of the plate power transformer for the keyed stage or stages is shown in Fig. 603-B. This and the method at A inherently have a keying lag because of the time constant (§ 2-6) of the smoothing filter. If enough filter is provided to reduce ripple to a low percentage (§ 8-4) the lag (§ 6-1) is too great to permit crisp keying at speeds above about 25 words per minute, although this type of keying is very effective in eliminating key clicks. A single-section plate-supply filter (§ 8-6) is about the most elaborate type that can be used if a reasonably good keying characteristic is to be achieved.

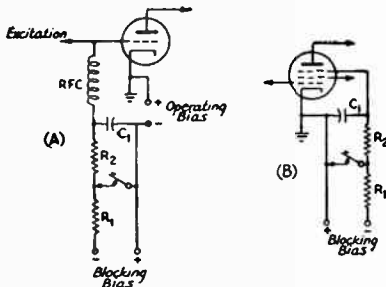


Fig. 604 — Blocked-grid keying. R_1 , the current-limiting resistor, should have a value of about 50,000 ohms. C_1 may have a capacity of 0.1 to 1 $\mu\text{fd.}$ depending upon the keying characteristic desired. R_2 also depends on the performance characteristic desired, values being of the order of 5000 to 10,000 ohms in most cases.

Blocked-grid keying — Keying may be accomplished by applying sufficient negative bias voltage to a control or suppressor grid to cut off plate current flow when the key is open, and by removing this *blocking* bias when the key is closed. The blocking bias voltage must be sufficient to overcome the r.f. grid voltage, in the case where the bias is applied to the control grid, and hence must be considerably higher than the nominal cut-off value for the tube at the operating d.c. plate voltage. The fundamental circuits are shown in Fig. 604.

In both circuits the key is connected in series with a resistor, R_1 , which limits the current drain on the blocking-bias source when the key is closed. R_2C_1 is a resistance-capacity filter (§ 2-11) for controlling the lag on make and break of the key circuit. The lag increases as the time constant (§ 2-6) of this circuit is made larger. Since grid current flows through R_2 when the key is closed in Fig. 604-A, additional

operating bias is developed, hence somewhat less bias is needed from the regular bias supply. The operating and blocking biases can be obtained from the same supply, if desired, by

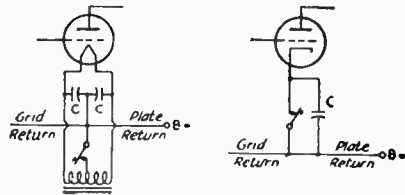


Fig. 605 — Center-tap and cathode keying. The condensers, C , are r.f. by-pass condensers. Their capacity is not critical, values of 0.001 to 0.01 $\mu\text{fd.}$ ordinarily being used.

utilizing suitable taps on a voltage divider (§ 8-10). For circuits in which no fixed bias is used R_2 can be the regular grid leak (§ 3-6) for the stage.

With blocked-grid keying a relatively small direct current is broken as compared to other systems. Thus any sparking at the key is reduced. The keying characteristic (lag) readily can be controlled by a suitable choice of values for C_1 and R_2 .

Cathode keying — Opening the d.c. circuits of both plate and grid simultaneously is called *cathode keying*. It is usually called *center-tap keying* with a directly heated filament-type tube, since in this case the key is placed in the filament-transformer center-tap lead. Typical circuits for this type of keying are shown in Fig. 605.

Cathode keying results in less sparking at the key contacts, for the same plate power, as compared with keying in the plate-supply lead. When used with an oscillator it does not respond as readily to key-click filtering (§ 6-3) as does plate keying, but there is little difference in this respect between the two systems when an amplifier is keyed.

6-3 Key-Click Reduction

R.f. filters — A spark at the key contacts, even though minute, will cause a damped oscillation to be set up in the keying circuit which may modulate the transmitter output or may simply be radiated by the wiring in the keying circuit. Interference from the latter source is usually confined to the immediate vicinity of the transmitter, and is similar in nature and effects to the click which is frequently heard in a receiver when an electric light is turned on or off. It can be minimized by isolating the key from the wiring by means of a low-pass filter (§ 2-11), which usually consists of an r.f. choke in each key lead, placed as close as possible to the key, and by-passed on the keying-line side by a condenser, as shown in Fig. 606. Suitable values must be determined by experiment. Choke values may range from 2.5 to 80 millihenrys, and condenser capacities from 0.001 to 0.1 $\mu\text{fd.}$

This type of r.f. filter is required in nearly every keying installation, in addition to the

lag circuits which are discussed in the next paragraph.

Lag circuits — A filter used to give a desired shape to the keying character, to eliminate unnecessary sidebands and consequent interference, is called a *lag circuit*. In one form, suitable for the circuits of Figs. 602 and 605, it consists of a condenser across the key terminals and an inductance in series with one of the leads. This is shown in Fig. 607. The optimum values of capacity and inductance must be found by experiment, but are not especially critical. If a high-voltage low-current circuit is being keyed a small condenser and large inductance will be necessary, while if a low-voltage high-current circuit is keyed the capacity required will be high and the inductance

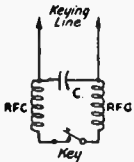


Fig. 606 — R.f. filter used for eliminating the effects of sparking at key contacts. Suitable values for best results with individual transmitters must be determined by experiment. Values for RFC range from 2.5 to 80 millihenries and for C from 0.001 to 0.1 μ fd.

small. For example, a 300-volt 6-ma. circuit will require about 30 henrys and 0.05 μ fd., while a 300-volt 50-ma. circuit needs about 1 henry and 0.5 μ fd. For any given circuit and fixed values of current and voltage, increasing the inductance will reduce the clicks on "make" and increasing the capacity will reduce the clicks on "break."

Blocked-grid keying is adjusted by changing the values of resistors and condensers in the circuit. In Fig. 604, the click on "make" is reduced by increasing the capacity of C_1 , and the click on break is reduced by increasing C_1 and/or R_2 . The values required for individual installations will vary with the amount of blocking voltage and the grid current. The constants given in Fig. 604 will serve as a first approximation.

Tube keying — A tube keyer is a convenient adjunct to the transmitter, because it allows the keying characteristic to be adjusted easily without necessitating condenser and inductance values which may not be readily available. It uses the plate resistance of a tube (or tubes in parallel) to replace the key in a plate or cathode circuit, the keyer tube (or tubes) being keyed by the blocked-grid method (§ 6-2). A typical circuit is shown in Fig. 608. Type 45 tubes are suitable because of their low plate resistance and consequent small voltage drop between plate and cathode. When a tube keyer is used to replace the key in a plate or cathode circuit, the power output of the stage will be somewhat reduced because of the voltage drop across the keyer tube, but this can be compensated for by a slight increase in the supply voltage. The use of a tube keyer makes the key itself entirely safe to handle, since the high resistance in series with the key and blocking voltage prevents possible danger of shock through contact with high-voltage circuits.

6-4 Checking Transmitter Keying

Clicks — Transmitter keying can be checked by listening to the signal on a superheterodyne receiver. The antenna should be disconnected, so that the receiver does not overload, and, if necessary, the r.f. gain may be reduced as well. Listening with the beat oscillator and a.v.c. off, the keying should be adjusted so that a slight click is heard as the key is closed but practically none can be heard when the key is released. When the keying constants have been adjusted to meet this condition, the clicks will be about optimum for all normal amateur work. If the clicks are too pronounced, they will cause interference with other amateur transmissions, and possibly to nearby broadcast receivers.

Chirps — Keying chirps (instability) may be checked by tuning in the signal or one of its harmonics on the highest frequency range of the receiver and listening with the b.f.o. on and the a.v.c. off. The gain should be sufficient to give moderate signal strength, but it should be low enough to preclude the possibility of overloading. Adjust the tuning to give a low-frequency beat note and key the transmitter. Any chirp introduced by the keying adjustment will be readily apparent. Listening to a harmonic will magnify the effect of any instability by the order of the harmonic, and thus make it more perceptible.

Oscillator keying — The keying of an amplifier is relatively straightforward and requires no special treatment, but a few additional pre-

cautions will be found necessary with oscillator keying. Any oscillator, either self-excited or crystal, will key well if it will oscillate at low plate voltages (of the order of one or two volts) and if its change in frequency with plate-voltage change is negligible. A crystal oscillator will oscillate at low plate voltages if a regenerative type of circuit such as the Tri-tet or grid-plate (§ 4-5) is used and if an r.f. choke is connected in series with the grid leak, to reduce loading on the crystal. Crystal oscillators of this type generally are free from chirp unless there is a relatively large air-gap between the crystal and top plate of the crystal holder, as is the case with a variable-frequency crystal set at the high-frequency end of its range.

Self-controlled oscillators can be made to meet the same requirements by using a high C/L ratio in the tank circuit, low plate and screen currents, and judicious feed-back adjustment (§ 3-7). A self-controlled oscillator intended to be keyed should be designed for good keying rather than maximum output.

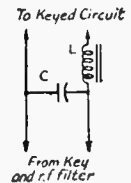


Fig. 607 — Lag circuit used for shaping the keying character to eliminate unnecessary sidebands. Actual values for any given circuit must be determined by experiment, and may range from 1 to 30 henrys for L and from 0.05 to 0.5 μ fd. for C, depending on the keyed current.

Stages following keying — When a keying filter is being adjusted, the stages following the keyed tube should be made inoperative by removing the plate voltage. This facilitates monitoring the keying without the introduction of additional effects. The following stages should then be added, one at a time, checking the keying after each addition. An increase in click intensity (for the same carrier strength) indicates that the clicks are being added in the stages following the one being keyed. The fixed bias on such stages should be sufficient to reduce the idling plate current (no excitation) to a low value, but not to zero. Under these conditions, any instability or tendency toward parasitic oscillations, either of which can adversely affect the keying characteristic, usually will evidence itself.

Monitoring of keying — Most operators find a keying monitor helpful in developing and maintaining a good "fist," especially if a "bug" or semi-automatic key is used. While several types have been devised, the most popular consists of an audio oscillator the output of which is coupled to the receiver loud speaker or headphones, and which is keyed simultaneously with the transmitter. Fig. 609 shows the circuit diagram of a simple keying-monitor oscillator. The plate voltage, as well as the heater voltage, is supplied by a 6.3-volt filament transformer. One section of the 6F8G dual triode is used as the rectifier to supply d.c. for the plate of the second section, which is used as the oscillator. A change in the value of R_1 will alter the output tone. The output terminal labeled *Gnd* should be connected directly to the receiver chassis, while P_1 should be connected to the "hot" side of the headphones. Shunting of the 'phones by the oscillator may cause some loss of volume on received signals, unless the coupling capacity, C_3 , is made sufficiently small. However, the capac-

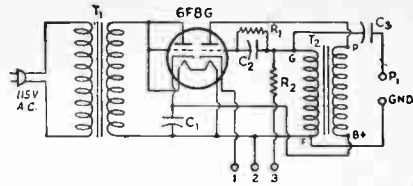


Fig. 609 — Circuit diagram of a keying monitor of the audio-oscillator type, with self-contained power supply. C_1 — 25- μ fd, 25-volt electrolytic. C_2 — 250- μ fd, mica. C_3 — Approximately 0.01 μ fd. (see text). R_1 — 0.15 megohm, $\frac{1}{2}$ watt. R_2 — Approximately 0.1 megohm, 1 watt (see text). T_1 — 6.3-volt 1-ampere filament transformer. T_2 — Small audio transformer, interstage type.

ity should be made large enough to provide good transfer of the oscillator signal.

If the transmitter oscillator is keyed for break-in, the keying terminals of the oscillator may be connected in parallel with those of the transmitter. With cathode keying, terminals 1 and 2 will be connected across the key, with terminal 2 going to the ground side of the key. With blocked-grid keying, terminals 2 and 3 go to the key and a resistance of 0.1 megohm or so is inserted in series with terminal 3.

Electronic keys — Several electronic circuits have been devised for producing automatic dots and dashes. A typical example is shown in Fig. 610. The values provide for a maximum speed of 60 w.p.m. with a 300-volt supply. R_1 and R_2 should be of the same type and ganged to form the speed control. To adjust for proper operation, ground the right cathode and adjust R_7 until the left plate current is zero. Do the same thing with the sections reversed, biasing the right section to cut-off temporarily. Adjust R_5 until the plate voltages are equal. Return the circuit to normal and check the average plate voltages with the key on the "dot" side. If they are unequal, adjust a fixed resistor connected in series with R_1 or R_2 until they are equal. On dashes, the plate voltage of the right section should drop one-third and that of the left section should increase by one-third. Adjust the size of C_3 until this condition is met. (See *QST* for March, 1944.)


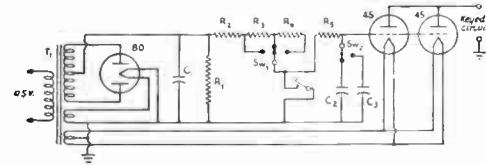


Fig. 608 — Vacuum-tube keyer circuit. The voltage drop across the tubes will be approximately 90 volts with the two Type 45 tubes shown, when the keyed current is 100 milliamperes. More tubes can be connected in parallel to reduce the drop. Suggested values are as follows: C_1 — 2- μ fd, 600-volt paper. C_2 — 0.003- μ fd, mica. C_3 — 0.005- μ fd, mica. R_1 — 0.25 megohm, 2 watt. R_2 — 50,000 ohms, 10 watt. R_3, R_4 — 5 megohms, $\frac{1}{2}$ watt. R_5 — 0.5 megohm, $\frac{1}{2}$ watt. Sw_1, Sw_2 — 1-circuit 3-position rotary switch. T_1 — Power transformer, 325 volts each side of center-tap, with 5-volt and 2.5-volt filament windings. A wider range of lag adjustment can be obtained by using additional resistors and condensers. Suggested values of capacity, in addition to C_2 and C_3 , are 0.001 and 0.002 μ fd. Resistors in addition to R_2 could be 2, 2.3 and 5 megohms. More switch positions will be required.

Fig. 610 — A multivibrator-type electronic key.

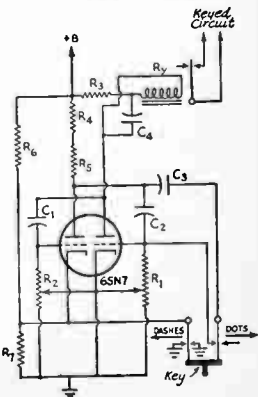- C_1, C_2 — 0.005- μ fd, mica.
- C_3 — 0.01- μ fd, 400-volt paper.
- C_4 — 0.01- μ fd, approximately.
- R_1, R_2 — 2-megohm variable (see text).
- R_3, R_4 — 50,000 ohms, $\frac{1}{2}$ watt.
- R_5 — 3000 ohms (or resistance equal to resistance of R_7).
- R_6 — 0.25 megohm, $\frac{1}{2}$ watt.
- R_7 — 75,000 ohms, $\frac{1}{2}$ watt.
- R_y — Sensitive relay (Elby).



Receiver Principles and Design

¶ 7-1 Elements of Receiving Systems

Basic requirements—The purpose of a radio receiving system is to abstract energy from passing radio waves and convert it into a form which conveys the intelligence contained in the transmitted signal. The receiver also must be able to select a desired signal and eliminate those not wanted. The fundamental processes involved are those of amplification and detection.

Detection—The high frequencies used for radio signaling are well beyond the audio-frequency range (§ 2-7), and therefore cannot be used to actuate a loudspeaker directly. Neither can they be used to operate other devices, such as relays, by means of which a message might be transmitted. The process of converting a modulated radio-frequency wave to a usable low frequency, called *detection* or *demodulation*, is essentially that of rectification (§ 3-1). The modulated carrier (§ 5-1) is thereby converted to a unidirectional current, the amplitude of which will vary at the same rate as the modulation. These low-frequency variations are readily amplified, and can be applied to the headphones, loudspeaker or other form of electromechanical device.

Code signals—The dots and dashes of code (c.w.) transmissions are rectified as described, but in themselves can produce no audible tone in the headphones or loudspeaker because they are of constant amplitude. For aural reception it is necessary to introduce a second radio frequency, differing from the signal frequency by a suitable audio frequency, into the detector circuit to produce an audible beat (§ 2-13). The frequency difference, and hence the *beat note*, is generally of the order of 500 to 1000 cycles, since these tones are within the range of optimum response of both the ear and the headset. If the source of the second radio frequency is a separate oscillator, the system is known as *heterodyne* reception; if the detector itself is made to oscillate and produce the second frequency, it is known as an *autodyne* detector.

Amplification—To build up weak signals to usable output level, modern receivers employ considerable amplification—often of the order of hundreds of thousands of times. Amplifiers are used at the frequency of the incoming signal (*r.f. amplifiers*), after detection (*a.f. amplifiers*), and, in superheterodyne receivers, at one or more intermediate radio frequencies (*i.f. amplifiers*). R.f. and i.f. amplifiers practically always employ tuned circuits.

Types of receivers—Receivers may vary in complexity from a simple detector with no amplification to multi-tube arrangements having amplification at several different radio frequencies as well as at audio frequency. A regenerative detector (§ 7-4) with or without audio-frequency amplification (§ 7-5) is known as a *regenerative receiver*; if the detector is preceded by one or more tuned r.f. amplifier stages (§ 7-6), the combination is known as a *r.f. (tuned radio frequency) receiver*. The *superheterodyne receiver* (§ 7-8) employs r.f. amplification at a fixed intermediate frequency as well as at the frequency of the signal itself, the latter being converted by the heterodyne process to the intermediate frequency.

At very-high frequencies the superregenerative detector (§ 7-4), usually with audio amplification, is used in the *superregenerative receiver* or *superregenerator*, providing large amplification of weak signals with simple circuit arrangements.

¶ 7-2 Receiver Characteristics

Sensitivity—Sensitivity is defined as the strength of the signal (usually expressed in microvolts) which must be applied to the input terminals of the receiver to produce a specified audio-frequency power output at the loudspeaker or headphones (§ 7-5). It is a measure of the amplification or gain of the receiver.

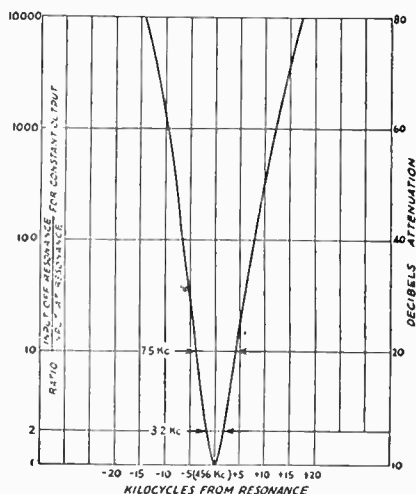


Fig. 701—Selectivity curve of a modern superheterodyne receiver. Relative response is plotted against deviations above and below the resonance frequency. The scale at the left is in terms of voltage ratios; the corresponding decibel steps are shown at the right.

Signal-to-noise ratio — Every receiver generates some noise of a hiss-like character, and signals weaker than the noise cannot be separated from it no matter how much amplification is used. This relation between noise and a weak signal is expressed by the term *signal-to-noise ratio*. It can be defined in various ways, one simple way being to give it as the ratio of signal power output to noise output from the receiver at a specified value of modulated carrier voltage applied to the input terminals.

The hiss-like noise mentioned above is inherent in the circuits and tubes of the receiver, and its amplitude depends upon the selectivity of the receiver. The greater the selectivity the smaller the noise, other things being equal (§ 7-6). In addition to inherent receiver noise, atmospheric electricity (natural "static") and electrical devices in the vicinity of the receiver also cause noise which adversely affects the signal-to-noise ratio.

Selectivity — Selectivity is the ability of a receiver to discriminate against signals of frequencies differing from that of the desired signal. The over-all selectivity will depend upon the selectivity of the individual tuned circuits and the number of such circuits.

The selectivity of a receiver is shown graphically by drawing a curve which gives the ratio of signal strength required at various frequencies off resonance to the signal strength at resonance, to give constant output. A *resonance curve* of this type (taken on a typical communications-type superheterodyne receiver) is shown in Fig. 701. The *band-width* is the width of the resonance curve (in cycles or kilocycles) of a receiver at a specified ratio; in Fig. 701, the band-widths are indicated for ratios of response of 2 and 10 ("2 times down" and "10 times down").

Selectivity for signals within a few kilocycles of the desired-signal frequency is called *adjacent-channel selectivity*, to distinguish it from the discrimination against signals considerably removed from the desired frequency.

Stability — The stability of a receiver is its ability to give constant output, over a period of time, from a signal of constant strength and frequency. Primarily, it means the ability to stay tuned to a given signal. However, a receiver which at some settings of its controls has a tendency to break into oscillation, or "howl," also is said to be unstable.

The stability of a receiver is affected principally by temperature variations, supply-voltage changes, and constructional features of a mechanical nature.

Fidelity — Fidelity is the relative ability of the receiver to reproduce in its output the modulation (keying, 'phone, etc.) carried by the incoming signal. For exact reproduction the band-width must be great enough to accommodate the highest modulation frequency transmitted, and the relative amplitudes of the various frequency components within the band must not be changed in the output.

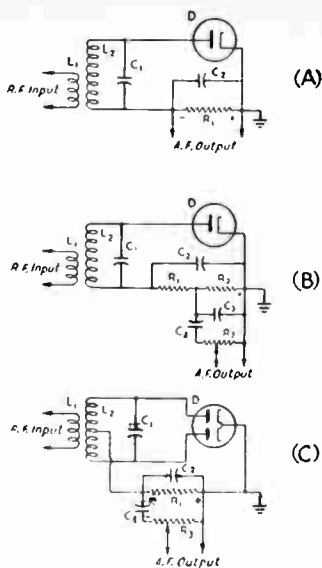


Fig. 702 — Simplified and practical diode detector circuits. A, the elementary half-wave diode detector; B, a practical circuit, with r.f. filtering and audio output coupling; C, full-wave diode detector, with output coupling indicated. The circuit, L_2C_1 , is tuned to the signal frequency; typical values for C_2 and R_1 in A and B are 250 μpfd , and 250,000 ohms, respectively; in B, C_2 and C_3 are 100 μpfd , each; R_1 , 50,000 ohms; and R_2 , 250,000 ohms. C_4 is 0.1 μfd , and R_3 may be 0.5 to 1 megohm.

7-3 Detectors

Characteristics — The important characteristics of a detector are its sensitivity, fidelity or linearity, resistance or impedance, and signal-handling capability.

Detector sensitivity is the ratio of audio-frequency output to radio-frequency input. *Linearity* is a measure of the ability of the detector to reproduce, as an audio frequency, the exact form of the modulation on the incoming signal. The *resistance* or *impedance* of the detector is important in circuit design, since a relatively low resistance means that power is consumed in the detector. The *signal-handling capability* means the ability of the detector to accept signals of a specified amplitude without overloading.

Diode detectors — The simplest detector is the diode rectifier. Circuits for both half-wave and full-wave (§ 8-3) diodes are given in Fig. 702. The simplified half-wave circuit at 702-A includes the r.f. tuned circuit, L_2C_1 , a coupling coil, L_1 , from which the r.f. energy is fed to L_2C_1 , and the diode, D , with its load resistance, R_1 , and by-pass condenser, C_2 . The flow of rectified r.f. current through R_1 causes a d.c. voltage to develop across its terminals, and this voltage varies with the modulation on the signal. The - and + signs show the polarity of the voltage. The variation in amplitude of the r.f. signal with modulation causes corresponding variations in the value of the d.c. voltage across R_1 . The load resistor, R_1 , usually

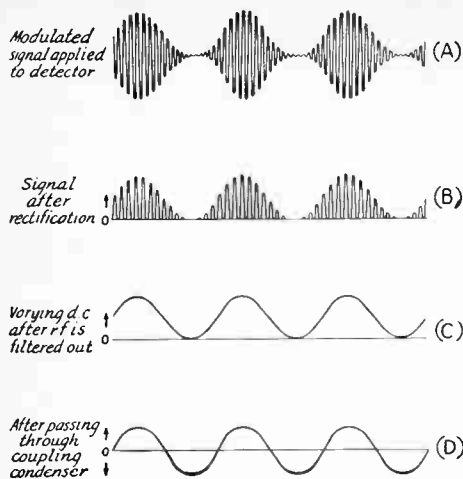


Fig. 703 — Diagrams showing the detection process.

has a rather high value of resistance, so that a fairly large voltage will develop from a small rectified-current flow.

The progress of the signal through the detector or rectifier is shown in Fig. 703. A typical modulated signal as it exists in the tuned circuit is shown at A. When applied to the rectifier tube, current flows from plate to cathode only during the part of the r.f. cycle when the plate is positive with respect to the cathode, so that the output of the rectifier consists of half-cycles of r.f. still modulated as in the original signal. These current "pulses" flow in the load circuit comprised of R_1 and C_2 , the resistance of R_1 and the capacity of C_2 being so proportioned that C_2 charges to the peak value of the rectified voltage on each pulse and retains enough charge between pulses so that the voltage across R_1 is smoothed out, as shown in C. C_2 thus acts as a filter for the radio-frequency component of the output of the rectifier, leaving a d.c. component which varies in the same way as the modulation on the original signal. When this varying d.c. voltage is applied to a following amplifier through a coupling condenser (C_1 in Fig. 702-B), only the variations in voltage are transferred, so that the final output signal is a.c., as shown in D.

In the circuit at 702-B, R_1 and C_2 have been divided for the purpose of providing a more effective filter for r.f. It is important to prevent the appearance of any r.f. voltage in the output of the detector, because it may cause overloading of a succeeding amplifier tube. The audio-frequency variations can be transferred to another circuit through a coupling condenser, C_1 in Fig. 702, to a load resistor, R_3 , which usually is a "potentiometer" (§ 8-10) so that the volume can be adjusted to a desired level.

The full-wave diode circuit at 702-C differs in operation from the half-wave circuit only in that both halves of the r.f. cycle are utilized. The full-wave circuit has the advantage that very little r.f. voltage appears across the load resistor, R_1 ,

because the midpoint of L_2 is at the same potential as the cathode, or "ground" for r.f.

The reactance of C_2 must be small compared to the resistance of R_1 at the radio frequency being rectified, but at audio frequencies must be relatively large compared to R_1 (§ 2-8, 2-13). This condition is satisfied by the values shown. If the capacity of C_2 is too large, response at the higher audio frequencies will be lowered.

Compared with other detectors, the sensitivity of the diode is low. Since the diode consumes power, the Q of the tuned circuit is reduced, bringing about a reduction in selectivity (§ 2-10). The linearity is good, however, and the signal-handling capability is high.

Grid-leak detectors — The grid-leak detector is a combination diode rectifier and audio-frequency amplifier. In the circuit of Fig. 704-A, the grid corresponds to the diode plate and the rectifying action is exactly the same as just described. The d.c. voltage from rectified-current flow through the grid leak, R_1 , biases the grid negatively with respect to cathode, and the audio-frequency variations in voltage across R_1 are amplified through the tube just as in a normal a.f. amplifier. In the plate circuit, R_2 is the plate load resistance (§ 3-3) and C_3 is a by-pass condenser to elim-

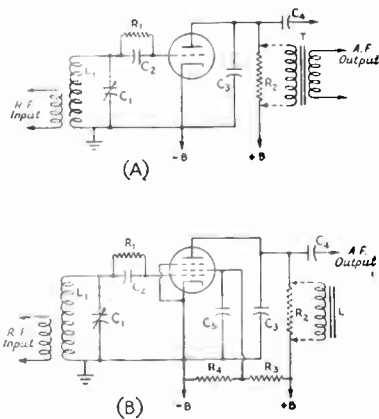


Fig. 704 — Grid-leak detector circuits, A, triode; B, pentode. A tetrode may be used in the circuit of B by neglecting the suppressor-grid connection. Transformer coupling may be substituted for resistance coupling in A, or a high-inductance choke may replace the plate resistor in B. L_1C_1 is a circuit tuned to the signal frequency. The grid leak, R_1 , may be connected directly from grid to cathode instead of across the grid condenser as shown. The operation with either connection will be the same. Representative values for components are:

Component	Circuit A	Circuit B
C_2	100 to 250 $\mu\text{fd.}$	100 to 250 $\mu\text{fd.}$
C_3	0.001 to 0.002 $\mu\text{fd.}$	250 to 500 $\mu\text{fd.}$
C_4	0.1 $\mu\text{fd.}$	0.1 $\mu\text{fd.}$
C_5		0.5 $\mu\text{fd.}$ or larger.
R_1	1 to 2 megohms.	1 to 5 megohms.
R_2	50,000 ohms.	100,000 to 250,000 ohms.
R_3		50,000 ohms.
R_4		20,000 ohms.
T	Audio transformer.	
L		500-henry choke.

The plate voltage in A should be about 50 volts for best sensitivity. In B, the screen voltage should be about 30 volts and the plate voltage from 100 to 250.

inate r.f. in the output circuit. C_4 is the output coupling condenser. With a triode, the load resistor, R_2 , may be replaced by an audio transformer, T , in which case C_4 is not used.

Since audio amplification is added to rectification, the grid-leak detector has considerably greater sensitivity than the diode. The sensitivity can be further increased by using a screen-grid tube instead of a triode, as at 704-B. The operation is equivalent to that of the triode circuit. The screen by-pass condenser, C_5 , should have low reactance (§ 2-8, 2-13) for both radio and audio frequencies. R_3 and R_4 constitute a voltage divider (§ 8-10) from the plate supply to furnish the proper d.c. voltage to the screen. In both circuits, C_2 must have low r.f. reactance and high a.f. reactance compared to the resistance of R_1 ; the same applies to C_3 with respect to R_2 .

Because of the high plate resistance of the screen-grid tube (§ 3-5), transformer coupling from the plate circuit of a screen-grid detector is not satisfactory. An impedance (L in Fig. 704-B) can be used in place of a resistor, with a gain in sensitivity because a high value of load impedance can be developed with little loss of plate voltage as compared to the voltage drop through a resistor. The coupling coil, L_2 , for a screen-grid detector should have an inductance of the order of 300 to 500 henrys.

The sensitivity of the grid-leak detector is higher than that of any other type. Like the diode, it "loads" the tuned circuit and reduces its selectivity. The linearity is rather poor, and the signal-handling capability is limited.

Plate detectors — The plate detector is arranged so that rectification of the r.f. signal takes place in the plate circuit of the tube, as contrasted to the grid rectification just described. Sufficient negative bias is applied to the grid to bring the plate current nearly to the cut-off point, so that the application of a signal to the grid circuit causes an increase in average plate current. The average plate current follows the changes in signal amplitude in a fashion similar to the rectified current in a diode detector.

Circuits for triodes and pentodes are given in Fig. 705. C_3 is the plate by-pass condenser, R_1 is the cathode resistor which provides the operating grid bias (§ 3-6), and C_2 is a by-pass for both radio and audio frequencies across R_1 (§ 2-13). R_2 is the plate load resistance (§ 3-3), across which a voltage appears as a result of the rectifying action described above. C_4 is the output coupling condenser. In the pentode circuit at B, R_3 and R_4 form a voltage divider to supply the proper potential (about 30 volts) to the screen, and C_5 is a by-pass condenser between screen and cathode. C_5 must have low reactance for both radio and audio frequencies.

In general, transformer coupling from the plate circuit of a plate detector is not satisfactory, because the plate impedance even of a triode is very high when the bias is set near the plate-current cut-off point (§ 3-2, 3-3). Im-

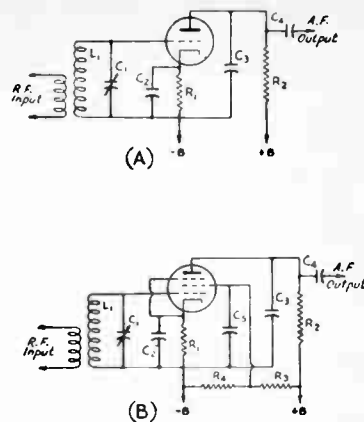


Fig. 705 — Circuits for plate detection. A, triode; B, pentode. The input circuit, L_1C_1 , is tuned to the signal frequency. Typical values for the other constants are:

Component	Circuit A	Circuit B
C_2	0.5 μ fd. or larger.	0.5 μ fd. or larger.
C_3	0.001 to 0.002 μ fd.	250 to 500 μ fd.
C_4	0.1 μ fd.	0.1 μ fd.
C_5		0.5 μ fd. or larger.
R_1	25,000 to 150,000 ohms.	10,000 to 20,000 ohms.
R_2	50,000 to 100,000 ohms.	100,000 to 250,000 ohms.
R_3		50,000 ohms.
R_4		20,000 ohms.

Plate voltages from 100 to 250 volts may be used. Effective screen voltage in B should be about 30 volts.

pedance coupling may be used in place of the resistance coupling shown in Fig. 705. The same order of inductance is required as with the screen-grid detector described previously.

The plate detector is more sensitive than the diode since there is some amplifying action in the tube, but less so than the grid-leak detector. It will handle considerably larger signals than the grid-leak detector, but is not quite so tolerant in this respect as the diode. Linearity, with the self-biased circuits shown, is good. Up to the overload point the detector takes no power from the tuned circuit, and so does not affect its Q and selectivity (§ 2-10).

Infinite-impedance detector — The circuit of Fig. 706 combines the high signal-handling capabilities of the diode detector with low distortion (good linearity), and, like the plate detector, does not load the tuned circuit to which it is connected. The circuit resembles that of the plate detector, except that the load resistance, R_1 , is connected between cathode and ground and thus is common to both grid and plate circuits, giving negative feed-back for the audio frequencies. The cathode resistor is by-passed for r.f. (C_1) but not for audio (§ 2-13), while the plate circuit is by-passed to ground for both audio and radio frequencies. R_2 forms, with C_3 , an RC filter (§ 2-11) to isolate the plate from the "B" supply at a.f.

The plate current is very low at no signal, increasing with signal as in the case of the plate detector. The voltage drop across R_1 similarly increases with signal, because of the

increased plate current. Because of this and the fact that the initial drop across R_1 is large, the grid cannot be driven positive with respect to the cathode by the signal, hence no grid current can be drawn.

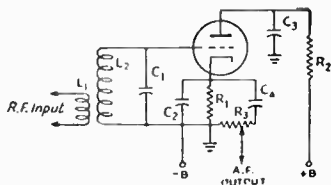


Fig. 706—The infinite-impedance linear detector. The input circuit, L_2C_1 , is tuned to the signal frequency. Typical values for the other constants are:
 C_2 —250 μfd . R_1 —0.15 megohm.
 C_3 —0.5 μfd . R_2 —25,000 ohms.
 C_4 —0.1 μfd . R_3 —0.25-megohm volume control.
 A tube having a medium amplification factor (about 20) should be used. Plate voltage should be 250 volts.

7-4 Regenerative Detectors

Circuits—By providing controllable r.f. feed-back or regeneration (§ 3-3) in a triode or pentode detector circuit, the incoming signal can be amplified many times, thereby greatly increasing the sensitivity of the detector. Regeneration also increases the effective Q of the circuit, and hence increases the selectivity (§ 2-10) by virtue of the fact that the maximum regenerative amplification takes place only at the frequency to which the circuit is tuned. The grid-leak type of detector is most suitable for the purpose. Except for the regenerative connection, the circuit values are identical with those previously described for this type of detector, and the same considerations apply. The amount of regeneration must be controllable, because maximum regenerative amplification is secured at the critical point where the circuit is just about to oscillate (§ 3-7) and the critical point in turn depends upon circuit conditions, which may vary with the frequency to which the detector is tuned.

Fig. 707 shows the circuits of regenerative detectors of various types. The circuit of A is for a triode tube, with a variable by-pass condenser, C_3 , in the plate circuit to control regeneration. When the capacity is small the tube does not regenerate, but as it increases toward maximum its reactance (§ 2-8) becomes smaller until a critical value is reached where there is sufficient feed-back to cause oscillation. If L_2 and L_3 are wound end-to-end in the same direction, the plate connection is to the outside of the plate or "tickler" coil, L_3 , when the grid connection is to the outside of L_2 .

The circuit of B is for a screen-grid tube, regeneration being controlled by adjustment of the screen-grid voltage. The tickler, L_3 , is in the plate circuit. The portion of the control resistor between the rotating contact and ground is by-passed by a large condenser (0.5 μfd . or more) to filter out scratching noise when the arm is rotated (§ 2-11). The feed-

back is adjusted by varying the number of turns on L_3 or the coupling (§ 2-11) between L_2 and L_3 , until the tube just goes into oscillation at a screen voltage of approximately 30 volts.

Circuit C is identical with B in principle of operation, except that the oscillating circuit is of the Hartley type (§ 3-7). Since the screen and plate are in parallel for r.f. in this circuit, only a small amount of "tickler"—that is, relatively few turns between the cathode tap and ground—-is required for oscillation.

Adjustment for smooth regeneration—The ideal regeneration control would permit the detector to go into and out of oscillation smoothly, would have no effect on the frequency of oscillation, and would give the same value of regeneration regardless of frequency and the loading on the circuit. In practice, the effects of loading, particularly the loading that occurs when the detector circuit is coupled to an antenna, are difficult to overcome. Likewise, the regeneration is affected by the frequency to which the grid circuit is tuned.

In all circuits it is best to wind the tickler at the ground or cathode end of the grid coil, and to use as few turns on the tickler as will allow the detector to oscillate easily over the whole tuning range at the plate (and screen, if a pentode) voltage which gives maximum sensitivity. Should the tube break into oscillation suddenly as the regeneration control is advanced, making a click, the operation often can be made smoother by changing the grid-leak resistance to a higher or lower value. The wrong grid leak plus too-high plate and screen voltage are the most frequent causes of lack of smoothness in going into oscillation.

Antenna coupling—If the detector is coupled to an antenna, slight changes in the antenna constants (as when the wire swings in a breeze) affect the frequency of the oscillations generated, and thereby the beat frequency when c.w. signals are being received. The tighter the antenna coupling is made, the greater will be the feed-back required or the higher will be the voltage necessary to make the detector oscillate. The antenna coupling should be the maximum that will allow the detector to go into oscillation smoothly with the correct voltages on the tube. If capacity coupling (§ 2-11) to the grid end of the coil is used, only a very small amount of capacity will be needed to couple to the antenna. Increasing the capacity increases the coupling.

At frequencies where the antenna system is resonant the absorption of energy from the oscillating detector circuit will be greater, with the consequence that more regeneration is needed. In extreme cases it may not be possible to make the detector oscillate with normal voltages, causing so-called "dead spots." The remedy for this is to loosen the antenna coupling to the point which permits normal oscillation and smooth regeneration control.

Body capacity—A regenerative detector occasionally shows a tendency to change fre-

quency slightly as the hand is moved near the dial. This condition (*body capacity*) can be caused by poor design of the receiver, or by the antenna if the detector is coupled directly to it. If body capacity is present when the antenna is disconnected, it can be eliminated by better shielding, and sometimes by r.f. filtering of the 'phone leads. Body capacity which is present only when the antenna is connected is caused by resonance effects in the antenna, which tend to cause a portion of a standing wave (§ 2-12) of r.f. voltage to appear on the ground lead and thus raise the whole detector circuit above ground potential. A good, short ground connection should be made to the receiver and the length of the antenna varied electrically (by adding a small coil or variable condenser in the antenna lead) until the effect is minimized. Loosening the coupling to the antenna circuit also will help.

Hum — Hum at the power-supply frequency may be present in a regenerative detector, especially when it is used in an oscillating condition for c.w. reception, even though the plate supply itself is free from ripple (§ 8-4). The hum may result from the use of a.c. on the tube heater, but effects of this type normally are troublesome only when the circuit of Fig. 707-C is used, and then only at 1.4 Mc. and higher frequencies. Connecting one side of the heater supply to ground, or grounding the center-tap of the heater transformer winding, is good practice to reduce hum, and the heater wiring should be kept as far as possible from the r.f. circuits.

House wiring, if of the "open" type, will have a rather extensive electrostatic field which may cause hum if the detector tube, grid lead, and grid condenser and leak are not electrostatically shielded. This type of hum is easily recognizable because of its rather high pitch, a result of harmonics (§ 2-7) in the power-supply system. The hum is caused by a species of grid modulation (§ 5-4).

Antenna resonance effects frequently cause a hum of the same nature as that just described which is most intense at the various resonance points, and hence varies with tuning. For this reason it is called tunable hum. It is prone to occur with a rectified a.c. plate supply (§ 8-1) when a standing wave effect of the type described in the preceding paragraph occurs, and is associated with the non-linearity of the rectifier tube in the plate supply. Elimination of antenna resonance effects as described and by-passing the rectifier plates to cathode (using by-pass condensers of the order of 0.001 μ fd.) usually will cure it.

Tuning — For c.w. reception, the regeneration control is advanced until the detector breaks into a "hiss," which indicates that the detector is oscillating. Further advancing the regeneration control after the detector starts oscillating will result in a slight decrease in the strength of the hiss, indicating that the sensitivity of the detector is decreasing.

The proper adjustment of the regeneration control for best reception of c.w. signals is where the detector just starts to oscillate, when it will be found that c.w. signals can be tuned in and will give a tone with each signal depending on the setting of the tuning control. As the receiver is tuned through a signal the tone first will be heard as a very high pitch, then will go down through "zero beat" (the region where the frequencies of the incoming signal and the oscillating detector are so nearly alike that the difference or beat is less than the lowest audible tone) and rise again on the other side, finally disappearing at a very high pitch. This behavior is shown in Fig. 708. It will be found that a low-pitched beat-note cannot be obtained from a strong signal because the detector "pulls in" or "blocks"; that is, the signal tends to control the detector in such a way that the latter oscillates at the signal frequency, despite the fact that the circuit may not be tuned exactly to resonance. This phenomenon, commonly observed when an oscillator is coupled to a source of a.c. voltage of approximately the

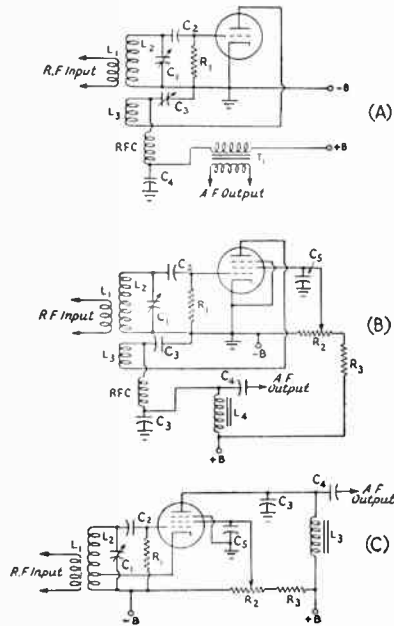


Fig. 707 — Triode and pentode regenerative detector circuits. The input circuit, L_2C_1 , is tuned to the signal frequency. The grid condenser, C_2 , should have a value of about 100 μ fd. in all circuits; the grid leak, R_1 , may range in value from 1 to 5 megohms. The tickler coil, L_3 , ordinarily will have from 10 to 25 per cent of the number of turns on L_2 ; in C, the cathode tap is about 10 per cent of the number of turns on L_2 above ground. Regeneration control condenser C_3 in A should have a maximum capacity of 100 μ fd. or more; by-pass condensers C_3 in B and C are likewise 100 μ fd. C_5 is ordinarily 1 μ fd. or more; R_2 , a 50,000-ohm potentiometer; R_3 , 50,000 to 100,000 ohms, L_4 in B (L_3 in C) is a 500-henry inductance, C_4 is 0.1 μ fd. in both circuits. T_1 in A is a conventional audio transformer for coupling from the plate of a tube to a following grid. RFC is 2.5 mh. In A, the plate voltage should be about 50 volts for best sensitivity. Pentode circuits require about 30 volts on the screen; plate voltage may be 100 to 250 volts.

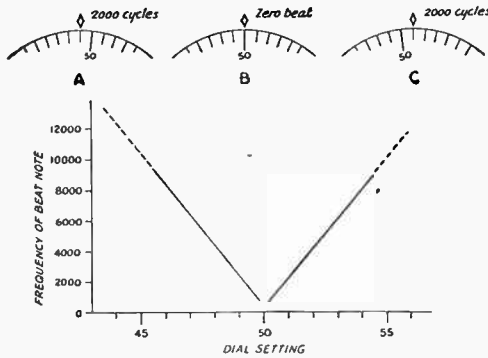


Fig. 708 — As the tuning dial of a receiver is turned past a c.w. signal, the beat-note varies from a high tone down through "zero beat" (no audible frequency difference) and back up to a high tone, as shown at A, B and C. The curve is a graphical representation of the action. The beat exists past 8000 or 10,000 cycles but usually is not heard because of the limitations of the audio system.

frequency at which the oscillator is operating, is called "locking-in"; the more stable of the two frequencies assumes control over the other. "Blocking" usually can be corrected by advancing the regeneration control until the beat-note occurs again. If the regenerative detector is preceded by an r.f. amplifier stage, the blocking can be eliminated by reducing the gain of the r.f. stage. If the detector is coupled to an antenna, the blocking condition can be eliminated by advancing the regeneration control or loosening the antenna coupling.

The point just after the receiver starts oscillating is the most sensitive condition for c.w. reception. Further advancing the regeneration control makes the receiver less prone to blocking by strong signals, but also less capable of receiving weak signals.

If the receiver is in the oscillating condition and a 'phone signal is tuned in, a steady audible beat-note will result. While it is possible to listen to 'phone if the receiver can be tuned to exact zero beat, it is more satisfactory to reduce the regeneration to the point just before the receiver goes into oscillation. This is also the most sensitive operating point.

Superregeneration — The limit to which ordinary regenerative amplification can be carried is the point at which oscillations commence, since at that point further amplification ceases. The *superregenerative* detector overcomes this limitation by introducing into the detector circuit an alternating voltage of a frequency somewhat above the audible range (of the order of 20 to 200 kilocycles), in such a way as to vary the detector's operating point (§ 3-3). As a consequence of the introduction of this *quench* or *interruption* frequency, the detector can oscillate only when the varying operating point is in a region suitable for the production of oscillations. Because the oscillations are constantly being interrupted, the regeneration can be greatly increased, and the amplified signal will build up to tremendous proportions. A one-tube superregenerative de-

detector is capable of an inherent sensitivity approaching the thermal-agitation noise level of the tuned circuit, and may have an antenna input sensitivity of two microvolts or better.

Because of its inherent characteristics, the superregenerative circuit is suitable only for the reception of modulated signals, and operates best on the very-high frequencies. Typical superregenerative circuits for the very-high frequencies are shown in Fig. 709.

The basic regenerative detector circuit is the ultraudion oscillator (§ 3 7). In Fig. 709-A the quench frequency is obtained from a separate oscillator and introduced into the plate circuit of the detector. The quench oscillator, operating at a low radio frequency, alternately allows oscillations to build up in the regenerative circuit and then causes them to die out. In the absence of a signal, the thermal agitation noise in the input circuit produces the voltage that initiates the build-up process. However, when an incoming signal provides the initiating pulse, it has the effect of advancing the starting time of the oscillations. This causes the area within the envelope to increase, as indicated in Fig. 710-C.

If regeneration in an ordinary regenerative circuit is carried sufficiently far, the circuit will break into a low-frequency oscillation simultaneously with that at the operating radio frequency. This low-frequency oscillation has much the same quenching effect as that from a separate oscillator, hence a circuit so operated is called a *self-quenching* superregenerative detector. The frequency of the quench oscillation depends upon the feed-back and upon the time constant of the grid leak and condenser, the oscillation being a "blocking" or "squegging" in which the grid accumulates a strong negative charge which does not leak off rapidly enough through the grid leak to prevent a relatively slow variation of the operating point.

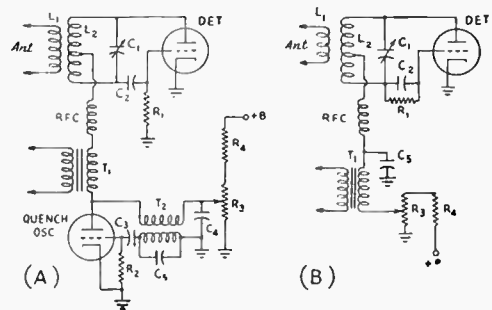


Fig. 709 — (A) Superregenerative detector circuit using a separate quench oscillator. (B) Self-quenched superregenerative detector circuit. L_2C_1 is tuned to the signal frequency. Typical values for other components are: $C_2 = 50 \mu\text{fd.}$, $R_4 = 50,000 \text{ ohms.}$ $C_3 = 500 \mu\text{fd.}$, $T_1 = \text{Audio transformer, plate-to-grid type.}$ $C_4 = 0.1 \mu\text{fd.}$ $R_1 = 2-10 \text{ megohms.}$ $R_2 = 50,000 \text{ ohms.}$ $R_3 = 50,000\text{-ohm potentiometer.}$ $RFC = \text{R.f. choke, value depending upon frequency. Small low-capacity chokes are required for v.h.f. operation.}$

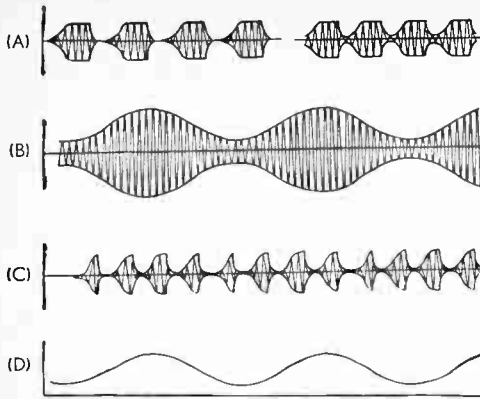


Fig. 710 — R.f. oscillation envelopes in a self-quenched superregenerative detector. Without signal (A at left) oscillations are completely quenched after each period, resuming in random phase depending on momentary noise voltages. At right, when the initiating pulses are supplied by a received signal the starting time of the oscillations is advanced causing the build-up period to begin before damping is complete. This advance is proportional to the carrier amplitude when modulated (B). Since the building-up period varies in accordance with modulation (C), when these wave trains are rectified the average rectified current is proportional to the amplitude of the signal. Amplitude modulation is therefore reproduced as an audio wave in the output circuit (D).

The greater the difference between the quenching and signal frequencies the greater the amplification, because the signal then has a longer period in which to build up during the nonquenching half-cycle when the resistance of the circuit is negative. This ratio should not exceed a certain limit, however, for during the quenched or nonregenerative intervals the input selectivity is merely that of the Q of the tuned circuit alone. The optimum quench frequency is in the neighborhood of 150 kc. for the 60-Mc. band and 250 kc. for 112 Mc.

The superregenerative detector has relatively little selectivity as compared to a regular regenerative detector, but discriminates against noise such as ignition interference. It also has marked a.v.c. action, strong signals being amplified much less than weak signals.

Adjustment of superregenerative detectors — Because of the greater amplification, the hiss noise when a superregenerative detector goes into oscillation is much stronger than with the ordinary regenerative detector. The most sensitive condition is at the point where the hiss first becomes marked. When a signal is tuned in, the hiss will disappear to a degree which depends upon the signal strength.

Lack of hiss indicates insufficient feedback at the signal frequency, or inadequate quench voltage. Antenna loading effects will cause dead spots which are similar to those in regenerative detectors and can be overcome by the same methods. The self-quenching detector may require critical adjustment of the grid leak and grid condenser values for smooth operation, since these determine the frequency and amplitude of the quench voltage.

7-5 Audio-Frequency Amplifiers

General — The ordinary detector does not produce very much audio-frequency power output — usually not enough to give satisfactory sound volume, even in headphone reception. Consequently, audio-frequency amplifiers are used after the detector to increase the power level. One amplifier usually is sufficient for headphones, but two stages generally are used where the receiver is to operate a loudspeaker. A few milliwatts of a.f. power is sufficient for headphones, but a loudspeaker requires a watt or more for good room volume.

In all except battery-operated receivers, the negative grid bias of audio amplifiers usually is secured from the voltage drop in a cathode resistor (§ 3-6). The cathode resistor must be bypassed by a condenser having low reactance at the lowest audio frequency to be amplified, compared to the resistance of the cathode resistor (10 per cent or less) (§ 2-8, 2-13). In battery-operated receivers, a separate grid-bias battery generally is used.

Headset and voltage amplifiers — The circuits shown in Fig. 711 are typical of those used for voltage amplification and for providing sufficient power for operation of headphones (§ 3-3). Triodes usually are preferred to pentodes because they are better suited to working into an audio transformer or headset, the input impedances of which are of the order of 20,000 ohms.

In these circuits, R_2 is the cathode bias resistor and C_1 the cathode by-pass condenser. The grid resistor, R_1 , gives volume control action (§ 5-9). Its value ordinarily is from 0.25 to 1 megohm. C_2 is the input coupling condenser, already discussed under detectors; it is, in fact, identical to C_4 in Figs. 704 and 705, if the amplifier is coupled to a detector.

Power amplifiers — A popular type of power amplifier is the single pentode, operated Class A or AB; the circuit diagram is given in Fig. 711-A. The grid resistor, R_1 , may be a potentiometer for volume control, as shown at

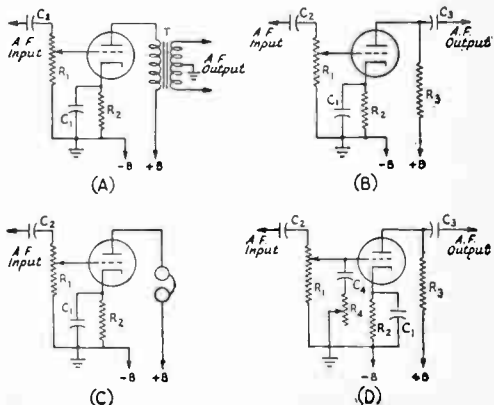


Fig. 711 — Audio amplifier circuits used for voltage amplification and to provide power for headphone output. The tubes are operated as Class-A amplifiers (§ 3-4).

R_1 in Fig. 711. The output transformer, T , should have a turns ratio (§ 2-9) suitable for the loudspeaker used; many of the small loudspeakers now available are furnished complete with output transformer.

When greater volume is needed, a pair of pentodes or tetrodes may be connected in push-pull (§ 3-3), as shown in Fig. 712-B. Transformer coupling to the voltage-amplifier stage is the simplest method of obtaining push-pull input for the amplifier grids. The inter-stage transformer, T_1 , has a center-tapped secondary with a secondary-to-primary turns ratio of about 2 to 1. An output transformer, T_2 , with a center-tapped primary must be used. No by-pass condenser is needed across the cathode resistor, R , since the a.f. current does not flow through the resistor as it does in single-tube circuits (§ 3-3).

Tone control—A tone control is a device for changing the frequency response (§ 3-3) of an audio amplifier; usually it is simply a method for reducing high-frequency response. This is helpful in reducing hissing and crackling noises without disturbing the intelligibility of the signal. R_4 and C_4 , in Fig. 711-D, together form an effective tone control of this type. The maximum effect is secured when the resistance of R_4 is entirely out of the circuit, leaving C_4 connected directly between grid and ground. R_4 should be large compared to the reactance of C_4 (§ 2-8) so that when its resistance is all in circuit the effect of C_4 on the frequency response is negligible.

Headphones and loudspeakers—Two types of headphones are in general use, the *magnetic* and *crystal* types. They are shown in cross-section in Fig. 713. In the magnetic type the signal is applied to a coil or pair of coils having a great many turns of fine wire wound on a permanent magnet. (Headphones having one coil are known as the "single-pole" type, while those having two coils, as shown in Fig. 713, are called "double-pole.") A thin circular diaphragm of iron is placed close to

the open ends of the magnet. It is tightly clamped by the earpiece assembly around its circumference, and the center is drawn toward the permanent magnet under some tension. When an alternating current flows through the windings the field set up by the current alternately aids and opposes the steady field of the permanent magnet, so that the diaphragm alternately is drawn nearer to and allowed to spring farther away from the magnet. Its motion sets the air into corresponding vibration. Although the d.c. resistance of the coils may be of the order of 2000 ohms, the a.c. impedance of a magnetic type headset will be of the order of 20,000 ohms at 1000 cycles.

In the crystal headphone, two piezoelectric crystals (§ 2-10) of Rochelle salts are cemented together in such a way that the pair tends to be bent in one direction when a voltage of a certain polarity is applied and to bend in the other direction when the polarity is reversed. The crystal unit is rigidly mounted to the earpiece, with the free end coupled to a diaphragm. When an alternating voltage is applied, the alternate bending as the polarity of the applied voltage reverses makes the diaphragm vibrate back and forth. The impedance is several times that of the magnetic type.

Magnetic-type headsets tend to give maximum response at frequencies of the order of 500 to 1000 cycles, with a considerable reduction of response (for constant applied voltage) at frequencies both above and below this region. The crystal type has a "flatter" frequency-response curve, and is particularly good at reproducing the higher audio frequencies. The peaked response curve of the magnetic type is advantageous in code reception, since it tends to reduce interference from signals having beat tones lying outside the region of maximum response, while the crystal type is better for the reception of voice and music. Magnetic headsets can be used in circuits in which d.c. is flowing, such as the plate circuit of a vacuum tube, providing the current is not too large to be carried safely by the wire in the coils; the limit is a few milliamperes. Crystal headsets must be used only on a.c. (since a steady d.c. voltage will damage the crystal unit), and consequently must be coupled to the tube through a device, such as a condenser, which isolates the d.c. voltage but permits the passage of an alternating current.

The most common type of loudspeaker is the *dynamic* type, shown in cross-section in Fig. 713. The signal is applied to a small coil (the *voice coil*) which is free to move in the gap between the ends of a magnet. The magnet is made in the form of a cylindrical coil slightly smaller than the form on which the voice coil is wound, with the magnetic circuit completed through a pole piece which fits around the outside of the voice coil leaving just enough clearance for free movement of the coil. The path of the flux through the magnet is as shown by the dotted lines in the figure.

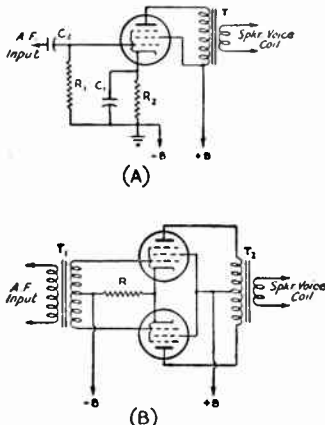


Fig. 712 — Power-output audio amplifier circuits. Either Class A or AB amplification (§ 3-4) may be used.

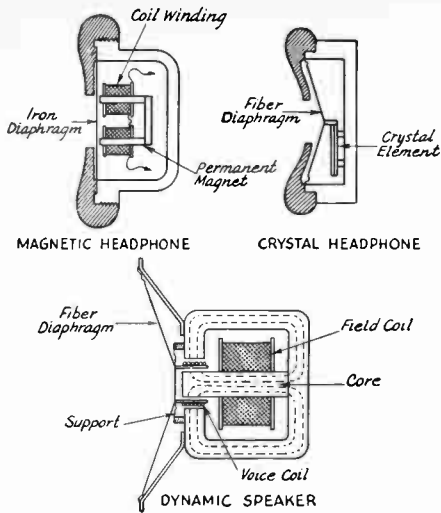


Fig. 713 — Headphone and loudspeaker construction.

The voice coil is supported so that it is free to move along its axis but not in other directions, and is fastened to a fiber or paper conical diaphragm. When current is sent through the coil it moves in a direction determined by the polarity of the current (§ 2-5), and thus moves back and forth when an alternating voltage is applied. The motion is transmitted by the diaphragm to the air, setting up sound waves.

The type of speaker shown in Fig. 713 obtains its fixed magnetic field by electromagnetic means, direct current being sent through the field coil for this purpose. Other types use permanent magnets to replace the electromagnet, and hence do not require a source of d.c. power. The voice coils of dynamic speakers have few turns and therefore low impedance, values of 3 to 15 ohms being representative.

7-6 Radio-Frequency Amplifiers

Circuits — Although there may be variations in detail, practically all r.f. amplifiers conform to the basic circuit shown in Fig. 714. A screen-grid tube, usually a pentode, is used, since a triode will oscillate when its grid and plate circuits are tuned to the same frequency (§ 3-5). The amplifier operates Class A, without grid current (§ 3-4). The tuned grid circuit, L_1C_1 , is coupled through L_2 to the antenna (or, in some cases, to a preceding stage). R_1 and C_2 are the cathode bias resistor and by-pass condenser, C_3 is the screen by-pass condenser, and R_2 is the screen dropping resistor. L_3 is the primary of the output transformer (§ 2-11), tightly coupled to L_4 , which, with C_5 , constitutes the tuned circuit feeding the detector or following amplifier. The input and output circuits, L_1C_1 and L_4C_5 , are both tuned to the signal frequency.

Shielding — The screen-grid construction of the amplifier tube prevents feed-back (§ 3-3) from plate to grid inside the tube, but in addition

it is necessary to prevent transfer of energy from the plate circuit to the grid circuit external to the tube. This is accomplished by enclosing the coils in grounded shielding containers and by keeping the plate and grid leads well separated. With "single-ended" tubes, care in laying out the wiring to obtain the maximum possible physical separation between plate and grid leads is necessary to prevent capacity coupling.

The shield around a coil will reduce the inductance and Q of the coil (§ 2-11) to an extent which depends upon the shielding material and the distance it is placed from the coil. Adjustments therefore must be made with the shield in place.

By-passing — In addition to shielding, good by-passing (§ 2-13) is imperative. This is not simply a matter of choosing the proper type and capacity of by-pass condenser. Short separate leads from C_3 and C_4 to cathode or ground are a prime necessity. At the higher radio frequencies even an inch of wire will have enough inductance to provide feed-back coupling, and hence cause oscillation, if the wire happens to be common to both the plate and grid circuits.

Gain control — The gain of an r.f. amplifier usually is varied by varying the grid bias. This method works best with variable- μ type tubes (§ 3-5), hence this type usually is found in r.f. amplifiers. In Fig. 714, R_3 and R_4 comprise the gain-control circuit. R_3 is the control resistor (§ 3-6) and R_4 a dropping resistor of such value as to make the voltage across the outside terminals of R_3 about 50 volts (§ 8-10). The gain is maximum with the variable arm on R_3 all the way to the left (grounded), and minimum at the right. R_3 could simply be placed in series with R_1 , omitting R_4 entirely, but the range of control with this connection is limited because it depends on the cathode current alone.

In a multi-tube receiver the gain of several stages may be varied simultaneously, a single control sufficing for all. The lower ends of the several cathode resistors (R_1) are then connected together and to the movable contact on R_3 in Fig. 714.

Circuit values — The value of the cathode resistor, R_1 , should be calculated for the minimum recommended bias for the tube used. The capacities of C_2 , C_3 and C_4 must be such that the reactance is low at radio frequencies; this condition is easily met by using 0.01- μ fd. condensers at communication frequencies, or 0.001 to 0.002 mica units at very-high fre-

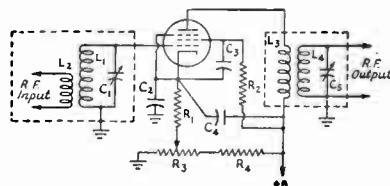


Fig. 714 — Basic circuit of a tuned radio-frequency amplifier. Component values are discussed in the text.

quencies up to 112 Mc. R_2 is found by taking the difference between the recommended plate and screen voltages, then substituting this and the rated screen current in Ohm's Law (§ 2-6). R_3 must be selected on the basis of the number of tubes to be controlled; a resistor must be chosen which is capable of carrying, at its low-resistance end, the sum of all the tube currents plus the bleeder current. A resistor of suitable current-carrying capacity being found, the bleeder current necessary to produce a drop through it of about 50 volts can be calculated by Ohm's Law. The same formula will give R_4 , using the plate voltage less 50 volts for E and the bleeder current previously found for I .

The constants of the tuned circuits will depend upon the frequency range, or band, to be covered. A fairly high L/C ratio (§ 2-10) should be used on each band; this is limited, however, by the irreducible minimum capacities. To an allowance of 10 to 20 μfd . for tube and stray capacities should be added the minimum capacity of the tuning condenser.

If the input circuit of the amplifier is connected to an antenna, the coupling coil, L_2 , should be adjusted to provide critical coupling (§ 2-11) between the antenna and grid circuit. This will give maximum energy transfer. The turns ratio of L_1/L_2 will depend upon the frequency, the type of tube used, the Q of the tuned circuit and the constants of the antenna system, and in general is best determined experimentally. The selectivity will increase as the coupling is reduced below this "optimum" value, a consideration which it is well to keep in mind if selectivity is of more importance than maximum gain.

The output-circuit coupling depends upon the plate resistance (§ 3-2) of the tube, the input resistance of the succeeding stage, and the Q of the tuned circuit, L_3C_6 . L_3 usually is coupled as closely as possible to L_4 (avoiding the necessity for an additional tuning condenser across L_3) and the energy transfer is maximum when L_3 has $\frac{2}{3}$ to $\frac{4}{5}$ as many turns as L_4 , with ordinary receiving pentodes.

Tube and circuit noise — In any conductor electrons will be moving in random directions simultaneously and, as a result, small irregular voltages are developed across the conductor terminals. The voltage is larger the greater the resistance of the conductor and the higher its temperature. This is known as the *thermal-agitation* effect, and it produces a hiss-like noise voltage distributed uniformly throughout the radio-frequency spectrum. The thermal-agitation noise voltage appearing across the terminals of a tuned circuit will be the same as in a resistor of a value equal to the parallel impedance (§ 2-10) of the tuned circuit, even though the actual circuit resistance is low. Hence, the higher the Q of the circuit, the greater the thermal agitation noise.

Another component of hiss noise is developed in the tube because the rain of electrons on the plate is not entirely uniform. Small ir-

regularities caused by gas in the tube also contribute to the effect. Tube noise varies with the type of tube: in general, the higher the cathode current and the lower the mutual conductance of the tube, the more internal noise it will generate.

To obtain the best signal-to-noise ratio, the signal must be made as large as possible at the grid of the tube, which means that the antenna coupling must be adjusted to that end and also that the Q of the grid tuned circuit must be high. A tube with low inherent noise obviously should be chosen. In an amplifier having good signal-to-noise ratio, the thermal-agitation noise will be greater than the tube noise. This can easily be checked by disconnecting the antenna so that no outside noise is being introduced into the receiver, then grounding the grid through a 0.01- μfd . condenser and observing whether there is a decrease in noise. If there is no change the tube noise is greatly predominant, indicating a poor signal-to-noise ratio in the stage. The test is valid only if there is no regeneration in the amplifier. The signal-to-noise ratio will decrease as the frequency is raised, because it becomes increasingly difficult to obtain a tuned circuit of high effective Q (§ 7-7).

The first stage of the receiver is the important one from the standpoint of signal-to-noise ratio. Noise generated in the second and subsequent stages, while comparable in magnitude to that generated in the first, is masked by the amplified noise and signal from the first stage. After the second stage, further contributions by tubes and circuits to the total noise are inconsequential in any normal receiver.

Tube input resistance — At high radio frequencies the tube may consume power from the tuned grid circuit, even though the grid is not driven positive by the signal. Above 7 Mc. all tubes "load" the tuned circuit to some extent, the amount of loading varying with the type of tube. This effect comes about because of the transit time necessary for electrons to travel from the cathode to the grid becomes comparable to the time of one r.f. cycle, and because of the degenerative effect (§ 3-3) of the cathode lead inductance. It becomes more pronounced as the frequency is increased. Certain types of tubes may have an input resistance of only a few thousand ohms at 28 Mc. and as little as a few hundred ohms at very-high frequencies. The input resistance of the same tubes at 7 Mc. and lower frequencies may be so high as to be considered infinite.

This *input-loading* effect is in addition to the normal decrease in the Q of the tuned circuit alone, because of increased losses in the coil and condenser at the higher frequencies. Thus the selectivity and gain of the circuit both are affected adversely by increasing frequency.

Comparison of tubes — At 7 Mc. and lower frequencies, the signal-to-noise ratio, gain, and selectivity of an r.f.-amplifier stage are sufficiently high with any of the standard receiving

tubes. At 14 Mc. and higher, however, this is no longer true, and the choice of a tube must be based on several conflicting considerations.

Gain is highest with high mutual-conductance pentodes, the 6AB7 and 6AC7 being examples of this type. These tubes also develop less noise than any of the others. The input-loading effect is greatest with them, however, so that selectivity is decreased and the tuned-circuit gain is lowered.

Pentodes, such as the 6K7, 6J7 and corresponding types in glass, have lesser input-loading effects at high frequencies, moderate gain, and relatively high inherent noise.

"Acorn" and equivalent miniature pentodes are excellent from the input-loading standpoint; gain is about the same as with standard types, and the inherent noise is somewhat lower.

Where selectivity is paramount the acorns are best, the standard pentodes second, and the 6AB7-6AC7 types worst. On signal-to-noise ratio the latter tubes are first, acorns are second and standard pentodes third. The same order of precedence holds for over-all gain.

At 56 Mc. the standard types are usable, but acorns are capable of better performance because of lesser loading. The 954 and 956 and the corresponding types, 9001 and 9003, are examples of types satisfactory for r.f. amplification at 100 Mc. and higher.

7-7 Tuning and Band-Changing Methods

Band-changing — The resonant circuits which are tuned to the frequency of the incoming signal constitute a special problem in the design of amateur receivers, since the amateur frequency assignments consist of groups or bands of frequencies at widely spaced intervals. The same LC combination cannot be used for, say, 14 Mc. to 3.5 Mc., because of the impracticable maximum-minimum capacity ratio required, and also because the tuning would be excessively critical with such a large frequency range. It is necessary, therefore, to provide a means for changing the circuit constants for various frequency bands. As a matter of convenience the same tuning condenser usually is retained, but new coils are inserted in the circuit for each band.

There are two favorite methods of changing inductances. One is to use a switch having an appropriate number of contacts, which connects the desired coil and disconnects the others. The second is to use coils wound on forms with contacts (usually pins) which can be plugged in and removed from a socket.

Bandspreading — The tuning range of a given coil and variable condenser will depend upon the inductance of the coil and the change in tuning capacity. For ease of tuning, it is desirable to adjust the tuning range so that practically the whole dial scale is occupied by the band in use. This is called *bandspreading*. Because of the varying widths of the bands, special tuning methods must be devised to give

the correct maximum-minimum capacity ratio on each band. Several of these methods are shown in Fig. 715.

In A, a small *bandspread condenser*, C_1 (15 to 25 μfd . maximum capacity), is used in parallel with a condenser, C_2 , which is usually large enough (140 to 175 μfd .) to cover a 2-to-1 frequency range. The setting of C_2 will determine the minimum capacity of the circuit, and the maximum capacity for bandspread tuning will be the maximum capacity of C_1 plus the setting of C_2 . The inductance of the coil can be adjusted so that the maximum-minimum ratio will give adequate bandspread. In practicable circuits it is almost impossible, because of the non-harmonic relation of the various bands, to get full bandspread on all bands with the same pair of condensers, especially when the coils are wound to give continuous frequency coverage on C_2 , which is variously called the *band-setting* or *main-tuning* condenser. C_2 must be reset each time the band is changed.

The method shown at B makes use of condensers in series. The tuning condenser, C_1 , may have a maximum capacity of 100 μfd . or more. The minimum capacity is determined principally by the setting of C_3 , which usually has low capacity, and the maximum capacity by the setting of C_2 , which is of the order of 25 to 50 μfd . This method is capable of close adjustment to practically any desired degree of bandspread. Either C_2 and C_3 must be adjusted for each band or separate pre-adjusted condensers must be switched in.

The circuit at C also gives complete spread on each band. C_1 , the bandspread condenser, may have any convenient value of capacity; 50 μfd . is satisfactory. C_2 may be used for continuous frequency coverage ("general coverage") and as a band-setting condenser. The effective maximum-minimum capacity ratio depends upon the capacity of C_2 and the point at which C_1 is tapped on the coil. The nearer the tap to the bottom of the coil, the greater the bandspread, and vice versa. For a given coil and tap, the bandspread will be greater if C_2 is set at larger capacity. C_2 may be mounted in the plug-in coil form and pre-set, if desired. This requires a separate condenser for each band, but eliminates the necessity for resetting C_2 each time the band is changed.

Ganged tuning — The tuning condensers of the several r.f. circuits may be coupled together mechanically and operated by a single control. However, this operating convenience involves more complicated construction, both

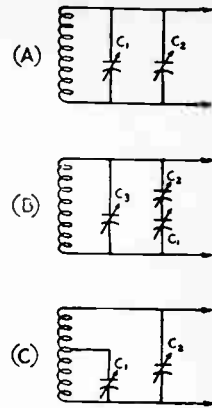


Fig. 715 — Essentials of the three basic band-spread tuning systems.

electrically and mechanically. It becomes necessary to make the various circuits *track* — that is, tune to the same frequency at each setting of the tuning control.

True tracking can be obtained only when the inductance, tuning condensers, and circuit minimum and maximum capacities are identical in all "ganged" stages. A small *trimmer* or *padding* condenser may be connected across the coil, so that variations in minimum capacity can be compensated. The fundamental circuit is shown in Fig. 716, where C_1 is the trimmer and C_2 the tuning condenser. The use of the trimmer necessarily increases the minimum circuit capacity, but it is a necessity for satisfactory tracking. Midget condensers having maximum capacities of 15 to 30 μfd . are commonly used.

The same methods are applied to bandspread circuits which must be tracked. The circuits are identical with those of Fig. 715. If both general-coverage and bandspread tuning are to be available, an additional trimmer condenser must be connected across the coil in each circuit shown. If only amateur-band tuning is desired, however, then C_3 in Fig. 715-B, and C_2 in Fig. 715-C serve as trimmers.

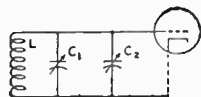


Fig. 716 — Showing the use of a trimmer condenser, to set the minimum circuit capacity in order to obtain true tracking for gang-tuning.

The coil inductance can be adjusted by starting with a larger number of turns than necessary and removing a turn or fraction of a turn at a time until the circuits track satisfactorily. An alternative method, provided the inductance is reasonably close to the correct value initially, is to make the coil so that the last turn is variable with respect to the whole coil, or to use a single short-circuited turn the position of which can be varied with respect to the coil. The application of these methods is shown in Fig. 717.

V.h.f. circuits — Interelectrode capacities are practically constant for a given tube regardless of the operating frequency, and the same is approximately true of stray circuit capacities. Hence, at very-high frequencies these capacities become an increasingly larger part of the usable tuning capacity, and reasonably high L/C ratios (§ 2-10) are more difficult to secure as the frequency is raised. Because of this irreducible minimum capacity, standard types of tubes cannot be tuned to frequencies higher than about 200 Mc., even when the inductance in the circuit is simply that of a straight wire between the tube elements.

Along with these capacity effects, the input loading (§ 7-6) increases rapidly at very-high frequencies, so that ordinary tuned circuits have very low effective Q s when connected to the grid circuit of a tube. The effect is still further aggravated by the fact that losses in the tuned circuit itself are higher, causing a

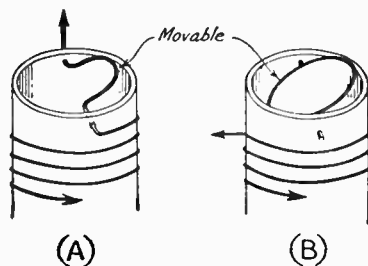


Fig. 717 — Methods of adjusting the inductance for ganging. The half turn in A can be moved so that its magnetic field either aids or opposes the field of the coil. The shorted loop in B is not connected to the coil, but operates by induction. It will have no effect on the coil inductance when the plane of the loop is parallel to the axis of the coil, and will give maximum reduction of the coil inductance when perpendicular to the coil axis.

still further reduction in Q . For these reasons, the frequency limit at which an r.f. amplifier will give any gain is in the vicinity of 60 Mc. with standard tubes. At higher frequencies there will be a loss, instead of amplification. This condition can be mitigated somewhat by taking steps to improve the effective Q of the circuit, either by tapping the grid down on the coil, as shown in Fig. 718-A, or by using a lower L/C ratio (§ 2-10). The Q of the tuned circuit alone can be greatly improved by using a linear circuit (§ 2-12), which when properly constructed will give Q s much higher than those attainable at lower frequencies with conventional coils and condensers. The concentric type of line, Fig. 718-B, is best both from the standpoint of Q and of adaptability to nonsymmetrical circuits such as are used in receivers. Since the capacity and resistance loading effects of the tube are still present, the Q of such a circuit will be destroyed if the grid-cathode circuit of the tube is connected directly across it. Hence, tapping down on the line, as shown, is necessary.

Very-high-frequency amplifiers employ tubes of the acorn or miniature type, which have the least loading effect as well as low interelectrode capacities. The smaller loading effect means higher input resistance, and, for a given loaded Q of the tuned circuit, a higher voltage is developed between the grid and cathode. Thus the amplification of the stage is higher and the noise level lower.

A concentric circuit may be tuned by varying the length of the inner conductor (usually by using close-fitting tubes, one sliding inside the other) or by connecting an ordinary tuning condenser across the line. Tapping the condenser down, as shown in Fig. 718-B, gives a bandspread effect, which is advantageous. It also helps to keep the Q of the circuit higher than it would be with the condenser connected directly across the open end of the line, since at very-high frequencies most condensers have losses which cannot be neglected.

Ordinary bakelite-based receiving-type tubes will function quite satisfactorily as oscillators

and superregenerative detectors at frequencies where r.f. amplification is impossible with standard tubes (as in the 112-Mc. band), since tube losses are compensated for by energy taken from the power supply. Ordinary coil and condenser circuits are practicable with such tubes at 112 Mc. At higher frequencies, however, the special v.h.f. tubes are essential.

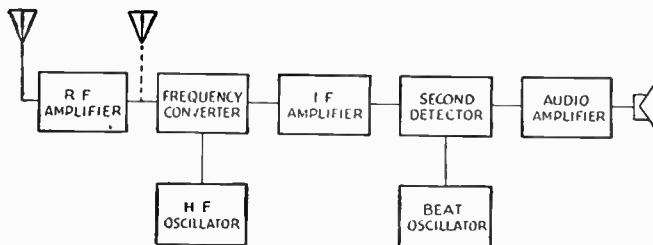


Fig. 719 — Block diagram of the basic elements of the superheterodyne

7-8 The Superheterodyne

Principles — In the *superheterodyne*, or *superhet*, receiver the frequency of the incoming signal is changed to a new radio frequency, the *intermediate frequency* (i.f.), then amplified, and finally detected. The frequency is changed by means of the heterodyne process (§ 7-1), the output of an adjustable *local oscillator* (the *h.f. oscillator*) being combined with the incoming signal in a *mixer* or *converter* stage (*first detector*) to produce a beat frequency equal to the intermediate frequency.

Fig. 719 gives the essentials of the superheterodyne in block form. C.w. signals are made audible by heterodyning the signal at the second detector by the *beat-frequency oscillator* (b.f.o.) or *beat oscillator*, set to differ from the i.f. by a suitable audio frequency.

As a numerical example, assume that an intermediate frequency of 455 kc. is chosen and that the incoming signal is on 7000 kc. Then the h.f. oscillator frequency may be set to 7455 kc., in order that the beat frequency (7455 minus 7000) will be 455 kc. The h.f. oscillator also could be set to 6545 kc., which will give the same frequency difference. To produce an audible c.w. signal of, say, 1000 cycles at the second detector, the beat oscillator would be set to either 454 kc. or 456 kc.

Characteristics — The frequency-conversion process permits r.f. amplification at a relatively low frequency. Thus high selectivity can be obtained, and this selectivity is constant regardless of the signal frequency. Higher gain also is possible at the lower frequency. The separate oscillators can be designed for

stability, and, since the h.f. oscillator is working at a frequency considerably removed from the signal frequency, its stability is practically unaffected by the incoming signal.

Images — Each h.f. oscillator frequency will cause i.f. response at two signal frequencies, one higher and one lower than the oscillator frequency. If the oscillator is set to 7455 kc. to respond to a 7000-ke. signal, for example, it will respond also to a signal on 7910 kc., which likewise gives a 455-ke. beat. The undesired signal of the two is called the *image*.

The radio-frequency circuits of the receiver (those used before the frequency is converted to the i.f.) normally are tuned to the desired signal, so that the selectivity of the circuits reduces the response to the image signal. If the desired signal and image have equal strengths at the input terminals of the receiver, the ratio of the receiver voltage output from the desired signal to that from the image is called the *signal-to-image ratio*, or *image ratio*.

The image ratio depends upon the selectivity of the r.f. tuned circuits preceding the mixer tube. Also, the higher the intermediate frequency, the higher the image ratio, since raising the i.f. increases the frequency separation between the signal and the image and places the latter farther away from the peak of the resonance curve (§ 2-10) of the signal-frequency input circuits.

Other spurious responses — In addition to images, other signals to which the receiver is not ostensibly tuned may be heard. Harmonics of the high-frequency oscillator may beat with signals far removed from the desired frequency to produce output at the intermediate frequency; such spurious responses can be reduced by adequate selectivity before the mixer stage, and by using sufficient shielding to prevent signal pick-up by any means other than the antenna. When a strong signal is received, the harmonics (§ 2-7) generated by rectification in the second detector may, by stray coupling, be introduced into the r.f. or mixer circuit and converted to the intermediate frequency, to go through the receiver in the same way as an ordinary signal. These "birdies" appear as a heterodyne beat on the desired signal, and are principally bothersome when the frequency of the incoming signal is not greatly different from the intermediate frequency. The cure is proper circuit isolation and shielding.

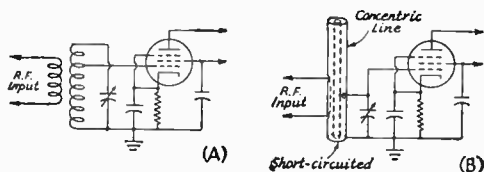


Fig. 718 — Circuits of improved Q for very-high frequencies. A, reducing tube loading by tapping down on the resonant circuit; B, use of a concentric-line circuit, with the tube similarly tapped down. The line should be a quarter-wave long, electrically; because of the additional shunt capacity represented by the tube, the physical length will be somewhat less than given by the formula (§ 10-5). In general, this reduction in length will be greater the higher the grid tap on the inner conductor. The coupling turn should be parallel to the axis of the line and must be insulated from the outer conductor.

Harmonics of the beat oscillator also may be converted in similar fashion and amplified through the receiver; these responses can be reduced by shielding the beat oscillator and operating it at low output level.

The double superheterodyne — At high and very-high frequencies it is difficult to secure an adequate image ratio when the intermediate frequency is of the order of 455 kc. To reduce image response the signal frequently is converted first to a rather high (1500, 5000, or even 10,000 kc.) intermediate frequency, and then — sometimes after further amplification — reconverted to a lower i.f. where higher adjacent-channel selectivity can be obtained. Such a receiver is called a *double superheterodyne*.

¶ 7-9 Frequency Converters

Characteristics — The first detector or mixer resembles an ordinary detector. A circuit tuned to the intermediate frequency is placed in the plate circuit of the mixer, so that the highest possible i.f. voltage will be developed. The signal- and oscillator-frequency voltages appearing in the plate circuit are bypassed to ground, since they are not wanted in the output. The i.f. tuned circuit should have low impedance for these frequencies, a condition easily met if they do not approach the intermediate frequency.

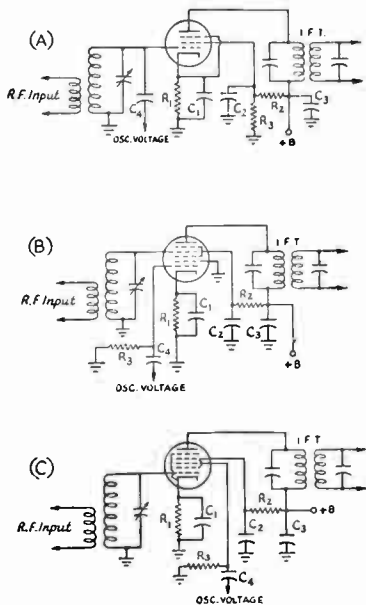


Fig. 720 — Mixer or converter circuits. A, grid injection with a pentode plate detector; B and C, separate injection circuits for converter tubes. Circuit values are:

Component	Circuit A	Circuit B	Circuit C
C ₁ , C ₂ , C ₃ —	0.01–0.1 μfd.	0.01–0.1 μfd.	0.01–0.1 μfd.
C ₄ —	Approx. 1 μμfd.	50–100 μμfd.	50–100 μμfd.
R ₁ —	10,000 ohms.	300 ohms.	500 ohms.
R ₂ —	0.1 megohm.	50,000 ohms.	15,000 ohms.
R ₃ —	50,000 ohms.	50,000 ohms.	50,000 ohms.

Plate voltage should be 250 in all circuits. If a 6AB7 or 6AC7 tube is used in Circuit A, R₁ should be 500 ohms.

The *conversion efficiency* of the mixer is the ratio of i.f. output voltage from the plate circuit to r.f. signal voltage applied to the grid. High conversion efficiency is desirable. The mixer tube noise also should be low if a good signal-to-noise ratio is wanted, particularly if the mixer is the first tube in the receiver.

The mixer should not require too much r.f. power from the h.f. oscillator, since it may be difficult to supply the power and yet maintain good oscillator stability (§ 3-7). Also, the conversion efficiency should not depend too critically on the oscillator voltage (that is, a small change in oscillator output should not change the gain), since it is difficult to maintain constant output over a wide frequency range.

A change in oscillator frequency caused by tuning of the mixer grid circuit is called *pulling*. If the mixer and oscillator could be completely isolated, mixer tuning would have no effect on the oscillator frequency; but in practice this is a difficult condition to attain. Pulling should be minimized, because the stability of the whole receiver depends critically upon the stability of the h.f. oscillator. Pulling decreases with separation of the signal and h.f. oscillator frequencies, being less with high i.f.s.

Circuits — Typical frequency-conversion circuits are given in Fig. 720. The variations are chiefly in the way in which the oscillator voltage is introduced. In Fig. 720-A, the screen-grid pentode functions as a plate detector; the oscillator is capacity-coupled to the grid of the tube, in parallel with the tuned input circuit. Inductive coupling may be used instead. The conversion gain and input selectivity generally are good, so long as the sum of the two voltages (signal and oscillator) impressed on the mixer grid does not exceed the grid bias. It is desirable to make the oscillator voltage as high as possible without exceeding this limitation. The oscillator power required is negligible.

A pentagrid-converter tube is used in the circuit at B. Although intended for combination oscillator-mixer use, this type of tube usually will give more satisfactory performance when used in conjunction with a separate oscillator, the output of which is coupled in as shown. The circuit gives good conversion efficiency, and, because of the electron coupling, affords desirable isolation between the mixer and oscillator circuits. A small amount of power is required from the oscillator.

Circuit C is for the 6L7 mixer tube. The oscillator voltage can vary over a considerable range without affecting the conversion gain. There are no critical adjustments, and the oscillator-mixer isolation is good. The oscillator must supply somewhat more power than in B.

A more stable receiver generally results, particularly at the higher frequencies, when separate tubes are used for the mixer and oscillator. Practically the same number of circuit components is required whether or not a combination tube is used, so that there is little difference from the cost standpoint.

Tubes for frequency conversion—Any sharp cut-off pentode may be used in the circuit of Fig. 720-A. The 6AB7 and 6AC7 give high conversion gain and excellent signal-to-noise ratio—comparable, in fact, to the gain and signal-to-noise ratio obtainable with r.f. amplifiers—and in these respects are far superior to any other tubes used as mixers, particularly between 14 and 100 Mc. However, this type of tube loads the circuit more (§ 7-6) and thus decreases the selectivity.

The 6K8 is a good tube for the circuit at B; its oscillator plate connection may be ignored. The 6SA7 also is excellent in this circuit, although it has no anode grid (No. 2 grid, in the diagram). In addition to these two types, any pentagrid converter tube may be used.

V.h.f. and U.h.f. converters.—At frequencies above the 30-Mc. region the performance of the special mixer and converter tubes employed on the lower frequencies falls off because of greatly reduced input resistance which, by loading the tuned circuit connected to the tube and thus reducing its Q , lowers the signal-to-noise ratio. However, the high-transconductance pentodes such as the 6AC7 and 6AB7 will perform fairly effectively in the circuit of Fig. 720-A up to 100 Mc. or so.

Above about 100 Mc. the loading effect, in addition to the relatively large input capacity which limits the amount of inductance that can be used in the tuned circuit, makes these tubes markedly inferior to the special high-frequency pentodes such as the 9000 and acorn series. The latter perform successfully up to 400 Mc.

At still higher frequencies—or, for that matter, anywhere above 200 Mc.—other types of converters are preferred. At these frequencies triode mixers, when operated as plate-rectifier detectors in suitable circuits, give the least noise and maximum conversion transconductance.

Fig. 721-A shows the elementary circuit for a single triode with cathode oscillator-voltage injection. In such an arrangement the cathode connection usually terminates (with as short a lead as possible) in a small link near the oscillator tank, one end of which is grounded. Alternatively, direct capacity-coupled grid injection may be used in an arrangement similar to that of Fig. 720-A, C_4 being a very small coupling condenser of perhaps 1 or 2 μfd .—often merely the free end of the coupling lead placed within the field of the oscillator coil or near the oscillator tube plate or grid.

The balanced triode circuit of Fig. 721-B affords the added advantages of symmetry to ground and complete cancellation of both the received-signal and oscillator voltages in the plate circuit. This serves further to improve the signal/noise ratio as well as to stabilize operation. For optimum performance the oscillator-voltage input should be carefully adjusted, by means of the coupling between the two coils, to give maximum converter gain. The balanced converter circuit is most frequently

used with miniature dual triodes such as the 6J6, with which it performs effectively up to 600 Mc. or higher. The oscillator may be operated either on its fundamental or a harmonic. At frequencies above 200 Mc. coaxial or “trough”-line circuits are chiefly used.

At still higher frequencies converters employing conventional tubes are inferior to other, basically different types, including highly specialized versions of velocity-modulation tubes of various types. These techniques, however, are beyond the scope of the present treatment; information concerning practical tubes and circuits is largely held confidential by the military services.

For amateur work on these higher frequencies the use of special small u.h.f. diodes with

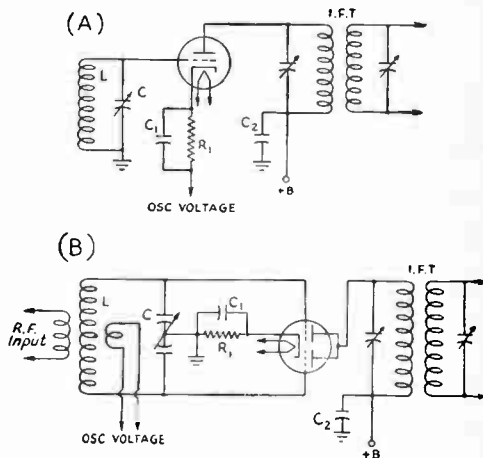


Fig. 721—V.h.f. frequency converter circuits. A, triode mixer with separate oscillator tube; B, balanced square-law mixer using a dual triode tube with push-pull input circuit. L and C are tuned to the signal frequency.

C_1 —100- μfd . silvered mica.

C_2 —0.005- μfd .

R_1 —10,000-50,000 ohms.

extremely close element spacing as converters is a logical solution. Crystal detectors have also been used extensively because of their ready availability and independence of frequency limitations. Crystal detectors are not susceptible to the transit time limitations of electronic tubes. Silicon is the most popular material for such applications; the crystals are ground to minute dimensions and permanently mounted in fixed miniature holders with tungsten contacts. Fig. 722-A shows a typical crystal mixer circuit with inductive coupling to a triode oscillator (955 or 9002).

Because stability of a crystal detector can be achieved only at the expense of sensitivity, diode detectors are preferred up to the limit of frequency at which they can be made to function. Diodes have the further advantage that they will function as mixers by using a harmonic of the oscillator voltage, making possible the use of conventional triode oscillators for receivers operating up to the 2000-Mc.

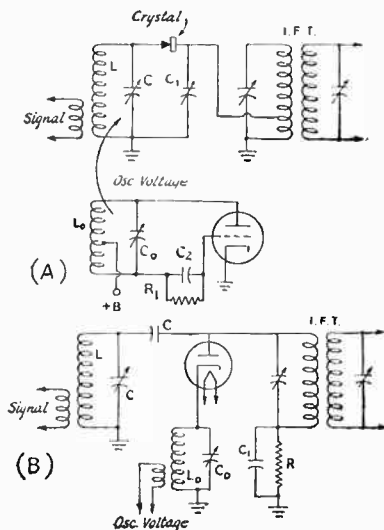


Fig. 722 — U.h.f. frequency converter circuits. A, crystal-detector mixer with an inductively coupled triode oscillator; B, diode mixer with cathode-link coupling to the oscillator circuit. *L* and *C* are tuned to the signal frequency; *L_o* and *C_o* to the oscillator frequency.

- C*₁ — 3–30- μ fd. mica trimmer.
- C*₂ — 25- μ fd. silvered mica.
- C*₃ — 10- μ fd. silvered mica.
- C*₄ — 0.005- μ fd.
- R*₁ — 50,000 ohms (metallized carbon).
- R*₂ — 5000–20,000 ohms.

region or higher. While operation of the oscillator on a fundamental is the more efficient method, the loss in conversion efficiency does not exceed 2 to 1 even with third harmonic operation provided the oscillator input is sufficient to establish a diode current of 0.2 to 0.5 ma. Diode mixers are considerably more tolerant as concerns oscillator voltage and other circuit conditions than the crystal type.

In the circuit of Fig. 722-B the cathode tuned circuit, *L_oC_o*, is tuned to the oscillator fundamental. *C_o* is being made large enough so that it is effectively a cathode by-pass condenser for the signal frequency.

7-10 The High-Frequency Oscillator

Design considerations — Stability of the receiver (§ 7-2) is dependent chiefly upon the stability of the h.f. oscillator, and particular care should be given this part of the receiver. The frequency of oscillation should be insensitive to changes in voltage, loading, and mechanical shock. Thermal effects (slow change in frequency because of tube or circuit heating) should be minimized. These ends can be attained by the use of good insulating materials and circuit components, suitable electrical design, and careful mechanical construction.

In addition, the oscillator must be capable of furnishing sufficient r.f. voltage and power for the particular mixer circuit chosen, at all frequencies within the range of the receiver, and its harmonic output should be as low as possible to reduce spurious response (§ 7-8).

It is desirable to make the *L/C* ratio in the oscillator tuned circuit low (high-*C*), since this results in increased stability (§ 3-7). Particular care should be taken to insure that no part of the oscillator circuit can vibrate mechanically. This calls for short leads and "solid" mechanical construction. The chassis and panel material should be heavy and rigid enough so that pressure on the tuning dial will not cause torsion and a shift in the frequency. Care in mechanical construction is well repaid by increased frequency stability.

Circuits — Several oscillator circuits are shown in Fig. 723. The point at which output voltage is taken for the mixer is indicated in each case by *X* or *Y*. Circuits A and B will give about the same results, and require only one coil. However, in these two circuits the cathode is above ground potential for r.f., which often is a cause of hum modulation of the oscillator output at 14 Mc. and higher frequencies when 6.3-volt heater tubes are used. Hum usually is not bothersome with 2.5-volt tubes, nor, of course, with tubes which are heated by direct current. The circuit of Fig. 723-C overcomes hum, since the cathode is

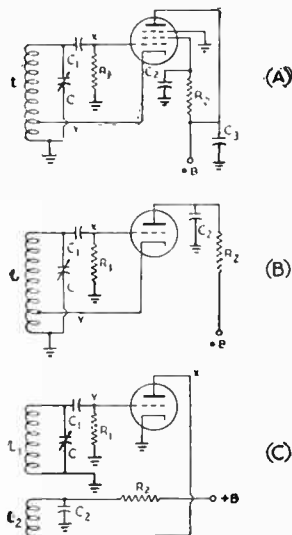


Fig. 723 — High-frequency oscillator circuits. A, screen-grid grounded-plate oscillator; B, triode grounded-plate oscillator; C, triode oscillator with tickler circuit. Coupling to the mixer may be taken from points *X* and *Y*. In A and B, coupling from *Y* will reduce pulling effects, but gives less voltage than from *X*; this type is best adapted to mixer circuits with small oscillator-voltage requirements. Typical values for components are as follows:

	Circuit A	Circuit B	Circuit C
<i>C</i> ₁ —	100 μ fd.	100 μ fd.	100 μ fd.
<i>C</i> ₂ —	0.1 μ fd.	0.1 μ fd.	0.1 μ fd.
<i>C</i> ₃ —	0.1 μ fd.		
<i>R</i> ₁ —	50,000 ohms.	50,000 ohms.	50,000 ohms.
<i>R</i> ₂ —	50,000 ohms.	10,000 to 25,000 ohms.	10,000 to 25,000 ohms.

The plate-supply voltage should be 250 volts. In circuits B and C, *R*₂ is used to drop the supply voltage to 100–150 volts; it may be omitted if voltage is obtained from a voltage divider in the power supply (§ 8-10).

grounded. The two-coil arrangement is advantageous in construction, since the feed-back adjustment (altering the number of turns on L_2 or the coupling between L_1 and L_2) is simple mechanically.

Besides the use of a fairly high C/L ratio in the tuned circuit, it is necessary to adjust the feed-back to obtain optimum results. Too much feed-back will cause the oscillator to "squeg," or operate at several frequencies simultaneously (§ 7-4); too little feed-back will cause the output to be low. In the tapped-coil circuits (A, B), the feed-back is increased by moving the tap toward the grid end of the coil; in C, by increasing the number of turns on L_2 or by moving L_2 closer to L_1 .

The oscillator plate voltage should be as low as is consistent with adequate output. Low plate voltage will cause reduced tube heating and thereby reduce frequency drift. The oscillator and mixer circuits should be well isolated, preferably by shielding, since coupling other than by the means intended may result in pulling.

To avoid plate-voltage changes which may cause the oscillator frequency to change, it is good practice to use a voltage-regulated plate supply employing a gaseous VR tube (§ 8-8).

Tracking — For ganged tuning, there must be a *constant difference* in frequency between the oscillator and mixer circuits. This difference must be exactly equal to the intermediate frequency (§ 7-8).

Tracking methods for covering a wide frequency range, suitable for general-coverage receivers, are shown in Fig. 724. The tracking capacity, C_b , commonly consists of two condensers in parallel, a fixed one of somewhat less capacity than the value needed and a smaller variable in parallel to allow for adjustment to the exact proper value. In practice, the trimmer, C_4 , is first set for the high-frequency end of the tuning range, and then the tracking condenser is set for the low-frequency end. The tracking capacity becomes larger as the percentage difference between the oscillator and signal frequencies becomes smaller (that is, as the signal frequency becomes higher). Typical circuit values are given in the tables under Fig. 724.

In amateur-band receivers, tracking is simplified by choosing a bandspread circuit which gives practically straight-line-frequency tuning (equal frequency change for each dial division), and then adjusting the oscillator and mixer tuned circuits so that both cover the same total number of kilocycles. For example, if the i.f. is 455 kc. between two given points on the dial, then the oscillator must tune from 7455 to 7755 kc. between the same two dial readings. With the bandspread arrangement of Fig. 715-C, the tuning will be practically straight-line-frequency if the capacity actually in use at C_2 is not too small; the same is true of 715-A if C_1 is small compared to C_2 .

§ 7-11 The Intermediate-Frequency Amplifier

Choice of frequency — The selection of an intermediate frequency is a compromise between various conflicting factors. The lower the i.f. the higher the selectivity and gain, but a low i.f. brings the image nearer the desired signal and hence decreases the image ratio (§ 7-8). A low i.f. also increases pulling of the oscillator frequency (§ 7-9). On the other hand, a high i.f. is beneficial to both image ratio and pulling, but the selectivity and gain are lowered. The difference in gain is least important.

An i.f. of the order of 455 kc. gives good selectivity and is satisfactory from the standpoint of image ratio and oscillator pulling at frequencies up to 7 Mc. The image ratio is poor at 14 Mc. when the mixer is connected to the antenna, but adequate when there is a

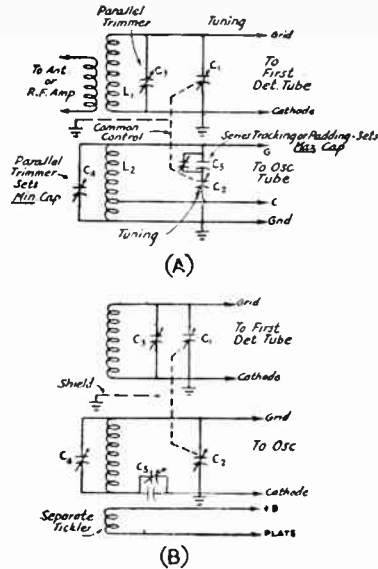


Fig. 724 — Converter-circuit tracking methods. Following are approximate circuit values for 450- to 465-kc. i.f.s with tuning ranges of approximately 2.15-to-1 and C_2 having 140 μfd . maximum, and the total minimum capacitance, including C_3 or C_4 , being 30 to 35 μfd .

Tuning Range	L_1	L_2	C_b
1.7-4 Mc.	50 μh .	40 μh .	0.0013 μfd .
3.7-7.5 Mc.	14 μh .	12.2 μh .	0.0022 μfd .
7-15 Mc.	3.5 μh .	3 μh .	0.0045 μfd .
14-30 Mc.	0.8 μh .	0.78 μh .	None used

Approximate values for 450- to 465-kc. i.f.s with a 2.5-to-1 tuning range, C_1 and C_2 being 350- μfd . maximum, minimum including C_3 and C_4 being 40 to 50 μfd .

Tuning Range	L_1	L_3	C_b
0.5-1.5 Mc.	240 μh .	130 μh .	425 μfd .
1.5-4 Mc.	32 μh .	25 μh .	0.00115 μfd .
4-10 Mc.	4.5 μh .	4 μh .	0.0028 μfd .
10-25 Mc.	0.8 μh .	0.75 μh .	None used

tuned r.f. amplifier between antenna and mixer. At 28 Mc. and on the very-high frequencies, the image ratio is very poor unless several r.f. stages are used. Above 14 Mc., pulling is likely to be bad unless very loose coupling can be used between mixer and oscillator.

With an i.f. of about 1600 kc., satisfactory image ratios can be secured on 14, 28 and 56 Mc., and pulling can be reduced to negligible proportions. However, the i.f. selectivity is considerably lower, so that more tuned circuits must be used to increase the selectivity. For very-high frequencies, including 28 Mc., the best solution is to use a double superheterodyne (§ 7-8), choosing one high i.f. for image reduction (5 and 10 Mc. are frequently used) and a lower one for gain and selectivity.

In choosing an i.f. it is wise to avoid frequencies on which there is considerable activity by the various radio services, since such signals may be picked up directly on the i.f. wiring. The frequencies mentioned are fairly free of such interference.

Fidelity, sideband cutting — As described in § 5-2, modulation of a carrier causes the generation of sideband frequencies numerically equal to the carrier frequency plus and minus the highest modulation frequency present. If the receiver is to give a faithful reproduction of modulation which contains, for instance, audio frequencies up to 5000 cycles, it must be capable of amplifying equally all frequencies contained in a band extending from 5000 cycles above to 5000 cycles below the carrier frequency. In a superheterodyne, where all carrier frequencies are changed to the fixed intermediate frequency, this means that the i.f. amplifier should amplify equally well all frequencies within that band. In other words, the amplification must be uniform over a band 10 kc. wide, with the i.f. at its center. The signal-frequency circuits usually do not have enough over-all selectivity to affect materially the "adjacent channel" selectivity (§ 7-2), so that only the i.f. amplifier selectivity need be considered.

A 10-kc. band is considered sufficient for reasonably faithful reproduction of music, but much narrower band-widths can be used for communication work where intelligibility rather than fidelity is the primary objective.

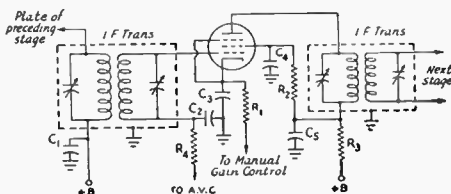


Fig. 725 — Typical intermediate-frequency amplifier circuit for a superheterodyne receiver. Representative values for components are as follows:

C_1 — 0.1 μ fd. at 455 kc.; 0.01 μ fd. at 1600 kc. and higher.
 C_2 — 0.01 μ fd.
 C_3, C_4, C_5 — 0.1 μ fd. at 455 kc.; 0.01 μ fd. above 1600 kc.
 R_1 — 300 ohms. R_2 — 2000 ohms.
 R_3 — 2000 ohms.
 R_4 — 0.25 megohm.

If the selectivity is too great to permit uniform amplification over the band of frequencies occupied by the modulated signal, the higher modulating frequencies are attenuated as compared to the lower frequencies; that is, the upper-frequency sidebands are "cut." While sideband cutting reduces fidelity, it is frequently preferable to sacrifice naturalness of reproduction in favor of greater selectivity.

The selectivity of an i.f. amplifier, and hence the tendency to cut sidebands, increases with the number of amplifier stages and also is greater the lower the intermediate frequency. From the standpoint of communication, sideband cutting is not serious with two-stage amplifiers at frequencies as low as 455 kc.

Circuits — I.f. amplifiers usually consist of one or two stages. Two stages at 455 kc. give all the gain usable, in view of the minimum receiver noise level, and also give suitable selectivity for good-quality 'phone reception.

A typical circuit arrangement is shown in Fig. 725. A second stage would simply duplicate the circuit of the first. In principle, the i.f. amplifier is the same as the tuned r.f. amplifier (§ 7-6). However, since a fixed frequency is used, the primary as well as the secondary of the coupling transformer is tuned, giving higher selectivity than is obtainable with a closely coupled untuned primary. The cathode resistor, R_1 , is connected to a gain control circuit of the type previously described (§ 7-6); usually both stages, if two are used, are controlled by a single variable resistor. The decoupling resistor, R_3 (§ 2-11), helps isolate the amplifier, and thus prevents stray feed-back. C_2 and R_4 are part of the automatic volume-control circuit (§ 7-13); if no a.v.c. is used, the lower end of the i.f. transformer secondary is simply connected to ground.

In a two-stage amplifier the screen grids of both stages may be fed from a common supply, either through a resistor (R_2) as shown, the screens being connected in parallel, or from a voltage divider (§ 8-10) across the plate supply. Separate screen voltage-dropping resistors are preferable for preventing undesired coupling between stages.

When two stages are used the high gain will tend to cause instability and oscillation, so that good shielding, by-passing, and careful circuit arrangement to prevent stray coupling, with exposed r.f. leads well separated, is necessary.

I.f. transformers — The tuned circuits of i.f. amplifiers are built up as transformer units consisting of a metal-shield container in which the coils and tuning condensers are mounted. Both air-core and powdered-iron-core universal-wound coils are used, the latter having somewhat higher Q s and, hence, greater selectivity and gain per unit. In universal windings the coil is wound in layers with each turn traversing the length of the coil, back and forth, rather than being wound perpendicular to the axis as in ordinary single-layer coils. In a straight multi-layer winding, the turns on ad-

adjacent layers at the edges of the coil have a rather large potential difference between them as compared to the difference between any two adjacent turns in the same layer: hence a fairly large capacity current can flow between layers. Universal winding, with its "criss-crossed" turns, tends to avoid building up such potential differences, and hence reduces distributed-capacity effects (§ 2-8).

Variable tuning condensers are of the midget type, air-dielectric condensers being preferable because their capacity is practically unaffected by changes in temperature and humidity. Iron-core transformers may be tuned by varying the inductance (permeability tuning), in which case stability comparable to that of variable air-condenser tuning can be obtained by use of high-stability fixed mica condensers. Such stability is of great importance, since a circuit whose frequency "drifts" with time eventually will be tuned to a different frequency than the other circuits, thereby reducing the gain and selectivity of the amplifier. Typical i.f. transformer construction is shown in Fig. 726.

Besides the type of i.f. transformer shown in Fig. 726, special units to give desired selectivity characteristics are available. For higher than ordinary adjacent-channel selectivity (§ 7-2) *triple-tuned* transformers, with a third tuned circuit inserted between the input and output windings, are used. The energy is transferred from the input to the output windings via this *tertiary* winding, thus adding its selectivity to the over-all selectivity of the transformer. *Variable-selectivity* transformers also can be obtained. These usually are provided with a third (untuned) winding which can be connected to a resistor, thereby loading the tuned circuits and decreasing the *Q* and selectivity (§ 2-10) to broaden the selectivity curve. The variation in selectivity is brought about by switching the resistor in and out of the circuit. Another method is to vary the coupling between primary and secondary, overcoupling being used to broaden the selectivity curve and undercoupling to sharpen it (§ 2-11).

Selectivity — The over-all selectivity of the i.f. amplifier will depend on the frequency and the number of stages. The following figures are indicative of the band-widths (§ 7-2) to be expected with good-quality transformers in amplifiers so constructed as to keep regeneration to a minimum:

Intermediate frequency	Band-width in kilocycles		
	2 times down	10 times down	100 times down
One-stage, 455 kc. (air core) . . .	8.7	17.8	32.3
One-stage, 455 kc. (iron core) . . .	4.3	10.3	20.4
Two stages, 455 kc. (iron core) . . .	2.9	6.4	10.8
Two stages, 1600 kc.	11.0	16.6	27.4
Two stages, 5000 kc.	25.8	46.0	100.0

Tubes for i.f. amplifiers — Variable- μ pentodes (§ 3-5) are almost invariably used in i.f. amplifier stages, since grid-bias gain control (§ 7-6) is practically always applied to the i.f. amplifier. Tubes with high plate resistance will

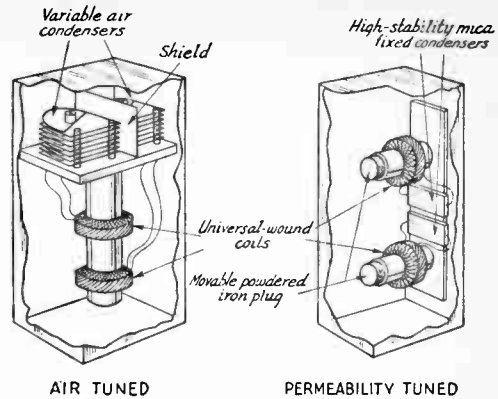


Fig. 726 — Representative i.f. transformer construction. Coils are supported on insulating tubing or (in the air-tuned type) on wax-impregnated wooden dowels. The shield in the air-tuned transformer prevents capacity coupling between the tuning condensers. In the permeability-tuned transformer the cores consist of finely divided iron particles supported in an insulating binder, formed into cylindrical "plugs." The tuning capacity is fixed, and the inductances of the coils are varied by moving the iron plugs in and out.

have least effect on the selectivity of the amplifier, and those with high mutual conductance will give greatest gain. The choice of i.f. tubes has practically no effect on the signal-to-noise ratio, since this is determined by the preceding mixer and r.f. amplifier (if the latter is used).

When single-ended tubes (§ 3-5) are used, care should be taken to keep the plate and grid leads well separated. With these tubes it is advisable to mount the screen by-pass condenser directly on the bottom of the socket, cross-wise between the plate and grid pins, to provide additional shielding. The outside foil of the condenser should be connected to ground.

Single-signal effect — In heterodyne c.w. reception with a superheterodyne receiver, the beat oscillator is set to give a suitable audio-frequency beat note when the incoming signal is converted to the intermediate frequency. For example, the beat oscillator may be set to 456 kc. (the i.f. being 455 kc.) to give a 1000-cycle beat note. Now, if an interfering signal appears at 457 kc., it will also be heterodyned by the beat oscillator to produce a 1000-cycle beat. This *audio-frequency image* corresponds to the high-frequency images already discussed (§ 7-8). It can be reduced by providing enough i.f. selectivity, since the image signal is off the peak of the i.f. resonance curve.

When this is done, tuning through a given signal will show a strong response at the desired beat note on one side of zero beat only, instead of the two beat notes on either side of zero beat characteristic of less-selective reception; hence the name, "single-signal" reception.

The necessary selectivity is difficult to obtain with non-regenerative amplifiers using ordinary tuned circuits unless a very low intermediate frequency or a large number of circuits is used. In practice it is secured either by regenerative amplification or by a crystal filter.

Regeneration — Regeneration can be used to give a pronounced single-signal effect, particularly when the i.f. is 455 kc. or lower. The resonance curve of an i.f. stage at critical regeneration (just below the oscillating point) is extremely sharp, a band-width of 1 kc. at 10 times down and 5 kc. at 100 times down being obtainable in one stage. The audio-frequency image of a given signal thus can be reduced by a factor of nearly 100 for a 1000-cycle beat note (image 2300 cycles from resonance).

Regeneration is easily introduced into an i.f. amplifier by providing a small amount of capacity coupling between grid and plate. Bringing a short length of wire, connected to the grid, into the vicinity of the plate lead usually will suffice. The feed-back may be controlled by the regular cathode-resistor gain control. When the i.f. is regenerative, it is preferable to operate the tube at reduced gain (high bias) and depend on regeneration to bring up the signal strength. This prevents overloading and increases selectivity.

The higher selectivity with regeneration reduces the over-all response to noise generated in the earlier stages of the receiver, just as does high selectivity produced by other means, and therefore improves the signal-to-noise ratio. The disadvantage is that the regenerative gain varies with signal strength, being less on strong signals, and the selectivity varies accordingly.

Crystal filters — The most satisfactory method of obtaining high selectivity is by the use of a piezoelectric quartz crystal as a selective filter in the i.f. amplifier (§ 2-10). Compared to a good tuned circuit, the Q of such a crystal is extremely high. The dimensions of the crystal are made such that it is resonant at the desired intermediate frequency. It is then used as a selective coupler between i.f. stages.

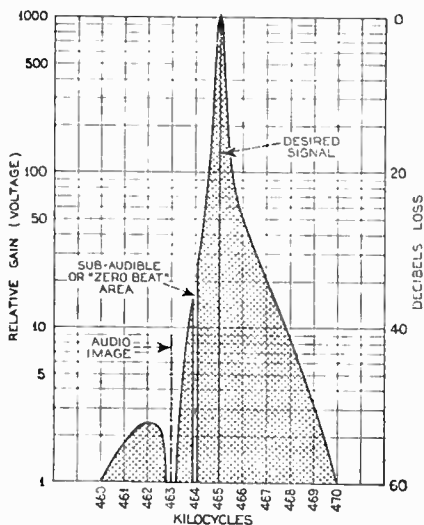


Fig. 727 — Graphical representation of single-signal selectivity. The shaded area indicates the overall band-width, or region in which response is obtainable.

Fig. 727 gives a typical crystal-filter resonance curve. For single-signal reception, the audio-frequency image can be reduced by a factor of 1000 or more. Besides practically eliminating the a.f. image, the high selectivity of the crystal filter provides great discrimination against signals very close to the desired signal in frequency, and, by reducing the band-width, reduces the response of the receiver to noise both from sources external to the receiver and in the r.f. stages of the receiver itself.

Crystal filter circuits: phasing — Several crystal filter circuits are shown in Fig. 728. Those at A and B are practically identical in performance, although differing in details. The crystal is connected in a bridge circuit (§ 2-11), with the secondary side of T_1 , the input transformer, balanced to ground either through a pair of condensers, C_1 - C_2 (A) or by a center-tap on the secondary, L_2 (B). The bridge is completed by the crystal, X , and the phasing condenser, C_3 , which has a maximum capacity somewhat higher than the capacity of the crystal in its holder. When C_3 is set to balance the crystal-holder capacity, the resonance curve of the crystal circuit is practically symmetrical; the crystal acts as a series-resonant circuit of very high Q and thus allows signals of the desired frequency to be fed through C_3 to L_3 - L_4 , the output transformer. Without C_3 , the holder capacity (with the crystal acting as a dielectric) would pass signals of undesired frequencies.

The phasing control has an additional function besides neutralization of the crystal-holder capacity. The holder capacity becomes a part of the crystal circuit and causes it to act as a parallel-tuned resonant circuit at a frequency slightly higher than its series-resonant frequency. Signals at the parallel-resonant frequency thus are prevented from reaching the output circuit. The phasing control, by varying the effect of the holder capacity, permits shifting the parallel-resonant frequency over a considerable range, providing adjustable rejection of interfering signals. The effect of rejection is illustrated in Fig. 727, where the audio image is reduced, by proper setting of the phasing control, far below the value that would be expected if the resonance curve were symmetrical.

Variable selectivity — In circuits such as A and B, Fig. 728, variable selectivity is obtained by adjustment of the variable input impedance, which is effectively in series with the crystal resonator. This is accomplished by varying C_1 (the *selectivity control*), which tunes the balanced secondary circuit of T_1 . When the secondary is tuned to i.f. resonance the parallel impedance of the L_2 - C_1 combination is maximum and is purely resistive (§ 2-10). Since the secondary circuit is center-tapped, approximately one-fourth of this resistive impedance is in series with the crystal through C_3 and L_4 . This lowers the Q of the crystal circuit and makes its selectivity minimum. At the same time, the voltage applied to the crystal circuit is maximum.

When the input circuit is detuned from the crystal resonant frequency the resistance component of the input impedance decreases, and so does the total parallel impedance. Accordingly, the selectivity of the crystal circuit becomes higher and the applied voltage falls off. At first the resistance decreases faster than the applied voltage, with the result that the e.v. output from the filter *increases* as the selectivity is increased. The output falls off gradually as the input circuit is detuned further from resonance, however, and the selectivity becomes still higher.

In the circuits of A and B in Fig. 728, the minimum selectivity is still much greater than that of a normal two-stage 455-ke. amplifier and it is desirable to provide a wider range of selectivity, particularly for 'phone reception. A circuit which does this is shown at Fig. 728-C. The principle of operation is similar, but a much higher value of resistance can be introduced in the crystal circuit to reduce the selectivity. The output tuned circuit, L_3C_3 , must have high Q . A compensated condenser is used at C_2 (phasing) to maintain circuit balance, so that the phasing control does not affect the resonant frequency. The output circuit functions as a voltage divider in such a way that the amplitude of the carrier delivered to the next grid does not vary appreciably with the selectivity setting. The variable resistor, R , may consist of a series of separate fixed resistors selected by a tap switch.

¶ 7-12 The Second Detector and Beat Oscillator

Detector circuits — The second detector of a superheterodyne receiver performs the same function as the detector in the simple receiver, but usually operates at a higher input level because of the relatively great r.f. amplification. Therefore, the ability to handle large signals without distortion is preferable to high sensitivity. Plate detection is used to some extent, but the diode detector is most popular. It is especially adapted to furnishing automatic gain or volume control (§ 7-13). The basic circuits are as described in § 7-3, although in many cases the diode elements are incorporated in a multi-purpose tube which contains an amplifier section in addition to the diode unit.

The beat oscillator — Any standard oscillator circuit (§ 3-7) may be used for the beat oscillator. Special beat-oscillator transformers are available, usually consisting of a tapped coil with adjustable tuning; these are most conveniently used with circuits such as those shown at Fig. 723-A and -B, with the output taken from Y . A variable condenser of about 25- μfd . capacity may be connected between cathode and ground to provide fine adjustment. The beat oscillator usually is coupled to the second-detector tuned circuit through a fixed condenser of a few μfd . capacity.

The beat oscillator should be well shielded, to prevent coupling to any part of the circuit

except the second detector and to prevent its harmonics from getting into the front end of the receiver and being amplified like regular signals. To this end, the plate voltage should be as low as is consistent with sufficient audio-frequency output. If the beat oscillator output is too low, strong signals will not give a proportionately strong audio response.

An oscillating second detector may be used to give the audio beat note, but, since the detector must be detuned from the i.f., the selectivity and signal strength will be reduced, while blocking (§ 7-1) will be pronounced because of the high signal level at the second detector.

¶ 7-13 Automatic Volume Control

Principles — Automatic regulation of the gain of the receiver in inverse proportion to the signal strength is a great advantage, especially in 'phone reception, since it tends to keep the output level of the receiver constant regardless of input signal strength. It is readily accomplished in superheterodyne receivers by using the average rectified d.c. voltage, developed by the received signal across a resistance in a detector circuit (§ 7-3), to vary the bias on the r.f. and i.f. amplifier tubes.

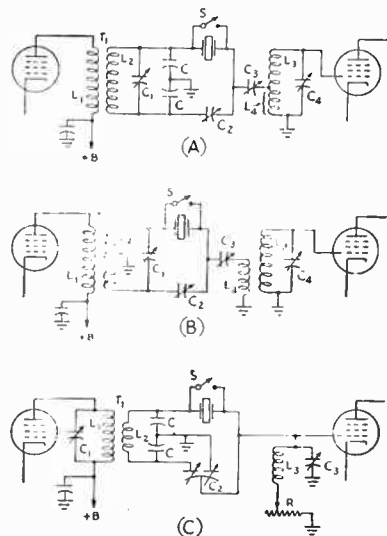


Fig. 728 — Crystal filter circuits of three types. All give variable band-width, with C having the greatest range of selectivity. Their operation is discussed in the text. Suitable circuit values are as follows: Circuit A, T_1 , special i.f. input transformer with high-inductance primary, L_1 , closely coupled to tuned secondary, L_2 ; C_1 , 50- μfd . variable; C_2 , each 100- μfd . fixed (mica); C_3 , 10- to 15- μfd . (max.) variable; C_4 , 50- μfd . trimmer; L_3C_3 , i.f. tuned circuit, with L_3 tapped to match crystal-circuit impedance. In circuit B, T_1 is the same as in circuit A except that the secondary is center-tapped; C_1 is 100- μfd . variable; C_2 , C_3 and C_4 , same as for circuit A; L_3L_4 is a transformer with primary, L_4 , corresponding to tap on L_3 in A. In circuit C, T_1 is a special i.f. input transformer with tuned primary and low-impedance secondary; C_1 , each 100- μfd . fixed (mica); C_2 , opposed stator phasing condenser, approximately 8 μfd . maximum capacity each side; L_3C_3 , high- Q i.f. tuned circuit; R , 0 to 3000 ohms (selectivity control).

Since this voltage is proportional to the average amplitude of the signal, the gain is reduced as the signal strength becomes greater. The control will be more complete as the number of stages to which the a.v.c. bias is applied is increased. Control of at least two stages is advisable.

Circuits—A typical circuit using a diode-triode type tube as a combined a.v.c. rectifier, detector and first audio amplifier is shown in Fig. 729. One plate of the diode section of the tube is used for signal detection and the other for a.v.c. rectification. The a.v.c. diode plate is fed from the detector diode through the small coupling condenser, C_3 . A negative bias voltage resulting from the flow of rectified carrier current is developed across R_4 , the diode load resistor. This negative bias is applied to the grids of the controlled stages through the filtering resistors (§ 2-11), R_5 , R_6 , R_7 and R_8 . When S_1 is closed the a.v.c. line is grounded, thereby removing the a.v.c. bias from the amplifier without disturbing the detector circuit.

It does not matter which of the two diode plates is selected for audio and which for a.v.c. Frequently the two plates are connected together and used as a combined detector and a.v.c. rectifier. This could be done in Fig. 729. The a.v.c. filter and line would connect to the junction of R_2 and C_2 , while C_3 and R_4 would be omitted from the circuit.

Delayed a.v.c.—In Fig. 729 the audio diode return is made directly to the cathode and the a.v.c. diode return to ground. This places negative bias on the a.v.c. diode equal to the d.c. drop through the cathode resistor (a volt or two) and thus delays the application of a.v.c. voltage to the amplifier grids, since no rectification takes place in the a.v.c. diode circuit until the carrier amplitude is large enough to overcome the bias. Without this delay the a.v.c. would start working even with a very small signal. This is undesirable, because the full amplification of the receiver then could not be realized on weak signals. In the audio diode circuit this fixed bias would cause distortion, and must be avoided; hence, the return is made directly to the cathode.

Time constant—The time constant (§ 2-6) of the resistor-condenser combinations in the a.v.c. circuit is an important part of the system. It must be high enough so that the modulation on the signal is completely filtered from

the d.c. output, leaving only an average d.c. component which follows the relatively slow carrier variations with fading. Audio-frequency variations in the a.v.c. voltage applied to the amplifier grids would reduce the percentage of modulation on the incoming signal, and in practice would cause frequency distortion. On the other hand, the time constant must not be too great or the a.v.c. would be unable to follow rapid fading. The capacity and resistance values indicated in Fig. 729 will give a time constant which is satisfactory for high-frequency reception.

Signal-strength and tuning indicators—

A useful accessory to the receiver is an indicator which will show relative signal strength. Not only is it an aid in giving reports to transmitting stations, but it is helpful also in aligning the receiver circuits, in conjunction with a test oscillator or other steady signal.


Three types of indicators are shown in Fig. 730. That at A uses an electron-ray tube (§ 3-5), several types of which are available. The grid of the triode section usually is connected to the a.v.c. line. The particular type of tube used depends upon the voltage available for its grid; where the a.v.c. voltage is large, a remote cut-off type (6G5 or 6N5) should be used in preference to the more sensitive sharp cut-off type (6E5).

In B, a milliammeter is connected in series with the d.c. plate lead to one or more r.f. and i.f. tubes, the grids of which are controlled by a.v.c. voltage. Since the plate current of such tubes varies with the strength of the incoming signal, the meter will indicate relative signal intensity and may be calibrated in "S" points. The scale range of the meter should be chosen to fit the number of tubes in use; the maximum plate current of the average remote cut-off r.f. pentode is from 7 to 10 milliamperes. The shunt resistor, R , enables setting the plate current to the full-scale value ("zero adjustment"). With this system the ordinary meter reads downwards from full scale with increasing signal strength, which is the reverse of normal pointer movement (clockwise with increasing reading). Special instruments in which the zero-current position of the pointer is on the right-hand side of the scale are used in commercial receivers.

The system at C uses a 0-1 ma. milliammeter in a bridge circuit, arranged so that the

Fig. 729—Automatic volume control circuit using a dual-diode-triode as a combined a.v.c. rectifier, second detector and first audio-frequency amplifier.

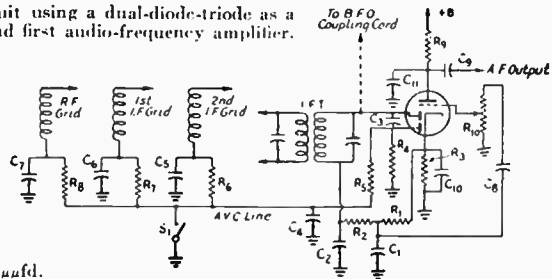- R_1 — 0.25 megohm.
- R_2 — 50,000 to 250,000 ohms.
- R_3 — 2000 ohms.
- R_4 — 2 to 5 megohms.
- R_5 — 0.5 to 1 megohm.
- R_6, R_7, R_8, R_9 — 0.25 megohm.
- R_{10} — 0.5-megohm variable.
- C_1, C_2, C_3 — 100 μ fd.
- C_4 — 0.1 μ fd.
- C_5, C_6, C_7 — 0.01 μ fd.
- C_8, C_9 — 0.01 to 0.1 μ fd.
- C_{10} — 5- to 10- μ fd. electrolytic. C_{11} — 250 μ fd.



meter reading and the signal strength increase together. The current through the branch containing R_1 should be approximately equal to the current through that containing R_2 . In some manufactured receivers this is brought about by draining the screen voltage-divider current and the current to the screens of three r.f. pentodes (r.f. and i.f. stages) through R_2 , the sum of these currents being about equal to the maximum plate current of one a.v.c.-controlled tube. Typical values for this type of circuit are given. The sensitivity can be increased by increasing the resistance of R_1 , R_2 and R_3 . The initial setting is made with the manual gain control set near maximum, when R_3 should be adjusted to make the meter read zero with no signal.

§ 7-14 Preselection

Purpose — Preselection is added signal-frequency selectivity incorporated before the mixer stage is reached. An r.f. amplifier preceding the mixer generally is called a *preselector*, its purpose, in part at least, being to discriminate in favor of the signal against the image. The preselector may consist of one or more r.f. amplifier stages. When its tuning control is ganged with those of the mixer and oscillator, its circuits must track with the mixer circuit.

The circuit is the same as discussed earlier (§ 7-6). An external preselector stage may be used with receivers having inadequate image ratios. In this case it is built as a separate unit, often with a tuned output circuit which gives a further improvement in selectivity. The output circuit usually is link-coupled (§ 2-11) to the receiver.

Signal noise ratio — An r.f. amplifier will have a better signal-to-noise ratio (§ 7-2) than a mixer because the gain is higher and because the mixer-tube electrode arrangement results in higher internal tube noise than does the ordinary pentode structure. Hence, a preselector is advantageous in increasing the signal-to-noise ratio over that obtainable when the mixer is fed directly from the antenna.

Image suppression — The image ratios (§ 7-8) obtainable at frequencies up to and including 7 Mc. with a single preselector stage are high enough, when the intermediate frequency is 455 kc., so that for all practical purposes there is no appreciable image response. Average image ratios on 14 Mc. and 28 Mc. are 50-75 and 10-15, respectively. This is the overall selectivity of the r.f. and mixer tuned circuits. A second preselector stage, adding another tuned circuit, will increase the ratios to several hundred at 14 Mc. and to 30-40 at 28 Mc.

On very-high frequencies, it is impracticable to attempt to secure a good image ratio with a 455-ke. i.f. Good performance can be secured only by using a high i.f. or a double superheterodyne (§ 7-8) with a high-frequency first i.f.

Regeneration — Regeneration may be used in a preselector stage to increase both gain and selectivity. Since its use makes tuning more critical and increases ganging problems, regener-

ation is seldom employed except at 14 Mc. and above, where adequate image suppression is difficult to obtain with non-regenerative circuits. The same disadvantages exist as in the case of a regenerative i.f. amplifier (§ 7-11). The effect of regeneration is roughly equivalent to adding another non-regenerative preselector stage.

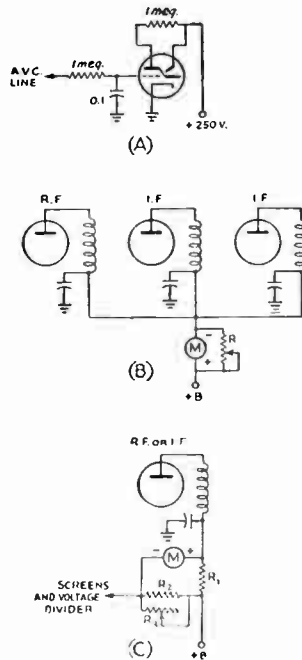


Fig. 730 — Timing indicator or "S"-meter circuits for superhet receivers. A, electron-ray indicator; B, plate-current meter for tubes on a.v.c.; C, bridge circuit for a.v.c.-controlled tube. In B, resistor R should have a maximum resistance several times that of the milliammeter. In C, representative values for the components are: R_1 , 250 ohms; R_2 , 350 ohms; R_3 , 1000-ohm variable.

Regeneration may be introduced by the same method as used in regenerative i.f. amplifiers (§ 7-11). The manual gain control of the stage will serve as a volume control.

Regeneration in a preselector does not improve the signal-to-noise ratio, since the tube noise is fed back to the grid circuit along with the signal to add to the thermal-agitation noise originally present. This noise also is amplified.

§ 7-15 Noise Reduction

Types of noise — In addition to tube and circuit noise (§ 7-6), much of the noise interference experienced in reception of high-frequency signals is caused by domestic electrical equipment and by automobile ignition systems. The interference is of two types in its effects. The first is the "hiss" type, consisting of overlapping pulses similar in nature to the receiver noise. It is largely reduced by high selectivity in the receiver, especially for code reception. The second is the "pistol-shot" or "machine-gun" type, consisting of separated impulses of high amplitude. The "hiss"

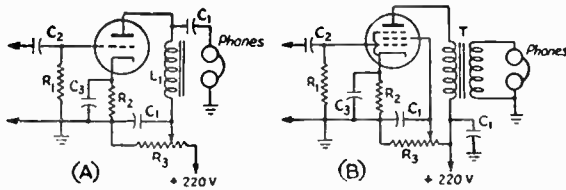


Fig. 731 — Audio output-circuit amplitude-limiting noise-reducing circuits for c.w. reception.

- C_1 — 0.25 μ fd.
 C_2 — 0.01 μ fd.
 C_3 — 5 μ fd.
 R_1 — 0.5 megohm.
 R_2 — 2000 ohms.
 R_3 — 50,000-ohm potentiometer.
 T — Output transformer.
 L_1 — 15-henry choke.

type of interference usually is caused by commutator sparking in d.c. and series-wound a.c. motors, while the "shot" type results from separated spark discharges (a.c. power leaks, switch and key clicks, ignition sparks, and the like).

Impulse noise — Impulse noise, because of the extremely short duration of the pulses as compared to the time between them, must have high pulse amplitude to contain much average energy. Hence, noise of this type strong enough to cause much interference generally has an instantaneous amplitude much higher than that of the signal being received. The general principle of devices intended to reduce such noise is that of allowing the signal amplitude to pass through the receiver unaffected, but making the receiver inoperative for amplitudes greater than that of the signal. The greater the amplitude of the pulse compared to its time of duration the more successful the noise reduction, since more of the constituent energy can be suppressed.

In passing through selective receiver circuits, the time duration of the impulses is increased, because of the Q or flywheel effect (§ 2-10) of the circuits. Hence, the more selectivity ahead of the noise-reducing device, the more difficult it becomes to secure good noise suppression.

Audio limiting — A considerable degree of noise reduction in code reception can be accomplished by amplitude-limiting arrangements applied to the audio output circuit of a receiver. Such limiters also maintain the signal output nearly constant with fading. Diagrams of typical output-limiter circuits are shown in Fig. 731. Circuit A employs a triode tube operated at reduced plate voltage (approximately 10 volts), so that it saturates at a low signal level. The arrangement of B has better limiting characteristics. A pentode audio tube is operated at reduced screen voltage (35 volts or so), so that the output power remains practically constant over a grid excitation-voltage range of more than 100 to 1. These output-limiter systems are simple, and adaptable to most receivers. However, they cannot prevent noise peaks from overloading previous circuits.

Second-detector circuits — The circuit of Fig. 732 "chops" noise peaks at the second detector of a superhet receiver by means of a biased diode, which becomes non-conducting above a predetermined signal level. The audio output of the detector must pass through the diode to the grid of the amplifier tube. The diode normally would be non-conducting with the connections shown were it not for the fact that it is given positive bias from a 30-volt

source through the adjustable potentiometer, R_3 . Resistors R_1 and R_2 must be fairly large in value to prevent loss of audio signal.

The audio signal from the detector can be considered to modulate (§ 5-1) the steady diode current, and conduction will take place so long as the diode plate is positive with respect to the cathode. When the signal is sufficiently large to swing the cathode positive with respect to the plate, however, conduction ceases, and that portion of the signal is cut off from the audio amplifier. The point at which cut-off occurs can be selected by adjustment of R_3 . By setting R_3 so that the signal just passes through the "valve," noise pulses higher in amplitude than the signal will be cut off. The circuit of Fig. 732-A, using an infinite-impedance detector (§ 7-3), gives a positive voltage on rectification. When the rectified voltage is negative, as it is from the usual diode detector (§ 7-3), the circuit arrangement shown in Fig. 732-B must be used.

An audio signal of about ten volts is required for good limiting action. When a beat oscillator is used for c.w. reception the b.f.o. voltage should be small, so that incoming noise will not have a strong carrier to beat against and so produce large audio output.

A second-detector noise-limiting circuit which automatically adjusts itself to the received carrier level is shown in Fig. 733. The diode load circuit (§ 7-3) consists of R_6 , R_7 , R_8 (shunted by the high-resistance audio volume control, R_4) and R_5 in series. The cathode of the 6N7 noise limiter is tapped on the load resistor at a point such that the average rectified carrier voltage (negative) at its grid is approximately twice the negative voltage at the cathode, both measured with reference to ground. A filter network, R_1C_1 , is inserted in the grid circuit, so that the audio modulation on the carrier does not reach the grid; hence, the grid potential is maintained at substantially the rectified carrier voltage alone. The cathode, however, is free to follow the modulation, and when the modulation is 100 per cent the peak cathode voltage will just equal the steady grid voltage.

At all modulation percentages below 100 per cent the grid is negative with respect to cathode, and current cannot flow in the 6N7 plate-cathode circuit. A noise pulse exceeding the peak voltage which represents 100 per cent modulation will, however, make the grid positive with respect to cathode. The relatively low plate-cathode resistance of the 6N7 then shunts the high-resistance audio output circuit,

effectively short-circuiting it, so that there is practically no response for the duration of the peak over the 100 per cent modulation limit.

R_5 is used to make the noise-limiting tube more sensitive by applying to the plate an audio voltage out of phase with the cathode voltage, so that, at the instant the grid goes positive with respect to cathode, the highest positive potential also is applied to the plate, thus further lowering the effective plate-cathode resistance.

I.f. noise silencer — In the circuit shown in Fig. 734, noise pulses are made to decrease the gain of an i.f. stage momentarily and thus silence the receiver for the duration of the pulse. Any noise voltage in excess of the desired signal's maximum i.f. voltage is taken off at the grid of the i.f. amplifier, amplified by the noise amplifier stage, and rectified by the full-wave diode noise rectifier. The noise circuits are tuned to the i.f. The rectified noise voltage is applied as a pulse of negative bias to the No. 3 grid of the 6L7 i.f. amplifier, wholly or partially disabling this stage for the duration of the individual noise pulse, depending on the amplitude of the noise voltage. The noise amplifier-rectifier circuit is biased by means of the "threshold control," R_2 , so that rectification will not start until the noise voltage exceeds the desired-signal amplitude. With automatic volume control the a.v.c. voltage can be applied to the grid of the noise amplifier, to augment this threshold bias. This system improved the signal-to-noise ratio some 30 db. (power ratio of 1000) with heavy ignition interference, raising the signal-to-noise ratio from -10 db. without the silencer to +20 db. with the silencer in a typical instance.

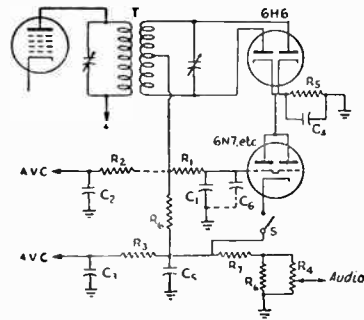


Fig. 733 — Automatic noise-limiter for superheterodynes. T — I.f. transformer with a balanced secondary for working into a diode rectifier.
 R_1, R_2, R_3 — 1 megohm. C_1 — 0.1- μ fd. paper.
 R_4 — 1-megohm variable. C_2, C_3 — 0.05- μ fd. paper.
 R_5 — 250,000 ohms. C_4, C_5 — 50- μ fd. mica.
 R_6, R_8 — 100,000 ohms. C_6 — 0.001- μ fd. mica (for r.f. filtering, if needed).
 R_7 — 25,000 ohms. C_7 — r.f. filtering, if needed.
 S — S.p.s.t. toggle (on-off switch).

The switch should be mounted close to the circuit elements and controlled by an extension shaft if necessary.

Circuit values are normal for i.f. amplifiers (§ 7-11), except as indicated. The noise-rectifier transformer, T_1 , has an untuned secondary closely coupled to the primary and center-tapped for full-wave rectification. The center-tap rectifier (§ 8-3) is used to reduce the possibility of r.f. feed-back into the i.f. amplifier (noise-silencer) stage. The time constant ($R_1C_1C_2$) of the noise-rectifier load circuit, $R_1C_1C_2$, must be small, to prevent disabling the noise-silencer stage for a longer period than the duration of the noise pulse. The r.f. choke, RFC , must be effective at the intermediate frequency.

Adequate shielding and isolation of the noise-amplifier and rectifier circuits from the noise-silencer stage must be provided to prevent possible self-oscillation and instability. This circuit should be applied to the first i.f. stage of the receiver, before the high-selectivity circuits are reached. On the other hand, it is most effective when the signal and noise levels are fairly high (meaning one or two r.f. stages before the mixer) since several volts must be obtained from the noise rectifier for good silencing.

7-16 Operating Superheterodyne Receivers

C.w. reception — For making code signals audible, the beat oscillator should be set to a frequency slightly different from the intermediate frequency (§ 7-8). To adjust the beat-oscillator frequency, first tune in a moderately weak but steady carrier with the beat oscillator turned off. Adjust the receiver tuning for maximum signal strength, as indicated by maximum hiss. Then turn on the beat oscillator and adjust its frequency (leaving the receiver tuning unchanged) to give a suitable beat note. The beat oscillator need not subsequently be touched, except for occasional checking to make certain the frequency has not drifted from the

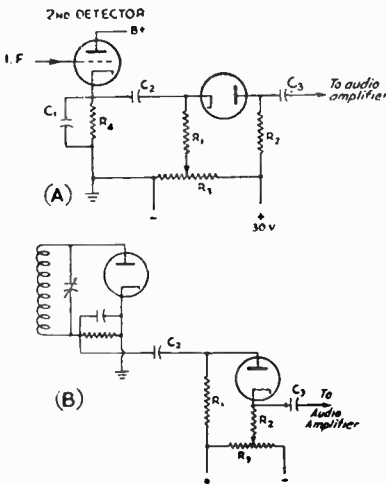


Fig. 732 — Series-valve noise-limiter circuits. A, as used with an infinite-impedance detector; B, with a diode detector. Typical values for components are as follows:

- R_1 — 0.25 megohm.
- R_2 — 50,000 ohms.
- R_3 — 10,000-ohms.
- R_4 — 20,000 to 50,000 ohms.
- C_1 — 250 μ fd.
- C_2, C_3 — 0.1 μ fd.

All other diode-circuit constants in B are conventional.

initial setting. The b.f.o. may be set on either the high- or low-frequency side of zero beat.

The use of a.v.c. (§ 7-13) is not generally satisfactory in c.w. reception because the receiver gain rises in the spaces between the dots and dashes, giving an increase in noise in the same intervals, and because the rectified beat-oscillator voltage in the second detector circuit also operates the a.v.c. circuit. This gives a constant reduction in gain and prevents utilization of the full sensitivity of the receiver. Hence, the gain preferably should be manually adjusted to give suitable audio-frequency output.

To avoid overloading in the i.f. circuits, it is usually better to control the i.f. and r.f. gain and keep the audio gain at a fixed value than to use the a.f. gain control as a volume control and leave the r.f. gain fixed at its highest level.

Tuning with the crystal filter — If the receiver is equipped with a crystal filter the tuning instructions in the preceding paragraph still apply, but more care must be used both in the initial adjustment of the beat oscillator and in tuning. The beat oscillator is set as described above, but with the crystal filter in operation and adjusted to its sharpest position, if variable selectivity is available. The initial adjustment should be made with the phasing control (§ 7-11) in the intermediate position. After it is completed, the beat oscillator should be left set and the receiver tuned to the other side of zero beat (audio-frequency image) on the same carrier to give a beat note of the same tone. This beat will be considerably weaker than the first, and may be "phased out" almost completely by careful adjustment of the phasing control. This is the adjustment for normal operation; it will be found that one side of zero beat has practically disappeared, leaving maximum response on the desired side.

An interfering signal having a beat note differing from that of the a.f. image can be

similarly phased out, provided its carrier frequency is not too near the desired carrier.

Depending upon the filter design, maximum selectivity may cause the dots and dashes to lengthen out so that they seem to "run together." This, plus the fact that tuning is quite critical with extremely high selectivity, may make it desirable to use somewhat less selectivity in ordinary operation. However, it must be emphasized that, to realize the benefits of the crystal filter in reducing interference, it is necessary to do *all* tuning with it in the circuit. Its selectivity is so high that it is almost impossible to find the desired station quickly, should the filter be switched in only when interference is present.

'Phone reception — In reception of 'phone signals, the normal procedure is to set the r.f. and i.f. gain at maximum, switch on the a.v.c., and use the audio gain control for setting the volume. This insures maximum effectiveness of the a.v.c. system in compensating for fading and maintaining constant audio output on either strong or weak signals. On occasion a strong signal close to the frequency of a weaker desired station may take control of the a.v.c., in which case the weaker station will practically disappear because of the reduced gain. In this case better reception may result if the a.v.c. is switched off, using the manual r.f. gain control to set the gain at a point which prevents "blocking" by the stronger signal.

A crystal filter will do much toward reducing interference in 'phone reception. Although the high selectivity cuts sidebands (§ 7-11) and thereby reduces the audio output, especially at the higher audio frequencies, it is possible to use quite high selectivity without destroying intelligibility even though the "quality" of the transmission may suffer. As in the case of c.w. reception, it is advisable to do all tuning with the filter in the circuit. Variable-selectivity filters permit a choice of selectivity to suit interference conditions.

An undesired carrier close in frequency to a desired carrier will heterodyne with it to produce a beat note equal to the frequency difference. Such a heterodyne can be reduced by adjustment of the phasing control in the crystal filter. It cannot be prevented in a "straight" superheterodyne having no crystal filter.

A tone control often will be of help in reducing the effects of high-pitched heterodynes, sideband splatter (§ 5-2) and noise, by cutting off the higher audio frequencies. This, like sideband cutting with high selectivity, causes some reduction in naturalness.

Spurious responses — Spurious responses can be recognized without a great deal of difficulty. Often it is possible to identify an image by the nature of the transmitting station, if the frequency assignments applying to the frequency to which the receiver is tuned are known. However, an image also can be recognized by its behavior with tuning. If the signal causes a heterodyne beat note with the

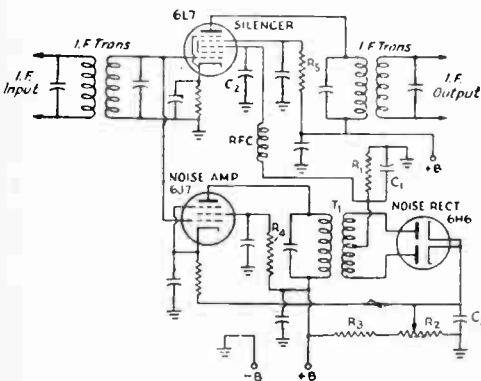


Fig. 734 — I.f. noise-silencing circuit. The plate supply should be 250 volts. Typical values for components are: C_1 — 50–250 μfd . (use smallest value possible without r.f. feedback).

C_2 — 50 μfd . R_2 — 5000-ohm variable.
 C_3 — 0.1 μfd . R_3 — 20,000 ohms.
 R_1 — 0.1 megohm. R_4, R_5 — 0.1 megohm.
 T_1 — Special i.f. transformer for noise rectifier.

desired signal and is actually on the same frequency, the beat note will not change as the receiver is tuned through the signal; but if the interfering signal is an image, the beat will vary in pitch as the receiver is tuned. The beat oscillator in the receiver must be turned off for this test. Using a crystal filter with the beat oscillator on, an image will peak on the side of zero beat opposite that on which the desired signal peaks.

Harmonic response can be recognized by the "tuning rate," or movement of the tuning dial required to give a specified change in beat note. Signals getting into the i.f. via high-frequency oscillator harmonics tune more rapidly (less dial movement) through a given change in beat note than do signals received by normal means.

Harmonics of the beat oscillator can be recognized by the tuning rate of the beat-oscillator pitch control. A smaller movement of the control will suffice for a given change in beat note than is necessary with legitimate signals.

7-17 Servicing Superheterodyne Receivers

Troubleshooting—Two basic methods are employed. One is the "point-by-point" system of static analysis, requiring chiefly a multirange volt-ohm-milliammeter. Beginning at the power transformer, the operating voltages at each point in the circuit are measured. Abnormally low or high voltages, or the absence of indication at a given point in the circuit, presumably indicate a defective component at that point. The analysis may then be completed with the aid of the ohmmeter and a little deduction, ending with repair or replacement of unserviceable components.

An alternative method, commonly employed by professional radio servicemen, is that of "dynamic" or "channel" analysis. The principle is that of applying a test signal to the r.f. input and tracing it stage-by-stage through the receiver. The r.f. and i.f. stages are checked by tuned amplifiers feeding a linear detector which operates an indicator such as vacuum-tube voltmeter, electron-ray voltmeter, or cathode-ray tube. A probe on the end of a shielded lead with a very small condenser (1-2 $\mu\text{mfd.}$) in series is used to pick up the signal in the output of any stage, and the tuned amplifiers are adjusted to the frequency of the stage. Thus the presence or absence of the signal at any point in the receiver may be determined, as well as the relative level.

I.f. alignment—A calibrated signal generator or test oscillator is a practical necessity for initial alignment of an i.f. amplifier. Some means for measuring the output of the receiver also is needed. If the receiver has a tuning meter, its indications will serve for this purpose. Alternatively, if the signal generator is of the modulated type, an a.c. output meter (high-resistance voltmeter with copper-oxide rectifier) can be connected across the primary of the output transformer, or from the plate of

the last audio amplifier through a 0.1- $\mu\text{fd.}$ blocking condenser (§ 2-13) to the receiver chassis. The intensity of sound from the loudspeaker can be judged by ear, if no output meter is available, but this method is not as accurate as those using instruments.

The procedure is as follows: The test oscillator is adjusted to the desired intermediate frequency, and the "hot" or ungrounded output lead is clipped on the grid terminal of the last i.f. amplifier tube. The grounded lead is connected to the receiver chassis. The trimmer condensers of the transformer feeding the second detector are then adjusted for maximum signal output. The hot lead from the generator is next clipped on the grid of the next-to-last i.f. tube, and the second from last i.f. transformer is brought into alignment by adjusting its trimmers for maximum output. This process is continued, working back from the second detector, until all of the i.f. transformers have been aligned. It will be necessary to reduce the output of the signal generator as more of the i.f. amplifier is brought into use, because the increased gain otherwise may cause overloading and consequent inaccurate results. It is desirable always to use the minimum signal strength which gives useful output readings.

The i.f. transformer in the plate circuit of the mixer is aligned with the signal-generator output lead connected to the mixer grid. Since the tuned circuit feeding the mixer grid is tuned to a considerably higher frequency, it can effectively short-circuit the signal-generator output, and therefore it may be necessary to disconnect this circuit. With tubes having a top grid-cap connection, this can be done by simply removing the grid clip from the tube cap.

If the tuning indicator is used as an output meter the a.v.c. should be on; if the audio-output method is used, the a.v.c. should be off. The beat oscillator should be off in either case.

If the i.f. amplifier has a crystal filter, the filter should be switched out. Alignment is then carried out as described above, setting the signal generator as closely as possible to the frequency of the crystal. After alignment, the crystal should be switched in and the oscillator frequency varied back and forth over a small range either side of the crystal frequency to find its exact frequency, which will be indicated by a sharp rise in output. Leaving the signal generator set on the crystal peak, the i.f. trimmers may be realigned for maximum output. The necessary readjustment should be small. The signal generator frequency should be checked frequently, to make sure it has not drifted from the crystal peak.

A modulated signal is not of much value for aligning a crystal-filter i.f. amplifier, since the high selectivity cuts sidebands and the results may be inaccurate if the audio output of the receiver is used as a criterion of alignment. Lacking an a.v.c. tuning meter the transformers may be aligned by ear, using a weak unmodulated signal adjusted to the crystal

peak. Switch on the beat oscillator, adjust to a suitable tone, and align the transformers for maximum audio output.

An amplifier which is only slightly out of alignment, as a result of normal drift from temperature, humidity or aging effects, can be realigned by using any steady signal, such as a local broadcasting station, in lieu of a test oscillator. Allow the receiver to warm up thoroughly (an hour or so), tune in the signal as usual, and "touch up" the i.f. trimmers.

R.f. alignment—The objective in aligning the r.f. circuits in a gang-tuned receiver is to secure adequate tracking over each tuning range. The adjustment may be carried out with a test oscillator of suitable frequency range, or even on noise or such signals as may be heard. First set the tuning dial at the high-frequency end of the range in use. Then set the test oscillator to the frequency indicated by the receiver dial. The test-oscillator output may be connected to the antenna terminals of the receiver for this test. Adjust the oscillator trimmer condenser in the receiver to give maximum response on the test-oscillator signal, then reset the receiver dial to the low-frequency end of the range. Set the test-oscillator frequency near the frequency indicated by the receiver dial and carefully tune the test oscillator until its signal is heard in the receiver. If the frequency of the signal as indicated by the test-oscillator calibration is higher than that indicated by the receiver dial, more inductance (or more capacity in the tracking condenser) is needed in the receiver oscillator circuit; if the frequency is lower, less inductance (less tracking capacity) is required in the receiver oscillator. Most commercial receivers provide some means for varying the inductances of the coils

or the capacity of the tracking condenser, to permit aligning the receiver tuning with the dial calibration. Set the test oscillator to the frequency indicated by the receiver dial, and then adjust the tracking capacity or inductance of the receiver oscillator coil to obtain maximum response. After making this adjustment, recheck the high-frequency end of the scale as previously described. It may be necessary to go back and forth between the ends of the range several times before the proper combination of inductance and capacity is secured. In many cases, better over-all tracking will result if frequencies near but not actually at the ends of the tuning range are selected, instead of taking the extreme dial settings.

After the oscillator range is properly adjusted, set the receiver and test oscillator to the high-frequency end of the range. Adjust the mixer trimmer condenser for maximum hiss or signal, then the r.f. trimmers. Reset the tuning dial and test oscillator to the low-frequency end of the range, and repeat; if the circuits are properly designed, no change in trimmer settings should be necessary. If it is necessary to increase the trimmer capacity in any circuit, it indicates that more inductance is needed; if less capacity resonates the circuit, less inductance is required.

Tracking seldom is perfect throughout a tuning range, so that a check of alignment at intermediate points in the range may show it to be slightly off. Normally the gain variation from this cause will be small, however, and it will suffice to bring the circuits into line at both ends of the range. If most reception is in a particular part of the range, such as an amateur band, the circuits may be aligned for maximum performance in that region, even though the ends of the frequency range as a whole may be slightly out of alignment.

Visual alignment—More accurate and efficient alignment of receiver circuits may be performed with the aid of a visual curve-tracer or "wobbulator" which traces out the response curve visually on a cathode-ray oscilloscope. This is accomplished by using a special signal generator in which the oscillator frequency is varied over a suitable range at a low audio rate. The horizontal sweep of the oscilloscope is synchronized with the rate of variation of the test frequency, so that the horizontal deflection is a function of frequency. The rectified output of the second detector is connected to the vertical deflection plates of the oscilloscope. The spot on the screen therefore traces a curve proportional to the receiver response in terms of the instantaneous value of the oscillator frequency. This visual response curve, which may be that of the entire receiver or of any stage, is continually visible as a whole. Thus the effect of any adjustment of the circuits may be observed much more rapidly than is possible with an ordinary signal generator and output meter, particularly in the case of wide-band i.f. circuits.

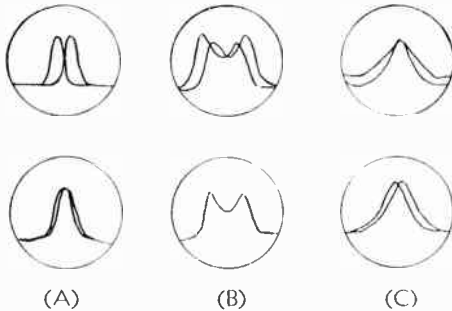


Fig. 735—Oscilloscope patterns of response characteristics on a visual curve tracer. The upper row illustrates various kinds of misalignment; the lower row shows the same stages properly aligned. A, i.f. curve of a selective communications-type receiver, with all transformers mistuned on one side of resonance (top). Below, the peaks coincide when properly aligned, even though skirts do not precisely match. B, at the top, a broadband f.m. receiver curve taken after alignment by the fixed-frequency and output-meter method; the lower curve shows the improvement after careful visual alignment. C, the pattern of a medium-selectivity receiver with transformers misaligned symmetrically on either side of resonance (top); below, the same i.f. correctly aligned but with the test oscillator tuned slightly off frequency to displace the return trace for better examination.

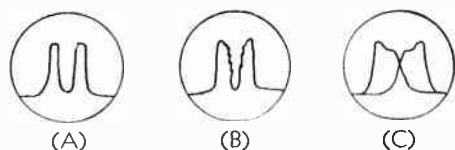


Fig. 736 — A, a typical single-trace response curve of a selective high-fidelity i.f. system. B, pattern of the amplifier in A made highly regenerative, illustrating instability. C, double trace of a single overcoupled i.f. stage with the return trace displaced. A similar "knee" located lower on the skirts would indicate regeneration.

Apparatus and methods for obtaining visual curve traces are described in Chapter Nineteen. The simplest arrangement is that which employs a reactance-tube modulated oscillator operating on 1000 kc., the output of which is combined with that from an unmodulated variable-tuning r.f. oscillator in a mixer tube, to provide a heterodyned signal at the desired center frequency.

Either "double trace" and "single trace" patterns may be used. The double trace pattern is obtained by applying a triangular sweep to the f.m. oscillator at a frequency half that of the sawtooth sweep on the horizontal plates of the cathode-ray tube. The return sweep produces a reversed pattern superimposed on the first, and is useful for checking symmetry and frequency calibration. The single-trace pattern shows the same two opposite-sequence resonance curves, but with the second curve displaced by a half cycle of the audio sweep frequency. It is useful in displaying irregularities in the pattern which might be obscured by superposition of the traces.

The alignment procedure follows that described for the oscillator-output-meter method. Assuming a diode second detector, run a shielded lead to the vertical input terminals of the oscilloscope from the "high" side of the diode load resistor — usually the audio volume control. With a triode biased detector, the bias resistor and by-pass condenser circuit should be opened and the vertical terminal connected to the cathode of the detector tube across a 0.5-megohm leak to ground, bypassed with a 250- μ fd. condenser. The plate load should be shorted out. This will make the resonance patterns appear upside down, but does not change their interpretation.

The r.f. output from the mixer should connect directly to the grid of the last i.f. tube. Add the i.f. frequency to 1000 kc. and set the unmodulated signal generator to this frequency. For example, if the i.f. is 465 kc., set the a.m. signal generator to 1465 kc. At the usual bandwidth of 30 kc., the signal at the grid of the last i.f. stage will swing from 450 kc. to 480 kc. and back. If the signal generator is set to the exact i.f., a double-trace pattern should appear on the screen. Center this pattern with the oscilloscope sweep vernier. Adjust the i.f. trimmers until these peaks coincide. For single-trace analysis, the oscilloscope sweep frequency should be reduced one half.

To align the next i.f. stage, move the r.f. output lead to the grid of the tube and adjust the next i.f. transformer. It may be necessary to readjust the output transformer after this operation. When aligning triple-tuned or high-fidelity i.f. circuits, it is most important that the peaks in the double pattern coincide and have nearly equal amplitude.

To align the r.f. and mixer input circuits, the variable-frequency signal generator should be set to a frequency which, by addition to 1000 kc., produces the desired r.f. signal frequency. As each stage is added, the output level must be reduced to keep the pattern on the screen. To avoid overloading, only enough signal should be used to overcome local interference. Adjust the r.f. trimmers for maximum vertical amplitude of the pattern, as with an output meter. Dial calibration can be checked by setting the test oscillator on frequency and adjusting the h.f. oscillator trimmer in the receiver to center the pattern on the screen.

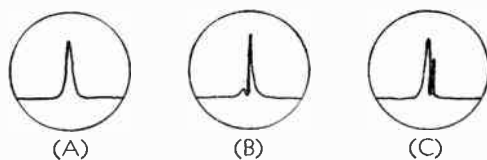


Fig. 737 — Response curves of a superheterodyne with crystal filter (made at a very low repetition rate). A, crystal in "broad" position, phasing control at center. B, phasing control set to place the rejection slot on low-frequency side. C, with slot on high-frequency side.

Oscillation in r.f. or i.f. amplifiers — Oscillation in high-frequency amplifier and mixer circuits may be evidenced by squeals or "birdies" as the tuning is varied, or by complete lack of audible output if the oscillation is strong enough to cause the a.v.c. system to reduce the receiver gain drastically. Oscillation can be caused by poor connections in the common ground circuits, especially to the tuning-condenser rotors. Inadequate or defective by-pass condensers in cathode, plate and screen-grid circuits also can cause such oscillation. In some cases it may be advisable to provide a shield between the stators of pre-r.f. amplifier and first-detector ganged tuning condensers, in addition to the usual tube and interstage shielding. A metal tube with an ungrounded shell will cause trouble. Improper screen-grid voltage, resulting from a shorted or too-low screen-grid series resistor, also may be responsible for such instability.

Oscillation in the i.f. circuits is independent of high-frequency tuning, and is indicated by a continuous squeal which appears when the gain is advanced with the c.w. beat oscillator on. It can result from similar defects in i.f. amplifier circuits. Inadequate cathode by-pass capacitance is a common cause of such oscillation. An additional by-pass condenser of 0.1 to 0.25 μ fd. usually will remedy the trouble. Similar treatment can be applied to the screen-grid and plate by-pass filters of i.f. stages.

Instability — “Birdies” or a mushy hiss occurring with tuning of the high-frequency oscillator may indicate that the oscillator is “squegging” or oscillating simultaneously at high and low frequencies (§ 7-4). This may be caused by a defective tube, too-high oscillator plate or screen-grid voltage, excessive feedback, or too-high grid-leak resistance.

A varying beat note in c.w. reception indicates instability in either the h.f. oscillator or beat oscillator, usually the former. The stability of the beat oscillator can be checked by introducing a signal of intermediate frequency (from a test oscillator) into the i.f. amplifier; if the beat note is unstable, the trouble is in the beat oscillator. Poor connections or defective parts are the likely cause. Instability in the high-frequency oscillator may be the result of poor circuit design (§ 7-10), loose connections, defective tubes or circuit components, or poor voltage regulation in the oscillator plate and/or screen supply circuits. Mixer pulling of the oscillator circuit (§ 7-9) also will cause the beat-note to “chirp” on strong c.w. signals because the oscillator load changes slightly.

In 'phone reception with a.v.c., a peculiar type of instability (“motorboating”) may appear if the h.f. oscillator frequency is sensitive to changes in plate voltage. As the a.v.c. voltage rises the electrode currents of the controlled tubes decrease, decreasing the load on the power supply and causing its output voltage to rise. Since this increases the voltage applied to the oscillator, its frequency changes correspondingly, throwing the signal off the peak of the i.f. resonance curve and reducing the a.v.c. voltage, thus tending to restore the original conditions. The process then repeats itself, at a rate determined by the signal strength and the time constant of the power-supply circuits. This effect is most pronounced with high i.f. selectivity, as when a crystal filter is used, and can be cured by making the oscillator relatively insensitive to voltage changes and by regulating the plate voltage supply (§7-10).

¶ 7-18 Reception of Frequency-Modulated Signals

F.m. receivers — A frequency-modulation receiver differs in circuit design from one designed for amplitude modulation chiefly in the arrangement used for detecting the signal. Detectors for amplitude-modulated signals do not respond to frequency modulation. It is also necessary, for full realization of the noise-reducing benefits of the f.m. system, that the signal applied to the detector be completely free from amplitude modulation. In practice, this is attained by preventing the signal from rising above a given amplitude by means of a limiter (§ 3-10, 7-15). Since the weakest signal must be amplitude-limited, high gain must be provided ahead of the limiter; the superheterodyne type of circuit almost invariably is used to provide the necessary gain.

The r.f. and i.f. stages in a superheterodyne for f.m. reception are practically identical in circuit arrangement with those in an a.m. receiver. Since the use of f.m. is confined to the very-high frequencies (above 28 Mc.) a high intermediate frequency is employed, usually between 4 and 5 Mc. This not only reduces image response but also provides the greater band-width necessary to accommodate wide-band frequency-modulated signals.

Receiver requirements — The primary requirements are sufficient r.f. and i.f. gain to “saturate” the limiter even with a weak signal, sufficient band-width (§ 7-2) to accommodate the full frequency deviation either side of the carrier frequency without undue attenuation at the edges of the band, a limiter circuit which functions properly on both rapid and slow variations in amplitude, and a detector which gives a linear relationship between frequency deviation and amplitude output. The audio circuits are the same as in other receivers (§ 7-5), except that in communications-type receivers it is desirable to cut off the upper audio range by a low-pass filter (§ 2-11) because higher-frequency noise components have the greatest amplitude in an f.m. receiver.

The limiter — Limiter circuits generally are of the plate-saturation type (§ 7-15), where low plate and screen voltage are used to limit the plate-current flow at high signal amplitudes. Fig. 738-A is a typical circuit. The tube is self-biased (§ 3-6) by a grid leak, R_1 , and condenser, C_1 . R_2 , R_3 and R_4 form a voltage divider

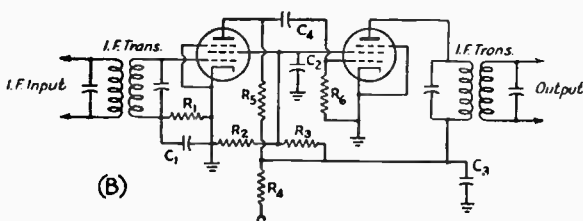
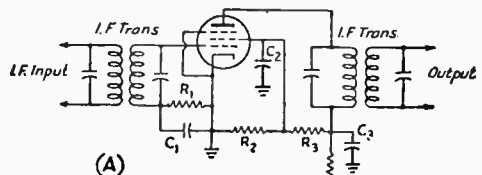


Fig. 738 — F.m. limiter circuits. A, single-tube plate-saturation limiter; B, cascade limiter. Typical values are:

	Circuit A	Circuit B
C_1 —	100 μ fd.	100 μ fd.
C_2, C_3 —	0.1 μ fd.	0.1 μ fd.
C_4 —	250 μ fd.	250 μ fd.
R_1 —	0.1 megohm.	50,000 ohms.
R_2 —	2000 ohms.	2000 ohms.
R_3 —	50,000 ohms.	50,000 ohms.
R_4 —	0-50,000 ohms.	0-50,000 ohms.
R_5 —	4000 ohms.	4000 ohms.
R_6 —	0.2 megohm.	0.2 megohm.

Plate-supply voltage is 250 in both circuits.

(§ 8-10) which puts the desired voltages on the screen and plate. The lower the voltages the lower the signal level at which limiting occurs, but the r.f. output voltage of the limiter also is lower. C_2 and C_3 are the plate and screen by-pass condensers, of conventional value for the intermediate frequency used. The time constant (§ 2-6) of R_1C_1 determines the behavior of the limiter with respect to rapid and slow amplitude variations. For best operation on impulse noise (§ 7-15) the time constant should be small, but a too-small time constant limits the range of signal strengths the limiter can handle without departing from the constant-output condition. A larger time constant is better in this respect but is not so effective for rapid variations. Compromise constants are shown in Fig. 738.

The cascade limiter, Fig. 738-B, overcomes this by making the time constant in the first grid circuit suitable for effective operation on impulse noise, and that in the second grid (C_4R_6) optimum for a wide range of input signal strengths. This results, in addition, in more constant output over a very wide range of input signal amplitudes because the voltage at the grid of the second stage already is partially amplitude-limited. Resistance coupling ($R_5C_4R_6$) is used for simplicity and to prevent unwanted regeneration, additional gain at this point being unnecessary.

The rectified voltage developed across R_1 in either circuit may be applied to the i.f. amplifier for a.v.c. (§ 7-13).

Discriminator circuits and operation—

The f.m. detector commonly is called a *discriminator*, because of its ability to discriminate between frequency deviations above and those below the carrier frequency.

A rectifier connected to an ordinary tuned circuit adjusted so that the signal frequency falls on one side of the response curve constitutes an elementary discriminator, because the rectifier output will vary with a change in the carrier frequency. If two such circuits are used with a balanced rectifier, one tuned above and the other below the signal frequency, amplitude variations are balanced out and the combined rectified current is proportional to the frequency deviation.

The circuit most widely used is the "series" or center-tuned discriminator shown in Fig. 739-A. A special i.f. coupling transformer is used between the limiter and detector. Its secondary, L_1 , is center-tapped and is connected back to the plate side of the primary circuit, which otherwise is conventional. C_4 is the tuning condenser. The load circuits of the two diode rectifiers ($R_1C_1R_2C_2$) are connected in series; constants are the same as in ordinary diode detector circuits (§ 7-3). Audio output is taken from across the two load resistances.

The primary and secondary circuits are both adjusted to resonance in the center of the i.f. pass-band. The voltage applied to the rectifiers consists of two components, that induced in the

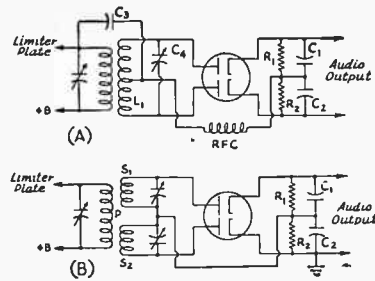


Fig. 739 — F.m. discriminator circuits. In both circuits typical values for C_1 and C_2 are $100 \mu\text{fd.}$ each; R_1 and R_2 , 0.1 megohm each. C_3 in A is approximately $50 \mu\text{fd.}$, depending upon the intermediate frequency; RFC should be of a type designed for the i.f. in use (2.5 mh. is satisfactory for i.f.s of 4 to 5 Mc.). In either circuit the ground may be moved from the lower end of C_2 to the junction of C_1 and C_2 , for push-pull audio output.

secondary by the inductive coupling and that fed to the center of the secondary through C_2 . The phase relations between the two are such that at resonance the rectified load currents are equal in amplitude but flow in opposite directions through R_1 and R_2 , hence the net voltage across the terminals marked "audio output" is zero. When the carrier deviates from resonance the induced secondary current either lags or leads, depending upon whether the deviation is to the high- or low-frequency side, and this phase shift causes the induced current to combine with that fed through C_2 in such a way that one diode gets more voltage than the other when the frequency is below resonance, while the second diode gets the larger voltage when the frequency is higher than resonance. The voltage appearing across the output terminals is the difference between the two diode voltages. Thus a characteristic like that of Fig. 740 results, where the net rectified output voltage has opposite polarity for frequencies on either side of resonance, and up to a certain point becomes greater in amplitude as the frequency deviation is greater. The straight-line portion of the curve is the useful detector characteristic. The separation between the peaks which mark the ends of the linear portion of the curve depends upon the Q s of the primary and secondary circuits and the degree of coupling. The separation becomes greater with low Q s and close coupling. The circuit ordinarily is designed so that the peaks fall just outside the limits of the pass-band, thus utilizing most of the straight portion of the curve. Since the audio output is proportional to the change in d.c. voltage with deviation, it is advantageous for maximum output to keep the frequency separation between peaks down to the minimum value necessary for a linear characteristic.

A second type of discriminator is shown in Fig. 739-B. Two secondary circuits are used, one tuned above the center frequency of the i.f. pass-band and the other below. They are coupled equally to the primary, which is tuned to the center frequency. As the carrier fre-

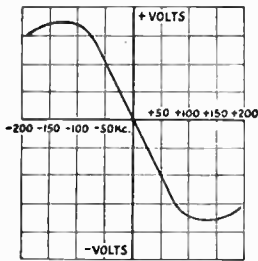


Fig. 740 — Characteristic of a typical f.m. detector. The vertical axis represents the voltage developed across the load resistor as the frequency varies from the exact resonance frequency. This detector would handle f.m. signals up to a band-width of 150 kc. over the linear portion of the curve.

quency deviates the voltages induced in the secondaries will change in amplitude, the larger voltage appearing across the secondary being nearer resonance with the instantaneous frequency. The detection characteristic is similar to that of the center-tuned discriminator. The peak separation is determined by the Q s of the circuits, the coefficient of coupling, and the tuning of the secondaries. High Q s and loose coupling are required for close peak separation.

A simple self-quenched superregenerative receiver may be used as a frequency detector if it is tuned so that the carrier frequency falls along the slope of the resonance curve. Two such detectors, off-tuned on either side of the carrier, may be used in push-pull. An alternative arrangement employing a superregenerative stage as a first i.f. amplifier at 75 Mc., following a converter unit, provides high gain and linear response with relatively few stages.


F.m. receiver alignment — Alignment of f.m. receivers up to the limiter is carried out as described in § 7-17. For output measurement, a 0-1 milliammeter or 0-500 microammeter should be connected in series with the limiter grid resistor (R_1 in Fig. 738) at the grounded end; or, if the voltage drop across R_1 is used for a.v.c. and the receiver is provided with a tuning meter (§ 7-13), the tuning meter may be used as an output meter. An accurately calibrated signal generator or test oscillator is desirable, since the i.f. should be aligned to be as symmetrical as possible; that is, the output reading should be the same for any two test oscillator settings the same number of kilocycles above or below resonance. It is not necessary to have uniform response over the whole band to be received, although the output at the edges of the band (limit of deviation (§ 5-11) of the transmitted signals) should not be less than 25 per cent of the voltage at resonance. In communications work, a band-width of 30 kc. or less (15 kc. or less deviation) is commonly used. Output readings should be taken with the oscillator set at intervals of a few kilocycles either side of resonance up to the band limits.

After the i.f. (and front-end) alignment, the limiter operation should be checked. This can be done by temporarily disconnecting C_3 , if the discriminator circuit of Fig. 739-A is used, disconnecting R_1 and C_1 on the cathode side, and inserting the milliammeter or microammeter in series with R_2 at the grounded end. This converts the discriminator to an ordinary

diode rectifier. Varying the signal-generator frequency over the channel, with the discriminator transformer adjusted to resonance, should show no change in output (at the bandwidths used for communications purposes) as indicated by the rectified current read by the meter. At this point various plate and screen voltages can be tried on the limiter tube or tubes, to determine the set of conditions which gives maximum output with adequate limiting (no change in rectified current).

When the limiter has been checked the discriminator connections can be restored, leaving the meter connected in series with R_1 . Provision should be made for reversing the connections to the meter terminals, to take care of the reversal in polarity of the rectified current. Set the signal generator to the center frequency of the band and adjust the discriminator transformer trimmer condensers to resonance, which will be indicated by zero rectified current. Then set the test oscillator at the deviation limit (§ 5-11) on one side of the center frequency, and note the meter reading. Reverse the meter terminals and set the test oscillator at the deviation limit on the other side. The two readings should be the same. If they are not, they can be made so by a slight adjustment of the primary trimmer. This will necessitate rechecking the response at resonance to make sure it is still zero. Generally, the secondary trimmer will chiefly affect the zero-response frequency, while the primary trimmer will have most effect on the symmetry of the discriminator peaks. A detector curve having satisfactory linearity can be obtained by cut-and-try adjustment of both trimmers.

Fig. 741 — Oscilloscope patterns in f.m. i.f. alignment. A — I.f. amplifier response. B — Over-all characteristic through the f.m. detector.

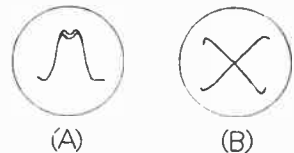

A visual curve tracer is particularly advantageous in aligning the wide-band i.f. amplifiers of f.m. receivers. The i.f. is first aligned with the discriminator circuit converted into an a.m. diode detector, as described above, the pattern appearing as in Fig. 741-A. The over-all characteristic, including the f.m. detector, is shown in Fig. 741-B.

Tuning and operation — An f.m. receiver gives greatest noise reduction when the carrier is tuned exactly to the center of the receiver pass-band and to the point of zero response in the discriminator. Because of the decrease in noise, this point is readily recognized.

When an amplitude-modulated signal is tuned in its modulation practically disappears at exact resonance, only those nonsymmetrical modulation components which may be present being detected. If the signal is to one side or the other of resonance, however, it is capable of causing interference to an f.m. signal.

Power Supply

§ 8-1 Power-Supply Requirements

Filament supply — Except for tubes designed for battery operation, the filaments or heaters of vacuum tubes used in both transmitters and receivers are universally operated on alternating current obtained from the power line through a step-down transformer (§ 2-9) delivering a secondary voltage equal to the rated voltage of the tubes used. The transformer should be designed to carry the current taken by the number of tubes which may be connected in parallel (§ 2-6) across it. The filament or heater transformer generally is center-tapped, to provide a balanced circuit for eliminating hum (§ 3-6).

For medium- and high-power r.f. stages of transmitters, and for high-power audio stages, it is desirable to use a separate filament transformer for each section of the transmitter, installed near the tube sockets. This avoids the necessity for abnormally large wires to carry the total filament current for all stages without appreciable voltage drop. Maintenance of rated filament voltage is highly important, especially with thoriated-filament tubes, since under- or over-voltage may reduce filament life.

Plate supply — Direct current must be used for the plates of tubes, since any variation in plate current arising from power-supply causes will be superimposed on the signal being received or transmitted, giving an undesirable type of modulation (§ 5-1) if the variations occur at an audio-frequency (§ 2-7) rate. Unvarying direct current is called *pure d.c.*, to distinguish it from current which may be unidirectional but of pulsating character. The use of pure d.c. on the plates of transmitting tubes is required by FCC regulations on all frequencies below 60 Mc.

Sources of plate power — D.c. plate power is usually obtained from rectified and filtered alternating current, but in low-power and portable installations may be secured from batteries. Dry batteries may be used for very low-power portable equipment, but in many cases a storage battery is used as the primary power source, in conjunction with an interrupter giving pulsating d.c. which is applied to the primary of a step-up transformer (§ 8-10).

Rectified-a.c. supplies — Since the power-line voltage ordinarily is 115 or 230 volts, a step-up transformer (§ 2-9) is used to obtain the desired voltage for the plates of the tubes in the equipment. The alternating secondary current is changed to unidirectional current by means of diode rectifier tubes (§ 3-1), and

then passed through an inductance-capacity filter (§ 2-11) to the load circuit. The *load resistance* in ohms is equal to the d.c. output voltage of the power supply divided by the current in amperes (Ohm's Law, § 2-6).

Voltage regulation — Since there is always some resistance in power-supply circuits, and since the filter normally depends to a considerable extent upon the energy storage of inductance and capacity (§ 2-3, 2-5), the output voltage will depend upon the current drain on the supply. The change in output voltage with change in load current is called the *voltage regulation*. It is expressed as a percentage:

$$\% \text{ Regulation} = \frac{100 (E_1 - E_2)}{E_2}$$

where E_1 is the no-load voltage (no current in the load circuit) and E_2 the full-load voltage (rated current in load circuit).

§ 8-2 Rectifiers

Purpose and ratings — A rectifier is a device which will conduct current only in one direction. The diode tube (§ 3-1) is used almost exclusively for rectification in d.c. power supplies used with radio equipment. The important characteristics of tubes used as power-supply rectifiers are the voltage drop between plate and cathode at rated current, the maximum permissible inverse peak voltage, and the permissible peak plate current.

Voltage drop — Tube voltage drop depends upon the type of tube. In vacuum-type rectifiers it increases with the current flowing because of space-charge effect (§ 3-1), but can be minimized by using very small spacing between plate and cathode as is done in some rectifiers for receiver power supplies. Mercury-vapor rectifiers (§ 3-5) have a constant drop of about 15 volts, regardless of current. This is much smaller than the voltage drops encountered in vacuum-type rectifiers.

Inverse peak voltage — This is the maximum voltage developed between the plate and cathode of the rectifier when the tube is not conducting; i.e., when the plate is negative with respect to the cathode.

Peak plate current — This is the maximum *instantaneous* current through the rectifier. It can never be smaller than the load current in ordinary circuits, and may be several times higher.

Operation of mercury-vapor rectifiers — Because of its constant voltage drop, the mercury-vapor rectifier is more susceptible to damage than the vacuum type. With the latter, the increase in voltage drop tends to

limit current flow on heavy overloads, but the mercury-vapor rectifier does not have this limiting action and the cathode may be damaged under similar conditions.

In mercury-vapor rectifiers a phenomenon known as "arc-back," or breakdown of the mercury vapor and conduction in the opposite direction to normal, occurs at high inverse peak voltages, hence such tubes always should be operated within their inverse-peak voltage ratings. Arc-back also may occur if the cathode temperature is below normal; therefore the heater or filament voltage should be checked to make sure that the rated voltage is applied. This check should be made at the tube socket, to avoid errors caused by voltage drop in the leads. For the same reason, the cathode should be allowed to come up to its final temperature before plate voltage is applied; the time required for this is of the order of 15 to 30 seconds. When a tube is first installed, or is put into service after a long period of idleness, the cathode should be heated for a period of 10 minutes or so before application of plate voltage.

¶ 8-3 Rectifier Circuits

Half-wave rectifiers — The simple diode rectifier (§ 3-1) is called a *half-wave rectifier*, because it can pass only half of each cycle of alternating current. Its circuit is shown in Fig. 801-A. At the top of the figure is a representation of the applied a.c. voltage, with positive and negative alternations (§ 2-7) marked.

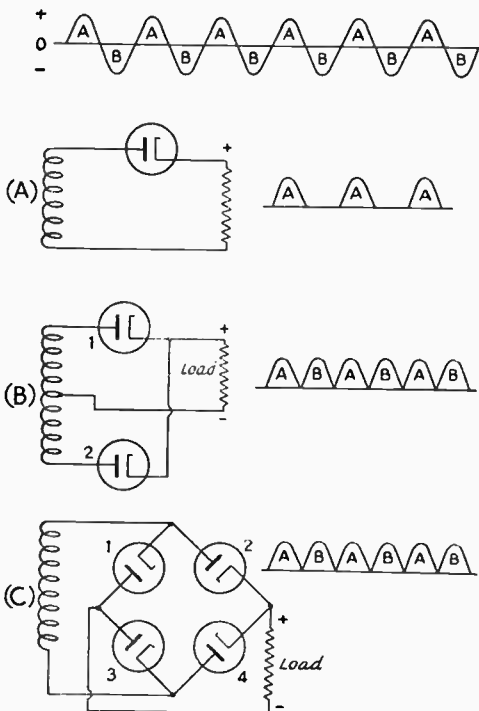


Fig. 801 — Fundamental vacuum-tube rectifier circuits.

When the plate is positive with respect to cathode, plate current flows through the load as indicated in the drawing at the right, but when the plate is negative with respect to cathode no current flows. This is indicated by the gaps in the output drawing. The output current is unidirectional but pulsating.

In this circuit the inverse peak voltage is equal to the maximum transformer voltage, which in the case of a sine wave is 1.41 times the r.m.s. voltage (§ 2-7).

Full-wave center-tap rectifier — Fig. 801-B shows the "full-wave center-tap" rectifier circuit, so called because both halves of the a.c. cycle are rectified and because the transformer secondary winding must consist of two equal parts with a connection brought out from the center. When the upper end of the winding is positive, current can flow through rectifier No. 1 to the load; this current cannot pass through rectifier No. 2 because its cathode is positive with respect to its plate. The circuit is completed through the transformer center-tap. When the polarity reverses the upper end of the winding is negative and no current can flow through No. 1, but the lower end is positive and therefore No. 2 passes current to the load, the return connection again being the center-tap. The resulting waveshape is shown at the right.

Since the two rectifiers are working alternately in this circuit, each half of the transformer secondary must be wound to deliver the full-load voltage; hence the total voltage across the transformer terminals is twice that required with the half-wave rectifier. Assuming negligible voltage drop in the particular rectifier which may be conducting at any instant, the inverse peak voltage on the other rectifier is equal to the maximum voltage between the outside terminals of the transformer. In the case of a sine wave, this is 1.41 times the total secondary r.m.s. voltage (§ 2-7).

Because energy is delivered to the load at twice the average rate as in the case of a half-wave rectifier, each tube carries only half the load current.

The bridge rectifier — The "bridge" type of full-wave rectifier is shown in Fig. 801-C. Its operation is as follows: When the upper end of the winding is positive, current can flow through No. 2 to the load but not through No. 1. On the return circuit, current flows through No. 3 by way of the lower end of the transformer winding. When the polarity reverses and the lower end of the winding becomes positive, current flows through No. 4 and the load and through No. 1 by way of the upper side of the transformer. The output waveshape is shown at the right.

The inverse peak voltage is equal to the maximum transformer voltage, or 1.41 times the r.m.s. secondary voltage in the case of a sine wave (§ 2-7). Energy is delivered to the load at the same average rate as in the case of the full-wave center-tap rectifier, each pair of tubes in series carrying half the load current.

8-4 Filters

Purpose of filter — As shown in Fig. 801, the output of a rectifier is pulsating d.c., which would be unsuitable for most vacuum-tube applications (§ 8-1). A *filter* is used to smooth out the pulsations so that practically unvarying direct current flows through the load circuit. The filter utilizes the energy-storage properties of inductance and capacity (§ 2-3, 2-5), by virtue of which energy stored in electromagnetic and electrostatic fields when the voltage and current are rising is restored to the circuit when the voltage and current fall, thus filling in the “gaps” or “valleys” in the rectified output.

Ripple voltage and frequency — The pulsations in the output of the rectifier can be considered to be caused by an alternating current superimposed on a steady direct current (§ 2-13). Viewed from this standpoint, the filter may be considered to consist of bypass condensers which short-circuit the a.c. while not interfering with the flow of d.c., and chokes or inductances which permit d.c. to flow through them but which have high reactance for the a.c. (§ 2-13). The alternating component is called the *ripple*. The effectiveness of the filter may be measured by the *per cent ripple*, which is the r.m.s. value of the a.c. ripple voltage expressed as a percentage of the d.c. output voltage. With an effective filter, the ripple percentage will be low. Five per cent ripple is considered satisfactory for c.w. transmitters, but lower values (of the order of 0.25 per cent) are necessary for hum-free speech transmission and for receiver plate supplies.

The ripple frequency depends upon the line frequency and the type of rectifier. In general, it consists of a fundamental plus a series of harmonics (§ 2-7), the latter being relatively unimportant since the fundamental is hardest to smooth out. With a half-wave rectifier, the fundamental is equal to the line frequency; with a full-wave rectifier, the fundamental is equal to twice the line frequency, or 120 cycles in the case of a 60-cycle supply.

Types of filters — Inductance-capacity filters are of the low-pass type (§ 2-11), using series inductances and shunt capacitances. Practical filters are identified as *condenser-input* and *choke-input*, depending upon whether a capacity or inductance is used as the first element in the filter. Resistance-capacity filters (§ 2-11) are used in applications where the current is very low and the voltage drop in the resistor can be tolerated.

Bleeder resistance — Since the condensers in a filter will retain their charge for a considerable time after power is removed (provided the load circuit is open at the time), it is good practice to connect a resistor across the output of the filter to discharge the condensers when the power supply is not in use. The resistance usually is high enough so that only a relatively small percentage of the total output current is consumed in it during normal operation.

Components — Filter condensers are made in several different types. Electrolytic condensers, which are available for voltages up to about 800, combine high capacity with small size, since the dielectric is an extremely thin film of oxide on aluminum foil. Condensers for higher voltages usually are made with a dielectric of thin paper impregnated with oil. The *working voltage* of a condenser is the voltage which it will withstand continuously.

Filter chokes or inductances are wound on iron cores, with a small gap in the core to prevent magnetic saturation of the iron at high currents. When the iron becomes saturated its permeability (§ 2-5) decreases, consequently the inductance also decreases. Despite the air-gap, the inductance of a choke usually varies to some extent with the direct current flowing in the winding; hence it is necessary to specify the inductance at the current which the choke is intended to carry. Its inductance with little or no direct current flowing in the winding may be considerably higher than the load value.

8-5 Condenser-Input Filters

Ripple voltage — The conventional condenser-input filter is shown in Fig. 802-A. No simple formulas are available for computing

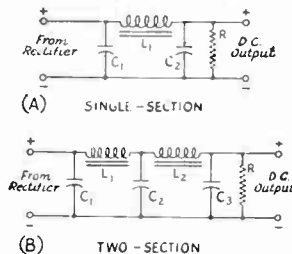


Fig. 802 — Condenser-input filter circuits.

the ripple voltage, but it will be smaller as both capacity and inductance are made larger. Adequate smoothing for transmitting purposes can be secured by using 4 to 8 $\mu\text{fd.}$ at C_1 and C_2 and 20 to 30 henrys at L_1 , for full-wave rectifiers with 120-cycle ripple (§ 8-4). A higher ratio of inductance to capacity may be used at higher load resistances (§ 8-1).

For receivers, as shown in Fig. 802-B, an additional choke, L_2 , and condenser, C_3 , of the same approximate values, are used to give additional smoothing. In such supplies the three condensers generally are 8 $\mu\text{fd.}$ each, although the input condenser, C_1 , sometimes is reduced to 4 $\mu\text{fd.}$ Inductances of 10 to 20 henrys each will give satisfactory filtering with these capacity values.

For ripple frequencies other than 120 cycles, the inductance and capacity values should be multiplied by the ratio $120/F$, where F is the actual ripple frequency.

The bleeder resistance, R , should be chosen to draw 10 per cent or less of the rated output current of the supply. Its value is equal to $1000E/I$, where E is the output voltage and I the bleeder current in milliamperes.

Rectifier peak current—The ratio of rectifier peak current to average load current is high with a condenser-input filter. Small rectifier tubes designed for low-voltage supplies (type 80, etc.) generally carry load-current ratings based on the use of condenser-input filters. With rectifiers for higher power, such as the 866-866-A, the load current should not exceed 25 per cent of the rated peak plate current for one tube when a full-wave rectifier is used, or one-eighth the half-wave rating.

Output voltage—The d.c. output voltage from a condenser-input supply will, with light loads or no load, approach the peak transformer voltage. This is 1.41 times the r.m.s. voltage (§ 2-7) of the transformer secondary, in the case of Figs. 801-A and C, or 1.41 times the voltage from the center-tap to one end of the secondary in Fig. 801-B. At heavy loads, it may decrease to the *average* value of secondary voltage or about 90 per cent of the r.m.s. voltage, or even less. Because of this wide range of output voltage with load current, the voltage regulation (§ 8-1) is inherently poor.

The output voltage obtainable from a given supply cannot readily be calculated, since it depends critically upon the load current and filter constants. Under average conditions it will be approximately equal to or somewhat less than the r.m.s. voltage between the center-tap and one end of the secondary in the full-wave center-tap rectifier circuit (§ 8-3).

Ratings of components—Because the output voltage may rise to the peak transformer voltage at light loads, the condensers should have a working-voltage rating (§ 8-4) at least as high and preferably somewhat higher, as a safety factor. Thus, in the case of a center-tap rectifier having a transformer delivering 550 volts each side of the center-tap, the minimum safe condenser voltage rating will be 550×1.41 or 775 volts. An 800-volt, or preferably a 1000-volt, condenser should be used. Filter chokes should have the inductance specified at full-load current, and must have insulation between the winding and the core adequate to withstand the maximum output voltage.

§ 8-6 Choke-Input Filters

Ripple voltage—The circuit of a single-section choke-input filter is shown in Fig. 803-A. For 120-cycle ripple, a close approximation of the ripple to be expected at the output of the filter is given by the formula:

$$\left. \begin{array}{l} \text{Single} \\ \text{Section} \\ \text{Filter} \end{array} \right\} \% \text{ Ripple} = \frac{100}{LC}$$

where L is in henrys and C in μfd . The product, LC , must be equal to or greater than 20 to reduce the ripple to 5 per cent or less. This figure represents, in most cases, the economical limit for the single-section filter. Smaller percentages of ripple usually are more economically obtained with the two-section filter of Fig.

803-B. The ripple percentage (120-cycle ripple) with this arrangement is given by the formula:

$$\left. \begin{array}{l} \text{Two} \\ \text{Section} \\ \text{Filter} \end{array} \right\} \% \text{ Ripple} = \frac{650}{L_1 L_2 (C_1 + C_2)^2}$$

For a ripple of 0.25 per cent or less, the denominator should be 2600 or greater.

These formulas can be used for other ripple frequencies by multiplying each inductance and capacity value in the filter by the ratio $120/F$, where F is the actual ripple frequency.

The distribution of inductance and capacity in the filter will be determined by the value of input-choke inductance required (next paragraph), and the permissible a.c. output impedance. If the supply is intended for use with an audio-frequency amplifier, the reactance (§ 2-8) of the last filter condenser should be small (20 per cent or less) compared to the other a.f. resistance or impedance in the circuit, usually the tube plate resistance and load resistance (§ 3-2, 3-3). On the basis of a lower a.f. limit of 100 cycles for speech amplification (§ 5-9), this condition is usually satisfied when the output capacity (last filter capacity) of the filter is 4 to 8 μfd ., the higher value being used for the lower tube and load resistances.


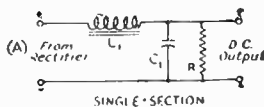


Fig. 803 Choke-input filter circuits.

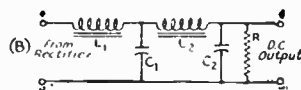

The input choke—The rectifier peak current and the power-supply voltage regulation depend almost entirely upon the inductance of the input choke in relation to the load resistance (§ 8-1). The function of the choke is to raise the ratio of average to peak current (by its energy storage), and to prevent the d.c. output voltage from rising above the average value (§ 2-7) of the a.c. voltage applied to the rectifier. For both purposes, its impedance (§ 2-8) to the flow of the a.c. component (§ 8-4) must be high.

The value of input-choke inductance which prevents the d.c. output voltage from rising above the average of the rectified a.c. wave is its *critical inductance*. For 120-cycle ripple, it is given by the approximate formula:

$$L_{crit.} = \frac{\text{Load resistance (ohms)}}{1000}$$

For other ripple frequencies, the inductance required will be the above value multiplied by the ratio of 120 to the actual ripple frequency.

With inductance values less than critical, the d.c. output voltage will rise because the filter tends to act as a condenser-input filter (§ 8-5). With critical inductance, the peak

plate current of one tube in a center-tap rectifier will be approximately 10 per cent higher than the d.e. load current taken from the supply.

An inductance of twice the critical value is called the *optimum* value. This value gives a further reduction in the ratio of peak to average plate current, and represents the point at which further increase in inductance does not give correspondingly improved operating characteristics.

Swinging chokes — The formula for critical inductance indicates that the inductance required varies widely with the load resistance. In the case where there is no load except the bleeder (§ 8-4) on the power supply, the critical inductance required is highest; much lower values are satisfactory when the full-load current is being delivered. Since the inductance of a choke tends to rise as the direct current flowing through it is decreased (§ 8-4), it is possible to effect an economy in materials by designing the choke to have a "swinging" characteristic such that it has the required critical inductance value with the bleeder load only, and about the optimum inductance value at full load. If the bleeder resistance is 20,000 ohms and the full-load resistance (including the bleeder) is 2500 ohms, a choke which swings from 20 henrys to 5 henrys over the full output-current range will fulfill the requirements.

Resonance — Resonance effects in the series circuit across the output of the rectifier which is formed by the first choke (L_1) and first filter condenser (C_1) must be avoided, since the ripple voltage would build up to large values (§ 2-10). This not only is the opposite action to that for which the filter is intended, but also may cause excessive rectifier peak currents and abnormally high inverse peak voltages. For full-wave rectification the ripple frequency will be 120 cycles for a 60-cycle supply (§ 8-4), and resonance will occur when the product of choke inductance in henrys times condenser capacity in microfarads is equal to 1.77. The corresponding figure for 50-cycle supply (100-cycle ripple frequency) is 2.53, and for 25-cycle supply (50-cycle ripple frequency), 13.5. At least twice these products should be used to ensure against resonance effects.

Output voltage — Provided the input-choke inductance is at least the critical value, the output voltage may be calculated quite closely by the equation:

$$E_o = 0.9E_t - \frac{(I_b + I_L)(R_1 + R_2)}{1000} - E_r$$

where E_o is the output voltage; E_t is the r.m.s. voltage applied to the rectifier (r.m.s. voltage between center-tap and one end of the secondary in the case of the center-tap rectifier); I_b and I_L are the bleeder and load currents, respectively, in milliamperes; R_1 and R_2 are the resistances of the first and second filter chokes; and E_r is the drop between rectifier plate and cathode (§ 8-2). These voltage drops are shown in Fig. 804.

At no load I_L is zero, hence the no-load voltage may be calculated on the basis of bleeder current only. The voltage regulation may be determined from the no-load and full-load voltages (§ 8-1).

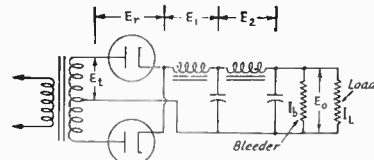


Fig. 804 — Voltage drops in the power-supply circuit.

Ratings of components — Because of better voltage regulation, filter condensers are subjected to smaller variations in d.e. voltage than in the condenser-input filter (§ 8-5). However, it is advisable to use condensers rated for the peak transformer voltage in case the bleeder resistor should burn out when there is no external load on the power supply, since the voltage then will rise to the same maximum value as with a condenser-input filter.

The input choke may be of the swinging type, the required no-load and full-load inductance values being calculated as described above. The second choke (*smoothing choke*) should have constant inductance with varying d.e. load currents. Values of 10 to 20 henrys ordinarily are used. Since chokes usually are placed in the positive leads, the negative being grounded, the windings should be insulated from the core to withstand the full d.e. output voltage of the supply.

§ 8-7 The Plate Transformer

Output voltage — The output voltage of the plate transformer depends upon the required d.e. load voltage and the type of rectifier circuit. With condenser-input filters, the r.m.s. secondary voltage usually is made equal to or slightly more than the d.e. output voltage, allowing for voltage drops in the rectifier tubes and filter chokes as well as in the transformer itself. The full-wave center-tap rectifier requires a transformer giving this voltage each side of the secondary center-tap (§ 8-3).

With a choke-input filter, the required r.m.s. secondary voltage (each side of center-tap for a center-tap rectifier) can be calculated by the equation:

$$E_t = 1.1 \left[E_o + \frac{I(R_1 + R_2)}{1000} + E_r \right]$$

where E_o is the required d.e. output voltage, I is the load current (including bleeder current) in milliamperes, R_1 and R_2 are the resistances of the filter chokes, and E_r is the voltage drop in the rectifier. E_t is the full-load r.m.s. (§ 2-7) secondary voltage; the open-circuit voltage usually will be 5 to 10 per cent higher.

Volt-ampere rating — The volt-ampere rating (§ 2-8) of the transformer depends upon the type of filter (condenser or choke input).

With a condenser-input filter the heating effect in the secondary is higher because of the high ratio of peak to average current, consequently the volt-amperes consumed by the transformer may be several times the watts delivered to the load. With a choke-input filter, provided the input choke has at least the critical inductance (§ 8-6), the secondary volt-amperes can be calculated quite closely by the equation:

$$\text{Sec. V.A.} = 0.00075 EI$$

where E is the total r.m.s. voltage of the secondary (between the outside ends in the case of a center-tapped winding) and I is the d.c. output current in milliamperes (load current plus bleeder current). The primary volt-amperes will be 10 to 20 per cent higher because of transformer losses.

8-8 Voltage Stabilization

Gaseous regulator tubes — There is frequent need for maintaining the voltage applied to a low-voltage low-current circuit (such as the oscillator in a superhet receiver or the frequency-controlling oscillator in a transmitter) at a practically constant value, regardless of the voltage regulation of the power supply or variations in load current. In such applications, gaseous regulator tubes (VR105-30, VR150-30, etc.) can be used to good advantage. The voltage drop across such tubes is constant over a moderately wide current range. The first number in the tube designation indicates the terminal voltage, the second the maximum permissible tube current.

The fundamental circuit for a gaseous regulator is shown in Fig. 805-A. The tube is connected in series with a limiting resistor, R_1 , across a source of voltage which must be higher than the starting voltage, or voltage required for ionization of the gas in the tube. The starting voltage is about 30 per cent higher than the operating voltage. The load is connected in parallel with the tube. For stable operation, a minimum tube current of 5 to 10 ma. is required. The maximum permissible current with most types is 30 ma.; consequently, the load current cannot exceed 20 to 25 ma. if the voltage is to be stabilized over a range from zero to maximum load current.

The value of the limiting resistor must lie between that which just permits minimum tube current to flow and that which just passes the maximum permissible tube current when there is no load current. The latter value is generally used. It is given by the equation:

$$R = \frac{1000 (E_s - E_r)}{I}$$

where R is the limiting resistance in ohms, E_s is the voltage of the source across which the tube and resistor are connected, E_r is the rated voltage drop across the regulator tube, and I is the maximum tube current in milliamperes (usually 30 ma.).

Fig. 805-B shows how two tubes may be

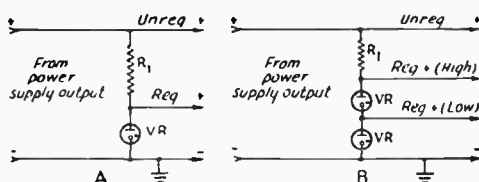


Fig. 805 — Voltage-stabilizing circuits using VR tubes.

used in series to give a higher regulated voltage than is obtainable with one, and also to give two values of regulated voltage. The limiting resistor may be calculated as above, using the sum of the voltage drops across the two tubes for E_r . Since the upper tube must carry more current than the lower, the load connected to the low-voltage tap must take small current. The total current taken by the loads on both the high and low taps should not exceed 20 to 25 milliamperes.

Voltage regulation of the order of 1 per cent can be obtained with circuits of this type.

Electronic voltage regulation — A voltage regulator circuit suitable for higher voltages and currents than the gaseous tubes, and also having the feature that the output voltage can be varied over a rather wide range, is shown in Fig. 806. A high-gain voltage amplifier tube (§ 3-3), usually a sharp cut-off pentode (§ 3-5) is connected in such a way that a small change in the output voltage of the power supply causes a change in grid bias, and thereby a corresponding change in plate current. Its plate current flows through a resistor (R_5), the voltage drop across which is used to bias a second tube — the “regulator” tube — whose plate-cathode circuit is connected in series with the load circuit. The regulator tube therefore functions as an automatically variable series resistor. Should the output voltage increase slightly the bias on the control tube will become more positive, causing the plate current of the control tube to increase and the drop across R_5 to increase correspondingly. The bias on the regulator tube therefore becomes more negative and the effective resistance of the regulator tube increases, causing the terminal voltage to drop. A decrease in output voltage causes the reverse action. The time lag in the action of the system is negligible, and with proper circuit constants the output voltage can be held within a fraction of a per cent throughout the useful range of load currents and over a wide range of supply voltages.

An essential in this system is the use of a constant-voltage bias source for the control tube. The voltage change which appears at the grid of the tube is the difference between a fixed negative bias and a positive voltage which is taken from the voltage divider across the output. To get the most effective control, the negative bias must not vary with plate current. The most satisfactory type of bias is a dry battery of 45 to 90 volts, but a gaseous regulator tube (VR75-30) or a neon bulb of the type without a resistor in the base may be used

instead. If the gas tube or neon bulb is used, a negative-resistance type of oscillation (§ 3-7) may take place at audio frequencies or higher, in which case a condenser of 0.1 μ fd. or more should be connected across the tube. A similar condenser between the control-tube grid and cathode also is frequently helpful in this respect.

The variable resistor, R_3 , is used to adjust the bias on the control tube to the proper operating value. It also serves as an output voltage control, setting the value of regulated voltage within the existing operating limits.

The maximum output voltage obtainable is equal to the power-supply voltage minus the minimum drop through the regulator tube. This drop is of the order of 50 volts with the tubes ordinarily used. The maximum current also is limited by the regulator tube; 100 milliamperes is a safe value for the 2A3. Two or more regulator tubes may be connected in parallel to increase the current-carrying capacity, with no change in the circuit.

§ 8-9 Bias Supplies

Requirements — A bias supply is not called upon to deliver current to a load circuit, but simply to furnish a fixed grid voltage to set the operating point of a tube (§ 3-3). However, in most applications it is nevertheless true that current flows through the bias supply, because such supplies are used chiefly in connection with power amplifiers of the Class-B and Class-C type, where grid-current flow is a feature of operation (§ 3-4). In circuit design a bias supply resembles the rectified-a.c. plate supply (§ 8-1), having a transformer-rectifier-filter system employing similar circuits. Bias supplies may be classified in two types, those furnishing only *protective bias*, intended to prevent excessive plate current flow in a power tube in case of loss of grid leak bias (§ 3-6) from excitation failure, and those which furnish the actual *operating bias* for the tubes. In the former type, voltage regulation (§ 8-1) is relatively unimportant; in the latter it may be of considerable importance.

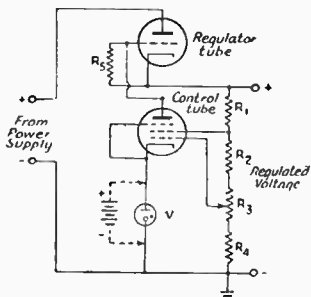


Fig. 806 — Electronic voltage regulator. The regulator tube is ordinarily a 2A3 or a number of them in parallel, the control tube a 6SJ7 or similar type. The filament transformer for the regulator tube must be insulated for the plate voltage, and cannot supply current to other tubes when a filament-type regulator tube is used. Typical values: R_1 , 10,000 ohms; R_2 , 25,000 ohms; R_3 , 10,000-ohm potentiometer; R_4 , 5000 ohms; R_5 , 0.5 megohm.

In general, a bias supply should have well-filtered d.c. output, especially if it furnishes the operating bias for the stage, since ripple voltage may modulate the signal on the grid of the amplifier tube (§ 5-1). Condenser-input filters are generally used, since the regulation of the supply is not a function of the filter. The constants given in § 8-5 are applicable.

Voltage regulation — A bias supply must always have a bleeder resistance (§ 8-4) connected across its output terminals, to provide a d.c. path from grid to cathode of the tube being biased. Although the grid circuit takes no current from the supply, grid current flows through the bleeder resistor and the voltage across the resistor therefore varies with grid current. This variation in voltage is practically independent of the bias-supply design unless special voltage-regulating means are used.

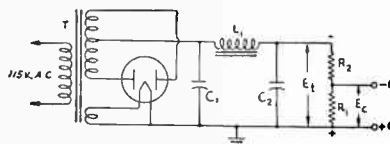


Fig. 807 — Supply for furnishing protective bias to a power amplifier. The transformer, T , should furnish peak voltage at least equal to the protective bias required.

Protective bias — This type of bias supply is designed to give an output voltage sufficient to bias the tube to which it is applied at or near the plate-current cut-off point (§ 3-2). A typical circuit is given in Fig. 807. The resistance, R_1 , is the grid-leak resistor (§ 3-6) for the amplifier tube with which the supply is used, and the normal operating bias is developed by the flow of grid current through this resistor. R_2 is connected in series with R_1 across the output of the supply, to reduce the voltage across R_1 , when there is no grid-current flow, to the cut-off value for the tube being biased. The value of R_2 is given by the formula:

$$R_2 = \frac{E_t - E_c}{E_c} \times R_1$$

where E_t is the output voltage of the supply with R_2 and R_1 in series as a load, E_c is the cut-off bias, and R_1 is as described above.


When such a supply is used with a Class-C amplifier, the voltage across R_1 from grid-current flow will normally be higher than that from the bias supply itself, since the latter is adjusted to cut-off while the operating bias will be twice cut-off or higher (§ 3-4). In some cases the grid-leak voltage may even exceed the peak output voltage of the transformer (1.41 times half the total secondary voltage, in the circuit shown). The filter condensers in such a bias supply must, therefore, be rated to stand the maximum operating bias voltage on the Class-C amplifier, if this voltage exceeds the nominal output voltage of the supply.

Voltage stabilization — When the bias supply furnishes operating rather than simply protective bias, the value of bias voltage

should be as constant as possible even when the grid current of the biased tube varies. A simple method of improving bias voltage regulation is to make the bleeder resistance low enough so that the current through it from the supply is several times the maximum grid current to be expected. By this means, the percentage variation in current is reduced. This method requires, however, that a considerable amount of power be dissipated in the bleeder, which in turn calls for a relatively large power transformer and filter choke.

Bias-voltage variation may also be reduced by means of a regulator tube, as shown in Fig. 808. The regulator tube usually is a triode having a plate-current rating adequate to carry the expected grid current. It is cathode-biased

Fig. 808 — Automatic voltage regulator for bias supplies. For best operation the tube used should be one having high mutual conductance (§3-2).

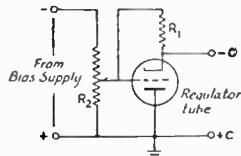


(§3-6) by the resistor, R_1 , which is of the order of several hundred thousand ohms or a few megohms, so that with no grid current the tube is biased practically to cut-off. Because of this high resistance, the grid current will flow through the plate resistance of the regulator tube, which is comparatively low, rather than through R_1 and R_2 ; hence the voltage from the supply, across R_1 and the cathode-plate circuit of the regulator tube in series, can be considered constant. The bias voltage is equal to the voltage across the tube alone. When grid current flows, the voltage across the tube will tend to increase; hence the drop across R_1 decreases, lowering the bias on the regulator and reducing its plate resistance. This, in turn, reduces the tube voltage drop, and the bias voltage tends to remain constant over a fairly wide range of grid current values.

At low bias voltages it may be necessary to use a number of tubes in parallel to get sufficient variation of plate resistance for good regulating action. The bias supply must furnish the required bias voltage plus the voltage required to bias the regulator tube to cut-off, considering the output bias voltage as the plate voltage applied to the regulator. The current taken from the bias supply is negligible. R_2 may be tapped to provide a range of bias voltages to meet different tube requirements.

Multistage bias supplies — Where several power amplifier tubes are to be biased from a single supply, the various bias circuits must be isolated by some means. If the grid currents of all stages should flow through a single bleeder resistor, a variation in grid current in one stage would change the bias on all, a condition which would interfere with effective adjustment and operation of the transmitter.

When protective bias is to be furnished several stages, the circuit arrangement of Fig.

Fig. 809 — Isolating circuit for multiple bias supply.

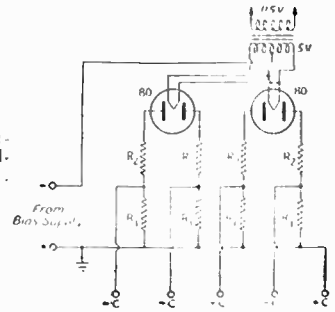

809, using rectifier tubes to isolate the individual grid-leaks of the various stages, may be employed. In the diagram, two type 80 rectifiers are used to furnish bias to four stages. Each pair of resistors (R_1R_2) constitutes a separate bleeder across the bias supply. R_1 is the grid-leak for the biased stage; R_2 is a dropping resistor to adjust the voltage across R_1 to the cut-off value (without grid-current flow) for the biased tube. The values of R_1 and R_2 may be calculated as described in the paragraph on protective bias. In this case, the bias supply should be designed to have inherently good voltage regulation; i.e., a choke-input filter with appropriate filter and bleeder constants (§8-6) should be used, the bleeder being separate from those associated with the rectifier tubes. When the voltage across R_1R_2 rises because of grid-current flow through R_1 , the load on the supply will vary (hence the necessity for good voltage regulation in the supply), but there is no interaction of grid currents in the separate bleeders because the rectifiers can pass current only in one direction.

When a single supply is to furnish operating bias for several stages, a separate regulator-tube circuit (Fig. 808) may be used for each one. Individual voltages for the various stages can be obtained by appropriate taps on R_2 .

Well-regulated bias for several stages may be obtained by the use of gaseous regulator tubes, when the voltage and current ratings of the tubes permit their use. This is shown in Fig. 810. A single tube or two or more in series can be used to give the desired bias-voltage drop; the bias supply voltage must be high enough to provide starting voltage for the tubes in series. R_1 is the protective resistance (§8-8); its value should be calculated for minimum stable tube current. The maximum grid current that can be handled is 20 to 25 milliamperes with available regulator tubes.

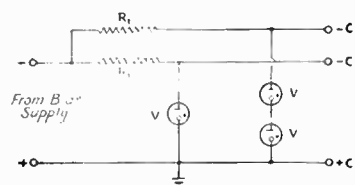


Fig. 810 — Use of VR tubes to stabilize bias voltage.

8-10 Miscellaneous Power-Supply Circuits

Voltage dividers—A voltage divider is a resistor connected across a source of voltage and tapped at appropriate points (§ 2-6). Since the voltage at any tap depends upon the current drawn from the tap, the voltage regulation (§ 8-1) is inherently poor. Hence, a voltage divider is best suited to applications where the currents drawn are constant, or where separate voltage-regulating circuits (§ 8-8) are used to compensate for voltage variations at the taps.


A typical voltage-divider arrangement is shown in Fig. 811. The terminal voltage is E , and two taps are provided to give lower voltages, E_1 and E_2 , at currents I_1 and I_2 respectively. The smaller the resistance between taps in proportion to the total resistance, the smaller the voltage between the taps. For convenience, the voltage divider in the figure is considered to be made up of separate resistances, R_1 , R_2 , R_3 , between taps. R_1 carries only the bleeder current, I_b . R_2 carries I_1 in addition to I_b ; R_3 carries I_2 , I_1 and I_b . To calculate the resistances required, a bleeder current,

Fig. 811—Typical voltage-divider circuit.

$$R_1 = \frac{E_1}{I_b}$$

$$R_2 = \frac{E_2 - E_1}{I_b + I_1}$$
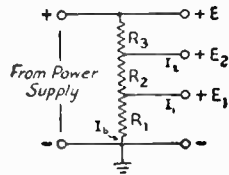
$$R_3 = \frac{E - E_2}{I_b + I_1 + I_2}$$



I_b , must be assumed; generally it is low compared to the total load current (10 per cent or so). Then the required values can be calculated as shown below, I being in amperes.

The method may be extended to any desired number of taps, each resistance section being calculated by Ohm's Law (§ 2-6) using the voltage drop across it and the total current through it. The power dissipated by each section may be calculated by multiplying I and E .

Transformerless plate supplies—The line voltage is rectified directly, without a step-up power transformer, for certain applications (such as some types of receivers) where the low voltage so obtained is satisfactory. A simple power supply of this variety, often called the "a.c.-d.c." type, is shown in Fig. 812. Rectifier tubes for this purpose have heaters operating at relatively high voltages (12.6, 25, 35, 45, 50, 70 or 115 volts), which can be connected across the a.c. line in series with other tube filaments and/or a resistor, R , of suitable value to limit the current to the rated value for the tubes.

The half-wave circuit shown has a fundamental ripple frequency equal to the line frequency (§ 8-4) and hence requires more inductance and capacity in the filter for a given ripple percentage (§ 8-5) than the full-wave rectifier. A condenser-input filter generally is used. The input condenser should be at least

16 μ f., and preferably 32 or 40 μ f., to keep the output voltage high and to improve voltage regulation. Frequently a second filter section (§ 8-5) is sufficient to provide smoothing.

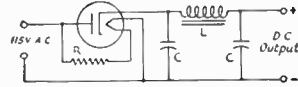


Fig. 812—Transformerless plate supply with half-wave rectifier. Other filaments are connected in series with R .

No ground connection can be used on the power supply unless the grounded side of the power line is connected to the grounded side of the supply. Receivers using an a.c.-d.c. supply usually are grounded through a low capacity (0.05 μ f.) condenser, to avoid short-circuiting the line should the line plug be inserted in the socket the wrong way.

Voltage multiplier circuits—Transformerless voltage multiplier circuits make it possible to obtain d.c. voltages higher than the line voltage without using step-up transformers. By alternately charging two or more condensers to the peak line voltage and allowing them to discharge in series, the total output voltage becomes the sum of the voltages appearing across the individual condensers. The required switching operation is performed automatically by diode rectifier tubes associated with the condensers.

A half-wave voltage doubler is shown in Fig. 813-A. In this circuit when the plate of the lower diode is positive the tube passes current, charging C_1 to a voltage equal to the peak line voltage less the tube drop. When the line polarity reverses at the end of the half cycle the voltage resulting from the charge in C_1 is added to the line voltage, the upper diode meanwhile similarly charging C_2 . C_2 , however, does not receive its full charge because it be-

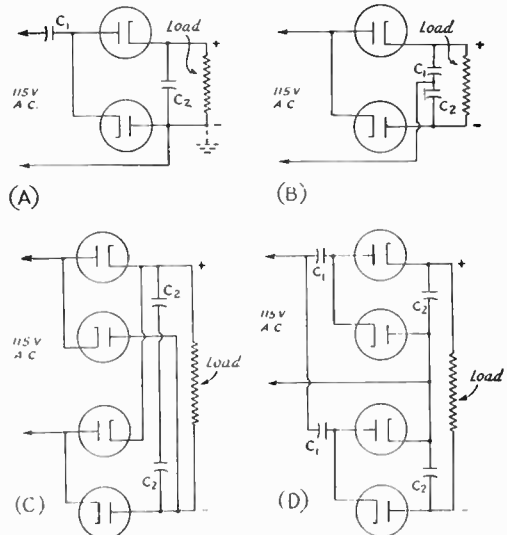


Fig. 813—Voltage multiplier circuits. A, half-wave voltage doubler. B, full-wave doubler. C, tripler. D, quadrupler. Dual diode rectifier tubes may be used.

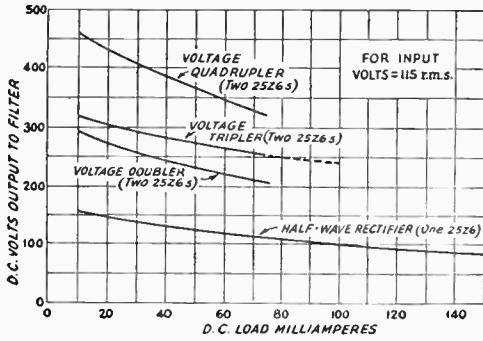


Fig. 814 — Curves showing the d.c. output voltage and the regulation under load for voltage-multiplier circuits.

gins discharging into the load resistance as soon as the upper diode becomes conductive. For this reason, the output is somewhat less than twice the line peak voltage. As with any half-wave rectifier, the ripple frequency corresponds to the line frequency.

The full-wave voltage doubler at B is more popular than the half-wave type. One diode charges C_1 when the polarity between its plate and cathode is positive while the other section charges C_2 when the line polarity reverses. Thus each condenser is charged separately to the same d.c. voltage, and the two discharge in series into the load circuit. The ripple frequency with the full-wave doubler is twice the line frequency (§ 8-1). The voltage regulation is inherently poor and depends critically upon the capacities of C_1 and C_2 , being better as these capacities are made larger. A typical supply with 16 μ fd. at C_1 and C_2 will have an output voltage of approximately 300 at light loads, as shown in Fig. 814.

The voltage tripler in Fig. 813-C' comprises four diodes in a full-wave doubler and full-wave rectifier combination. The ripple frequency is that of the line as in a half-wave circuit, because of the unbalanced arrangement, but the output to the first filter condenser is very nearly three times the line voltage, and the regulation is better than in other voltage multiplier arrangements, as shown in Fig. 811.

Fig. 813-D is a voltage quadrupler with two half-wave doublers connected in series, discharging the sum of the accumulated voltages in the associated condensers into the filter input. The quadrupler is by no means the ultimate limit in voltage multiplication. Practical power supplies have been built using up to twelve doubler stages in series.

In the circuits of Fig. 813, C_2 should have a working voltage rating of 350 volts and C_1 of 250 volts for a 115-volt line. Their capacities should be at least 16 μ fd. each. Subsequent filter condensers must, however, withstand the peak total output voltage — 450 volts in the case of the tripler and 600 for the quadrupler.

No direct ground can be used on any of these supplies or on associated equipment. If an r.f. ground is made through a condenser the ca-

capacity should be small (0.05 μ fd.), since it is in shunt from plate to cathode of one rectifier.

Duplex plate supplies — In some cases it may be advantageous economically to obtain two plate-supply voltages from a single power supply, making one or more of the components serve a double purpose. Circuits of this type are shown in Figs. 815 and 816.

In Fig. 815, a bridge rectifier is used to obtain the full transformer voltage, while a connection is also brought out from the center-tap to obtain a second voltage corresponding to half the total transformer secondary voltage. The sum of the currents drawn from the two taps should not exceed the d.c. ratings of the rectifier tubes and transformer. Filter values for each tap are computed separately (§ 8-6).

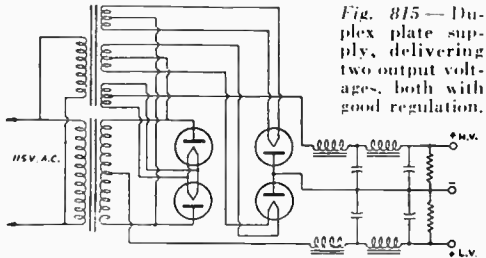


Fig. 815 — Duplex plate supply, delivering two output voltages, both with good regulation.

Fig. 816 shows how a transformer with multiple secondary taps may be used to obtain both high and low voltages simultaneously. A separate full-wave rectifier is used at each tap. The filter chokes are placed in the common negative lead, but separate filter condensers are required. The sum of the currents drawn from each tap must not exceed the transformer rating, and the chokes must be rated to carry the total load current. Each bleeder resistance should have a value in ohms 1000 times the maximum rated inductance in henrys of the swinging choke, L_1 , for best regulation (§ 8-6).

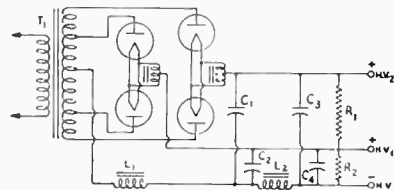


Fig. 816 — Power supply in which a single transformer and set of chokes serve for two different output voltages.

Rectifiers in parallel — Vacuum-type rectifiers may be connected in parallel (plate to plate and cathode to cathode) for higher current-carrying capacity with no circuit changes.

When mercury-vapor rectifiers are connected in parallel, slight differences in tube characteristics may make one ionize at a slightly lower voltage than the other. Since the ignition voltage is higher than the operating voltage the first tube to ionize carries the whole load, as the voltage drop is then too low to ignite the second tube. This can be prevented by connect-

ing 50- to 100-ohm resistors in series with each plate, thereby insuring that a high-enough voltage for ignition will be available.

Vibrator power supplies—The vibrator type of power supply consists of a special step-up transformer combined with a vibrating interrupter (*vibrator*). When the unit is connected to a storage battery, plate power is obtained by passing current from the battery through the primary of the transformer. The circuit is made and reversed rapidly by the vibrator contacts, interrupting the current at regular intervals to give a changing magnetic field which induces a voltage in the secondary (§ 2-5). The resulting square-wave d.c. pulses in the primary of the transformer cause an alternating voltage to be developed in the secondary. This high-voltage a.c. in turn is rectified, either by a vacuum-tube rectifier or by an additional synchronized pair of vibrator contacts. The rectified output is pulsating d.c., which may be filtered by ordinary means (§ 8-5). The smoothing filter can be a single-section affair, but the filter output capacity should be fairly large — 16 to 32 μfd .

Fig. 817 shows the two types of circuits. At A is shown the *nonsynchronous* type of vibrator. When the battery is disconnected the reed is midway between the two contacts, touching neither. On closing the battery circuit the magnet coil pulls the reed into contact with one contact point, causing current to flow through the lower half of the transformer primary winding. Simultaneously, the magnet coil is short-circuited, deenergizing it, and the reed swings back. Inertia carries the reed into contact with the upper point, causing current to flow through the upper half of the transformer primary. The magnet coil again is energized, and the cycle repeats itself.

The synchronous circuit of Fig. 817-B is provided with an extra pair of contacts which rectify the secondary output of the transformer, thus eliminating the need for a separate rectifier tube. The secondary center-tap furnishes the positive output terminal when the relative polarities of primary and secondary windings are correct. The proper connections may be determined by experiment.

The buffer condenser, C_2 , across the transformer secondary absorbs the surges which occur on breaking the current, when the magnetic field collapses practically instantaneously and hence causes very high voltages to be induced in the secondary (§ 2-5). Without this condenser excessive sparking occurs at the vibrator contacts, shortening the vibrator life. Correct values usually lie between 0.005 and 0.03 μfd , and for 250–300-volt supplies the condenser should be rated at 1500 to 2000 volts d.c. The exact capacity is critical, and should be determined experimentally. The optimum value is that which results in least battery current for a given rectified d.c. output from the supply. In practice the value can be determined by observing the degree of vibrator

sparking as the capacity is changed. When the system is operating properly there should be practically no sparking at the vibrator contacts. A 5000-ohm resistor in series with C_2 will limit the secondary current to a safe value should the condenser fail.

A more exact check on the operation can be secured with an oscilloscope having a linear sweep circuit which can be synchronized with the vibrator. The vertical plates should be connected across the outside ends of the transformer primary winding to show the input voltage waveshape. Fig. 818-C shows an idealized trace of the optimum waveform when the buffer capacity is adjusted to give proper operation throughout the life of the vibrator. The horizontal lines in the trace represent the voltage during the time the vibrator contacts are closed, which should be approximately 90 per cent of the total time. When the contacts are open the trace should be partly tilted and partly vertical, the tilted part being 60 per cent of the total connecting trace. The oscilloscope will show readily the effect of the buffer capacity on the percentage of tilt. In actual patterns the horizontal sections are likely to droop somewhat because of the resistance drop in the battery leads as the current builds up through the primary inductance (Fig. 818-D).

Sparking at the vibrator contacts causes r.f. interference ("hash," which can be distinguished from hum by its harsh, sharper pitch) when used with a receiver. To minimize this, r.f. filters are incorporated, consisting of RFC_1 and C_1 in the battery circuit and RFC_2 with C_3 in the d.c. output circuit. C_1 is usually from 0.5 to 1 μfd ., a 50-volt rating being adequate. RFC_1 consists of about 50 turns of No. 12 or No. 14 wound to about half-inch diameter, large wire being required to carry the rather heavy battery current without undue loss of voltage. A choke of these specifications should

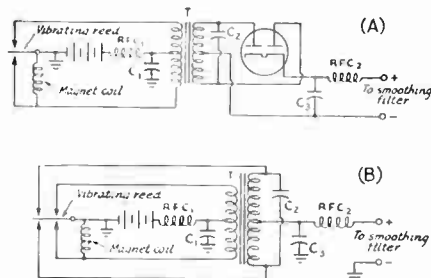


Fig. 817—Basic types of vibrator power-supply circuits.

be adequate, but if there is persistent trouble with hash it may be beneficial to experiment with other sizes. Bank-wound chokes are more compact and give higher inductance for a given resistance. In the secondary filter, C_3 may be of the order of 0.01 to 0.1 μfd ., and RFC_2 a 2.5-millihenry r.f. choke of ordinary design.

A 100- μfd . mica condenser, connected from the positive output lead to the "hot" side

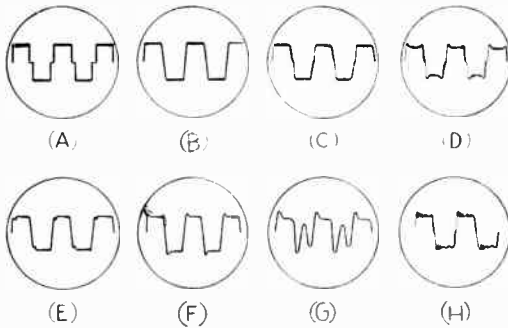


Fig. 818 — Characteristic vibrator waveforms as viewed on the oscilloscope. A, ideal theoretical trace for resistive load; current flow stops instantly when vibrator contacts open and resumes approximately 1 microsecond later (for standard 115-cycle vibration frequency) after interrupter arm moves across for the next half-cycle. B, ideal practical waveform for inductive load (transformer primary) with correct buffer capacity. C, practical approximation of B for loaded nonsynchronous vibrator. D, satisfactory practical trace for synchronous (self-rectifying) vibrator under load; the peaks result from voltage drop in the primary when the secondary load is connected, not from faulty operation.

Faulty operation is indicated in traces E through H: E, effect of insufficient buffering capacity (not to be mistaken for "bouncing" of contacts). The opposite condition — excessive buffering capacity — is indicated by slow build-up with rounded corners, especially on "open." F, overclosure caused by too-small buffer condenser (same condition as in E) with vibrator unloaded. G, "skipping" of worn-out or misadjusted vibrator, with interrupter making poor contact on one side. H, "bouncing" resulting from worn-out contacts or sluggish reed. G and H usually call for replacement of the vibrator.

of the "A" battery, may be helpful in reducing hash in certain power supplies. A trial is necessary to see whether or not it is required. It should be mounted right at the output socket.


Equally as important as the hash filter is thorough shielding of the power supply and its connecting leads, since even a small piece of wire or metal will radiate enough r.f. to cause interference in a sensitive receiver.

Testing in connection with hash elimination should be carried out with the supply operating a receiver. Since the interference usually is picked up on the receiving antenna leads by radiation from the supply itself and from the battery leads, it is advisable to keep the supply and battery as far from the receiver as the connecting cables will permit. Three or four feet should be ample. The microphone cord likewise should be kept away from the supply and leads.

The power supply should be built on a metal chassis, with all unshielded parts underneath. A bottom plate to complete the shielding is advisable. The transformer case, vibrator cover and the metal shell of the tube all should be grounded to the chassis. If a glass tube is used it should be enclosed in a tube shield. The battery leads should be evenly twisted, since these leads are more likely to radiate hash than any other part of a well-shielded supply. Experimenting with different values in the hash filters should come *after* radiation from the battery leads has been reduced to a minimum. Shielding the leads is not particularly helpful.

Line-voltage adjustment — In some localities the line voltage may vary considerably from the nominal 115 volts as the load on the power system changes. Since it is desirable to operate tube equipment, particularly filaments and heaters, at constant voltage for maximum life, a means of adjusting the line voltage to the rated value is desirable. This can be accomplished by the circuit shown in Fig. 819, utilizing a step-down transformer with a tapped secondary connected as an autotransformer (§ 2-9). The secondary preferably should be tapped in steps of two or three volts, and should have sufficient total voltage to compensate for the widest variations encountered. Depending upon the end of the secondary to which the line is connected, the voltage to the load can be made either higher or lower than the line voltage. A secondary winding capable of carrying five amperes will serve for loads up to 500 volt-amperes on a 115-volt line.

Fig. 819 — Line-voltage compensation by a tapped step-down auto-transformer.

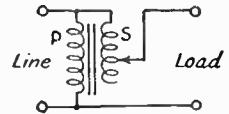

§ 8-11 — Emergency Power Supply

Dry batteries — Dry-cell batteries are ideal for emergency receiver and low-power transmitter supplies because they provide steady, pure, direct current. Their disadvantages are weight, high cost, and limited current capability. In addition, they will lose their power even when not in use if allowed to stand idle for periods of a year or more. This makes them uneconomical if not used more or less continuously.

Table I in Chapter Eighteen gives service life of representative types of batteries for various current drains, based on intermittent service simulating typical operation. The continuous-service life will be somewhat greater at very low current drains and from one-half to two-thirds the intermittent life at higher drains.

The secret of long battery life at normal current drains lies in intermittent operation. The duration of "on" periods should be reduced to a minimum. The more frequent the rests given a dry-cell battery, the longer it will last. As an example, one standard type will last 50 per cent longer if it is operated for periods of one minute, with five-minute rest intervals, in 24-hour intermittent operation than if it is operated continuously for four hours per day, although the actual energy consumption in the 24-hour period is the same in both cases.

Storage batteries — The most universally acceptable self-contained power source is the storage battery. It has high initial capacity and can be recharged, so that its effective life is practically indefinite. It can be used to provide filament or heater power directly, and plate power through associated devices such as vibrator-transformers, dynamotors and generotors, and a.c. converters. For emergency

work a storage battery is a particularly convenient power source, since such batteries are universally available. In a serious emergency it is possible to obtain 6-volt storage batteries so long as there are automobiles to borrow them from, and for this reason the 6-volt storage battery makes an excellent unit around which to design a low-powered emergency station.

For maximum efficiency and usefulness the power drain on the storage battery should not exceed 15 or 20 amperes from the ordinary 100- or 120-ampere-hour 6-volt battery. Heavy connecting leads should be used to minimize the voltage drop; similarly, heavy-duty low-resistance switches are required.

Vibrator power supplies — For portable or mobile work, the most common source of power for both filaments and plates is the 6-volt automobile-type storage battery. Filaments may be heated directly from the battery, while plate power is obtained by passing current from the battery through the primary of a suitable transformer, interrupting it at regular intervals and rectifying the secondary output (§ 2-5) providing outputs as high as 400 volts at 200 ma. The high-voltage filter circuit usually is identical with that of an equivalent power source operating from the a.c. line (§ 8-5). Noise suppression filters, serving to minimize r.f. interference caused by the vibrator, are incorporated in manufactured units.

Although vibrator supplies are ordinarily used with 6-volt tubes, their use with 2-volt tubes is quite possible provided additional filament filtration is incorporated. This filter may consist of a small low-resistance iron-core filter choke or the voice-coil winding of a speaker transformer. The field coil of a loudspeaker designed to operate on 4 volts at the total filament current of the receiver may be used. The filaments are then connected in parallel, as usual, and placed in series with this winding across the 6-volt battery. In both 6- and 2-volt receivers, "hash" can be reduced by heavily by-passing the battery at the vibrator supply terminals, using fixed condensers of 0.25 to 1 μ fd. capacity or more, and by including an r.f. choke of heavy wire in the battery lead near the condenser. Noise will be minimized if a single ground, consisting of a short, heavy copper strap, is used. Thorough shielding of the vibrator also will contribute to the noise reduction.

Table II in Chapter Eighteen lists standard commercial vibrator supplies suitable for use as emergency or portable power sources. Those units which include a hum filter are indicated. The vibrator supplies used with automobile receivers are satisfactory for receiver applications and for use with transmitters where the power requirements are small.

The efficiency of vibrator packs runs between about 60 to 75 per cent.

Dynamotors and genmotors — A dynamotor is a double-armature high-voltage generator, the additional winding serving as a driving motor. Dynamotors usually are op-

erated from 6-, 12- or 32-volt storage batteries, and deliver from 300 to 1000 volts or more.

The genmotor is a refinement of the dynamotor, designed especially for automobile receiver, sound truck and similar applications. It has good regulation and efficiency, combined with economy of operation. Standard models of genmotors have ratings ranging from 135 volts at 30 ma. to 300 volts at 200 ma. or 500 volts at 200 ma. (See Table III in Chapter Eighteen.) The normal efficiency averages around 50 per cent, increasing to better than 60 per cent in the higher-power units. The voltage regulation of a genmotor is comparable to that of well-designed a.c. supplies.

Successful operation of dynamotors and genmotors requires heavy, direct leads, mechanical isolation to reduce vibration, and thorough r.f. and ripple filtration. The shafts and bearings should be thoroughly "run in" before regular operation is attempted, and thereafter the tension of the bearings should be checked occasionally.

In mounting the genmotor, the support should be in the form of rubber mounting blocks, or equivalent, to prevent the transmission of vibration mechanically. The frame of the genmotor should be grounded through a heavy flexible connector. The brushes on the high-voltage end of the shaft should be by-passed with 0.002- μ fd. mica condensers to a common point on the genmotor frame, preferably to a point inside the end cover close to the brush holders. Short leads are essential. It may prove desirable to shield the entire unit, or even to remove the unit to a distance of three or four feet from the receiver.

When the genmotor is used for receiving, a filter should be used similar to that described for vibrator supplies. A 0.01- μ fd. 600-volt (d.c.) paper condenser should be connected in shunt across the output of the genmotor, followed by a 2.5-mh. r.f. choke in the positive high-voltage lead. From this point the output should be run through a "brute force" smoothing filter using 4- to 8- μ fd. electrolytic condensers with a 15- or 30-henry choke having low d.c. resistance.

A.c.-d.c. converters — In some instances it is desirable to utilize existing equipment built for 115-volt a.c. operation. To operate such equipment with any of the power sources outlined above would require a considerable amount of rebuilding. This can be obviated by using a rotary converter capable of changing the d.c. from 6-, 12- or 32-volt batteries to 110-volt 60-cycle a.c. Such converter units are built to deliver output ranging from 40 to 300 watts.

The conversion efficiency of these units averages about 50 per cent. In appearance and operation they are similar to genmotors of equivalent rating. The over-all efficiency of the converter will be lower, however, because of losses in the a.c. rectifier-filter circuits and the necessity for converting heater as well as plate power.

Wave Propagation

9-1 Characteristics of Radio Waves

Relation to other forms of radiation —

Radio waves differ from other forms of electromagnetic radiation principally in the order of their wavelength, which ranges from approximately 30,000 meters to a small fraction of a centimeter; i.e., their frequency ranges between about 10 kc. and 1,000,000 Mc. They travel at the same velocity as light waves (about 300,000,000 meters per second in free space) and can be similarly reflected, refracted and diffracted.

The total energy in a radio wave is evenly divided between traveling electrostatic and electromagnetic fields. The lines of force of these fields are at right angles to each other in a plane perpendicular to the direction of travel, as shown in Fig. 901.

Polarization — The polarization of a radio wave is taken as the direction of the lines of force in the electrostatic field. If the plane of this field is perpendicular to the earth, the wave is said to be *vertically polarized*; if it is parallel to the earth, the wave is *horizontally polarized*. The longer waves, when traveling along the ground, usually maintain their polarization in the same plane as was generated at the antenna. The polarization of shorter waves may be altered during travel, however, and sometimes will vary quite rapidly.

Reflection — Radio waves may be reflected from any sharply defined discontinuity of suitable characteristics and dimensions encountered in the medium in which they are traveling. Any conductor (or any insulator having a dielectric constant differing from that

of the medium) offers such a discontinuity if its dimensions are at least comparable to the wavelength. The surface of the earth and the boundaries between ionospheric layers are examples of such discontinuities. Objects as small as an airplane, a tree or even a man's body will readily reflect the shorter waves.

Refraction — As in the case of light, a radio wave is bent when it moves obliquely into any medium having a different refractive index from that of the medium which it leaves. Since the velocity of propagation or travel differs in the two mediums, that part of the wave front which enters first travels faster or slower than the part which enters last, and so the wave front is turned or refracted (usually downward in the vertical plane). Refraction may take place in either the ionosphere (ionized upper atmosphere) or the troposphere (lower atmosphere).

Diffraction — When a wave grazes the edge of an object in passing, it tends to be bent around that edge. This effect, called *diffraction*, results in a diversion of part of the energy of those waves which normally follow a straight or line-of-sight path, so that they may be received at some distance below the summit of an obstruction, or around its edges.

Types of waves — According to the altitude of the paths along which they are propagated, radio waves may be classified as *ionospheric waves*, *tropospheric waves* or *ground waves*.

The ionospheric wave (sometimes called the "sky wave,") is that part of the total radiation which is directed toward the ionosphere. Depending upon variable conditions in that region, as well as upon wavelength (or frequency), the ionospheric wave may or may not be returned to earth by the effects of refraction and reflection.

The tropospheric wave is that part of the total radiation which undergoes refraction and reflection in regions of abrupt change of dielectric constant in the troposphere, such as the boundaries between air masses of differing temperature and moisture content.

The ground wave is that part of the total radiation which is directly affected by the presence of the earth and its surface features. The ground wave has two components. One is the *surface wave*, which is an earth-guided wave, and the other is the *space wave* (not to be confused with the ionospheric or "sky wave.") The space wave is itself the resultant of two components — the *direct wave* and the *ground-reflected wave*, as shown in Fig. 902.

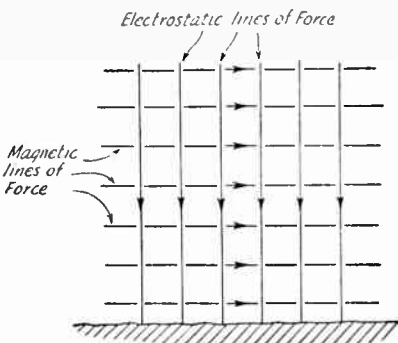


Fig. 901 — Representation of electrostatic and electromagnetic lines of force in a radio wave. Arrows indicate instantaneous directions of the fields for a wave traveling toward the reader. Reversing the direction of one set of lines would reverse the direction of travel.

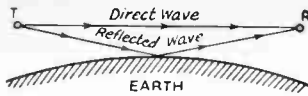


Fig. 902 — Showing how both direct and reflected waves may be received simultaneously in v.h.f. transmission.

¶ 9-2 Ionospheric Propagation

The ionosphere — Communication between distant points by means of radio waves of frequencies ranging between 3 and 30 Mc. depends principally upon the ionospheric wave. Upon leaving the transmitting antenna, this wave travels upward from the earth's surface at such an angle that it would continue out into space were its path not bent sufficiently to bring it back to earth. The medium which causes such bending is the ionosphere, a region in the upper atmosphere, above a height of about 60 miles, where free ions and electrons exist in sufficient quantity to cause a change in the refractive index. This condition is believed to be the effect of ultraviolet radiation from the sun. The ionosphere is not a single region but is composed of a series of layers of varying densities of ionization occurring at different heights. Each layer consists of a central region of relatively dense ionization which tapers off in intensity both above and below.

Refraction, absorption and reflection — For a given density of ionization, the degree of refraction becomes less as the wavelength becomes shorter (or as the frequency increases). The bending therefore is less at high than at low frequencies, and if the frequency is raised to a sufficiently high value, a point is finally reached where the refractive bending becomes too slight to bring the wave back to earth, even though it may enter the ionized layer along a path which makes a very small angle with the boundary of the ionosphere.

The greater the density of ionization, the greater the bending at any given frequency. Thus, with an increase in ionization, the minimum wavelength which can be bent sufficiently for long-distance communication is lessened and the maximum usable frequency is increased.

The wave necessarily loses some of its energy in traveling through the ionosphere, this absorption loss increasing with wavelength and also with ionization density. Unusually high ionization, especially in the lower strata of the ionosphere, may cause complete absorption of the wave energy.

In addition to refraction, reflection may take place at the lower boundary of an ionized layer if it is sharply defined; i.e., if there is an appreciable change in ionization within a relatively short interval of travel. For waves approaching the layer at or near the perpendicular, the change in ionization must take place within a difference in height comparable to a wavelength; hence, ionospheric reflection is more apt to occur at longer wavelengths (lower frequencies).

Critical frequency — When the frequency is sufficiently low, a wave sent vertically upward to the ionosphere will be bent sharply enough to cause it to return to the transmitting point. The highest frequency at which such reflection can occur, for a given state of the ionosphere, is called the *critical frequency*. Although the critical frequency may serve as an index of transmission conditions, it is not the highest useful frequency, since other waves of the same frequency which enter the ionosphere at angles smaller than 90 degrees (less than vertical) will be bent sufficiently to return to earth. The *maximum usable frequency*, for waves leaving the earth at very small angles to the horizontal, is in the vicinity of three times the critical frequency.

Besides being directly observable, the critical frequency is of more practical interest than the ionization density because it includes the effects of absorption as well as refraction.

Virtual height — Although an ionospheric layer is a region of considerable depth it is convenient to assign to it a definite height, called the *virtual height*. This is the height from which a simple reflection would give the same effect as the gradual refraction which actually takes place, as illustrated in Fig. 903. The wave traveling upward is bent back over a path having an appreciable radius of turning, and a measurable interval of time is consumed in the turning process. The virtual height is the height of a triangle formed as shown, having equal sides of a total length proportional to the time taken for the wave to travel from T to R.

Normal structure of the ionosphere — The lowest normally useful layer is called the E layer. The average height of the region of maximum ionization is about 70 miles. The ionization density is greatest around local noon; the layer is only weakly ionized at night, when it is not exposed to the sun's radiation. The air at this height is sufficiently dense so that free ions and electrons very quickly meet and recombine.

The second principal layer is the F layer, which has a height of about 175 miles at night. At this altitude the air is so thin that recombination of ions and electrons takes place very slowly, inasmuch as particles can travel relatively great distances before meeting. The ionization decreases after sundown, reaching a minimum just before sunrise. In the daytime

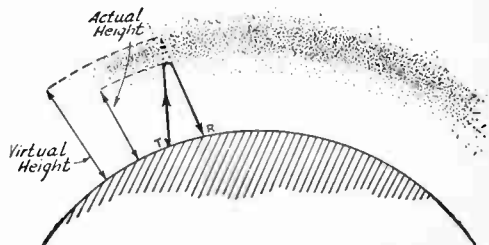


Fig. 903 — Showing bending in the ionosphere and the echo or reflection method of determining virtual height.

the F layer splits into two parts, the F_1 and F_2 layers, with average virtual heights of, respectively, 140 miles and 200 miles. These layers are most highly ionized at about local noon, and merge again at sunset into the F layer.

Cyclic variations in the ionosphere — Since ionization depends upon ultraviolet radiation, conditions in the ionosphere vary with changes in the sun's radiation. In addition to the daily variation, seasonal changes result in higher critical frequencies in the E layer in summer, averaging about 4 Mc, as against a winter average of 3 Mc. The F layer shows little variation, the critical frequency being of the order of 4 to 5 Mc, in the evening. The F_1 layer, which has a critical frequency near 5 Mc, in summer, usually disappears entirely in winter. The critical frequencies for the F_2 are highest in winter (11 to 12 Mc.) and lowest in summer (around 7 Mc.). The virtual height of the F_2 layer, which is about 185 miles in winter, averages 250 miles in summer.

Seasonal transition periods occur in spring and fall, when ionospheric conditions are found highly variable.

There are at least two other regular cycles in ionization. One such cyclic period covers 28 days, which corresponds with the period of the sun's rotation. For a short time in each 28-day cycle, transmission conditions reach a peak. Usually this peak is followed by a fairly rapid drop to a lower level, and then a slow building up to the next peak. The 28-day cycle is particularly evident in the 14- and 28-Mc. amateur bands.

The longest cycle yet observed covers about 11 years, corresponding to a similar cycle of sunspot activity. The effect of this cycle is to shift upward or downward the values of the critical frequencies for F_1 and F_2 -layer transmission. The critical frequencies are highest during sunspot maxima and lowest during sunspot minima. It is during the period of minimum sunspot activity when long-distance transmissions occur on the lower frequencies. At such times the 28-Mc. band is seldom useful for DX work, while the 14-Mc. band performs well in the daytime but is not ordinarily useful at night. The most recent sunspot maximum is considered to have occurred in 1938.

Magnetic storms and other disturbances — Unusual disturbances in the earth's magnetic field (magnetic storms) usually are ac-

companied by disturbances in the ionosphere, when the layers apparently break up and expand. There is usually also an increase in absorption during such a period. Radio transmission is poor and there is a drop in critical frequencies so that lower frequencies must be used for communication. A storm may last for several days.

Unusually high ionization in the region of the atmosphere below the normal ionosphere may increase absorption to such an extent that sky-wave transmission becomes impossible on high frequencies. The length of such a disturbance may be several hours, with a gradual falling off of transmission conditions at the beginning and an equally gradual building up at the end of the period. *Fadeouts*, similar to the above in effect, are caused by sudden disturbances on the sun. They are characterized by very rapid ionization, with sky-wave transmission disappearing almost instantly, occur only in daylight, and do not last as long as the first type of absorption.

Magnetic storms frequently are accompanied by unusual auroral displays, creating an ionized "curtain" in the polar regions which can act as a reflector of radio waves. Auroral reflection is occasionally observed at frequencies as high as 60 Mc.

Sporadic E-layer ionization — Occasionally scattered patches or clouds of relatively dense ionization appear at heights approximately the same as that of the E layer. The effect is to raise the critical frequency to a value perhaps twice that which is returned from any of the regular layers by normal refraction. Distances of about 500 to 1250 miles may be covered at 56 Mc, if the ionized cloud is situated midway between transmitter and receiver, or is of any very considerable extent. This effect, while infrequently observed in winter, is prevalent during the late spring and early summer, with no apparent correlation of the condition with the time of day.

The presence of sporadic- E refraction on the 14- and 28-Mc. bands is indicated by an abnormally short distance between the transmitter and the point where the wave first is returned to earth as when, for example, 14-Mc. signals from a transmitter only 100 miles distant may arrive with an intensity usually associated with distances of this order on 7 and 3.5 Mc.

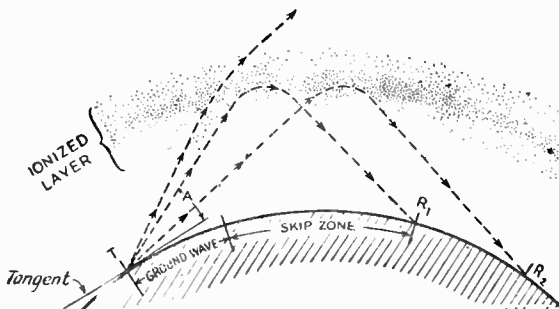


Fig. 901 — Refraction of sky waves, showing the critical wave angle and the skip zone. Waves leaving the transmitter at angles above the critical (greater than A) are not bent enough to be returned to earth. As the angle is increased, the waves return to earth at increasingly greater distances.

Wave angle—The smaller the angle at which a wave leaves the earth, the less will be the bending required in the ionosphere to bring it back and, in general, the greater the distance between the point where it leaves the earth and that at which it returns. This is shown in Fig. 904. The vertical angle which the wave makes with a tangent to the earth is called the *wave angle* or *angle of radiation*.

Skip distance—Since greater bending is required to return the wave to earth when the wave angle is high, at the higher frequencies the refraction frequently is not enough to give the required bending unless the wave angle is smaller than a certain angle called the *critical angle*. This is illustrated in Fig. 904, where waves at angles of A or less give useful signals while waves sent at higher angles penetrate the layer and are not returned. The distance between T and R_1 is, therefore, the shortest possible distance over which communication by normal ionospheric refraction can be accomplished.

The area between the end of the useful ground wave and the beginning of ionospheric wave reception is called the *skip zone*. The extent of skip zone depends upon the frequency and the state of the ionosphere, and is greater the higher the transmitting frequency and the lower the critical frequency. Skip distance depends also upon the height of the layer in which the refraction takes place, the higher layers giving longer skip distances for the same wave angle. Wave angles at the transmitting and receiving points are usually, although not always, approximately the same for any given wave path.

It is readily possible for the ionospheric wave to pass through the E layer and be refracted back to earth from the F_1 or F_2 layers. This is because the critical frequencies are higher in the latter layers, so that a signal too high in frequency to be returned by the E layer can still come back from one of the others, depending upon the time of day and the existing conditions. Depending upon the wave angle and the frequency, it is sometimes possible to carry on communication via either the E or F_1 - F_2 layers on the same frequency.

Multihop transmission—On returning to the earth the wave can be reflected upward and travel again to the ionosphere. There it may once more be refracted, and again bent back to earth. This process may be repeated several times. Multihop propagation of this nature is necessary for transmission over great distances because of the limited heights of the layers and the curvature of the earth, since at the lowest useful wave angles (of the order of a few degrees, waves at lower angles generally being absorbed rapidly at high frequencies by being in contact with the earth) the maximum one-hop distance is about 1250 miles for refraction from the E layer and around 2500 miles for the F_2 layer. However, ground losses absorb some of the energy from the wave on each re-

flection (the amount of the loss varying with the type of ground and being least for reflection from sea water). Thus, when the distance permits, it is better to have one hop rather than several, since the multiple reflections introduce losses which are higher than those caused by the ionosphere alone.

Fading—Two or more parts of the wave may follow slightly different paths in traveling to the receiving point, in which case the difference in path lengths will cause a phase difference to exist between the wave components at the receiving antenna. The field strength therefore may have any value between the numerical sum of the components (when they are all in phase) and zero (when there are only two components and they are exactly out of phase). Since the paths change from time to time, this causes a variation in signal strength called *fading*. Fading can also result from the combination of single-hop and multi-hop waves, or the combination of a ground wave with an ionospheric or tropospheric wave. Such a condition gives rise to an area of severe fading near the limiting distance of the ground wave, better reception being obtained at both shorter and longer distances where one component or the other is considerably stronger. Fading may be rapid or slow, the former type usually resulting from rapidly changing conditions in the ionosphere, the latter occurring when transmission conditions are relatively stable.

It frequently occurs that transmission conditions are different for waves of slightly different frequencies, so that in the case of voice-modulated transmission, involving side-bands differing slightly from the carrier in frequency, the carrier and various side-band components may not be propagated in the same relative amplitudes and phases they had at the transmitter. This effect, known as *selective fading*, causes severe distortion of the signal.

9-3 Tropospheric Propagation

Air masses and fronts—In the lower atmosphere wave propagation is affected by the changes in refractive index between differing air masses. A mass of air hundreds of miles in area may remain at rest over one region until it becomes affected by the surface temperature and humidity characteristic of that region. Eventually being moved on by the forces of atmospheric circulation, the mass may travel over regions quite different from its origin and retain for some time its original characteristics. When it meets a dissimilar air mass, the lighter, warmer and drier mass overruns the heavier, cold, moist mass creating a boundary between the two called a *front*. This front, which represents a discontinuity in the dielectric constant of the troposphere, serves to refract and reflect the higher-frequency radio waves in much the same manner as the ionospheric layers, but at lesser heights and more restricted angles. As a result frequencies above 50 Mc. are returned to

earth at distances considerably beyond the range of ground-wave propagation, sometimes up to 400 miles.

Temperature inversions — The temperature of the lower atmosphere normally decreases at a constant rate with increasing height. When for any reason the normal variation or *lapse rate* of approximately 3° F. per 1000 feet of elevation is altered, a *temperature inversion* is said to take place. The resulting change in the dielectric constants of the air masses affected causes reflection and refraction similar to that in the ionosphere.

Types of inversion other than the *dynamic* type described in the preceding paragraph include the *subsidence* inversion, caused by the sinking of an air mass which has been heated by compression; the *nocturnal* inversion, brought about by the rapid cooling of surface air after sunset; and the *cloud-layer* inversion, caused by the heating of air above a cloud layer by reflection of the sun's rays from the upper surface of the clouds. Refraction and reflection of v.h.f. waves are brought about also, although to a lesser degree, by the presence of sharp transitions in the water-vapor content of the atmosphere. Fig. 905 illustrates the conditions existing when the air is "normal" and when a temperature inversion is present.

9-4 Ground-Wave Propagation

Surface wave — The surface wave is continuously in contact with the surface of the earth and, in cases where the distance of transmission makes the curvature of the earth a factor, extends its range by diffraction. The surface wave is practically independent of seasonal and day and night effects at frequencies above 1500 kc.

The surface wave must be vertically polarized because the electrostatic field of a horizontally polarized wave would be short-circuited by the ground, which acts as a conductor at the frequencies for which the surface wave is of most interest.

The wave induces a current in the ground in traveling along its surface. If the ground

were a perfect conductor there would be no loss of energy, but actual ground has appreciable resistance, so that the current flow causes some energy dissipation. This loss must be supplied by the wave which is correspondingly weakened. Hence, the transmitting range depends upon the ground characteristics. Because sea water is a good conductor, the range will be greater over the ocean than over land. The losses increase with frequency, so that the surface wave is rapidly attenuated at high frequencies and above about 2 Mc. is of little importance, except in purely local communication. The range at frequencies in the vicinity of 2 Mc. is of the order of 200 miles over average land and perhaps two or three times as far over sea water, for a medium-power transmitter (500 watts or so) using a good antenna. At higher frequencies the range drops off rapidly.

Space wave — In the v.h.f. portion of the spectrum (above 30 Mc.) the bending of the waves in the normal ionosphere is so slight that the ionospheric wave (§9-2) is not ordinarily useful for communication. The range of the surface wave also is extremely limited, as stated above. Hence, normal v.h.f. transmission is by means of the space wave in which the *direct-wave* component travels directly from the transmitter to the receiver through the atmosphere along a line-of-sight path.

Part of the space wave strikes the ground between the transmitter and receiver and is reflected upward at a slight angle, as was shown in Fig. 902. The effect of this *ground-reflected wave*, which is out of phase with the direct wave, is to reduce the net field strength at the receiving point. The degree of cancellation depends upon the heights of the transmitting and receiving antennas above the point of reflection, the ground losses when reflection takes place, and the frequency — the cancellation decreasing with an increase in any of these.

The energy lost in ground absorption by a wave traveling close to the ground decreases very rapidly with its height in terms of wavelengths above the ground. A v.h.f. direct wave, therefore, can be relatively close (in physical height) to the ground without suffering the absorption effects which would occur at the same physical heights with longer wave-lengths.

Normal refraction — There is normally some change in the refractive index of the air with height above ground, its nature being such as to cause the wave to bend slightly towards the ground. Where curvature of the earth must be considered, this has the effect of lengthening the distance over which it is possible to transmit a direct wave. It is convenient to consider the effect of this "normal refraction" as equivalent to an increase in the earth's radius, in determining the antenna heights necessary to provide a clear path for the wave. The equivalent radius, taking refraction into account, is 4/3 the actual radius.

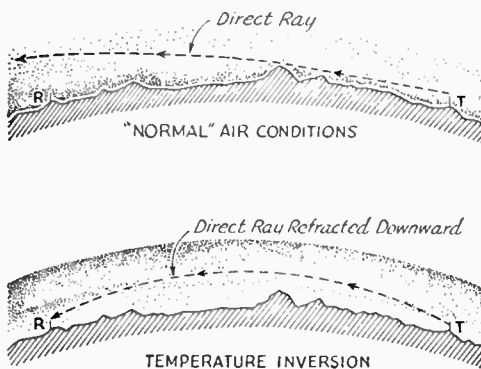


Fig. 905 — Illustrating the effect of a temperature inversion in extending the range of v.h.f. signals.

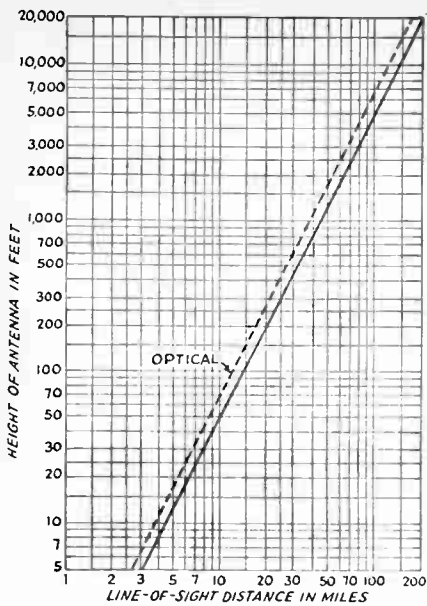


Fig. 906 — Chart for determining line-of-sight distance for v.h.f. transmission. The solid line includes effect of refraction, while the dotted line is the optical distance.

Range vs. height — Since the direct wave travels in practically a straight line, the maximum signal strength can be obtained only when there is an unobstructed atmospheric path between the transmitter and receiver. This means that antennas should be sufficiently elevated to provide such a path. On long paths the curvature of the earth, as well as the intervening terrain, must be taken into account.

The height required to provide a clear line-of-sight path over level terrain from an elevated transmitting point to a receiving point on the surface, not including the effect of refraction, is

$$h = \frac{d^2}{1.51}$$

where h is the height of the transmitting antenna in feet and d the distance in miles. Conversely, the line-of-sight distance in miles for a given height in feet is determined by

$$d = 1.23\sqrt{h}$$

Taking refraction into account, this equation becomes

$$d = 1.41\sqrt{h}$$

Fig. 906 gives the answer directly when either value is known.

When transmitter and receiver both are elevated, the maximum direct-wave distance to ground level can be determined separately for each. Adding the two distances thus obtained will give the maximum distance by which they can be separated for direct-wave communication. This is shown in Fig. 907.

9-5 Optimum Wave Angles

One of the requirements in high-frequency radio transmission is to send a wave to the ionosphere in such a way that it will have the best chance of being returned to earth. This is chiefly a matter of the angle at which the wave enters the layer, although in some cases polarization may be of importance. Furthermore, the desirable conditions may change considerably with frequency.

The desirable conditions for waves of different frequencies can be summarized as follows, in terms of the various amateur bands:

1.75 Mc. — Low-angle radiation is indicated for the longer distances. High-angle radiation may cause fading toward the limit of the ground-wave signal, because the downcoming waves add in random phase to the ground wave. Vertical polarization is to be preferred.

3.5 Mc. — Waves at all angles of radiation usually will be reflected, so that no energy is lost by high-angle radiation. However, the lower-angle waves will, in general, give the greatest distances. Polarization on this band is not of great importance.

7 Mc. — Under most conditions, angles of radiation up to about 45 degrees will be returned to earth; during the sunspot maximum still higher angles are useful. It is best to concentrate the radiation below 45 degrees. Polarization is not important, except that losses probably will be higher with vertical polarization.

14 Mc. — For long-distance transmission, most of the energy should be concentrated at angles below about 20 degrees. Higher angles are useful for comparatively short distances (300–400 miles), although 30 degrees is about the maximum useful angle. Aside from the probable higher losses with vertical polarization, the polarization may be of any type.

28 Mc. — Angles of 10 degrees or less are most useful. As in the case of 14 Mc., polarization is not important.

56 Mc. — The lowest possible angle of radiation is most useful for all types of transmission. Vertical polarization has been chiefly used for line-of-sight and lower atmosphere transmission, although horizontal polarization may be slightly better for long distances. In any event, the same polarization should be used at both transmitter and receiver.

Higher frequencies — As in the case of 56 Mc. either horizontal or vertical polarization may be used, so long as the same type is employed at both ends of the circuit.

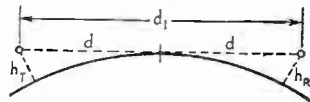


Fig. 907 — Method of determining total line-of-sight distance when both transmitter and receiver are elevated, based on Fig. 906. Since only earth curvature is taken into account in Fig. 906, irregularities in the ground between the transmitting and receiving points must be considered when computing each actual path.

Antenna Systems

10-1 Antenna Properties

Wave propagation and antenna design — For most effective transmission, the propagation characteristics of the frequency under consideration must be given due consideration in selecting the type of antenna to use. These have been discussed in Chapter Nine. On some frequencies the angle of radiation and polarization may be of relatively little importance; on others they may be all-important. On a given frequency, the particular type of antenna best suited for long-distance transmission may not be as good for shorter-range work as would a different type.

The important properties of an antenna or antenna system are its polarization, angle of radiation, impedance, and directivity.

Polarization — The polarization of a straight-wire antenna is its position with respect to the earth. That is, a vertical wire transmits vertically polarized waves and a horizontal antenna generates horizontally polarized waves (§ 9-1). The wave from an antenna in a slanting position contains both vertical and horizontal components.

Angle of radiation — The wave angle (§ 9-4) at which an antenna radiates best is determined by its polarization, height above ground, and the nature of the ground. Radiation is not all at one well-defined angle, but rather is dispersed over a more or less large angular region, depending upon the type of antenna. The angle is measured in a vertical plane with respect to a tangent to the earth at the transmitting point.

Impedance — The impedance (§ 2-8) of the antenna at any point is the ratio of voltage to current at that point. It is important in connection with feeding power to the antenna, since it constitutes the load resistance represented by the antenna. At high frequencies the antenna impedance consists chiefly of radiation resistance (§ 2-12). It is understood to be measured at a current loop (§ 2-12), unless otherwise specified.

Directivity — All antennas radiate more power in certain directions than in others. This characteristic, called *directivity*, must be considered in three dimensions, since directivity exists in the vertical plane as well as in the horizontal plane. Thus, the directivity of the antenna will affect the wave angle as well as the actual compass directions in which maximum transmission takes place.

Current — The field strength produced by an antenna is proportional to the current flow-

ing in it. When there are standing waves on an antenna, the parts of the wire carrying the higher current have the greatest radiating effect.

Power gain — The ratio of power required to produce a given field strength, with a "comparison" antenna, to the power required to produce the same field strength with a specified type of antenna is called the *power gain* of the latter antenna. The term is used in connection with antennas intentionally designed to have directivity, and the field is measured in the optimum direction of the antenna under test. The comparison antenna almost always is a half-wave antenna having the same polarization as the antenna under consideration. Power gain usually is expressed in decibels (§ 3-3).

10-2 The Half-Wave Antenna

Physical and electrical length — The fundamental form of antenna is a single wire whose length is approximately equal to half the transmitting wavelength. It is the unit from which many more complex forms of antennas are constructed. It is sometimes known as a *Hertz* or *doublet* antenna.

The length of a half wave in space is:

$$\text{Length (feet)} = \frac{492}{\text{Freq. (Mc.)}} \quad (1)$$

The actual length of a half-wave antenna will not be exactly equal to the half wave in space, but is usually about 5 per cent less because of capacitance at the ends of the wire (*end effect*). The reduction factor increases slightly as the frequency is increased. Under average conditions the following formula will give the length of a half-wave antenna to sufficient accuracy for frequencies up to 30 Mc.:

$$\begin{aligned} \text{Length of half-wave antenna (feet)} &= \\ \frac{492 \times 0.95}{\text{Freq. (Mc.)}} &= \frac{468}{\text{Freq. (Mc.)}} \end{aligned} \quad (2)$$

At 56 Mc. and higher frequencies the somewhat larger end effects cause a slightly greater reduction in length, so that, for these higher frequencies,

$$\begin{aligned} \text{Length of half-wave antenna (feet)} &= \\ \frac{492 \times 0.94}{\text{Freq. (Mc.)}} &= \frac{462}{\text{Freq. (Mc.)}} \end{aligned} \quad (3)$$

$$\text{or length (inches)} = \frac{5540}{\text{Freq. (Mc.)}} \quad (4)$$

Current and voltage distribution — When power is fed to such an antenna the current and voltage vary along its length (§ 2-12). The

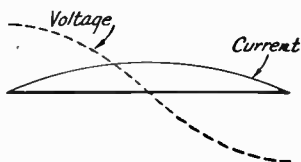


Fig. 1001 — Current and voltage distribution on a half-wave antenna. Current is maximum in center, nearly zero at ends. Voltage distribution is just the opposite.

distribution, which is practically a sine curve, is shown in Fig. 1001. The current is maximum at the center and nearly zero at the ends, while the opposite is true of the r.f. voltage. The current does not actually reach zero at the current nodes (§ 2-12), because of the end effect; similarly, the voltage is not zero at its node because of the resistance of the antenna, which consists of both the r.f. resistance of the wire (*ohmic resistance*) and the radiation resistance (§ 2-12). Usually the ohmic resistance of a half-wave antenna is small enough, in comparison with the radiation resistance, to be neglected for all practical purposes.

Impedance — The radiation resistance of a half-wave antenna in free space — that is, sufficiently removed from surrounding objects so that they do not affect the antenna's characteristics — is 73 ohms, approximately. The value under practical conditions will vary with the height of the antenna, but is commonly taken to be in the neighborhood of 70 ohms. It is pure resistance, and is measured at the center of the antenna. The impedance is minimum at the center, where it is equal to the radiation resistance, and increases toward the ends (§ 10-1). The actual value at the ends will depend on a number of factors, such as the height, the physical construction, and the position with respect to ground.

Conductor size — The impedance of the antenna also depends upon the diameter of the conductor in relation to its length. The figures above are for wires of practicable sizes. If the diameter of the conductor is made large, of the order of 1 per cent or more of the length, the capacity per unit length increases and the inductance per unit length decreases. Since the radiation resistance is affected little, if at all, by the diameter/length ratio, the decreased L/C ratio causes the Q of the antenna to decrease, so that the resonance curve becomes less sharp. Hence, the antenna is capable of working over a wide frequency range. This effect is greater as the diameter/length ratio is increased, and is a property of some importance at the very-high frequencies where the wavelength is small.

Radiation characteristics — The radiation from a half-wave antenna is not uniform in all directions but varies with the angle with respect to the axis of the wire. It is most intense in directions at right-angles to the wire and zero along the direction of the wire itself, with intermediate values at intermediate angles. This is shown by the sketch of Fig. 1002,

which represents the radiation pattern in free space. The relative intensity of radiation is proportional to the length of a line drawn from the center of the figure to the perimeter. If the antenna is vertical, as shown in the figure, then the field strength (§ 9-1) will be uniform in all horizontal directions; if the antenna is horizontal, the relative field strength will depend upon the direction of the receiving point with respect to the direction of the antenna wire.

10-3 Ground Effects

Reflection — When the antenna is near the ground the free-space pattern of Fig. 1002 is modified by reflection of radiated waves from the ground, so that the actual pattern is the resultant of the free-space pattern and ground reflections. This resultant is dependent upon the height of the antenna, its position or orientation with respect to the surface of the ground, and the electrical characteristics of the ground. The reflected waves may be in such phase relationship to the directly radiated waves that the two completely reinforce each other, or the phase relationship may be such that complete cancellation takes place. All intermediate values also are possible. Thus, the effect of a perfectly reflecting ground is such that the original free-space field strength may be multiplied by a factor which has a maximum value of 2, for complete reinforcement, and having all intermediate values to zero, for complete cancellation. Since waves are always reflected upward from the ground (assuming that the surface is fairly level), these reflections only affect the radiation pattern in the vertical plane — that is, in directions upward from the earth's surface — and not in the horizontal plane, or the usual geographical directions.

Fig. 1003 shows how the multiplying factor varies with the vertical angle for several representative heights for horizontal antennas. As the height is increased the angle at which complete reinforcement takes place is lowered, until for a height equal to one wavelength it occurs at a vertical angle of 15 degrees. At still greater heights, not shown on the chart, the first maximum will occur at still smaller angles.

When the half-wave antenna is vertical the maximum and minimum points in the curves of Fig. 1003 exchange positions, so that the nulls become maxima, and vice versa. In this

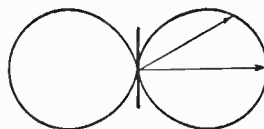


Fig. 1002 — The free-space radiation pattern of a half-wave antenna. The antenna is shown in the vertical position. This is a cross-section of the solid pattern described by the figure when rotated on its vertical axis. The "doughnut" form of the solid pattern can be more easily visualized by imagining the drawing glued to a piece of cardboard, with a short length of wire fastened on it to represent the antenna. Twirling the wire will give a visual representation of the solid radiation pattern.

case, the height is taken as the distance from ground to the center of the antenna.

Radiation angle — The vertical angle, or angle of radiation, is of primary importance, especially at the higher frequencies (§ 9-2, 9-4).

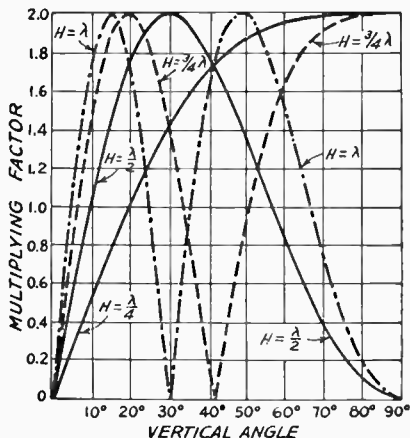


Fig. 1003 — Effect of ground on radiation of horizontal antennas at vertical angles for four antenna heights. This chart is based on perfectly conducting ground.

It is advantageous, therefore, to erect the antenna at a height which will take advantage of ground reflection in such a way as to reinforce the space radiation at the most desirable angle. Since low radiation angles usually are desirable, this generally means that the antenna should be high — at least $\frac{1}{2}$ wavelength at 14 Mc., and preferably $\frac{3}{4}$ or 1 wavelength; at least 1 wavelength, and preferably higher, at 28 Mc. and the very-high frequencies. The physical height decreases as the frequency is increased, so that good heights are not impracticable; a half wavelength at 14 Mc. is only 35 feet, approximately, while the same height represents a full wavelength at 28 Mc. At 7 Mc. and lower frequencies the higher radiation angles are effective, so that again a reasonable antenna height is not difficult of attainment. Heights between 35 and 70 feet are suitable for all bands, the higher figures generally being preferable where circumstances permit their use.

Imperfect ground — Fig. 1003 is based on ground having perfect conductivity, whereas the actual earth is not a perfect conductor. The principal effect of actual ground is to make the curves inaccurate at the lowest angles; appreciable high-frequency radiation at angles smaller than a few degrees is practically impossible to obtain at heights of less than several wavelengths. Above 15 degrees, however, the curves are accurate enough for all practical purposes, and may be taken as indicative of the sort of result to be expected at angles between 5 and 15 degrees.

The effective ground plane — that is, the plane from which ground reflections can be considered to take place — seldom is the actual surface of the ground but is a few feet below it, depending upon the character of the soil.

Impedance — Waves which are reflected directly upward from the ground induce a current in the antenna in passing, and, depending on the antenna height, the phase relationship of this induced current to the original current may be such as either to increase or decrease the total current in the antenna. For the same power input to the antenna, an increase in current is equivalent to a decrease in impedance, and vice versa. Hence, the impedance of the antenna varies with height. The theoretical curve of variation of radiation resistance for an antenna above perfectly reflecting ground is shown in Fig. 1004. The impedance approaches the free-space value as the height becomes large, but at low heights may differ considerably from it.

Choice of polarization — Polarization of the transmitting antenna is generally unimportant on frequencies between 3.5 and 30 Mc. However, the question of whether the antenna should be installed in a horizontal or vertical position deserves consideration for other reasons. A vertical half-wave antenna will radiate equally well in all horizontal directions, so that it is substantially non-directional, in the usual sense of the word. If installed horizontally, however, the antenna will tend to show directional effects, and will radiate best in the direction at right angles, or broadside, to the wire. The radiation in such a case will be least in the direction toward which the wire points. This can be readily seen by imagining that Fig. 1002 is lying on the ground, and that the pattern is looked at from above.

The vertical angle of radiation also will be affected by the position of the antenna. If it were not for ground losses at high frequencies, the vertical half-wave antenna would be preferred because it would concentrate the radiation horizontally. In practice, however, this theoretical advantage over the horizontal antenna is of little or no consequence, and both types work about alike at low angles.

Below 2 Mc., vertical polarization will give more low-angle radiation, and hence is better for long-distance transmission; at this fre-

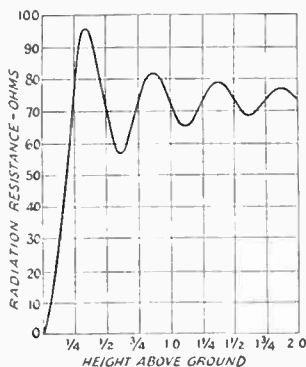


Fig. 1004 — Theoretical curve of variation of radiation resistance for a half-wave horizontal antenna, as a function of height above perfectly reflecting ground.

quency the ground wave also is useful, and must be vertically polarized. On very-high frequencies, direct-ray and lower troposphere transmission require the same type of polarization at both receiver and transmitter, since the waves suffer no appreciable change in polarization in transmission (§ 9-1). Either vertical or horizontal polarization may be used, the latter being slightly better for longer distances.

Effective radiation patterns — In determining the radiation pattern it is necessary to consider radiation in both the horizontal and vertical planes. When the half-wave antenna is vertical, the vertical angle of radiation chosen does not affect the *shape* of the horizontal pattern, but only its relative amplitude. When the antenna is horizontal, however, both the shape and amplitude are dependent upon the angle of radiation chosen.

Fig. 1005 — Illustrating the importance of vertical angle of radiation in determining antenna directional effects. Ground reflection is neglected in this drawing of the free-space field pattern of a horizontal antenna.

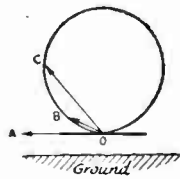


Fig. 1005 illustrates this point. The “free-space” pattern of the horizontal antenna shown is a section cut vertically through the solid pattern. In the direction *O.A.*, horizontally along the wire axis, the radiation is zero. At some vertical angle, however, represented by the line *O.B.*, the radiation is appreciable, despite the fact that this line runs in the same geographical direction as *O.A.* At some higher angle, *O.C.*, the radiation, still in the same geographical direction, is still more intense. The effective radiation pattern therefore depends upon which angle of radiation is most useful, and for long-distance transmission is dependent upon the conditions existing in the ionosphere. These conditions may vary not only from day to day and hour to hour, but even from minute to minute. Obviously, then, the effective directivity of the antenna will change along with transmission conditions.

At very-high frequencies, where only extremely low angles are useful for any but sporadic-*E* transmission (§ 9-2), the effective radiation pattern of the antenna approaches the free-space pattern. A horizontal antenna therefore shows more marked directive effects than it does at lower frequencies, on which high radiation angles are effective.

Theoretical horizontal-directivity patterns for half-wave horizontal antennas at vertical angles of 9, 15, and 30 degrees (representing average useful angles at 28, 14 and 7 Me. respectively) are given in Fig. 1006. At intermediate angles the values in the affected regions also will be intermediate. Relative field strengths are plotted on a decibel scale (§ 3-3), so that they represent as nearly as possible the actual aural effect at the receiving station.

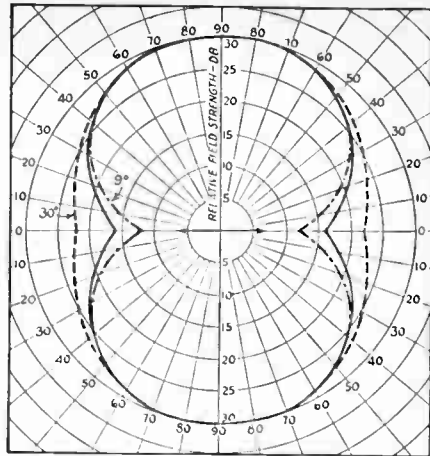


Fig. 1006 — Horizontal pattern of a horizontal half-wave antenna at three vertical radiation angles. The solid line is relative radiation at 15 degrees. Dotted lines show deviation from the 15-degree pattern for angles of 9 and 30 degrees. The patterns are useful for shape only, since the amplitude will depend upon the height of the antenna above ground and the vertical angle considered. The patterns for all three angles have been proportioned to the same scale, but this does not mean that the maximum amplitudes necessarily will be the same. The arrow indicates the direction of the horizontal antenna wire.

10-4 Applying Power to the Antenna

Direct excitation — When power is transferred directly from the source to the radiating antenna, the antenna is said to be directly excited. While almost any coupling method (§ 2-11) may be used, those most commonly employed are shown in Fig. 1007. Power usually is fed to the antenna at either a current or voltage loop (§ 10-2). If power is fed at a current loop, the coupling method is called *current feed*; if at a voltage loop, the method is called *voltage feed*.

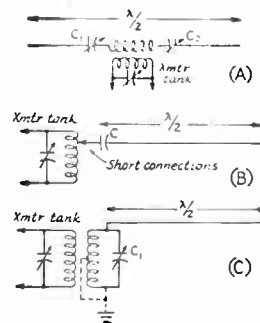


Fig. 1007 — Methods of directly exciting the half-wave antenna. A, current feed, series tuning; B, voltage feed, capacity coupling; C, voltage feed, with an inductively coupled antenna tank. In A, the coupling circuit is not included in the effective electrical length of the antenna system proper.

Current feed — This method is shown in Fig. 1007-A. The antenna is cut at the center and a small coil coupled to the output tank circuit of the transmitter, with adjustable coupling so that the transmitter loading can be controlled. Since the addition of the coil “loads” the antenna, or increases its effective length because of the additional inductance, the series condensers, *C*₁ and *C*₂, are used to

provide electrical means for reducing the length to its original unloaded value; in other words, their capacitive reactance serves to cancel the effect of the inductive reactance of the coil (§ 2-10).

Voltage feed—In Fig. 1007, at B and C the power is introduced into the antenna at a point of high voltage. In B, the end of the antenna is coupled to the output tank circuit through a small condenser, C; in C, a separate tank circuit, connected directly to the antenna, is used. This tank is tuned to the transmitter frequency, and should be grounded at one end or at the center of the coil, as shown.

Adjustment of coupling—Methods of tuning and adjustment of direct-feed systems correspond to those used with transmission lines, which are discussed in § 10-6.

Disadvantages of direct excitation—Direct excitation seldom is used except on the lowest amateur frequencies, because it involves bringing the antenna proper into the operating room and hence into close relationship with the house and electric wiring. This usually means that some of the power is wasted in heating poor conductors in the field of the antenna. Also, it often means that the shape of the antenna must be distorted, so that the expected directional effects are not realized, and likewise that the height will be limited. For these reasons, in high-frequency work practically all amateurs use transmission lines or feeder systems, which permit placing the antenna in a desirable location.

¶ 10-5 Transmission Lines

Requirements—A transmission line (§ 2-12) is used to transfer power, with a minimum of loss, from the transmitter to the antenna from which the power is to be radiated. At radio frequencies, where every wire carrying r.f. current tends to radiate energy in the form of electromagnetic waves, special design is necessary to minimize radiation and thus cause as much of the power as possible to be delivered to the receiving end of the line.

Radiation can be minimized by using a line in which the current is low, and by using two conductors carrying currents of equal magnitudes but opposite phase so that the fields about the conductors cancel each other. For good cancellation of radiation, the two conductors should be kept parallel and quite close to each other.

Types—The most common form of transmission line consists of two parallel wires, maintained at a fixed spacing of two to six inches by insulating spacers or spreaders placed at suitable intervals (*open-wire line*). A second type consists of insulated wires twisted together to form a flexible line, without spacers (*twisted-pair line*). A third uses a wire inside of and coaxial with a tubing outer conductor, separated from the outer conductor by insulating spacers or "beads" at regular intervals (*coaxial or concentric line*). A variation of this

type uses flexible insulating material between the inner and outer conductors, the latter usually being made of metal braid rather than of solid tubing, so that the line will be flexible. Still another type of line uses only a single wire, without a second conductor (*single-wire feeder*): in this type, radiation is minimized by keeping the line current low.

Spacing of two-wire lines—The spacing between the wires of an open-wire line should be small in comparison to the operating wavelength, to prevent appreciable radiation. It is impracticable to make the spacing too small, however, because when the wires swing with respect to each other in a wind the line constants (§ 2-12) will vary, and thus cause a variation in tuning or loading on the transmitter. It is also desirable to use as few insulating spacers as possible, to keep the weight of the line to a minimum. In practice, a spacing of about six inches is used for 14 Mc, and lower frequencies, with four- and two-inch spacings being common on the very-high frequencies.

Balance to ground—For maximum cancellation of the fields about the two wires, it is necessary that the currents be equal in amplitude and opposite in phase. Should the capacity or inductance per unit length in one wire differ from that in the other, this condition cannot be fulfilled. Insofar as the line itself is concerned, the two wires will have identical characteristics only when the two have exactly the same physical relationships to ground and to other objects in the vicinity. Thus, the line should be symmetrically constructed and the two wires should be at the same height. Line unbalance can be minimized by keeping the line as far above the ground and as far from other objects as possible.



Fig. 1008—Transposing a two-wire open transmission line preserves balance to ground and to near-by objects.

To overcome unbalance the line sometimes is transposed, which means that the positions of the wires are interchanged at regular intervals (Fig. 1008). This procedure is more helpful on long than on short lines, and usually need not be resorted to for lines less than a wavelength or so long.

Losses—Air-insulated lines operate at quite high efficiency. Parallel-conductor lines average 0.12 to 0.15 db. (§ 3-3) loss per wavelength of line. These figures hold only if the standing-wave ratio is 1. The losses increase with the standing-wave ratio, rather slowly up to a ratio of 15 to 1, but rapidly thereafter. For standing-wave ratios of 10 or 15 to 1, the increase is inconsequential provided the line is well balanced.

Concentric lines with air insulation are excellent when dry, but losses increase if there is moisture in the line. Provision should be

therefore made for making such lines airtight, and they should be thoroughly dry when assembled. This type of line has the least radiation loss. The small lines (3/8-inch outer conductor) should not be used at high voltages; hence, it is desirable to keep the standing-wave ratio down.

Good quality rubber-insulated lines, both twisted pair and coaxial, average about 1 db. loss per wavelength of line. At the higher frequencies, therefore, such lines should be used only in short lengths if losses are important. These lines have the advantages of compactness, ease of installation, and flexibility. Ordinary lamp cord has a loss of approximately 1.4 db. per wavelength when it is dry, but its losses become excessive when wet. The parallel moulded-rubber type is best from the standpoint of withstanding wet weather. The characteristic impedance of lamp cord is between 120 and 140 ohms.

The loss in db. is directly proportional to the length of the line. Thus, a line which has a loss of 1 db. per wavelength will have an actual loss of 3 db. if the line is three wavelengths long. In the case of line losses, the length is not expressed in terms of electrical length but in physical length; that is, a wavelength of line, in feet, is equal to 984/frequency (Mc.) for computing loss. This permits a direct comparison of lines having the same physical length. The electrical lengths, of course, may differ considerably.

Resonant and nonresonant lines — Lines are classified as *resonant* or *nonresonant*, depending upon the standing-wave ratio. If the ratio is near 1, the line is said to be nonresonant. Reactive effects will be small, and consequently no special tuning provisions need ordinarily be made for canceling them even when the line length is not an exact multiple of a quarter wavelength. Such a line must be terminated in its characteristic impedance (§ 2-12).

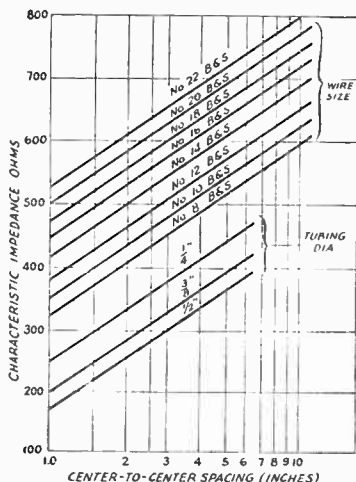


Fig. 1009 — Chart showing the characteristic impedance of typical spaced-conductor parallel transmission lines. Tubing sizes given are for outside diameters.

If the standing-wave ratio is fairly large, the input reactance must be canceled or “tuned out” unless the line is a multiple of a quarter wavelength, and the line is said to be resonant.

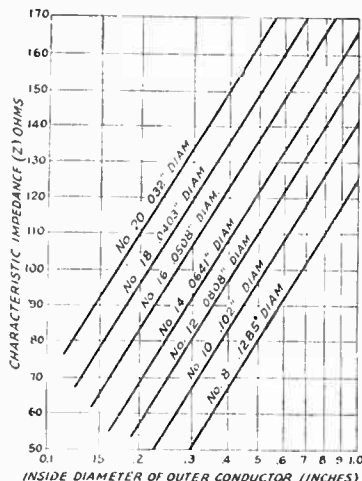


Fig. 1010 — Chart showing characteristic impedance obtained with various air-insulated concentric lines.

10-6 Coupling to Transmission Lines

Requirements — The coupling system between a transmitter and the input end of a transmission line must provide means for adjusting the load on the transmitter to the proper value (impedance matching), and for tuning out any reactive component that may be present (§ 2-9, 2-10, 2-11). The resistance and reactance considered are those present at the *input end of the line*, and hence have nothing to do with the antenna itself except insofar as the antenna load may affect the operation of the line.

Untuned coil — One of the simplest systems, shown in Fig. 1011-A, uses a coil of a few turns tightly coupled to the plate tank coil. Since no provision is made for tuning, this system is suitable only for non-resonant lines which show practically no reactance at the input end. Loading on the transmitter may be varied by varying the coupling between the tank inductance and the *pick-up coil*, as it is frequently called, or by changing the number of turns on the pick-up coil. A slight amount of reactance is coupled into the tank circuit by the pick-up coil, since the flux leakage (§ 2-11) is high, so that some slight retuning of the plate tank condenser may be necessary when the load is connected.

Taps on tank circuit — A method suitable for use with open-wire lines is shown in Fig. 1011-B, where the line is tapped on a balanced tank circuit with taps equidistant from the center or ground point. This symmetry is necessary to maintain line balance to ground (§ 10-5). Loading is increased by moving the taps outward from the center. Any reactance

present may be tuned out by readjustment of the plate tank condenser, but this method is not suitable for large values of reactance and therefore direct tapping is best confined to use with non-resonant lines.

Adjustment of untuned systems — Adjustment of either of the above systems is quite simple. Starting with loose coupling, apply power to the transmitter, and adjust the plate tank condenser for minimum plate current. If the current is less than the desired load value, increase the coupling and again resonate the plate condenser. Continue until the desired plate current is obtained, always keeping the plate tank condenser at the setting which gives minimum current.

Pi-section coupling — A coupling system which is electrically equivalent to tapping on the tank circuit, but using a capacity voltage divider in the plate tank circuit for the purpose, is shown in Fig. 1011-C. Since one side of the condenser across which the line is connected is grounded, some unbalance will be introduced into the transmission line. This method is used chiefly with low-power portable sets, because it is readily adjustable to meet a fairly wide range of impedance values. A single-ended amplifier, using either a screen-grid tube or a grid-neutralized triode (§ 4-7), is required, since the plate tank circuit is not balanced. Coupling is adjusted by varying C_1 , re-resonating the circuit each time by means of C_2 until the desired amplifier plate current is obtained. In general, the coupling will increase as C_1 is made smaller with respect to C_2 . Relatively large-capacity condensers are required to give a suitable impedance-matching range while maintaining resonance.

Pi-section filter — The coupling circuit shown in Fig. 1011-D is a low-pass filter capable of coupling between a fairly wide range of impedances. The method of adjustment is as follows: First, with the filter disconnected from the transmitter tank, tune the transmitter tank to resonance, as evidenced by minimum plate current. Then, with trial settings of the clips on L_1 and L_2 (few turns for high frequencies, more for lower), tap the input clips on the final tank coil at points equidistant from the center, so that about half the coil is included between them. A balanced tank circuit must be used. Set C_2 at about half scale, apply power, and rapidly rotate C_1 until the plate current drops to minimum. If this minimum is not the desired full-load plate current, try a new setting of C_2 and repeat. If, for all settings of C_2 , the plate current is too high or too low, try new settings of the taps on L_1 and L_2 , and also of the taps on the transmitter tank. Do not touch the tank condenser during these adjustments. When, finally, the desired plate current is obtained, set C_1 carefully to the exact minimum plate-current point. *This adjustment is important in minimizing harmonic output.*

With some lengths of resonant lines, particularly those which are not exact multiples of a

quarter wavelength, it may be difficult to get proper loading with the pi-section coupler. Usually antennas of these lengths also will be difficult to feed with other systems of coupling. In such cases, the proper output loading often can be obtained by varying the L/C ratio of the filter over a considerably wider range than is necessary for normal loads as specified on page 204.

Series tuning — When the input impedance of the line is low, the coupling method shown in Fig. 1011-E may be used. This system, known as *series tuning*, places the coupling coil, tuning condensers and load all in series, and is particularly suitable for use with resonant lines when a current loop appears at the input end. As shown, two tuning condensers are used, to keep the line balanced to ground. However, one will suffice, the other end of the line being connected directly to the end of L_1 .

The tuning procedure with series tuning is as follows: With C_1 and C_2 at minimum capacity, couple the antenna coil, L_1 , loosely to the transmitter output tank coil, and observe the plate current. Then increase C_1 and C_2 simultaneously until a setting is reached which gives maximum plate current, indicating that the antenna system is in resonance with the transmitting frequency. Readjust the plate tank condenser to minimum plate current. This is necessary because tuning the antenna circuit will have some effect on the tuning of the plate tank. The new minimum plate current will be higher than with the antenna system detuned, but should still be well below the rated value for the tube or tubes. Increase the coupling between L_1 and L_2 by a small amount, readjust C_1 and C_2 for maximum plate current, and again set the plate tank condenser to minimum. Continue this process until the minimum plate current is equal to the rated plate current for the amplifier. Always use the degree of coupling between L_1 and L_2 which will just bring the amplifier plate current to rated value when C_1 and C_2 pass through resonance.

Parallel tuning — When the line has high input impedance, the use of parallel tuning, as shown in Fig. 1011-F, is required. Here the coupling coil, tuning condenser and line all are in parallel, the load represented by the line being directly across the tuned coupling circuit. If the line is non-reactive, the coupling circuit will be tuned independently to the transmitter frequency; line reactance can be compensated for by tuning of C_1 and, if necessary, adjustment of L_1 by means of taps. Parallel tuning is suited to resonant lines when a voltage loop appears at the input end.

The tuning procedure is quite similar to that with series tuning. Find the value of coupling between L_1 and L_2 which will bring the plate current to the desired value as C_1 is tuned through resonance. Again, a slight readjustment of the amplifier tank condenser may be necessary to compensate for the effect of coupled reactance.

Link coupling — Where tuning of the circuit connected to the line is necessary or desirable, it is possible to separate physically the line-tuning apparatus and the plate tank circuit by means of link coupling (§ 2-11). This is often convenient from a constructional standpoint, and has the advantage that there will be somewhat less harmonic transfer to the antenna, since stray capacity coupling is lessened with the smaller link coils.

Figs. 1011-G and H show a method which can be considered to be a variation of Fig. 1011-B. The first (G) is suitable for use with a single-ended plate tank, the second (H) for a balanced tank. The auxiliary tank on which the transmission line is tapped may have adjustable inductance as well as capacity, to provide a wide range of reactance variation for compensating for line reactance. The center of the auxiliary tank inductance may be grounded, if desired. The link windings should be placed at the grounded parts of the coils, to reduce capacity coupling and consequent harmonic transfer. With this inductively coupled system, the loading on the auxiliary tank circuit increases as the taps are moved outward from the center, but, since this decreases the *Q* of the circuit, the coupling to the plate tank simultaneously decreases (§ 2-11). Hence, a compromise adjustment giving proper loading must be found in practice. Loading also may be varied by changing the coupling between one link winding and its associated tank coil; either tank may be used for this purpose. When the auxiliary tank is properly tuned to compensate for line reactance, the plate tank tuning will be practically the same as with no load; hence, the plate tank condenser need be re-

adjusted only slightly to compensate for the small reactance introduced by the link.

Link coupling also may be used with series tuning, as shown in Fig. 1011-I. The coupling between one link and its associated coil may be made variable, to give the same effect as changing the coupling between the plate tank and antenna coils in the ordinary system. The tuning procedure is the same as described above for series tuning. In the case of single-ended tank circuits the input link is coupled to the grounded end of the tank coil, as in Fig. 1011-G.

Circuit values — The values of inductance and capacity to use in the antenna coupling system will depend upon the transmitting frequency, but are not particularly critical. With series tuning (Fig. 1011-E, I), the coil may consist of a few turns of the same construction as is used in the final tank; average values will run from one or two turns at very-high frequencies to perhaps 10 or 12 at 3.5 Mc. The number of turns preferably should be adjustable so that the inductance can be changed should it not be possible to reach resonance with the condensers used. The series condensers should have a maximum capacity of 250 or 350 $\mu\text{fd.}$ at the lower frequencies; the same values will serve even at 28 Mc., although 100 $\mu\text{fd.}$ will be ample for this and the 14-Mc. band. Still smaller condensers can be used at very-high frequencies. Since series tuning is used at a low-voltage point in the feeder system, the plate spacing of the condensers does not have to be large. Ordinary receiving-type condensers are large enough for plate voltages up to 1000, and the smaller transmitting condensers have high-enough voltage ratings for higher-power

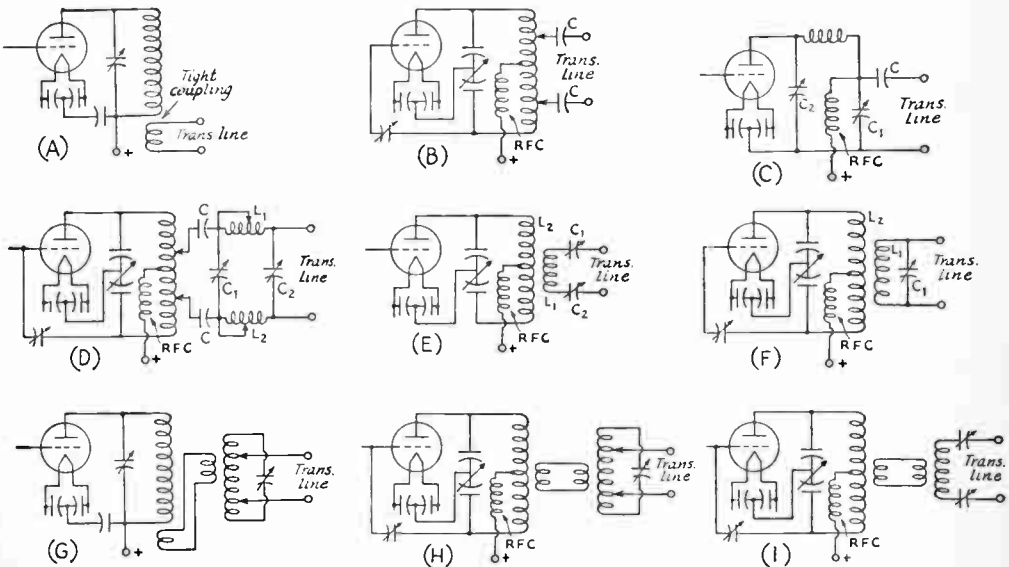


Fig. 1011— Methods of coupling the transmitter output to the transmission line. Application, circuit values and adjustment are discussed in the text. The coupling condensers, *C*, are fixed blocking condensers used to isolate the transmitter plate voltage from the antenna. Their capacity is not critical, 500 $\mu\text{fd.}$ to 0.002 $\mu\text{fd.}$ being satisfactory values, but their voltage rating should at least equal the plate voltage on the final stage.

applications. In high-power radiotelephone transmitters it may be necessary to use condensers having a plate spacing of approximately 0.15 to 0.2 inch.

In parallel-tuned circuits (F, G, H) the antenna coil and condenser should be approximately the same as those used in the final tank circuit. The antenna tank circuit must be capable of being tuned independently to the transmitting frequency, and, if possible, provision should be made for tapping the coil, so that the L/C ratio can be varied to the optimum value (§ 2-11) as determined experimentally.

In Fig. 1011-D, C_1 and C_2 may be 100 to 250 μfd . each, the higher-capacity values being used for lower-frequency operation (3.5 Mc. and lower). Plate spacing should be, in general, at least half that of the final-amplifier tank condenser. For operation up to 14 Mc., L_1 and L_2 each may consist of 15 turns, 2½ inches in diameter, spaced to occupy 3 inches length, and tapped every three turns. Approximate settings are 15 turns for 1.75 Mc., 9 turns for 3.5 Mc., 6 turns for 7 Mc., and 3 turns for 14 Mc. The coils may be wound with No. 14 or No. 12 wire. This method of coupling is very seldom used at very-high frequencies.

Harmonic reduction — It is important to prevent, insofar as possible, harmonics in the output of the transmitter from being transferred to the antenna system. Untuned (Fig. 1011-A) and directly coupled (Fig. 1011-B) systems do not discriminate against harmonics, and hence are more likely to cause harmonic radiation than the inductively coupled tuned systems. Low-pass filter arrangements, such as those at C and D, Fig. 1011, do discriminate against harmonics, but the direct coupling frequently is a source of trouble in this respect.

In inductively coupled systems, care must be taken to prevent capacity coupling between coils. Link coils always should be coupled at a point of ground potential (§ 2-13) on the plate tank coil, as also should series- and parallel-tuned coils (E and F), when possible. Capacity coupling can be practically eliminated by the use of a Faraday shield (§ 4-9) between the plate tank and antenna coils.

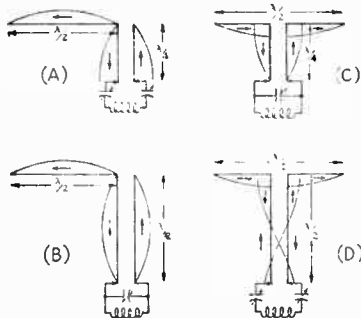


Fig. 1012—Half-wave antennas fed from resonant lines. A and B are end-feed systems for use with quarter- and half-wave lines; C and D are center-feed systems. The current distribution is shown for all four cases, arrows indicating the instantaneous direction of current flow.

¶ 10-7 Resonant Lines

Two-wire lines — Because of its simplicity of adjustment and flexibility with respect to the frequency range over which an antenna system will operate, the resonant line is widely used with simple antenna systems. Constructionally, the spaced or "open" two-wire line is best suited to resonant operation; rubber-insulated lines, such as twisted pair, have excessive losses when operated with standing waves.

Connection to antenna — A resonant line is usually — in fact, practically always — connected to the antenna at either a current or voltage loop. This is advantageous, especially when the antenna is to be operated at harmonic frequencies, since it simplifies the problem of determining the coupling system to be used at the input end of the line.

Half-wave antenna with resonant line — It is often helpful to look upon the resonant line simply as an antenna folded back on itself. Such a line may be any whole-number multiple of a quarter wave in length; in other words, any total wire length which will accommodate a whole number of standing waves. (The "length" of a two-wire line is, however, always taken as the length of one of the wires.)


Quarter- and half-wave resonant lines feeding half-wave antennas are shown in Fig. 1012. The current distribution on both antenna and line is indicated. It will be noted that the quarter-wave line has maximum current at one end and minimum current at the other, determined by the point of connection to the antenna. The half-wave line, however, has the same current (and voltage) values at both ends.

If a quarter-wave line is connected to the end of an antenna, as shown in Fig. 1012-A, then at the transmitter end of the line the current is high and the voltage low (low impedance), so that series tuning (§ 10-6) can be used. Should the line be a half-wave long, as at 1012-B, current will be minimum and voltage maximum (high impedance) at the transmitter end of the line, just as it is at the end of the antenna. Parallel tuning therefore is required (§ 10-6). The line could be coupled to a balanced final tank through small condensers, as in Fig. 1011-B, but the inductively coupled circuit is preferable. An end-fed antenna with resonant feeders, as in 1011-A and B, is known as the "Zeppelin" or "Zepp" antenna.

The line also may be inserted at the center of the antenna at the maximum-current point. Quarter- and half-wave lines used in this way are shown at Fig. 1012-C and D. In C, the antenna end of the line is at a high-current low-voltage point (§ 10-2); hence, at the transmitter end the current is low and the voltage high. Parallel tuning therefore is used. The half-wave line at D has high current and low voltage at both ends, so that series tuning is used at the transmitter end.

The four arrangements shown in Fig. 1012 are thoroughly useful antenna systems, and are

Fig. 1013 — Practical half-wave antenna systems using resonant-line feed. In the center-fed systems, the antenna length, X , does not include the length of the insulator at the center. Line length is measured from the antenna to the tuning apparatus; leads in the latter should be kept short enough so their effect can be neglected. The use of two r.f. ammeters, M , as shown is helpful for balancing feeder currents; however, one meter is sufficient to enable tuning for maximum output, and may be transferred from one feeder to the other, if desired. The systems at (A) and (C) are for feeders an odd number of quarter waves in length; (B) and (D) are for feeders a multiple of a half wavelength. The detailed drawings shown here correspond electrically to the elementary schematic half-wave antenna systems shown in Fig. 1012.

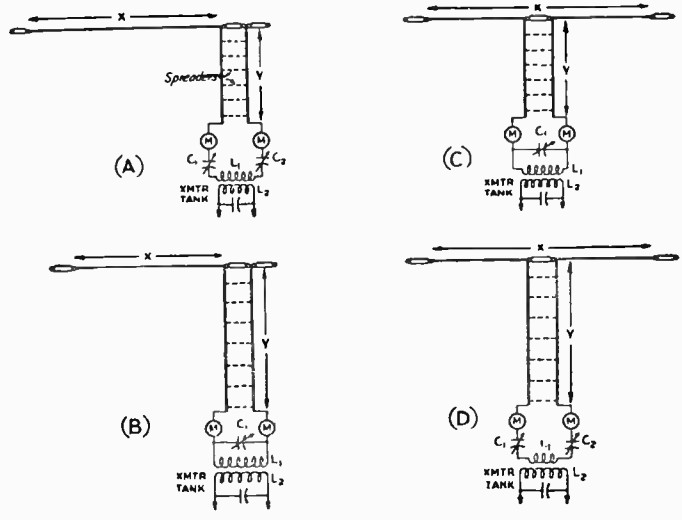

shown in more practical form in Fig. 1013. In each case the antenna is a half wavelength long, the exact length being calculated from Equations 2, 3 or 4 (§ 10-2) or taken from the charts of Fig. 1016. The line length should be an integral multiple of a quarter wavelength and may be calculated from equation 5 (§ 10-5), the result being multiplied by any whole number which gives a total length convenient for reaching from the antenna to the transmitter. If there is an *odd* number of quarter waves on the line in the case of the end-fed antenna, series tuning should be used at the transmitter end; if an *even* number of quarter waves, then parallel tuning should be used. With the center-fed antenna the reverse is true.

Practical line lengths — In general, it is best to use line lengths that are integral multiples of a quarter wavelength. Intermediate lengths will give intermediate impedance values and will show reactance (§ 2-12-A) as well. The tuning apparatus is capable of compensating for reactance, but it may be difficult to get suitable transmitter loading because simple series and parallel tuning are suitable for only low and high impedances, respectively, and neither will perform well with impedances of the order of a few hundred ohms. Such values of impedance may reduce the Q of the coupling circuit to a point where adequate coupling cannot be obtained (§ 2-11). However, some departure from the ideal length is possible — even as much as 25 per cent of a quarter wave in many cases — without undue difficulty in tuning and coupling. In such cases the tuning to use, whether series or parallel, depends on whether the feeder length is an odd number of quarter waves or near an even number, as well as on the point at which the feeder is connected to the antenna — at the end or in the center.

Line current — The feeder current as read by the r.f. ammeters is useful for tuning purposes only; the absolute value is of little im-

portance. When series tuning is used the current will be high, but very little current will be indicated in a parallel-tuned system. This is because of the current distribution on the feeders, as shown by Fig. 1012. With a given antenna and tuning system, of course, the greatest power will be delivered to the antenna when the readings are highest. However, should the feeder length be changed no useful conclusions can be drawn from comparison between the new and old readings. For this reason, any indicator which registers the relative intensity of r.f. current can be used for tuning purposes. Many amateurs, in fact, use flashlight or dial lamps for this purpose instead of meters. Such lamps are inexpensive indicators, and, when shunted by short lengths of wire so that considerable current can be passed without danger of burn-out, will serve very well even with high-power transmitters.

Antenna length and line operation — Insofar as the operation of the antenna itself is concerned, departures of a few per cent from the exact length for resonance are of negligible consequence. However such inaccuracies may influence the behavior of the feeder system, and as a result may have an adverse effect on the operation of the system as a whole. This is true particularly of end-fed antennas, such as are shown in Fig. 1013-A and -B.

For example, Fig. 1014-A shows the current distribution on the half-wave antenna and quarter-wave feeder when the antenna length is correct. At the junction of the "live" feeder to the antenna the current is minimum, so that the currents in the two feeder wires are equal at all corresponding points along their length. When the antenna is too long, as in B, the current minimum occurs at a point on the antenna proper, so that at the top of the live feeder there is already appreciable current flowing, whereas at the top of the "dead" feeder the current must be zero. As a result the

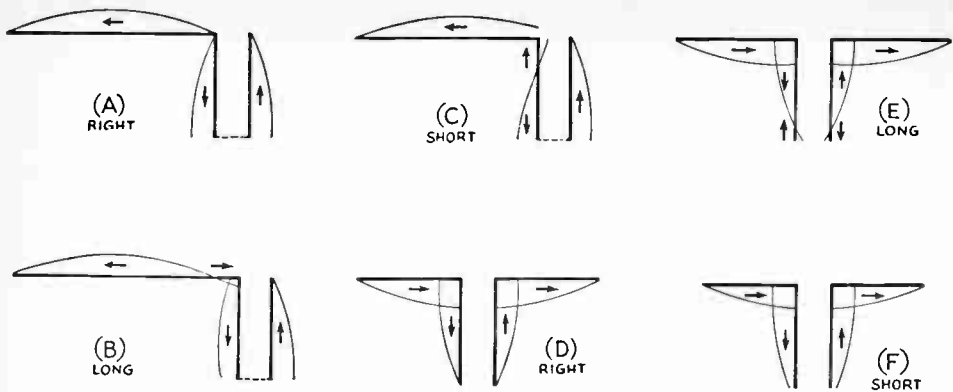


Fig. 1014 — Illustrating the effect on feeder balance of incorrect antenna length for various types of antenna systems. In end-feed systems, the current minimum shifts above or below the feeder junction, unbalancing the line. With center feed, incorrect antenna length does not unbalance the transmission line as it does with end feed.

feeder currents are not balanced, and some power will be radiated from the line. In C, the antenna is too short, bringing the current minimum to a point on the live feeder, so that again the currents are unbalanced. The more serious the unbalance, the greater the radiation from the line.

Strictly speaking, a line having an unbalanced connection, such as the one-way termination at the end of an antenna, cannot be truly balanced even though the antenna length is correct. This is because of the difference in loading on the two sides. The effect of this difference is fairly small when the currents are balanced, however.

If the antenna is fed at the center the undesirable effects of incorrect antenna length balance out, so that the line operates properly under all conditions. This is shown in Fig. 1014 at D, E and F. So long as the two halves of the antenna are of equal length the distribution of current on the feeders will be symmetrical, so that no unbalance exists even for antenna lengths considerably removed from the correct value.

10-8 Nonresonant Lines

Requirements — The advantages of nonresonant transmission lines — minimum losses, and elimination of the necessity for tuning — make the use of this type of line attractive. The chief disadvantage of the nonresonant line, aside from the necessity for more care in initial adjustment, is that when “matched” to the ordinary antenna the match is perfect only for one frequency, or at most for a small band of frequencies on either side of the frequency for which the matching is done. Except for a few special systems, such an antenna is unsuitable for work on more than one amateur band.

Adjustment of a nonresonant line is simply a process of adjusting the terminating resistance to match the characteristic impedance of the line. To accomplish this the antenna itself must be resonant at the selected frequency, and the line must then be connected to it in such a

way that the antenna impedance as looked at by the line is the right value. The matching may be done by connecting the line at the proper spot along the antenna, by inserting an impedance-transforming device between the antenna and line, or by using a line having an impedance equal to the center impedance of the antenna.

An impedance mismatch of several per cent is of little consequence so far as power transfer to the antenna is concerned. It is relatively easy to get the standing-wave ratio down to 2 or 3 to 1, a perfectly satisfactory condition in practice. Of considerably greater importance is the necessity for getting the currents in the two wires balanced, both as to amplitude and phase. If the currents are not the same at corresponding points on adjacent wires and the loops and nodes do not also occur at corresponding points, there will be considerable radiation loss. Perfect balance can be brought about only by perfect symmetry in the line, particularly with respect to ground. This symmetry should extend to the coupling apparatus at the transmitter. An electrostatic shield between the line and the transmitter coupling coils often will be of value in preventing capacity unbalance, and at the same time will reduce harmonic radiation.

In the following discussion of ways in which different types of lines may be matched to the antenna, a half-wave antenna is used as an example. Other types of antennas may be

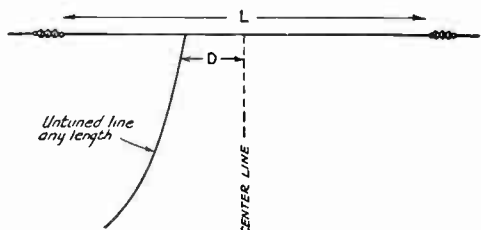


Fig. 1015 — Single-wire-feed system. The length, L , (one-half wavelength) and the feeder location, D , for various bands are determined from the charts of Fig. 1016.

Fig. 1016 — Charts for determining the length of half-wave antennas for use on various amateur frequencies. Solid lines indicate antenna length in feet (lower scale); dotted lines indicate the point of connection for a single-wire feeder (upper scale) measured from center of antenna.

treated by the same methods, making due allowance for the order of impedance that appears at the end of the line when more elaborate systems are used.

Single-wire feed — In the single-wire-feed system, the return circuit is through the ground. There will be no standing waves on the feeder when its characteristic impedance is matched by the impedance of the antenna at the connection point. The principal dimensions (Fig. 1015) are the length of the antenna, L , and the distance, D , from the exact center of the antenna to the point at which the feeder is attached. Approximate dimensions for both antenna length and the feeder connection point can be obtained from Fig. 1016 for an antenna system having a fundamental frequency in any of the most-used amateur bands.

In constructing an antenna system of this type, the feeder must run straight away from the antenna (at a right angle) for a distance of at least one-third the length of the antenna. Otherwise the field of the antenna will affect the feeder and cause faulty operation. There should be no sharp bends in the feeder wire at any point.


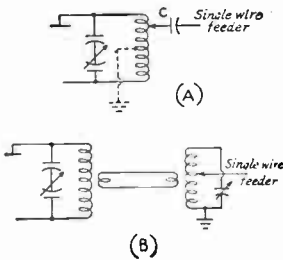
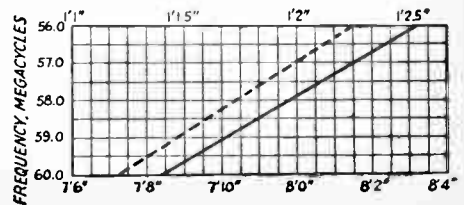
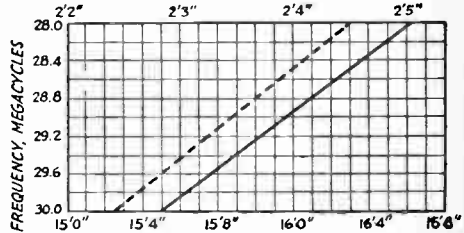
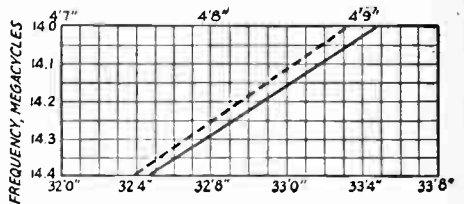
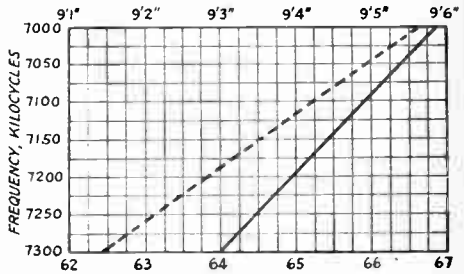
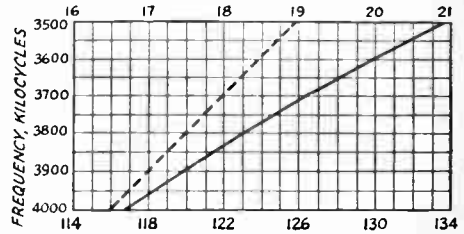


Fig. 1017 — Methods of coupling the feeder to the transmitter in a single-wire-feed system. Circuits are shown for both single-ended and balanced tank circuits.

With the coupling system shown in Fig. 1017-A, the process of adjustment is as follows: Starting at the ground point on the tank coil, the tap is moved towards the plate end until the amplifier draws the rated plate current. The plate tank condenser should be readjusted each time the tap is changed, to bring the plate current back to minimum. The amplifier is loaded properly when this "minimum" value is equal to the rated current. The condenser, C , in the feeder is for the purpose of insulating the antenna system from the high-voltage plate supply when series plate feed is used. It should have a voltage rating somewhat higher than that of the plate supply. Almost any capacity greater than 500 $\mu\mu\text{fd.}$ will be satisfactory. The condenser is unnecessary, of course, if parallel plate feed is used.

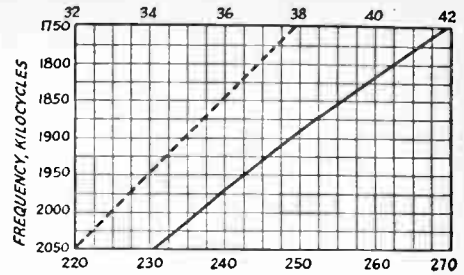Inductive coupling to the output circuit is shown in Fig. 1017-B. The antenna tank circuit



should tune to resonance at the operating frequency, and the loading is adjusted by varying the coupling between the two tanks, both being kept tuned to resonance.

Regardless of the type of coupling employed, a good ground connection is essential with this system. Single-wire feed works best over moist ground, and comparatively poorly over rock and sand.

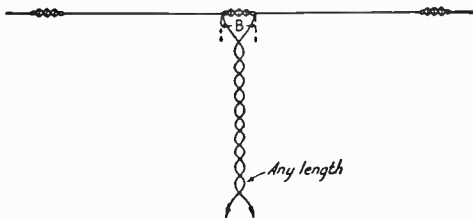


Fig. 1018 — Half-wave antenna center-fed by a twisted-pair line. Fanning (*B*) compensates for line impedance.

Twisted-pair feed — A two-wire line composed of twisted rubber-covered wires can be constructed to have a surge impedance approximately equal to the 70-ohm impedance at the center of the antenna itself, thus permitting connecting the line to the antenna as shown in Fig. 1018. Any discrepancy which may exist between line and antenna impedance can be compensated for by a slight fanning of the line where it connects to the two halves of the antenna, as indicated at *B* in Fig. 1018.

The twisted-pair line is a convenient type to use, since it is easy to install and the r.f. voltage on it is low because of the low impedance. Special twisted line for transmitting purposes, having lower losses than ordinary rubber-covered wire, is available.

The antenna should be one-half wavelength long for the frequency of operation, as determined by charts of Fig. 1016 or the formulas (§ 10-2). The amount of "fanning" (dimension *B*) will depend upon the kind of cable used; the required spacing usually will be between 6 and 18 inches. It may be checked by inserting ammeters in each antenna leg at the junction of the feeder and antenna; the value of *B* which gives the largest current is correct. Alternatively, the system may be operated continuously for a time with fairly high r.f. power input, after which the feeder may be

inspected (by touch) for hot spots. These indicate the presence of standing waves, and the fanning should be adjusted until they are eliminated or minimized. Each leg of the feeder forming the triangle at the antenna should be equal in length to dimension *B*.

Coupling between the transmitter and the transmission line is ordinarily accomplished by the untuned coil method shown in Fig. 1011-A (§ 10-6).

Concentric-line feed — A concentric transmission line can be constructed to have a surge impedance equal to the 70-ohm impedance at the center of a half-wave antenna. Such a line can be connected directly to the center of the antenna, therefore, forming the system shown in Fig. 1019.

An air-insulated concentric line will have a surge impedance of 70 ohms when the inside diameter of the outer conductor is approximately 3.2 times the outside diameter of the inner conductor. This condition can be fulfilled by using standard $\frac{5}{16}$ -inch (outside diameter) copper tubing for the outer conductor and No. 14 wire for the inner. Ceramic insulating spacers are available commercially for this combination. Rubber-insulated concentric line having the requisite impedance for connection to the center of the antenna also is available.

The operation of such an antenna system is similar to that of the twisted-pair system just described, and the same transmitter coupling arrangements may be used (§ 10-6).

The outer conductor of the line may be grounded, if desired. The feeder system is slightly unbalanced, because the inner and outer conductors do not have the same capacity to ground. There should be no radiation from a line having a correct surge impedance, however.

Delta matching transformer — Because of the extremely close spacing required, it is impracticable to construct an open-wire transmission line which will have a surge impedance low enough to work directly into the center of a half-wave antenna. Such wire lines usually have impedances between 400 and 700 ohms, 600 ohms being a widely used value. It is necessary, therefore, to use other means for matching the line to the antenna.

One method of matching is illustrated by the system shown in Fig. 1020. The matching section, *E*, is "fanned" to have a gradually increasing impedance so that its impedance at the antenna end will be equal to the impedance of the antenna section, *C*, while the impedance at the lower end matches that of a practicable transmission line.

The antenna length, *L*, the feeder clearance, *E*, the spacing between centers of the feeder wires, *D*, and the coupling length, *C*, are the important dimensions of this system. The system must be designed for exact impedance values as well as frequency values, and the dimensions therefore are fairly critical.

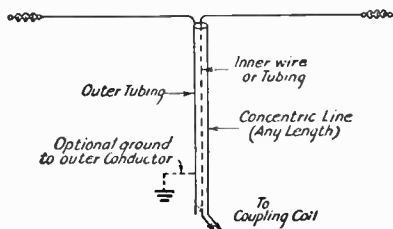


Fig. 1019 — Half-wave antenna center-fed by a concentric transmission line of 70 ohms surge impedance.

The length of the antenna is figured from the formula (§ 10-2) or taken from Fig. 1016. The length of section *C* is computed by the formula:

$$C \text{ (feet)} = \frac{148}{\text{Freq. (Mc.)}}$$

The feeder clearance, *E*, is found from the equation:

$$E \text{ (feet)} = \frac{123}{\text{Freq. (Mc.)}}$$

The above equations are for feeders having a characteristic impedance of 600 ohms and will not apply to feeders of any other impedance. The proper feeder spacing for a 600-ohm transmission line is computed to a sufficiently close approximation by the following formula:

$$D = 75 \times d$$

where *D* is the distance between the centers of the feeder wires and *d* is the diameter of the wire. If the wire diameter is in inches the spacing also will be in inches, and if the wire diameter is in millimeters the spacing also will be in millimeters.

Methods of coupling to the transmitter are discussed in § 10-6, those shown in Figs. 1011-C, D, G and H being suitable.

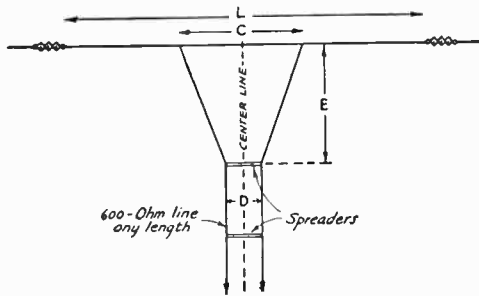


Fig. 1020 — Delta-matched antenna system. The dimensions *C*, *D*, and *E* are found by formulas given in the text. It is important that the matching section, *E*, come straight away from the antenna without any bends.

“Q”-section transformer — The impedance of a two-wire line of ordinary construction (400 to 600 ohms) can be matched to the impedance of the center of a half-wave antenna by utilizing the impedance-transforming properties of a quarter-wave line (§ 10-5). The matching section must have low surge impedance and therefore is commonly constructed of large-diameter conductors such as aluminum or copper tubing, with fairly close spacing. This system is known as the “Q” antenna. It is shown in Fig. 1021. The important dimensions are the length of the antenna, the length of the matching section, *B*, the spacing between the two conductors of the matching section, *C*, and the impedance of the untuned transmission line connected to the lower end of the matching section.

The required surge impedance for the matching section is

$$Z_0 = \sqrt{Z_1 Z_2} \tag{9}$$

where *Z*₁ is the input impedance and *Z*₂ the output impedance. Thus a quarter-wave section matching a 600-ohm line to the center of a half-wave antenna (72 ohms) should have a surge impedance of 208 ohms. The spacings between conductors of various sizes of tubing and wire for different surge impedances are given in graphical form in Fig. 1009. With ½-inch tubing, the spacing should be 1.5 inches for an impedance of 208 ohms.

The length of the matching section, *B*, should be equal to a quarter wavelength, and is given by

$$\text{Length of quarter-wave line (feet)} = \frac{234}{\text{Freq. (Mc.)}}$$

The length of the antenna can be calculated from the formula (§ 10-2), or taken from the charts of Fig. 1016.

This system has the advantage of the simplicity of adjustment of the twisted-pair feeder system and at the same time the superior insulation of an open-wire system. Figs. 1011-B, D, G and H (§ 10-6) represent suitable methods of coupling to the transmitter.

Linear transformers — Fig. 1022 shows two methods of coupling a non-resonant line to a half-wave antenna through a quarter-wave linear transformer or matching section. In the case of the center-fed antenna, the free end of the matching section, *B*, is open (high impedance) since the other end is connected to a low-impedance point on the antenna. With the end-fed antenna, the free end of the matching section is closed through a shorting bar or link; this end of the section has low impedance, since the other end is connected to a high-impedance point on the antenna (§ 10-7).

When the connection between the matching section and the antenna is unbalanced, as in the end-fed system, it is important that the antenna be the right length for the operating frequency if a good match is to be obtained (§ 10-7). The balanced center-fed system is less critical in this respect. The shorting-bar method of tuning the center-fed system to resonance may be used if the matching section

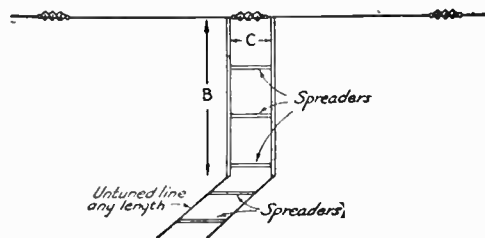


Fig. 1021 — The “Q” antenna, using a quarter-wave impedance-matching section with close-spaced conductors.

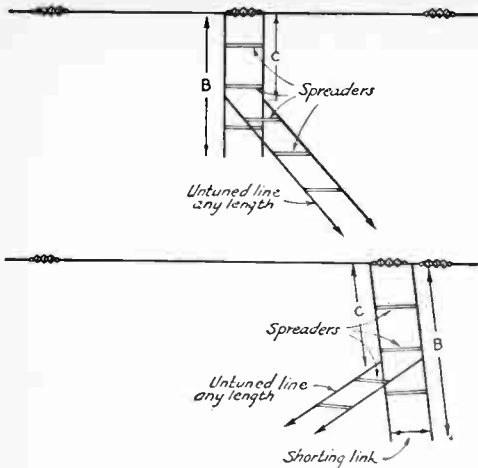


Fig. 1022 — Half-wave antenna systems with quarter-wave open-wire linear impedance-matching transformers.

is extended to a half wavelength, bringing a current loop at the free end.

In the center-fed system, the antenna and matching section should be cut to lengths found from the equations in §10-2 and §10-5. Any necessary on-the-ground adjustment can be made by adding to or clipping off the open ends of the matching section. In the end-fed system the matching section can be adjusted by making the line a little longer than necessary and adjusting the system to resonance by moving the shorting link up and down. Resonance can be determined by exciting the antenna at the proper frequency from a temporary antenna near by and measuring the current in the shorting bar by a low-range r.f. ammeter or galvanometer using one of the devices of this type described in Chapter Nineteen. The position of the bar should be adjusted for maximum current reading. This should be done before the transmission line is attached to the matching section.

The position of the line taps will depend upon the impedance of the line as well as on the antenna impedance at the point of connection. The procedure is to take a trial point, apply power to the transmitter, and then check the transmission line for standing waves. This can be done by measuring the current in or voltage along the wires. At any one position along the line the currents in the two wires should be identical. Readings taken at intervals of a quarter wavelength will indicate whether or not standing waves are present.

It will not usually be possible to obtain complete elimination of standing waves when the matching stub is exactly resonant, but the line taps should be adjusted for the smallest obtainable standing-wave ratio. Then a further "touching up" of the matching-stub tuning will eliminate the remaining standing wave, provided the adjustments are carefully made. The stub must be readjusted, because when

resonant it exhibits some reactance as well as resistance at all points except at the ends, and a slight lengthening or shortening of the stub is necessary to tune out this reactance.

Since the line impedance is ordinarily between 500 and 600 ohms, the same methods of coupling may be used between the transmitter and the line as are recommended for the delta-matching system and the *Q* matching transformer.

Matching stubs — The operation of the quarter-wave matching transformer of Fig. 1022 may be considered from another — and more general — viewpoint. Suppose that section C is looked upon simply as a continuation of the transmission line. Then the "free" end of the transformer becomes a "stub" line, shunting a section of the main transmission line. From this viewpoint, matching the line to the antenna becomes a matter of selecting the right type and length of stub and attaching it to the proper spot along the line.

Referring to Fig. 1023, at any distance (*X*) from the antenna, the line will have an impedance which may be considered to be made up of reactance (either inductive or capacitive) and resistance, in parallel. The reactive component can be eliminated by shunting the line at distance *X* from the antenna with another reactance equal in value but opposite in sign to the reactance presented by the line at that point. If distance *X* is such that the line presents an inductive reactance, a corresponding shunting capacitive reactance will be required.

The required compensating reactance may be supplied by shunting the line with a stub cut to proper length, *Y*. With the reactances canceled only a pure resistance remains as a termination for the remainder of the line between the sending end and the stub, and this resistance can be adjusted to match the characteristic impedance of the line by adjusting the distance *X*.

Distances *X* and *Y* may be determined experimentally, but since their values are interdependent the cut-and-try method is somewhat laborious. If the standing-wave ratio and the positions of the current loops and nodes can be measured, the length and position of the stub can be found from Figs. 1024 and 1025.

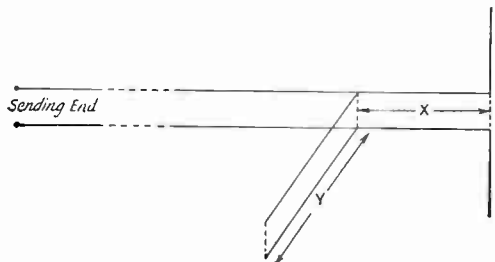


Fig. 1023 — When antenna and transmission line differ in impedance, they may be matched by a short length of transmission line, *Y*, called a stub. Determination of the critical dimensions, *X* and *Y*, for proper matching depends on whether the stub is open or closed at the end.

Although the standing-wave ratio can be measured in terms of either current or voltage, measurement of current usually is more convenient. (If the measurements are made with a current-squared galvanometer an appropriate correction must be made, since scale readings with this type of meter are proportional to power.) With the antenna connected to the line but with the stub disconnected, the r.f. meter should be moved along the line from the antenna toward the sending end until a current loop or node is found. Its location should be marked and the value of the current recorded. Then the meter should be moved along toward the sending end until the next loop or node is located (if the first was a loop the second will be a node, and vice versa), and the current at this point recorded. As a cross-check for wavelength, the distance between a loop and node should be $\frac{1}{4}$ wavelength. The standing-wave ratio is the ratio of current at a loop to current at a node.

Once the standing-wave ratio is known, the length and position of the stub, in terms of wavelength, can be found directly from Figs. 1024 and 1025. The wavelength in feet for any frequency can be found from Equation 1.

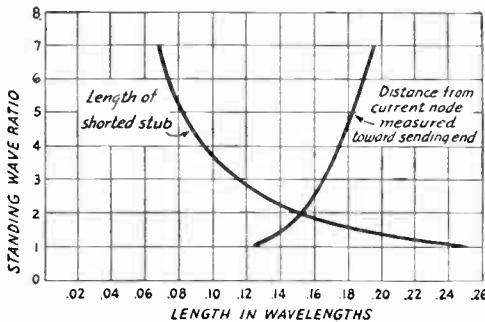


Fig. 1024 — Graphs for determining position and length of a shorted stub. Dimensions may be converted to linear units after values have been taken from the graph.

Methods of coupling to the line shown in Figs. 1011-B, D, G and H (§ 10-6) can be used.

Measuring standing waves — Equipment for measuring the standing-wave ratio along the transmission line is described in Chapter 18. At frequencies below 30 megacycles the thermomilliammeter probably is the most reliable instrument and the easiest to use. The absolute value of the current in the line is not important; the ratio between the maximum and minimum currents is what is required.

When the standing-wave ratio is low it may be difficult to determine the exact location of a node or loop since the current changes rather slowly at these points. In such a case the following procedure may be adopted: Measure the minimum current, then choose a somewhat higher value and locate two points on either side of the minimum at which the current equals the chosen value. For example, if the minimum current is 0.1 ampere, a value of 0.15

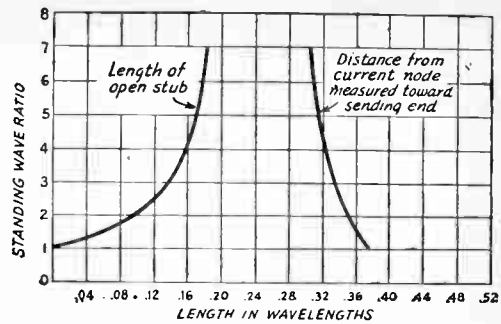


Fig. 1025 — Graphs for determining position and length of an open stub. Dimensions may be converted to linear units after values have been taken from the graph.

ampere might be chosen and the meter moved first to one side and then the other of the minimum point until two spots are found where the reading is 0.15 ampere. Then the node will be just half-way between these two points and may be determined very easily by measuring the distance. The same method may be used to locate a current loop with more exactness than by trying to locate the actual point of maximum current. In this case, of course, a value of current slightly lower than the maximum value should be chosen.

A crystal-detector probe pick-up measures maximum and minimum voltage rather than current. The standing-wave ratio may be measured in terms of voltage equally as well as in terms of current. However, in using the charts for the matching stub system it must be kept in mind that a voltage loop occurs at the same point as a current node, and vice versa.

10-9 Long-Wire Antennas

Definition — An antenna will be resonant so long as an integral number of standing waves of current and voltage can exist along its length; in other words, so long as its length is some integral multiple of a half wavelength. When the antenna is more than a half wave long it usually is called a long-wire antenna, or a harmonic antenna.

Current and voltage distribution — Fig. 1026 shows the current and voltage distribution along a wire operating at its fundamental frequency (where its length is equal to a half wavelength) and at its second, third and fourth harmonics. For example, if the fundamental frequency of the antenna is 7 Mc., the current and voltage distribution will be as shown at A. The same antenna excited at 14 Mc. would have current and voltage distribution as shown at B. At 21 Mc., the third harmonic of 7 Mc., the current and voltage distribution would be as in C; and at 28 Mc., the fourth harmonic, as in D. The number of the harmonic is the number of half waves contained in the antenna at the particular operating frequency.

The polarity of current or voltage in each standing wave is opposite to that in the ad-

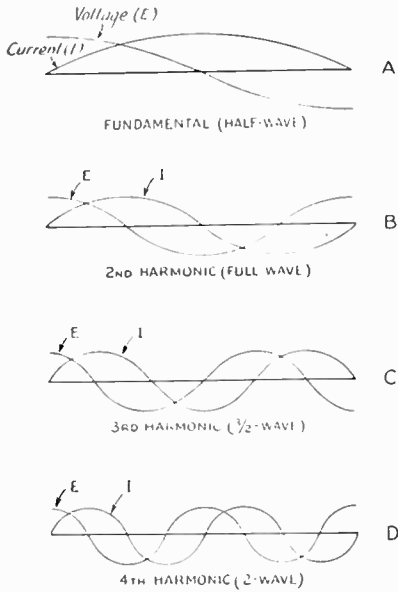


Fig. 1026 Standing-wave current and voltage distribution along an antenna when it is operated at various harmonics of its fundamental resonant frequency.

adjacent standing waves. This is shown in the figure by drawing the current and voltage curves successively above and below the antenna (taken as a zero reference line), to indicate that the polarity reverses when the current or voltage goes through zero. Currents flowing in the same direction are *in phase*; in opposite directions, *out of phase*.

It is evident that one antenna may be used for harmonically related frequencies, such as the various amateur bands. The long-wire or harmonic antenna is the basis of multi-band operation with one antenna.

Physical lengths — The length of a long-wire antenna is not an exact multiple of that of a half-wave antenna because the end effects (§ 10-2) operate only on the end sections of the antenna; in other parts of the wire these effects are absent, and the wire length is approximately that of an equivalent portion of the wave in space. The formula for the length of a long-wire antenna, therefore, is

$$\text{Length (feet)} = \frac{492 (N-0.05)}{\text{Freq. (Mc.)}} \quad (10)$$

where *N* is the number of *half waves* on the antenna. From this, it is apparent that an antenna cut as a half wave for a given frequency will be slightly off resonance at exactly twice that frequency (on the second harmonic) because of the different behavior of end effects when there is more than one standing wave on the antenna. For instance, if the antenna is cut to have exact fundamental resonance on the second harmonic (full-wave operation) it should be 2.6 per cent longer, and on the fourth harmonic (two-wave), 4 per cent longer. The

effect is not very important except for a possible unbalance in the feeder system (§ 10-7), which may result in some radiation from the feeder in end-fed systems.

Impedance and power gain — The radiation resistance as measured at a current loop becomes larger as the antenna length is increased. Also, a long-wire antenna radiates more power in its most favorable direction than does a half-wave antenna in its most favorable direction. This power gain is secured at the expense of radiation in other directions. Fig. 1027 shows how the radiation resistance and the power in the lobe of maximum radiation vary with the antenna length.

Directional characteristics — As the wire is made longer in terms of the number of half wavelengths, the directional effects change. Instead of the "doughnut" pattern of the half-wave antenna, the directional characteristic splits up into "lobes" which make various angles with the wire. In general, as the length of the wire is increased the direction in which maximum radiation occurs tends to approach the line of the antenna itself.

Directional characteristics for antennas one wavelength, three half-wavelengths, and two wavelengths long are given in Figs. 1028, 1029 and 1030, for three vertical angles of radiation. Note that, as the wire length increases, the radiation along the line of the antenna becomes more pronounced. Still longer antennas can be considered to have practically "end-on" directional characteristics, even at the lower radiation angles.

Methods of feeding — In a long-wire antenna, the currents in adjacent half-wave sections must be out of phase, as shown in Fig.

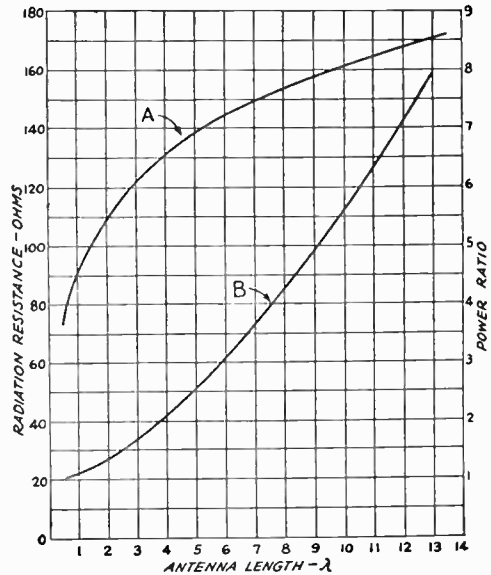


Fig. 1027 — Curve A shows variation in radiation resistance with antenna length. Curve B shows power in lobes of maximum radiation for long-wire antennas as a ratio to the maximum radiation for a half-wave antenna.

1031 and Fig. 1026. The feeder system must not upset this phase relationship. This requirement is met by feeding the antenna at either end or at any current *loop*. A two-wire feeder cannot be inserted at a current *node*, however, because this invariably brings the currents in two adjacent half-wave sections in phase; if the phase in one section could be reversed, then the currents in the feeders necessarily would have to be in phase and the feeder radiation would not be canceled out.

Either resonant or non-resonant feeders may be used. With the latter, the systems employing a matching section (§ 10-8) are best. The non-resonant line may be tapped on the matching section, as in Fig. 1022, or a "Q" type section, Fig. 1021, may be employed. In such case, Fig. 1032 gives the required surge impedance for the matching section. It can also be calculated from Equation 9 (§ 10-8) and the radiation resistance data in Fig. 1027.

Methods of coupling the line to the transmitter are the same as described in § 10-6 for the particular type of line used.

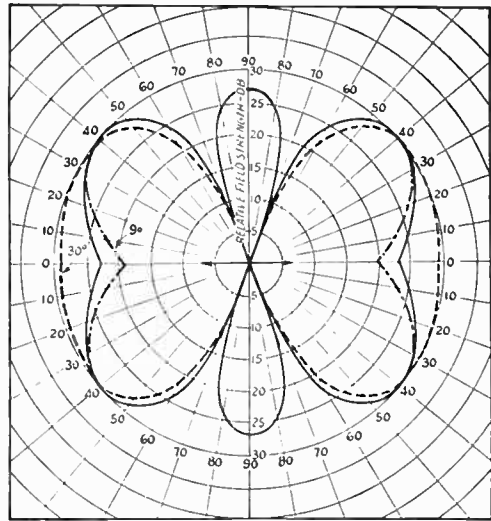


Fig. 1029 — Horizontal patterns of radiation from an antenna three half-waves long. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. Minor lobes coincide for all three angles.

Furthermore, the current loops shift to a new position on the antenna when it is operated on harmonics, further complicating the feed situation. It is for this reason that a half-wave antenna which is center-fed by a rubber-insulated line is practically useless for harmonic operation; on all even harmonics there is a voltage maximum occurring right at the feed point, and the resultant impedance mismatch is so bad that there is a large standing-wave ratio and consequently high losses arise in the rubber dielectric.

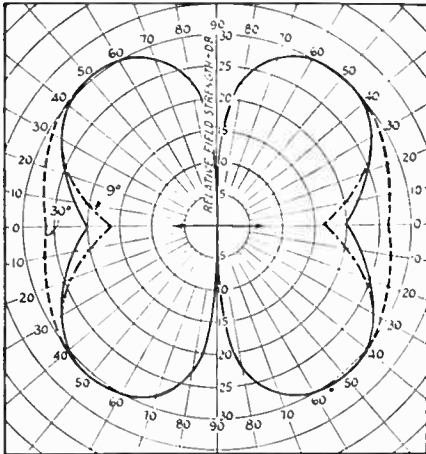


Fig. 1028 — Horizontal patterns of radiation from a full-wave antenna. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. All three patterns are drawn to the same relative scale; actual amplitudes will depend upon the height of the antenna.

10-10 Multiband Antennas

Principles — As suggested in the preceding section, the same antenna may be used for several bands by operating it on harmonics. When this is done it is necessary to use resonant feeders, since the impedance matching for non-resonant feeder operation can be accomplished only at one frequency unless means are provided for changing the length of a matching section and shifting the point at which the feeder is attached to it. A matching section which is only a quarter-wavelength long at one frequency will be a half-wavelength long at twice that frequency, and so on; and changing the length of the wires, even by switching, is so inconvenient as to be impracticable.

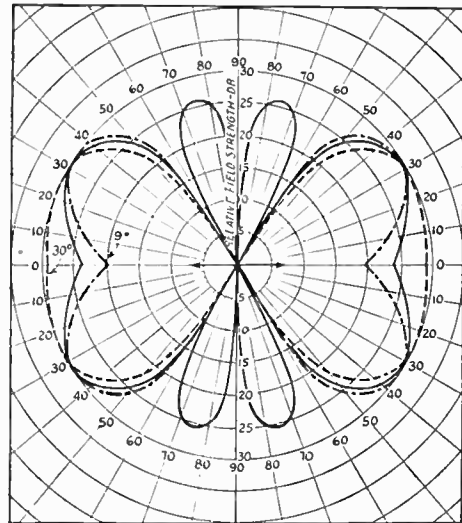


Fig. 1030 — Horizontal patterns of radiation from an antenna two wavelengths long. The solid line shows the pattern for a vertical angle of 15 degrees; dotted lines show deviation from the 15-degree pattern at 9 and 30 degrees. The minor lobes coincide for all three angles.

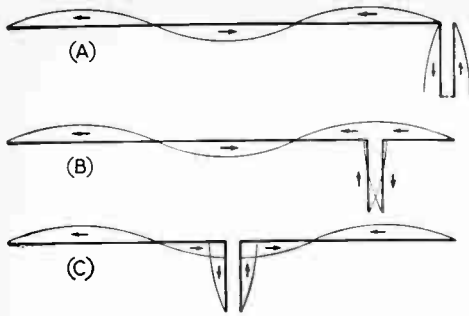


Fig. 1031 — Current distribution and feed points for long-wire antennas. A 3/2-wave antenna is used as an illustration. With two-wire feed, the line may be connected at the end of the antenna or at any current loop (but not at a current node) for harmonic operation.

When the same antenna is used for work in several bands, it must be realized that the directional characteristic will vary with the band in use.

Simple systems — Any of the antenna arrangements shown in § 10-7 may be used for multiband operation by making the antenna a half wave long at the lowest frequency to be used. The feeders should be a quarter wave long, or some multiple of a quarter wave, at the same frequency. Typical examples, together with the type of tuning to be used, are given in Table I. The figures given represent a compromise designed to give satisfactory operation on all the bands considered, taking into account the change in required length as the order of the harmonic goes up.

A center-fed half-wave antenna will not operate as a long wire on harmonics, because of the phase reversal at the feeders previously mentioned (§ 10-9). On the second harmonic the two antenna sections are each a half wave long, and, since the currents are in phase, the directional characteristic is different from that

Fig. 1032 — Required surge impedance of quarter-wave matching sections for radiators of various lengths. Curve A is for a transmission-line impedance of 440 ohms, Curve B is for 470 ohms, Curve C for 530 ohms and Curve D for 600 ohms. Dimensions for matching sections of the required impedance are obtained from Fig. 1009.

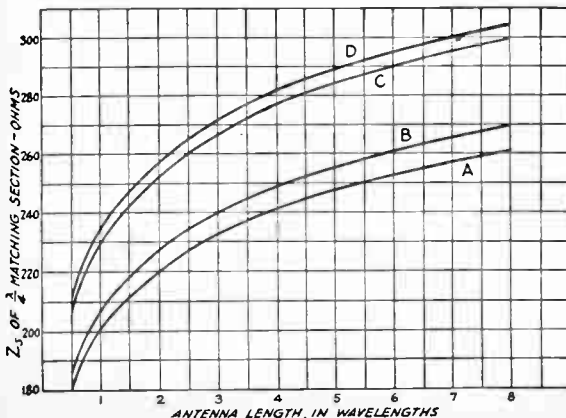


TABLE I
MULTIBAND RESONANT-LINE-FED ANTENNAS

Antenna Length (ft.)	Feeder Length (ft.)	Band	Type of Tuning
With end feed: 243	120	1.75-Mc. 'phone	series
		4-Mc. 'phone	parallel
		14 Me.	parallel
		28 Me.	parallel
136	67	3.5-Mc. c.w.	series
		7 Me.	parallel
		14 Me.	parallel
		28 Me.	parallel
134	67	3.5-Mc. c.w.	series
		7 Me.	parallel
67	33	7 Me.	series
		14 Me.	parallel
		28 Me.	parallel
With center feed: 272	135	1.75 Mc.	parallel
		3.5 Me.	parallel
		7 Me.	parallel
		14 Me.	parallel
137	67	3.5 Me.	parallel
		7 Me.	parallel
		14 Me.	parallel
		28 Me.	parallel
67.5	34	7 Me.	parallel
		14 Me.	parallel
		28 Me.	parallel

The antenna lengths given represent compromises for harmonic operation because of different end effects on different bands. The 136-foot end-fed antenna is slightly long for 3.5 Mc., but will work well in the region which quadruples into the 14-Mc. band (3500-3600 kc.). Bands not listed are not recommended for the particular antenna. The center-fed systems are less critical as to length; the 272-foot antenna, for instance, may be used for both c.w. and 'phone on either 1.75 or 4 Mc. without loss of efficiency.

On harmonics, the end-fed and center-fed antennas will not have the same directional characteristics, as explained in the text.

of a full-wave antenna even though the over-all length is the same. On the fourth harmonic each section is a full wave long, and, again because of the direction of current flow, the system will not operate as a two-wavelength antenna. It should not be assumed that these systems are not effective radiators; it simply means that the directional characteristic will not be that of a long wire having the same over-all length. Rather, it will resemble the characteristic of one side of the antenna, although not necessarily having the same exact form.

Antennas with a few other types of feed systems may be operated on harmonics for the higher-frequency bands, although their performance is some-

what impaired. The single wire-fed antenna (§ 10-8) may be used in this way; the feeder and antenna will not be matched exactly on harmonics, with the result that standing waves will appear on the feeder, but the system as a whole will radiate. A better match will be obtained if the point of connection of the feeder to the antenna is made exactly one-third the over-all antenna length from one end. While this disagrees slightly with the figures given for a half-wave antenna, it has been found to work better on the harmonic frequencies.

The "Q" antenna system (§ 10-8) also can be operated on harmonics, but the line cannot

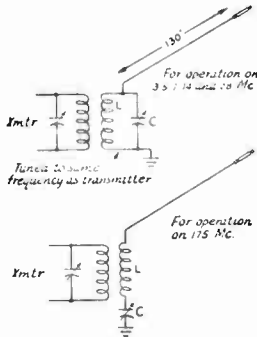


Fig. 1033 -- A simple antenna system for five amateur bands. The antenna is voltage fed on 3.5, 7, 14 and 28 Mc., working on the fundamental, second, fourth and eighth harmonics, respectively. For 1.75 Mc. the system is a quarter-wave grounded antenna, in which case series tuning must be used. The antenna wire should be kept well in the clear and should be as high as possible. If the length of the antenna is increased to approximately 260 feet, voltage feed can be used on all five bands.

operate as a non-resonant line except at the fundamental frequency of the antenna. For harmonic operation the line must be tuned, and therefore the feeder length is important. The tuning system will depend upon the number of quarter waves on the line, including the "Q" bars. The concentric-line-fed antenna (§ 10-8) may be used on harmonics, if the concentric line is air-insulated. Its operation on harmonics is similar to that of the "Q." This antenna is not recommended for multi-band operation with a rubber-insulated line, however.

The delta-match system (§ 10-8) can be used on harmonics, although some standing waves will appear on the line. For that matter, any antenna system can be used on harmonic frequencies by tying the feeders together at the transmitter end and feeding the system as a single wire by means of a tuned circuit coupled to the transmitter.

A simple antenna system without feeders, useful for operation on five bands, is shown in Fig. 1033. On all bands from 3.5 Mc. upward it operates as an end-fed antenna — half wave on 3.5 Mc., long wire on the other bands. On 1.75 Mc. it is only a quarter wave in length, and must be worked against ground (§ 10-14). On this band, since it is fed at a high-current point, series tuning (§ 10-6) must be used.

Antennas for restricted space — If the space available for the antenna is not large enough to accommodate the length necessary for a half wave at the lowest frequency to be used, quite satisfactory operation can be secured by using a shorter antenna and making up the missing length in the feeder system. The antenna itself may be as short as a quarter wavelength and still radiate fairly well, although of course it will not be as effective as one a half wave long. Nevertheless, such a system is useful where operation on the desired band otherwise would be impossible.

Resonant feeders are a practical necessity with such an antenna system, and a center-fed antenna will give best all-around performance. With end feed the feeder currents become badly unbalanced, and, since lengths midway between those requiring series or parallel tuning ordinarily must be used to bring the entire system to resonance, coupling to the transmitter often becomes difficult.

With center feed practically any convenient length of antenna can be used, if the feeder length is adjusted to accommodate at least one half wave around the whole system. Typical cases are shown in Fig. 1034, one for an antenna having a length of one quarter wave (A) and the other for an antenna somewhat longer (C) but still not a half wave long. Current distribution is shown for both fundamental and second harmonic. From the points marked X, resonant feeders any convenient number of quarter waves in length may be extended to the operating room. The sum of the distances on each wire from X to the antenna end must equal a half wave. It is sufficiently accurate to use Equation 2 (§ 10-2) in calculating this length. Note that X-X is a high-current point on these shortened antennas, corresponding to the center of a half-wave antenna. It is also apparent that the antenna at A is a half-wave antenna on the next higher-frequency band (B).

A practical antenna of this type can be made as shown in Fig. 1035. Table II gives a few

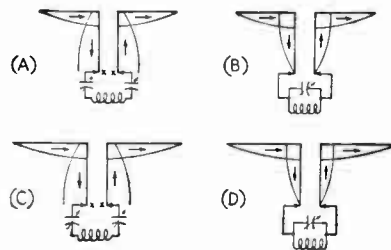


Fig. 1034 — Current distribution on short antennas. Those at the left are too short for fundamental operation, one (A) having an over-all length of one quarter wave; the other (C) being longer but not a half-wave long. These systems may be used wherever space to erect a full half-wave antenna is not available. The current distribution for second harmonic-operation is shown at the right of each figure (B and D). In A and C, the total length around the system is a half-wave at the fundamental. In B and D, the over-all length is a full wave. Arrows show the instantaneous direction of current flow.

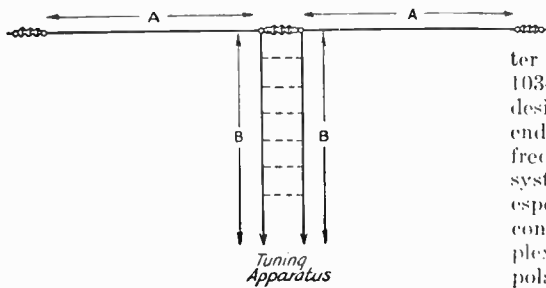


Fig. 1035 — Practical arrangement of a shortened antenna. The total length, $A + B + B + A$, should be a half wavelength for the lowest-frequency band, usually 3.5 Mc. See Table II for lengths and tuning data.

recommended lengths. Remembering the preceding discussion, however, the antenna can be made any convenient length, provided the feeder is considered to "begin" at X-X and the line length is adjusted accordingly.

Bent antennas — Since the field strength at a distance is proportional to the current in the antenna, the high-current part of a half-wave antenna (the center quarter wave, approximately) does most of the radiating (§ 10-1). Advantage can be taken of this fact when the space available does not permit erecting an antenna a half-wave long. In this case the ends may be bent, either horizontally or vertically, so that the total length equals a half wave, even though the straightaway horizontal length may be as short as a quarter wave.

The operation is illustrated in Fig. 1036. Such an antenna will be a somewhat better radiator than the arrangement of Fig. 1034-A on the lowest frequency, but is not so desirable for multi-band operation because the ends play an increasingly important part as the frequency is raised. The performance of the system in such a case is difficult to predict, especially if the ends are vertical (the most convenient arrangement), because of the complex combination of horizontal and vertical polarization which results as well as the dissimilar directional characteristics.



Fig. 1036 — Folded arrangement for shortened antennas. The total length is a half wave, not including the feeders. The horizontal part is made as long as convenient and the ends dropped down to make up the required length. The ends may be bent back on themselves like feeders to cancel radiation partially. The horizontal section should be at least a quarter-wave long.

¶ 10-11 Long-Wire Directive Arrays

The "V" antenna — It has been emphasized that, as the antenna length is increased, the lobe of maximum radiation makes a more acute angle with the wire (§ 10-9). Two such wires may be combined in the form of a horizontal "V" so that the main lobes from each wire will reinforce along a line bisecting the angle between the wires. This increases both gain and directivity, since the lobes in directions other than along the bisector cancel to a greater or lesser extent. The horizontal "V" antenna therefore transmits best in either direction (is bidirectional) along a line bisecting the "V" made by the two wires. The power gain depends upon the length of the wires. Provided the necessary space is available, the "V" is a simple antenna to build and operate. It can also be used on harmonics, so that it is suitable for multi-band work. The "V" antenna is shown in Fig. 1037.

Fig. 1038 shows the dimensions that should be followed for an optimum design to obtain maximum power gain for different-sized "V" antennas. The longer systems give good performance in multiband operation. Angle α

Antenna length (ft.)	Feeder length (ft.)	Band	Type of tuning
137	68	1.75 Mc. 3.5 Mc. 7 Mc. 14 Mc. 28 Mc.	series parallel parallel parallel parallel
100	38	3.5 Mc. 7 Mc. 14 Mc. 28 Mc.	parallel series series series or parallel
67.5	34	3.5 Mc. 7 Mc. 14 Mc. 28 Mc.	series parallel parallel parallel
50	43	7 Mc. 14 Mc. 28 Mc.	parallel parallel parallel
33	51	7 Mc. 14 Mc. 28 Mc.	parallel parallel parallel
33	31	7 Mc. 14 Mc. 28 Mc.	parallel series parallel

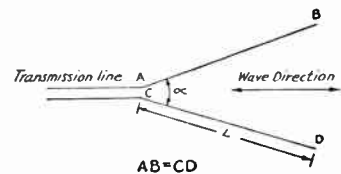


Fig. 1037 — The "V" antenna, made by combining two long wires in such a way that each reinforces the radiation from the other. The important quantities are the length of each leg and the angle between the legs.

is approximately equal to twice the angle of maximum radiation for a single wire equal in length to one side of the "V."

The wave angle referred to in Fig. 1038 is the vertical angle of maximum radiation (§ 10-1). Tilting the whole horizontal plane of the "V" will tend to increase the low-angle radiation off the low end and decrease it off the high end.

The gain increases with the length of the wires, but is not exactly twice the gain for a single long wire as given in Fig. 1029. In the longer lengths the gain will be somewhat increased, because of mutual coupling between the wires. A "V" eight wavelengths on a leg, for instance, will have a gain of about 12 db. over a half-wave antenna, whereas twice the gain of a single 8-wavelength wire would be only approximately 9 db.

The two wires of the "V" must be fed out of phase, for correct operation. A resonant line may simply be attached to the ends, as shown in Fig. 1037. Alternatively, a quarter-wave matching section may be employed and the antenna fed through a non-resonant line (§ 10-8). If the antenna wires are made multiples of a half wave in length (use Equation 10, § 10-9, for computing the length), the matching section will be closed at the free end.

The rhombic antenna — The horizontal rhombic or "diamond" antenna is shown in Fig. 1039. Like the "V," it requires a good deal of space for erection, but it is capable of giving excellent gain and directivity. It also can be used for multi-band operation. In the terminated form shown in Fig. 1039, it operates like a non-resonant transmission line, without standing waves, and is unidirectional. It may also be used without the terminating resistor,

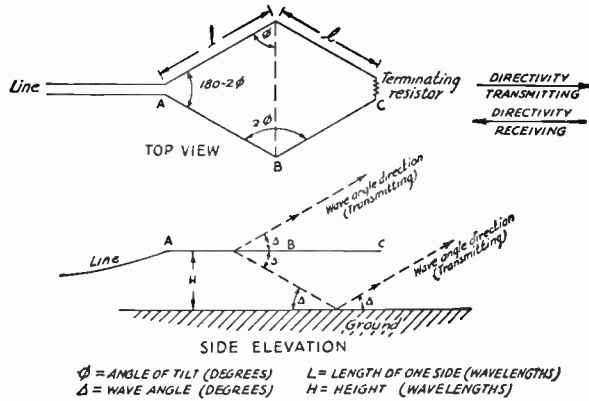


Fig. 1039 — The horizontal rhombic or diamond antenna, terminated. Important design dimensions are indicated; details in text.

in which case there are standing waves on the wires and the antenna is bidirectional.

The important quantities influencing the design of the rhombic antenna are shown in Fig. 1039. While several design methods may be used, the one most applicable to the conditions existing in amateur work is the so-called "compromise" method. The chart of Fig. 1040 gives design information based on a given length and wave angle to determine the remaining optimum dimensions for best operation. Curves for values of length of 2, 3 and 4 wavelengths are shown, and any intermediate values may be interpolated.

With all other dimensions correct, an increase in length causes an increase in power gain and a slight reduction in wave angle. An increase in height also causes a reduction in wave angle and an increase in power gain, but not to the same extent as a proportionate increase in length. For multiband work, it is satisfactory to design the rhombic antenna on the basis of 14-Mc. operation, which will permit work from the 7- to the 28-Mc. bands as well.

A value of 800 ohms is correct for the terminating resistor for any properly constructed rhombic, and the system behaves as a pure resistive load under this condition. The terminating resistor must be capable of safely dissipating one-half the power output (to eliminate the rear pattern), and should be noninductive. Such a resistor may be made up from a carbon or graphite rod or from a long 800-ohm transmission line using resistance wire. If the carbon rod or a similar form of lumped resistance is used, the device should be suitably protected from weather effects, i.e., it should be covered with a good asphaltic compound and sealed in a small, light-weight box or fibre tube. Suitable nonreactive terminating resistors are also available commercially.

For feeding the antenna, the antenna impedance will be matched by an 800-ohm line, which may be constructed


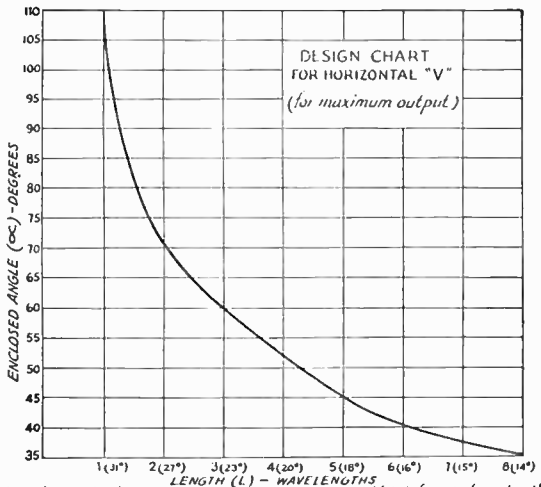


Fig. 1038 — Design chart for horizontal "V" antennas, giving the enclosed angle between sides vs. the length of the wires.

Fig. 1010 — Compromise-method design chart for rhombic antennas of various leg lengths and wave angles. The following examples illustrate the use of the chart:

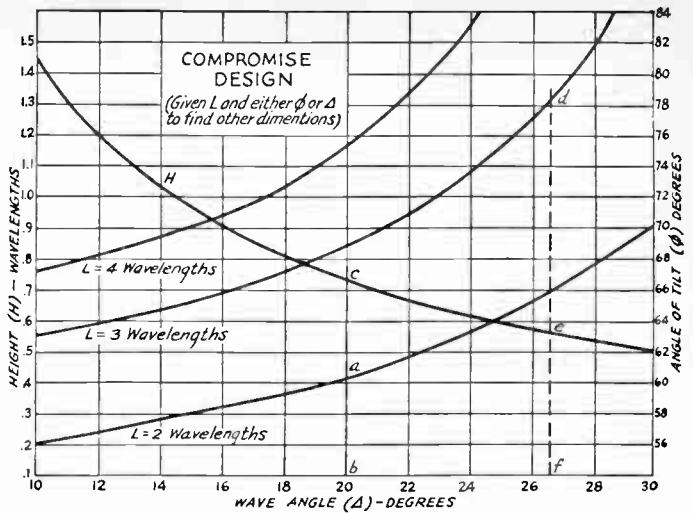
- (1) Given:
 Length (L) = 2 wavelengths.
 Desired wave angle (Δ) = 20° .
 To Find: H, ϕ .
 Method:
 Draw vertical line through point *a* (L = 2 wavelengths) and point *b* on abscissa ($\Delta = 20^\circ$). Read angle of tilt (ϕ) for point *a* and height (H) from intersection of line *ab* at point *c* on curve H.
 Result:
 $\phi = 60.5^\circ$.
 H = 0.73 wavelength.
- (2) Given:
 Length (L) = 3 wavelengths.
 Angle of tilt (ϕ) = 78° .
 To Find: H, Δ .
 Method:
 Draw a vertical line from point *d* on curve L = 3 wavelengths at $\phi = 78^\circ$. Read intersection of this line on curve H (point *e*) and intersection at point *f* on the abscissa for Δ .
 Result:
 H = 0.56 wavelength.
 $\Delta = 26.6^\circ$.



from No. 16 wire spaced 20 inches or from No. 18 wire spaced 16 inches. The 800-ohm line is somewhat ungainly to install, however, and may be replaced by an ordinary 600-ohm line with only a negligible mismatch. Alternatively, a matching section may be installed between the antenna terminals and a low-impedance line. However, when such an arrangement is used, it will be necessary to change the matching-section constants for each different band on which operation is contemplated.

The same design details apply to the unterminated rhombic as to the terminated type. When used without a terminating resistor, the system is bidirectional. Resonant feeders are preferable for the unterminated rhombic. A non-resonant line may be used by incorporating a matching section at the antenna, but is not readily adaptable to multiband work.

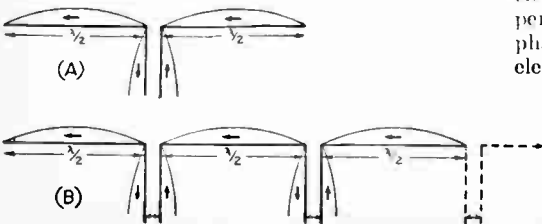Rhombic antennas will give a power gain of 8 to 12 db. or more for leg lengths of two to four wavelengths, when constructed according to the charts given. In general, the larger the antenna, the greater the power gain.



10-12 Directive Arrays with Driven Elements

Principles — By combining individual half-wave antennas into an *array* with suitable spacing between the antennas (called *elements*) and feeding power to them simultaneously, it is possible to make the radiated fields from the individual elements add in a favored direction, thus increasing the field strength in that direction as compared to that produced by one antenna element alone. In other directions the fields will more or less oppose each other, giving a reduction in field strength. Thus a power gain in the desired direction is secured at the expense of a power reduction in other directions.

Besides the spacing between elements, the instantaneous direction of current flow (*phase*) in individual elements determines the directivity and power gain. There are several methods of arranging the elements. If they are strung end to end, so that all lie on the same straight line, the elements are said to be *collinear*. If they are parallel and all lying in the same plane, the elements are said to be *broadside* when the phase of the current is the same in all, and *end-fire* when the currents are not in phase. Elements which receive power from the transmitter through the transmission line are called *driven elements*.

The power gain of a directive system increases with the number of elements. The proportionality between gain and number of elements is not simple, however. The gain depends upon the effect which the spacing and phasing has upon the radiation resistance of the elements, as well as upon their number.

Fig. 1011 — Collinear half-wave antennas in phase. The system at A is generally known as "two half waves in phase." B is an extension of the system; in theory the number of elements may be carried on indefinitely, but practical considerations usually limit the elements to four.

Collinear arrays—Simple forms of collinear arrays, with the current distribution, are shown in Fig. 1041. The two-element array at A is popularly known as “two half waves in phase.” It will be recognized as simply a center-fed antenna operated at its second harmonic. The way in which the number of elements may be extended for increased directivity and gain is shown in Fig. 1041-B. Note that quarter-wave transmission lines are used between each element; these give the reversal in phase necessary to make the currents in

Spacing between centers of adjacent half waves	Number of half waves in array vs. gain in db.				
	2	3	4	5	6
$\frac{1}{2}$ Wave	1.8	3.3	4.5	5.3	6.2
$\frac{3}{4}$ Wave	3.2	4.8	6.0	7.0	7.8

individual antenna elements all flow in the same direction at the same instant. Another way of looking at it is to consider that the whole system is a long wire, with alternate half-wave sections folded so that they do not radiate. Any phase-reversing section may be used as a quarter-wave matching section for attaching a nonresonant feeder (§ 10-8), or a resonant transmission line may be substituted for any of the quarter-wave sections. Also, the antenna may be end-fed by any of the systems previously described (§ 10-7, 10-8), or any element may be center-fed. It is best to feed at the center of the array, so that the energy will be distributed as uniformly as possible among the elements.

The gain and directivity depend upon the number of elements and their spacing, center-to-center. This is shown by Table III. Although $\frac{3}{4}$ -wave spacing gives greater gain, it is difficult to construct a suitable phase-reversing system when the ends of the antenna elements are widely separated. For this reason, the half-wave spacing is most generally used in actual practice.

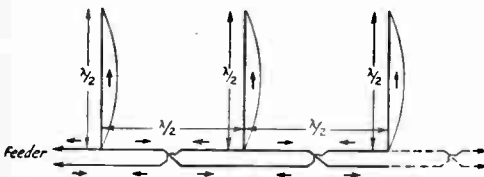


Fig. 1042 — Broadside array using parallel half-wave elements. Arrows indicate the direction of current flow. Transposition of the feeders is necessary to bring the antenna currents in phase. Any reasonable number of elements may be used. The array is bidirectional, with maximum radiation “broadside” or perpendicular to the plane of the antennas (perpendicularly through this page).

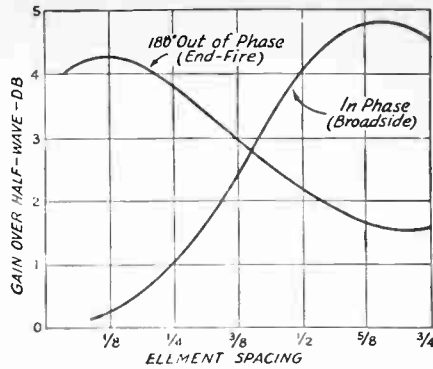


Fig. 1043 — Gain vs. spacing for two parallel half-wave elements combined as either broadside or end-fire arrays.

Collinear arrays may be mounted either horizontally or vertically. Horizontal mounting gives increased horizontal directivity, while the vertical directivity remains the same as for a single element at the same height. Vertical mounting gives the same horizontal pattern as a single element, but concentrates the radiation at low angles. It is seldom practicable to use more than two elements vertically at frequencies below 14 Mc. because of the excessive height required.

No. of elements	Gain
2	4 db.
3	5.5 db.
4	7 db.
5	8 db.
6	9 db.

Broadside arrays—Parallel antenna elements with currents in phase may be combined as shown in Fig. 1042 to form a *broadside* array, so named because the direction of maximum radiation is broadside to the plane containing the antennas. Again the gain and directivity depend upon the number of elements and the spacing, the gain for different spacings being shown in Fig. 1043. Half-wave spacing generally is used, since it simplifies the problem of feeding the system when the array has more than two elements. Table IV gives theoretical gain as a function of the number of elements with half-wave spacing.

Broadside arrays may be suspended either with the elements all vertical or with them horizontal and one above the other (*stacked*). In the former case the horizontal pattern becomes quite sharp, while the vertical pattern is the same as that of one element alone. If the array is suspended horizontally, the horizontal pattern is equivalent to that of one element

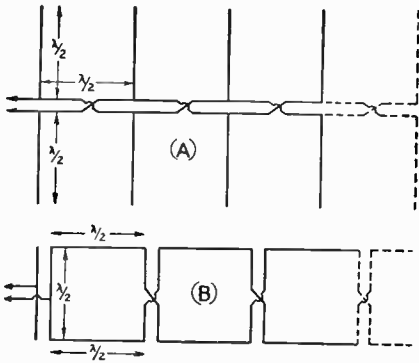


Fig. 1044 — Combination broadside and collinear arrays. A, with vertical elements; B, with horizontal elements. Both arrays give low-angle radiation. Two or more sections may be used. The gain in db. will be equal, approximately, to the sum of the gain for one set of broadside elements (Table IV) plus the gain of one set of collinear elements (Table III). For example, in A each broadside set has four elements (gain 7 db.) and each collinear set two elements (gain 1.8 db.), giving a total gain of 8.8 db. In B, each broadside set has two elements (gain 4 db.) and each collinear set three elements (gain 3.3 db.), making the total gain 7.3 db. The result is not strictly accurate, because of mutual coupling between the elements, but is good enough for practical purposes.

while the vertical pattern is sharpened, giving low-angle radiation.

Broadside arrays may be fed either by resonant transmission lines (§ 10-7) or through quarter-wave matching sections and non-resonant lines (§ 10-8). In Fig. 1042, note the "crossing over" of the feeders, which is necessary to bring the elements in proper phase relationship.

Combined broadside and collinear arrays

— Broadside and collinear arrays may be combined to give both horizontal and vertical directivity, as well as additional gain. The general plan of constructing such antennas is shown in Fig. 1044. The lower angle of radiation resulting from stacking elements in the vertical plane is desirable at the higher frequencies. In general, doubling the number of elements in an array by stacking will raise the gain from 2 to 4 db., depending upon whether vertical or horizontal elements are used — that is, whether the stacked elements are of the broadside or collinear type.

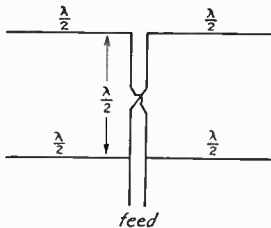


Fig. 1045 — A four-element combination broadside-collinear array, popularly known as the "lazy H" antenna. A closed quarter-wave stub may be used at the feed point to match into a 600-ohm transmission line, or resonant feeders may be attached at the point indicated. The gain over a half-wave antenna is 5 to 6 db.

The arrays in Fig. 1044 are shown fed from one end, but this is not especially desirable in the case of large arrays. Better distribution of energy between elements, and hence better all-around performance, will result when the feeders are attached as nearly as possible to the center of the array. Thus, in the 8-element array at A, the feeders could be introduced at the middle of the transmission line between the second and third set of elements, in which case the connecting line would not be transposed. Alternatively, the antenna could be constructed with the transpositions as shown and the feeder connected between the adjacent ends of either the second or third pair of collinear elements.

A four-element array of the general type shown in Fig. 1044-B, known as the "lazy H" antenna, has been quite frequently used. This arrangement is shown, with the feed point indicated, in Fig. 1045.

End-fire arrays — Fig. 1046 shows a pair of parallel half-wave elements with currents out of phase. This is known as an *end-fire* array, because it radiates best along the line of the antennas, as shown.

The end-fire array may be used either vertically or horizontally (elements at the same height), and is well adapted to amateur work because it gives maximum gain with relatively close element spacing. Fig. 1043 shows how the gain varies with spacing. End-fire elements may be combined with additional collinear and

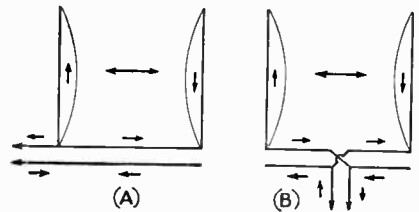


Fig. 1046 — End-fire arrays — using parallel half-wave elements. The elements are shown with half-wave spacing to illustrate feeder connections. In practice, closer spacings are desirable, as shown by Fig. 1043. Direction of maximum radiation is shown by the large arrows.

broadside elements to give a further increase in gain and directivity.

Either resonant or nonresonant lines may be used with this type of array. Nonresonant lines preferably are matched to the antenna through a quarter-wave matching section (§ 10-8).

Checking phasing — Figs. 1044 and 1046 illustrate a point in connection with feeding a phased antenna system which sometimes is confusing. In Fig. 1046, when the transmission line is connected as at A there is no cross-over in the line connecting the two antennas, but when the transmission line is connected to the center of the connecting line the cross-over becomes necessary (B). This is because in B the two halves of the connecting line are simply *branches* of the same line. In other

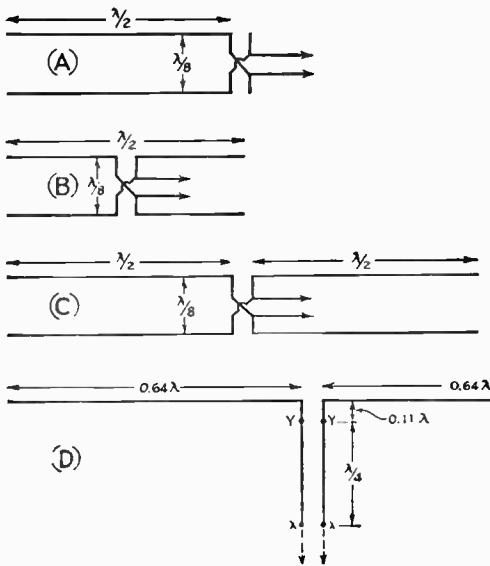


Fig. 1047 — Simple directive antenna systems. A is a two-element end-fire array; B is the same array with center feed, which permits use of the array on the second harmonic, where it becomes a four-element array with quarter-wave spacing. C is a four-element end-fire array with $\lambda/2$ spacing. D is a simple two-element broadside array using extended in-phase antennas ("extended double-Zepp"). The gain of A and B is slightly over 1 db. On the second harmonic, B will give about 5 db. gain. With C, the gain is approximately 6 db., and with D, approximately 3 db. In A, B and C, the phasing line contributes about 1/10th wavelength to the transmission line; when B is used on the second harmonic, this contribution is $1/8$ wavelength. Alternatively, the antenna ends may be bent to meet the transmission line, in which case each feeder is simply connected to one antenna. In D, points Y-Y' indicate a quarter-wave point (high current) and X-X' a half-wave point (high voltage). The line may be extended in multiples of quarter waves, if resonant feeders are to be used. A, B, and C may be suspended on wooden spreaders. The plane containing the wires should be parallel to the ground.

words, even though the connecting line in B is a half wave in length, it is not actually a half-wave line but *two quarter-wave lines in parallel*. The same thing is true of the untransposed line of Fig. 1044. Note that, under these conditions, the antenna elements are in phase when the line is not transposed, and out of phase when the transposition is made. The opposite is the case when the half-wave line simply joins two antenna elements and does not have the feed line connected to its center, as in Fig. 1042.

Adjustment of arrays — With arrays of the types just described, using half-wave spacing between elements, it will usually suffice to make the length of each element that given by the equation for a half-wave antenna in § 10-2, while the half-wave phasing lines between the parallel elements can be calculated from the formula:

$$\text{Length of half-wave line (feet)} = \frac{492 \times 0.975}{\text{Freq. (Mc.)}} = \frac{480}{\text{Freq. (Mc.)}}$$

The spacing between elements can be made equal to the length of the phasing line. No special adjustments of line or element length or spacing are needed, provided the formulas are followed carefully.

With collinear arrays of the type shown in Fig. 1041-B, the same formula may be used for the element length while the quarter-wave phasing section can be calculated from Equation 7 (§ 10-5). If the array is fed at its center it should not be necessary to make any particular adjustments, although, if desired, the whole system can be resonated by connecting an r.f. ammeter in the shorting link on each phasing section and moving the link back and forth to find the maximum current position. This refinement is hardly necessary in practice, however, so long as all elements are the same length and the system is symmetrical.

Simple arrays — Several simple directive antenna systems using driven elements have achieved rather wide use among amateurs. Four of these systems are shown in Fig. 1047. Tuned feeders are assumed in all cases; however, a matching section (§ 10-8) readily can be substituted if a nonresonant transmission line is preferred. Dimensions given are in terms of wavelength; actual lengths can be calculated from the equations in § 10-2 for the antenna and from Equation 7 (§ 10-5) for the resonant transmission line or matching section. In cases where the transmission-line proper connects to the mid-point of a phasing line, only half the length of the latter should be added to the line to find the quarter-wave point.

At A and B are two-element end-fire arrangements using close spacing. They are electrically equivalent; the only difference is in the method of connecting the feeders. B may also be used as a four-element array on the second harmonic, although the spacing is not quite optimum (Fig. 1043) for such operation.

A close-spaced four-element array is shown at C. It will give about 2 db. more gain than the two-element array.

The antenna at D, commonly known as the "extended double Zepp," is designed to take advantage of the greater gain possible with collinear antennas having greater than half-wave center-to-center spacing, but without introducing feed complications. The elements are made longer than a half wave in order to bring this about. The gain is 3 db. over a single half-wave antenna, and the broadside directivity is quite sharp.

The antennas of A and B may be mounted either horizontally or vertically; horizontal suspension (with the elements in a plane parallel to the ground) is recommended, since this tends to give low-angle radiation without an unduly sharp horizontal pattern. Thus these systems are useful for coverage over a wide horizontal angle. The system at C, when mounted horizontally, will have a sharper horizontal pattern than the two-element arrays.

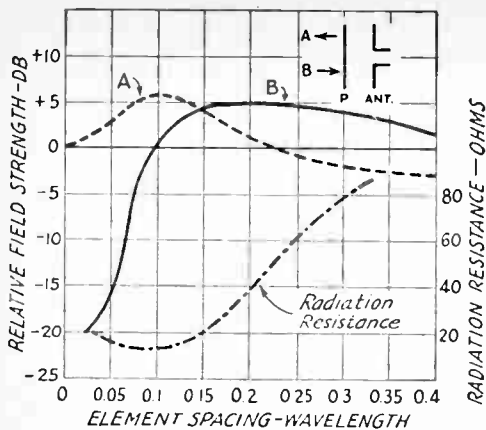


Fig. 1048 — Gain vs. element spacing for an antenna and one parasitic element. The reference point, 0 db, is the field strength from a half-wave antenna alone. The greatest gain is in direction A at spacings of less than 0.14 wavelength, and in direction B at greater spacings. The front-to-back ratio is the difference in db. between curves A and B. Variation in radiation resistance of the driven element also is shown. These curves are for a self-resonant parasitic element. At most spacings the gain as a reflector can be increased by slight lengthening of the parasitic element; the gain as a director can be increased by shortening. This also improves the front-to-back ratio.

10-13 Directive Arrays with Parasitic Elements

Parasitic excitation — The antenna arrays described in § 10-12 are bidirectional; that is, they will radiate in directions both to the "front" and to the "back" of the antenna system. If radiation is wanted in only one direction (for instance, north only, instead of north-south), it is necessary to use different element arrangements. In most of these arrangements the additional elements receive power by induction or radiation from the driven element, generally called the "antenna," and re-radiate it in the proper phase relationship to achieve the desired effect. These elements are called *parasitic* elements, as contrasted to the driven elements which receive power directly from the transmitter through the transmission line.

The parasitic element is called a *director* when it reinforces radiation on a line pointing to it from the antenna, and a *reflector* when the reverse is the case. Whether the parasitic element is a director or reflector depends upon the parasitic element tuning (which usually is adjusted by changing its length), and, particularly when the element is self-resonant, upon the spacing between it and the antenna.

Gain vs. spacing — The gain of an antenna-reflector or an antenna-director combination varies chiefly with the spacing between the elements. The way in which gain varies with spacing is shown in Fig. 1048. For the special case of self-resonant parasitic elements. This chart also shows how the attenuation to the "rear" varies with spacing. The same spacing does not necessarily give both maximum forward gain and maximum backward attenua-

tion. Backward attenuation is desirable when the antenna is used for receiving, since it greatly reduces interference coming from the opposite direction to the desired signal.

Element lengths — The antenna length is given by the formulas in § 10-2. The director and reflector lengths must be determined experimentally for maximum performance. The preferable method is to aim the antenna at a receiver a mile or more distant and have an observer check the signal strength (on the receiver "S" meter) while the reflector or director is adjusted a few inches at a time, until the length which gives maximum signal is found. The attenuation may be similarly checked, the length being adjusted for minimum signal. In general, for best front-to-back ratio the length of a director will be about 4 per cent less than that of the antenna. The reflector will be about 5 per cent longer than the antenna.

Simple systems: the rotary beam — Four practical combinations of antenna, reflector and director elements are shown in Fig. 1049. Spacings which give maximum gain or maximum front-to-back ratio (ratio of power radiated in the desired direction to power radiated in the opposite direction) may be taken from Fig. 1048. In the chart, the front-to-back ratio in db. will be the sum of gain and attenuation at the same spacing.

Systems of this type are popular for rotary-beam antennas, where the entire antenna system is rotated, to permit its gain and directiv-

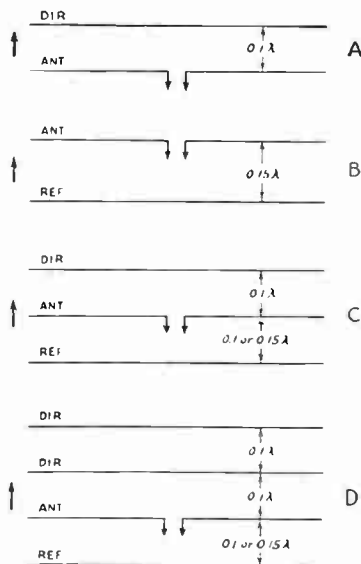


Fig. 1049 — Half-wave antennas with parasitic elements. A, with reflector; B, with director; C, with both director and reflector; D, two directors and one reflector. Gain is approximately as shown by Fig. 1048, in the first two cases, and depends upon the spacing and length of the parasitic element. In the three- and four-element arrays a reflector spacing of 0.15 wavelength will give slightly more gain than 0.1-wavelength spacing. Arrows show direction of maximum radiation. The array should be mounted horizontally (top views are shown).

ity to be utilized for any compass direction. They may be mounted either horizontally (with the plane containing the elements parallel to the earth) or vertically.

Arrays using more than one parasitic element, such as those shown at C and D in Fig. 1049, will give more gain and directivity than is indicated for a single reflector and director by the curves of Fig. 1048. The gain with a properly adjusted three-element array (antenna, director and reflector) will be 5 to 7 db. over a half-wave antenna. Somewhat higher gain still can be secured by adding a second director to the system, making a four-element array. The front-to-back ratio is correspondingly improved as the number of elements is increased.

The elements in close-spaced (less than one-quarter wavelength element spacing) arrays preferably should be made of tubing of one-half to one-inch diameter, both to reduce the ohmic resistance (§ 10-2) of the conductors and to secure mechanical rigidity. If the elements are free to move with respect to each other, the array will tend to show detuning effects under windy conditions.

Feeding close-spaced arrays — While any of the usual methods of feed may be applied to the driven element of a parasitic array, the fact that, with close spacing, the radiation resistance as measured at the center of the driven element drops to a very low value makes some systems more desirable than others. The preferred methods are shown in Fig. 1050. Resonant feeders are not recommended for lengths greater than a half wavelength.

The quarter- or half-wave matching stubs shown at A and B in Fig. 1050 preferably should be constructed of tubing with rather close spacing, in the manner of the "Q" section. This lowers the impedance of the matching section and makes the position of the line taps somewhat less difficult to determine accurately. The line adjustment should be made only with the parasitic elements in place, and after the correct element lengths have been determined, it should be checked to compensate for changes likely to occur because of element tuning. The procedure is the same as that described in § 10-8.

The concentric-line matching section at C will work with fair accuracy into a close-spaced parasitic array of 2, 3 or 4 elements without necessity for adjustment. The line is used as an impedance-inverting transformer, and, if its characteristic impedance is 70 ohms, it will give an exact match to a 600-ohm line when the resistance at the termination is about 8.5 ohms. Over a range of 5 to 15 ohms the mismatch, and therefore the standing-wave ratio, will be less than 2 to 1. The length of the quarter-wave section may be calculated from Equation 7 (§ 10-5).

The delta matching transformer shown at D is an excellent arrangement for parasitic arrays, and is probably easier to install, mechanically, than any of the others. The positions of

the taps (dimension a) must be determined experimentally, along with the length, b , by checking the standing-wave ratio on the line as adjustments are made. Dimension b should be about 15 per cent longer than a .

Sharpness of resonance — Peak performance of a multi-element directive array depends upon proper phasing or tuning of the elements, which in all but the simplest systems can be exact for one frequency only. However, there is some latitude, and most arrays will work well over a relatively narrow region such as the 14 Mc. band. If frequencies in all parts of the band are to be used, the antenna system should be designed for the mid-frequency; on the other hand, if only one frequency in the band will be used for the greater portion of the time, the antenna might be designed for that frequency and some degree of misadjustment tolerated on the occasionally used spare frequencies.

When reflectors or directors are used the tolerance is usually less than in the case of driven elements, partly because the parasitic-element lengths are fixed and the operation may change appreciably as the frequency passes from one side of resonance to the other, and partly be-

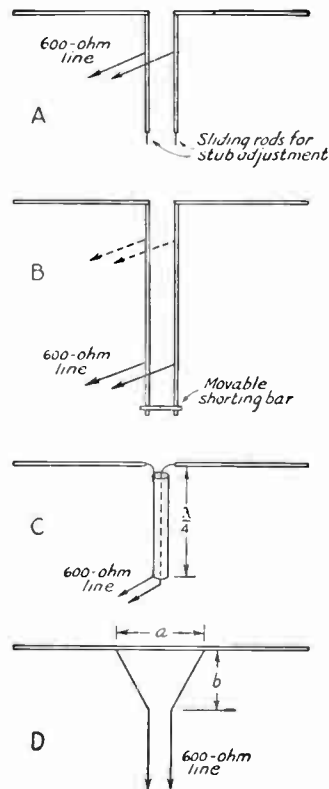


Fig. 1050 — Recommended methods of feeding the driven antenna element in close-spaced parasitic arrays. The parasitic elements are not shown. A, quarter-wave open stub; B, half-wave closed stub; C, concentric-line quarter-wave matching section; D, delta matching transformer. Adjustment details are discussed in the text.

cause the close spacing ordinarily used results in a sharp-tuning system. With parasitic elements, operation should be confined to a small region about the frequency for which the antenna is adjusted if peak performance is to be secured.

Combination arrays—It is possible to combine parasitic elements with driven elements to form arrays composed of collinear driven and parasitic elements and combination broadside-collinear-parasitic elements. Thus two or more collinear elements might be provided with a collinear reflector or director set, one parasitic element to each driven element. Or both directors and reflectors might be used. A broadside-collinear array could be treated in the same fashion.

When combination arrays are built up, a rough approximation of the gain to be expected may be obtained by adding the gains for each type of combination. Thus the gain of two broadside sets of four collinear arrays with a set of reflectors, one behind each element, at quarter-wave spacing for the parasitic elements, would be estimated as follows: From Table III, the gain of four collinear elements is 4.5 db. with half-wave spacing; from Fig. 1043 or Table IV, the gain of two broadside elements at half-wave spacing is 4.0 db.; from Fig. 1048, the gain of a parasitic reflector at quarter-wave spacing is 4.5 db. The total gain is then the sum, or 13 db. for the sixteen elements. Note that using two sets of elements in broadside is equivalent to using two elements, so far as gain is concerned; similarly with sets of reflectors, as against one antenna and one reflector. The actual gain of the combination array will depend, in practice, upon the way in which the power is distributed between the various elements and upon the effect which mutual coupling between elements has upon the radiation resistance of the array, and may be somewhat higher or lower than the estimate.


A great many directive antenna combinations can be worked out by combining elements according to these principles.

¶ 10-14 Miscellaneous Antenna Systems

Grounded antenna—The grounded antenna is used almost exclusively for 1.75-Mc. work, where the length required for a half-wave antenna would be excessive for most locations. An antenna worked "against ground" need be only a quarter-wave long, approximately, because the earth acts as an electrical "mirror" which supplies the missing quarter wave. The current is maximum at the ground connection with a quarter-wave antenna, just as it is at the center of a half-wave antenna.

On 1.75 Mc. the most useful radiation is from the vertical part of the antenna, since vertically polarized waves are characteristic of ground-wave transmission. It is therefore desirable to make the down-lead as nearly verti-

Fig. 1051—Typical grounded antenna for 1.75 Mc., consisting of a vertical section and a horizontal section having a total length (including the ground lead, if the latter is more than a few feet long) of one-quarter wavelength. Coil L should have about 20 turns of No. 12 wire on a 3-inch diameter form, tapped every two or three turns for adjustment. C is a 250 to 500 $\mu\text{fd.}$ variable. The coupling between L and the final tank coil should be variable.

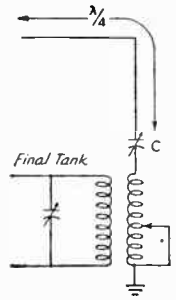

cal as possible, and also as high as possible. This gives low-angle sky-wave transmission, which is most useful for long-distance work at night, in addition to a good ground wave for local work. The horizontal portion contributes to high-angle sky-wave transmission, which is useful for covering short distances on this band at night.

Fig. 1051 shows a grounded antenna with the top folded to make the length equal to a quarter wave. The antenna coupling apparatus consists of the coil L , tuned by the series condenser, C , with L inductively coupled to the transmitter tank circuit (§ 10-4, 10-6).

For computation purposes, the *over-all* length of a grounded system is given by

$$\text{Length (feet)} = \frac{236}{f \text{ (Mc.)}}$$

This is the *total* length from the far end of the antenna to the ground connection. The length is not critical, since departures of the order of 10 to 20 per cent can be compensated by the tuning apparatus.

The ground should preferably be one with conductors buried deep enough to reach natural moisture. In urban locations, good grounds can be made by connecting to the water mains where they enter the house; the pipe should be scraped clean and a low-resistance connection made with a tightly fastened ground clamp. If no water supply pipes are available, several rods or pipes six to eight feet long may be driven into the ground at intervals of six or eight feet, all being connected together. The transmitter should be located so as to make the ground lead as short as possible.

In locations where it is impossible to secure a good ground connection, because of sandy soil or other considerations, it is preferable to use a counterpoise or capacity ground instead of an actual ground connection. The counterpoise consists of a system of wires, insulated from ground and running horizontally above the earth beneath the antenna. The counterpoise should have a sufficient number of wires of sufficient length to cover well the area immediately under the antenna. The wires may be formed into any convenient shape; i.e., they may be spread out fan-shape, in a radial pattern, or as three or more parallel wires sepa-

rated a few feet and running beneath the antenna. The counterpoise may be elevated six feet or so above the ground, so that it will not interfere with persons walking under it. A low-resistance connection should be made between the usual ground terminal of the transmitter and each of the wires in the counterpoise.


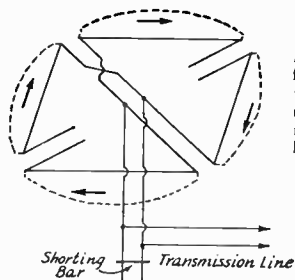


Fig. 1052 — The Alford loop antenna for v.h.f. and u.h.f., made up of resonant elements fed in phase, has high radiation efficiency.

Fig. 1053 — Various feed and phasing arrangements may be used with v.h.f. loops. The shorted ends of the closed quarter-wave matching stubs may be grounded to a metal mast or other support.

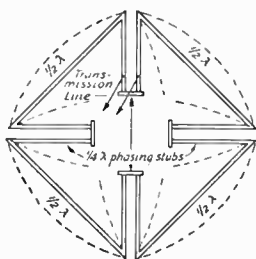

Loaded antennas — Methods of securing maximum usable radiation from a grounded vertical antenna of limited height utilize loading coils and capacity tops. The latter may be in the form of a ring or spider or a top-mounted outrigger. Capacity effect raises the maximum current point nearer the top of the antenna.

Another form of top loading which involves the insertion of an inductance coil near the top, enclosed within a shield can for protection and to increase the top capacity, is particularly suited to mobile installations.

The advantage of top loading in short vertical antennas is that it forces the upper portion of the antenna to carry a more substantial current, making the effective height approach more closely to the actual physical height.

V.h.f. loop antennas — Although the radiation resistance of an ordinary loop transmitting antenna is very low, at the very-high frequencies, the Alford loop shown in Fig. 1053 permits the use of resonant dimensions of the order of $\frac{1}{8}$ to $\frac{1}{4}$ wavelength on each side, resulting in relatively high radiation efficiency as compared with ordinary loop antennas for the lower frequencies.

Various configurations and feed methods are possible, following this general pattern. In the form shown in Fig. 1054, the sides of the loop are half-wave resonant sections linked by quarter-wave transmission-line matching stubs so arranged that there is a current loop at the center of each side, with the currents in the various sections all in phase. Since the shorted ends of the quarter-wave stubs are at a voltage

node, the system may be directly attached at these points to a grounded metal tower or similar structure.

Center-fed dipoles with low impedance coaxial lines or delta-matched lines may be used, the correct phasing for each line being arranged at the feed-line terminals.

“J” antenna — This type of antenna, frequently used on the very-high frequencies when vertical polarization is desired, is simply a half-wave radiator fed through a quarter-wave matching section (§ 10-8), the whole being mounted vertically as shown in Fig. 1054. Adjustment and tuning are as described in § 10-8. The bottom of the matching section, being at practically zero r.f. potential, can be grounded for lightning protection.

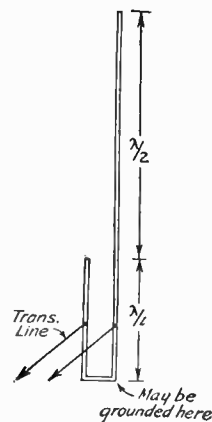


Fig. 1054 — The “J” antenna, usually constructed of hard-drawn metal tubing. The $\frac{3}{4}$ -wave vertical section may be mounted as an extension of a grounded metal mast. The matching stub may be adjusted by a sliding shorting bar.

Coaxial antenna — With the “J” antenna radiation from the matching section and the

transmission line tends to combine with the radiation from the antenna in such a way as to raise the angle of radiation. At v.h.f., the lowest possible radiation angle is essential, and the coaxial antenna shown in Fig. 1055 was developed to eliminate feeder radiation. The center conductor of a 70-ohm concentric transmission line is extended one quarter wave beyond the end of the line, to act as the upper half of a half-wave antenna. The lower half is provided by the quarter-wave sleeve, the upper end of which is connected to the outer conductor of the concentric line. The sleeve acts as a shield about the transmission line and very little current is induced on the outside of the line by the antenna field. The line is non-resonant, since its characteristic impedance is the same as the center impedance of the half-wave antenna (§ 10-2).

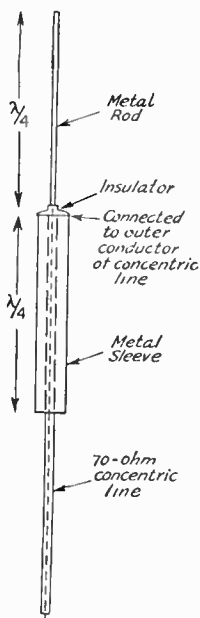


Fig. 1055 — Coaxial antenna. The insulated inner conductor of the 70-ohm concentric line is connected to the quarter-wave metal rod which forms the upper half of the antenna.

The sleeve may be made of copper or brass tubing of suitable diameter to clear the transmission line. The coaxial antenna is somewhat difficult to construct, but is superior to simpler systems in its performance at low radiation angles.

Turnstile antenna — The turnstile antenna consists of two half-wave radiators crossing each other at right angles and excited 90 degrees out of phase. A number of these are sometimes arranged in an array in which the individual turnstiles in a horizontal plane are spaced one above another at half-wave inter-

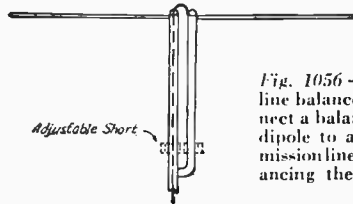


Fig. 1056 — A "bazooka" line balancer, used to connect a balanced center-fed dipole to a coaxial transmission line without unbalancing the antenna load.

vals. Such an array gives nearly uniform radiation in all horizontal directions together with directivity in a vertical plane.

Line balancing — A coaxial line connected to the center of a half-wave antenna introduces some unbalance because the outer conductor has higher capacity to ground than the inner. At lower frequencies this unbalance may not be important, but at v.h.f. and u.h.f. a small difference in capacity between the two halves of the antenna may have a considerable effect upon current distribution.

Proper balance may be restored by the use of a quarter-wave line section as shown in Fig. 1056. The outer conductor of the transmission line is duplicated by a quarter-wave section of the same diameter, the two being connected

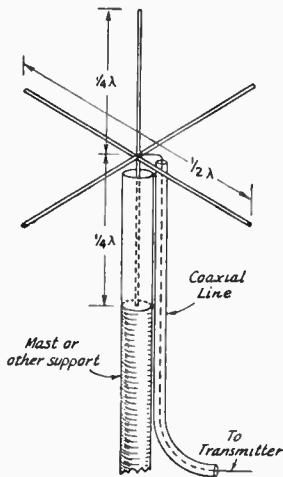


Fig. 1057 — The "ground-plane" antenna gives low vertical-angle radiation with a circular horizontal pattern. The quarter-wave mounting section of large-diameter tubing may be mounted on a metal mast or other support.

together at the bottom. The inner conductor of the line is connected to the extra tubing section and to the antenna as shown. This terminates both halves of the antenna in tubing of the same capacity. The quarter-wave section, when adjusted to resonance by the shorting bar at the bottom, has high impedance when viewed from the antenna terminals and therefore has no effect on the normal operation of the system.

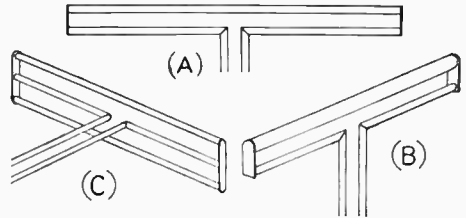


Fig. 1058 — Folded dipoles are an elementary form of broad-band antenna, simply constructed and easily fed.

Wide-band Antennas

Cylindrical antennas — Radiators such as are used for television and broad-band f.m. are of interest in amateur v.h.f. operation because they work at high efficiency without adjustment throughout the width of an amateur band.

At the very-high frequencies an ordinary dipole or equivalent antenna made of small wire is purely resistive only over a very small frequency range. Its Q, and therefore its selectivity, is sufficient to limit its optimum per-

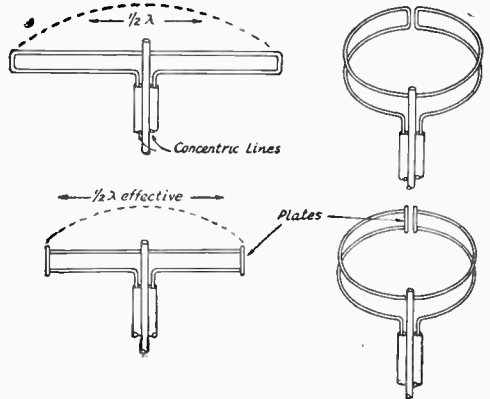


Fig. 1059 — The compact circular loop antenna is derived from a folded dipole by bending it into a circle. To reduce length and concentrate current distribution, capacity-loading end plates are added as in lower view. Circular loops may be stacked at one-half wavelength intervals for increased vertical directivity. Circular arrays of three or four folded dipoles, bent into 120° or 90° arcs and fed in phase are extensively used for u.h.f.

formance to a narrow frequency range, and readjustment of the length or tuning is required for each narrow slice of the spectrum. With tuned transmission lines, the effective length of the antenna can be shifted by retuning the whole system. However, in the case of antennas fed by matched-impedance lines, any appreciable frequency change requires an actual mechanical adjustment of the system. Otherwise the resulting mismatch with the line will be sufficient to cause a significant reduction in power input to the antenna.

A properly designed and constructed wide-band antenna, on the other hand, will exhibit very nearly constant input impedance over a range of several megacycles.

The simplest method of obtaining a broad-band characteristic is the use of what is termed

a "cylindrical" antenna. This is no more than a conventional doublet in which large-diameter tubing is used for the elements. The use of a relatively large diameter-to-length ratio lowers the Q of the antenna, thus broadening the resonance characteristic.

As the diameter-to-length ratio is increased, end effects also increase, with the result that the antenna must be made shorter than a thin-wire antenna resonating at the same frequency. The reduction factor may be as much as 20 per cent with the tubing sizes commonly used for amateur antennas at v.h.f.

Folded dipoles — A system combining the radiation characteristics of a half-wave antenna with the impedance-transforming properties of a quarter-wave line (§ 10-5) is shown in Fig.

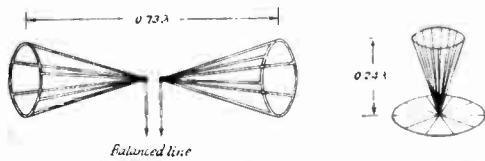


Fig. 1060 — Conical broad-band antennas have relatively constant impedance over a wide frequency range. The three-quarter wavelength dipole at left and the quarter-wave vertical with ground plane at right have the same input impedance — approximately 65 ohms. Sheet-metal or spine-type construction may be used.

1058-A. Essentially, it is a center-fed half-wave antenna with another half-wave element connected directly between its ends. The spacing between the two sections should be quite close — not more than a few per cent of the wavelength. As used at very-high frequencies, the spacing is of the order of an inch or two when the elements are constructed of metal tubing. The total required length around the loop may be calculated by Equation 10 (§ 10-9) for a total length of one wavelength.

The impedance at the terminals of the dipole is four times that of a half-wave antenna, or nearly 300 ohms, when the antenna conductors are both the same diameter. A 300-ohm line will therefore be nonresonant when the antenna is connected to its output end (§ 10-5), while the standing-wave ratio with a 600-ohm line will be only of the order of 2 to 1.

An exact match with a 600-ohm line can be obtained by either of two modifications. One is

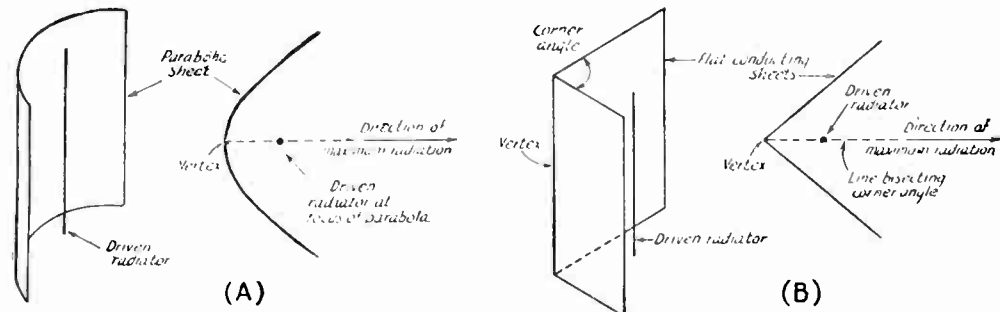


Fig. 1061 — Plane-sheet reflectors for v.h.f. and u.h.f. A shows a parabolic sheet and B a square-corner reflector.

to double the size of one of the elements, as shown in Fig. 1058-B; the other is to add an additional element in parallel, as in Fig. 1058-C.

Cone antennas — From the cylindrical antenna various specialized forms of broadly resonant radiators have been evolved, including the ellipsoid, spheroid, cone, diamond and double diamond. Of these, the conical antenna is perhaps the most interesting. With large angles of revolution the characteristic impedance can be reduced to a very low value suitable for extremely wide-band operation. The cone may be made up either of sheet metal or of multiple wire spines, as in Fig. 1060.

Plane Reflector Antennas

Plane-sheet reflectors — The small physical size of v.h.f. antennas makes practical many methods not feasible on lower frequencies. For example, a plane flat-sheet reflector may be used with a half-wave dipole, obtaining gains of 5 to 7 db. Much higher gains are attainable with a number of stacked dipoles, spaced $\frac{1}{4}$ or $\frac{3}{4}$ wave-length apart, and a larger reflecting sheet; such an arrangement is called a "billboard" array.

Plane reflectors need not be constructed of solid sheets. Wire mesh or a grid of a closely spaced parallel wire spines are not only more easily erected but offer less wind resistance.

Parabolic reflectors — Sheets formed into the shape of a section of a parabolic cylinder are used with a driven radiator situated at the focus as highly directive antenna systems. If the parabolic reflector is sufficiently large so that the distance to the focal point is a number of wavelengths, optical conditions are approached and the wave across the mouth of the reflector is a plane wave. However, if the reflector is of the same order of dimensions as the operating wavelength, or less, the driven radiator is appreciably coupled to the reflecting sheet and minor lobes occur in the pattern.

Plane sheets shaped to a parabolic curve are used to obtain high directivity in a single plane. With apertures of the order of 10 or 20 wavelengths, a beam width of 5° may be achieved.

A reflecting paraboloid must be carefully designed and constructed to obtain ideal performance. The antenna must be located at the focal point. The most desirable focal length of

TABLE V

Frequency Band	Length of Side	Length of Reflector Elements	Number of Reflector Elements	Spacing of Reflector Elements	Spacing of Driven Dipole to Vertex
224-230 Mc. (1 $\frac{1}{4}$ meter)	4' 2"	4' 7"	20	5"	2' 2"
112-116 Mc. (2 $\frac{1}{2}$ meter)	8' 4"	5' 2"	20	10"	4' 4"
112-116 Mc.* (2 $\frac{1}{2}$ meter)	6' 8"	5' 2"	16	10"	3' 6"
56-60 Mc. (5 meter)	16' 8"	10' 4"	20	1' 8"	8' 8"
56-60 Mc.* (5 meter)	13' 4"	10' 4"	16	1' 8"	6' 11"

Dimensions of square-corner reflector for the 224-, 112-, and 56-Mc. bands. Alternative designs are listed for the 112- and 56-Mc. bands. These designs, marked (*), have fewer reflector elements and shorter sides, but the effectiveness is only slightly reduced. There is no reflector element at the vertex in any of the designs.

the parabola is that which places the radiator along the plane of the mouth; this length is equal to one-half the mouth radius. At other focal distances interference fields may deform the pattern or cancel a portion of the radiation.

Corner reflector antenna — The "corner" reflector consists of two flat conducting sheets which intersect at a designated angle. The corner reflector antenna is particularly useful at v.h.f. where structures one or two wavelengths in maximum dimensions are more practical to build than larger systems.

The plane surfaces are set at an angle of 90°, with the antenna set on a line bisecting this angle. For maximum performance, the distance of the antenna from the vertex should be 0.5 wavelength, but compromise designs can be built with closer spacings (see Table V). The plane surfaces need not be solid sheets; spines spaced about 0.1 wavelength apart will serve as well. The spines do not have to be connected together electrically.

If the driven radiator is situated on a line bisecting the corner angle, as shown in Fig. 1061, maximum radiation is in the direction of this line. There is no focus point for the driven radiator, as with a parabolic reflector, and the radiator can be placed at a variety of positions along the bisecting line.

Corner angles larger than 90° can be used, with some decrease in gain. A 180° "corner" is equivalent to a single flat-sheet reflector. With angles smaller than 90°, the gain theoretically increases as the corner angle is decreased. However, to realize this gain the size of the reflecting sheets must also be increased.

At a spacing of 0.5 wavelength from the driven dipole to the vertex, the radiation resistance of the driven dipole is approximately twice the radiation resistance of the same dipole in free space. Smaller spacings of driven

dipole and vertex are practical, but at a slight sacrifice in efficiency. The alternative design for the 112- and 56-Mc. square-corner reflector in Table V has a dipole-to-vertex spacing of 0.4 wavelength. At this spacing the driven dipole radiation resistance is still somewhat higher than its free space value, but is considerably less than when the spacing is 0.5 wavelength.

Horn radiators — On the ultrahigh frequencies a metal horn can be used to guide and concentrate the wave in a sharp beam. Highest directivity is secured when the mouth of the horn has a dimension large compared with the wavelength. Factors governing the gain include flare angle, length and mouth diameter.

Various types of horn radiators include the simple *sectoral* horn, flared linearly in only one dimension; the *pyramidal* horn, flared in two dimensions; the *conical* horn, a section of a cone whose apex is terminated in a cylindrical wave guide or cylindrical coupling section; and the *biconical* horn, consisting of two cones joined back to back at the apex.

Receiving antennas — Nearly all of the properties possessed by an antenna as a radiator also apply when it is used for reception. Current and voltage distribution, impedance, resistance and directional characteristics are the same in a receiving antenna as if it were used as a transmitting antenna. This reciprocal behavior makes possible the design of a receiving antenna of optimum performance based on the same considerations that have been discussed for transmitting antennas.

The simplest receiving antenna is a wire of random length. The longer the wire, the more energy it abstracts from the wave. Because of the high sensitivity of modern receivers, a large antenna is not necessary for picking up signals at good strength. An indoor wire only 15 to 20 feet long will serve; although a longer wire outdoors is better.

The use of a tuned antenna improves the operation of the receiver, however, because the signal strength is raised more in proportion to the stray noises picked up than is the case with wires of random length. Since the transmitting antenna usually is given the best location, it can also be expected to serve best for receiving. This is especially true when a directive antenna is used, since the directional effects and power gain of directive transmitting antennas are the same for receiving as for transmitting. A change-over switch or relay, connected in the antenna leads, can be used to transfer the connections from the receiver to the transmitter.

In selecting a directional receiving antenna it is preferable to choose a type which gives very little response in all but the desired direction (small minor lobes). This is even more important than high gain in the desired direction, because the cumulative response to noise and unwanted-signal interference in the smaller lobes may offset the advantage of increased desired-signal gain.

Construction Practice

IN CONTRAST to the earlier days of amateur radio, when many components were obtainable only at prohibitive prices or not at all, the construction of a piece of equipment these days resolves itself chiefly into the proper assembly and wiring of manufactured components from the wide assortment available.

Tools

While an easier, and perhaps a better, job can be done with a greater variety of tools available, by taking a little thought and care it is possible to turn out a fine piece of equipment with only a few of the common hand tools. A list of tools which will be found indispensable in the construction of radio equipment will be found on this page. With these tools it should be possible to perform any of the required operations in preparing panels and metal chassis for assembly and wiring. A few additional tools will make certain operations easier, so it is a good idea for the amateur who does constructional work at intervals to add to his supply of tools from time to time. The following list will be found helpful in making a selection:

- Bench vise, 4-inch jaws.
- Tin shears, 10-inch, for cutting thin sheet metal.
- Taper reamer, 1/2-inch, for enlarging small holes.
- Taper reamer, 1-inch, for enlarging holes.
- Countersink for brace.
- Carpenter's plane, 8- to 12-inch, for wood-working.
- Carpenter's saw, cross-cut.
- Motor-driven emery wheel for grinding.
- Long-shank screwdriver with screw-holding clip for tight places.
- Set of "Spintite" socket wrenches for hex nuts.
- Set of small, flat, open-end wrenches for hex nuts.
- Wood chisel, 1/2-inch.
- Cold chisel, 1/2-inch.
- Wing dividers, 8-inch, for scribing circles.
- Set of machine-screw taps and dies.
- Folding rule, 6-foot.
- Dusting brush.

Several of the pieces of light woodworking machinery, often sold in hardware stores and mail-order retail stores, are ideal for amateur radio work, especially the drill press, grinding head, band and circular saws, and joiner. Although not essential, they are desirable for anyone in a position to acquire them.

Care of Tools

The proper care of tools is not alone a matter of pride to a good workman. He also realizes the energy which may be saved and the annoyance which may be avoided by the possession of well-kept, sharp-edged tools. A few minutes spent with the oil stone or emery wheel now and then will maintain the fine cutting edges of knives, drills, chisels, etc.

Drills should be sharpened at frequent intervals so that grinding is kept at a minimum each time. This makes it easier to maintain the rather critical surface angles required for best cutting with least wear. Occasional oil-stoning of the cutting edges of a drill or reamer will extend the time between grindings. Stoned cutting edges also will stand more feed and speed.

The soldering iron can be kept in good condition by keeping the tip well tinned with solder and not allowing it to run at full voltage for long periods when it is not being used. After each period of use, the tip should be removed and cleaned of any scale which may have accumulated. An oxidized tip may be cleaned by dipping it in sal ammoniac while hot and then wiping it clean with a rag. If the tip becomes pitted, it should be filed until smooth and bright, and then tinned by dipping it in solder.

All tools should be wiped occasionally with an oily cloth to prevent rust.

INDISPENSABLE TOOLS

- Long-nose pliers, 6-inch.
- Diagonal cutting pliers, 6-inch.
- Screwdriver, 6- to 7-inch, 1/4-inch blade.
- Screwdriver, 4- to 5-inch, 3/8-inch blade.
- Scratch awl or scriber for marking lines.
- Combination square, 12-inch, for laying out work.
- Hand drill, 1/4-inch chuck or larger, 2-speed type preferable.
- Electric soldering iron, 100 watts.
- Hacksaw, 12-inch blades.
- Center punch for marking hole centers.
- Hammer, ball peen, 1-lb. head.
- Heavy knife.
- Yardstick or other straight-edge.
- Carpenter's brace with adjustable hole cutter or socket-hole punches (see text).
- Pair of small C-clamps for holding work.
- Large, coarse, flat file.
- Large round or rat-tail file, 1/2-inch diameter.
- Three or four small and medium files—flat, round, half-round, triangular.
- Drills, particularly 1/4-inch and Nos. 18, 28, 33, 42 and 50.
- Combination oil stone for sharpening tools.
- Solder and soldering paste (non-corroding).
- Medium-weight machine oil.

☞ Useful Materials

Small stocks of various miscellaneous materials will be required in constructing radio apparatus, most of which are available from hardware or radio supply stores. A representative list follows:

$\frac{1}{2} \times 1/16$ -inch brass strip for brackets, etc. (half-hard for bending).

$\frac{1}{4}$ -inch square brass rod or $\frac{1}{2} \times \frac{1}{2} \times 1/16$ -inch angle brass for corner joints.

$\frac{1}{4}$ -inch diameter round brass rod for shaft extensions.

Machine screws: Round-head and flat-head, with nuts to fit. Most useful sizes: 4-36, 6-32 and 8-32, in lengths from $\frac{1}{4}$ -inch to $1\frac{1}{2}$ -inch. (Nickel-plated iron will be found satisfactory except in strong r.f. fields, where brass should be used.)

Bakelite and hard rubber scraps.

Soldering lugs, panel bearings, rubber grommets, terminal-lug wiring strips, varnished-cambrie insulating tubing.

Machine screws, nuts, washers, soldering lugs, etc., are most reasonably purchased in quantities of a gross.

☞ Construction Planning

The construction of any piece of radio equipment requires careful planning, proper coordination of parts, circuit and layout to achieve the desired result.

Equipment can be divided into three main classifications — experimental, temporary and permanent. Each class has its own peculiarities and limitations affecting design and constructional details.

Experimental equipment, such as the gear thrown together to investigate the possibilities of some newly published circuit, or an original idea, requires a simpler approach and less work than a unit to be used in the regular station. Experimental equipment may be built "bread-board" style on a board faced with a thin sheet of metal for grounding purposes, or even on an old chassis from the junk box. If the chassis has been previously used the old socket and screw holes may save time and effort. Random parts and a semi-makeshift arrangement can be used. Plenty of space for changes in wiring and components must be available. While temporary equipment such as a power supply built in an emergency, to replace a defective transmitter bias supply, does not require the same amount of planning and care in assembly as did the original bias supply, it should be attached firmly to the chassis and wired securely to prevent breakdowns. Connections should be soldered and safety precautions taken since it is difficult to anticipate the exact use or required length of service life of this type of equipment.

Permanent equipment requires the most careful planning and assembly since it must necessarily fit in with other units. Permanent

equipment consists of three main classes — fixed station, mobile and portable.

In fixed-station usage, several types of construction are available. For example, take the case of a proposed exciter power supply. Will this unit be made a permanent part of the exciter but not located adjacent to it; will it be removed and used as a source of power for some other equipment such as an experimental amplifier; or will it be constructed as an integral part of the exciter? The type of construction chosen for any given unit must depend on the foreseeable uses that will be made of it. Thus, in the case of the exciter power supply, if it is to be used with but not attached to the exciter, it should be packaged so it can be moved and connected to other equipment. For maximum utility, both screw-type terminals and plug- and socket-type connections should be available. If it is desirable to use the supply in the field such as on Field Day, it must be more sturdily built and should be provided with a protective cabinet or box.

If the exciter supply is made a permanent part of the exciter, its design must be coordinated with the exciter unit as a whole, a chassis of suitable size and form must be selected and a layout made to fit all the components into the available space.

In fixed-station applications, assemblies of small units built to conform with the available space may prove to have more convenience and utility than large masses of assembled parts, such as a cabinet type, in which it is extremely difficult to replace defective parts or to make changes readily. This type of equipment includes power supplies, volt-ohmmeter units, audio amplifiers and any type equipment which may have more than one use in or around the station. For example, if the speech amplifier were designed to be removed readily it could perform double duty as a public-address amplifier and used for a club "jam" session. This would be feasible, however, only if provisions were made for quick and easy removal, and connection to the normal gear. Such an amplifier should be built self-contained, with power supply, and terminated with plug-in type connectors to fit both the phonograph pick-up and the 'phone-rig connections. All multi-purpose equipment must be built solidly, readily demountable and with some system of universal connections.

The desirable features of portable equipment combine those of fixed and mobile station apparatus plus lightness and compactness. Portables are usually packaged in at least two units, one containing the transmitter-receiver (or transceiver) and the other, the power supply or source.

☞ Specialized Construction Technique

Mobile equipment must be laid out and assembled to prevent damage due to vibration and shock. In addition to the standard good practices of construction, mobile equipment

requires additional care in the mounting of components, the placement of parts to prevent detrimental heating effects and in the arrangement of the wiring. Heavy leads should be pre-formed to fit between the connecting points in order to prevent mechanical strain on the components. Fixed resistors and condensers should be fastened at both ends, clipping the wire leads short and attaching them to terminal strips or blocks, and large units should also be fastened at the center. Transformers should be securely bolted to the chassis, using bolts that fill the mounting holes in the transformer. Chassis should be solidly constructed of heavy metal. Ordinary chassis spot-welded in the corners will not be satisfactory for mobile sets. The chassis should be of the type in which the corners are bent over and securely riveted, then welded, and should have a lip at the bottom for rigidity. Cast chassis are usually excellent for mobile units. Cross-bracing of a chassis will strengthen it. Coils should be wound on rigid low-loss forms and securely mounted. For example, the output tank coil of a 50-Mc. transmitter can be wound on a solid grooved dielectric rod, which is then mounted vertically on the chassis, adjacent to the plate tank condenser, using one large-size brass machine screw. The antenna coil can be wound also on the same rod.

Detuning and loss of efficiency might result if, for example, the same coils were mounted directly on the terminals of their respective variable condensers without having a solid support and mounting.

Ground connections must not be spot-soldered to the chassis. Instead, they should be made to ground lugs or straps provided for that purpose. Lockwashers or locknuts must be used on all screws. Stranded hook-up wire, laced into cables and securely fastened down, has been found highly desirable in mobile sets.

The use of tube locks is almost imperative on any tubes except the smaller metal types (such as 6C5, 6H6, etc.). Certain common types of ceramic sockets require tube locks for all tubes. Fiber wafer sockets should be avoided because of their lack of mechanical strength and holding ability.

Mobile installations are affected by shock and vibration and every effort must be taken to prevent mechanical or electrical damage and to prevent parts from shaking loose. Special components such as variable condensers, coils and transformers are available for such use and should be included in this type of equipment.

In the construction of v.h.f. equipment many familiar practices must be discarded or modified. Actual physical relationships between components becomes extremely important since every inch of wire constitutes a tuned circuit and every condenser is also an inductance. Stray capacitance and inductance may lead to a loss of gain or sensitivity and

may cause detuning and instability. Grounds must be grouped and connected to definite points rather than indiscriminately to the chassis. Special by-pass technique is required since the condensers ordinarily employed for that purpose will not function in the same manner as on the lower frequencies. For example, the following table shows the approximate value of the usual postage-stamp condenser capacity which, together with the inductance of the leads, will be approximately self-resonant in the amateur bands shown. At signal frequencies, no greater by-pass capacity should be used (for an indicated lead length) than the one shown for the highest frequency to be covered.

Max. Frequency	Lead Length (total)			
	¼"	½"	1"	2"
28-30 Mc. . .	3000 μ fd.	2000 μ fd.	1000 μ fd.	500 μ fd.
56-60	750	500	350	150
112-116	200	150	75	40
224-230	80	40	20	10
448	15	8	4	—

Symmetry of push-pull circuits is essential in v.h.f., both from an electrical and a mechanical viewpoint.

Copper straps may be utilized for connections in place of straight copper wire, which has considerable inductance at the higher frequencies.

More effective by-pass condensers for v.h.f. may be made by attaching a square inch or so of flat copper or brass strip, insulated by mica or polystyrene, to the chassis, immediately adjacent to the connection to be by-passed.

Allowance must be made for the capacity and inductance of components, such as tube elements, leads, chassis, and metal shielding.

All joints must be soldered, using plenty of heat and care to ensure a good sweated joint.

Particular care must be taken to provide adequate conductor size where large r.f. currents are present such as in tuned lines.

All vibration and movement of components must be completely eliminated since the slightest change in capacity will affect the critical circuits. The elements in resonant cavities must be rigidly fastened.

Wire-wound resistors must be avoided in any circuit where r.f. is present. Carbon resistor values will not be reliable as the frequency is increased and the metallized-filament type resistor must be used where critical values are required.

Since the successful performance of v.h.f. equipment largely depends on the absence of stray and undesired capacities and inductance, extreme care must be taken in the mechanical as well as the electrical organization of the chassis. For example, the correct rotation of a socket may shorten an important tube lead as much as an inch — which may have enough inductance to resonate with the tube-element capacity at 500 Mc.

◀ Chassis Construction

With a few essential tools and proper procedure, it will be found that building radio gear on a metal chassis is no more of a chore than building with wood, and a more satisfactory job results.

The placing of components on the chassis is shown quite clearly in the photographs in this *Handbook*. Aside from certain essential dimensions, which usually are given in the text, exact duplication is not necessary.

Much trouble and energy can be saved by spending sufficient time in planning the job. When all details are worked out beforehand the actual construction is greatly simplified.

Cover the top of the chassis with a piece of wrapping paper or, preferably, cross-section paper, folding the edges down over the sides of the chassis and fastening with adhesive tape. Then assemble the parts to be mounted on top of the chassis and move them about until a satisfactory arrangement has been found, keeping in mind any parts which are to be mounted underneath, so that interferences in mounting may be avoided. Place condensers and other parts with shafts extending through the panel first, and arrange them so that the controls will form the desired pattern on the panel. Be sure to line up the shafts squarely with the chassis front. Locate any partition shields and panel brackets next, and then the tube sockets and any other parts, marking the mounting-hole centers of each accurately on the paper. Watch out for condensers whose shafts are off center and do not line up with the mounting holes. Do not forget to mark the centers of socket holes and holes for leads under i.f. transformers, etc., as well as holes for wiring leads.

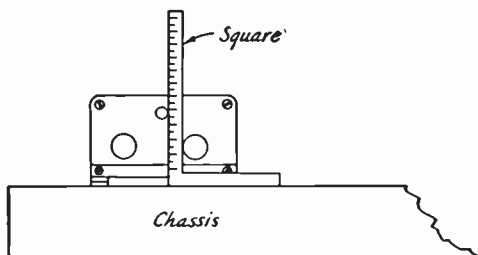


Fig. 1101 — Method of measuring the heights of condenser shafts, etc. If the square is adjustable, the end of the scale should be set flush with the face of the head.

By means of the square, lines indicating accurately the centers of shafts should be extended to the front of the chassis and marked on the panel at the chassis line, the panel being fastened on temporarily. The hole centers may then be punched in the chassis with the center punch. After drilling, the parts which require mounting underneath may be located and the mounting holes drilled, making sure by trial that no interferences exist with parts mounted on top. Mounting holes along the front edge of the chassis should be transferred to the

panel, by once again fastening the panel to the chassis and marking it from the rear.

Next, mount on the chassis the condensers and any other parts with shafts extending to the panel, and measure accurately the height of the center of each shaft above the chassis, as illustrated in Fig. 1101. The horizontal displacement of shafts having already been marked on the chassis line on the panel, the vertical displacement can be measured from this line. The shaft centers may now be marked on the back of the panel, and the holes drilled. Holes for any other panel equipment coming above the chassis line may then be marked and drilled, and the remainder of the apparatus mounted.

◀ Cutting and Bending Sheet Metal

If a sheet of metal is too large to be cut conveniently with a hacksaw, it may be marked with scratches as deep as possible along the line of the cut on both sides of the sheet and then clamped in a vise and worked back and forth until the sheet breaks at the line. Do not carry the bending so far that the break begins to weaken; otherwise the edge of the sheet may become bent. A pair of iron bars or pieces of heavy angle stock, as long or longer than the width of the sheet, to hold it in the vise will make the job easier. C-clamps may be used to keep the bars from spreading at the ends. The rough edges may be smoothed up with a file or by placing a large piece of emery cloth or sandpaper on a flat surface and running the edge of the metal back and forth over the sheet.

Bends may be made similarly. The sheet should be scratched on both sides, but not so deeply as to cause it to break.

◀ Drilling and Cutting Holes

When drilling holes in metal with a hand drill it is important that the centers first be located with a center punch, so that the drill point will not "walk" away from the center when starting the hole. Care should be taken not to use too much pressure with small drills, which bend or break easily. When the drill starts to break through, special care must be used. Often it is an advantage to shift a two-speed drill to low gear at this point. Holes more than $\frac{1}{4}$ -inch in diameter may be started with a smaller drill and reamed out with the larger drill.

The chuck on the usual type of hand drill is limited to $\frac{1}{4}$ -inch drills. Although it is rather tedious, the $\frac{1}{4}$ -inch hole may be filed out to larger diameters with round files. Another method possible with limited tools is to drill a series of small holes with the hand drill along the inside of the diameter of the large hole, placing the holes as close together as possible. The center may then be knocked out with a cold chisel and the edges smoothed up with a file. Taper reamers which fit into the carpenter's brace will make the job easier. A large rat-tail file clamped in the brace makes a very good

reamer for holes up to the diameter of the file, if the file is revolved counter-clockwise.

For socket holes and other large round holes, an adjustable cutter designed for the purpose may be used in the brace. The cutter should be kept well-sharpened. Occasional application of machine oil in the cutting groove will help. The cutter first should be tried out on a block of wood, to make sure that it is set for the correct diameter. Probably the most convenient device for cutting socket holes is the socket-hole punch. The best type is that which works by turning a take-up screw with a wrench.

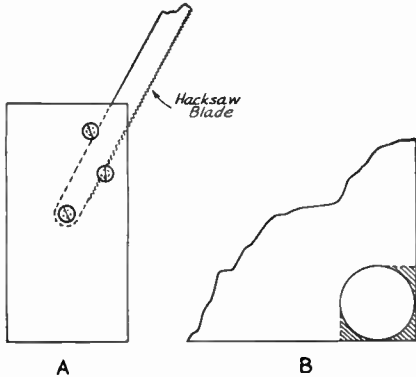


Fig. 1102 — To cut rectangular holes in a chassis, corner holes may be filed out as shown in the shaded portion of B, making it possible to start the hacksaw blade along the cutting line. A shows how a single-ended handle may be constructed for a hacksaw blade.

Square or rectangular holes may be cut out by making a row of small holes as previously described, but is more easily done by drilling a 1/2-inch hole inside each corner, as illustrated in Fig. 1102, and using these holes for starting and turning the hacksaw. The socket-hole punch also may be of considerable assistance in cutting out large rectangular openings.

The burrs or rough edges which usually result after drilling or cutting holes may be removed with a file, or sometimes more conveniently with a sharp knife or chisel. It is a good idea to keep an old wood chisel sharpened and available for this purpose. A burr reamer will also be useful.

Crackle Finish

Wood or metal parts can be given a crackle finish by applying one coat of clear Duco or Tri-Seal and allowing it to dry over night. A coat of Kem-Art Metal Finish is then sprayed or applied thickly with a brush, taking care that the brush marks do not show. This should be allowed to dry for two or three hours and the part should then be baked in the kitchen oven at 225 degrees one and one-half hours. This will produce a regular commercial job. This finish, which comes in several different colors, is made by Sherwin-Williams Paint Co.

NUMBERED DRILL SIZES

Number	Diameter (mils)	Will Clear Screw	Drilled for Tapping Iron, Steel or Brass*
1	228.0	—	—
2	221.0	12-24	—
3	213.0	—	14-24
4	209.0	12-20	—
5	205.0	—	—
6	201.0	—	—
7	201.0	—	—
8	199.0	—	—
9	196.0	—	—
10	193.5	10-32	—
11	191.0	10-24	—
12	189.0	—	—
13	185.0	—	—
14	182.0	—	—
15	180.0	—	—
16	177.0	—	12-24
17	173.0	—	—
18	169.5	8-32	—
19	166.0	—	12-20
20	161.0	—	—
21	159.0	—	10-32
22	157.0	—	—
23	154.0	—	—
24	152.0	—	—
25	149.5	—	10-24
26	147.0	—	—
27	144.0	—	—
28	140.0	6-32	—
29	136.0	—	8-32
30	128.5	—	—
31	120.0	—	—
32	116.0	—	—
33	113.0	4-36 4-40	—
34	111.0	—	—
35	110.0	—	6-32
36	106.5	—	—
37	104.0	—	—
38	101.5	—	—
39	99.5	3-48	—
40	98.0	—	—
41	96.0	—	—
42	93.5	—	4-36 4-40
43	89.0	2-56	—
44	86.0	—	—
45	82.0	—	3-48
46	81.0	—	—
47	78.5	—	—
48	76.0	—	—
49	73.0	—	2-46
50	70.0	—	—
51	67.0	—	—
52	63.5	—	—
53	59.5	—	—
54	55.0	—	—

*Use one size larger for tapping bakelite and hard rubber.

Twist Drills

Twist drills are made of either high-speed steel or carbon steel. The latter type are more common and will usually be supplied unless specific request is made for high speed drills. The carbon drill will suffice for most ordinary equipment construction work and costs less than the high speed type.

While twist drills are available in a number of sizes those listed in bold-faced type above will be the drills most commonly used in construction of amateur radio equipment. It is usually desirable to purchase several of each of the commonly used sizes rather than a quantity of odd sizes, most of which will be used infrequently, if at all.

☞ Cutting Threads

Brass rod may be threaded, or the damaged threads of a screw repaired, by the use of *dies*. Holes of suitable size (see drill chart) may be threaded for screws by means of *taps*. Taps and dies are obtainable in all standard machine-screw sizes. A set usually consists of taps and dies for 4-36, 6-32, 8-32, 10-32 and 14-20 sizes, with a holder suitable for use with either tap or die. The die may be started easily by first filing a sharp taper or bevel on the end of the rod. In tapping a hole, extreme care should be used to prevent breaking the tap. The tap should be kept at right angles to the surface of the material, and rotation should be reversed a revolution or two whenever the tap begins to turn hard. With care, holes can be tapped rapidly by clamping the tap in the chuck of the hand drill and using slow speed. Machine oil applied to the tap usually makes cutting easier and sticking less troublesome.

☞ Cleaning and Finishing Metal

Parts made of aluminum can be cleaned up and given a satin finish, after all holes have been drilled, by placing them in a solution of lye for one-half to three-quarters of an hour. Three or four tablespoonfuls of lye should be used to each gallon of water. If more than one piece is treated in the same bath, each piece should be separated from the others so as to expose all surfaces to the solution. Overlapping of pieces may result in spots or stains.

☞ Hook-Up Wire

A popular type of wire for receivers and low-power transmitters is that known as "push-back" wire. It comes in sizes No. 16, 18, 20, etc., which is sufficiently large for all power circuits except filament. The insulating covering, which is sufficient for circuits where voltages do not exceed 400 or 500, can be pushed back a few inches at the end, making

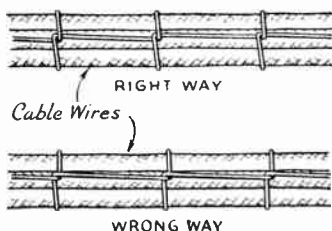


Fig. 1103 — Right and wrong methods of lacing cable. With the right way the leading line is pinched under each turn and will not loosen if a break occurs in the lacing.

cutting of the insulation unnecessary when making a connection. Filament wiring should be done with sufficiently large conductors to carry the required current without appreciable voltage drop (see Copper Wire Table in the Appendix). Rubber-covered house-wire sizes No. 14 to No. 10 are suitable for heavy-current

transmitting tubes, while No. 18 to No. 14 flexible wire is satisfactory for receivers and low-drain transmitting tubes where the total length of the leads is not excessive.

Stiff bare wire, sometimes called *bus wire* or *bus bar*, is most favored for the high r.f.-potential wiring of transmitters and, where practicable, in receivers. It comes in sizes No. 14 and No. 12 and is usually tin-dipped. Soft-drawn antenna wire also may be used. Kinks or bends can be removed by stretching 10 or 15 feet of the wire and then cutting it into small usable lengths.

The insulation covering power wiring which is to carry high transmitter voltages should be appropriate for the voltage involved. Wire with rubber and varnished cambric covering, similar to ignition cable, is available from radio parts dealers. The smaller sizes have sufficient insulation to be safe at 1000 to 1500 volts, while the more heavily insulated types should be used for voltages above 1500.

☞ Wiring Transmitters and Receivers

It is usually advisable to do the power-supply wiring first. The leads should be bunched together as much as possible and kept down close to the surface of the chassis. The lacing of power wiring in cable form not only improves its appearance but also strengthens the wiring. Fig. 1103 shows the correct way of lacing cabled wires. When done correctly the leading line is held tightly pinched in place after tension has been removed, and therefore does not loosen readily. When the wrong method is used the turns will loosen up as soon as tension is removed.

Chassis holes for wires should be lined with *rubber grommets* which fit the hole, to prevent chafing of the insulation. In cases where power-supply leads have several branches, it is often convenient to use fibre *terminal strips* as anchorages. These strips also form handy mountings for wire-terminal resistors, etc. When any particular unit is provided with a nut or thumb-screw terminal, soldering-lug wire terminals to fit are useful.

High-potential r.f. wiring should be well spaced from the chassis or other grounded metal surfaces and should be run as directly as possible between the points to be connected, without fancy bends. When wiring balanced or push-pull circuits, care should be taken to make the r.f. wiring on each side of the circuit as symmetrical as possible. Where it is necessary to pass r.f. wiring through the chassis, either a *feed-through* insulator of low-loss material should be used or the hole in the chassis should be of sufficient size to provide plenty of air space around the wire. Large-diameter rubber grommets can be used to prevent accidental short-circuits to the chassis.

By-pass condensers should be connected directly to the point to be by-passed and grounded immediately at the nearest available mounting screw, making certain that the screw

makes good electrical contact with the chassis. Care should be taken to connect the marked side of tubular paper by-pass condensers to ground. Blocking and coupling condensers should be well spaced from the chassis.

High-voltage wiring should have exposed points kept at a minimum and those which cannot be avoided rendered as inaccessible as possible to accidental contact.

☞ Soldering

The secret of good soldering is in allowing time for the *joint*, as well as the solder, to attain sufficient temperature. Enough heat should be applied so that the solder will melt when it comes in contact with the wires being joined, without touching the solder to the iron.

Wartime solder, which has a much smaller ratio of tin to lead, requires considerably more heat, and it becomes especially important to keep the iron clean at all times. More care must be exercised in making the joint because the new solder does not flow as readily, and also has a tendency to crystallize.

Soldering paste, if of the non-corroding type, is extremely helpful when used correctly. In general, it should not be used for radio work except when necessary. The joint should first be warmed slightly and the soldering paste applied with a piece of wire. Only the bit of paste which melts from the warmth of the joint should be used. If the soldering iron is clean it will be possible with one hand to pick up a drop of solder on the tip of the iron which can be applied to the joint, while the other hand is used to hold the connecting wires together. The use of excessive soldering paste causes the paste to spread over the surface of adjacent insulation, causing leakage or breakdown of the insulation. Except where absolutely necessary, solder should never be depended upon for the mechanical strength of the joint; the wire should be wrapped around the terminals or clamped with soldering terminals.

Do not attempt to make ground connections to a cadmium-plated chassis by soldering to the surface of the chassis, since the plating may be loosened by the heat and later fall off, breaking the connection. Drill a hole in the chassis and solder the wire in the hole.

☞ Construction Notes

Lockwashers should be used under nuts to prevent loosening with use, particularly when mounting tube sockets or plug-in coil receptacles subject to frequent strain.

If a control shaft must be extended or insulated, a flexible shaft coupling with adequate insulation should be used. Satisfactory support for the shaft extension can be provided by means of a *metal* panel bearing made for the purpose. Never use panel bearings of the non-metal type unless the condenser shaft is grounded. *The metal bearing should be connected to the chassis with a wire or grounding strip.* This prevents any possible danger of shock.

The standard way of mounting toggle switches is with the switch "On" when the lever is in the upward position.

Variable condensers and resistors, having one-hole mountings, should be firmly fastened using the special lockwashers provided for shaft nuts.

The use of fiber washers between ceramic insulation and metal brackets, screws or nuts will prevent the ceramic parts from breaking.

☞ Coil Winding

Dimensions for coils for the various units described in the constructional chapters are given under the circuit diagrams. Where no wire size is given, the power is sufficiently low to permit use of any available size within reason.

Unless a close-wound winding is definitely specified, the number of turns indicated should be spaced out to fill the specified length on the form. The length should be marked on the form and holes drilled opposite the pins to which the ends of the winding are to connect. Scrape one end of the wire and pass it through the lower hole in the form to the pin to which the bottom end of the winding is to connect, and solder this end fast. Unroll a length of wire approximately sufficient for the winding, and clamp the spool in a vise so it will not turn. The wire should be pulled out straight and the winding started by turning the form in the hands and walking toward the vise. A fair tension should be kept on the wire at all times. The spacing can be judged by eye. If, as the winding progresses, it becomes evident that the spacing is going to be incorrect to fill the required length, the winding can be started over again with a different spacing. If the spacing is only slightly off, the winding may be finished, the top end fastened, and the spacing corrected by pushing each turn. When complete, the turns should be fastened in place with coil cement. After a little practice, the job of determining the correct spacing will not be difficult.

Sometimes it is necessary to adjust the number of turns on a coil experimentally. The easiest way to do this is to bring a wire up from one of the pins, extending it through a hole in the form for a half-inch or so. The end of the winding may then be soldered to this extension rather than to the pin itself, and the nuisance of repeatedly fishing the wire through the pin avoided until the correct size of the winding has been determined.

☞ Coil Cement

Duco cement, obtainable universally at hardware, stationery or 5-and-10-cent stores, is satisfactory for fastening coil turns. For small coils, a better-looking job will result if it is thinned out with acetone (amyl acetate), sometimes referred to as banana oil. If desired, the solution may be made thin enough to permit application with a brush.

Special low-loss coil "dopes" are available, including some with a polystyrene base.

Receiver Construction

¶ A Two-Tube Regenerative Receiver

THE regenerative-detector receiver has long been a favorite with beginners, since it is comparatively easy to construct and adjust. A receiver of this type is shown in Figs. 1201, 1202 and 1204. It is designed to operate with tubes of either battery or a.c. type, and covers a total frequency range of 550 kc. to 32 Mc. with a series of plug-in coils. Sufficient audio output is available to operate a small permanent-magnet loudspeaker.

The circuit diagram appears in Fig. 1203. The antenna is coupled to the input circuit of the detector by means of the adjustable mica condenser, C_1 . The input circuit is tuned to the frequency of the incoming signal by means of the variable condensers, C_2 and C_3 . C_3 is used for general-coverage tuning, while C_2 is provided for bandspread tuning over a narrow band of frequencies anywhere within the total receiver range. C_3 serves also as the band-set condenser to locate the starting point of the range covered by C_2 . C_3 has sufficient capacity range to cover the entire broadcast band with a single coil when used for general-coverage tuning.

Feed-back for regeneration is supplied by L_2 . The amount of regeneration may be adjusted by means of R_4 which varies the screen voltage.

The output of the detector is coupled to the input of the audio amplifier by means of the audio reactor L_3 , and the coupling condenser, C_8 . While it is preferable to use a high-inductance (up to 1000 henries) reactance designed for this purpose, an ordinary filter choke of 15 to 30 henries will make an acceptable substitute. Volume may be adjusted for speaker or headphones by R_2 . T is the output transformer coupling the plate of the audio

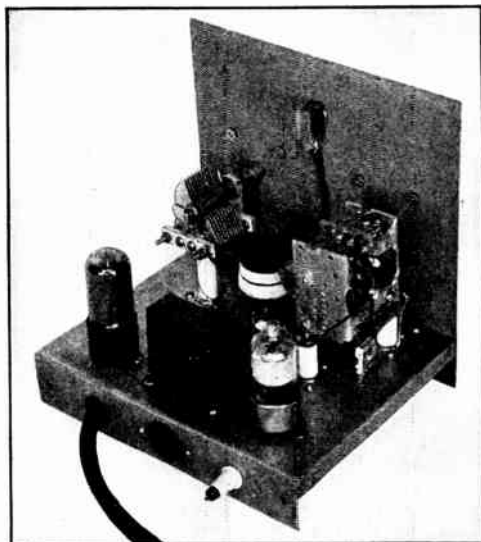


Fig. 1202 — Rear view of the two-tube regenerative receiver. Near the panel, from left to right are the bandspread tuning condenser, C_2 , the plug-in coil and the general-coverage tuning condenser, C_3 . The audio-amplifier tube, the output transformer, T , and the detector tube are lined up along the rear. The 4-prong socket set in the rear edge of the chassis is for connecting a small p.m. loudspeaker. The antenna terminal is at the right. The heater switch is mounted on the panel.

amplifier to the speaker. When headphones are used they are plugged into the closed-circuit jack, J , which automatically opens the voice-coil circuit thereby silencing the speaker.

The components for the receiver shown in the photographs were assembled on an $8 \times 6\frac{1}{2} \times 2$ -inch chassis bent up from sheet metal, although a standard steel chassis $7 \times 7 \times 2$ inches will accommodate the parts equally well without any change in the relative positions shown in the photographs. The two tuning condensers are mounted on ceramic


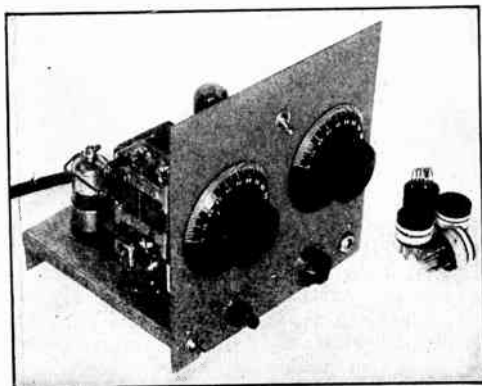


Fig. 1201 — Panel view of the two-tube regenerative receiver. The dial to the left controls the general-coverage or band-set tuning condenser, C_3 , while the one to the right is the bandspread tuning dial which controls C_2 . At the bottom the regeneration control is on the right and the audio volume control, R_2 , at the left. The stand-by switch, S_1 , is in the lower left-hand corner and the headphone jack occupies the opposite corner. The toggle switch at the top of the panel is the heater switch, S_2 . Tube-base coils are shown at the right. This view shows also the method of mounting the antenna coupling condenser, C_1 , the grid condenser, C_5 , and the grid-leak resistor, R_1 , on the frame of C_3 .

Fig. 1203 — Circuit diagram of the two-tube regenerative receiver.

- C_1 — 3–30- μ fd. mica trimmer.
 C_2 — 100- μ fd. midjet variable condenser (National EX-100).
 C_3 — 365- μ fd. variable (in the unit pictured, one section of a dual b.c. replacement variable, Meissner 21-5214).
 C_4 — 0.001- μ fd. mica.
 C_5 — 250- μ fd. mica.
 C_6, C_7 — 100- μ fd. mica.
 C_8 — 0.05- μ fd. paper.
 C_9 — 10- μ fd., 25-volt electrolytic.
 C_{10} — 0.1- μ fd. paper.
 R_1 — 2 megohms, $\frac{1}{2}$ watt.
 R_2 — 500,000-ohm volume control.
 R_3 — Cathode resistor, see text.
 R_4 — 25,000-ohm potentiometer.
 R_5 — 15,000 ohms, 1 watt.
 RFC — 15-mh. r.f. choke.
 L_1, L_2 — See text and coil table.

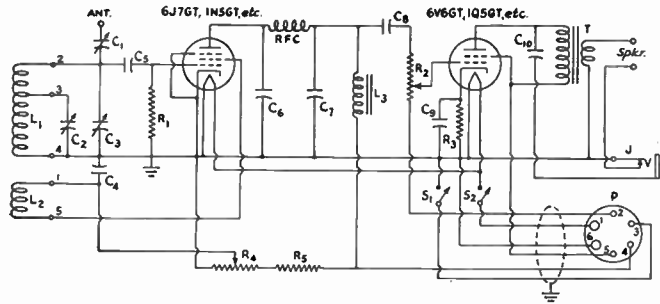

- L_3 — Audio coupling reactor, see text.
 T — Pentode output-to-speaker transformer, universal type.
 S_1, S_2 — Single-throw, single-pole toggle switch.
 J — Closed-circuit jack.
 P — 6-prong tube socket.

pillars or metal spacers so that the two shafts are elevated to the same height above the chassis level while their centers are separated by a distance of $4\frac{1}{4}$ inches.


The coil socket is located midway between the two variable condensers and also is elevated above the chassis on small metal pillars so that its terminals will be accessible for connections to the condensers. One side of the antenna coupling condenser, C_1 , is fastened to a stator terminal of C_3 , while a wire running through a small hole in the chassis directly underneath connects the opposite side of C_1 to the feed-through antenna terminal set in the rear edge of the chassis.

The grid condenser, C_5 , is supported on a small fibre lug strip fastened near the top of the frame of C_3 to bring it up to the level of the grid terminal of the detector tube, while the grid leak, R_1 is supported by its leads between one terminal of C_5 and one of the mounting screws in the chassis.

The two tubes and the audio reactor, L_3 are mounted in line along the rear edge of the chassis. The tube sockets are submounted by cutting holes to fit in the chassis so that their terminals will come below the surface of the chassis. Connections between the coil and detector-tube sockets are made with insulated wire running through a $\frac{1}{4}$ -inch hole drilled directly underneath the coil socket.

Most of the small components, such as resistors, by-pass condensers and the r.f. choke, as well as the speaker coupling transformer are placed underneath the chassis as shown in the bottom-view photograph of Fig. 1204. One side of each by-pass condenser is connected as close as possible to the point to be by-passed and the other terminal grounded at the nearest point on the chassis.

Fig. 1204 — Bottom view of the regenerative receiver. At the left above the detector-tube socket are the r.f. choke and the two by-pass condensers, C_6 (right) and C_7 (left). Above C_6 are C_8 to the left and C_4 to the right. Of the two resistors slightly to the right of center, R_5 is to the left and R_3 to the right with C_9 in between. To the right are the output transformer and C_{10} . The audio-tube socket is in the lower right-hand corner.

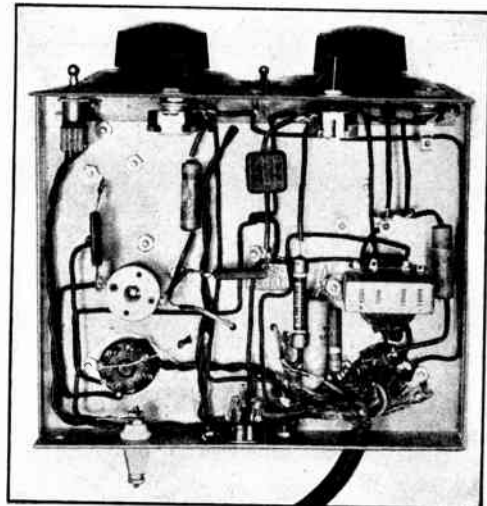

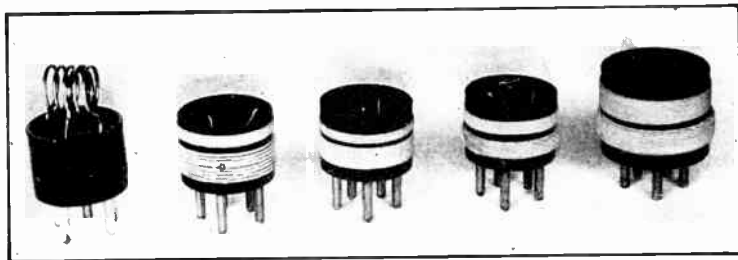


Fig. 1205 — A close-up view of the tube-base coils for the regenerative receiver. Band-spread taps are required on only the two highest-frequency coils. A special air-wound coil is necessary to cover the highest-frequency range of 12.8 to 32 Mc.

inch-diameter coil forms and for old bakelite tube bases, as shown in Fig. 1205, which may be used in case standard coil forms are not available. If tube bases are used, it will be necessary to wind the two largest coils in layers, since the base will not accommodate a sufficiently large single-layer winding. After winding the turns of the first layer in the conventional manner, the second layer is wound over the first in zig-zag fashion, taking one-half turn to cross back to the starting edge of the first layer and another half turn to cross back over the first layer to the finishing edge. Each successive turn of the zig-zag winding overlaps preceding turns at each reversal of the cross over. The finished coil actually has more than two layers at some points which explains the larger number of turns given for the "second layer" in the coil table. While an ordinary "scramble-wound" coil is not as neat in appearance, it will work almost as well if the constructor does not wish to bother with the more complicated winding. Connections to the coil-form pins and the coil-socket prongs are shown in Fig. 1206.

The self-supporting air-core coil No. 5 is made by winding 5 turns of No. 18 wire around a half-inch form, such as the shank of a drill, and spreading the turns out to the required coil length of $\frac{5}{8}$ inch by running a screwdriver or knife between the turns after they have been removed from the form. The tickler winding also should be wound on a half-inch form and the turns should be fastened together with

Duco waterproof cement or low-loss coil "dope" before removing from the form. After the cement has dried, the coil is inserted inside the "ground" end of L_1 . Its position should be varied until smooth regeneration is obtained and then it may be fastened in place with cement. Care should be taken to make all tickler windings in the same direction as the turns of L_1 , otherwise the circuit will not regenerate with the coil connections shown.

Choice of tubes — A wide variety of tubes will work satisfactorily in this receiver. Any of the 6.3- or 2.5-volt a.c., or 2- or 1.4-volt battery r.f. amplifier pentodes listed in the tube tables of the appendix may be used as the detector, while any of the audio power pentodes or beam tubes listed with a similar filament- or heater-voltage rating may be used in the audio amplifier, providing its rated plate current does not exceed 50 ma. Among the more widely available types are 57, 58 and 78 for detector in the old 2.5-volt a.c. series, with the 2A5 or 59 as the corresponding audio-amplifier type. In the 6.3-volt series with old-style bases are the 6C6 and 6D6 as detector and the 41, 42 or 89 for the audio stage. In the more modern octal series are the 6J7 or 6K7 for detector and the 6F6 or 6V6 for output amplifier. Their glass equivalents are equally suitable, of course. In the loktal series, the 7A7, 7B7 or 7W7 may be used in the detector stage, while the 7A5 or 7135 will serve as audio amplifier.

For battery operation, the 1D5GP or 1E5GP in the 2-volt-filament class are suitable for

COIL TABLE FOR THE 2-TUBE REGENERATIVE RECEIVER

No.	Range Mc.	Amateur Band Mc.	Dimensions (inches)		Turns		
			A	B	L_1	L_2	Bandspread Tap
1	0.55-1.6		$1\frac{1}{8}$	$\frac{1}{8}$	$65\frac{1}{2}$ ¹ (No. 32 d.c.e.)	$16\frac{1}{2}$ (No. 32 d.c.e.)	
			$1\frac{1}{2}$	$\frac{1}{8}$	$90\frac{1}{2}$	$20\frac{1}{2}$	"
2	1.2-3.35	1.75	$1\frac{1}{2}$	$\frac{1}{8}$	$29\frac{1}{2}$ ²	9%	"
			$1\frac{1}{2}$	$\frac{1}{8}$	$32\frac{1}{2}$	10%	"
3	2.7-7.7	3.5	$1\frac{1}{2}$	$\frac{1}{8}$	$14\frac{1}{2}$	5%	"
			$1\frac{1}{2}$	$\frac{1}{8}$	$10\frac{1}{2}$ ³	5%	"
4	5.35-14.6	7.0	$1\frac{1}{2}$	$\frac{1}{8}$	$7\frac{1}{2}$ ⁴ (No. 24 d.c.e.)	5%	" 4%
			$1\frac{1}{2}$	$\frac{1}{8}$	$6\frac{1}{2}$ ⁴	5%	" 3%
5	12.8-32	14-28	$\frac{5}{8}$	$\frac{1}{2}$	5^5 (No. 18 d.c.e.)	6 (No. 28 d.c.e.)	2%

Coil dimensions A and B and socket connections are shown in Fig. 1206. Specifications for standard $1\frac{1}{2}$ " diameter coil forms are also shown. Direction of winding is the same for all coils. All windings are close-wound unless otherwise indicated. Taps are counted from the ground end of the coil.

¹ First layer, 18 turns, close-wound; second layer $47\frac{1}{2}$ turns (see text).

² First layer, 12 turns, close-wound; second layer $17\frac{1}{2}$ turns (see text).

³ Spaced to cover $\frac{1}{4}$ inch.

⁴ Spaced to cover $\frac{3}{8}$ inch.

⁵ Self-supporting (see text).

detector, while the 1F5GP or 1G5G of the same class may be used in the audio stage. In the 1.5-volt octal series there are the 1N5G and 1P5G for detector and the 1A5G and 1C5G for audio amplifier. The loktal types 1LC5 and 1LN5 will make satisfactory detectors with a 1LA4 or 1LB4 amplifier.

When the receiver is to be used for portable as well as home-station operation the selection of a.c. and battery tubes whose sockets and connections make them interchangeable is desirable. In the detector circuit the 1D5GP, 1D5GT and the 1E5GP in the 2-volt battery series, or the 1N5G and 1P5G in the 1.5-volt battery series are directly interchangeable with the 6M7G, 6T6GM, 6U7G, 6W7G, 6J7GT/G, 6K7GT/G and the 687 in the 6.3-colt octal-base series. If loktal-base tubes are preferred, the 1LC5 and 1LN5 battery tubes are directly interchangeable with the 7V7, 7A7, 7B7, 7C7, 7G7, 7H7, 7L7 or 7T7 types.

In the audio amplifier the 1G5G and 1J5G of the 2-volt battery series or the 1A5G, 1C5G, 1Q5G and 1T5G in the 1.5-volt battery series are directly interchangeable with the 6AG6G, 6K6G, 6M6G or 6V6 with octal bases. The loktal types 1LA4 and 1LB4 also are interchangeable with the indirectly-heated types 7A5 and 7B5 of the loktal series.

It may pay to try different values of grid-leak resistance if detector-tube types other than those mentioned in Fig. 1203 are used and some slight alteration in the number of turns in L_2 may be necessary for best performance. The audio tube selected will require a certain biasing voltage which may be taken from the tube tables. With battery tubes, this means simply selecting the proper "C"-battery voltage. With a.c. tubes, however, bias is obtained from the voltage drop across the cathode resistor, R_3 . A satisfactory resistance value for any particular audio tube may be easily calculated by adding the rated plate and screen currents given in the tube tables and then dividing the required biasing voltage by this sum. If the current value is in terms of milliamperes, the answer from the above operation must be multiplied by 1000 to obtain the required resistance value in ohms. For example, the tube table shows that a 7C5 requires a biasing voltage of 12.5 and that the screen cur-

rent averages about 6 ma., while the plate current averages 46 ma. Adding the two currents gives a total of 52 ma. Dividing 12.5 by 52 gives a result of 0.24. When this is multiplied by 1000, the answer of 240 ohms is obtained.

Power supply— Suitable power-supply diagrams are shown in Fig. 1207. The VR75 in the a.c. circuit in Fig. 1207-A provides a regulated voltage of 75 for the detector which will help materially in obtaining smooth regeneration. However, if one is not available, it may be omitted, if R is increased to 150,000 ohms, at some sacrifice in smoothness of regeneration control. The small condensers, C_1 and C_2 are to help reduce "tunable hum"

which may occur at certain points in the frequency range of the receiver. Components for the a.c. power supply may be mounted on a $7 \times 7 \times 2$ -inch steel chassis or a baseboard made of wood. The placement of parts is not important. If the steel chassis is used, the smaller components may be mounted underneath. The voltage of the filament winding should, of course, correspond to the rated heater voltage of the tubes used (6.3 or 2.5 volts). In Fig. 1207-B is shown the proper connections for a battery supply. The voltage of the "A" battery will depend upon the rated filament voltage of the tubes selected (1.5 or 2 volts), while the "B" battery should consist of two 45-volt "B" batteries connected in series. The voltage of the "C" battery will depend upon the biasing voltage required for the tube in the audio


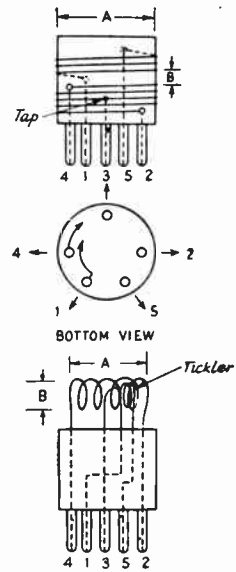


Fig. 1206 — Sketch showing coil-form and coil-socket connections for the plug-in coils for the two-tube regenerative receiver. The bottom sketch shows the special construction for Coil No. 5 listed in the accompanying coil table.

Fig. 1207 — Circuit diagram of a power supplies suitable for small receivers. The a.c. supply shown at A is suggested for the two-tube regenerative and the three-tube superheterodyne receivers described in this chapter. The battery supply shown at B is arranged especially to fit the plug connections of the regenerative receiver of Fig. 1201. The low-voltage tap is regulated by the VR75 tube.

- C_1, C_2 — 0.001- μ fd., 1,000-volt mica.
- C_3, C_4, C_5 — 8- μ fd., 450-volt electrolytic.
- R — 10,000-ohm, 10-watt wire-wound for the 2-tube regenerative receiver, 5000 ohms, 10 watts for the 3-tube superheterodyne receiver of Fig. 1213. If the VR-75 is omitted, R should be increased to 100,000 and 50,000 ohms respectively.
- T — Standard replacement-type power transformer with 6.3-volt, 5-volt, and 600-volt center-tapped windings, 70 ma. d.c. output rating.

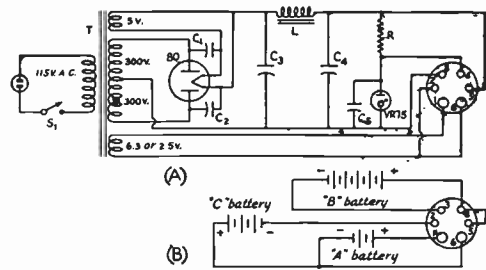

- L — Standard replacement-type filter choke, 15-30 henries at 70 ma.
- S_1 — S.p.s.t. toggle switch.

amplifier as mentioned previously. The 6-prong socket for connections to the receiver may be mounted on a board or connected to one end of a short cable, the wires at the other end of the cable being connected to the batteries as shown.

Adjustment — The most difficult part of adjusting the receiver after it has been constructed and the power supply connected is that of adjusting the coils for proper regeneration. It is perhaps best to start out with the lowest-frequency coil (b.c. band) and work up through the higher frequencies. One end of a single-wire antenna should be connected to the antenna terminal and the chassis connected to the nearest water pipe or other ground connection. The antenna preferably should be 50 to 100 feet in length. With the antenna connected, R_4 should be set for maximum screen voltage (to the right toward R_5 in Fig. 1203), C_3 should be turned to maximum capacity (plates completely meshed) and C_2 at minimum capacity. With these adjustments, a click should be heard in the headphones each time the grid terminal of the detector tube is touched with the finger. If no click is heard, the capacity of C_1 should be reduced a bit at a time, by loosening up on the adjusting screw, until the click is heard. If no click is heard with C_1 at minimum capacity, it will be necessary to add a turn or two to L_2 .

After the click has been obtained, it should be possible to turn R_4 back and forth with a "plop" in the headphones each time R_4 passes through a certain point in its range. On the high-voltage side of the "plop" point, the click should be heard when the grid terminal is touched with the finger, while it will not be heard when R_4 is turned to the low-voltage side of this point. The detector is oscillating under the condition where the click is heard and is not oscillating when the click cannot be obtained. With correct circuit adjustments

it should be possible to bring the detector into oscillation with a soft rushing noise and not a loud "plop." For c.w. code reception R_4 is adjusted so that the detector is oscillating, but very close to the point where oscillation ceases. On the other hand for the reception of modulated signals ('phone or music) the detector is adjusted to a non-oscillating condition, but very close to the point where it goes into oscillation.

In listening over any band for signals, it is common practice to set the detector into oscillation for both 'phone and c.w. signals. When the steady whistle of a 'phone station is tuned in, the regeneration control is then backed off to stop oscillation when the whistle will disappear, and only the modulation will be heard.

C_3 is used for general-coverage tuning, while C_2 is used for bandspread tuning. If the coil dimensions given in the table have been followed closely, C_3 should be set at approximately the following points on the dial for each of the amateur bands: 1.75-Mc. band, 52; 3.5-Mc. band, 39; 7-Mc. band, 34; 14- and 28-Mc. bands, 93. These dial settings assume the use of a dial which reads 100 at *minimum* capacity. C_2 then should be used for tuning over the band. Coil No. 5 is used for both the 14- and 28-Mc. bands. At the higher frequencies especially, it may be necessary to retune each time the regeneration control is adjusted to keep the signal tuned in.

⌋ A Two-Tube Superheterodyne Receiver

Although all the advantages of the superheterodyne-type receiver cannot be secured without going to rather elaborate multi-tube circuits, it is possible to use the superhet principle to overcome most of the disadvantages of the simple regenerative receiver. These are chiefly the necessity for critical adjustment of the regeneration control with tuning, antenna "dead spots," lack of stability (both in the detector circuit itself and because of slight changes in frequency when the antenna swings with the wind), and blocking, or the tendency for strong signals to pull the detector into zero beat. These effects can be largely eliminated by making the regenerative detector operate on a fixed low frequency and designing it for maximum stability. The incoming signal is then converted to the fixed detector frequency before being detected.

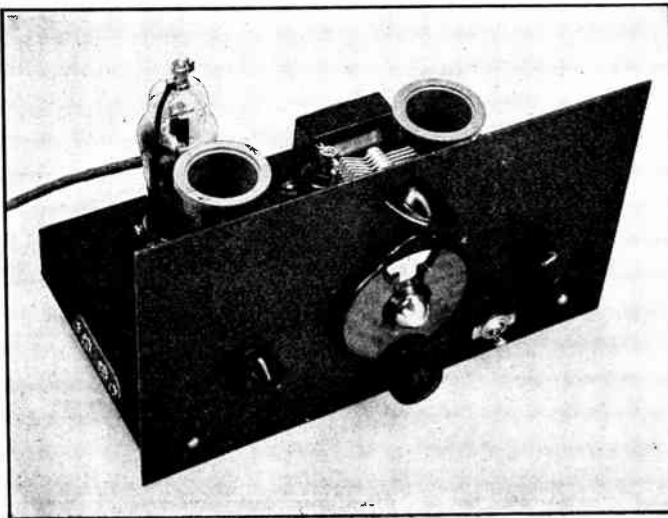


Fig. 1208 — The two-tube superheterodyne shown here has one more operating control than the ordinary regenerative-detector receiver, but it is more stable.

A two-tube receiver operating on this principle is shown in Figs. 1208 to 1212.

The circuit diagram is given in Fig. 1210. A 6K8 is used to convert the frequency of the incoming signal to the fixed or intermediate frequency, and the two triode sections of a 6C8G serve as the regenerative detector and audio amplifier respectively. L_1C_1 is the r.f. circuit, tuned to the signal, and L_2 is the antenna coupling coil. C_7 is a by-pass condenser across the 1.5-volt battery used to bias the signal grid of the 6K8. The high-frequency oscillator tank circuit is $L_3C_3C_4$, with C_3 for band-setting and C_4 for bandspread.

The i.f. tuned circuit (or regenerative detector circuit) is L_5C_5 . This must be a high- C circuit if stability better than that of an ordinary regenerative detector is to be secured. The frequency to which it is tuned should be in the vicinity of 1600 kc.; the exact frequency does not matter so long as it falls on the low-frequency side of the 1750-ke. band. L_5 and its tickler coil, L_6 , are wound on a small form, and L_5 is tuned by a fixed mica condenser of the low-drift type. Since these condensers are rated with a capacity tolerance of 5 per cent, it is sufficient to wind L_5 as specified under Fig. 1210. The resulting resonant frequency will be in the correct region. No manual tuning is necessary, and therefore the frequency of this circuit need not be adjusted. C_2 is the regeneration-control condenser, isolated from the d.c. supply by the choke, RFC. Only enough turns need be used on L_6 to make the detector oscillate readily when C_2 is at half capacity or more.

The second section of the 6C8G is transformer-coupled to the detector. The grid is biased by the same battery which furnishes bias for the 6K8.

Looking at the top of the chassis from in front, the r.f. or input circuit is at the left, with C_1 on the panel and L_1L_2 just behind it. The 6C8G is directly to the rear of the coil.

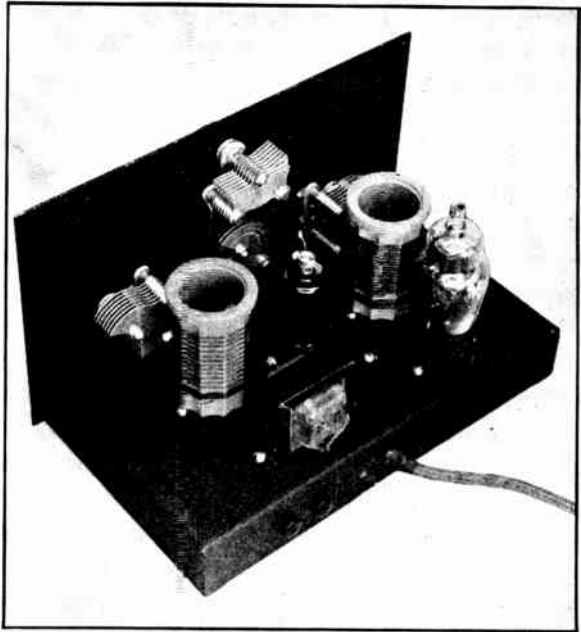


Fig. 1209 — A back-of-panel view of the two-tube superhet, showing the arrangement of parts on top of the $5\frac{1}{2} \times 9\frac{1}{2} \times 1\frac{1}{2}$ -inch chassis.

The 6K8 converter tube is centered on the chassis, with C_3 and C_4 on the panel directly in front of it. C_4 is driven by the vernier dial and C_3 is toward the top of the panel. The coil at the right is L_3L_4 , in the oscillator tuned circuit. The regeneration-control condenser, C_2 , is at the right on the panel. The audio transformer, T_1 , is behind the oscillator coil.

Looking at the bottom of the chassis, the antenna-ground terminals are at the left, with a lead going directly to L_2 on the coil socket. The bias battery is fastened to a two-lug insulating strip by means of wires soldered to the battery. The zinc can is the negative end and the small cap the positive terminal. By-pass condenser C_7 is mounted on the coil socket.

The i.f. coil is mounted on the chassis midway between the socket for the 6C8G and that for the 6K8. In winding the coil the ends of the wires are left long enough to reach to the various tie-in points. The grid condenser, C_9 , is

Fig. 1210 — Circuit diagram of the two-tube superheterodyne.

C_1, C_2, C_3 — 100- μ fd. variable (Hammarlund SM-100).

C_4 — 15- μ fd. variable (Hammarlund SM-15).

C_5 — 250- μ fd. silvered mica (Dubilier Type 5-R).

C_6 — 0.01- μ fd. paper.

C_7 — 0.005- μ fd. mica.

C_8, C_9 — 100- μ fd. mica.

R_1 — 50,000 ohms, $\frac{1}{2}$ watt.

R_2 — 1 megohm, $\frac{1}{2}$ watt.

RFC — 2.5-mh. r.f. choke.

T_1 — Audio transformer, interstage type, 3:1 ratio (Thordarson


T-13A34).

L_1-L_4 , inc. — See coil table.

L_5 — 55 turns No. 30 d.s.c., close-wound on $\frac{3}{4}$ -inch diameter form (National PRF-2); inductance 40 microhenrys.

L_6 — 18 turns No. 30 d.s.c., close-wound, on same form as L_5 ; see Fig. 1212.

S — S.p.s.t. toggle switch.

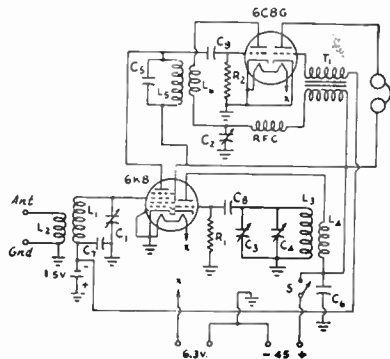

TWO-TUBE SUPERHET COIL DATA

Coil Grid Winding (L_1 and L_2) Antenna (L_2) or Ticker (L_4)

A	56 turns No. 22 enameled	10 turns No. 24 enameled
B	32 " " " "	8 " " " "
C	18 " " " "	7 " " " "
D	12 " " " "	7 " " " "
E	10 " " " "	7 " " " "

All coils wound on $1\frac{1}{2}$ -inch diameter forms (Hammarlund SWF-4). Grid windings on coils B-E, inclusive, are spaced to occupy a length of $1\frac{1}{2}$ inches; grid winding on coil A is close-wound. Antenna-tickler coils are all close-wound, spaced $\frac{1}{4}$ -inch from bottom of grid winding. See Fig. 1212.

Frequency Range	Coil at L_1 - L_2	Coil at L_3 - L_4
1700 to 3200 ke.	A	B
3000 to 5700 ke.	B	C
5400 to 10,000 ke.	C	D
9500 to 14,500 ke.	E	D

supported by the grid terminal on the tube socket and the end of the grid winding, L_5 . R_2 is mounted over the 6C8G socket. The i.f. tuning condenser, C_5 , is mounted between the plate and screen prongs on the 6K8 socket, the ends of L_5 being brought to the same two points.

The oscillator grid condenser, C_8 , is connected between the coil-socket prong and the oscillator grid prong on the 6K8 socket. By-pass condenser C_6 is mounted alongside the oscillator coil socket, as shown. The connections to the rotors of the tuning condensers for both coils go through holes in the chassis near the front edge. Grounds are made directly to the chassis in all cases; make sure that there is an actual connection to the metal.

The "B" switch is a single-pole single-throw toggle. 'Phone-tip jacks on the rear chassis edge provide means for connecting the audio output to the headphones.

The method of winding coils is indicated in Fig. 1212; if the connections to the circuit are made as shown, there will be no trouble in

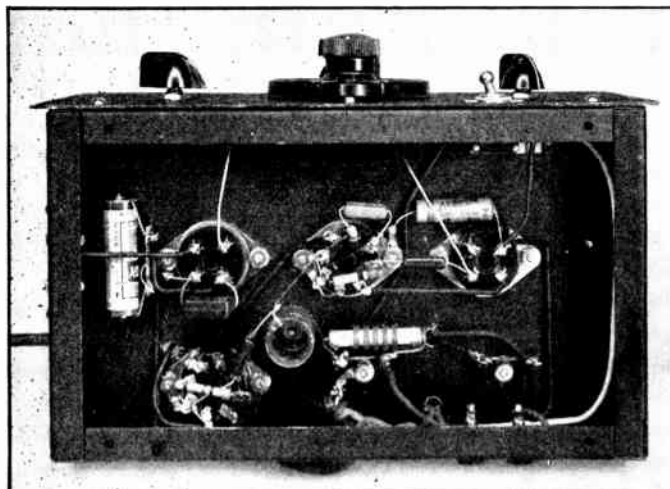


Fig. 1211 — Below-chassis view of the two-tube superhet. The i.f. circuit is underneath the chassis; no adjustment of its frequency is necessary. Since few parts are required, the construction, assembly and wiring are quite simple.

obtaining the necessary oscillation. Both coils on each form should be wound in the same direction.

Adjustment — To test the receiver, first try out the i.f. circuit. Connect the filament and "B" supply and place both tubes in their sockets. Put a high-frequency coil in the r.f. socket, but do not insert a coil in the oscillator socket. The only test which need be made is to see if the detector oscillates properly. Advance C_2 from minimum capacity until the detector goes into oscillation, which will be indicated by a soft hiss. This should occur at around half scale on the condenser. If it does not occur, check the coil (L_5 L_6) connections

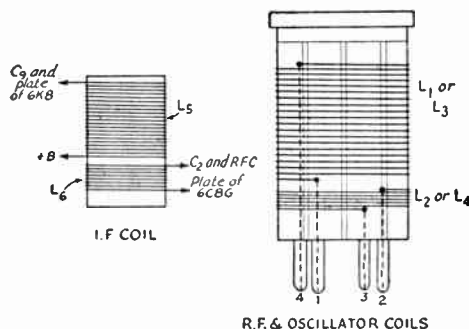


Fig. 1212 — How the coils for the two-tube superheterodyne are wound. The bottom end of the i.f. coil in this drawing is the end mounted adjacent to the chassis. L_5 and L_6 are wound in the same direction. On the r.f. socket, pin 4 connects to the No. 3 grid (top cap) of the 6K8 and stator of C_1 , pin 1 to C_7 , pin 2 to ground and pin 3 to the antenna post. On the oscillator socket, pin 4 goes to C_8 and the stators of C_3 and C_4 , pin 1 to ground, pin 2 to "B" + and pin 3 to the 6K8 oscillator plate. Both windings are in the same direction on each coil.

and winding direction and, if these seem right, add a few turns to the tickler, L_6 . If the detector oscillates with very low capacity at C_2 , it will be advisable to take a few turns off L_6 until oscillation starts at about midscale.

After the i.f. has been checked, plug in an oscillator coil for a range on which signals are likely to be heard at the time. The 5400-10,000-ke. range is usually a good one. The coils are arranged so that a minimum number is needed, even though two are used at a time. With coil C in the r.f. socket and D in the oscillator circuit, set C_1 at about half scale and turn C_3 slowly around midscale until a signal is heard. Then tune C_1 for maximum volume. Should no signals be heard, the probability is that the oscillator section of the 6K8 converter tube is not

working, in which case the same method of testing is used as described above for the i.f. detector — check wiring, direction of windings of coils, and finally, add turns to the tickler, L_4 , if necessary.

The same oscillator coil, D, is used for two frequency ranges. This is possible because the oscillator frequency is placed on the low-frequency side of the signal on the higher range. This gives somewhat greater stability at the highest-frequency range. Some pulling — a change in beat-note as the r.f. tuning is varied by means of C_1 — will be observed on the highest-frequency range, but it is not serious in the region of resonance with the incoming signal frequency.

The receiver will respond to signals either 1600 kc. lower or 1600 kc. higher than the oscillator frequency. The unwanted response is discriminated against by the selectivity of the r.f. circuit. On the three lower-frequency ranges, when it is possible to find two tuning spots on C_1 at which incoming noise peaks up, the lower-frequency peak is the right one. The oscillator frequency is 1600 kc. higher than that of the incoming signal on these three ranges and 1600 kc. lower on the fourth range. Bandspread is not needed in the r.f. circuit.

The regeneration control may be set to give desired sensitivity and left alone while tuning; only when an exceptionally strong signal is encountered is it necessary to advance it more to keep the detector in oscillation. It should be set just on the edge of oscillation for 'phone reception.

The heater requirements of the set are 0.6 amperes at 6.3 volts, approximately. Either a.c. or d.c. may be used. The "B" battery current is between 4 and 5 ma., so that a standard 45-volt block will last hundreds of hours.

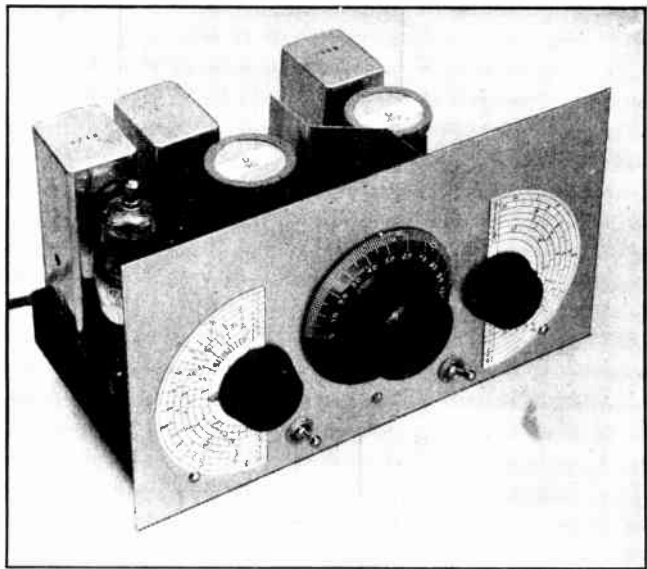


Fig. 1213 — A three-tube superheterodyne receiver, designed for either a.c. or d.c. heater operation and for 90-volt "B" battery plate supply.


A Three-Tube General Coverage and Bandspread Superheterodyne

A superhet receiver of simple construction, having a wide frequency range for general listening-in as well as full bandspread for amateur-band reception, is shown in Figs. 1213 to 1217. The circuit uses only three tubes and gives continuous frequency coverage from about 75 kc. (4000 meters) to 60 Mc. (5 meters). The receiver is intended for operation from either a 6.3-volt transformer or 6-volt storage battery for filament supply, and a 90-volt "B" battery for plate supply.

The circuit diagram is given in Fig. 1214. A 6K8 is used as a combined oscillator-mixer followed by a 6SK7 i.f. amplifier. The intermediate frequency is 1600 kc., a frequency which reduces image response on the higher frequencies and simplifies the design for low-frequency operation in the region below the broadcast band. One section of the 6C8G dou-

Fig. 1214 — Wiring diagram for the three-tube general coverage and bandspread superheterodyne receiver.

- C_1 — 100- μ fd. variable (Hammarlund MC-100-M).
- C_2 — 140- μ fd. variable (Hammarlund MC-140-M).
- C_3 — 35- μ fd. variable (Hammarlund HF-35).
- C_4 — Oscillator padder; see coil table.
- C_5 — 0.1- μ fd. paper.
- C_6 — 0.002- μ fd. mica.
- C_7 — 250- μ fd. mica.
- C_8 — 0.002- μ fd. mica.
- C_9, C_{10} — 0.01- μ fd. paper.
- C_{11} — 5- μ fd. electrolytic, 50 volts.
- C_{12}, C_{13} — 0.002- μ fd. mica.
- R_1 — 50,000 ohms, $\frac{1}{2}$ watt.
- R_2, R_3 — 250 ohms, $\frac{1}{2}$ watt.
- R_4 — 12,000 ohms, $\frac{1}{2}$ watt.
- R_5 — 50,000 ohms, $\frac{1}{2}$ watt.
- T_1, T_2 — 1600-kc. i.f. transformer (Millen 64161).
- T_3 — 1600-kc. oscillator transformer (Millen 65163).
- L_1, L_2, L_3, L_4 — See coil table.

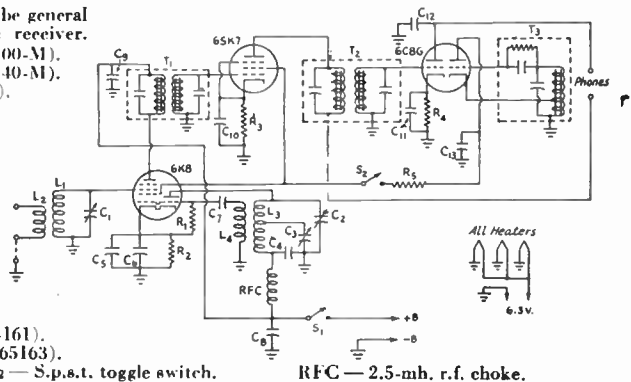

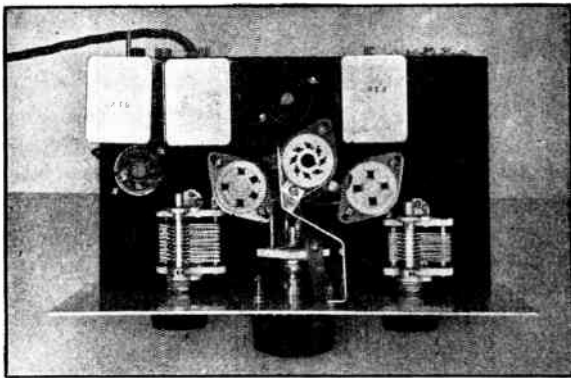


Fig. 1215 — A plan view of the three-tube superheterodyne with the coils and tubes removed. The chassis measures $5\frac{1}{2} \times 9\frac{1}{2} \times 1\frac{1}{2}$ inches and the panel size is $10\frac{1}{2} \times 6$ inches.

ble triode is used as a second detector and the other section as a beat-frequency oscillator. Headphone output is taken from the plate circuit of the second detector.

To simplify construction, the antenna and oscillator circuits are separately tuned. The antenna tuning control, C_1 , may be used as a volume control by detuning from resonance. The oscillator circuit, $L_3C_2C_3$, is tuned 1600 kc. higher than the signal on frequencies up to 5 Mc.; above 5 Mc. the oscillator is 1600 kc. lower than the signal. C_2 is the general coverage or band-setting condenser, C_3 the band-spread or tuning condenser. C_4 is a tracking condenser which sets the oscillator tuning range on each band so that it coincides with the tuning range in the mixer grid circuit.

The i.f. stage uses permeability-tuned transformers with silvered-mica fixed padding condensers. The second detector is cathode-biased by R_4 , by-passed by C_{11} for audio frequencies.

The second 6CS6G section is the beat oscillator, using a permeability-tuned transformer. The grid condenser and leak are built into the transformer. The plate is fed through the b.o. on-off switch and a dropping resistor, R_5 , the latter serving both to reduce the "B" current drain and to cut down the output of the oscillator to a value suitable for good heterodyning.

No special coupling is needed between the beat oscillator and the second detector.

The plates and screens of all tubes except the beat oscillator are operated at the same voltage — 90 volts. The "B" current drain is approximately 15 milliamperes, which is about the normal drain for medium-size "B" batteries. The receiver will operate satisfactorily, although with somewhat reduced volume, using a single 45-volt battery for "B" supply.

The parts arrangement is shown in the photographs of Figs. 1215 and 1216. The mixer tuning condenser, C_1 , is at the right. The band-spread oscillator tuning condenser, C_3 , is in the center, controlled by the National Type-A $3\frac{1}{2}$ -inch dial, and the band-set condenser, C_2 , is at the left.

Referring to the top view, Fig. 1215, the i.f. section is along the rear edge, with T_1 at the right. Next is the socket for the 6SK7, then T_2 , and finally T_3 at the extreme left. The socket for the 6CS6G is just in front of T_3 . The triode section in which the grid is brought out to the top cap is the one which is used for the beat oscillator.

The r.f. section has been arranged for short leads to favor high-frequency operation. The three sockets grouped closely together in the center are, from left to right, the oscillator-coil socket, socket for the 6K8, and the mixer-coil socket. All are mounted above the chassis by means of mounting pillars, so that practically all r.f. leads are above deck. The oscillator grid leak, R_{11} , and the high-frequency cathode by-pass condenser, C_6 , should be mounted directly on the socket before it is installed. So also should the oscillator grid condenser, C_7 , which can be seen extending to the left toward the oscillator-coil socket in Fig. 1215. Power-supply connections should be soldered to the 6K8 socket prongs before the socket is mounted, and these leads brought down through a hole in the chassis.

The general-coverage condensers, C_1 and C_2 , are mounted directly on the chassis. C_3 is held from the panel by means of a small bracket made from metal strip, bent so that the condenser shaft lines up with

the oscillator-coil socket in Fig. 1215. Power-supply connections should be soldered to the 6K8 socket prongs before the socket is mounted, and these leads brought down through a hole in the chassis.

The general-coverage condensers, C_1 and C_2 , are mounted directly on the chassis. C_3 is held from the panel by means of a small bracket made from metal strip, bent so that the condenser shaft lines up with

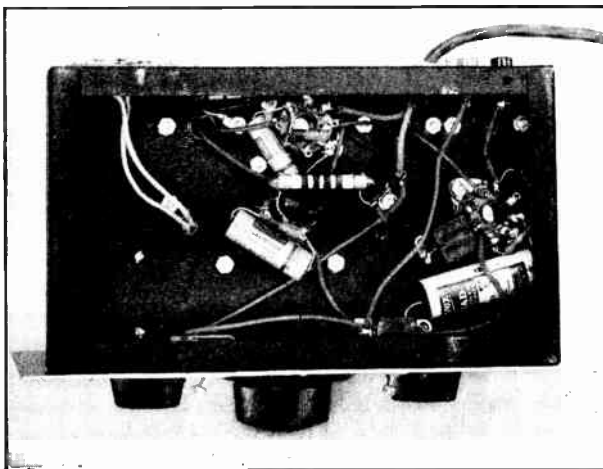


Fig. 1216 — Below the chassis of the three-tube receiver. The r.f. choke is mounted near the oscillator coil socket to keep the r.f. leads short. In the i.f. stage, care should be taken to keep the plate and grid leads from the i.f. transformer short and well separated. A four-wire cable is used for power-supply connections. The headphone-tip jacks may be seen near the upper right-hand corner.

the dial coupling. A baffle shield made of aluminum separates the oscillator and mixer sections; this shield is essential to prevent coupling between the two circuits which might otherwise cause interaction and poor performance.

The first step in putting the receiver into operation is to align the i.f. amplifier. This should preferably be done with the aid of a test oscillator, but if one is not available the circuits may be aligned on hiss or noise. The beat oscillator can also be used to furnish a signal for alignment. Further information on alignment may be found in Chapter Seven.

The coils are wound as shown in Fig. 1217. A complete set of specifications is given in the coil table. Ordinary windings are used for all oscillator coils, and for all mixer coils for frequencies above 1600 kc. Below 1600 kc., readily available r.f. chokes are used for the tuned circuits. For the broadcast band and the 600-750-meter ship-to-shore channels, the mixer coil is a Hammarlund 2.5-mh. r.f. choke, with the pies tapped as shown in Fig. 1217. The grid end and the intermediate tap are connected to machine screws mounted near the top of the coil form, and a flexible lead is brought out from the grid pin in the coil form to be fastened to either lead as desired. Mixer coils for the two lowest-frequency ranges are constructed as shown. The antenna winding in each case is a coil taken from an old 465-kc. i.f. transformer, having an inductance of about 1 millihenry. The inductance is not particularly critical, and a pie from a 2.5-mh. choke may be used instead.

With the i.f. aligned, the mixer grid and oscillator coils for a band can be plugged in. C_3 should be set near minimum capacity and C_2 tuned from minimum capacity until a signal is heard. Then C_1 is adjusted for maximum signal strength. If C_2 is set at the high-frequency end of an amateur band, further tuning should be done with C_3 , and the band should be found to

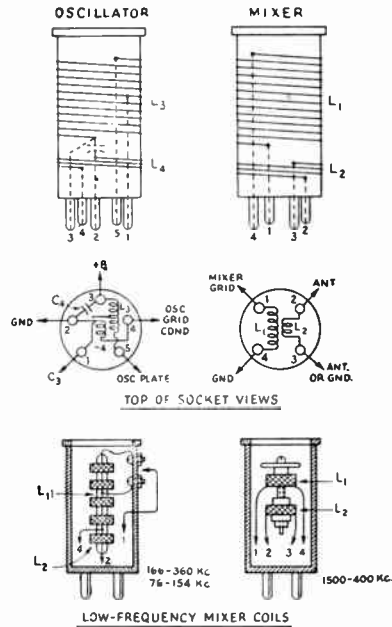


Fig. 1217 — How the coils for the three-tube superheterodyne are constructed. On the hand-wound oscillator and mixer coils, all windings are in the same direction.

cover about seventy-five per cent of the dial. C_3 can of course be used for bandspread tuning outside as well as inside the amateur bands. It is convenient to calibrate the receiver, using homemade paper scales for the purpose as shown in Fig. 1213. Calibration points may be taken from incoming signals whose frequencies are known, from a calibrated test oscillator, or from the harmonics of a 100-kc. oscillator as described in Chapter Nineteen. The mixer calibration need be only approximate, since tuning of the mixer circuit has little effect on the oscillator frequency. It is sufficient to make a

COIL DATA FOR THE THREE-TUBE SUPERHETERODYNE

Range	Turns					C_4
	L_1	L_2	L_3	L_4	L_3 Tap	
A — 76-154 kc.	30 mh.	1 mh. }	65	12	Top	300 μ fd.
166-360 kc.	8 mh.	1 mh. }				
400-1500 kc.	2.5 mh.*	*				
B — 1.6 to 3.2 Mc. (160 meters)	56	10	42	11	Top	75 μ fd.
C — 3.0 to 5.7 Mc. (80 meters)	32	8	27	9	Top	100 μ fd.
D — 5.4 to 10.0 Mc. (40 meters)	18	8	22	9	12	0.002 μ fd.
E — 9.5 to 18.0 Mc. (20 meters)	10	8	12	3½	6	400 μ fd.
F — 15.0 to 30 Mc. (10 meters)	6	4	6	2½	2½	400 μ fd.
G — 30 to 60 Mc. (5 meters)	3	3	3½	1	1	300 μ fd.

* See Fig. 1217 and text for details. C_4 is mounted inside oscillator coil form; see Fig. 1217. Bandsread taps on L_3 measured from bottom ("B" + end) of coil. L_3 -A and L_1 -B coils close-wound with No. 22 enameled wire; L_3 -B close-wound with No. 20 enameled; all other L_1 and L_3 coils wound with No. 18 enameled, spaced to give a length of 1½ inches on a 1½-inch diameter form (Hammarlund SWF) except the G coils, which are spaced to a length of 1 inch on 1-inch diameter forms (Millen 45004 and 45005). Antenna and tickler coils, L_2 and L_4 , are close-wound with No. 24 enameled, spaced about ¼-inch from bottoms of grid coils, except for L_4 -G, which is interwound with L_3 .

calibration which ensures that the mixer is tuned to the desired signal rather than to the image.

On the broadcast band, the tuning range is such that, with C_2 set at 1500 ke., the entire band will be covered on C_3 . It is necessary, however, to change the tap on the mixer coil to make the antenna circuit cover the entire band. Only one oscillator coil is needed for the range from 75 to 1500 ke., but a series of coils is needed to cover the same range in the mixer circuit.

Adding an audio stage to the three-tube superheterodyne — The three-tube receiver just described is designed for headphone operation, but readily can be converted to a four-tube set for use with a speaker. For this purpose a 6F6 pentode can be added to the circuit diagram, as shown in Fig. 1219. Figs. 1218 and 1220 show the receiver when completed.

For the purpose of driving the audio stage, resistance coupling is used from the plate of the second detector to the grid of the 6F6. A volume control is used for the grid resistor of the 6F6, and a jack is installed in the second-detector plate circuit so that a headphone plug may

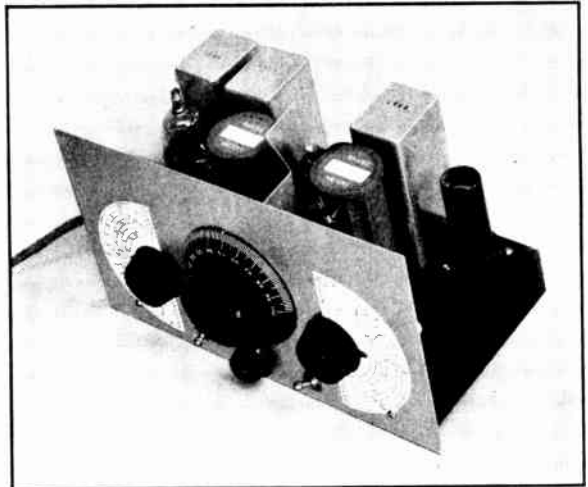
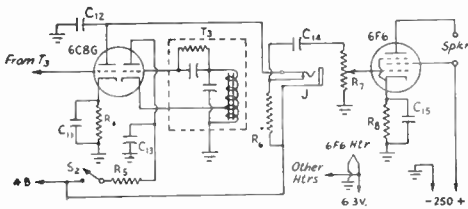


Fig. 1218 — The modified three-tube superheterodyne receiver with the audio amplifier stage added for loudspeaker operation.

C_{14} , and the plate resistor, R_6 , are mounted on an insulated lug strip near the volume control.

The 6F6 will require a plate supply of 250 volts at about 40 milliamperes. This may be taken from a regular power pack, and a five-wire connection cable is used to provide an extra lead for the purpose. The first three tubes

Fig. 1219 — Circuit diagram of the single-tube pentode audio-amplifier stage which may be added for loudspeaker operation of the three-tube superheterodyne. Except as noted below, the values for components correspond to those bearing the same designations in Fig. 1214.
 C_{14} — 0.1- μ fd. paper.
 C_{15} — 25- μ fd. electrolytic, 50 volts.
 R_6 — 120,000 ohms, $\frac{1}{2}$ watt.
 R_7 — 500,000-ohm volume control.
 R_8 — 100 ohms, 1 watt.
 J — Closed-circuit jack.

be inserted. The volume control, R_7 , should be of the midjet type so that it will fit in the chassis; it is installed with its shaft projecting under the tuning dial. In the bottom view, Fig. 1220, the 6F6 socket is in the upper left corner, along with the cathode resistor and by-pass condenser, R_8 and C_{15} . The coupling condenser,

may be operated from a "B" battery, as before. Alternatively, the power supply may be constructed with a tap giving 90 or 100 volts for these tubes, the tap being connected to the proper wire in the connection cable. For best performance, the output voltage should be regulated by a VR105-30 regulator tube.

A suitable power-supply circuit is shown in Fig. 1207-A. In this case the value of R should be 5000 ohms, 10 watts.

The primary winding of the speaker output transformer always should be connected in the plate circuit of the 6F6. Operation without the plate circuit closed is likely to damage the screen-grid. Any speaker having a transformer with a primary impedance of 7000 ohms will be satisfactory; a permanent-magnet dynamic is convenient, since no field supply for the speaker is necessary.

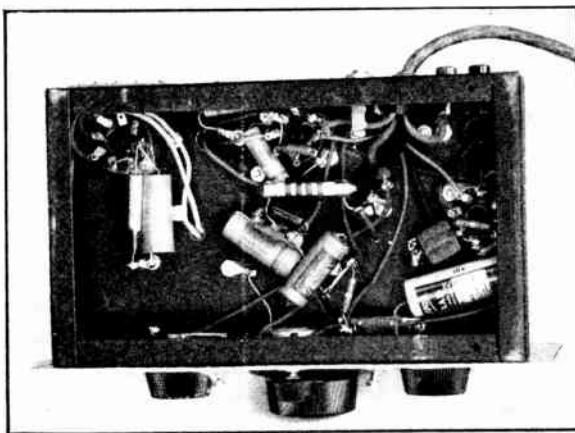


Fig. 1220 — The additional parts for the audio output stage can be identified in this sub-chassis view of the three-tube receiver.

□ A Regenerative Single-Signal Receiver

An inexpensive amateur-band receiver using i.f. regeneration for single-signal reception is shown in Fig. 1221. Fig. 1223 gives the circuit diagram. Regeneration also is used in the mixer circuit to improve the signal-to-image ratio and to give added gain. This receiver is designed to give the maximum of performance, in the hands of a capable operator, at minimum cost; selectivity, stability and sensitivity are the primary considerations.

The mixer, a 6SA7, is coupled to the antenna and is separately excited by a 6J5 oscillator. There is a single 460-ke. i.f. stage, using a 6SK7 and permeability-tuned transformers. The second detector and first audio amplifier is a 6SQ7, and the audio output tube for loud-speaker operation is a 6F6. The separate beat-oscillator circuit uses a 6C5. A VR105-30 voltage-regulator tube is used to stabilize the plate voltage on the oscillators and the screen voltage on the mixer and i.f. tubes.

To make construction easy and to avoid the necessity for additional trimmer condensers on each coil, the mixer and high-frequency oscillator circuits are separately tuned. Main tuning is by the oscillator bandspread condenser, C_3 , which is operated by the calibrated dial. C_2 is the oscillator band-setting condenser. The mixer circuit is tuned by C_1 . Regeneration in this circuit is controlled by R_{15} , connected across the mixer tickler coil, L_3 .

R_{16} is the i.f.-amplifier gain control, which also serves as an i.f. regeneration control when this stage is made regenerative. C_{15} is the regeneration condenser; it is adjusted to feed back a small amount of i.f. energy from the plate to the grid of the 6SK7, and thus produce regeneration. If the high selectivity afforded by i.f. regeneration is not wanted, C_{15} may be omitted.

Diode rectification is used in the second-detector circuit. One of the two diode plates in the 6SQ7 is used for developing a.v.c. voltage, being coupled through C_{22} to the detector diode. The detector load resistor consists of R_5 and R_7 in series, the tap being used for r.f. filtering of the audio output to the triode section of the tube. R_{18} is the a.v.c. load resistor; R_9 , C_{14} and C_{12} constitute the a.v.c. filter circuit. S_2 cuts the a.v.c. out of circuit by grounding the rectifier

output. The headphones are connected in the plate circuit of the triode section of the 6SQ7. R_{17} is the audio volume control potentiometer.

The top and bottom views, Figs. 1222 and 1224, show the layout clearly. The bandspread tuning condenser, C_3 , is at the front center; at the left is C_1 , the mixer tuning condenser; and at the right, C_2 , the oscillator band-set condenser. The oscillator tube is directly behind C_3 , with the mixer tube to the left on the other side of a baffle shield which separates the two r.f. sections. This shield, measuring $4\frac{1}{4} \times 4\frac{1}{2}$ inches, is used to prevent coupling between oscillator and mixer. The mixer coil socket is at the left behind C_1 ; the oscillator coil socket is between C_2 and C_3 .


The i.f. and audio sections are along the rear edge of the chassis. The transformer in the rear left corner is T_1 ; next to it is the i.f. tube, then T_2 . Next in line is the 6SQ7, followed by the 6C5 beat oscillator, the b.o. transformer, T_3 , and finally the 6F6. The VR105-30 is just in front of T_3 . The i.f. transformers should be mounted with their adjusting screws projecting to the rear where they are easily accessible.

The beat oscillator is coupled to the second detector by the small capacity formed by running an insulated wire from the grid of the 6C5 close to the detector diode plate prong on the 6SQ7 socket. Very little coupling is needed for satisfactory operation.

In wiring the i.f. amplifier, keep the grid and plate leads from the i.f. transformers fairly close to the chassis and well separated. Without C_{15} , the i.f. stage should be perfectly stable and should show no tendency to oscillate at full gain.

The method of winding the plug-in coils is shown in Fig. 1225, and complete specifications are given in the coil table. Ticklers (L_3) for the mixer circuit are scramble-wound to a diameter which will fit readily inside the coil form and mounted on stiff leads going directly

Fig. 1221 — A 7-tube superheterodyne using regeneration in the i.f. amplifier to give single-signal reception and improved image ratio. The dial (National ACN) may be directly calibrated for each amateur band. The chassis is $11 \times 7 \times 2$ inches and the panel 7×12 inches. The controls along the bottom edge of the panel are, from left to right, the mixer regeneration control, R_{15} , the i.f. gain control, R_{16} , the audio volume control, R_{17} , and the beat-oscillator vernier condenser, C_{21} . The latter has the corner of one rotor plate bent over so that when the condenser plates are fully meshed the tuned circuit is short-circuited, thus stopping the b.f.o. oscillation.

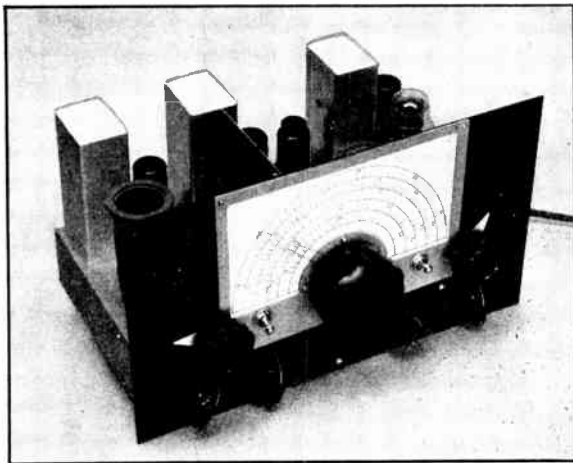

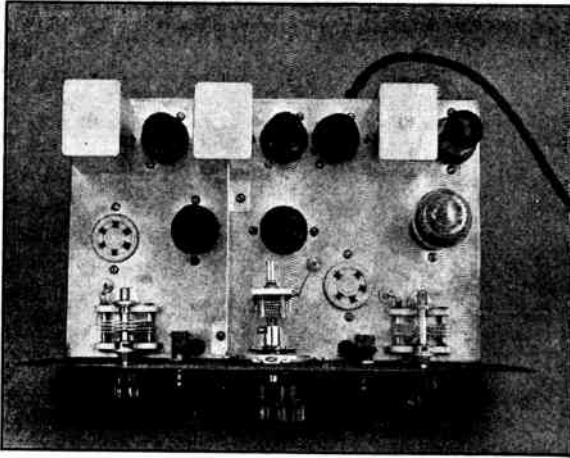


Fig. 1222 — Top view of the 7-tube superheterodyne with plug-in coils removed. Placement of the parts is discussed in the text.

to the proper pins in the form. The leads should be long enough to bring the coils inside the grid winding at the bottom. The amount of feed-back is regulated by bending the tickler coil with respect to the grid coil. Maximum feed-back is secured with the two coils coaxial, minimum when the tickler axis is at right angles to the axis of L_1 . The position of L_3 should be adjusted so that the mixer goes into oscillation with R_{15} set at one-half to three-fourths of its maximum resistance.

Alignment — The oscillator circuit has been adjusted to make the proper value of rectified grid current flow in the 6SA7 injection-grid (No. 1) circuit on each amateur band. This calls for a fairly strong value of feedback, with the result that when the band-set condenser is set toward the high-frequency end of its range the oscillator may "squeg." This is of no consequence unless the receiver is to be used for listening outside the amateur bands, in which case it may be corrected by taking a few turns off the tickler coil, L_5 . This can be done only at some sacrifice of conversion efficiency in the amateur band for which the coil was designed, however.

The i.f. amplifier can be aligned most conveniently with the aid of a modulated test oscillator. The initial alignment should be made with C_{15} disconnected so that the performance of the amplifier in a non-regenerative condition can be checked. Headphones or a loudspeaker may be used as an output indicator. The mixer and oscillator coils should be out of their sockets, and R_{15} should be set at zero resistance.

Connect the test oscillator output across C_1 , which should be set at minimum capacity. Adjust the test-oscillator frequency to 460 kc. Then, using a modulated signal, adjust the trimmers on T_1 and T_2 for maximum volume.

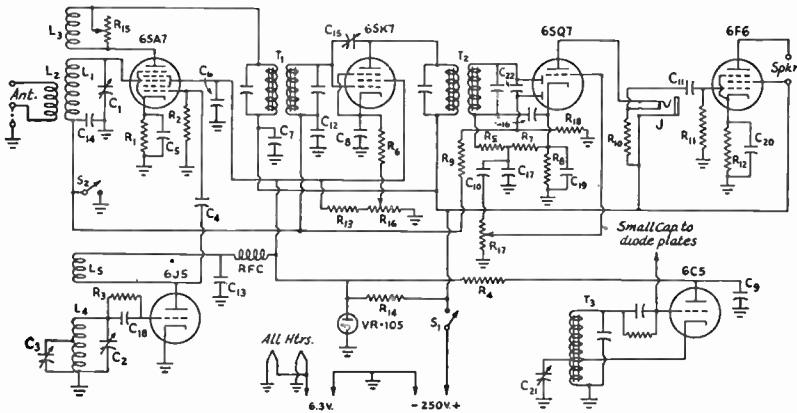


Fig. 1223 — Circuit diagram of the single-signal superheterodyne receiver with regenerative i.f. and mixer stages.

- C_1, C_2 — 50- μ fd. variable (Hammarlund MC-50-S).
- C_3 — 35- μ fd. variable (National UM-35).
- C_4 — 50- μ fd. mica.
- C_5, C_6, C_7, C_8 — 0.1- μ fd. paper, 600 volts.
- $C_9, C_{10}, C_{11}, C_{12}$ — 0.01- μ fd. paper, 600 volts.
- C_{13}, C_{14} — 0.005- μ fd. mica.
- C_{15} — 3-30- μ fd. trimmer (National M-30); see text.
- C_{16} — 250- μ fd. mica.
- C_{17}, C_{18}, C_{22} — 100- μ fd. mica.
- C_{19}, C_{20} — 25- μ fd. electrolytic, 50 volts.
- C_{21} — 25- μ fd. variable (Hammarlund SM-25).
- R_1 — 200 ohms, $\frac{1}{2}$ watt.
- R_2 — 20,000 ohms, $\frac{1}{2}$ watt.
- R_3, R_4, R_5 — 50,000 ohms, $\frac{1}{2}$ watt.
- R_6 — 300 ohms, $\frac{1}{2}$ watt.
- R_7 — 0.2 megohm, $\frac{1}{2}$ watt.
- R_8 — 2000 ohms, $\frac{1}{2}$ watt.
- R_9 — 1 megohm, $\frac{1}{2}$ watt.
- R_{10} — 0.1 megohm, $\frac{1}{2}$ watt.
- R_{11} — 0.5 megohm, $\frac{1}{2}$ watt.
- R_{12} — 450 ohms, 1 watt.
- R_{13} — 75,000 ohms, 1 watt.
- R_{14} — 5000 ohms, 10 watts.
- R_{15} — 10,000-ohm volume control (mixer regeneration).
- R_{16} — 25,000-ohm volume control (i.f. regeneration).
- R_{17} — 2-megohm volume control.
- R_{18} — 2 megohms, $\frac{1}{2}$ watt.
- T_1 — 460-ke. permeability-tuned i.f. transformer, interstage type (Millen 64456).
- T_2 — 460-ke. permeability-tuned i.f. transformer, diode type (Millen 64454).
- T_3 — 460-ke. heat-oscillator transformer (Millen 65456).
- RFC — 2.5-mh. r.f. choke.
- J — Closed-circuit jack.
- S_1, S_2 — S.p.s.t. toggle.
- L_1-L_5 , inc. — See coil table.

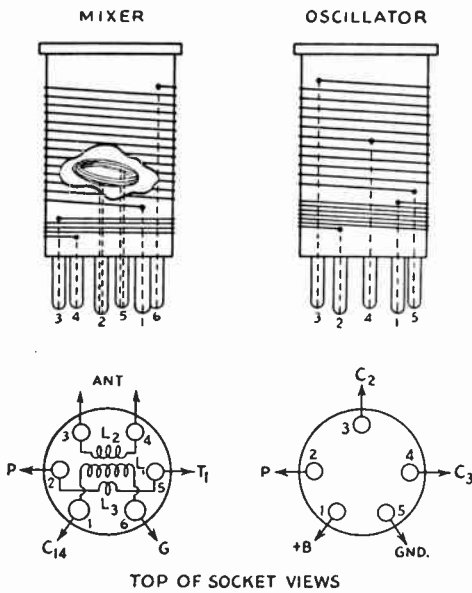


Fig. 1225 — Mixer and oscillator coil and socket connections for the seven-tube superheterodyne receiver.

R_{16} should be set for maximum gain, and the beat oscillator should be off. As the successive circuits are brought into line, reduce the oscillator output to keep from overloading any of the amplifiers, since overloading might cause a false indication.

After the i.f. is aligned, plug in a set of coils for some band on which there is a good deal of activity. Set the oscillator padding condenser, C_2 , at approximately the right capacity; with the coil specifications given, the proportion of the total capacity of C_2 in use on each band will be about as follows: 1.75 Mc., 90 per cent; 3.5 Mc., 75 per cent; 7 Mc., 95 per cent; 14 Mc., 90 per cent; 28 Mc., 45 per cent. Set the mixer regeneration control, R_{15} , for minimum regeneration — i.e., with no resistance left in the circuit.

Now connect an antenna to the input terminals for L_2 . Switch the beat oscillator on by turning C_{21} out of the maximum position, and adjust the trimmer screw on T_3 until the characteristic beat-oscillator hiss is heard.

Next tune C_1 slowly over its scale, starting from maximum capacity. Using the 7-Mc. coils as an example, when C_1 is at about half scale there should be a definite increase in the noise level as well as in the strength of the signals which may be heard. Continue on past this point toward minimum capacity until a second peak is reached on C_1 ; at this peak the input circuit is tuned to the frequency which represents an image

in normal reception. The oscillator in the receiver is designed to work on the high-frequency side of the incoming signal, so that C_1 always should be tuned to the peak which occurs with most capacity.

After the signal peak on C_1 has been identified, tune C_3 over its whole range, following with C_1 to keep the mixer circuit in tune, to see how the band fits the dial. With C_2 properly set, the band edges should fall the same number of main dial divisions from 0 and 100; if the band runs off the low-frequency edge, less capacity is needed at C_2 , while the converse is true if the band runs off the high edge. Once the band is properly centered on the dial, the panel may be marked at the appropriate point so that C_2 may be reset readily when changing bands.

To check the operation of the mixer regeneration, tune in a signal on C_3 , adjust C_1 for maximum volume, and slowly advance the regeneration control, R_{15} . As the resistance is increased, retune C_1 to maximum volume, since the regeneration control will have some effect on the mixer tuning. As regeneration is increased signals and noise both will become louder, and C_1 will tune more sharply. Finally the mixer circuit will break into oscillation and, when C_1 is right at resonance, a loud carrier will be heard, since the oscillations generated will go through the receiver in exactly the same way as an incoming signal. As stated before, oscillation should occur with R_{15} set at from one-half to three-quarters full scale. In practice, it is best always to work with the mixer somewhat below the critical regeneration point and never permit it actually to oscillate. On the lower frequencies, where images are less serious, the tuning is less critical if the mixer is made non-regenerative. In this case, always set the regeneration control at zero, since there will be a range on the resistor where, without definite regeneration, the signal strength will be less than it is with zero resistance.

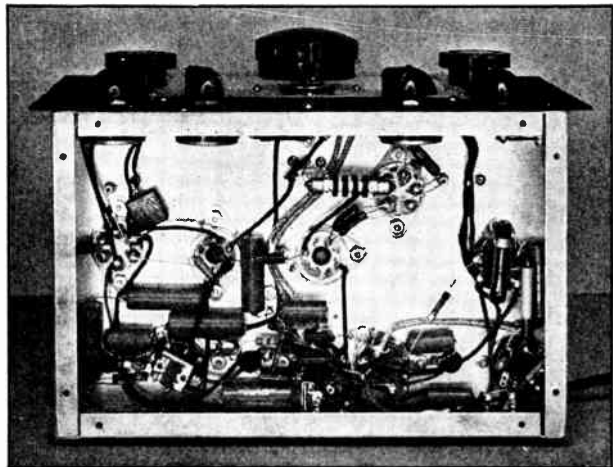


Fig. 1224 — The below-chassis wiring and location of parts is shown in this bottom view of the seven-tube regenerative single-signal receiver.

Should the mixer fail to oscillate, adjust the coupling by changing the position of L_3 with respect to L_1 . If the two coils happen to be "poled" incorrectly, the circuit will not oscillate. This condition can be cured by rotating L_3 through 180 degrees. It is recommended that the mixer regeneration be tested first with the antenna disconnected, since antenna loading effects may give misleading results until it is known that L_3 is properly adjusted to produce oscillation.

After the preceding adjustments have been completed the i.f. regeneration may be added. Install C_{15} , taking out the adjusting screw and bending the movable plate to make an angle of about 45 degrees with the fixed plate. Realign the i.f. As the circuits are tuned to resonance the amplifier will oscillate, and each time this happens the gain control, R_{16} , should be backed off until oscillations cease. Adjust the trimmers to give maximum output with the lowest setting of R_{16} . At peak regeneration the signal strength should be about the same with this setting, despite reduced gain in the amplifier, as it is without regeneration at full gain. Too much gain with regeneration will have an adverse effect on the selectivity.

For single-signal c.w. reception, set the beat oscillator so that, when R_{16} is advanced to make the i.f. stage just go into oscillation, the resulting tone is the desired beat-note frequency. Then back off on R_{16} to obtain the desired degree of selectivity. Maximum selectivity will be

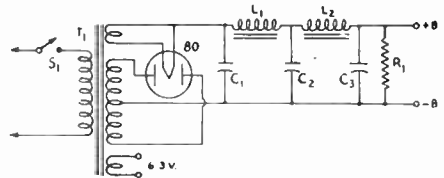


Fig. 1226 — Power-supply for the regenerative superhet.

- C_1, C_2 — 8- μ fd. electrolytic, 450 volts.
- C_3 — 16- μ fd. electrolytic, 450 volts.
- R_1 — 25,000 ohms, 10 watts.
- L_1, L_2 — 12 henrys, 80 ma., 400 ohms.
- T_1 — 350 volts each side of center-tap, 80–90 ma.; 6.3 volts at 2.5 amperes or more; 5-volt 2-ampere rectifier-filament winding.
- S_1 — S.p.s.t. toggle switch.

Dual-unit electrolytic condensers may be used. This supply will give 275 to 300 volts with full receiver load.

secured with the i.f. amplifier just below the oscillating point. The "other side of zero beat" will be much weaker than the desired side.

A useful feature of the bandspread dial is that it can be directly calibrated in frequency for each band. These calibrations may be made with the aid of a 100-ke. oscillator, such as is described in Chapter Twenty. Ten-kilocycle points can be plotted if a 10-ke. multivibrator is available, but, since the tuning is almost linear in each band, a fairly accurate plot will result if each 100-ke. interval is simply divided off into ten equal parts when the dial calibrations are marked.

The power-supply requirements for the receiver are 2.2 amperes at 6.3 volts for the heaters and 80 ma. at 250 volts for the plates. Without the 6F6 pentode output stage, a supply giving 6.3 volts at 1.5 amperes and 250 volts at 40 ma. would be sufficient. The circuit of a suitable power supply is given in Fig. 1226.

◀ A 12-Tube Crystal-Filter Receiver

The 12-tube single-signal super heterodyne receiver with crystal filter shown in the photographs of Figs. 1227, 1228 and 1230 was built by W4CBD. It is representative of the more elaborate amateur-constructed receivers. The circuit diagram is shown in Fig. 1229.

The r.f. section consists of two stages of tuned r.f. amplification using 6SK7s, a 6SA7 mixer and a 6J5 h.f. oscillator. The tuning condensers of these stages, C_1, C_2, C_3 and C_4 are ganged together and operated by the main tuning dial. The two r.f. stages are similar except that the first stage is not tied into the a.v.c. circuit. While the first tube runs at maximum gain all the time, a grid resistor inserted in the ground return protects the tube against strong r.f. fields. A.v.c. is applied only to the second r.f. tube and the mixer. This provides sufficient a.v.c. action while it also produces a greater deflection of the signal meter than would be obtained with more stages tied to the a.v.c. line. The manual r.f. gain control, R_{11} , controls all stages except the second r.f. stage. C_{18} is used to neutralize the

COIL DATA FOR 7-TUBE SUPERHET				
Band	Coil	Wire		Tap
		Size	Turns	
1.75 Mc.	L_1	24	70	Close-wound
	L_2	24	15	" "
	L_3	22	15	" "
	L_4	22	42	Close-wound
3.5 Mc.	L_5	24	15	" "
	L_1	22	35	" "
	L_2	22	9	" "
	L_3	22	12	" "
7 Mc.	L_4	22	25	1 inch
	L_5	22	10	Close-wound
	L_1	18	20	1 inch
	L_2	22	5	Close-wound
	L_3	22	9	" "
14 Mc.	L_4	18	14	1 inch
	L_5	22	6	Close-wound
	L_1	18	10	1 inch
	L_2	22	5	Close-wound
	L_3	22	7	" "
28 Mc.	L_4	18	7	1 inch
	L_5	22	4	Close-wound
	L_1	18	4	1 inch
	L_2	22	4	Close-wound
	L_3	22	1.5	" "
	L_4	18	3 6	1 inch
	L_5	22	2 4	Close-wound

All coils except L_3 are 1 1/2 inches in diameter, wound with enameled wire on Hammarlund SWF forms. Spacing between L_1 and L_2 , and between L_4 and L_5 , is approximately 1/2 inch. Bandspread taps are counted from bottom (ground) end of L_4 .

L_3 for 28 Mc. is interwound with L_1 at the bottom end. L_3 for all other coils is self-supporting, scramble-wound to a diameter of 3/4 inch, mounted inside the coil form near the bottom of L_1 .

space-charge coupling between No. 1 grid and the signal grid of the mixer tube.

For general coverage the tuning condensers in the r.f. and mixer stages are connected across the entire coil. C_5 , C_6 and C_7 are air trimmers ganged to one of the small controls along the lower part of the panel. Since the stray capacities in the mixer stage are slightly higher than in the r.f. stages, C_8 and C_9 are added to permit compensation. Two sets of coils are required to cover the frequencies between one amateur band and the next. Although this means quite a few coils, it provides a good degree of bandsread for even the general-coverage ranges.

When bandsread tuning is desired, the main tuning condensers are tapped down on the coils of the r.f. and mixer stages by a switching system in the bottom of the coil form, as shown in the detail photograph and the sketch of Fig. 1231. This connection would cause considerable non-linearity in calibration, with crowding at one end of the scale, were it not for the fixed padder condensers C_{15} , C_{16} , C_{17} , and C_{18} . C_{18} is an air-insulated condenser which is mounted inside the oscillator shield compartment. After it is set initially to about 25 $\mu\text{fd.}$, no further adjustment is required. The other condensers are mica units, especially selected for equal capacities.


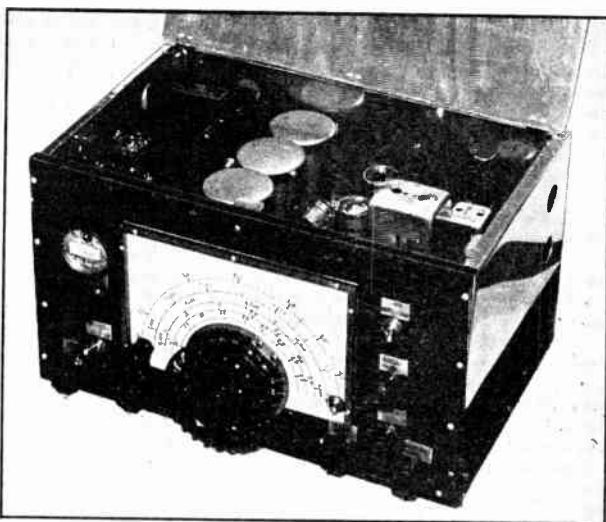


Fig. 1227 — Panel view of the completed 12-tube receiver. Below the "S" meter are the b.f.o. tuning control, the power switch, the stand-by switch and the r.f. gain control. The ganged-trimmer control is in the lower left-hand corner of the dial chart. To the right are the b.f.o. switch, the audio gain control and the crystal-filter and noise-silencer adjusting knobs. The a.v.c. switch is in the lower right-hand corner of the dial chart. This view shows the shield cans in place over the coils.

The mixer output transformer feeds the grids of the first i.f. stage and the 6J7 noise-amplifier stage in parallel while the crystal filter is coupled to the output of the 6L7. The 6J7 amplifies the noise and the 6H6 rectifies the noise and applies the d.c. impulse to the injector grid of the 6L7, cutting it off for the duration of the noise impulse. K_{20} provides the threshold adjustment. The output of the crystal filter is coupled to the input of the second i.f. amplifier which feeds the diode second detector.

The 6H6 second detector is connected so that one section handles the audio signal while the other section supplies a.v.c. voltage. In this arrangement a bias of several volts is placed on the a.v.c. side, since the cathode of the 6H6 is returned to the 6J5 au-flo cathode rather than

Fig. 1228a — Plan view of the crystal-filter, single-signal superhet receiver. To the left, from front to rear are the "S" meter, filter condensers, b.f.o. tube and tank circuit (T_1), filter choke, rectifier tube and power transformer. The line of empty sockets are for the plug-in coils of the first and second r.f. stages, the mixer and the h.f. oscillator in order from front to rear. The parallel line of corresponding tubes is to the right. The h.f. oscillator tube is hidden by the voltage-regulator tube mounted on the panel. The two shielded transformers to the right near the panel are the crystal-filter input and output transformers, T_4 and T_5 . In line in back of T_4 are the 6L7, the first i.f. transformer, T_3 , the 6J7 and the 6H6 noise rectifier. Along the right-hand edge of the chassis, from front to back, are the 6K7, the diode coupling transformer, T_6 , the 6H6 second detector and the two audio tubes. Between the two lines are the crystal and noise-silencer transformer, T_7 .

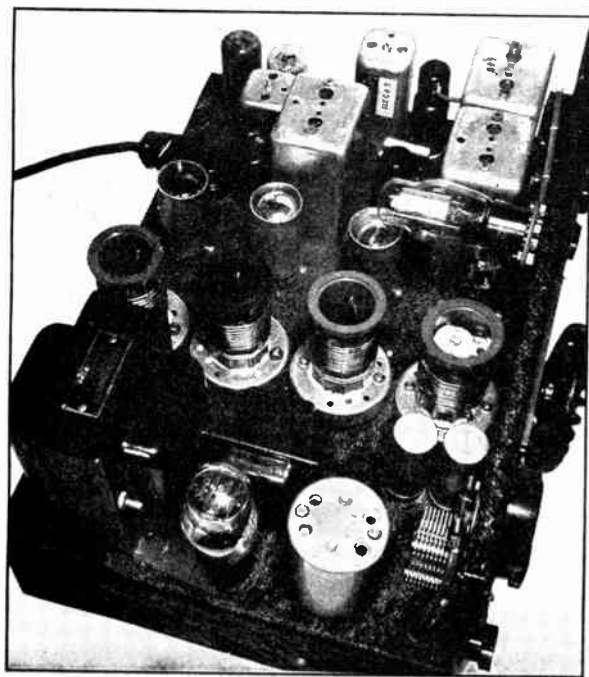

to ground. Because the 6J5 cathode is above ground for d.c., no a.v.c. action is obtained until the signal level exceeds the bias. Thus a.v.c. action causes no reduction in sensitivity for weak signals. The delayed a.v.c. effect can be further manipulated by adjustment of the r.f. and audio gain controls.

The beat-oscillator circuit is similar to that used in the h.f. oscillator. It is operated at a fairly low level and the output to the diode detector is taken from the cathode. Thorough shielding of the lead to the 6H6 is important, since it is about 24 inches long. The tuning condenser, C_{14} , is connected from cathode to

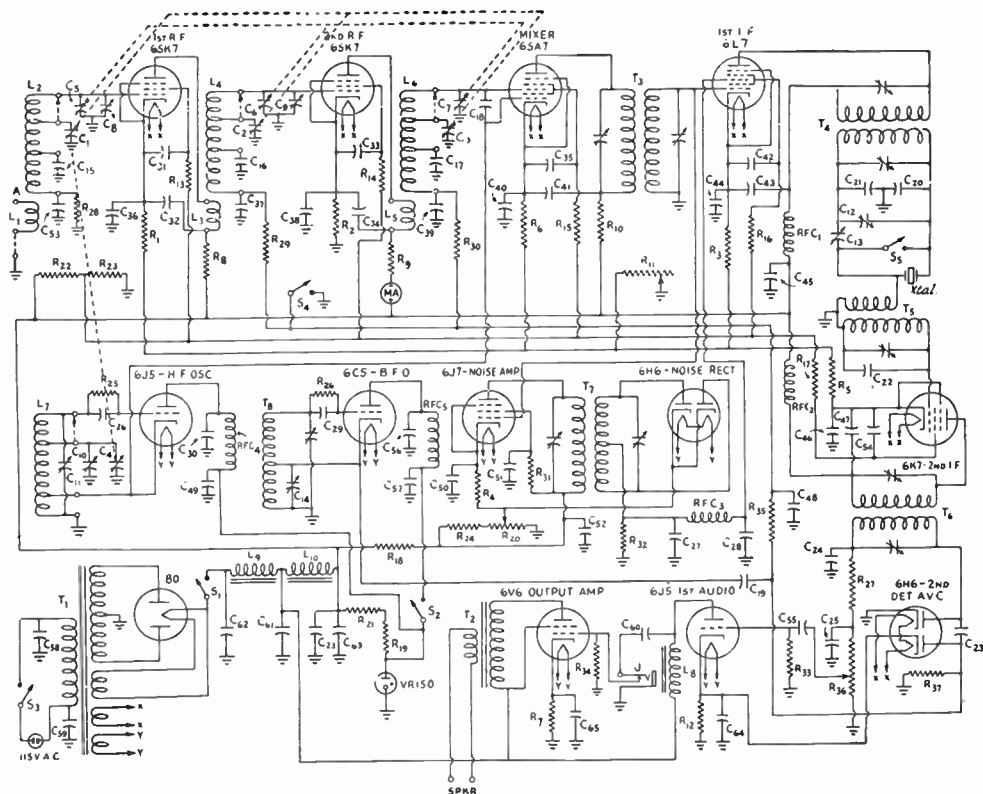


Fig. 1229 — Circuit diagram of the ham-band receiver.

- C_1, C_2, C_3, C_4 — 50- μ fd. ganged tuning condensers.
- C_5, C_6, C_7 — 15- μ fd. ganged r.f. and mixer trimmers.
- C_8, C_9 — 15- μ fd. variable (stray-capacity equalizer).
- C_{10} — 50- μ fd. variable air padder (see text).
- C_{11} — Oscillator padder inside L_7 (see coil table).
- C_{12} — 50- μ fd. variable (crystal selectivity control).
- C_{13} — 15- μ fd. variable (rejection control).
- C_{14} — 140- μ fd. variable (b.o. tuning control).
- C_{15}, C_{16}, C_{17} — 25- μ fd. fixed mica padder.
- C_{18} — Approximately 1 μ fd. (twisted insulated leads).
- C_{19} — 10- μ fd. mica.
- C_{20}, C_{21}, C_{22} — 50- μ fd. mica.
- $C_{23}, C_{24}, C_{25}, C_{26}, C_{27}, C_{28}$ — 100- μ fd. mica.
- C_{29} — 0.001- μ fd. mica.
- $C_{30}, C_{31}, C_{32}, C_{33}, C_{34}$ — 0.002- μ fd. paper, 600 volts.
- $C_{35}, C_{36}, C_{37}, C_{38}, C_{39}, C_{40}, C_{41}, C_{42}, C_{43}, C_{44}, C_{45}, C_{46}$ — 47, 48, 49, 50, 51 — 0.01- μ fd. paper.
- $C_{52}, C_{53}, C_{54}, C_{55}, C_{56}, C_{57}, C_{58}, C_{59}, C_{60}$ — 0.1- μ fd. paper.
- C_{61}, C_{62}, C_{63} — 8- μ fd. electrolytic, 450 volts.
- C_{64}, C_{65} — 40- μ fd. electrolytic, 25 volts.
- R_1, R_2, R_3 — 250 ohms, 1 watt.
- R_4, R_5 — 100 ohms, 1 watt.
- R_6 — 500 ohms, 1 watt.
- R_7 — 500 ohms, 10 watts, wire-wound.
- R_8, R_9, R_{10} — 1000 ohms, 1 watt.
- R_{11} — 1000-ohm r.f. gain control, wire-wound.
- R_{12} — 1500 ohms, 1 watt.
- $R_{13}, R_{14}, R_{15}, R_{16}, R_{17}, R_{18}$ — 2000 ohms, 1 watt.
- R_{19} — 5000 ohms, 10 watts, wire-wound.
- R_{20} — 5000-ohm potentiometer (silencer gain control).

- R_{21} — 7000 ohms, 10 watts, wire-wound.
- R_{22} — 10,000 ohms, 10 watts, wire-wound.
- R_{23} — 15,000 ohms, 10 watts, wire-wound.
- R_{24} — 20,000 ohms, 1 watt.
- R_{25}, R_{26}, R_{27} — 50,000 ohms, 1/2 watt.
- $R_{28}, R_{29}, R_{30}, R_{31}, R_{32}$ — 100,000 ohms, 1 watt.
- R_{33}, R_{34} — 500,000 ohms, 1/2 watt.
- R_{35} — 1 megohm, 1/2 watt.
- R_{36} — 1-megohm audio gain control.
- R_{37} — 2 megohms, 1/2 watt.
- $L_1, L_2, L_3, L_4, L_5, L_6, L_7$ — See coil table.
- L_6 — Audio coupling impedance (primary winding of audio transformer).
- L_9 — Filter choke (Thorndarson T-849C41).
- T_1 — Power transformer (Thorndarson T-87R85).
- T_2 — Speaker output transformer, universal type.
- T_3 — 465-ke. air-tuned i.f. transformer.
- T_4 — 465-ke. i.f. transformer altered (see text).
- T_5 — 465-ke. b.f.o. unit (see text).
- T_6 — 465-ke. diode input transformer.
- T_7 — 465-ke. diode input transformer (see text).
- T_8 — 465-ke. b.f.o. unit.
- RFC1, RFC2, RFC3 — Approximately 11 mh. (replacement 175-ke. i.f. coil).
- RFC4, RFC5 — 2.5-mh. r.f. choke.
- S_1 — S.p.d.t. switch.
- S_2, S_3, S_4 — S.p.s.t. switch.
- S_5 — Crystal-filter switch (see text).
- J — Double-circuit jack.
- M — Signal-strength meter (7-ma. movement).

ground to keep the r.f. voltage across it low and thus minimize pickup in neighboring r.f. circuits. This connection makes it necessary to use the unusually large capacity of 140 μfd . to cover the desired frequency range. The amount of oscillator voltage fed into the detector is low enough so that good limiting of volume on c.w. signals is obtained, and the hiss level is low.

A power-supply unit is built into the receiver. High voltage for the audio section is taken from a tap at the output of the first filter section. The field of the external speaker is used as the inductance in an additional filtering section for the voltage which supplies the other stages. The VR150 voltage-regulator tube holds the plate voltage for the two oscillators constant.

Construction — The chassis is formed from 0.050-inch sheet steel. Reinforcing braces were spot welded in the corners and L-shaped strips are added along the bottom edges of the chassis for reinforcement and to form a shelf to which the bottom cover could be attached with sheet-metal screws. The cover plate is equipped with rubber mounting feet, one at each corner. The panel is formed from 0.062-inch sheet steel. A $\frac{1}{2}$ -inch edge with a slight radial bend was formed along the top. All holes

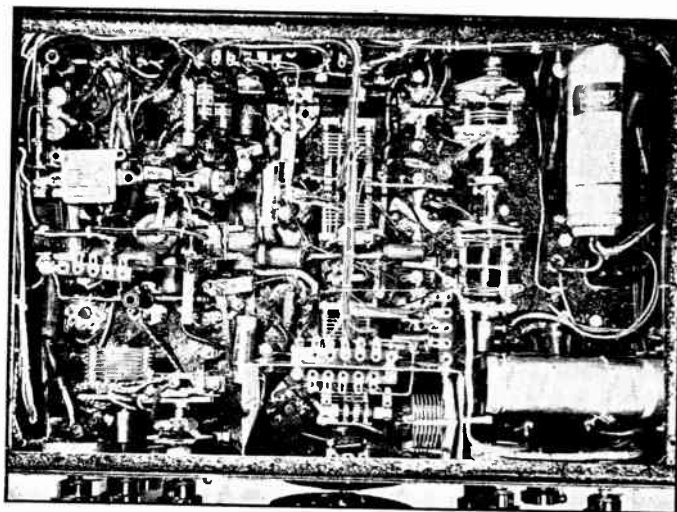


Fig. 1230 — Bottom view of the twelve-tube superheterodyne. The four gang tuning-condenser is at the center. The ganged trimmers, C_5 , C_6 and C_7 , are at the right, while the crystal-filter selectivity control, C_{12} , and phasing condenser, C_{13} , are near the front at the left. C_8 and C_9 are fastened to C_5 and C_6 , respectively. A separate shielded compartment at the center contains the h.f. oscillator components, with C_{10} at the right. By-pass condensers are placed close to the points to be by-passed and other small parts are placed in the nearest available space. The electrolytic units at the right are power filter condensers.

are drilled first, and later everything is given a thick coat of baked-on crackle enamel.

The tuning control, built around a National Velvet Vernier dial mechanism, is similar to the ACN model except that it is larger. The ACN may be substituted if available. The handwheel is a 4-inch valve-control knob.

The general lay-out plan of the receiver is shown quite clearly in the photographs. The main essential is, of course, the close grouping of components in the high-frequency stages. All parts, especially those forming the various tuned circuits, should be mounted with good mechanical anchoring to prevent any slight movement which might cause a noticeable change in frequency. Care should be exercised in lining up the units of the ganged condensers so that they will not spring when the shaft is turned. All r.f. wiring should be made as short as possible and kept well spaced from the chassis. Power wiring may be cabled and laid flat against the chassis wherever it is convenient to do so.

Coils — All of the coils in each set shown in the table are wound to be as nearly identical as possible. The r.f. and mixer coils are then adjusted to exactly the same inductance by spacing the turns and heavily doping all but one or two turns at one end with clear nail polish. When the dope has set, a further adjustment may be made by moving the free turns on the end and then cementing them firmly in place. The inductance of the coils can be checked by interchanging two coils at a time in the r.f. stages. If there is a difference in inductance, the stray-capacity equalizers, C_8 and C_9 , will have to be readjusted when the

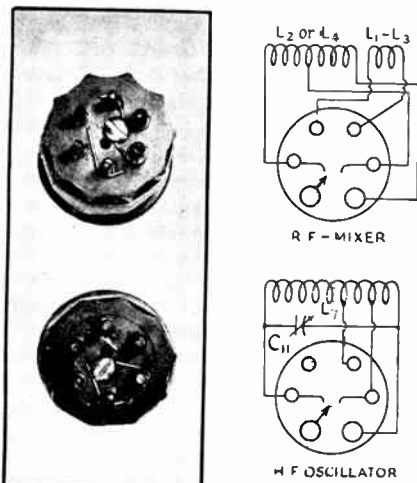


Fig. 1231 — Pin connections for the r.f. and h.f. coil forms for the 12-tube superhet.

The bottom views of the coil forms in the photograph show the bandspread switching arrangement. The screw head completes the connection between either pair of pins, depending upon its position (see sketch at right).

coils are interchanged. When the inductance of the three coils is adjusted correctly, it should be possible to place the coils in the three positions in any sequence without necessity for readjustment of any trimmer to restore resonance.

The i.f. coupling transformers are modified to fit the circuits. About one-fourth of the turns should be removed from the secondary of T_4 , and C_{20} and C_{21} are mounted inside the shield can. The primary and secondary windings should be pushed a little closer together. T_5 is a b.f.o. unit. The tie-ker winding should be replaced with a 100-turn coil of No. 34 enameled wire, which becomes the new primary. The two windings are placed close together for tight coupling. A 50- μ fd. fixed condenser, C_{22} , must be added to the secondary to hit resonance at 465 kc. An auxiliary brass contact is added to C_{13} , so that the crystal may be shorted out for straight operation. T_6 is tuned by a mica trimmer, but may be replaced by an air-insulated trimmer if drift is excessive.

Adjustment — With the minimum and stray capacities in each stage set at the same

value, it is easy to secure good tracking of the r.f. circuits. It is necessary for them to track accurately, since the over-all selectivity of the three resonant r.f. circuits is high. If one of the circuits is detuned by moving a trimmer 2 or 3 μ fd. away from resonance, the signal meter will indicate a drop of several db.

When the adjustment of C_{18} is correct, there is no observable interaction between the oscillator and mixer tuning. Should there be any, the bias on the signal grid should be checked. It should be at least 5 volts.

If during the adjustment of the crystal filter it is found that the rejection control allows rejection of interference on one side of the desired signal but not on the other it may be necessary to add a little capacity, consisting of a pair of twisted wires across the crystal holder, to get the rejection slot to move to the other side of the signal.

◀ The Panoramic Receiver

The panoramic receiver incorporates two signal channels, the channel for audio-output signals normal to a communications-type receiver and an additional channel for reproducing the received signal in visual form on the screen of a cathode-ray tube. The effective acceptance bandwidth of the channel for visual signals usually is made much wider than the channel for audio output — 50 to 100 kc. or more, so that it is possible to observe simultaneously signals over a wide frequency range without destroying the high selectivity for signals delivered to the audio amplifier.

The circuit diagram of an adapter which may be applied to any existing communications-type receiver is shown in Fig. 1234. The signal input to the adapter is taken from the output of the mixer in the receiver. It then passes through a broadly-tuned i.f. stage (6SJ7) at the receiver's i.f. and thence into a second mixer (6SA7) whose output is tuned to 100 kc. The tuning of the oscillator section of this stage is varied over a range of 50 kc. either side of 356 kc. (456 kc., the usual receiver i.f. minus 100 kc.) at a supervisable rate — 25 to 30 times per second — by the 6AC7 reactance modulator. The reactance tube and the horizontal sweep of the 902 cathode-ray tube are driven in synchronism by the 7F7 saw-tooth oscillator. C_{18} is for the purpose of adjusting the phasing between the r.f. plate current and tank voltage of the 6AC7 to the desired value of 90 degrees.

Since the tuning of the r.f. circuits at the front end of the receiver is not swept in this system, the first i.f. stage in the adapter is designed to give a rising characteristic either side of the center frequency to compensate as much as possible for the decreasing characteristic introduced by the selectivity of the r.f. stages. This is done by overcoupling in the input and output transformers of the first 6SJ7 stage.

The 6SA7 mixer is followed by a 6SJ7 i.f. stage tuned to 100 kc. This stage is tuned

COIL TABLE FOR THE 12-TUBE SUPERHETERODYNE

Band	Coil	Turns	Wire Size	Cathode Tap	B.S. Tap
1.7-2.4 Mc.	L_2, L_4, L_6	60	26 d.c.e.	x	x
	L_1, L_3, L_5	8	28 enam.	x	x
	L_7	51	26 d.c.e.	6	47
2.7-4 Mc.	L_2, L_4, L_6	42	22 d.c.e.	x	24
or					
3.5-4 Mc.	L_1, L_3, L_5	8	28 enam.	x	x
	L_7	37	22 d.c.e.	5	20
3.4-4.8 Mc.	L_2, L_4, L_6	30	22 d.c.e.	x	x
	L_1, L_3, L_5	4	22 d.c.e.	x	x
	L_7	25	22 d.c.e.	4	x
4.8-7.2 Mc.	L_2, L_4, L_6	19	22 d.c.e.	x	6 $\frac{3}{4}$
or					
7.0-7.3 Mc.	L_1, L_3, L_5	4	22 d.c.e.	x	x
	L_7	15	22 d.c.e.	3	5 $\frac{3}{4}$
7.0-10 Mc.	L_2, L_4, L_6	14	22 d.c.e.	x	x
	L_1, L_3, L_5	4	22 d.c.e.	x	x
	L_7	12 $\frac{1}{2}$	22 d.c.e.	3	x
10-14.2 Mc.	L_2, L_4, L_6	10 $\frac{1}{2}$	16 bare	x	4
or					
14.0-14.4 Mc.	L_1, L_3, L_5	4	22 d.c.e.	x	x
	L_7	9 $\frac{3}{4}$	16 bare	2 $\frac{3}{4}$	3
22-30 Mc.	L_2, L_4, L_6	5	16 bare	x	x
	L_1, L_3, L_5	4	22 d.c.e.	x	x
	L_7	4 $\frac{1}{2}$	16 bare	2	x

NOTE: All coils are close-wound on 1 $\frac{1}{2}$ -inch diameter forms except L_2, L_4, L_6 and L_7 for the 10- to 14.2-Mc. range, where the turns are spaced the diameter of the wire, and the same coils for the 22- to 30-Mc. range, where the turns are spaced to make the coil length 1 $\frac{1}{4}$ inches. Taps are made the specified number of turns from the bottom or ground ends of the windings.

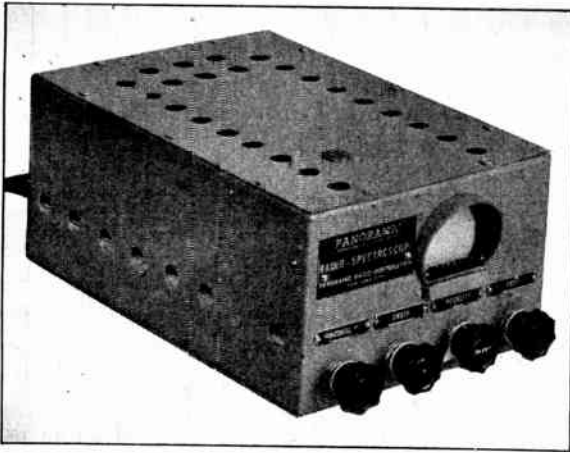


Fig. 1232 — A commercial panoramic adapter. The cathode-ray tube is provided with a scale calibrated in kc. The four controls are for horizontal positioning (R_{19}), sweep (R_{35}), intensity (R_{47}) and gain (R_2). The controls for vertical positioning (R_{17}) and focusing (R_{22}) are mounted in the rear and adjustable by screwdriver.

quite sharply. Thus, while the preceding stages are broadly tuned to cover the "sweep" range, the "instantaneous" selectivity is controlled by this 6SJ7 stage. This selectivity controls the definition or sharpness of the individual signal patterns on the screen.


The signal is rectified and amplified in the 6SQ7 and then applied to the vertical deflection plates of the cathode-ray tube. A typical pattern showing several signals of different amplitudes is shown in Fig. 1235.

Plate and screen voltages for all of the tubes in the adapter as well as anode voltages for the cathode-ray tube are obtained from a voltage-doubling circuit using a 117Z6GT rectifier. The screen voltage for the 6AC7 is held constant by the neon voltage-regulator tube. The various adjusting controls are indicated in the diagram.

The unit shown in Figs. 1232, 1233 and 1236 is a commercial model, but the amateur may build one following the same general lines.

Testing and Alignment — At the positive terminal of C_{22} the voltage to ground should measure 300 volts, approximately, and the

Fig. 1233 — Top view of the panoramic adapter. The socket of the 902 is mounted on a metal plate provided with slots so that the tube may be rotated to place the screen in proper position. The power transformer is immediately behind this plate. Along the top edge, from left to right, are the filter choke, horizontal size control (R_{37}), sweep-oscillator transformer (T_6), the 7F7, sweep-frequency control (R_{33}), and the input i.f. transformer (T_1). In the line of components below the 902, from left to right, are the neon voltage-regulator tube, the 6AC7, a triple condenser unit (C_{21} , C_{22} , C_{23}), the 6SQ7, the mixer-oscillator transformer (T_5) and the first 6SJ7 i.f. tube. In the bottom row, from left to right, are the power rectifier tube, the i.f. output transformer (T_4), the second 6SJ7 i.f. tube, the third i.f. transformer (T_3), the 6SA7 and the second i.f. transformer (T_2).

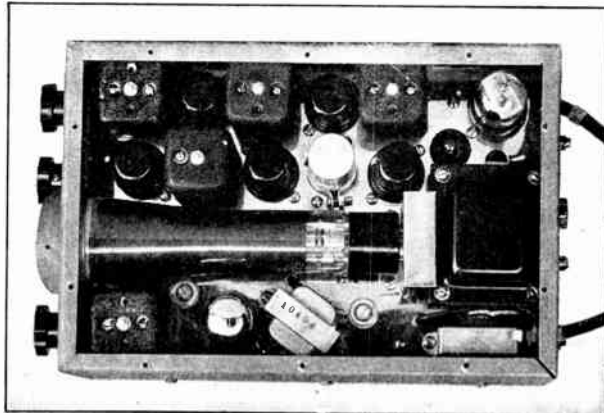

same voltage should appear between the negative terminal of C_{25} and chassis. The screen voltage on the two 6SJ7s should be approximately 100 (at full gain).

The cathode-ray tube makes a convenient indicating device in alignment of the r.f. and i.f. stages. The sweep generator should give no difficulty, although it will be helpful to check the shape of the saw-tooth. A scope having the regular complement of amplifiers and a linear sweep is necessary for this. Connect the grounded side of the vertical input of the scope to chassis and the high side through a condenser (0.1 μ fd. or so) to the ungrounded side of C_{10} , when a saw-tooth should appear on the oscilloscope screen, if the oscilloscope sweep frequency is of the order of 30 cycles. With the vertical amplifier connected to the grid of the saw-tooth oscillator a sharp pulse should appear on the screen. Synchronization can be checked by connecting the scope across R_{34} and adjusting the oscilloscope sweep to include three or more cycles of the 60-cycle voltage which appears across R_{34} . At each oscillator grid pulse a small transient will appear in the pattern (it may be only a small gap in the 60-cycle trace) and when R_{33} is adjusted so that one of these appears at the same point on every other cycle the saw-tooth oscillator is synchronized at 30 cycles.

The saw-tooth should be reasonably straight (make allowance for possible poor linearity of the sweep in the oscilloscope at this low frequency) and the fly-back time, or horizontal duration of the vertical part of the saw-tooth, should be very short. Should the oscillator not operate at all, reverse the leads of the plate winding of T_6 .

With the saw-tooth oscillator in operation, apply voltages to the 902. The saw-tooth applied to the horizontal deflection plates should give a horizontal line on the screen, focusing and intensity being adjustable by means of R_{22} and R_{47} , respectively. The width of the line can be adjusted by the horizontal size control,

R_{37} , and its position on the screen by R_{19} , the horizontal positioning control, and R_{17} , the vertical positioning control.

A test oscillator is practically a necessity for the preliminary alignment of the r.f. and i.f. amplifiers, if only to get them on the right frequency. The i.f. should be aligned first, tuning the trimmers in T_3 and T_4 for maximum response throughout. As a trimmer is tuned through resonance the line on the cathode-ray tube screen will move upward, the extent of the movement indicating the amplitude of the output voltage from the 6SQ7.

The r.f. circuits (T_1 and T_2) can be aligned with the help of a test oscillator tuned to the intermediate frequency in the receiver. Connect the oscillator output between the plate of the 6SJ7 amplifier and ground, using a blocking condenser in the hot lead to isolate the

plate voltage. Then adjust C_{29} in the oscillator transformer, T_5 , to give a beat of 100 kc., which will be amplified and give maximum deflection on the cathode-ray tube screen. The sweep control, R_{35} , should be set at zero so that the oscillator will not be frequency modulated. Adjust the secondary trimmer in T_2 for maximum response. Then move the test oscillator output to the grid of the 6SJ7 and adjust the primary trimmer of T_2 to resonance. Align T_1 similarly with the test oscillator connected between ground and the clip which goes to the receiver mixer plate prong.

The next step is to adjust the oscillator sweep, and for the sake of illustration we will assume that the receiver i.f. is 456 kc. With the test oscillator at 456 kc., and with the sweep padder, R_{36} , at about half scale, increase R_{35} slowly from zero. As the amplitude

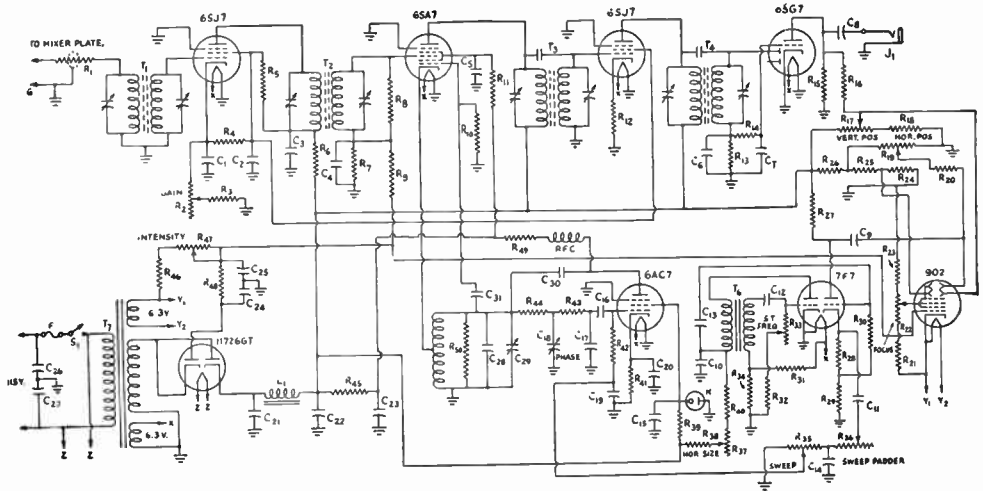


Fig. 1234 — Circuit diagram of the panoramic adapter.

$C_1, C_2, C_3, C_4, C_5, C_8, C_{15}, C_{20}, C_{26}, C_{27}$ — 0.01- μ fd. paper, 600 volts.
 C_6, C_7, C_{14} — 500- μ fd. mica.
 C_9, C_{13} — 0.05- μ fd. 400-volt paper.
 C_{10} — 0.1- μ fd. 400-volt paper.
 C_{11} — 0.25- μ fd. 400-volt paper.
 C_{12} — 0.01- μ fd. mica.
 C_{16} — 100- μ fd. mica.
 C_{17} — 30- μ fd. mica.
 C_{18} — 1-10- μ fd. mica padder.
 C_{19} — 250- μ fd. mica.
 C_{21}, C_{22}, C_{23} — 10- μ fd. 450-volt electrolytic.
 C_{24}, C_{25} — 4- μ fd. 450-volt electrolytic.
 C_{28}, C_{31} — 100- μ fd. mica (in oscillator unit, T_5).
 C_{29} — 30-240- μ fd. mica padder (in oscillator unit, T_5).
 C_{30} — 500- μ fd. mica (in oscillator unit, T_5).
 R_1, R_{16}, R_{27} — 0.25 megohm, $\frac{1}{2}$ watt.
 R_2 — 10,000-ohm potentiometer.
 R_3, R_{12}, R_{34} — 200 ohms, $\frac{1}{2}$ watt.
 R_4, R_{43}, R_{44} — 50,000 ohms, $\frac{1}{2}$ watt.
 R_5, R_{29} — 25,000 ohms, $\frac{1}{2}$ watt.
 R_6, R_7, R_{28}, R_{45} — 5000 ohms, $\frac{1}{2}$ watt.

$R_8, R_{18}, R_{21}, R_{23}$ — 0.1 megohm, $\frac{1}{2}$ watt.
 $R_9, R_{13}, R_{14}, R_{38}, R_{40}$ — 1 megohm, $\frac{1}{2}$ watt.
 R_{10} — 0.11 megohm, $\frac{1}{2}$ watt.
 R_{11} — 45,000 ohms, $\frac{1}{2}$ watt.
 R_{15}, R_{32} — 0.5 megohm, $\frac{1}{2}$ watt.
 R_{17}, R_{35}, R_{47} — 0.1-megohm potentiometer.
 R_{19}, R_{22} — 0.25-megohm potentiometer.
 R_{20}, R_{30} — 2 megohms, $\frac{1}{2}$ watt.
 R_{24} — 25,000 ohms, 1 watt.
 R_{25} — 33,000 ohms, $\frac{1}{2}$ watt.
 R_{26} — See note.
 R_{31} — 500 ohms, $\frac{1}{2}$ watt.
 R_{33}, R_{36}, R_{37} — 1-megohm potentiometer.
 R_{39} — 75,000 ohms, $\frac{1}{2}$ watt.
 R_{41} — 1000 ohms, $\frac{1}{2}$ watt.
 R_{42} — 0.2 megohm, $\frac{1}{2}$ watt.
 R_{46}, R_{48} — 10,000 ohms, $\frac{1}{2}$ watt.
 R_{49} — 3000 ohms, $\frac{1}{2}$ watt (in oscillator unit, T_5).
 R_{50} — 25,000 ohms, $\frac{1}{2}$ watt (in oscillator unit, T_5).
 T_1 — R.f. input transformer, 456 kc.
 T_2 — R.f. interstage transformer, 456 kc.
 T_3 — I.f. input transformer, 100 kc.

T_4 — I.f. output transformer, 100 kc.
 T_5 — Oscillator transformer, 356 kc.
 T_6 — Saw-tooth oscillator transformer (2:1 or 3:1 midget audio).
 T_7 — Power transformer; two 6.3-v. windings, h.v. winding, 300-v. a.c., 40 ma.
 L_1 — Filter choke, 40 ma., 350 ohms (app. 5-10 henrys).
 F — 2-amp. fuse.
 S_1 — Toggle switch (on R_{47}).
 J_1 — Open circuit jack.
 N — $\frac{1}{2}$ -watt neon bulb without base resistor.

RFC — 30-mh. r.f. choke (in oscillator unit, T_5).
 Note: R_{28} needed only in case horizontal positioning control (R_{19}) is critical in adjustment or total plate voltage exceeds 300, approximately. It may be omitted in this circuit, the junction of R_{25} and R_{19} being connected directly to +B.

Transformers T_1 - T_4 , inclusive, are available from Panoramic Radio Corp., New York City.

of the sweep voltage applied to the grid of the 6AC7 reactance modulator increases, the pattern on the cathode-ray tube screen should change, showing the signal as a hump on the horizontal base line, which should move downward to the position it had originally when no signal was applied to the vertical plates. A suitable height for the signal trace can be obtained by adjustment of the gain control, R_2 , or the output of the test oscillator.

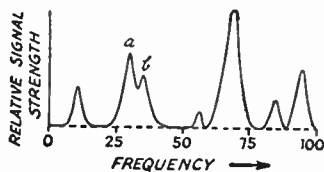


Fig. 1235 — Representation of panoramic reception over a 100-ke. band. The cathode-ray tube beam traces the pattern which would result from plotting instantaneous response of the receiver to signals of differing amplitude and frequency, assuming that such a plot could be made instantaneously. The signals represented by peaks *a* and *b* are so close that the i.f. selectivity is not sufficient to make them appear as isolated peaks.

Should the signal trace not be in the center of the screen, or should it move horizontally as the sweep amplitude is increased (either or both probably will be the case at first trial), adjust C_{29} while varying R_{35} until the signal remains fixed in position on the horizontal base line, regardless of the setting of R_{15} . When the proper adjustment is found the signal will not necessarily appear in the center of the screen, but it can be brought to center by readjusting the horizontal positioning control, R_{19} . The phasing control (C_{18}) adjustment is not critical, and this control may be set simply near but not quite at maximum capacity.

With a 456-ke. signal centered on the screen, tune the test oscillator slowly toward 506 ke., watching the signal trace move horizontally on the screen as the oscillator frequency is changed. R_{35} should be set at maximum. With the oscillator frequency at 506 ke. the signal trace should be just at the edge of the screen; if it is not, it can be brought there by adjustment of the sweep padder, R_{36} . Tuning in the opposite direction to 406 ke. then should move the trace to the opposite end of the screen. When this adjustment is made the maximum sweep will be 100 ke. It may be set at any desired figure between 100 and zero ke. by adjustment of R_{35} .

The next and final step in adjustment is to align T_1 and T_2 to compensate for the r.f. selectivity of the receiver. Set

the receiver at about 3 Mc., set the test oscillator to the same frequency and tune the signal to the center of the screen, using the regular receiver tuning control. Then move the test oscillator frequency 50 ke. higher or lower, putting the signal at one edge of the cathode-ray tube screen. Note the amplitude as compared to the amplitude at the center, and adjust the i.f. transformer trimmers to make the amplitude approximately equal to that at the center. Then move the test oscillator 50 ke. on the other side of the center frequency and readjust the trimmers to make the amplitude equal to that at the center. This will upset the first adjustment, so it will be necessary to go back and forth, making compromise adjustments which finally result in making the gain as uniform as possible over the whole 100-ke. band. The desirable condition, of course, is one in which the height of the test signal does not change as the frequency is varied over the 100-ke. range. Probably it will not be possible to get perfect compensation, but there should be no difficulty in coming reasonably close to it. At frequencies higher than 3 Mc. it is to be expected that the signal amplitude will increase toward the edges of the pattern, and that it will decrease at frequencies lower than 3 Mc.

The frequency-modulated oscillator in the unit provides an excellent means for final alignment of the 100-ke. amplifier. Tune in a test signal to the center of the screen and adjust the trimmers in T_3 and T_4 to give the sharpest and most symmetrical pattern. The signal on the screen is actually a trace of the selectivity curve of the 100-ke. amplifier, and corresponds exactly to the similar type of trace obtained when aligning an ordinary superhet with the aid of a frequency-modulated test oscillator and oscilloscope.

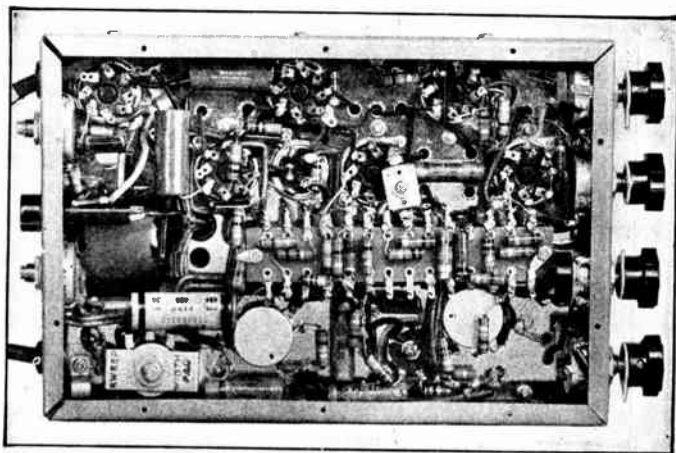


Fig. 1236 — Bottom view of the panoramic adapter. Condensers and resistors in the r.f. circuits are placed close to associated circuits following usual practice. C_{24} and C_{25} are in the upper left-hand corner. The sweep padder (R_{36}) is mounted on a bracket in the lower left-hand corner. R_{33} and R_{37} are the two volume controls near the bottom edge. Near the center, over the 6AC7 socket, is the phasing trimmer condenser, C_{18} . R_{17} and R_{22} may be seen mounted at the left-hand edge with their shafts protruding to the rear of the cabinet.

Transmitter Construction

IN THE descriptions of apparatus to follow, not only the electrical specifications but also the manufacturer's name and type number have been given for most components. This is for the convenience of the builder who may wish to make an exact copy of some piece of equipment. However, it should be understood that a component of different manufacture, provided it is of equivalent quality and has the same electrical specifications, may be substituted in most cases.

Any unusual characteristics in tuning or operation are explained in the text material in these pages describing the construction of each unit. For information concerning straightforward transmitter adjustments, such as the tuning and neutralizing of standard circuits, the reader should consult Chapter Four. Chapter Ten contains information on the adjustment of antenna tuners for the various types of antennas. Keying systems are treated in Chapter Six. The construction of meter shunts is covered in Chapter Nineteen, while operating data on transmitting tubes not specifically included in this chapter will be found in the vacuum-tube tables in Chapter Twenty.

To reduce repetition and make possible a treatment of wider scope, liberal reference will be made to material appearing in other chapters in this *Handbook*.

A Simple Crystal-Oscillator Transmitter

The unit shown in Figs. 1301 and 1302 represents one of the simplest types of amateur transmitters. The various parts are assembled

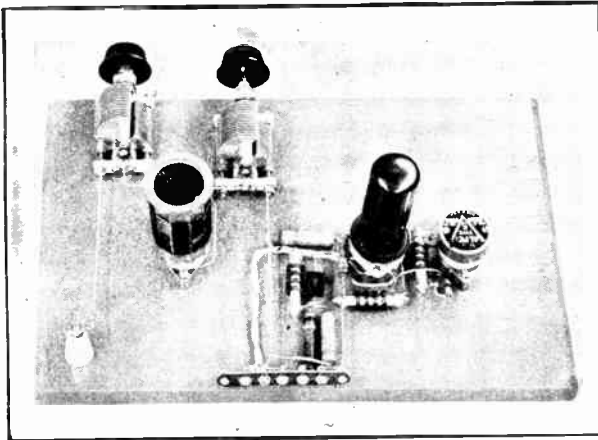


Fig. 1301 — A simple "breadboard" crystal-controlled oscillator transmitter which is capable of a power output of approximately 10 watts.

on a 9 × 14-inch board which has been squared up and given a coat of enamel.

The circuit is of the grid-plate oscillator type with a tank circuit inserted in the cathode lead tuned to a frequency lower than the

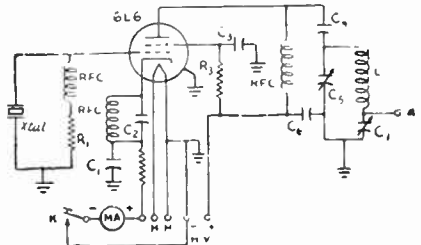


Fig. 1302 — Circuit of the crystal-oscillator transmitter.

- C₁, C₃, C₆ — 0.01- μ fd. paper.
- C₂ — 100- μ fd. mica.
- C₄ — 0.001- μ fd. mica.
- C₅, C₇, 250- μ fd. variable (National STH250).
- R₁ — 7500 ohms, $\frac{1}{2}$ watt.
- R₂ — 200 ohms, 2 watts.
- R₃ — 15,000 ohms, 2 watts.
- RFC — 2.5-mh. r.f. choke.
- L — 1.75 Mc. — 65 turns No. 22 d.s.c., close-wound.
- 3.5 Mc. — 32 turns No. 20 enam., 1 $\frac{1}{2}$ inches long.
- 7 Mc. — 16 turns No. 20 enam., 1 $\frac{1}{2}$ inches long.
- All coils wound on 4-prong Hammarlund coil forms, 1 $\frac{1}{2}$ inches in diameter.
- A — Antenna terminal.
- K — Key.
- MA — Milliammeter, 100- or 200-ma. scale.
- Xtal — Crystal for desired frequency.

crystal frequency. This facilitates tuning adjustments for proper keying under load. Bias is obtained principally from the cathode resistor, R_2 , since the chief purpose of R_1 is to eliminate parasitic oscillation as a result of using r.f. chokes in both plate and grid circuits.

Parallel feed is used in the plate circuit to remove d.c. voltage from the tuning condenser. A "pi-section" tank circuit is used to provide a simple means of adjusting the coupling to the antenna. This arrangement will feed power into a wire of almost any random length, although it should be remembered that a good antenna, wherever possible, is still required for maximum results.

The photograph of Fig. 1301 shows most of the constructional details. The antenna-coupling condenser, C_7 , is to the left and the tuning condenser, C_5 , to the right with the tank coil in between. Above

the terminal strip at the rear are the cathode resistor, R_2 , its by-pass condenser, C_1 , and the cathode-circuit r.f. choke with the parallel mica condenser, C_2 , and the screen by-pass condenser, C_3 . The r.f. choke below the tube is in the plate circuit with the screen resistor, R_3 , to the left of the 6L6. To the right of the 6L6 are the grid r.f. choke and resistor, R_1 , and the crystal. The plate blocking condenser is hidden behind the tube.

Although a 6L6 tube is shown in the photographs and diagram, a 6V6 or 6F6 might be used at a lower plate voltage without circuit alteration. Any available power supply delivering up to 450 volts may be used with the 6L6, the power output obtainable increasing with the voltage applied. The one shown in Fig. 1303 is suitable. The two units may be connected together by a four-wire battery cable and a four-pin plug to fit the outlet on the power supply.

Since the circuit is not designed for frequency doubling, a separate crystal will be required for each frequency desired.

A milliammeter with a scale of 100 or 200 ma. should be connected in series with the key, as shown in Fig. 1302, as an aid in tuning. With a suitable coil and crystal in place, the antenna connected and the high voltage turned on, a rise in plate current should occur when the key is closed. With C_7 set at maximum capacity, C_5 should be adjusted until the milliammeter shows a dip in plate current indicating resonance. If no dip is found, the capacity of C_7 should be reduced slightly, step by step, rotating C_5 through its range each time, until the dip is found. The loading may be varied within limits by the same process, first setting C_7 and then retuning C_5 to resonance. As the loading is increased, the value of plate current at minimum dip will increase, indicating that the tube is taking more power. If the loading is made too heavy, the circuit will not key well, or it may fail to oscillate at all. In this case the loading should be reduced, of course.

The coupling system provided is designed primarily to feed into a single-wire antenna

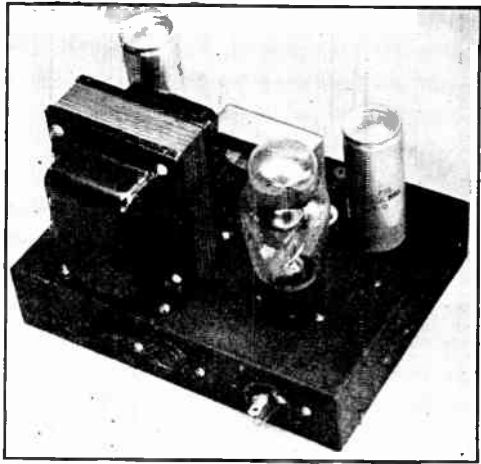


Fig. 1304 — This power supply delivers 450 volts at a full-load current of 130 ma., with 0.3 per cent ripple and measured regulation of 17 per cent. If converted to a choke-input filter by inserting a similar choke between the rectifier and present filter, the output voltage is reduced to about 300 volts. The chassis measures $7 \times 9 \times 2$ inches. Filament and plate voltages are brought out to a four-prong socket. The circuit is given in Fig. 1303.

of random length. In general, the wire should be as long as possible, although there is little point in making it over 250 feet in length. As much of the total length as possible should be elevated as high as available supports will permit. When restriction in space makes it necessary, or for local work, the coupling arrangement shown will feed power into a wire only a few feet long.

If the antenna is to be fed at the center, or if tuned feeders are used as described in Chapter Ten, a link line may be connected across the coupling condenser, C_7 , and used to couple to a series-parallel antenna tuner, such as the one shown in Fig. 1317. The tuning condensers specified for this tuner may be of the midget type with smaller plate spacing and the coils may be wound on standard receiver forms.

With a 6L6 tube and a plate supply delivering 400 volts, the screen voltage will be about 250 volts. The tube will draw about 85 ma. non-oscillating, dipping to about 40 ma. at resonance with the antenna disconnected. It should be possible to load up the circuit until the tube draws about 70 ma. at resonance. Under these conditions, the power output on each band should be 15 to 20 watts.

◀ A Two-Tube Plug-In Coil Exciter

In the two-tube exciter or low-power transmitter pictured in Figs. 1305, 1307 and 1308, a 6L6 oscillator is used to drive an 807 as an amplifier-doubler. As shown in Fig. 1306, a Tri-tet circuit, used to obtain harmonic output, is reduced to a simple tetrode circuit for oscillator output at the crystal fundamental by short-circuiting the cathode tank circuit. Sufficient oscillator output at the fourth harmonic

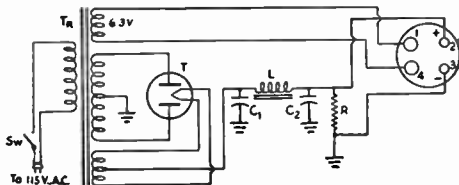


Fig. 1303 — Circuit of the 450-volt power supply.
 C_1 — 4- μ fd. 600-volt electrolytic (Mallory HS691).
 C_2 — 8- μ fd. 600-volt electrolytic (Mallory HS693).
 L — Filter choke, 10 henrys, 175 ma., 100 ohms (Utah 4667).
 R — 15,000 ohms, 25-watt.
 T — Type 80 rectifier tube.
 Tr — Power transformer, 400 volts each side of center-tap; rectifier filament winding, 5 volts, 3 amperes; r.f. filament winding, 6.3 volts, 6 amperes (Utah Y616).

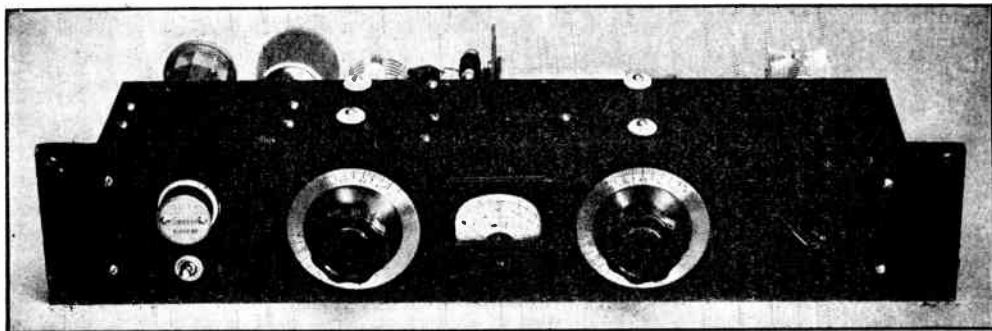


Fig. 1305 — The two-tube plug-in coil exciter is built to conserve space in the relay rack. The panel is $3\frac{1}{2} \times 19$ inches. A clearance hole is cut in the left end of the panel for the crystal socket, which is mounted in the chassis directly above the cathode-circuit switch. The left-hand dial controls the tuning of the oscillator plate-tank circuit; the dial to the right tunes the output tank circuit. The switch at the right-hand end is for the 200-ma. milliammeter.

of the crystal frequency is obtainable to drive the 807, which may be operated as either a straight amplifier or frequency doubler, providing output of 25 to 50 watts or more in four bands from a single crystal.

The entire unit is designed to operate from a single 250-ma. power supply delivering up to 750 volts (see Fig. 1316), the maximum rating for the 807. Fixed bias of 45 volts, which may be obtained from a dry battery, is required for the 807. In the system shown, both oscillator and amplifier are keyed simultaneously in the common cathode lead. A single 200-ma. milliammeter may be switched to read the plate current of either stage.

Tuning — Because it is possible to double

or quadruple frequency in the plate circuit of the oscillator and to double in the plate circuit of the 807 as well, there are several possible combinations of coils and crystals which will produce the same output frequency. Since much better efficiencies are obtainable, it is advisable to operate the 807 as a straight amplifier rather than as a doubler. This is possible in all cases except where it is necessary to obtain output at the eighth harmonic of the crystal frequency — 14-Mc. output from a 1.75-Mc. crystal, or 28-Mc. output from a 3.5-Mc. crystal. The chart shown on page 60 shows the combination required for the desired output from any given crystal. This chart also indicates the position for Sw_1 . Be sure that the

Fig. 1306 — Circuit diagram of the two-tube plug-in coil exciter unit.

C_1 — 140- μ fd. variable (Hammarlund MC-14M).

C_2 — 150- μ fd. variable (Cardwell MR150BS).

C_3 — 100- μ fd. mica.

C_4 — 20- μ fd. mica.

$C_5, C_6, C_7, C_8, C_9, C_{10}$ — 0.01- μ fd. 600-volt paper.

C_{11} — 0.01- μ fd. 1000-volt paper.

C_{12} — 100- μ fd. mica (used only on 3.5 Mc.).

MA — Milliammeter, 0-200-ma.

R_1 — 20,000 ohms, 1-watt.

R_2 — 25,000 ohms, 2-watt.

R_3 — 200 ohms, 2-watt.

R_4 — 10,000 ohms, 25-watt.

R_5 — 3500 ohms, 25-watt.

R_6, R_7 — 15,000 ohms, 25-watt.

R_8, R_9 — 1250 ohms, 50-watt.

R_{10}, R_{11} — 10 ohms, 1-watt.

RFC — 2.5-mh. r.f. choke.

Sw_1 — S.p.s.t. toggle switch.

Sw_2 — D.p.d.t. rotary switch

(Mallory 3222J).

L_1 — 1.75-Mc. crystals — 32 turns

No. 22 d.s.c., close-wound.

3.5-Mc. crystals — 10 turns

No. 22 d.s.c., 1-inch long.

Note: C_x mounted in form.

7-Mc. crystals — $6\frac{1}{2}$ turns

No. 22 d.s.c., $\frac{3}{4}$ -inch long.

All wound on Hammarlund


$1\frac{1}{2}$ -inch diam. 4-pin forms.

L_2 — 1.75 Mc. — 56 turns, $1\frac{1}{4}$ -

inch diameter, $1\frac{3}{4}$ inches

long, 54 μ h. (National

AR30 — no link).

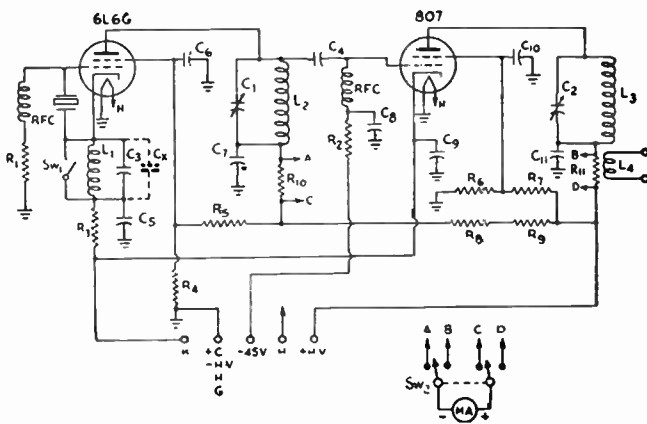

3.5 Mc. — 28 turns, $1\frac{1}{4}$ -inch diameter, $1\frac{1}{2}$ inches long, 15 μ h. (National AR40 — no link).

7-Mc. — 14 turns, $1\frac{1}{2}$ -inch diameter, $1\frac{3}{4}$ inches long, 4.2 μ h. (National AR20 — no link).

14 Mc. — 8 turns, $1\frac{1}{4}$ -inch diameter, $1\frac{1}{2}$ inches long, 1.25 μ h. (National AR10 — no link).

28 Mc. — 4 turns, $1\frac{1}{4}$ -inch diameter, $\frac{3}{4}$ -inch long, 0.5 μ h. (National AR10, 1 turn removed — no link).

L_3 — 1.75 Mc. — 50 turns, $1\frac{1}{2}$ -inch diameter, $2\frac{1}{8}$ inches long, 52 μ h. (Coto CS616 E).

3.5 Mc. — 25 turns, $1\frac{1}{2}$ -inch diameter, $1\frac{5}{8}$ inches long, 16 μ h. (Coto CS60E).

7 Mc. — 16 turns, $1\frac{1}{2}$ -inch diameter, $1\frac{7}{8}$ inches long, 5.7 μ h. (Coto CS640E).

14 Mc. — 8 turns, $1\frac{1}{2}$ -inch diameter, $1\frac{5}{8}$ inches long, 1.5 μ h. (Coto CS620E).

28 Mc. — 4 turns, $1\frac{1}{2}$ -inch diameter, $1\frac{1}{2}$ inches long, 0.7 μ h. (Coto CS610E).

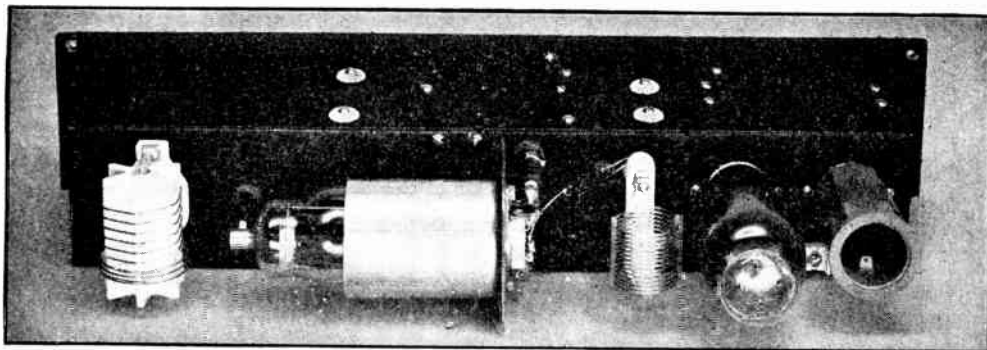


Fig. 1397 — The four-prong socket for the cathode coil, the octal socket for the 6L6 oscillator and the five-prong socket for the Coto coils used in the output tank circuit are sub-mounted along the rear of the chassis. The mounting for the National AR coils used in the oscillator plate circuit is fastened on short cone insulators, while the socket for the 807 is submounted in the small steel partition. The grid r.f. choke and screen and cathode by-pass condensers are fastened directly to the socket. Large clearance holes lined with grommets are provided for passing the connections through the chassis from the oscillator plate coil to the tank condenser and for the 807 plate lead. A pair of pin jacks serves as the link output terminals. Power-supply connections are made to a terminal strip at the right.


harmonics of the crystal frequency fall in the band in which operation is to occur.

With the proper coils and crystal in place, Sw_1 in the correct position and both condensers set at minimum capacity (100 on the dial), the plate voltage should be applied with the meter reading plate current to the 807. If all resistances are correct and the plate voltage is 750, the plate current should run approximately 25 ma. With the key closed, tune the oscillator tank condenser for maximum amplifier plate current. (Do not hold the key closed for long periods under this high-current condition.) As soon as the peak has been obtained, tune the amplifier plate tank condenser for resonance as indicated by a pronounced dip in plate current. Should the points of response on either condenser be found at points on the scale differing appreciably from those given in the accompanying table, each circuit should be checked with an absorption frequency meter to make sure that it is tuned to the correct frequency, since the ranges covered by some of the coils include odd harmonics falling outside the amateur bands. Once checked, the dial settings can be logged for quick resetting.

When the amplifier has been tuned, the meter switch may be set to read oscillator plate current and the oscillator tank circuit tuned for minimum plate current consistent with satisfactory keying. Active crystals usually will oscillate continuously in the Tri-tet circuit, regardless of the setting of the tank condenser. With the tetrode circuit, however, the circuit will oscillate only within relatively narrow limits. Sw_1 must be closed when the oscillator plate circuit is tuned to the crystal frequency. The oscillator plate current will vary widely, depending upon whether output is taken at the fundamental, second harmonic or fourth harmonic. At the specified plate voltage, it should run between 40 and 50 ma. with the plate circuit tuned to the crystal fundamental or second harmonic. When tuned to the fourth harmonic, the plate current will normally run between 85 and 95 ma.

Because the plate and screen of the 6L6 are operated from a voltage divider, their voltages vary with tuning. Plate voltage varies between 400 and 450, except at the fourth harmonic when it falls to 340 volts or so. The screen voltage varies from 280 to 210 volts.

Fig. 1398 — Bottom view of the plug-in exciter. Space inside the $4 \times 17 \times 3$ -inch chassis has been utilized to the greatest extent possible while preserving accessibility. Voltage divider resistors R_8 and R_9 are to the right of the oscillator tank condenser, while R_4 , R_5 , R_6 and R_7 are mounted to the rear of the meter. The oscillator r.f. choke and grid leak are fastened to the crystal socket. Connections between the crystal socket and cathode switch are made directly and kept well spaced. The oscillator circuit may be arranged for v.f.o. input as shown in Fig. 1385. Meter-shunting resistances are fastened to the meter switch. Both tank-condenser shafts must be fitted with insulated couplings and panel bearings.

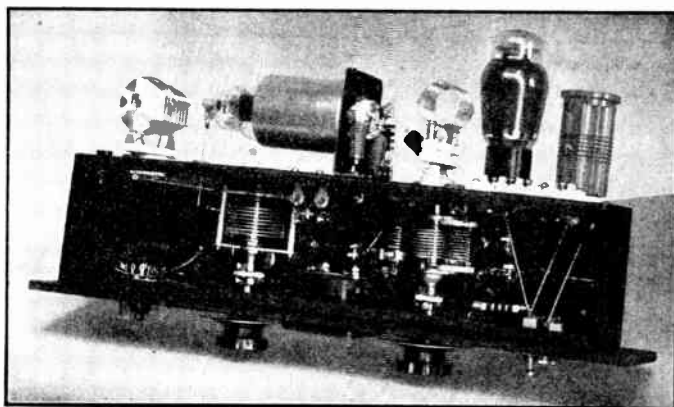

COIL AND TUNING TABLE FOR TWO-TUBE PLUG-IN COIL EXCITER							
Crystal Band Mc.	Output Band Mc.	Sw ₁	L ₁ Band Mc.	C ₁ L ₂ Band Mc.	C ₂ L ₃ Band Mc.	C ₁ *	C ₁ *
1.75	1.75	Closed	1.75	1.75	1.75	10	10
1.75	3.5	Open	1.75	3.5	3.5	10	30
3.5	3.5	Closed	3.5	3.5	3.5	10	30
1.75	7	Open	1.75	7	7	20	50
3.5	7	Open	3.5	7	7	20	50
7	7	Closed	7	7	7	20	50
1.75	14	Open	1.75	7	14	20	70
3.5	14	Open	3.5	14	14	35	70
7	14	Open	7	14	14	35	70
3.5	28	Open	3.5	14	28	35	80
7	28	Open	7	28	28	75	80

* Approximate settings for low-frequency ends of bands with dial reading zero at full capacity of condenser.

The plate current should be limited to 70 ma. at 28 Mc. and 80 ma. at 14 Mc. when doubling frequency in the output stage, and to 90 ma. when operating the 807 as a straight amplifier at 28 Mc. Power output under these conditions should average 40 to 55 watts on all bands. When doubling frequency in the output circuit to 14 and 28 Mc., the output will be reduced to about 27 and 18 watts respectively.

If the exciter is operated from a power supply of lower voltage, the values of resistance specified for the voltage dividers may be altered to increase the voltages on the oscillator plate and screen and also the screen of the 807. With a 600-volt supply, R_8 and R_9 should be 1000 ohms each, R_4 , 20,000 ohms, and R_5 , 10,000 ohms. Power output will average 30 to 35 watts from the 807 as a straight amplifier.

Complete 75-Watt All-Band Transmitter with Plug-in Coils

If it is desired to feed the unit of Fig. 1305 into an antenna as a complete transmitter, it may be combined with the power-supply unit of Fig. 1316, which will furnish heater and plate voltages, and the antenna-tuning unit of Fig. 1318 using the large condensers. A 45-volt dry battery will be required for bias. The three units may be placed in a small table rack with a total height of only 17½ inches.

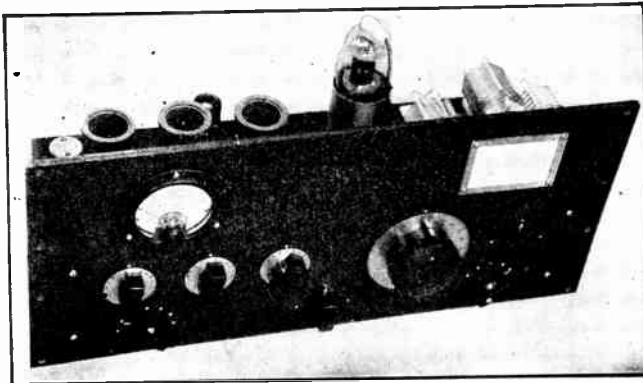


Fig. 1309 — An 807 exciter or low-power transmitter combining the flexibility of plug-in coils with the convenience of band-switching. A band-switching plug-in coil assembly changes tank coils in the 807 plate circuit. Crystal switching and meter switching also are provided. Plate currents for all tubes and screen current for the 807 are read on a 200-ma. meter which can be switched to any circuit. Keying is in the oscillator cathode circuit, for break-in operation. The panel is 8¾ inches high and of standard rack width. The chassis measures 8 × 17 × 2 inches. The unit requires two power supplies, one delivering 250 volts at approximately 75 ma. and the other 750 volts at 100 ma.


A Band-Switching Exciter with 807 Output Stage

The exciter or low-power transmitter pictured in Figs. 1309, 1310 and 1312 is designed for flexibility, being adaptable for use on all bands from 1.75 to 28 Mc., with crystals cut for different bands, and also for quick band changing over three bands. It consists of a 6C5 triode oscillator followed by two triode doubler stages in one tube, a 6N7; by means of a switch, S_2 , the output of any of the three stages can be connected to the grid of the final tube, which is an 807 beam tetrode. The circuit diagram is given in Fig. 1311.

The oscillator coil and the first and second doubler plate coils, L_1 , L_3 and L_2 respectively, need not be changed for crystals ground for a given band. The switching circuit is so arranged that the grids of unused stages are automatically disconnected from the preceding stage and grounded, so that excitation is not applied to the idle doubler tubes.

Capacity coupling between stages is used throughout. The plates of the first three stages are parallel-fed so that the plate tuning condensers can be mounted directly on the metal chassis. The 6C5, 6N7, and the 807 screen all operate from a 250-volt supply. Series feed is used in the 807 plate circuit, the tank con-

Fig. 1310—Top view of the hand-switching exciter with coils removed. At the left rear are the spare crystal socket, the 6C5 and the 6N7. Directly in front of these are the tuning condensers (mounted directly on the chassis) and the coil sockets (mounted on pillars) for the oscillator and doubler stages. Grouped to the right are the 807, the amplifier tank condenser (which must be insulated from the chassis) and the switch assembly. The "hot" leads from the coils are brought through grommeted holes in the chassis. The amplifier switch assembly should be mounted far enough back from the panel so that the coils will clear the side of the relay rack or cabinet. Leads between the switch and C₄ should be kept as short as possible.

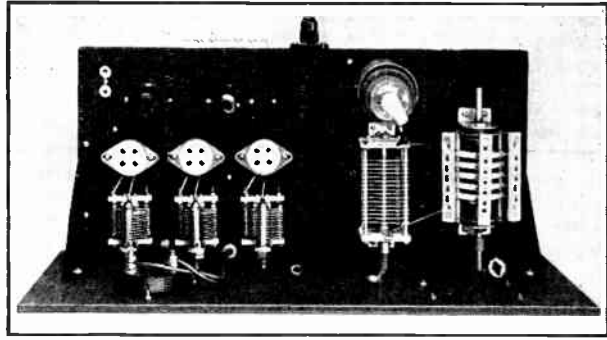

denser being of the type which is insulated from the chassis. Fixed bias of about 75 volts is used on the 807 grid.

Plate currents for all tubes are read by a 200-ma. meter which can be switched to any circuit by means of S₄. Keying is done in the oscillator cathode circuit providing break-in operation.

Since in normal operation the crystal tank circuit, C₁L₁, is tuned well on the high-frequency side of resonance, there is a tendency for the first doubler section to break into a "tuned-grid tuned-plate" type of oscillation when the key is up; this is prevented by a small amount of inductive neutralization provided by the single-turn coils, L₅ and L₆, wound as closely as possible to the ground end of each tank coil. The 28-Mc. coil does not need such

a neutralizing winding, since it is used only in the second doubler stage. L₅ and L₆ should be so connected as to prevent self-oscillation of the first 6N7 section when the key is open; the proper connections should be found by trial.

In the bottom view, Fig. 1312, the meter switch with its shunting resistors is at the left, with the 807 plate by-pass condenser, C₁₁, just above it. The stage switch, S₂, is in the center. R.f. leads to this switch should be kept separated as much as the layout will permit. R.f. junction points are insulated by small ceramic pillars. In this view, the right-hand section of the 6N7 is the first doubler. The rotor contact of the section of S₂ nearest the panel goes to the grid of the first doubler, the middle section to the second-doubler grid, and the third section to the 807 grid.

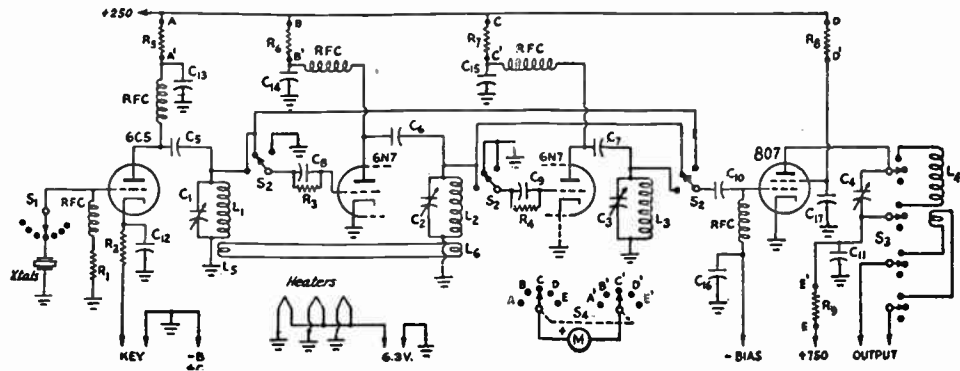


Fig. 1311—Circuit diagram of the crystal-controlled 807 hand-switching exciter or low-power transmitter.

- C₁, C₂, C₃—100- μ fd. variable (National ST-100).
- C₄—150- μ fd. variable, 0.05-inch plate spacing (Hammarlund HFB-150-C).
- C₅, C₆, C₇—0.002- μ fd. 500-volt mica.
- C₈, C₉, C₁₀—100- μ fd. 500-volt mica.
- C₁₁—0.002- μ fd. 2500-volt mica.
- C₁₂—C₁₇, inc.—0.01- μ fd. 600-volt paper.
- R₁—10,000 ohms, 1/2-watt.
- R₂—300 ohms, 1-watt.
- R₃, R₄—25,000 ohms, 1/2-watt.
- R₅—R₉, inc.—25 ohms, 1/2-watt.
- RFC—2.5-mh. r.f. choke.
- S₁—Ceramic wafer switch, 6 or more positions.
- S₂—Three-gang three-position ceramic wafer switch (Yaxley 163C).
- S₃—Band-switch in coil assembly (Coto type 700).
- S₄—Two-gang 6-position (5 used) ceramic wafer switch.
- M—0-200 d.c. milliammeter, bakelite case.

- L₁, L₂, L₃—1.75 Mc.: 50 turns No. 22 d.s.c. close-wound.
- 3.5 Mc.: 26 turns No. 18, length 1 1/2 inches.
- 7 Mc.: 17 turns No. 18, length 1 1/2 inches.
- 14 Mc.: 8 turns No. 18, length 1 1/2 inches.
- 28 Mc.: 3 turns No. 18, length 1 inch.
- All wound on 1 1/2-inch diameter forms (Hammarlund SWF-4); turns spaced evenly to fill specified winding length.
- L₄—1.75 Mc.—50 turns, 1 1/2-inch diameter, 2 3/8 inches long, 52 μ h. (Coto CI6160E).
- 3.5 Mc.—25 turns, 1 1/2-inch diameter, 1 5/8 inches long, 16 μ h. (Coto CI680E).
- 7 Mc.—16 turns, 1 1/2-inch diameter, 1 1/8 inches long, 5.7 μ h. (Coto CI640E).
- 14 Mc.—8 turns, 1 1/2-inch diameter, 1 5/8 inches long, 1.5 μ h. (Coto CI620E).
- 28 Mc.—4 turns, 1 1/2-inch diameter, 1 1/2 inches long, 0.7 μ h. (Coto CI610E).
- L₅, L₆—One turn at bottom of L₁ and L₂. See text.

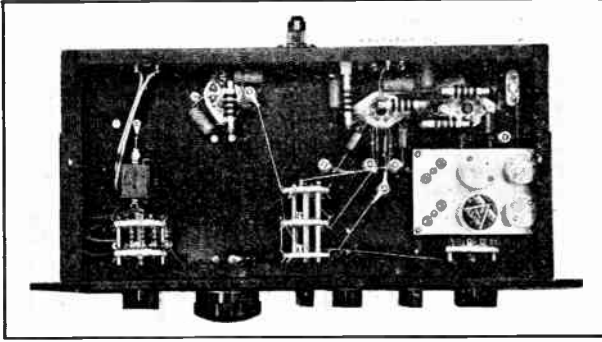


Fig. 1312 — Bottom view of the band-switching exciter, showing the meter switch at the left, the band-switch in the center and the crystal switch at the right. The multiple crystal mounting, which holds six crystals, is made of a $3 \times 4\frac{1}{2}$ -inch aluminum plate fitted with Amphenol crystal sockets, the assembly being elevated from the chassis by metal pillars. A seventh socket is provided on top of the chassis for a spare crystal or for c.c.o. input. The 750-volt lead is brought through a Millen safety terminal, and all other power connections come to a terminal strip at the rear which has barriers between the terminals to prevent accidental contact. All grounds are made directly to the $8 \times 17 \times 2$ -inch chassis.

Figs. 1313 and 1316 show suitable 250- and 750-volt power-supply units for this transmitter. Heater voltage and grid bias are obtained from the 250-volt supply. If desired, both these power units may be assembled on one large chassis.

Tuning — To operate the exciter, coils for consecutively higher-frequency bands are plugged in at L_1 , L_2 and L_3 ; only five are necessary for operation with any crystal from 1.75 to 7 Mc. and for output from 1.75 to 28 Mc. For example, with 3.5-Mc. crystals, the 3.5-, 7- and 14-Mc. coils would be plugged in at L_1 , L_2 and L_3 respectively. For 1.75-Mc. crystals, the 1.75-, 3.5- and 7-Mc. coils would be used, and so on. The plate coils for the 807 should cover the same bands as the low-level coils.

Preliminary tuning should be done with the plate voltage for the 807 disconnected. Set S_2 so that all tubes are in use. Switch the milliammeter to the oscillator circuit and close the key. Rotate C_1 for the dip in plate current which indicates oscillation. The non-oscillating plate current should be between 20 and 25 ma., dropping to 15 or 20 when oscillating. Switch the meter to the doubler plate and adjust C_2 to minimum plate current, or resonance. The off-resonance plate current should be about 30 ma. or more and the reading should be between 10 and 15 at resonance. Check the second-doubler plate current and tuning similarly; the off-resonance plate current should again be around 30 ma., dropping to 15 or 20 at resonance. At this point the 807 screen current should be measured; with too much excitation it will be considerably higher than the rated value (about 12 ma.) and the excitation should not be kept on for more than a second or two.

Next, the plate voltage may be applied to the 807. The amplifier should not be operated without load for more than a few moments at a time, because under these conditions the screen dissipation is excessive. Use a 70-ohm dummy antenna or a 60-watt lamp connected to the output link. The three bands may be checked in order by appropriate switching of S_2 and S_3 . With the 807 fully loaded, check the screen current to make sure it does not exceed 10 or 12 ma. If it is too high, reduce the excitation by detuning the crystal oscillator until it reaches the proper value. The 807 grid current

may be measured with a lower-range milliammeter connected in series with the bias source, if desired. Maximum output will be secured with a grid current of about 3 or 4 milliamperes, a value which also will give about rated screen current. The screen current is, in fact, a very good indicator of excitation. The 807 should show no tendency to oscillate by itself when the key is open.

The current to each section of the 6N7 should be 20 ma. with the key open (no excitation). If the two currents are not the same or show changes when C_2 and C_1 are tuned with key open, the first doubler may be acting as a t.p.t.g. oscillator, as previously mentioned, and the neutralizing circuit should be checked. Do not use more than 250 volts for the low-voltage supply, as higher values will cause excessive 807 screen dissipation. Care also should be taken to avoid excessive excitation. In normal operation, with C_1 detuned to reduce excitation to the proper value, the doubler plate currents will show little change between resonance and off-resonance tuning.

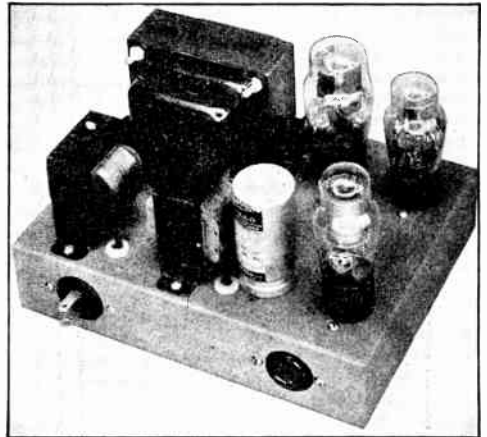


Fig. 1313 — A combination power-supply unit delivering 250 or 300 volts for exciter plate supply and 75 volts of fixed bias. The unit is designed especially to work with the band-switching exciter, the diagram of which is shown in Fig. 1311. If desired, the components may be combined with the components for a high-voltage plate supply on a single chassis. The circuit diagram of the combination unit is shown in Fig. 1314.

With maximum input to the 807 plate (75 watts) the output is approximately 50 watts on all bands except 28 Mc., where greater circuit losses decrease it to about 40 watts. The excitation provided by the 6N7 doubler is more than ample on all bands.

The oscillator circuit may be arranged for v.f.o. input as in Fig. 1385.

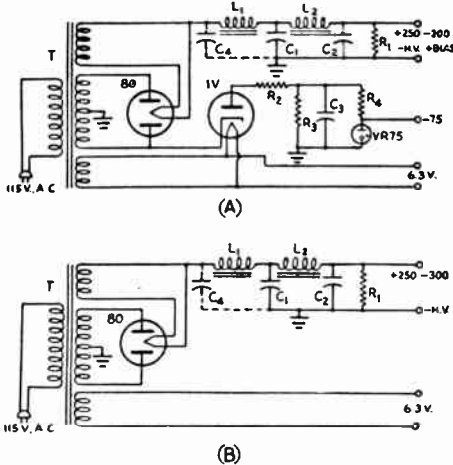


Fig. 1314 — Circuit diagram of the combination plate, screen and grid-bias power supply shown in Fig. 1313.


- C₁, C₂ — Sections of 8- μ fd. 450-volt dual electrolytic.
- C₃ — 8- μ fd. 450-volt paper.
- C₄ — Same as C₃ (used only for 300-volt output).
- L₁, L₂ — 6-henry, 80-ma. 138-ohm filter choke (Thor-darson T-57C51).
- R₁ — 20,000 ohms, 10-watt.
- R₂ — 20,000 ohms, 2-watt.
- R₃ — 25,000 ohms, 2-watt.
- R₄ — 15,000 ohms, 2-watt.
- T — 300 volts r.m.s., each side of centertap, 90 ma.; 5 volts, 3 amperes; 6.3 volts, 3.5 amperes (Thordarson T-13R13).

If desired, the bias branch may be omitted, as shown in the alternative diagram at B. All values remain as above.

A Combination Low-Voltage Plate or Screen Supply and Fixed-Bias Pack

Fig. 1316 illustrates a combination pack which will deliver 250 or 300 volts, 75 ma., for

Fig. 1316 — This power-supply unit delivers either 620 or 780 volts at a full-load current of 260 ma. with 0.4 per cent ripple and regulation of 22 per cent. Voltage is changed by a tap on the plate-transformer primary winding. The filter chokes are at the left and the plate power transformer at the right on the panel side of the chassis. The can-type 1000-volt filter condensers are at the left in front and the rectifier tubes at the right, with the rectifier filament transformer in between. All exposed component terminals are underneath the chassis. The panel is 8 $\frac{3}{4}$ × 19 × 3 inches. The 2.5-volt 10-ampere rectifier filament transformer should have 10,000-volt insulation. A 6.3-volt filament transformer is included for heating the filaments of r.f. tubes. This transformer is mounted underneath the chassis; its output terminals are brought out to a standard a.c. receptacle in the rear. The circuit diagram is shown in Fig. 1315.

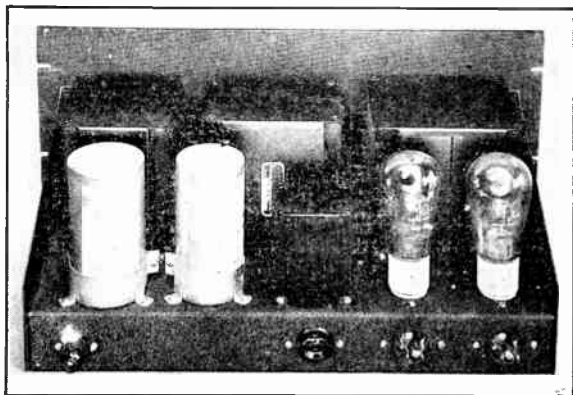

supplying plate voltage for receiving-tube exciter stages as well as screen and fixed-bias voltage for a beam-tube driver stage.

The circuit diagram is shown in Fig. 1314-A. In addition to the usual full-wave rectifier circuit employing a type 80 tube, a 1V half-wave rectifier also is connected across one half of the transformer secondary in reverse direction to provide a negative biasing voltage which is held constant at 75 volts by the VR75-30 regulator tube. With the dropping resistor shown, the regulator tube will pass a grid current of 25 ma. without overload. The 1V rectifier is indirectly heated, so that it may be operated from the same 6.3-volt winding provided to supply the r.f. tubes in the transmitter.

The output voltage at a normal load current of about 75 ma. can be increased from 250 to about 300 by the addition of an input filter condenser, C₄, the connections for which are shown in dotted lines.

If the bias section is not needed, plate or screen voltage may be obtained with the simplified circuit shown in Fig. 1314-B, eliminating the bias section.

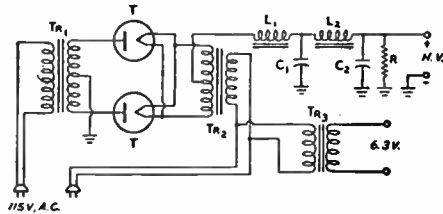


Fig. 1315 — Circuit of the power supply in Fig. 1316.

- C₁ — 2- μ fd. 1000-volt paper (Sprague OT21).
- C₂ — 4- μ fd. 1000-volt paper (Sprague OT41).
- L₁ — Input choke, 6-19 henrys, 300 ma., 125 ohms (Kenyon T-510).
- L₂ — Smoothing choke, 11 henrys, 300 ma., 125 ohms (Kenyon T-166).
- R — 20,000 ohms, 50 watts.
- T — Type 866 Jr. rectifier.
- Tr₁ — 925 or 740 volts r.m.s. each side of centertap, 300 ma. d.c. (Kenyon T-656).
- Tr₂ — 2.5 volts, 10 amperes, 2000-volt insulation (Kenyon T-352).
- Tr₃ — 6.3-volt 3-ampere filament transformer.

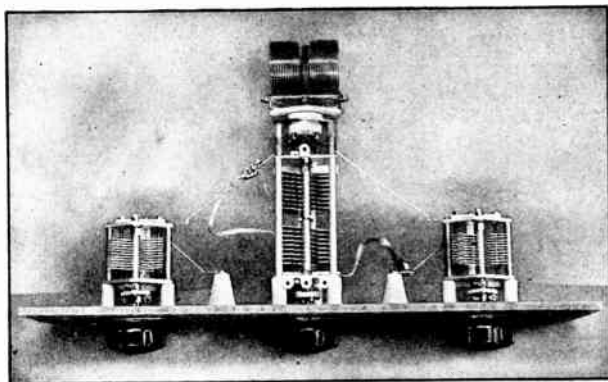


Fig. 1317—A rack-mounting antenna tuner for low-power transmitters. C_1 is in the center, with C_2 and C_3 on either side. All of the components are mounted directly on the $5\frac{1}{4}$ -inch panel. The variable condensers are mounted on the assembly rods on National type GS-1 insulating pillars which are fastened to the condenser end plates with machine screws from which the heads have been removed. Small Isolantite shaft couplings are used to insulate the controls. The coil socket is fastened to the rear end plate of the parallel condenser, C_1 , with spacers to clear the prongs. Clips with flexible leads are provided for the split-stator parallel condenser, C_1 , so that its sections may be connected either in parallel or in series to form either a high- or low-capacity tank circuit as required.

◀ A Low-Power Antenna Tuner for Rack Mounting

In the rack-mounted low-power antenna tuner shown in Fig. 1317, separate series and parallel condensers are used. This arrangement, while requiring three variable condensers, has the advantage that no switching is necessary when changing over from series to parallel tuning. It also makes possible the use of the tuner to cover a considerably wider range of antenna and transmission-line conditions, because the series condensers can be adjusted in conjunction with the parallel condenser to shorten the electrical length of the feeders whenever this is required to make parallel tuning effective. In addition, the series condensers also are useful in that they provide a

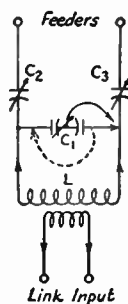


Fig. 1318—Circuit of the rack-mounting antenna tuner for use with transmitters having final amplifiers which are operated at less than 1000 volts on the plate.

- C_1 —100 μ fd. per section, 0.045-inch spacing (National TMK-100-D) for higher voltages; receiving-type for lower voltages (Hammarlund MCD-100).
- C_2, C_3 —250 μ fd., 0.026-inch spacing (National TMS-250) for higher voltages; receiving-type for lower voltages (Hammarlund MC250).
- L.—B&W JVL series coils. Approximate dimensions for parallel tuning for each band are as follows:
 - 1.75-Mc. band—56 turns No. 24.
 - 3.5-Mc. band—40 turns No. 20.
 - 7-Mc. band—24 turns No. 16.
 - 14-Mc. band—14 turns No. 16.
 - 28-Mc. band—8 turns No. 16.

All coils are $1\frac{1}{2}$ inches in diameter and $2\frac{1}{4}$ inches long, with the variable link located at the center. For series tuning, use the coil specified for the next-higher frequency band, which will be approximately correct.

measure of control over the amplifier loading when parallel tuning is used.

Clips with flexible leads attached are provided for the parallel condenser, C_1 , so that the sections may be connected either in parallel or in series to form either a high- or low-capacity tank circuit, as required. When the high-C parallel tank is desired, the two stators are clipped together, as shown by the dotted lines in the circuit diagram of Fig. 1318, and the rotor is connected to the opposite feeder. When the two sections are connected in series, for low-C operation, the break-down voltage is increased.

Below the circuit diagram, Fig. 1318, two sets of variable condensers are suggested. The smaller receiving-type condensers with 0.03-inch air gap should be satisfactory for low-power transmitters operating at plate voltages of 400 to 450 volts, while the larger condensers with 0.045-inch spacing will be required for transmitters using plate voltages up to about 750 or 1000 volts.


◀ Complete 75-Watt Multiband Transmitter

If it is desired to use the band-switching 807 exciter unit shown in Fig. 1309 as a complete transmitter feeding the antenna, it may be combined with the power-supply units of Figs. 1313 and 1316 and the antenna tuner of Fig. 1317 (using the large 0.045-inch spacing condensers) to make a complete 75-watt transmitter unit.

The combination 250-volt power supply of Fig. 1313 will supply plate voltage for the oscillator and doubler stages, as well as screen and bias voltages for the 807. Filament supply also is obtainable from this unit. Plate voltage for the 807 is furnished by the power supply unit of Fig. 1316.

The combined height of all units (assuming the power-supply unit of Fig. 1313 to be mounted on a 7-inch panel) will be $29\frac{3}{4}$ inches. The separate filament transformer, T_3 , shown in the diagram of Fig. 1315 will not be required since the necessary heater power for the transmitter can be obtained from the 250-volt supply.

Fig. 1319 — A 90-watt c.w. transmitter using a 6L6 Tri-tet oscillator and a push-pull 6L6 amplifier. The rack-width panel of the transmitter is 7 inches high. The single milliammeter is switched from the oscillator to the amplifier by the rotary switch at the lower left. The three remaining controls are for tuning the oscillator plate, amplifier plate and antenna tank circuits. All sockets, except those for the amplifier- and antenna-tank coils are sub-mounted. The three insulated terminals just visible at the right rear behind the antenna coil, L_4 , are the binding-post output connections for the antenna tuner.

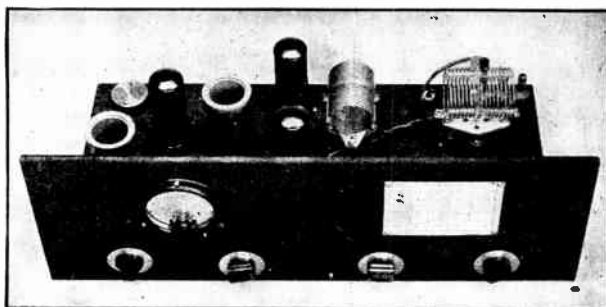

Ⓢ A 90-Watt C.W. Transmitter Using Push-Pull 6L6s

In the 90-watt c.w. transmitter shown in Figs. 1319 and 1320, a 6L6 Tri-tet oscillator drives a pair of 6L6s in a push-pull inverted amplifier circuit (also known as cathode coupling — § 3-3 and 4-7). The circuit diagram appears in Fig. 1321.

The sockets for the crystal and the cathode coil are wired as shown in Fig. 1385, to permit feeding with a v.f.o. unit if desired. The plate circuit of the oscillator is parallel-fed to permit grounding of the rotor of C_2 in mounting. A high-capacity tank condenser is used so that two bands may be covered with one coil, reducing coil-changing when shifting from one band to another. The cathode coil, L_5 , by which the oscillator and amplifier are coupled, is center-tapped to provide push-pull input to the amplifier stage.

While neutralization is not required, a certain amount is introduced through the fixed condensers C_9 and C_{10} from plates to cathodes partially to nullify the effects of degeneration inherent in this type of circuit and thereby reduce excitation requirements. Neutralization is not carried to the point where there is danger of instability. All r.f.-wiring leads in the amplifier should be made as short and direct as possible. The individual grid condensers, C_7 and C_8 , should be connected directly to the grid terminals at each socket.

The output of the amplifier is link-coupled to an antenna tuner. The lower stator of C_4 is


fitted with a flexible lead terminated in an insulated banana plug which may be plugged into any one of the antenna terminals, which are jack-top binding posts. These posts are insulated from the chassis by mounting them in National polystyrene button-type insulators which have been drilled out. Series tuning with high capacity is obtained by placing the plug in terminal No. 1 and connecting the feeders to terminals Nos. 2 and 3, and series tuning with low capacity by leaving the plug free and connecting the feeders to terminals Nos. 2 and 3. High-capacity parallel tuning is obtained by placing the plug in terminal 1, shorting terminals 2 and 3, and connecting the feeders between 1 and 3, while parallel tuning with low capacity is obtained by placing the plug in terminal 3 and connecting to 1 and 3.

Both stages are keyed simultaneously in the cathode return leads. The milliammeter, MA , can be switched from the oscillator-cathode circuit to that of the amplifier. Switching of the meter is simplified by inclusion of the shunting resistances, R_6 and R_7 , which are sufficiently high in value to have negligible effect upon the reading of the meter.

The transmitter can be operated at maximum input from the 450-volt power supply shown in Fig. 1304, provided a 200-ma. power transformer (Utah Y620E) and filter choke (Utah 4668) are substituted for those specified.

Tuning — Tuning of the transmitter is quite simple. It should be borne in mind that output from the oscillator may be obtained at

Fig. 1320 — The three tank condensers are mounted underneath the chassis of the 90-watt transmitter. The two split-stator condensers are mounted from the rear edge with insulating pillars, and their shafts are fitted with insulating couplings and panel bearings. They must be mounted so their shafts come level with that of C_2 to the left, which is mounted directly on the chassis. Heavy bare-wire leads through grommeted holes connect the amplifier and antenna tank condensers and coils.

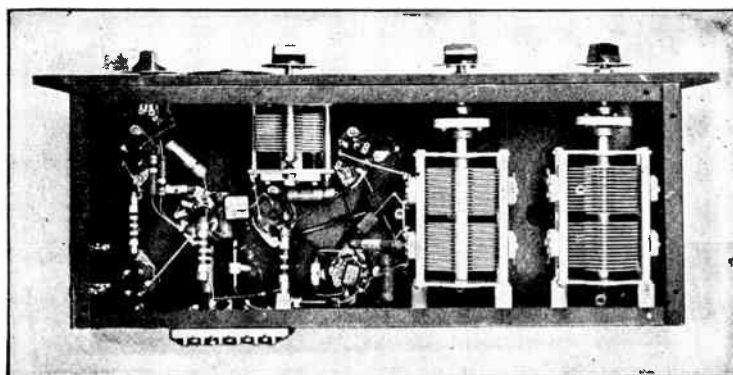

either the fundamental frequency of the crystal or at the second harmonic of that frequency, and that the selection of the proper coil for L_1 depends upon the crystal frequency and not the output frequency of the oscillator. Using the oscillator plate coils listed below Fig. 1321, the lowest-frequency band will be found near the maximum-capacity end on the dial of C_2 , while the higher-frequency bands will be found near the minimum capacity end of its tuning range.

With the milliammeter switched to the oscillator circuit, the plate-current reading should be about 60 ma. when the key is closed if a full 350 volts is used on the plate. As C_2 is tuned through resonance, the oscillator plate current will dip to about 25 ma. at the lower frequencies and to about 50 ma. at the higher frequencies.

When the meter is switched to the amplifier stage, a plate-current reading of about 260 ma. should be obtained with the key closed. A plate-current dip to 50 ma. or less should be obtained when C_3 is tuned to resonance.

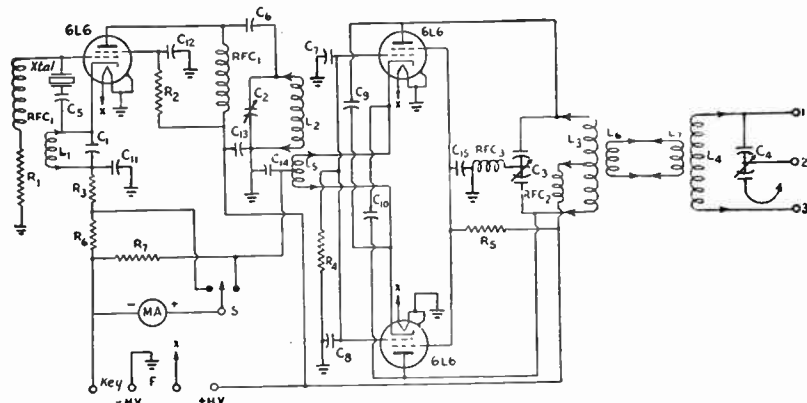


Fig. 1321 — Circuit diagram of the 90-watt push-pull 6L6 transmitter with built-in antenna coupler.

- | | | |
|--|---|---|
| C_1 — 100- μ fd. mica. | C_9, C_{10} — 10- μ fd. mica. | R_6, R_7 — 25 ohms, 1-watt. |
| C_2 — 250- μ fd. variable (National TMS-250). | $C_{11}, C_{12}, C_{13}, C_{14}, C_{15}$ — 0.01 μ d. paper. | MA — 0-300 milliammeter. |
| C_3, C_4 — 250 μ fd. per section (Hammarlund MTC-D-250-C). | R_1 — 0.1 megohm, $\frac{1}{2}$ -watt. | S — S.p.d.t. switch. |
| C_5, C_6 — 0.001- μ fd. mica. | R_2 — 50,000 ohms, 2-watt. | RFC ₁ — 2.5-mh. r.f. choke, 100-ma. |
| C_7, C_8 — 50- μ fd. mica. | R_3 — 500 ohms, 1-watt. | RFC ₂ — 1-mh. r.f. choke, 300-ma. (National R300). |
| L_1 * — For 1.75-Mc. crystals: 32 turns No. 24 d.s.c., close-wound. | R_4 — 25,000 ohms, 1-watt. | RFC ₃ — v.h.f. parasitic choke (Ohmite Z-1). |
| For 3.5-Mc. crystals: 10 turns No. 22, 1 inch long; 100- μ fd. mica condenser mounted in form, connected across winding. | R_5 — 12,000 ohms, 10-watt. | |
| For 7-Mc. crystals: 6 turns No. 22, $\frac{5}{8}$ -inch long. | | |
| L_2 * — For 1.75- and 3.5-Mc. bands — 38 turns No. 18 d.s.c. close-wound. | | |
| For 3.5- and 7-Mc. bands — 20 turns No. 18, $1\frac{1}{2}$ inches long. | | |
| For 7- and 14-Mc. bands — 9 turns No. 18, $1\frac{1}{2}$ inches long. | | |
| L_3 ** — B & W JCL series coils, dimensions as follows: | | |
| 1.75 Mc. — 60 turns No. 24, $2\frac{1}{4}$ inches long. | | |
| 3.5 Mc. — 44 turns No. 20, $2\frac{1}{4}$ inches long. | | |
| 7 Mc. — 26 turns No. 16, $2\frac{1}{8}$ inches long. | | |
| 14 Mc. — 16 turns No. 16, $1\frac{1}{8}$ inches long. | | |
| | L_4 *** — B & W JVL series coils, dimensions as follows: | |
| | 1.75 Mc. — 56 turns No. 24. | |
| | 3.5 Mc. — 40 turns No. 20. | |
| | 7 Mc. — 24 turns No. 16. | |
| | 14 Mc. — 14 turns No. 16. | |
| | 14 Mc. (series) — 8 turns No. 16. | |
| | L_5 — 1.75- and 3.5-Mc. bands — 20 turns, centertapped, No. 24 e., close-wound, wound close to bottom of L_2 on same form. | |
| | 3.5- and 7-Mc. bands — 14 turns, centertapped, No. 22 e., close-wound, wound $\frac{1}{8}$ -inch from bottom of L_2 on same form. | |
| | 7- and 14-Mc. bands — 8 turns, centertapped, No. 20 e., close-wound, wound $\frac{1}{8}$ -inch from bottom of L_2 on same form. | |
| | L_6, L_7 — 3 turns at center of L_3 and L_4 . | |

* All wound on Hammarlund $1\frac{1}{2}$ -inch diameter 4-prong forms.

** All $1\frac{1}{2}$ inches in diameter.

Once these adjustments have been completed, the antenna may be coupled and tuned. When the plate current of the amplifier under load increases to 200 ma. as C_4 is tuned to resonance, this represents about the optimum loading condition. Using a plate voltage of 450 and with proper adjustment of the amplifier, it should be possible to obtain a power output of 50 to 60 watts on all bands.

Because of the oscillator reaction caused by modulation, resulting from use of the inverted amplifier circuit, this transmitter is recommended for c.w. work only.

Complete 90-Watt C.W. Transmitter

The 90-watt 6L6 r.f. unit of Fig. 1319 may be combined with the power-supply unit showing Fig. 1316 (with the separate 6.3-volt filament transformer, Tr_3 , included to supply the greater heater power requirements of the 6L6s) to form a complete c.w. transmitter. The two units will have a combined height of $15\frac{3}{4}$ inches when they are mounted in a standard relay rack or cabinet.

*** All $1\frac{1}{8}$ -inch diameter, $2\frac{1}{4}$ inches long. Dimensions are approximate for parallel tuning for the band indicated. For series tuning, the coil for the next-higher frequency band is approximately correct.

A Three-Stage 100-Watt Transmitter for Five Bands

The three-stage transmitter shown in Figs. 1322, 1324 and 1325 is designed to use a single 1000-volt 100-ma. tube such as the 1623, 809, HY40, or higher-voltage tubes at reduced ratings in the output stage.

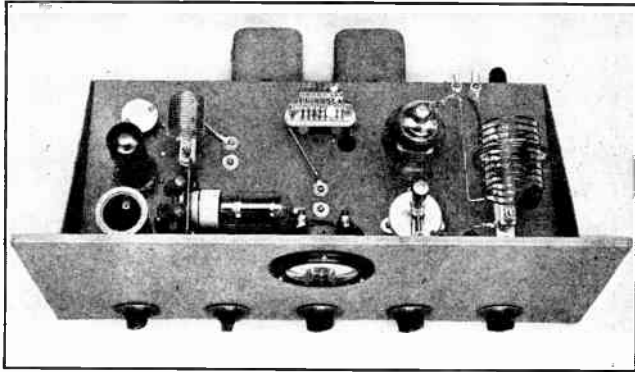


Fig. 1322 — All controls for the 100-watt five-band transmitter are below the chassis level. From left to right, they are the oscillator screen-voltage potentiometer, the oscillator plate-tank condenser, the buffer-doubler plate-tank condenser, the meter switch and the final-amplifier plate-tank condenser. The panel is of standard rack width and is 8 3/4 inches high.

Referring to the circuit diagram of Fig. 1323, a 6L6, operating at a plate voltage of 400 but at reduced input, is used in the Tri-tet oscillator circuit. A potentiometer in the screen circuit provides a means of varying the screen voltage and, ultimately, the excitation to the final amplifier. The HY65 buffer-doubler circuit is capacitively coupled to the oscillator. This second stage makes it possible to obtain excitation for the final amplifier in a third band

from a single crystal, operation in the second band being available by doubling frequency in

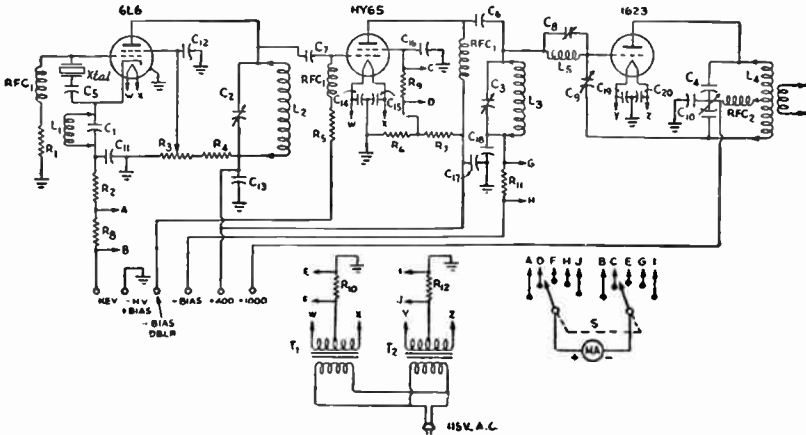


Fig. 1323 — Wiring diagram of the three-stage five-band 100-watt transmitter for 1000-volt operation.

- C₁ — 100- μ fd. mica.
- C₂, C₃ — 150- μ fd. variable (National ST-150).
- C₄ — 100 μ fd. per section, 0.05-inch spacing (Hammarlund HFBD-100-C).
- C₅, C₆ — 0.001- μ fd. mica.
- C₇ — 100- μ fd. mica.
- C₈ — 6 60- μ fd. mica trimmer (two National M-30 in parallel).
- C₉ — Neutralizing condenser (National NC-300).
- C₁₀ — 0.001 μ fd., 5000 volts test.
- C₁₁, C₁₂, C₁₃, C₁₄, C₁₅, C₁₆, C₁₇, C₁₈, C₁₉, C₂₀ — 0.01- μ fd. mica.
- R₁ — 0.1 megohm, 1/2-watt.
- R₂ — 300 ohms, 1-watt.
- R₃ — 20,000-ohm 10-watt potentiometer (Mallory E20MP).
- R₄ — 25,000 ohms, 10-watt.
- R₅ — 50,000 ohms, 1-watt.
- R₆ — 20,000 ohms, 10-watt.
- R₇ — 10,000 ohms, 10-watt.
- R₈, R₉, R₁₀, R₁₁, R₁₂ — 25 ohms, 1-watt.
- RFC₁ — 2.5-mh. r.f. choke.
- RFC₂ — 1-mh., 300-ma. r.f. choke (National R-300U).
- S — Double-gang, 5-circuit switch (Mallory 3226J).
- T₁, T₂ — Filament transformer, 6.3-volt, 3 amperes (UTCS-55).
- L₁ — 1.75-Mc. crystals — 32 turns No. 24 d.s.c., close-wound.
3.5-Mc. crystals — 9 turns No. 22, 1 inch long; 100- μ fd. mica in form, connected across winding.
7-Mc. crystals — 6 turns No. 22, 5/8-inch long. All on Hammarlund 1 1/2-inch diameter forms.
- L₂, L₃ — 1.75 Mc. — 56 turns, 1 1/4-inch diameter, 1 3/4 inches long, 54 μ h. (National AR80, no link).
3.5 Mc. — 28 turns, 1 1/4-inch diameter, 1 1/2 inches long, 15 μ h. (National AR40, no link).
7 Mc. — 14 turns, 1 1/4-inch diameter, 1 1/4 inches long, 4.2 μ h. (National AR20, no link).
14 Mc. — 8 turns, 1 1/4-inch diameter, 1 1/2 inches long, 1.25 μ h. (National AR10, no link).
28 Mc. — 4 turns, 1-inch diameter, 3/4-inch long, 0.5 μ h. (National AR5, turns close, no link).
- L₄ — 1.75 Mc. — 40 turns No. 18, 2 1/2-inch diameter, 2 1/2 inches long, 78 μ h. (B & W 160 BCL). An 80- μ fd. fixed air padder (Cardwell J10-80-OS) is placed in right-rear corner of chassis and attached to coil with flexible leads and clips.
3.5 Mc. — 32 turns No. 16, 2 1/2-inch diameter, 2 3/4 inches long, 39 μ h. (B & W 80 BCL).
7 Mc. — 20 turns No. 14, 2-inch diameter, 2 1/2 inches long, 12 μ h. (B & W 40 BCL).
14 Mc. — 8 turns No. 14, 2-inch diameter, 2 inches long, 2.5 μ h. (B & W 20 BCL). One removed turn from each end.
28 Mc. — 4 turns No. 12, 2-inch diameter, 1 3/4 inches long, 0.7 μ h. (B & W 10 BCL). One turn removed from each end.
L₅ — 5 turns No. 14, 1/2-inch diameter, 1/2-inch long.

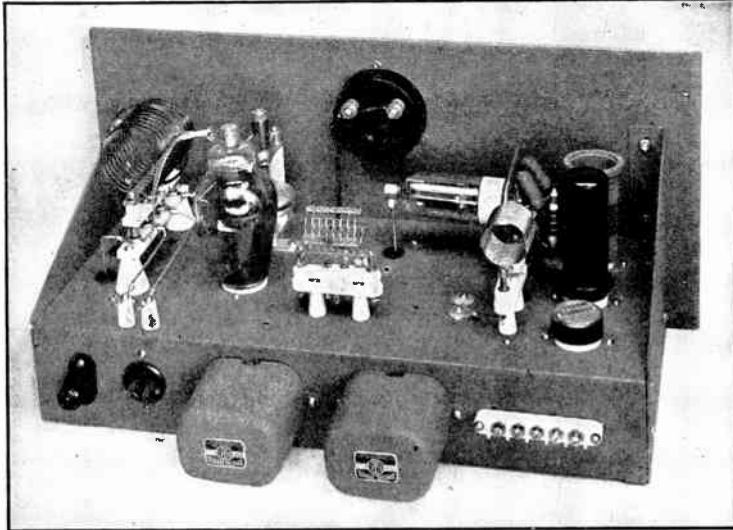


Fig. 1324 — On top of the chassis of the 100-watt transmitter, the cathode coil, L_1 , the 6L6 and the crystal are in line at the right-hand end. The 11Y65 is mounted horizontally on a small panel which also provides mounting space for the filament and screen-by-pass condensers, the coupling condenser, C_7 , the grid leak, R_6 , and the grid choke. L_2 is just to the left of the 6L6 and to the right of C_2 underneath. L_3 is in the center at right angles to L_2 and L_4 and just to the rear of C_3 underneath. The 1623 socket is submounted to lower the plate terminal. The neutralizing condenser, C_6 , is directly in front of the tube. RFC_2 is just to the left of L_4 . The two filament transformers are mounted on the rear edge.

the oscillator itself. Parallel plate feed is used in the second stage to permit series grid feed to the final amplifier, thereby avoiding the probability of low-frequency parasitic oscillations.

The neutralized final amplifier is directly coupled to the driver stage. C_8 and L_5 form a trap for v.h.f. parasitic oscillations.

The meter switch, S , shifts the milliammeter to read oscillator cathode current, driver screen current, driver cathode current, final-amplifier grid current and final-amplifier cathode current. The individual filament transformers permit independent metering of the cathode currents of the last two stages.

Power supply — This transmitter is designed to operate from the combination 1000-volt and 400-volt plate supply shown in Fig. 1327. Both fixed bias of 75 volts for the 11Y65 and cut-off bias for the final amplifier may be obtained from the unit shown in Fig. 1351. For the 1623 tube, resistors R_2 and R_3 should be 6000 ohms and 7000 ohms, respectively.

Tuning — Coils for the desired output frequency, consistent with the crystal frequency, should be plugged in the various stages, bearing in mind that frequency may be doubled in the plate circuit of the oscillator and again in the second stage, if desired. It should also be remembered that the selection of the cathode coil, L_1 , depends upon the crystal frequency and not necessarily the output frequency of the oscillator, the same cathode coil being used for both fundamental and second-harmonic output from the crystal stage. Since much better efficiencies can be obtained with the 11Y65 operating as a straight amplifier, it is advisable to avoid doubling in this stage.

The first two stages should be tested first, with all voltages applied except the plate voltage for the final amplifier. Tuning the oscillator to resonance, with the key closed, should cause a slight dip in cathode current accompanied by an abrupt rise in the screen and cathode current of the second stage.

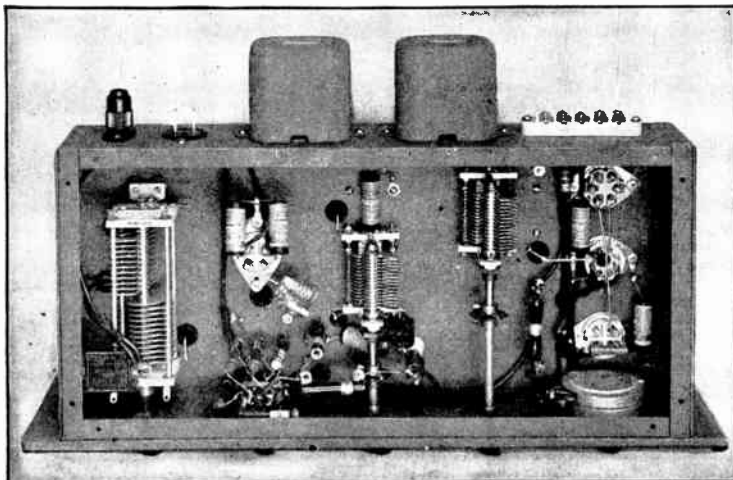


Fig. 1325 — Underneath the 8 x 17 x 3-inch chassis of the 100-watt transmitter. C_2 to the right and C_3 in the center are insulated from the chassis by polystyrene button insulators. C_4 to the left also is insulated and is spaced from the chassis to bring all shafts at the same level. Leads to the coils immediately above the tank condensers pass through large grommeted clearance holes. Mcter-shunt resistances are soldered directly to the switch terminals. R_3 at the right is insulated from the chassis by extruded bakelite washers. The v.h.f. parasitic trap is suspended in the amplifier grid lead to the left of C_3 . Insulating couplings are required for C_2 and C_3 .

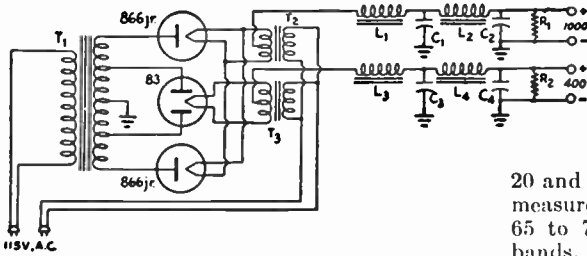


Fig. 1326 — Circuit diagram of the combination 1000- and 400-volt power supply for the 100-watt transmitter.

- C₁, C₂ — 2- μ fd. 1000-volt paper (Mallory TX805).
- C₃ — 4- μ fd. 600-volt electrolytic. (C-1) 604).
- C₄ — 8- μ fd. 600-volt electrolytic. (C-1) 608).
- L₁, L₃ — 5/20-henry swinging choke, 150 ma. (Thordarson T-19C39).
- L₂, L₄ — 12-henry smoothing choke, 150 ma. (Thordarson T-19C46).
- R₁ — 20,000 ohms, 75-watt.
- R₂ — 20,000 ohms, 25-watt.
- T₁ — High-voltage transformer, 1075 and 500 volts r.m.s. each side, 125- and 150-ma. simultaneous current rating (Thordarson T-19P57).
- T₂ — 2.5 volts, 5 amperes (Thordarson T-19F88).
- T₃ — 5 volts, 4 amperes (Thordarson T-63F99).

Tuning the HY65 plate circuit to resonance should produce a good dip in cathode current, with a simultaneous reading of maximum grid current to the final amplifier.

The amplifier should then be neutralized and tested for parasitic oscillation. The latter is done by shifting the final-amplifier plate-voltage lead to the 400-volt tap and turning off the bias supply. No plate voltage should be applied to the exciter stages.

C₄ is then varied through its entire range for several settings of C₃. If at any point a change in the final-amplifier cathode current is observed, C₃ should be adjusted to eliminate it. During this process, plate voltage should not be applied long enough to cause appreciable heating of the tube.

Normal operating voltages may now be replaced and the final amplifier tuned up in the usual manner. A plate current of 100 ma. will indicate normal loading of the final amplifier. (Plate current will be the difference between grid and cathode currents under operating conditions.) With all stages tuned and the amplifier loaded normally, the oscillator cathode current should run between 16 and 30 ma., HY65 screen current between 6 and 11 ma., HY65 cathode current between 45 and 70 ma., HY65 grid voltage between 125 and 260 volts, oscillator screen voltage between 100 and 250

volts, and HY65 screen voltage between 210 and 250 volts, exact values depending upon whether the stage is operating at the fundamental or doubling frequency. Excitation should be adjusted to keep the amplifier grid current between

20 and 25 ma., when the grid voltage should measure 130 to 150 volts. Power output of 65 to 75 watts should be obtainable on all bands. The oscillator circuit may be arranged for optional v.f.o. input as shown in Fig. 1385.

If the output stage is to be plate-modulated, the plate voltage should be reduced to 750. Operating data for suitable tubes of other types will be found in the tables in the Chapter Twenty.

Complete 100-Watt 5-Band Transmitter

The transmitter of Fig. 1322 may be combined in a standard rack with other units to form a complete transmitter. Plate voltage for oscillator and driver as well as for the final-amplifier stage may be obtained from the duplex power supply shown in Fig. 1327. Bias voltage for both driver and final-amplifier stages may be obtained from the combination unit shown in Fig. 1351, with fixed bias for the HY65 being taken from the VR75-30 branch. A suitable antenna tuner is the one shown in Fig. 1317. The larger variable condensers should be used. The total height of the various units combined is 29³/₄ inches, allowing a 7-inch panel for the bias-supply unit.

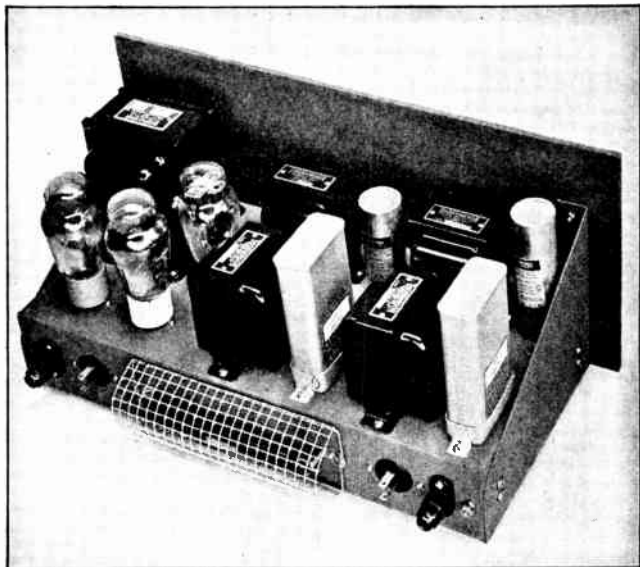


Fig. 1327 — This power supply makes use of a combination transformer and dual filter system delivering 1000 volts at 125 ma. and 400 volts at 150 ma., simultaneously. The circuit diagram is given in Fig. 1326. The 1000-volt bleeder resistor is mounted on the rear edge of the chassis, with a protective guard made of a piece of galvanized fencing material to provide ventilation. Millen safety terminals are used for the two high-voltage terminals. Ceramic sockets should be used for the 866 Jrs. The chassis measures 8 x 17 x 3 inches and the standard rack panel is 8³/₄ inches high.

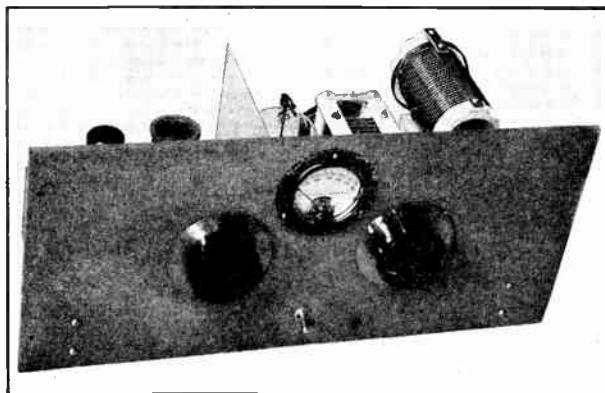


Fig. 1328 — Panel view of the two-tube medium-power transmitter. The switch shifts the meter from one stage to the other.

◀ A Two-Stage Medium-Power Beam-Tube Transmitter

The simplicity of the 300-watt transmitter shown in Figs. 1328, 1330, and 1331 will appeal to many amateurs. As the circuit of Fig. 1329 shows, a 6L6 Tri-tet oscillator supplies excitation at either the crystal fundamental frequency or its second harmonic for the HK257B in the output stage. Since the latter is a screened tube, no neutralizing is required.

The chassis is divided into two sections by a metal baffle shield with the oscillator at the left-hand end of the chassis and the amplifier to the right. The two tuning condensers are placed so that their dials are symmetrical on the panel.

On the other side of the shield, the amplifier tube is submounted by cutting a large hole in the chassis and spacing the socket on pillars so that it comes about 1¾ inches below. The glass envelope should just clear the top of the chassis. A spring contact strip is required so that the base shell of the tube is grounded to the chassis when it is plugged into the socket. The plate tank condenser is mounted in an inverted position on National type GS-2 ceramic pillars to bring its shaft up level with that of C_6 . The plate tank coils are wound on National type XR-10-A ceramic forms. Since the full form length is required for the 3.5-Mc. coil, the link winding for this band is preformed and held in place with ¼-inch bakelite strips. The link windings for the other bands may be wound on the form itself.


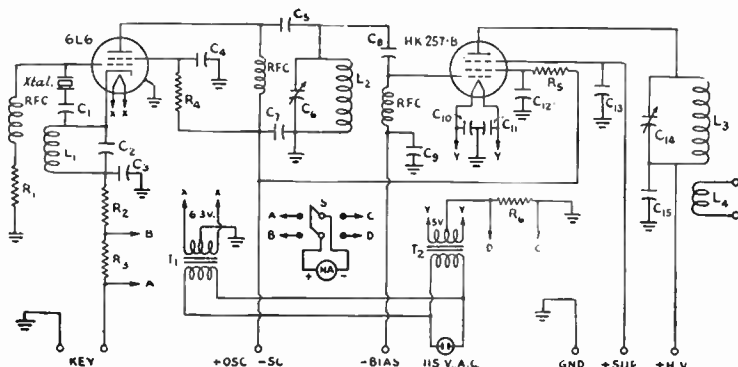


Fig. 1329 — Circuit diagram of the two-stage medium-power transmitter.

- C_1, C_5 — 0.001- μ fd. mica.
 C_2, C_8 — 100- μ fd. mica.
 $C_3, C_4, C_7, C_9, C_{10}, C_{11}, C_{12}, C_{13}$ — 0.01- μ fd. paper.
 C_6 — 250- μ fd. variable (National TMS-250).
 C_{14} — 100- μ fd. variable, 0.085-inch plate spacing (National TMH-100).
 C_{15} — 0.001- μ fd. 5000-volt mica.
 R_1 — 0.1 megohm, ½-watt.
 R_2 — 500 ohms, 1-watt.
 R_3 — 25 ohms, 1-watt.
 R_4 — 50,000 ohms, 10-watt.
 R_5 — 50 ohms, 1-watt.
 R_6 — 25 ohms, 10-watt.
kFC — 2.5-mh. r.f. choke.
MA — D.C. milliammeter, 300-ma. scale.
S — D.P.D.T. toggle switch.
 T_1 — Filament transformer, 6.3 volts, 2 amperes.
 T_2 — Filament transformer, 5 volts, 7.5 amperes.
 L_1 — For 3.5-Mc. crystals — 10 turns No. 22, 1 inch

- long, 100- μ fd. mica mounted in form connected across winding.
For 7-Mc. crystals — 6 turns No. 22, 5/8 inch long.
 L_2 — 3.5 and 7 Mc. — 15 turns No. 18 enameled, 7/8-inch long.
7 and 14 Mc. — 6 turns No. 18 enameled, 7/8 inch long.
Above coils wound on Hammarlund 1½-inch-diameter forms.
 L_3 — All coils wound on national NR-10-A 2½-inch-diameter forms.
3.5 Mc. — 25 turns No. 14 enameled, wound in successive grooves.
7 Mc. — 14 turns No. 12 enameled, wound in successive grooves.
14 Mc. — 6 turns No. 12 enameled, wound in alternate grooves.
 L_4 — Output link winding: 4 turns for 3.5 Mc., 3 turns for 7 Mc., 2 turns for 14 Mc. (see text).

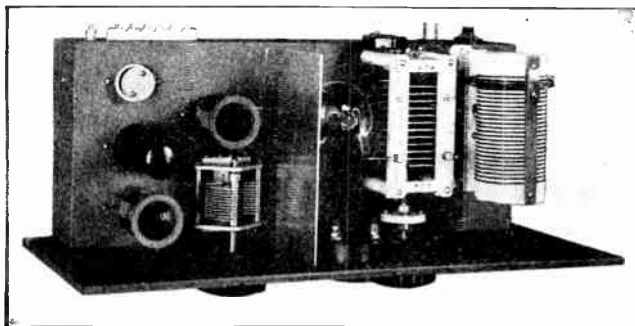


Left — Fig. 1330 — The oscillator and amplifier stages of the medium-power beam-tube transmitter are divided by a baffle shield. Oscillator components are to the left while the amplifier parts are assembled to the right.

Two filament transformers are required, 6.3 volts for the 6L6 and 5 volts for the 11K257B. Room for these will be found underneath the chassis. By means of the d.p.d.t. toggle switch, *S*, the meter may be connected to read either oscillator or amplifier cathode current.

The oscillator tuning condenser, *C*₆, has a sufficient capacity range to cover both the crystal fundamental frequency and the second harmonic. When tuning to the second harmonic, the plate current will show a smooth dip at resonance, similar to amplifier tuning. At the crystal fundamental, however, more care must be used in tuning the plate circuit, since if it is tuned too close to resonance oscillation will break off entirely or keying will be chirpy.

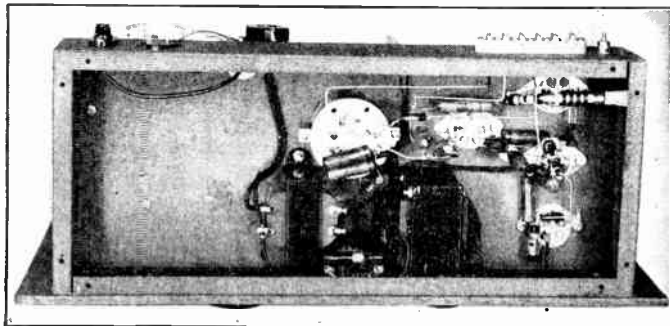The amplifier should be provided with sufficient fixed bias to cut off plate current with excitation removed but plate voltage applied. The additional bias required for proper operating conditions, depending upon the screen and plate voltages used, may be obtained from a grid-leak resistance of suitable value.



Below — Fig. 1331 — The filament transformers for the two-tube medium-power transmitter are mounted underneath the chassis along with all by-pass condensers and resistors. The socket for the amplifier tube is dropped to bring the glass envelope close to the top surface of the chassis.

Antenna Tuner for Medium Power

The antenna tuner shown in Fig. 1334 will usually be satisfactory for amplifiers operating at plate voltages not in excess of 1250 volts.

The two condensers are mounted from the panel by means of insulating pillars taken from National GS-1 insulators, which are fastened to the end plates with small sections of machine screws from which the heads have been cut. The variable link coil is mounted between the two rear end plates. The size of the coil is varied by short-circuiting turns, using clips which are attached to the condensers with flexible leads. As shown by the circuit diagram, Fig. 1333, the condensers are connected

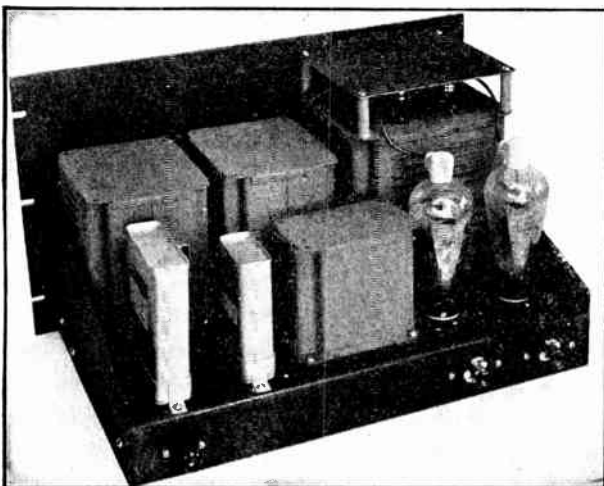


Fig. 1332 — This power supply unit delivers 830, 1060 or 1250 volts at 250 ma. The required voltage is selected by taps on the secondary. Ripple is only 0.25 per cent and the regulation is about 10 per cent. The transformer terminal board is covered with a panel mounted on pillars at the four corners. Insulating caps are provided for the tube plate terminals. A Millen safety terminal protects the high-voltage connection. The chassis measures 11 × 17 × 2 inches and the panel size is 10½ × 19 inches. The circuit is the same as that in Fig. 1350, the following components being used:

- C*₁ — 2 μfd, 500 volt (Aerovox Hyvol).
- C*₂ — 4 μfd, 1500 volt (Aerovox Hyvol).
- L*₁ — Input choke, 5.25 henrys, 300 ma., 90 ohms (UTC S34).
- L*₂ — Smoothing choke, 15 henrys, 300 ma., 90 ohms (UTC S33).
- r* — 25,000 ohms, 100-watt.
- T*₁ — 1500-1250-1000 volts r.m.s. each side, 300 ma. d.c. (UTC S47).
- T*₂ — 2.5 volts, 10 amperes, 10,000-volt insulation (UTC S57).

in parallel when the second pair of clips connects each rotor to the stator of the opposite condenser. The feeders are connected to the two large stand-off insulators mounted on the panel.

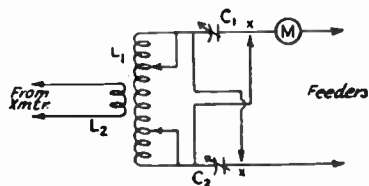


Fig. 1333 — Circuit diagram of the link-coupled antenna-tuning unit for use with medium-power transmitters. C_1 , C_2 — 100- μ fd. variable, 0.07-inch spacing (National TMC-100).

L_1 — 22 turns No. 14, diameter $2\frac{3}{4}$ inches, length 4 inches (Coto with variable link).

L_2 — 4 turns, rotating inside L_1 .

M — R.f. ammeter, 0-2.5-ampere range for medium-power transmitters.

¶ A Push-Pull Amplifier for 200 to 500 Watts Input

Figs. 1335, 1337 and 1338 show various views of a compact push-pull amplifier using tubes of the 1500-volt 150-ma. class, although the design is also suitable for use with tubes of the 1000-volt 100-ma. class. With the lower plate voltages, a plate tank condenser with a spacing between plates of 0.05 inch and smaller tank coils may be used.

The circuit, shown in Fig. 1336, is quite conventional, with link coupling at both input and output. The tuned circuits, L_3C_6 and L_4C_5 , are traps important for the prevention of v.h.f. parasitic oscillations. The 100-ma. meter may be shifted between the grid and cathode circuits for reading either grid current or cathode current. When shifted to read cathode current, the meter is shunted by a resistor, R_2 , which multiplies the scale reading by five. This resistor is wound with No. 26 copper wire, the length being determined experimentally to give the desired scale multiplication.

Construction — The mechanical arrangement shown in the photographs results in a compact unit requiring a minimum of panel space. The tank condenser is mounted on the

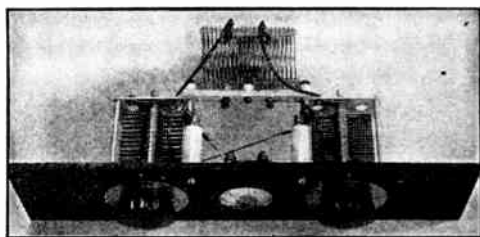


Fig. 1334 — A link-coupled antenna-tuning unit for use with resonant feed systems and medium-power amplifiers. The inductance, with variable link, is mounted on the condenser frames. Clips are provided for changing the number of turns and for switching the condensers from series to parallel. The panel is $5\frac{1}{4} \times 19$ inches.

left-hand partition (Fig. 1337) at a height which brings its shaft down $2\frac{5}{8}$ inches from the top of the panel. The plate tank-coil jack bar is mounted centrally with the condenser on spacers which give a $\frac{1}{2}$ -inch clearance between the strip and the partition. C_{10} is mounted with a small angle on the partition under the center of C_2 . Leads from both ends of the rotor shaft are brought to one side of C_{10} for symmetry.

The two tube sockets are mounted in a line through the center of the chassis and at opposite ends of the plate tank condenser. They are spaced about one inch below the chassis on long machine screws. The neutralizing condensers are placed between the two tubes, so that the leads from the plate of one tube to the grid of the other are short. The r.f. choke is mounted just above the tank condenser.

The right-hand partition is cut out at the forward edge to clear the meter. This cut-out can be readily made with a socket punch and a hacksaw. The socket for the grid tank coil is mounted $4\frac{1}{2}$ inches behind the panel, just above the chassis line.

The grid tank condenser, C_1 , is mounted under the chassis without insulation. Large clearance holes, lined with rubber grommets, are drilled for connecting wires which must be run through the chassis or partitions. The parasitic traps are made self-supporting in the plate leads from the tank condensers to the


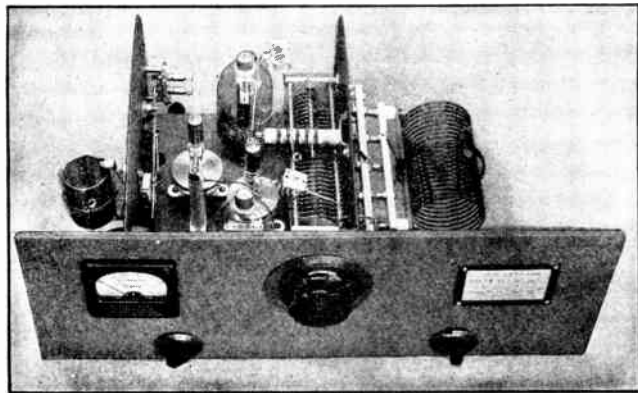


Fig. 1335 — A general view of the compact 450-watt push-pull amplifier, showing the front panel and top-of-chassis arrangement. Mounted on a standard relay rack, the height is only 7 inches and the depth 9 inches. Grid and plate tank circuits are isolated from each other by the double shielding partitions. On the panel are the 0-100 ma. milliammeter, which is switched to read current in all circuits, the plate-tank tuning dial, and a chart giving coil and tuning data. The small knob at the left below is the grid-circuit tuning control, while the one to the right is for the meter switch. The tube sockets are mounted adjacent to the stator terminals of the plate-tank condenser, C_2 , in the center, with the neutralizing condensers between, providing short leads.

Fig. 1336 — Circuit diagram of the 450-watt push-pull amplifier.

- C₁ — 100 μ fd. per section, 0.03-inch spacing (Hammarlund HFAD-100-B).
- C₂ — 100 μ fd. per section, 0.07-inch spacing (Hammarlund HFBD-100-E).
- C₃, C₄ — Neutralizing condensers (National NC-800).
- C₅, C₆ — 3-30- μ fd. mica trimmers (National M-30).
- C₇, C₈, C₉ — 0.01- μ d. mica.
- C₁₀ — 0.001- μ d. mica, 7500-volt rating (Aerovox 1653).
- R₁ — 25 ohms, 1-watt.
- R₂ — Meter-multiplier resistance for 5-times multiplication, wound with No. 26 wire.
- RFC — 1-mh. r.f. choke (National R-154U).
- MA — Milliammeter, 100-ma.

- I₁ — B & W JCL series, dimensions as follows: *
 - 3.5 Mc. — 44 turns No. 20, 2 $\frac{1}{8}$ inches long.
 - 7 Mc. — 26 turns No. 16, 2 $\frac{1}{8}$ inches long.
 - 14 Mc. — 14 turns No. 16, 1 $\frac{7}{8}$ inches long (remove 2 turns from B & W coil).
 - 28 Mc. — 6 turns No. 16, 1 $\frac{7}{8}$ inches long (remove 2 turns from B & W coil).
- I₂ — B & W TCL series, dimensions as follows: **
 - 3.5 Mc. — 26 turns No. 12, 3 $\frac{1}{2}$ -inch diameter, 4 $\frac{1}{2}$ inches long.
 - 7 Mc. — 22 turns No. 12, 2 $\frac{1}{2}$ -inch diameter, 4 $\frac{1}{2}$ inches long.
 - 14 Mc. — 10 turns No. 12, 2 $\frac{1}{2}$ -inch diameter, 4 $\frac{1}{2}$ inches long, remove one turn from each end.
 - 28 Mc. — 4 turns $\frac{1}{8}$ -inch copper tubing, 2 $\frac{1}{2}$ -inch diameter, 4 $\frac{1}{2}$ inches long. Remove one turn from each end.

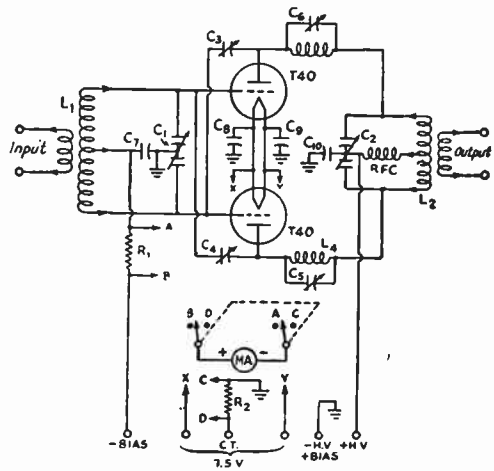

L₃, L₄ — 4 turns No. 14, $\frac{1}{2}$ -inch diameter, $\frac{3}{4}$ -inch long.

- * All 1 $\frac{1}{2}$ -inch diameter, 3-turn links.
- ** All coils fitted with 2-turn links.

tube caps. The panel is placed so that the plate tank-condenser shaft comes at the center. The meter switch is mounted to balance the knob controlling C₁.

Power supply and excitation — The T40 tubes shown in the photographs operate at a maximum plate voltage of 1500 for c.w. work. For this, the unit shown in Fig. 1349 is suitable. The supply shown in Fig. 1352, minus the VR-tube branch, will provide the biasing voltage required for plate-current cut-off. R₂ should have a resistance of 2500 ohms and R₃ of 1500 ohms. A filament transformer delivering 7.5 volts at 5 amperes also will be required. The exciters of Figs. 1305 or 1309 will furnish adequate excitation.


Tuning — After the amplifier has been neutralized, a test should be made for parasitic oscillation. The bias should be reduced until the amplifier draws a plate current of about 100 ma. without excitation. With C₁ adjusted to various settings, C₂ should be varied through

its range and the plate current watched closely for any abrupt change. Any change will indicate oscillation, in which case C₅ and C₆ should be adjusted simultaneously in slight steps until the oscillation disappears. Unless the wiring differs appreciably from the original, complete suppression will be obtained with the two condensers at full capacity. Changing bands should have no effect upon this adjustment.

With normal bias replaced, the amplifier should now be tuned up and the excitation adjusted so that a grid current of 60 ma. is obtained with the amplifier fully loaded. Full loading will be indicated when the cathode-current meter registers 360 ma., which includes the 60-ma. grid current. Under these conditions the biasing voltage should rise to 150 volts, dropping to about 70 volts without excitation when the plate current will fall to almost zero.

If the amplifier is to be plate-modulated, the plate voltage should be reduced to 1250 and the loading decreased to reduce the plate

Fig. 1337 — All components of the 450-watt push-pull amplifier are assembled around a small metal chassis 7 × 2 × 9 inches deep. The partitions are standard 6 $\frac{1}{2}$ × 10-inch interstage shields. The plate tank condenser is mounted on the left-hand partition. The plate tank-coil jack-bar is mounted centrally, opposite the condenser, on spacers which give $\frac{1}{2}$ -inch clearance between the strip and the partition. C₁₀ is mounted with a small angle bracket on the partition under the center of C₂. The socket for the grid tank coil is mounted just above the chassis line. Millen safety terminals are used for the external high-voltage plate and bias connections.

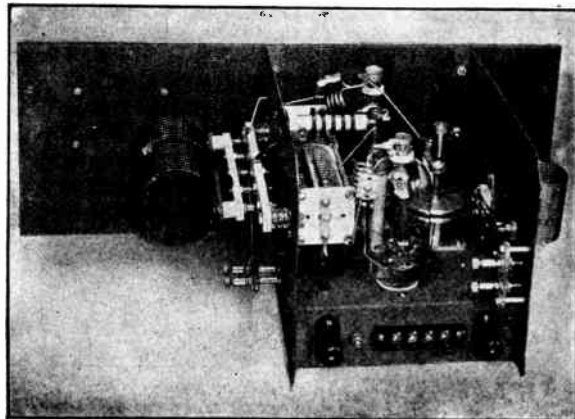

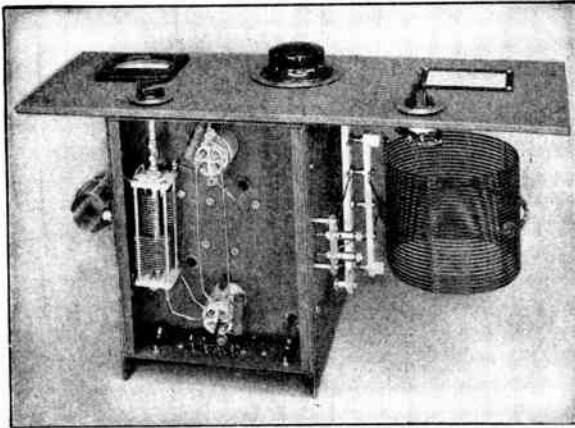


Fig. 1338 — Bottom view of the 450-watt push-pull amplifier, showing the grid tank condenser between the two tube sockets.

current to 250 ma. The same bias-supply adjustment will be satisfactory for this type of operation but excitation may be reduced to give a grid current of 40 ma., bringing the total cathode current to 290 ma. The antenna tuner shown in Fig. 1334 or the pi-section network of Fig. 1340 may be used.

Operating conditions for tubes of other characteristics will be found in Chapter Twenty.

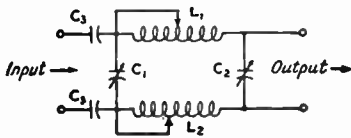


Fig. 1339 — Diagram of the pi-section antenna coupler. C₁-C₂ — 300- μ fd. variable, 0.07-inch spacing (National TMC-300). C₃ — 0.01- μ fd. mica., 5000-volt rating. L₁, L₂ — 26 turns No. 14, 2 $\frac{1}{2}$ -inch diameter, 3 $\frac{1}{2}$ inches long (National XR10A form wound full).

□ A Pi-Section Antenna Coupler

The photograph of Fig. 1340 shows the constructional details of a pi-section type antenna coupler. The wiring diagram appears in Fig. 1339. All parts are mounted directly on the panel using flathead machine screws. The condensers each are supported on three ceramic pillars from National type GS-1 stand-off insulators. A $\frac{3}{4}$ -inch 6-32 machine screw is inserted in one end of each pillar and turned tight. The head of the screw is then cut off with a hacksaw and the protruding quarter-inch or so is threaded into the mounting holes in the end plate of the condenser. The shaft is cut off about $\frac{1}{4}$ inch from the frame and fitted with a Johnson rigid insulated shaft coupling (No. 252). Since the coupling will extend beyond the stand-off insulators, a $\frac{3}{4}$ -inch clearance hole should be

cut in the panel for each shaft. Alternatively, metal washers could be used between the panel and each pillar to extend the mounting.

Each coil form is supported on 1 $\frac{1}{2}$ -inch cone insulators. The two high-voltage blocking condensers, C₃, also are mounted on pillars from GS-1 stand-offs. A copper clip on a flexible lead, connected permanently to one end of each coil, permits adjustment of the coil inductance by short-circuiting turns.

Output connections are made to the two terminal insulators at the right, while input connections are made to the terminals of the two voltage-blocking condensers. When single-wire output is desired, the output terminal connected to the condenser rotors is grounded and the coil in that side short-circuited by the clip and lead.

Under most circumstances the components specified will work satisfactorily with transmitters of 400 or 500 watts input, operating at plate voltages up to 1500. For higher power, the condensers should have greater spacing and the coils should be wound with No. 12 or larger wire. Couplers for lower power may be made using smaller components of equal values.

□ Complete 300- to 400-Watt Compact Plug-In Coil Transmitter

The compact exciter and amplifier units of Figs. 1305 and 1335 may be combined as a complete transmitter. Plate and filament supply for the exciter may be obtained from the unit of Fig. 1316. Plate voltage for the amplifier may be obtained either from the unit of Fig. 1332 or that of Fig. 1349. A 7.5-volt 5-ampere filament transformer may be combined on a 5 $\frac{1}{4}$ -inch panel with the unit of Fig. 1351 (minus the VR75-30 branch), which will furnish bias for the amplifier. A 45-volt "B" battery will be required for biasing the 807.

Suitable antenna tuners are those of Figs. 1334, 1353 or 1340. The height of all units, including a 5 $\frac{1}{4}$ -inch meter panel is 49 inches.

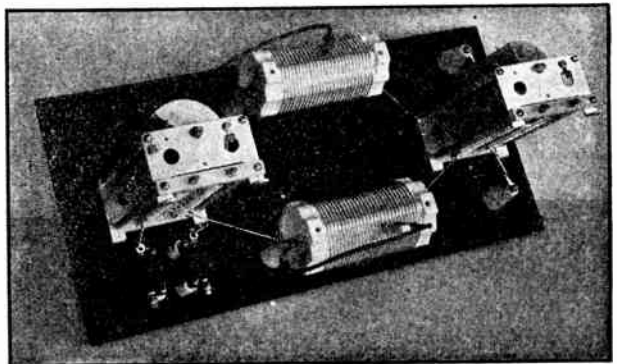


Fig. 1340 — Pi-section type antenna coupler. All parts are mounted on a Presdwood panel 8 x 19 inches. The circuit is given in Fig. 1339.

◀ A Compact 450-Watt Push-Pull Amplifier

The photographs of Figs. 1342, 1343 and 1344 show an amplifier designed along the lines of the type of construction often referred to as "dish type." This type of construction has many advantages, although its use normally is confined to components of moderate physical dimensions and weight.

The tank coils may be mounted so that very little metal of the normal rack structure is in the immediate fields of the tank coils — a condition almost impossible to approach in the usual form of construction with metal panels and side brackets. Plug-in coils are made much more accessible for changing and the direction of "pull" in removing coils is outward away from the rack rather than upward into the next rack unit above. Terminals may be mounted so that the wiring between rack

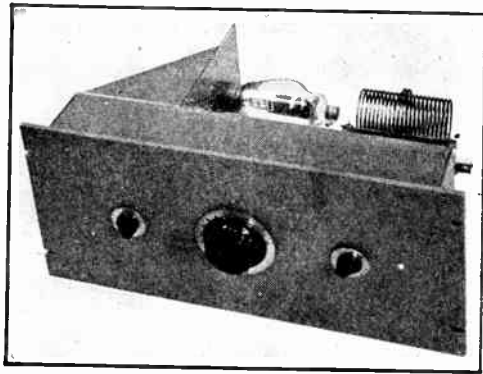


Fig. 1342 — The three controls of the 450-watt "dish-type" amplifier are arranged symmetrically. The meter switch is at the right, the control for the plate tank condenser at the center and the grid-circuit control at the left. The panel which is $8\frac{3}{4} \times 19$ inches is fitted with panel bearings for the condenser-shaft extensions. It is fastened to the chassis by flat-head screws after the bottom edges of the chassis have been drilled and tapped.

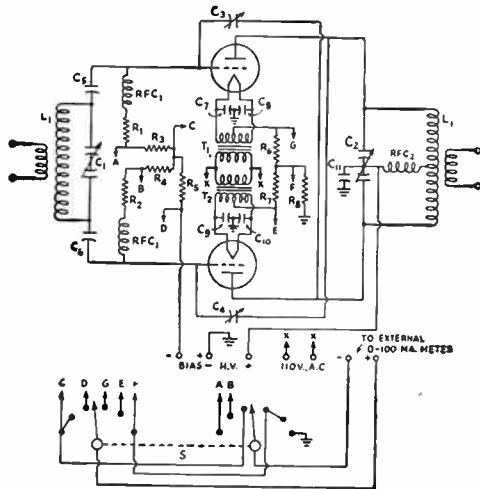


Fig. 1341 — Circuit diagram of the "dish-type" push-pull 450-watt amplifier.

- C₁ — 100 μ fd. per section (Hammarlund MCD100M).
- C₂ — 100 μ fd. per section (Cardwell MT100GD), 0.07-inch spacing.
- C₃, C₄ — Neutralizing condenser, 10 to 15 μ fd. (Hammarlund N10).
- C₅, C₆ — 500- μ fd. 600-volt mica.
- C₇, C₈, C₉, C₁₀ — 0.01- μ fd. 600-volt paper.
- C₁₁ — 0.002- μ fd. 5000-volt mica.
- R₁, R₂ — 6000 ohms, 10-watt.
- R₃, R₄, R₅ — 25 to 50 ohms, 2-watt.
- R₆, R₇, R₈ — Cathode-current meter shunts (see text).
- S — 2-gang, 6-position rotary switch (Mallory).
- T₁, T₂ — 6.3 volts, 6 amperes.
- L₁ — National AR series coils with center link (variable-link type recommended).

Substitute coils may be wound on $1\frac{1}{2}$ -inch diameter forms as follows:

- 3.5 Mc. — 44 turns, 2 inches long.
- 7 Mc. — 22 turns, 2 inches long.
- 14 Mc. — 10 turns, $1\frac{1}{2}$ inches long.
- 28 Mc. — 6 turns, $1\frac{1}{2}$ inches long.

L₂ — Barker and Williamson TL series with center links.

Substitute coils may be wound as follows on $2\frac{1}{2}$ -inch diameter forms:

- 3.5 Mc. — 36 turns, 4 inches long.
- 7 Mc. — 18 turns, 4 inches long.
- 14 Mc. — 10 turns, 3 inches long.
- 28 Mc. — 6 turns, 3 inches long.

units may be made inconspicuous and so that the chances of personal injury from accidental contact with exposed terminals at the rear are greatly reduced. Lastly, this form of construction usually reduces the required height of the unit which is a particular advantage in table racks where vertical space is at a premium.

The circuit of the amplifier shown in the diagram of Fig. 1341 is standard in every way except in the method of metering. By means of the two-gang six-position switch, it is possible to measure the individual grid and cathode currents of each tube as well as total grid or total cathode currents. To accomplish this, two small filament transformers are used, one for each tube, instead of a single large transformer. The meter is switched across shunting resistances in each circuit to simplify switching. In the cathode circuits, the shunting resistors should be carefully adjusted to provide a scale multiplication of ten, giving a full-scale reading of 1000 ma.

In doing the r.f. wiring, care should be taken to keep it as symmetrical as possible. In forming the long wires between the neutralizing condensers and the tank-condenser stators, the lengths should be made identical. The wire connecting to the rear condenser stator should go directly in a straight line, while the one going to the front stator section may be bent to make up for the difference in distance between the neutralizing condensers and the two stators. The plate leads to the tubes should be tapped on these long wires at points which will make the wire length between neutralizing condenser and plate and between tank condenser and plate equal on each side.

The positive high-voltage lead, run inside the chassis with high-voltage cable, comes up through a feed-through insulator near the plate choke.

The rotors of the grid tank condenser are not grounded, since experience has shown that

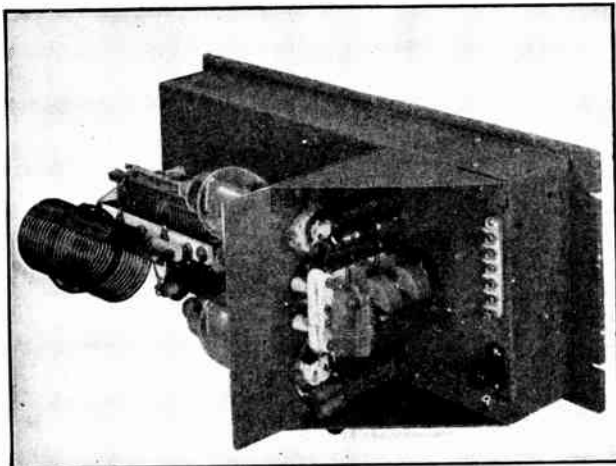



Fig. 1343 — The grid-circuit components of the "dish-type" 450-watt amplifier are mounted on this side of the partition which is braced by standard 5-inch triangular brackets. The tank condenser is mounted by means of a screw in the hole which remains when the shield between the stators is removed. The ceramic terminal strip is for all external connections except for positive high voltage for which a special safety terminal is provided. A large clearance hole should be cut in the chassis for the condenser shaft. The shaft, which should come at the center line of the chassis, should be provided with a flexible insulating coupling.

an amplifier of this type usually neutralizes more readily without the ground connection and excitation usually divides more evenly between the two tubes.

The leads from the neutralizing condensers to the grid terminals are crossed over before they pass through small feed-through points mounted in the partition. The grid r.f. chokes are self-supporting between the tube grid terminals and the feed-through points in the chassis which carry the biasing leads inside to the individual grid leaks. Filament wires are run through $\frac{3}{8}$ -inch holes lined with rubber grommets.

Inside the chassis, the leaks and meter-shunting resistances are supported on fibre lug strips. The leads going to the switch should be soldered in place, formed into cables and the other ends connected to the switch on

Fig. 1344 — The plate tank-coil jack strip of the 450-watt push-pull amplifier is fastened to the tank-condenser frame with strip-metal brackets. The assembly, mounted on $\frac{3}{8}$ -inch stand-off insulators is placed at the center of the chassis as far to the left as possible. The condenser shaft is extended at right angles through the bearing in the center of the chassis by means of two Millen 45-degree shaft joints connected together by a short length of bakelite shafting. The sockets for the tubes are submounted on the 6 × 8-inch partition $3\frac{1}{2}$ inches up from the chassis and $1\frac{1}{8}$ inch from each edge and are orientated so that the plates of the tubes will be in a vertical plane.

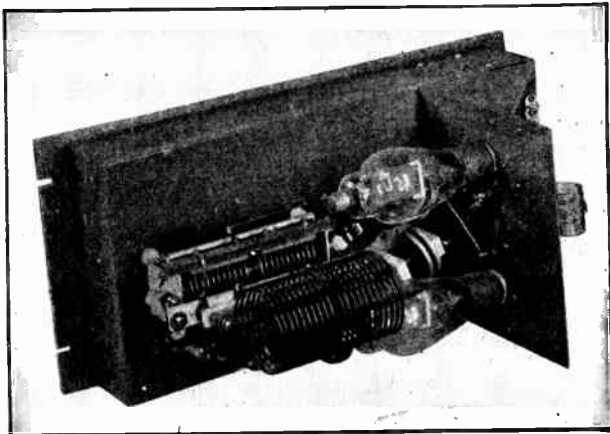

the panel as the last operation before putting the panel in place.

If the layout and wiring have been followed carefully, no difficulties should be encountered in neutralizing nor with parasites. Both grid and plate currents should check the same within ten per cent.

The meter when switched to read grid current forms a good neutralizing indicator. Both neutralizing condensers should be kept at equal settings and adjusted simultaneously until the grid current remains perfectly steady as the plate tank condenser is tuned through resonance. Neutralizing is always done with plate voltage removed.

The amplifier requires a driver delivering 25 to 40 watts. If the amplifier is to be protected with fixed bias against failure of excitation, the grid-leak resistance of each tube should be adjusted so the total grid voltage under operating conditions will be not less than 125 volts without exceeding the maximum grid-current rating of 25 ma. per tube when the amplifier is loaded to rated plate current.

□ A 450-Watt Band-Switching Amplifier

The photographs of Figs. 1345, 1347, and 1348 illustrate a 450-watt push-pull band-switching amplifier capable of handling a power input of 450 watts at 1500 volts for c.w. operation or 375 watts with plate modulation. While the type T55 is shown, any of the comparable triodes in the 1000- or 1500-volt class, such as the 809, T40, HY40, RK35, UH50, 808, 812, RK51 or 35T, may be used in a similar arrangement.

The circuit is shown in Fig. 1346. Band-switching is accomplished by short-circuiting turns of both plate and grid coils by means of tap switches. Any three adjacent bands may

be covered in this manner. By plugging in another pair of coils, a second set of three adjacent bands may be covered. Thus the 3.5-, 7- and 14-Mc. bands may be covered with one pair, and 7-, 14- and 28-Mc. bands with another pair. C_9L_3 and $C_{10}L_4$ are parasitic traps to eliminate v.h.f. parasitic oscillations. Fixed-link coupling is used at the input, with variable-link output coupling.

Coils — The plate-tank coils listed under the circuit diagram are of a special series designed primarily for use with a multisection tank condenser. They are provided with four extra plugs which are used, in this case, for the short-circuiting taps. The coil covering 7, 14 and 28 Mc. requires slight alteration, however. Two turns on each side of center are cut free from the supporting strips and left self-supporting; otherwise, the coil heating which usually occurs at 28 Mc. may be sufficient to ruin the base strip. At the same time, these two turns on each side should be reduced in diameter to $1\frac{1}{8}$ inches. This may be done quite readily by unsoldering the central ends, twisting the turns to the smaller diameter, and cutting off the excess wire. While the lower-frequency taps may be soldered, it is advisable to use clamps on the wire for the 28-Mc. taps. Johnson coil clips are suitable for this purpose.

Grid coils with sufficient mounting pins being unobtainable the taps for the grid coils are brought out to a five-prong Millen coil-

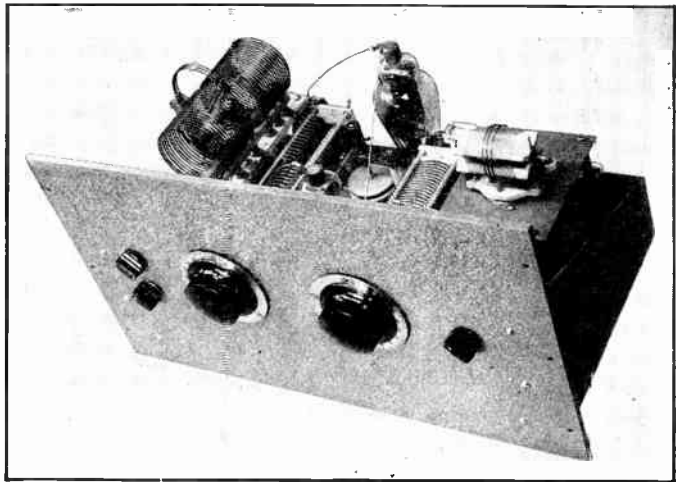


Fig. 1345 — A 450-watt band-switching amplifier. The panel size is $10\frac{1}{2} \times 19$ inches. The large dials on the panel control the plate and grid tank condensers. The uppermost of the two small knobs to the left is for adjusting the variable-link output coupling, while the lower knob is for the plate band-switch. The grid band-switch knob is to the right. All controls should be well insulated.

mounting bar (Type 40205). A plug-in socket for the bar is sub-mounted in back of the coil socket.

Wiring — All of the wiring, except for the power wiring underneath the chassis, is done with No. 14 tinned bus wire. Wherever possible, connections are made with short, straight pieces of wire running directly from point to point. Of most importance are the leads to the tube grids and plates. The leads to the tank condensers and those to the neutralizing condensers must be kept entirely separate; at no point should these leads be common. This practice helps in the prevention of parasitic oscillations. The grid by-pass condenser is mounted close to the grid-coil socket.

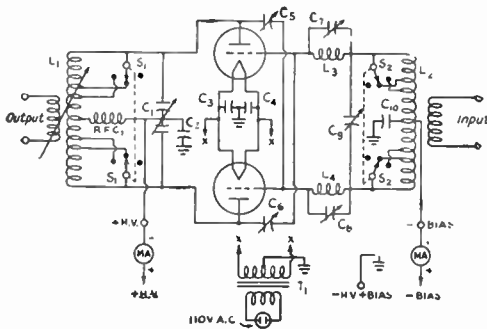


Fig. 1346 — Circuit diagram of the 450-watt amplifier. C_1 — 100 μ fd. per section, 0.07-inch plate spacing (Hammarlund HFBD-100-E). C_2 — 0.001- μ fd. 7500-volt mica (Aerovox 1623). C_3, C_4 — 0.01- μ fd. paper. C_5, C_6 — Neutralizing condenser (National NC800). C_7, C_8 — Isolantite mica trimmer, 20–100 μ fd. (Mallory CTX954). C_9 — 150 μ fd., 0.05-inch plate spacing (Hammarlund HFBD-150-C). C_{10} — 0.01- μ d. paper. RFC_1 — 1-mh. r.f. choke, 600 ma. (National R154).

- S_1 — Ganged sections of Ohmite BC-3 band-change switch.
- S_2 — Ganged sections of Mallory 162C Hamband switch.
- T_1 — 7.5-volt 6-ampere filament transformer (Thordarson T-19F94).
- L_1 — For 3.5-, 7- and 14-Mc. bands — 38 turns No. 14, $5\frac{1}{4}$ inches long, 2 $\frac{1}{2}$ -inch diameter, tapped at the 4th and 9th turn each side of center (B & W TVH-80 35 μ h., tapped each side of center at $2/19$ and $9/38$ of the total turns in each half).
- For 7-, 14- and 28-Mc. bands — 24 turns No. 12, $5\frac{1}{4}$ inches long, 2 $\frac{1}{2}$ -inch diameter, tapped at 2nd and 5th turns each side of center (see text for alterations) (B & W TVH-40) 13 μ h., tapped each side of center at approximately $1/6$ and $1/5\frac{1}{2}$ of the total turns in each half.
- L_2 — For 3.5-, 7- and 14-Mc. bands — 26 turns, $1\frac{1}{2}$ inches long, $1\frac{1}{2}$ -inch diameter, tapped at 5th and 9th turns from each side of center. (Coto CS80C) (17 μ h., tapped each side of center at $5/13$ and $9/13$ of the total turns in each half).
- For 7-, 14- and 28-Mc. bands — 16 turns $1\frac{1}{8}$ inches long, $1\frac{1}{2}$ -inch diameter, tapped at 1st and 3rd turns each side of center. (Coto CS40C) (5 μ h., tapped each side of center at $1/8$ and $3/8$ of the total turns in each half).
- L_3, L_4 — 8 turns No. 12, $1/2$ -inch inside diameter, $1\frac{1}{8}$ inches long.

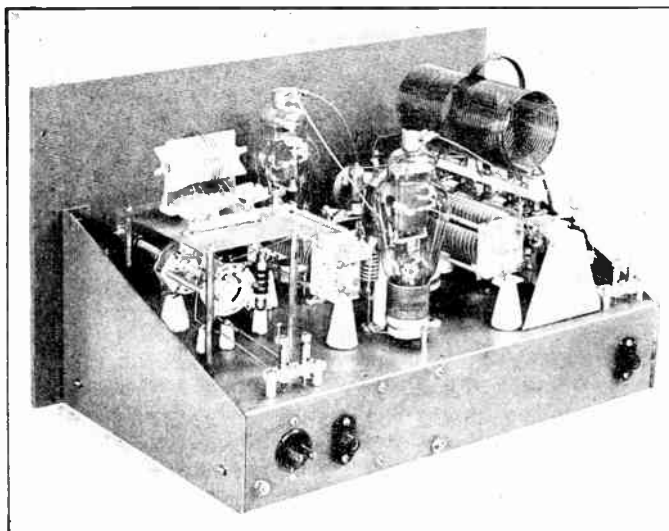



Fig. 1347—A view of the grid-circuit end of the band-switching push-pull amplifier, showing the coil-switching arrangement and the grid-coil-socket support.

Fig. 1346 shows how d.c. milliammeters of suitable ranges may be connected for reading the grid and plate currents. These are not included in the unit, but may be mounted in a separate meter panel constructed as shown in Fig. 1395. The grid-current meter should have a 100 ma. scale, while the plate-current meter should have a range of 500 ma.

Tuning—Any one of the r.f. units shown in Figs. 1305, 1309 or 1322 will furnish sufficient excitation for this amplifier, the band-switching exciter of Fig. 1309 being recommended as an excellent companion unit.

Before excitation is applied, the two parasitic-trap condensers, C_9 and C_{10} , should be set at maximum capacity. With excitation applied and plate voltage off, grid current to the amplifier stage should run between 60 and 90 ma.

Fig. 1348—Rear view of the 450-watt amplifier. The plate tank-coil jack bar at the right is mounted on brackets 27 inches high so that the variable-link shaft will clear the switches. These are mounted on 1-inch cone insulators after their brackets have been revamped to bring the shafts $1\frac{1}{2}$ inches above the chassis. The units are spaced so as to be central with the jack-bar terminals. The shafts are coupled with a section of $\frac{3}{8}$ -inch bakelite shaft fitted with brass reducing couplings at each end. The tank condenser is mounted on $1\frac{1}{2}$ -inch cone insulators. The plate r.f. choke and a feed-through insulator for high-voltage line are placed beneath the jack bar. The grid switch is mounted on insulators to balance the plate switch. The grid coil mounting is elevated directly over the switch. The tubes and the two neutralizing condensers are placed symmetrically between the two tank circuits.

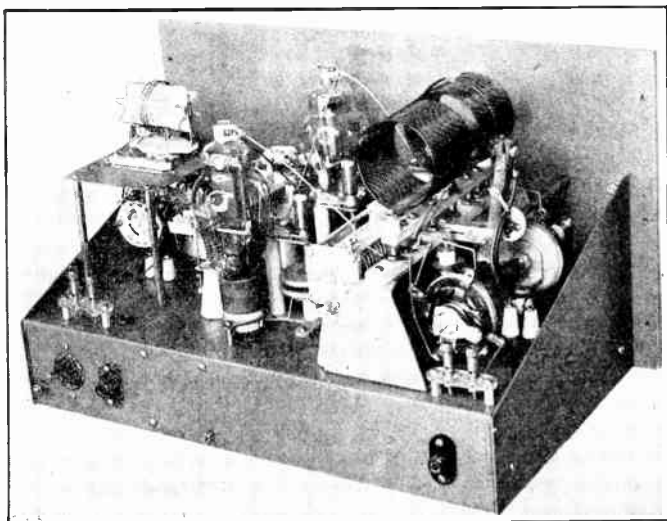

As the next step the amplifier should be neutralized, using the grid-current meter as a neutralization indicator. To test the amplifier for parasitic oscillation, the bias should be reduced to a point which will allow a plate current of 100 ma. or so to flow without excitation. This may be done by moving the biasing tap of the amplifier down toward the positive terminal of the bias supply. It is advisable to lower the plate voltage for this test, either by inserting a resistance of about 2500 ohms in series with the plate-voltage source or by inserting a 200-watt lamp in series with the primary winding of the plate transformer. The grid tank condensers should be set at various points while the plate tank condenser is swung through its range. The plate current should remain perfectly stationary while this is done. If a point is found where a sudden change in plate current takes place, C_9 and C_{10} should be adjusted, bit by bit, until the variation in plate current disappears. C_9 and C_{10} should be as close to maximum capacity as it is possible to set them and yet eliminate the parasitic oscillation.

Normal biasing voltage may now be replaced and the amplifier tuned up and loaded. For c.w. operation, the output should exceed 300 watts when operated at the maximum rated input of 1500 volts, 300 ma. With plate modulation, the plate current should be reduced to 250 ma. and the output should exceed 250 watts. The amplifier will operate satisfactorily with a grid current of 40 to 70 ma.

Fig. 1349 — This power supply delivers 1500 or 1250 volts at a full-load current of 425 ma., with 0.25 per cent ripple and regulation of 10 per cent. Voltages are selected by taps on the transformer secondary. The secondary terminal board is covered with a section of steel panel supported by brackets fastened underneath the core clamps and insulating caps are provided for the tube plate terminals. A special safety terminal (Millen) is used for the positive high-voltage connection. The panel is 10½ × 19 inches and the chassis size is 13 × 17 × 2 inches. The circuit for this supply is shown in Fig. 1350.

Reference should be made to the vacuum-tube tables in Chapter Twenty for data on the operation of other types of tubes.

◀ A Simple Combination Bias Supply

Fig. 1352 shows the circuit diagram of the simple transformerless bias unit, pictured in Fig. 1351, which may be used to supply cut-off bias voltages up to 100 volts or so. Through grid-leak action it will also provide the additional operating bias voltage required, if the resistor values are correctly proportioned. The circuit also includes a second branch, consisting of R_1 and a VR75-30 voltage-regulator tube, supplying regulated voltage. This branch may not be required in all cases, but will be convenient in many applications for providing fixed cut-off or protective bias for a low-power stage independent of the main output voltage.


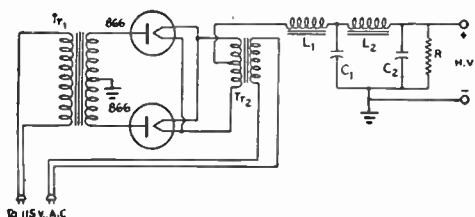


Fig. 1350 — Circuit diagram of the 1500-volt 42¹/₂-ma. plate power supply for the band-switching amplifier. C_1, C_2 — 4- μ fd. 2000-volt paper (C-1) TJI 20010). L_1 — 5–20 henrys, 500 ma., 75 ohms (Stancor C1405). L_2 — 8 henrys, 500 ma., 75 ohms (Stancor C1415). R — 20,000 ohms, 150-watt. Tr_1 — 1820–1520 volts r.m.s. each side of center-tap, 500 ma. d.c. (Stancor type P6157). Tr_2 — 2.5 volts, 10 amperes, 10,000-volt insulation (Stancor type P3025). This circuit is also used for the 1250-volt supply shown in Fig. 1332 and the 2500-volt supply shown in Fig. 13.0.

Adjustment — The voltage-divider resistances, R_2 and R_3 , are combined in a single resistor with two sliding taps. One of these taps alters the total resistance by short-circuiting a portion of the resistance at the negative end, while the other adjusts the cut-off voltage. The method of determining the values of resistance in each section is as follows:

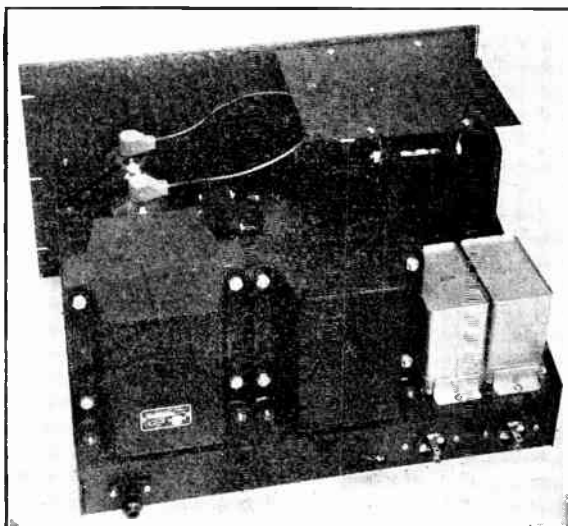The bias section, R_3 , is adjusted to equal the recommended grid-leak resistance for the tube or tubes in use. The value of resistance between



the biasing tap and the short-circuiting tap is determined by the following formula:

$$R_3 = \frac{160 - E_{co}}{E_{co}} \times R_2,$$

where E_{co} is the voltage required for plate-current cut-off. This value may be determined to a close approximation for triodes by dividing the plate voltage by the amplification factor of the tube. No supplementary grid-leak bias should be used in the stage being supplied by the pack.

The resistance in each section should be first set at the values determined by the formula. The biased amplifier should then be turned on, without excitation. If the plate current is not

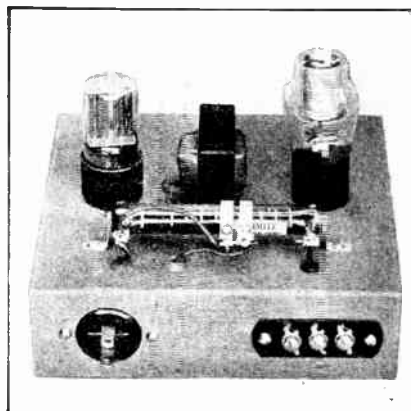


Fig. 1351 — A transformerless combination bias supply suitable for supplying bias for r.f. stages requiring 125 volts or less for cut off. A second branch, controlled by a VR75-30 regulator tube, provides 75 volts fixed bias for a second stage whose grid current does not exceed 20 ma. The unit above is constructed on a 7 × 7-inch chassis, although the components may easily be fitted into any spare space on another power-supply chassis. The regulated VR-tube branch may be omitted if not required. The circuit diagram is shown in Fig. 1352.

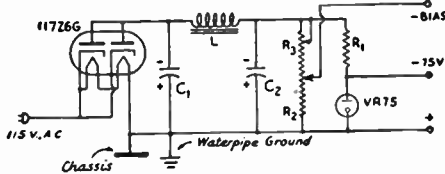


Fig. 1352 — Circuit diagram of the transformerless bias supply with voltage-regulated output shown in Fig. 1351. C_1, C_2 — 16- μ fd. 450-volt electrolytic. L — 60-ma. replacement filter choke. R_1 — 7500 ohms, 10-watt. $R_2 + R_3$ — 15,000-ohm 50-watt wire-wound resistor, with two sliders. See text for details of adjustment and operation.

almost completely cut off, or at least reduced to a safe value, the biasing tap should be moved upward (in the negative direction). With the amplifier in operation and drawing rated grid current, the biasing voltage should be measured, using a high-resistance voltmeter. If the grid voltage is higher than that recommended in the tube operating tables, both the biasing tap and the short-circuiting tap on the upper section should be moved, bit by bit, toward the positive end until the correct operating bias is obtained. The bias voltage should then be measured again. A final adjustment may be necessary to again arrive at cut-off voltage without excitation.

Fig. 1351 shows the components assembled separately on a small chassis. They may, however, be combined with plate-supply components on a single chassis, since little additional space will be required.

It will be noticed in the circuit diagram that only one wire is shown connected to the power plug. The return connection for circuit is made through an actual ground connection to the chassis, to prevent possible short-circuit of the 115-volt line should the power plug happen to be incorrectly polarized when inserted.

❏ A Wide-Range Antenna Coupler

The photograph of Fig. 1353 shows the constructional details of a wide-range antenna coupler suitable for use with high-power transmitters. Various combinations of parallel and series tuning, with high- and low- C tanks and high- and low-impedance outputs, are available. Diagrams of these various circuit com-

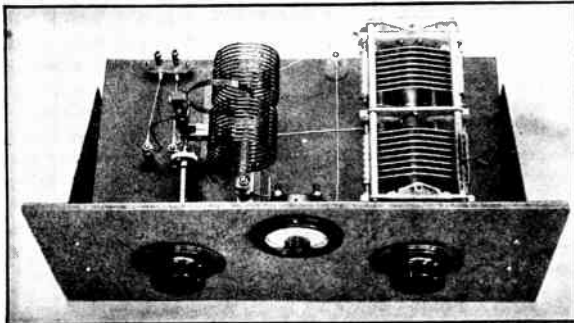


Fig. 1353 — Wide-range antenna coupler. The unit is assembled on a metal chassis measuring $10 \times 17 \times 2$ inches, with a panel $8\frac{3}{4} \times 19$ inches in size. The variable condenser is a split-stator unit having a capacity of 200 μ fd. per section and 0.07-inch plate spacing (Johnson 200E130). The plug-in coils are the B & W TVL series. The r.f. ammeter has a 4-ampere scale. If desired, the coils may be wound with fixed links on standard transmitting ceramic forms. The links will have to be provided with flexible leads which can be plugged into a pair of jack-top insulators mounted near the coil jack strip, unless a special mounting is made providing for the seven plug-in connections required.

binations possible with this arrangement are given in Fig. 1354.

A separate coil is used for each band, and the desired connections for series or parallel tuning with high or low C , or for low-impedance output with high or low C , are automatically made when the coil is plugged in. Coil connections to the pins for various circuit arrangements are shown in Fig. 1354.

The tuning condenser specified, together with a set of standard plug-in transmitting coils, should cover practically all coupling conditions likely to be encountered.

Because the switching connections require the use of a central pin, a slight alteration in the B & W coil-mounting unit is required. The central link mounting unit should be removed from the jack bar and an extra jack placed in the central hole thus made available. The link assembly should then be mounted on a 2-inch cone insulator to one side of the jack bar.

Correspondingly, the central nut on each coil plug base must be removed and a Johnson tapped plug, similar to those furnished with the coils, substituted. An extension shaft may then be fitted on the link shaft and a control brought out to a knob on the panel.

The split-stator tank condenser is mounted by means of angle brackets on four 1-inch cone-type ceramic insulators, and an insulated flexible coupling is provided for the shaft.


If desired, the coils may be wound with fixed links on ceramic transmitting coil forms. The links should be provided with flexible leads which can be plugged into a pair of jack-top insulators mounted near the coil jack strip, unless a special mounting is made providing for seven connections.

The unit as described should be satisfactory for transmitters operating at a plate voltage of up to 1500 with modulation and somewhat more on c.w. For appreciably higher voltages, a tank condenser with larger plate spacing should be used.

❏ Complete 450-Watt Band-Switching Transmitter

The various units shown in Figs. 1309, 1314-B, 1316, and 1345 through 1354, assembled together, form a complete high-power push-pull band-switching transmitter for any three adjacent bands selected.

Fig. 1354 — Circuit diagram of the wide-range antenna coupler for use with the band-switching amplifier. A — Parallel tuning, low C. B — Parallel tuning, high C. C — Series tuning, low C. D — Series tuning, high C. E — Parallel tank, low-impedance output, low C. F — Parallel tank, low-impedance output, high C. For single-wire matched-impedance feeders, the arrangements of E or F would be used with a single tap instead of the double tap shown. For simple voltage-fed antennas, the arrangement of A would be used with the end of the antenna connected at "X." After the inductance required for each of the various bands has been determined experimentally, the connections to the coils can be made permanent. Then it will be necessary merely to plug in the right coil for each band, tune the condenser for resonance, and adjust the link for loading.

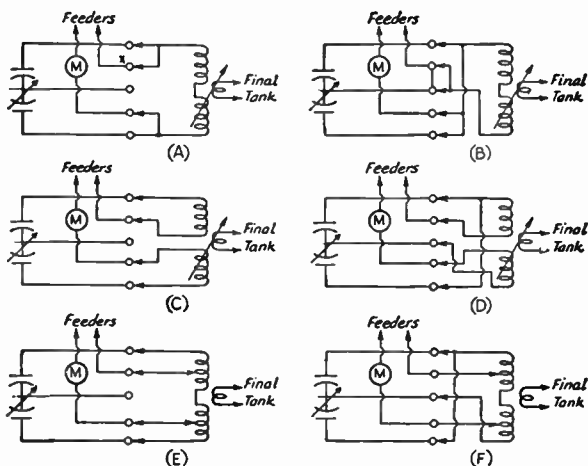

Heater, low-voltage plate and the 807 screen-voltage supply for the exciter may be obtained from the simplified 250-volt pack of Fig. 1314-B, while plate voltage for the 807 is furnished by the unit of Fig. 1316. Bias voltages for both amplifier and exciter are obtainable from the unit of Fig. 1351, while amplifier plate voltage is furnished by the unit of Fig. 1349. The units of Figs. 1314-B and 1351 may be combined in a single unit with a 7-inch panel. The addition of a 5¼-inch panel for the amplifier grid and plate meters and the antenna tuner of Fig. 1353 completes the transmitter.

The most logical arrangement for the units, from top to bottom, is as follows: (1) antenna tuner, (2) final amplifier, (3) meter panel, (4) exciter, (5) low-voltage and bias supplies, (6) 750-volt power supply, (7) high-voltage power supply. The combined height of all of these units will be 59½ inches.

Information on a suitable control circuit for such a transmitter will be found on pages 303-304.

A Single-Tube Medium-Power Pentode Amplifier

A 200- to 300-watt single-tube amplifier is shown in the photographs of Figs. 1356, 1357 and 1358. The tube is a Heintz and Kaufman type 257B, a beam pentode which may be operated at power inputs up to 300 watts for c.w. operation or up to 240 watts with plate and screen modulation.

The circuit is shown in the diagram of Fig. 1355. Link coupling is provided for both input and output. The amplifier requires a driving power of only a few watts.

The grid and plate tuning condensers are placed with their dials symmetrical on the panel. Grid tank-circuit components occupy the left-hand half of the chassis. The tuning

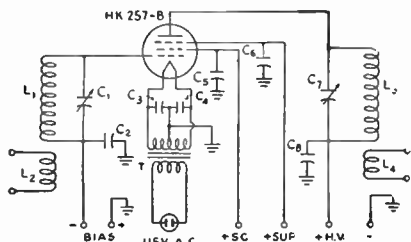


Fig. 1355 — Circuit of the single-tube pentode amplifier

- C₁ — 150- μ fd. variable (National TMS-150).
- C₂, C₃, C₄, C₅, C₆ — 0.01- μ fd. paper.
- C₇ — 65- μ fd. variable, 0.2-inch spacing (Cardwell X.C.-65-NS).
- C₈ — 0.001- μ fd. 5000-volt mica.
- T — Filament transformer, 5 volts, 7.5 amperes.
- L₁ — 3.5 Mc. — 36 turns No. 22 enameled, close-wound.
- 7 Mc. — 21 turns No. 20 enameled, 1¼ inches long.
- 14 Mc. — 17 turns No. 18 enameled, 1¼ inches long.
- 28 Mc. — 11 turns No. 18 enameled, 1¼ inches long, self-supporting.

Above coils wound on Millen 1-inch-diameter forms, mounted in National PB10 shields.

- L₂ — Input link winding, wound over ground end of L₁; 5 turns for 3.5 Mc., 3 turns for 7 and 14 Mc., 2 turns for 28 Mc.
- L₃ — Barker and Williamson BX1 series. If substitute coils are used, they should have the following approximate values of inductance: 3.5 Mc., — 35 μ h.; 7 Mc. — 13 μ h.; 14 Mc. — 5 μ h.; 28 Mc. — 1.25 μ h.
- L₄ — Output link winding — Same number of turns as for L₂, wound at ground end of L₃.

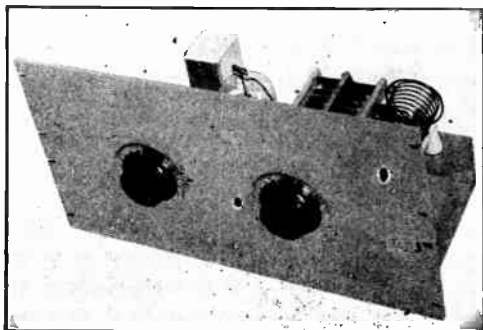


Fig. 1356 — The panel of the single-tube pentode amplifier is 10½ inches high and of standard rack width, while the chassis measures 8 × 17 × 3 inches.

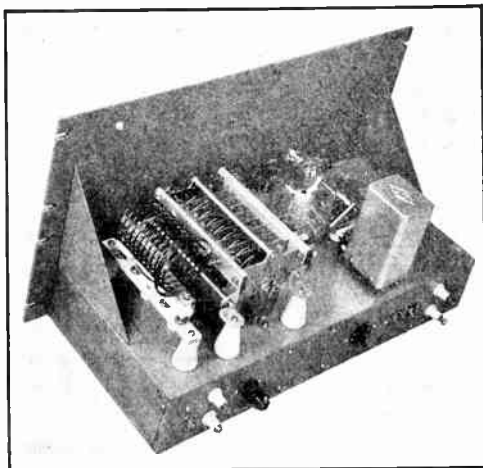


Fig. 1357 — Rear view of the single-tube pentode amplifier, showing the plate tank-circuit components to the left and those for the grid tank circuit to the right. The chassis is supported from the panel by means of triangular-panel brackets. Power-supply terminals are at the rear.

condenser, C_2 , is insulated from the chassis by mounting it on ceramic button-type feed-through insulators. The lower insulator shown in Fig. 1358 is used for making the connection between the stator of C_1 and the coil-socket terminal underneath. The coils are mounted in National PB10 shielded plug-in units with the socket submounted directly behind the tuning condenser. The tube socket also is submounted and a contact strip fastened to the chassis is required to ground the base shell of the tube to which all internal shielding is connected.

The plate tank-circuit components are to the right. Both condenser and coil-mounting strips are supported on $1\frac{1}{2}$ -inch ceramic cone stand-off insulators. The by-pass condenser, C_3 , is fastened between the rear stator plate of the tank condenser and the chassis. A high-volt-

age insulating shaft coupling is necessary. The suppressor and screen of this tube each is provided with two leads to separate pins. The two pins in each case should be connected together and by-passed close to the socket.

Power-supply and r.f. input and output connections are made at the rear. A filament transformer is included in the unit.

A fixed screen voltage, which may be taken from the exciter plate supply in most instances, is advisable. Suppressor voltage may be taken from a tap on a voltage divider connected across this supply. Sufficient fixed bias to cut off plate current without excitation should be provided. The additional bias necessary for proper operation may be obtained by a grid-leak resistance of suitable size. Maximum plate-voltage ratings are 2000 for c.w. or 1800 for 'phone. The amplifier may be loaded until the plate current rises to 150 ma. or 135 ma., respectively for each type of service.

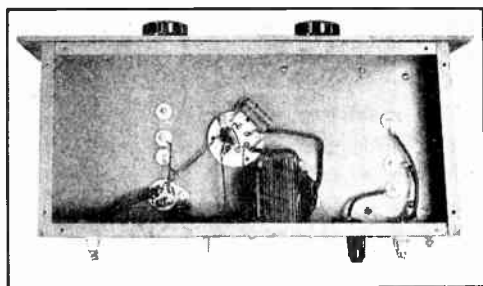


Fig. 1358 — Bottom view of the pentode amplifier.

Ⓐ A Single-Tube 500-Watt Amplifier

A single-tube amplifier which may be operated at inputs up to 500 watts at voltages as high as 3000 is shown in Figs. 1360, 1361 and 1362. The circuit, shown in Fig. 1359, is strictly conventional, with link coupling for both input

Fig. 1359 — Circuit of the 500-watt input amplifier.

C_1 — 250- μ fd. variable, 0.017-inch spacing (National TMK-250).

C_2 — 100 μ fd. per section, 0.171-inch spacing (National TMA-100-DA).

C_3 — Neutralizing condenser (National NC-800).

C_4 — High-voltage insulating condenser, 0.001- μ fd. mica, 12,500-volt rating (Cornell-Dubilier 21A-86).

C_5 , C_6 , C_7 — 0.01- μ fd. mica.

RFC — 1-mh. r.f. choke, 300 ma. (National R-300U mounted on GS-1 insulator).

MA₁ — Grid milliammeter, 100 ma.

MA₂ — Plate milliammeter, 300 ma.

T — Filament transformer — 5 volts, 8 amperes. (Thordarson T-19F84).


L₁ — 3.5 Mc. — 26 turns No. 16, $1\frac{1}{2}$ -inch diameter, $2\frac{1}{8}$ inches long, 3-turn link (B & W JCL-10).

7 Mc. — 16 turns No. 16, $1\frac{1}{2}$ -inch diameter, $1\frac{1}{8}$ inches long, 3-turn link (B & W JCL-20).

14 Mc. — 8 turns No. 16, $1\frac{1}{2}$ -inch diameter, $1\frac{1}{8}$ inches long, 3-turn link (B & W JCL-10).

28 Mc. — 6 turns No. 16, $1\frac{1}{2}$ -inch diameter, $1\frac{1}{8}$ inches long, 2-turn link (B & W JCL-10, 1 turn removed from each end).

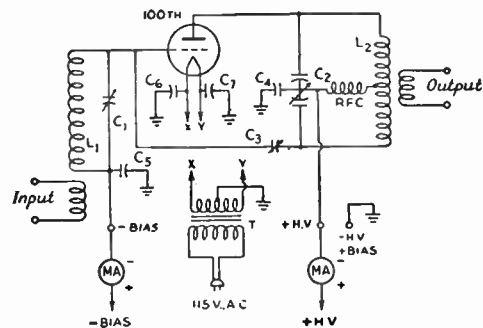L₂ — 3.5 Mc. — 26 turns No. 12, $3\frac{1}{2}$ -inch diameter,



$4\frac{1}{2}$ -inches long, 2-turn link (B & W TGL-80).

7 Mc. — 22 turns No. 12, $2\frac{1}{8}$ -inch diameter,

$4\frac{1}{2}$ -inches long, 2-turn link (B & W TGL-10).

14 Mc. — 12 turns No. 12, $2\frac{1}{8}$ -inch diameter,

$4\frac{1}{2}$ -inches long, 2-turn link (B & W TGL-20).

28 Mc. — 6 turns $\frac{1}{8}$ -inch copper tubing, $2\frac{1}{2}$ -inch diameter, $4\frac{1}{2}$ inches long, 2-turn link (B & W TGL-10).

and output circuits. While a Type 100TH tube is shown in the photographs, almost any other tube of similar physical size and shape which is designed to operate at plate voltages of 3000 or less may be used in a similar circuit arrangement.

Power supply and tuning — The plate power supply shown in Fig. 1370 may be used with this unit. Bias may be obtained from the unit shown in Fig. 1351. For this purpose, the VR75-30 branch may be omitted and a single resistor of 5000 ohms connected across the output of the pack, with the bias lead connected to the extreme negative end of the resistor.

The transmitter shown in Fig. 1322 should provide sufficient excitation. Fig. 1359 shows milliammeters connected in grid and plate leads. These meters are not included in the unit. They should be mounted on a separate well-insulated panel protected with a glass cover (see Fig. 1394).

An amplifier operating at high voltage should always, after neutralizing, be tuned up at reduced plate voltage. This may be obtained by connecting a lamp bulb in series with the primary of the plate transformer. Coupling between the exciter and the amplifier should be adjusted so that the grid current does not exceed 40 to 50 ma. with the amplifier tuned and loaded to the rated plate current of 167 ma. Power output of 225 to 300 watts should be obtainable on all bands at plate voltages from 2000 to 3000.

The tube tables in Chapter Twenty should be consulted for data on the operation of other tubes suitable for use in this amplifier.

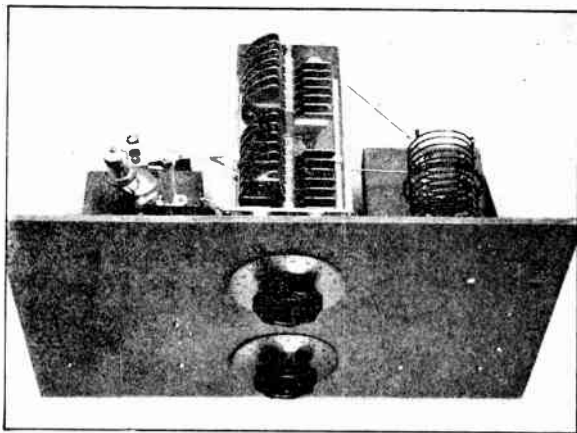


Fig. 1360 — A single-tube high-power amplifier for high-voltage inputs up to 500 watts. The standard rack panel is $12\frac{1}{4}$ inches high.

□ A High-Power Push-Pull Tetrode Amplifier

A push-pull amplifier using Eimac type 4-125A tetrodes is shown in Figs. 1363, and 1365. It will handle a power input of 700 to 800 watts at a plate voltage of 2000. Driver-power requirements are very small, 2 watts or so being sufficient for efficient operation. The circuit diagram is shown in Fig. 1364. Adjustment is simplified because no neutralizing is required at the frequencies for which the unit is designed.

Construction is simple and straightforward. The grid tank circuit is at the left, with the coil in the shielded plug-in unit. The variable condenser, C_1 , is fastened directly to the chassis. Small baffle shields of sheet metal are placed between each tube and the nearest end


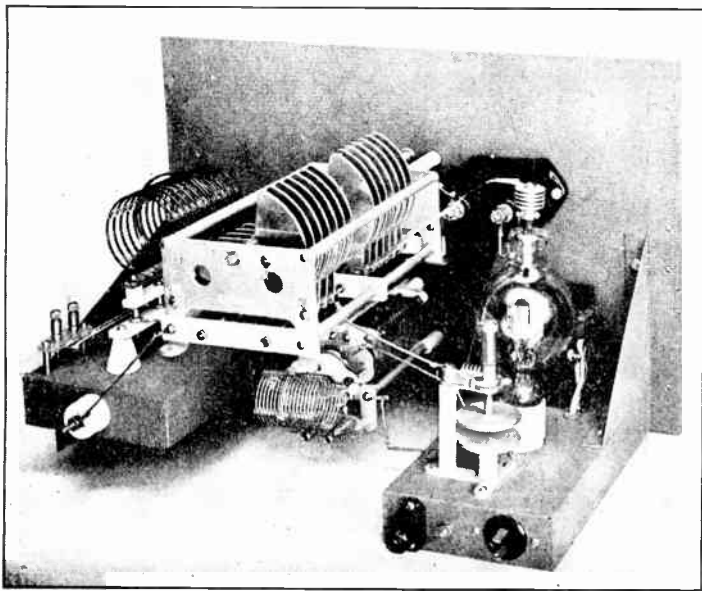


Fig. 1361 — Rear view of the high-power single-tube amplifier. The two tank condensers are mounted, one above the other, in the center of the panel by means of Isolantite pillars from stand-off insulators. Four National type GS-2 insulators are used to support the plate tuning condenser, while three type GS-1 insulators are used for the grid tuning condenser. Insulated flexible couplings and panel bearings are used on each shaft to insulate the controls. One of high break-down voltage rating should be used for the plate condenser, and the panel bearings must be grounded! The socket for the grid tank coil is mounted, using insulated spacers and a small metal plate as a base, on the rear end plate of C_1 . Metal strips, also fastened to the end plate, support the input-link terminal strip. The insulating by-pass condenser, C_4 , is mounted just to the right of C_2 .

Fig. 1362 — Bottom view of the single-tube 500-watt amplifier. In the lower right-hand corner of the panel is fastened a chassis $9\frac{1}{2} \times 5 \times 1\frac{1}{2}$ inches, on which are mounted, in line, the filament transformer, the tube socket and the neutralizing condenser. A chassis of similar size to the left supports the plate tank coil and the output-link terminals. A large feed-through insulator in the rear edge of this chassis serves as the high-voltage terminal. In wiring the amplifier unit, the importance of well-spaced leads carrying high voltage cannot be stressed too greatly. It must be remembered that the arcing distances and break-down capabilities of voltages as high as 3000 are considerably greater than with the lower plate voltages more commonly used by amateurs.

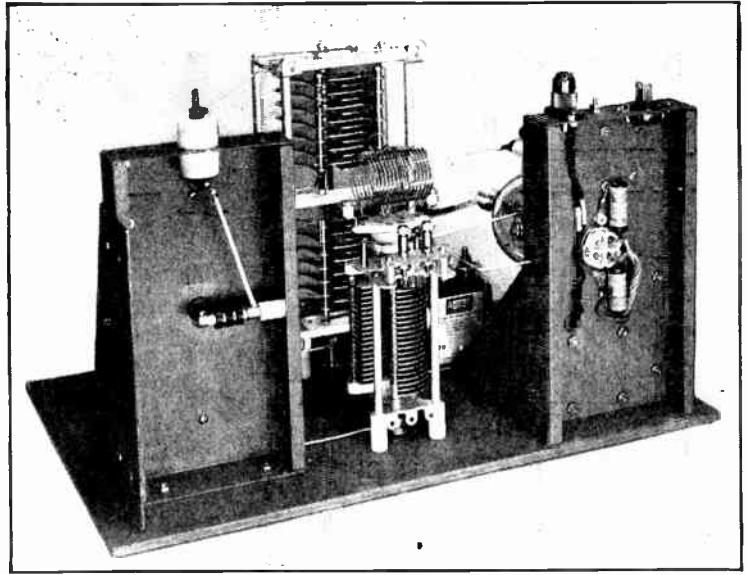

of the grid tuning condenser to eliminate capacitive feed-back from plate to grid. Leads between the tank condenser and coil pass through half-inch clearance holes in the chassis. The plate tank-circuit components occupy the remainder of the chassis. The condenser is mounted on $1\frac{1}{4}$ -inch ceramic stand-off insulators, while those supporting the coil jack strip are 1 inch high. In the rear-view photograph the high-voltage insulating condenser, C_7 , may be seen fastened between the variable-condenser frame and the chassis. The control shaft of the plate tank condenser *must* be fitted with a good high-voltage insulating coupling.

The grid tank condenser and the plate tank-coil mounting are placed so that their controls are symmetrical on the panel. Power-supply connections are made at the rear. The filament transformer, plate-circuit r.f. choke and fila-

ment by-pass condensers are underneath.

It is preferable to obtain the required screen voltage from a separate supply rather than

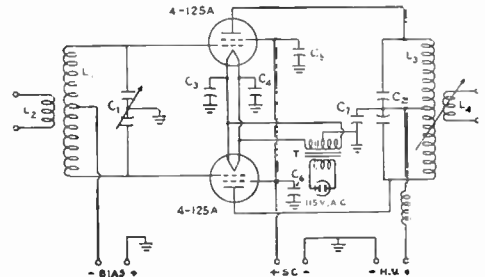


Fig. 1364 — Circuit diagram of the high-power push-pull tetrode amplifier pictured in Figs. 1363 and 1365. C_1 — 150- μ fd. per section variable (Hammarlund HFAD-150-B).

C_2 — 100- μ fd. per section variable, 0.17-inch spacing (National TMA100DA).

C_3, C_4 — 0.01- μ fd. paper.

C_5, C_6 — 0.001- μ fd. 600-volt mica.

C_7 — 0.001- μ fd. 10,000-volt mica.

T — Filament transformer, 5.25 volts, 15 amperes.

L_1 — Grid coils, all wound on Millen 1-inch-diameter forms mounted in National PB10 shields with 6-pin bases; all coils tapped at center.

3.5 Mc. — 46 turns No. 22 enameled, close-wound.

7 Mc. — 30 turns No. 22 enameled, $1\frac{1}{4}$ inches long.

14 Mc. — 16 turns No. 22 enameled, $1\frac{1}{4}$ inches long.

28 Mc. — 10 turns No. 18 enameled, 1 inch long.

L_2 — Input link winding — 5 turns for 3.5 Mc., 3 turns for 7 Mc. and 14 Mc., 2 turns for 28 Mc.

L_3 — B & W HDJ L series coils with variable-link coupling. Appropriate inductance values are as follows:

3.5 Mc., — 40 μ h.; 7 Mc. 15 μ h.; 14 Mc. — 5 μ h.; 28 Mc. — 1.2 μ h.

L_3 — Output link winding.

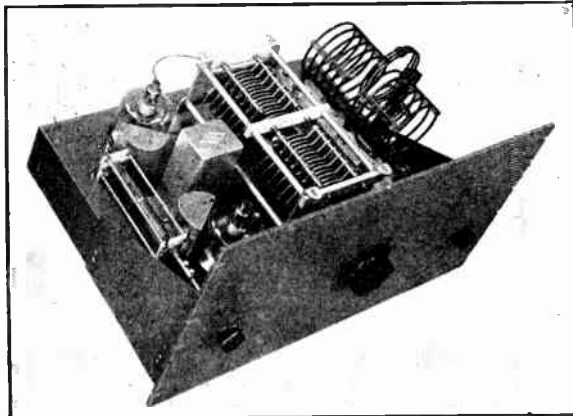


Fig. 1363 — The panel of the high-power push-pull tetrode amplifier is $10\frac{1}{2}$ inches high and of standard 19-inch rack width. The 3-inch chassis is 13 inches deep and 17 inches wide. The sockets for the shielded grid coil and the tubes are mounted under the chassis.

through the use of a voltage divider or series resistances from the plate supply. In many cases, it will be possible to supply the screens from the driver supply. A combination of grid-leak and fixed bias is recommended for the grid, with sufficient fixed bias to cut plate current off or to a very-low value when excitation is removed, the additional bias required under operating conditions being obtained from a grid-leak resistance of proper value, depending upon the screen and plate voltages used.

□ A Push-Pull 1-Kilowatt Amplifier

The push-pull amplifier using type 810s shown in the photographs of Figs. 1367, 1368 and 1369 is capable of handling a power input of 1000 watts for c.w. operation or 900 watts with plate modulation.

The circuit is shown in Fig. 1366. Plug-in coils with fixed links are used in the grid circuit, while the output-coil mounting is provided with variable link coupling. L_3C_3 and L_4C_4 form traps against v.h.f. parasitic oscillation. Special multisection plate tank condenser, C_2 , provides a low minimum capacity for operation at the higher frequencies and the high maximum capacity needed for operation at the lower frequencies.

Construction — The plate-tank tuning condenser is mounted on $1\frac{1}{4}$ -inch ceramic cone insulators. The rotor is grounded through a high-voltage fixed condenser at the front end of the variable-condenser frame. The shaft is cut off and is fitted with a large Isolantite flexible shaft coupling. This is important, since the rotor is at high voltage. A panel-bearing assembly is fitted in the panel. The jack bar for the plate tank coil is mounted on a pair of angle brackets fastened to the condenser end plates. Two 300-ma. r.f. chokes in parallel are

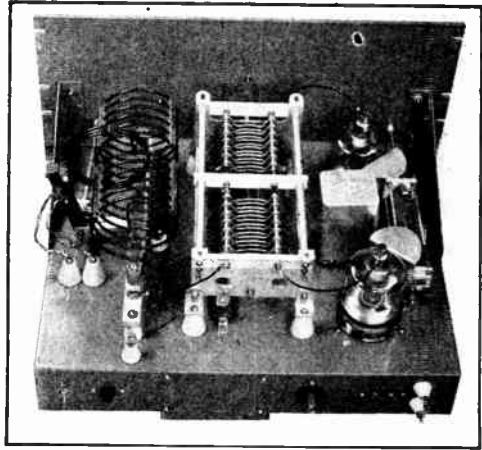



Fig. 1365 — Rear view of the high-power push-pull tetrode amplifier. The plate tank condenser is mounted in an inverted position on stand-off insulators by means of small angle pieces. The terminals at the rear, from left to right are ground, plate voltage, 115 volts a.c., screen voltage, bias and low-impedance link output.

used, one being connected between each condenser end plate and the center connections of the coil jack bar. The positive high voltage comes up through the chassis through a feed-through insulator at the rear of the condenser.

The grid tank condenser is mounted on $\frac{5}{8}$ -inch cone insulators topped with spacers which bring its shaft up level with that of the plate tank condenser. The two variable condensers are mounted with their shafts $3\frac{1}{8}$ inches from the chassis edges. The jack bar for the grid tank coil is mounted on U-shaped brackets made from $\frac{1}{2}$ -inch brass strip, and these, in turn, are mounted on 2-inch cone insulators. The rotor of the grid tank condenser is grounded to

Fig. 1366 — Circuit diagram for the high-power 1-kilowatt input push-pull amplifier.

- C_1 — 150 μ fd. per section, 0.05-inch spacing (Johnson 150F120).
- C_2 — Multi-section, maximum capacity 228 μ fd. per section, 0.84-inch spacing (Cardwell XE-160-70-XQ).
- C_3, C_4 — 3-30- μ fd. mica trimmer condensers with Isolantite insulation (Millen 28030).
- C_5, C_6 — Neutralizing condensers (Johnson N250).
- C_7 — 0.01- μ fd. 600-volt paper.
- C_8 — 0.001- μ fd. mica, 10,000-volt rating (Aerovox 1624).
- C_9, C_{10} — 0.01- μ fd. paper.
- RFC₁ — 2.5-mh. r.f. choke.
- RFC₂ — 1-mh. 300-ma. r.f. choke (National R-300).
- T₁ — 10-volt 10-ampere filament transformer (Thordarson T-19F87).
- L_1 — 3.5 Mc. — 32 turns No. 16, 2 $\frac{3}{4}$ inches long, 2 $\frac{1}{2}$ -inch diameter (40 μ h.) (B & W 80BL).
- 7 Mc. — 20 turns No. 14, 2 $\frac{1}{2}$ inches long, 2-inch diameter (12 μ h.) (B & W 40BL).
- 14 Mc. — 10 turns No. 14, 2 $\frac{1}{2}$ inches long, 2-inch diameter (3 μ h.) (B & W 20BL).
- 28 Mc. — 6 turns No. 12, 2 $\frac{1}{2}$ inches long, 2-inch diameter (1 μ h.) (B & W 10BL).
- L_2 — 3.5 Mc. — 32 turns No. 10, 6 $\frac{3}{4}$ inches long, 3 $\frac{1}{2}$ -inch diameter (40 μ h.) (B & W 80H1DV1).

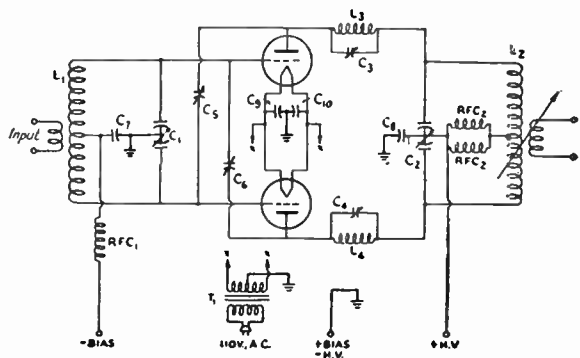

- 7 Mc. — 20 turns No. 8, 6 $\frac{3}{4}$ inches long, 3 $\frac{1}{2}$ -inch diameter (15 μ h.) (B & W 40H1DV1).
- 14 Mc. — 8 turns No. 8, 4 $\frac{3}{4}$ inches long, 3 $\frac{1}{2}$ -inch diameter (3 μ h.) (B & W 20H1DV1 with one turn removed from each end).
- 28 Mc. — 4 turns 3/16-inch copper tubing or No. 4 wire, 5 $\frac{1}{4}$ inches long, 2 $\frac{3}{8}$ -inch inside diameter (0.8 μ h.) (B & W 10H1DV1 with one turn removed from each end).
- L_3, L_4 — 6 turns No. 12, $\frac{1}{2}$ -inch inside diameter, $\frac{3}{4}$ -inch long.

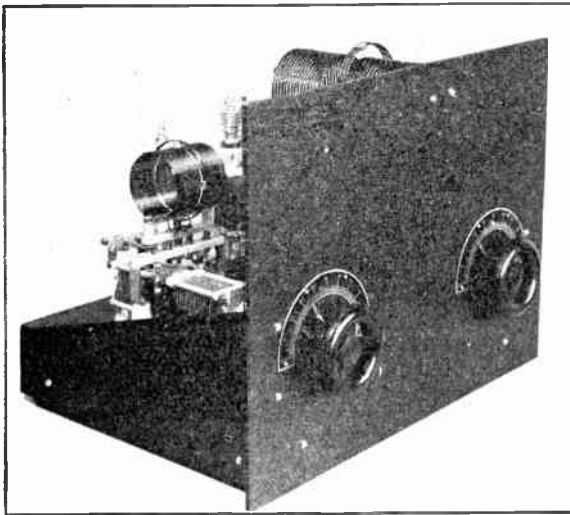


Fig. 1367 — The panel for the 1-kilowatt push-pull amplifier is 14 inches high and 19 inches wide. The chassis size is 13 × 17 inches.

for the positive high voltage and negative bias terminals. A male plug is set in the rear edge of the chassis for the 115-volt line connection to the filament transformer.

Power supply — A plate-supply unit suitable for this amplifier is shown in Fig. 1370. For bias, the unit shown in Fig. 1351 is suggested. The branch including the VR75-30 may be omitted and resistance values for R_2 and R_3 should be approximately 2000 and 2500 ohms, respectively. The transmitter shown in Fig. 1322 will furnish adequate excitation.

Tuning — The only departure from ordinary procedure in tuning is that of adjusting the parasitic traps.

the chassis at the center. The grid r.f. choke is mounted on a feed-through insulator carrying the biasing voltage up through the chassis. The grid by-pass condenser is soldered between the top of the r.f. choke and the rotor ground connection for the condenser.

The two tubes are mounted centrally with respect to the two tank condensers, the neutralizing condensers being placed between the tubes and the grid tank condenser. The sockets for the tubes are sub-mounted beneath the chassis on $\frac{5}{8}$ -inch spacers to lower the plate terminals. The parasitic-trap condensers and coils are self-supporting and are fastened to the heat-radiating plate connectors.

The filament transformer is mounted underneath the chassis, and the filament by-pass condensers are wired in directly at the socket terminals. Millen safety terminals are provided


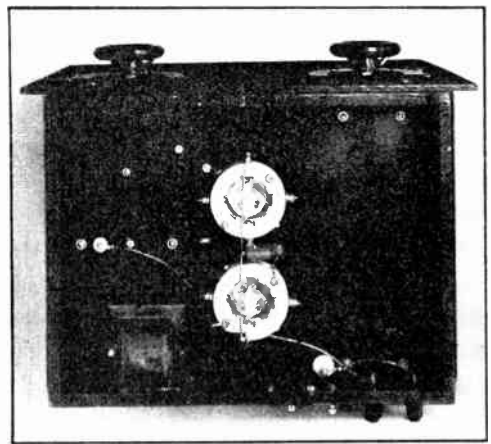


Fig. 1368 — The tube sockets in the 1-kilowatt amplifier are sub-mounted. The filament transformer is mounted close to the sockets.

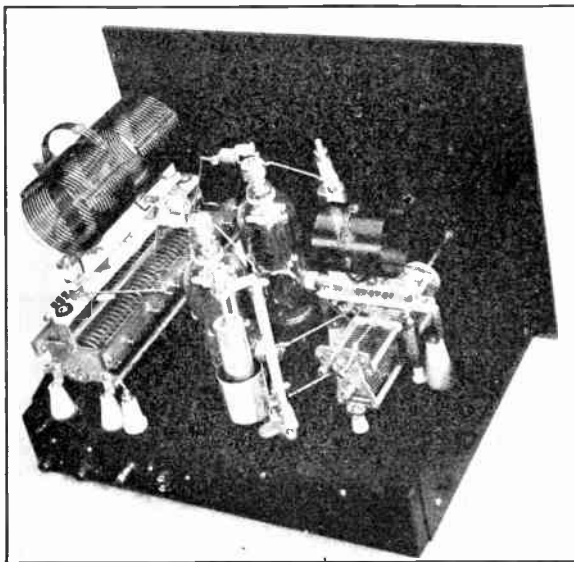


The trap condensers, C_3 and C_4 , should be set near maximum capacity, but not screwed up tight. After the amplifier has been neutralized, a bias voltage of about $22\frac{1}{2}$ volts should be applied to the grid and the plate voltage applied through a 2500-ohm series resistance. With a pair of coils for any band plugged in, the plate current should not vary with any setting of the grid or plate condensers. If the plate current changes suddenly at any point, the trap condensers should be adjusted equally until the change disappears. The trap condensers should be set as near to maximum capacity as is possible consistent with parasitic suppression. If the r.f. wiring has been

Fig. 1369 — Rear view of the 1-kw. amplifier, showing wiring and the placement of parts.

Fig. 1370 — This power supply unit delivers 2025 and 2480 volts at full-load current of 450 ma. with ripple of 0.5 per cent and regulation of 19 per cent. Voltages are selected by taps on the secondary. All exposed high-voltage terminals are covered with Sprague rubber safety caps and the tube plate terminals with moulded caps. The rectifier tubes are placed away from the plate transformer to avoid induction troubles. The panel is 14 × 19 inches and the chassis 13 × 17 × 2 inches. The exposed high-voltage terminal should be covered with a rubber-tubing sleeve. The circuit is the same as that shown in Fig. 1350, the components being as follows:

- C₁ — 1- μ fd, 2500-volt oil-filled (G.E. Pyranol).
- C₂ — 4- μ fd, 2500-volt oil-filled (G.E. Pyranol).
- L₁ — Input choke, 5–20 henrys, 500 ma., 75 ohms (Thordarson T-19C38).
- L₂ — Smoothing choke, 12 henrys, 500 ma., 75 ohms (Thordarson T-19C45).
- R — 50,000 ohms, 200-watt.
- Tr₁ — 3000–2450 volts r.m.s., each side of center, 500 ma. d.c. (Thordarson T-19P68).
- Tr₂ — 2.5 volts, 10 amperes, 10,000-volt insulation (Thordarson T-64F33).

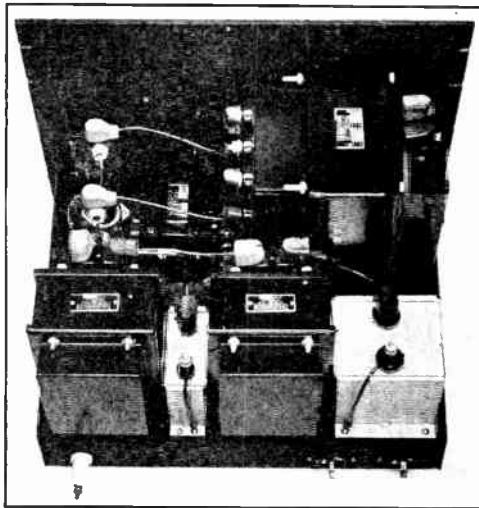Note: The voltage regulation may be improved by the use of a lower value of bleeder resistance, *R*, although at some sacrifice in maximum permissible load current.



carefully duplicated, the initial adjustment of the parasitic traps as described above should be sufficient.

After the above adjustment is complete, excitation may be applied and the amplifier loaded. The high-capacity sections of the plate tank condensers are required only for the 3.5-Mc. band. If parasitic oscillations are encountered, C₃ and C₄ should be adjusted, bit by bit, until they are suppressed.

With correct excitation grid current should run about 100 ma. on all bands, and the amplifier with the antenna connected may be loaded until the plate current increases to 500 ma. The power output with a plate voltage of 2000 should be approximately 750 watts.

Complete High-Power Transmitters

The 100-watt transmitter of Fig. 1322 may be used as a driver for either of the high-power amplifiers in Figs. 1360 and 1367. In addition to the power-supply units of Figs. 1351 and 1327 required for the exciter, a separate bias supply for the high-power amplifier will be necessary. A second bias-supply unit similar to that of Fig. 1351, minus the VR-tube branch, will be satisfactory. Plate voltage for either amplifier may be obtained from the large power-supply unit shown in Fig. 1370. The antenna tuner may be the one shown in Fig. 1353 with the substitution of a condenser of 0.1-inch plate spacing and coils of higher power rating. The same capacity and inductance values should be maintained.

For a combination using the single-tube amplifier of Fig. 1360, the combined heights of all units will be 66½ inches. If the push-pull amplifier of Fig. 1367 is used in the complete transmitter, the total height will be 68¼ inches.

A Four-Band V.F.O. Bandswitching Exciter

A variable-frequency exciter giving an average power output of approximately 2 watts over the 3.5-, 7-, 14- or 28-Mc. bands is shown in the photographs of Figs. 1371, 1373 and 1374. The circuit diagram is shown in Fig. 1372.

The oscillator is a 6J5 triode operating at 1.75 Mc. with low-power battery input to maintain maximum frequency stability. The tuned circuits are designed to give practically full-scale bandspread on each band. The oscillator is isolated from succeeding stages by the 1853 untuned Class-A amplifier. An 1853, whose tuning is gauged with that of the oscillator, doubles frequency to the 3.5-Mc. band with sufficient power output to drive the 2E25 3.5-Mc. pretuned output stage. Successive pretuned 6L6 doubler stages may be switched in following the 2E25 to provide out-

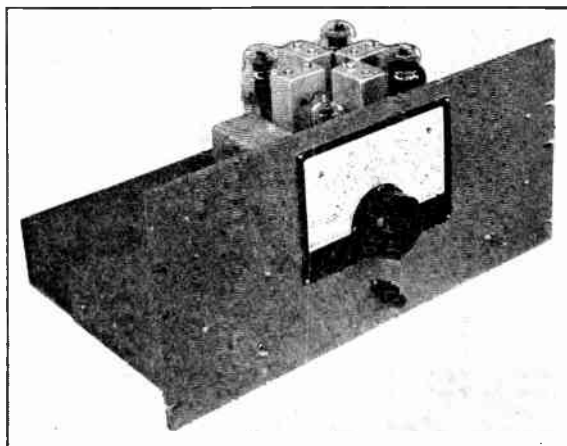


Fig. 1371 — Panel view of the v.f.o. exciter. The key jack is to the left, bandswitch at the center and the monitor-transmit switch to the right. The chassis measures 12 × 7 × 3 inches.

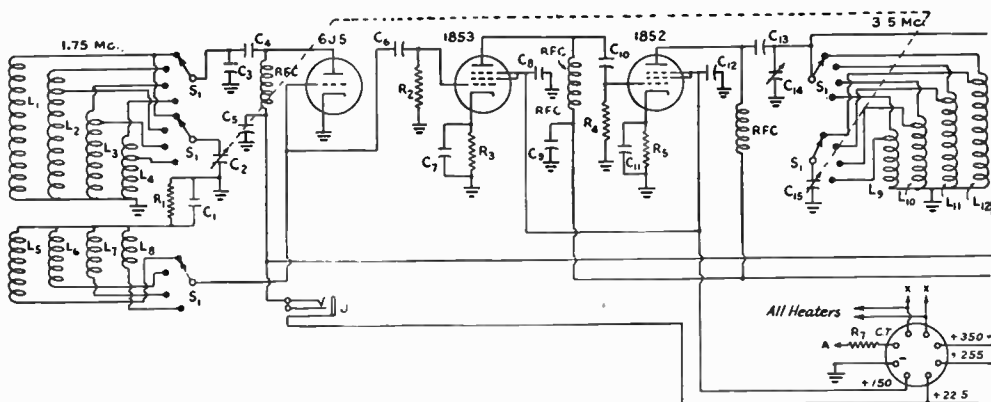


Fig. 1372 — Circuit diagram of the bandswitching v.f.o. exciter.

C_1 — 200- μ fd. zero-temp. mica.
 C_2 — 200- μ fd. variable (Bud MC-1858).
 C_3 — 500- μ fd. zero-temp. mica.
 C_4, C_{13} — 0.002- μ fd. mica.
 $C_5, C_7, C_8, C_9, C_{11}, C_{12}, C_{17}, C_{18}, C_{19}, C_{20}, C_{22}, C_{23}, C_{24}, C_{26}, C_{27}, C_{28}, C_{30}, C_{31}, C_{32}$ — 0.01- μ fd. paper.
 $C_6, C_{10}, C_{16}, C_{21}$ — 100- μ fd. mica.
 C_{14} — 50- μ fd. variable (Cardwell ZR-50-AS).
 C_{15} — 35- μ fd. variable (Hammarlund MC-35-S) ganged with C_2 .
 C_{25}, C_{29} — 50- μ fd. mica.
 R_1 — 50,000 ohms, $\frac{1}{2}$ -watt.

R_2, R_4 — 150,000 ohms, $\frac{1}{2}$ -watt.
 R_3, R_5 — 500 ohms, 1-watt.
 R_6 — 20,000 ohms, $\frac{1}{2}$ -watt.
 R_7, R_9, R_{11}, R_{12} — 400 ohms, 1-watt.
 R_8, R_{10}, R_{13} — 100,000 ohms, 1-watt.
RFC — 2.5-mh. r.f. choke.
J — Open-circuit jack.
 S_1 — Section of 4-gang 4-position tap switch, ceramic insulation.
 S_2 — 4-point short-circuiting switch ganged with S_1 on single control.
 S_3 — D.p.d.t. toggle switch.

put in the higher-frequency bands, switch sections being ganged so that the oscillator gives the correct bandspread range for the band in use. Doublers are cut out simply by opening the cathode and link circuits. With S_3 thrown to the right, the exciter is ready for transmitting with a key plugged in at J. When S_3 is thrown to the left, the key is short-circuited and voltage is removed from the doubler stages so that the oscillator frequency may be set without operating the output stage and putting a signal on the air.

The unit is built on a chassis measuring 12 × 17 × 3 inches. The panel is 8 $\frac{3}{4}$ inches high and of standard 19-inch rack width. Referring to the top-view photograph of Fig. 1373, the oscillator and 1852 doubler tuning condensers, C_2 and C_{15} , are mounted on $\frac{1}{2}$ -inch metal pillars so that the dial mechanism will clear the chassis. They are enclosed in a shield made from sheet aluminum and are mounted at the center of the chassis. To the right are grouped closely the 2E5 and the 6L6 doubler tubes with their respective pretuned tank circuits in individual shields.


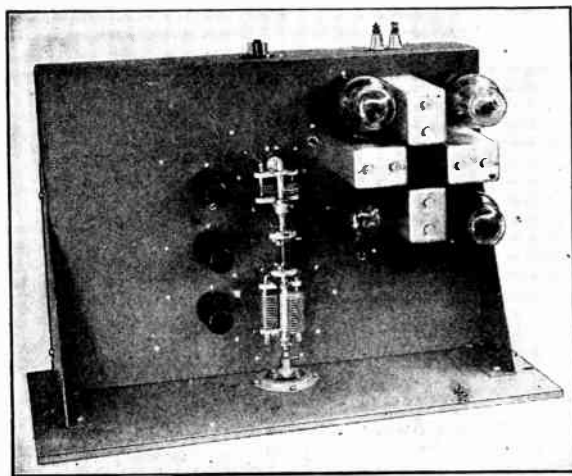


Fig. 1373 — Top view of the v.f.o. exciter behind the panel. The shield cover for the condenser gang has been removed. In line from front to rear at the left are the 6J5, 1853 and 1852. In the upper right-hand corner from lower left clockwise are the 2E5, the 7-Mc. 6L6 doubler, the 14-Mc. 6L6 doubler and the 28-Mc. 6L6 doubler.

The tuning dial is a National type ACN which may be hand calibrated. The switch, S_3 , is to the right and the keying jack to the left. An eight-pin terminal is mounted in the rear edge of the chassis to provide a connection for the power cable. A separate pair of small feed-through insulators serves for the low-impedance output terminals.

Underneath, the band-changing switch is at the center. Metal brackets are provided at each corner of the switch frame so that the assembly may be fastened securely to the chassis to eliminate any distortion of the switch frame or bending of coil leads which might cause a frequency change. At the front part of the chassis are the four oscillator coils grouped around the switch. Connecting leads from the coils are extensions of the wire with which the coils are wound. A slight amount of slack should be left in these leads, rather than pulling them tight,

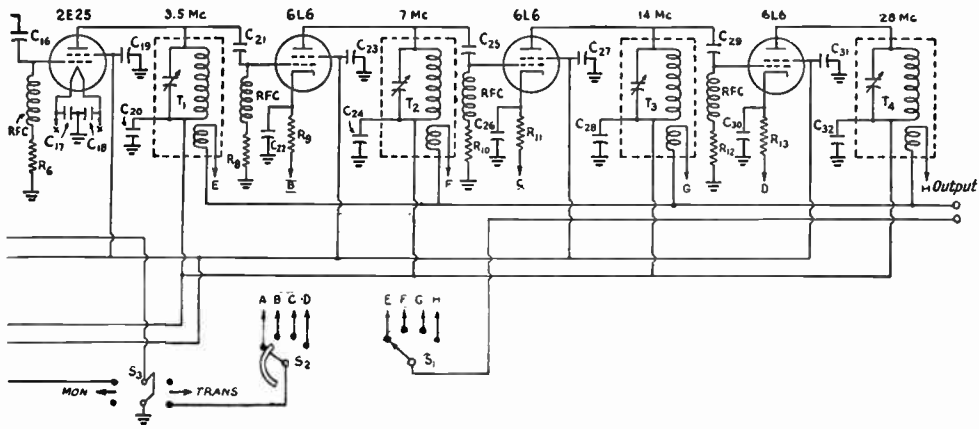

- L₁ — 3.5-Mc. bandsread — 26 turns, no tap.
 - L₂ — 7-Mc. bandsread — 28 turns, tapped 14 turns from ground end.
 - L₃ — 14-Mc. bandsread — 29 turns, tapped 14 turns from ground end.
 - L₄ — 28-Mc. bandsread — 28 turns, tapped 18 turns from ground end.
- All above coils are wound on Millen 1-inch-diameter forms with No. 24 enameled wire, turns spaced to an approximate length of 1 inch, then adjusted by spreading turns to give full dial-scale bandsread.
- L₅, L₆, L₇, L₈ — 19 turns No. 28 enameled, close-wound.

- L₉ — 28-Mc. bandsread — 39 turns, tapped at 20 turns from ground end.
 - L₁₀ — 14-Mc. bandsread — 42 turns, tapped 18 turns from ground end.
 - L₁₁ — 7-Mc. bandsread — 41 turns, tapped 19 turns from ground end.
 - L₁₂ — 3.5-Mc. bandsread — 35 turns, tapped 33 turns from ground end.
- All above coils wound on Millen 1-inch-diameter forms with No. 24 enameled wire, turns spaced to an approximate length of 1 inch, then adjusted by spreading turns to give proper tracking.

since this practice helps to eliminate frequency changes with vibration. The leads should be covered with small-diameter spaghetti. The coils to the rear are the 1852 plate coils. The 1852 padding condenser, C₁₄, is immediately behind the switch gang. Its position may be reversed so that its shaft may be adjusted by screwdriver through a clearance hole drilled in the rear edge of the chassis. The entire unit should be mounted on a sheet of sponge rubber to minimize effects of vibration, or the chassis may be provided with standard shock mountings of the type used with military equipment.

The oscillator operates at 1.75 Mc. regardless of the exciter output frequency. Four separate coils, L₁, L₂, L₃ and L₄, are provided so that each may be adjusted to give the desired amount of band-spread in covering each of the output-frequency bands. This system eliminates the necessity for separate trimming and padding condensers and also permits the LC ratio to remain essentially constant regardless of the amount of bandsread. The position of the tap and the inductance of each coil may have to be varied slightly by changing the spacing of a few turns near the top of the form to get full-dial bandsread.

If the coil dimensions given are followed closely, it should not be necessary to change the position of the taps on L₉ through L₁₂ to obtain tracking with the oscillator.

Tracking can be checked by inserting a milliammeter in the plate circuit of the 1852. With the desired coil oscillator and buffer switched in, the v.f.o. should be tuned to the high-frequency end of the band and the padding condenser, C₁₄, adjusted for minimum plate current. Then the tuning should be shifted to the low-frequency end of the band and C₁₄ swung through resonance to make sure that minimum plate current occurs at the same setting as it did at the high-frequency end of the band. If an increase in the capacity of C₁₄ is required to regain resonance, the tap on the coil should be moved slightly toward the plate


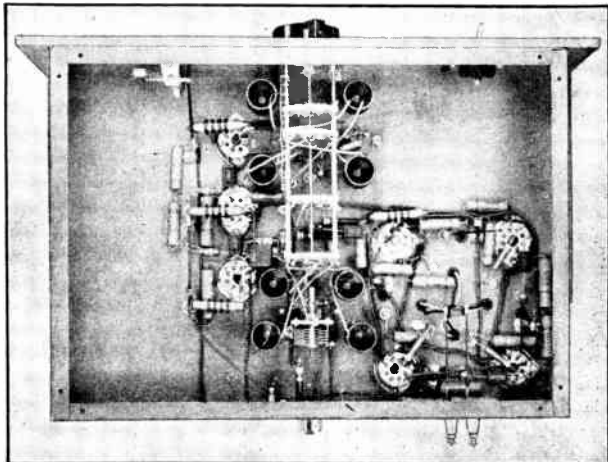


Fig. 1374 — Bottom view of the v.f.o. exciter. The ganged band switch is at the center. Toward the front are grouped the four oscillator coils with the four corresponding 1852 buffer coils and padder to the rear.

Fig. 1375 — Circuit of a suitable power supply for the bandswitching v.f.o. exciter.

C_1, C_2 — Section of dual 20- μ fd. electrolytic.
 L_1 — 25-h., 250-ma. swinging filter choke.
 L_2 — 15-h. smoothing filter choke, 250 ma.
 T_1 — Plate transformer, 350 volts d.c. (Kenyon T-655).
 T_2 — 5-volt rectifier filament transformer.
 T_3 — 6.3-volt filament transformer, 6 amperes.
 B — 22.5-volt "B" battery, large size.
 R — 2500 ohms, 50 watts, with slider for S_1, S_2 — S.p.s.t. toggle adjustment.

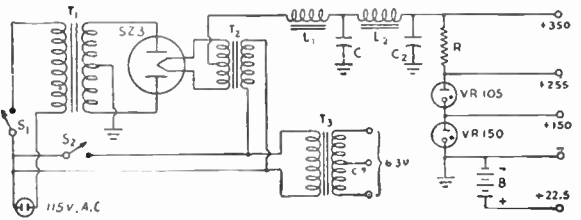

end of the winding; if a decrease in the capacity of C_{14} is necessary, the tap should be moved away from the plate end of the coil.

The pretuned tank circuits should be adjusted to give as flat output as possible over each band. To arrive at the best adjustment it may be necessary to "stagger" the tuning, adjusting one circuit for the high-frequency end of the band and the next toward the low-frequency end.

With such an arrangement, which eliminates tuning of the individual circuits for each band, constant output cannot be expected. The use of comparatively large tubes for the small average output is necessary to take care of abnormal plate dissipation when operating in portions of the bands to which the stages may not be tuned accurately. This unit should be followed by a "power-leveling" stage using a tube, such as the 807, which will give essentially constant output over a wide range of excitation levels. The plate current of the stages with pretuned tank circuits will vary from about 15 ma. to approximately 80 ma., depending upon the amount of off-resonance tuning required for best average output over the band.

A suitable power-supply circuit is shown in Fig. 1375. A supply delivering 350 volts d.c. at 250 ma. is required. A 22.5-volt "B" battery supplies the oscillator, while voltage-regulated taps provide 150 volts for the screens

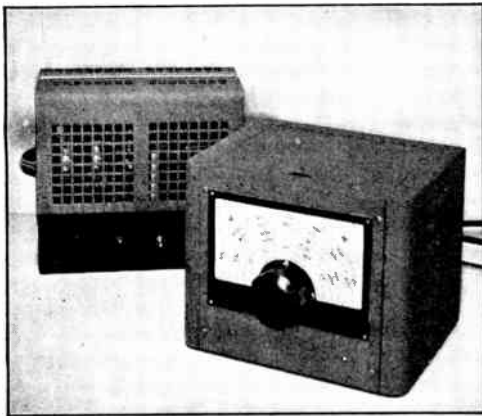


Fig. 1376 — The variable-frequency exciter is enclosed in an 8 × 8 × 10-inch Paracetal cabinet. The dial is the National type ACN, suitable for calibrating. The voltage-regulated power supply is mounted in an amplifier-foundation case with a 5 × 3 × 10-inch chassis.

of the 1852 and 1853 and 255 volts for the plates of these tubes and the screens of the 2E25 and 6L6s. The regulator tubes are used to prevent a wide fluctuation in voltage as doubler stages are cut in and out. The slider on R should be adjusted to the point where the voltage-regulating tubes will just stay ignited with full load applied.

¶ A Variable-Frequency Crystal Substitute

The photographs of Figs. 1376, 1379 and 1380 illustrate the construction of a variable-frequency unit which is designed to take the place of the crystal as a frequency control in most of the common forms of crystal-oscillator circuits. The power output of the unit is approximately one and one-half watts, which is sufficient for this purpose, or for driving an 807. By means of plug-in coils, output at any frequency in the 1.75-, 3.5-, or 7-Mc. bands may be obtained.


Referring to the circuit diagram of Fig. 1377, a 6F6 is used in the e.c.o. circuit. Since the buffer stage provides adequate isolation, the use of a well-screened tube in the oscillator circuit is not a requirement. The cathode is connected to a feed-back winding, L_2 , rather than to a direct tap on L_1 , to make adjustment of feed-back less difficult. A high- C tank circuit is obtained by the fixed padders, C_1 and C_2 , which are of the zero-drift type. Bandspread tuning is obtained by the split-stator condenser, C_3 .

When coils 1 and 1A (see coil charts) are plugged in, the two sections of the tuning condenser, C_3 , are connected in parallel and the output-frequency spread is 1760 to 2000 kc. to cover, through a doubler, the 3.5-Mc. band. Similarly, with coils 2 and 2A, the two sections of C_3 are in parallel and the output-frequency spread is 3500 to 4000 kc. to cover the 3.5-Mc. band.

When coils 1B and 1AB are plugged in, the sections of C_3 are in series and the output-frequency range is 1750 to 1825 kc. for obtaining, through doublers, the frequency ranges of 7000 to 7300 and 14,000 to 14,400 kc. Similarly, when coils 2B and 2AB are plugged in, the output-frequency range is 3500 to 3650 kc. for obtaining, through doublers, the same frequency ranges of 7000 to 7300 and 14,000

Fig. 1377 — Circuit diagram of the v.f.o. exciter unit.

- C₁, C₂ — 300 μ fd. each, zero-drift type (Centralab 316Z).
- C₃ — 140 μ fd. per section (Hammarlund MCD-110-S).
- C₄ — 100- μ fd. mica.
- C₅ — 250- μ fd. mica.
- C₆ — 45-260- μ fd. mica trimmer (Hammarlund CTS-160).
- C₇ — Approximately 65 μ fd. (Hammarlund MC-100-S with two stator and two rotor plates removed).
- C₈, C₉, C₁₀, C₁₁, C₁₂ — 0.01- μ fd. paper.
- J — Closed-circuit jack.
- R₁ — 0.1 megohm, $\frac{1}{2}$ -watt.
- R₂ — 0.1 megohm, $\frac{1}{2}$ -watt.
- R₃ — 500 ohms, 1-watt.
- L₁, L₂, L₃, L₄ — See Fig. 1378.

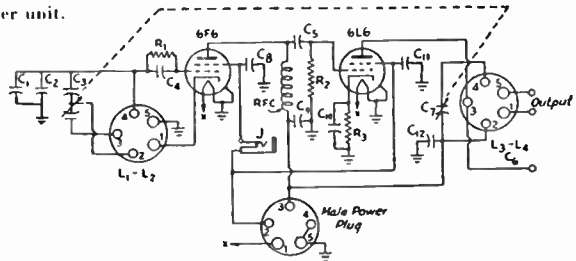

to 14,400 kc. The two sections of C₃ are also connected in series when coils 3 and 3A are plugged in, and the output-frequency range then becomes 7000 to 7300 kc. This is suitable for covering the 7-Mc. band and, through a doubler, the 14-Mc. band.

When coils 3B and 3AB are plugged in, only one section of C₃ is in use and the output-frequency range of 7000 to 7500 kc. is useful in obtaining, through doublers, the range of 28,000 to 30,000 kc.

Proper connections to C₃ are made automatically when each oscillator coil is plugged in, as shown in Fig. 1378.

Choke coupling is used between the oscillator and the 6L6 isolating stage. This stage is operated very close to Class-A conditions and is tuned to the second harmonic of the oscillator frequency. Thus, the oscillator operates at half the desired output frequency. The type 6L6 tube is used to take care of the unusually high dissipation resulting from this type of operation. The tuning of the output tank circuit is gauged with that of the oscillator. Tracking taps on the output coil, L₃, are required only for spreading the higher-frequency bands. Adjustable mica trimmers, C₆, are mounted in each coil form.

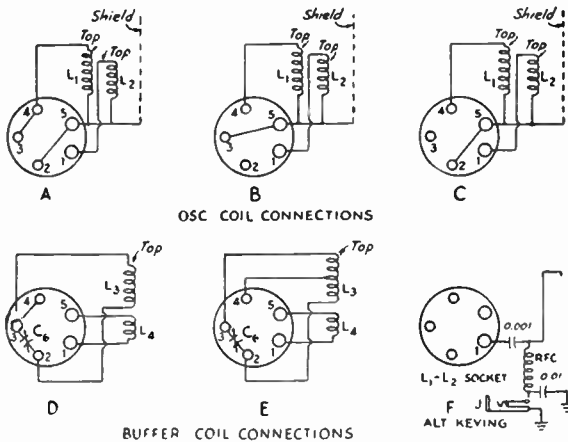


Fig. 1378 — Coil-form connections for the v.f.o. circuit of Fig. 1377. Connections shown at A are for coils 1 and 2. Those shown at B are for coils 3, 1B and 2B. Connections shown at C are for coil No. 3B. Buffer coils 1A and 2A should be connected as shown at D, while coils 3A, 1AB, 2AB and 3AB should be connected as shown at E. F shows the circuit for optional cathode keying instead of screen keying, as mentioned in text. RFC is an ordinary 2.5-mh. r.f. choke. Coil dimensions are as follows:

Oscillator (L₁ and L₂)*

- Coil No. 1 — (875 to 1000 kc.) — 47 turns No. 26 d.s.c., $\frac{7}{8}$ -inch long; 6 turns for L₂.
- Coil No. 2 — (1750 to 2000 kc.) — 23 turns No. 20 d.s.c., $1\frac{1}{4}$ inches long; 2 turns for L₂.
- Coil No. 3 — (3500 to 3650 kc.) — 14 turns No. 20 d.s.c., $1\frac{1}{4}$ inches long; 2 turns for L₂.
- Coil No. 1B — (875 to 912.5 kc.) — 57 turns No. 26 d.s.c., $1\frac{1}{8}$ inches long; 5 turns for L₂.
- Coil No. 2B — (1750 to 1825 kc.) — 28 turns No. 20 d.s.c., 1 inch long; 2 turns for L₂.
- Coil No. 3B — (3500 to 3750 kc.) — $13\frac{1}{2}$ turns No. 20 d.s.c., 1-inch long; 2 turns for L₂.

* Wound on Millen 1-inch diameter forms, L₂ wound turn-for-turn over bottom end of L₁ in same direction.
 ** Wound on Hammarlund $1\frac{1}{2}$ -inch diameter forms, L₄ close-wound below L₃.

Buffer Coils (L₃ and L₄)**

- Coil No. 1A — (1750 to 2000 kc.) — 41 turns No. 24, $1\frac{3}{4}$ inches long; approximately 12 turns for L₄.
- Coil No. 2A — (3500 to 4000 kc.) — 21 turns No. 18, $1\frac{1}{2}$ inches long; approximately 6 turns for L₄.
- Coil Co. 3A — (7000 to 7300 kc.) — 14 turns No. 18, $1\frac{1}{2}$ inches long, tapped at 3 turns from bottom; approximately 4 turns for L₄.
- Coil No. 1AB — (1750 to 1825 kc.) — 46 turns No. 24, $1\frac{3}{4}$ inches long, tapped at 19 turns from bottom; approximately 12 turns for L₄.
- Coil No. 2AB — (3500 to 3650 kc.) — 24 turns No. 18, $1\frac{1}{2}$ inches long, tapped at $9\frac{1}{2}$ turns from bottom; approximately 6 turns for L₄.
- Coil No. 3AB — (7000 to 7500 kc.) — 14 turns No. 18, $1\frac{1}{2}$ inches long, tapped at 5 turns from bottom; approximately 4 turns for L₄.



Fig. 1379 — Components for the v.f.o. exciter are assembled on a 7 × 7 × 2-inch chassis. The dual-section condenser is mounted by removing the shield between sections and fastening to the chassis with a single machine screw. The smaller condenser, C₇, is mounted on National polystyrene button insulators and metal spacers to insulate it from the chassis and bring its shaft in line with that of the dual condenser. It is reverse-mounted, with its tail shaft extension coupled to the tail shaft extension of the dual condenser to reduce the overall mounting space. The stop pin on the shaft must be removed. Leads from the tuning condensers to the sub-mounted coil sockets pass through the chassis via 1/2-inch holes lined with rubber grommets. The jack for the key, which must be insulated, and the male power connector mount in the side of the cabinet. The chassis is fastened firmly in place with long machine screws running through the chassis and the bottom of the cabinet. The terminals at the rear are for link-output connections, the binding post for capacity coupling.

To solve some of the difficulties often encountered in key-filtering an oscillator of this type, the oscillator stage is keyed in the screen circuit. This means that both sides of the key are at a potential of 150 volts above ground potential. It is, therefore, preferable to use a relay to isolate the key contacts from this voltage. Otherwise, due caution should be exercised. If preferred, cathode keying may be used as shown in Fig. 1378-F, but it is more difficult to obtain soft keying without introducing chirp with this system. With cathode keying, the

screen connection will go directly to pin No. 2 on the power plug, eliminating the jack in the screen circuit.

A link winding, L₄, is provided for coupling the output of the exciter unit to the input of the amplifier stage which it is to drive.

Coils — Coil dimensions for several oscillator ranges are given in the coil table below Fig. 1378. Only those which suit the conditions under which the unit is to be operated need be constructed. This will depend upon the type of transmitter with which the unit is to be used. To begin with, only coils need be provided giving output in bands for which crystals, formerly used, are ground. For instance, if the oscillator stage to be driven is designed for 1.75-Mc. crystals only, coils need be wound for this band only. If the transmitter operates only in the 3.5-Mc. band, only the 1.75-Mc. coils for the first bandspread range will be required. If, however, the transmitter is designed to cover the 7-Mc. band, as well as the lower frequency bands, from a 1.75-Mc. crystal, coils for the second bandspread range also will be necessary to get full bandspread at 7 Mc. An examination of the coil-selection table will show what coils are required, depending upon the crystal frequency normally used to secure output in the desired band. If full bandspread at 7-Mc. and higher frequencies is not deemed necessary, the wide-bandspread coils for these frequencies need not be constructed.

The oscillator coils are wound on Millen one-inch diameter coil forms which are mounted in National PB-10 five-prong shielded plug-in bases. The feed-back coils, L₂, are wound over the bottom turns of L₁, and in the same direction. Connections to the base pins are given in Fig. 1378-A, B and C.

The buffer coils are wound on Hammarlund 1 1/2-inch diameter five-prong forms. The padding condensers, C₆, are mounted inside the coil forms, fastened in place with a 4-36 machine screw. Buffer coils for the higher-frequency ranges must be tapped as directed. One satisfactory way of making this tap is to drill a hole near the bottom of the form for a wire which may be brought outside from the pin to which the tap must be connected. The turn which is being tapped, as indicated in the table of coil dimensions, may be scraped and the tap wire soldered to this turn. Pin connections are shown in Fig. 1378-D and E.

COIL-SELECTION TABLE FOR VARIABLE-FREQUENCY UNIT *				
Transmitter Output Freq.	3.5 Mc.	7 Mc.	14 Mc.	28 Mc.
Crystal Freq. 1.75 Mc.	1 & 1A	1B & 1AB	1B & 1AB	—
3.5 Mc.	2 & 2A	2B & 2AB	2B & 2AB	—
7 Mc.	—	3 & 3A	3 & 3A	3B & 3AB

* Numbers refer to coils in coil-dimension table.

Tuning — Before an attempt is made to tune the circuits, the dropping resistor, R_2 , in the power supply should be adjusted. This is done with any pair of coils plugged in and the key closed. Starting with maximum resistance, the slider should be adjusted, bit by bit, until the VR tubes ignite. As much resistance as possible should be left in the circuit consistent with the maintenance of reliable operation of the VR tubes. If the tubes ignite with maximum resistance in the circuit further adjustment will not be required, unless the output voltage of the pack used happens to be unusually high. If this is the case, the value of dropping resistance should first be increased until the VR tubes no longer ignite, and then brought back to the point where they just ignite.

The first step in adjusting the unit is to check the frequency range of the oscillator. It is probable that differences in wiring inductances and capacities will make it necessary to make slight alterations in the oscillator coil dimensions given in the table. Unless the construction differs widely from the original, however, no more than adjustment of the spacing of a few turns at the top of L_1 should be required.

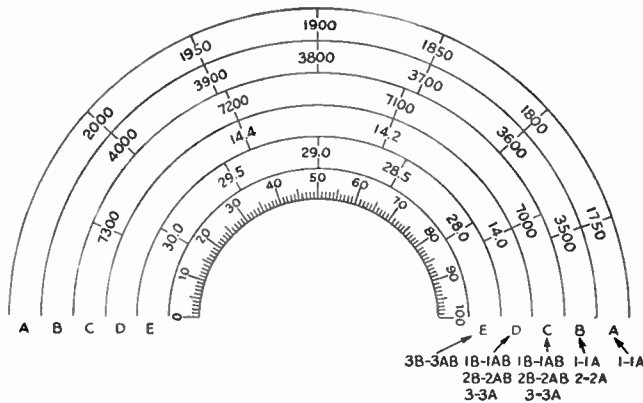


Fig. 1381 — Typical dial calibration for the v.f.o. unit. Notations at lower right indicate the calibrated ranges of the coil sets listed under Fig. 1378 and in the coil-selection table. Details of calibration are given in the text.

If close calibration is desired, a 100-ke. frequency standard checked against WWV (see Chapter Nineteen) or equivalent frequency-checking means should be provided. The approximate range of the oscillator coil under adjustment may be determined by listening to the exciter on a calibrated receiver. The 1.75-Mc. range of the receiver should be used for checking coil No. 1. The ranges of other coils may be checked with the receiver tuned to the 3.5-Mc. band. Care should be exercised, when a superheterodyne receiver is used, that it is tuned to the signal and not the image.

If no signal is heard at any point in the band with any setting of the v.f.o. dial, run a wire from the receiver antenna post to a point near the oscillator coil. If it is still impossible to pick up the signal, it is possible that the oscillator may not be functioning. This can be verified by absence of rectified d.c. grid voltage between the 6F6 grid and ground. One turn should then be added to the feed-back winding. More than the single additional turn should not be required. If the winding is larger than is needed for reliable operation with the key closed, the 6F6 may continue to oscillate weakly even with the key open. This condition is to be avoided, of course, if break-in operation is contemplated.

When the oscillator is functioning satisfactorily, the spacing of the top turn or two of L_1 should be adjusted until the desired band is centered on the dial of the unit. This can be done by spreading a turn or two, as mentioned previously. The shield can should be replaced each time a check is made. When the adjustment is final, the turns should be cemented permanently in place. The v.f.o. unit should be warmed up thoroughly before making a permanent calibration.



Fig. 1380 — High-frequency connections underneath the chassis of the v.f. exciter unit are made with short, straight sections of heavy wire. The two zero-temperature padding condensers are soldered directly to the oscillator-coil socket. All components are mounted firmly with no opportunity to support mechanical vibration. Washers 1/16-inch thick are placed between the panel and the chassis to provide space for the lower lip of the cabinet opening.



Fig. 1382 — Voltage-regulated power supply for the v.f. exciter unit. L_2 is mounted underneath the chassis.

The National ACN dial has imprinted scales for calibrating five ranges. Since the bandspread ratio is the same for the two lowest-frequency sets of coils, the oscillator coils for each of these ranges may be adjusted so that the 3.5-Mc. harmonics of the 1.75-Mc. range (1 and 1A) will coincide with the fundamental frequencies of the 3.5-Mc. range (2 and 2A) and one scale on the dial will serve for both calibrations. It is only necessary to adjust the oscillator coil of the 3.5-Mc. range so that the low-frequency end of the band falls at the same point as the second harmonic of 1750 of the 1.75-Mc. range falls when the 1.75-Mc. coils are plugged in. With similar adjustments, the 7-Mc. and 14-Mc. ranges of the coils 1B and 1AB, 2B and 2AB and 3 and 3A may be made to coincide. In the end there will be a single calibration on the dial for each band, and only five calibrations will be required for the complete set of coils listed in the coil table. A typical dial calibration is shown in Fig. 1381. Intermediate points may be marked in as desired. While the 14-Mc. band does not cover as much of the dial as do the other bands, nevertheless the bandspread is entirely adequate to enable accurate setting to zero-beat in this band.

With the oscillator ranges adjusted, the next step is to adjust the tracking of the buffer stage. A 6.3-volt (150-ma.) dial lamp with one or two turns of wire should be coupled to the output tank coil to act as an indicator. With the condenser gang set at minimum capacity, the padder, C_6 , in the coil form should be adjusted for maximum brilliance of the lamp. The gang should now be turned to maximum capacity. If the lamp decreases in brilliance, readjust C_6 , noting carefully whether an increase or decrease in capacity of C_6 is required to bring the lamp up to its original brilliance. (If the padders suggested in the parts table are used, and if they are mounted in the coil forms with their terminals downward, clockwise rotation of the adjusting screw will decrease capacity, while counter-clockwise rotation will increase capacity. If mounted with the ter-

minals upward, the action will be reversed.) If an increase in the capacity of C_6 is required with coils having no bandspread tap, C_7 is not tuning fast enough and a turn should be added to L_3 . If a decrease in the capacity of C_6 is required, a turn should be removed from L_3 . On the tapped coils the tap should be moved upward a turn toward the top of L_3 , if an increase in C_6 is required, or a turn downward toward the bottom of the coil, if C_6 is decreased.

After each adjustment of the coil, tracking should again be checked by adjusting C_6 for maximum brilliance with the condenser gang at minimum capacity and then checking at maximum capacity. These adjustments are simple and no trouble should be experienced in speedily arriving at the correct adjustments. When proper adjustments have been made, there should be no appreciable change in the brilliance of the lamp at any setting of the gang condenser.

If a check on plate currents is desired, meters may be inserted temporarily by opening up the wiring underneath the chassis. With correct adjustments of the tickler windings, L_2 , the oscillator plate current should run between 12 and 15 ma. The buffer plate current should run at about 19 ma. with the key open and increase one milliamperere or less with the key closed. Large changes in this plate current indicate that there are too many turns on L_2 .

Power supply — The v.f.o. unit operates from the power supply shown in Fig. 1382 and whose circuit is shown in Fig. 1383. The two are connected with a length of five-conductor shielded battery cable fitted with a five-prong female connector at the unit and a similar male plug at the power-supply end. The shield is connected to pin No. 5 at each end. Almost any of the usual type of well-filtered receiver power supplies delivering 325 to 350 volts with a 50-ma. or better rating may be made to serve the purpose equally well, merely by the addition of the VR150-30 regulator tubes and the dropping resistor, R_2 .

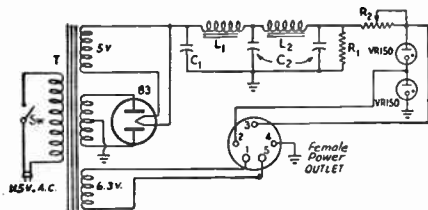


Fig. 1383 — Circuit diagram of the voltage-regulated power supply for the variable-frequency exciter unit. C_1 — 8- μ fd. 500-volt electrolytic (Mallory HD683). C_2 — Dual-section 450-volt electrolytic, 40 μ fd. per section, one section on each side of L_2 (Mallory FPI238).

L_1 , L_2 — 15 henrys, 100 ma. (UTC R19).

R_1 — 25,000 ohms, 10-watt.

R_2 — 2500 ohms, 25-watt with slider.

T — Combination power transformer: 375 volts r.m.s. each side of center-tap, 100 ma.; 5 volts, 3 amperes; 6.3 volts, 6 amperes (UTC R12).

Sw — S.p.s.t. toggle switch.

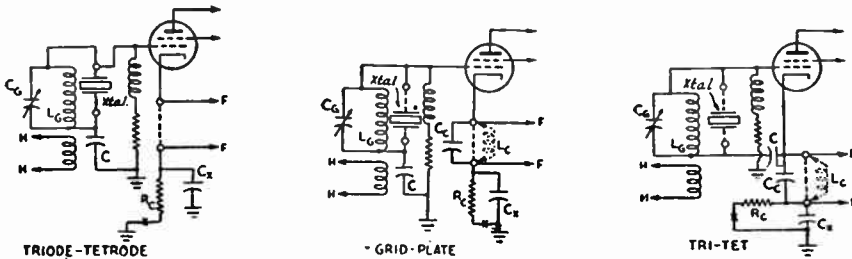


Fig. 1384 — Methods of coupling the output of the v.f.o. to crystal-oscillator stages of various types. See text for details. C is a mica condenser of $0.001 \mu\text{fd.}$ to prevent short-circuit of the grid leak. R_c and C_c are the usual oscillator cathode resistor and by-pass. C_c and L_c are the usual cathode-circuit tanks in the grid-plate and Tri-tet circuits. The v.f.o. link output is connected at H-H for harmonic operation and to F-F for fundamental operation. C_0 is $100 \mu\text{fd.}$ for the 1.75-Mc. band and $50 \mu\text{fd.}$ for the 3.5- and 7-Mc. bands. Dimensions for L_g are as follows:

1.75-Mc. input — 64 turns No. 24 d.s.c., close-wound, $1\frac{1}{2}$ -inch diameter.
 3.5-Mc. input — 40 turns No. 24, $1\frac{1}{2}$ -inch diameter, $1\frac{1}{2}$ -inches long.

7-Mc. input — 20 turns No. 18, $1\frac{1}{2}$ -inch diameter, $1\frac{1}{2}$ inches long.

Link windings consist of 8, 6 and 5 turns respectively for the 1.75-, 3.5- and 7-Mc. bands, close-wound below L_g .

Ⓐ Feeding Crystal-Oscillator Stages

The output of the v.f.o. unit is sufficient to drive an 807 or similar type of tube. Such a stage may be link coupled to the exciter unit by means of L_g or capacity coupled by connecting a small coupling condenser to the plate terminal of the 6L6. In the latter case, some readjustment of C_0 will be required to restore resonance, but retracking of the stage should not be necessary.


However, it is expected that the unit will be used more frequently to drive the crystal-oscillator stage of a crystal-controlled transmitter already in operation. While other methods of coupling between the crystal-oscillator stage and the v.f.o. unit may be devised, one satisfactory system which reduces the possibility of instability of the crystal-oscillator tube when coupled to the v.f.o. unit will be described in detail. Most crystal-oscillator stages are not sufficiently well-screened to permit operating the stage as a conventional straight amplifier with input and output circuits tuned to the same frequency. While the substitution for the crystal of a tuned circuit link-coupled to the output of the v.f.o. unit is the recommended method of coupling when the crystal stage is to be used as a frequency doubler, the stage will invariably break into oscillation if the same

system is used for fundamental operation. One satisfactory method of preventing this is to switch the link line to the cathode circuit for fundamental operation. The practical application of this system is shown applied to several typical varieties of crystal-oscillator circuits in Fig. 1384.

In each case, a tank circuit, C_0L_0 , tuned to the frequency of the crystal which it supplants, replaces the crystal when the stage is to be operated as a frequency doubler. The insertion of the condenser C is required to prevent short-circuit of the grid leak. The tank circuit is coupled to the output of the v.f.o. through a link line connecting at the points marked H-H. The openings indicated in the cathode circuits may be closed by a shorting bar. It is important to keep the shorting-bar leads as short as possible, otherwise there is danger of self oscillation even though the tuning of the grid and plate tanks may differ widely. In Tri-tet and grid-plate circuits, the cathode tanks must be shorted as indicated.

When the crystal stage is to be operated as a straight amplifier, the grid tank is removed, leaving the crystal position open. The link line from the v.f.o. is shifted to the points marked F-F and the cathode shorts indicated by the dotted lines removed. In Tri-tet or grid-plate

Fig. 1385 — Circuit arrangements for a plug-in coil system planned for most conveniently making connections in a Tri-tet oscillator circuit for optional crystal or v.f.o. operation. The grid tank for doubler operation is plugged into the same six-prong tube socket used by the crystal. The circuit at A shows the connections of the plug-in grid tank for frequency-doubler operation of the crystal stage with v.f.o. input. Values for L_g , C_0 , and the associated link coils are given under Fig. 1384. B shows connections for the plug-in cathode coil, L_c , which is the usual Tri-tet cathode winding. C shows the adapter circuit complete with all socket connections. C_c is the Tri-tet cathode-tank condenser and R_c and C_x are the usual cathode resistor and by-pass condenser.

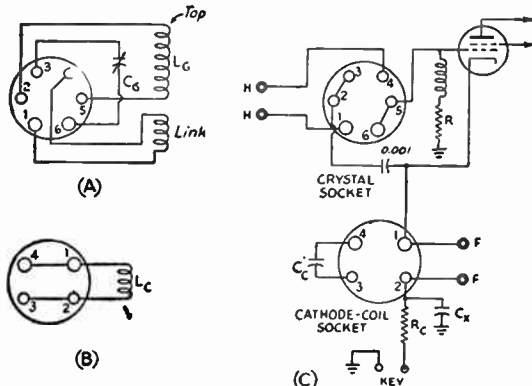

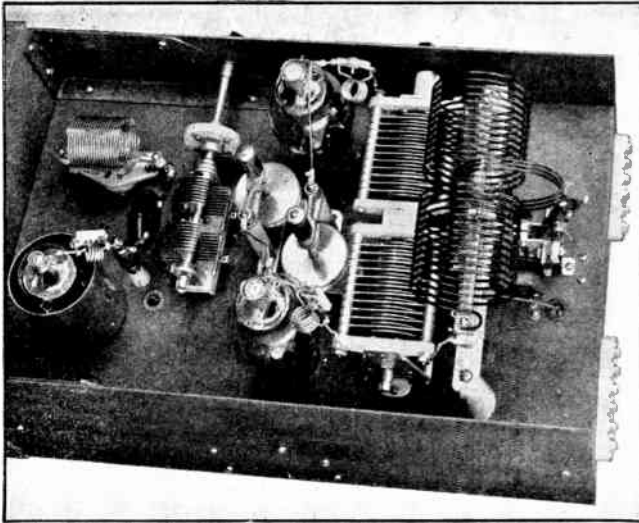


Fig. 1386 — Top view of the gang-tuned driver and push-pull amplifier designed to work with the v.f.o. unit of Fig. 1376. The chassis is elevated by 17×8 -inch panels on each side. The 807 socket, which is mounted an inch below the chassis top on spacers, and the socket for the coupling transformer, L_1L_2 , at the left-hand end of the chassis, are on either side of the bandspread condenser, C_2 , underneath. The 807 padding condenser, C_1 , is next to the right with an insulating coupling on its shaft which is $5\frac{1}{2}$ inches from the left-hand end of the chassis. The shaft of the final-amplifier padding condenser, $5\frac{1}{2}$ inches from the right-hand end of the chassis, is also fitted with an insulating coupling. The condenser is mounted on National polystyrene button insulators to bring its shaft level with that of C_1 . The sockets for the 812s are at either end of C_3 , with the neutralizing condensers between to make neutralizing leads short. The jack bar for the tank coil, L_3 , is mounted on 2-inch cone insulators.

oscillators, the cathode inductances and preferably the cathode tuning condensers also must be removed. If a cathode resistor is used, the excitation should be introduced in series between the cathode and the junction of the cathode resistor and its by-pass condenser as shown in Fig. 1385-C.

If the v.f.o. is to be keyed, the key terminals of the crystal stage must be shorted. A small amount of fixed bias may have to be connected between grid leak and ground to prevent excessive plate current when the key in the v.f.o. circuit is open. If break-in keying is not desired, the v.f.o. may be operated continuously and the crystal stage keyed in the usual manner.

Values for the substitute grid tank coil are given in Fig. 1384. A fairly-high L/C ratio has been chosen and, in most cases, any one band may be covered without retuning of the grid tank, if it is set to resonance in the middle of the band. The remainder of the transmitter will be tuned as usual.

The details of a convenient plug-in system which takes care of all connections in shifting from Tri-tet crystal operation (used in most of the transmitters described in this chapter) to either fundamental or doubler operation when using the v.f.o. unit are shown in Fig. 1385. The grid tank for doubler operation is plugged into the same six-prong tube socket used for the crystal. Link connections to the v.f.o. are made through pin jacks H-H. A short-circuiting wire connects pin jacks F-F into the cathode circuit. The leads from the cathode-coil socket to these jacks and the shorting wire should be kept as short as possible. The cathode coil should be removed from its socket.

For fundamental operation with the v.f.o. unit, the tank is removed from the grid-circuit and the shorting wire removed from F-F, to which the link line from the v.f.o. is shifted.

For crystal operation, the crystal is plugged into the grid circuit between prongs 6 and 3, or between 5 and 2, and the cathode coil is plugged into its socket, automatically connecting in the cathode condenser, C_c . The v.f.o. link line must be disconnected. Similar combinations may be worked out for other oscillator circuits not shown in the diagrams.

◀ A Gang-Tuned 450-Watt Push-Pull Amplifier and Driver

Figs. 1386, 1387 and 1389 show a gang-tuned unit which may be added to the v.f.o. unit of Fig. 1376. As shown in Fig. 1388, it consists of a push-pull amplifier and a driver stage, the tuning controls of which are coupled to the tuning shaft of the v.f.o. unit. Once adjusted for any given band, the four stages of the transmitter can be tuned with the single dial of the v.f.o. unit.


The two stages are coupled inductively with the tuning condensers connected across the grid winding. The use of inductive coupling solves the problem of balanced excitation to the amplifier without the dual tuning controls required with link coupling. C_1 and C_3 are the tank condensers, used for setting the circuits to the desired band. C_2 and C_4 are the band-tuning condensers. The two stages are adjusted for tracking by varying the portion of the coils across which the bandspread condensers, C_2 C_4 , are connected.

The trap circuits, L_4C_5 , L_5C_6 and L_6C_7 are for the purpose of suppression of v.h.f. parasitic oscillations.

The milliammeter may be switched to read 807 cathode or screen current, amplifier grid current, or amplifier cathode current by means of the dual-gang tap switch S .

Coils — While homemade coils of equivalent dimensions may be substituted, it may be found more convenient to alter manufactured

Fig. 1387 — Bottom view of the gang-tuned unit. The final amplifier bandspread condenser, C_4 , is mounted as far to the left as possible, on National polystyrene button insulators stacked level with that of the driver bandspread condenser, C_2 , to the right. The shafts of the two condensers are connected with flexible ceramic insulating couplings and also to the tail shaft of C_7 in the v.f.o. unit through a hole cut in the rear of the v.f.o. cabinet. C_2 is turned around so that its tail shaft couples to the shaft of the v.f.o. unit. The mounting hole of the condenser should come $2\frac{1}{2}$ inches from the left-hand edge of the chassis. The shaft stop pin should be removed. The remaining below-chassis wiring is simple and direct. Heavy tinned wire is used for all r.f. leads. The filament transformer is mounted below the chassis at the center rear. Insulated or protected terminals are used for all external power supply connections.

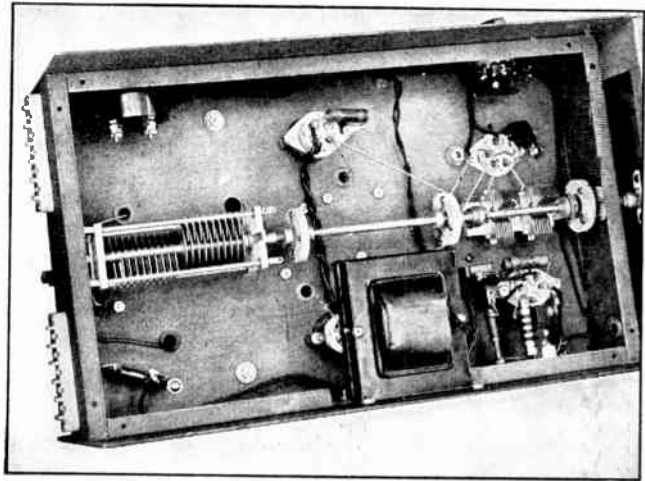

coils. The National coils suggested for L_1 should be obtained minus the links and mountings. Stripped, it will be found that these coils fit snugly inside the B & W coils used for L_2 , and that the plastic strips on each coil hold them central to prevent short circuits between L_1 and L_2 . The link winding should be removed from L_2 . The free base-pins thus provided will serve for the connections to C_2 . The tubular rivets at each end of the bottom spacing strip of the coil should be drilled or filed out, and $\frac{3}{4}$ -inch 6-32 machine screws substituted. A Johnson banana plug is fastened at each end of the base and the ends of L_1 are connected to these plugs.

In the chassis, on either side of the coil socket and directly below the banana plugs, a hole should be drilled. The one on the right-hand side should be $\frac{1}{4}$ -inch in diameter, while the one on the left-hand side should be $\frac{1}{2}$ -inch in diameter. A jack to fit the banana plug should be placed in a National polystyrene button-type insulator with the shoulder filed off and the hole drilled out to fit the jack. This jack, mounted in the $\frac{1}{4}$ -inch hole with the insulator as a spacer, then serves to make the ground connection for L_1 . The $\frac{1}{2}$ -inch hole is for a second jack insulated from the chassis by a pair of button-type feed-through insulators. This jack serves as the connection for the other end of L_1 .

The B & W type TVII coils are selected not only because they are of the proper size for the power involved, but also because they are supplied with extra plugs which may be used for the ganging taps for C_4 .

Combining Units

Fig. 1389 shows how the two units are joined together. The output of the v.f.o. and the input of the 807 driver stage are coupled capacitively, a short wire connecting the binding post in the v.f.o. unit with the coupling condenser, C_{10} , in the ganged unit. Large holes are made in the rear of the v.f.o. cabinet and the end of the chassis to clear a small National rigid shaft coupling. The height of the chassis should be adjusted so that the shafts of the two units line up perfectly. If the condenser gangs in each unit have been mounted as described, the shafts will be lined up when the bottom edge of the $10 \times 17 \times 3$ -inch chassis is $2\frac{1}{4}$ inches above the bottom edges of the supporting panels.

The two units are fastened together with 7-inch triangular brackets, the tops of which have been cut off to fit, on each side of the chassis. The excitation lead to the grid of the 807 passes through a grommet-lined hole in the back of the v.f.o. cabinet and a similar one in the front edge of the chassis.

Power-supply requirements are covered in the section of the complete gang-tuned transmitter the description of which follows in the next section.

Tuning — If coil dimensions have been followed carefully, there should be little difficulty in lining up the various stages. The shaft couplings must be adjusted so that all condensers of the gang arrive at maximum or minimum capacity simultaneously. Coils should be plugged in the various stages for the desired band, using the coil-selection table as a guide.

With the tuning control set for the high-frequency edge of the band, the voltage-regulated supply and the bias supply should be turned on simultaneously. This will apply plate voltage to the v.f.o. unit and screen voltage to the 807. Using the 807 screen current as an indicator, the trimmer of the buffer stage in the v.f.o. unit should be lined up. Maximum

COIL-SELECTION TABLE FOR GANGED UNIT

Band	Osc.	Buffer	Driver	Final
3.5 Mc.	No. 2	No. 2A	3.5 Mc.	3.5 Mc.
7 Mc.	No. 3	No. 3A	7 Mc.	7 Mc.

screen current indicates resonance. The key should not be held closed for excessively long periods, to limit screen heating. Tuning to the low-frequency end of the band should show negligible change in screen current. Should there be evidence of poor tracking, the buffer stage can be brought into line again as discussed in the section describing the tuning of the v.f.o. unit.

Plate voltage may now be applied to the 807 and the stage tuned to resonance with C_1 . A check should be made for parasitic oscillation, with a lamp of sufficient size to reduce the plate voltage to about half in series with the primary of the 750-volt transformer. At several settings of the v.f.o. unit C_1 should be varied throughout its range, carefully noting any change in cathode current which would indicate oscillation. An additional check may be made by touching a neon bulb to the plate of the 807. Should oscillation occur, the parasitic trap condenser, C_5 , should be adjusted until the oscillation is suppressed.

Turning now to the tracking of the driver stage, tuning C_1 to resonance should result in a showing of amplifier grid current. Again starting at the high-frequency end of the band, C_1 should be adjusted for maximum grid current. If there is a serious falling off of grid current as

the unit is tuned to the low-frequency end of the band, a check should be made to determine if readjusting C_1 will bring the grid current back up. If it does not, the size of L_1 must be increased by one or two turns. If, however, retuning of C_1 shows the tuning to be off resonance at the low-frequency end of the band, it should be carefully noted whether an increase or a decrease in the capacity of C_1 is necessary to restore resonance. If an increase in C_1 is required, the taps of C_2 should be spread slightly farther apart; if a decrease is required, they should be brought closer together. After each check the tuning of the unit should be returned again to the high-frequency end and realigned, before again checking the low-frequency end of the band.

However, should the first check at the low-frequency end of the band show an increase in grid current over that obtained at the high-frequency end a turn or two should be removed from L_1 , after which the tracking should again be checked as previous described.

With substantially constant grid current over the band, the amplifier may be neutralized in the usual manner. With the amplifier operating at reduced plate voltage, a check similar to that described for the 807 stage should be made to eliminate any tendency toward para-


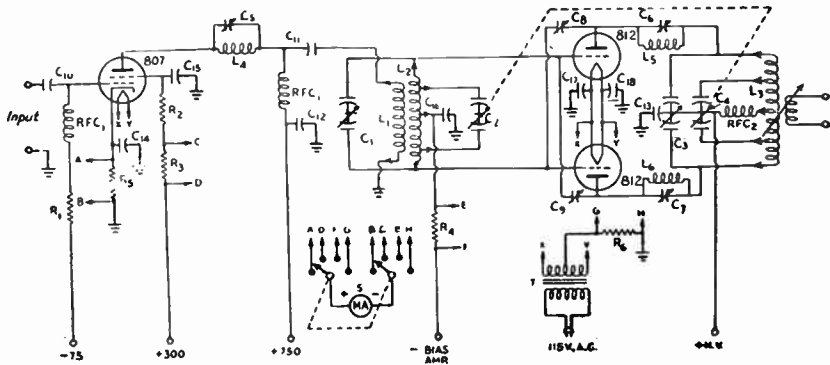


Fig. 1388 — Circuit diagram of the 450-watt gang-tuned driver and push-pull amplifier unit.

- C_1 — 110 μfd . per section (Hammarlund MCD-140-S).
- C_2 — 100 μfd . per section (Hammarlund MCD-100-S).
- C_3 — 150 μfd . per section, 0.07-inch spacing (Johnson 150FD30).
- C_4 — 65 μfd . per section, 0.07-inch spacing (Hammarlund HFB-D-65-F).
- C_5, C_6, C_7 — 3–30- μfd . mica trimmer (National M-30).
- C_8, C_9 — Neutralizing condensers (National NC-800).
- C_{10} — 100- μfd . mica.
- C_{11}, C_{12} — 0.001- μfd . mica, 1000-volt rating.
- C_{13} — 0.001- μfd . mica, 7500-volt (Aerovox 1623).
- $C_{14}, C_{15}, C_{16}, C_{17}, C_{18}$ — 0.01- μfd . mica.
- MA — Millimeter, 100-ma. scale.
- R_1 — 25,000 ohms, 1-watt.
- R_2 — 20,000-ohm, 10-watt variable.
- R_3, R_4 — 25 ohms, 1-watt.
- R_5 — Meter-multiplier resistance, 2 times, wound with No. 26 wire.
- R_6 — Meter-multiplier resistance, 5 times, wound with No. 24 wire.
- RFC₁ — 2.5-mh. r.f. choke.
- RFC₂ — 500-ma. r.f. choke (Hammarlund CH500).
- S — Two circuit, 4-contact switch (Mallory 3234J).
- T — 6.3 volts, 10 amperes (Thordarson T-19F99).

- L_1 — Mounted inside L_2 :
3.5 Mc. — 22 turns No. 22, 1¼-inch diameter, 1¼ inches long (National AR40, unmounted, 6 turns removed).
- 7 Mc. — 14 turns No. 20, 1¼-inch diameter, 1¼ inches long (National AR20, unmounted).
- L_2 — 3.5 Mc. — 28 turns No. 22, 1½-inch diameter, 1½ inches long, taps at 3 turns from each end (B & W JCL-80, no link, 8 turns removed from each end).
- 7 Mc. — 18 turns No. 16, 1½-inch diameter, 1½ inches long, taps at 6 turns from each end (B & W JCL-40, no link, 5 turns removed from each end).
- L_3 — 3.5 Mc. — 38 turns No. 14, 5¼ inches long, 2½-inch diameter, ¾-inch space at center for link, taps at 3¾ turns from each end (B & W TVH-80).
- 7 Mc. — 24 turns No. 12, 5¼ inches long, 2½-inch diameter, ¾-inch space at center for link, taps at ¾ turns from each end (B & W TVH-40).
- L_4 — 5 turns No. 14, ¾-inch diameter, 1 inch long.
- L_5, L_6 — 4 turns No. 14, ¾-inch diameter.

Fig. 1389—The v.f.o. unit of Fig. 1376 combined with the gang-tuned driver and push-pull final amplifier. The two units are fastened together with 7-inch triangular brackets, the tops of which have been cut off to fit, on each side of the chassis. The excitation lead to the grid of the 807 passes through a grommet-lined hole in the back of the v.f.o. cabinet. The milliammeter and the meter switch are placed on the panel to balance each other at opposite ends of the chassis. Holes for these components must be cut in the chassis edge. The control at the left is for setting the final-amplifier padder or band-setting condenser, C_3 , while the control to the right is for the driver padder, C_1 . The $10 \times 17 \times 3$ -inch chassis is elevated approximately $2\frac{1}{4}$ inches by supporting it on panels 8 inches high running the length of the chassis. The clearance and assembly holes through the panel and chassis should be made slightly oversize to permit accurate adjustment of the chassis height for lining up the tuning-condensers shafts.

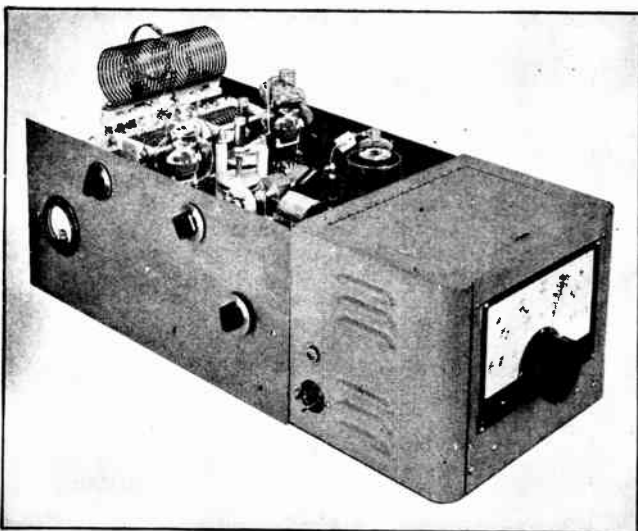

sitic oscillation. For several settings of the ganged control, C_3 should be varied throughout its range. If oscillation occurs, the parasitic trap condensers, C_6 and C_7 , should be adjusted in equal steps until it ceases.

Still operating at reduced plate voltage, the amplifier should be loaded with a lamp bulb of 150 to 200 watts connected to the output link. C_3 should be adjusted for resonance at the high-frequency end of the band. Tuning across the band should now show no appreciable change in power input or output. If a check, by retuning C_3 at the low-frequency end of the band, shows the stage to be off resonance, a note should be made as to whether an increase in the capacity of C_3 or a decrease is necessary to restore resonance. If an increase is required, the taps of C_4 should be spread slightly, while a decrease in C_3 indicates that the taps of C_4 should be brought slightly closer together. Again, each adjustment of tracking should be followed by realigning at the high-frequency end of the band before making a check on the new adjustment at the low-frequency end.

If coil dimensions have been followed carefully these tracking adjustments should not be required. They are described to take care of cases in which the constructor may have gone astray at some point, or in which the design has been changed to suit other requirements. Naturally, the adjustments for the higher-frequency bands must be made in smaller steps than those required for the lower-frequency bands.

At the plate voltages recommended, the screen current, when lining up the v.f.o. output stage, should run between 5 and 10 ma. Cathode current to the driver stage when tuned and loaded should be between 70 and 100 ma., while grid current to the final amplifier should exceed 50 ma. with the amplifier loaded to the rated plate current of 300 ma. at 1500 volts.

Under operating conditions the driver screen voltage should run close to 250 volts. When correctly adjusted, the power output across any of the three bands should remain constant at 300 watts.

For 'phone operation with plate modulation, the input to the final amplifier should be reduced to 250 ma. at 1250 volts.

The tube tables in Chapter Twenty should be consulted for the operating conditions of other types of tubes should they be used in the final amplifier.

Complete Variable-Frequency Gang-Tuned Transmitter

Fig. 1389 shows the two units of Figs. 1376 and 1386 combined for gang tuning. The voltage-regulated supply of Fig. 1382 may be used to furnish screen voltage for the 807 by bringing out a tap from the junction of resistors R_1 and R_2 . The unit of Fig. 1351 will furnish biasing voltages for both 807 and final amplifier. The voltage-divider resistance of the bias unit should be adjusted with 4000 ohms in the R_2 portion and 4000 ohms in the R_3 portion. Plate voltage for the 807 may be obtained from the unit of Fig. 1316, while the unit of Fig. 1349 will furnish plate voltage for the amplifier. A suitable antenna tuner is shown in the photograph of Fig. 1353.

To facilitate rapid setting of the band-set condensers, their dials may be provided with scales upon which the correct setting for each band is marked.

Similarly, to simplify antenna tuning and make it possible to adjust the antenna without putting a signal on the air, the antenna-tuner dial may be provided with a scale which may be calibrated in terms of receiver- or v.f.o.-dial settings. Since antenna tuning should not be critical, the dial need be calibrated for only several scattered points throughout each band.

□ A Practical Vacuum-Tube Keyer

Fig. 1391 shows a practical vacuum-tube keyer unit. The circuit diagram is shown in Fig. 1390. T_1 , the rectifier, with C_1 and R_1 form the power-supply section for producing the blocking voltage necessary for cutting off the keyer tubes. With only R_2 in the circuit and Sw_2 in the open position, there will be no lag. As Sw_2 is turned to introduce more capacity in the circuit, the keying characteristic is "softened" at both make and break. Adding resistance by turning Sw_1 to the right affects the "break" only. The use of high resistances and small capacities results in small demand on the power supply and makes the key safe to handle.

As many 45s may be added in parallel as desired. The voltage drop through a single tube varies from 90 volts at 50 ma. to 52 volts at 20 ma. Tubes in parallel will reduce the drop in proportion to the number of tubes. If rated voltage is important in the operation of the keyed circuit, the drop through the keyer tubes must be taken into account and the transmitter voltage boosted to compensate for the drop.

If desired, a greater angle of lag can be obtained by using a rotary switch with more points and additional resistors and condensers. Suggested values of capacity, in addition to C_2 and C_3 , are 0.001 and 0.002 μ fd. From R_2 , resistors of 2, 3 and 5 megohms may be added.

When connecting the output terminals of the keyer to the circuit to be keyed, care must be used to connect the grounded output terminal to the negative side of the keyed circuit.

□ Rack Construction

Most of the units described in the constructional chapters of this *Handbook* are designed for standard rack mounting. The assembly of a selected group of units to form a complete transmitter is, therefore, a relatively simple matter. While standard metal racks are available on the market, many amateurs prefer to build their own less expensively from wood. With care, an excellent substitute can be made.

The plan of a rack of standard dimensions is shown in Fig. 1392. The rack is constructed entirely of 1 \times 2-inch stock of smooth pine, spruce or redwood, with the exception of the trimming strips, *M*, *N*, *O* and *P*. Since the actual size of standard 1 \times 2-inch stock runs appreciably below these dimensions, a much sturdier job will result if pieces are obtained cut to the full dimensions.




Fig. 1391 — A vacuum-tube keyer, built up on a 7 \times 9 \times 2-inch chassis with space for four or more keyer tubes and the power-supply rectifier. The resistors and condensers which produce the lag are mounted underneath, controlled by the knobs at the right. The jack is for the key, while terminals at left are for the keyed circuit.

The main vertical supporting members of the wooden rack each is comprised of two pieces (*A* and *B*, and *I* and *J*) fastened together at right angles. Each pair of these members is fastened together by No. 8 flathead screws, with heads countersunk.

Before fastening these pairs together, pieces *A* and *J* should be made exactly the same length and drilled in the proper places for the mounting screws, using a No. 30 drill. The length of pieces *A*, *J*, *B* and *I* should equal the total height of all panels required for the transmitter plus twice the sum of the thickness and width of the material used. If the dimensions of the stock are exactly 1 \times 2 inches, then 6 inches must be added to the sum of the panel heights. An inspection of the top and bottom of the rack in the drawing will reveal the reason for this. The first mounting hole should come at a distance of $\frac{1}{4}$ inch plus the sum of the thickness and width of the material from either end of pieces *A* and *J*. This distance will be $3\frac{1}{4}$ inches for stock exactly 1 \times 2 inches. The second hole will come $1\frac{1}{4}$ inches from the first, the third $\frac{1}{2}$ inch from the second, the fourth $1\frac{1}{4}$ inches from the third and so on, alternating spacings between $\frac{1}{2}$ inch and $1\frac{1}{4}$ inch (see detail drawing *D*, Fig. 1392). All holes should

Fig. 1390 — Wiring diagram of the practical vacuum-tube keyer unit and power supply shown in Fig. 1391.

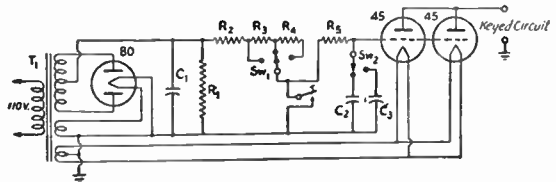- C_1 — 2- μ fd. 600-volt paper.
- C_2 — 0.003- μ fd. mica.
- C_3 — 0.005- μ fd. mica.
- R_1 — 0.25 megohm, 1-watt.
- R_2 — 50,000 ohms, 10-watt.
- R_3 , R_4 — 5 megohms, 1-watt.
- R_5 — 0.5 megohm, 1-watt.
- Sw_1 , Sw_2 — 3-position 1-circuit rotary switch.
- T_1 — 325-0-325 volts, 5 volts and 2.5-volts (Thordarson T-13R01).



be placed $\frac{3}{8}$ inch from the inside edges of the vertical members.

The two vertical members are fastened together by cross-member *K* at the top and *L* at the bottom. These should be of such a length that the inside edges of *A* and *J* are exactly $17\frac{1}{2}$ inches apart at all points. This will bring the lines of mounting holes $18\frac{1}{4}$ inches center to center. Extending back from the bottoms of the vertical members are pieces *G* and *D* connected together by cross-members *L*, *Q* and *E*, forming the base. The length of the pieces *D* and *G* will depend upon space requirements of the largest power supply unit which will rest upon it. The vertical members are braced against the base by diagonal members *C* and *H*.

Rear support for heavy units placed above the base may be provided by mounting angles on *C* and *H* or by connecting these members with cross-braces as shown at *F*.

To finish off the front of the rack pieces of $\frac{1}{4}$ -inch oak strip (*M*, *N*, *O*, *P*) are fastened around the edges with small-head finishing nails. The heads are set below the surface and the holes plugged with putty or plastic wood.

The top and bottom edges of *M* and *O* should be $\frac{1}{4}$ inch from the first mounting holes, and the distance between the inside edges of the vertical strips, *N* and *P*, $19\frac{1}{16}$ inches.

To prevent the screw loosening from wearing out when panels are changed frequently, $\frac{1}{2} \times \frac{1}{16}$, or $\frac{1}{32}$ inch iron or brass strip may be used to back up the vertical members of the frame.

The outside surfaces should be sandpapered thoroughly and given one or two coats of flat black sandpapering between coats. A finishing surface of two coats of glossy black "Duco" is then applied, again sandpapering between coats. It is very important to allow each coat to dry thoroughly before applying the next, or sandpapering.

Since the combined weights of power supplies, modulator equipment, etc., may total to a surprising figure, the rack should be provided with rollers or wheels so that it may be moved about when necessary after the transmitter has been assembled. Ball bearing roller-skate wheels are suitable for the purpose.

Standard metal chassis are 17 inches wide. Standard panels are 19 inches wide and multiples of $1\frac{3}{4}$ inches high. Panel mounting holes start with the first one $\frac{1}{4}$ inch from the edge of the panel, the second $1\frac{1}{4}$ inches from the first, the third $\frac{1}{2}$ inch from the second, the fourth $1\frac{1}{4}$ inches from the third, and the distances between holes from there on alternated between $\frac{1}{2}$ inch and $1\frac{1}{4}$ inches. (See detail D, Fig. 1392.) In a panel higher than two or three rack units ($1\frac{3}{4}$ inch per unit), it is common practice to drill only sufficient holes to provide a secure mounting. All panel holes should be drilled $\frac{3}{8}$ inch in from the edge.

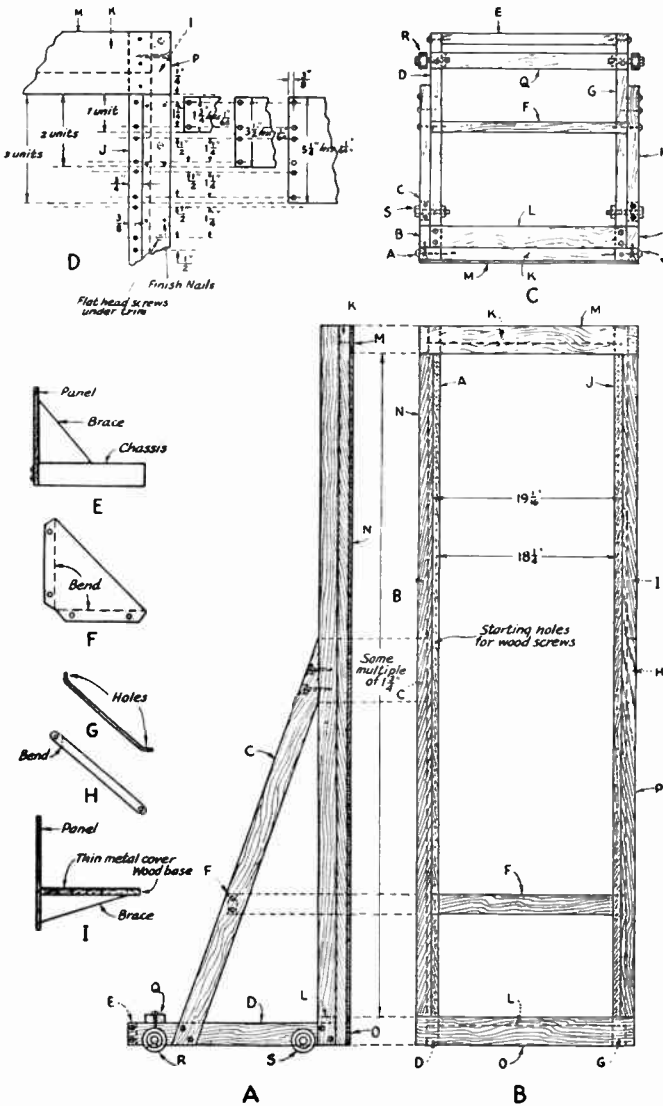


Fig. 1392 — The standard rack. A — Side view. B — Front view. C — Top view. D — Upper right hand corner detail. E — Panel and chassis assembly. F, G, H — Various types of panel brackets. I — Substitute for metal chassis.

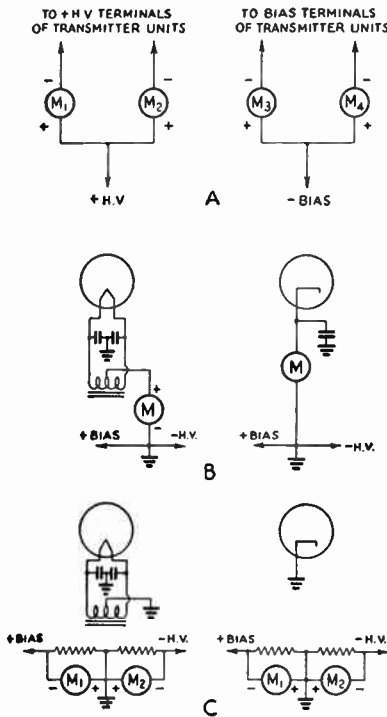


Fig. 1393 — Various methods of connecting milliammeters in grid and plate currents. A — High-voltage metering. B — Cathode metering. C — Shunt metering.

Ⓜ Metering

Various methods of metering are shown in Fig. 1393. A shows the meters placed in the high-voltage plate and bias circuits. M_1 and M_2 are for plate current and M_3 and M_4 for grid current. When more than one stage operates from the same plate-voltage or bias-voltage supply, each stage may be metered as shown. If this system of metering is used, the meters should be mounted so that the meter dials are not accessible to accidental contact with the adjusting screw. One method of mounting is shown in Fig. 1394, where the meters are mounted behind a glass panel.

When plate milliammeters are to be mounted on metal panels, care must be taken to see that

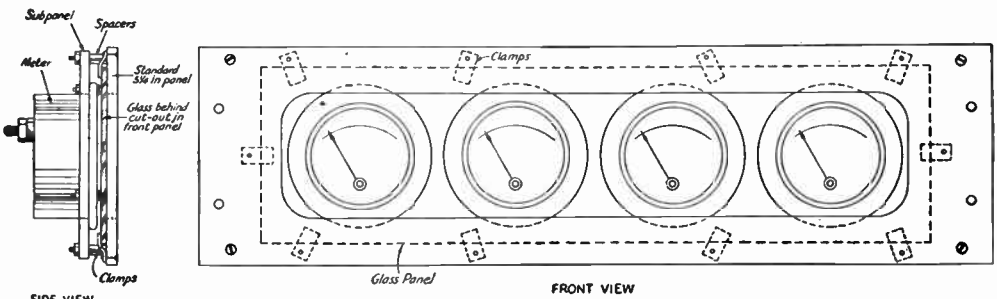


Fig. 1394 — Safety panel for meters. The meters are mounted in the usual manner on an insulating sub-panel spaced back of a glass-covered opening in the front panel. The glass is fastened in place with metal clamps or tabs, fastened to the front panel with small screws or pins. The front panel is of standard rack size, $19 \times 5\frac{1}{4}$ inches.

the insulation is sufficient to withstand the plate voltage. Metal-case instruments should not be mounted on a grounded metal panel if the difference in potential between the meter and the panel is to be more than 300 volts; bakelite-case instruments can be used under similar circumstances at voltages up to 1000. At higher voltages than these an insulating panel should be used.

The placing of meters at high-voltage points in the circuit may be overcome by the use of the connections shown in Fig. 1393-B and -C. The disadvantage of the arrangements at B is that the meter reads total cathode current and the grid and plate currents cannot be metered individually. This disadvantage is overcome in C, where the meters are connected across low resistances in the grid and plate return circuits. M_1 reads grid current and M_2 plate current. The parallel resistors should have a value of not less than 10 to 20 times the resistance of the meter, and should be of sufficient power rating so that there will be no possibility of resistor burn-out. If desired, the resistance values may be adjusted to form a multiplier scale for the meter (see Chapter Nineteen). The same principle is used in the meter-switching system shown in Fig. 1395.

Meters may also be shifted from one stage to another by a plug-and-jack system, but this

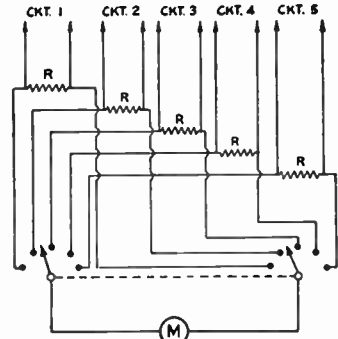


Fig. 1395 — Method of switching a single milliammeter to various circuits with a two-gang switch. The control shaft should be well insulated from the switch contacts, and should be grounded. The resistors, R , should have values of resistance ten to twenty times the internal resistance of the meter; 20 ohms will usually be satisfactory.

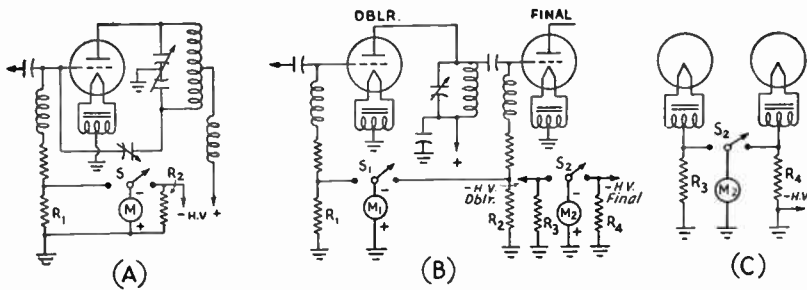


Fig. 1396 — Toggle-switch meter switching. At A is a circuit for switching meter from grid to plate circuit of same stage. At B is a circuit for switching grid meter between two stages and plate meter between two stages. At C is an alternative circuit, similar to the one at B, in which separate filament transformers permit the use of a common plate supply. R₁ and R₂ are grid-circuit meter shunt resistors, while R₃ and R₄ are the plate-circuit shunt resistors.

system should not be used unless it is possible to ground the frame of the jack or unless a suitable guard is provided around the meter jacks to make personal contact with high voltages impossible in normal use of the plug.

Another metering system based upon the use of simple s.p.d.t. toggle switches is shown in the diagram of Fig. 1396. In each case provision is made for metering two circuits with a single milliammeter. Grid returns should be made to filament center tap or cathode rather than to ground or negative high voltage. If currents included in the meter range are to be measured, the resistors should have a value of about 50 ohms each, otherwise they should be adjusted to give the desired scale multiplication.

Control Circuits

Proper arrangement of controls is important if maximum convenience in operation is to be attained. If the transmitter is to be of fairly high power, it is desirable to provide a special service line leading directly from the public utility meter board to the operating room. This line should be run in conduit or BX cable, and

the conductors should be of ample size to carry the maximum load without undue voltage drop. The line should be terminated with an enclosed entrance switch, properly fused.

Fig. 1397 shows the wiring diagram of a simple control system. It will be noticed that, because the control switches are connected in series, none of the high-voltage supplies can be turned on until the filament switch has been closed, and that the high-power plate supply cannot be turned on until the low-power plate supply switch has been closed. Furthermore, the modulator power cannot be applied until the final-amplifier plate voltage has been applied. Sw₅ places a 100- to 300-watt lamp, L_p, in series with the primary winding of the high-voltage plate transformer for use during the process of preliminary tuning and for local c.w. work. The final amplifier should first be tuned to resonance at low voltage and Sw₃ then closed, short-circuiting the lamp. Experience will determine what the low-voltage plate-current reading should be to have it increase to the full-power value when Sw₅ is closed, so that the proper antenna-coupling and tuning adjustments may be made.

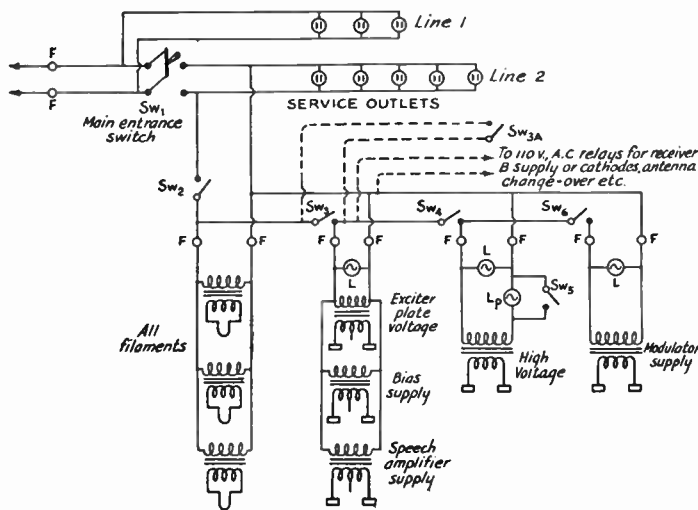


Fig. 1397 — A station control system. No high-voltage supply can be turned on until the filament switch has been closed; the high-power plate supply cannot be turned on until the low-power plate supply switch has been closed; and modulator power cannot be applied until the final-amplifier plate voltage has been applied. With all switches except Sw₃ closed, Sw₂ serves as the main control switch. Sw₁ — Enclosed entrance switch. Sw₂ — Filament switch. Sw₃ — Low plate voltage and main control switch, preferably of the push-button type which remains closed only so long as pressure is applied. Sw₄ — High plate-voltage switch. Sw₅ — Low-power and tune-up switch short-circuiting L_p. Sw₆ — Modulator plate-voltage switch. F — Fuse. L — Warning light. L_p — 100- to 300-watt voltage-reducing lamp.

Preferably, Sw_3 should be of the non-locking push-button type which remains closed only so long as pressure is applied. A switch of this type provides one of the simplest and most effective means of protection against accidents from high voltage. In the form which is usually considered most convenient, it consists of a switch, located underneath the operating table, which may be operated by pressure of the foot. When used in this manner the operator must be in the operating position, well removed from danger, before high voltage can be applied. If desired, Sw_{3a} may be wired in parallel on the front of the transmitter panel, so that it can be used while tuning the transmitter. Sw_3 also should be of the push-button type.

In more elaborate installations, and in remote control systems where the transmitter is located some distance from the operating position, similarly arranged switches may be used to control relays whose contacts serve to perform the actual switching at the transmitter.

Two strings of utility outlets, one on each side of the entrance switch, are provided for operation of the receiver and such accessories as the monitor, lights, electric clock, soldering iron, etc. Closing the entrance switch should close those circuits which place the station in readiness for operation. Sw_2 and Sw_4 are normally closed and Sw_3 is normally open. When Sw_1 is closed upon entering the operating room, the transmitter filaments are turned on as also is the receiver, which should be plugged into line No. 2. With Sw_1 closed (as well as Sw_5 and Sw_6), Sw_3 performs the job of turning all plate supplies on and off during successive periods of transmission and reception.

All continuously operating accessories, such as the station clock, should be plugged into line No. 1. This is so that they will not be turned off when Sw_1 is opened. Line No. 1 is of use also for supplying the soldering iron, lights, etc., when it is desired to remove all voltage from the transmitter by opening Sw_1 .

Line-Voltage Adjustment

In certain communities trouble is sometimes experienced from fluctuations in line voltage. Usually these fluctuations are caused by a

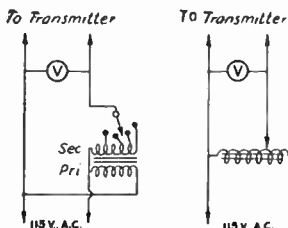


Fig. 1938 — Two methods of transformer primary control. At the left is a tapped 1-to-1 transformer with the possibilities of considerable variation in the secondary output. At the right is indicated a variable transformer or autotransformer, often referred to as a "variac," in series with the transformer primaries.

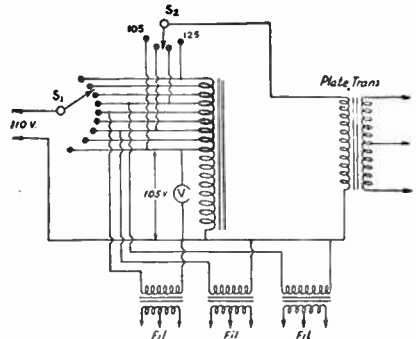


Fig. 1399 — With this circuit, a single adjustment of the tap switch S_1 places the correct primary voltage on all transformers in the transmitter. Information on constructing a suitable autotransformer at negligible cost is contained in the text. The light winding represents the regular primary winding of a revamped transformer, the heavy winding the voltage-adjusting section.

variation in the load on the line and, since most of the variation comes at certain fixed times of the day or night, such as the times when lights are turned on and off for the night, they may be taken care of by the use of a manually-operated compensating device. A simple arrangement is shown in Fig. 1398. A toy transformer is used to boost or buck the line voltage as required. The transformer should have a tapped secondary varying between 6 and 2.0 volts in steps of 2 or 3 volts and its secondary should be capable of carrying the full load current of the entire transmitter.

The secondary is connected in series with the line voltage and, if the phasing of the windings is correct, the voltage applied to the primaries of the transmitter transformers can be brought up to the rated 115 volts by setting the toy transformer tap-switch on the right tap. If the phasing of the two windings of the toy transformer happens to be reversed, the voltage will be reduced instead of increased. This connection may be used in cases where the line voltage may be above 115 volts. This method is preferable to using a resistor in the primary of a power transformer since it does not affect the voltage regulation as seriously.

Another scheme by which the primary voltage of each transformer in the transmitter may be adjusted to deliver the desired secondary voltage with a master control for compensating for changes in line voltage is shown in Fig. 1399.

This arrangement has the following features:

1. Adjustment of S_1 to make the voltmeter read 105 volts automatically adjusts all primaries to the predetermined correct voltage.
2. The necessity for having all primaries work at the same voltage is eliminated. Thus, 110 volts can be applied to the primary of one transformer, 115 to another, etc.
3. Independent control of the plate transformer is afforded by the tap switch S_2 . This permits power input control and does not require an extra auto-transformer.

Modulation Equipment

TO PROVIDE the modulating power necessary in radiotelephone communication, audio power amplifiers or modulators are required. The units described in this chapter have been designed to give the required power output as simply and economically as possible, while still observing good design principles.

In many respects the arrangement of components is less critical in audio than in r.f. equipment; nevertheless, certain principles must be observed if difficulties are to be avoided. The selection of suitable modulation equipment for any of the transmitters in the preceding chapter is not difficult, if the fundamental principles of modulation as described in Chapter Five are understood. If the transmitter is to be plate-modulated and the power input to the modulated stage is to be of the order of 100 watts or higher, a Class-B modulator invariably will be selected. A pair of modulator tubes of any type capable of the required power output may be used. The tables in this chapter give the necessary information on the most popular tube types. The driving-power requirements for the modulator stage also are given, so that from this point on the speech amplifier tube line-up can be selected according to the principles outlined in Chapter Five.

The apparatus to be described is representative of current design practice for speech amplification, with units to provide the various output levels required to drive high- and low-power Class-B modulators. In some cases the power output of these amplifier units will be sufficient to modulate low-power transmitters directly, without additional power amplification. Also, practically any of the speech amplifiers shown can be used to grid-modulate transmitters up to the highest power input permitted in amateur transmitters.

Speech-amplifier equipment, especially voltage amplifiers, should be constructed on metal chassis, with all wiring kept below the chassis to take advantage of the shielding afforded. Exposed leads, particularly to the grids of low-level high-gain tubes, are likely to pick up hum from the electrostatic field which usually exists in the vicinity of house wiring. Even with the chassis, additional shielding of the input circuit of the first tube in a high-gain amplifier usually is necessary. In addition, such circuits should be separated as much as possible from power-supply transformers and chokes and also from audio transformers

operating at fairly high power levels, to prevent magnetic coupling to the grid circuit which might cause hum or audio-frequency feed-back.

If a low-level microphone such as the crystal type is used, the microphone, its connecting cable, and the plug or connector by which it is attached to the speech amplifier, all should be shielded. The microphone and cable usually are constructed with suitable shielding. The cable shield should be connected to the speech amplifier chassis, and it is advisable — as well as frequently necessary — to connect the chassis to a ground such as a water pipe. Heater wiring should be kept as far as possible from grid leads, and either the center-tap or one side of the heater transformer secondary winding should be connected to the chassis. In a high-gain amplifier the first tube preferably should be of the type having the grid connection brought out to a top cap rather than to a base pin, since in the latter type the grid lead is exposed to the heater leads inside the tube and hence will pick up more hum. With the top-cap tubes, complete shielding of the grid lead and grid cap is a necessity.

□ A 10-Watt Class-B Modulator for Low-Power Transmitters

A receiving-tube modulator, with a speech amplifier for either crystal or carbon microphones, is shown in Figs. 1401–1403, inclusive. It is suitable for modulating transmitters of 20 watts input or less, such as the low-power equipment frequently used on the very-high frequencies. Type 6A6 tubes are used throughout in the audio circuits, although any equivalent twin triode such as the 6N7 could be substituted. An inexpensive power supply is included, so that the unit is complete and ready for connection to the transmitter.

Fig. 1403 shows the circuit diagram of the speech amplifier-modulator. One section of the

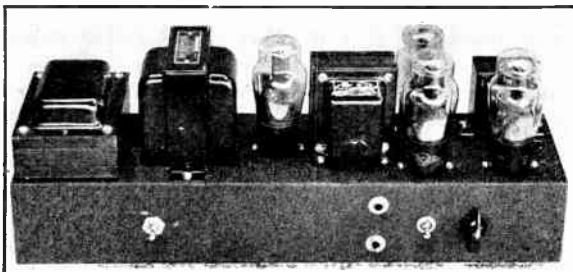


Fig. 1401 — A 10-watt audio unit complete with power supply. Three dual-triode 6A6 tubes provide a four-stage amplifier with Class-B output. Any of the popular types of microphones may be used.

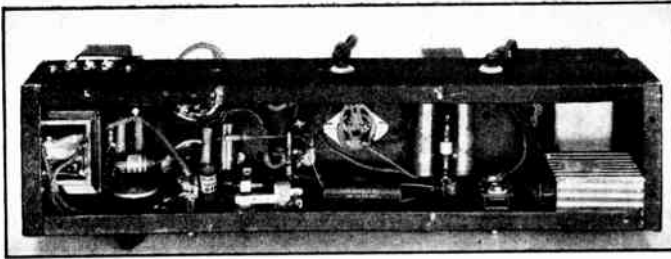


Fig. 1402 — The below-chassis wiring is visible in this view of the 10-watt modulator. The microphone input leads are kept short to reduce hum pick-up.

first 6A6 is used as the input amplifier for a crystal microphone, the other half being a second speech-amplifier stage. Carbon microphones, which need less gain, are transformer-coupled to the second section of the first 6A6. The type of jack shown at J_2 in the circuit diagram must be installed if a double-button carbon microphone is to be used. J_2 may be the same as J_1 if a single-button microphone is to be used exclusively.

The gain control is connected in the grid circuit of the second section of the first 6A6 tube, which is resistance-coupled to the driver. The driver tube, also a 6A6, has its two sections connected in parallel.

The modulation transformer specified is designed to work between 6A6 plates and a 6500-ohm load; the impedance ratio used will, of course, depend on the load into which the modulator will work. A milliammeter can be connected across the shunt resistor, R_{11} , provided to measure the Class-B plate current.

The power supply is of the condenser-input type. Using the components specified, it will

deliver 350 volts at 90 ma. A switch in the transformer center-tap lead is used for turning the plate voltage on and off without affecting the filament supply.

The power transformer is submounted at the left-hand end of the chassis. Next to it is the filter choke, L_1 , followed by the rectifier tube and T_3 , the modulation output transformer. The driver

tube is at the extreme right-hand end, with T_2 , the driver transformer, behind it. The Class-B tube is to the rear and in line with the speech-amplifier tube. For convenience in wiring, the audio tube sockets should be mounted with the filament prongs facing the right-hand end of the chassis.

The plate-voltage switch is on the front of the chassis toward the left in Fig. 1401. The microphone switch, gain control and microphone jacks are grouped at the right. Power input and output terminals are at the rear.

The bottom-view photograph, Fig. 1402, shows the layout for the components mounted below the chassis. T_1 is mounted at the left end. Wiring to the driver tube socket and the transformer secondary winding should be completed before the transformer is bolted in place, since it is difficult to reach the connecting points with a soldering iron afterwards. Short leads between the gain control, the microphone switch and the tube socket can be obtained by making the gain-control contacts face toward the switch, as shown in the photograph.

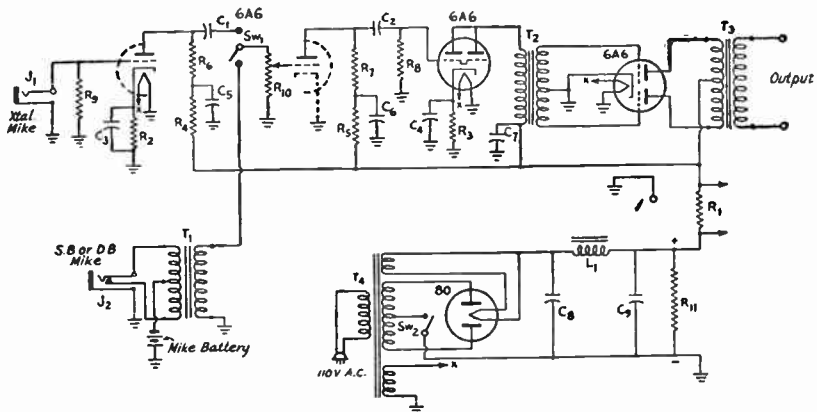


Fig. 1403 — Circuit diagram of the complete 10-watt Class-B audio modulator system for low-power transmitters.

- C_1, C_2 — 0.1- μ fd. 600-volt paper.
- C_3, C_4 — 10- μ fd. 50-volt electrolytic.
- C_5, C_6, C_7, C_8, C_9 — 8- μ fd. 450-volt electrolytic.
- R_1 — 25 ohms, $\frac{1}{2}$ -watt.
- R_2, R_3 — 900 ohms, 1-watt.
- R_4, R_5 — 50,000 ohms, $\frac{1}{2}$ -watt.
- R_6, R_7 — 0.25 megohm, $\frac{1}{2}$ -watt.
- R_8 — 1 megohm, $\frac{1}{2}$ -watt.
- R_9 — 5 megohms, $\frac{1}{2}$ -watt.
- R_{10} — 500,000-ohm volume control.
- R_{11} — 25,000 ohms, 10-watt.
- Sw1 — S.p.d.t. toggle switch.
- Sw2 — S.p.s.t. toggle switch (see text).
- J_1 — Closed-circuit jack for crystal microphone.
- J_2 — 2- or 3-circuit jack for single-button or double-button carbon microphone.
- T_1 — S.b. or d.b. microphone transformer (Stancor A-4351).
- T_2 — Driver transformer, parallel 6A6 plates to 6A6 Class-B (Stancor A-4216).
- T_3 — Output transformer, 6A6 Class-B to 6500-ohm load (Stancor A-3845).
- T_4 — Power transformer, 700-0-700 volts, 90 ma.; 5 volts at 3 amperes; 6.3 volts at 3.5 amperes.
- L_1 — Filter choke, 5 henrys, 200 ma., 80 ohms (Thorlarsen T-67C49).

The compact microphone battery (Burgess type 3A2) will be held securely in place without brackets or clips if it is wedged in between the bottom of the power transformer and the lips on the bottom of the chassis. A 3-volt battery is sufficient for most carbon microphones, and low current frequently will give better speech quality. The 115-volt a.c. and the meter leads (rubber-covered lamp cord) enter the chassis through rubber grommets. A three-contact terminal strip is located at the right end of the base (left end in the bottom view). One of the contacts on this terminal strip is for an external ground connection and the other two are connected to the modulation-transformer output winding.

The actual measured power output of the unit shown in the photographs is 11 watts, as recorded at the point where distortion just begins to be noticeable. This order of audio power output is ample for modulating a low-power transmitter operating with 20 watts or so input to the final stage.

□ A 20-Watt Speech Amplifier or Modulator

The amplifier shown in Figs. 1404-1406 will deliver audio power outputs up to 20 watts (from the output transformer secondary) with ample gain for ordinary communications-type crystal microphones. Class-AB 6L6s are used in the output stage, preceded by a 6J5 and a 6J7 preamplifier.

The unit is built up on a 5 × 10 × 3-inch chassis, with the parts arranged as shown in the photographs. About the only constructional precaution necessary is to use a short lead from the microphone socket (a jack may be used instead of the screw-on type, if desired), and to shield thoroughly the input circuit to the grid of the 6J7. This shielding is necessary to reduce hum. In this amplifier, the 6J7 grid resistor, R_1 , is enclosed along with the input jack in a National type J-1 jack shield,

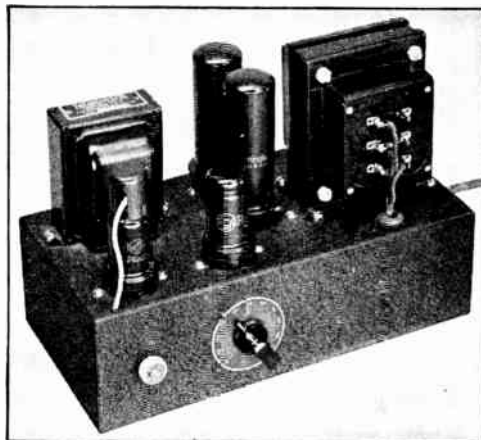


Fig. 1404—A low-cost speech-amplifier or low-power modulator unit with a maximum audio output of 20 watts. The 6J7 is at the left near corner of the chassis, with the 6J5 to its right, just above the volume control.

and a shielded lead is run from the jack shield to the grid of the 6J7. A metal slip-on shield covers the grid cap of the tube.

To realize maximum power output, the "B" supply should be capable of delivering about 145 ma. at 360 volts. A condenser-input supply of ordinary design (Chapter Eight) may be used, since the variation in plate current is relatively small. The current is approximately 120 ma. with no input signal and 145 ma. at full output. If an output of 12 or 13 watts will be sufficient, R_9 and R_{10} may be omitted and all tubes fed directly from a "B" supply giving 270 volts at approximately 175 ma.

The output transformer shown is a universal modulation type suitable for coupling into the plate circuit of a low-power r.f. amplifier (input 40 watts maximum for 100 per cent modulation) for plate modulation. For cathode modulation, the r.f. input power that can be modulated can be determined from the data in

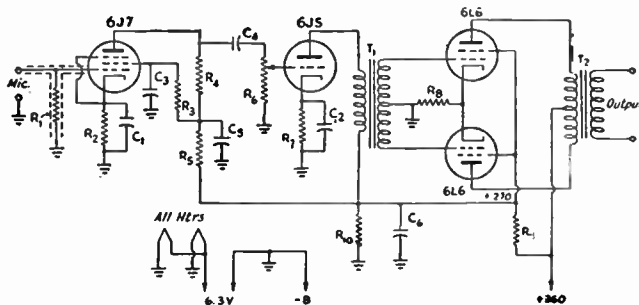


Fig. 1405—Circuit diagram of the low-cost speech amplifier or modulator capable of power outputs up to 20 watts.

- C_1, C_2 —20- μ fd. 50-volt electrolytic.
- C_3 —0.1- μ fd. 200-volt paper.
- C_4 —0.01- μ fd. 400-volt paper.
- C_5, C_6 —8- μ fd. 450-volt electrolytic.
- R_1 —5 megohms, $\frac{1}{2}$ -watt.
- R_2 —1300 ohms, $\frac{1}{2}$ -watt.
- R_3 —1.5 megohms, $\frac{1}{2}$ -watt.
- R_4 —0.25 megohm, $\frac{1}{2}$ -watt.
- R_5 —50,000 ohms, $\frac{1}{2}$ -watt.
- R_6 —1-megohm volume control.
- R_7 —1500 ohms, 1-watt.
- R_8 —250 ohms, 10-watt.
- R_9 —2000 ohms, 10-watt.
- R_{10} —20,000 ohms, 25-watt.
- T_1 —Interstage audio transformer, single plate to p.p. grids, ratio 3:1 (Thordarson T-57A41).
- T_2 —Output transformer, type depending on requirements. A multi-tap modulation transformer (Thordarson T-19M14) is shown.

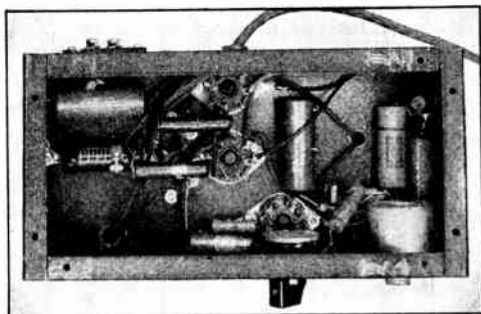


Fig. 1406 — Bottom view of the 20-watt speech amplifier or modulator chassis. The most important constructional point is complete shielding of the microphone input circuit up to the grid of the 6J7 first amplifier.

Chapter Five. The amplifier may also be used for grid-bias modulation with the transformer specified. If the unit is to be used to drive a Class-B modulator, it is recommended that the Class-B tubes be of the zero-bias type rather than a type requiring fixed bias. A suitable output transformer must be substituted for this purpose; data may be found in transformer manufacturers' catalogs.

The frequency response of the amplifier is ample for the range of frequencies encountered in voice communication. It may be extended for high-quality reproduction of music by using higher-priced audio transformers.

◀ A 40-Watt Output Speech Amplifier or Modulator

The 40-watt amplifier shown in Figs 1407-1409 resembles in many respects the 20-watt amplifier just described. The first two stages are, in fact, identical in circuit and construc-

tion. To obtain the higher output, however, it is necessary to drive the 6L6s into the grid-current region (Class-AB₂ operation), so that a driver stage capable of furnishing sufficient power is required. A pair of transformer-coupled 6J5s in push-pull is used for this purpose, inserted between the single 6J5 stage and the push-pull 6L6s. Decoupling is provided (R_9 and C_5) to prevent motorboating because of the higher over-all gain of the amplifier.

A $6 \times 14 \times 3$ -inch chassis is used for the 40-watt amplifier. The photographs show the arrangement of parts. As in the case of the 20-watt unit, complete shielding of the microphone input circuit is essential. The amplifier has ample gain for crystal microphones.

This unit may be used to plate-modulate 80 watts input to an r.f. amplifier. For cathode modulation, the input that can be modulated will depend upon the type of operation chosen.

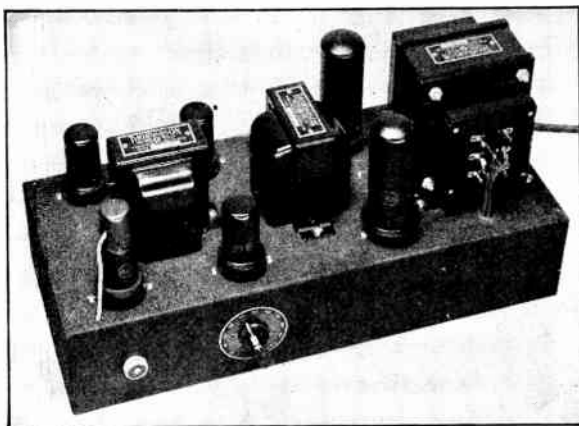


Fig. 1407 — A 40-watt speech amplifier or modulator of inexpensive construction. The 6J7 and first 6J5 are at the front, near the microphone socket and volume control, respectively. T_1 is behind them, and the push-pull 6J5s are at the rear of the chassis behind T_1 . T_2 , in the center, the push-pull 6L6s, and T_3 follow in order to the right.

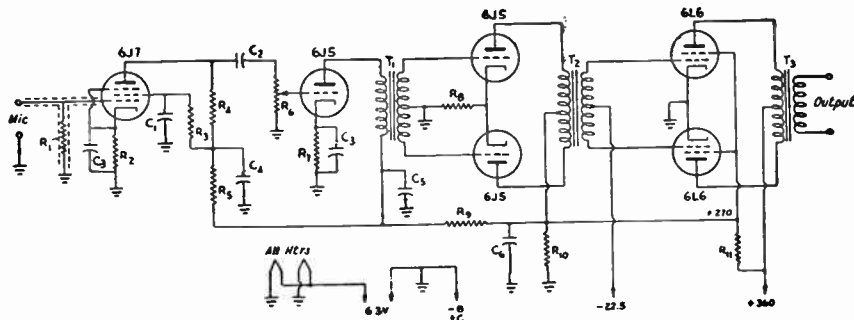


Fig. 1408 — Circuit diagram of the Class AB₂ push-pull 6L6 40-watt output speech amplifier or modulator.

C_1 — 0.1- μ fd. 200-volt paper.

C_2 — 0.01- μ fd. 400-volt paper.

C_3 — 20- μ fd. 50-volt electrolytic.

C_4, C_5, C_6 — 8- μ fd. 450-volt electrolytic.

R_1 — 5 megohms, $\frac{1}{2}$ -watt.

R_2 — 1300 ohms, $\frac{1}{2}$ -watt.

R_3 — 1.5 megohm, $\frac{1}{2}$ -watt.

R_4 — 0.25 megohm, $\frac{1}{2}$ -watt.

R_5 — 50,000 ohms, $\frac{1}{2}$ -watt.

R_6 — 1-megohm volume control.

R_7 — 1500 ohms, 1-watt.

R_8 — 750 ohms, 1-watt.

R_9 — 12,000 ohms, 1-watt.

R_{10} — 20,000 ohms, 25-watt.

R_{11} — 1500 ohms, 10-watt.

T_1 — Interstage audio, single plate to p.p. grids, 3:1 ratio

(Thordarson T-57A41).

T_2 — Driver transformer, p.p. 6J5s to 6L6s Class AB₂ (Thordarson T-84D59).

T_3 — Output transformer, type depending on requirements. A multi-tap modulation transformer (Thordarson T-19M15) is shown.

as described in Chapter Five; with 55 per cent plate efficiency in the r.f. stage, for instance, the input may be of the order of 200 watts, making an allowance for the small amount of audio power taken by the grid circuit.

A high-power Class-B modulator can be driven by the unit; data on suitable modulator tubes are given later in this chapter. Zero-bias tubes should be used, because they present a more constant load to the 6L6s than do relatively low amplification-factor tubes which require fixed bias for Class-B operation. A suitable Class-B driver transformer should be substituted for the universal modulation transformer shown.

The power supply should have good voltage regulation, since the total "B" current varies from approximately 140 ma. with no signal to 265 ma. at full output. A heavy-duty choke-input plate supply should be used; general design data will be found in Chapter Eight. The heater requirements are 6.3 volts at 3 amperes. Bias for the 6L6 stage is most conveniently supplied by a 22.5-volt "B" battery block; a small-sized unit will be satisfactory, since no current is drawn.

Ⓒ A Push-Pull 2A3 Amplifier with Volume Compression

Ideally, a Class-B modulator should be driven by an amplifier having exceptionally good voltage regulation, to minimize distortion (see Chapter Five). For average amateur work, the 6L6 amplifiers just described will give entirely satisfactory results as drivers for Class-B stages when operated well within their capabilities, especially with zero-bias Class-B tubes. However, somewhat better performance can be secured by using triode drivers, especially when the grid power requirements of the Class-B stage are modest enough to make the use of triodes such as the 2A3 practicable.

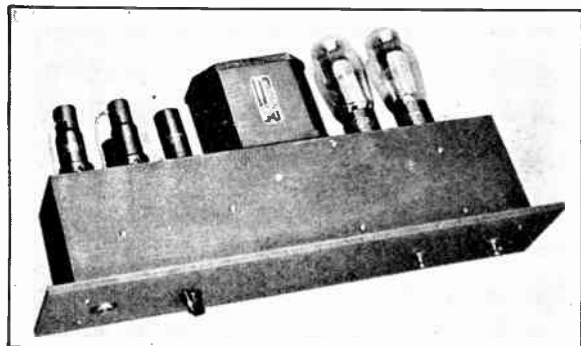


Fig. 1410 — A push-pull 2A3 speech amplifier having an output of approximately 6 watts. A volume-compression circuit is included.

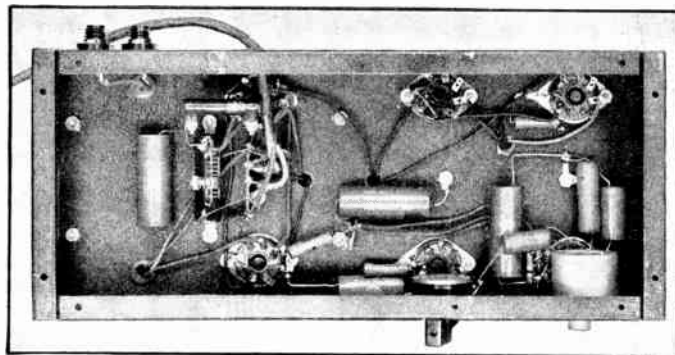


Fig. 1409 — Underneath the chassis of the 40-watt speech amplifier-modulator

The amplifier shown in Figs. 1410-1412, inclusive, has an output (from the transformer secondary) of 6 watts with negligible distortion, and thus is suitable for driving Class-B stages of 100 to 250 watts output.

The amplifier also incorporates an automatic volume-compression circuit to maintain a high average percentage of modulation (Chapter Five). This feature is of considerable value in practical communications work where interference conditions require maximum carrier power level to transmit intelligence successfully. Volume compression overcomes to some extent the general tendency of even the best operators to accentuate or otherwise vary the syllabic intensity. This is particularly true when talking close to the microphone, under which conditions slight movements of the head will cause a change in the modulation level.

A practical audio volume compression circuit functions much like the r.f. automatic gain control familiarly employed in superheterodyne receivers (§7-13).

In Fig. 1412, the side amplifier and rectifier, combined in the 6SQ7 tube, rectifies a portion of the voice current. The rectified output of this circuit is filtered and applied to the Nos. 1 and 3 grids of a pentagrid amplifier tube, thereby varying its gain in inverse proportion to the signal strength. With proper adjustment, an average increase in modulation level of about 7 db. can be secured without exceeding 100 per cent modulation on peaks.

The amplifier proper consists of a 6J7 first stage followed by a 6L7 amplifier-compressor. The 2A3 grids are driven by a 6N7 self-balancing phase inverter. The operation of the 2A3s is purely Class A, without grid current.

The amount of compression is controlled by the potentiometer, R_{20} , in the grid circuit of the 6SQ7. A switch, S_1 , is provided to short-circuit the rectified output of the compressor when normal amplification is required.

The construction of the amplifier resembles that of the unit shown in

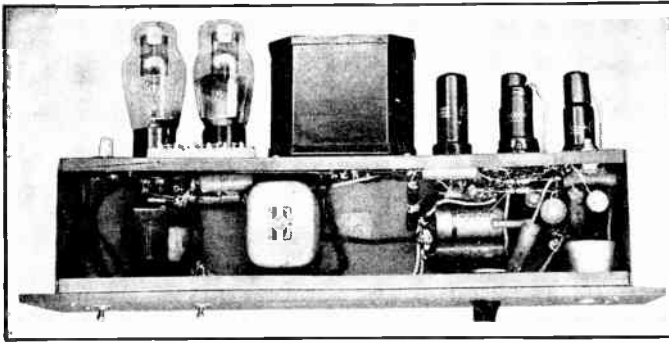


Fig. 1411 — Bottom view of the push-pull Class-A 2A3 speech amplifier with automatic volume compression. The circuit diagram is shown in Fig. 1412.

Fig. 1401, the tubes and output transformer being mounted on the rear edge of a 17 × 4 × 3-inch chassis to save panel height in relay-rack mounting. Looking at the amplifier from the front, the 6J7 first amplifier is in the upper left corner, with the 6L7 to its right. The 6N7 is below the 6L7. The 6N7 is followed by the output transformer, the latter being placed in the middle of the chassis in order to assist in distributing the weight evenly. The 2A3 tubes and the power-supply and audio output terminals are at the right with the 115-volt male plug for filament power at the extreme end.

In the underneath view the input circuit is at the left, the grid resistor, R_1 , and the microphone connector socket being shielded to minimize hum pick-up by the National JS-1 jack shield. The lead to the 6J7 grid is shielded, as are also the top caps of this tube and the 6L7. The volume compressor control, R_{20} , is mounted beside the 6J7, and is screwdriver adjusted; a midget control should be used, since the space is rather limited. The other parts are mounted

as close as possible to the points in the circuit to which they connect. The filament transformers should be kept well separated from the wiring in the low-level stages, particularly that of the microphone input and the low-level grid circuits.

Adjustment of the compressor control is rather critical. First set R_{20} at zero and adjust the gain control, R_6 , for full modulation with the particular microphone used. Then advance the compressor control until the amplifier just "cuts off" (output decreasing to a low value) on peaks; when this point is reached, back off the compressor control until the cut-off effect is gone but an obvious decrease in gain follows each peak.

Because of the necessity for filtering out the audio-frequency component in the rectifier output, there will be a slight delay (amounting to a fraction of a second) before the decrease in gain "catches up" with the peak. This is caused by the time constant of the circuit, and so is unavoidable.

When a satisfactory setting is secured, as indicated by good speech quality with a definite reduction in gain on peaks, the gain control, R_6 , should be advanced to give full output with normal operation. Too much volume compression, indicated by the cut-off effect following each peak, is definitely undesirable, and the object of adjustment of the compressor control should be to use as much compression as possible without danger of over-compression.

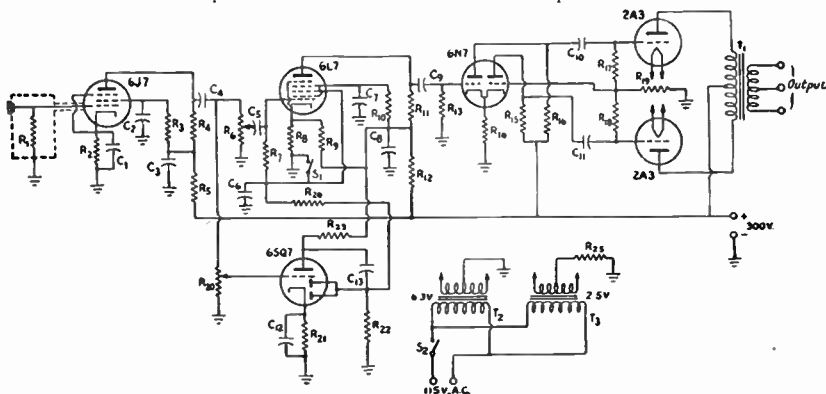


Fig. 1412 — Circuit diagram of the Class-A 2A3 volume-compression speech amplifier.

- | | | |
|--|--|---|
| C_1, C_{12} — 10- μ fd. 50-volt electrolytic. | $R_4, R_{13}, R_{22}, R_{24}$ — 0.5 megohm, $\frac{1}{2}$ -watt. | R_{17}, R_{18}, R_{19} — 0.25 megohm, $\frac{1}{2}$ -watt. |
| $C_2, C_4, C_5, C_6, C_9, C_{10}, C_{11}, C_{13}$ — 0.1- μ fd. 400-volt paper. | R_5 — 50,000 ohms, $\frac{1}{2}$ -watt. | R_{21} — 5000 ohms, $\frac{1}{2}$ -watt. |
| C_3, C_8 — 8- μ fd. 450-volt electrolytic. | R_6, R_{20} — 0.5-megohm variable. | R_{25} — 750 ohms, 10-watt. |
| C_7 — 0.5- μ fd. 400-volt paper. | R_9 — 0.25 megohm, 1-watt. | T_1 — Output transformer to match pp. 2A3s to Class-B grids. (UTC PA-53AX). |
| R_1 — 5 megohms, $\frac{1}{2}$ -watt. | R_{10}, R_{11}, R_{23} — 0.1 megohm, $\frac{1}{2}$ -watt. | T_2 — Filament transformer, 6.3 volts, 2 amperes. |
| R_2, R_8 — 1200 ohms, $\frac{1}{2}$ -watt. | R_{12} — 10,000 ohms, $\frac{1}{2}$ -watt. | T_3 — Filament transformer, 2.5 volts, 5 amperes. |
| R_3, R_7 — 2 megohms, $\frac{1}{2}$ -watt. | R_{14} — 1500 ohms, $\frac{1}{2}$ -watt. | |
| | R_{15}, R_{16} — 0.1 megohm, 1-watt. | |

TABLE I — RESISTANCE-COUPLED VOLTAGE AMPLIFIER DATA

Data are given for a plate-supply of 300 volts, departures of as much as 50 per cent from this supply voltage will not materially change the operating conditions or the voltage gain, but the output voltage will be in proportion to the new voltage. Voltage gain is measured at 400 cycles; condenser values given are based on 100-cycle cut-off. For increased low-frequency response, all condensers may be made larger than specified (cut-off frequency in inverse proportion to condenser values provided all are changed in the same proportion). A variation of 10 per cent in the values given has negligible effect on the performance.
 High-frequency cut-off with pentodes is approximately 20,000 cycles with a plate resistor of 0.1 megohm, 10,000 cycles with 0.25 megohm, and 5000 cycles with 0.5 megohm. With triode amplifiers, the high-frequency cut-off is well above the audio range.

	Plate Resistor Megohms	Next-Stage Grid Resistor Megohms	Screen Resistor Megohms	Cathode Resistor Ohms	Screen By-pass μ fd.	Cathode By-pass μ fd.	Blocking Condenser μ fd.	Output Volts (Peak) ²	Voltage Gain ³
6A6, 6N7 53	0.1	0.1	—	1150 ¹	—	—	0.03	60	20
		0.25	—	1500 ¹	—	—	0.015	83	22
		0.5	—	1750 ¹	—	—	0.007	86	23
	0.25	0.25	—	2650 ¹	—	—	0.015	75	23
		0.5	—	3400 ¹	—	—	0.0055	87	24
		1.0	—	4000 ¹	—	—	0.003	100	24
0.5	0.5	—	4850 ¹	—	—	0.0055	76	23	
	1.0	—	6100 ¹	—	—	0.003	94	24	
	2.0	—	7150 ¹	—	—	0.0015	104	24	
6C5 (also 6J7, 6C6, 57, 6W7, 7C7 as triodes) ⁴	0.05	0.05	—	9100	—	3.16	0.075	57	11
		0.1	—	2600	—	2.3	0.04	70	11
		0.25	—	3100	—	2.2	0.015	83	12
	0.1	0.1	—	3800	—	1.7	0.035	65	12
		0.25	—	5300	—	1.3	0.015	84	13
		0.5	—	6000	—	1.17	0.008	88	13
0.25	0.25	—	9600	—	0.9	0.015	73	13	
	0.5	—	12,300	—	0.59	0.008	85	14	
	1.0	—	14,000	—	0.37	0.003	97	14	
6C6, 6J7, 6W7, 7C7, 57 (pentode)	0.1	0.1	0.44	500	0.07	8.5	0.02	55	61
		0.25	0.5	450	0.07	8.3	0.01	81	82
		0.5	0.53	600	0.06	8.0	0.006	96	94
	0.25	0.25	1.18	1100	0.04	5.5	0.008	81	104
		0.5	1.18	1200	0.04	5.4	0.005	104	140
		1.0	1.45	1300	0.05	5.8	0.005	110	185
0.5	0.5	2.45	1700	0.04	4.2	0.005	75	161	
	1.0	2.9	2900	0.04	4.1	0.003	97	350	
	2.0	2.95	2300	0.04	4.0	0.0025	100	240	
6C8G (one triode unit)	0.1	0.1	—	2120	—	3.93	0.037	55	22
		0.25	—	2840	—	2.01	0.013	73	23
		0.5	—	3250	—	1.79	0.007	80	25
	0.25	0.25	—	4750	—	1.29	0.013	64	25
		0.5	—	6100	—	0.96	0.0065	80	26
		1.0	—	7100	—	0.77	0.004	90	27
0.5	0.5	—	9000	—	0.67	0.007	67	27	
	1.0	—	11,500	—	0.48	0.004	83	27	
	2.0	—	14,500	—	0.37	0.002	96	28	
6F5, 6SF5, 7B4	0.1	0.1	—	1300	—	5.0	0.025	33	42
		0.25	—	1600	—	3.7	0.01	43	49
		0.5	—	1700	—	3.2	0.006	48	52
	0.25	0.25	—	2600	—	2.5	0.01	41	56
		0.5	—	3200	—	2.1	0.007	54	63
		1.0	—	3500	—	2.0	0.004	63	67
0.5	0.5	—	4500	—	1.5	0.006	50	65	
	1.0	—	5400	—	1.2	0.004	62	70	
	2.0	—	6100	—	0.93	0.002	70	70	
6F8G (one triode unit), 6J5, 6J5G, 7A4, 7N7	0.05	0.05	—	1020	—	3.56	0.06	41	13
		0.1	—	1270	—	2.96	0.034	51	14
		0.25	—	1500	—	2.15	0.012	60	14
	0.1	0.1	—	1900	—	2.31	0.035	43	14
		0.25	—	2440	—	1.42	0.0125	56	14
		0.5	—	2700	—	1.2	0.0065	64	14
0.25	0.25	—	4590	—	0.87	0.013	46	14	
	0.5	—	5770	—	0.64	0.0075	57	14	
	1.0	—	6950	—	0.54	0.004	64	14	
6L5G	0.05	0.05	—	1740	—	2.91	0.06	56	11 ⁵
		0.1	—	2160	—	2.18	0.032	68	12 ⁵
		0.25	—	2600	—	1.82	0.015	79	12 ⁵
	0.1	0.1	—	3070	—	1.64	0.032	60	12 ⁵
		0.25	—	4140	—	1.1	0.014	79	13 ⁵
		0.5	—	4700	—	0.81	0.0075	89	13 ⁵
0.25	0.25	—	6900	—	0.57	0.013	64	13 ⁵	
	0.5	—	9100	—	0.46	0.0075	80	13 ⁵	
	1.0	—	10,750	—	0.4	0.005	88	13 ⁵	

¹ Value for both triode sections, assuming both are working under same conditions. In phase inverter service, the cathode resistor should not be by-passed.

² Voltage across next-stage grid resistor at grid-current point.

³ At 5 volts r.m.s. output.

⁴ Screen and suppressor tied to plate

⁵ At 4 volts r.m.s. output.

TABLE I—RESISTANCE-COUPLED VOLTAGE AMPLIFIER DATA—Continued

	Plate Resistor Megohms	Next-Stage Grid Resistor Megohms	Screen Resistor Megohms	Cathode Resistor Ohms	Screen By-pass μ f.	Cathode By-pass μ f.	Blocking Condenser μ f.	Output Volts (Peak) ²	Voltage Gain ¹
6R7, 6R7G, 7E6	0.05	0.05	—	1600	—	2.6	0.055	50	9
		0.1	—	2000	—	2.0	0.03	62	9
		0.25	—	2400	—	1.6	0.015	71	10
	0.1	0.1	—	2900	—	1.4	0.03	52	10
		0.25	—	3800	—	1.1	0.015	68	10
		0.5	—	4400	—	1.0	0.007	71	10
0.25	0.25	—	6300	—	0.7	0.015	54	10	
	0.5	—	8400	—	0.5	0.007	62	11	
	1.0	—	10,600	—	0.44	0.004	74	11	
6S7	0.1	0.1	0.59	430	0.077	8.5	0.0167	57	57 ⁵
		0.25	0.67	440	0.071	8.0	0.01	73	78 ⁵
		0.5	0.71	440	0.071	8.0	0.0066	82	89 ⁵
	0.25	0.25	1.7	620	0.058	6.0	0.0071	54	98 ⁵
		0.5	1.95	650	0.057	5.8	0.005	66	122 ⁵
		1.0	2.1	700	0.055	5.2	0.0036	76	136 ⁵
0.5	0.5	3.6	1000	0.04	4.1	0.0037	58	136 ⁵	
	1.0	3.9	1080	0.041	3.9	0.0029	66	162 ⁵	
	2.0	4.1	1120	0.043	3.8	0.0023	73	174 ⁵	
6SC7	0.1	0.1	—	750 ¹	—	—	0.033	35	39
		0.25	—	930 ¹	—	—	0.014	50	34
		0.5	—	1040 ¹	—	—	0.007	54	36
	0.25	0.25	—	1400 ¹	—	—	0.012	45	39
		0.5	—	1680 ¹	—	—	0.006	55	42
		1.0	—	1840 ¹	—	—	0.003	64	45
0.5	0.5	—	2330 ¹	—	—	0.006	50	45	
	1.0	—	2980 ¹	—	—	0.003	62	48	
	2.0	—	3280 ¹	—	—	0.002	72	48	
6SJ7	0.1	0.1	0.35	500	0.10	11.6	0.019	72	67
		0.25	0.37	530	0.09	10.9	0.016	96	98
		0.5	0.47	590	0.09	9.9	0.007	101	104
	0.25	0.25	0.89	850	0.07	8.5	0.011	79	139
		0.5	1.10	860	0.06	7.4	0.004	88	167
		1.0	1.18	910	0.06	6.9	0.003	98	185
0.5	0.5	2.0	1300	0.06	6.0	0.004	64	200	
	1.0	2.2	1410	0.05	5.8	0.002	79	238	
	2.0	2.5	1530	0.04	5.2	0.0015	89	263	
6SQ7, 686G, 7B6, 2A6, 75	0.1	0.1	—	1900	—	4.0	0.03	31	31
		0.25	—	2200	—	3.5	0.015	41	39
		0.5	—	2300	—	3.0	0.007	45	42
	0.25	0.25	—	3300	—	2.7	0.015	42	48
		0.5	—	3900	—	2.0	0.007	51	53
		1.0	—	4200	—	1.8	0.004	60	56
0.5	0.5	—	5300	—	1.6	0.007	47	58	
	1.0	—	6100	—	1.3	0.004	62	60	
	2.0	—	7000	—	1.2	0.002	67	63	
6T7G	0.1	0.1	—	1950	—	2.85	0.0245	44	27 ⁵
		0.25	—	2400	—	2.55	0.0135	58	32 ⁵
		0.5	—	2640	—	2.25	0.008	64	33 ⁵
	0.25	0.25	—	3760	—	1.57	0.012	57	37 ⁵
		0.5	—	4580	—	1.35	0.0075	69	40 ⁵
		1.0	—	5220	—	1.23	0.005	80	41 ⁵
0.5	0.5	—	6570	—	1.02	0.008	62	42 ⁵	
	1.0	—	8200	—	0.82	0.0055	77	43 ⁵	
	2.0	—	9600	—	0.70	0.004	86	44 ⁵	
56, 76	0.05	0.05	—	2400	—	2.8	0.08	65	8.3
		0.1	—	3100	—	2.2	0.045	80	8.9
		0.25	—	3800	—	1.8	0.02	95	9.4
	0.1	0.1	—	4500	—	1.6	0.04	74	9.5
		0.25	—	6400	—	1.2	0.02	95	10.0
		0.5	—	7500	—	0.98	0.009	104	10.0
0.25	0.25	—	11,100	—	0.69	0.02	82	10.0	
	0.5	—	15,200	—	0.5	0.009	96	10.0	
	1.0	—	18,300	—	0.4	0.005	108	10.0	

¹ Value for both triode sections, assuming both are working under same conditions. In phase inverter service, the cathode resistor should not be by-passed.

² Voltage across next-stage grid resistor at grid-current point.

³ At 5 volts r.m.s. output.

⁴ Screen and suppressor tied to plate.

⁵ At 4 volts r.m.s. output.

TABLE II—CLASS-B MODULATOR DATA

Class-B Tubes (2)	Fil. Volts	Plate Volts	Grid Volts App.	Peak A.F. Grid-to-Grid Voltage	Zero-Sig. ¹ Plate Current Ma.	Max.-Sig. ¹ Plate Current Ma. ²	Load Res. Plate-to-Plate Ohms	Max.-Sig. Driving Power Watts ³	Max.-Sig. ¹ Power Output Watts ³
RK59 ⁴	6.3	500	-17	64	16	90	15,000	0.9	30
HY60 ⁷	6.3	300	-22.5	63	75	120	5,000	4.0	22
		400	-22.5	57	75	120	6,000	3.0	30
HY65 ⁴	6.3	450	—	—	—	125	—	0.4	34
801-A, 801	7.5	600	-75	320	8	130	10,000	3.0	45
HY31Z ^{4, 5}	6.3	300	0	104	20	100	5,000	1.4	18
HY1231Z ^{4, 6}	12.6	400	0	140	26	150	5,000	2.0	40
		500	0	131	36	150	7,000	1.8	51
815 ⁸	6.3	400	-15	60	22	150	8,000	0.36	42
		500 ⁶	-15	60	20	150	6,200	0.36	54
1624 ⁷	2.5	400	-16.5	77	75	150	6,000	0.4	36
		600	-25	106	42	180	7,500	1.2	72
HY6L6GX ⁷	6.3	400	-25	80	100	230	3,800	0.35	60
		500	-25	80	100	230	4,550	0.6	75
TZ20	7.5	800	0	160	40	136	12,000	1.8	70
HY61 / 807 ⁷	6.3	400	-25	80	100	230	3,800	0.35	60
RK807	6.3	500	-25	80	100	230	4,550	0.6	75
		600	-30	80	60	200	6,600	0.4	80
HY69 ^{7, 7}	6.3	300	-25	106	60	150	4,000	0.25	30
HY1269 ^{7, 7}	12.6	400	-25	145	60	170	4,000	0.4	40
		600	-35	183	65	120	4,500	0.3	65
		500	-25	120	65	200	5,000	0.7	97
RK12	6.3	750	0	129	50	200	9,600	3.4	100
		750	-40	320	26	210	6,400	6.0	90
800	7.5	1000	-55	300	28	160	12,500	4.4	100
		1250	-70	300	30	130	21,000	3.4	106
		600	0	171	18	180	6,000	Note 9	75
HY30Z	6.3	750	0	167	22	180	8,000	"	95
		850	0	171	28	180	10,000	"	110
807 ¹⁰	6.3	400	-25	78	100	240	3,200	0.2	55
1625 ¹⁰	12.6	500	-25	78	100	240	4,240	0.2	75
		600	-30	78	60	200	6,400	0.1	80
		750 ⁶	-32	92	60	240	6,950	0.2	120
HK24	6.3	1000	-29	248	30	150	15,000	4.5	105
		1250	-42	256	24	136	21,200	4.2	120
809	6.3	500	-10	170	40	200	5,200	3.5	60
		750	-25	200	35	200	8,400	4.0	100
		1000 ⁶	-40	230	30	200	12,000	4.2	145
830-B	10	800	-27	250	20	280	6,000	5.0	135
		1000	-35	270	20	280	7,600	6.0	175
HY40Z	7.5	750	0	171	32	225	6,000	Note 9	110
		850	0	185	40	250	7,000	"	155
		1000	0	185	45	250	9,000	"	185
RK31	7.5	1000	0	141	25	230	11,000	3.7	160
808	7.5	1250	0	141	35	220	18,000	4.4	190
		1250	-15	240	40	230	12,700	7.8	190
RK37	7.5	1500	-25	220	30	190	18,300	4.8	185
RK37	7.5	1250	-35	282	25	235	18,000	7.2	200
		1250	0	140	48	200	15,000	3.8	175
811	6.3	1500 ⁶	-9	160	20	200	18,000	4.2	225
35T	5.0 to 5.1	1000	-22	—	—	—	7,200	—	150
		1250	-30	—	—	—	9,600	—	200
		1500	-40	—	—	—	12,800	—	230
TZ40 ⁴	7.5	1000	0	220	—	280	7,350	5.5	175
		1250	- 4.5	269	—	280	10,000	6.0	225
		1500	- 9	265	—	250	12,000	6.0	250
RK52	7.5	1250	0	180	40	300	10,000	7.5	250
203-A	10	1000	-35	310	26	320	6,900	10	200
		1250	-45	330	26	320	9,000	11	260
211	10	1000	-77	380	20	320	6,900	7.5	200
		1250	-100	410	20	320	9,000	8.0	260
838	10	1000	0	200	106	320	6,900	7.0	200
		1250	0	200	148	320	9,000	7.5	260
HK158	12.6	750	-25	300	50	330	4,500	17	155
		1250	-50	280	35	225	12,500	10	200
		2000	-90	340	30	180	3,200	10	265
HK54	5.0	1500	-45	300	40	198	16,800	5.0	200
		2000	-70	360	24	180	36,000	6.0	260
		2500	-85	360	20	150	40,000	5.0	275
HY51Z	7.5	850	0	148	48	300	5,000	Note 9	160
		1000	0	170	60	350	6,000	"	260
		1250	0	155	90	300	10,000	"	285
203-Z	10	1000	0	206	50	350	6,200	6.5	230
		1250	- 4.5	215	60	350	8,000	6.75	300
ZB120	10	1000	0	190	70	310	6,900	5.0	200
		1250	0	180	95	300	9,000	4.0	245
		1500	- 9	196	60	296	11,200	5.0	300

TABLE II — CLASS-B MODULATOR DATA — Continued

Class-B Tubes (2)	Fil. Volts	Plate Volts	Grid Volts App.	Peak A.F. Grid-to-Grid Voltage	Zero-Sig. ¹ Plate Current Ma.	Max.-Sig. ¹ Plate Current Ma. ²	Load Res. Plate-to-Plate Ohms	Max.-Sig. Driving Power Watts ³	Max.-Sig. ¹ Power Output Watts ³	
8005	10	1250	-55	990	40	320	8,000	4.0	250	
		1500 ⁴	-80	310	40	310	2,500	4.0	300	
HF100	10 to 11	1500	-52	264	50	270	12,000	2.0	260	
		1750	-62	324	40	270	16,000	9.0	350	
805 RK57	10	1250	0	235	148	400	6,700	6.0	300	
		1500	-16	280	84	400	8,200	7.0	370	
828 ¹¹	10	1700	-120	240	50	248	16,200	0	300	
		2000	-120	240	50	270	18,300	0	385	
		2000	-80	270	16	80	55,500	0.7	110	
		1500	-55	230	21	94	33,700	0.8	90	
25T	5.0	1000	-30	210	32	120	15,800	1.2	70	
		750	-20	205	43	133	9,200	1.4	50	
		Same as 25T								
3C24	6.3	Same as 25T								
75T	5.0	1000	—	—	—	—	6,800	—	200	
		1500	—	—	—	—	10,000	—	300	
		2000	—	—	—	—	12,500	—	400	
8003	10	1350	-100	480	40	490	6,000	10.5	460	
		Bias adjusted for maximum rated plate dissipation under no-signal conditions. Zero bias up to 1250 v. plate							16,000	380
100TH	5.0 to 5.1	2000					22,000	May be driven by push-pull 6L6s	460	
		2500					30,000		500	
		3000								
HD203-A	10	1500	-40	—	36	425	8,000	Note 12	400	
		1750	-67	—	36	425	9,000		500	
HK254	5.0	2000	-65	400	50	260	16,000	7.0	328	
		2500	-80	420	50	248	22,000	7.0	418	
		3000	-100	456	40	240	30,000	7.0	520	
810	10	1500	-30	345	80	500	6,600	12	510	
1627	5.0	2000	-50	345	60	420	11,000	10	590	

¹ Values are for both tubes.
² Sinusoidal signal values; speech values are approximately one-half for tubes biased to approximate cut-off and 80 per cent for zero-bias tubes.
³ Values do not include transformer losses. Somewhat higher power is required of the driver to supply losses and provide good regulation. Input transformer ratios must be chosen to supply required power at specified grid-to-grid voltage with ample reserve for losses and low distortion levels. Driver stage should have good regulation.
⁴ Dual tube. Values are for one tube, both sections.
⁵ Instant-heating filament type.
⁶ Intermittent amateur and commercial service rating.
⁷ Beam tube. Class AB. Screen voltage: 300.
⁸ Beam tube. Class AB. Screen voltage: 125 at 32 ma.
⁹ Driver: one or two 45s at 275 volts, self-biased (-55 volts).
¹⁰ Beam Tube. Class AB. Screen voltage: 300 at 10 ma. Effective grid circuit resistance should not exceed 500 ohms.
¹¹ Pentode. Class AB. Suppressor voltage: 60 at 9 ma. Screen voltage: 750, 4/43 ma. at 1700 plate volts, 2/60 ma. at 2000.
¹² Can be driven by a pair of 2A3s in push-pull Class AB at 300 volts with fixed bias.

Class-B Modulators

Class-B modulator circuits are practically identical no matter what the power output of the modulator. The diagrams of Fig. 1313 therefore will serve for any modulator of this type that the amateur may elect to build. The triode circuit is given at A and the circuit for tetrodes at B. When small tubes with indirectly heated cathodes are used, the cathode should be connected to ground.

Design considerations for Class-B stages are discussed in Chapter Five, and data on the performance of various tubes suitable for the purpose are given in the accompanying tables. Once the requisite audio power output has been determined and a pair of tubes capable of giving that output selected, an output transformer should be secured which will permit matching the rated modulator load impedance to the modulating impedance of the r.f. amplifier. Similarly, a driver transformer should be selected which will properly couple the driver stage to the Class-B grids.

The plate power supply for the modulator should have good voltage regulation and must be well filtered. It is particularly important, in the case of a tetrode Class-B stage, that

the screen-voltage power-supply source have excellent regulation, to prevent distortion. The screen voltage should be set as exactly as possible

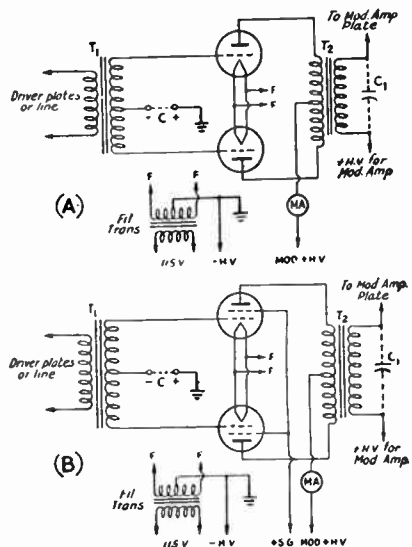


Fig. 1413 — Class-B modulator circuit diagrams. Tubes and circuit considerations are discussed in the text.

ble to the recommended value for the tube.

In estimating the output of the modulator, it should be remembered that the figures given in the tables are for the tube output only, and do not include output-transformer losses. The efficiency of the output transformer will vary with its construction, and may be assumed to be in the vicinity of 80 per cent for the less expensive units and somewhat higher for higher-priced transformers. To be adequate for modulating the transmitter, therefore, the modulator should have a theoretical power capability about 25 per cent greater than the actual power needed for modulation.

The input transformer, T_1 , may couple directly between the driver tube and the modulator grids or may

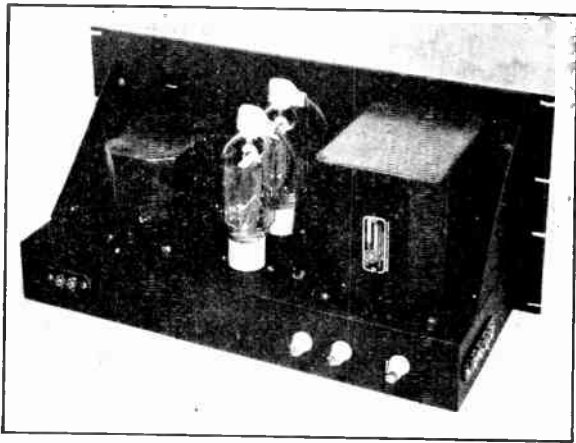


Fig. 1111 — A conventional chassis arrangement for low- and medium-power Class-B modulator stages. The mechanical layout in general follows the typical circuit diagrams given in Fig. 1313.

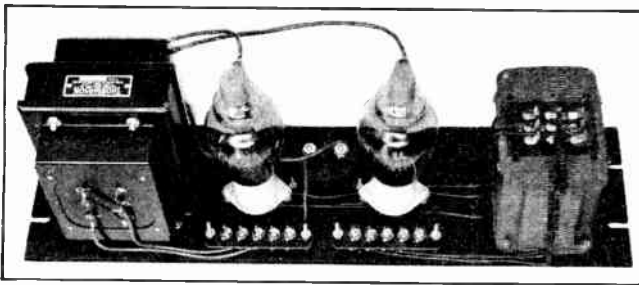


Fig. 1115 — Chassis-less construction for a low-power Class-B modulator. Small tubes and transformers capable of an audio output of the order of 100 watts can be mounted directly on the panel, eliminating the chassis.

be designed to work from a low-impedance (200- or 500-ohm) line. In the latter case, a tube-to-line output transformer must be used at the input to the driver stage. This type of coupling is recommended only when the driver must be at a considerable distance from the modulator, since the second transformer not only introduces additional losses but also further impairs the voltage regulation.

The bias source for the modulator must have very low resistance. Batteries are the most suitable source. In cases where the voltage values are correct, regulator tubes such as the VR75-30, VR105-30, etc., may be connected across a tap on an a.c. bias supply to hold the bias voltage steady under grid-current conditions. Generally, however, zero-bias modulator tubes are preferable, not only because no bias supply is required but also because the loading on the driver stage is less variable and consequently distortion in the driver is reduced.

Condenser C_1 in these diagrams will give a "tone-control" effect and filter

out high-frequency side-bands (splatter) caused by distortion in the modulator or preceding speech-amplifier stages. Values in the neighborhood of 0.002 to 0.005 $\mu\text{fd.}$ are suitable. Its voltage rating should be adequate for the peak voltage across the transformer secondary. The plate by-pass condenser in the modulated amplifier will serve the same purpose.

The photographs illustrate different types of construction which may be used for Class-B modulators. The actual placement of parts in filling the requirements of any given unit is not critical.

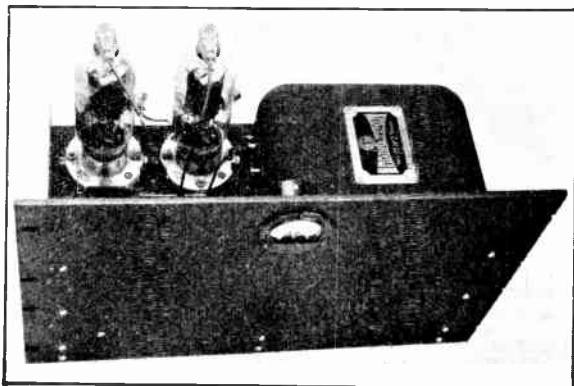


Fig. 1116 — A chassis arrangement for a higher-power Class-B modulator. This unit has the filament transformer for the tubes mounted on the chassis. Where the input transformer is included with the speech amplifier, less chassis space will be needed. The tubes are placed near the rear, where the ventilation is good. The plate milliammeter is provided with a small plate over the adjusting screw, to prevent touching the screw accidentally. A Preswood panel was used for this modulator; with a metal panel, the meter should be mounted behind glass on a well-insulated mount (the meter insulation is not intended for voltages above a few hundred) or connected in the filament center-tap rather than in the high-voltage lead.

V.H.F. Receivers

IN ITS essentials most modern receiving equipment for the 28- and 50-Mc. bands differs very little from that used on lower frequencies. The 28-Mc. band serves as the meeting ground between what are ordinarily termed "communications frequencies" and the very-highs, and it will be found that most of the receivers described in Chapter Twelve are capable of working on 28 Mc. In this chapter are described receivers and converters capable of good performance on 50 Mc. and higher.

Federal regulations impose identical requirements on all frequencies below 54 Mc. respecting stability of frequency and, when amplitude modulation is used, freedom from frequency modulation. Thus receivers for 50-Mc. a.m. reception may have the same selectivity as those designed for the lower frequencies. This order of selectivity is not only possible but desirable, since it permits a considerable increase in the number of transmitters which can work in the band without undue interference. High selectivity also aids greatly

in improving the signal-to-noise ratio, both as concerns noise originating in the receiver itself and in its response to external noise. The effective sensitivity of such a receiver can be made considerably higher than is possible with non-selective receivers.

Receivers for f.m. signals usually are designed with less selectivity, so that they can accommodate the full swing of the transmitter. At least for 28- and 50-Mc. f.m. reception, however, the h.f. oscillator must be as stable as in a narrow-band a.m. receiver.

The superheterodyne system of reception is used almost universally on frequencies below 54 Mc. because it is the only type that fulfills the stability requirements. A.m. superheterodynes and those for f.m. reception differ only in the i.f. amplifier and second detector, so that a single high-frequency converter may be used for either a.m. or f.m.

Superheterodynes for 50 Mc. should have fairly high intermediate frequencies to reduce both image response and oscillator "pulling." For example, a difference between signal and image frequencies of 900 kc. (the difference when the i.f. is 450 kc.) is a very small percentage of the signal frequency; consequently, the response of the r.f. circuits to the image frequency is nearly as great as to the desired signal frequency. To obtain discrimination against the image equal to that obtainable at 3.5 Mc. would require an i.f. 16 times as high, or about 7 Mc. However, the Q of tuned circuits is less at 50 Mc. than it is at the lower frequencies, chiefly because the tube loading is considerably greater, and thus still higher i.f.s are desirable. A practical compromise is reached at about 10 Mc.

To obtain high selectivity with a reasonable number of i.f. stages, the double superheterodyne principle is often employed. A 10-Mc. intermediate frequency, for example, is changed to a second i.f. of perhaps 450 kc. by an additional oscillator-mixer combination.

Few amateurs build complete 50-Mc. superheterodyne receivers. General practice in this band has been to use a conventional communications receiver to handle the i.f. output of a simple 50-Mc. frequency-converter. Even an all-wave broadcast receiver may be used with excellent results on 50 Mc. by the addition of a relatively simple converter.

The simplest type of v.h.f. receiver is the superregenerator, long favored in amateur work. It affords good sensitivity with few tubes and elementary circuits. Its disadvan-

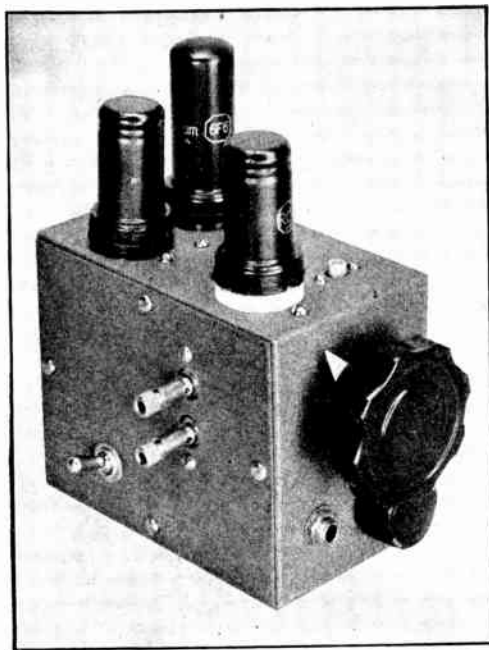


Fig. 1501 — A compact 144-Mc. receiver built in a 3 × 4 × 5-inch metal box. The detector trimming condenser's slotted shaft is on the top, beside the 6J5 detector (front tube). The tuning knob, headphone jack and regeneration control are to be seen in the front, with the "on-off" switch and the antenna terminals on the side.

tages are lack of selectivity and, if the oscillating detector is coupled to an antenna, a tendency to radiate a signal which may cause interference to other receivers. To some extent the lack of selectivity is advantageous, since it increases the chances of hearing a call even though transmitter and receiver may have drifted in frequency between contacts. To reduce radiation, the detector should be operated at the lowest plate voltage that will give satisfactory superregeneration; means for controlling regeneration is essential in any superregenerative receiver.

Although superheterodynes can be built to work successfully on 144 Mc., up to now the superregenerative type of receiver has been much more widely used. The superregenerator has the advantages of low cost and good sensitivity, but its selectivity does not compare with that of the superheterodyne.

From a practical aspect, superregenerative receivers may be divided into two general types. In the first the quenching voltage is developed by the detector tube functioning as a "self-quenched" oscillator. In the second, a separate oscillator tube is used to generate the quench voltage. Self-quenched superregenerators have found wide favor in amateur work. The simpler types are particularly suited for portable equipment, which must be kept as simple as possible. Many amateurs have "pet" circuits claimed to be superior to all others, but the probability is that the arrangement of a particular circuit has led to correct operating conditions. Time spent in minor adjustments will result in a smooth-working receiver.


¶ A Simple Superregenerative Receiver

One variety of simple superregenerative receiver is pictured in Figs. 1501 through 1504. As shown in the wiring diagram, Fig. 1504, a 6J5 superregenerative detector is followed by resistance-coupled 6J5 and 6F6 audio stages. The detector circuit departs from the orthodox in the use of inductive tuning and the resistance coupling to the audio stage.

The receiver is built in a $3 \times 4 \times 5$ -inch metal box, one 3×4 -inch face serving as the "front" panel. The panel controls include the tuning knob and the regeneration control; the headphone jack is also mounted on the panel. The power-cable plug is mounted at the rear of the box, as are the speaker terminals. The "on-off" switch and the antenna terminals are mounted on the left-hand side of the box.

The detector trimmer condenser, C_1 , is mounted on the upper face of the box, so that it can be adjusted from the top of the receiver. The quench-frequency r.f. choke, RFC_2 , is supported from the under side of the upper face of the box by a long screw, with a brass sleeve over the screw furnishing sufficient spacing from the box. This r.f. choke is essential because the resistance-coupled amplifiers afford but slight attenuation of the quench frequency, and the quench voltage otherwise would overload the output audio tube at relatively low signal levels. Where transformer coupling is used between the detector and first audio stage, the transformer serves to keep much of the quench voltage out of the following stages; consequently, the quench-frequency choke may not be necessary.

◆
Fig. 1502 — Inside the small 144-Mc. superregenerative receiver. This left-hand view shows how the tuning-loop assembly, regeneration control and headphone jack are mounted on one of the end panels, and also illustrates the placement of some of the parts not visible in the other views. The power-supply plug and the loud-speaker binding posts may be seen at the rear of the chassis. The side panel which carries the antenna coupling loop and the send-receive switch is shown at the left, partially dismantled.
◆

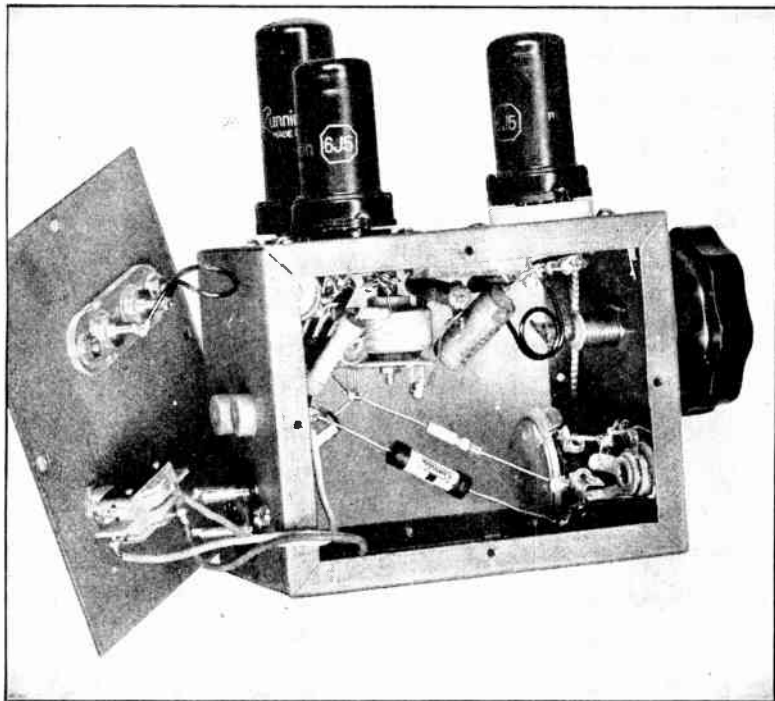

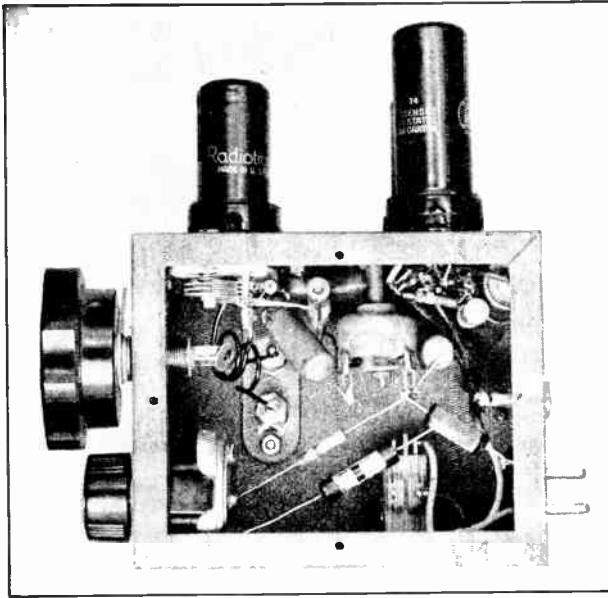


Fig. 1503 — A right-hand side view of the simple 144-Mc. receiver.

A soldering lug under each socket mounting screw furnishes a convenient ground for the components of that stage. All condensers and resistors are mounted directly to socket or other terminals. An exception is the coupling condenser, C_6 , one side of which must be run down to the headphone jack with an extra length of wire. The leads running to the toggle switch should be made of extra-length flexible wire so that the side of the box can be removed without unsoldering the connections. All wiring should be completed before L_1 and L_2 are put in place.

The detector coil is constructed by winding the wire around a $\frac{1}{2}$ -inch diameter drill or dowel, used as a former. After the coil is removed the ends are trimmed and bent until it can be soldered in place in proper alignment with the panel bushing used to support the tuning-loop shaft. The plate lead of the trimmer socket is connected to the rotor of the trimmer


condenser by means of a short length of wire, L_1 being connected to the center of this wire and to the stator connection of the condenser. A length of $\frac{1}{4}$ -inch rod pushed through the shaft bearing will serve as a guide in soldering the coil in place. The axis of the coil should make an angle of 45 degrees with the shaft.

The inductive tuning loop is a small copper washer cemented to the end of a $\frac{1}{4}$ -inch shaft of insulating material (Lucite or bakelite). The copper washer, acting as a single shorted turn, decreases the effective inductance of the coil as it becomes more closely coupled, and consequently tunes the system. The end of the shaft is cut at an angle of 45 degrees to mount the washer at the same angle with respect to the axis of the shaft. Thus 180-degree rotation of the shaft turns the copper washer from a position coaxial with the coil to one at right angles to it. The copper washer is made by drilling a $\frac{1}{8}$ -inch hole in a small piece of sheet copper and then cutting around the hole to form a washer of $7\frac{1}{16}$ -inch outside diameter. The washer is fastened to the angled face of the shaft by Duco cement. Because the copper washer is larger than the shaft, the shaft must be pushed through the panel bearing from the inside of the box. This can be done easily by loosening the panel bearing while sliding the shaft through. A fiber washer should be placed on the shaft before it is pushed through the panel bearing, and later cemented to the shaft to serve as a collar which prevents it from pulling through the bearing.

It is easier to check the performance of the receiver before the tuning loop is added. With the large trimmer condenser specified there should be no difficulty in finding the 144-Mc. band. The trimmer setting will be at about one-tenth capacity if the coil is right. The detector should go into the hiss condition when the re-

Fig. 1504 — Circuit diagram of the compact 144-Mc. superregenerative receiver.

- C_1 — 25- μ fd. air trimmer (Hammarlund APC-25).
 C_2 — 50- μ fd. midget mica.
 C_3, C_4, C_6 — 0.01- μ fd. 600-volt paper.
 C_5, C_7 — 10- μ fd. 25-volt electrolytic.
 C_8 — 8- μ fd. 450-volt electrolytic.
 R_1 — 5 megohms, $\frac{1}{2}$ watt.
 R_2 — 25,000 ohms, $\frac{1}{2}$ watt.
 R_3 — 0.25 megohm, $\frac{1}{2}$ watt.
 R_4 — 1500 ohms, $\frac{1}{2}$ watt.
 R_5 — 50,000-ohm wire-wound potentiometer.
 R_6, R_7 — 50,000 ohms, 1 watt.
 R_8 — 0.1 megohm, $\frac{1}{2}$ watt.
 R_9 — 500 ohms, 1 watt.
 R_{10} — 2000 ohms, 10-watt wire-wound.
 J — Closed-circuit jack.
 SI — S.p.d.t. toggle switch.
 RFC_1 — V.h.f.r.f. choke (Ohmite Z-1).
 RFC_2 — 80-mh. r.f. choke (Meissner 19-2709).

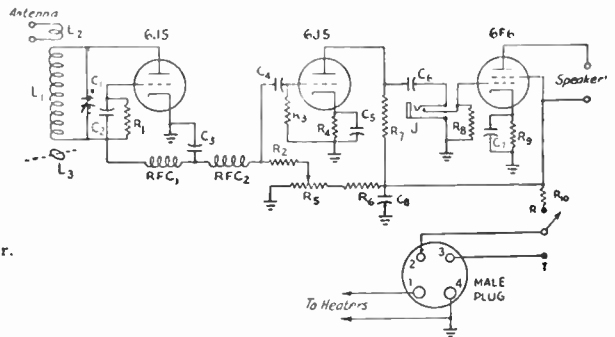

- L_1 — $1\frac{2}{3}$ turns No. 14 e., $\frac{1}{2}$ -inch inside diameter.
 L_2 — $\frac{3}{4}$ turn No. 14 e., $\frac{1}{2}$ -inch inside diameter.
 L_3 — Tuning loop (see text).

generation control is advanced not more than two-thirds of its travel. Several values of capacity should be tried at C_3 , using that which allows the detector to oscillate at minimum regeneration control setting without excessive audio by-passing.

With the receiver working and the tuning loop installed, the tuning range can be adjusted by moving the shaft in its panel bearing to bring the loop nearer to or farther from the coil. Moving the loop closer will increase the tuning range. The tuning rate will be slow with the loop at right angles to the coil and faster as the loop and coil become more nearly coaxial. If the setting is adjusted so the receiver tunes from about 143.5 to 149 Mc., the band will be spread over the major portion of the dial.

Once the shaft position giving the right band spread has been found, the fiber washer is fastened to the shaft with Duco cement. After this is dry, the dial or knob can be attached to the outside end of the shaft. Play of the shaft in the bearing can be cured by slipping two metal washers and a half-slice of rubber grommet on the shaft before the dial is attached. The dial set screw should be tightened with the shaft pushed out from the inside: the rubber grommet then will hold the fiber washer tightly against the inside of the panel bearing.

A paper scale may be glued to the box, with the megacycle and half-megacycle points marked on it for ease in resetting.

The antenna coupling should be adjusted with the antenna connected. It should be as close to L_1 as will permit sufficient margin in the regeneration-control range to take care of low supply voltages and other variables.



Fig. 1506 — A superregenerative receiver with built-in speaker, constructed on a standard chassis base as a cabinet. The detector trimming condenser is mounted on the left end. The audio gain control is at the right of the tuning dial. The regeneration control is between the gain control and the 'phone jack and on-off switch.

A Superregenerative Receiver with Built-In Loudspeaker

The receiver shown in Figs. 1505, 1506 and 1507 is built on a 10 × 5 × 3-inch metal chassis. The tubes and speaker are mounted on one 5 × 10-inch face. One side is used for a panel, the opposite side being left clear in the event it is desired to operate with the receiver resting on this side.

The antenna terminals and the detector padding condenser are mounted on the left-hand end of the chassis, and the four-prong power plug is mounted on the right-hand end. The only care necessary in laying out the chassis is to mount the tuning condenser and the padding condenser so that their respective terminals come close together, to make the

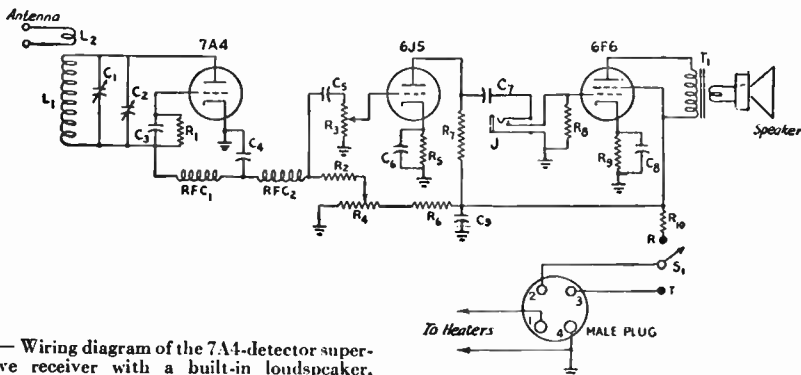


Fig. 1505 — Wiring diagram of the 7A4-detector superregenerative receiver with a built-in loudspeaker.

- C_1 — 25- μ fd. air trimmer (Hammarlund APC-25).
- C_2 — 5- μ fd. midjet variable (National U.M-15 with 2 stator and 2 rotor plates removed).
- C_3 — 50- μ fd. midjet mica.
- C_4 — 0.006- μ fd. mica.
- C_5, C_7 — 0.01- μ fd. 600-volt paper.
- C_6, C_8 — 10- μ fd. 25-volt electrolytic.
- C_9 — 8- μ fd. 450-volt electrolytic.

- R_1 — 5 megohms, 1/2 watt.
- R_2 — 25,000 ohms, 1 watt.
- R_3 — 0.5-megohm volume control.
- R_4 — 50,000-ohm wire-wound variable.
- R_5 — 1500 ohms, 1/2 watt.
- R_6, R_7 — 50,000 ohms, 1 watt.
- R_8 — 0.1 megohm, 1/2 watt.
- R_9 — 500 ohms, 1 watt.
- R_{10} — 2000-ohm, 10-watt wire-wound. See text.

- J — Closed-circuit jack.
- RFC₁ — V.h.f. choke (Ohmite Z-1).
- RFC₂ — 80-mh. r.f. choke.
- S_1 — S.p.d.t. toggle switch.
- T_1 — Pentode output transformer.
- Speaker — 4-inch p.m. type.
- L_1 — 13 1/4 turns No. 14 enam., 3/8-inch inside diameter, spaced diameter of wire.
- L_2 — 7/8 turn No. 14 enam., 3/8-inch inside diameter.

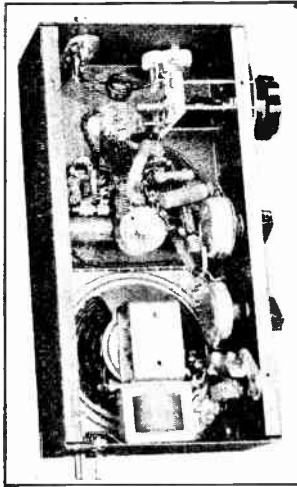


Fig. 1507 This underside view of the 7-Mc. detector superregenerative receiver shows the loud-speaker mounted at one end of the 5 x 10 x 3-inch chassis. The detector tuning condenser is mounted on long machine screws from the front "panel." The r.f. chokes may be seen in the clear at the left center. The male plug for the power-supply cable is to be seen mounted on one end, at the corner near the loud-speaker.

leads as short as possible. The tuning condenser, C_2 , is supported back of the panel on long (4 3/4 inch) 6-32 screws. The padding condenser, C_1 , is mounted directly on the end of the chassis. A bakelite shaft extension is attached to the tuning condenser shaft and brought out through a panel bearing assembly. The quench-frequency filter choke, RFC_2 , is supported on a 1/2-inch metal pillar between the two audio tube sockets.

All grounds for each separate stage are made to a soldering lug placed under one socket-mounting screw. Most of the resistors and condensers can be mounted directly on socket terminals or the variable resistor lugs.

The tuned-circuit coil, L_1 , may be trimmed slightly by squeezing the turns or pulling them apart until the desired bandspread is obtained. Antenna coupling is adjusted by moving the antenna coil, L_2 , closer to L_1 until the regeneration control must be set at about two-thirds of maximum for "supering" to start. This adjustment is made with the antenna connected.

€ A 144/220-Mc. Superregenerator

The receiver in Figs. 1508, 1509 and 1510 affords excellent sensitivity on both 144 and 220 Mc. For the amateur who wishes to experiment on these bands, it will provide satisfactory reception at minimum expense. The circuit is the familiar self-quenched superregenerative detector, followed by two stages of audio amplification.

The receiver is built on a 7 x 7 x 2-inch chassis. The tuning condenser is mounted on a metal bracket, cut in the shape of a U to clear the stator connections. The dial is connected to the condenser by a flexible bakelite coupling.

The improvised socket for the plug-in coil utilizes contacts obtained from an Amphelol miniature-type tube socket, by the process of squeezing the socket in a vise until the bakelite cracks. One contact is soldered to each of the tuning condenser connections and a third to a lug supported by one of the extra holes in the Isolantite base of the condenser. The contacts must all be placed at exactly the same height, so that the plug-in coil will seat properly. The band-set condenser, C_2 , is mounted by soldering short strips of wire between the lugs and the tuning condenser terminals.

The polystyrene tube socket for the 9002 is mounted on a metal bracket, placed near the tuning condenser so as to allow a very short lead from the condenser to the plate terminal and just enough room between the rotor connection and the grid terminal for the grid condenser. Heater and cathode leads are brought through the chassis in a rubber grommet.


The variable antenna coupling coil, L_1 , is mounted on a polystyrene rod supported by a shaft bearing. The rod is prevented from moving axially in the bearing by cementing a fiber washer to the shaft and tightening the knob on the other side. The antenna coupling loop should be adjusted so that, when rotated, it will just clear the coils plugged into the socket.



Fig. 1508 — *Left* — The panel of the two-band superregenerative receiver measures 7 inches square. The knob in the upper right-hand corner adjusts antenna coupling, while the knob below the tuning dial controls regeneration. *Right* — Rear view of the two-band superregenerative receiver. The 220-Mc. plug-in coil is in the foreground.

Fig. 1509 — Wiring diagram of the super-regenerative receiver for 112 and 224 Mc.

- C₁ — 5- μ fd. midget variable (National UM-15, 4 plates removed).
- C₂ — 3-30- μ fd. mica trimmer.
- C₃ — 50- μ fd. mica.
- C₄ — 0.003- μ fd. mica.
- C₅, C₇ — 10- μ fd. 25-volt electrolytic.
- C₆ — 0.01- μ fd. 400-volt paper.
- R₁ — 10 megohms, $\frac{1}{2}$ watt.
- R₂ — 50,000-ohm wire wound variable.
- R₃, R₅, R₆, R₇ — 0.1 megohm, $\frac{1}{2}$ watt.
- R₄ — 2500 ohms, $\frac{1}{2}$ watt.
- R₈ — 500 ohms, 1 watt.
- J — Closed-circuit jack.
- S — S.p.s.t. toggle switch.
- T₁ — Plate to grid interstage audio transformer (Thordarson T-57A36).
- RFC₁ — 25 turns No. 24 d.c.c., close-wound, $\frac{1}{4}$ -inch diameter.

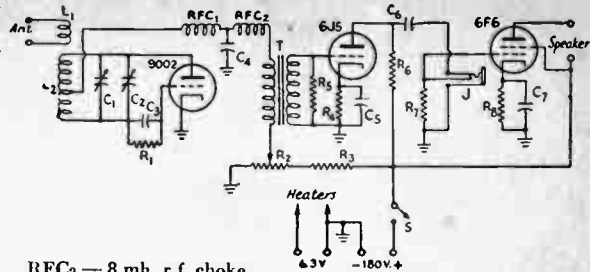

- RFC₂ — 8 mh. r.f. choke.
- L₁ — 1 turn No. 14 e., $\frac{3}{8}$ -inch inside diameter.
- L₂ — 112 Mc.: 3 turns No. 18 e., $\frac{1}{2}$ -inch diameter, spaced over $\frac{1}{4}$ inch. Tapped 1 $\frac{1}{4}$ turns from plate end.
- 224 Mc.: 2 turns No. 18 e., $\frac{1}{4}$ -inch diameter, spaced over $\frac{1}{2}$ inch. Tapped at center of coil.

The coils are mounted on small strips of $\frac{1}{8}$ -inch polystyrene (Millen Quartz Q) which have three small holes drilled in them corresponding exactly with the coil socket. Each coil is cemented to the strip with Duco cement at the points where the wire passes through the base. The No. 18 wire used for the coils will fit snugly in the sockets if the contacts are pinched slightly. The coils are trimmed to fit the bands by spreading or squeezing the turns slightly by the procedure previously described. However, in this case the band-set condenser gives some further range of adjustment. In the receiver as described, it is screwed down fairly tightly for the 112-Mc. band and loosened about four revolutions for 224 Mc. In the absence of good marker stations, an absorption frequency meter or a Lecher wire system (described in Chapter Nineteen) may be used for spotting the band limits.

Two factors which will be found to influence sensitivity are the value of C₄ and the degree of antenna coupling. Values of C₄ from 0.001 to 0.005 μ fd. should be tried. The antenna coupling will vary greatly with the setting of L₁ and the type of antenna used; it is well worth while to tune the antenna circuit and then vary the coupling with the panel control. Tight coupling usually will give better results than loose coupling. The coupling can be increased almost up to the point where the detector no longer oscillates, with no ill effects except increased radiation and possible QRM for other receivers in the vicinity.

An audio volume control could be installed in place of the fixed grid resistor, R₇, if desired. In the original model of this receiver, the value of R₇ was adjusted until normal loudspeaker output was obtained; this value may be varied to meet any particular requirements.

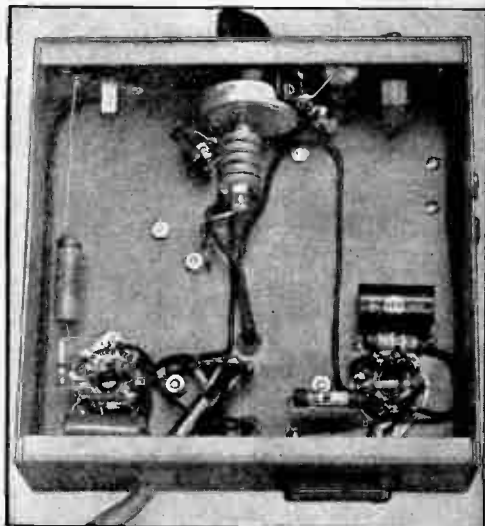
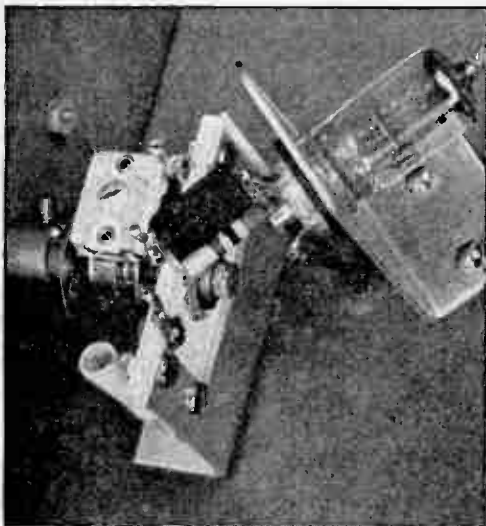


Fig. 1510 — Left — A close-up view of the tuning assembly, showing how the leads from the tuning condenser to the tube socket have been kept short and how the coil socket is mounted on the tuning condenser. Hidden by the grid condenser (the 50- μ fd. condenser so prominent in the picture), the plate terminal of the tube socket goes to a lug which has been added to the rotor of the tuning condenser. Right — The arrangement of parts under the chassis may be seen in this photograph. The 6J5 socket is at the left and the 6F6 socket is at the right, near the speaker terminals. The 8-mh. r.f. choke, seen just under the regeneration control at the top center, is supported by tie strips.

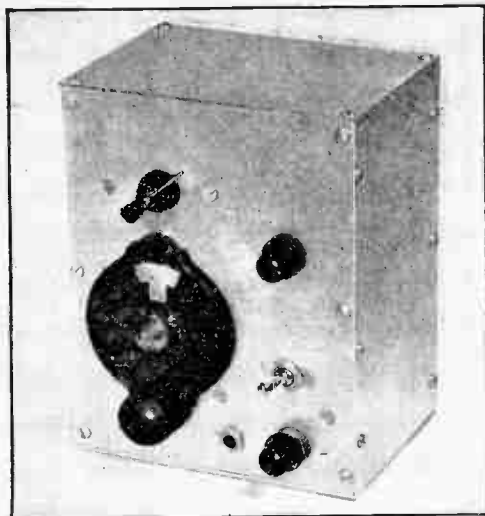


Fig. 1511 — Front view of the 144-Mc. r.f. receiver. The pointer knob above the vernier dial tunes the r.f. stage. The small round knobs are for audio volume (lower right) and detector plate voltage variation. Outside dimensions of the handmade case are $7 \times 5\frac{1}{2} \times 4$ inches.

□ T.R.F. Superregenerative Receiver

The receiver shown in Figs. 1511, 1512, 1513, 1514 and 1515 uses miniature tubes throughout and is intended for either home or portable/mobile use. The r.f. amplifier stage furnishes some additional gain over a straight superregenerative detector, affords freedom from antenna effects, and — most important of all — prevents radiation from the receiver. Although the r.f. and detector circuits are individually tuned, the broad tuning of the r.f. stage makes the receiver essentially a single-dial affair — important in mobile work — and the low-priced miniature tubes permit compact assembly and low current consumption. Heater current is 625 ma. at 6.3 volts, and the total plate drain from 135 volts of "B" battery is less than 10 ma.

The tuned r.f. amplifier stage uses a 6AK5 pentode which is coupled through C_5 to the 6C4 superregenerative triode detector. This in turn is transformer coupled to a 6C4 audio stage which drives the 6AK6 output stage. A plate coupling choke, L_4 , and the coupling condenser C_{12} remove d.c. from the output jack J_2 and eliminate the possibility of short-circuiting the plate supply at this point.

The receiver chassis and partitions are built from pieces of $\frac{1}{16}$ -inch aluminum held together at the corners with machine screws and strips of $\frac{1}{4}$ -inch square brass rod. The overall dimensions are 7 by 5 by 4 inches — the chassis that mounts the audio components is 4 by 5 inches with a $1\frac{3}{4}$ -inch folded lip. To eliminate oscillation in the r.f. stage and radiation from the detector, completely separate compartments are used for the r.f. and detector stages.

These compartments consist of identical boxes that measure $1\frac{1}{8}$ inches square and 3 inches long. The tube sockets are mounted on the end plates, and all of the connections to the sockets are made before the boxes are completely assembled. The wire between C_5 and L_3 runs through two Millen 32150 bushings in the walls of the two shield compartments. This inter-connection, the only one except for the power circuits, is made by running separate leads from the condenser and coil through the bushings and then soldering the two ends together after the two units are mounted on the front panel.

The detector tuning condenser, C_8 , is a regular Cardwell ZV-5-TS modified by adding a single circular plate to the regular two-plate rotor. This additional constant capacity across the circuit increases the bandwidth and, because it decreases the L to C ratio, smooths out the regeneration so that the regeneration control, R_{10} , does not have to be readjusted within the 144-Mc. band.

The two r.f. chokes, RFC, are homemade affairs wound on 1-watt IRC composition resistors — 0.25 megohm or higher — the insulated type that is $\frac{1}{4}$ inch in diameter and $2\frac{1}{32}$ inches long. The ends are notched with a small file or saw, to prevent the ends of the coil wire from slipping after they have been soldered to the pigtail leads of the resistor, and a single layer of No. 30 d.s.c. is wound on for a length of $1\frac{17}{32}$ inches. No lacquer or dope should be used on the winding because of the increased distributed capacity that will result.


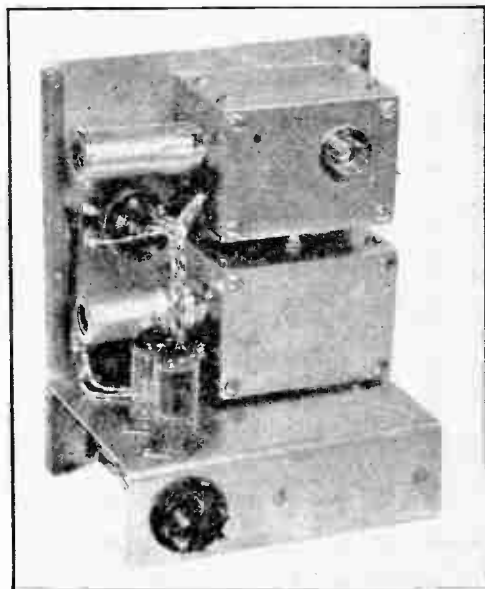


Fig. 1512 — Rear view of the complete receiver. Note that the r.f. stage and superregenerative detector circuit components are in separate completely-enclosed compartments, for elimination of radiation. Miniature tubes are used throughout, for compactness and low current consumption.

Fig. 1513 — Wiring diagram of the four-tube r.f. superregenerative receiver. Boundaries of shield compartments housing r.f. and detector stages are shown in dotted lines.

- C₁, C₈ — Split-stator condenser (Cardwell ZV-5-TS). See text.
- C₂, C₃, C₄ — 500- μ fd. midget mica.
- C₅, C₇ — 50- μ fd. midget mica.
- C₆ — 0.002 μ fd. midget mica.
- C₉, C₁₁ — 10- μ fd. 25-volt midget electrolytic.
- C₁₀, C₁₂ — 0.1- μ fd. paper.
- R₁ — 1500 ohms, $\frac{1}{2}$ -watt.
- R₂, R₇, R₈ — 100,000 ohms, $\frac{1}{2}$ -watt.
- R₃ — 3.3 megohms, $\frac{1}{2}$ -watt.
- R₄ — 40,000 ohms, $\frac{1}{2}$ -watt. See text.
- R₅ — 500,000-ohm potentiometer.
- R₆ — 2000 ohms, $\frac{1}{2}$ -watt.
- R₉ — 600 ohms, $\frac{1}{2}$ -watt.
- R₁₀ — 50,000-ohm potentiometer.
- R₁₁ — 25,000 ohms, 1 watt.
- S₁ — S.p.s.t. switch on R₁₀.
- S₂, S₃ — D.p.s.t. toggle switch.
- J₁ — Coaxial socket (Jones S-201). Matching plug for antenna is P-101 or P-201.
- J₂ — Headphone or speaker jack.
- L₁ — 2 t. $\frac{3}{8}$ -inch i.d. No. 18 enam. inserted between turns of L₂ at cold end.
- L₂ — 4 t. $\frac{3}{8}$ -inch i.d. $\frac{3}{4}$ -inch long. No. 18 tinned.
- L₃ — 5 t., center tapped, $\frac{1}{2}$ -inch long, No. 18 tinned. R.f. coupling tap, 1 t. from grid end.
- L₄ — Midget audio or filter choke (Inca D-92).

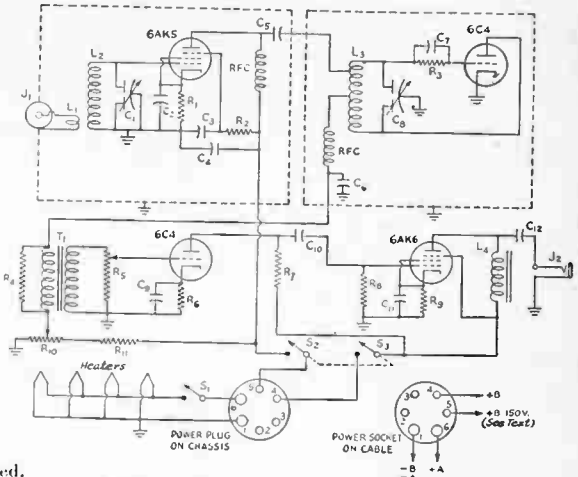

T₁ — Midget audio transformer (Thordarson T-13A34). RFC — See text.

When the receiver is completely wired the first move should be to check detector operation. With the 6AK5 in its socket, but with no plate or screen voltage applied to it, apply the plate voltage to the detector and check for the customary hiss. Try the regeneration control, R₁₀, to determine whether the detector goes in and out of superregeneration smoothly. Some variation in values of R₃, R₄ and C₆ may be necessary to attain this end, and some 6C4s work better than others in this respect.

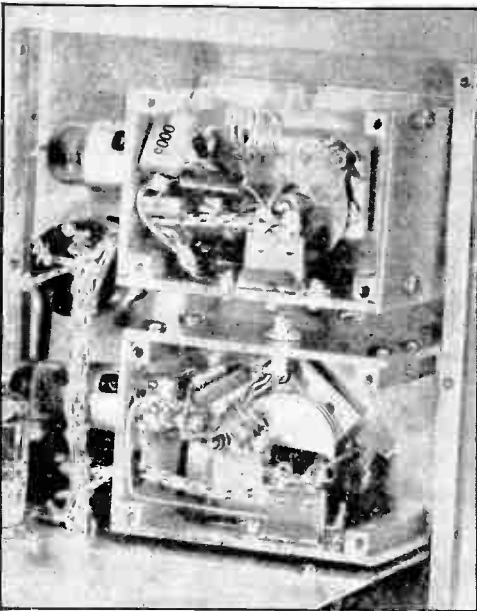


Fig. 1514 — Closeup view of the r.f. and superregenerative detector compartments, with back plates removed to show details. Top, back, and right side may be removed from either assembly, providing accessibility despite compact design.

Next, the tuning range should be checked by means of Lecher wires or an absorption-type wavemeter. With the values given, 144 Mc. should fall at about 80 on the dial, with 148 Mc. at around 60. The position of the r.f. coupling tap on L₃ will have considerable effect on the resonant frequency of the combination. Its position is not critical, except for its effect on the tuning range of the detector circuit, but the spacing of the turns in the coil will have to be changed if the position of the tap is materially different from that given.

When the detector is found to be in the band, the r.f. stage may be put into operation. With any of the shields removed, or with no antenna connected, the 6AK5 will probably oscillate, blocking the detector, but this effect will disappear when the two compartments are completely assembled and an antenna attached by means of the coaxial connector. If the r.f. stage is operating properly there will be slight change in the character of the hiss when the stage is tuned through resonance. Using a signal generator (the harmonic of any oscillator which falls in the 144-Mc. band will do) or the signal of a 144-Mc. station, there will be a pronounced drop in background noise and a slight change in dial setting of the detector when the r.f. stage is tuned "on the nose." Once the r.f. tuning is adjusted for maximum response, preferably on a weak signal near the middle of the band, it may be left at that setting for all except the very weakest signals at either end.

Power supply filtering and regulation are important factors in attaining smooth and efficient performance with superregenerative detectors. The power plug mounted on the back of the chassis provides a separate connection (pin 5) for the detector and r.f. B+, in order that this may be drawn from a regulated source, such as a VR-150. The other pin

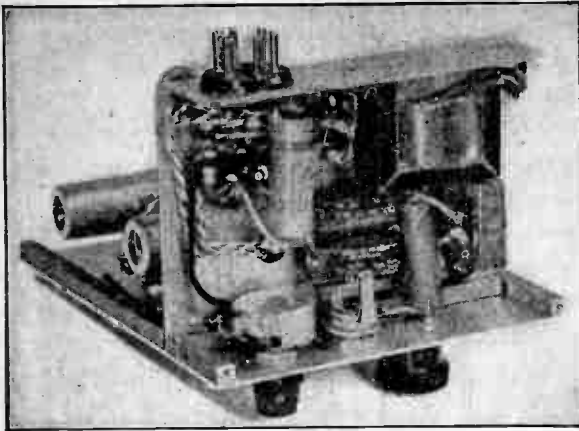


Fig. 1515 — Bottom view, showing audio component arrangement.

marked "B + " (pin 4) supplies the audio tubes, and the voltage used here need not be regulated. If "B" batteries are used — and they are highly recommended for mobile operation — pins 4 and 5 may be connected together in the power socket on the cable. The use of "B" batteries in mobile work will result in better sensitivity and more quiet operation than will be available with any sort of mobile power supply, vibrator or dynamotor, and the drain from the car battery will be negligible during receiving periods. A set of medium-size "B" batteries (135 volts is sufficient for good speaker volume) will last through a year or more of normal operation. When batteries are used, the on-off switch, S_2-S_3 , should be thrown to the "off" position when the receiver is not in use, otherwise there will be a small continuous drain on the batteries through the $R_{10}-R_{11}$ bleeder.

Ⓒ A 144-Mc. Superregenerative Superheterodyne Receiver

The ordinary 144-Mc. superregenerative receiver is not very selective, and often a more selective type of receiver is desirable to minimize interference. Furthermore, the radiation from a superregenerator can cause an annoying type of interference when stations are fairly close together. Both of these disadvantages can be overcome by using a superheterodyne. The well-known advantages of the superregenerator — simplicity, sensitivity and economy of tubes and components — can in large part be retained by using a superregenerative detector as the i.f. system of the superheterodyne. Since the intermediate frequency will be considerably lower than the signal frequency, the selectivity will be increased in proportion; yet the receiver as a whole is increased in com-

plexity only by the addition of one or two tubes and relatively simple accompanying circuits.

A superheterodyne of this type is shown in Figs. 1516, 1517, 1518 and 1519. A 6J6 miniature twin triode is used as local oscillator and mixer, and its high transconductance (5300 μ mhos) and small size make for good performance in the 2-meter band. The superregenerative second detector is a 6J5 working at 25 Mc., and this is followed by a 6J5 for headphone output and 6F6 for speaker operation. The wiring diagram, Fig. 1518, shows no coupling condenser between oscillator and mixer because stray coupling between grid pins at the socket gives adequate injection. Since the 6J6 has a common cathode connection, it

is necessary to return the grid of the oscillator portion to cathode, and the grid of the mixer is returned to ground through R_1 . The mixer plate is by-passed for signal frequency by C_4 , which also serves to tune the primary, L_4 , of the i.f. transformer. The i.f. transformer is adjustable only in the secondary circuit, since with just one stage there is no tuning requirement other than that the primary and secondary be tuned to the same frequency. A switch, S_1 , removes the plate voltage from the second detector and following stages during transmission periods, but plate voltage is left on the oscillator (and mixer) to avoid drift. This is an unnecessary refinement, however, since the oscillator drift is considerably less than the band width of the i.f. amplifier.

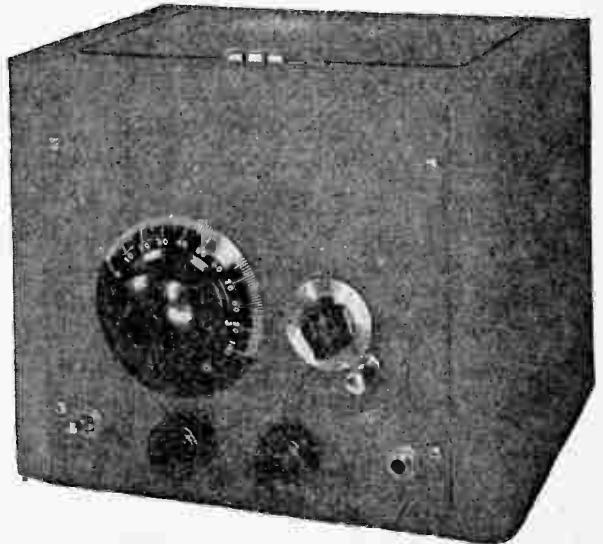


Fig. 1516 — The four-tube 144-Mc. superheterodyne, dressed up in a modern cabinet. The large dial is oscillator tuning, and the small dial and lock is for mixer tuning. The two knobs control regeneration (right) and volume (left).

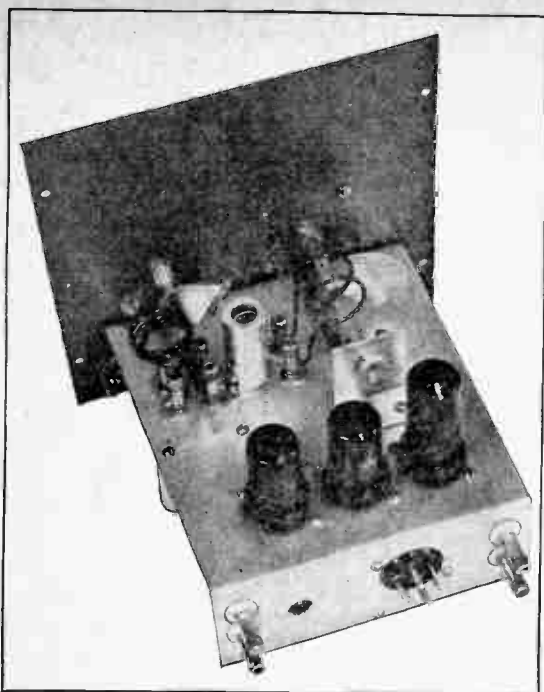


Fig. 1517 — A top view of the receiver shows the construction of the inductive-tuning devices used in the oscillator and mixer circuits. The tubes along the back, from left to right, are super-regenerative second detector, audio and output.

Inductive tuning of the oscillator and mixer circuits is used, by moving a copper vane which acts as a low-resistance shorted turn in the field of the coil. As the vane is moved into the field of the coil, the inductance is reduced. No current flows through the insulated shaft supporting the vane, and consequently there is no "jumping" of frequency such as is caused by erratic contact to a condenser rotor.

The receiver is built to mount in an 8 by 10 by 8-inch cabinet, but the cabinet is a refinement that is not absolutely necessary. The panel, part of the standard cabinet, measures 8 by 8 inches. The chassis was bent out of $\frac{1}{16}$ -inch aluminum and is $6\frac{1}{4}$ inches wide and 7 inches deep. A $2\frac{1}{2}$ -inch lip is bent down at the rear and a $1\frac{3}{4}$ -inch lip is formed at the front. The front bend is made shorter to avoid the lip at the bottom of the cabinet. The chassis is held to the panel by the two potentiometers (regeneration and volume controls) while a $\frac{3}{8}$ -inch square dural bar bolted to the edge of the $2\frac{1}{2}$ -inch lip picks up two screws through the bottom of the cabinet to give a rigid structure.

Bakelite sockets (Amphenol MIP) are used for the octal tubes, and the miniature tube socket is the ceramic one made by Eby. A metal shield to match the socket also acts as a tube lock. The socket is mounted with the No. 5 pin towards the panel. National FWA binding posts mounted on National XP-6 polystyrene buttons support the mixer, antenna

and oscillator coils, and allow the coils to be changed readily for experimental purposes. The antenna and loudspeaker leads are brought out to similar posts at the rear of the chassis.

The $\frac{1}{4}$ -inch diameter polystyrene rod used for the oscillator tuning vane shaft is supported at the panel end by the National A dial and at the other by a panel bushing mounted in an aluminum bracket. The vane is made of a piece of thin copper soldered to a brass shaft coupling. After soldering the vane to the coupling, the copper is cut roughly in the form of a straight-line-wave-length condenser rotor plate. It can be trimmed up later to give something resembling straight-line-frequency tuning, but this is hardly essential. By moving the vane closer to the coil the tuning range can be increased, and vice versa. The tuning vane for the mixer coil is fastened to a piece of $\frac{1}{8}$ -inch polystyrene by small machine screws and nuts, and the poly is fastened to a shaft which is filed flat on one side and tapped for two 6-32 screws. The shaft is part of an ICA No. 1248 panel bearing assembly. A Millen 10050 dial lock working against the small metal dial prevents any undesired change in the position of the mixer tuning vane.

RFC_1 and RFC_2 are wound on $\frac{1}{4}$ -inch diameter 1-megohm resistors. A small notch is filed at each end of the resistor to keep the wire in place, and the wires for the chokes are soldered to the leads of the resistor. A 1-watt size is used for RFC_1 and a 2-watt size for RFC_2 . RFC_3 is made by mounting a single pie from a 2.5-mh. 4-pic r.f. choke on a 1-megohm 1-watt resistor similar to that used for RFC_1 . The easiest way to remove the pies from the ceramic form on which they come is to melt the metal from one end of the choke with a hot soldering iron and then force a sharp ice pick or nail down the hole in the center of the ceramic form until the ceramic splits. The pies can then be removed and one mounted on the resistor with Duco cement.

The i.f. transformer is wound on a National PRE-3 polystyrene form. Two additional small holes, 90 degrees apart, are drilled in the form between the two windings, and one lead of C_5 is snaked through to furnish a support for one end of the condenser as well as a tie point for one end of L_4 and the isolating resistor R_4 .

In wiring the receiver, it is convenient to wire the heater circuits first. On the metal tubes, pins Nos. 1 and 2 are grounded to lugs fastened under the screws holding the sockets to the chassis. On the miniature socket a jumper goes from pin No. 4 to the central shield of the socket and thence to a lug under one of the screws fastening the socket to the chassis, on the pin No. 7 side. Some care should be

taken in wiring the r.f. components on the miniature socket, to insure short leads. One connection of R_2 , R_3 , C_4 , C_5 and C_1 goes to pin No. 7. C_2 (two condensers in parallel) mounts between pin No. 2 and the binding post supporting the grid side of L_3 , and C_3 is mounted from this post to pin No. 5. C_6 , C_9 and R_1 return to the ground lug for the 6J6 heater circuit mentioned above. A small tie point is used at the junction of RFC_1 and R_3 .

The two wires from the antenna binding posts to the posts supporting the antenna coil are No. 14 enameled, and further support is given them by running them through holes in a PRE-3 form.

Checking of the receiver is best done by starting at the output and working toward the input. Connect heater voltage and high voltage to check the superregenerative detector operation. With a speaker or headset connected, advancing the regeneration control should result in the familiar superregenerative hiss. At this point the 105 volts for the mixer and oscillator can be connected, because the adjustment on C_7 should be made with plate voltage on the mixer. With the regeneration control only slightly beyond the point where the hiss starts to be heard, adjust C_7 for the

point which requires maximum advancing of R_7 for oscillation. This brings L_5C_7 into resonance with L_4C_4 . If it is found that the second detector won't oscillate at one very sharp setting of C_7 , the coupling between L_4 and L_5 is too tight. In this event the coils should be backed away from each other, if possible, or else C_7 can be detuned slightly. The former procedure is preferable. The setting of C_7 where the primary circuit pulls the detector out of oscillation should be quite sharp — if it isn't, the setting isn't right. When the detector is oscillating and C_7 is not set properly, it is quite likely that the hiss will also contain some unpleasant high-frequency whistles. The exact frequency of the i.f. can be checked on a calibrated communications-frequency receiver, if desired, but a frequency check is not essential. With the constants given the i.f. will be around 25 Mc.

Knowing the i.f. makes it a bit easier to adjust the oscillator portion of the 6J6, because an absorption wavemeter or Lecher wires can be used to put the oscillator on the right frequency. If one knows the i.f. and has some means of checking the oscillator frequency, the oscillator can be adjusted to give a tuning range from 143 Mc. minus the i.f. to 149 Mc.

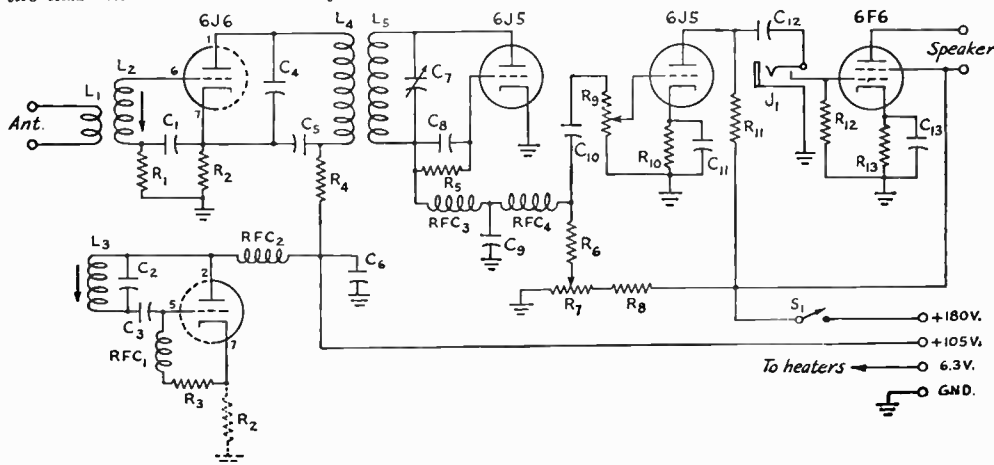


Fig. 1518 — Wiring diagram of the 141-Mc. superheterodyne.

- C_1 — 250- μ fd. mica.
- C_2 — 40- μ fd. silver mica (two 20- μ fd. silver mica in parallel).
- C_3, C_4 — 10- μ fd. mica.
- C_5 — 500- μ fd. mica.
- C_6, C_8 — 100- μ fd. mica.
- C_7 — 4 — 20- μ fd. adjustable ceramic trimmer (Cen-tralab or Eric).
- C_9 — 0.002- μ fd. mica.
- C_{10} — 0.01- μ fd. 400-volt paper.
- C_{11}, C_{13} — 25- μ fd. 25-volt electrolytic.
- C_{12} — 0.1- μ fd. 400-volt paper.
- J_1 — Closed circuit telephone jack.
- L_1 — 2 turns No. 12 enam., 1-inch diam., spaced wire diameter.
- L_2 — 2 turns No. 12 enam., $1\frac{1}{8}$ -inch diam., spaced twice wire diameter.
- L_3 — 2 turns No. 12 enam., $1\frac{1}{8}$ -inch diam., spaced to occupy $\frac{7}{8}$ inch.
- L_4 — 16 turns No. 22 enam., close-wound on 9/16-inch diam. form.

- L_5 — 10 turns No. 22 enam., close-wound on same form as L_4 and spaced $\frac{1}{2}$ inch from L_4 .
- R_1 — 0.25 megohm, $\frac{1}{2}$ -watt.
- R_2 — 50 ohms, $\frac{1}{2}$ -watt.
- R_3 — 7500 ohms, $\frac{1}{2}$ -watt.
- R_4 — 1000 ohms, $\frac{1}{2}$ -watt.
- R_5 — 5.0 megohms, $\frac{1}{2}$ -watt.
- R_6 — 75,000 ohms, $\frac{1}{2}$ -watt.
- R_7 — 50,000-ohm 2-watt potentiometer, preferably wire-wound.
- R_8 — 50,000 ohms, 1-watt.
- R_9 — 0.5-megohm volume control.
- R_{10} — 2500 ohms, $\frac{1}{2}$ -watt.
- R_{11}, R_{12} — 0.1 megohm, $\frac{1}{2}$ -watt.
- R_{13} — 500 ohms, 1-watt.
- RFC_1 — 21 turns No. 22 enam., close-wound on $\frac{1}{4}$ -inch diam. form. See text.
- RFC_2 — 48 turns No. 22 enam., close-wound on $\frac{1}{4}$ -inch diam. form. See text.
- RFC_3 — One pie from 4-pie 2.5-mh. choke. See text.
- RFC_4 — 80-ml. iron-core r.f. choke (Meissner 19-6846).
- S_1 — S.p.s.t. toggle switch.

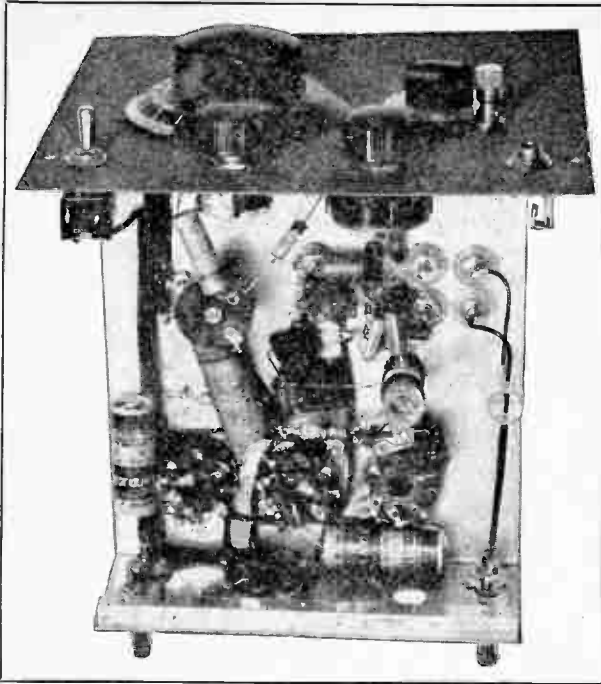


Fig. 1519 — A view underneath the chassis, showing the arrangement of parts. Note the ceramic trimmer condenser between the second detector socket and the i.f. transformer. This trimmer condenser is adjustable from above the chassis. To the left of the ceramic condenser can be seen $RF C_3$, the single-pie r.f. choke.

minus the i.f. The tuning range is adjusted by spacing the turns of L_3 and by moving the vane on the shaft. Moving the vane closer to the coil will increase the tuning range but increases the minimum frequency a trifle, and vice versa. If a calibrated 144-Mc. superregenerative receiver or transmitter is available, it can be used as a signal source and the oscillator tuning range can be adjusted without knowing the i.f.

The mixer coil and antenna coupling can be checked by listening to a weak signal (whose weakness is under your control, however), or to ignition noises, and it will be found that best sensitivity will be obtained with quite tight coupling. The mixer circuit will not tune sharply, and it is only necessary to retrim it when going from one end of the 144-Mc. band to the other.

☛ An Acorn-Tube Superregenerative Superheterodyne

Another superheterodyne receiver of medium selectivity and good sensitivity is shown in Figs. 1520 and 1521. The circuit appears in Fig. 1522. The 955 mixer tunes from 144 to 148 Mc., while the

h.f. oscillator, using a second 955, tunes from 123 to 127 Mc. The 6AC7/1852 i.f. amplifier and the 6J5 superregenerative detector operate on 21 Mc. Transformer coupling is used between the detector and the 6J5 first audio stage. The output tube which feeds the speaker is resistance coupled to the preceding stage. The power supply is a simple choke-input affair with a VR105-30 regulator tube controlling the plate voltage of the h.f. oscillator and mixer stages. R_9 is the detector superregeneration control, and R_{11} is the audio volume control.

Most of the constructional details are apparent from Figs. 1520 and 1521. The chassis measures $3 \times 7 \times 15$ inches. All components for the v.h.f. circuits, including the tubes, are mounted underneath the chassis. In Fig. 1521 the ganged tuning condenser, $C_1 C_2$, is mounted near the top. By removing one of the two rotor plates originally in each section and double-spacing the single stator, a tuning rate is obtained which spreads the 144-148-Mc. band over a good portion of the dial. If less band spread is desired, the stator plates need not be double spaced.

Immediately above the tuning condenser are the two acorn tubes, the oscillator tube being nearer to the panel. The self-supporting mixer and oscillator coils, L_2 and L_3 , are mounted at right angles to each other and soldered to their respective condenser terminals.

The 6AC7/1852 i.f. tube is mounted on the chassis. The first i.f. transformer is composed of two windings, $L_4 L_5$, on a $\frac{3}{4}$ -inch polystyrene form placed underneath the chassis as close as



Fig. 1520 — Top view of the superheterodyne receiver. The i.f. amplifier tube and output transformer are in the rear right-hand corner. The detector and audio tubes are in line to the right. Power-supply components and loudspeaker are at the left-hand end of the chassis.

possible to the sub-mounted i.f. tube socket and at right angles to L_2 and L_3 . No shielding of these windings, other than that provided by the chassis, is necessary.

The second i.f. transformer, L_6L_7 , is built in the shield can mounted on top of the chassis. The i.f. tuning condenser, C_{15} , is mounted inside the shield and is adjusted by a screwdriver inserted in a hole in the top of the can. The plate lead of the 6AC7/1852 is kept as short as possible and shielded to prevent regeneration. All ground connections for the i.f. amplifier are brought to a single point on the metal ring holding the socket to the chassis. Particular care should be exercised in grounding the can shielding the second i.f. transformer.

The 6J5 superregenerative detector is at the left of the second i.f. transformer. The regeneration control, R_9 , is located underneath the

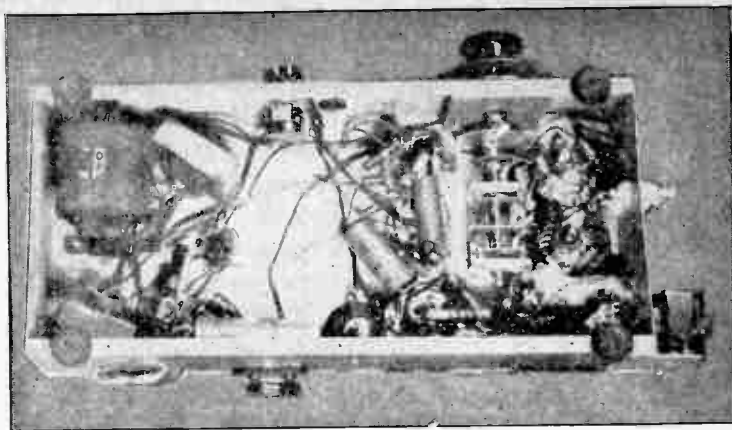


Fig. 1521 — Bottom view of the acorn-tube superheterodyne receiver. The two acorn tubes are visible above the tuning condenser, near the top of the chassis.

chassis since it does not require attention once it has been adjusted for proper operation. The two audio tubes are in line in front of the detector tube. The audio transformer, T_2 , was mounted outside the chassis because it picked up hum in any other position. With a shielded transformer this trouble probably would not occur.

The receiver may be lined up with the aid of an all-wave receiver or any other source which will serve as a signal generator. Before aligning the i.f. amplifier and adjusting the superregenerative detector, the 955 oscillator tube should be removed from its socket and a two-foot length of wire attached to the plate lead of the mixer tube where it connects to the

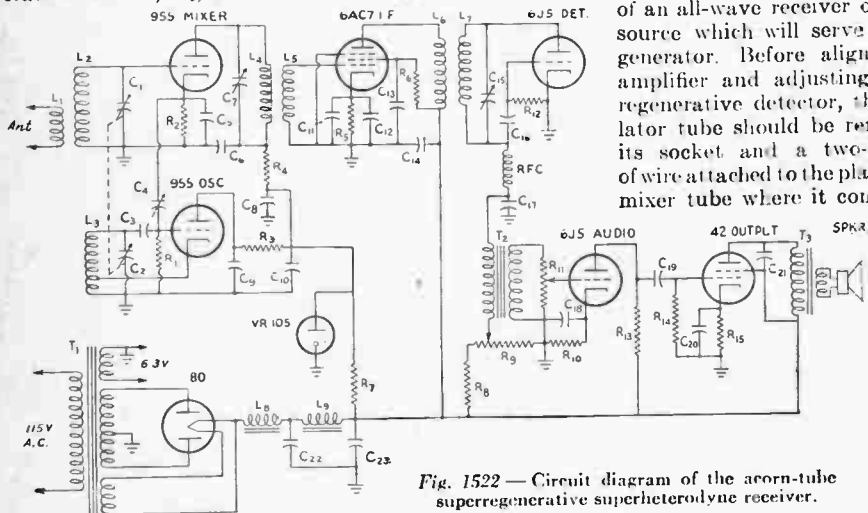


Fig. 1522 — Circuit diagram of the acorn-tube superregenerative superheterodyne receiver.

- C_1, C_2 — 10- μ fd. midget variable. (See text.)
- C_3, C_6, C_{10} — 100- μ fd. midget mica.
- C_4, C_7, C_{15} — 3-30- μ fd. trimmer.
- C_5 — 50- μ fd. midget mica.
- C_8, C_{10}, C_{17} — 0.001- μ fd. mica.
- C_9 — 500- μ fd. midget mica.
- C_{11} — 0.002- μ fd. midget mica.
- C_{12}, C_{13}, C_{14} — 0.01- μ fd. 400-volt paper.
- C_{18}, C_{20} — 25- μ fd. 25-volt electrolytic.
- C_{19} — 0.05- μ fd. 400-volt paper.
- C_{21} — 0.002- μ fd. 400-volt paper.
- C_{22}, C_{23} — 8- μ fd. 450-volt electrolytic.
- R_1 — 20,000 ohms, $\frac{1}{2}$ -watt.

- R_2, R_3, R_4 — 10,000 ohms, $\frac{1}{2}$ -watt.
- R_5 — 200 ohms, $\frac{1}{2}$ -watt.
- R_6 — 60,000 ohms, $\frac{1}{2}$ -watt.
- R_7 — 7000 ohms, 10-watt.
- R_8 — 250,000 ohms, 1-watt.
- R_9 — 75,000-ohm wire-wound potentiometer.
- R_{10} — 2000 ohms, 1-watt.
- R_{11} — 0.5-megohm volume control.
- R_{12} — 2 megohms, $\frac{1}{2}$ -watt.
- R_{13} — 50,000 ohms, 1-watt.
- R_{14} — 0.5 megohm, $\frac{1}{2}$ -watt.
- R_{15} — 500 ohms, 1-watt.
- L_1 — 4 turns No. 20, $\frac{1}{2}$ -inch diameter.
- L_2 — 5 turns No. 12, $\frac{1}{2}$ -inch diameter, 1 inch long.

- L_3 — 3 turns No. 12, $\frac{1}{2}$ -inch diameter, $\frac{1}{2}$ inch long, tapped 1 turn above ground.
- L_4 — 12 turns No. 18, $\frac{3}{4}$ -inch diameter, close-wound.
- L_5 — Same as L_4 , spaced 3/16 inch from L_4 on same form.
- L_6 — 40 turns No. 18, $\frac{3}{4}$ -inch diameter, close-wound.
- L_7 — 15 turns No. 18, $\frac{3}{4}$ -inch diameter, close-wound, spaced $\frac{1}{2}$ inch from L_3 on same form.
- L_8, L_9 — 20-henry filter choke.
- T_1 — Power transformer, 700 volts, c.t., 60 ma., with 5- and 6.3-volt heater windings.
- T_2 — Interstage audio transformer.
- T_3 — Pentode output transformer.
- RFC — 2.5-mb. r.f. choke.

top of L_4 . The regeneration control, R_9 , should be advanced until the 6J5 detector goes into superregeneration. If an all-wave receiver is used as the test-signal source, it should be tuned slowly between 20 and 30 Mc. with its antenna attached. At some point between these limits the signal from the oscillator in the all-wave receiver should block the detector. The all-wave receiver should then be tuned to approximately 21 Mc. and the detector adjusted to this frequency by listening for a "dead spot" as C_{15} is turned through its range. After this initial adjustment, the all-wave receiver should be moved some distance away, its antenna disconnected and C_{15} readjusted on the weaker signal. After tuning the input circuit of the i.f. amplifier by adjusting C_7 , R_9 should be readjusted for maximum hiss reduction when the test signal is tuned in.

Next replace the 955 oscillator tube and remove the antenna from L_4 . Optimum operation will be obtained with a detector plate voltage of about 20. If direct frequency-measuring apparatus for putting the oscillator on 123 to 127 Mc. is not available, the signal from a very low-power 144-Mc. oscillator or a harmonic from the oscillator in the all-wave receiver may be used as a test signal at the operating frequency. If the signal cannot be heard at some point as C_2 is tuned, adjust the inductance of L_3 by squeezing or spreading the turns. The coupling condenser, C_4 , should be set at about three-quarters of maximum capacity and adjusted for maximum mixer response (minimum hiss) when the weak test signal is tuned in. C_2 must be readjusted each time C_4 is changed. When the right amount of injection has been determined, the turns of L_3 should be spaced so that a 144-Mc. signal is heard with C_2 at half its maximum capacity. Finally C_7 and R_9 should be readjusted for maximum signal response consistent with good quality.

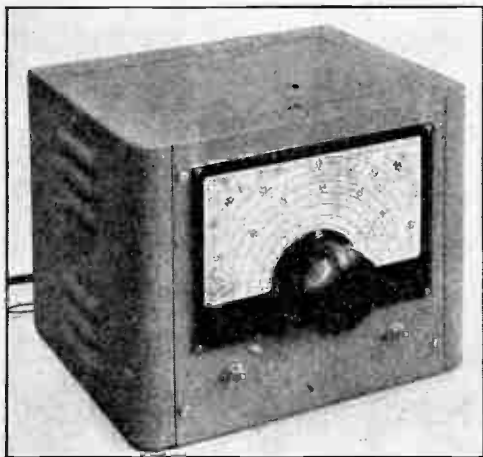


Fig. 1523 — This 144- and 50-Mc. converter, complete with self-contained power supply, is mounted in an 8 × 8 × 10-inch cabinet. Plug-in coils give bandspread coverage of the 50- and 144-Mc. amateur bands.

As a last adjustment, the mixer should be checked for tracking. Squeeze or spread the turns of L_2 slightly while tuning in signals at 144 and 148 Mc. alternately, to determine if more or less capacity is required to peak the signal. By bending one end of the rotor plate of C_1 , the mixer tuning can be adjusted to track over the entire band.

¶ V.H.F. Converters

For the amateur who already possesses a communications-type high-frequency receiver or even a reasonably good all-wave broadcast receiver capable of tuning to either 5 or 10 Mc. there is little or no necessity for building an elaborate separate v.h.f. receiver, particularly for operation on the 50-Mc. band. It is not only easier but often more satisfactory to build a v.h.f. converter which, in conjunction with the already existing receiver, can be used as a double superheterodyne. This arrangement is particularly successful if the receiver has controllable or broad-band selectivity to permit reception of the less-stable signals on the higher frequency bands.

The output transformer for such a converter should be designed to tune to an i.f. of either 5 or 10 Mc. (the higher frequency being preferable for operation on bands above 50 Mc.), with a low-impedance secondary. The output from the converter may be coupled through a low-impedance shielded line to the input circuit of the communications receiver, in much the same manner as link coupling is used between stages in a transmitter. The r.f. and mixer circuits of the receiver must be tuned to the same frequency as the output transformer — 5 or 10 Mc. — which then becomes the first i.f. Thereafter the receiver dial remains untouched, all tuning being done with the converter. The volume control, however, will be the gain control on the receiver into which the converter works.

¶ A High-Performance Converter for 50 and 144 Mc.

The converter shown in Figs. 1523, 1524, 1526 and 1527 uses the 9000-series "button" tubes. As may be seen from the diagram in Fig. 1525, the 9001 r.f. stage is transformer-coupled to a 9001 mixer. The h.f. oscillator, using a 9002, is capacity-coupled to the mixer grid through C_{15} . The output circuit (C_{14} , C_{16} and L_7) tunes to 10.2 Mc., although the converter could be made to work at another i.f. with suitable changes in the output circuit and oscillator constants.

As indicated in the diagram, the screen and plate by-pass condensers are returned to one cathode lead (the one to which the suppressor is connected) while the other lead is grounded through a condenser to serve as the grid return. In the mixer plate circuit a low-drift mica condenser, C_{14} , connected directly from plate

to cathode by-passes the signal-frequency component in the plate circuit. This condenser is part of the i.f. tuned circuit, and its capacity must be included in calculating the inductance required at L_7 .

The mixer and r.f. tuned circuits are made as low- C as is possible under the circumstances; the use of plug-in coils unavoidably introduces some stray capacity that would not be present if the circuits were made to operate on one frequency only. The tuning condensers are cut down to two plates each, and have just about enough capacity range to cover the 50-Mc. band with a little to spare. The trimmers are mica units operated at nearly minimum capacity, so that the mica is a negligible factor in the operation of the condenser; for all practical purposes, the dielectric is purely air. The L/C ratio compares favorably with those commonly attained in acorn receivers.

The oscillator circuit is of the grid-tickler type, with the tuned tank in the plate circuit. The tuned circuit is made higher- C than the signal-frequency circuits to improve the stability, and as a consequence somewhat more tuning capacity is needed to cover the frequency range. The tuning condenser is a 15- μfd . unit cut down to three plates and the trimmer is a 25- μfd . air-dielectric unit. The oscillator and mixer circuits are coupled through a small homemade condenser, C_{15} , tailored to give suitable injection of oscillator voltage into the mixer grid circuit.

The oscillator is tuned to the low side of the signal frequency on both 50 and 144 Mc., to give slightly better oscillator stability. A VR105-30 voltage-regulator in the power supply adds further to the stability of the oscillator.

The "chassis" on which the converter is assembled is a piece of sheet copper, somewhat less than $\frac{1}{16}$ inch thick, 5 $\frac{1}{2}$ inches long, and bent as shown in the photographs. The width on top is 1 $\frac{3}{4}$ inches, the height 2 $\frac{1}{4}$ inches, and the bottom lip, for fastening to the main chassis, is $\frac{3}{4}$ -inch wide. The tubes are mounted on top near the bent edge, allowing just enough room to insert the socket mounting ring, and are 1 $\frac{3}{4}$ inches apart, center to center, with the r.f. tube 1 $\frac{3}{8}$ inches in from the rear edge. The coil sockets are mounted on the side, $\frac{3}{4}$ inch down from the top, so that connections between the socket prongs and the tuning condenser terminals can be made very short. The lead from the stator connection on the condenser to the grid prong on the tube socket is only about $\frac{1}{4}$ -inch long.

In building an assembly of this type it is a

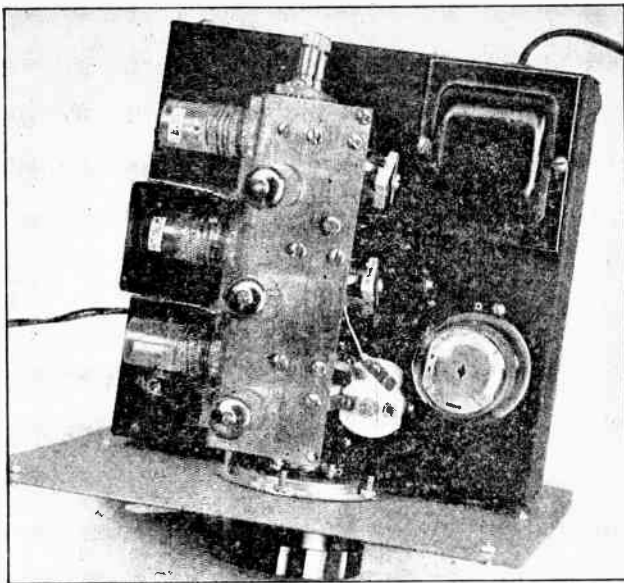


Fig. 1524—A top view of the converter, showing arrangement of tubes and coils. The shaft projecting through the main chassis at the lower left is the i.f. transformer tuning control. The power transformer is sub-mounted so it does not interfere with adjustment of the r.f. trimmer.

practical necessity to do all the wiring before the tuning condensers are mounted. The inside view gives some idea of the arrangement of by-pass condensers; the chief consideration in placing them is to eliminate leads, insofar as possible. Each stage has its own ground point, which, in the case of the r.f. and mixer stages, is on the side of the chassis directly below the tube socket and the length of the cathode by-pass condenser away from it. The screws which hold the ground lugs in place are threaded into the copper, and on the outside also help support the vertical interstage shields. The oscillator ground is also on the side but close to the cathode pin, which is grounded directly; the plate by-pass condenser, C_{13} , is brought to the same point. In the other two stages the ground leads from the tuned circuits are strips of thin copper, $\frac{3}{8}$ -inch wide, this being used in preference to wire to reduce the inductance.

Care must be used in making soldered connections on the polystyrene sockets and forms, since the material will soften with the application of heat. Have all surfaces well cleaned before attempting to solder the connections, and heat the lugs only enough to get a good joint.

In assembling the tuning-condenser gang, the screw-on shafts are likely to come loose unless they are anchored. Soldering is about the simplest scheme. It is important to line up the shafts of the three condensers accurately so that the rotors will turn freely. Any twist, particularly at the oscillator condenser shaft, will tend to bend the rotor out of line slightly with respect to the stator, which means that the assembly will have bad backlash. Similarly, the dial must be lined up accurately with the

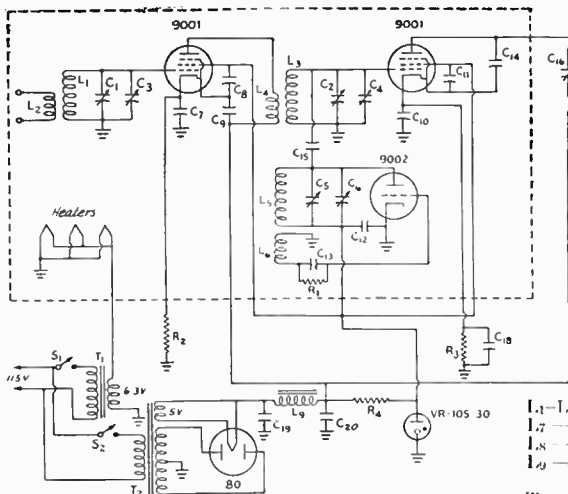


Fig. 1525 — Circuit diagram of the high-performance plug-in coil 50-144-Mc. converter using 9000 tubes.

- C₁, C₂ — 5- μ fd. variable (National UM-15 cut down to 2 plates).
- C₃, C₄ — 3-30- μ fd. mica trimmer.
- C₅ — 8- μ fd. variable (National UM-15 cut down to 3 plates).
- C₆, C₁₆ — 25- μ fd. air trimmer (Hau-marlund APC-25).
- C₇-C₁₂ — 500- μ fd. midget mica.
- C₁₃ — 100- μ fd. mica.
- C₁₄ — 50- μ fd. silvered mica.
- C₁₅ — (See text.)
- C₁₇ — 0.002- μ fd. mica.
- C₁₈ — 0.01- μ fd. 400-volt paper.
- C₁₉, C₂₀ — 8- μ fd. 450-volt electrolytic.
- R₁ — 50,000 ohms, $\frac{1}{2}$ watt.
- R₂ — 1200 ohms, $\frac{1}{2}$ watt.
- R₃ — 10,000 ohms, $\frac{1}{2}$ watt.
- R₄ — 6000 ohms, 10 watt.

- L₁-L₆ — See coil table below.
- L₇ — 18 turns No. 22 c., close-wound on $\frac{5}{8}$ -inch form.
- L₈ — 8 turns similar to L₇, at ground end of L₇.
- L₉ — Filter choke, 8 henrys, 55 ma. (Thordarson T-14C62).
- T₁ — Filament transformer, 6.3 volts, 1.2 amperes.
- T₂ — Power transformer, 280-0-280 volts, 30 ma. (Thordarson T-60R19).
- S₁, S₂ — S.p.s.t. toggle switch.

condenser shafts. First line up the shafts to run as true as possible and then fix the stators where they want to come on the chassis, using shims if necessary.

For electrostatic shielding between the r.f. and mixer stages, two baffle plates are used. One small plate, not visible in the photograph, is fastened to the side of the chassis directly opposite the tube socket and is soldered to the shield cylinder in the center of the socket. It effectively shields the grid wiring from the plate circuit, and is about an inch square. Since it crosses the tube socket and should be placed as close to it as possible, care must be taken to see that the socket prongs are bent away so they cannot touch it. The other shield is almost all on the outside and is used chiefly to prevent electrostatic coupling between the r.f. and mixer trimmer condensers, which are mounted on the sides of the tuning condensers. A transverse shield plate completely boxing off the two stages would be better, but it is an awkward job mechanically in view of the necessity for assembling the condenser gang.

No shielding is required between the mixer and oscillator; in fact, the stray coupling is too small to give good frequency conversion. The trimmer condenser is supported from the top of the chassis by a small bracket made from brass strip, bent to such a size that the rotor connection of the trimmer comes right at the rotor spring on the tuning condenser, where the two are soldered together. A small strip of copper is soldered between the two sets of stator plates, using the soldered mounting on top of the trimmer for its connection. The coupling condenser is a small piece of copper bolted to the trimmer end plate and bent to face the other soldered mounting. The separation is about a sixteenth of an inch.

The vertical shield plates between the coils are $2\frac{3}{8} \times 1\frac{3}{8}$ inches, with bent-over edges to fasten to the side of the chassis. To complete the magnetic shielding the end of the mixer

coil must be boxed in, which is done by a piece of copper in the shape of a shallow U, held in place simply by making it fit tightly between the vertical shields. This piece must be removable for changing the mixer coil.

The bottom view shows the arrangement of the power supply and the i.f. output circuit. The transformer for the latter is wound on a National PRE-3 polystyrene form. It is mounted on a bracket to keep it about equally spaced from the top of the chassis and the bottom of the cabinet in which the chassis fits. The various a.c. and d.c. supply connections from the converter are brought to lug strips, as shown; cathode resistors for the r.f. and mixer stages are mounted where they are readily accessible for trying different values. The power-supply parts are arranged to fit in the remaining space. The rubber feet at the rear of the chassis give a little space for circulation of air, since a fair amount of heat is developed by the transformers and regulator tube.

Alignment of the converter will involve some cut-and-try. It is best to line up the set on 50 Mc. first before tackling the 144-Mc. band. The first step is to make the oscillator cover the proper range, the object being to spread the band over about 75 per cent of the dial scale. With the 10.2-Mc. i.f., the oscillator range, to cover 50 to 54 Mc., will be from 39.8 to 43.8 Mc.; this may be checked on another receiver, if available. If not, probably it will be necessary to use actual signals in the band for the purpose, which also will involve having at least the mixer hooked up. With the circuit specifications given, the oscillator padding condenser should be set at about half-scale. The inductance of L₅ may be adjusted by closing up or opening out the turn spacing, which can be done within limits without moving the ends of

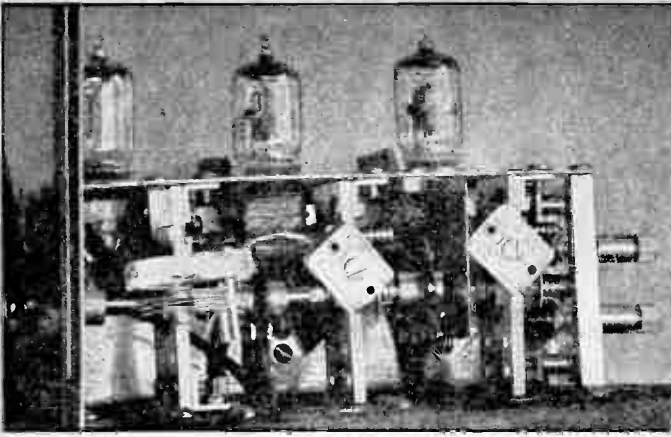


Fig. 1526 — Inside the converter unit, showing arrangement of the tuning condensers. The layout is quite compact, with leads kept as short as possible.

the coil. Once the right spacing is secured, the turns should be cemented in place. An alternative method is to make the coil slightly large and then cut down its inductance with a shorted turn of wire, slid along the coil form.

The oscillator tickler, L_6 , should be adjusted to give stable oscillation without squegging. Squegging is evidenced by a whole series of signals instead of one and can be cured by reducing the feed-back, either by using a smaller number of tickler turns or by moving the tickler further away from the plate coil. Incidentally, the oscillator should deliver a steady d.c. note when heard on another receiver. For this check to mean anything, the receiver used must introduce no modulation on incoming signals.

Once the oscillator range is set, the mixer should be lined up to match. To do this, place the r.f. tube in its socket but connect a resistor of a few hundred ohms from its grid to ground, instead of using L_1 . The mixer primary, L_4 , must be in place, since it will have some effect on the tuning range of L_3C_2 . Connect the r.f. output leads to the doublet posts on the communications receiver, set the latter to 10.2 Mc. and adjust C_{16} for maximum hiss, with the oscillator tube out of its socket. Then replace the tube and, with the oscillator set for 50 Mc., adjust the trimmer, C_4 , for maximum hiss; reset the oscillator to 54 Mc. and readjust C_4 . If more capacity is needed at C_4 , the inductance of L_3 is too large; if less, L_3 is too small. Make an appropriate small change in the coil by the means described above and try again, continuing the process until C_4 peaks at the same setting at both ends of the band.

When this process is finished, C_4 should be well in the air-dielectric portion of its range. Should the movable plate be close to the mica, L_3 is considerably too small. However, this would be accompanied by reduced tuning range on C_2 , and it is doubtful if high padding capacity would permit full band coverage.

The r.f. stage is aligned in the same way as the mixer circuit. During the initial alignment there should be nothing connected to the antenna posts. If oscillation occurs, reduce the size of L_4 until the stage is stable. Some trace of regeneration may remain (indicated by exaggerated peaking of the r.f. stage) but this will disappear when any sort of antenna load is connected.

The procedure for the 144-Mc. coils is similar to that for 50 Mc. It is desirable to adjust the oscillator coil so that the trimmer, C_6 , does not need resetting when changing bands.

COIL DATA

Band	Coil	No. of Turns	Wire Size	Length Inches	Remarks
144 Mc.	L ₁	1 1/8	18	1 5/16	
	L ₂	1 1/8	24		1/8" from L ₁
	L ₃	1 1/8	18	1 5/16	
	L ₄	1 1/8	24	1/8	1/8" from L ₃
	L ₅	1/2	18		
	L ₆	1	24		1/8" from L ₅
50 Mc.	L ₁	4 5/8	18	3/8	
	L ₂	2 7/8	24	1/8	1/8" from L ₁
	L ₃	4 1/2	18	7/16	
	L ₄	2 7/8	24	1/8	1/8" from L ₃
	L ₅	3 5/8	18	3/8	
	L ₆	2 7/8	24	5/32	1/8" from L ₅

All coils wound on 3/4-inch diameter forms (Amphenol type 24-5H, 5-prong).

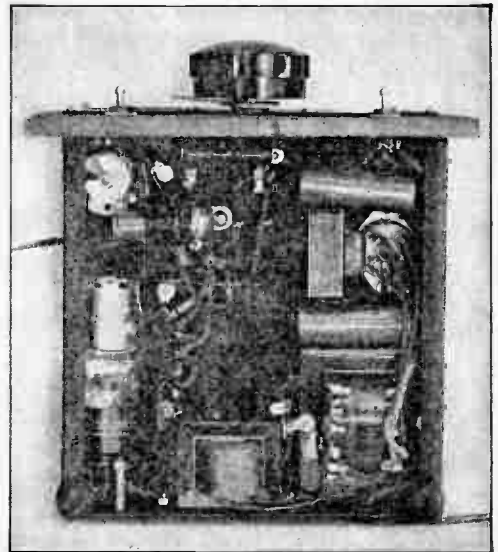


Fig. 1527 — The converter power supply occupies the right-hand section of the chassis in this bottom view. The i.f. output section is in the upper left-hand corner.

◄ F.M. I.F. Amplifiers

As was pointed out earlier in this chapter, an f.m. superheterodyne receiver differs from an a.m. receiver mainly in that the pass-band of the intermediate-frequency amplifier must be wider, and in that a limiter and discriminator are used instead of a second detector. The front end of an f.m. receiver usually follows the conventional pattern, and any v.h.f. converter can be used for the purpose if its output frequency is that of the i.f. amplifier.

The f.m. i.f. amplifier employed with the converter may be either the i.f. amplifier of a standard f.m. broadcast receiver or one built especially for the purpose by the amateur himself.

If the i.f. system of an f.m. broadcast receiver is used, the intermediate frequency should first be determined so that the output of the converter can be designed to tune to this frequency and coupled to the grid of the mixer tube of the receiver. The i.f. amplifiers of most f.m. broadcast receivers currently in use are designed to operate on a frequency in the vicinity of 5 Mc. although earlier models may be found with i.f.s as low as 3 Mc. In a few instances higher i.f.s of the order of 8 to 10 Mc. may be encountered. If the output transformer in an existing converter does not tune to the required frequency, it is usually feasible to add or remove enough turns from the coil to enable it to be tuned to the receiver i.f. A change in the h.f. oscillator tuning will also be required.

For operation on the 144-Mc. band or higher, a system of the double superheterodyne type

may be desirable if the f.m. receiver's i.f. is lower than 5 Mc. In that case, a simple 6K8 oscillator-mixer might be used as an intermediate converter operating on 10 or 20 Mc.

◄ A 5-Mc. F.M. I.F. System

The i.f. amplifier shown in Figs. 1528, 1529 and 1530 is a broad-band combination affair working on 5 Mc. which can be used for either f.m. or a.m. reception merely by switching the connection to the grid lead of the first audio tube from across the discriminator load (for f.m.) to the limiter grid resistor (for a.m.).

With any converter or combination capable of working into a 5-Mc. amplifier, this system can be used for the reception of a.m. and f.m. signals in the 88-Mc. band, a.m. and f.m. amateur signals in the 56-Mc. band, or f.m. and a.m. signals in the 144-Mc. band. When operators of 144-Mc. stations using modulated oscillators reduce the modulation percentage and thus bring the frequency deviation down to a reasonable range, the system constitutes an excellent receiver for the reception of modulated-oscillator transmissions. When operated with reduced modulation even the smallest transceiver will sound many times better; moreover, audio power will be saved.

As shown in Fig. 1529, the two stages of high-gain amplification using 6AC7/1852 tubes are unconventional only in that resistors are used across the transformer windings to widen the pass band, and no gain control is included. No means of controlling gain is required, because it is always desirable to work the stages preceding the limiter at their highest level.

The limiter stage uses a 6SJ7, with provision through a variable resistor, R_{18} , to control the plate and screen voltage to set the limiting action to meet operating conditions. The use of a grid leak and condenser, R_{16} and C_7 , together with the low screen and plate voltages allows the tube to saturate quickly, even at low signal levels, and the tube wipes off any amplitude modulation (including noise) and passes only frequency modulation. For a.m. reception, the audio system is switched by Sw_1 to the grid leak, R_{16} , and the grid and cathode of the tube are used as a diode rectifier to feed the audio system. The jack, J , in series with the grid leak, is used for plugging in a low-range milliammeter so that the limiter current can be read. The limiter-current indication is invaluable in aligning the amplifier, and the meter can be used as a tuning meter during operation.

The discriminator circuit uses a 6H6 double diode in the conventional circuit. Audio from the discriminator (or from the limiter stage, in a.m.

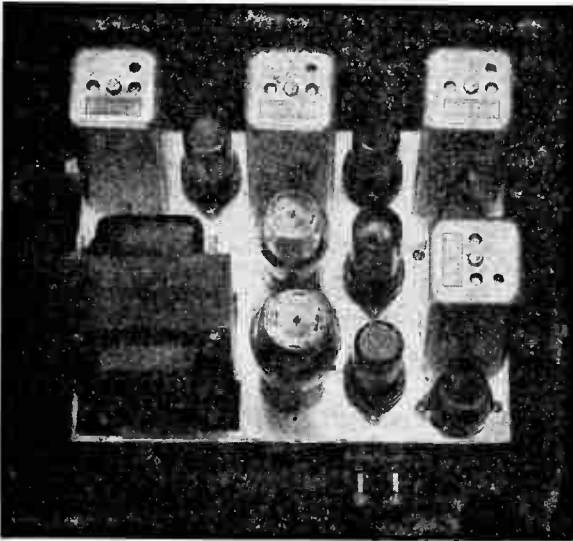


Fig. 1528 — A top view of the f.m./a.m. amplifier. Along the rear, from left to right, are the input transformer, first 1852 tube, interstage transformer, second 1852 tube, and second interstage transformer. In the second row of tubes, from right to left, are the 6SJ7 limiter, 6F6 audio output and VR150-30 voltage regulator. At the right front is the discriminator transformer, with the 6H6 detector below it. To the left of the 6H6 is the 6SF5 first audio. Output terminals, power socket, and 115-volt line cord are on the lower edge.

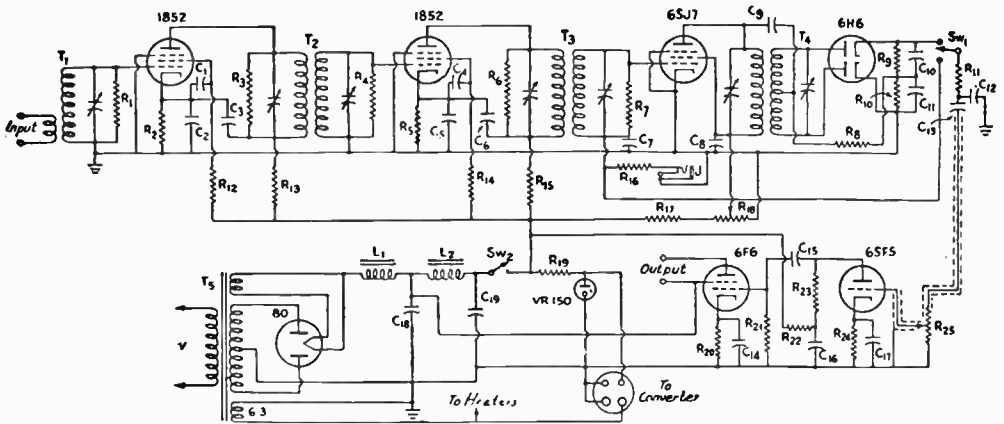


Fig. 1529 — Wiring diagram of the broad-band 5-Mc. f.m./a.m. i.f. amplifier.

- | | | |
|---|---|---|
| $C_1, C_2, C_3, C_4, C_5, C_6, C_8, C_{13}, C_{15}$ — 0.01- μ fd. 600-volt paper. | R_9, R_{10}, R_{16} — 0.15 megohm, $\frac{1}{2}$ -watt. | T_2, T_3 — 5-Mc. f.m. interstage i.f. transformer (Millen 67503). |
| C_7, C_{10}, C_{11} — 100- μ fd. midget mica. | R_{12}, R_{14} — 60,000 ohms, $\frac{1}{2}$ -watt. | T_4 — 5-Mc. f.m. discriminator transformer (Millen 67504). |
| C_9 — 50- μ fd. midget mica. | R_{13}, R_{15} — 100 ohms, $\frac{1}{2}$ -watt. | T_5 — 350-0-350-volt 90-ma. power transformer with 6.3- and 5-volt filament windings. |
| C_{12} — 0.001- μ fd. midget mica. | R_{17} — 25,000 ohms, 10-watt wire-wound. | I_1 — 9-henry 85-ma. filter choke (Thordarson T-13C29). |
| C_{14}, C_{17} — 10- μ fd. 25-volt electrolytic. | R_{18} — 3000-ohm wire-wound potentiometer. | I_2 — 10-henry 65-ma. filter choke (Thordarson T-13C28). |
| C_{16}, C_{18}, C_{19} — 16- μ fd. 450-volt electrolytic. | R_{19} — 5000 ohms, 10-watt wire-wound. | Sw_1 — S.p.d.t. switch (Yaxley 32112-J). |
| R_1, R_4 — 55,000 ohms, $\frac{1}{2}$ -watt. | R_{20} — 500 ohms, 1-watt. | Sw_2 — S.p.s.t. toggle switch. |
| R_2 — 200 ohms, $\frac{1}{2}$ -watt. | R_{21}, R_{23} — 0.25 megohm, $\frac{1}{2}$ -watt. | J — Closed-circuit jack. |
| R_3, R_6 — 50,000 ohms, $\frac{1}{2}$ -watt. | R_{24} — 5000 ohms, $\frac{1}{2}$ -watt. | |
| R_5 — 300 ohms, $\frac{1}{2}$ -watt. | R_{25} — 0.5-megohm volume control. | |
| R_7 — 40,000 ohms, $\frac{1}{2}$ -watt. | T_1 — 5-Mc. i.f. input transformer (see text) (Millen 67503). | |
| R_8, R_{11}, R_{22} — 75,000 ohms, $\frac{1}{2}$ -watt. | | |

reception) is fed through the volume control, R_{25} , into a two-stage audio amplifier using a 6SF5 and 6F6 output pentode. The resistor, R_{11} , and condenser, C_{12} , in the audio input circuit, serve as a combined r.f. filter and compensating network to attenuate the higher audio frequencies. This is necessary when listening to 88-Mc. broadcast stations, since all use "predistortion" (accented higher frequencies). A 0.01- μ fd. condenser across the output terminals will give further high frequency compensation, if necessary.

The amplifier is built on a $7 \times 9 \times 2$ -inch chassis. Reference to Figs. 1528 and 1530 will show the location of the parts on the chassis. After all holes have been drilled the sockets and the transformer should be fastened in place on the chassis, leaving off the variable resistors, switches, binding posts, jack and chokes until after most of the wiring has been done.

If low-impedance input coupling is to be used, as with a converter removed some distance from the amplifier, the first i.f. transformer must be modified. A link winding is made by first winding a short half-inch wide strip of paper over the cardboard tubing used as a former in the i.f. transformer. Eleven turns of No. 30 d.s.c. wire are then close-wound flat over the center of the paper ring. Holding the wire in place with a finger, paint the coil with Duco cement to secure the turns in place. When the cement has dried, slip the coil

off the form. The plate and "B+" wires may be removed from the trimmer condenser in the transformer, and the wires from the plate coil to the trimmer condenser disconnected. By unwinding and cutting off a turn or two of paper from the inside of the paper ring, the 11-turn coil can be slipped easily over the grid coil and fastened in position so that it covers the ground end of the grid coil. A piece of paper between the grid coil and the ground lead will avoid any possibility of this lead shorting against the turns of the coil when the paper ring is slipped in place. The two ends of the link are brought out at the bottom of the shield can, later to be wired to the input terminals of the amplifier unit.

It is possible to use the transformer by merely running the plate lead to the mixer tube in the converter, but this makes it less convenient to use the converter with other i.f. amplifiers since it requires soldering and unsoldering wires each time a change is made. A long lead to the mixer tube also would increase the likelihood of stray pick-up of signals near 5 Mc.

The screen by-pass condensers, C_1, C_4 and C_8 , are placed across the sockets to serve as partial shields between the plate and grid terminals of the single-ended tubes. Tie-points are used wherever needed for mounting the resistors and condensers. The 6AC7/1852, 6SJ7 and 6H6 stages are wired first, so that all leads carrying r.f. can be made as short and direct as possible. The remaining wiring is filled in wherever convenient. The leads from the audio

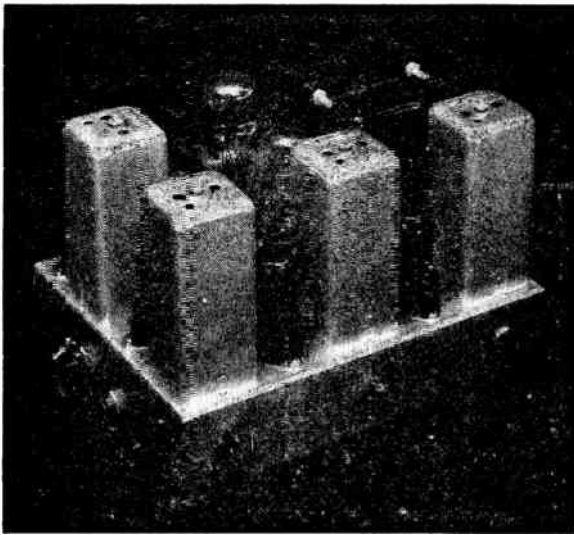


Fig. 1530 — A 5-Mc. f.m./a.m. amplifier complete with power supply. Controls on the front, from left to right, are the audio volume control, "B" + switch, and the limiter control. The f.m./a.m. switch is on the end. The jack beside it is for the limiter-current meter.

volume control, R_{25} , are shielded by a length of flexible copper braid. Whenever convenient, spare terminals on sockets are used to support fixed resistors, condensers, etc.

With a 5-Mc. signal source, preferably a signal generator, alignment of the amplifier is an easy matter. If no such source is available a simple e.c.o. can be built using an ordinary receiving pentode such as a 6K7, with the grid circuit on 2.5 Mc. and the plate on 5 Mc. Or, if a converter is available, tune the regular receiver to 5 Mc., couple in the converter and tune in a strong, steady signal. The converter output can then be transferred to the f.m./a.m. i.f. and the transformers aligned. This is done by plugging a 0-1 ma. meter into the jack, J , and tuning the trimmers of the transformers for maximum current. It may be necessary to hunt around a bit before the meter shows any indication, but once it starts to read the rest is easy. With a variable-frequency signal source the signal is swung back and forth until some indication is obtained, and then the amplifier alignment is completed. The exact frequency of alignment is unimportant provided every stage can be tuned *through* resonance, which means that each trimmer can be adjusted through a maximum reading of the tuning meter. With the resistors across the circuits, it will be found that the transformers tune somewhat broader than normal; the correct setting is in the midpoint of the broad region. Once the i.f. transformers, T_1 , T_2 and T_3 , are aligned, it should be possible to switch Sw_1 to a.m. reception and hear signals, or at least noise, provided the converter is on 50 or 88 Mc. There isn't much noise to be heard on 144 Mc. except automobile ignition.

The alignment procedure can be carried out with a loudspeaker connected to the 6F6 through an output transformer. If no speaker is used at this point, however, the output terminals should be shorted; otherwise, the 6F6 may be injured. The use of a meter for alignment is a practical necessity, and no attempt should be made to line up the amplifier by ear except possibly for only a very rough initial alignment.

If there is an f.m. broadcast station within range, adjustment of the discriminator transformer, T_4 , is a simple matter. Switch the amplifier to a. m., plug in the proper coils in the converter, and tune in the f.m. station. Then switch the amplifier to f.m. and tune the trimmers on T_4 until the signal reappears. This is best done with the audio gain almost open and the limiter control at about half-scale. Use an insulated alignment tool, to reduce body capacity effects, and adjust the trimmers until the b.c. signal is clearest and loudest. It will be found that the plate-circuit trimmer will affect the volume

most, while the diode trimmer will have a greater effect on the quality. During this adjustment the receiver should be kept tuned exactly to the signal, as indicated by maximum limiter current. An audio output meter may be used to indicate maximum audio output, if available, but it is not essential.

In the event that there is no local f.m. broadcasting station, the amplifier can be aligned on a local amateur f.m. station if it is one with good stability and not too much deviation. A 144-Mc. modulated oscillator is not recommended unless it is running well under rating, because usually it is modulated too heavily and also doesn't stay on one frequency long enough to allow the amplifier to be aligned properly.

If a stable amplitude-modulated signal, modulated by a single tone, is avoidable either at i.f. or single frequency, the discriminator can be aligned fairly well by first detuning the secondary of T_4 and, with the signal peak through the amplifier as indicated by maximum limiter current, then peaking the primary of T_4 for maximum audio output. The secondary of T_4 is then brought into tune, and resonance will be indicated by a sharp null in the audio output. If the test signal is then detuned just enough to bring back the signal a bit, the primary of T_4 can be trimmed for maximum output. Then setting the test oscillator back to the frequency that gives maximum limiter current, the secondary may require slight trimming to give a null. At this second trimming, the discriminator will be aligned.

The final adjustment of the discriminator tuning can be checked by tuning in an a.m.

signal. If the discriminator is properly tuned, the audio output (signal and noise) should practically disappear at the point where the signal, as indicated by limiter current, is a maximum. This is an indication that the discriminator characteristic crosses the axis at the mid-resonance point of the amplifier. Tuning the signal (by tuning the converter), it should be possible to understand the audio output at points either side of this minimum-volume setting. These points should appear symmetrically on either side of the minimum-volume point and should have about the same volume. Slight readjustment of the discriminator-transformer setting will accomplish this result.

In using the amplifier it may be observed that a.m. signals appear to be louder than those from f.m. stations, comparing audio volume-control settings on stations showing equal limiter current. This does not indicate that the amplifier is not working properly or that more audio is obtained on a.m. than from an f.m. signal of similar strength. It is, rather, an indication that the discriminator characteristic should have a steeper slope and that the peaks are too far apart.

The performance of the amplifier on a.m. reception could be improved somewhat by applying a.v.c. to the two 6AC7/1852 tubes, taking the a.v.c. voltage from the limiter grid leak through the usual filter circuit. However, this is an unnecessary refinement if the amplifier is intended to be used primarily on f.m. since the amplifier should always be run "wide open" for f.m. reception.

The use of an f.m. i.f. amplifier of this type, in conjunction with a suitable converter, is highly recommended for reception of modulated-oscillator signals such as are common on the 144-Mc. and higher-frequency bands. If the received station holds down its modulation to the point where the signal just fills the pass band of the i.f. amplifier, best quality and signal-to-noise ratio will be obtained. Under these conditions weaker signals can be received more intelligibly than with the simpler types of receiving systems, and one's receiving range can be extended considerably. On the 50- and 28Mc. bands, the discrimination against automobile ignition noise obtained with f.m. reception is a definite advantage if one is troubled by ignition interference.

V.H.F. Transmitters

THE very-high frequency region is generally considered to have its lower frequency limit in the vicinity of the 28-Mc. band, and it is also in about this region that it becomes desirable to adopt more compact methods of construction and to select tubes with particular care. As the frequency becomes higher the length of connecting leads becomes more important, because a length of a few inches may represent a considerable fraction of the operating wavelength. Tube interelectrode capacities, as well as the usual stray capacities, must be given particular attention. Unduly high shunt capacity in the circuit not only may reduce the efficiency but also will ultimately set the upper limit of frequency at which the transmitter can be made to work. For best results at very-high frequencies, tubes designed to operate well in that region must be used. All of these considerations indicate the advisability of building separate r.f. equipment for transmission at very-high frequencies, rather than attempting to adapt for v.h.f. use a transmitter primarily designed for operation at ordinary frequencies.

Transmitter stability requirements for operation in the 50-Mc. band are the same as for the lower-frequency bands. Above 144 Mc. there are no restrictions as to frequency stability except that the whole of the emission must be confined within the band limits. Modulated-oscillator type transmitters therefore can be used above 144 Mc. and, in fact, constitute a large proportion of the amateur transmitters working in the 144-Mc. and higher-frequency bands. However, up to the 50-Mc. band methods similar to those employed in the transmitters described in Chapter Thirteen are generally used. By proper choice of tubes and circuits, crystal control is applicable to 144 Mc. as well; this is also true of the band at 220 Mc., but the limited use that has been made of this and higher-frequency bands has deferred the necessity for a high degree of transmitter stability — a necessity that always arises once the exploratory period is over and a band begins to have substantial occupancy.

In the v.h.f. and u.h.f. regions, frequency modulation as well as amplitude modulation is permitted by the amateur regulations. Most of the 50-Mc. transmitters shown in this chapter are crystal controlled, for use with amplitude modulation. However, they can be adapted for f.m. by replacing the crystal with excitation from a frequency-modulated oscillator similar to that described later in the chapter.

The transmitters shown in this chapter are designed for the new v.h.f. and u.h.f. frequency allocations. As of the date of going to press amateurs are operating temporarily on the prewar 56- to 60-Mc. band in lieu of the new assignment from 50 to 51 Mc., pending a shift of other services to new frequencies. It is expected that the new 50-Mc. band will be opened for amateur use early in 1946.

As of this writing, a few of the bands above 200 Mc. have not yet been released. Before putting a transmitter on the air in this frequency range be sure to check the status of the band you want to use. Up-to-date information can be secured from *QST* or by dropping a postcard to A.R.R.L., West Hartford 7, Conn.

Above 300 Mc. it is no longer possible to use standard types of transmitting tubes with any degree of success. Instead, special tubes designed for the ultra-high frequencies must be used. Such tubes have extremely close spacing between elements to reduce transit-time effects, and are constructed with leads having virtually no inductance so that the circuit is not, as a matter of necessity, entirely within the tube itself. The problem of making suitable tubes has been solved in two ways: by adopting the "acorn" type of construction, using miniature tube elements with leads brought out through the envelope in as short and direct a manner as possible, and by designing tubes of the "lighthouse" variety in which larger elements have disc-type leads of extremely low inductance. Acorn tubes, because of their small size, are limited to a few watts in power-handling capacity. The lighthouse or disc-seal types are available in sizes capable of handling up to 100 watts or so with forced-air cooling. Acorn tubes can be made to oscillate at frequencies up to the vicinity of 1000 megacycles, while disc-seal tubes will function to about twice that frequency.

Above about 2000 Mc. the most useful present types of tubes are the klystron and the magnetron. These are essentially one-band devices, the frequency-determining circuits being an integral part of the tube. Tuning over a small frequency range — such as an amateur band — is possible, but the tubes are by no means independent of frequency in the sense that tubes of more conventional design are independent. The newly-opened amateur bands in the ultra-high and superhigh regions, as yet practically

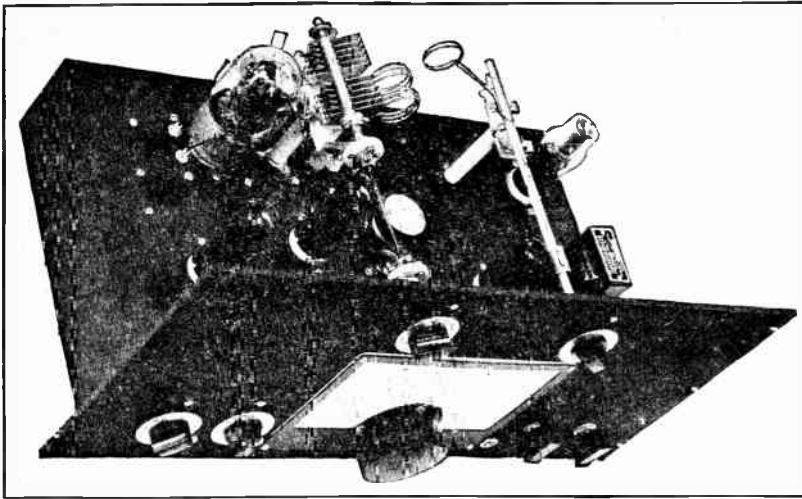


Fig. 1601
Front view of 50-Mc. a.m./f.m. transmitter. The r.f. section of unit occupies the left-hand portion of the chassis. The VR-150, 6SA7 reactance modulator, and microphone transformer are at the right. Note neutralizing capacity wires at the left of the 815.

unexplored by amateurs, offer possibilities of great interest to the experimentally inclined.

□ A 40-watt A.M.—F.M. 50-Mc. Transmitter

The transmitter shown in Figs. 1601-1603, inclusive, has an output of approximately 40 watts in the 50-Mc. band and is so designed that either frequency or amplitude modulation may be used. Aside from power supplies, no auxiliary apparatus is needed for f.m. transmission, since the primary frequency control is a variable-frequency oscillator and a reactance modulator is included in the unit. For amplitude modulation, a modulator having an audio power output of about 30 watts is required.

As an alternative to electron-coupled v.f.o. control, provision also is made for crystal control, using a Tri-tet oscillator. As shown in the circuit diagram, Fig. 1602, the crystal oscillator and c.c. oscillator have a common plate circuit, the frequency being doubled in this circuit in both cases. The oscillators are followed by a 6V6 doubler, and this in turn drives the final amplifier, an 815.

The tuned circuits are designed to cover a little more than the range required for the 50-Mc. band so that the transmitter as shown can be used to drive a power frequency multiplier tripling into the 144-Mc. band. The v.f.o. grid circuit tunes from 12 to 13.5 Mc., the range from 12.5 to 13.5 Mc. being used for the 50-Mc. band, and the range from 12 to 12.35 Mc. being available for the 144-Mc. band. When crystal control is to be used, frequencies within the appropriate ranges should be selected, since the oscillator portion of the Tri-tet circuit works over the same frequency range as the grid circuit of the v.f.o. The common oscillator plate circuit tunes to the second harmonic of the range, or from 24 to 27 Mc., while the 6V6 doubler output circuit is tunable from 48 to 54 Mc. Either oscillator may be selected by means of a switch, S_2 , which closes

the cathode circuit of the desired oscillator tube. To prevent any possibility of accidental frequency modulation when amplitude modulation is being used, a three-position switch is employed, giving a front-panel choice of either crystal or v.f.o. control for a.m. or c.w., or v.f.o. control with f.m.

Stability under changes in supply voltage is attained by supplying the v.f.o. screen from a VR-150. This holds the screen voltage at 150 when the plate voltage is varied from 150 to 600 volts. The cathode current to the oscillator, measured in J_2 , remains practically constant when the plate voltage is varied over this wide range, and the total frequency shift is only a few hundred cycles. With variations in plate voltage which would result from even the most severe line-voltage fluctuations, the frequency shift in the oscillator is only a few cycles.

Other sources of v.f.o. instability are excessive tube and component heating, variations in circuit capacity due to non-rigid mechanical design, and interaction because of improper placement of components. In this design, oscillator input is held to less than half the rated plate dissipation of the tube, keeping drift due to tube heating to a minimum. All circuit components are mounted below the chassis, away from the heat given off by the metal tubes, and in such position as to prevent interaction so far as possible without extensive shielding. A silvered-mica fixed condenser is used in parallel with the grid coil, and rigid components are used throughout. The result of these precautions is a v.f.o. whose stability compares favorably with that of the associated crystal oscillator.

The transmitter is built on a 10 × 17 × 3-inch chassis, with all components except tubes, crystal and the final-stage output circuit mounted below the deck. Viewing the unit from the top front, the microphone transformer and 6SA7 reactance modulator are at the right

front, with the VR-150 at the rear, adjacent to the antenna coupling assembly. The crystal, crystal oscillator, and v.f.o. are grouped near the middle of the chassis, with the doubler and final tubes at the left.

The front panel is a standard $8\frac{3}{4} \times 19$ -inch crackle-finished masonite unit. The v.f.o. tuning dial is centrally placed, with the oscillator and doubler tuning condensers at the left, and the a.m./f.m. switch and deviation control at the right. The final plate tuning knob is above the v.f.o. dial, at the left, and the swinging-link adjustment is at the right. Jacks, from left to right, are J_1 , J_3 , J_2 and J_4 .

R.f. wiring is of No. 16 and 18 tinned wire, with other circuits being wired with No. 18 "push-back." R.f. leads should be made as short and direct as possible, though the balance of the wiring may be arranged for neatness.

The two wires protruding through the chas-

sis close to the 815 are neutralizing "condensers," labeled C_{n1} and C_{n2} on the schematic diagram. They consist of two pieces of No. 14 enameled wire, soldered to the grid prongs of the 815 socket, crossed under the chassis, and brought through the chassis and held in position by two small isolantite feed-through bushings (Millen 32150).

Adjustment is simple and straightforward. The tuning range of the v.f.o. should be checked first. This may be done with only the two oscillator tubes in place, and the a.m./f.m. switch on the v.f.o. position. The oscillator plate condenser should be tuned for maximum r.f. indication in a neon bulb adjacent to L_2 , and the frequency checked in a receiver having a fairly accurate calibration for the region around 12, 24, or 48 Mc.

The size of the v.f.o. grid coil, L_1 , is extremely critical, and if some pruning of this

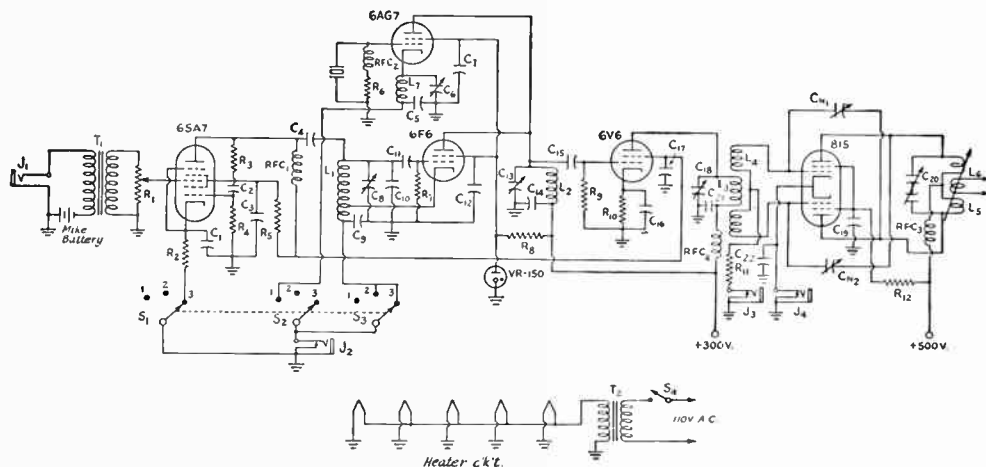


Fig. 1602 — Wiring diagram of 50-Mc. a.m./f.m. transmitter.

- C_1 — 0.01- μ fd. 400-volt paper tubular.
- C_2 — 0.001- μ fd. mica.
- C_3 — 8- μ fd. 150-volt electrolytic and 0.005- μ fd. mica in parallel.
- C_4 , C_{19} — 500- μ fd. mica.
- C_5 , C_7 , C_9 , C_{12} , C_{14} , C_{16} , C_{17} , C_{21} , C_{22} — 0.002- μ fd. mica.
- C_6 — 100- μ fd. midget variable, screwdriver adjustment (Hammarlund APC-100).
- C_8 — 50- μ fd. variable, "straight-line-frequency" type (Hammarlund MC-50-M).
- C_{10} — 100- μ fd. and 50- μ fd. in parallel (Sickles Silver-cap). See text.
- C_{11} — 100- μ fd. mica.
- C_{13} , C_{18} — 50- μ fd. variable (Hammarlund MC-50-S).
- C_{15} — 50- μ fd. mica.
- C_{20} — 35- μ fd. per section, split stator (Hammarlund MCD-35-MN).
- C_{n1} , C_{n2} — Neutralizing capacity. See text.
- R_1 — 0.5-megohm volume control, switch type.
- R_2 — 750-ohm, $\frac{1}{2}$ -watt.
- R_3 — 50,000-ohm, $\frac{1}{2}$ -watt.
- R_4 , R_6 — 0.25-megohm, $\frac{1}{2}$ -watt.
- R_5 — 5000-ohm, $\frac{1}{2}$ -watt.
- R_7 , R_9 — 0.1-megohm, $\frac{1}{2}$ -watt.
- R_8 — 5000-ohm, 5-watt.
- R_{10} — 250-ohm, 1-watt.
- R_{11} — 15,000-ohm, 1-watt.

- R_{12} — 15,000-ohm, 5-watt.
- RFC_1 , RFC_2 , RFC_4 — 2.5-m.h. r.f. choke (National R-100).
- RFC_3 — 2.5-m.h. r.f. choke, end mounting (National R-100-U).
- J_1 — Open-circuit jack.
- J_2 , J_3 , J_4 — Closed-circuit jack.
- S_1 , S_2 , S_3 — 3-position, 3-contact rotary switch (Mal-lory).
- S_4 — Switch on deviation control, R_1 .
- T_1 — Single-button microphone transformer (Thordar-son T-83A78).
- T_2 — 6.3-volt, 4-amp. filament transformer.
- L_1 — 8 turns No. 18 tinned, $\frac{3}{4}$ -inch diameter, 1-inch length, on National PRF-2 form.
- L_2 — 10 turns No. 14 e., $\frac{1}{2}$ -inch diameter, spaced one diameter, air-wound.
- L_3 — 4 turns, No. 14 e., $\frac{1}{2}$ -inch diameter, spaced one diameter, air-wound.
- L_4 — 5 turns each section, No. 14 e., $\frac{1}{2}$ -inch diameter. Adjust spacing for best transfer of energy. See text.
- L_5 — 3 turns each section, No. 12, tinned, $1\frac{1}{8}$ -inch diameter, spaced one diameter.
- L_6 — 2 turns No. 14 e., 1-inch diameter, swinging link. See photos and text.
- L_7 — 35 turns, No. 24 d.c.c., close-wound on 9/16-inch diameter form (National PRE-3).

coil is to be avoided it would be advisable to make the 50- μ fd. section of C_{10} an adjustable padder condenser, such as a Hammarlund APC-50, which can then be adjusted until 12 Mc. appears at about 90 on the v.f.o. vernier dial. The high-frequency limit, 13.5 Mc., should then come at approximately 10, giving a spread of about 18 divisions for the 141-Mc. band and 54 divisions for the 50-Mc. band. Without such a variable condenser, the number of turns on L_1 must be adjusted by cut-and-try until the proper tuning range is secured. In either case, the final adjustment of band coverage should be made with the 6SA7 reactance modulator in its socket so that its plate-to-ground capacity will be across the tuned circuit.

Operation of the crystal oscillator may next be checked. With a 100-ma. meter connected through J_2 , and the a.m./f.m. switch on the "crystal" position, adjust the crystal-oscillator cathode tuning, C_6 , until the current dips sharply, indicating oscillation. This control should be set at the point which gives the lowest cathode current consistent with easy crystal starting. Cathode current should be similar for both oscillators — about 20 ma.

The doubler stage may next be tested by installing the 6V6 and 815 tubes, leaving the plate power off the 815. A meter having a 10-ma. range should be used to measure the grid current in the 815, at J_3 . The current should come up to about 6 ma. when the spacing between L_3 and L_4 is optimum, though this is more than is actually needed for satisfactory operation of the 815.

Next the position of the neutralizing wires can be adjusted. The 815 plate tuning condenser, C_{20} , should be rotated slowly, meanwhile watching the grid current for any varia-

tion. The position of the neutralizing wires should be adjusted until there is no sign of fluctuation in grid current as the tuning condenser is rotated. A length of wire extending about one inch above the metal ring on the 815, at a position about $\frac{3}{8}$ inch from the glass envelope, should be sufficient. If this should be inadequate, small tabs of copper or brass can be soldered to the ends of the wires to make additional capacity to the tube plates. The neutralizing capacity is necessary in order to ensure completely stable operation.

After neutralization, power may be applied to the 815 plates, while noting the cathode current as indicated on a 200-ma. meter plugged into J_4 . The dip at resonance should bring the current to about 50 ma. with no load. A 25-watt lamp connected across the swinging link terminals should then give a full-brilliance indication when the link is adjusted for maximum coupling. This is with 500 volts applied, which should be used only after it has been determined that everything is functioning properly. If trouble is encountered, further tests should be made with reduced voltage to avoid damaging the tube.

When the transmitter is put on the air, the full 500 volts at 150 ma. may be used for f.m. or c.w. operation. For plate modulation, the voltage should be reduced to about 400 for maximum tube life, even though the tube plates may show no color at the higher voltage.

For frequency modulation, the 6SA7 reactance modulator provides the simplest possible means of obtaining the desired swing in frequency. It may be operated with a single-button microphone plugged into J_1 , or the modulator may be driven from a speech amplifier and crystal or dynamic microphone. The

output of the speech amplifier should then be connected across potentiometer R_1 , and T_1 may be omitted. In either case, R_1 serves as a deviation control, the swing being adjusted to suit the receiver at the station being worked.

In addition to the filament transformer, T_2 , indicated in the circuit diagram, the transmitter requires two plate power supplies. One, for the 815, should have an output of 400 to 500 volts at 175 ma.; the other, for the remaining tubes, should deliver 300 volts at approximately 100 milliamperes.

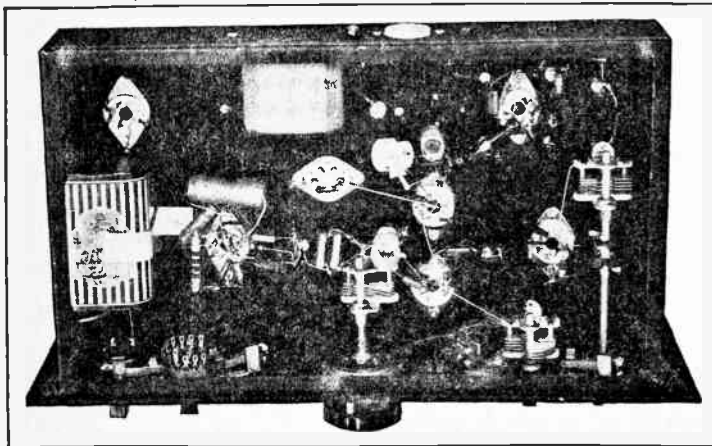


Fig. 1603 — Under-chassis view of the 50-Mc. a.m./f.m. transmitter. At the lower center are the v.f.o. grid coil and associated components. Over these are the crystal and cathode circuit for the 6AG7 crystal oscillator. At the upper right are the inductively-coupled doubler plate coil and final grid coil. The coil and condenser at the lower right comprise the plate circuit which is common to both oscillators. The doubler plate tuning condenser is at the far right.

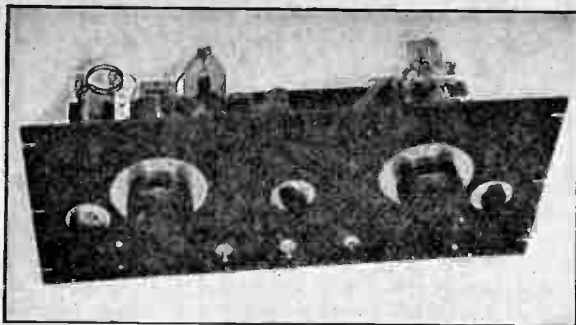


Fig. 1604—Front view of the 300-watt driver-amplifier for 50 and 144 Mc. The two large dials are the plate tuning controls. The small dial at the left adjusts the position of the output coupling link, the center dial is the grid tuning control for the final, and the third small dial is the tripler grid tuning control. Across the lower center are the filament switches and grid current meter jack.

300-watt Driver-Amplifier for 50 and 144 Mc.

A companion high-power driver-amplifier for the 50-Mc. transmitter described in the preceding section is shown in Figs. 1604 to 1607, inclusive. The amplifier uses a pair of 35TG tubes in push-pull while the driver, a frequency tripler used for 144 Mc. only, is a single 35TG. If operation on 144 Mc. is not desired the driver may be omitted, in which case everything to the left of terminals *B-B* in the circuit diagram, Fig. 1606, may be ignored.

Looking at the front-panel view, the two large dials are the plate tuning controls for both stages. The small dial at the left controls the swinging link, the center dial is the grid tuning control for the final stage, and the one at the far right is the tripler grid tuning control. All parts are mounted well back from the panel, and lucite rods are used for extension shafts.

The rear view shows the general placement of parts. At the left, attached to the back of the $7 \times 17 \times 3$ -inch chassis, is the jack bar containing terminals *A-A* and *C-C*, into which the link from the exciter is plugged to furnish drive for either the tripler or final. The tripler grid coil, L_1 , is just above the link socket, with the plate condenser, C_5 , and coil, L_2 , for this stage between the tube and the front panel. The link between L_3 and L_2 is a plug-in affair, and its socket (which is a mechanical mounting only) is between the tripler plate and final grid condensers. Between the grid tuning condenser and the final tubes are the ganged neutralizing condensers. These are triple-spaced midget condensers mounted back to back with coupled shafts. The final tank condenser is mounted as closely as possible to the two tubes, at the right. The jack bar for the final plate coil and the home-made swinging link assembly are at

the far right. All components are mounted as close together as possible without being so crowded that tubes cannot be removed from the sockets.

When the amplifier is to be used on 50 Mc. the switch S_1 is left open so that the filament of the tripler will not light when S_2 is closed. The link from the exciter is plugged into terminals *C-C* in the jack bar, which is a Millen Type 40205 coil socket. The output of the exciter is thus connected to the link terminals on the final grid-coil socket, L_3 , which is a National Type XB-16. The plug-in link is left out of its socket, *B-B*, which is a Millen Type 33002 crystal socket mounted on a small cone stand-off.

For operation on 144 Mc., switch S_1 is closed, lighting the filament of the tripler tube. The exciter link is inserted at terminals *A-A* on the link jack bar, coupling the exciter to the tripler grid coil, L_1 . The plug-in link which transfers the energy from L_2 to L_3 is inserted in its socket, and 144-Mc. coils are inserted in the sockets for L_3 and L_4 .

In order to eliminate the stray capacity and inductance usually encountered in any plug-in base, the 144-Mc. coils for L_3 and L_4 are made to plug directly into their respective sockets. The grid coil, being of No. 12 wire, fits the socket contacts; the plate coil is fitted with pins removed from an old tube base or plug-in coil form. For the same reason, the plug-in link terminals on the L_3 coil socket are not used for 144 Mc.

The final-stage plate tank condenser is made from a Cardwell dual neutralizing condenser,


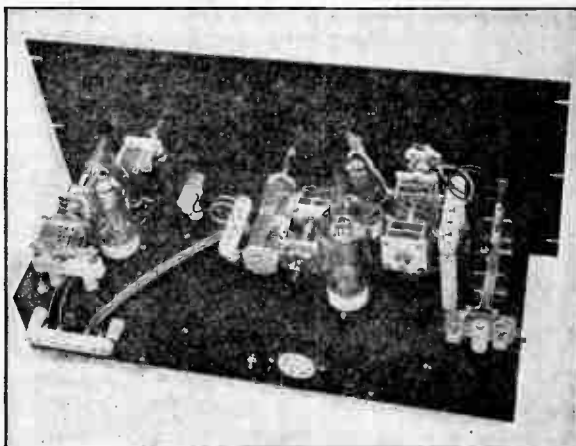


Fig. 1605—Rear view of the v.h.f. amplifier unit with 144-Mc. coils in place. All components are grouped for minimum lead length. Lucite rods are used for extension shafts on all tuning controls. Note the plug-in link between the tripler plate coil and the final grid circuit. Flexible links, for the final grid and output coupling circuits, are low-loss 300-ohm line (Amphenol 21-056).

Fig. 1606 — Schematic diagram of the 50 Mc. driver-amplifier using 35TGs.

- C₁, C₅ — 15- μ fd. variable (Hammarlund HFA-15-E).
 C₂, C₃, C₄, C₈, C₉ — 0.001- μ fd. mica.
 C₆, C₁₃ — 0.0005- μ fd., 5000-volt, mica.
 C₇ — 15- μ fd. per section, split stator (Hammarlund HF-15-X).
 C₁₀, C₁₁ — Neutralizing condensers (Cardwell Trimaire, 2-plates, triple spacing).
 C₁₂ — 4- μ fd. per section, split stator (Cardwell ED 4-41). See text.
 R₁ — 50000 ohms, 10-watt.
 R₂ — 3000 ohms, 10-watt.
 R₃ — 250 ohms, 10-watt.
 RFC₁, RFC₄ — V.h.f. r.f. choke (Ohmite Z-1).
 RFC₂ — 10 turns No. 14 c., self-supporting, close wound on $\frac{3}{8}$ -inch diameter.
 RFC₃ — V.h.f. r.f. choke (Ohmite Z-0).
 M₁ — 0-150 ma.
 M₂ — 0-50 ma.
 M₃ — 0-300 ma.
 J — Closed circuit jack.
 T₁ — Filament transformer, 5 volts, 4 amperes.
 T₂ — Filament transformer, 5 volts, 8 amperes.
 S₁, S₂ — S.p.s.t. toggle switch.
 L₁ — 6 turns No. 18, $1\frac{1}{4}$ -inch diameter, 1 $\frac{3}{16}$ inches long, 3-turn end link (National AR-16, 10-C, with two turns removed from one end).
 L₂ — 2 turns No. 14 c., 1-inch diameter, spaced $\frac{1}{8}$ -inch. Link, L₂, L₃ — 2 turns No. 14 c., each end. Plug-in device is for mechanical mounting only.
 L₃ — 50-60 Mc. — Same as L₁, but with one turn re-

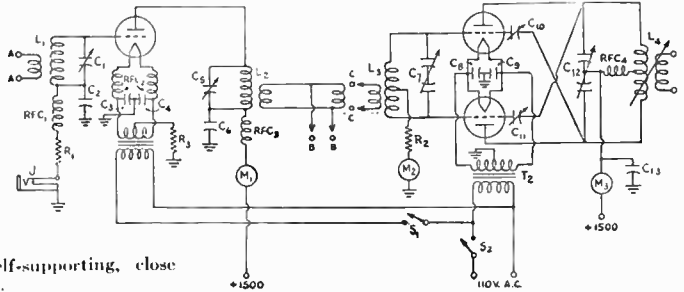

moved from each end of the original unit. 144 Mc. — 2 turns, No. 12 tinned, $\frac{3}{4}$ -inch diameter, spaced $\frac{1}{2}$ -inch. No plug-in base is used — coil leads plug directly into socket.

L₄ — 50-60 Mc. — 3 turns each side of center, No. 12 tinned, 2-inch diameter. Adjust turns spacing so that low frequency end of range comes with tuning condenser at maximum capacity. Base is a Millen Type 40205 Midget plug.

144 Mc. — 1 turn each side of center, No. 12 tinned, spaced to fit holes in jack bar (Millen type 41205 midget socket). Pins for this coil may be removed from an old tube base or plug-in coil form.

which originally had an insulated flexible coupling between the two rotor sections. This was removed and a section of $\frac{1}{4}$ -inch brass rod, tapped for $\frac{6}{32}$ thread, was inserted in its place. A piece of $\frac{1}{8}$ -inch thick lucite was fitted to the bottom of the condenser assembly and serves as a mounting base. The result is a split-stator condenser which has sufficiently wide spacing to eliminate the danger of flashover, yet is extremely compact.

There is really no necessity for a plug-in coil at L₁, inasmuch as it is never changed, but it was employed to permit the use of a standard commercial unit. Two turns were removed from one end, making it essentially an end-linked coil. The same type of coil (National AR-16, 10-C) assembly is used for the 50-Mc. coil for L₃. One turn was removed from each

end in this case, a center-linked assembly being needed at this point.

Meters should be provided for reading the tripler plate, final grid, and final plate currents, as indicated in the circuit diagram, although these meters are not included in the unit itself. The jack on the front panel is for a meter for measuring the tripler grid current, and is normally used only during initial tuning operations.

The final stage should be tuned up on 50 Mc. first. The exciter link should be plugged into terminals C-C' on the jack bar, and the 50-Mc. coils inserted at L₃ and L₄. With power on the exciter but no plate voltage on the amplifier, rotate C₇ for maximum grid current. Set the neutralizing condensers at maximum capacity and rotate C₁₂. If the final-stage plate circuit is capable of being tuned to resonance there will be a pronounced dip in the grid current. The neutralizing condensers, C₁₀ and C₁₁, should then be adjusted a small amount at a time until the dip in grid current disappears. Power may then be applied to the plate circuit. If everything is in order, the dip in plate current at resonance should bring the plate current down to less than 50 ma. The amplifier may be loaded up to nearly 300 ma., at a plate voltage of 1500 — an input 425 watts or more — before the plates of the 35TGs show more than their normal bright orange color.

Next, tripler operation should be

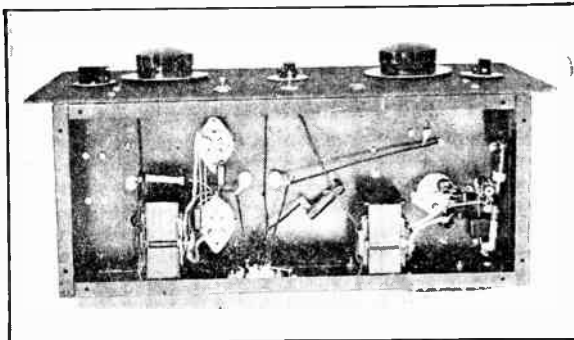


Fig. 1607 — Under-chassis view of the 35TG driver-amplifier. Separate filament transformers are used for the two stages. The driver tube socket with its two filament r.f. chokes is at the right.

checked. With the exciter on 48 Mc. and the link inserted in the terminals A-A, adjust C_1 for maximum grid current. This should be around 20 ma. when no plate voltage is applied to the tripler. For initial tests 750 volts is sufficient — the maximum voltage should not be used until everything is in order. Apply the plate voltage and tune C_5 for resonance, which should occur near minimum capacity. As this stage is being driven hard, harmonics will show up all along the line, hence the output frequency should be checked with Lecher wires or a reliable absorption-type wave meter.

When it has been determined that the output is actually the third harmonic, or 144 Mc., insert the plug-in link at B-B and the coils for 144 Mc. at L_3 and L_4 . Repeat the process of checking the final stage as outlined above for 50 Mc. Some change in the setting of the neutralizing condensers may be required for complete neutralization at 144 Mc. (the setting for this band is much more critical than for 50 Mc.), but the adjustment for 144 will usually be found to be satisfactory for the lower frequency as well.

Tests on 144 Mc. should be conducted at a lower voltage than is used for 50 Mc. Up to 2000 volts may be used at the lower frequency after everything is tuned up, but with the somewhat lower efficiency at 144 Mc., 1300 volts is the recommended maximum. Tuning operations should be conducted at not more than 1000 volts. A load should be kept coupled to the final stage when high voltages are used, otherwise the circuit losses at this frequency will cause sufficient tank circuit heating to melt soldered connections.

Circuit losses make the dip in plate current high (about 100 ma. at 1000 volts) at 144 Mc., but the resonance dip is not a true indication of performance. Lamp loads, too, are unreliable at this frequency. The best test is the color of the tube plates. If the color does not indicate greater heat than is shown when 150 watts input is run with no excitation, then there is no cause to worry about harming the tubes.

Ⓢ A 10-Watt 50-Mc. Transmitter

The inexpensive transmitter shown in Figs. 1608, 1609 and 1610 uses dual-triode 6A6-type tubes throughout. One section of the first tube is used as a crystal oscillator on 6.25 Mc. while the second half doubles to 12.5 Mc. The two sections of the second tube are used as 25- and 50-Mc. doublers, and the third tube is a push-pull final amplifier. Capacitive interstage coupling is employed throughout except between

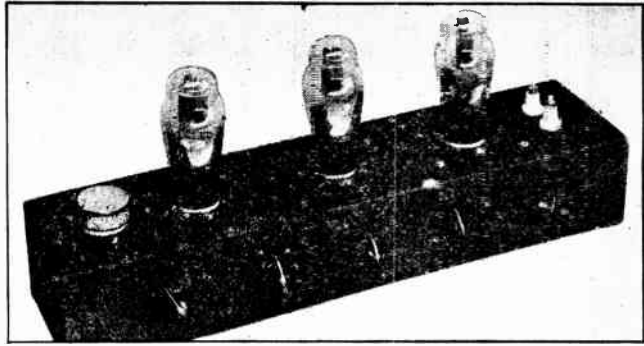


Fig. 1608 — In this front view of the 10-watt 50-Mc. transmitter the oscillator, doubler and amplifier tubes are from left to right. The crystal socket is at the left end of the chassis and the output terminals are at the right. The tuning controls are arranged in line along the front wall of the chassis. Plate-voltage terminal, meter switch, meter core, 115-volt line cord, and the crystal-current bulb, mounted in a rubber grommet, are at the rear.

the 50-Mc. doubler and the final.

In the oscillator, parallel plate feed permits grounding the rotor plates of the tuning condenser. Cathode bias allows the tube to operate at low plate current; it is not necessary to obtain much power from the oscillator, since the excitation requirements of the first doubler are low.

The 12.5- and 25-Mc. doubler circuits are identical except for the cathode resistor, R_2 , in the first doubler stage. The second doubler has no cathode bias, because as much output as possible is desirable to drive the 50-Mc. doubler. Parallel plate feed is used in both stages. The 50-Mc. doubler is series fed through an untuned plate coil. The coil is made nearly self-resonant to transfer maximum energy.

Meter switching with shunt resistors (R_7 through R_{12}) provides for measuring the plate current in each stage, although the meter is not incorporated in the transmitter itself.

The transmitter is built on a chassis measuring $3 \times 4 \times 17$ inches. The oscillator and doubler tube sockets are mounted with the filament prongs toward the front of the chassis and the amplifier socket with its filament prongs facing the right end. The crystal socket and output terminals each are centered $1\frac{3}{4}$ inches in from the ends of the chassis. The second-doubler tuning condenser, C_3 , is mounted in the center of the front wall of the chassis. The other variable condensers are located to the left and right, with 2-inch spacing between shaft centers. C_1 , C_2 and C_3 are supported by the chassis wall, but C_4 and C_5 are mounted on small metal pillars from the upper side of the chassis. This mounting arrangement brings the shafts of C_4 and C_5 in line with the other three.

Wiring to the meter switch is simplified if the switch is located $6\frac{1}{2}$ inches in from the output end. This point is also convenient to the supply ends of the plate chokes for the first three stages, so that these chokes can be mounted directly on the switch points. The shunt re-

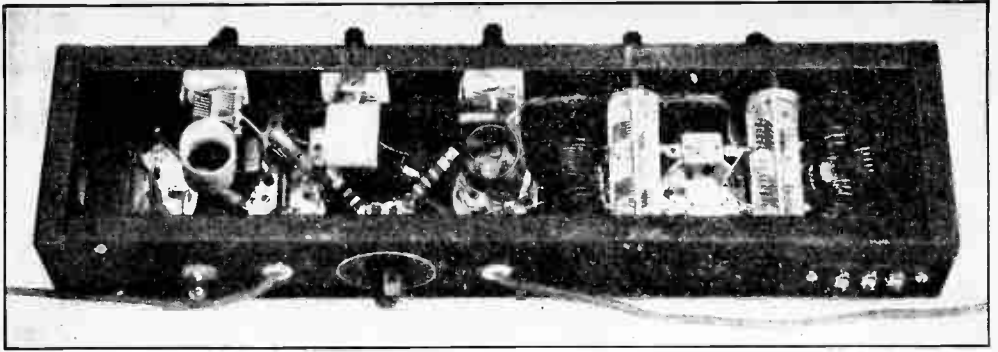


Fig. 1609 — This bottom view shows how the tuning condensers are mounted with respect to the tube sockets. The self-supporting coils mount directly on the tuning condensers. Filament transformer is in lower left-hand corner.

sistors should be soldered to the switch contacts before the switch is installed.

The filament transformer and crystal lamp are at the left end of the chassis, in the bottom view. The transformer should be kept as far as possible to the left so that it will not be near the r.f. circuits. The lamp is held firmly in the grommet by stiff leads soldered to its base. The plate-supply terminals are out of the way at the extreme left end of the base. Two positive terminals are provided, so that a modulator transformer secondary may be connected in the plate lead of the final amplifier.

The rest of the parts are mounted so r.f. leads will be short and direct, particularly in the last two stages. The grid connections in the amplifier should be made directly between the grid prongs of the socket and the stator plate terminals of the grid tank condenser. The plate prongs and the stator sections of C_5 should be cross-connected, so that the neutralizing condensers, C_6 and C_7 , may be supported by the

condenser lugs, as shown in Fig. 1609. This gives leads of negligible length and perfect symmetry, both of which contribute to good neutralizing. Trimmer-type condensers can be used for neutralizing since the neutralizing capacity required is small and the effective dielectric is mostly air. The output coupling coil has its ends soldered to lugs which are held in place by the feed-through terminals. The lugs will bend as the position of the coil is varied to change the coupling.

Each tank circuit will be in resonance when adjusted for minimum plate current to the tube with which it is associated. The current values should be 10, 18, 18 and 40 ma., in the order listed, for the first four stages. It is quite possible that the values will vary slightly in different layouts, but they should be approximately as given. Tuning of the various tanks should be adjusted to obtain maximum output from the 50-Mc. doubler, as indicated by maximum grid current in the final-amplifier grid

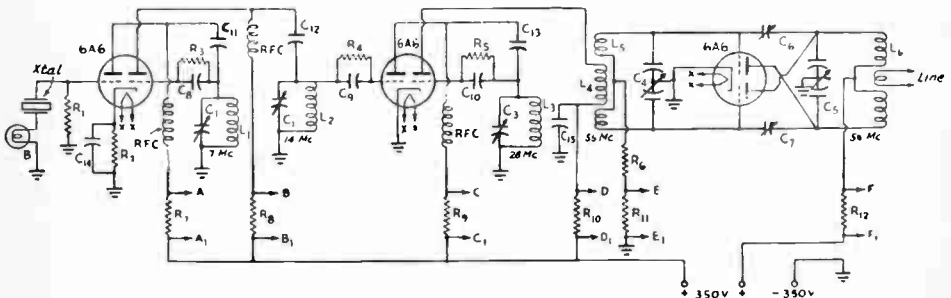


Fig. 1610 — Wiring diagram of the 10-watt 6A6 dual triode crystal-controlled 50-Mc. transmitter-exciter unit.

C_1 — 50- μ fd. variable (Hammarlund HF-50).
 C_2 — 35- μ fd. variable (Hammarlund HF-35).
 C_3 — 15- μ fd. variable (Hammarlund HF-15).
 C_4 — 50- μ fd. per section dual variable (Hammarlund HFD-50).
 C_5 — 15- μ fd. per section dual variable (Hammarlund HFD-15-N).
 C_6, C_7 — 3-30- μ fd. mica trimmer (National M-30).
 C_8, C_9, C_{10} — 100- μ fd. midget mica.
 $C_{11}, C_{12}, C_{13}, C_{14}, C_{15}$ — 500- μ fd. midget mica.
 R_1 — 15,000 ohms, $\frac{1}{2}$ -watt.
 R_2 — 500 ohms, 1-watt.
 R_3, R_4, R_5 — 30,000 ohms, $\frac{1}{2}$ -watt.
 R_6 — 1000 ohms, 1-watt.

$R_7, R_8, R_9, R_{10}, R_{11}, R_{12}$ — 25 ohms, $\frac{1}{2}$ -watt.
 RFC — 2.5-mh. r.f. choke (National R-100).
 B — 60-ma. dial light.
 L_1 — 23 turns No. 22 d.s.c., close wound, 1-inch diameter.
 L_2 — 13 turns No. 22 s.d.c., 1 inch long, 1-inch diameter.
 L_3 — 7 turns No. 14, $\frac{3}{4}$ -inch long, 1-inch diameter.
 L_4 — 11 turns No. 14, $\frac{3}{4}$ -inch long, $\frac{3}{4}$ -inch diameter.
 L_5 — 2 turns No. 12 each side of L_4 , 1-inch diameter, center opening $\frac{3}{4}$ inch. Turns spaced diameter of wire.
 L_6 — 3 turns No. 12 each side of coupling link, $\frac{3}{8}$ -inch diameter, center opening $\frac{3}{4}$ inch. Turns spaced diameter of wire.
 Link — 5 turns No. 12, $\frac{7}{8}$ -inch diameter, $\frac{1}{2}$ inch long.

leak, R_6 . If no grid current is obtained, it is probably an indication that the coupling between L_4 and L_5 is either too tight or too loose; this coupling is quite critical, and therefore deserves careful adjustment. The amplifier grid current should be 25 ma. or more when the coupling is optimum. Each time the coupling is changed, the grid condenser, C_3 , as well as the preceding tuning condensers should be readjusted.

After a grid-current indication is obtained, the amplifier should be neutralized. Plate voltage must be removed from the final amplifier but the rest of the circuits should be in normal operating condition. Start with the plates of the neutralizing condensers screwed up tight and then back off a full three turns on each condenser. This places the neutralizing capacities at approximately the correct values. Condenser C_5 is then rotated through resonance, which will be indicated by a kick in the grid current. Adjust the neutralizing condensers in small steps, turning both screws in the same direction and the same amount each time, until the grid current remains stationary when C_5 is rotated. This indicates complete neutralization. Retune the grid circuit after neutralization, so that maximum excitation will be secured; also recheck the coupling between L_4 and L_5 , since neutralization will change the load on the driver somewhat.

Plate voltage may now be applied to the amplifier. When the plate tank is tuned to resonance, the plate current should fall to 20 or 25 ma. A load, such as an antenna or feeder system or a 10-watt lamp used as a dummy antenna, should be connected and the coupling adjusted until the plate current reaches the full-load value of 60 ma. The grid current will fall off to 10 ma. or so when the amplifier is loaded.

At the recommended input of 21 watts (60 ma. at 350 volts), the output as measured in a dummy antenna is something over 10 watts.

To modulate the transmitter 100 per cent, about 11 watts of audio power is required. The modulator output transformer must match an impedance of 5833 ohms (modulated-amplifier plate voltage divided by modulated-amplifier plate current expressed in amperes). A 6000-ohm output winding will be close enough to provide a satisfactory match. A modulator using a Class-B 6A6 makes an excellent companion unit for the transmitter, because it maintains the uniformity of tube types. Such a unit is described in Chapter Fourteen. A power supply capable of delivering 350 volts at 150 ma. is needed for this transmitter.

The circuit as shown in Fig. 1610 requires the use of crystals having frequencies lying between 6250 and 6750 kc. for operation in the 50–54-Mc. band. If preferred, the circuit may be changed so that crystals having frequencies between 12.5 and 13.5 Mc. may be utilized. The crystal and grid leak, R_1 , may be con-

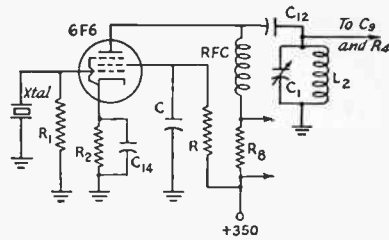


Fig. 1611 — Alternative crystal oscillator circuit for the transmitter of Fig. 1610 when crystals in the frequency range 12.5 to 13.5 Mc. are to be used. Circuit values correspond to those given in Fig. 1610 except for the screen by-pass condenser, C_1 , 0.01 μ f., and the screen dropping resistor, R_8 , 50,000 ohms, 10-watt.

nected to the grid of the second section of the first 6A6, in which case all the components associated with the plate circuit of the first section of the tube may be omitted. The grid and plate of this section may be left idle. This procedure converts the second section of the tube into a crystal oscillator instead of a frequency doubler. Alternatively, a 6F6 pentode crystal oscillator may be substituted for the first 6A6, using the circuit shown in Fig. 1611. The use of the pentode oscillator is recommended because there is less heating of the crystal and consequently less frequency drift during operation.

□ A Low-Power 50-Mc. F.M. Transmitter

The transmitter shown in Figs. 1612, 1613 and 1614 will yield a frequency-modulated carrier output of approximately 7 watts on 50 Mc., using a plate power supply delivering 300 volts.

A reactance modulator stage, utilizing a 6SA7 reactance tube to modulate a 6F6 oscillator, is incorporated in the unit, along with a microphone input transformer. A single-button microphone is sufficient to drive the 6SA7, no additional speech amplification being required.

For complete flexibility and wider utility, provision for alternative amplitude modulation may be made as well. If it is desired to use amplitude modulation, the gain control on the reactance modulator should be set at zero and the necessary 6 watts of audio connected in series to the plate and screen lead of the 7C5 output amplifier. Used as an f.m. transmitter, the entire unit requires 300 volts at about 90 ma., making it ideal to run from a vibrator pack for portable/mobile work.

A single-button carbon microphone is transformer-coupled to the 6SA7 reactance modulator, which is connected across the tank circuit of the 6F6 e.c.o. A VR150-30 stabilizes the voltage across the oscillator and modulator and aids materially in keeping the mean frequency constant. The grid circuit of the e.c.o. tunes from 12.5 to 13.5 Mc. with a slight margin at either end of the tuning range, and the plate circuit of the e.c.o. is tuned to 25 Mc. by means of a self-resonant coil which is adjusted for

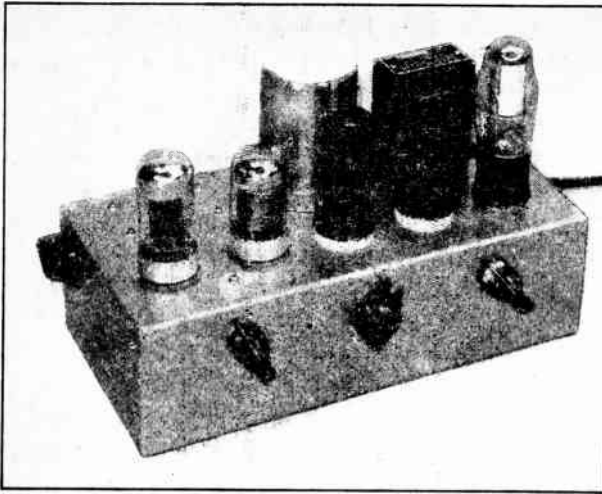


Fig. 1612 — The complete 50-Mc. f.m. transmitter has all r.f. components mounted under the chassis with the exception of the oscillator grid coil, which is housed in the shield can in the rear center of the chassis. The tubes, from left to right, are 7C5 output amplifier, 7G7 doubler, 6F6 e.c.o., 6SA7 reactance modulator and VR150-30 voltage regulator.

maximum output by squeezing the turns together or spreading them apart. Once adjusted, it need not be touched for any change in tuning conditions. The 25-Mc. output of the e.c.o. drives a 7G7/1232 doubler to 50 Mc., which in turn drives the output amplifier.

With a 300-volt supply, the 7C5 final-amplifier grid current should be about 0.6 ma. under load for linear amplitude modulation. If f.m. is used exclusively, the grid current can be lower with no harmful effect other than a

slight decrease in output of the amplifier. The 7C5 final amplifier is plate neutralized by running a length of stiff wire from the plate side of the doubler tuning condenser over to a point near the open side of the final-amplifier split-stator tuning condenser. The capacity from this wire to the stator of the condenser may be adjusted to neutralize the final amplifier by cutting the end of the wire, a bit at a time, until the plate-tank tuning shows no reaction on the grid current (with both plate and screen voltage off).

No difficulty should be encountered in adjusting the transmitter other than setting the e.c.o. coils to the proper frequencies. The grid coil should be adjusted to cover the proper range with the reactance modulator tube in the circuit. The range can be varied by pushing the turns together or spreading them apart, while checking the resulting frequency on a calibrated receiver.

The e.c.o. plate coil can best be adjusted by reading grid current to the final amplifier (by connecting a 0-1 ma. d.c. milliammeter between R_8 and ground) and adjusting L_2 until the 7C5 grid current is a maximum with the oscillator set at 13 Mc.

The plate current of the final amplifier will be about 45 ma. when the stage is properly loaded. The loading is varied by changing the position of the "swinging link" fastened to the

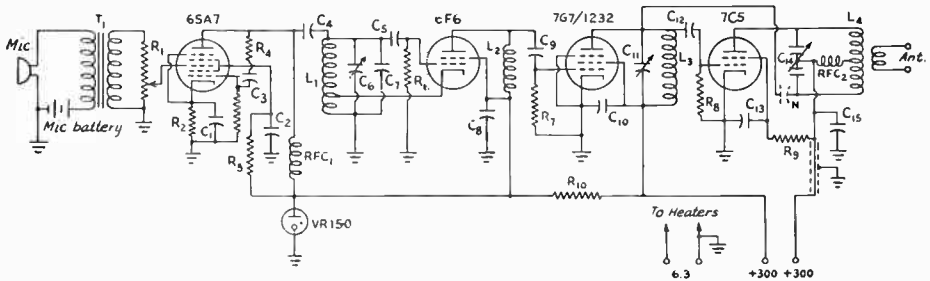



Fig. 1613 — Wiring diagram of the complete 50-Mc. 7-watt frequency-modulated transmitter.

- C₁ — 0.01- μ fd. 400-volt paper.
- C₂ — 8- μ fd. 150-volt electrolytic and 0.005- μ fd. mica in parallel.
- C₃ — 0.001- μ fd. mica.
- C₄ — 500- μ fd. mica.
- C₅, C₉, C₁₂ — 100- μ fd. mica.
- C₆ — 15- μ fd. midjet variable (Hammarlund HF-15).
- C₇ — 25- μ fd. silvered mica.
- C₈, C₁₀, C₁₃ — 0.005- μ fd. mica.
- C₁₁ — 35- μ fd. midjet variable (Hammarlund HF-35).
- C₁₄ — 35- μ fd. per section dual variable (Cardwell ER-35-A1).
- C₁₅ — Two 500- μ fd. mica, one at each end of rotor of C₁₄.

- N — Neutralizing condenser (see text).
- R₁ — 100,000-ohm volume control.
- R₂ — 750 ohms, 1/2-watt.
- R₃ — 0.25 megohm (not marked in diagram).
- R₄ — 50,000 ohms, 1/2-watt.
- R₅ — 5000 ohms, 1/2-watt.
- R₆ — 25,000 ohms, 1/2-watt.
- R₇ — 0.1 megohm, 1/2-watt.
- R₈ — 75,000 ohms, 1/2-watt.
- R₉ — 5090 ohms, 1-watt.
- R₁₀ — 3000 ohms, 10-watt.
- RFC₁ — 2.5-mh. r.f. choke.
- RFC₂ — V.h.f. choke (Ohmite Z-1).
- T₁ — Microphone transformer (Thordarson T-58A37).

- L₁ — 12 turns No. 20 e., spaced to occupy 1 inch on a 1-inch diameter form; cathode tap 2 3/4 turns up. Plugged into socket on chassis.
- L₂ — 16 turns No. 20 e., spaced to occupy 1 5/8 inches, 9/16-inch diameter; self-supporting (see text).
- L₃ — 1 turns No. 20 e., 1/2-inch diameter, 1/4-inch long.
- L₄ — 6 turns No. 14 e., 3/8-inch inside diameter, wound to occupy 1-inch length, with 3/8-inch gap in center for swinging link of 2 turns No. 14 e., same diameter.

Fig. 1614 — A view underneath the chassis of the 50-Mc. f.m. transmitter shows the volume control at the left, the oscillator control at the center, the doubler tuning control at the right, and the final amplifier tuning control at the side. The microphone connector is on the left side of the chassis, and the four-prong plug and flexible wire connect to the power supply and microphone battery, respectively. Note the shield between the final tuning condenser and the oscillator tuning condenser, to reduce reaction between the two circuits, and the wire running from the doubler tuning condenser to near the final tank condenser which is used as a neutralizing condenser (X in Fig. 1613). The output connects to two binding posts on a Victron strip.

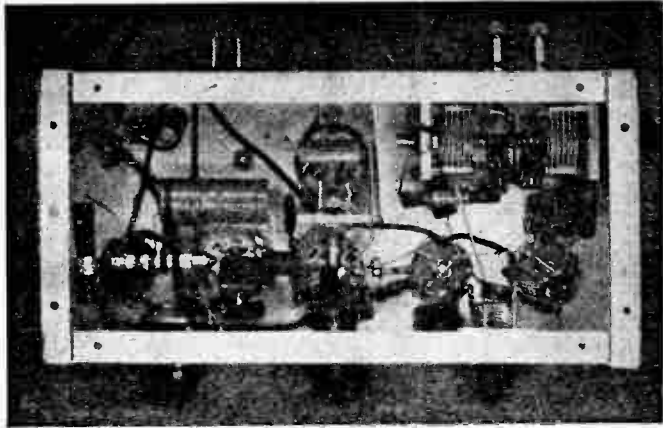

antenna output binding posts.

When using f.m. the amount of deviation is controlled by the setting of the gain control, R_1 . With the gain control wide open the deviation is over 30 kc. on 53 Mc., which is more than adequate for all purposes. When the receiving station does not have a regular f.m. receiver, the signal can be received on a conventional receiver by reducing the deviation at the transmitting end and tuning the signal off to one side of resonance at the receiving end.

◄ An F.M. Modulator-Oscillator Unit

Apart from the requirement for a means of varying the frequency of the oscillator output in accordance with the applied modulating voltage, the r.f. circuits of a frequency-modulation transmitter for amateur use differ little from standard v.h.f. practice, with the exception of the oscillator circuit. Any of the multi-stage exciter or amplifier units described in this chapter, therefore, may be adapted for use on f.m. as well as a.m.

Where a crystal- or e.c.o.-controlled transmitter for the 28-, 50- or 144-Mc. band is available, it is a relatively easy matter to disconnect the regular plate modulator and substitute for the crystal or e.c.o. the f.m. oscillator-modulator shown in Figs. 1615, 1616 and 1617. The r.f. output of the unit is intended to be fed through a link to a tuned-circuit coil wound on a coil form which substitutes for the crystal holder in the crystal oscillator. This tuned circuit is resonant at the same frequency as the output tank of the control unit, L_2C_3 in Fig. 1616, and is, in fact, identical in construction.

In transmitters using triode oscillators, or pentode crystal oscillators in which the tubes are not well screened, it is advisable to use the crystal oscillator tube as a doubler rather than as a straight amplifier. If

the transmitter uses a crystal oscillator operating in the vicinity of 14 Mc., for example, the output of the unit may be on 7 Mc. and the grid circuit of the ex-crystal tube also tuned to 7 Mc. This will avoid difficulty with self-oscillation in the ex-crystal stage. With a pentode oscillator it is possible to work straight through, provided the grid tank substituted for the crystal is tuned well on the high-frequency side of resonance, but this procedure is not advisable since it may make the modulation non-linear. It is rather important that all circuits in the transmitter be tuned "on the nose" for best performance. Of course, if the crystal tube is a well-screened transmitting type it can be used as a straight amplifier.

With harmonic-type crystal oscillators the input frequency can be the same as that of the

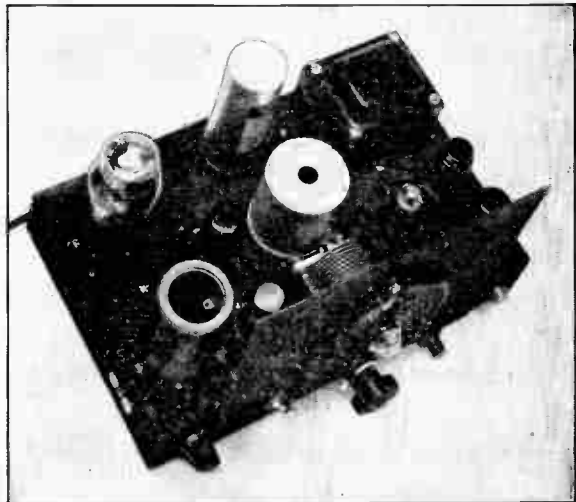


Fig. 1615 — This modulator-oscillator unit is used with normally crystal-controlled v.h.f. transmitters for frequency-modulated output. It contains a speech amplifier and power supply, so that no additional equipment is needed. The oscillator coil is in the round shield can in the center. The coil in the left foreground is the buffer output circuit. The speech amplifier and modulator are at the right, with the power supply along the rear. A 7 × 11-inch chassis is used.

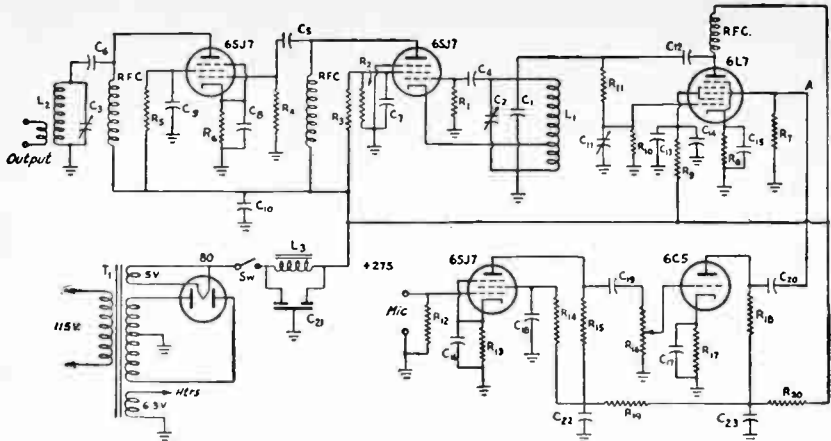


Fig. 1616 — Circuit diagram of the f.m. control unit for use with normally crystal-controlled v.h.f. transmitters.

- | | | |
|--|---|--|
| C ₁ — 150- μ fd. silvered mica for 7 Mc. | R ₁ — 0.1 megohm, 1-watt. | length $\frac{3}{4}$ inch, 1-inch diameter, tapped 3rd turn from ground. |
| C ₂ — 100- μ fd. variable (National SE-100). | R ₂ — 25,000 ohms, 1-watt. | L ₂ — 14 Mc.; 10 turns No. 18. |
| C ₃ — 50- μ fd. variable (Hammarlund HF-50). | R _{3, R_{4, R_{5, R₁₁} — 50,000 ohms, 1-watt.}} | All coils wound with enameled wire on $\frac{1}{2}$ -inch diameter forms (Hammarlund SW F-4). 1.75-Mc. coil close-wound; others spaced to a length of $1\frac{1}{2}$ inches. |
| C ₄ — 100- μ fd. mica. | R _{6, R₈} — 300 ohms, $\frac{1}{2}$ -watt. | Link 3 to 5 turns (not critical). |
| C _{5, C₁₂} — 250- μ fd. mica. | R _{7, R₁₀} — 0.5 megohm, $\frac{1}{2}$ -watt. | L ₃ — Filter choke, 10 henrys, 40 ma. |
| C ₆ — 0.001- μ fd. mica. | R ₉ — 30,000 ohms, 1-watt. | T ₁ — 250-0-250 volts, 10 ma.; 6.3 volts at 2 amperes; 5 volts at 2 amperes. (Thordarson T-13R11). |
| C _{7, C_{8, C_{9, C_{10, C_{13, C_{15, C_{19, C₂₀}}} — 0.01-μfd. paper.}}}} | R ₁₂ — 5 megohms, $\frac{1}{2}$ -watt. | Sw — S.p.s.t. toggle switch. |
| C ₁₁ — 3-30- μ fd. mica trimmer. | R ₁₃ — 900 ohms, $\frac{1}{2}$ -watt. | |
| C _{14, C_{22, C₂₃} — 8-μfd. 450-volt electrolytic.} | R ₁₄ — 1 megohm, $\frac{1}{2}$ -watt. | |
| C _{16, C₁₇} — 10- μ fd. 25-volt electrolytic. | R _{15, R₁₉} — 0.25 megohm, $\frac{1}{2}$ -watt. | |
| C ₁₈ — 0.1- μ fd. 200-volt paper. | R ₁₆ — 0.5-megohm volume control. | |
| C ₂₁ — Dual 450-volt 8- μ fd. electrolytic. | R ₁₇ — 2000 ohms, $\frac{1}{2}$ -watt. | |
| | R ₁₈ — 50,000 ohms, $\frac{1}{2}$ -watt. | |
| | R ₂₀ — 0.15 megohm, 1-watt. | |
| | RFC — 2.5-mh. r.f. choke. | |
| | L ₁ — 7 Mc.; 11 turns No. 18 e. | |

crystal, since the output frequency of the crystal tube is already a harmonic. In the Tri-tet oscillator, the cathode tank should be short-circuited; in the types using a cathode im-

pedance to provide feed-back, this impedance also should be shorted. Care should be taken to avoid short-circuiting the grid bias, whether from a cathode resistor or grid leak. In the latter case this usually will mean that a blocking condenser (500 μ fd. or larger) should be connected between the "hot" end of the grid tank and the grid of the ex-crystal tube, with the grid lead (and choke) connected on the grid side of the condenser. Such a blocking condenser may be incorporated in the plug-in tank. The grid-tank tuning condenser may be a small air padder mounted in the coil form.

Where a suitable power supply and speech amplifier are already available, the lower part of Fig. 1616 can be omitted and only the oscillator, buffer and modulator units need be built. With transformer input, the transformer and gain control should be connected between ground and point "A" of Fig. 1616, R₇ being omitted. Any of the conventional meth-

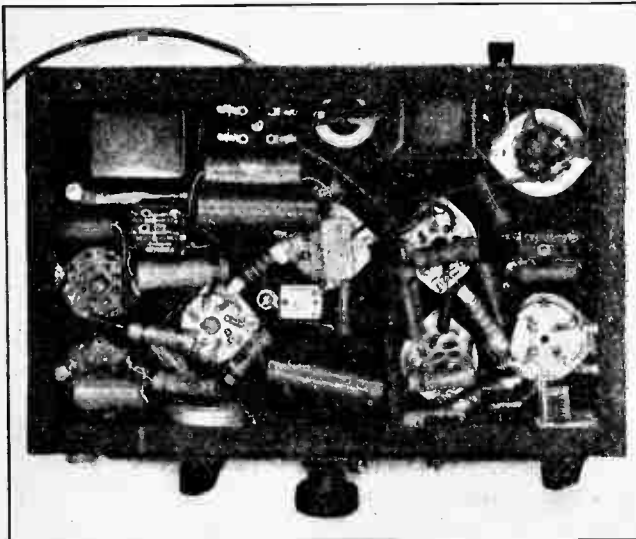


Fig. 1617 — In this bottom view of the f.m. modulator unit, the r.f. section is at the right and the audio at the left. The oscillator socket is to the right of the coil socket in the center.

ods may be used to couple the modulator to an available speech amplifier, with one precaution — if a high-impedance connection is used, the "hot" lead should be shielded to prevent hum pick-up.

If the transmitter to be used has a self-excited oscillator, electron-coupled or otherwise, a separate oscillator need not be built. The reactance modulator can be connected directly across the tank circuit of the oscillator. If the oscillator has too high a C/L ratio, not enough deviation may be obtained without distortion. It is advisable to use an L/C ratio in the oscillator comparable to that given in Fig. 1616.

The circuit constants of the oscillator in the unit pictured are adjusted to cover the frequency range 6000–7425 kc. so that the output can be multiplied into the 28-, 50- and 144-Mc. bands. For 28-Mc. operation a multiplication of 4 is required; for 50 Mc., a multiplication of 8; and for 144 Mc., a multiplication of 24. The output circuit, L_2C_3 , is tunable over the range 12–15 Mc., and thus is adapted to feeding into a transmitter using crystals operating in this range. For replacing crystals operating at half this frequency, L_2 should have 20 turns with all other coil dimensions remaining the same.

The sensitivity of the modulator is controlled by the setting of C_{11} . The higher the capacity of this condenser the smaller the frequency deviation for a given audio input voltage to the modulator. At maximum sensitivity, with C_{11} at minimum capacity, the linear deviation is approximately 1.5 kc. with an a.f. input to the modulator grid of 2 volts peak. The actual deviation at the output frequency of the transmitter depends upon the amount of frequency multiplication following the modulated oscillator. The maximum linear deviation is approximately 6 kc. at 28 Mc., 12 kc. at 50 Mc., and 36 kc. at 144 Mc.

◀ A 12-Watt 50-Mc. Transmitter for Mobile Work

The transmitter shown in Figs. 1618 to 1621, inclusive, is designed to work from a power supply delivering 125 ma. at 325 volts and, since there are vibrator packs available which deliver this output, it is quite suitable for installation in a car for mobile work. Since maximum economy is desired in the exciter and audio stages, high-gain doubler tubes and Class-B audio for modulation are used.

From the diagram in Fig. 1619 it can be seen that a 6AG7 Tri-tet oscillator using a 12.5-Mc. crystal doubles frequency in its plate circuit to drive a 6AG7 doubler to 50 Mc., and this latter tube drives a 6V6 amplifier on 50 Mc. A 6L6 can be substituted for the 6V6 but it gives no

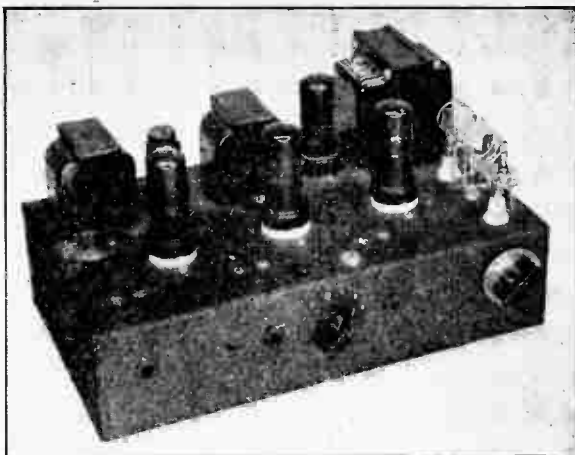


Fig. 1618 — A complete 12-watt 50-Mc. 'phone transmitter, ready for installation in car or home. The tubes along the front, from left to right, are 6AG7 Tri-tet oscillator, 6AG7 doubler and 6V6 final amplifier. The 6C5 driver (left) and the 6N7 Class-B modulator are at the rear between the transformers. The knob on the right controls the final tank condenser — the other tuning condensers are adjusted by screw driver through the rubber grommets. The meter switch is mounted on the front center, just under the meter pin jacks.

Note that the antenna coil is mounted on the antenna binding post strip — coupling is adjusted by swinging the coil.

improvement in performance at the input (12 watts) permitted by the vibrator supply. Provision for neutralizing the 6V6 was included in the design of this unit but it was found unnecessary with this particular parts arrangement. It is not to be assumed, however, that the 6V6 will work well without neutralization in every arrangement. The grid of the 6V6 is tapped down on the driver plate coil to lighten the loading and give a better match.

The modulation equipment consists of a 6C5 driver stage and a 6N7 Class-B modulator. Any arrangement except one using a single-button microphone would require more audio gain and hence mere possibility of "hash" pick-up.

The transmitter is built on a 7- by 12- by 3-inch chassis, thus providing plenty of room for the parts. Reference to Figs. 1618 and 1620 will show the placement of parts, but some of the minor constructional points should be pointed out. The tuning condensers, C_1 , C_2 and C_3 are mounted on the underside of the chassis on the small brackets that are furnished with them, and they are set far enough back from the front so that the ends of the shafts do not quite touch the metal. They are adjusted by a screw driver that is prevented from shorting to the chassis by rubber grommets in the holes. The final tank condenser, C_4 , is supported on the panel.

All of the inductances are mounted on or near their respective tuning condensers except the final tank coil, L_4 , which is mounted above the chassis on feel-through insulators. This makes it more convenient to adjust the antenna coupling coil, L_5 , after installing the trans-

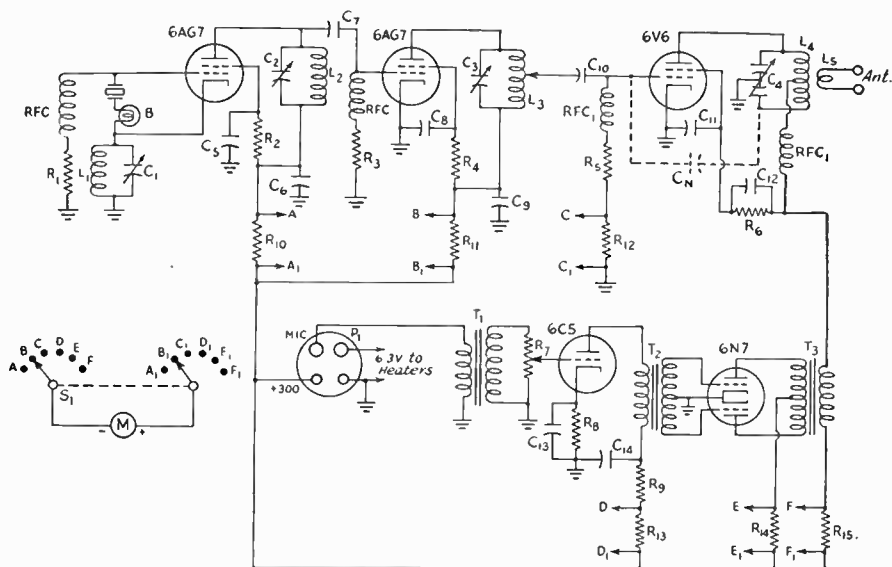


Fig. 1619 — Wiring diagram of the 50-Mc. phone transmitter.

- B — 60-ma. dial light.
 C₁ — 50- μ fd. variable (National UM-50).
 C₂, C₃ — 25- μ fd. variable (National UMA-25).
 C₄ — 30- μ fd. per section variable (Hammarlund HFD-30-X).
 C₅, C₈ — 0.01- μ fd., 400-volt paper.
 C₆, C₉, C₁₁ — 0.002- μ fd. mica.
 C₇, C₁₀ — 250- μ fd. mica.
 C₁₂, C₁₄ — 8- μ fd., 450-volt electrolytic.
 C₁₃ — 25- μ fd., 25-volt electrolytic.
 CN — See text.
 R₁, R₃ — 0.2 megohms, 1 watt.
 R₂, R₄ — 40,000 ohms, 1 watt.
 R₅ — 30,000 ohms, 1 watt.
 R₆ — 5,000 ohms, 2 watt.
 R₇ — 0.1-megohm volume control.
 R₈ — 1000 ohms, $\frac{1}{2}$ watt.
 R₉ — 6000 ohms, 1 watt.
 R₁₀—R₁₅ — 25 ohms, $\frac{1}{2}$ watt.
 RFC — 2.5-mh. r.f. choke (National R-100U).
 RFC₁ — 1 h.f. r.f. choke (Ohmite Z1).
 Sw₁ — 2-circuit, 5-position rotary switch, non-shorting (Malory 3226J).
 T₁ — Microphone transformer (Stancor A-1726).
 T₂ — Driver transformer (Stancor A-1721).
 T₃ — Modulation transformer (Stancor A-3845).
 L₁ — 19 turns No. 18 enam., spaced slightly to occupy $\frac{3}{8}$ -inch winding length, on $\frac{3}{4}$ -inch diam. form (National PRF-2).
 L₂ — 8 turns No. 14, spaced to occupy $1\frac{7}{8}$ inch, $\frac{7}{8}$ -inch diam., self-supporting.
 L₃ — $3\frac{1}{2}$ turns No. 14, spaced to occupy $\frac{7}{8}$ inch, $\frac{7}{8}$ -inch diam., self-supporting, 6V6 grid tap 1 turn from plate end.
 L₄ — 3 turns No. 14, each side center, spaced to occupy $\frac{3}{4}$ inch, $\frac{7}{8}$ -inch diam.
 L₅ — 2 turns, No. 14, $\frac{7}{8}$ -inch diam.
 P₁ — 4-prong base-mounting plug (Amphenol RCP-4).

mitter in the car.

The plate circuits and the final grid circuit can be metered by plugging in the meter leads to the two pin jacks on the front center of the chassis and setting the meter switch to the proper position. This is a convenience when tuning up with a different crystal or antenna. The power leads are terminated at a four-prong plug mounted on the back of the chassis.

One problem in connection with mobile units is the drop in the line from the battery to the vibrator or motor-generator unit, and these leads must be kept as short as possible. This transmitter is intended to be mounted in the trunk rack of the car, with the control box mounted on the dashboard of the car and the vibrator pack mounted under the hood on the fire wall. This is, of course, for a car with the battery under the hood — for cars with the battery elsewhere the vibrator pack and control box might have to be mounted differently. The voltage drop in the leads running back to the heaters of the tubes from the battery

will be small if heavy wire is used, and the drop in the 325-volt line from the vibrator pack is negligible.

The wiring diagram of the control box is shown in Fig. 1621. As can be seen, the microphone battery is mounted in this box, and a jack is provided for the microphone. The switch S₁ turns on the vibrator pack and the heaters of the tubes, while switch S₂ is used as an "on-off" switch for the transmitter, since it controls the microphone battery and the plate supply lead. The control box is $\frac{3}{4}$ -by-4-by-2-inch box and takes up very little room.

An alternative system is to mount the vibrator pack and an additional storage battery in the trunk rack and to control both the "on-off" of the heaters and vibrator pack and of the plate power through suitable relays controlled from the dash. However, the storage battery must be removed from the car for charging, and thus the installation may not be always "ready to go."

The adjustment of the transmitter is conven-

tional in every way, the tuning procedure being the same as with other crystal-controlled transmitters. With 325 volts from the power supply, the total plate and screen currents of the 6AG7 Tri-tet and the 6AG7 doubler will be 12 and 16 ma. respectively, and the final grid current should run about 2 ma. If, when the voltage is removed from the screen and plate of the 6V6 final, there is no flicker in the grid current as the final tank is tuned through resonance, there is no need to worry about neutralizing the final amplifier. However, if a flicker (of 0.1 ma. or so) does show up, the amplifier can be neutralized readily by running a stiff wire from the free end of the final tank over near the grid terminal on the 6V6 socket to form a neutralizing condenser (shown by dotted lines in Fig. 1619). The stage is then neutralized in the usual manner, varying the neutralizing capacity by moving the free end of the wire. Connecting the voltage to the screen and plate of the 6V6 and tuning to resonance, the total plate and screen current should be under 35 ma. unloaded and about 39 or 40 ma. loaded.

The 6C5 plate current will be about 8 ma., and the no-signal 6N7 plate current around 35 ma., kicking up to about 50 ma. on peaks. The antenna can be anything from 0.25 to 0.6 wavelength long, depending upon what one has available. Since the transmitter can be mounted close to the end of the antenna, there is no particular problem in feeding the antenna aside from finding a suitable insulator to run through the side of the car. If something near a quarter wavelength long is used for the antenna, one side of the antenna coil, L_5 , should be grounded to the car and a variable condenser connected in series with the antenna and the other side of L_5 . When the antenna is near a

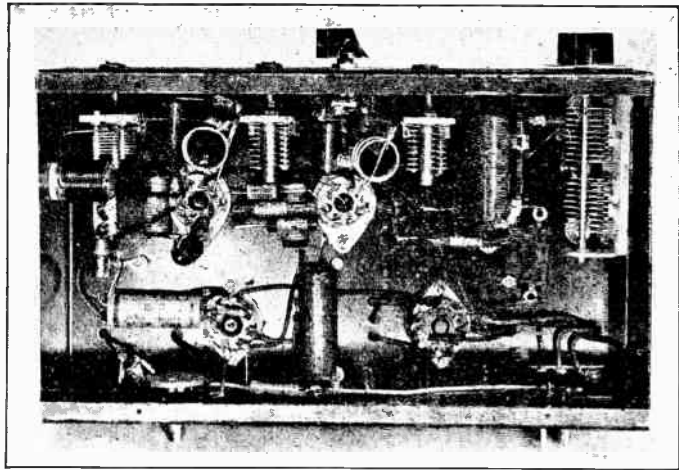


Fig. 1620 — A view under the chassis of the 50-Mc. transmitter shows the straightforward arrangement of parts. The coils L_2 and L_3 are self-supporting and are mounted on their respective condensers. Note the audio volume control and the power supply plug mounted at the rear of the chassis. The microphone lead from the plug to the microphone transformer is run through grounded shield braid.

half wavelength long, parallel tuning of L_5 should be used. The center of L_5 can be grounded or the whole thing can be left floating. Regardless of the length of antenna, the antenna coupling is varied by movement of L_5 with respect to L_4 after tuning both amplifier and tank circuit to resonance.

◀ A 6C4 Oscillator for 144 Mc.

Figs. 1622 to 1625, inclusive, show the details of construction of a low-power oscillator using a 6C4, a miniature triode power tube having a plate dissipation rating of 5 watts and designed for use as an oscillator in the v.h.f. range. At the rated plate input of 300 volts at 25 milliamperes the oscillator develops an r.f. output of about 2 watts in the 144-Mc. band.

As shown by the diagram, Fig. 1623, the circuit is the ultracon with an adjustable feedback condenser, C_3 , connected between grid and cathode. To reduce frequency modulation when the oscillator is amplitude-modulated, the tuned circuit has a fairly high C/L ratio,

using a tuning condenser having a fixed as well as a variable section. The condenser rotor consists of three circular plates and two "butterfly" plates. The circular plates rotate between two sets of stators having plates of regular shape and thus provide a fixed capacity. The butterfly plates rotate between two sets of opposed 90-degree stator plates, each set consisting of two plates. The assembly (now available as Cardwell Type ER-14-BF/SL) is made from a Cardwell ER double condenser, with only the front isolantite plate used for a mounting. This method of construction results in a split-stator condenser having a minimum of

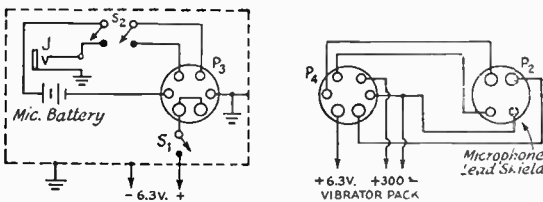


Fig. 1621 — Circuit diagram of control box.

- J — Small microphone jack (Mallory 702B).
 - S_1 — D.p.s.t. high-current toggle with sections in parallel.
 - S_2 — D.p.s.t. toggle.
 - P_2 — 4-prong cable socket (Amphenol PF-4).
 - P_3 — 6-prong cable plug (Amphenol RCP-6).
 - P_4 — 6-prong socket (Amphenol PF-6).
- Battery is Burgess 3A2. Microphone lead is shielded throughout.

inductance, since the r.f. current flows over the rotor plates without having to travel along the shaft. The plate shapes and details of assembly are shown in Fig. 1624.

Lead lengths in the circuit are reduced to a minimum by the construction shown in Fig. 1625. The entire oscillator assembly is mounted on a piece of $\frac{3}{32}$ -inch thick aluminum bent in the general shape of a U. The mounting is $1\frac{7}{8}$ inches wide and the bent-over top portion is $1\frac{7}{8}$ inches deep. The overall height is $2\frac{1}{4}$ inches. The bottom lip dimension can be anything convenient so long as enough area is provided to make a solid mechanical mounting. The tuning condenser, C_1 , is centered on the vertical portion and is mounted on the screws and spacers provided with the condenser. The hole for the shaft is made amply large so that the condenser rotor is not grounded. The condenser is mounted so that the two sets of stator plates are at top and bottom.

The tube socket is mounted so that the plate lead can drop in as straight a line as possible to the terminal at the right on the upper stator plates of C_1 . The grid condenser, C_2 , is supported at one end by the grid prong on the tube socket and at the other by the left-hand terminal on the lower stator plates. The excitation control, C_3 , has its movable-plate tab bent at a right angle so it can be bolted to the vertical support, and the stationary-plate tab is soldered directly to the grid prong on the tube socket. The grid choke, grid leak, and

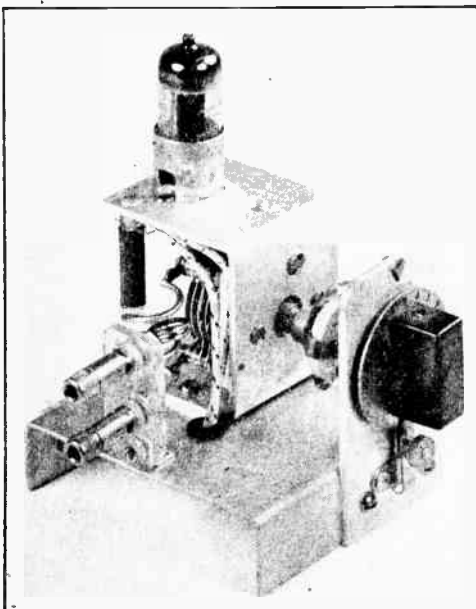


Fig. 1622 — A low-power 144-Mc. oscillator using a 6C4 v.h.f. miniature triode. With the construction shown, connecting leads in the r.f. circuit are reduced to negligible length. Filament and plate-supply leads are brought through the bottom chassis to a connection strip on the rear lip. The excitation control is adjusted through a hole in the top of the supporting member.

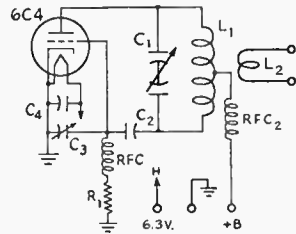


Fig. 1623 — Circuit diagram of the 6C4 oscillator.

- C_1 — Tuning condenser; see text.
- C_2 — 50- μ fd. midget mica.
- C_3 — 3-30- μ fd. ceramic trimmer (National M-30).
- C_4 — 500- μ fd. midget mica.
- L_1 — 2 turns No. 12 bare wire; inside diameter $\frac{9}{16}$ inch, length 1 inch; plate-supply tap at center.
- L_2 — 2 turns No. 14 enameled; inside diameter $\frac{3}{8}$ inch, slight spacing between turns.
- RFC $_1$, RFC $_2$ — 1-inch winding of No. 24 d.s.c. or s.c.c. on $\frac{1}{4}$ -inch diameter polystyrene rod.
- R_1 — 20,000 ohms, $\frac{1}{2}$ watt.

plate choke are supported as shown in the photograph. The condenser along the rear edge of the assembly is the heater by-pass condenser, C_4 .

The oscillator assembly is mounted on a $3\frac{1}{4}$ by $3\frac{1}{4}$ -inch aluminum channel $\frac{3}{4}$ of an inch deep. A small panel at the front provides a place for a tuning dial which drives the condenser shaft through an insulated coupling. A dial lock is provided so the condenser can be locked at a given frequency setting.

A polystyrene-insulated double binding post assembly mounted vertically from a small bracket provides output terminals and a support for the antenna coupling coil, L_2 . The coupling can be varied by bending the soldering lugs that support the coil so that L_2 is moved nearer to or farther away from L_1 .

The condenser construction provides just enough capacity variation to cover the 144-148-Mc. band adequately. Because of slight differences in the construction of similar units, it may be necessary to vary the inductance of L_1 slightly to bring the band on the dial; this can be done by squeezing the turns together or pulling them apart. The frequency range can be checked with Lecher wires or a calibrated absorption wavemeter. (See chapter on frequency measurement.) Final adjustment to L_1 should be made after C_3 has been adjusted for optimum output from the oscillator, since the setting of this condenser has some effect on the frequency of oscillation.

To adjust C_3 , solder two pieces of wire about $\frac{3}{4}$ inch long to the terminals of a small flashlight lamp or dial light and connect them to the output terminals. A milliammeter of 0-50 or 0-100 range should be connected in the plate-supply lead. Adjust the coupling between the L_2 and L_1 for maximum glow in the lamp and then vary the capacity of C_3 until the best output is obtained. C_3 need not be touched again after the proper setting is determined.

In using the oscillator for transmitting, the

coupling between L_1 and L_2 should be kept as loose as possible, particularly if the antenna or feeders can swing in a breeze, because any change in the antenna circuit will be reflected as a change in the oscillator frequency. In any event, the coupling should not be increased beyond the setting that makes the oscillator plate current 25 milliamperes. At 300 volts the plate current should be about 20 ma. without any r.f. load.

The oscillator can be modulated by any audio power amplifier having an output of 3 watts or so — a single Class-A 6F6, for example. The modulator coupling transformer should have the proper ratio to work from the modulator tube chosen into a 12,000-ohm load. For a Class-A pentode modulator taking a 7000-ohm load this requires a step-up turns ratio of 1.3 to 1.

□ A High-C 144-Mc. Oscillator

The inherent instability of a modulated oscillator — that is, the change in frequency with the change in plate voltage under modulation — can be markedly reduced if the oscillator tank circuit is made to have as high a C/L ratio as possible. Although this usually entails some sacrifice of power output, the overall effectiveness of the transmitter is increased because the radiated energy is more nearly on

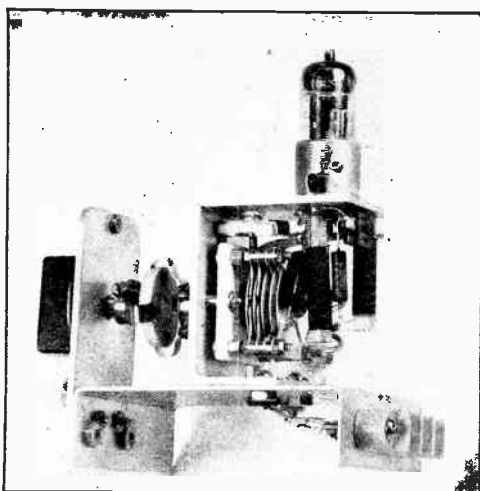


Fig. 1625 — A view showing the assembly of components of the 6C4 144-Mc. oscillator. The r.f. chokes are mounted by drilling and tapping the ends of the polystyrene rod. The grid choke is held in place by one of the socket mounting screws.

one frequency. This is a particularly important consideration when selective receivers are used. In addition, the fact that there is less frequency modulation also means that there is less interference to other stations operating in the same band.

A high-C 144-Mc. oscillator is shown in Figs. 1626, 1627, and 1628. It uses an HY75 tube and a tank circuit consisting of a low-inductance v.h.f. condenser and a one-turn tank coil of heavy conductor. The circuit, shown in Fig. 1627, is the ultraudion with a tuned filament circuit to provide control of excitation. The oscillator is mounted on a 3-by-4-by-5-inch box, with the tube socket mounted below the top by means of pillars so that only the glass bulb is protruding. To bring the condenser terminals on the same level as the grid and plate terminals of the tube the condenser is mounted on 5/8-inch high blocks. The tube socket is positioned so that the plate cap of the tube is near one set of the stator plates of C_1 . This leaves room to mount the grid condenser, C_2 , between the grid cap and the other stator terminal, thus making the leads between the tank circuit and the tube as short as possible. The output coupling coil, L_2 , is soldered to lugs under the binding posts of a two-post assembly mounted on a 2 1/2-inch isolantite stand-off insulator. A friction-type vernier dial is used to tune the circuit, because the tuning is rather critical with the high-C circuit and because the type of condenser used requires this or a similar type of dial to hold the setting, since the shaft turns on ball bearings.

The tuned filament circuit consists of L_3 , L_4 and C_3 . L_3 is wound between the turns of L_4 so that the coupling is very tight; thus both filament leads can be tuned by one condenser, C_3 . C_3 is adjusted for maximum output as

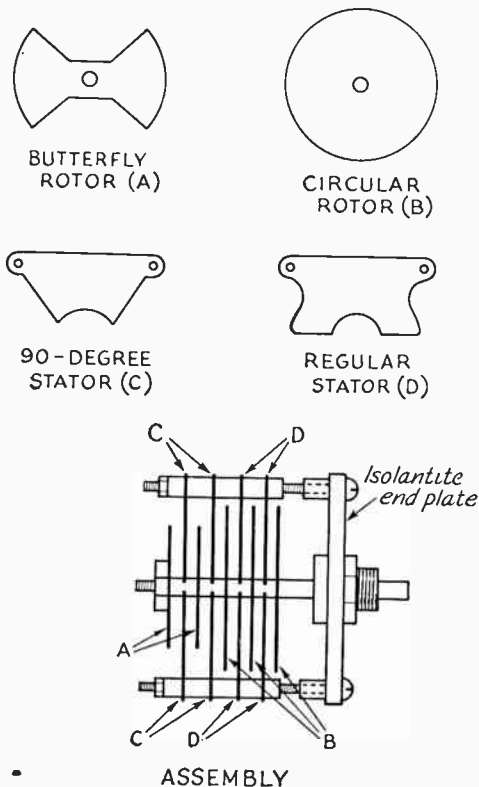


Fig. 1624 — Plate shapes and assembly of C_1 , the tuning condenser used in the 6C4 oscillator.

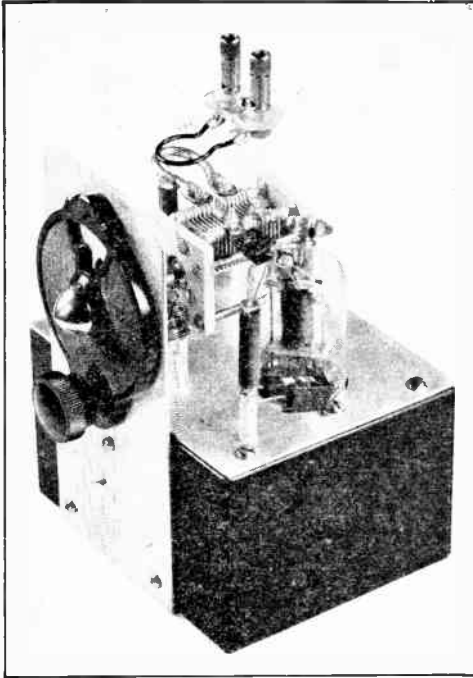


Fig. 1626 — A high-C 144-Mc. oscillator using an 6Y75. This type of oscillator has considerably less frequency modulation than those using low-C circuits, consequently causes less interference and can be more effectively received on selective receivers.

judged by the brilliance of a lamp connected to the output terminals; it has relatively little effect on the frequency of oscillation.

The inductance of L_1 should be adjusted so that the low-frequency end of the 144-Mc.

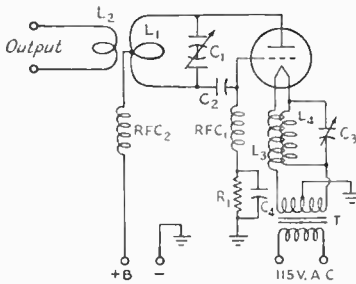


Fig. 1627 — Circuit diagram of the high-C 144-Mc. oscillator.

- C_1 — Split-stator condenser, 31.5 μ fd. total (Hammond VC-30).
- C_2 — 50- μ fd. midget mica.
- C_3 — 3-30- μ fd. ceramic trimmer.
- C_4 — 100- μ fd. midget mica.
- L_1 — 1 turn of 5/32-inch copper tubing, approximately horseshoe shape; overall length from mounting holes in lugs, 1 3/8 inches; outside diameter at widest point, 13/16 inches; plate tap at center.
- L_2 — 1 turn No. 14 enameled; diameter 3/4 inch.
- L_3, L_4 — 6 turns No. 13 d.s.c. on 1/2-inch form; L_3 interwound with L_4 , no spacing between turns.
- R_1 — 5000 ohms, 1 watt.
- RFC_1, RFC_2 — 1-inch winding of No. 24 d.s.c. or s.c.c. on 1/4-inch diameter polystyrene rod.
- T — 6.3-volt filament transformer.

band is reached with C_1 set as close as possible to maximum capacity. It is advisable to start with the coil a little larger than necessary and cut a little at a time off the ends until the proper inductance is found. The connections between the coil and the condenser are made by means of lugs fashioned from tubing just enough larger in diameter than the coil so that the ends of the coil will fit inside. One end of each lug is flattened and drilled to fit the condenser terminals, and the coil is soldered in the unflattened ends.

With a plate input of 350 volts at about 60 milliamperes the power output of the oscillator is approximately 4 watts. When received on a superheterodyne-type receiver with a beat-

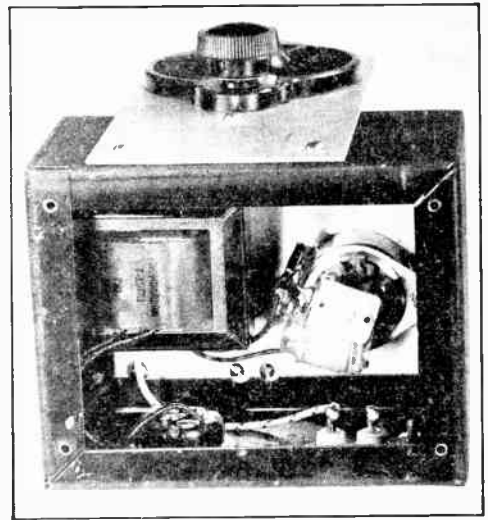


Fig. 1628 — Below-chassis view of the high-C 144-Mc. oscillator. The filament transformer and filament tuned circuit are mounted inside the box.

frequency oscillator, the carrier will be quite clean and stable provided the mechanical construction is rigid. Under modulation, the frequency band occupied is only about a fifth as much as that taken up by a low-C oscillator operated at the same plate voltage.

◀ A Stabilized 144-Mc. Transmitter

In general, a modulated oscillator is not a desirable type of transmitter for use in a band such as 144 Mc. where there is considerable activity. Even when stabilized by the use of a high-C tank circuit this type of transmitter leaves much to be desired, because there is still a great deal more frequency modulation than is present in a master oscillator-power amplifier transmitter. In addition, an oscillator coupled to an antenna is subject to frequency change whenever the antenna constants change slightly, as they will with changes in weather and with any vibration or swinging of the feeder wires. Besides, an oscillator cannot be modulated 100% without considerable distur-

tion because in most cases oscillation cannot be sustained at plate voltages below 50 to 100 volts. Finally, the efficiency of an oscillator is quite low compared to the efficiency of a properly-driven amplifier, so that considerably more power output can be obtained from the same tube when it is used as an amplifier than when it is used as an oscillator.

An amplifier driven by an oscillator, although more stable than an oscillator alone, is still subject to frequency-modulation effects because the change in power input to the amplifier with modulation causes a change in the grid impedance of the amplifier, and this in turn reacts on the oscillator to change the frequency. Hence it is desirable to use at least one buffer amplifier stage between the oscillator and amplifier. If this is done it is quite possible to get satisfactory performance with inexpensive low-power tubes in both oscillator and buffer stages, while if the buffer is omitted it is necessary to use a fairly high-power oscillator. This is because the coupling between the oscillator and modulated amplifier must be very loose if the oscillator frequency is not to be affected by whatever happens in the amplifier plate circuit; consequently the oscillator must develop much greater power than actually is needed to drive the amplifier since only a small part of the power can be utilized with the loose coupling required.

A three-stage transmitter in which frequency-modulation effects are quite small is shown in Figs. 1629 to 1632, inclusive. It includes a 6C4 oscillator, 6C4 neutralized buffer amplifier, and 815 final amplifier, as shown in

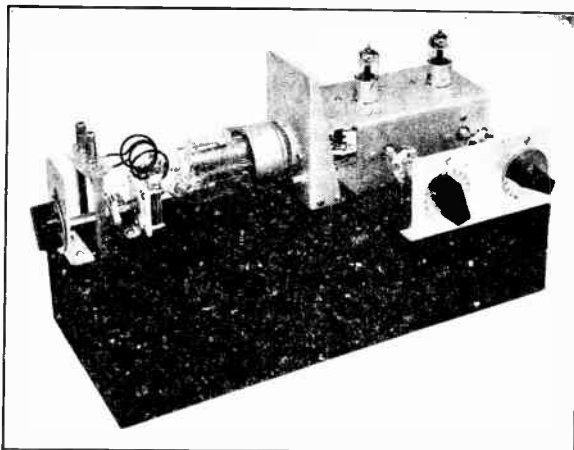



Fig. 1629 — A three-stage transmitter using a 6C4 master oscillator, 6C4 buffer amplifier, and 815 final amplifier, for stabilized transmission in the 144-Mc. band. The oscillator and buffer are built as a unit on the folded aluminum chassis at the right. The transmitter develops a carrier output of about 10 watts.

the circuit diagram, Fig. 1630. The oscillator and buffer are built as a unit on a U-shaped piece of aluminum $6\frac{1}{2}$ inches long on top, $2\frac{3}{8}$ inches high, and $2\frac{7}{8}$ inches deep on the top. The 815 is mounted on a vertical aluminum piece measuring $1\frac{1}{4}$ inches high and 3 inches wide, reinforced by bending side lips as shown in the photographs. The two sections are assembled on a 6- by 14- by 3-inch chassis.

The oscillator circuit and components are identical with those already described in Figs. 1622 to 1625. The construction of the buffer amplifier is quite similar to that of the oscillator. The buffer tuning condenser consists of a rotor having three butterfly plates (A in Fig. 1621) and two stators each having two 90-degree plates (C in Fig. 1624). The grid circuit

Fig. 1630 — Circuit diagram of the stabilized 144-Mc. transmitter.

- C₁ — 3–30- μ fd, trimmer.
- C₂, C₆, C₁₁, C₁₃ — 500- μ fd, midget mica.
- C₃, C₅ — 50- μ fd, midget mica.
- C₄ — Oscillator tuning; see text.
- C₇ — Neutralizing; see text.
- C₈ — Buffer tuning; see text.
- C₉, C₁₀ — Amplifier neutralizing; see text.
- C₁₂ — Amplifier tuning; see text.
- C₁₄ — 100 μ fd., 2500 volts.
- L₁ — 2 turns No. 12 bare wire; inside diameter $\frac{9}{16}$ inch, length 1 inch; plate-supply tap at center.
- L₂ — 2 turns No. 14, inside diameter $\frac{1}{2}$ inch; turns spaced wire diameter.
- L₃ — 4 turns No. 11, inside diameter $\frac{3}{4}$ inch, length 1 inch; plate-supply tap at center.
- L₄ — 2 turns No. 11, inside diameter $\frac{1}{2}$ inch; turns spaced diameter of wire; tapped at center.
- L₅ — 2 turns No. 12, inside diameter 1 inch, length 1 inch; plate supply tap at center.
- L₆ — 2 turns No. 12, inside diameter $\frac{3}{4}$ inch.

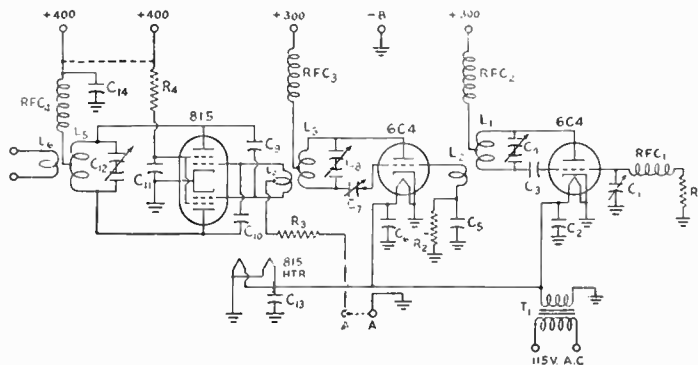

- R₁ — 20,000 ohms, $\frac{1}{2}$ watt.
- R₂ — 25,000 ohms, $\frac{1}{2}$ watt.
- R₃ — 15,000 ohms, 1 watt.
- R₄ — 15,000 ohms, 10 watts.
- T₁ — 6.3-volt, 2-amp. filament transformer.

of the buffer is self-resonant, the tuning being adjusted by squeezing the turns of the grid coil, L_2 , together or prying them apart. The buffer neutralizing condenser, C_7 , mounted directly between the grid of the 6C4 and the lower set of stator plates of C_8 , is a 3-30- μ fd. trimmer with the movable plate removed and a washer soldered under the head of the adjusting screw. The washer, by replacing the movable plate, reduces the capacity of the condenser to a value suitable for neutralizing the 6C4.

The grid coil of the final amplifier also is resonant with the input capacity of the 815, just as the buffer grid circuit is self-resonant. For best operation, the 815 requires neutralization at this frequency. The neutralizing "condensers," C_9 and C_{10} in the circuit diagram, are simply pieces of No. 14 wire extending from the grid of one section of the 815 to the vicinity of the plate of the other section. The wires are crossed at the bottom of the tube socket and go through Millen 32150 bushings in the metal partition. The screen and filament by-pass condensers are mounted so that the leads between the socket prongs and the nearest ground point are as short as possible.

The amplifier plate tank circuit uses a condenser of the same construction as that used in the buffer tank. It is mounted as closely as possible to the plate caps on the 815, and to preserve circuit symmetry the condenser is tuned from the left-hand edge of the chassis. If the transmitter is to be equipped with a regular panel this condenser may be operated by a right-angle drive from the front.

The output terminals are a standard binding-post assembly on polystyrene, mounted on metal posts 2 $\frac{3}{8}$ inches high to bring the coupling coil in proper relation to the amplifier plate tank coil, L_5 . Coupling is adjusted by bending L_6 toward or away from L_5 .

The plate by-pass condenser and screen dropping resistor are mounted underneath the

chassis, as shown in Fig. 1636, together with the filament transformer. Separate power-supply terminals are provided for the oscillator plate, buffer plate, amplifier grid, amplifier screen, and amplifier plate so that the currents can be measured separately.

In putting the transmitter into operation, the first step is to adjust the frequency range of the oscillator as described in connection with the 6C4 oscillator discussed earlier in this chapter. Then, using loose coupling between the buffer grid coil, L_2 , and the oscillator tank coil, L_1 (the coupling may be adjusted by bending L_2 away from L_1 on its mounting lugs) adjust L_2 by changing the turn spacing until the grid circuit is resonant. Resonance will be indicated by maximum oscillator plate current; it can also be checked by measuring the voltage across the buffer grid leak, R_2 , with a high-resistance voltmeter. The maximum voltmeter reading (about 40 volts) indicates resonance. The buffer should next be neutralized by varying the capacity of C_7 until there is no change in the voltage across R_2 when the buffer tank condenser, C_8 , is tuned through resonance. The point of correct neutralization also can be determined by coupling a sensitive absorption wavemeter such as is described in the chapter on frequency measurement to the buffer plate coil and adjusting C_7 for minimum reading. With this method, care must be used to avoid coupling between the wavemeter and the oscillator; link coupling between L_3 and the wavemeter, with the latter far enough away so that it does not give a reading from the oscillator alone, should be used. Another method of checking neutralization is to adjust the turn spacing of the amplifier grid coil, L_4 , to resonance and measure the 815 grid current (with no plate or screen voltage on the tube) and adjust C_7 for zero grid current.

After the buffer is neutralized, plate voltage may be applied and C_8 adjusted to resonance, as indicated by minimum plate current. If the

coupling to the final amplifier is quite loose, the minimum plate current should be approximately 17 ma. The amplifier grid coil may next be resonated (by adjusting the spacing between turns) and the coupling increased until the maximum grid current is secured. The grid current should be 4 milliamperes or more and the buffer plate current should rise to about 28 ma.

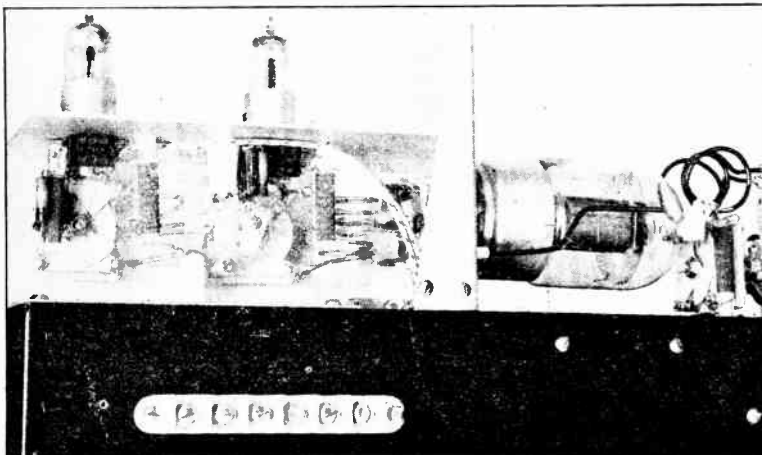


Fig. 1631 — A rear view of the three-stage 144-Mc. transmitter. The oscillator is at the left, with the buffer amplifier to the right.

Neutralization of the 815 is the next step. If the grid current changes when the plate condenser, C_{12} , is tuned through resonance, the neutralizing wires should be moved closer to or farther away from the tube plates until tuning C_{12} has no effect on the grid current. When this condition is reached the amplifier is neutralized. Plate and screen voltage may then be applied. With no load on the amplifier the plate current should dip to approximately 65 ma. at resonance. Loading the amplifier to a plate current of 150 ma. should not cause the grid current to drop below about 3.5 ma. A 40-watt lamp used as a dummy load should light to practically normal brightness at this input, using a plate-supply voltage of 400.

For greatest stability, the coupling between the oscillator and buffer should be as loose as possible. It is better to obtain the rated 815 grid current of 3 milliamperes by using tight coupling between the buffer and amplifier and loose coupling between the oscillator and buffer than vice versa. With normal operation the oscillator plate current should be approximately 25 ma. and the buffer plate current 28 ma., using a plate voltage of 300.

A modulator for the transmitter should have an audio output of 35 watts, using a coupling transformer designed to work into a 2500-ohm load.

◀ A 144-Mc. Double Beam Tetrode Power Amplifier

An amplifier set-up suitable for use with double beam-tetrode tubes is shown in Figs. 1633, 1634 and 1635. The tube in the photographs is an 829, but an 815 or 832 can be used in the same layout. The only change that might be required would be in the inductances of the grid and plate coils, L_2 and L_3 ; these may have to be made slightly smaller or larger in diameter to compensate for the differences in input and output capacitances in the various types.

The physical arrangement of the components is similar to that used for the 815 amplifier incorporated in the three-stage transmitter described in the preceding section.

The amplifier of Fig. 1633 is built on an aluminum chassis formed by bending the long edges of a 5 by 10-inch piece of aluminum to form vertical lips $\frac{3}{4}$ inch high, so that the top-of-chassis dimensions are $3\frac{1}{2}$ by 10 inches. The tube socket is mounted on a vertical aluminum partition measuring $3\frac{1}{2}$ inches high by $3\frac{1}{4}$ inches wide on the flat face, with the sides bent as shown in the photographs to provide bracing. The partition is mounted to the chassis by right-angle brackets fastened to the sides. The socket is mounted with the cathode connection at the top, the cathode prong being directly grounded to the nearest mounting screw for the socket. The heater by-pass condenser, C_6 , is mounted directly over the center of the tube socket, extending between the paralleled heater prongs at the bottom and the cathode prong at the top. The screen by-pass is connected with as short leads as possible between the screen prong and the nearest socket mounting screw.

The grid coil, L_2 , is supported by the grid prongs on the socket. The two turns of the coil are spaced about one-half inch to allow room for the input coupling coil, L_1 , to be inserted between them. The coupling is adjusted by bending L_1 into or out of L_2 . The grid tuning condenser, C_1 , is mounted between the socket prongs; although the condenser has mica insulation it is used essentially as an air-dielectric condenser since the movable plate does not actually contact the mica at any setting inside the band. The coupling link is soldered to lugs under binding posts on a National FWG strip, the strip being mounted on metal pillars $1\frac{1}{2}$ inches high to bring the link to the same height as the grid coil.

Although the shielding between the input and output circuits of the tube is sufficiently

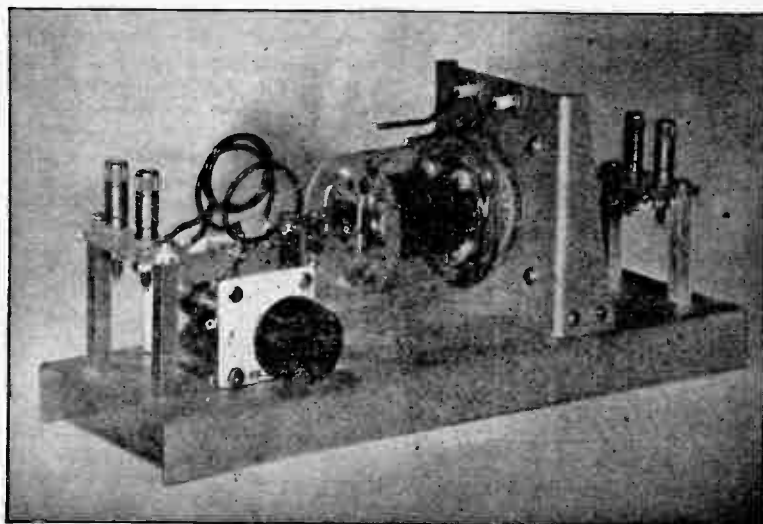


Fig. 1633 — A 144-Mc. amplifier using a double beam tetrode. This type of construction is suitable for the 815 and 832 as well as the 829 shown. The vertical partition provides support for the tube as well as shielding between the input and output circuits. Note the neutralizing "condensers" formed by the wires near the tube plates.

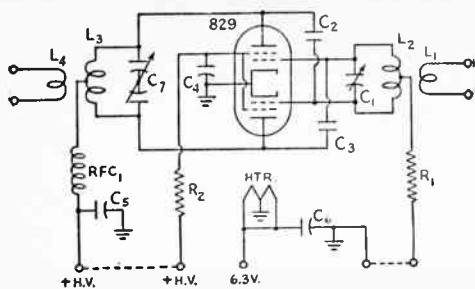


Fig. 1634 — Circuit of the 829 amplifier for 141 Mc.

- C_1 — 3–30- μ fd. ceramic trimmer.
 C_2, C_3 — Neutralizing condensers; see text.
 C_4 — 500- μ fd. mica, 1000-volt.
 C_5 — 500- μ fd. mica, 2500-volt.
 C_6 — 500- μ fd. mica.
 C_7 — Split-stator, 15 μ fd. per section (Cardwell ER-15-AD).
 L_1 — 2 turns No. 12, diameter $\frac{1}{2}$ inch.
 L_2 — 2 turns No. 12, diameter $\frac{1}{2}$ inch, length $\frac{1}{2}$ inch.
 L_3 — 2 turns No. 12, diameter $1\frac{1}{8}$ inches, length 1 inch.
 L_4 — 2 turns No. 12, diameter 1 inch.
 R_1 — 5000 ohms, 1 watt.
 R_2 — 10,000 ohms, 10-watt.
 RFC_1 — 1-inch winding of No. 21 d.s.c. or s.c.c. on $\frac{1}{4}$ -inch diameter polystyrene rod.

good so that the circuit will not self-oscillate, tuning of the plate circuit will react on the grid circuit to some extent because the grid-plate capacity, although small, is not zero. To eliminate this reaction it is necessary to neutralize the tube. The neutralizing “condensers” are lengths of No. 12 wire soldered to the grid prongs on the socket. The wires are crossed over the socket and then go through small ceramic feed-throughs at the top of the vertical shield, projecting over the tube plates on the other side as shown in Fig. 1633.

Connections between the plate tank condenser, C_7 , and the tube plate terminals are made by means of small Fahnestock clips soldered to short lengths of flexible wire. The tank coil, L_3 , is mounted on the same condenser terminals to which the plate clips make con-

nection. The output link, L_4 , is mounted similarly to the grid link except that the posts are $1\frac{1}{8}$ inches high. The plate choke, RFC_1 , is mounted vertically on the chassis midway between the plate prongs of the tube, the mounting means being a short machine screw threaded into the end of the polystyrene rod. The “cold” lead of the choke is by-passed by C_5 underneath the chassis, directly below the point where the lead passes through.

Supply connections are made through a 5-post strip on the rear edge of the chassis. The dotted lines between connections in Fig. 1634 indicates that these connections are normally short-circuited; separate leads are brought out from the grid and screen so that the currents can be measured separately.

In adjusting the amplifier, the plate and screen voltages should be left off and the d.c. grid circuit closed through a milliammeter of 0–25 or 0–50 range. The driver should be coupled to the amplifier input circuit through a link (Amphenol Twin-Lead is suitable, because of its constant impedance and low r.f. losses). Use loose coupling between L_1 and L_2 at first, and adjust C_1 to make the grid circuit resonate at the driver frequency, as indicated by maximum grid current. The coupling between L_1 and L_2 may then be increased to make the grid current slightly higher than the rated load value for the tube used. This is approximately 12 ma. for the 829. If the driver is an oscillator, the coupling between L_1 and L_2 should be kept as loose as possible so long as the proper grid current is obtained.

Neutralization can be checked by rotating C_7 through resonance. A flicker in grid current as C_7 is rotated indicates that the neutralizing capacity is not correct. The neutralizing wires should be bent in relation to the tube plates until the grid current remains constant when C_7 is tuned through resonance. Care should be used to keep the wires symmetrical with re-

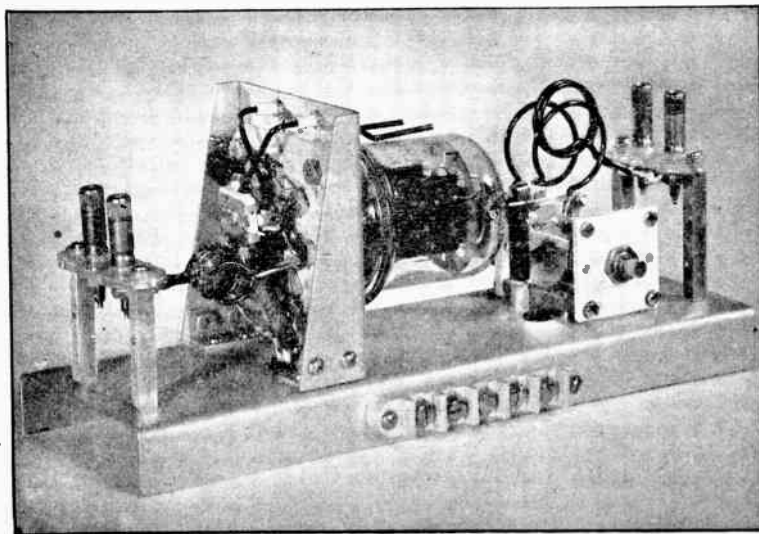


Fig. 1635 — Another view of the 141-Mc. amplifier. The neutralizing wires are crossed over the socket before going through the feed-through insulators. The input circuit is designed for link coupling to the driver stage.

spect to the two sections of the tube.

After neutralization, plate and screen voltage may be applied. If possible, the plate voltage should be low at first trial so there will be no danger of overloading the tube. Adjust C_7 to resonance, as indicated by minimum plate current (this should be measured independently of the screen); with the 829, the minimum plate current should be in the neighborhood of 80 milliamperes with 400 volts on the plate and no load on the circuit. A dummy load such as a 60-watt lamp should light to something near full brilliance when the coupling between L_3 and L_1 is adjusted to make the tube draw a plate current of 200 ma. When the loading is set, the grid current should be checked to make sure it is up to the rating for the tube. If it has decreased, the coupling between L_1 and L_2 should be increased to bring it back to normal.

Power-supply and modulator requirements will depend upon the particular tube used. For the 829, the plate supply should have an output voltage of 400 to 500 with a current capacity of 250 milliamperes. With a 400-volt supply the modulator power required is 50 watts, with an output transformer designed to work into a 1600-ohm load; with a 500-volt supply slightly over 60 watts of audio power is needed, the load being 2000 ohms.

Ⓒ Transceivers

The transceiver is a combination transmitter-receiver in which, by suitable switching of d.c. and audio circuits, the same tube and r.f. circuit functions either as a modulated transmitting oscillator or as a superregenerative detector. The advantages of the transceiver are compactness, circuit simplicity, and the use of the same antenna for both transmitting and receiving without the necessity for switching the r.f. circuits. Transceivers have been widely used for portable and mobile work.

In general, switching means must be provided in the transceiver so that when reception is desired the audio-frequency amplifier is connected as in a normal receiver; simultaneously the microphone must be disconnected from the a.f. amplifier. Insofar as the oscillator is concerned, the value of the grid leak must be changed when switching from receive to transmit, since a high value is required when the tube is to act as a superregenerative detector and a relatively low value as a transmitting oscillator. The plate voltage also must be changed from the low value required by the detector to the high value needed for transmission. A special audio transformer ("transceiver transformer") having a microphone winding in addition to the normal windings, is required.

The disadvantages of the transceiver, from the standpoint of work in an amateur band, are largely the result of the circuit simplicity. As with any modulated oscillator, the signal from a transceiver is broad; in the type of con-

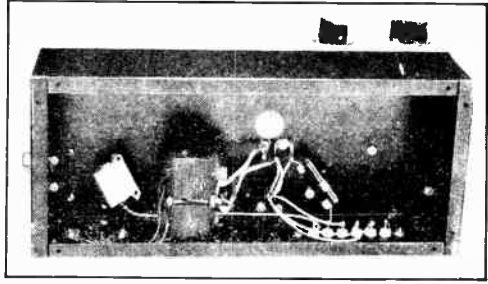


Fig. 1636 — Underneath the chassis of the 144-Mc. m.o.p.a. transmitter. The filament transformer, amplifier plate by-pass condenser, and screen dropping resistor are mounted here.

struction used there is relatively little opportunity for the stabilization that can be obtained with the high- C' oscillators described earlier in the chapter. When receiving, the superregenerative detector radiates and causes interference to other stations operating in the vicinity; in fact, in many cases the radiation from the receiver covers almost as much distance range as the oscillator does when intentionally being used for transmitting. This is because the degree of antenna coupling used, when adjusted for good transmitting, is such that rather high plate voltage must be used on the tube to make it superregenerate when receiving, with the result that the power input to the tube is relatively high.

The transceiver also has an operating disadvantage in that, since the tuned circuit is common to both the transmitter and receiver, the transmitting frequency is necessarily the same as that on which receiving is done. However, the transmitting and receiving frequencies are not *exactly* the same because the plate voltages used for transmitting and receiving differ. Consequently there is a frequency change each time there is a changeover from receiving to transmitting. The result of this is that when two transceiver stations are in communication their frequencies tend to "walk through" the band because either must retune for best reception when the other transmits, and this retuning in turn changes the transmitting frequency. In the course of a contact it is readily possible for both stations to move entirely outside the band limits.

As a matter of good amateur practice the use of transceivers should be confined to very low-power operation — as in "walkie-talkie" or "handie-talkie" equipment — in the 144-Mc. band, and to experimental low-power operation in the higher-frequency bands. The use of transceiver-type equipment should be avoided entirely for regular operation on 144 Mc. in areas where there is considerable activity on this frequency.

The transceivers shown in this chapter are intended primarily for portable or portable-mobile operation, using batteries as a source of power supply.

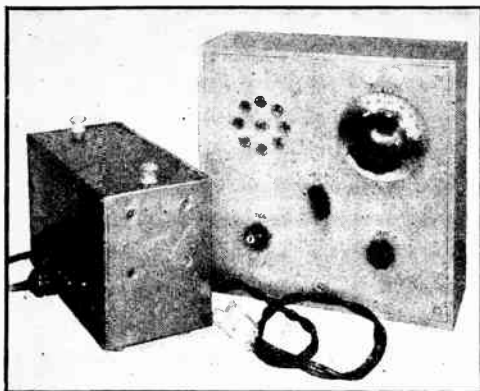


Fig. 1636 — An inexpensive low-power 144-Mc. transceiver and vibrator power supply.

□ A Simple 144-Mc. Transceiver

The transceiver shown in Figs. 1636, 1637 and 1638, constructed from inexpensive parts, can be used either as a piece of fixed-station equipment or for portable-mobile work. The panel is a 10×10 -inch piece of $\frac{1}{4}$ -inch tempered Presdwood, while the shelf which holds the audio circuits is a $3\frac{1}{2} \times 10$ -inch piece of the same material. The shelf is mounted $1\frac{1}{2}$ inches above the bottom of the panel, leaving room for the resistors and condensers underneath. The box in which the transceiver is housed is made of $\frac{1}{4}$ -inch plywood, the inside dimensions being $10 \times 10 \times 3\frac{1}{2}$ inches. At the back a door, hinged at the bottom, gives access to the tubes and r.f. section.

The oscillator is all in one unit, built on a 3×4 -inch piece of aluminum with $\frac{1}{2}$ inch bent over at one end to form a mounting lip. The metal base projects $3\frac{1}{2}$ inches behind the

panel, the same depth as the shelf for the audio section. In general, the oscillator circuit has been arranged to make the leads between the tube and tuned circuit as short as possible. The mechanical layout may have to be varied for tuning condensers of different construction. A condenser having a maximum capacity of 10 to 15 $\mu\text{fd.}$ is required for C_1 . The one used in this unit is a Hammarlund MC-20-S (originally having a maximum of 20 $\mu\text{fd.}$) with one plate removed. To reduce capacity to ground, the rear bearing assembly should be removed by sawing off the rotor shaft and the side rods holding the stator plate. Removing this excess material noticeably increases the efficiency.

The tuned-circuit coil, L_1 , is mounted under the condenser panel-mounting nut, the other end being soldered to the side rod holding the stator plate. Since both sides of the condenser must be insulated from ground, the condenser is mounted on a midget stand-off insulator. An insulated coupling and extension shaft connect the rotor to the tuning dial.

The plate and grid chokes are mounted from insulated lugs at the "cold" ends, the hot ends being placed as close as possible to the points in the circuit where they connect. The power leads from the r.f. section are cabled and brought down to the switch.

To protect the speaker cone from damage, the grille holes are backed by a piece of window-screen material which is held in place by the bolts which are used to fasten the speaker to the panel.

A metal strip running from top to bottom of the panel serves as a shield to prevent body capacity and also as a low-inductance ground

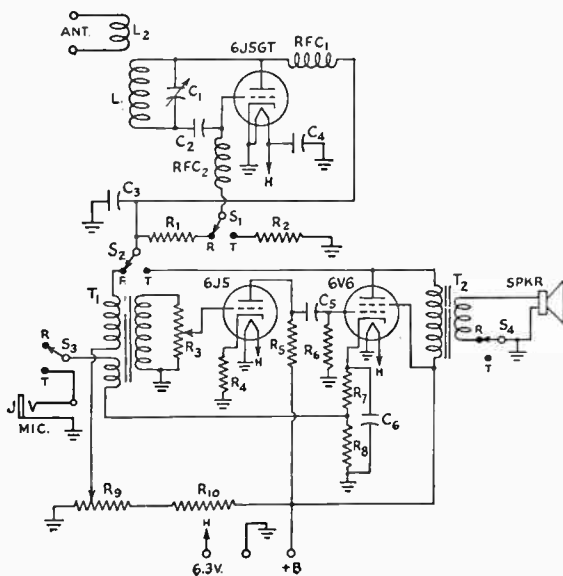


Fig. 1637 — Circuit diagram of the 144-Mc. transceiver.

- C_1 — Midget variable, 10–15 $\mu\text{fd.}$ maximum capacity.
- C_2 — 50- $\mu\text{fd.}$ mica.
- C_3 — 0.005- $\mu\text{fd.}$ mica.
- C_4 — 250- $\mu\text{fd.}$ mica.
- C_5 — 0.1- $\mu\text{fd.}$ paper, 400 volts.
- C_6 — 25 to 50 $\mu\text{fd.}$ electrolytic, 50 volts.
- R_1 — 5 megohms, $\frac{1}{2}$ -watt.
- R_2 — 5000 ohms, 1-watt (for 6J5, 6C5); 10,000 ohms, 1-watt (for 6V6, etc.).
- R_3 — 0.5-megohm volume control.
- R_4 — 1000 ohms, $\frac{1}{2}$ -watt.
- R_5 — 0.1 megohm, 1-watt.
- R_6 — 0.5 megohm, $\frac{1}{2}$ -watt.
- R_7 — 250 ohms, 1-watt.
- R_8 — 200 ohms, 1-watt.
- R_9 — 50,000-ohm volume control.
- R_{10} — 50,000 ohms, 1-watt.
- L_1 — 3 turns No. 12, 9/16-inch inside diameter, $\frac{1}{2}$ -inch long.
- L_2 — 1 turn No. 12 or No. 14.
- RFC $_1$, RFC $_2$ — 55 turns No. 30 d.c.e., close-wound, $\frac{1}{4}$ -inch diameter.
- T_1 — Transceiver transformer (see text).
- T_2 — Output transformer, pentode to voice coil.
- S_{1-4} — 4-pole double-throw switch.
- J — Open-circuit jack.
- Spkr — 3-inch permanent-magnet dynamic speaker.

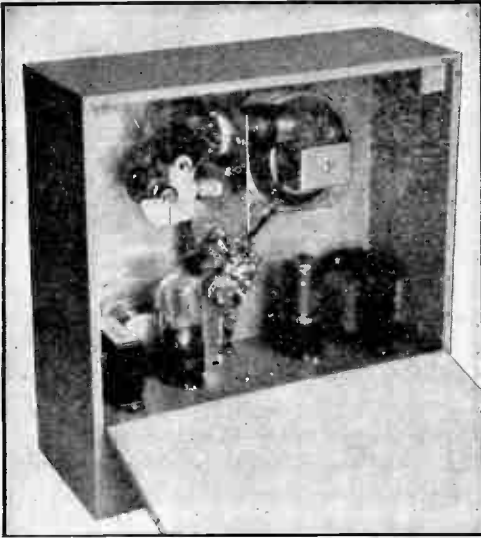


Fig. 1638 — Rear view of the 144-Mc. transceiver installed in its case. The oscillator-detector is constructed as a unit.

connection between the oscillator and the audio section. It makes direct contact with the oscillator support, the rotor of R_5 , and the metal frames of the switch and microphone jack.

In the rear view the transformer at the left is T_1 , the transceiver transformer. The audio gain control, R_3 , is on the panel between R_1 and the 6J5 first audio. The modulator tube and speaker transformer are at the right, with the regeneration control, R_9 , behind them on the panel. All leads from the switch are cabled and pass through a hole in the shelf near the panel. The two grid leaks, R_1 and R_2 , are mounted directly on the switch contacts, but all other resistors are below the shelf. The below-shelf arrangement is of no particular consequence, since there are no r.f. circuits underneath, but the grid leads to both tubes should be kept short, so that hum pick-up will be minimized. The dropping resistor, R_{10} , for the regeneration control circuit is mounted on the lug strip at the rear; the other two resistors which connect together at this strip are the two sections of the modulator cathode resistor. Spare terminals on the tube sockets are used as tie points wherever convenient.

It is possible that in a particular layout the proper choke specifications will differ from those given. The grid choke is the more critical. In the case of either choke, the number of turns should be adjusted so that the cold end can be touched with the finger without disturbing the operation of the oscillator. Effective superregene-

ration depends considerably on the grid choke and on the capacity of the plate by-pass condenser, C_3 . The circuit may not superregenerate at all with less than $0.002 \mu\text{fd.}$ at C_3 , while values higher than 0.005 tend to cut down the audio output.

The inductance of the tuned-circuit coil, L_1 , should be adjusted to bring the band on the dial by spreading the turns apart or squeezing them together. The frequency may be checked by means of an absorption wavemeter or Lecher wires as described in Chapter Nineteen. Antenna coupling is adjusted by bending the leads of the antenna coil, L_2 , to bring the coil nearer to or farther away from L_1 . The coupling should be adjusted so that with the switch in the "receive" position the oscillator goes into superregeneration smoothly; if the coupling is too tight it may not be possible to obtain superregeneration at all.

The transceiver requires a filament supply of 6.3 volts at 1.05 amp., and a plate supply capable of delivering 30 to 60 milliamperes at 135 to 200 volts. A suitable vibrator-type supply is shown in Chapter Eighteen.

Q A 144-Mc. Handie-Talkie

For short-range work the "handie-talkie" type of equipment, where the transmitter and receiver are built as a unit light and compact enough to be held in one hand and operated in much the same fashion as an ordinary telephone handset, frequently is useful. Figs. 1640, 1641 and 1642 show a unit of this type, designed for operation in the 144-Mc. band. It uses dry-cell acorn tubes in a simple transceiver circuit.

As shown in the circuit diagram, Fig. 1641, a three-pole two-position switch, S_1 , accomplishes the changeover from send to receive. One section connects or disconnects the microphone; the second section connects the proper

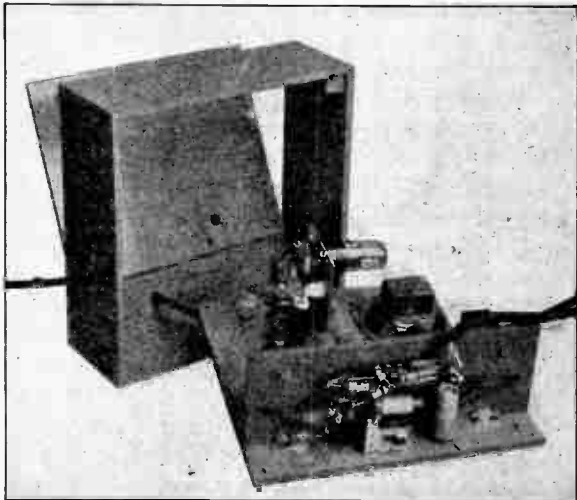


Fig. 1639 — Bottom view of the 144-Mc. transceiver.

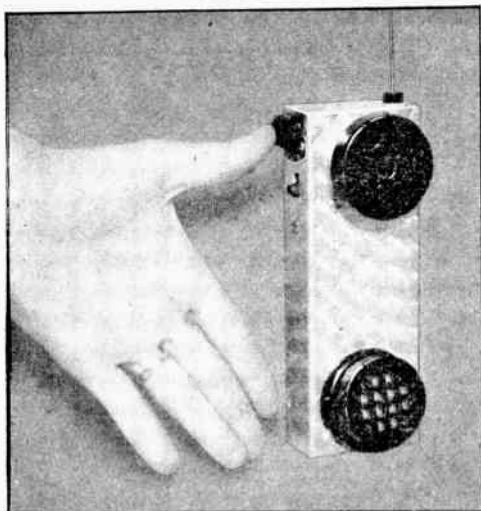


Fig. 1610 — A "handie-talkie" for the 144-Mc. band, using dry-cell type acorn tubes. It is small enough to be slipped into a pocket, but has a range up to a mile or so in reasonably open terrain (W6TWL).

grid leak, and the third section shifts the oscillator plate circuit from the primary of the transceiver transformer, T_1 , in the receive position, to the plate of the audio amplifier-modulator, for transmitting. The headphone serves as a modulation choke during transmission.

The case for the handie-talkie is $7\frac{1}{8}$ inches

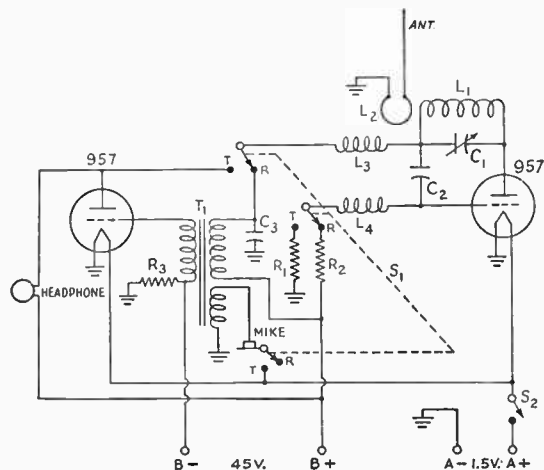


Fig. 1611 — Circuit diagram of the 144-Mc. handie-talkie.

- C_1 — 3–30 μfd . ceramic trimmer (see text).
- C_2 — 50- μfd . ceramic condenser.
- C_3 — 0.002- μfd ., 200-volt midjet paper.
- L_1 — 5 turns No. 16 tinned copper, $\frac{3}{8}$ inch inside diameter, coil length $\frac{3}{8}$ inch.
- L_2 — 1 turn No. 16, $\frac{3}{8}$ inch inside diameter.
- L_3, L_4 — 50 turns No. 36 d.s.c. on 10-megohm, $\frac{1}{2}$ -watt resistor.
- R_1 — 25,000 ohms, $\frac{1}{4}$ watt.
- R_2 — 10 megohms, $\frac{1}{4}$ watt.
- R_3 — 400 ohms, $\frac{1}{4}$ watt.
- S_1 — Triple-pole double-throw slide switch.
- S_2 — Single-pole single-throw slide switch.
- T_1 — Transceiver transformer (Inca 1-45).

high, $2\frac{5}{8}$ inches wide and $1\frac{1}{8}$ inches deep. It is made from two pieces of aluminum; one, on which the parts are mounted, is in the form of a U-shaped channel as shown in Fig. 1642, while the other is bent at the ends to complete the enclosure. The tubes are mounted by soldering the P-pins (Nos. 4 and 5) to small brass angles which in turn are mounted on opposite sides of the case, as shown in Fig. 1642. The screws that hold the angles to the case also are used to mount the two switches, S_1

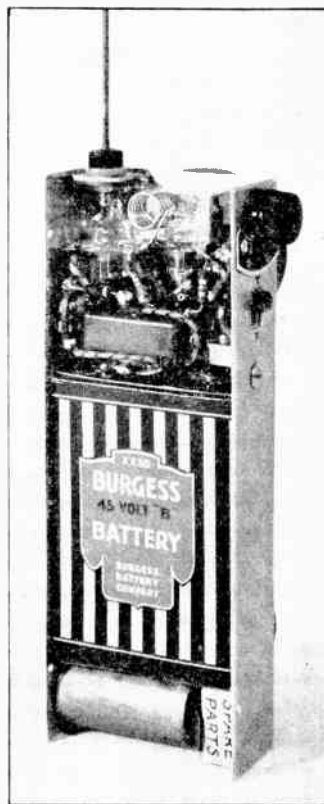


Fig. 1612 — A view inside the 144-Mc. handie-talkie. The flashlight battery for filament supply is at the bottom of the case.

and S_2 . S_1 is mounted underneath the tuning knob, while S_2 is on the opposite side.

The tuning condenser is a 3–30- μfd . trimmer with the adjusting screw removed and threaded tightly into a $\frac{3}{4}$ -inch length of $\frac{1}{4}$ -inch diameter round polystyrene rod. The head of the screw is cut off and the screw rethreaded into the condenser to make a miniature tuning condenser with the shaft extending outside the case for adjustment. Stops are provided on the dial so that the condenser knob can be rotated just enough to cover the 144–148-Mc. band. The con-

denser and tank coil, L_1 , are supported by their leads, one end of the tank circuit being soldered to the plate lead of the tube.

The microphone is a single-button unit (Universal Type W) mounted on a circular block cut at an angle so that it is properly tilted for voice pick-up when the headphone is held against the ear. The headphone is one unit of a 2000-ohm set mounted on the case.

The antenna plugs into the pin jack at the top of the transceiver. Steel or brass rod of $\frac{1}{16}$ -inch diameter may be used for the antenna; a length of approximately 18 inches is required for a quarter-wave antenna. The length may be pruned to the optimum figure by having another station check the signal strength while the length is changed, or by starting with the rod a little long and cutting off a bit at a time until the antenna shows the maximum tendency to throw the super-regenerative detector out of oscillation.

This unit uses a single No. 1 size flashlight cell for "A" power and a miniature 15-volt block (Burgess NX30) for "B" supply. The filament drain is 100 milliamperes and the plate drain 3 ma.

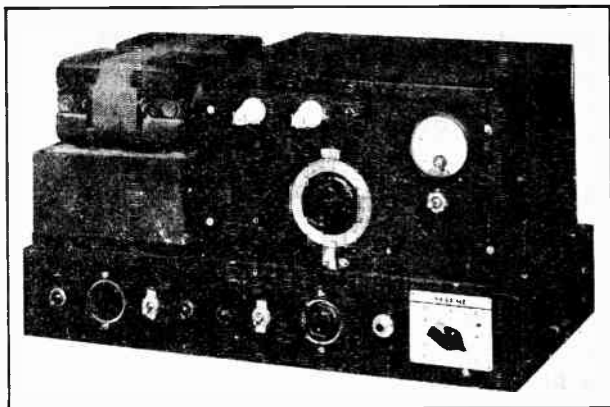


Fig. 1643 — A 144-Mc. mobile transmitter, constructed to be installed in the trunk of a car and operated by remote control from the driving position (W1DBM).

Ⓢ A Complete 144-Mc. Mobile Station

The 144-Mc. mobile equipment shown in Figs. 1643 to 1649, inclusive, offers two alternatives to the prospective user. It includes a transceiver designed for fitting into the glove compartment of a car, and this unit is a complete low-power station in itself; in addition, there is a higher-power transmitter (25 to 30 watts input) which can be installed in the car

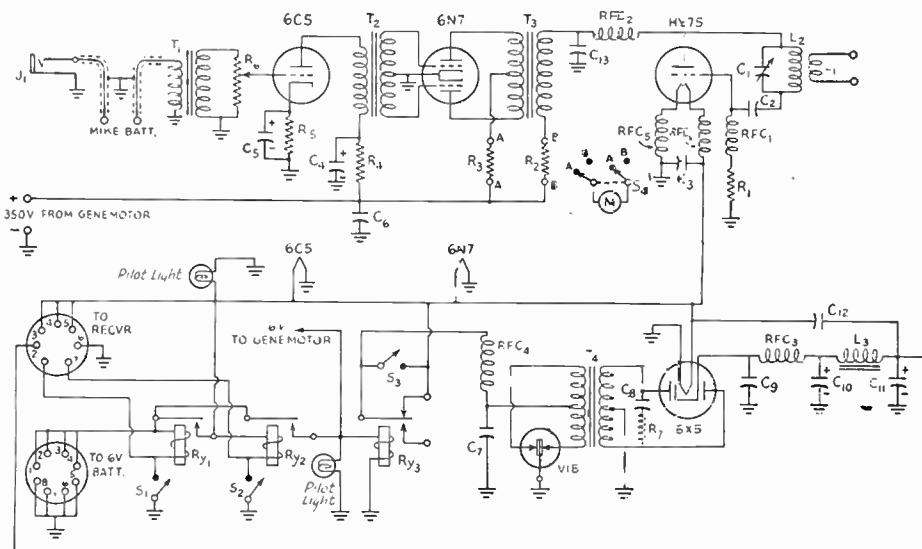


Fig. 1644 — Circuit diagram of the 144-Mc. mobile transmitter and control system.

- C_1 — 20- μ fd. variable.
- C_2 — 50- μ fd. mica.
- C_3 — 0.005- μ fd. mica.
- C_4, C_6, C_{10}, C_{11} — 16- μ fd. 150-volt electrolytic tie.
- C_5 — 25- μ fd. 25-volt electrolytic.
- C_7 — 0.5- μ fd. paper.
- C_8 — 0.015- μ fd., 1600-volt paper.
- C_9 — 0.01- μ fd. paper.
- C_{12} — 100- μ fd. mica.
- L_1 — 1 turn No. 14, $\frac{1}{2}$ inch diameter.
- L_2 — 2 turns $\frac{1}{8}$ -inch copper tubing,

- $\frac{1}{8}$ inch inside diameter, $\frac{1}{2}$ inch long.
- L_3 — 8 henrys, 150 ma.
- R_1, R_7 — 5000 ohms, 1 watt.
- R_2, R_3 — 25 ohms, $\frac{1}{2}$ watt.
- R_4 — 10,000 ohms, 1 watt.
- R_5 — 1000 ohms, $\frac{1}{2}$ watt.
- R_6 — 1-megohm potentiometer.
- RFC_1, RFC_2 — Ohmite Z-1.
- RFC_3 — 2.5 millihenrys.
- RFC_4 — 50 turns No. 12 enameled on 1-inch form.
- RFC_5, RFC_6 — 12 turns No. 14 en-

- ameled, $\frac{5}{8}$ inch inside diameter, 1 inch long.
- Ry_1, Ry_2 — S.p.s.t. relay, 6-volt coil.
- Ry_3 — S.p.d.t. relay, 6-volt coil.
- S_1, S_2, S_3 — S.p.s.t. toggle.
- S_4 — D.p.d.t. toggle.
- T_1 — Single-button microphone transformer.
- T_2 — Driver transformer, 6C5 to 6N7 grid.
- T_3 — Class-B output transformer, 6N7 to 5000-ohm load.

trunk and operated by remote control, in which case the glove-compartment transceiver is used for receiving only. The dual-transmitter plan has the advantage that the drain on the car battery is reduced when the low power output available from the transceiver is sufficient for short-distance work.

The transmitter, shown in Figs. 1643, 1645 and 1646, uses the circuit diagram given in Fig. 1644. In addition, this unit contains both a vibrator power supply for the transceiver and the control relays; installing the receiver power supply in the car trunk is helpful in reducing "hash" interference from the vibrator. The transmitting tube is an HY75 modulated by a Class-B 6N7, the modulator being driven by a 6C5 speech amplifier from a single-button carbon microphone. Current for the microphone is taken from a "C" battery in one corner of the main transmitter cabinet.

The 6N7 and HY75 plate currents are separated from one another by the output transformer, T_3 , and each may be measured by the milliammeter shown on the face of the main transmitter. The meter may be switched into the 6N7 or HY75 plate circuits at points *AA* and *BB*. Across each set of points is a 25-ohm resistor, the purpose of which is to maintain a closed plate circuit for each tube whether or not the meter is connected. The meter readings are not appreciably affected, since the 25-ohm resistors represent relatively a much higher resistance than that of the meter itself. On the panel just under the instrument is a switch, S_4 , with which this change-over may be made.

The vibrator and 6X5 rectifier circuits are thoroughly filtered. The r.f. choke, RFC_4 , is

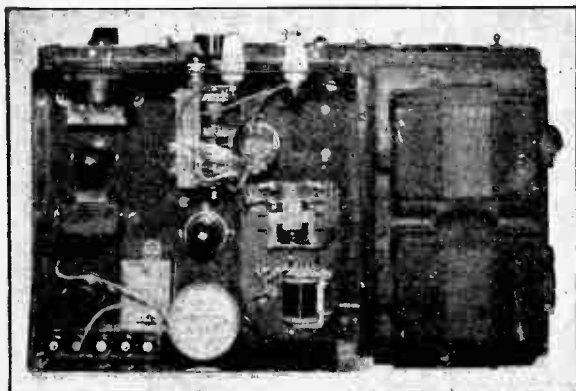


Fig. 1645 — Top view of the 144-Mc. mobile transmitter unit showing the HY75 and its tank circuit in the upper center. The relays are mounted on a sub-panel in the lower right-hand corner of the transmitter box while the audio equipment occupies the left-hand side. The vibrator for the transceiver supply is to the left of the relays.

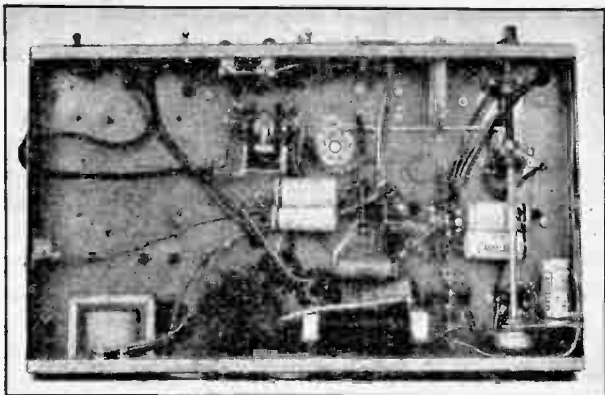


Fig. 1646 — Bottom view of the 144-Mc. mobile transmitter chassis showing the placement of the vibrator-supply components. The relay near the top of the photograph is the plate relay, Ry_2 .

by-passed by C_7 at the center-tap of the vibrator transformer primary for the purpose of killing a large portion of the hash immediately after it has been manufactured. Across the secondary is the series combination, C_8 and R_7 , to keep vibrator sparking to a minimum. The output hash is filtered by RFC_3 by-passed by C_9 at the rectifier cathode. Ordinary filtering of the rectified output voltage is done with the filter composed of L_3 , C_{10} , and C_{11} . Hash which might get through to the output via the heater of the 6X5 is by-passed by C_{12} .

There are three control switches on the transmitter, all associated with the remote-control relays. S_1 opens or closes the winding of the filament relay, Ry_1 . S_2 does the same with the plate relay, Ry_2 . If it is desired to listen on the transceiver while the main transmitter is on, S_3 can be thrown on to short the two active contacts of Ry_3 and thereby start the vibrator. The contacts of relay Ry_3 open when Ry_2 goes on and puts the main transmitter in operation. In this way plate current for the receiver is cut off during operation of the main transmitter. However, when it is desired to listen to the main transmitter for testing purposes, S_3 may be thrown on to cause the vibrator to operate. The signal in the receiver will be broad, but it is possible to tell whether the main transmitter is radiating and approximately in what part of the band it is set.

The photographs indicate the relative positions of the parts of the transmitter on the 17 × 10 × 3 inch chassis. The tuning cabinet to the right of the two genemotors measures 10 × 9 × 7 inches.

The controls which require manipulation for a quick test are located on the front edge of the chassis. The main dial is provided with a dial lock for the purpose of preventing the frequency of the transmitter from changing under car vibration. The antenna coil is

mounted on an insulating rod supported in a shaft bushing, so that the antenna coupling may be varied by rotating the rod. The coupling control knob is just above the main tuning dial in Fig. 1643. The antenna comes in conveniently to the stand-off insulators at the upper left.

The top-view photograph shows two of the relays, those for the filament and vibrator, located in one corner of the cabinet on a common base. The relay which controls the generator is underneath the chassis. The 6Y75, with two topecaps, is placed next to the tank coil and condenser. Also, the 6X5 rectifier is placed close to the vibrator, shown in the cylindrical can, and the power transformer to which they connect is underneath the chassis at the same place. The plate meter and speech amplifier components are at the right-hand side of the cabinet.

In the under-chassis view, Fig. 1646, the volume control at the right has its shaft extended for the width of the chassis, to put the volume control connections near the control grid of the 6C5 speech input tube. The under side of the unit contains the assortment of filter and by-pass condensers required in the circuit shown in Fig. 1644.

To adjust the transmitter, close the filament switch, S_1 , and allow the tubes to come up to temperature. Then close the plate switch and check the oscillator and modulator plate currents, which should be in the vicinity of 60 ma. and 40 ma., respectively, at a plate voltage of 300 to 350. With S_4 connected to read oscillator plate current, tighten the antenna coupling. This should cause an increase in plate current. The antenna length (see Chapters Seventeen

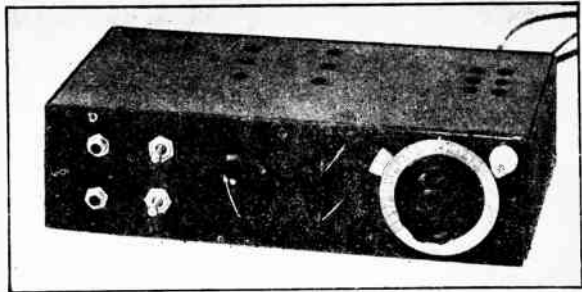



Fig. 1647 — Front view of the mobile transceiver. This unit fits into the glove compartment of the car. The toggle switches remotely control the filament and power supply circuits, both for this unit and for the main transmitter (Fig. 1643) in the rear compartment.

and Eighteen for information on mobile antennas) should now be adjusted to cause the maximum increase in oscillator plate current, indicating that the antenna is taking maximum power. For close adjustment it is advisable to move away from the antenna after each length adjustment to avoid the effects of body capacity. After the antenna has been resonated the antenna coupling should be varied to make the oscillator take the desired value of plate current. The modulation quality can be checked by having another person listen to the signal on the transceiver (S_3 being closed).

In the transmitter shown, plate power is furnished by two 175-volt motor-generators with the outputs connected in series to give 350 volts. Alternatively, a machine delivering 300-350 volts could be used, or a vibrator supply capable of furnishing 300 volts at 100 milliamperes or more.

The transceiver circuit, Fig. 1648, uses an 6Y615 as the oscillator-superregenerative tube. The speech equipment consists of a 6C5,

Fig. 1648 — Circuit diagram of the 144-Mc. mobile transceiver.

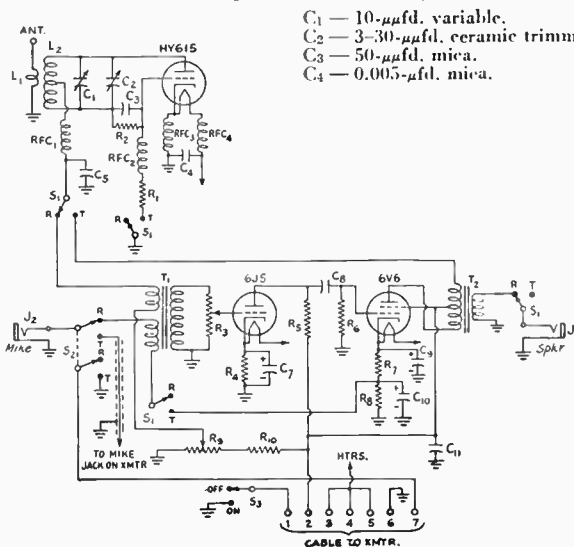

- C_1 — 10- μ fd. variable.
- C_2 — 3-30- μ fd. ceramic trimmer.
- C_3 — 50- μ fd. mica.
- C_4 — 0.005- μ fd. mica.

- C_5 — 0.003- μ fd. paper.
- C_7 — 25- μ fd., 25-volt electrolytic.
- C_8 — 0.01- μ fd. paper.
- C_9, C_{10} — 50- μ fd., 50-volt electrolytic.
- C_{11} — 8- μ fd., 450-volt electrolytic.
- L_1 — 2 turns No. 18, $\frac{1}{2}$ inch inside diameter, $\frac{3}{8}$ inch long.
- L_2 — 3 turns same as L_1 .
- J_1, J_2 — Open-circuit jack.
- R_1 — 20,000 ohms, 1 watt.
- R_2 — 10 megohms, $\frac{1}{2}$ watt.
- R_3 — 1-megohm potentiometer.
- R_4 — 2000 ohms, $\frac{1}{2}$ watt.
- R_5, R_{10} — 0.1 megohm, 1 watt.
- R_6 — 0.5 megohm.
- R_7 — 250 ohms, 1 watt.
- R_8 — 500 ohms, 1 watt.
- R_9 — 50,000-ohm potentiometer.
- RFC $_1, RFC_2$ — Ohmite Z-1.
- RFC $_3, RFC_4$ — 20 turns No. 18, $\frac{3}{16}$ inch inside diameter, $1\frac{1}{8}$ inches long.
- S_1 — 4-pole 2-position switch.
- S_2 — D.p.d.t. toggle.
- S_3 — S.p.s.t. toggle.
- T_1 — Transceiver transformer.
- T_2 — Speaker output transformer.

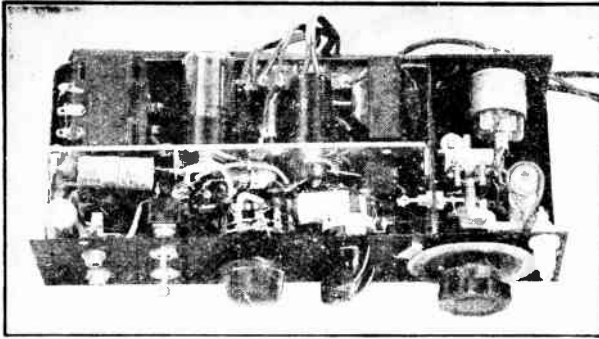


Fig. 1649 — Top view of the mobile transceiver showing the horizontal tube mountings for short leads. The oscillator-detector and associated r.f. components are in the shielded compartment to the right. The audio equipment is arranged along the rear.

working from a single-button microphone, driving a 6V6 as a modulator for the HY615. The 6C5 and 6V6 are used as an audio amplifier for a loud speaker when the unit is used for reception. The transceiver switch, S_1 , is a four-section, two-position rotary switch. One section transfers the plate of the HY615 from the input winding on the transceiver transformer, T_1 , to the plate of the 6V6 to switch from receive to transmit. The second section lowers the HY615 grid leak resistance to a suitable value for transmitting by connecting the lower end of R_1 to ground. The third section disconnects the microphone from the microphone input winding on T_1 for receiving, and connects it to the winding for transmitting, while the fourth section makes the appropriate connection between the speaker and the voice-coil winding on T_2 ; the audio output transformer. When the main transmitter is being used S_1 is left in the receive position all the time.

The send-receive switch used for the main transmitter is S_2 , a double-pole double-throw toggle switch. One section of S_2 disconnects the microphone jack from a shielded line which runs to the main transmitter, thereby opening the microphone circuit during reception. The other section of S_2 turns on the main transmitter through relay R_{y2} , Fig. 1644, in the sending position and disconnects the relay in the receiving position. S_3 , a foggle switch, operates a relay in the main transmitter (R_{y1} , Fig. 1644) which controls the transmitter filament circuits.

The front view of the transceiver, Fig. 1647, shows a cabinet with dimensions of approximately $9 \times 6 \times 4$ inches. This allows ample space on the panel for the gain and regeneration controls which are shown with pointer knobs, and for the adjacent send-receive switch with its circular knob. The two toggle switches at the left control the filament and main transmitter plate supplies through two relays, R_{y1} and R_{y2} in Fig. 1644. A speaker is plugged into one of the jacks at the left and the single-button microphone goes into the other. Cables to

the power supply from the panel of the main transmitter are shown in the rear. Several half-inch holes drilled in the top of the case provide ventilation for the tubes inside. Tubes are mounted horizontally. This arrangement places the terminals of the sockets right at the connections to component parts which are mounted within the front section of the unit. Exceptions are the microphone and output-stage transformers, T_1 and T_2 . They are mounted at the opposite ends of the top section and as far from one another as space will permit. All of the r.f. equipment is confined to the compartment at the right. Fairly close coupling between the antenna and tank coils is provided in the transceiver.

To test the operation of the transceiver as a receiver, first throw on the filament switch, S_2 . Relay R_{y1} then closes and simultaneously the vibrator starts, through the action of relay R_{y2} . The familiar background hiss should then be heard and some stations might come in as the main dial is rotated. Sometimes, just manipulation of the regeneration control will cause the receiver to "come alive," if it seems dead at the start. As a simple test of operation, touch the antenna. The receiver noise should diminish instantly as an indication that the circuit is operating properly. In order to set the tuning so that the bandspread condenser can cover the band properly, the adjustment screw on C_1 may be reached from the top of the cabinet just to the left of the HY615.

Once the receiver operation has been checked, it is practically certain that the tube will function as a transmitting oscillator, barring any errors in the transceiver switching circuit.

When a mobile transmitter and its power supply are installed in the car trunk — usually the place where the most room is available,

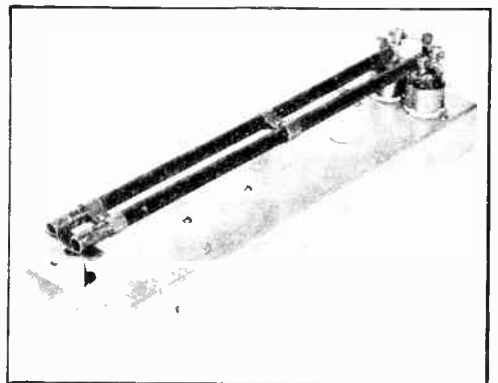


Fig. 1650 — A parallel-line push-pull HY615 oscillator which operates on either 144 or 220 Mc. by changing the positions of the primary and secondary shorting bars.

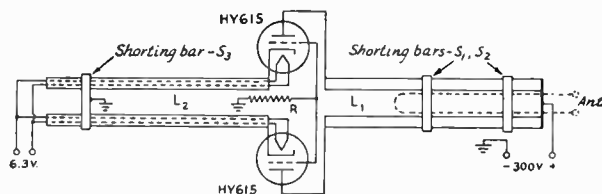


Fig. 1651 — Circuit diagram of the push-pull 144-220-Mc. oscillator. R — 5000 ohms, 10-watt. L₁ — Plate line: $\frac{1}{2}$ -inch o.d. copper tubing, length 12 inches, spaced diameter of tubing. L₂ — Cathode line: $\frac{1}{4}$ -inch diameter copper tubing, length 10 inches, spaced $\frac{1}{2}$ inch.

and most convenient to the best antenna location — it is advisable to use a separate storage battery to operate the equipment rather than to attempt to run a long lead from the regular car battery. Since the current drain is rather high, the voltage drop in such a lead will be excessive. However, the separate battery readily may be connected to the car battery so that it will “float” across the latter, thus avoiding the necessity for periodic recharging.

Parallel-Line Push-Pull 144- and 220-Mc. Oscillators

Figs. 1650-1652 show a low-powered push-pull oscillator using a linear tank circuit of the “tuned-plate tuned-cathode” variety, which gives reasonably good stability and efficiency on 144 and 220 Mc. Using HY615 tubes, the unit is capable of about five watts output at 144 Mc. and somewhat less at 220 Mc.

The transmitter is built on a $2\frac{1}{2} \times 4\frac{1}{2} \times 15$ inch chassis bent from sheet aluminum. The sockets for the tubes are oriented so that the plate caps face the left-hand end of the chassis. The plate lines are held together rigidly by a sturdy copper strap at the shorted end and by a polystyrene bar at a high-potential point near the tubes.

The cathode lines are mounted underneath the chassis. At one end they are connected directly to the cathode terminals on the tube sockets, the other ends being strapped together and supported by a small ceramic pillar. The heater leads, of rubber-covered hook-up wire, go through these lines as shown in Fig. 1651.

The cathode line is equipped with a sliding clamp-type shorting bar, while two similar bars are installed on the plate line. These are made of brass strip, bent around the parallel rods. Machine screws and nuts hold the clamp firmly in place.

In preliminary adjustment for 144 Mc. operation, the cathode bar is set near the end of the line most distant from the tube sockets. Both plate bars are first set at the shorted end of the line. To provide protection for the tubes, a 1000- or 2000-ohm protective resistor should

be connected in series with the plate supply lead. A 0-100 or equivalent milliammeter also should be placed in series with the high voltage lead. With heater power applied, check for oscillation as indicated by a dip in plate current when one of the conductors is touched with an insulated screwdriver or a neon bulb. If no oscillation is apparent, the effective length of the cathode line should be extended by moving the sliding bar toward the tube end.

The frequency of the oscillator may be adjusted to resonance, using Lecher wires or equivalent measuring means, by moving the primary sliding bar (the one nearest the tubes) on the plate line toward the tubes until the desired operating frequency is reached.

For 220 Mc. operation the primary bar is advanced about six inches toward the tubes. The secondary bar is also moved, until oscillations occur. Some shortening of the effective length of the cathode line may be necessary. If the resulting frequency is not the desired operating frequency, adjust the two plate shorting bars simultaneously until the correct points for maximum output at the desired frequency have been determined.

The function of the primary shorting bar is to establish a length of line which, with the self-capacity of the tubes, will be correct for the desired frequency. The secondary shorting bar establishes an isolating quarter-wave section equivalent to an r.f. choke. The position of the secondary bar has some effect upon the frequency of oscillation, although the spacing between the two bars need not bear an exact quarter-wave relationship.

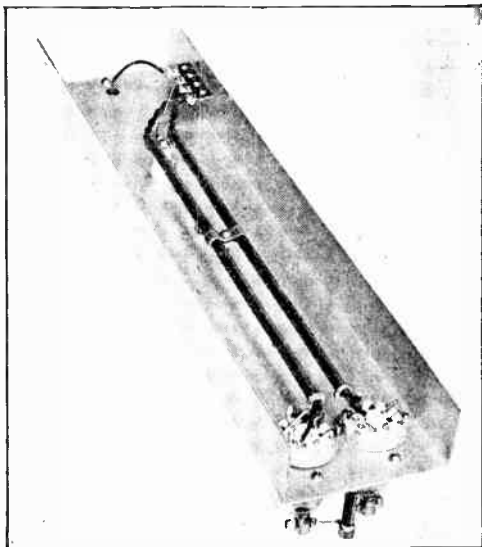


Fig. 1652 — Underneath view of the 144/220-Mc. linear oscillator showing placement of the cathode lines.

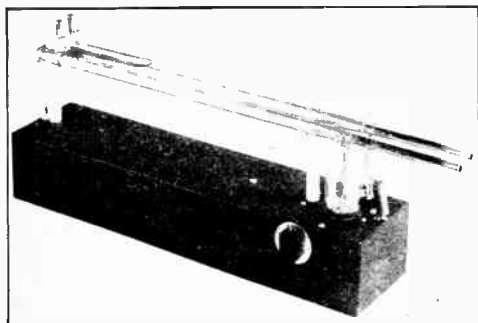


Fig. 1653 — A 144- and 220-Mc. oscillator using linear tank circuits in the plate and cathode circuits. The cathode line is tuned by a condenser. The setting of the cathode condenser is critical both in securing oscillation and maximum output, but has almost no effect on the generated frequency, the latter being determined by the length of the plate line. The output coupling is adjusted by bending the link toward or away from the line.

Higher-Power Linear Oscillators

The general method of construction illustrated in the push-pull 6Y615 oscillator may be followed in building higher-power oscillators for the 144- and 220-Mc. bands. A representative oscillator is shown in Figs. 1653, 1654, and 1655. It uses type 24G tubes, but may readily be adapted to any of the several types of tubes having similar terminal arrangements; that is, with the plate lead out of the top of the bulb and the grid lead coming from the side.

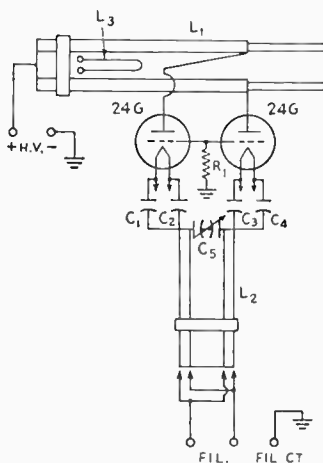


Fig. 1654 — Circuit diagram of the 24G linear oscillator.

- C_1, C_2, C_3, C_4 — 500- μ fd. midget mica.
 C_5 — 25 μ fd. per section (Cardwell ER-25-AD).
 L_1 — Plate line; $\frac{3}{8}$ -inch o.d. copper tubing 15 $\frac{1}{4}$ inches long, with adjustable extensions of $\frac{1}{4}$ -inch o.d. tubing 6 $\frac{1}{4}$ inches long. Approximate total line length for 144 Mc., 19 $\frac{3}{4}$ inches; for 220 Mc., 10 $\frac{3}{4}$ inches (with extensions removed).
 L_2 — Cathode line; $\frac{3}{8}$ -inch o.d. copper tubing 14 $\frac{3}{4}$ inches long. Approximate length from filament end to shorting bar with C_5 at half capacity: for 144 Mc., 7 $\frac{3}{4}$ inches; for 220 Mc., 5 inches.
 R_1 — 2000 ohms, 10 watts (see text).

In this oscillator, which uses tubes having directly-heated filaments, the filaments are connected to the cathode line through by-pass condensers; there is no direct connection between the filament supply leads and the line. Filament-supply leads from each tube run through the pipe nearest that filament. The filament or cathode line is provided with a shorting bar for coarse adjustment to the band in use, but actual tuning of the line is done with C_5 . This is convenient, since the adjustment of the cathode line is critical for best operation.

The plate line, L_1 in Fig. 1654, is equipped with sliding extensions for adjustment to the 144-Mc. band, since a standard 17-inch chassis is too short to accommodate the whole line even with the shorting bar at the end. With

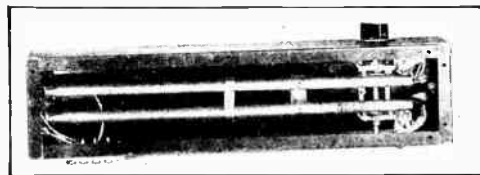


Fig. 1655 — Underneath the chassis of the 24G linear oscillator. The shorting bars are made from two pieces of 1/16-inch thick brass strip $\frac{1}{2}$ inch wide, formed to fit the pipes and held together by a machine screw, the lower strip being tapped.

the extension pipes all the way in (protruding length 4 $\frac{1}{2}$ inches) the shorting bar may be set so that the oscillator is at 148 Mc. Other frequencies in the band then can be reached by pulling out the extensions until the desired frequency is reached.

Connections between the tube elements and the lines should be kept as short as possible. However, flexible leads should be used to the tube plates to avoid danger of breaking the seals during adjustment of line length.

With the 24G tubes the plate-supply should furnish about 900 to 1000 volts at 100 milliamperes or so. An input of about 100 watts can be used on 144 Mc. without exceeding the plate dissipation ratings of the tubes. If other tubes are used the input should be held to the point at which the plate dissipation rating is not exceeded. In general, tubes of this type require relatively high plate voltage and low plate current to work at optimum efficiency. The value of plate current can be regulated to a considerable extent by choice of grid-leak resistance, higher values giving lower plate current.

A Simple Transmitter for 220 Mc.

At frequencies higher than about 150 Mc., considerable difficulty is found in getting good performance with tubes other than those designed expressly for v.h.f. operation. However, there are several inexpensive v.h.f. tubes available to the amateur that will perform well on 220 Mc. The transmitter in Figs. 1656-1658

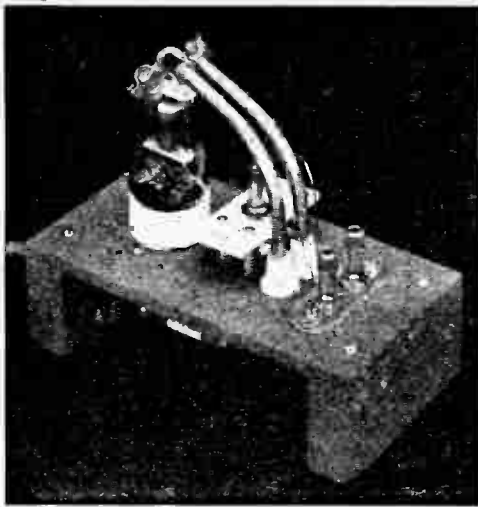


Fig. 1656 — A 220-Mc. transmitter using an HY75 tube. A rectangular clearance hole in the chassis allows the tuning condenser to be mounted for shortest leads. The condenser is adjusted by an insulated screw driver.

shows how one of these types, the HY75, may be put to work in a basically very simple oscillator circuit.

The transmitter is built on a $3\frac{1}{2} \times 6\frac{1}{2}$ -inch piece of $\frac{1}{4}$ -inch Presdwood supported by two strips of 1×2 -inch wood. A rectangular hole is cut in the center of the Presdwood to accommodate the tuning condenser, which is supported by two metal pillars at one end. The tuned circuit consists of two lengths of $\frac{1}{4}$ -inch copper tubing, $3\frac{1}{2}$ inches long, which are supported at one end by two feed-through insulators. The ends of the screws in the feed-through insulators are swaged into the ends of the tubing, and the tuning condenser is connected to two lugs right at this point. Connections from the tubing to the grid and plate terminals on the tube are made by $\frac{1}{2}$ -inch lengths of flexible shield braid. The filament chokes, the plate r.f. choke, and the grid leak are mounted under the chassis.

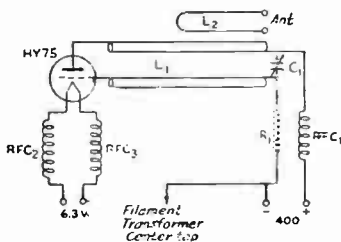


Fig. 1657 — Wiring diagram of the 220-Mc. oscillator. C_1 — 100- μ fd. midjet variable (National CM-130). R_1 — 5000 ohms, 10-watt wire-wound. L_1 — $\frac{1}{4}$ -inch copper tubing, $3\frac{1}{2}$ inches long, spaced $\frac{1}{2}$ -inch on centers. L_2 — 2-inch loop of No. 16 bare wire. RFC_1 — V.h.f. r.f. choke (Ohmite Z-1 or Z-0). RFC_2 , RFC_3 — 10 turns No. 18 e., close-wound on $\frac{1}{2}$ -inch diameter, self-supporting.

The antenna-coupling circuit consists of a loop of wire parallel to the copper tubing and terminating in the antenna binding posts. Coupling is varied by simply moving the hair-pin loop nearer to or farther away from the copper-tubing line.

The transmitter should first be tested with a dummy load. A 10-watt lamp bulb is excellent for the purpose. The load is connected to the antenna posts and the power supply turned on. If everything is connected properly the lamp will light, its brilliancy depending upon the tightness of coupling and the setting of C_1 . It will be found that the output is greater towards the maximum-capacity end of the range of C_1 . The frequency coverage of the transmitter should be checked, using Lecher wires or a frequency meter, to make sure that it will cover the desired range. The coverage can be adjusted slightly by changing the separation of the copper-tube conductors; if this does not effect enough change, the lines will have to be made either shorter or longer, as required. The tuning condenser is adjusted by means of an insulated screw driver.

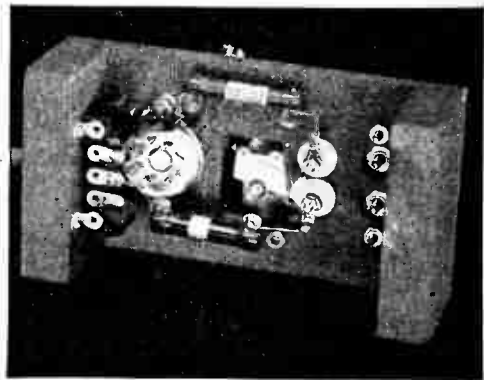


Fig. 1658 — The r.f. chokes and the grid leak are mounted under the chassis of the 220-Mc. transmitter. The power-supply cable is brought through a hole in the side piece to a tie strip mounted on the left-hand side.

The transmitter requires a plate power supply delivering 60 ma. at 400 volts, and the modulator unit should be capable of furnishing 12 watts of audio power. The 6A6 modulator described in Chapter Fourteen will be quite adequate for the purpose.

Because of its small size, a transmitter of this type can be built as a unit into a rotatable antenna for the 220-Mc. band, if desired. It is preferable not to use a long transmission line at this frequency, because of the possibility of radiation from the line.

Ⓢ A Disc-Seal Tube Oscillator for 144, 220 and 420 Mc.

At frequencies above 300 Mc. or so tubes of conventional construction will not operate, for the reasons outlined at the beginning of this chapter. The disc-seal or "lighthouse" tubes

will function nicely, however, in ordinary linear circuits at frequencies up to several hundred megacycles. No special types of circuit construction, (such as cavity resonators) are required, therefore, when disc-seal tubes are used in the 420-Mc. band.

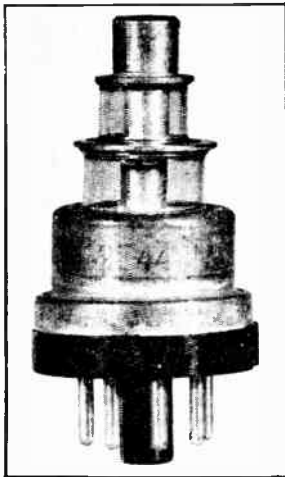


Fig. 1659 — One of the family of "lighthouse" tubes developed during the war for v.h.f. use. This particular tube (2C14) is a triode-rated at 20 watt-maximum input. The plate connection is at the top, the grid connection is the metal disc in the center, the metal part of the base is the r.f. cathode connection, and the heater and d.c. cathode connections are through the octal base.

A photograph of the 2C14, a low-power lighthouse triode, is given in Fig. 1659. The heater and d.c. cathode leads are brought out to pins in a conventional octal base. The wide metal band immediately above the base is the r.f. cathode connection, which is coupled by a built-in 100- $\mu\mu\text{f}$. condenser to the d.c. cathode connection (brought out through the Nos. 3, 5 and 8 pins). The cathode pillar extends up to within a few thousandths of an inch of the grid disc (the central metal disc) and has its emitting surface only on the flat end of this pillar. The heater is mounted inside the pillar directly under the cathode surface. The grid disc has a hole punched in its center (slightly larger in area than the cathode surface) across which is stretched the fine mesh of the grid. The plate pillar extends down to within a few thousandths of an inch of the grid, and connection to the plate is made at the top.

Details of construction of a transmitter

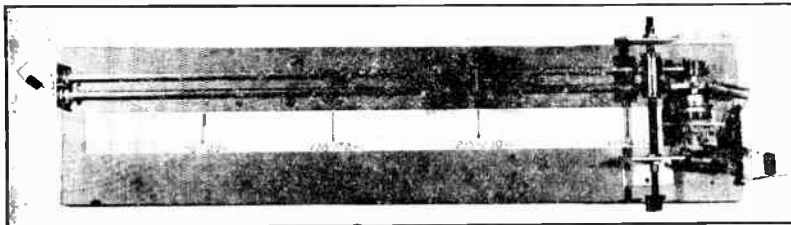


Fig. 1660 — A three-band oscillator (144, 220 and 420 Mc.) using the 2C14. The shorting bar on the parallel lines is moved to the proper point and locked, and tuning over the band is accomplished by the home-made variable condenser mounted at the ends of the lines near the tube.

using the 2C44, for operation in the 144-, 220-, and 420-Mc. bands, are given in Figs. 1660 to 1663, inclusive. Using parallel lines, it is only necessary to change the position of the shorting bar to obtain output on any of the three bands. The shorting bar is moved to a previously-calibrated point on the lines and locked, and then any frequency within the amateur band is obtained by proper setting of a tuning condenser connected across the lines at the point where they connect to the tube. The antenna coupling loop is connected to the shorting bar so that the two are moved simultaneously.

The circuit is shown in Fig. 1661. It will be recognized as the conventional circuit used in most 144-Mc. gear. The only critical component in the unit is RFC_2 , the grid choke. There is an optimum value of choke for any one frequency, with which maximum output will be obtained at that frequency, but the value shown is a good compromise for the three-band range of this transmitter. The cathode is above ground by RFC_1 and RFC_4 , but these inductors are not critical.

The transmitter is built on a 6- by 28- by 1-inch board. The "cold" ends of the $\frac{1}{4}$ -inch rods used in the line are supported by two panel bushings mounted in an aluminum bracket which is fastened to the baseboard. These two panel bushings are of the locking type and make it a simple matter to position the rods properly. The plate rod is terminated at the plate and in a hole in the plate cap. The

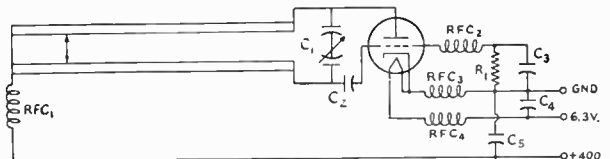


Fig. 1661 — Circuit diagram of the three-band oscillator.

- C_1 — See text and Fig. 2.
- C_2 — 10 $\mu\mu\text{f}$. ceramic.
- C_3, C_4, C_5 — 100 $\mu\mu\text{f}$. mica.
- R_1 — 3000 ohms, 1-watt composition.
- RFC_1 — 13 turns No. 18 enam., $\frac{1}{4}$ -inch diam., close-wound.
- RFC_2 — 25 turns No. 18 enam., $\frac{3}{8}$ -inch diam., spaced wire diam.
- RFC_3, RFC_4 — R.F. choke (Ohmite Z-1).

plate cap consists of a $\frac{1}{2}$ -inch length of $\frac{3}{4}$ -inch diameter brass rod with a $\frac{3}{8}$ -inch hole drilled in the center and a $\frac{1}{4}$ -inch hole drilled in the

side. Holes are drilled at right angles to the large holes and tapped for 6-32 set screws. The $\frac{3}{8}$ -inch hole fits over the plate cap of the tube, and the $\frac{1}{4}$ -inch hole slides over the end of the plate rod. The

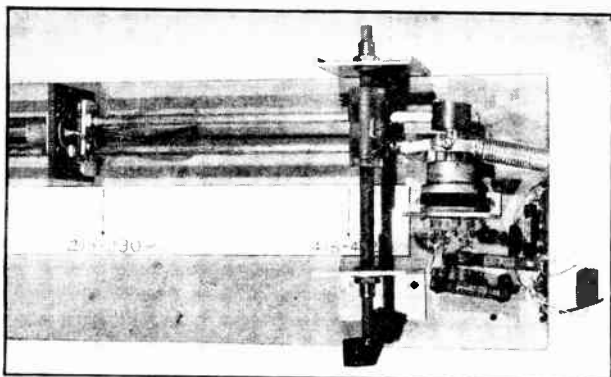


Fig. 1662 — A close-up view of the tuning condenser of the three-band oscillator also shows the details of the socket mounting and tube connections (WIDBMM).

thus counteracting the effect of the additional capacity and limiting the tuning range to only a small frequency variation. Two metal brackets with panel bushings are used to support the rotor shaft. It is a good idea to mount the panel bushings in slots rather than the usual clearance holes, so that the shaft can be moved toward the stator plates until the desired capacity range is obtained.

The tube socket is mounted on an aluminum bracket which is screwed to the baseboard. No connection is made to the r.f. cathode connection because the oscillator was found to work better over the entire range that way.

grid half of the parallel line is approximately one inch shorter than the plate rod, to provide room for the grid condenser, C_2 . The grid end of the line is supported by a small polystyrene post, and the grid socket is made by forming a narrow band of copper around the grid disc of the lighthouse tube and tightening it with a 2-56 machine screw and nut.

The shorting bar for the parallel lines is made of two locking-type panel bushings set in a copper strap. These bushings are tightened just enough to insure good contact and still allow the bar to slide without too much effort. It is imperative, therefore, that the two rods be smooth and straight, although they can be either brass rod or brass tubing. The coaxial-cable connector for the antenna feed line and the antenna loop are mounted to a piece of $\frac{1}{16}$ inch bakelite bolted to the shorting bar. The antenna loop rides under the lines so that it will not hit the tuning condenser when the shorting bar is near the condenser. The size of the loop may vary with different antennas but, in general, it should be about 2 inches long and spaced the same as the lines. The coupling can be increased by bending the loop closer to the lines.

The tuning condenser is of the split-stator type with the rotor floating. The stator plates consist of two strips of copper, $\frac{3}{16}$ inch wide by 1 inch long, formed in two arcs and soldered to the tuning rods (see Fig. 1663). The rotor uses a piece of $\frac{3}{4}$ -inch diameter polystyrene rod through which is drilled a $\frac{1}{4}$ -inch diameter hole for a bakelite or polystyrene shaft. If desired, the solid polystyrene can be replaced by a $\frac{3}{4}$ -inch diameter coil form by cementing a disc of polystyrene to the open end of the coil form.

The rotor plate, a U-shaped strip of copper one inch square, is formed and then cemented to the polystyrene form. A U-shaped piece is necessary because it was found that at 450 Mc. a cylindrical rotor acted as a capacitor plate as it was first brought near the stator plates, but as rotation continued the rotor began to act as a shorted turn in the field of the lines,

Forced ventilation must be used on the tube if anything like the rated maximum input of 20 watts is to be used. As much of the plate heat as possible must be conducted away by the plate rod, and for this reason the connection between plate and rod must be as good as possible from a heat as well as an electrical standpoint. The forced ventilation of the plate can best be obtained by the use of a small electric fan whose blast is directed at the plate connection whenever the plate power is applied. A small blower tube can be rigged up from stiff cardboard and attached to the fan.

Oscillation can be determined by using a small neon bulb or a flashlight lamp and loop of wire held close to the lines. Grid current is also an excellent oscillation indicator. If no oscillation is obtained, it probably means an incorrect grid choke, and its construction should be checked or modified slightly. To get the best efficiency, particularly on any one band, may require some slight revision in the inductance of the grid choke or in the value of the r.f. by-pass capacitors, the effect of such changes being checked by watching the output as indicated by the lamp load and the input as indicated by a plate milliammeter. Tuning up should be done at reduced plate voltage, say around 250 or 300, at which value the loaded plate current should run around 15 to 20 ma., after which the maximum input of 40 ma. at 500 volts can be applied if considered necessary.

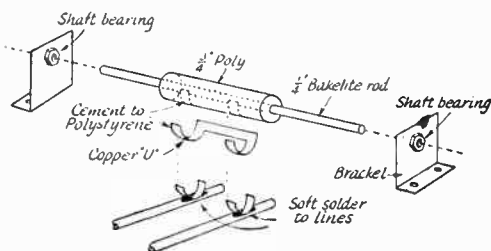


Fig. 1663 — Constructional and assembly details of the tuning capacitor for the 144/220/420-Mc. oscillator.

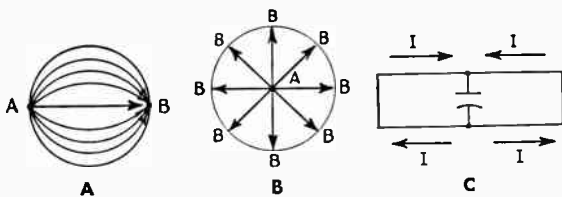


Fig. 1664 — The inductance in the circuit depends upon the path taken by the radio-frequency current, as explained in the text.

A good set of Lecher wires or an accurately-calibrated absorption wavemeter is essential for finding the different amateur bands. Although a wire line is probably the most convenient for the 144- and 220-Mc. bands, a more rigid line for the 420-Mc. band can be made by using 1/4-inch rod or tubing, supporting it in the same manner that the tuned circuit is supported for the oscillator. After the oscillator has been calibrated, a cardboard scale can be added to the baseboard and the positions marked for the three amateur bands. The approximate settings of the shorting bar follow:

Distance from Center of Plate of 3C44 to Shorting Bar	Frequency Range
14 inches	138-152 Mc.
8 1/4	215-230 "
2 1/2	418-432 "

Considerable care must be exercised in moving the shorting bar (and in removing the tube from its socket) because of the possibility of breaking the tube seals.

¶ A Tuned-Circuit Oscillator for 144, 200 and 420 Mc.

Oscillators in the 200- to 500-Mc. range usually are designed to use tank circuits of either the parallel-line or coaxial type, these linear circuits being employed because of their high Qs. In addition, there is the fact that at these frequencies the dimensions of ordinary

components are such that distributed inductance and capacity become an important factor in circuit operation; for example, a variable condenser of conventional construction is not a pure capacity but possesses appreciable inductance as well.

However, despite the high Q of resonant lines as such, the circuit Q at u.h.f. usually is not very great because much of the inductance and capacity in the circuits is contributed by the tube elements and leads. These elements are not particularly high-Q in themselves, and in combination with the loading effect of the tube they reduce the effective circuit Q to a low value compared with that obtainable with an unloaded line. Actually, the stability of an oscillator becomes more a function of rigid mechanical construction than the electrical properties of the circuit.

By proper design it is possible to use coil-and-condenser tuned circuits at these frequencies, although the physical construction of the circuits may differ considerably from practice at lower frequencies. The advantages are compact construction, readily-adjustable tuning without elaborate mechanical devices, and a high order of frequency stability. The guiding principle in design is the reduction of inductance in all parts of the circuit except where it is actually wanted.

Inductance can be reduced by making the r.f. current flow in paths such that the magnetic field set up by the current is as weak as possible. The general principle is illustrated by the discs shown in Figs. 1664-A and -B. If the current enters the disc at A in Fig. 1664-A and leaves at B, it spreads over the disc about as shown by the arrows and each current "filament" contributes to the total magnetic field. However, if the current enters at the center of the disc and leaves at the circumference, as in Fig. 1664-B, the field from current flowing outward in one direction is partially cancelled by the field from current flowing outward in the opposite direction. The total magnetic field, and therefore the inductance, is consequently less than in Fig. 1664-A. This principle of reducing inductance by cancellation of fields also can be applied as shown in Fig. 1664-C, where a half-wave line, shorted at both ends, is

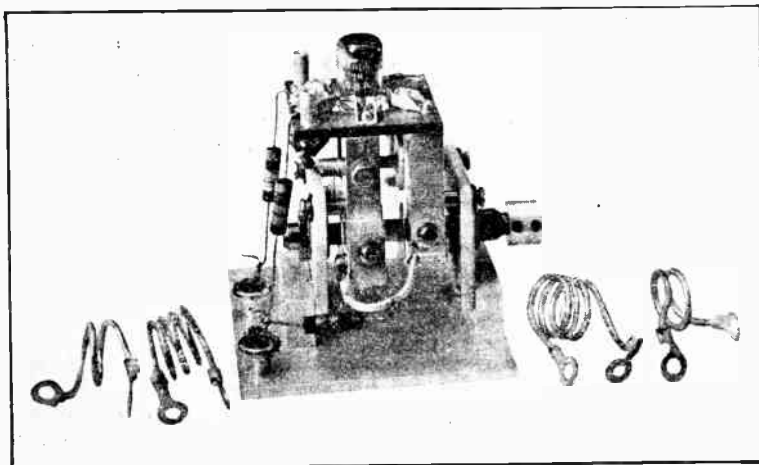


Fig. 1665 — Using an LC tank circuit, this oscillator generates about 1 1/2 watts of r.f. in the frequency range from 140 to 450 megacycles. Exceptionally solid construction results in excellent frequency stability. The tube is a 6F4 acorn triode.

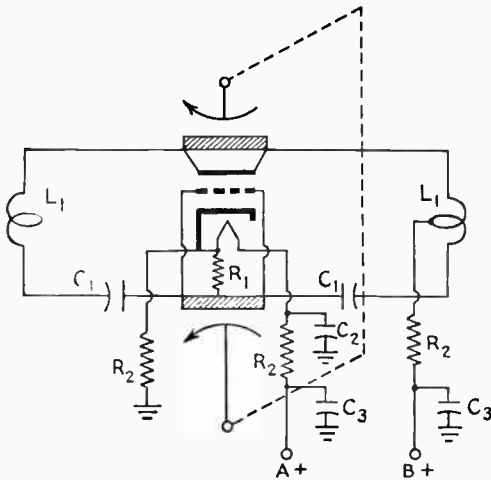


Fig. 1666 — Circuit diagram of the 140-450 Mc. oscillator. The oscillator tube is a 6F4, drawn here in unconventional fashion to show how the tube elements are tied in with circuit construction.

- C_1 — 30- μ fd. mica, constructed as described in the text.
 C_2 — 100- μ fd. midget mica.
 C_3 — 500 μ fd. (Eric Ceramicon)
 R_1 — 0.22 megohms, $\frac{1}{2}$ -watt.
 R_2 — 0.5 ohm, $\frac{1}{2}$ -watt.
 L_1 — 144 Mc.: 3 $\frac{1}{2}$ turns No. 12 silvered wire, $\frac{1}{2}$ inch inside diameter, $\frac{1}{2}$ inches long.
 220 Mc.: 1 $\frac{1}{2}$ turns No. 12 silvered wire, $\frac{1}{2}$ inch inside diameter, $\frac{1}{4}$ inches long.
 420 Mc.: $\frac{1}{2}$ turn No. 12 silvered wire, $\frac{1}{2}$ inch inside diameter.

Dimensions of the tuning condenser are given in Fig. 1665.

tuned by a condenser connected to the center (electrically equivalent to two shorted quarter-wave lines in parallel tuned by a condenser at their open ends). Currents flowing into or out of the condenser from the two sections of the line, I_1 and I_2 , enter or leave the condenser from opposite directions along the line, consequently there is partial cancellation of the fields in the region of the center of the line and the inductance is smaller than would be the case with either line alone.

In the oscillator shown in Figs. 1665 to 1668, inclusive, these principles are employed to obtain an extended high-frequency range with a coil-and-condenser tank circuit. The circuit diagram is shown in Fig. 1666, and the photographs show the details of construction. Basically, the assembly consists of two very heavy brass plates which do double duty, acting as tube mounting supports and as the stator plates of the tuning condenser. The tube is a 6F4, which in itself has symmetrically arranged grid and plate leads and thus carries out still further the principle of inductance cancellation. In addition, the method of connecting the tube to the line is such that the lead wires to the tube are shunted by low-inductance brass plates, causing lead length to have very little loading effect on the line.

On each end of the stator plates is mounted a small coil which represents most of the in-

ductance in the circuit. By making the coils self-supporting and of heavy gauge silver-plated wire, losses are kept to a minimum. Three amateur bands are covered by the three sets of coils shown, the one-turn set tuning from 417 to 456 Mc., the 2-turn set from 215.6 to 230.8 Mc., and the 4-turn set from 141.2 to 151.9 Mc. The coils are mounted to the stator blocks by means of 6-32 screws and soldering lugs so that they may be readily removed. On either side of the grid stator plate is a small brass block spaced off from the main assembly by a mica sheet. These act as low-inductance grid condensers.

In order to permit band setting for proper bandspread, two small disc-type trimmers are mounted between the stator blocks directly underneath the tube. When these are adjusted it is advisable to keep the airgaps approximately equal and thus avoid unbalancing the circuit.

The frequency stability of the oscillator is excellent because of its rigid construction. A sharp blow on the tube causes the frequency to shift only several hundred cycles at 400 megacycles. The warm-up period is very short and is mostly due to the effect of the heater in warming up the other tube elements. Once the tube reaches operating temperature, frequency drift is negligible.

With a plate voltage of 250 volts the 6F4 will deliver approximately 1.5 watts, which is much more power than can be obtained from the usual transceiver oscillator, and is ample for low power work at these frequencies. The oscillator also may be used as the high-frequency oscillator in a superheterodyne receiver. For maximum stability the 200,000-ohm grid leak should be used. By increasing the value of the grid leak the unit may be

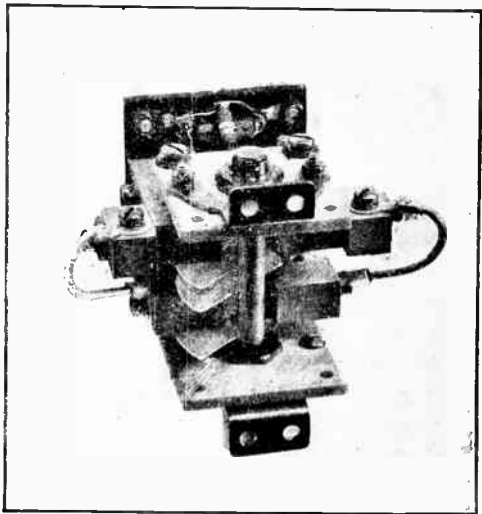


Fig. 1667 — A view from underneath the 6F4 oscillator, with the mounting plate taken off. This shows the construction of the tuning condenser rotor and the two grid condensers.

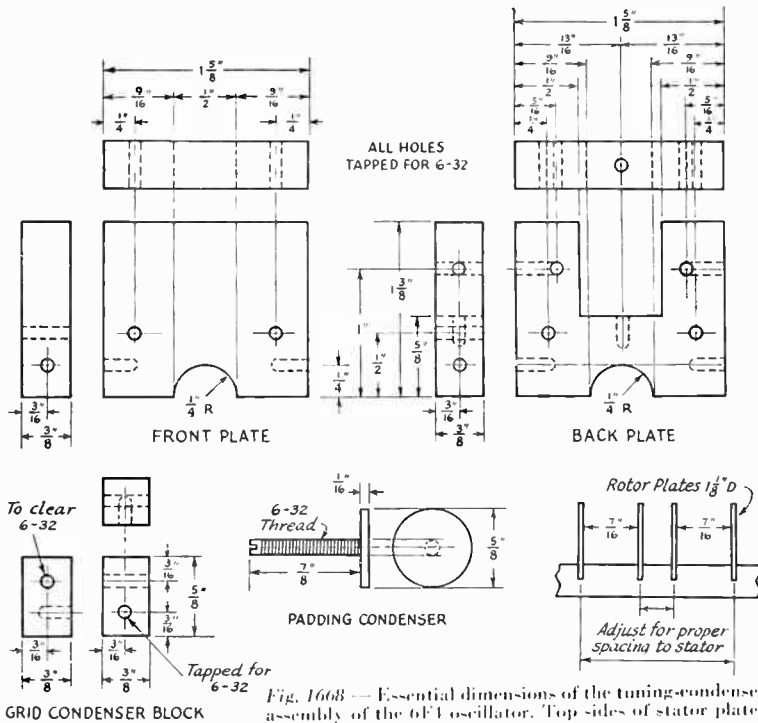


Fig. 166B — Essential dimensions of the tuning-condenser assembly of the 6F4 oscillator. Top sides of stator plates should be tapped to fit socket contacts.

used as a superregenerative receiver. Higher plate voltages, up to 300 volts, may be applied provided the rated plate dissipation of 2 watts and the maximum plate current of 20 ma. for the 6F4 are not exceeded. An important point

to remember is that the tuning condenser should not be grounded. A ceramic coupling or shaft is to be preferred to one made of bakelite, since bakelite is not a good insulator at the higher frequencies.

Antenna Construction

THE USE of good materials in the antenna system is important since the antenna is exposed to wind and weather. To keep electrical losses low, the wires in the antenna and feeder system must have good conductivity and the insulators must have low dielectric loss and surface leakage, particularly when wet.

For short antennas, No. 14 gauge hard-drawn enameled copper wire is a satisfactory conductor. For long antennas and directive arrays, No. 14 or No. 12 enameled copper-clad steel wire should be used. It is best to make feeders of ordinary soft-drawn No. 14 or No. 12 enameled copper wire, since hard-drawn or copper-clad steel wire is difficult to handle unless it is under considerable tension at all times. The wires should be all in one piece; where a joint cannot be avoided, it should be carefully soldered.

In building a resonant two-wire feeder, the spacer insulation should be of as good quality as in the antenna insulators proper. For this reason, good ceramic spacers are advisable. Wooden dowels boiled in paraffin may be used with untuned lines, but their use is not recommended for tuned lines. The wooden dowels can be attached to the feeder wires by drilling small holes and binding them to the feeders with wire.

The ends of tuned feeders or the ends of the antenna are points of maximum voltage. It is at these points that the insulation is most important, and Pyrex glass, Isolantite or steatite insulators with long leakage paths are recommended for the antenna. Glazed porcelain also is satisfactory. Insulators should be cleaned once or twice a year, especially if they are subjected to much smoke and soot.

In most cases poles or masts are desirable to lift the antenna clear of surrounding buildings, although in some locations the antenna will be sufficiently in the clear when strung from one chimney to another or from a chimney to a tree. Small trees usually are not satisfactory as points of suspension for the antenna because of their movement in windy weather. If the antenna is strung from a point near the center of the trunk of a large tree, this difficulty is not so serious. Where the antenna wire must be strung from one of the smaller branches, it is best to tie a pulley firmly to the branch and run a rope through the pulley to the antenna, with the other end of the rope attached to a counterweight near the ground. The counterweight will keep the tension on the antenna wire reasonably constant even when the branches sway or the rope tightens and stretches with varying climatic conditions.

The war has brought about the development of easily-erected portable masts made of plywood or metal in heights up to 100 feet. These promise to have widespread amateur application in postwar installations.

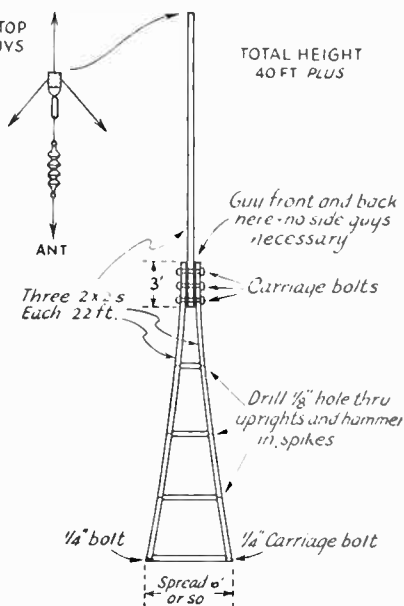


Fig. 1701 — Details of a simple 40-foot "A"-frame mast suitable for erection in locations where space is limited.

"A"-Frame Mast

The simple and inexpensive mast shown in Fig. 1701 is satisfactory for heights up to 35 or 40 feet. Clear, sound lumber should be selected. The completed mast may be protected by two or three coats of house paint.

If the mast is to be erected on the ground, a couple of stakes should be driven to keep the bottom from slipping and it may then be "walked up" by a pair of helpers. If it is to go on a roof, first stand it up against the side of the building and then hoist it from the roof, keeping it vertical. The whole assembly is light enough for two men to perform the complete operation — lifting the mast, carrying it to its permanent berth and fastening the guys — with the mast vertical all the while. It is entirely practicable, therefore, to erect this type of mast on any small, flat area of roof.

By using 2 × 3s or 2 × 4s, the height may be extended up to about 50 feet. The 2 × 2 is too flexible to be satisfactory at such heights.

Simple 40-Foot Mast

The mast shown in Fig. 1702 is relatively strong, easy to construct, readily dismantled, and costs very little. Like the "A" frame, it is suitable for heights of the order of 40 feet.

The top section is a single 2 × 3, bolted at the bottom between a pair of 2 × 3s with an overlap of about two feet. The lower section thus has two legs spaced the width of the narrow side of a 2 × 3. At the bottom the two legs are bolted to a length of 2 × 4 which is set in the ground. A short length of 2 × 3 is placed between the two legs about half way up the bottom section, to maintain the spacing.

The two back guys at the top pull against the antenna, while the three lower guys prevent buckling at the center of the pole.

The 2 × 4 section should be set in the ground so that it faces the proper direction, and then made vertical by lining it up with a plumb bob. The holes for the bolts should be drilled beforehand. With the lower section laid on the ground, bolt A should be slipped in place through the three pieces of wood and tightened just enough so that the section can turn freely on the bolt. Then the top section may be bolted in place and the mast pushed up, using a ladder or another 20-foot 2 × 3 for the job. As the mast goes up, the slack in the guys can be taken up so that the whole structure is in some measure continually supported. When the mast is vertical, bolt B should be slipped in place and both A and B tightened. The lower guys can then be given a final tightening, leaving those at the top a little slack until the antenna is

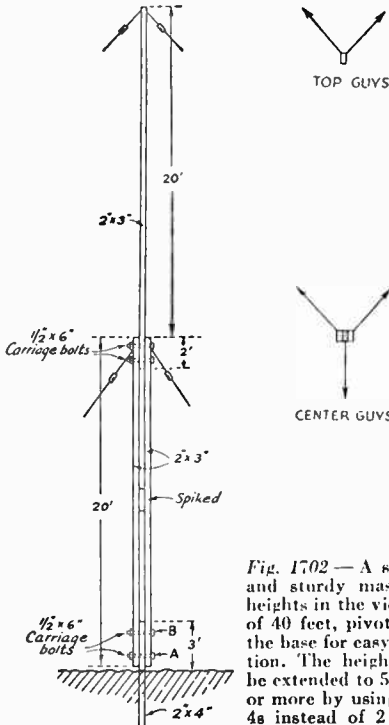


Fig. 1702 — A simple and sturdy mast for heights in the vicinity of 40 feet, pivoted at the base for easy erection. The height can be extended to 50 feet or more by using 2 × 4s instead of 2 × 3s.

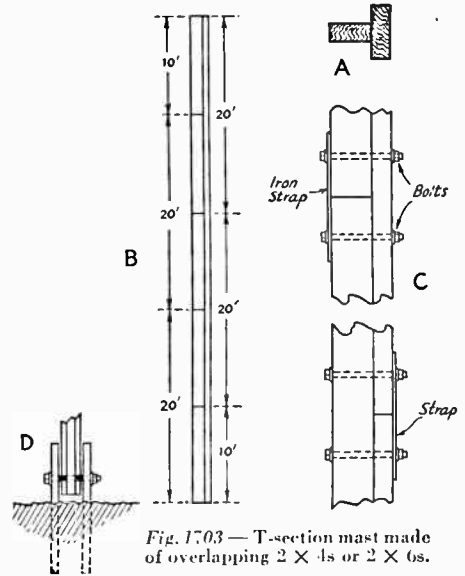


Fig. 1703 — T-section mast made of overlapping 2 × 4s or 2 × 6s.

pulled up, when they should be adjusted to pull the top section into line.

T-Section Mast

A type of mast suitable for heights up to about 80 feet is shown in Fig. 1703. The mast is built up by butting 2 × 4 or 2 × 6 timbers edgewise against a second 2 × 4, as shown at A, with alternating joints in the edgewise and flatwise sections. The construction can be carried out to greater lengths simply by continuing the 20-foot sections. Longer or shorter sections may be used, if more convenient.

The method of making the joints is shown at C. Quarter-inch or 3/16-inch iron, 1 1/2 to 2 inches wide, is recommended for the straps, with 1/2-inch bolts to hold the pieces together. One bolt should be run through the pieces midway between joints, to provide additional rigidity.

Although there are many ways in which such a mast can be secured at the base, the "cradle" illustrated at D has many advantages. Heavy timbers set firmly in the ground, spaced far enough apart so the base of the mast will pass between them, hold a large carriage bolt or steel bar which serves as a bearing. This bolt goes through a hole in the mast so that it is pivoted at the bottom.

Half of the guys can be put in place and tightened up before the mast leaves the ground. Four sets of guys should be used, one in front, one directly in the rear, and two on each side at right angles to the direction in which the mast will face. A set of guys should be used at each of the joints in the edgewise sections, the guy wires being wrapped around the pole for added strength.

For heights up to 50 feet, 2 × 4-inch members may be used throughout. For greater heights, use 2 × 6s for the edgewise sections; 2 × 4-inch pieces will do for the flat sections.

☞ Pole and Tower Supports

Poles, which often may be purchased at a reasonable price from the local telephone or power company, have the advantage that they do not require guying unless they are called upon to carry a very heavy load. The life of such a pole can be extended many years by proper precautions before erecting, and regular maintenance.

Before setting the pole, it should be given four or five coats of creosote, applying it liberally so it can soak into and preserve the wood. The bottom of the pole and the part which will be buried in the ground should have a generous coating of hot pitch, poured on while the pole is warm. This will keep termites out and prevent rotting.

The poles should be set in the ground four to eight feet depending upon the height. It is a good idea to pour concrete around the bottom three feet of the base, packing the rest of the excavation with soil. The concrete will help hold the pole against strong winds. After filling the hole with dirt, a stream from a hose should be played on the dirt slowly for several hours. This will help to settle the soil quickly.

If desired, the pole may be extended by the arrangement shown in Fig. 1704. Three 2 x 4s are required for the top section, two being 18 feet long and one 10 feet long. The 10-foot section is placed between the other two and bolted in place. A half-inch hole should be bored through the pole about 2 feet from its top and through both 18-foot 2 x 4s about 5 feet from their bottom ends, which are spread apart to fit the top of the pole. The bottom end of the extension is then hauled up to the top of the pole and bolted loosely so that the section can be swung up into place by the leverage of another 2 x 4 temporarily fastened to the

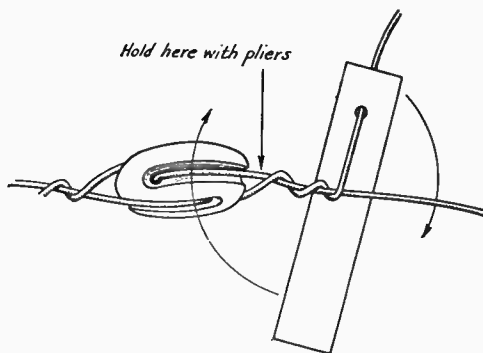


Fig. 1705 — Using a simple lever for twisting heavy guy wires.

section, as shown in Fig. 1704.

Lattice towers built of wood should be assembled with brass screws and casein glue, rather than with nails which work loose in a short time. A tower constructed in this manner will give trouble-free service if treated with a coat of paint every year.

In painting outside structures, use pure white lead, thinned with three parts of pure linseed oil to one part of turpentine, for the first coat on new wood. The use of a drier is not recommended if the paint will possibly dry without it, since it may cause the paint to peel after a short time. For the second and third coats pure white lead thinned only with pure linseed oil is recommended. Plenty of time for drying should be allowed between coats. White paint will last fifty per cent longer than any colored paint.

☞ Guys and Guy Anchors

For masts or poles up to about 50 feet, No. 12 iron wire is a satisfactory guy-wire material. Heavier wire or stranded cable may be used for taller poles or poles installed in locations where the wind velocity is high.

More than three guy wires in any one set usually are unnecessary. If a horizontal antenna is to be supported, two guy wires in the top set will be sufficient in most cases. These should run to the rear of the mast about 100 degrees apart to offset the pull of the antenna. Intermediate guys should be used in sets of three, one running in a direction opposite to that of the antenna, while the other two are spaced 120 degrees either side. This leaves a clear space under the antenna. The guy wires should be adjusted to pull the pole slightly back from vertical before the antenna is hoisted so that when the antenna is pulled up tight the mast will be straight.

When raising a mast which is big enough to tax the facilities

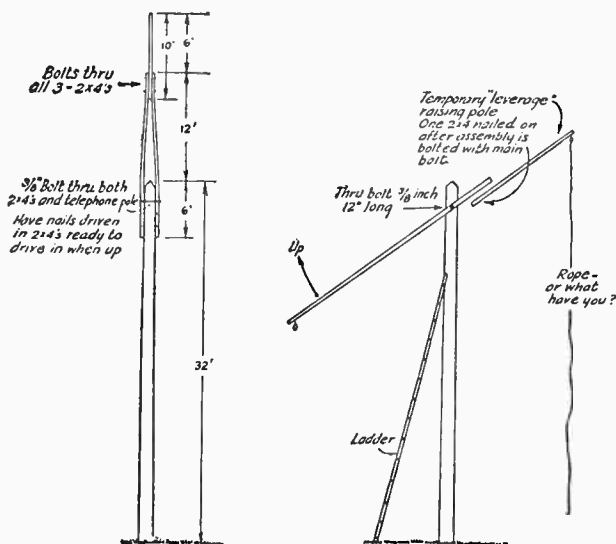


Fig. 1704 — This type of mast may be carried to a height of fifty feet or more. No guy wires are required.

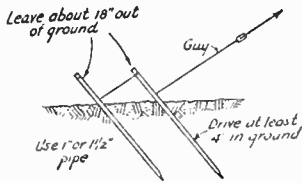


Fig. 1706 — Pipe-guy anchors. One pipe is sufficient for small masts, but two installed as shown will provide the additional strength required for the larger poles.

available, it is some advantage to know nearly exactly the length of the guys. Those on the side on which the pole is lying can then be fastened temporarily to the anchors beforehand, which assures that when the pole is raised, those holding opposite guys will be able to pull it into nearly vertical position with no danger of its getting out of control. The guy lengths can be figured by the right-angled-triangle rule that "the sum of the squares of the two sides is equal to the square of the hypotenuse." In other words, the distance from the base of the pole to the anchor should be measured and squared. To this should be added the square of the pole length to the point where the guy is fastened. The square root of this sum will be the length of the guy.

Guy wires should be broken up by strain insulators, to avoid the possibility of resonance at the transmitting frequency. Common practice is to insert an insulator near the top of each guy, within a few feet of the pole, and then cut each section of wire between the insulators to a length which will not be resonant either on the fundamental or harmonics. An insulator every 25 feet will be satisfactory for frequencies up to 30 Mc. The insulators should be of the "egg" type with the insulating material under compression, so that the guy will not part if the insulator breaks.

Twisting guy wires onto "egg" insulators may be a tedious job if the guy wires are long and of large gauge. The simple time- and finger-saving device shown in Fig. 1705 can be made from a piece of heavy iron or steel by drilling a hole about twice the diameter of the guy wire about a half inch from one end of the piece. The wire is passed through the insulator,

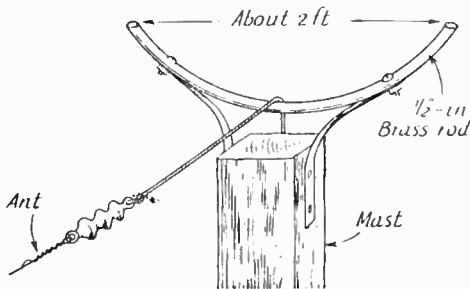


Fig. 1707 — This device is much easier than a pulley to "rethread" when the rope breaks.

given a single turn by hand, and then held with a pair of pliers at the point shown in the sketch. By passing the wire through the hole in the iron and rotating the iron as shown, the wire may be quickly and neatly twisted.

Guy wires may be anchored to a tree or building when they happen to be in convenient spots. For small poles, a 6-foot length of 1-inch pipe driven into the ground at an angle will suffice. Additional bracing will be provided by using two pipes, as shown in Fig. 1706.

Halyards and Pulleys

Halyards or ropes and pulleys are important items in the antenna-supporting system. Particular attention should be directed toward the choice of a pulley and halyards for a high mast since replacement, once the mast is in position, may be a major undertaking if not entirely impossible.

Galvanized-iron pulleys will have a life of only a year or so. Especially for coastal-area installations, marine-type pulleys with hard-

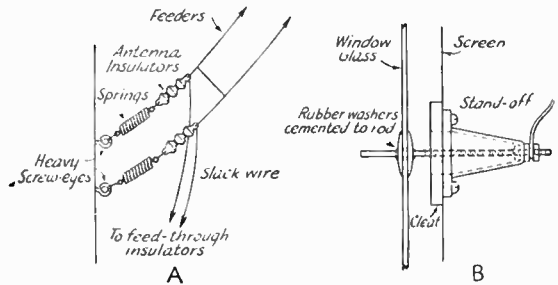


Fig. 1708 — (A) Anchoring feeders takes the strain from feed-through insulators or window glass. (B) Going through a full-length screen, a cleat is fastened to the frame of the screen on the inside. Clearance holes are cut in the cleat and also in the screen.

wood blocks and bronze wheels and bearings should be used.

An arrangement which has certain advantages over a pulley when a mast is used is shown in Fig. 1707. In case the rope breaks, it may be possible to replace it by heaving a line over the brass rod, making it unnecessary to climb or lower the pole.

For short antennas and temporary installations, heavy clothesline or window sash cord may be used. However, if the job is to be more or less permanent, 3/4-inch or 1/2-inch waterproof hemp rope should be used. Even this should be replaced about once a year to insure against breakage.

Nylon rope, used during the war as glider tow rope, is, of course, one of the best materials for halyards, since it is weatherproof and has extremely long life.

It is advisable to carry the pulley rope back up to the top in "endless" fashion in the manner of a flag hoist so that if the antenna breaks close to pole, there will be a means for pulling the hoisting rope back down where it is accessible.

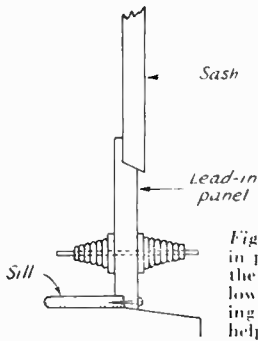


Fig. 1709 — An antenna lead-in panel may be placed over the top sash or under the lower sash of a window. Sealing the overlapping joint will help make it weatherproof.

⌚ Bringing the Antenna or Transmission Line into the Station

The antenna or transmission line should be anchored to the outside wall of the building, as shown in Fig. 1708, to remove strain from the lead-in insulators. Holes cut through the walls of the building and fitted with feed-through insulators are undoubtedly the best means of bringing the line into the station. The holes should have plenty of air clearance about the conducting rod, especially when using tuned lines which develop high voltages. Probably the best place to go through the walls is the trimming board at the top or bottom of a window frame which provides flat surfaces for lead-in insulators. Cement or rubber gaskets may be used to waterproof the exposed joints.

Where such a procedure is not permissible, the window itself usually offers the best opportunity. One satisfactory method is to drill holes in the glass near the top of the upper sash. If the glass is replaced by plate glass, a stronger job will result. Plate glass may be obtained from automobile junk yards and drilled before placing in the frame. The glass itself provides insulation and the transmission line may be fastened to bolts fitting the holes. Rubber gaskets cut from inner tube will render the

holes waterproof. The lower sash should be provided with stops at a suitable height to prevent damage when it is raised. If the window has a full-length screen, the scheme shown in Fig. 1708-B may be used.

As a less permanent method, the window may be raised from the bottom or lowered from the top to permit insertion of a board which carries the feed-through insulators. This lead-in arrangement can be made weatherproof by making an overlapping joint between the board and window sash, as shown in Fig. 1709, and covering the opening between sashes with a sheet of soft rubber from a discarded inner tube.

Unless a Zepp antenna is directly at right angles to a line running from the feeder end to the point where it enters the station, difficulty may be experienced in keeping both feeders tight, since one will always have a certain amount of slack, as shown in Fig. 1710. This

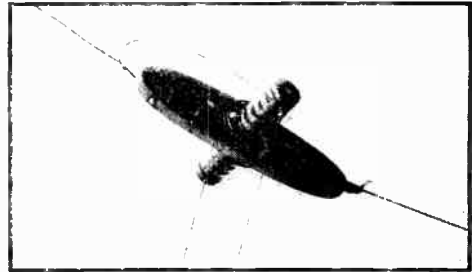


Fig. 1711 — Home-made "universal joint" for Zepp feeders.

can be overcome by constructing a "universal joint" as shown in Fig. 1711. This permits swinging the feeders at any angle with the antenna, while the feeders are kept taut at all points.

A piece of half-inch hard maple thoroughly boiled in paraffin acts as the antenna insulator, while the two stand-off insulators support the feeders.

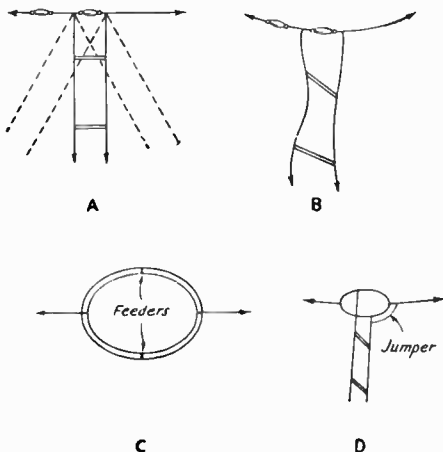


Fig. 1710 — Sketch showing the principles involved in the "universal joint" for Zepp feeders to prevent slack.

⌚ Rotary Beam Construction

Many amateurs mount the simpler types of directive antennas in such a way that the antenna can be rotated to shift the direction of the beam at will. Obviously the use of such rotary antennas is limited to the higher frequencies, if the structure is to be of practicable size. For this reason the majority of rotary-beam antennas are constructed for use on 14 Mc. and higher frequencies. The problems in rotary-beam construction are those of providing a suitable mechanical support for the antenna elements, furnishing a means of rotation, and attaching the transmission line so that it does not interfere with the rotation of the system. When the elements are horizontal a supporting structure is necessary, made usually of light but strong wood.

The antenna elements usually are made of metal tubing so that they will be at least partially self-supporting, thus simplifying the sup-

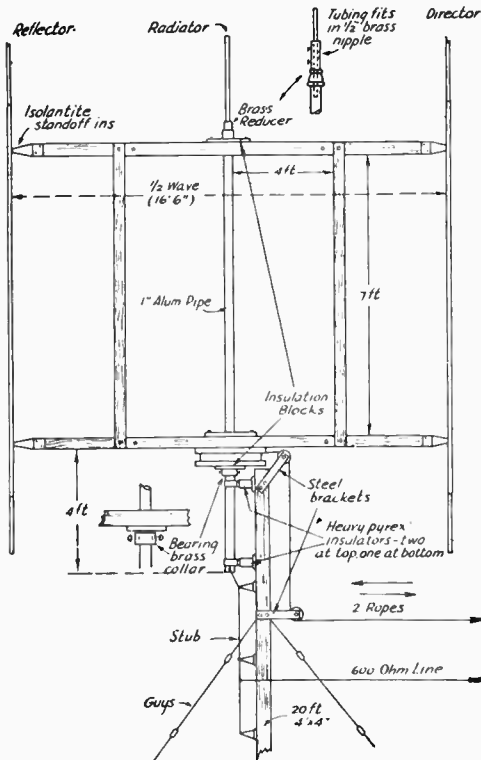


Fig. 1712 — A practical vertical-element rotatable array for 28 Mc. The driven antenna is fixed and the reflector and director elements, parasitically excited, rotate around it. Close-spaced elements may be used if desired.

porting structure. The large diameter of the conductor is beneficial also in reducing resistance, which becomes an important consideration when close-spaced elements are used.

Dural tubes often are used for the elements, and thin-walled corrugated steel tubes with copper coating also are available for this purpose. The elements frequently are constructed of sections of telescoping tubing, making length adjustments quite easy. Electricians' thin-walled conduit also is suitable for rotary beam elements.

If steel elements are used, special precautions should be taken to prevent rusting. Even copper-coated steel does not stand up indefinitely, since the coating usually is too thin. The elements should be coated both inside and out with slow-drying aluminum paint. For coating the inside, the spray gun may be used, or the paint may be poured in one end while rotating the tubing. The excess paint may be caught as it comes out the bottom end and poured through again until it is certain that the entire inside wall has been covered. The ends should then be plugged up with corks sealed with glyptal varnish.

Various means of rotation and of making contact to the transmission line have been devised. Fig. 1712 shows a mechanical arrangement suitable for use with vertical elements.

The antenna, which is a vertical section of metal tubing, is mounted in a fixed position and is provided with a director and reflector which rotate about it. The advantage of this arrangement is that no provision need be made for special contacts between the antenna and the feeder system, since the position of the antenna is fixed. A rope-and-pulley arrangement provides rotation from the operating room, so that, when a signal is picked up, the antenna can be rotated rapidly to the position which gives maximum response. It is then also pointing in the proper direction for transmission. The system can be varied in dimensions and details; for instance, close element spacing might be used to give greater gain.

Parts from junked automobiles often provide gear trains and bearings for rotating the antenna. Rear axles, in particular, can readily be adapted to the purpose. Some amateurs use motor-driven rotating mechanisms which, although complicating the construction, simplify remote control of the antenna. More or less elaborate indicating devices, which show the direction in which the antenna is pointed, often are used with motor-driven beams.

One method is shown in Fig. 1713. In this case the pole is rotated by a chain-and-sprocket arrangement, with the base resting on a bearing. Feeders are brought down the pole from the antenna to a pair of wire rings, against which sliding contacts press.

Driving motors and gear housings will stand the weather better if given a coat of aluminum paint followed by two coats of enamel and a coat of glyptal varnish. Even commercial units will last longer if treated with glyptal varnish.

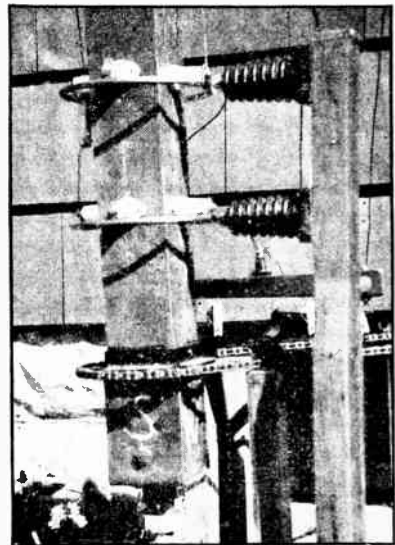


Fig. 1713 — One form of rotating mechanism. A bicycle sprocket and chain turn the pole which supports the beam antenna. Feeder connections from the antenna are brought to the metal rings, which slide against spring contacts mounted on the large stand-off insulators.

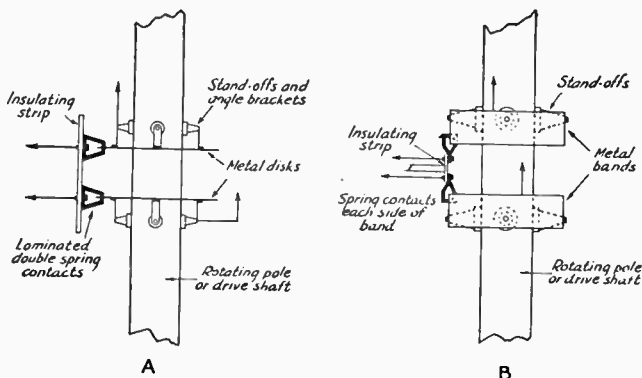


Fig. 1711 — Ideas in sliding contacts for rotatable antenna feeder connection to permit continuous rotation. The broad bearing surfaces take care of any wobble in the rotating mast or driving shaft.

Lead-sheathed twin conductor cable is recommended for power wiring to the motor to prevent r.f. pick-up.

⊖ Feeder Connections

For beams which rotate only 180 degrees, it is relatively simple to bring off feeders by making a short section of the feeder, just where it leaves the rotating member, of flexible wire. Enough slack should be left so that there is no danger of breaking or twisting. Stops should be placed on the rotating shaft of the antenna so that the feeders cannot "wind up." This method also can be used with antennas which rotate the full 360 degrees, but again a stop is necessary to avoid jamming the feeders.

For continuous rotation, the sliding contact is simple and, when properly built, quite practicable. Fig. 1714 shows two methods of making sliding contacts. The chief points to keep in mind are that the contact surfaces should be wide enough to take care of wobble in the rotating shaft, and that the contact surfaces should be kept clean. Spring contacts are essential, and an "umbrella" or other scheme for keeping rain off the contacts is a desirable addition. Sliding contacts preferably should be used with non-resonant open lines where the impedance is of the order of 500 to 600 ohms so that the current is low.

A good, but relatively expensive, contact system can be made by using mercury in ring-shaped grooves for the movable contact, with rods dipping in the mercury for the fixed contacts. A contact system of this type was described in May, 1938, *QST*.

The possibility of poor connections in sliding contacts can be avoided by using inductive coupling at the antenna, with one coil rotating on the antenna and the other fixed in position, the two coils being arranged so that the coupling does not change when the antenna is rotated. Such an arrangement is shown in Fig. 1715, adapted to an antenna system in which the pole itself rotates. A quarter-wave feeder system is

connected to a tuned pickup circuit whose inductance is coupled to a link. In the drawing, the link coil connects to a twisted-pair transmission line. The circuit would be adjusted in the same way as any link-coupled circuit, and the number of turns in the link should be varied to give proper loading on the transmitter. The rotating coupling circuit of course tunes to the transmitting frequency. The whole thing is equivalent to a link-coupled antenna tuner mounted on the pole, using a parallel-tuned tank at the end of a quarter-wave line to centerfeed the antenna. To maintain constant

coupling, the two coils should be quite rigid and the pole should rotate without wobble. The two coils might be made a part of the upper bearing assembly holding the rotating pole in position.

Other variations of the inductive-coupled system might be worked out. The tuned circuit might, for instance, be placed at the end of a 600-ohm line, and a one-turn link used to couple directly to the center of the antenna, if the construction of the rotary member permits. In this case the coupling can be varied by changing the L/C ratio in the tuned circuit. For mechanical strength the coils preferably should be made of copper tubing, well braced with insulating strips to keep them rigid.

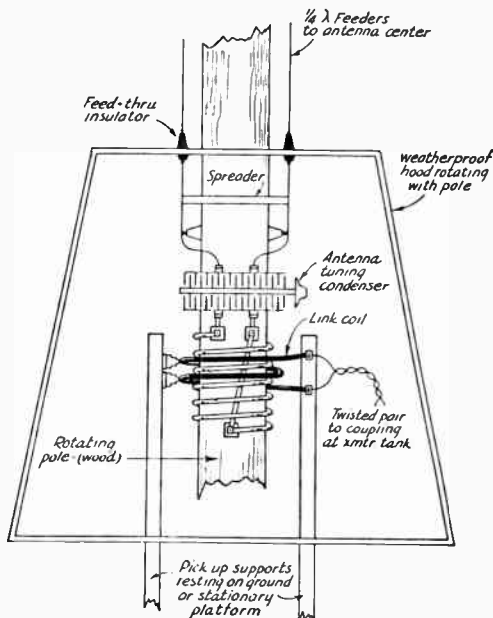


Fig. 1715 — One method of transmission line-antenna system coupling which eliminates sliding contacts. The low-impedance line is link-coupled to a tuned line.

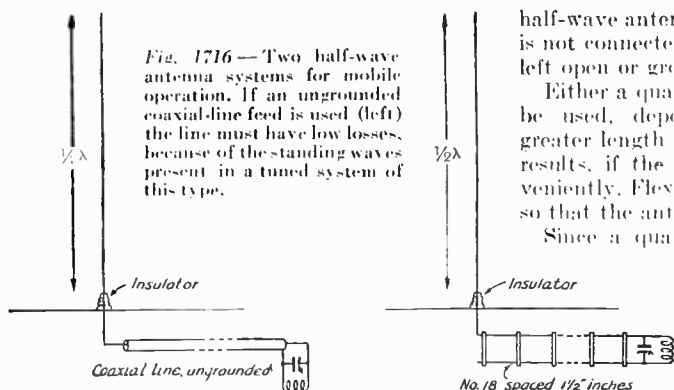


Fig. 1716 — Two half-wave antenna systems for mobile operation. If an ungrounded coaxial-line feed is used (left) the line must have low losses, because of the standing waves present in a tuned system of this type.

Mobile Antennas

For mobile work on the very-high frequencies, a flexible rod or "whip" antenna is commonly used, mounted vertically on stand-off or feed-through insulators attached to the car body. Where possible the antenna should be a half-wavelength long, since this length will give the best low-angle radiation. A quarter-wave antenna, working against the metal car body as a counterpoise or "ground," may be used but it is not so efficient a radiator as the half-wave antenna.

As in the case of antennas for fixed stations, it is important that the car antenna be mounted as high as possible, to avoid screening effects of the car and to give maximum range. The best location for mounting the antenna is in the middle of the roof in the case of a car with a metal top. If the antenna cannot be mounted so that it is entirely above the top of the car, it should still be made to have a major portion of its effective radiating length above the roof. The top forms a "ground" of good conductivity and improves the performance. Convertibles and coupés have a convenient spot for mounting the antenna on the deck in back of the rear window. The lead-in can be brought into either the luggage compartment or the driver's seat, depending upon the location of the radio gear. Sedans lend themselves more readily to mounting the antenna alongside the hood or on the rear bumper. An antenna mounted alongside the car body but projecting above the metal top will transmit best in the direction across the top of the car.

It is advantageous to mount the antenna as near the transmitter as possible, in order to simplify the feed system. Special feeder systems, such as low-loss coaxial lines, are necessary if the antenna is located at one end of the car and the transmitter at the other. A quarter-wave tuned line is a suitable system, using appropriate tuning methods. When used with an end-fed

half-wave antenna, the end of the feeder which is not connected to the antenna may either be left open or grounded to the car body.

Either a quarter- or half-wave antenna may be used, depending upon conditions. The greater length of the latter will lead to better results, if the installation can be made conveniently. Flexible metal rod is generally used, so that the antenna will be self-supporting.

Since a quarter-wave antenna normally is supported at a low-voltage point, hard-rubber insulators are satisfactory. However, a half-wave antenna will usually be supported at a high-voltage point and thus requires good insulation for best efficiency. Ceramic insulators usually can be obtained to fit any case. It is wise not to skip on size because of the greater chance of breakage with the smaller units. The feed-through types and the stand-off types with metal base rings are least likely to break.

The two methods of feeding the half-wave antenna shown in Fig. 1716 are probably the most convenient. Both systems use tuned feed lines, and thus require a tuning system at the transmitter end.

If a quarter-wave antenna is to be mounted permanently on the car it should be located on the roof, otherwise it is likely that the radiation pattern will be quite irregular. The resulting directional effects will be a help on some occasions but a definite hindrance on others. The antenna can be fed by a tuned line or by a coaxial line, as shown in Fig. 1717. The coaxial line can be of the 70- or 100-ohm type.

The coaxial line feed can be checked by observing its detuning effect on the transmitter; a good match will have been obtained when the detuning is a minimum. The antenna length and the capacity of the condenser should be varied until connecting the other end of the line to the transmitter causes a minimum of frequency change. Loading is controlled at the transmitter by adjusting the coupling coil, *not* by varying the condenser at the antenna. The antenna is made longer in small steps and the condenser adjusted until the concentric line introduces a minimum of reactance at the transmitter (shows the least detuning effect on the tank circuit). The method is simply to vary the length of the radiator until it shows an impedance near that of the line and then to cancel the reactance by adjusting capacity of the series condenser.

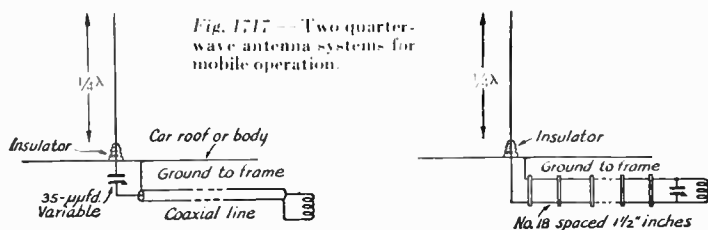


Fig. 1717 — Two quarter-wave antenna systems for mobile operation.

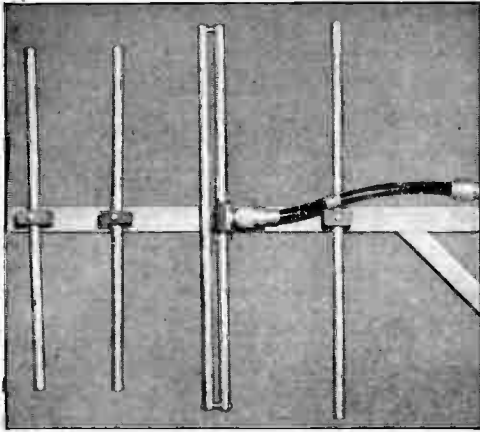


Fig. 1718 — A four-element beam with folded dipole antenna for 420 Mc.

◀ V.H.F. Antennas

Although antennas for the very-high frequencies are constructed on the same principles as those for lower frequencies, the smaller dimensions permit structural arrangements which would be unwieldy, if not impracticable, on lower frequencies. The extended double Zepp, used vertically, is particularly easy to mount, the elements being made of $\frac{1}{4}$ -inch copper or dural rod or tubing and fastened to the side of a pole by stand-off insulators.

A simple, practical application of the end-fire principle (§ 10-12) is the use of two lengths of copper tubing, bent to form a "pitchfork" one-half wavelength long (down to the bend) and with a quarter- to an eighth-wavelength separation. If the pole can be made to rotate 180 degrees, full advantage may be taken of the directivity of the system. Tuned feeders may be used if the length is not more than one or two wavelengths; for greater lengths, an untuned line and a matching stub are desirable.

Combination collinear and broadside arrays as described in Chapter Ten give good gain and are not difficult to construct. The elements can be made of wire or tubing. The assembly may consist simply of wires hung from a rope stretched between two supports.

The photograph of Fig. 1718 shows a four-element beam with one reflector and two directors. The elements are cut from $\frac{3}{8}$ -inch diameter aluminum rod. The antenna is a folded dipole consisting of two lengths of

rod bolted together at the ends with $\frac{1}{4}$ -inch brass spacers.

The elements are supported at their centers on bakelite blocks fastened to a frame made of wood. For 420 Mc., the antenna is 13 inches long, the reflector $13\frac{1}{2}$ inches long and the directors each $11\frac{1}{2}$ inches in length. The spacing between directors and between the first director and the antenna is 2.6 inches and between the antenna and the reflector 4 inches. The lengths of the elements and the spacing should be adjusted to obtain the greatest possible forward radiation as indicated on a field-strength meter.

Close spacing and balance are important factors in v.h.f. feeder operation to minimize radiation from the line. For this reason the coaxial line is the best type of feed for the v.h.f. antenna, but the open-wire line is quite effective if care is taken in its construction. If a matching section is used, it should be symmetrical and loaded on both sides, to maintain current balance in the matching section.

Corner reflector antenna — A type of highly directive antenna system for the v.h.f. and u.h.f. ranges above 50 Mc. which is comparatively easy to construct is the "corner" reflector, shown in Fig. 1719. It consists of two plane reflecting surfaces set at an angle of 90 degrees, with the antenna set on a line bisecting this angle. The distance of the antenna from the vertex should be 0.5 wavelength. The reflector surfaces are made of spines spaced about 0.1 wavelength apart.

The antenna used may be a center-fed full-wave affair with a two-wire line. Since the radiation resistance of the antenna is raised when the reflector is used, an impedance-matching system will be required if ordinary

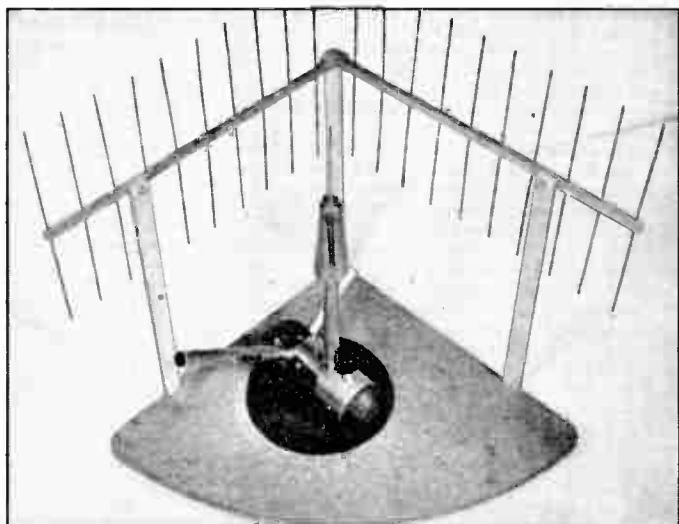


Fig. 1719 — Typical construction of a square-corner reflector for u.h.f. work. This is a photograph of an experimental set-up in which the u.h.f. oscillator is mounted directly under the antenna.

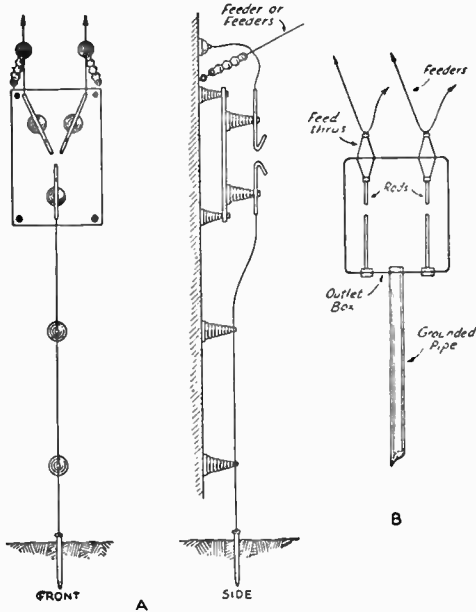


Fig. 1720 — Low-loss lightning arresters for transmitters. types of lines are used. For this reason a tuned line is advisable. Alternatively, a folded dipole (§ 10-14) may be used directly with a 500-ohm line (No. 12 wire spaced 2 inches).

The transmission line should be run out at the rear of the reflector, to keep the system symmetrical and thus avoid any unbalance.

The corner reflector antenna will give a gain of approximately 10 db. over a simple half-wave dipole. The front-to-back and front-to-side ratios are of the order of 35 and 25 db., respectively, in a typical case, and the directional pattern is relatively free from secondary lobes of appreciable amplitude.

⌚ Lightning Protection

An ungrounded radio antenna, particularly if large and well elevated, is a lightning hazard. When grounded, it provides a measure of protection. Therefore, grounding switches or lightning arresters should be provided. Examples of construction of low-loss arresters are shown in Fig. 1720. At A, the arrester electrodes are mounted by means of stand-off insulators on a fireproof asbestos board. At B, the electrodes are enclosed in a standard steel outlet box. The gaps should be made as small as possible without danger of breakdown during operation. Lightning-arrester systems require the best ground connection obtainable.

The most positive protection is to ground the antenna system when it is not in use; grounded flexible wires provided with clips for connection to the feeder wires may be used. The ground lead should be short and run, if possible, directly to a driven pipe or water pipe where it enters the ground outside the building.

⌚ Antenna Switching

It is often desirable, particularly in DX work, to use the same antenna for transmitting and receiving. This requires switching of antenna from transmitter to receiver. One of two general systems may be employed. In the first, the transmitter and receiver each are provided with an antenna tuner, and the antenna transmission line is switched from one to the other. In the second system, one antenna tuner is provided for each antenna and the switch is in the low-impedance coupling line. Several typical arrangements are shown in Fig. 1721. Frequently relays with low-capacity contacts are substituted for switches.

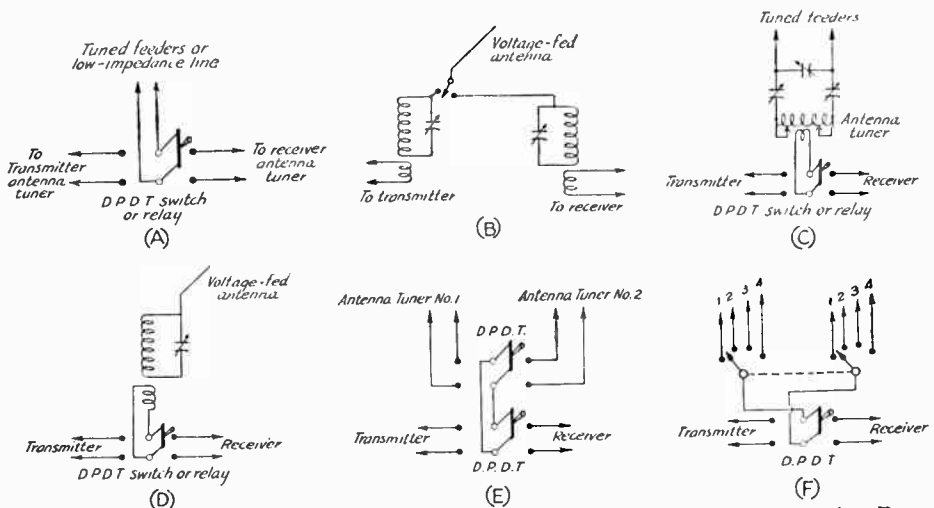


Fig. 1721 — Antenna-switching arrangements for various types of antennas and coupling systems. A — For tuned lines with separate antenna tuners or low-impedance lines. B — For a voltage-fed antenna. C — For a tuned line with a single antenna tuner. D — For a voltage-fed antenna with a single tuner. E — For two tuned-line antennas with a tuner for each antenna or for two low-impedance lines. F — For combinations of several two-wire lines.

Emergency and Portable

EMERGENCY self-powered equipment is no longer a nice toy to play with when regular amateur activities pall; it has become the moral obligation of every amateur to be prepared in case of any communications emergency. Large-scale disasters in the past have demonstrated the tremendous value of amateur emergency stations in relaying relief messages when all other communication channels are closed. Aside from the all-important emergency phase, the use of portable equipment has been extended through organized activity in the annual ARRL "Field Days," and the problem of providing equipment suitable for use in rural districts, where commercial power is not available, has always been with us.

The most vital need for self-powered equipment occurs in connection with emergency activity, and the basic design of all such equipment should be predicated on emergency use. Every amateur, no matter where he may be located, can reasonably expect that sometime he may be called upon to perform emergency communications duty, and it is his responsibility to the public welfare, to himself, and to amateur radio as a whole to see that he is in some measure prepared.

It is not to be expected that every amateur will prepare himself for an emergency by having available a complete and separate self-powered station, although a large number of individuals and club groups do so. There is, however, no reason why every amateur cannot prepare his station for an emergency by having an emergency power supply ready and a quick means for utilizing all or part of his regular station equipment as an emergency-powered station. The emergency power supply can be anything from a small vibrator supply and/or batteries to a large gasoline-driven generator.

Ⓐ Battery and Vibrator Data

The use of dry batteries, storage batteries and vibrator-transformer packs or genemotors is discussed in Chapter Eight. Table I shows the service which may be expected from standard-brand dry batteries under various load conditions. Various types of manufactured vibrator-transformer units are listed in Table II, while Table III is a listing of available dynamotors which are suitable for emergency and portable work.

Ⓑ Construction of Vibrator Supplies

Vibrator-type power supplies are not diffi-

cult to construct. The transformer usually is a special type designed for the purpose, although a heavy-duty receiver or low-power transmitter transformer may be pressed into service if it has suitable filament windings which may be connected as the 6-volt vibrator primary. A supply may be designed to operate from a 6-volt storage battery only, or a dual-primary transformer or separate transformers may be used so that the supply will operate interchangeably on either 115-v.a.c. or 6 v.d.c.

Typical circuit diagrams are shown in Fig. 1801. The one shown at (A) is the simplest, although it operates from a 6-volt d.c. source only. S_1 turns the high voltage on and off.

The circuit of (B) provides for both 6-volt d.c. and 115-volt a.c. operation with a dual-primary transformer. S_2 is the a.c. on-off switch while S_3 switches the heater of the 6X5 rectifier from the storage battery to the 6.3-volt winding on the transformer. Filament supply for the transmitter or receiver is switched by shifting the power plug to the correct output socket, X when operating from a 6-volt d.c. source and Y when 115-volt a.c. input is used.

The circuit of Fig. 1801 (C) may be used when a dual-primary transformer is not available. The filter is switched from one rectifier output to the other by means of the d.p.d.t. switch, S_4 , which also shifts filament connections from a.c. to d.c. The filter section of the switch could be eliminated if desired by connecting the filtering circuit permanently to the output terminals of both rectifiers and removing the unused rectifier tube from its socket. Similarly, the filament section of S_4 could be dispensed with by providing two output sockets as in the circuit at (B). If a separate rectifier-filament winding is available on T_3 , directly-heated rectifier types may be substituted for the 6X5 in the a.c. supply. In some cases where the required filament windings are not available, a rectifier of the cold-cathode type, such as the 0Z4, which requires no heater voltage, may be used to advantage.

If suitable filament windings are available, a regular a.c. transformer will make an acceptable substitute for a vibrator transformer. If the a.c. transformer has two 6.3-volt windings, they may be connected in series, their junction forming the required center tap. A 6.3-volt and a 5-volt winding may be used in a similar manner even though the junction of the two windings does not provide an accurate center tap. A better center tap may be obtained, if a 2.5-volt winding also is available, since half

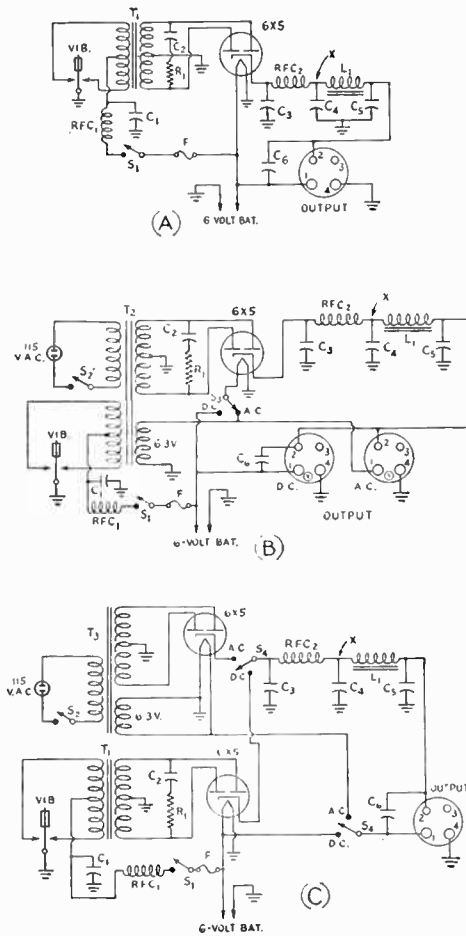


Fig. 1801 — Typical vibrator-transformer power-supply circuits. The circuit at (A) shows a simple arrangement for 6-volt d.c. input; the one at (B) illustrates the use of a combination transformer for operation from either 6 volts d.c. or 115 volts a.c. The circuit of (C) is similar to that of (B) but uses separate transformers.

- C₁ — 0.5- μ d. paper, 50-volt rating or higher.
 - C₂ — 0.005 to 0.01 μ d., 1600 volts (see text).
 - C₃ — 0.01- μ d. 600-volt paper.
 - C₄ — 8- μ d. 450-volt electrolytic.
 - C₅ — 32- μ d. 450-volt electrolytic.
 - C₆ — 100- μ d. mica.
 - L₁ — 10-12 henry 100 ma. filter choke, not over 100 ohms (Stancor C-2303 or equivalent).
 - R₁ — 5000 ohms, 1/2- or 1-watt.
 - RFC₁ — 55 turns No. 12 on 1-inch form, close-wound.
 - RFC₂ — 2.5-mh. r.f. choke.
 - F — 15-ampere fuse.
 - S₁ — S.p.s.t. toggle — battery switch.
 - S₂ — S.p.s.t. toggle — a.c. power switch.
 - S₃ — S.p.s.t. toggle — rectifier/heater change-over switch.
 - S₄ — D.p.d.t. toggle — a.c.-d.c. switch.
 - VIB — Vibrator unit (Mallory 500P, 294, etc.)
 - T₁ — Vibrator transformer.
 - T₂ — Special vibrator transformer with 115-volt and 6-volt primaries, to give approximately 300 volts at 100 ma. d.c. (Stancor P-6166 or equivalent).
 - T₃ — A.c. transformer, 275 to 300 volts each side of center tap, 100 to 150 ma.; 6.3-volt filament.
 - X — Insert a series resistor of suitable value to drop the output voltage to 300 at 100-ma. load, if necessary. If transformer gives over 300 volts d.c., a second filter choke may be used to give additional voltage drop as well as more smoothing.
- NOTE — All ground connections should be made to a single point on the chassis.

of this winding may be connected in series with the 5-volt winding to give 6.25 volts.

R.f. filters for reducing hash are incorporated in both primary and secondary circuits. The secondary filter consists of a 0.01- μ d. paper condenser directly across the rectifier output, with a 2.5-mh. r.f. choke in series ahead of the smoothing filter. In the primary circuit a low-inductance choke and high-capacity condenser are needed because of the low impedance of the circuit. A choke of the specifications given should be adequate, but if there is trouble with hash it may be beneficial to experiment with other sizes. The wire should be large — No. 12, preferably, and No. 14 as a minimum. Manufactured chokes such as the Mallory RF583 are more compact and give higher inductance for a given resistance because they are bank-wound, and may be substituted if obtainable. C₁ should be at least 0.5 μ d.; even more capacity may help in bad cases of hash.

The power supply should be built on a metal chassis, with all unshielded parts underneath. A bottom plate to complete the shielding is advisable. The transformer case, vibrator case

and metal shell of the tube all should be grounded to the chassis. If a glass tube is used it should be enclosed in a tube shield. The battery leads should be evenly twisted, since these leads are more likely to radiate hash than any other part of a reasonably well-shielded supply. A little care in this respect usually is more productive than experimenting with different values in the hash filters. Such experimenting should come *after* it has been found that radiation from the leads has been reduced to an absolute minimum. Shielding the leads is not particularly helpful.

The 100- μ d. mica condenser, C₆, connected from the positive output lead to the "hot" side of the "A" battery, may be helpful in reducing hash in certain power supplies. A trial is necessary to see whether or not it is required. It should be mounted right on the output socket.

Testing for methods of eliminating hash should be carried out with the supply operating a receiver. Since the interference usually is picked up on the receiver antenna leads by radiation from the supply itself and the battery leads, it is advisable to keep the supply and battery as far from the receiver as the connecting cables will permit. Three or four feet should be ample. The microphone cord likewise should be kept away from the supply and leads.

The smoothing filter for battery operation can be a single-section affair, but there will be some hum (readily distinguishable from hash because of its deeper pitch) unless the filter output capacity is fairly large — 16 to 32 μ d.

TABLE I—BATTERY SERVICE HOURS

Estimated to 34-volt end-point per nominal 45-volt section.
Based on intermittent use of 3 to 4 hours daily.
(For batteries manufactured in U. S. A. only.)

Manufacturer's Type No.		Weight		Current Drain in Ma.											
Burgess	Eveready	Lb.	Oz.	5	10	15	20	25	30	40	50	60	75	100	150
—	386	14	—	2000	1100	690	510	400	320	200	170	130	100	50	30
—	486	13	5	1700	880	550	395	300	240	165	125	100	70	45	20
21308	—	12	8	1600	1100	690	490	—	300	200	—	100	—	50	25
—	586	12	2	1400	800	530	380	260	185	130	85	60	40	30	14
10308	—	11	4	1300	700	520	350	—	—	130	—	90	—	42	18
—	585	8	13	900	450	290	210	130	100	60	45	25	20	11	5
2308	—	8	3	1100	500	330	180	—	100	65	—	34	—	—	—
B30	—	2	8	350	170	90	50	—	21	15	—	—	—	—	—
—	762	3	3	320	140	81	54	37	27	—	—	—	—	—	—
—	482	2	—	320	140	81	54	37	27	—	—	—	—	—	—
A30	—	2	—	210	80	44	24	—	14	5	—	—	—	—	—
—	738	1	2	160	70	30	20	10	7	—	—	—	—	—	—
Z30N	—	1	4	155	70	30	20	15	7.5	—	—	—	—	—	—
—	733	—	10	50	20	11	7	5.2	—	—	—	—	—	—	—
W30FL	—	—	11	45	19	12	7	—	3.5	—	—	—	—	—	—
—	455 ¹	—	8.6	70	20	11	7	5.2	—	—	—	—	—	—	—
XX30	—	—	9	70	20	12	7	—	3.5	—	—	—	—	—	—

¹ Same life figures apply to 467, 67½-volt, 10.5 oz.

Estimated to 1-volt end-point per nominal 1.5-volt unit. Based on intermittent use of 3 to 4 hours per day at room temperature. (For batteries manufactured in U. S. A. only.)

Manufacturer's Type No.		Weight		Volt- age	Current Drain in Ma.											
Burgess	Eveready	Lb.	Oz.		30	50	60	120	150	175	180	200	240	250	300	350
—	A-1300	8	4	1.25	—	—	—	—	2000	1715	1500	1333	1250	1200	1000	854
—	740	6	12	1.5	—	—	—	—	1400	1200	—	1050	—	775	625	—
—	741 ¹	2	14	1.5	—	—	1100	750	—	—	—	375	300	275	215	175
—	743	2	1	1.5	—	—	750	325	—	—	—	245	—	180	135	110
—	7111	2	2	1.5	—	—	700	320	—	—	200	—	120	—	90	—
—	742	1	6	1.5	—	—	500	325	—	—	155	135	100	95	85	50
8F ²	—	2	10	1.5	—	—	1100	680	450	—	—	400	—	320	230	190
4FA ³	—	1	4	1.5	—	—	600	350	220	—	—	160	—	110	90	60
—	A-2300	15	8	2.5	—	—	—	—	2000	1715	1500	1333	1250	1200	1000	854
—	723	1	—	3.0	—	—	240	100	—	—	70	—	40	—	30	—
20F2	—	13	12	3.0	—	—	—	—	1000	—	—	750	—	700	600	500
2F2H	—	1	6	3.0	600	—	340	130	95	—	—	60	—	42	30	—
2F2BP ⁴	—	1	5	3.0	600	—	340	130	95	—	—	60	—	42	30	—
F2BP	—	—	12	3.0	340	—	130	45	30	—	—	—	—	—	—	—
G3 ⁵	—	1	5	4.5	370	—	150	50	35	—	—	—	—	—	—	—
—	746	1	3	4.5	—	200	—	—	—	—	—	—	—	—	—	—
—	718 ⁶	3	—	6.0	—	375	—	—	—	—	—	—	—	—	—	—
F4PI	—	1	6	6.0	340	—	130	45	30	—	—	—	—	—	—	—

¹ Same life figures apply to 745, wt. 3 lbs.

² Same life figures apply to 8FL, wt. 2 lbs. 15 oz.

³ Same life figures apply to 4F, wt. 1 lb. 5 oz.

⁴ Same life figures apply to 2F4, volts 6, wt. 2 lbs. 11 oz.

⁵ Same life figures apply to G5, volts 7½, wt. 2 lbs. 2 oz.

⁶ Same life figures apply to 747, wt. 3 lbs.

If batteries of another make are to be used, locate ones of similar size and weight on these tables and comparable performance may be expected.

A typical example of vibrator-supply construction is shown in the photographs of Figs. 1802 and 1803.

All components in the supply with the exception of the four-prong outlet socket are mounted on a piece of quarter-inch tempered Masonite measuring 3¾ × 9 inches. This fits into a plywood box having inside dimensions (3¾ × 9 × 5½ inches) just large enough to contain the equipment. The Masonite shelf rests on ¾-inch square blocks, 1¼ inches long, glued to the corners of the box at the bottom. The top and bottom of the box are removable.

To provide shielding and thus reduce hash troubles, the box is covered with thin iron salvaged from 5-quart oil cans. Where the edges bend around the box to make a joint, the lacquer is rubbed off with steel wool so the pieces make electrical contact, and the metal is tacked to the plywood with escutcheon pins.

To make sure that the shielding will be complete, the top and bottom of the box slide into place from the side, with the metal covering extending out so that it fits tightly under a lip bent over from the metal on the sides. These lips also are cleaned of lacquer to permit

TABLE II—VIBRATOR SUPPLIES

Manufacturer's Type Number				Output		Rectifier	Output Filter
American Television and Radio Co.	Electronic Labs	Mallory	Radiart	Volts	Ma.		
VPM-F-7				90	10	Syn.	Yes
		VP-551 ¹		125-150- 175-200	100 max.	Syn.	No
			4201B ²	250	50	Syn.	Yes
		VP-540		250	60	Syn.	Yes
			4204F ³	100-150- 250	35-40- 60	Syn.	Yes
	605			150-200- 250-275	35-40- 50-65	Syn.	No
	604 ⁴	VP-552 ⁵		225-250- 275-300	50-65- 80-100	Syn.	No
			4201 ⁶	150-200- 250-275- 300	35-40- 50-70- 100	Syn.	No
	251 ⁷			300	100	Tube	Yes
		VP-555		300	200	Tube	Yes
VPM-6 ⁸	311 ⁹			250-275- 300-325	50-75- 100-125	Tube	Yes
		VP-557		400	150	Tube	Input cond.
			4202D	300- 400	200- 150	Tube	Yes
	606 ¹⁰			325-350- 375-400 and 110 a.c. 60 cycle	125-150- 175-200 20 watts	Tube	Input condenser

All inputs 6.3 volts d.c. unless otherwise noted.

¹ VP-553 same with tube rectifier.

² In weatherproof case. 4201B2 same with tube rectifier.

³ 180-cycle vibrator, lightweight. 4204 same without filter.

⁴ 601 same with tube rectifier; 602 same except 12 v. d.c. input and tube rectifier; 603 same except 32 v. d.c. input and tube rectifier.

⁵ VP-554 same with tube rectifier; VP-G556 same except 12 v. d.c. input; VP-F558 same except 32 v. d.c. input.

⁶ 4200D same with tube rectifier; 4200DF same with tube rectifier and output filter.

⁷ 551 same with 12 v. d.c. input.

⁸ Also available without filter.

⁹ 511 same except 12 v. d.c. input.

¹⁰ Input 6 v. d.c. or 110 v. a.c.; 607 same except 12 v. d.c. or 110 v. a.c. input; 608 same except 32 v. d.c. or 110 v. a.c. input; 609 same except 110 v. d.c. or 110 v. a.c. input.

TABLE III—DYNAMOTORS

Manufacturer's Type No.			Input		Output		Weight
Carter	Eicor	Pioneer	Volts	Amps.	Volts	Ma.	Lbs.
210A			6	6.1	200	100	6½
MA250	102 ¹	E1W272 ²	6	4.2	250	50	6½
251A		E1W332 ³	6	7.9	250	100	6½
301A	106 ¹	E2W351 ⁵	6	9.7	300	100	6½
315A	158 ⁶	E2W243 ²	6	13.4	300	150	7¾
320A		RAOW158 ⁷	6	10.2	300	200	9½
MA301			6	9	300	100	
351A			6	10.9	350	100	6½
355A	108	E2W256 ⁵	6	14	350	150	7¾
352A			6	22	350	200	9½
401A			6	13	400	100	7¾
		E2W4 8	6	14.2	400	125	9¼
415A	109 ⁴		6	18.2	400	150	7¾
420A			6	23.4	400	200	9½
425A		RA1W201 ⁹	6	26.4	400	225	9½
V450			5.5	29	400	250	
A430			6	31	400	300	13
		E3W413	6	15	500	100	11
520AS		RA1W189 ¹²	6	27.4	400	250	—
A650			6	40	600	250	13
AFS630			6	45.4	600	300	13
BS30050			12	25	3000 1500	50 100	

¹ Input current 4.6 amp.; wt. 4½ lbs.

² Wt. 7½ lbs.

³ Input current 7.5 amp.; wt. 7½ lbs.

⁴ Wt. 5 lbs.

⁵ Wt. 9¼ lbs.

⁶ Input current 14 amp.; wt. 5¾ lbs.

⁷ Wt. 16 lbs.; input current 18 amp.

⁸ Input current 17 amp.

⁹ Wt. 17½ lbs.; input current 25 amp.

¹⁰ Input current 27.5 amp.; wt. 7¾ lbs.

¹¹ Input current 21.5 amp.; wt. 7¾ lbs.

¹² Input current 27 amp.; wt. 17½ lbs.

TABLE IV—GASOLINE-ENGINE-DRIVEN GENERATORS, AIR-COOLED

Manufacturer				Output		Weight	Starter	
Eicor	Kato	Onan	Pioneer	Volts	Watts	Lbs.		
3AP6 ¹			BD-6 ¹	110 a.c. or 6 d.c.	300 200	100	Push-button	
	JR-35 ²			110 a.c.	300	65	Push-button	
	JRA-3 ²			110 a.c.	350	65	Rope crank	
	19-A			110 a.c. or 6 d.c.	350 200	95	Push-button	
		358 ^{1, 2}			115 a.c.	350	91	Push-button
	JR-10 ²				110 a.c.	400	—	Rope crank
6AP1	14A	5L ³		110 a.c.	500	165	Push-button	
				110 a.c. or 6 d.c.	500 200	105	Push-button	
			BA-6 ¹	110 a.c.	600	135	Push-button	
10AP1	26A	7L ³		115 a.c.	750	195	Push-button	
		10L ^{3, 4}		110 a.c.	1000	170	Push-button	
				110 a.c.	1000	265	Manual	
		OTC		110 a.c.	1500	135	Manual	
			BA-15	110 a.c.	1500	365	Push-button	

¹ Also available in remote-control models.
² Intermittent-duty model.

³ Also available in manual-started type.
⁴ 115-volt output; weight 200 lbs.

good electrical contact. The general construction should be quite apparent from the photographs. The bottom is provided with rubber feet, and the top has a small knob at each end so that it can be pushed out. This is essential, since the fit is good and there is no way to get either the top or bottom off, once on, without having some sort of handle to grip.

☞ Charging Storage Batteries

If access to a.c.-operated chargers is not possible at times between actual use, some form of self-powered charging system is essential.

This need is ordinarily best met by a gasoline- or wind-driven generator. Water-power generators have been used, but their dependence on special circumstances is obvious, and they are not available in small sizes.

The windcharger consists of a small generator driven by a suitable impeller, mounted to take advantage of the free energy offered by the wind. The standard type will supply up to 16 amperes to a 6-volt battery. It will ordinarily keep fully charged a battery used to power a typical receiver and small transmitter operated from vibrator or genemotor supply in intermittent operation.

Gasoline-driven generators are also available for use in charging 6-volt or larger batteries. These ordinarily are rated at 150 or 200 watts. A ½- or ¾-h.p. single-cylinder four-cycle engine is used, which will operate for twelve or fifteen hours on a gallon of gasoline.

☞ Gasoline-Engine-Driven Generators

For higher-power installations, such as for communications control centers during emergencies, the most practical form of independent power supply is the gasoline-engine-driven generator which provides standard 115-volt, 60-cycle supply.

Such generators are ordinarily rated at a minimum of 250 or 300 watts. They are available up to two kilowatts, or big enough to handle the highest-power amateur rig. Most are arranged to charge automatically an auxiliary 6- or 12-volt battery used in starting. Fitted with self-starters and adequate mufflers and filters, they represent a high order of performance and efficiency. Many of the larger models are liquid cooled, and they will operate continuously at full load. Ratings of typical gas-engine-driven generator units are given in Table IV.

A variant on the generator idea is the use of fan-belt drive. The disadvantage of requiring that the automobile must be running throughout the operating period has not led to general popularity of this idea amongst amateurs. Such generators are similar in construction and capacity to the small gas-driven units.

The home construction of generators of all the above types has been successfully attempted by amateurs at times, although the possession of a considerable knowledge of electric motor design is essential. One especially useful possibility is the rewinding of old automobile charging generators, several hundred watts capacity being obtainable from the largest sizes. Those originally used on the old 4-cylinder Dodge cars have been successfully adapted by amateurs. Trade schools will often have their students rewind these generators for only the cost of the material, and this possibility is worth investigating.

The output frequency of an engine-driven generator must fall between the relatively narrow limits of 50 to 60 cycles if standard 60-cycle transformers are to operate efficiently from this source. A 60-cycle electric clock provides a means of checking the output frequency with a fair degree of accuracy. The clock is connected across the output of the generator

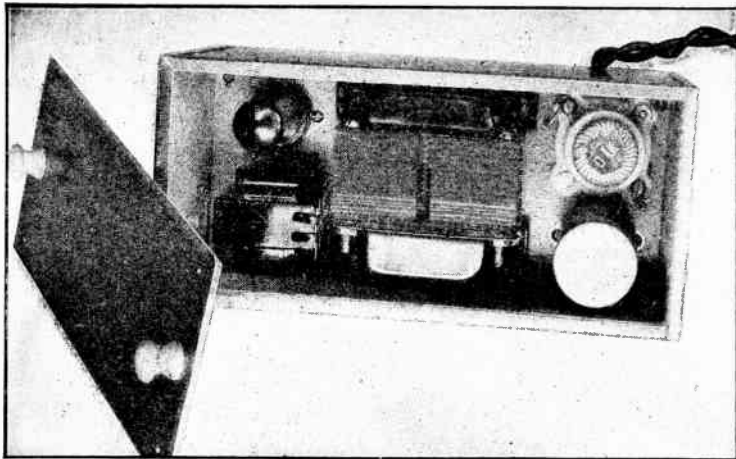


Fig. 1802 — A view inside a typical vibrator-type power-supply. The rectifier tube is at the upper left with the filter choke just below. The primary fuse socket and vibrator are at the right. A synchronous-type vibrator may be substituted for the interrupter-type if it is desired to eliminate the rectifier tube.

and the second hand is checked closely against the second hand of a watch. The speed of the engine is adjusted until the two second hands are in synchronism. If a 50-cycle clock is used to check a 60-cycle generator, it should be remembered that one revolution of the second hand will be made in 50 seconds and the clock will gain 4.8 hours in each 24 hours.

Output voltage should be checked with a voltmeter since a standard 115-volt lamp bulb, which is sometimes used for this purpose, is very inaccurate. Tests have shown that what appears to be normal brilliance in the lamp may occur at voltages as high as 150 if the check is made in bright sunlight.

⌚ Noise Elimination

Electrical noise which may interfere with receivers operating from engine-driven a.c. generators may be reduced or eliminated by taking proper precautions.

The most important point is that of grounding the frame of the generator and one side of the output line. The ground lead should be short to be effective, otherwise grounding may actually increase the noise. A water pipe may be used if a short connection can be made near the point where the pipe enters the ground, otherwise a good separate ground should be provided.

The next step is to loosen the brush-holder locks and slowly shift the position of

the brushes while checking for noise with the receiver. Usually a point will be found (almost always different from the factory setting) where there is a marked decrease in noise.

From this point on, if necessary, by-pass condensers from various brush holders to the frame, as shown in Fig. 1804, will bring the hash down to within 10 to 15 per cent of its original intensity, if not entirely eliminate it. Most of the remaining noise will be reduced still further if

the high-power audio stages are cut out and a pair of headphones are connected into the second detector.

⌚ High-Frequency Equipment

The use of high-frequency equipment for the handling of all intra-community emergency communications is recommended not only for the purpose of limiting the interference range but also because equipment for these frequencies may be built in easily-portable form. Low-power transceivers and transmitter-receivers in the form of glove-compartment units, walkie-talkies and handie-talkies find ready application in this type of work.

Glove-compartment units and other forms of mobile installations may be operated readily from a vibrator supply or genemotor connected to the car storage battery, although a separate battery is recommended for protracted operating periods, such as in an emergency, to

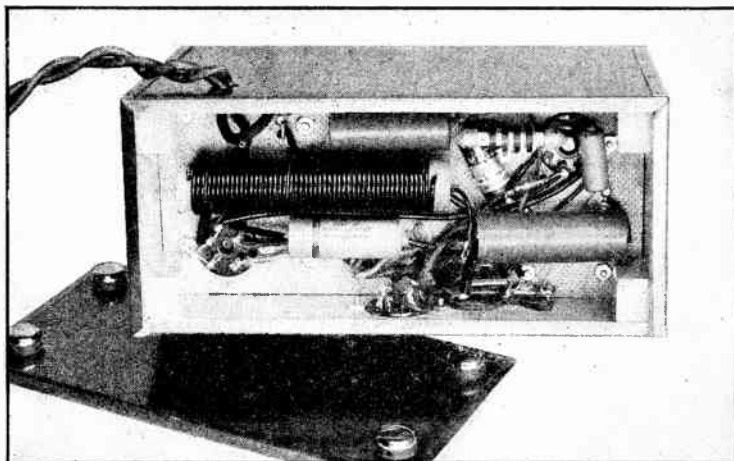


Fig. 1803 — Hash and smoothing filter components are mounted in the bottom of the low-voltage vibrator power supply. The 4-prong outlet socket is mounted on the side.

guard against discharging the car battery to the point where it will no longer start the car. The usefulness of a mobile unit in emergencies is apparent, since it constitutes a self-powered installation which may be placed in a strategic location with a minimum loss of time.

Handie-talkies and walkie-talkies, on the other hand have the advantage that they may be brought to points which for one reason or another may be inaccessible to a car. Handie-talkies universally operate from self-contained dry batteries, while the heavier walkie-talkie units may be designed to operate from either dry batteries or a small storage battery of the motorcycle type and a vibrator unit. In some cases, it may be desirable to build the power supply as a separate unit so that the weight which must be carried to the scene of an emergency may be distributed between two persons.

Higher-powered transmitters and more elaborate equipment of the type often used as permanent station equipment operating from a.c. are desirable as control-station equipment if a suitable source of power is available.

Portable Equipment — Low-Frequency

The weakest unit in a low-frequency portable or emergency communications installation often is the receiver.

An inadequate receiver, with poor selectivity, low sensitivity and insufficient stability, can ruin a QSO even under favorable conditions. When it is remembered that conditions in portable or emergency operation are often more severe than those at home, with poor antenna facilities, high noise levels, severe interference, etc., the fallacy of attempting to use an inferior portable receiver is apparent.

The best procedure of all is to use the home-station receiver for portable work. Headphones should be used and the output tube removed (if it isn't necessary for headphone operation), but this is no hardship. Headphones are far more satisfactory in such applications than the speaker in any event. This procedure not only ensures the availability of the high-performance receiver so vitally necessary, but the practice that has been obtained by using the receiver at home is invaluable in the specialized operating techniques of portable or emergency work. It takes as much experience to learn to run a receiver properly as it does to drive a car, and the middle of a crisis is no time to gain that experience. Even on lowered plate voltage the home superhet will be better than a makeshift.

If a special portable/emergency receiver is to be built, it should be a superheterodyne. With present-day tubes and components, it is possible to build a simple superheterodyne as cheaply as a t.r.f. receiver, and there is no comparison between the two in performance. The average communications superheterodyne can be operated with storage-battery heater supply and dry-cell or vibrator-pack "B"

supply. With the audio power tubes removed from the receiver, the power requirements are not too great. Some of the receivers on the amateur market have provision at the rear of the set for plugging in a d.c. supply, and those which do not can be easily modified by drilling a socket hole at the rear of the receiver and wiring it into the set. When regular a.c. operation is used, a plug in the socket completes the circuit.

The design of low-frequency transmitters for emergency, portable and rural transmitters, will depend almost entirely upon the power supply available. Considering possible defects in hastily-improvised radiation systems, etc., it seems unwise to use less than 10 watts input to a power amplifier or 15 watts to an oscillator.

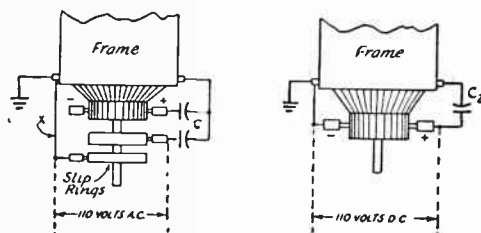


Fig. 1804 — Connections used for eliminating interference from gas-driven generator plants. C should be 1 μ f., 300 volts, paper, while C_2 may be 1 μ f., with a voltage rating of twice the d.c. output voltage delivered by the generator. "X" indicates an added connection between the slip ring on the grounded side of the line and the generator frame.

However, powers greater than two or three times these values are not usually necessary, so selection of the power supply will depend almost entirely upon the pocketbook and other resources. The 300-volt, 100-ma. vibrator supplies and genemotors represent a nice compromise unless it is possible to step into the 200- or 300-watt gasoline-driven generator class.

Perhaps the best plan in providing for an emergency and portable transmitter is to utilize the basic exciter unit in the regular station. This not only ensures the availability of a reliable, efficient unit at all times but means a saving in parts and equipment. It represents no hardship to the permanent station to construct the exciter so it is compact, readily removable, and, above all, solidly and dependably assembled. If your present exciter is not adaptable to this use, plan the new one so it will be. Provision for 6-volt tubes throughout is essential, with the heater circuit so arranged that it can be connected to a storage battery without change. A suitable plate supply using a vibrator or genemotor or similar system should be available separately, arranged for ready connection. The best method is to have a socket and plug connector assembly, with one plug built into the transmitter and another, wired identically, connected permanently to the emergency supply.

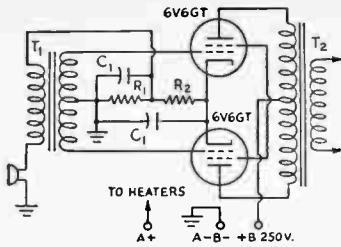


Fig. 1805 — Simple modulator for portable and general-utility work.

C_1 — 10- μ fd. 25-volt electrolytic.

R_1 — 100 ohms, 1-watt.

R_2 — 150 ohms, 1-watt.

T_1 — Input transformer (Thordarson T-83A78).

T_2 — Output transformer (Thordarson T-19M13).

□ A Simple Modulator for Portable Work

The circuit diagram of a simple modulator for portable or mobile work is shown in Fig. 1805. In this arrangement the microphone is used directly to drive a pair of 6V6GT modulators without intermediate speech amplifiers. Such a modulator works surprisingly well to modulate Class-C inputs up to 25 watts. The unit requires 75 to 100 ma. at 200 to 300 volts. Voltage for the single-button carbon microphone is taken from the junction of the two cathode-biasing resistors, R_1 and R_2 , thus eliminating the necessity for bulky microphone batteries. These two resistors could be replaced by a single resistor with a sliding contact. One side of the heater circuit is grounded so that only three power-supply wires are required. The complete unit may be assembled on a small chassis.

□ High-Frequency Antennas

In many cases, particularly at control stations, it will be necessary to use non-directive antennas because of the necessity for working field stations at random points of the compass. At field stations which normally work with only a single control station, however, it may be advantageous to use a simple form of directive array. The power gain will be worth while in bettering the signals in both directions, and in addition will minimize interference to and from other networks. The simpler forms of antennas described in Chapters Ten and Seventeen are quite suitable.

More important, perhaps, than the antenna itself is its location. Every effort should be made to get the antenna well above its surroundings and to provide, whenever possible, a clear path between the control station and the network stations with which it must communicate. Having a line of sight between antennas will ensure successful communication even though the power is very low and the antenna itself is nothing more than a simple half-wave wire. Where there are intervening obstructions, it will be helpful to use as much height as possible.

Vertical polarization is to be preferred to horizontal, since vertical polarization is better

suited to mobile operation. A simple vertical antenna has practically no horizontal directivity, therefore it will work equally well in all directions except for effects attributable to its surroundings and to the terrain over which the signal must travel. The signal strength will be poor if a horizontally polarized antenna is used to receive a vertically polarized signal.

A half-wave antenna, two half waves fed in phase stacked vertically, or an extended double Zepp, all will be satisfactory, and are very simple types to construct. Design details will be found in Chapter Ten. If the station is to be operated on a fixed frequency, the antenna length should be adjusted for that frequency. If the same antenna is to work on several frequencies, the length had best be chosen midway between the two extremes.

Mobile antennas — It is probable that most networks will have one or more stations installed in cars, for dispatching to points which may be in urgent need of communication. The equipment previously described is readily adaptable to car installations; the transceiver, in particular, can be set up with little difficulty, and can get its power from the car broadcast receiver, if there is one. This would require only the installation of a suitable power socket in the car receiver, together with a switch to cut the power from the receiver when the transceiver is in use. Antennas suitable for such mobile installations are described in Chapter Seventeen.

For a solid but easily detachable mounting for a mobile antenna, the arrangement shown in Fig. 1806 is suggested. It is held in place by a panel of wood, cut to the shape of the window,

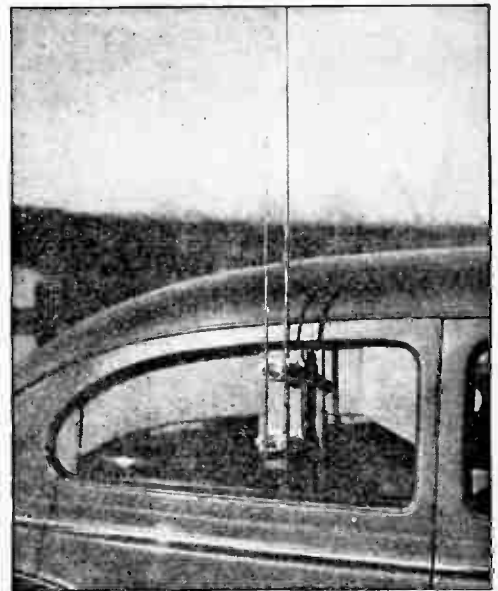


Fig. 1806 — A J-type antenna for 141-Mc. mobile operation can be mounted easily in the window of a car, allowing the radiator proper to be placed above the roof of the vehicle. The dimensions are given in the text.

on which the antenna is mounted. By running up the window the panel is held firmly in place. The antenna is of the "J" type. This type of installation places the radiator proper above the roof of the car, and has the advantage that it can be readily removed from the car when not in use or when needed elsewhere. Fig. 1808 shows a folded doublet.

The unit shown is built of $\frac{1}{4}$ -inch plywood, since the usual thickness of the window glass in cars is $\frac{1}{4}$ inch. Run down the window of the car about half way, or enough to leave at least a 6-inch opening, and make a pattern of cardboard using the top edge of the window glass for the guide. Trim the cardboard to this shape, and then push it up in the window and use the edge of the glass to mark the bottom edge of the pattern. From the pattern, mark the piece of plywood and cut it out with a saw. Additional small pieces to form stops in the corners are fastened to the main piece with glue and brads. A piece of plywood about $6 \times 8\frac{1}{2}$ inches should be fastened to the large piece at the point where the antenna is to be supported, using glue and brads, and the four stand-off insulators which support the antenna bolted to this piece. If the insulators are not long enough for the antenna to clear the side of the car, they can be raised by wood strips.

Two small strips should be nailed along the inside of the main piece so that they extend down below the edge a few inches and form, with the outside pieces, a yoke to keep the assembly in the proper position on the window.

The feeder can be made of flexible rubber-covered wire (obtained by splitting a length of parallel lamp cord) separated by small plastic or dry wood spacers. The antenna ends of the wires are soldered to the heads of the large bolts in the upper stand-off insulators, and the wire is run out through holes in the wood.

The antenna and matching-section rods are regular automobile whip antennas and are supported on the stand-off insulators by small loop-shaped metal clamps. The shorting bar is made along the same lines, with bars of heavy metal on both sides of the clamp loops.

The length of the half-wave "J" antenna itself should be 38 inches for a frequency of 146 Mc. — the center of the two-meter band. Since the length of the matching section should be a quarter wave-length, or 19 inches, the total length of the right-hand element shown in Fig. 1806 should be 57 inches, while the shorter left-hand element should be 19 inches long. The spacing between elements should be 2 inches. With an open-wire transmission line consisting of two No. 18 wires spaced 2 inches, the line should be connected $5\frac{1}{2}$ inches up from the shorting bar at the bottom of the elements.

The folded-doublet antenna shown in Fig. 1808 is another simple type of antenna which may be adapted for mobile use, especially where center feed is more convenient. It has the advantage of rather broad-band characteristic and moderately-high impedance at the

feeding point. It should have an over-all length of 38 inches for 146 Mc.

Ⓒ A Car-Roof Antenna

Fig. 1807 shows a sketch of a fitting for a vertical v.h.f. car-roof antenna which provides a good mechanical arrangement for folding the antenna parallel to the car roof when the antenna is not in use.

The pieces *A* and *B* are made from sections of brass rod $\frac{3}{4}$ inch in diameter. One end of piece *A*, which has an over-all length of $3\frac{1}{2}$ inches, is turned down for a length of 2 inches to the diameter required to fit the inside of the bottom of the tubular antenna, which is soldered fast. At the other end of piece *A* is cut a tongue, 1 inch long and $\frac{1}{4}$ inch wide as shown in sketch.

Piece *B* has an over-all length of 6 inches. One end is turned down and threaded with a $\frac{3}{4}$ -inch die, while a slot, 1 inch deep and $\frac{1}{4}$ inch wide to fit the tongue of *A*, is cut in the opposite end. The slotted end is then drilled and tapped on one side of the slot for a $\frac{1}{4}$ -inch thumb screw, *C*. A vertical elongated hole is drilled and filed out in the tongue of piece *A*, so that, with the thumb screw loosened, *A* can be lifted up slightly to clear the shoulders of *B* while the antenna is being folded down. The solid seating of the two pieces, *A* and *C*, against each other

when the antenna is erected in a vertical position provides little opportunity for the joint to work loose under vibration.

The threaded shank of piece *B* passes through a hole in the roof of the car. The polystyrene washers, *D* and *E*, provide the necessary insulation. Each is 2 inches in diameter and $\frac{1}{4}$ inch thick and has a collar or hub $\frac{1}{4}$ inch thick turned on one side to fit the hole in the car roof. The assembly is clamped to the roof of the car by means of the locking nuts either side of *F*. *F* is a soldering lug for making the connection to the antenna.

If the assembly is placed near the forward part of the roof, a two-meter half-wave antenna may be folded back at the hinge when not in use without the antenna overhanging the rear of the car.

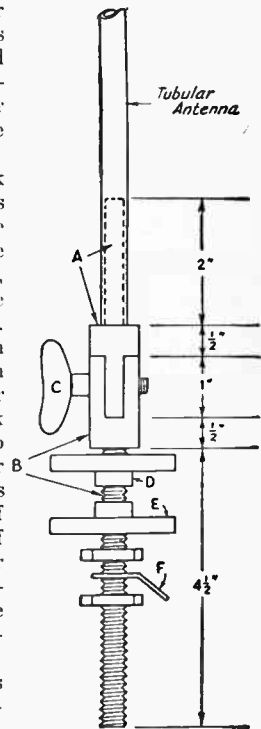


Fig. 1807 — Feed-through insulation and fittings for the folding car-roof mobile antenna. The joint hinges at *C* so that the antenna may be folded down parallel to the roof of the car.

Low-Frequency Emergency Antennas

Any of the simple low-frequency antennas described in Chapter Ten, or modifications of them, should be suitable for low-frequency portable and emergency work. End-fed antennas of the simple voltage-fed or Zepp types probably are the easiest to erect, although a center-fed antenna is more tolerant as to dimensions so long as the entire system including the feeders can be tuned to resonance. With such a center-fed arrangement, the feeders will stay in balance, even though the antenna portion of the system is much less than a half-wavelength long.

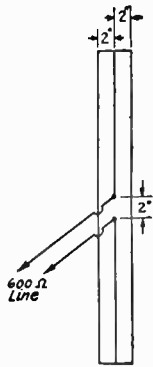


Fig. 1808 — Three-wire folded-doublet antenna for matching a 600-ohm line. The three conductors are connected together at the ends, as indicated. They may be made of wire, rod or tubing, and can be mounted on stand-off insulators on a wooden support.

For portable work at low frequencies a compact antenna which has been used successfully at 3.5 Mc. consists of about 60 feet of No. 18 enameled wire wound in a spiral around a long bamboo fishing pole. The turns are space-wound over the top 14 feet of the pole and then close-wound for about three feet. The remaining length of the pole is left free so that it may be lashed to a tree or other convenient upright, or simply stuck in the ground when no support is available. The bottom end of the winding is connected through an antenna tuner to ground.

The pi-section antenna coupler described in Chapter Ten and the pi-section tank circuit shown in Fig. 1302, Chapter Thirteen, are good devices for coupling random lengths of wire to either transmitter or receiver. An antenna of this type may be erected by tying a weight to one end of the wire and tossing it into a tree or over some other possible elevated support.

Transmission lines — At nearly all fixed locations it will be necessary to use a transmission line between the antenna and the radio equipment, since the latter will be indoors where it is easily accessible while the former will be placed on the roof of the building to secure adequate height. Low-loss concentric line is ideal for working into the center of a half-wave antenna, but there is little likelihood it can be obtained except in isolated instances. The alternative is an open-wire line

having an impedance of 500 to 600 ohms. It is advisable to keep the spacing between wires small, to prevent radiation loss; 2-inch spacing is about right, provided the line can be installed fairly rigidly so that it will not swing in a breeze and cause the transmitter frequency to change. This close separation also requires a fairly large number of spacers — at intervals of perhaps three to four feet.

To make such a line nonresonant it will be necessary to install a matching stub at the antenna. The design and adjustment of such stubs also is covered in Chapter Ten. As an alternative, a multi-wire doublet antenna may be used to couple directly to a line having an impedance of the order of 500 to 600 ohms without special matching provisions. Such an antenna is shown schematically in Fig. 1808. It gives a 9-to-1 impedance step-up at the line terminals, hence practically automatic matching to a 600-ohm line, assuming the normal doublet impedance of 70 ohms. In addition, it has a broad resonance characteristic and therefore is well suited to working anywhere in the band.

To avoid the necessity for impedance matching, two-wire lines may be operated as tuned lines if desired. Such operation has been successful with lines up to at least 100 feet long. Since in most cases the coupling device at the transmitter or receiver is a single-turn coil, the simplest method of tuning the line is to adjust the feeder length until the current in the line is maximum when the transmitter is operating on the chosen frequency. A small dial light or flashlight bulb, connected in series with one side of the line right at the transmitter terminals, may be used as a current indicator. The transmission line should be made about four feet longer than necessary, its length being adjusted by cutting off an inch or two at a time until maximum bulb brilliancy is obtained.

From a constructional standpoint it is desirable to use the same antenna for both transmitting and receiving. The change-over switch for this purpose should have low capacity, and preferably should have low-loss insulation. The ordinary type of wafer switch is satisfactory, particularly if it is ceramic insulated. A small porcelain-base d.p.d.t. knife switch also may be used for this purpose. If possible, the antenna switch should be combined mechanically with the power-supply change-over switches for the transmitter and receiver so that all the necessary switching from transmission to reception can be done in one simple operation.

Measurements and Measuring Equipment

TO COMPLY with FCC regulations it is necessary that the amateur station be equipped to make a few relatively simple measurements. For example, the regulations require that means be available for checking the transmitter frequency to make sure that it is inside the band. This means must be independent of the frequency control of the transmitter itself; it is not enough to depend on, say, the calibration of a crystal in the crystal-controlled oscillator that drives the transmitter. In addition, it is necessary to make sure that the plate power input to the final stage of the transmitter does not exceed one kilowatt. The regulations also impose certain requirements with respect to plate-supply filtering, stability and purity of the transmitted signal, and depth of modulation in the case of 'phone transmission.

In many cases all these measurements can be made to a satisfactory degree of accuracy with no more auxiliary equipment than the regular station receiver. However, a better job usually can be done by building and calibrating some relatively simple test gear. Too, the progressive amateur is interested in instruments as an aid to better performance.

Fundamentally, the process of measurement is that of comparing a quantity with a reference standard. Measuring equipment divides into two types: (1) fixed standards giving a reference point of known accuracy, used with associated equipment for making comparisons between the known and unknown quantities, and (2) direct-reading instruments or meters which have previously been calibrated in terms of the quantity being measured.

Methods of making the measurements required in the amateur station will be discussed in this chapter, and design and construction of representative types of the instruments used in making these measurements will be described.

Frequency Measurement

Frequency-measuring equipment can be divided into two broad classes: oscillators of various types that generate signals of known frequency that can be compared with the signal whose frequency is unknown, and adjustable resonant circuits.

Instruments in the first classification are the more accurate. Two types are commonly used by amateurs, the *secondary frequency standard* and the *heterodyne frequency meter*. The secondary frequency standard, nearly always crystal-controlled, usually generates a frequency of 100 kc. and employs a circuit that is rich in harmonic output. As a result, it supplies a series of frequencies, all multiples of 100 kc., which provide accurate calibration points throughout the communications spectrum. The more elaborate instruments of this type are provided with frequency dividers (multivibrators) to supply intermediate calibration points; a divisor commonly used is 10, thus furnishing signals at intervals of 10 kc. when the fundamental frequency is 100 kc.

The heterodyne frequency meter is a variable-frequency oscillator which is calibrated in frequency against a secondary standard or by other means. The oscillator usually is designed to cover the lowest frequency band in which measurements are to be made; measurements then can be made in higher-frequency bands by using the harmonic output of the oscillator. For example, when the oscillator is set to 3560 kc. its second harmonic is 7120 kc., its fourth harmonic is 14,240 kc., and so on. The proper frequency reading is determined by knowing the fundamental frequency of the oscillator and the number of the harmonic which falls in the desired frequency range.

Both the secondary standard and the heterodyne meter are ordinarily used in conjunction with a receiver, the signals from the instruments being picked up just as though they were from distant stations. In the case of the secondary standard, the frequency of the unknown signal can be determined by locating it between two known 100-ke. or 10-ke. multiples. With the heterodyne meter, the frequency is measured by adjusting the frequency meter until its signal is at zero-beat with the signal of unknown frequency, after which the frequency can be read from the frequency-meter calibration.

Since the secondary standard operates on a fixed frequency and can be crystal controlled, its accuracy can be quite high. However, it simply establishes a series of known frequencies at regular intervals, and thus auxiliary meth-

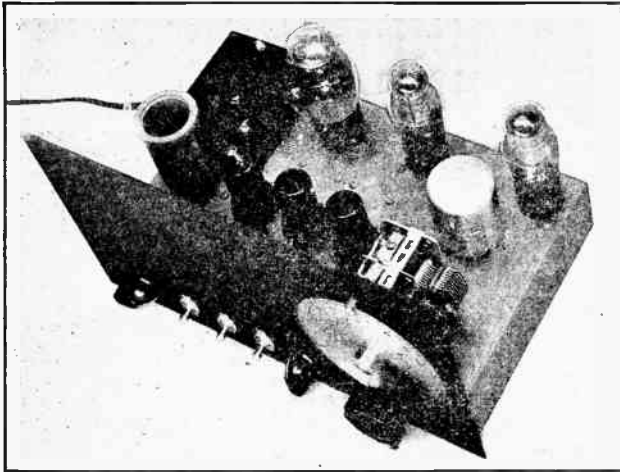


Fig. 1901 — A secondary frequency standard, incorporating a 100-ke. low-drift crystal oscillator, a 10-ke. multivibrator, and a harmonic amplifier-modulator. Controls along the bottom are, left to right: output tuning, C_{14} ; on-off switch, S_1 ; "B" switch, S_2 ; multivibrator switch, S_3 , and multivibrator control. R_8 , Power transformer, rectifier and regulator tubes are along the rear edge of the 7×12 -inch chassis. The crystal oscillator is at the right, multivibrator tube in the center, and output circuit at the left. The output circuit is tuned to the band in use, with output taken either through C_7 or a link winding. Output coupling is adjusted to give desired signal strength in the receiver. The crystal frequency can be adjusted to precisely 100 ke. by the vernier dial controlling C_1 . Switching the multivibrator section on or off will cause a frequency change of less than 1 part in a million.

ods must be used for determining frequencies between the known points. The series of fixed frequencies, when they mark the edges of amateur bands (as they do if they are multiples of 100 ke.), is quite sufficient for amateur work because the information that is required is whether or not the transmitter frequency is *inside* the band limits, rather than the exact frequency itself. On the other hand the heterodyne frequency meter, while capable of giving readings at any point in its calibrated range, is inherently less accurate than the crystal-controlled standard because of the lower stability of the variable-frequency oscillator.


In the absence of more elaborate frequency-measuring equipment, a calibrated receiver may be used to indicate the approximate frequency of the transmitter. If the receiver is well made and has good inherent stability a handsread dial calibration can be relied upon to within perhaps 0.2 per cent. Some manufactured receivers having factory calibration may

be used to even closer limits. For most accurate measurement maximum response in the receiver should be determined by means of a carrier-operated tuning indicator (S meter), the receiver beat oscillator being turned off.

When checking the transmitter frequency the receiving antenna should be disconnected, so that the signal will not overload or "block" the receiver. If the receiver still blocks without an antenna the frequency may be checked by turning off the power amplifier and tuning in the oscillator alone.

Secondary frequency standard — Amateur requirements for high-accuracy frequency checking, as well as for calibration of auxiliary frequency-measuring equipment, are best met by a crystal-controlled secondary standard. With a 100-ke. crystal, band edges as well as intermediate 100-kilocycle intervals can be marked quite accurately through the use of harmonics. Furthermore, if the standard is provided with a 10-ke. multivibrator for fre-

Fig. 1902 — Circuit diagram of the precision low-drift crystal-controlled 100-ke. secondary frequency standard.

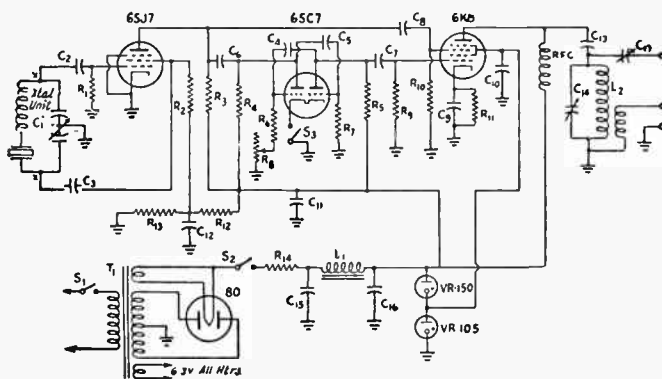

T₁ — Power transformer, 250 volts, 40 ma. L₁ — 7-henry, 40-ma. filter choke. L₂ — Specifications below.

550-1200 Kc. 130 turns No. 30 enamel.
1200-3300 Kc. 70 turns No. 22 enamel.
3.3-7.5 Mc. 22 turns No. 22 enamel, length 1 inch.

- C₁ — Dual 365- μ fd. variable.
- C₂, C₃ — 0.01- μ fd. 400-volt paper.
- C₄, C₅ — 0.001- μ fd. midget mica.
- C₆, C₇ — 10- μ fd. midget mica.
- C₈ — 50- μ fd. midget mica.
- C₉, C₁₀, C₁₁, C₁₂ — 0.1- μ fd. 400-volt.
- C₁₃ — 0.002- μ fd. midget mica.
- C₁₄ — 110- μ fd. variable.
- C₁₅, C₁₆ — 8- μ fd. 450-volt electrolytic.
- C₁₇ — 3-30- μ fd. mica trimmer.
- R₁ — 1 megohm, $\frac{1}{2}$ -watt.
- R₂, R₃ — 0.5 megohm, 1-watt.
- R₄, R₅ — 50,000 ohms, 1-watt.
- R₆, R₇ — 20,000 ohms, $\frac{1}{2}$ -watt.
- R₈ — 15,000-ohm potentiometer.
- R₉ — 0.3 megohm, $\frac{1}{2}$ -watt.
- R₁₀ — 0.1 megohm, $\frac{1}{2}$ -watt.
- R₁₁ — 800 ohms, $\frac{1}{2}$ -watt.
- R₁₂ — 25,000 ohms, 1-watt.
- R₁₃ — 50,000 ohms, 1-watt.
- R₁₄ — 1500 ohms, 10-watt.
- RFC — 2.5 mh. r.f. choke.
- S₁, S₂, S₃ — S.p.s.t. toggle.

6.8-15 Mc. 11 turns No. 22 enamel, length 1 inch.
13.5-32 Mc. 5 turns No. 22 enamel, length 1 inch.
All coils wound, on $\frac{1}{2}$ inch diameter forms.

quency division, calibration points can be obtained at 10-kilocycle intervals throughout the entire high-frequency spectrum up to the limit at which harmonics become too weak to be usable. It is readily possible to use harmonics from a 100-ke. crystal up to at least 30 megacycles.

Such a standard can be constructed at quite reasonable cost. An instrument of this type is illustrated in Figs. 1901-1903, inclusive. The frequency control is a Bliley SOC-100 unit, consisting of a low-drift 100-ke. bar with an oscillator coil in the same mounting. The oscillator tube is a 6SJ7, used in the circuit recommended for this crystal unit by the manufacturer. The output of the oscillator is coupled to a 6K8 harmonic amplifier through C_8 , Fig. 1902, and also to the 6SC7 multivibrator (a resistance-capacitance oscillator of the relaxation type) through C_6 . The multivibrator fundamental frequency is 10 kc. and it is locked at this frequency by the 100-ke. output of the crystal oscillator. The output of the multivibrator, consisting of 10 kc. plus a series of harmonics, is used to modulate the 6K8 output by coupling to the injection grid. This gives a series of 10-ke. signals between each pair of 100-ke. harmonics. The oscillator plate electrode in the 6K8 is not used.

The output circuit of the 6K8 is tuned to the particular frequency on which checking is to be done. This increases the harmonic output at that frequency. Plug-in coils are provided to cover the range from 550 kc. to 32 Mc. The output may be taken either from the small coupling condenser, C_{17} , or from a link winding on each coil. Sufficient coupling to the receiver usually will be obtained if a wire connected to C_{17} is simply brought near the receiving antenna lead-in.

A power supply is incorporated in the unit, with its output voltage regulated by means of the VR-150-30 and VR-105-30 tubes. The voltage regulation prevents changes in oscillator frequency with varying line voltage.

The crystal frequency can be adjusted to precisely 100 kc. by beating the output on 5000 kc. against the continuous transmissions on this frequency from WWV. After a warm-up period of 15 minutes or so, the frequency should stay within a few cycles of WWV over considerable periods of time. The multivibrator can be cut out of the circuit by means of S_3 when only 100-ke. points are wanted. A "B" switch, S_2 , is provided so that the unit may be made inoperative without cutting off the heater voltage.

Identification of 100-ke. points is sometimes difficult unless the receiver is already provided with a fairly accurate frequency calibration. On the other hand, it is easy to

WWV SCHEDULES

All U. S. frequency calibration is based on the standard frequency transmissions from the National Bureau of Standards standard-frequency station, WWV. This station is on the air continuously, day and night, its radio frequencies of 5, 10 and 15 Mc. (and 2.5 Mc. from 7 P.M. to 9 A.M. EST with 440-cycle modulation only) modulated by standard audio frequencies of 440 and 4000 cycles per second, the former corresponding to A above middle C. In addition, there is a 0.005-second pulse every second, heard as a faint tick, which provides an accurate time interval for purposes of physical measurements.

The audio frequencies are interrupted on the hour and every five minutes thereafter for one minute to give Eastern Standard Time in telegraphic code and to provide an interval for checking r.f. measurements. The station announcement is given by voice on the hour and half hour.

The accuracy of all frequencies is better than a part in 10,000,000. The 1-minute, 4-minute, and 5-minute intervals marked by the beginning and ending of the announcement periods are accurate to a part in 10,000,000. The beginnings of the periods when the audio frequencies are interrupted mark accurately the hour and the successive 5-minute periods.

identify a signal to the nearest megacycle on practically any receiver. It is therefore helpful to make provision for generating a frequency of 1 megacycle (1000 kc.) in the instrument for preliminary checking. For checking 1000-ke. points a coil of about 150 microhenrys ($1\frac{1}{2}$ -inch winding of No. 30 d.c.c. on a $1\frac{1}{2}$ -inch diameter form) may be substituted for the crystal unit, connecting it between points X-X in the diagram. The circuit will tune to 1000 kc. with C_1 near maximum capacity. The exact frequency may be set by adjusting so that the fifth harmonic coincides with WWV on 5 Mc.,

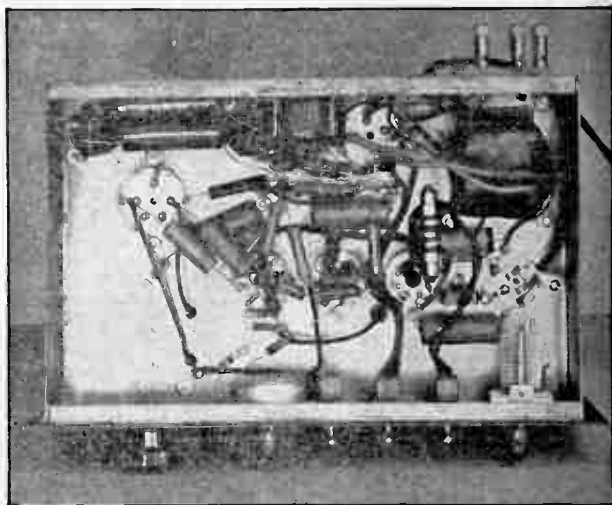


Fig. 1903 — Bottom view of the frequency standard. Reasonable care should be used to keep the circuits separated and leads short, but there are no critical wiring points. The filter choke is mounted on the rear edge of the chassis.

or so that the fundamental is at zero beat with a broadcast station on 1000 kc.

To adjust the multivibrator, first note the receiver dial readings for two adjacent 100-kc. harmonics with the multivibrator off. The receiver beat oscillator should be on, the tuning being adjusted for zero beat to obtain dial readings. Then turn on the multivibrator, set the frequency control, R_8 , at about half scale, and count the number of signals (zero-beat points) between the two marked 100-kc. points. If the number is other than nine (nine beats indicate 10-kc. intervals) readjust R_8 until nine are observed. In case the number of beats observed is considerably more than nine (possibly 18 or 20, some weaker than others) careful adjustment of R_8 should cause the spurious signals to disappear, leaving only the nine desired.

In using the standard for checking frequency, first locate the signal to be measured between two 100-kc. points with the multivibrator off. For example, it may be found that the signal lies between 7100 and 7200 kc. Then switch on the multivibrator and count the number of 10-kc. points between the lower of the two 100-kc. harmonics and the signal. Starting with 7100 kc. as zero, it may be found that six 10-kc. points are counted before the signal is reached. The frequency is therefore between 7160 and 7170 kc. A closer estimate of the frequency may be made by observing the number of receiver dial divisions between the 7160 and 7170 points. For instance, suppose there are six divisions between 7160 and 7170, and that the signal being measured is four divisions from 7160. The signal is therefore approximately $\frac{4}{6} \times 10$ kilocycles, or 7 kc. above 7160. Thus the frequency is 7167 kc.

100-1000-kc. frequency standard — A sim-

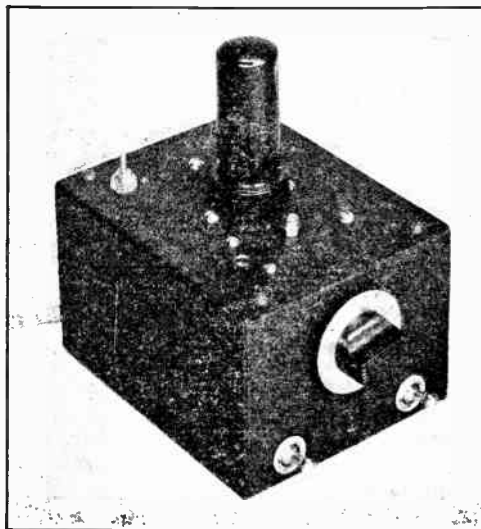


Fig. 1904 — 100-1000-kc. crystal calibrator. Output is taken through the insulated terminal bushing at left rear.

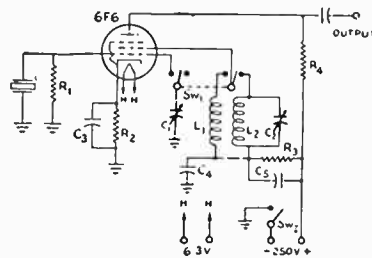


Fig. 1905 — Circuit diagram of a dual-frequency 100-1000-kc. crystal-controlled crystal calibrator.

- C₁ — 35- μ fd. midget variable (Hammarlund HF-35).
- C₂ — 100- μ fd. mica trimmer (Hammarlund CTS-85).
- C₃, C₄, C₅ — 0.1- μ fd. 400-volt paper.
- C₆ — 0.001- μ fd. midget mica.
- R₁ — 5 megohms, $\frac{1}{2}$ -watt.
- R₂ — 500 ohms, $\frac{1}{2}$ -watt.
- R₃ — 25,000 ohms, 1-watt.
- R₄ — 0.25 megohm, $\frac{1}{2}$ -watt.
- L₁ — 8-mh. r.f. choke (Meissner 1920-78).
- L₂ — 2.5-mh. r.f. choke (all but one pie removed).
- S₁ — D.p.d.t. toggle switch.
- S₂ — S.p.s.t. toggle switch.
- Crystal — Bliley SMC-100.

pler type of crystal-controlled frequency standard, using a special crystal capable of oscillating at either 100 or 1000 kc., is shown in Figs. 1904-1906, inclusive. This unit, which can be built at quite small cost, provides check points through the spectrum at 100-kc. intervals, sufficient for marking the edges of the amateur bands and for general calibration purposes.

The frequency of oscillation is shifted between 100 and 1000 kc. by tuning the oscillator tank circuit to the proper frequency. In the unit pictured, a d.p.d.t. toggle switch selects the desired frequency by making connection to either of two tank circuits. In the 100-kc. position this switch also connects a small trimmer condenser in parallel with the crystal. As the capacity of this condenser is increased the frequency of the crystal is lowered, so that if the crystal frequency is originally slightly high it becomes possible to set it to precisely 100 kc., as indicated by checking the 5-Mc. harmonic against WWV. In purchasing the crystal it should be specified that any error in frequency be on the high-frequency side of 100 kc.

The accuracy when the oscillator is operating on 1000 kc. is within 0.05 per cent. However, since this frequency is used only for identification of the 100-kc. harmonics, this amount of error is not important.

The oscillator output is taken through an insulated bushing from which a connecting lead can be run to the receiver input. Sw_2 opens the plate-supply lead when no signal is wanted; the heater is ordinarily left on continuously to keep the tube at operating temperature. Useful output may be obtained at harmonics up to about 30 Mc.

Heterodyne frequency meters — The basis of the heterodyne frequency meter is a completely shielded oscillator with a precise frequency calibration covering the lowest fre-

quency band in use. The oscillator must be so designed and constructed that it can be accurately calibrated and will retain its calibration over long periods of time.

The oscillator used in the frequency meter must be very stable. Mechanical considerations are most important in its construction. No matter how good the instrument may be electrically, its accuracy cannot be depended upon if the mechanical construction is flimsy. Inherent frequency stability can be improved by avoiding the use of phenolic compounds and thermoplastics (bakelite, polystyrene, etc.) in the oscillator circuit, and employing only high-grade ceramics for insulation. Plug-in coils or switches ordinarily are not acceptable; instead, a solidly built and firmly mounted tuned circuit should be permanently installed. The oscillator panel and chassis should be reinforced for rigidity.

To obtain high accuracy, the frequency meter must have a dial which can be read precisely to at least one part in 500; ordinary dials such as are used for transmitters and inexpensive receivers are not capable of such precision without the addition of vernier scales. Select a dial which has fine lines for division marks and an indicator close to the dial scale, so that the readings will not appear different because of parallax when viewed from different angles.

A stable oscillator circuit suitable for use in a heterodyne frequency meter is the electron-coupled circuit. The oscillation frequency is practically independent of moderate variations in supply voltages, provided the plate and screen voltages are properly proportioned, and it is possible to take output from the plate with but negligible effect on the frequency of the oscillator. A third feature is that strong harmonics are generated in the plate circuit.

A typical electron-coupled frequency meter is shown in Figs. 1907-1908. For convenience in checking the frequency of the transmitter or other local oscillators which generate suffi-

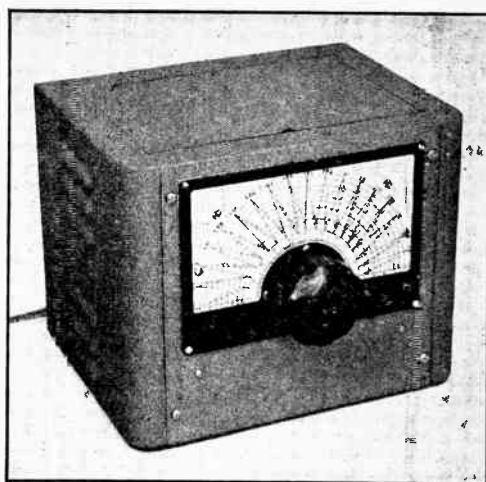


Fig. 1907 — Electron-coupled heterodyne frequency meter with harmonic amplifier and voltage regulator. The direct-reading dial is calibrated for every 10-kc. point from 1750 to 1900 kc. Axial lines passing through these points are intersected by ten semi-circular subdivision lines. Diagonal lines connecting the ends of adjacent 10-kc. lines, in conjunction with the subdivisions, enable reading the scale accurately to 1 kc. or better.

ciently strong signals, a detector is incorporated in the circuit of Fig. 1908 to combine the signals and deliver the audio beat-note output to headphones.

When the frequency meter is first turned on some little time is required for the tube to reach its final operating temperature, and during this period the frequency of oscillation will drift slightly. Although the drift will not amount to more than two or three kilocycles on the 3500-kc. band and proportionate amounts on the other bands, it is desirable to allow the frequency meter to "warm up" for about a half hour before calibrating or before making measurements in which utmost accuracy is desired. Better still, it may be left on permanently. The power consumption is negligible, and the long-time stability will be vastly improved.

Although some frequency drift is unavoidable, it can be minimized by the use of voltage-regulator tubes in the power supply and low-drift silvered-mica or zero temperature-coefficient fixed condensers in the tuned circuit. A small negative temperature-coefficient condenser may be included to compensate for residual drift.

Calibration of the frequency meter is readily accomplished if a secondary standard is available, the required calibration points being supplied by harmonics from the standard. The frequency meter is tuned to zero beat with these harmonics, using either a built-in detector or the station receiver to combine the two signals to provide an audible beat. When a sufficient number of points have been established they may be marked on graph paper and a calibration curve drawn. For maximum convenience a direct-reading dial scale can be constructed.


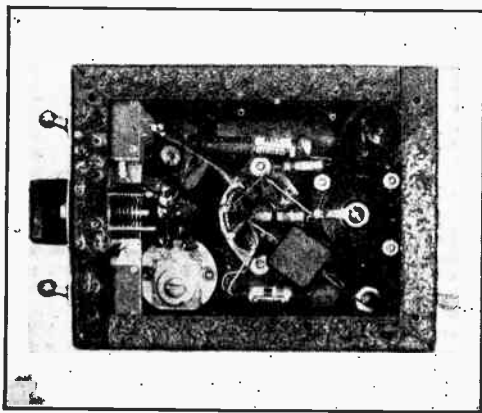


Fig. 1906 — Interior of 100-1000-kc. crystal calibrator. The crystal is mounted at top center, above the socket. Trimmer for 1000-kc. plate circuit at lower right, 8 mh. choke for 100 kc. at lower left.

Fig. 1908 — Circuit diagram of the electron-coupled heterodyne frequency meter.

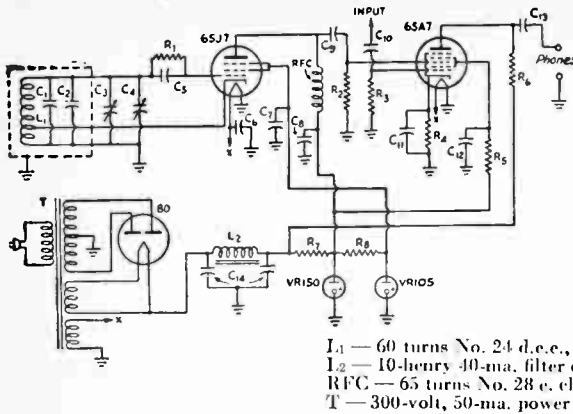

- C₁ — 350- μ fd. zero-drift.
- C₂ — 40- μ fd. negative-temperature.
- C₃ — 100- μ fd. midget.
- C₄ — 50- μ fd. trimmer.
- C₅ — 100- μ fd. silver-mica.
- C₆, C₈ — 0.005- μ fd. mica.
- C₇, C₉, C₁₀ — 0.002- μ fd. mica.
- C₁₁ — 25- μ fd. 25-volt electrolytic.
- C₁₂ — 0.01- μ fd. 400-volt paper.
- C₁₃ — 0.5- μ fd. 400-volt paper.
- C₁₄ — Dual 8- μ fd. 450-volt electrolytic.
- R₁, R₂ — 1 megohm, $\frac{1}{2}$ -watt.
- R₃ — 200,000 ohms, $\frac{1}{2}$ -watt.
- R₄ — 150 ohms, $\frac{1}{2}$ -watt.
- R₅ — 5000 ohms, 1-watt.
- R₆ — 50,000 ohms, 2-watt.
- R₇ — 3500-ohm, 10-watt wire-wound.
- R₈ — 2500-ohm, 5-watt wire-wound.
- L₁ — 60 turns No. 24 d.c.e., close-wound, 1 $\frac{1}{4}$ -inch diameter, tap at 12 turns.
- L₂ — 10-henry 40-ma. filter choke.
- RFC — 65 turns No. 28 e. close-wound, $\frac{5}{16}$ -inch diameter.
- T — 300-volt, 50-ma. power transformer.

If no frequency standard is available, calibration points may be obtained from other sources of known frequency, such as the transmitter crystal oscillator, harmonics of local broadcasting stations, etc. As many such points as possible should be secured, so that individual inaccuracies will average out.

With a stable oscillator, a precision dial and frequent and careful calibration, an over-all accuracy of 0.05 to 0.1 per cent may be expected of the heterodyne frequency meter. The principal limiting factors are the precision with which the calibrated dial can be read and the "reset" stability of the tuned circuit.

Absorption frequency meters — The frequency-checking devices described in the preceding sections all use vacuum-tube oscillators to generate a signal of known frequency, which then is compared to the signal to be measured in auxiliary apparatus such as a receiver. Although capable of high accuracy, heterodyne methods require considerable care in the identification of proper harmonics.

The simplest possible frequency-measuring device is a resonant circuit, tunable over the desired frequency range and having its tuning dial calibrated in terms of frequency. Such a frequency meter operates by extracting a small amount of energy from the oscillating circuit to be measured, the frequency then being determined by tuning the frequency-meter circuit to resonance and reading the frequency from the calibrated scale. This method is not capable of as high accuracy as the heterodyne methods for two reasons: First, the resonance indication is relatively "broad" as compared to the zero beat of a heterodyne; second, the necessarily close coupling between the frequency meter and the circuit being measured causes some detuning in both circuits, with the result that the calibration of the frequency-meter circuit depends to some degree on the coupling to the circuit being measured.

It is necessary to have some means for indicating resonance with an absorption frequency meter. When such a meter is used for checking a transmitter, the plate current of the tube

connected to the circuit being checked can provide the resonance indication. When the frequency meter is tuned through resonance the plate current will rise, and if the frequency meter is loosely coupled to the tank circuit the plate current will simply give a slight upward flicker as the meter is tuned through resonance. The greatest accuracy is secured when the loosest possible coupling — just enough to give an indication — is used.

A receiver oscillator may be checked by tuning in a steady signal and heterodyning it to give a beat note as in ordinary c.w. reception. When the frequency meter is coupled to the oscillator coil and tuned through resonance the beat note will change. Again, the coupling should be made loose enough so that a just-perceptible change in beat note is observed when the meter is tuned through resonance.

Another method of indicating resonance is shown in Fig. 1909. When the meter is tuned to resonance with the oscillating circuit being measured the flashlight lamp, *B*, will give the brightest glow. For maximum sensitivity a low-current lamp should be used. The circuit being measured must have enough power to light the lamp, naturally, so this type of indicator usually is most suitable for checking transmitters. Greater sensitivity can be obtained by connecting a detector, either vacuum-tube or crystal type, to the frequency meter circuit.

Although the absorption-type frequency

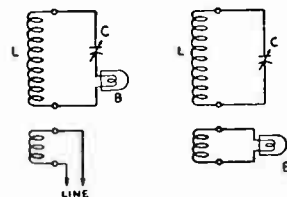


Fig. 1909 — The simple absorption frequency meter circuit at left is used chiefly in transmitter checking, with link-line coupling to the circuit being checked. Circuit at right uses a flashlight-bulb indicator loosely coupled to the tuned circuit, giving a sharper resonance point.

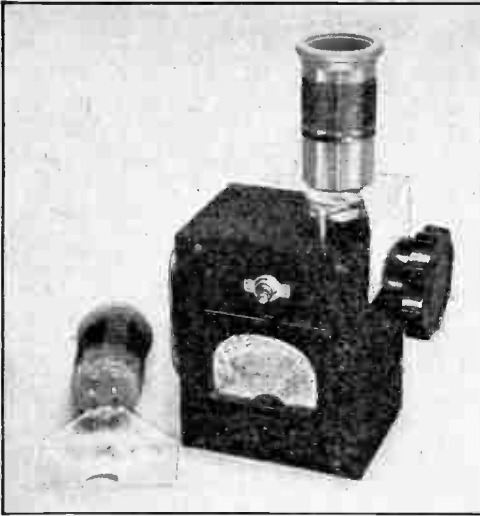


Fig. 1910 — A sensitive absorption-type frequency meter with a crystal-detector rectifier and d.c. milliammeter indicating circuit. Individual calibration charts mounted directly on each coil form make the meter direct-reading. The toggle switch places a 10-ma. shunt across the 0-1 ma. meter; this range is used for preliminary readings, to avoid burning out meter or crystal. The meter gives indications at several feet from a low-power oscillator.

meter should not be depended upon for accurate measurement, it is a highly-useful instrument to have in the station even when better frequency-measuring equipment is available. Since it generates no harmonics itself, it will respond only to the frequency to which it is

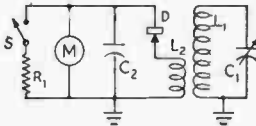


Fig. 1911 — Indicating frequency-meter circuit diagram.

- C₁ — 140- μ fd. variable (Hammarlund HFA-140-A).
- C₂ — 0.001- μ fd. mica.
- D — Fixed crystal detector.
- M — 0.1 d.c. milliammeter (Triplett Model 321).
- R₁ — 3-ohm shunt; see general data on meter shunts.
- S — S.p.s.t. toggle switch.
- L₁, L₂ — Plug-in coils wound on 1½-inch diameter forms:

Frequency Range	Wire Size	L ₁	Length	L ₂ ^{1,2}
1.1-3.5 Mc.	No. 28 e.	81¾	17 7/8"	17 turns
2.5-8.0 Mc.	No. 24 t.	37¾	15 5/8"	11 "
4.5-14 Mc.	No. 20 t.	17¾	11 1/2"	6 "
7.5-25 Mc.	No. 16 t.	8¾	11 1/4"	4 "
22-70 Mc.	No. 16 e.	2¾	1"	2 "

¹ Closewound, No. 30 d.s.c., ¼-inch from primary.
² Because the impedance of individual crystal detectors varies considerably, experiment with the number of turns on L₂ is necessary for maximum current indication. If meter reads backwards, reverse crystal connections.

tuned. It is therefore indispensable for distinguishing between fundamental and various harmonics, and for detecting harmonics and parasitic oscillations. When provided with a sensitive resonance indicator it is also useful for detecting r.f. in undesired places such as

power wiring, for making rough measurements of field strength in adjustment of antennas, and can likewise be used as a modulation monitor.

An absorption frequency meter must be calibrated against a more accurate frequency-measuring device such as those already described. For an approximate calibration — usually sufficient for the purposes for which an absorption meter is used — it may be calibrated by comparison with a calibrated receiver. The usual receiver dial calibration is sufficiently accurate. A simple oscillator circuit covering the same range as the frequency meter will be useful in calibration. Set the receiver to a given frequency, tune the oscillator to zero beat at the same frequency, and adjust the frequency meter to resonance with the oscillator as described above. This gives one calibration point. When a sufficient number of such points has been obtained a graph may be drawn to show frequency vs. dial settings on the frequency meter.

A sensitive absorption frequency meter — Figs. 1910 to 1912, inclusive, show an absorption frequency meter or "wavemeter" with a crystal detector-milliammeter resonance indicator which provides a relatively high degree of sensitivity. As shown in the circuit diagram, Fig. 1911, a pick-up coil coupled to the resonant circuit is connected in series with a crystal detector and 0-1 milliammeter. Plug-in coils are provided so that the unit covers the frequency spectrum from about 1 megacycle to 70 Mc. A switch, S, and shunt, R₁, are included so that the meter scale readings can be increased by a factor of 10, to reduce danger of overloading the milliammeter when making preliminary measurements. Any type of fixed crystal detector may be used, but the v.h.f. types are recommended when obtainable.

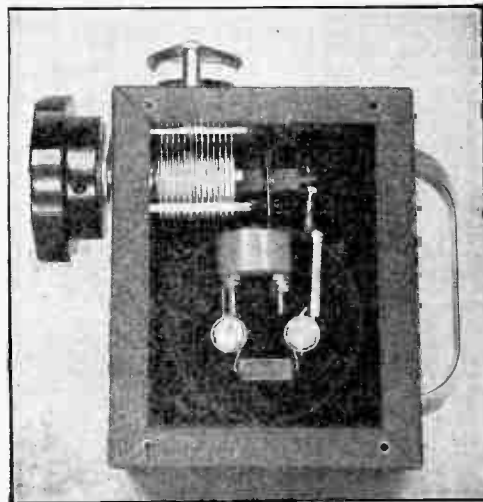


Fig. 1912 — Inside the absorption wavemeter. The tuning condenser and coil socket are mounted on the frame of the 3 by 4 by 5 box; remaining parts are fastened to one of the removable sides.

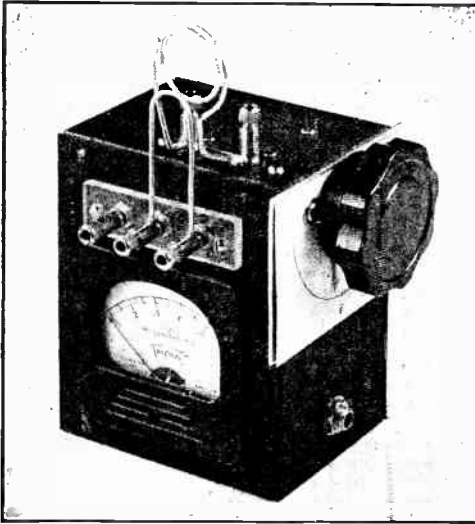


Fig. 1913 — A combination wavemeter, field-strength indicator and 'phone quality monitor for the 100-250-Mc. range. The two-turn coil is part of the wavemeter portion, and the hairpin loop provides pick-up for the 1N34 crystal detector. For field-strength work, a short antenna is connected to the binding post at the left of the hairpin loop.

The unit is constructed in a 3- by 4- by 5-inch metal box, the milliammeter being mounted on one of the side panels. The coil socket is on top near one edge, with the tuning condenser just below it inside the case. This arrangement keeps the tuned-circuit leads short. A handle is mounted on the side of the box opposite the tuning control for convenience in handling. A metal plate, on which an appropriate calibration scale is pasted, is fastened to each plug-in coil so that the proper calibration automatically comes under the knob pointer when the coil is plugged in. The unit may be calibrated as described in the preceding section.

A two- or three-foot rod antenna and head-phone jack may be added to the unit, using the connections shown in Fig. 1914. These additions permit the use of the instrument for field strength measurements and for monitoring 'phone transmissions. The rod antenna is not required for ordinary frequency measurement, and its use may be undesirable when the frequencies of individual simultaneously-operating circuits are to be checked — as in the case of a multistage transmitter with frequency multipliers — because the antenna increases the sensitivity to such an extent that it may be difficult to identify the output of a particular circuit.

In addition to the uses mentioned in the preceding section, a meter of this type may be used for final adjustment of neutralization in triode r.f. amplifiers when loosely coupled to the plate tank coil.

V.H.F. wavemeter-field strength indicator-monitor — For operation at very high

frequencies a different type of construction must be adopted for wavemeters of the type described in the preceding section. An instrument suitable for the range 100 to 250 Mc. is shown in Figs. 1913 to 1916, inclusive. Provision is made in this unit for attaching an antenna so relative field strength measurements can be made (for checking v.h.f. antenna patterns, for example) and the circuit includes a headphone jack so 'phone transmissions can be monitored.

The tuning condenser is a split-stator affair of 25 $\mu\text{pfd.}$ each section. It is mounted to give short leads to the coil, and the use of a split-stator condenser results in a low minimum capacity. The indication device includes a pick-up loop loosely coupled to the tuned circuit, a 1N34 crystal and a 0-1 milliammeter. The by-pass condenser, C_2 , furnishes a short r.f. return to the pick-up loop and avoids any resonances in this circuit within the frequency range of the wavemeter. For field-strength indication, an antenna is connected to one side of the pick-up loop and the wavemeter circuit, L_1C_1 , is detuned, resulting in a non-selective indicator.

The wavemeter is built in a 3- by 4- by 5-inch metal cabinet, with the tuning condenser, C_1 , mounted under the top. The condenser shaft comes out through a clearance hole in the side. An aluminum plate, 2 $\frac{5}{8}$ by 3 $\frac{3}{8}$ inches, is bolted on the side to back up the calibration scale. A polystyrene strip is used to mount the two National PWA binding posts that hold the coil, L_1 . The 'phone jack, J_1 , is mounted on the side of the case below the tuning knob.

The wavemeter may be calibrated by using Lecher wires (see next section) in conjunction with a v.h.f. oscillator. (The oscillator may be the 144- or 220-Mc. transmitter.) Attach a two-foot length of stiff wire to the antenna post of the wavemeter. With an oscillator capable of delivering 5 watts or so, a meter reading should be obtained several feet from the oscillator. The Lecher wires can then be very loosely coupled to the oscillator, and as the proper shorting points on the Lecher wires are

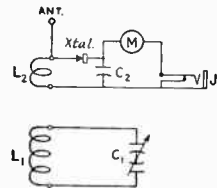


Fig. 1914 — Wiring diagram of the wavemeter and field-strength indicator.

C_1 — 25- $\mu\text{pfd.}$ per section split-stator variable. (Cardwell ER-25-A1).

C_2 — 100- $\mu\text{pfd.}$ midget mica.

J_1 — Closed-circuit telephone jack.

M — 0-1 milliammeter.

L_1 — 90-180 Mc.: 2 turns No. 12 wire, 1 $\frac{1}{8}$ -inch diam., spaced wire diameter.

125-250 Mc.: hairpin loop of No. 12, 1 $\frac{1}{4}$ -inch long, $\frac{3}{4}$ -inch spacing.

L_2 — Hairpin loop of No. 12, 2 $\frac{1}{4}$ -inch long, $\frac{3}{4}$ -inch spacing.

found, a dip will be observed in the wavemeter current. If now the tuning knob of the wavemeter is rotated, a sharp dip in wavemeter current will be found, and this point should be marked in pencil on the scale and the frequency, as calculated from the Lecher wires, should be noted for future calibration. As a double check on the calibration of the wavemeter, remove the antenna and tune the wavemeter for *maximum* meter reading. The two points should be identical. If they are not, the pick-up loop is coupled too closely to the tuned circuit of the wavemeter.

Lecher wires — At very-high and ultra-high frequencies it is possible to determine frequency by actually measuring the length of the waves generated. The measurement is made by observing standing waves on a two-wire parallel transmission line or Lecher wires. Such a line shows pronounced resonance effects, and it is possible to determine quite accurately the current loops (points of maximum current). The distance between two consecutive current loops is equal to one-half wavelength. Thus the wavelength can be read directly in meters (inches \times 39.37 if a yardstick is used), or in centimeters for the very short wavelengths.

The Lecher wire line should be at least a wavelength long — that is, 7 feet or more on 144 Mc. — and should be entirely air-insulated except where it is supported at the ends. It may be made of copper tubing or of wires stretched tightly between any two convenient supports. The spacing between wires should be approximately one to one and one-half inches. The positions of the current loops are found by

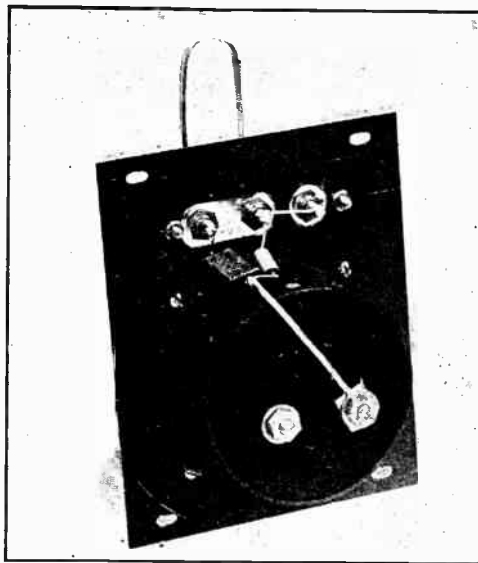


Fig. 1916 — A view of the back of the v.h.f. meter, showing the stiff supporting wire for the crystal and by-pass condenser.

means of a "shorting bar," which is simply a metal strip or knife edge which can be slid along the line to vary its effective length. The system can be used more conveniently and with greater accuracy if it is built up in permanent fashion and provided with a shorting bar maintained at right angles to the wires (Fig. 1918). The support may consist of two pieces of "1 by 2" pine fastened together with wood screws to form a T girder, this arrangement being used to minimize bending of the wood when the wires are tightened.

A slider holds the shorting bar and acts as a guide to keep the wire spacing constant. A piece of wood held in the hand can be used; it is an easy matter to regulate the pressure so that free movement is secured. A spring device may be arranged for the same purpose.

For convenience in measuring lengths directly in the metric system used for wavelength, the supporting beam may be marked off in decimeter (10-centimeter) units. A 10-centimeter transparent scale (obtainable at 5 & 10 cent stores) may be cemented to the slider, extending out from the front, so that readings can be taken to the nearest millimeter. The difference between any two readings gives the half wavelength directly.

Making measurements — Resonance indications can be obtained in several different ways. Let us suppose the frequency of a transmitter is to be measured. A convenient and fairly sensitive indicator can be made by soldering the ends of a one-turn loop of wire, of about the same diameter as the transmitter tank coil, to a low-current flashlight bulb, then coupling the loop to the tank coil to give a moderately-bright glow. A similar coupling

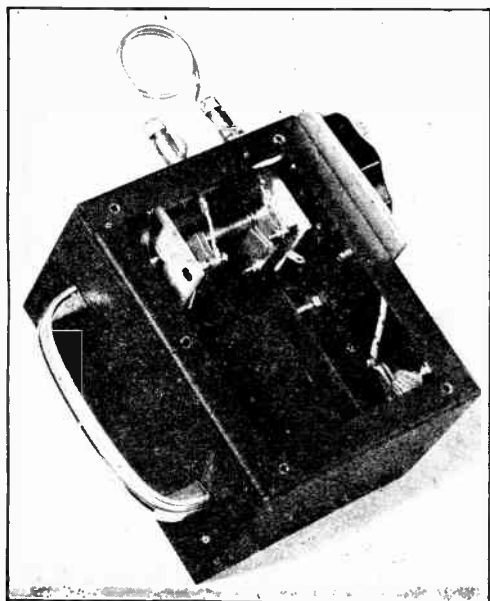


Fig. 1915 — Inside the v.h.f. wavemeter. The leads from the coil binding posts to the tuning capacitor are short and direct.

loop should be connected to the ends of the Lecher wires and brought near the tank coil, as shown in Fig. 1917. Then the shorting bar should be slid along the wires outward from the transmitter until the lamp gives a sharp dip in brightness. This point should be marked and the shorting bar moved out until a second dip is obtained. Marking the second spot, the distance between the two points can be measured and will be equal to half the wave-length. If the measurement is made in inches, the frequency will be

$$F_{Mc.} = \frac{5906}{\text{length (inches)}}$$

If the length is measured in meters,

$$F_{Mc.} = \frac{150}{\text{length (meters)}}$$

In checking a superregenerative receiver, the Lecher wires may be similarly coupled to the receiver coil. In this case the resonance indication may be obtained by setting the receiver just to the point where the hiss is obtained, then as the bar is slid along the wires a spot will be found where the receiver goes out of oscillation. The distance between two such spots is equal to a half wavelength.

In either case, the most accurate readings result only when the loosest possible coupling is used between the line and the tank coil. After taking a preliminary reading to find the regions along the line in which resonance occurs, loosen the coupling until the indications are just discernible and repeat the measurement. Unless this is done the tuning of the line will affect the frequency of the oscillator and inaccurate indications will be obtained. As the coupling is loosened the resonance points will become sharper, which is a further aid to accurate determination of the wavelength.

The shorting bar must be kept at right angles to the two wires. A sharp edge on the bar is desirable, since it not only helps make good contact but also definitely locates the *point* of contact.

The accuracy with which frequency can be measured by such a system depends principally upon the technique of measurement. The

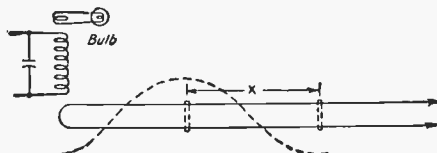


Fig. 1917 — Coupling a Lecher-wire system to a transmitter tank coil. Typical standing-wave distribution is shown by the dashed line. The distance between the positions of the shorting bar at the current loops equals one-half wavelength.

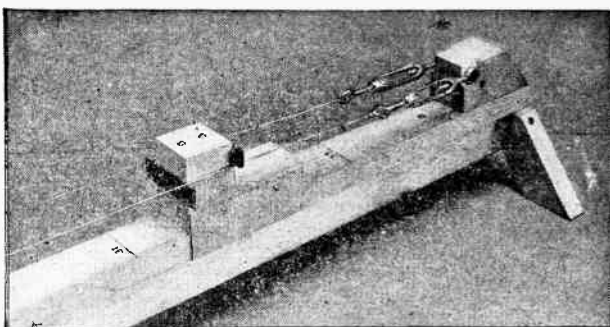


Fig. 1918 — One end of a typical Lecher-wire system. The feet at each end keep the assembly from tipping over when in use. The wires terminate in airplane-type strain insulators at one end, and at the other in small turnbuckles for maintaining tension. The wire is No. 16 bare solid copper antenna wire (hard-drawn). The turnbuckles are held in place by a $\frac{3}{16} \times 2$ -inch bolt through the anchor block. This end of the line is thus short-circuited; it does not matter whether it is open or shorted, since the other end is the one connected to the pick-up loop.

necessity for using very loose coupling to the transmitter or receiver has already been mentioned. In addition, careful measurement of the exact distance between two current loops also is essential. Even if all other sources of error are eliminated, measurements within 0.1 per cent require an accuracy within 1 part in 1000, or 1 millimeter in one meter, in measuring the distance along the wires. This means that an accurate standard of length is necessary — a good steel tape, for instance — and that care must be used in determining the length exactly.

Signal Monitoring

Every amateur station should make provision for checking the quality of the transmitter output. This requires that some means be available in the station for reproducing the conditions existing at a distant receiving station; that is, for reducing the strength of the signal from the transmitter to such a point that its characteristics can be examined without danger of false indications from overloading the receiving equipment.

The simplest method of checking the quality of c.w. transmissions is to use the regular station receiver. If the receiver is a superheterodyne the process may simply be that of reducing the r.f. gain to minimum and tuning to the transmitter frequency. If distant signals are stable and have "pure d.c." tone in normal reception, then the local transmitter should too, when the receiver gain is reduced to the point where the receiver does not overload. If the signal is too strong with the r.f. gain "off," shorting the antenna input terminals may reduce it to suitable proportions, or the mixer circuit in the receiver may be temporarily detuned to arrive at the same result.

An alternative method is to set the receiver on the next lower-frequency band than the one in use, then tune the receiver so that the second harmonic of its oscillator beats with the transmitter signal to produce the intermediate fre-

quency. Higher-order harmonics also may be used for this purpose. With this harmonic method there is ordinarily no danger that the receiver will overload, because the r.f. and mixer tuned circuits are so far from resonance with the transmitter frequency. The setting of the tuning dial bears no direct relation to the transmitter frequency under these conditions, since the oscillator harmonic must maintain a constant difference with the transmitter to produce the i.f. beat.

A 'phone signal may be monitored in the same way, provided a headset is used for reception. Use of a loud-speaker is not usually practicable because the sound output feeds back to the microphone and causes howling. A crystal detector and headset may also be used for the same purpose, as described in preceding sections. In monitoring a 'phone signal the best plan is to have another person speak into the microphone rather than to listen to one's own voice. It is difficult to judge quality when speaking and listening at the same time.

Measurement of Current, Voltage and Power

The amateur regulations require that when the power input to the final stage is above 900 watts means must be provided for measuring the power input. This may be done by measuring the d.c. voltage applied to the final stage plates and the d.c. current flowing to them. The instruments required are a milliammeter and voltmeter.

Although in lower-power transmitters power-input measurements are not required, it is nevertheless true that a milliammeter is an almost indispensable instrument in the amateur station. It is invaluable in the adjustment of transmitting amplifier stages; tuning a transmitter without measuring grid and plate currents is like working in the dark. A d.c. volt-

meter, although not essential, is useful in conjunction with the milliammeter in determining whether tube ratings are being exceeded or not and thus is helpful in prolonging tube life.

Besides d.c. measurements, it is also well to measure the filament voltages applied to transmitting tubes. Tube performance is dependent upon proper cathode emission, which in turn depends upon the voltage applied to the filament or heater. Also, the life of some transmitting tubes, particularly the thoriated-tungsten filament types, is critically dependent upon maintaining the filament voltage within rather close limits. Since most transmitting tube filaments are operated on a.c., an a.c. voltmeter is a worthwhile addition to amateur transmitting equipment.

Adjustment of a transmitter for maximum power output to the antenna or transmission line is facilitated by the use of instruments which measure radio-frequency current. Such instruments, although not actually essential, round out the measuring equipment used in transmitter adjustment.

D.c. instruments — D.c. ammeters and voltmeters are basically identical instruments, the difference being in the method of connection. An ammeter is connected in series with the circuit and measures the current flow. A voltmeter is a milliammeter which measures the current through a high resistance connected across the source to be measured; its calibration is in terms of the voltage drop in the resistance or *multiplier*.

If a single instrument must be used for measuring widely-different values of current or voltage, it is advisable to purchase one which will read, at about 75 per cent of full scale, the *smallest* value of current or voltage to be measured. Small currents cannot be read with any degree of precision on a high-scale instrument; on the other hand, the range of a

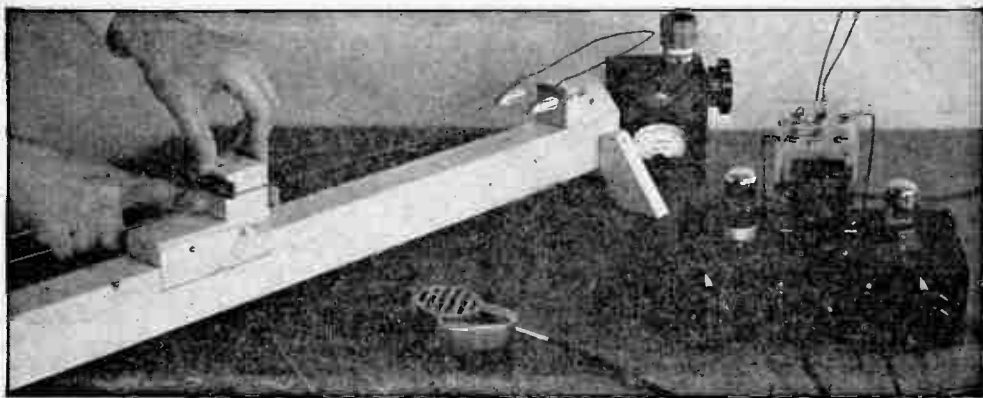


Fig. 1919 — A Lecher-wire system set up for frequency measurement, using a crystal-detector absorption frequency meter, loosely coupled to the oscillator tank, as a resonance indicator. Because only very loose coupling to the oscillator is required, this system will give more accurate results than coupling the wires directly to the transmitter tank. The shorting bar is of brass with a sharp edge for better contact and more precise indication; the wooden slider keeps it at right angles to the wires. Sheet metal pieces screwed to the sides of the sliding block are bent under the horizontal member of the T to keep the block in place.

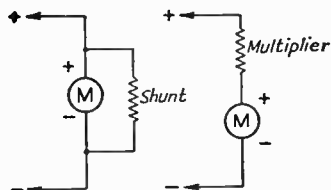


Fig. 1920 — How voltmeter multipliers and milliammeter shunts are connected to extend the range of a d.c. meter.

low-scale instrument can be extended as desired to take care of larger values. The ranges of both voltmeters and ammeters can be extended by the use of external resistors, connected in series with the instrument in the case of a voltmeter or in shunt in the case of an ammeter. Fig. 1920 shows at the left the manner in which a shunt is connected to extend the range of an ammeter and at the right the connection of a voltmeter multiplier.

To calculate the value of a shunt or multiplier it is necessary to know the resistance of the meter. If it is desired to extend the range of a voltmeter, the value of resistance which must be added in series is given by the formula:

$$R = R_m (n - 1)$$

where R is the multiplier resistance, R_m the resistance of the voltmeter, and n the scale multiplication factor. For example, if the range of a 10-volt meter is to be extended to 1000 volts, n is equal to 1000/10 or 100.

If a milliammeter is to be used as a voltmeter, the value of series resistance can be found by Ohm's law:

$$R = \frac{1000 E}{I}$$

where E is the desired full-scale voltage and I the full-scale reading of the instrument in milliamperes.

To increase the current range of a milliammeter, the resistance of the shunt is

$$R = \frac{R_m}{n - 1}$$

where the symbols have the same meanings as above.

Homemade milliammeter shunts can be constructed from any of the various special kinds of resistance wire, or from ordinary copper magnet wire if no resistance wire is available. The Copper Wire Table in Chapter Twenty gives the resistance per 1000 feet for various sizes of copper wire. After computing the resistance required, determine the smallest wire size which will carry the full-scale current (at 250 circular mils per ampere). Measure off enough wire (pulled tight but not stretched) to provide the required resistance. Accuracy can be checked by causing enough current to flow through the meter to make it read full-scale without the shunt; connecting the shunt should then give the correct reading on the new full-scale range.

Precision wire-wound resistors used as volt-

meter multipliers cannot readily be made by the amateur because of the much higher resistance required (as high as several megohms). As an economical substitute, standard fixed resistors may be used. Such resistors are supplied in tolerances of 5, 10 or 20 per cent \pm the marked values. By obtaining matched pairs from the dealer's stock, one of which is, for example, 4 per cent low while the other is 4 per cent high, and using the pairs in parallel or series to obtain the required value of resistance, good accuracy can be obtained at small cost. High-voltage multipliers are preferably made up of several resistors in series; this not only raises the breakdown voltage but tends to average out errors in the individual resistors due to manufacturing tolerances.

When d.c. voltage and current are known, the power in a d.c. circuit can be stated by simple application of Ohm's law: $P = EI$. Thus the voltmeter and ammeter are also the instruments used in measuring d.c. power.

Multi-range voltmeters and ohmmeters — A combination voltmeter-milliammeter having various ranges is extremely useful for experimental purposes and for trouble shooting in receivers and transmitters. As a voltmeter such an instrument should have high resistance so that very little current will be drawn in making voltage measurements. A voltmeter taking considerable current will give inaccurate readings when connected across a high-resistance source — as is often the case in various parts of a receiver circuit. For such purposes the instrument should have a resistance of at least 1000 ohms per volt; a 0-1 milliammeter or 0-500 microammeter (0-0.5 ma.) is the basis of most multirange meters of this type. Microammeters having a range of 0-50 μ a., giving a


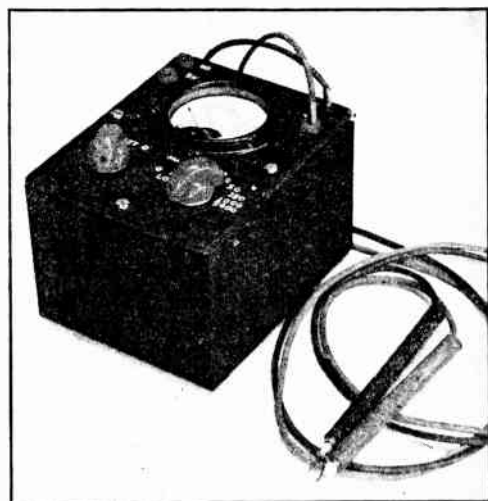


Fig. 1921 — An inexpensive multi-range volt-ohm-milliammeter housed in a standard 3 x 4 x 5 metal cabinet. Ranges are marked with number dies, the impressions being filled with white ink. High-voltage test leads are available for use on the 5000-volt range.

Fig. 1922 — Circuit of the low-cost V-O-M.

- R₁ — 2000-ohm wire-wound variable.
- R₂ — 3000 ohms, 1/2-watt.
- R₃ — 100-ma. shunt, 0.33 ohms (see text).
- R₄ — 10-ma. shunt, 3.6 ohms (see text).
- R₅ — 40,000 ohms, 1/2-watt.
- R₆ — 4 megohms, 4-watt (four 1-megohm 1-watt resistors in series).
- R₇ — 0.75 megohm, 1-watt (0.5 megohm and 0.25 megohm 1/2-watt in series).
- R₈ — 0.2 megohm, 1/2-watt.
- R₉ — 40,000 ohms, 1/2-watt.
- R₁₀ — 10,000 ohms, 1/2-watt.
- SW — 9-point 2-pole switch (Mallory-Yaxley 3109).
- B — 4.5 volts (Burgess 5360).

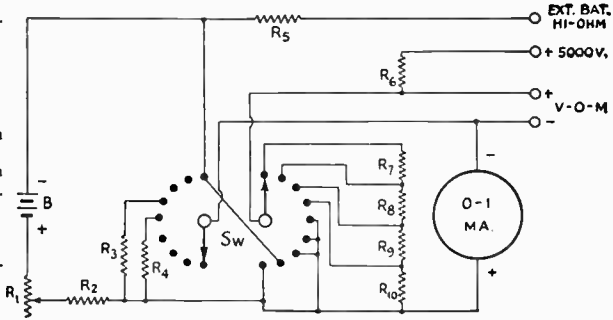

sensitivity of 20,000 ohms per volt, also are used.

The various current ranges on a multi-range instrument can be obtained by using a number of shunts individually switched in parallel with the meter. Care should be used to minimize contact resistance in the switch.

It is often necessary to check the value of a resistor or to find the value of an unknown resistance, particularly in receiver servicing. An "ohmmeter" is used for this purpose. The ohmmeter is simply a low-current d.c. voltmeter provided with a source of voltage (usually dry cells), the meter and battery being connected in series with the unknown resistance. If a full-scale deflection is obtained with the connections to the external resistance shorted, insertion of the resistance under measurement will cause the reading to decrease. The meter scale can be calibrated in ohms. When the resistance of the voltmeter is known, the following formula can be applied:

$$R = \frac{eR_m}{E} - R_m$$

where *R* is the resistance under measurement, *E* is the voltage read on the meter, *e* is the series voltage applied, *R_m* is the internal resistance of the meter.

A combination multirange volt-ohm-milliammeter, reduced to simple and inexpensive terms, is shown in Figs. 1921 to 1923, inclusive. Using a 0-1 milliammeter, the voltmeter has five ranges at 1000 ohms per volt: 0-10, 50, 250, 1000 and 5000 volts. Current ranges of 0-1, 10 and 100 ma. are provided. There are two resistance measurement ranges (three with external battery), a series range of 0-250,000 ohms, and a shunt range of 0-500 ohms. The "high-ohms" scale can be multiplied by 10 if the positive terminal of a 45-volt battery is connected to the terminal indicated in Fig. 1922, the unknown resistance being connected between the negative battery terminal and the negative terminal of the ohmmeter.

For economy, ordinary carbon resistors are used as voltmeter multipliers. These can be obtained with an accuracy within 5%. The 5000-volt multiplier is made up of four 1-watt resistors encased in heavy varnished cambric tubing to protect against flashovers. The tubing extends over the positive "5M" terminal, which is further insulated by a liberal wrapping of friction tape.

The 10-ma. and 100-ma. shunts are made with ordinary copper magnet wire wound on short lengths of 1/4-inch diameter bakelite rod.

◀ The Oscilloscope

The cathode-ray oscilloscope is an instrument of great versatility, and in conjunction with the instruments already described, rounds out the measuring equipment of the practical amateur station. The oscilloscope is useful on d.c., audio and radio frequencies, and is particularly suited to a.f. and r.f. measurements because, compared to other types of measuring equipment, it introduces relatively little error at such frequencies.

Probably the chief use of the oscilloscope in amateur work is in measuring the percentage

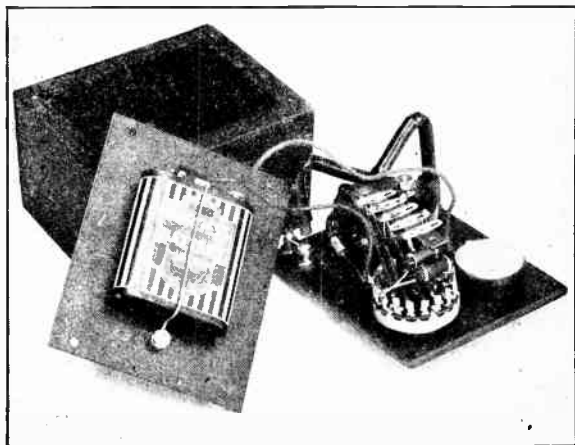


Fig. 1923 — Interior of low-cost volt-ohm-milliammeter. All parts except the internal ohmmeter battery are mounted on the 4 x 5-inch bakelite panel. The battery is attached to the bottom plate. The voltmeter multiplier is first assembled on an insulated tie strip, then wired into the circuit. The M-shaped object in the rear is the 5000-volt multiplier — four 1-watt resistors covered with varnished cambric tubing.

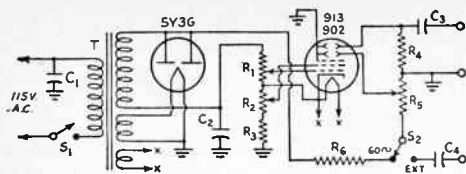


Fig. 1924 — An oscilloscope circuit for modulation monitoring.

- C₁ — 0.01- μ fd. 400-volt paper.
 C₂ — 0.5- μ fd. 800-volt paper or oil-filled.
 C₃ — 0.005- μ fd. mica.
 C₄ — 0.1- μ fd. 600-volt paper.
 R₁ — 50,000-ohm variable.
 R₂, R₅ — 0.5-megohm variable.
 R₃ — 1 megohm, 1-watt.
 R₄, R₆ — 0.5 megohm, 1-watt.
 S₁ — S.p.s.t. toggle switch.
 S₂ — S.p.d.t. toggle switch.
 T — Replacement-type transformer; 350 volts, 40 ma.;
 5 volts, 3 amperes; 6.3 volts, 2 amperes.

modulation in 'phone transmitters and in serving as a continuous monitor of modulation percentage. An oscilloscope for this purpose may be quite simple and inexpensive, consisting only of a small cathode-ray tube and an appropriate power supply. However, by providing amplifiers for the deflection plates and furnishing a linear sweep circuit, the possibilities of the instrument are greatly extended. It then becomes possible, for example, to examine audio-frequency waveforms and to check and locate the cause of distortion in a.f. amplifiers.

Constructional considerations —

In building an oscilloscope, care should be taken to see that the tube is shielded from stray electric and magnetic fields which might deflect the beam, and means should be provided to protect the operator from accidental shock, since the voltages employed with the larger tubes are quite high. In general, the preferable form of construction is to enclose the instrument completely in a metal cabinet. It is good practice to provide an interlock switch which automatically disconnects the high-voltage supply when the cabinet is opened for servicing or other reasons.

In laying out the unit, the cathode-ray tube must be placed so that the alternating magnetic field from the power transformer has no effect on the electron beam. The transformer should be mounted directly behind the base of the tube, with the axes of the transformer windings and of the tube on a common line.

It is important that provision be included either for switching off the electron beam or reducing the spot intensity, or for swinging the beam to one side of the screen with d.c. bias, when no signal voltage is being ap-

plied. A thin, bright line or a spot of high intensity will "burn" the screen of the cathode-ray tube.

If trouble is experienced in obtaining a clean pattern from a high-power transmitter because of r.f. voltage introduced by the 115-volt line, by-pass condensers (0.01 or 0.1 μ fd.) should be connected in series across the primary of the power transformer, the common connection between the two condensers being grounded to the case.

A simple oscilloscope — The circuit of a simple cathode-ray oscilloscope is shown in Fig. 1924. Either a 1-inch 913 or a 2-inch 902 tube can be used. The cathode-ray tube may be mounted, together with the associated rectifier tube and other components, in a cabinet made of a standard 3 \times 5 \times 10-inch steel chassis with bottom plate.

This circuit is useful primarily for modulation checking in radiotelephone transmitters. Horizontal sweep voltage may be obtained either from an audio-frequency source, such as the modulator stage of the transmitter, or from the 60-cycle a.c. line, as selected by S₂. Using the modulator output for the sweep, the pattern appearing on the screen will be in the form of a trapezoid, as described in Chapter Five.

R₃ controls the amplitude of the applied horizontal sweep. R₁ is the intensity control and R₂ the focusing control. If needed, a 2.5-mh. 125-ma. r.f. choke may be connected


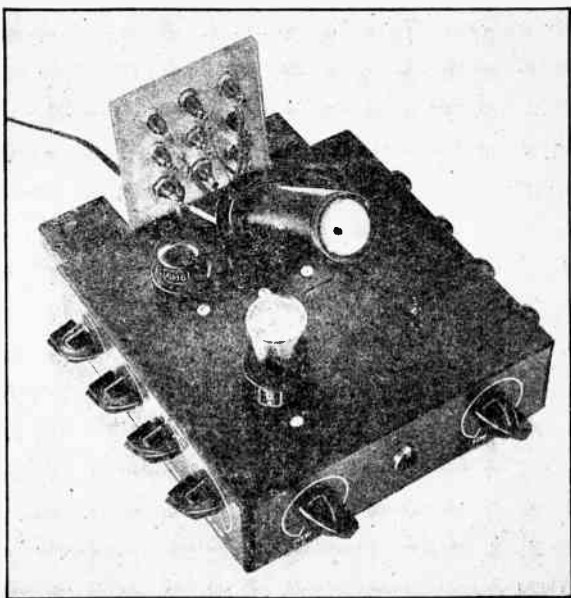


Fig. 1925 — A simple oscilloscope using a 1-inch tube. The controls on the front, from left to right, are "Sync Amplitude," pilot light and "Fine Frequency." Note the small neon tube, used for generating the sweep voltages, to the right of the 6SL7. A hood mounts over the 913 and the terminal panel at the rear of the chassis. The controls along the side, from back to front, are "Focus," "Vertical Centering," "Sync-Sweep" and "Vertical Gain."

Fig. 1926 — Wiring diagram of the 1-inch oscilloscope.

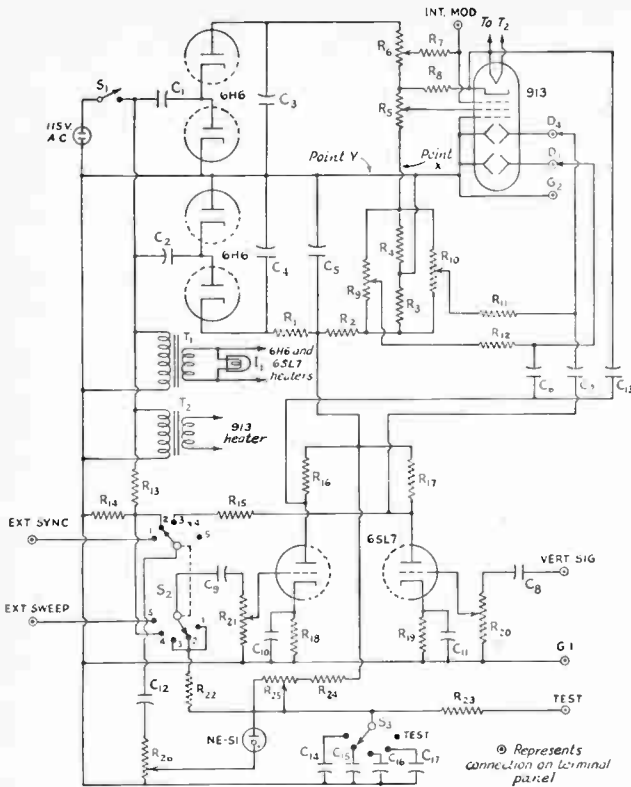

- C₁, C₂, C₃, C₄, C₅ — 8- μ fd, 250-volt electrolytic.
 - C₆, C₇, C₈, C₉ — 0.1- μ fd, 600-volt paper.
 - C₁₀, C₁₁ — 25- μ fd, 25-volt electrolytic.
 - C₁₂ — 0.001- μ fd, mica.
 - C₁₃ — 100- μ fd, mica.
 - C₁₄ — 0.05- μ fd, 400-volt paper.
 - C₁₅ — 0.02- μ fd, 400-volt paper.
 - C₁₆ — 0.006- μ fd, mica.
 - C₁₇ — 0.002- μ fd, mica.
 - I₁ — 6.3-volt pilot lamp.
 - R₁ — 10,000 ohms.
 - R₂, R₂₅ — 0.2 megohm.
 - R₃, R₄ — 0.1 megohm.
 - R₅ — 0.25-megohm variable, "Focus" control.
 - R₆ — 50,000 ohms, variable, "Intensity" control.
 - R₇, R₈ — 0.5 megohm.
 - R₉, R₁₀, R₂₀ — 1.0-megohm variable, "Horizontal Centering," "Vertical Centering" and "Vertical Gain" controls.
 - R₁₁, R₁₂, R₁₃ — 2.0 megohms.
 - R₁₄ — 50,000 ohms.
 - R₁₅ — 1.0 megohm.
 - R₁₆, R₁₇ — 0.25 megohm.
 - R₁₈, R₁₉ — 5000 ohms.
 - R₂₁ — 3-megohm variable, "Horizontal Gain" control.
 - R₂₂, R₂₄ — 3.0 megohms.
 - R₂₅ — 10.0 megohm variable, "Fine Frequency" control.
 - R₂₆ — 0.1-megohm variable, "Sync Amplitude" control.
- All fixed resistors are $\frac{1}{2}$ -watt carbon.
 S₁ — S.p.s.t. snap switch mounted on R₆.
 S₂ — Two-pole 5-position rotary, "Sync-Sweep."
 S₃ — Single-pole 5-position rotary, "Coarse Frequency."
 T₁, T₂ — 6.3-volt, 1.0-ampere heater transformer.

in series with the lead to the rotor of R₅ to correct leaning of patterns caused by r.f. coupling.

A complete oscilloscope — The usefulness of the oscilloscope is enhanced by providing a linear sweep circuit or time base, together with amplifiers for the horizontal and vertical deflection-plate signals so that sufficient voltage will be available at the deflection plates to give a pattern of suitable size. An inexpensive oscilloscope so equipped is shown in Figs. 1925 to 1928, inclusive. It uses the 1-inch Type 913 tube, but the 2-inch Type 902 readily can be substituted in the circuit.

As shown in Fig. 1926, the high-voltage d.c. is furnished by two 6H6s connected as half-wave voltage doublers. One supplies 300 volts positive for the amplifiers and sweep generator, and the other furnishes 300 volts negative for the cathode ray tube voltage-divider network. The current drain is 2 ma. from the positive and 0.75 ma. from the negative supply. The combination of R₁ and C₅ contributes additional filtering to the positive supply.

The horizontal sweep generator is a 1/25-watt neon bulb (General Electric NE-51) used in a saw-tooth oscillator circuit. The frequency is determined by R₂₄ plus R₂₅ and the shunt capacity selected by S₃, and is variable between 12 and 700 cycles. A synchronizing

voltage can be coupled in through C₁₂ and its amplitude adjusted by R₂₆. The "Sync-Sweep" switch, S₂, allows five different conditions of sweep and synchronization, as follows: (1) external synchronization (2) line synchronization (3) internal synchronization (4) line (sine-wave) sweep and (5) external sweep.

The positive sawtooth from the generator becomes a negative sawtooth after amplification through the horizontal amplifier (one section of a 6SL7), and to make the trace sweep from left to right in the conventional fashion the cathode-ray tube must be turned so that the No. 1 pin is at the bottom, with pins No. 3 and No. 7 horizontal. Used in this manner a waveform will appear in the correct polarity when passed through the vertical amplifier but it will be inverted when applied directly to the vertical plates.

The unit is built on a 7- by 7- by 2-inch chassis. The ten controls and the pilot light are mounted along the front and sides, and the two heater transformers are mounted on the back. The external connections are brought to nine tip jacks on a polystyrene panel which is also mounted on the back of the chassis. Mounting the jacks for connections at the back of the chassis keeps the leads clear of the controls.

The arrangement of the tubes on the chassis

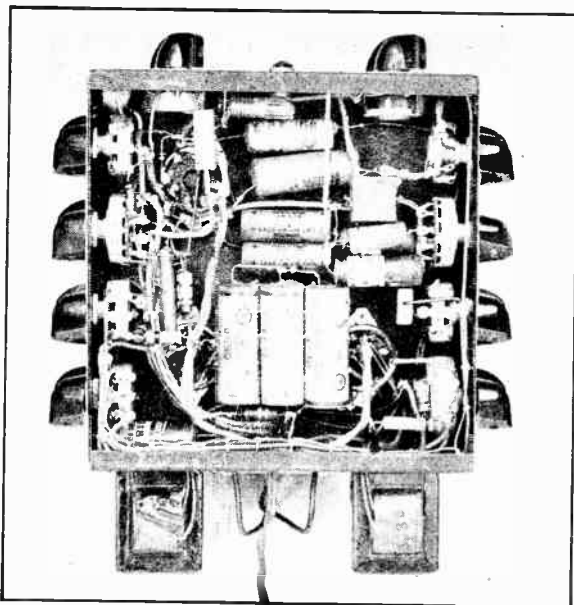


Fig. 1927 — View showing the arrangement of parts underneath the oscilloscope chassis. The controls along the left-hand side, from top to bottom, are "Intensity," "Horizontal Centering," "Coarse Frequency" and "Horizontal Gain."

can be seen in the photographs. The leads in the sweep generator, amplifier grid circuits and all heaters should be shielded to minimize a.c. pick-up. Too much pick-up in the sweep circuit will cause it to synchronize with the line frequency and produce unstable sweeps at other frequencies. The outputs of the amplifiers are brought out in flexible leads terminated in pin tips which can be plugged into the proper jacks on the terminal panel, thus making it a simple matter to remove them when working directly into the scope deflection plates.

Since one side of the a.c. line is common to the d.c. voltages and chassis of the scope, it is necessary to have a means of determining when the chassis is connected to the grounded side of the line. The "Test" terminal provides a means for checking this. With S_1 turned to the "Off" position and S_3 set to "Test," connect the "Test" terminal to an actual ground or the common of the unit to be tested with the scope. If the neon tube glows, the a.c. plug should be reversed.

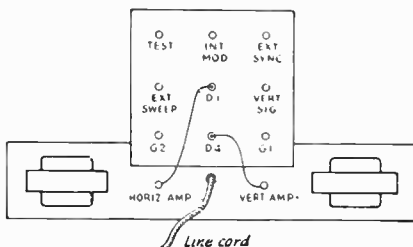


Fig. 1928 — A sketch of the back of the scope, showing the arrangement of terminals.

The direct sensitivity of the vertical plates is 125 volts/inch and 175 volts/inch for the horizontal. Working through the amplifiers at maximum gain, the vertical sensitivity is 0.9 volts/inch and 1.1 volts/inch for the horizontal. The a.c. power consumption of the unit is approximately 20 watts.

¶ Signal Generators

Test oscillators — A simple test oscillator for receiver checking and similar uses is shown in Fig. 1929. It uses the electron-coupled oscillator circuit with provision for suppressor-grid a.f. modulation. The output attenuator is a potentiometer so connected as to prevent a constant input resistance to the receiver.

For suppressor-grid modulation, apply approximately 10 volts of audio voltage (for 50 per cent modulation), as shown in the diagram. The suppressor-grid is biased 10 volts negative for modulated use; if an unmodulated signal is desired, the upper terminal may be grounded as indicated. This will increase the output from the oscillator. Conversely, if the output potentiometer does not attenuate the signal sufficiently, additional d.c. negative bias may be applied between the modulation terminals.

In aligning a receiver it is important that the test signal be prevented from entering circuits where it can cause false indications. This will occur if the signal can enter the receiver by any other means than through the output leads from the test oscillator. To prevent direct pick-up because of the relatively strong field about the oscillator, the test oscillator must be thoroughly shielded, and the output lead likewise should be a shielded cable with the center wire the "hot" lead. Make all ground returns to a heavy copper strap connected to the cabinet at the output ground terminal. The plug-in coil should be separately shielded.

The i.f. ranges of the test oscillator can be calibrated by beating against signals of known frequency in the b.c. band. Frequencies between 465 kc. and 275 kc. can be spotted by using the second harmonic of the oscillator, the remainder of the range to 175 kc. being checked by using the third harmonic.

The a.f. modulating source for the test oscillator can be any audio oscillator capable of delivering 10 to 20 volts at the standard receiver-checking frequency of 400 cycles.

A useful audio oscillator circuit is shown in Fig. 1930. It employs a two-terminal or "transitron" circuit using a pentagrid tube. A frequency of approximately 400 cycles is generated with the tuned-circuit values shown. The frequency may be changed by substituting a different value for C_1 ; several values of capacitance may be arranged to be selected by

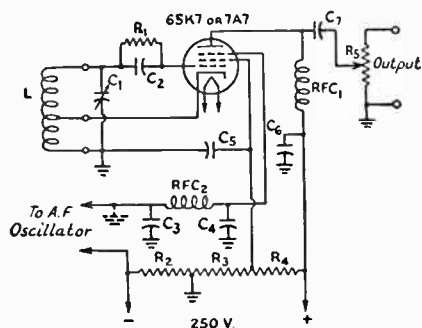


Fig. 1929 — Electron-coupled i.f. test oscillator circuit diagram.

- C₁ — 100- μ fd. variable with 200- μ fd. fixed silver-mica zero-drift in parallel.
- C₂ — 100- μ fd. midget mica.
- C₃, C₄ — 250- μ fd. midget mica.
- C₅ — 0.005- μ fd. mica.
- C₆ — 0.1- μ fd. 400-volt paper.
- C₇ — 500- μ fd. midget mica.
- R₁ — 50,000 ohms, $\frac{1}{2}$ -watt.
- R₂ — 2000 ohms, $\frac{1}{2}$ -watt.
- R₃ — 20,000 ohms, 1-watt.
- R₄ — 20,000 ohms, 2-watt.
- R₅ — 500-ohm carbon potentiometer.
- L — 440–510 kc.: 140 turns No. 30 enamelled, close-wound on $1\frac{1}{2}$ -inch diameter plug-in form. Cathode tap 35 turns from ground end.
- 1400–1550 kc.: 42 turns No. 20 d.s.c. tapped 10 turns from ground.
- 4500–5500 kc.: 11 turns No. 18 enamelled, turns spaced diameter of wire, tapped 3 turns from ground.
- RFC₁ — 2.5-mh. r.f. choke.
- RFC₂ — 25-mh. r.f. choke.

a switch so that an assortment of frequencies is available.

Antenna Measurements

Antenna measurements are made for the purpose (a) of securing maximum transfer of power to the antenna from the transmitter, and (b) of adjusting directional antennas to conform with design conditions. Related to measurements of the antenna system proper is the measurement of transmission-line performance.

Checking the transmission line for standing waves can be done by measuring the current in the wires, using a device of the type pictured in Fig. 1931. The hooks (which should be sharp

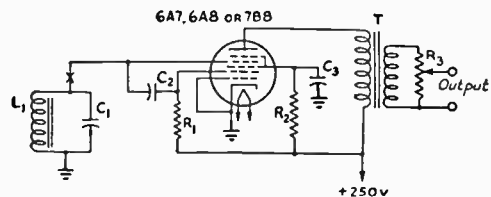


Fig. 1930 — Simple negative-resistance audio oscillator.

- C₁ — 0.15- μ fd. 400-volt paper.
- C₂ — 0.1- μ fd. 400-volt paper.
- C₃ — 0.25- μ fd. 200-volt paper.
- R₁, R₂ — 50,000 ohms, 1-watt.
- R₃ — 50,000-ohm volume control.
- L₁ — 1.2-henry choke (Thordarson T-14C61 with iron core removed).
- T — Output transformer (interstage audio, 1:3 ratio).

enough to cut through the insulation, if any, on the wires) are placed on one of the wires, the spacing between them being adjusted to give a suitable reading on the meter. At any one position along the line the currents in the two wires should be identical. Readings taken at intervals of a quarter wavelength will indicate whether or not standing waves are present.

Field-intensity meters — In adjusting antenna systems for maximum radiation and in determining radiation patterns, use is made of

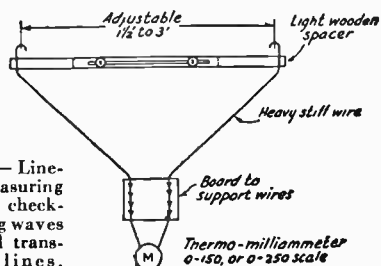


Fig. 1931 — Line-current measuring device for checking standing waves on untuned transmission lines.

field-intensity meters. Fundamentally the field-intensity meter consists of a small pick-up antenna and an indicating device such as a rectifier and microammeter or a vacuum-tube voltmeter provided with a tuned input circuit. It is used to indicate the relative intensity of the radiation field under actual radiating conditions. It is particularly useful on the very-high frequencies and in adjusting directional antennas. Field-intensity checks should be made at points several wavelengths distant from the antenna and at heights corresponding with the desired angle of radiation.

The absorption frequency meters shown in Figs. 1910 and 1913 may be used as field


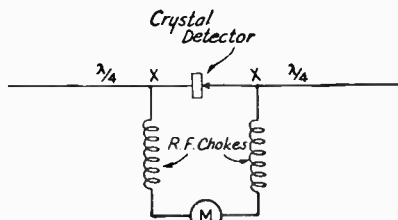


Fig. 1932 — Simple field-strength meter which may also be used as a sensitive indicator when making frequency measurements by connecting Lecher wires at X-X.

strength meters if provided with pick-up antennas. Alternatively, as shown in Fig. 1932, a crystal detector in the center of a half-wave pick-up antenna, coupled through r.f. chokes to a 0–1 ma. meter, will serve as a field-strength meter of ample sensitivity. When a signal is tuned in rectification occurs, and the rectified current is read on the microammeter. With this type of indicator, good readings may be obtained at distances of four or five wavelengths from a low-power transmitter with only a few watts input. The crystal detector does not have a linear characteristic, and a given increase in rectified current does not,

Fig. 1933 — Sensitive diode-triode field-intensity meter.

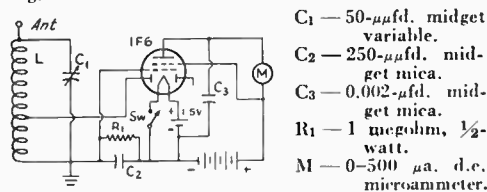


C₁ — 50- μ fd. midget variable.
C₂ — 250- μ fd. midget mica.
C₃ — 0.002- μ fd. midget mica.
R₁ — 1 megohm, $\frac{1}{2}$ -watt.
M — 0-500 μ a. d.c. microammeter.

L — 1.5-3 Mc.: 58 turns No. 28 d.s.c., close-wound.
 3-6 Mc.: 29 turns No. 20 e., close-wound.
 6-12 Mc.: 15 turns No. 20 e., spaced.
 11-22 Mc.: 8 turns No. 20 e., spaced.
 20-40 Mc.: 4 turns No. 20 e., spaced.
 All wound on $1\frac{1}{2}$ -inch coil forms, winding length $1\frac{1}{2}$ inches; diode tap in center of coil.

therefore, indicate a directly proportional increase in field strength.

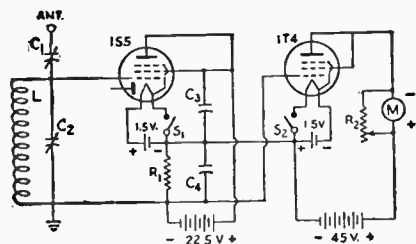A more sensitive field-intensity meter of use in examining the field-strength patterns of lower-frequency antenna systems, employing a diode rectifier and d.c. amplifier in the same envelope, is shown in Fig. 1933. The initial plate current reading is about 1.4 ma.; with signal input, the current dips downward. The



scale reading is linear with signal voltage. Radiated power variations will, of course, be as the square of the field-voltage indication.

Power gain in antenna systems usually is expressed in terms of decibels. A field-intensity meter circuit which reads directly in db. is shown in Fig. 1934. It consists of a self-biased

linear triode voltmeter followed by a variable- μ d.c. amplifier tube. Because of the nearly logarithmic grid-voltage/plate-current characteristic of this tube, a 0-1 ma. milliammeter in its plate circuit can be calibrated arbitrarily with a linear db. scale, as shown. For extreme accuracy an individual calibration should be made, applying known values of a.c. voltage to the 1S5 grid. The arbitrary scale shown will be found sufficiently accurate to be useful, however.

The scale covers approximately 25 db. and is linear over a range of about 20 db. At very small signals it departs from linearity, and therefore 0 db. is placed at 90 per cent of the scale. A variable meter shunt compensates for variations in tubes and battery voltages. In use, the balancing resistor is adjusted to give a full-scale reading of 1 ma. The signal pick-up is then made such as to cause the meter to indicate 0 db. Alternatively, the initial reading may be set arbitrarily at 10 db.; adjustments will then be indicated as losses or gains in relation to that figure.

Fig. 1934 — A logarithmic field-intensity meter with db. calibration, employing a variable- μ d.c. amplifier tube.

C₁ — 3-30- μ fd. mica trimmer.
C₂ — 50- μ fd. midget variable.
C₃, **C**₄ — 500- μ fd. midget mica.
R₁ — 10 megohms, $\frac{1}{2}$ -watt.
R₂ — 1000-ohm wire-wound.
S₁, **S**₂ — Two s.p.s.t. toggle switches or a single d.p.s.t.
L — See the coil data given under Fig. 1933.
M — 0-1 ma. d.c. milliammeter.



The range of the instrument may be extended to + 45 db. by inserting a 2-point tap switch in the connecting lead to the 1T4 amplifier from the self-biasing resistor **R**₁ and tapping that resistor by adding a 1-megohm unit to provide a 10-to-1 multiplier. Add 20 db. to all readings when the multiplier is used.

Vacuum Tube Characteristics and Miscellaneous Data

Inductance and Capacity

Inductance (L)—The formula for computing the inductance of air-core coils is:

$$L = \frac{0.2 a^2 n^2}{3a + 9b + 10c} \mu\text{h.}$$

where a is the mean diameter of the coil in inches, b is the length of the winding in inches, c is the radial depth of the winding in inches, and n is the number of turns. The quantity c may be neglected if the coil is a single-layer solenoid.

For example, assume a coil having 35 turns of No. 30 d.s.c. wire on a form 1.5 inches in diameter. Consulting the wire table (page 461), 35 turns of No. 30 d.s.c. will occupy 0.5 inch. Therefore, $a = 1.5$, $b = 0.5$, $n = 35$, and

$$L = \frac{0.2 \times (1.5)^2 \times (35)^2}{(3 \times 1.5) + (9 \times 0.5)} = 61.25 \mu\text{h.}$$

To calculate the number of turns of a single-layer coil for a required value of inductance:

$$N = \sqrt{\frac{3a + 9b}{0.2a^2} \times L}$$

Straight round wires:

To calculate the high frequency inductance of a straight round wire:

$$L = 0.00508 l (2.303 \log_{10} \frac{4l}{d} - 1)$$

- l = length in inches
- d = diameter in inches
- L = inductance in microhenrys

Condenser capacity (C)—The formula for determining the capacity of a condenser is:

$$C = 0.224 \frac{K.A}{d} (n - 1) \mu\mu\text{fd.}$$

where A is the area of one side of one plate in square inches, n is the total number of plates, d is the separation between plates in inches, and K is the dielectric constant ($= 1$ for air; see the table on page 458 for values for other materials).


The dielectric constant is the ratio of the capacity of a condenser with a given dielectric to its capacity with air dielectric.

ABBREVIATIONS FOR ELECTRICAL AND RADIO TERMS

Alternating current	a.c.	Medium frequency	m.f.
Ampere (amperes)	a.	Megacycles (per second)	Mc.
Amplitude modulation	a.m.	Megohm	MΩ
Antenna	ant.	Meter	m.
Audio frequency	a.f.	Microfarad	μfd.
Centimeter	cm.	Microhenry	μh.
Continuous waves	c.w.	Micromicrofarad	μμfd.
Cycles per second	c.p.s.	Microvolt	μv.
Decibel	db.	Microvolt per meter	μv/m.
Direct current	d.c.	Microwatt	μw.
Electromotive force	e.m.f.	Milliampere	ma.
Frequency	f.	Millivolt	mv.
Frequency modulation	f.m.	Milliwatt	mw.
Ground	gnd.	Modulated continuous waves	m.c.w.
Henry	h.	Ohm	Ω
High frequency	h.f.	Power	P.
Intermediate frequency	i.f.	Power factor	p.f.
Interrupted continuous waves	i.c.w.	Radio frequency	r.f.
Kilocycles (per second)	kc.	Ultrahigh frequency	u.h.f.
Kilovolt	kv.	Very-high frequency	v.h.f.
Kilowatt	kw.	Volt (volts)	v.
Magnetomotive force	m.m.f.	Watt (watts)	w.

RMA Radio Color Codes

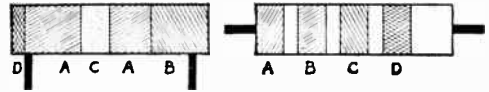Standard color codes have been adopted by the Radio Manufacturers Association for the ready identification of values and connections for standard components.



RESISTOR-CONDENSER COLOR CODE

Color	Significant Figure	Decimal Multiplier	Tolerance (%)	Voltage Rating *
Black	0	1	—	—
Brown	1	10	1*	100
Red	2	100	2*	200
Orange	3	1000	3*	300
Yellow	4	10,000	4*	400
Green	5	100,000	5*	500
Blue	6	1,000,000	6*	600
Violet	7	10,000,000	7*	700
Gray	8	100,000,000	8*	800
White	9	1,000,000,000	9*	900
Gold	—	0.1	5	1000
Silver	—	0.01	10	2000
No color	—	—	20	500

* Applies to condensers only.

Radial leads	Axial leads	Color
Body A	Band A	Indicates first significant figure.
End B	Band B	Indicates second significant figure.
Band C	Band C	Indicates decimal multiplier.
(or dot)		
Band D	Band D	Indicates tolerance in per cent.

Mica Condensers:

If one row of three colored markers appears on the condenser, the voltage rating is 500 volts and the capacity is expressed in $\mu\mu\text{fd}$. to two significant figures, in micromicrofarads as follows: First dot on left, first significant figure. Second dot, second significant figure. Third dot, decimal multiplier.

Example: A condenser has one row of colored markers, as follows: *brown*, *black* and *brown*. Its capacity is 100 $\mu\mu\text{fd}$.

When two rows of three colored markers appear on the condenser the top row represents the significant figures, reading from left to right; the bottom row indicates the decimal multiplier, tolerance and voltage rating, reading from right to left. Capacity is in $\mu\mu\text{fd}$.

Example: A condenser has two rows of colored markers, as follows: Top row: left, *brown*; center, *black*; right, *no color*. Bottom row: right, *brown*; center, *green*; left, *blue*. Its ratings are 100 $\mu\mu\text{fd}$.; $\pm 5\%$, 600 volts.

Tubular Condensers:

Two groups of colored bands are used on tubular condensers. Viewed with the wide bands on the right, the wide bands indicate significant figures (from left to right); narrow bands indicate the decimal multiplier, tolerance and voltage rating, from right to left, respectively.

Resistors:

Values of resistance and tolerances are indicated by colored dots, bands or stripes on the resistor.

Two types of resistors are commonly used, one having radial and the other axial leads. The following illustration shows the two types of resistors and the system of identification.

I.f. transformers:

- Blue — plate lead.
- Red — "B" + lead.
- Green — grid (or diode) lead.
- Black — grid (or diode) return.

NOTE: If the secondary of the i.f.t. is center-tapped, the second diode plate lead is green-and-black striped, and black is used for the center-tap lead.

A.f. transformers:

- Blue — plate (finish) lead of primary.
- Red — "B" + lead (this applies whether the primary is plain or center-tapped).
- Brown — plate (start) lead on center-tapped primaries. (Blue may be used for this lead if polarity is not important.)
- Green — grid (finish) lead to secondary.
- Black — grid return (this applies whether the secondary is plain or center-tapped).
- Yellow — grid (start) lead on center-tapped secondaries. (Green may be used for this lead if polarity is not important.)

NOTE: These markings apply also to line-to-grid, and tube-to-line transformers.

Loudspeaker voice coils:

- Green — finish.
- Black — start.


Field coils:

- Black and red — start.
- Yellow and red — finish.
- Slate and Red — tap (if any).

Power transformers:

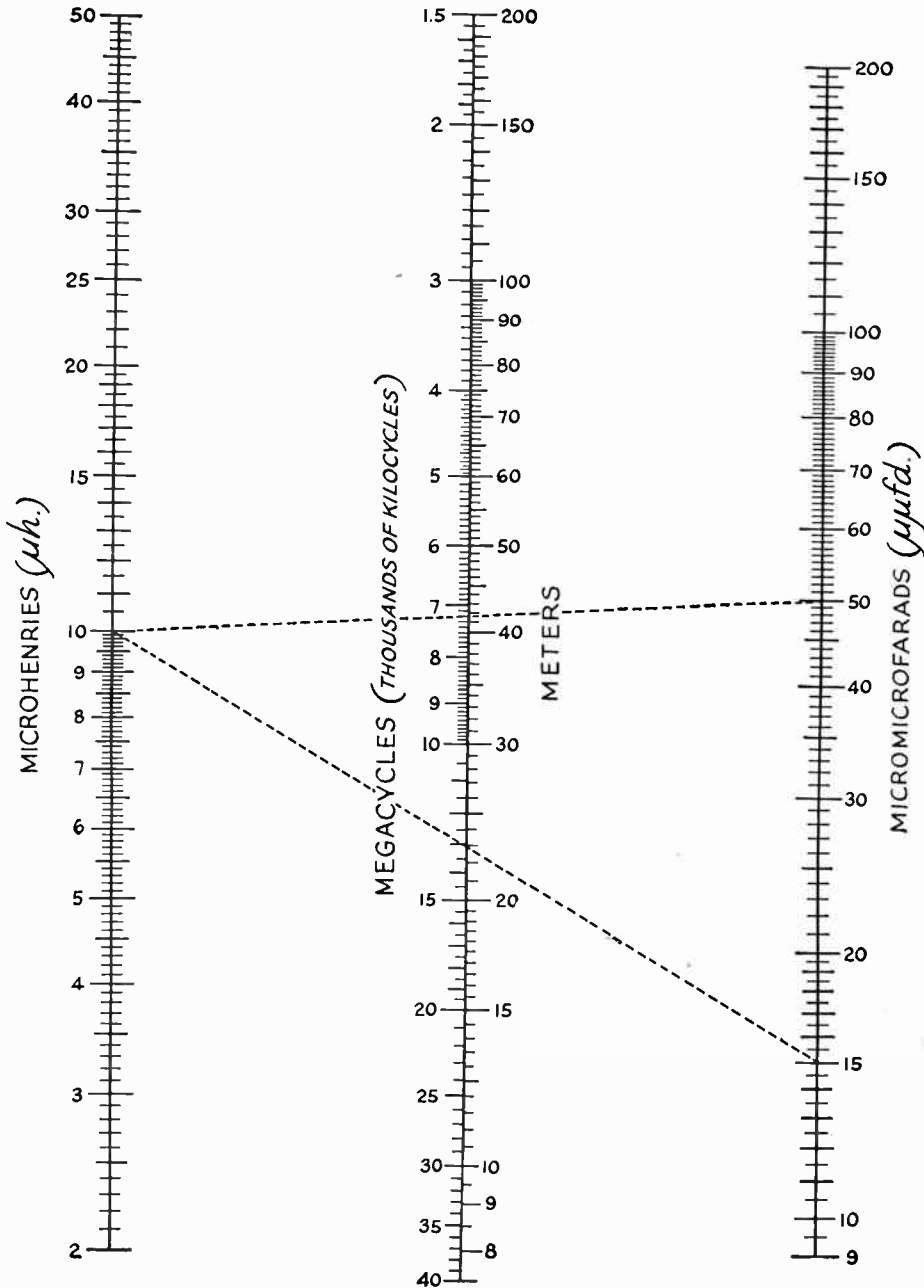- 1) Primary Leads Black
If tapped:
Common Black
Tap Black and Yellow Striped
Finish Black and Red Striped
- 2) High-Voltage Plate Winding Red
Center-Tap . . . Red and Yellow Striped
- 3) Rectifier Filament Winding Yellow
Center-Tap . . . Yellow and Blue Striped
- 4) Filament Winding No. 1 Green
Center-Tap . . . Green and Yellow Striped
- 5) Filament Winding No. 2 Brown
Center-Tap . . . Brown and Yellow Striped
- 6) Filament Winding No. 3 Slate
Center-Tap . . . Slate and Yellow Striped


INDUCTANCE, CAPACITY AND FREQUENCY — CHART I, 1.5–40 MC.



This chart may be used to find the values of inductance and capacity required to resonate at any given frequency in the medium- or high-frequency ranges; or, conversely, to find the frequency to which any given coil-condenser combination will tune. In the example shown by the dashed lines, a condenser has a minimum capacity of 15 $\mu\mu\text{fd.}$ and a maximum capacity of 50 $\mu\mu\text{fd.}$ If it is to be used with a coil of 10- $\mu\text{h.}$ inductance, what frequency range will be covered? The straight-edge is connected between 10 on the left-hand scale and 15 on the right, giving 13 Mc. as the high-frequency limit. Keeping the straight-edge at 10 on the left-hand scale, the other end is swung to 50 on the right-hand scale, giving a low-frequency limit of 7.1 Mc. The tuning range would, therefore, be from 7.1 Mc. to 13 Mc., or 7100 kc. to 13,000 kc. The center scale also serves to convert frequency to wavelength.

The range of the chart can be extended by multiplying each of the scales by 0.1 or 10. In the example above, if the capacities are 150 and 500 $\mu\mu\text{fd.}$ and the inductance 100 $\mu\text{h.}$, the range becomes approximately 231 to 422 meters or 0.7 to 1.3 Mc. Alternatively, 1.5 to 5 $\mu\mu\text{fd.}$ and 1 $\mu\text{h.}$ will give a range of approximately 71 to 130 Mc.

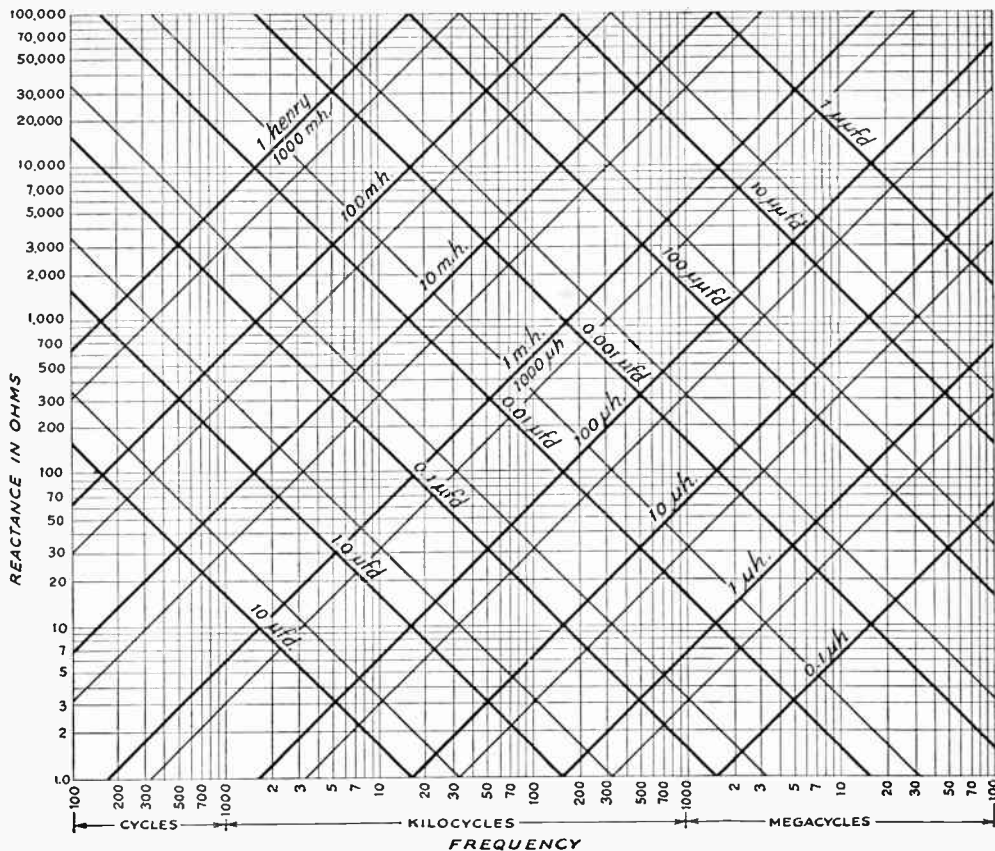INDUCTIVE AND CAPACITIVE REACTANCE VS. FREQUENCY CHART



By use of the chart above, the approximate reactance of any capacity from 1.0 $\mu\text{fd.}$ to 10 $\mu\text{fd.}$ at any frequency from 100 cycles to 100 megacycles, or the reactance of any inductance from 0.1 $\mu\text{h.}$ to 1.0 henry, can be read directly. Intermediate values can be estimated by interpolation. In making interpolations, remember that the rate of change between lines is logarithmic. Use the frequency or reactance scales as a guide in estimating intermediate values on the capacity or inductance scales.

This chart also can be used to find the approximate resonance frequencies of LC combinations, or the frequency to which a given coil and condenser combination will tune. First locate the respective slanting lines for the capacity and inductance. The point where they intersect, i.e., where the reactances are equal, is the resonant frequency (projected downward and read on the frequency scale).

Electrical Conductivity of Metals

	Relative Conductivity ¹	Temp. Coeff. ² of Resistance		Relative Conductivity ¹	Temp. Coeff. ² of Resistance
Aluminum (2S; pure)	59	0.0049	Lead	7	0.0041
Aluminum (alloys):			Manganese	3.7	0.00002
Soft-annealed	45-50		Mercury	1.66	0.00089
Heat-treated	30-45		Molybdenum	33.2	0.0033
Brass	28	0.002-0.007	Monel	4	0.0019
Cadmium	19		Nichrome	1.45	0.00017
Chromium	55		Nickel	12-16	0.005
Climax	1.83		Phosphor Bronze	36	0.004
Cobalt	16.3		Platinum	15	
Constantin	3.24	0.00002	Silver	106	0.004
Copper (hard drawn)	89.5	0.004	Steel	3-15	
Copper (annealed)	100		Tin	13	0.0042
Everdur	6		Tungsten	28.9	0.0045
German Silver (18%)	5.3	0.00019	Zinc	28.2	0.0035
Gold	65				
Iron (pure)	17.7	0.006			
Iron (cast)	2-12				
Iron (wrought)	11.4				

Approximate relations:
 An increase of 1 in A. W. G. or B. & S. wire size increases resistance 25%.
 An increase of 2 increases resistance 60%.
 An increase of 3 increases resistance 100%.
 An increase of 10 increases resistance 10 times.

¹ At 20° C., based on copper as 100. ² Per °C. at 20° C.

Table of Dielectric Characteristics

Dielectric material ¹	Dielectric constant (K)	Power factor					Dielectric strength (puncture voltage) ²	Volume resistivity ³ (ρ)
		60 cycles	1 kc.	1 Mc.	10 Mc.	100 Mc.		
Air (normal pressure).....	1.0						19.8-22.8	
AlSiMag A196.....	5.7-6.3	2.9		0.21	0.15		240	10 ¹⁴
Aniline formaldehyde.....	3-5	1-6					400	
Asphalts.....	2.7-3.1		2.3				25-30	
Bakelite—See Phenol.....								
Beeswax.....	2.9-3.2							
Cascin plastics ⁴	6.1-6.4			5.2-6			165	
Castor oil.....	4.3-4.7			7			380	
Celluloid.....	4-16			5-10				
Cellulose acetate ⁵	6-8	3-6	4-6	4-6	5.5		300-1000	4.5 × 10 ¹⁰
Cellulose nitrate ⁶	4-7			2.8-5			300-780	2-30 × 10 ¹⁰
Ceresin wax.....	2.5-2.6			0.12-0.21				
Cresol formaldehyde.....	6	10					400	
Dilectene.....	3.57					0.33		
Ethyl cellulose.....	2-2.7	0.7	1.2	1.5			1500	10 ¹⁵
Fiber.....	5-7.5			4.5-5			150-180	5 × 10 ⁹
Formica MF-66.....	4.6-4.9		1.5	1.1			450	
Glass:								
Cobalt.....	7.3			0.7				
Common window.....	7.6-8			1.4			200-250	
Crown.....	6.2-7		1	1 ³			500	
Electrical.....	4-5			0.5			2000	8 × 10 ¹⁴
Flint.....	7-10		0.45	0.4				
Nonex.....	4.2			0.25		0.28		
Photographic.....	7.5			0.8-1				
Plate.....	6.8-7.6			0.6-0.8				
Pyrex.....	4.2-4.9		0.5	0.7		0.54	335	10 ¹⁴
Gutta percha.....	2.5-4.9						200-500	5 × 10 ¹⁴ -10 ¹⁵
Lucite ⁷	2.5-3	7	5	1.5-3	1.9		480-500	
Melamine formaldehyde.....	8	16					300	
Mica.....	2.5-8	0.2	0.3	0.2-6	0.02			2 × 10 ¹⁷
Mica (clear India).....	6.4-7.5	2	2	2	2		600-1500	
Mycalex.....	7.4			0.18			250	10 ¹³
Mycalex (British).....	6			0.3			350	
Mykroy.....	6.5-7			0.1-0.2			630	
Nylon.....	3.6			2.2				
Paper.....	2.0-2.6						1250	
Paraffin wax (solid).....	1.9-2.6			0.1-0.3			300	10 ¹⁵ -10 ¹⁹
Penique.....	7.21			0.2				
Phenol: ⁸								
Pure.....	5			1			400-475	1.5 × 10 ¹²
Asbestos base.....	7.5			15			90-150	
Black molded.....	5-5.5			3.5			400-500	
Fabric base.....	5-6.5			3.5-11			150-500	
Mica-filled.....	5-6			0.8-1			475-600	
Paper base.....	3.8-5.5			2.5-4			650-750	10 ¹⁰ -10 ¹³
Yellow.....	5.3-5.4			0.36-0.7			500	
Polyethylene.....	2.3-2.4	0.02	0.02	0.02-0.05			1000	10 ¹⁷
Polyindene.....	3	0.04						
Polyisobutylene.....	2.4-2.5	0.04-5	0.05				500	10 ¹⁶
Polystyrene ⁹	2.4-2.9(2.6)	0.02	0.018	0.02	0.02	0.02	500-2500	10 ²⁰
Porcelain (dry process).....	6.2-7.5			0.7-15			40-100	5 × 10 ⁸
Porcelain (wet process).....	6.5-7			0.6			150	
Pressboard (untreated).....	2.9-4.5						125-300	
Pressboard (oiled).....	5						750	
Quartz (fused).....	3.5-(3.8)	0.01	0.01	0.015-0.03	0.01	0.05	200	10 ¹⁴ -10 ¹⁸
Rubber (hard) ¹⁰	2-3.5(3)			0.5-1			450	10 ¹² -10 ¹⁵
Shellac.....	2.5-4			0.09			900	10 ¹⁶
Steatite: ¹¹								
"Commercial" grade.....	4.9-6.5	0.02	0.2	0.2	0.4	0.5		
"Low-loss" grade.....	4.4	0.02	0.2	0.2	0.18	0.13	150-315	10 ¹⁴ -10 ¹⁵
Titanium dioxide ¹²	90-170		0.1	0.1				
Urea formaldehyde ¹³	5-7	3-5	2-3	2-4	4		300-550	10 ¹² -10 ¹³
Varnished cloth ¹⁴	2-2.5			2-3			440-550	
Vinyl resins.....	4			1.4-1.7			400-500	10 ¹⁴
Vitrolex.....	6.4			0.3				
Wood (dry oak).....	2.5-6.8(3)		3.8	4.2				
Wood (paraffined maple).....	4.1						115	

¹ Most data taken at 25° C.

² Puncture voltage, in volts per mil. Most data applies to relatively thin sections and cannot be multiplied directly to give breakdown for thicker sections without added safety factor.

³ In ohm-cm.

⁴ Includes such products as Aladdinite, Ameroid, Galalith, Erinoid, Lactoid, etc.

⁵ Includes Fibestas, Lumerith, Nixonite, Plastacel, Tenite, etc.

⁶ Includes Amerith, Nitron, Nixonoid, Pyralin, etc.

⁷ Methylmethacrylate resin.

⁸ Phenolaldehyde products include Acrolite, Bakelite,

Catalin, Celeron, Dielecto, Durez, Durite, Formica, Gemstone, Heresite, Indur, Makalot, Marblette, Micarta, Opalon, Prystal, Resinox, Synthane, Textolite, etc. Yellow bakelite is so-called "low-loss" bakelite.

⁹ Includes Amphphenol 912A, Distrene, Intelin IN 45, Loalin, Lustron, Quartz Q, Rezoglas, Rhodolene M, Ronilla L, Styraflex, Styron, Trolitul, Vietron, etc.

¹⁰ Also known as Ebonite.

¹¹ Soapstone — Alberene, Alsmag, Isolantite, Lava, etc.

¹² Rutile. Used in low temperature-coefficient fixed condensers.

¹³ Includes Aldur, Beetle, Plaskon, Pollopas, Prystal, etc.

¹⁴ Includes Empire cloth.

COPPER WIRE TABLE

Gauge No. B. & S.	Diam. in Mils ¹	Circular Mil Area	Turns per Linear Inch ²				Turns per Square Inch ²			Feet per Lb.		Ohms per 1000 ft. 25° C.	Current Carrying Capacity at 1500 C.M. per Amp. ³	Diam. in mm.	Nearest British S.W.G. No.
			Enamel	S.C.C.	D.S.C. or S.C.C.	D.C.C.	S.C.C.	Enamel S.C.C.	D.C.C.	Bare	D.C.C.				
1	289.3	83690	—	—	—	—	—	—	—	3.947	—	.1204	55.7	7.348	1
2	257.6	66370	—	—	—	—	—	—	—	4.977	—	.1593	44.1	6.544	3
3	229.4	52640	—	—	—	—	—	—	—	6.276	—	.2009	35.0	5.827	4
4	204.3	41740	—	—	—	—	—	—	—	7.914	—	.2533	27.7	5.189	5
5	181.9	33100	—	—	—	—	—	—	—	9.980	—	.3195	22.0	4.621	7
6	162.0	26250	—	—	—	—	—	—	—	12.58	—	.4028	17.5	4.115	8
7	144.3	20820	—	—	—	—	—	—	—	15.87	—	.5080	13.8	3.665	9
8	128.5	16510	7.6	—	7.4	7.1	—	—	—	20.01	19.6	.6405	11.0	3.264	10
9	114.4	13090	8.6	—	8.2	7.8	—	—	—	25.23	24.6	.8077	8.7	2.906	11
10	101.9	10380	9.6	—	9.3	8.9	87.5	84.8	80.0	31.82	30.9	1.018	6.9	2.588	12
11	90.74	8234	10.7	—	10.3	9.8	110	105	97.5	40.12	38.8	1.284	5.5	2.305	13
12	80.81	6530	12.0	—	11.5	10.9	136	131	121	50.59	48.9	1.619	4.4	2.053	14
13	71.96	5178	13.5	—	12.8	12.0	170	162	150	63.80	61.5	2.042	3.5	1.828	15
14	64.08	4107	15.0	—	14.2	13.8	211	198	183	80.44	77.3	2.575	2.7	1.628	16
15	57.07	3257	16.8	—	15.8	14.7	262	250	223	101.4	97.3	3.247	2.2	1.450	17
16	50.82	2583	18.9	18.9	17.9	16.4	321	306	271	127.9	119	4.094	1.7	1.291	18
17	45.26	2048	21.2	21.2	19.9	18.1	397	372	329	161.3	150	5.163	1.3	1.150	18
18	40.30	1624	23.6	23.6	22.0	19.8	493	454	399	203.4	188	6.510	1.1	1.024	19
19	35.89	1288	26.4	26.4	24.4	21.8	592	553	479	256.5	237	8.210	.86	.9116	20
20	31.96	1022	29.4	29.4	27.0	23.8	775	725	625	323.4	298	10.35	.68	.8118	21
21	28.46	810.1	33.1	32.7	29.8	26.0	940	895	754	407.8	370	13.05	.54	.7230	22
22	25.35	642.4	37.0	36.5	34.1	30.0	1150	1070	910	514.2	461	16.46	.43	.6438	23
23	22.57	509.5	41.3	40.6	37.6	31.6	1400	1300	1080	648.4	584	20.76	.34	.5733	24
24	20.10	404.0	46.3	35.3	41.5	35.6	1700	1570	1260	817.7	745	26.17	.27	.5106	25
25	17.90	320.4	51.7	50.4	45.6	38.6	2060	1910	1510	1031	903	33.00	.21	.4547	26
26	15.94	254.1	58.0	55.6	50.2	41.8	2500	2300	1750	1300	1118	41.62	.17	.4049	27
27	14.20	201.5	64.9	61.5	55.0	45.0	3030	2780	2020	1639	1422	52.48	.13	.3606	29
28	12.64	159.8	72.7	68.6	60.2	48.5	3670	3350	2310	2067	1759	66.17	.11	.3211	30
29	11.26	126.7	81.6	74.8	65.4	51.8	4300	3900	2700	2607	2207	83.44	.084	.2859	31
30	10.03	100.5	90.5	83.3	71.5	55.5	5040	4660	3020	3287	2534	105.2	.067	.2546	33
31	8.928	79.70	101	92.0	77.5	59.2	5920	5280	—	4145	2768	132.7	.053	.2268	34
32	7.950	63.21	113	101	83.6	62.6	7060	6250	—	5227	3137	167.3	.042	.2019	36
33	7.080	50.13	127	110	90.3	66.3	8120	7360	—	6591	4697	211.0	.033	.1798	37
34	6.305	39.75	143	120	97.0	70.0	9600	8310	—	8310	6168	266.0	.026	.1601	38
35	5.615	31.52	158	132	104	73.5	10900	8700	—	10480	6737	335.0	.021	.1426	38-39
36	5.000	25.00	175	143	111	77.0	12200	10700	—	13210	7877	423.0	.017	.1270	39-40
37	4.453	19.83	198	154	118	80.3	—	—	—	16660	9309	533.4	.013	.1131	41
38	3.965	15.72	224	166	126	83.6	—	—	—	21010	10666	672.6	.010	.1007	42
39	3.531	12.47	248	181	133	86.6	—	—	—	26500	11907	848.1	.008	.0897	43
40	3.145	9.88	282	194	140	89.7	—	—	—	33410	14222	1069	.006	.0799	44

¹ A mil is 1/1000 (one thousandth) of an inch.

² The figures given are approximate only, since the thickness of the insulation varies with different manufacturers.

³ The current-carrying capacity at 1000 C.M. per ampere is equal to the circular-mil area (Column 3) divided by 1000.

RECEIVING TUBE CLASSIFICATION CHART

		Cathode Volts		1.4	2.0	2.5 to 5.0	6.3	12.6 to 117
DIODE DETECTORS & RECTIFIERS								
Detectors	single			1A3				
	twin						(6H6, 6H6-GT, G), 7A6	12H6
	half-wave					1-v		12Z3, 35Z3, 35Z4-GT, 35Z5-GT, G, 45Z3, 45Z5-GT
	half-wave, with beam power amplifier							32L7-GT, 70L7-GT, 117L M7-GT, 117N7-GT, 117P7-GT
Rectifiers	half-wave, with power pentode							12A7, 25A7-GT, G
	full-wave	vacuum			(514, 5U4-G, 5X4-G, 5Z3), (5W4, 5W4-GT, G, 5Y3-GT, G, 5Z4, 5Y4-G, 80), (5V4-G, 83-v)	(6X5, 6X5-GT, G, 84), 6Y5, 6Z5, 6ZY5-G, 7Y4		
mercury gas						82, 83		
Rectifier-Doubles				Cold-Cathode Types: 0Z4, 0Z4-G.				(95Z6, 25Z6-GT, G, 25Z5, 25Y5), 50Y6-GT, G, 50Z7-G, 117Z6-GT, G
DIODE DETECTORS with AMPLIFIERS								
One Diode	with high-mu triode		(1H5-G, 1H5-GT), 1LH4					
	with high-mu triode, r-f pentode		3A8-GT*					
	with medium-mu triode, power pentode		1D8-GT					
	with pentode		155					
Two Diodes	with power pentode		1N6-G					
	with medium-mu triode		(1B5, 1H6-G)	55	(6SR7, 6R7, 6R7-G, 6R7-GT, 6S17, 6V7-G, 85), 6C7, 7E6		12SR7	
	with high-mu triode			2A6	(6SQ7, 6SQ7-GT, G, 6Q7, 6O7-G, 6O7-GT, 6B6-G, 617-G, 75), 7B6, 7C6	(12SQ7, 12SQ7-GT, G, 12O7-GT)		
with pentode		(1F7-G, 1F6)	2B7	(6B8, 6B8-G, 6B7, 6B7-S), 65F7, 7E7		12C8, 125F7		
CONVERTERS & MIXERS								
Pentagrid Converters		(1A7-G, 1A7-GT), 1R5, 1B7-GT, 1LA6	(1C7-G, 1C6), (1D7-G, 1A6)	2A7	(6SA7, 6SA7-GT, G, 6A8, 6A8-G, 6A8-GT, 6B8-G, 6A7, 6A7S), 7B8, 7Q7	(12SA7, 12SA7-GT, G, 12AB-GT)		
Triode-Hexode Converters					(6K8, 6K8-G, 6K8-GT)		12K8	
Triode-Heptode Converters					6J8-G, 7J7			
Octode Converters					7A8			
Pentagrid Mixers					(6L7, 6L7-G)			

Courtesy of R.C.A.

		VOLTAGE AMPLIFIERS, DETECTORS, OSCILLATORS		1G4-GT/G	(1H4-G, 30)	27, 56, 485	(6C5, 6C5-GT/G), (6J5, 6J5-GT, G, 7A4), (6P5-GT, G, 76), 6L5-G, 6AE5-GT, G, 37,	12J5-GT	
Triodes	medium-mu	single unit							
		twin unit		3A5*					
		twin plate					6C8-G, 6F8-G, 6J6, 65N7-GT	12AH7-GT, 12SN7-GT	
	high-mu	twin input					6AE6-G		
		with power pentode					6AE7-GT		
		with diode, power pentode			1D8-GT		6AD7-G		
Tetrodes	single unit						65F5, 65F5-GT, 6F5, 6F5-G, 6F5-GT), 6K5-G, 7B4	(125F5, 125F5-GT, 125F5-GT)	
	twin unit						(65C7, 7F7), 65L7-GT	125C7, 125L7-GT	
	with diode, r-f pentode			3A8-GT*					
Pentodes	remote cut-off					1D5-GT	35		
	sharp cut-off					32	24-A		
	remote cut-off			1T4, 1P5-GT	(1D5-GP, 1A4-P), 34	58	36	65S7, (6SK7, 6SK7-GT/G, 6K7, 6K7-G, 6K7-GT, 7B), (657, 657-G), (6U7-G, 6D6, 6E7), 6W7-G, 39, 44, 7A7, 6AB7, 6AC7, 7H7, 7B7	(125K7, 125K7-GT, 125K7-GT), 14A7, 12B7
	sharp cut-off, with triode						6F7, 6P7-G	128B-GT, 258B-GT	
Beam Tubes	semi-remote cut-off						65G7	125G7	
	sharp cut-off			(1N5-G, 1N5-GT), 1L4, 1LN5	(1E5-GP, 1B4-P), 15	57	6AG5, 65H7, (65J7, 65J7-GT, 6J7-G, 6J7-GT, 6D7), 77, 6C6, 7C7, 7G7, 1232	125H7, (125J7, 125J7-GT, 12J7-GT)	
	sharp cut-off, with diode, high-mu triode			3A8-GT*					
POWER AMPLIFIERS									
Triodes	low-mu	single unit				31	2A3, 45, 183, 483	6A3, 6B4-G	
		twin unit						6E6	
	high-mu	single unit			1G6-GT, G	(1J6-G, 19)	46, 53	6AC5-GT/G, 6C4, (6N7, 6N7-GT/G, 6A6), (6Y7-G, 79), 6Z7-G	25AC5-GT/G
Beam Tubes	without rectifier			(1O5-GT, G, 3O5-GT, G*), 115-GT			(6L6, 6L6-G), (6V6, 6V6-GT, G), 6Y6-G, 7A5, 7C5	(25L6, 25L6-GT, G), 25C6-G, 35A5, 35L6-GT/G, 50L6-GT	
	with rectifier							32L7-GT, 70L7-GT, 117L M7-GT, 117N7-GT, 117P7-GT	
Pentodes	single unit			1A5-GT, G, (154, 354*), 1C5-GT, G, 1LA4, 1LB4, (3A4*, 3O4*)	(1F5-G, 1F4), 1C5-G, 1J5-G, (3A4*, 3O4*)	2A5, 47, 59	(6F6, 6F6-G, 42), (6K6-GT, G, 41), 6G6-G, 38, 6A4, 89, 7B5	12A5, (25A6, 25A6-GT, G, 43), 25B6-G	
	twin unit								
	with diode & triode			1D8-GT				6AD7-G	
Direct-Coupled Amplifiers	with medium-mu triode								
	with rectifier							6AG7, 6B5, 6N6-G	
ELECTRON-RAY TUBES									
Single	with remote cut-off triode							6AB5/6N5, 6J5/6G5	
	with sharp cut-off triode							6E5	
Twin, without triode								6AD6-G, 6AF6-G	
GAS-TRIODES						2A4-G			

* Two 1F5-G's in one bulb.

* Filament arranged for either 1.4 volt or 2.8-volt operation.

VACUUM-TUBE BASE DIAGRAMS

The diagrams on the following pages show standard socket connections corresponding to the base designations in the column headed "Socket Connections" in the classified tube data tables. Footnotes under each table indicate in which group a given base diagram is to be found. Bottom views are shown throughout. Terminal designations are as follows:


- | | | | | |
|-------------------------|-------------------------------|--------------------------------|--------------------------------|-----------------------------------|
| A = Anode | G = Grid | K = Cathode | PBF = Beam-Form-
ing Plates | TA = Target
= Gas-Type
Tube |
| BP = Bayonet Pin | H = Heater | NC = No Conne-
ction | RC = Ray-Control
Electrode | U = Unit |
| D = Deflecting
Plate | IC = Internal Con-
nection | P = Plate (Anode) | S = Shell | SH = Internal Shield |
| F = Filament | IS = Internal Shield | P ₁ = Starter-Anode | | |

Alphabetical subscripts D, P, T and HX indicate, respectively, diode unit, pentode unit, triode unit or hexode unit in multi-unit types. Subscript M, T or CT indicates filament or heater tap.

Wherever the No. 1 pin of a metal-type tube in Table I is shown connected to the shell, the No. 1 pin in the glass (G or GT) equivalent is connected to an internal shield.


RECEIVING TUBE DIAGRAMS

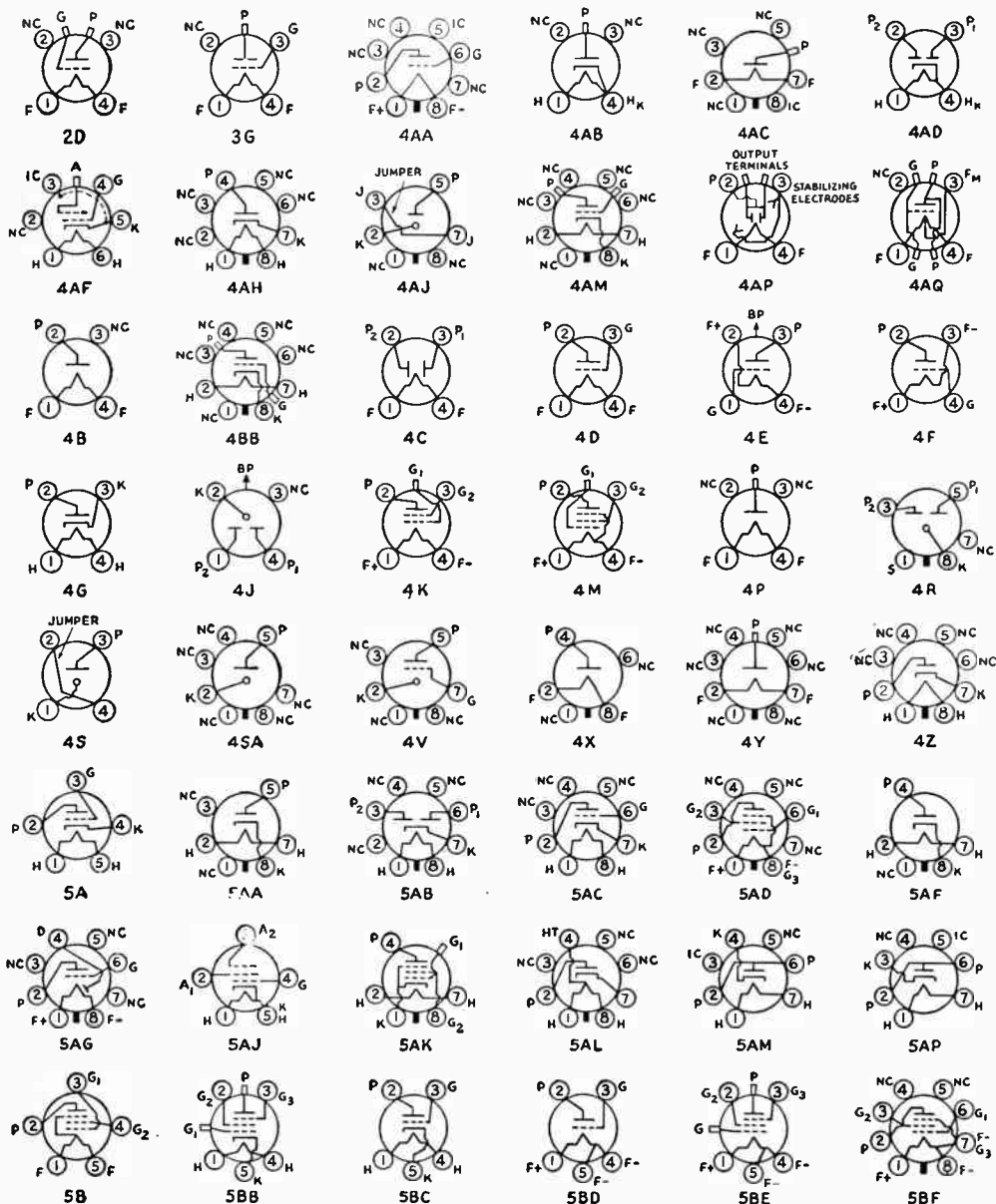Bottom views are shown. Terminal designations on sockets are shown above.




RECEIVING TUBE DIAGRAMS

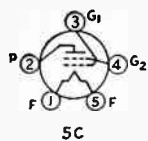
Bottom views are shown. Terminal designations on sockets are given on page 420.




5C

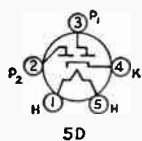


5D

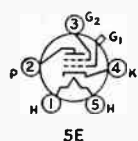


5E

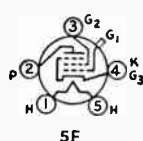


5F

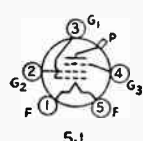


5J

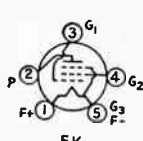

5K

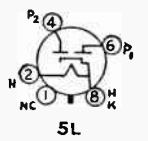

5L

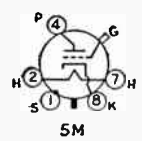


5M




5Q



5R

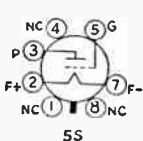

5S

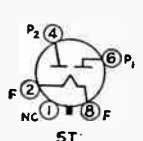


5T




5U



5Y

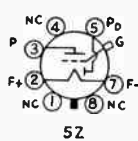

5Z

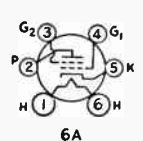


6A



6AA




6AB

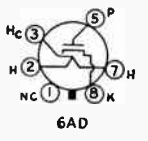


6AD




6AE

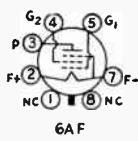


6AF

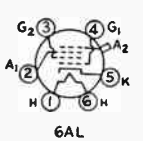


6AL

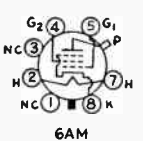


6AM

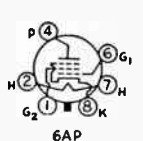


6AP

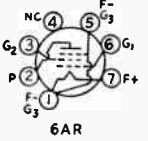


6AR

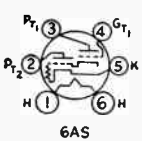

6AS

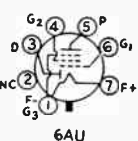


6AU

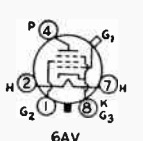

6AV




6AX

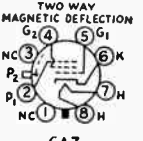


6AZ


TWO WAY MAGNETIC DEFLECTION

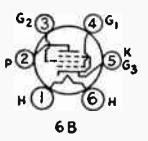


6B

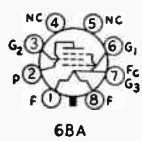

6BA

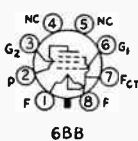


6BB

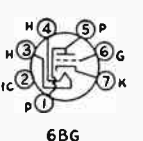


6BG




6BH

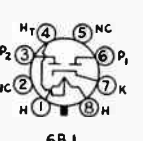


6BJ

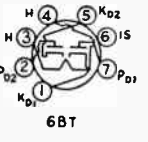


6BT

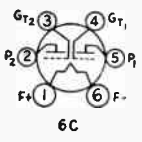


6C

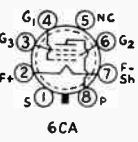


6CA

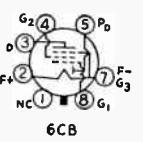


6CB

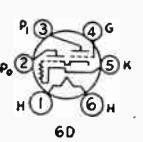


6D

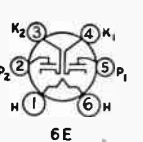


6E

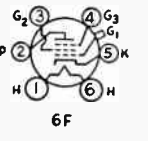


6F

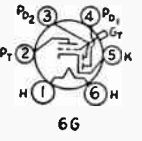


6G

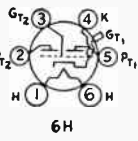


6H

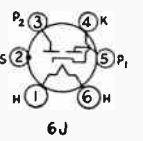


6J

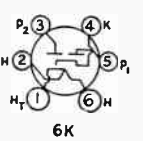


6K

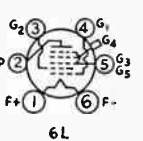


6L

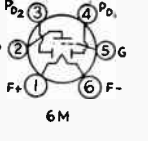


6M

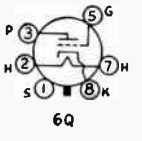


6Q

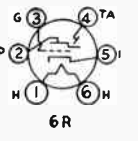


6R

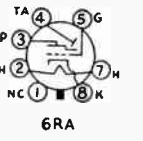


6RA

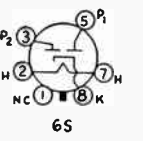


6S

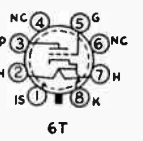


6T

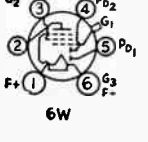


6W

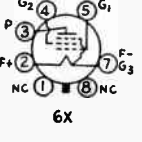


6X

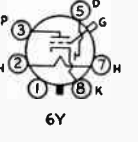


6Y

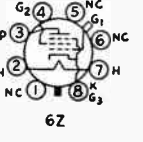

6Z

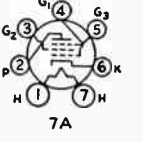


7A

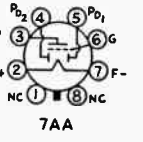

7AA

RECEIVING TUBE DIAGRAMS

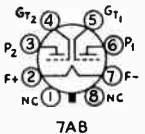Bottom views are shown. Terminal designations on sockets are given on page 420.




7AB



7AC




7AD

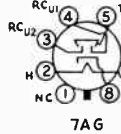


7AG



7AH

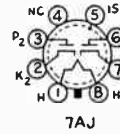


7AJ

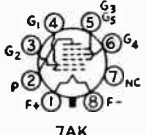

7AK



7AL

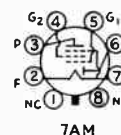


7AM




7AN




7AO

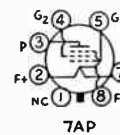


7AP

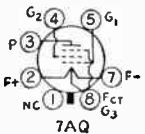


7AQ

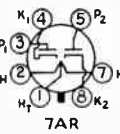

7AR

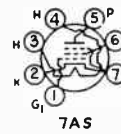

7AS

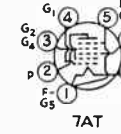


7AT



7AU



7AV

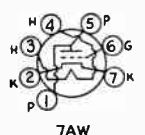


7AW



7AX



7AZ

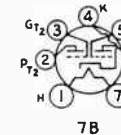


7B




7BA




7BB

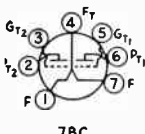

7BC

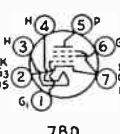

7BD

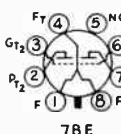

7BE




7BF




7BH




7BK

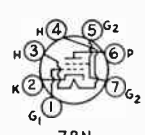


7BN

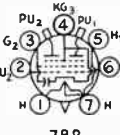


7BP

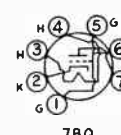

7BQ

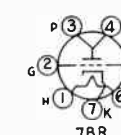


7BR

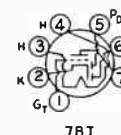


7BT




7C

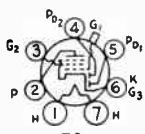


7D

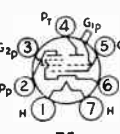

7E

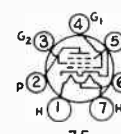


7F

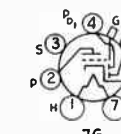


7G




7H

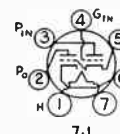


7J

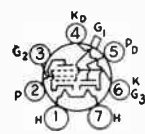


7K

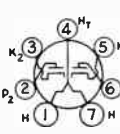


7L

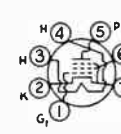


7PM

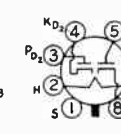


7Q

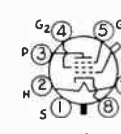


7R

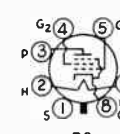

7S

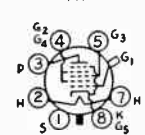


7T

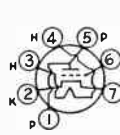


7TM



7U

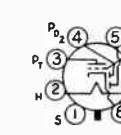


7V

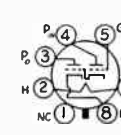

7W



7X

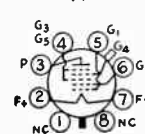


7Z




8A




8AA

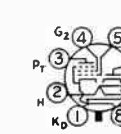

8AB

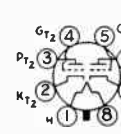


8AC

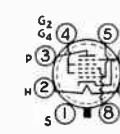


8AD

RECEIVING TUBE DIAGRAMS

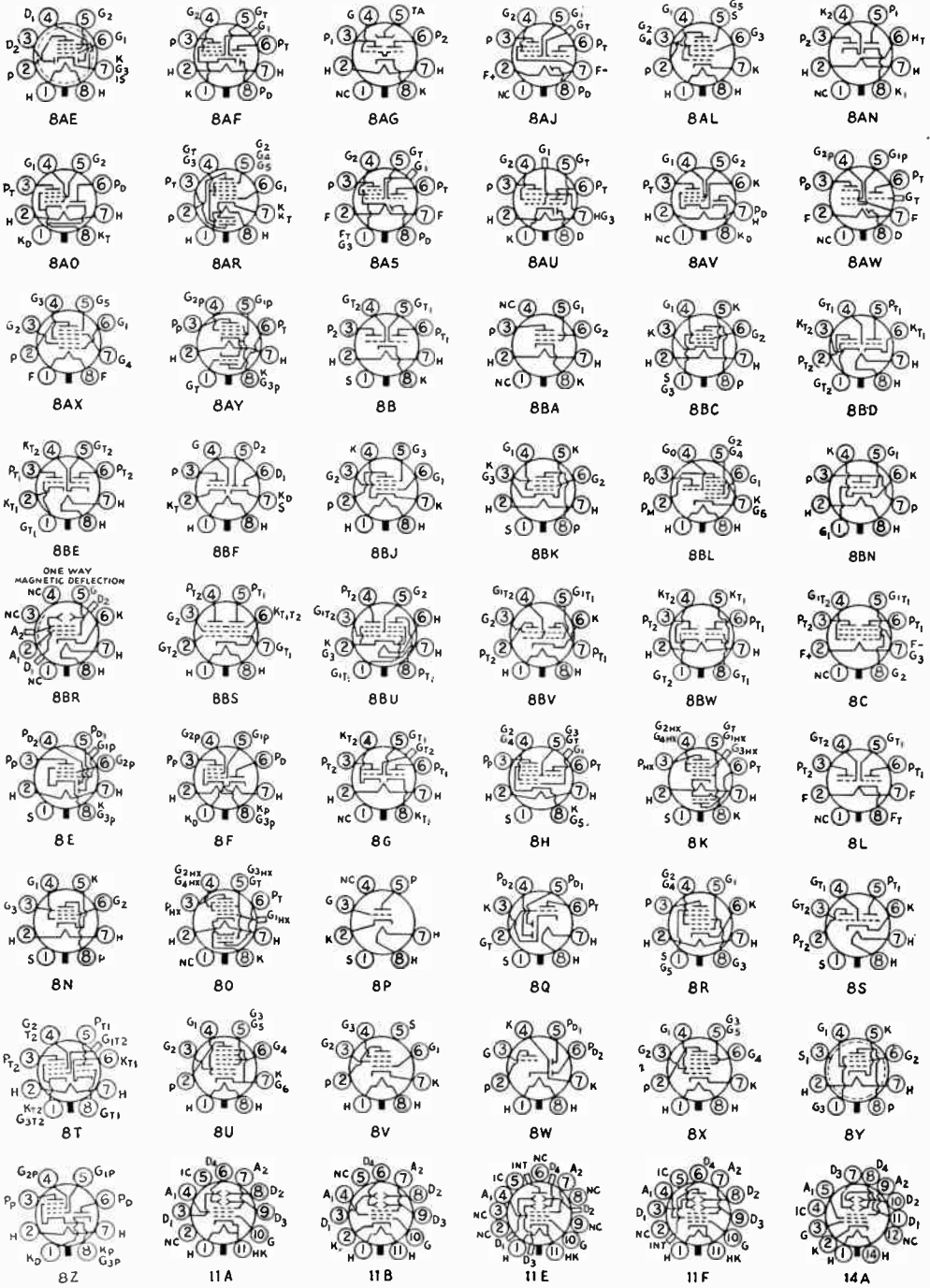Bottom views are shown. Terminal designations on sockets are given on page 120.



SUPPLEMENTARY BASE DIAGRAMS

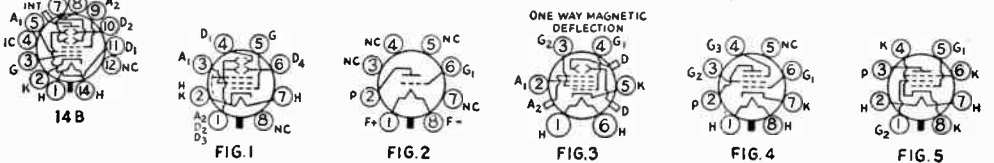

SUPPLEMENTARY BASE DIAGRAMS

Bottom views are shown. Terminal designations on sockets are given on page 420.

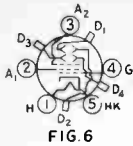


FIG. 6

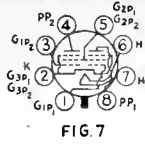


FIG. 7

TWO WAY MAGNETIC DEFLECTION

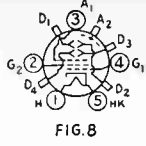


FIG. 8

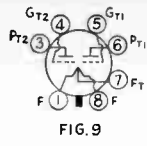


FIG. 9

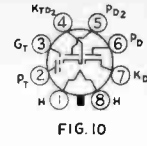


FIG. 10

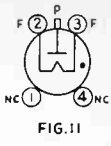


FIG. 11

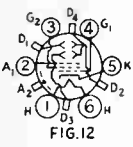


FIG. 12

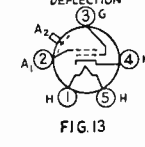


FIG. 13

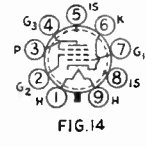


FIG. 14

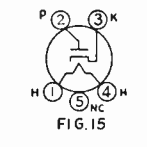


FIG. 15

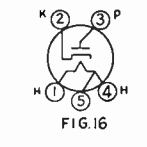


FIG. 16

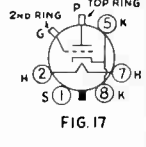


FIG. 17

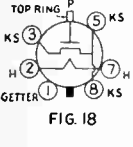


FIG. 18

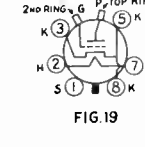


FIG. 19

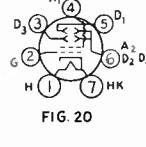


FIG. 20

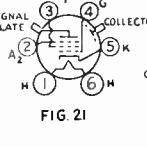


FIG. 21

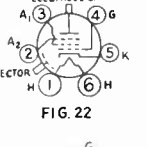


FIG. 22

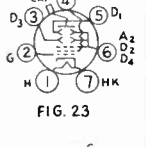


FIG. 23

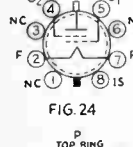


FIG. 24

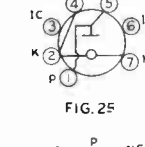


FIG. 25

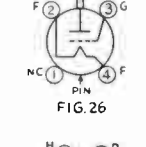


FIG. 26

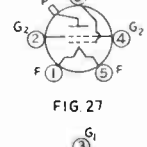


FIG. 27

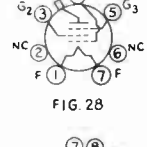


FIG. 28

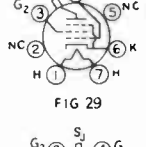


FIG. 29

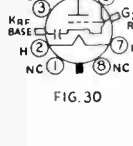


FIG. 30

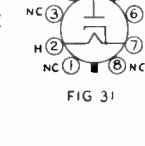


FIG. 31

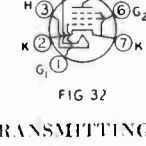


FIG. 32

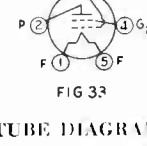


FIG. 33

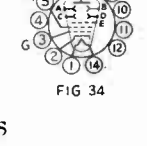


FIG. 34


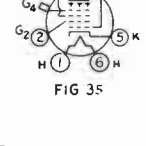


FIG. 35

TRANSMITTING TUBE DIAGRAMS

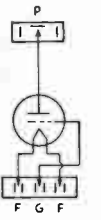
Bottom views are shown. Terminal designations on sockets are given on page 420.



T-1A




T-1AA

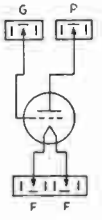


T-1AB




T-1B

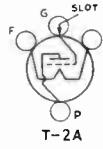


T-2A

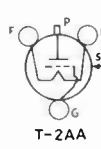


T-2AA

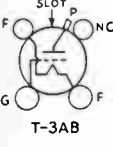


T-3AB

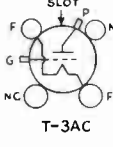


T-3AC

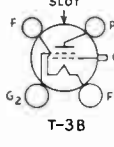


T-3B

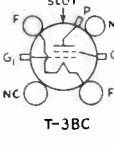

T-3BC

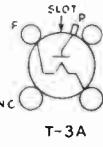


T-3A

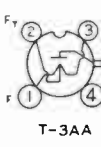


T-3AA




T-4AF

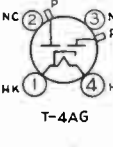


T-4AG

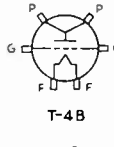


T-4B

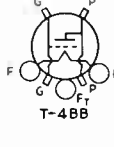


T-4BB

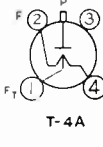


T-4A

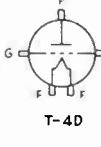

T-4D

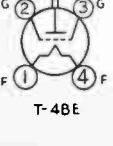


T-4BE

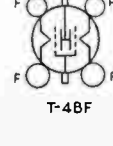


T-4BF




T-4BG

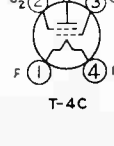


T-4C

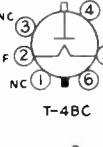


T-4BC

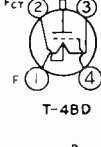

T-4BD

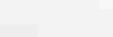


T-4CE

 


T-4CF



T-4CG

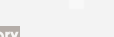

T-4CH

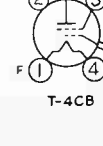


T-4CE



T-4CF

TRANSMITTING TUBE DIAGRAMS

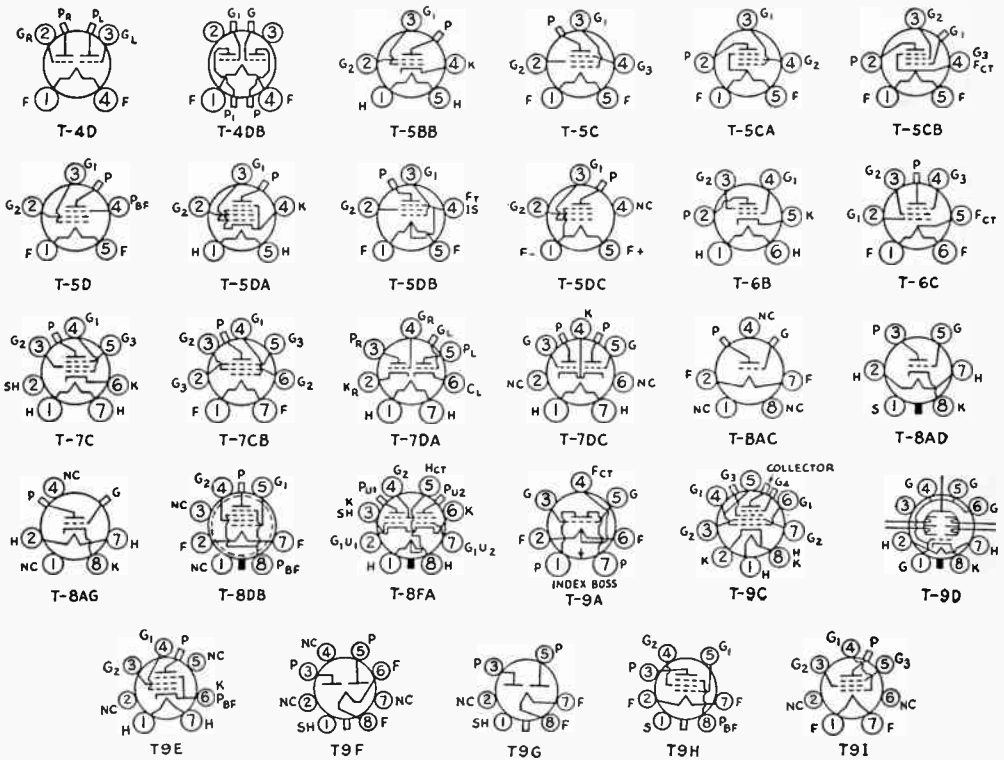Bottom views are shown. Terminal designations on sockets are given on page 420.



TUBE RATINGS

The data in the classified tube tables are of two kinds, maximum ratings, and typical operating conditions.

Vacuum tubes are designed to be operated within definite maximum (and minimum) ratings. These ratings are the maximum safe operating voltages and currents for the electrodes, based on inherent limiting factors such as permissible cathode temperature, emission, and power dissipation in electrodes. In addition to the maximum ratings for each type, performance data are given in the form of typical operating conditions.

In the transmitting-tube tables, maximum ratings for electrode voltage, current and dissipation are given separately from the typical operating conditions for the recommended classes of operation. In the receiving-tube tables, because of space limitations, ratings and operating data are combined. Where only one set of operating conditions appears, the positive electrode voltages shown (plate, screen, etc.) are, in general, also the maximum rated voltages for those electrodes.

The maximum ratings given for each transmitting type apply only when the tube is operated at frequencies lower than some specified value which depends on the design of the type. As the frequency is raised above the specified value, the radio-frequency current,

dielectric losses, and heating effects increase rapidly. Most types can be operated above their specified maximum frequency provided the plate voltage and plate input are reduced in accordance with the information given by the footnotes on maximum operating frequencies for full ratings.

For certain air-cooled transmitting tubes, there are two sets of maximum values, one designated as CCS (Continuous Commercial Service) ratings, the other ICAS (Intermittent Commercial and Amateur Service) ratings. Continuous Commercial Service is defined as that type of service in which long tube life and reliability of performance under continuous operating conditions are the prime consideration. Intermittent Commercial and Amateur Service is defined to include the many applications where the transmitter design factors of minimum size, light weight, and maximum power output are more important than long tube life. ICAS ratings are considerably higher than CCS ratings. They permit the handling of greater power, and although such use involves some sacrifice in tube life, the period over which tubes will continue to give satisfactory performance in intermittent service can be extremely long. Typical operating conditions given in the tables are ICAS ratings when applicable.

TABLE I — METAL RECEIVING TUBES

Characteristics given in this table apply to all tubes having type numbers shown, including metal tubes, glass tubes with "G" suffix, and bantam tubes with "GT" suffix. For "G" and "GT" tubes not listed (not having metal counterparts), see Tables II, VII, VIII and IX.

Type	Name	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
6A8	Pentagrid Converter	8A	Htr.	6.3	0.3	Osc.-Mixer	250	- 3.0	100	3.2	3.3	Anode-grid (No. 2) 250 volts max. thru 20,000-ohms				6A8	
6AB7 1853	Television Amp. Pentode	8N	Htr.	6.3	0.45	Class-A Amplifier	300	- 3.0	200 ²	3.2	12.5	700000	5000	3500	—	—	6AB7 1853
6AC7 1852	Television Amp. Pentode	8N	Htr.	6.3	0.45	Class-A Amplifier	300	- 2.0 ⁴	150 ²	2.5	10	750000	9000	6750	—	—	6AC7 1852
6AG7	Video Beam Power Amp.	8Y	Htr.	6.3	0.65	Class-A ₁ Amplifier ⁵	300	- 3.0	150	7.9	30.30.5	130000	11000	—	10000	3.0	6AG7
6B8	Duplex-Diode Pentode	8E	Htr.	6.3	0.3	Class-A Amplifier	250	- 3.0	125	2.3	9.0	650000	1125	730	—	—	6B8
6C5 ¹⁰	Triode Detector, Amplifier	6Q	Htr.	6.3	0.3	Class-A Amplifier	250	- 8.0	—	—	8.0	10000	2000	20	—	—	6C5
6F5	High-μ Triode	5M	Htr.	6.3	0.3	Class-A Amplifier	250	- 1.3	—	—	0.2	Plate current adjusted to 0.2 ma. with no signal				6F5	
6F6	Pentode Power Amplifier	7S	Htr.	6.3	0.7	Class-A Pentode	250	-16.5	250	6.5	34	80000	2500	100	7000	3.0	6F6
							315	-22.0	315	8.0	42	75000	2650	200	7000	5.0	
							250	-20.0	—	—	31	2600	2700	7.0	4000	0.85	
							375	-26.0	250	2.5	17	Power output for 2 tubes at stated load, plate-to-plate				10000	
350	-38.0	—	—	22.5	—	—	—	—	—	—	6000	18.0	—				
6H6 ¹⁵	Twin Diode	7Q	Htr.	6.3	0.3	Rectifier	Max. a.c. voltage per plate = 100 r.m.s. Max. output current 4.0 ma. d.c.										6H6
6J5	Detector Amplifier Triode	6Q	Htr.	6.3	0.3	Class-A Amplifier	250	- 8.0	—	9	7700	2600	20	—	—	6J5	
6J7 ¹⁵	Triple-Grid Detector, Amplifier	7R	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	100	0.5	2.0	1.5 meg.	1225	1500	—	—	6J7
							250	- 4.3	100	Cathode current 0.43 ma.			—	—	0.5 meg.	—	—
6K7	Triple-Grid Variable-μ Amplifier	7R	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	125	2.6	10.5	600000	1650	990	—	—	6K7
							250	-10.0	100	—			Oscillator peak volts = 7.0				
6K8	Triode Hexode Converter	8K	Htr.	6.3	0.3	Osc.-Mixer	250	- 3.0	100	6	2.5	Triode Plate (No. 2) 100 volts, 3.8 ma.				6K8	
							300	— ⁷	250	5.4-7.2	75-78	—	—	—	2500	6.5	
							200	— ⁸	200	3.0-4.6	51-54.5	—	—	—	4500	6.5	
							250	-14.0	250	5.0-7.3	72-79	22500	6000	—	2500	6.5	
							350	-18.0	250	2.5-7.0	54-66	33000	5200	—	4200	10.8	
							270	— ⁹	270	11-17	134-145	—	—	—	5000	18.5	
							250	-16.0	250	10-16	120-140	24500	5500	—	5000	14.5	
							270	-17.5	270	11-17	134-155	23500	5700	—	5000	17.5	
							360	— ¹⁰	270	5-17	88-100	—	—	—	9000	24.5	
							360	-22.5	270	5-15	88-132	Power output for 2 tubes. Load plate-to-plate				6600 ¹¹	26.5
360	-18.0	225	3.5-11	78-142	6000	31.0	—	—	—								
360	-22.5	270	5-16	88-205	3800	47.0	—	—	—								
6L6	Beam Power Amplifier	7AC	Htr.	6.3	0.9	Single-Tube A ₁ ⁶ Cathode Bias	250	—	250	5.5	5.3	800000	1100	—	—	6L6	
6L7	Pentagrid Mixer Amplifier	7T	Htr.	6.3	0.3	Mixer	250	- 3.0	100	5.5	5.3	800000	1100	—	—	6L7	
							250	- 6.0	150	8.3	3.3	Over 1 meg.	Oscillator-grid (No. 3) voltage = -15.0				
6N7	Twin Triode	8B	Htr.	6.3	0.8	Class-B Amplifier	300	0	—	35-70	—	—	—	8000	10.0	6N7	
6Q7	Duplex-Diode Triode	7V	Htr.	6.3	0.3	Triode Amplifier	250	- 3.0	—	—	1.1	58000	1200	70	—	—	6Q7
6R7	Duplex-Diode Triode	7V	Htr.	6.3	0.3	Triode Amplifier	250	- 9.0	—	—	9.5	8500	1900	16	10000	0.28	6R7
6S7 ¹²	Triple-Grid Variable-μ	7R	Htr.	6.3	0.15	Class-A Amplifier	250	- 3.0	100	2.0	8.5	1000000	1750	1750	—	—	6S7
6SA7	Pentagrid Converter	8R ¹²	Htr.	6.3	0.3	Osc.-Mixer	250	0 ¹³	100	8.0	3.4	800000	Grid No. 1 Resistor 20000 ohms				6SA7
6SC7	Twin Triode Amplifier	8S	Htr.	6.3	0.3	Class-A Amplifier	250	- 2.0	—	—	2.0	53000	1325	70	—	—	6SC7
6SF5	High-μ Triode	6AB	Htr.	6.3	0.3	Class-A Amplifier	250	- 2.0	—	—	0.9	66000	1500	100	—	—	6SF5
6SF7	Diode Variable-μ Pentode	7AZ	Htr.	6.3	0.3	Class-A Amplifier	250	- 1.0	100	3.3	12.4	700000	2050	—	—	—	6SF7
6SG7	Triple-Grid Semi-Variable-μ	8BK	Htr.	6.3	0.3	H. F. Amplifier	250	- 2.5	150	3.4	9.2	Over 1 meg.	4000	—	—	—	6SG7
6SH7	Triple-Grid Amplifier	8BK	Htr.	6.3	0.3	H. F. Amplifier	250	- 1.0	150	4.1	10.8	900000	4900	—	—	—	6SH7

TABLE I—METAL RECEIVING TUBES—Continued

Type	Name	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
6SJ7 ¹⁶	Triple-Grid Amplifier	8N	Htr.	6.3	0.3	Class-A Amplifier	250	- 3.0	100	0.8	3	1500000	1650	2500	—	—	6SJ7
6SK7	Triple-Grid Variable- μ	8N	Htr.	6.3	0.3	Class-A Amplifier	250	- 3.0	100	2.4	9.2	800000	2000	1600	—	—	6SK7
6SQ7	Duplex-Diode Triode	8Q	Htr.	6.3	0.3	Class-A Amplifier	250	- 2.0	—	—	0.8	91000	1100	100	—	—	6SQ7
6SR7	Duplex-Diode Triode	8Q	Htr.	6.3	0.3	Class-A Amplifier	250	- 9.0	—	—	9.5	8500	1900	16	—	—	6SR7
6SS7	Triple-Grid Variable- μ	8N	Htr.	6.3	0.15	Class-A Amplifier	250	- 3.0	100	2.0	9.0	1000000	1850	—	—	—	6SS7
6ST7	Duplex-Diode Triode	8Q	Htr.	6.3	0.15	Class-A Amplifier	250	- 9.0	—	—	9.5	8500	1900	16	—	—	6ST7
6T7	Duplex-Diode Triode	7V	Htr.	6.3	0.15	Class-A Amplifier	250	- 3.0	—	—	1.2	62000	1050	65	—	—	6T7
6V6	Beam Power Amplifier	7AC	Htr.	6.3	0.45	Class-AB Amplifier 2 Tubes	250	-12.5	250	4.5 7.0	45-47	52000	4100	218	5000	4.5	6V6
							250	-15.0	250	5 13	70-79	60000	3750	—	10000	10.0	
							285	-19.0	285	4 13.5	70-92	65000	3600	—	8000	14.0	
1611	Pentode Power Amplifier	7S	Htr.	6.3	0.7	Relay Tube	Characteristics same as 6F6										1611
1612	Pentagrid Amplifier	7T	Htr.	6.3	0.3	Class-A Amplifier	250	- 3.0	100	6.5	5.3	600000	1100	880	—	—	1612
1620	Triple-Grid Det.-Amp.	7R	Htr.	6.3	0.3	Class-A Amplifier	Characteristics same as 6J7										1620
1621	Power Amplifier Pentode	7S	Htr.	6.3	0.7	Class-A, Pentode P. P. Class-A Triode ² P. P.	300	- 30.0	300	6.5 13	38 69	—	—	—	4000	5.0	1621
							327.5	- 27.5 ¹⁴	—	—	55 59	—	—	—	5000	2.0	
1622	Beam Power Amplifier	7AC	Htr.	6.3	0.9	Class-A Amplifier	300	- 20.0	250	4 10.5	86 125	—	—	4000	10.0	1622	
1851	Television Amp. Pentode	7R	Htr.	6.3	0.45	Class-A Amplifier	300	- 2.0 ⁴	150 ²	2.5	10	750000	9000	6750	—	—	1851

¹ See Receiving Tube Diagrams.

² From fixed screen supply. If series resistor from plate supply is used, value for 6A87/1853 is 30,000 ohms, for 6AC7/1852 and 1851 60,000 ohms. Series resistor gives variable- μ characteristic, fixed screen supply gives sharp cut-off.

³ Screen tied to plate.

⁴ Cathode bias resistor should be adjusted for plate current of 10 ma.; minimum value 160 ohms.

⁵ Typical operation for 4-Mc.-bandwidth video voltage amplifier; 70 volts output with 4 volts input.

⁶ Subscript 1 indicates no grid-current flow.

Subscript 2 indicates grid-current flow over part of input cycle.

⁷ Cathode resistor 170 ohms. ⁸ Cathode resistor 220 ohms.

⁹ Cathode resistor 125 ohms.

¹⁰ Cathode resistor 250 ohms.

¹¹ Output 18 watts with 3800-ohm load.

¹² For 6SA7GT, use Base Diagram 8AD.

¹³ Grid bias - 2 volts if separate oscillator excitation is used.

¹⁴ Cathode resistor 500 ohms.

¹⁵ Types G or GT have internal shield connected to number one pin.

¹⁶ Also type "6SJ7Y".

TABLE II—6.3-VOLT GLASS TUBES WITH OCTAL BASES

(For "G" and "GT" -Type Tubes Not Listed Here, See Equivalent Type in Table I; Characteristics and Connections Will Be Identical)

Type	Name	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
2C22	Triode Amplifier	4AM	Htr.	6.3	0.3	Class-A Amplifier	300	- 10.5	—	—	11	6600	3000	20	—	—	2C22
						Class-A Amplifier	250	- 45.0	—	—	60	800	—	4.2	2500	3.75	
6A5G	Triode Power Amplifier	6T	Htr.	6.3	1.0	Push-Pull Class AB	325	- 68.0	—	—	80 ²	—	5250	—	3000	15.0	6A5G
						Push-Pull Class AB	325	850-ohm cathode resistor	80 ²	—	5000	10.0					
						—	250	0	Input	5.0	40000	1800	72	8000	3.5		
6AB6G	Direct-Coupled Amplifier	7AU	Htr.	6.3	0.5	Class-A Amplifier	250	0	—	—	34	—	—	—	—	6AB6G	
						—	250	0	Output	5.0 ²	—	—	—	—			
6AC5G	High- μ Power Amplifier Triode	6Q	Htr.	6.3	0.4	Push-Pull Class-B	250	0	—	—	32	36700	3400	125	10000	8.0	6AC5G
						Dynamic-Coupled Amp.	250	—	—	—	—	—	—	7000	3.7		
6AC6G	Direct-Coupled Amplifier	7AU	Htr.	6.3	1.1	Class-A Amplifier	180	0	—	—	7.0	—	3000	54	4000	3.8	6AC6G
						—	180	0	Output	45	—	—	—	—			
6AD5G	High- μ Triode	6Q	Htr.	6.3	0.3	Class-A Amplifier	250	- 2.0	—	—	0.9	—	1500	100	—	6AD5G	
6AD6G	Electron-Ray Tube	7AG	Htr.	6.3	0.15	Indicator Tube	100	—	—	—	—	—	0 for 90°, - 23 for 135°, 45 for 0°. Target current 1.5 ma.			6AD6G	
6AD7G	Triode-Pentode	8AY	Htr.	6.3	0.85	Triode Amplifier	250	- 25.0	—	—	4.0	19000	325	—	—	6AD7G	
						Pentode Amplifier	250	- 16.5	250	6.5	34	80000	2500	—	7000		3.2
6AE5G	Triode Amplifier	6Q	Htr.	6.3	0.3	Class-A Amplifier	95	- 15.0	—	—	7.0	3500	1200	4.2	—	6AE5G	
6AE6G	Twin-Plate Triode	7AH	Htr.	6.3	0.15	Indicator Control	250	- 1.5	—	—	6.5 ⁴	25000	1000	25	—	6AE6G	
							250	- 1.5	—	—	4.5 ⁵	35000	950	33	—		

TABLE II—6.3-VOLT GLASS TUBES WITH OCTAL BASES—Continued

Type	Name	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
6AE7GT	Twin-Input Triode	7AX	Htr.	6.3	0.5	Driver Amplifier	250	-13.5	—	—	5.0	9300	1500	14	—	—	6AE7GT
6AF5G	Triode Amplifier	6Q	Htr.	6.3	0.3	Class-A Amplifier	180	-18.0	—	—	7.0	—	1500	7.4	—	—	6AF5G
6AF7G	Twin Electron Ray	8AG	Htr.	6.3	0.3	Indicator Tube	—	—	—	—	—	—	—	—	—	—	6AF7G
6AG6G	Power Amplifier Pentode	7S	Htr.	6.3	1.25	Class-A Amplifier	250	-6.0	250	6.0	32	—	10000	—	8500	3.75	6AG6G
6AH5G	Beam Power Amplifier	6AP	Htr.	6.3	0.9	Class-A Amplifier	350	-18	250	—	—	33000	5200	—	4200	10.8	6AH5G
6AH7GT	Twin Triode	8BE	Htr.	6.3	0.3	Converter and Amp.	250	-9.0	—	—	12 ³	6600	2400	16	—	—	6AH7GT
6AL6G	Beam Power Amplifier	6AM	Htr.	6.3	0.9	Class-A Amplifier	250	-14.0	250	5.0	72	22500	6000	—	2500	6.5	6AL6G
6B4G	Triode Power Amplifier	5S	Fil.	6.3	1.0	Power Amplifier	—	—	—	—	—	—	—	—	—	—	6B4G
6B6G	Duplex-Diode High- μ Triode	7V	Htr.	6.3	0.3	Detector-Amplifier	—	—	—	—	—	—	—	—	—	—	6B6G
6C8G	Twin Triode	8G	Htr.	6.3	0.3	Amp. 1 Section	250	-4.5	—	—	3.1	26000	1450	38	—	—	6C8G
6D8G	Pentagrid Converter	8A	Htr.	6.3	0.15	Converter	250	-3.0	100	Cathode current 13.0 Ma.			Anode grid (No. 2) Volts = 250 ³			6D8G	
6E8G	Triode-Hexode Converter	8O	Htr.	6.3	0.3	Osc.-Mixer	250	-2.0	—	—	—	Triode Plate 150 volts			6E8G		
6F8G	Twin Triode	8G	Htr.	6.3	0.6	Amplifier	250	-8.0	—	—	9 ³	7700	2600	20	—	—	6F8G
6G6G	Pentode Power Amplifier	7S	Htr.	6.3	0.15	Class-A Amplifier	180	-9.0	180	2.5	15	175000	2300	400	10000	1.1	6G6G
6H4GT	Diode Rectifier	5AF	Htr.	6.3	0.15	Detector	180	-12.0	—	—	—	4750	2000	9.5	12000	0.25	6H4GT
6H8G	Duo-Diode High- μ Pentode	8E	Htr.	6.3	0.3	Class-A Amplifier	100	—	—	—	4.0	—	—	—	—	—	6H8G
6J8G	Triode Heptode	8H	Htr.	6.3	0.3	Converter	250	-2.0	100	—	8.5	650000	2400	—	—	—	6J8G
6K5G	High- μ Triode	5U	Htr.	6.3	0.3	Class-A Amplifier	250	-3.0	—	—	1.1	50000	1400	70	—	—	6K5G
6K6G	Pentode Power Amplifier	7S	Htr.	6.3	0.4	Class-A Amplifier	—	—	—	—	—	—	—	—	—	—	6K6G
6L5G	Triode Amplifier	6Q	Htr.	6.3	0.15	Class-A Amplifier	250	-9.0	—	—	8.0	—	1900	17	—	—	6L5G
6M6G	Power Amplifier Pentode	7S	Htr.	6.3	1.2	Class-A Amplifier	250	-6.0	250	4.0	36	—	9500	—	7000	4.4	6M6G
6M7G	Triple-Grid Amplifier	7R	Htr.	6.3	0.3	R. F. Amplifier	250	-2.5	125	2.8	10.5	900000	3400	—	—	—	6M7G
6M8GT	Diode Triode Pentode	8AU	Htr.	6.3	0.6	Triode Amplifier	100	—	—	—	0.5	91000	1100	—	—	—	6M8GT
6N6G	Direct-Coupled Amplifier	7AU	Htr.	6.3	0.8	Pentode Amplifier	100	-3.0	100	—	8.5	200000	1900	—	—	—	6N6G
6P5G	Triode Amplifier	6Q	Htr.	6.3	0.3	Power Amplifier	250	-13.5	—	—	5.0	9500	1450	13.8	—	—	6P5G
6P7G	Triode-Pentode	7U	Htr.	6.3	0.3	Class-A Amplifier	—	—	—	—	—	—	—	—	—	—	6P7G
6P8G	Triode-Hexode Converter	8K	Htr.	6.3	0.8	Osc.-Mixer	250	-2.0	75	1.4	1.5	Triode Plate 100 v. 2.2 ma.			6P8G		
6Q6G	Diode-Triode	6Y	Htr.	6.3	0.15	Class-A Amplifier	250	-3.0	—	—	1.2	—	1050	65	—	—	6Q6G
6R6G	Pentode Amplifier	6AA	Htr.	6.3	0.3	Class-A Amplifier	250	-3.0	100	1.7	7.0	—	1450	1160	—	—	6R6G
6S6GT	Triple-Grid Variable- μ	5AK	Htr.	6.3	0.45	R.F. Amplifier	250	-2.0	100	3.0	13	350000	4000	—	—	—	6S6GT
6SD7GT	Triple-Grid Semi-Variable- μ	8N	Htr.	6.3	0.3	R.F. Amplifier	250	-2.0	100	1.9	6.0	1000000	3600	—	—	—	6SD7GT
6SE7GT	Triple-Grid Amplifier	8N	Htr.	6.3	0.3	R.F. Amplifier	250	-1.5	100	1.5	4.5	1100000	3400	3750	—	—	6SE7GT
6SL7GT	Twin Triode	8BD	Htr.	6.3	0.3	Amplifier	250	-2.0	—	—	2.3 ³	44000	1600	70	—	—	6SL7GT
6SN7GT	Twin Triode	8BD	Htr.	6.3	0.6	Amplifier	250	-8.0	—	—	9.0 ³	7700	2600	20	—	—	6SN7GT
6T6GM	Triple-Grid Amplifier	6Z	Htr.	6.3	0.45	R.F. Amplifier	250	-1.0	100	2.0	10	1000000	5500	—	—	—	6T6GM
6U6GT	Beam Power Amplifier	7AC	Htr.	6.3	0.75	Class-A Amplifier	200	-14.0	135	3.0	56	20000	6200	—	3000	5.5	6U6GT
6U7G	Triple-Grid Variable- μ	7R	Htr.	6.3	0.3	R.F. Amplifier	—	—	—	—	—	—	—	—	—	—	6U7G
6V7G	Duplex Diode-Triode	7V	Htr.	6.3	0.3	Detector-Amplifier	—	—	—	—	—	—	—	—	—	—	6V7G
6W6GT	Beam Power Amplifier	7AC	Htr.	6.3	1.25	Class-A Amplifier	135	-9.5	135	12.0	61.0	—	9000	215	2000	3.3	6W6GT
6W7G	Triple-Grid Det. Amp.	7R	Htr.	6.3	0.15	Class-A Amplifier	250	-3.0	100	2.0	0.5	1500000	1225	1850	—	—	6W7G
6X6G	Electron-Ray Tube	7AL	Htr.	6.3	0.3	Indicator Tube	250	—	—	—	—	—	—	—	—	—	6X6G
6Y6G	Beam Power Amplifier	7AC	Htr.	6.3	1.25	Class-A Amplifier	135	-13.5	135	3.0	60.0	9300	7000	—	2000	3.6	6Y6G
6Y7G	Twin Triode Amplifier	8B	Htr.	6.3	0.3	Class-B Amplifier	—	—	—	—	—	—	—	—	—	—	6Y7G

TABLE II — 6.3-VOLT GLASS TUBES WITH OCTAL BASES — *Continued*

Type	Name	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
6Z7G	Twin Triode Amplifier	8B	Htr.	6.3	0.3	Class-B Amplifier	180	0	—	—	8.4 ²	—	—	—	12000	4.2	6Z7G
							135	0	—	—	6.0 ³	—	—	—	9000	2.5	
717A	Pentode Amplifier	8BK ¹²	Htr.	6.3	0.175	Class-A Amplifier	120	- 2.0	120	2.5	7.5	390000	4000	—	—	—	717A
1223	Pentode Amplifier	7R	Htr.	6.3	0.3	Class-A Amplifier	Characteristics same as 6C6 — Table IV										1223
1231	Pentode Amplifier	8V	Htr.	6.3	0.45	Class-A Amplifier	300	- 2.5 ⁴	150	2.5	10	700000	5500	3850	—	—	1231
1635	Twin Triode Amplifier	8B	Htr.	6.3	0.6	Class-B Amplifier	400	0	—	—	10 ² 63	—	—	—	14000	17	1635
2C21/ 1642	Twin-Triode Amplifier	7BH	Htr.	6.3	0.6	Class-A Amplifier	250	-16.5	—	—	8.3	7600	1375	10.4	—	—	2C21/ 1642
7000	Low-Noise Amplifier	7R	Htr.	6.3	0.3	Class-A Amplifier	Characteristics same as Type 6J7 — Table I										7000

¹ Refer to Receiving Tube Diagrams. No connection to Pin No. 1.
² No-signal value for 2 tubes.
³ Plate No. 1, remote cut-off.

⁴ Plate No. 2, sharp cut-off.
⁵ Through 200-ohm cathode resistor.
⁶ Common plate.

⁷ Metal-sprayed glass envelope.
⁸ Through 20,000-ohm dropping resistor.
¹⁰ Also type MG.

¹¹ Screen tied to plate.
¹² Low-loss phenolic base.

TABLE III — 7-VOLT LOKTAL-BASE TUBES

For other loktal-base types see Tables VIII, IX, X and XIII.

Type	Name	Socket Connections	Cathode	Heater*		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen ² Current Ma.	Plate ¹ Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
7A4	Triode Amplifier	5 AC	Htr.	7.0	0.32	Class-A Amplifier	250	- 8.0	—	—	9.0	7700	2600	20	—	—	7A4
7A5	Beam Power Amplifier	6 AT	Htr.	7.0	0.75	Class-A ¹ Amplifier	125	- 9.0	125	3.2 8	37.5 40	17000	6100	—	2700	1.9	7A5
7A6	Twin Diode	7 AJ	Htr.	7.0	0.16	Rectifier	Max. A.C. volts per plate — 150. Max. Output current — 10 ma.										7A6
7A7	Remote Cut-off Pentode	8 V	Htr.	7.0	0.32	R.F. Amplifier	250	- 3.0	100	2.0	8.6	800000	2000	1600	—	—	7A7
7A8	Multigrid Converter	8 U	Htr.	7.0	0.16	Osc.-Mixer	250	- 3.0	100	3.1	3.0	50000	Anode-grid 250 volts max. ²			7A8	
7B4	High- μ Triode	5 AC	Htr.	7.0	0.32	Class-A Amplifier	250	- 2.0	—	—	0.9	66000	1500	100	—	—	7B4
7B5	Pentode Power Amplifier	6 AE	Htr.	7.0	0.43	Class-A ¹ Amplifier	250	-18.0	250	5.5 10	32 33	68000	2300	—	7600	3.4	7B5
7B6	Duo-Diode Triode	8 W	Htr.	7.0	0.32	Class-A Amplifier	250	- 2.0	—	—	1.0	91000	1100	100	—	—	7B6
7B7	Remote Cut-off Pentode	8 V	Htr.	7.0	0.16	R.F. Amplifier	250	- 3.0	100	2.0	8.5	700000	1700	1200	—	—	7B7
7B8	Pentagrid Converter	8 X	Htr.	7.0	0.32	Osc.-Mixer	250	- 3.0	100	2.7	3.5	360000	Anode-grid 250 volts max. ²			7B8	
7C5	Tetrode Power Amplifier	6 AA	Htr.	7.0	0.48	Class-A ¹ Amplifier	250	-12.5	250	4.5 7	45 47	52000	4100	—	5000	4.5	7C5
7C6	Duo-Diode Triode	8 W	Htr.	7.0	0.16	Class-A Amplifier	250	- 1.0	—	—	1.3	100000	1000	100	—	—	7C6
7C7	Pentode Amplifier	8 V	Htr.	7.0	0.16	R.F. Amplifier	250	- 3.0	100	0.5	2.0	2 mes.	1300	—	—	—	7C7
7D7	Triode-Hexode Converter	8 AR	Htr.	7.0	0.48	Osc.-Mixer	250	- 3.0	Triode Plate (No. 3) 150 v. 3.5 ma.								7D7
7E6	Duo-Diode Triode	8 W	Htr.	7.0	0.32	Class-A Amplifier	250	- 9.0	—	—	9.5	8500	1900	16	—	—	7E6
7E7	Duo-Diode Pentode	8W	Htr.	7.0	0.32	Class-A Amplifier	250	- 3.0	100	1.6	7.5	700000	1300	—	—	—	7E7
7F7	Twin Triode	8AC	Htr.	7.0	0.32	Class-A Amplifier ³	250	- 2.0	—	—	2.3	44000	1600	70	—	—	7F7
7F8	Twin Triode	8BW	Htr.	6.3	0.30	R.F. Amplifier	250	- 2.5	—	—	10.0	10400	5000	—	—	—	7F8
							180	- 1.0	—	—	12.0	8500	7000	—	—		
7G7/ 1232	Triple-Grid Amplifier	8 V	Htr.	7.0	0.48	Class-A Amplifier	250	- 2.0	100	2.0	6.0	800000	4500	—	—	—	7G7/ 1232
7G8/ 1206	Dual Tetrode	8BV	Htr.	6.3	0.30	R.F. Amplifier ³	250	- 2.5	100	0.8	4.5	225000	2100	—	—	—	7G8/ 1206
7H7	Triple-Grid Semi-Variable- μ	8 V	Htr.	7.0	0.32	R.F. Amplifier	250	- 2.5	150	2.5	9.0	1000000	3500	—	—	—	7H7
7J7	Triode-Hexode Converter	8 AR	Htr.	7.0	0.32	Osc.-Mixer	250	- 3.0	100	2.9	1.3	Triode Plate 250 v. Max. ²					7J7
7K7	Duo-Diode High- μ Triode	8BF	Htr.	7.0	0.32	Class-A Amplifier	250	- 2.0	—	—	2.3	44000	1600	70	—	—	7K7
7L7	Triple-Grid Amplifier	8 V	Htr.	7.0	0.32	Class-A Amplifier	250	- 1.5	100	1.5	4.5	100000	3100	Cathode Resistor 250 ohms		7L7	

TABLE III—7-VOLT LOKTAL-BASE TUBES—Continued

Type	Name	Socket Connections	Cathode	Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current ¹ Ma.	Plate Current ¹ Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
7N7	Twin Triode	8AC	Htr.	7.0	0.6	Class-A Amplifier ²	250	- 8.0	—	—	9.0	7700	2600	20	—	—	7N7
7Q7	Pentagrid Converter	8AL	Htr.	7.0	0.32	Osc.-Mixer	250	0	100	8.0	3.4	800000	Grid No. 1 resistor	20000 ohms	—	—	7Q7
7R7	Duo-Diode Pentode	8AE	Htr.	7.0	0.32	Class-A Amplifier	250	- 1.0	100	1.7	5.7	1000000	3200	—	—	—	7R7
7S7	Triode Hexode Converter	8BL	Htr.	7.0	0.32	Osc.-Mixer	250	- 2.0	100	2.2	1.7	2000000	Triode Plate 250 v. Max. ²		—	—	7S7
7T7	Triple-Grid Amplifier	8V	Htr.	7.0	0.32	Class-A Amplifier	250	- 1.0	150	4.1	10.8	900000	4900	—	—	—	7T7
7V7	Triple-Grid Amplifier	8V	Htr.	7.0	0.48	Amplifier	300	— ¹	150 ²	3.9	9.6	300000	5800	—	—	—	7V7
7W7	Triple-Grid Variable- μ	8BJ	Htr.	7.0	0.48	Class-A Amplifier	300	- 2.2	150	3.9	10	300000	5800	—	—	—	7W7
XXL	Triode Oscillator	5AC	Htr.	7.0	0.32	Oscillator	250	- 8.0	—	—	8.0	—	2300	20	—	—	XXL

¹ Values to left of diagonal lines are for "no-signal" condition; values to right are "with signal." ² Applied through 20000-ohm dropping resistor. ³ Each section. ⁴ Cathode bias resistor, 160 ohms. ⁵ From fixed screen supply. If series resistor from plate supply is used, value should be 40,000 ohms. Series resistor gives extended cut-off (variable- μ) characteristic, fixed screen supply gives sharp cut-off.

TABLE IV—6.3-VOLT GLASS RECEIVING TUBES

Type	Name	Base ¹	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
					Volts	Amps.												
6A3	Triode Power Amplifier	4-pin M.	4D	Fil.	6.3	1.0	Class-A Amplifier	250	- 45	—	—	60	800	5250	4.2	2500	3.5	6A3
							Push-Pull Amplifier	300	- 62	Fixed Bias Self Bias ³		40	Power output for 2 tubes load plate-to-plate		3000	15		
6A4 ³	Pentode Power Amplifier	5-pin M.	5B	Fil.	6.3	0.3	Class-A Amplifier	180	- 12.0	180	3.9	22	45500	2200	100	8000	1.4	6A4
6A6	Twin Triode Amplifier	7-pin M.	7B	Htr.	6.3	0.8	Class-B Amplifier	250	0	—	—	Power output is for one tube at stated load, plate-to-plate		—	8000	8.0	6A6	
6A7 ¹¹	Pentagrid Converter	7-pin S.	7C	Htr.	6.3	0.3	Converter	250	- 3.0	100	2.2	3.5	360000	Anode grid (No. 2) 200 volts max.		10000	10.0	6A7
6A8S 6A9S	Electron-Ray Tube	6-pin S.	6R	Htr.	6.3	0.15	Indicator Tube	180	Cut-off Grid Bias = -12 v.		0.5	Target Current 2 ma.		—	—	—	6A8S 6A9S	
6A6F6G	Electron-Ray Tube Twin Indicator Type	7-pin S.	7AG	Htr.	6.3	0.15	Indicator Tube	135	Ray Control Voltage = 81 for 0° Shadow Angle. Target current 1.5 ma.								4.0	6A6F6G
							100	= 60 " " "										
6B5	Direct-Coupled Power Amplifier	6-pin M.	6AS	Htr.	6.3	0.8	Class-A Amplifier	300	0	—	—	45	241000	2400	58	7000	4.0	6B5
							Push-Pull Amplifier	400	- 13.0	4.5 ⁵		40	—	—	10000	20		
6B7 ¹¹	Duplex-Diode Pentode	7-pin S.	7D	Htr.	6.3	0.3	Pentode R.F. Amplifier	250	- 3.0	125	2.3	9.0	650000	1125	730	—	—	6B7
6C6	Triple-Grid Amplifier	6-pin S.	6F	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	100	0.5	2.0	1500000	1225	1500	—	—	6C6
6C7	Duplex Diode Triode	7-pin S.	7G	Htr.	6.3	0.3	Class-A Amplifier	250	- 9.0	—	—	4.5	—	20	1250	—	—	6C7
6D6	Triple-Grid Variable- μ	6-pin S.	6F	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	100	2.0	8.2	800000	1600	1280	—	—	6D6
6D7	Triple-Grid Amplifier	7-pin S.	7H	Htr.	6.3	0.3	Class-A Amplifier	250	- 3.0	100	0.5	2.0	—	1600	1280	—	—	6D7
6E5	Electron-Ray Tube	6-pin S.	6R	Htr.	6.3	0.3	Indicator Tube	250	0	—	—	0.25	Target Current 4 ma.		—	—	6E5	
6E6	Twin Triode Amplifier	7-pin M.	7B	Htr.	6.3	0.6	Class-A Amplifier	250	- 27.5	Per plate - 18.0		—	3500	1700	6.0	14000	1.6	6E6
6E7	Triple-Grid Variable- μ	7-pin S.	7H	Htr.	6.3	0.3	R.F. Amplifier	Characteristics same as 6U7G—Table II										6E7
6F7 ¹¹	Triode Pentode	7-pin S.	7E	Htr.	6.3	0.3	Triode Unit Amplifier	100	- 3.0	—	—	3.5	16000	500	8	—	—	6F7
							Pentode Unit Amplifier	250	- 3.0	100	1.5	6.5	850000	1100	900	—	—	
6U5/6G5	Electron-Ray Tube	6-pin S.	6R	Htr.	6.3	0.3	Indicator Tube	250	Cut-off Grid Bias = -22 v.		0.24	Target Current 4 ma.		—	—	—	6U5/6G5	
6H5	Electron-Ray Tube	6-pin S.	6R	Htr.	6.3	0.3	Indicator Tube	100	" " " = - 8 v.		0.19	" " " 1 "		—	—	—	6H5	
6T5	Electron-Ray Tube	6-pin S.	6R	Htr.	6.3	0.3	Indicator Tube	Same characteristics as Type 6G5—Circular Pattern										6T5
36	Tetrode R.F. Amplifier	5-pin S.	5E	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	90	1.7	3.2	550000	1080	595	—	—	36
37	Triode Detector Amplifier	5-pin S.	5A	Htr.	6.3	0.3	Class-A Amplifier	250	- 18.0	—	—	7.5	8400	1100	9.2	—	—	37
38	Pentode Power Amplifier	5-pin S.	5F	Htr.	6.3	0.3	Class-A Amplifier	250	- 25.0	250	3.8	22.0	100000	1200	120	10000	2.5	38

TABLE IV—6.3-VOLT GLASS RECEIVING TUBES—Continued

Type	Name	Base ⁴	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
					Volts	Amps.												
39/44	Variable- μ R.F. Amplifier	5-pin S.	5F	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	90	1.4	5.8	1000000	1050	1050	—	—	39/44
41	Pentode Power Amplifier	6-pin S.	6B	Htr.	6.3	0.4	Class-A Amplifier	250	-18.0	250	5.5	32.0	68000	2200	150	7600	3.4	41
42	Pentode Power Amplifier	6-pin M.	6B	Htr.	6.3	0.7	Class-A Amplifier	250	-16.5	250	6.5	34.0	100000	2200	220	7000	3.0	42
52	2-Grid Triode	5-pin M.	Fig. 33	Fil.	6.3	0.3	Class-A Preamp. ¹² Class-B, 2 tubes ¹³	110	0	—	—	43.0	1750	3000	5.2	2000	1.5	52
								180	0	—	—	3.0	—	—	—	—	10000	
56AS ¹¹	Triode Amplifier	5-pin S.	5A	Htr.	6.3	0.4	Class-A Amplifier	Characteristics same as 56										56AS
57AS ¹¹	Pentode	6-pin S.	6F	Htr.	6.3	0.4	R.F. Amplifier	Characteristics same as 57										57AS
58AS ¹¹	Triple-Grid Variable- μ	6-pin S.	6F	Htr.	6.3	0.4	R.F. Amplifier	Characteristics same as 58										58AS
75	Duplex-Diode Triode	6-pin S.	6G	Htr.	6.3	0.3	Triode Amplifier	250	- 1.35	—	—	0.4	91000	1100	100	—	—	75
76	Triode Detector Amplifier	5-pin S.	5A	Htr.	6.3	0.3	Class-A Amplifier	250	-13.5	—	—	5.0	9500	1450	13.8	—	—	76
77	Triple-Grid Detector	6-pin S.	6F	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	100	0.5	2.3	1500000	1250	1500	—	—	77
78	Triple-Grid Variable- μ	6-pin S.	6F	Htr.	6.3	0.3	R.F. Amplifier	250	- 3.0	100	1.7	7.0	800000	1450	1160	—	—	78
79	Twin Triode Amplifier	6-pin S.	6H	Htr.	6.3	0.6	Class-B Amplifier	250	0	—	—	—	Power output is for one tube			14000	8.0	79
85	Duplex-Diode Triode	6-pin S.	6G	Htr.	6.3	0.3	Class-A Amplifier	250	-20.0	—	—	8.0	7500	1100	8.3	20000	0.35	85
85AS ¹¹	Duplex-Diode Triode	6-pin S.	6G	Htr.	6.3	0.3	Class-A Amplifier	250	- 9.0	—	—	5.5	—	1250	20	—	—	85AS
89	Triple-Grid Power Amplifier	6-pin S.	6F	Htr.	6.3	0.4	Triode Amplifier ⁶ Pentode Amplifier ⁷	250	-31.0	—	—	32.0	2600	1800	4.7	5500	0.9	89
								250	-25.0	250	5.5	32.0	70000	1800	125	6750	3.4	
1603 ⁹	Triple-Grid Amplifier	6-pin M.	6F	Htr.	6.3	0.3	Class-A Amplifier	Characteristics same as 6C6										1603
7700 ⁹	Triple-Grid Amplifier	6-pin S.	6F	Htr.	6.3	0.3	Class-A Amplifier	Characteristics same as 6C6										7700
RK100	Mercury-vapor Triode	6-pin M.	6A	Htr.	6.3	0.6	Amplifier	100	- 2.5	Cathode (G ₁) current 250 ma.		20000	50	—	—	—	RK100	

¹ Refer to Receiving Tube Diagrams.

² Suppressor grid, connected to cathode inside tube, not shown on base diagram.

³ Also known as Type LA.

⁴ S. — small, M. — medium.

⁵ Current to input plate (P₁).

⁶ Grids Nos. 2 and 3 connected to plate.

⁷ Grid No. 2, screen; grid No. 3, suppressor.

⁸ Cathode resistor, 780 ohms.

⁹ Low noise, non-microphonic, tubes.

¹⁰ Cathode bias resistor-ohms. Fixed bias not recommended.

¹¹ Types with final letter "S" have external shield connected to cathode pin.

¹² G₂ tied to plate.

¹³ G₁ tied to G₂.

TABLE V—2.5-VOLT RECEIVING TUBES

Type	Name	Base ³	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
					Volts	Amps.												
2S/4S	Duodiode	5-pin M.	5D	Htr.	2.5	1.35	Detector	At 50 D.C. Volts per plate, cathode ma. = 80										2S/4S
2A3	Triode Power Amplifier	4-pin M.	4D	Fil.	2.5	2.5	Class-A Amplifier	Characteristics same as Type 6A3, Table IV										2A3
2A5	Pentode Power Amplifier	6-pin M.	6B	Htr.	2.5	1.75	Class-A Amplifier	Characteristics same as Type 42, Table IV										2A5
2A6	Duplex-Diode Triode	6-pin S.	6G	Htr.	2.5	0.8	Class-A Amplifier	Characteristics same as Type 75, Table IV										2A6
2A7 ⁸	Pentagrid Converter	7-pin S.	7C	Htr.	2.5	0.8	Osc.-Mixer	Characteristics same as Type 6A7, Table IV										2A7
2B6	Direct-Coupled Amplifier	7-pin M.	7J	Htr.	2.5	2.25	Amplifier	250	-24.0	—	—	40.0	5150	3500	18.0	5000	4.0	2B6
2B7 ⁸	Duplex-Diode Pentode	7-pin S.	7D	Htr.	2.5	0.8	Pentode Amplifier	Characteristics same as Type 6B7—Table IV										2B7
2E5	Electron-Ray Tube	6-pin S.	6R	Htr.	2.5	0.8	Indicator Tube	Characteristics same as Type 6E5—Table IV										2E5
2G5	Electron-Ray Tube	6-pin S.	6R	Htr.	2.5	0.8	Indicator Tube	Characteristics same as 6U5 6G5—Table IV										2G5
24-A	Tetrode R.F. Amplifier	5-pin M.	5E	Htr.	2.5	1.75	Screen-Grid R.F. Amp. Bias Detector	250	- 3.0	90	1.7	4.0	600000	1050	630	—	—	24-A
								250	- 5.0	20/45	Plate current adjusted to 0.1 ma. with no signal							
27 ⁸	Triode Detector-Amplifier	5-pin M.	5A	Htr.	2.5	1.75	Class-A Amplifier Bias Detector	250	-21.0	—	—	5.2	9250	975	9.0	—	—	27
								250	-30.0	—	Plate current adjusted to 0.2 ma. with no signal							
35 51 ¹	Variable- μ Amplifier	5-pin M.	5E	Htr.	2.5	1.75	Screen-Grid R.F. Amp.	250	- 3.0	90	2.5	6.5	400000	1050	420	—	—	35/51

TABLE V—2.5-VOLT RECEIVING TUBES—Continued

Type	Name	Base ¹	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
					Volts	Amps.												
45	Triode Power Amplifier	4-pin M.	4D	Fil.	2.5	1.5	Class-A Amplifier	275	-56.0	—	—	36.0	1700	2050	3.5	4600	2.00	45
46	Dual-Grid Power Amplifier	5-pin M.	5C	Fil.	2.5	1.75	Class-A Amplifier ⁴ Class-B Amplifier ⁵	250 400	-33.0 0	— —	— —	22.0	2380	2350	5.6	6400	1.25	46
47	Pentode Power Amplifier	5-pin M.	5B	Fil.	2.5	1.75	Class-A Amplifier	250	-16.5	250	6.0	31.0	60000	2500	150	7000	2.7	47
53	Twin Triode Amplifier	7-pin M.	7B	Htr.	2.5	2.0	Class-B Amplifier	Characteristics same as Type 6A6, Table IV										53
55 ^b	Duplex-Diode Triode	6-pin S.	6G	Htr.	2.5	1.0	Class-A Amplifier	Characteristics same as Type 85, Table IV										55
56 ^c	Triode Amplifier, Detector	5-pin S.	5A	Htr.	2.5	1.0	Class-A Amplifier	Characteristics same as Type 76, Table IV										56
57 ^b	Triple-Grid Amplifier	6-pin S.	6F	Htr.	2.5	1.0	R.F. Amplifier	250	-3.0	100	0.5	2.0	1500000	1225	1500	—	—	57
58 ^b	Triple-Grid Variable- μ	6-pin S.	6F	Htr.	2.5	1.0	Screen-Grid R.F. Amp.	250	-3.0	100	2.0	8.2	800000	1600	1280	—	—	58
59	Triple-Grid Power Amplifier	7-pin M.	7A	Htr.	2.5	2.0	Class-A Triode ⁶	250	-28.0	—	—	26.0	2300	2600	6.0	5000	1.25	59
							Class-A Pentode ⁷	250	-18.0	250	9.0	35.0	40000	2500	100	6000	3.0	
RK15	Triode Power Amplifier	4-pin M.	4D ²	Fil.	2.5	1.75	Characteristics same as Type 46 with Class-B connections										RK15	
RK16	Triode Power Amplifier	5-pin M.	5A	Htr.	2.5	2.0	Characteristics same as Type 59 with Class-A triode connections										RK16	
RK17	Pentode Power Amplifier	5-pin M.	5F	Htr.	2.5	2.0	Characteristics same as Type 2A5										RK17	

¹ Refer to Receiving Tube Diagrams.

² Grid connection to cap; no connection to No. 3 pin.

³ S.—small; M.—medium.

⁴ Grid No. 2 tied to plate.

⁵ Grids Nos. 1 and 2 tied together.

⁶ Grids Nos. 2 and 3 connected to plate.

⁷ Grid No. 2, screen; grid No. 3, suppressor.

⁸ Types with final letter "S" indicate external shield connected to cathode pin.

TABLE VI—2.0-VOLT BATTERY RECEIVING TUBES

Type	Name	Base ²	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
					Volts	Amps.												
1A4P	Variable- μ Pentode	4-pin S.	4M	Fil.	2.0	0.06	R.F. Amplifier	180	-3.0	67.5	0.8	2.3	1000000	750	750	—	—	1A4P
1A4T	Variable- μ Tetrode	4-pin S.	4K	Fil.	2.0	0.06	R.F. Amplifier	180	-3.0	67.5	0.7	2.3	960000	750	720	—	—	1A4T
1A6	Pentagrid Converter	6-pin S.	6L	Fil.	2.0	0.06	Converter	180	-3.0	67.5	2.4	1.3	500000	Anode grid (No. 2) 180 max. volts			1A6	
1B4P/951	Pentode R.F. Amplifier	4-pin S.	4M	Fil.	2.0	0.06	R.F. Amplifier	180	-3.0	67.5	0.6	1.7	1500000	650	1000	—	—	1B4P/951
								90	-3.0	67.5	0.7	1.6	1000000	600	550	—	—	
1B5 ² 25S	Duplex-Diode Triode	6-pin S.	6M	Fil.	2.0	0.06	Triode Class-A Amplifier	135	-3.0	—	—	0.8	35000	575	20	—	—	1B5 25S
1C6	Pentagrid Converter	6-pin S.	6L	Fil.	2.0	0.12	Converter	180	-3.0	67.5	2.0	1.5	750000	Anode grid (No. 2) 135 max. volts			1C6	
1F4	Pentode Power Amplifier	5-pin M.	5K	Fil.	2.0	0.12	Class-A Amplifier	135	-4.5	135	2.6	8.0	200000	1700	340	16000	0.34	1F4
1F6	Duplex-Diode Pentode	6-pin S.	6W	Fil.	2.0	0.6	R.F. Amplifier	180	-1.5	67.5	0.6	2.0	1000000	650	650	—	—	1F6
							A.F. Amplifier	135	-1.0	135	—	—	Plate, 0.25 megohm; screen, 1.0 megohm		Amp. = 48	—	—	
15	R.F. Pentode	5-pin S.	5F	Htr.	2.0	0.22	R.F. Amplifier	135	-1.5	67.5	0.3	1.85	800000	750	600	—	—	15
19	Twin-Triode Amplifier	6-pin S.	6C	Fil.	2.0	0.26	Class-B Amplifier	135	0	—	—	—	Load plate-to-plate			10000	2.1	19
30	Triode Detector Amplifier	4-pin S.	4D	Fil.	2.0	0.06	Class-A Amplifier	180	-13.5	—	—	3.1	10300	900	9.3	—	—	30
31	Triode Power Amplifier	4-pin S.	4D	Fil.	2.0	0.13	Class-A Amplifier	180	-30.0	—	—	12.3	3600	1050	3.8	5700	0.375	31
32	Tetrode R.F. Amplifier	4-pin M.	4K	Fil.	2.0	0.06	R.F. Amplifier	180	-3.0	67.5	0.4	1.7	1200000	650	780	—	—	32
33	Pentode Power Amplifier	5-pin M.	5K	Fil.	2.0	0.26	Class-A Amplifier	180	-18.0	180	5.0	22.0	55000	1700	90	6000	1.4	33
34	Variable- μ Pentode	4-pin M.	4M	Fil.	2.0	0.06	R.F. Amplifier	180	-3.0	67.5	1.0	2.8	1000000	620	620	—	—	34
							Class-A Amplifier ³	135	-20.0	—	—	6.0	4175	1125	4.7	11000	0.17	
49	Dual-Grid Power Amplifier	5-pin M.	5C	Fil.	2.0	0.12	Class-B Amplifier ⁴	180	0	—	—	—	Power output for 2 tubes			12000	3.5	49

TABLE VI—2.0-VOLT BATTERY TUBES — Continued

Type	Name	Base ²	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
					Volts	Amps.												
840	R.F. Pentode	5-pin S.	5J	Fil.	2.0	0.13	Class-A Amplifier	180	-3.0	67.5	0.7	1.0	1000000	400	400	—	—	840
950	Pentode Power Amplifier	5-pin M.	5B	Fil.	2.0	0.12	Class-A Amplifier	135	-16.5	135	2.0	7.0	100000	1000	100	13500	0.45	950
RK24	Triode Amplifier	4-pin M.	4D	Fil.	2.0	0.12	Class-A Amplifier	180	-13.5	—	—	8.0	5000	1600	8.0	12000	0.25	RK24

¹ See Receiving Tube Diagrams.

² S.—small, M.—medium.

³ Grid No. 2 tied to plate.

⁴ Grids Nos. 1 and 2 tied together.

TABLE VII—2.0-VOLT BATTERY TUBES WITH OCTAL BASES

Type	Name	Socket Connections ²	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
				Volts	Amps.													
1C7G	Pentagrid Converter	7Z	Fil.	2.0	0.06	Converter												1C7G
1D5GP	Variable- μ R.F. Pentode	5Y	Fil.	2.0	0.06	R.F. Amplifier												1D5GP
1D5GT	Variable- μ R.F. Tetrode	5R	Fil.	2.0	0.06	R.F. Amplifier	180	-3.0	67.5	0.7	2.2	600000	650					1D5GT
1D7G	Pentagrid Converter	7Z	Fil.	2.0	0.06	Converter												1D7G
1E5GP	R.F. Amplifier Pentode	5Y	Fil.	2.0	0.06	R.F. Amplifier												1E5GP
1E7G	Double Pentode Power Amp.	8C	Fil.	2.0	0.24	Class-A Amplifier	135	-7.5	135	2.0 ²	6.5 ²	220000	1600	350	24000	0.65		1E7G
1F5G	Pentode Power Amplifier	6X	Fil.	2.0	0.12	Class-A Amplifier												1F5G
1F7GV ³	Duplex-Diode Pentode	7AD	Fil.	2.0	0.06	Detector-Amplifier												1F7GV
1G5G	Pentode Power Amplifier	6X	Fil.	2.0	0.12	Class-A Amplifier	135	-13.5	135	2.5	8.7	1600000	1550	250	9000	0.55		1G5G
1H4G	Triode Amplifier	5S	Fil.	2.0	0.06	Detector-Amplifier												1H4G
1H6G	Duplex-Diode Triode	7AA	Fil.	2.0	0.06	Detector-Amplifier												1H6G
1J5G	Pentode Power Amplifier	6X	Fil.	2.0	0.12	Class-A Amplifier	135	-16.5	135	2.0	7.0	—	950	100	13500	0.45		1J5G
1J6G	Twin Triode	7AB	Fil.	2.0	0.24	Class-B Amplifier												1J6G
4A6G	Twin Triode	8L	Fil. ⁵	2.0	0.12	Class-A, 1 section	90	-1.5	—	—	1.1	26600	750	20				1J6G
				4.0	0.06	Class-B, 2 sections	90	-1.5	—	—	1.1 ⁴	—	—	—	—	8000	1.0	4A6G

¹ Refer to Receiving Tube Diagrams.

² Total current for both sections; no signal.

³ Also type G or GH.

⁴ Max. signal plate current = 10.8 Ma.

⁵ Center-tapped.

TABLE VIII—1.5-VOLT FILAMENT DRY-CELL TUBES

See also Table X for Special 1.4-volt Tubes

Type	Name	Base	Socket Connections ¹	Filament		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Milliwatts	Type	
				Volts	Amps.													
1A3	H. F. Diode	7-pin B. ¹⁰	5AP	1.4	0.15	Detector F.M. Discriminator												1A3
1A5G	Pentode Power Amplifier	7-pin O.	6X	1.4	0.05	Class-A ₁ Amplifier	90	-4.5 ³	90	0.8	4.0	300000	850	240	25000	115		1A5G
1A7G	Pentagrid Converter	8-pin O.	7Z	1.4	0.05	Osc.-Mixer	90	0	45 ⁴	0.6	0.55	600000	Anode-grid volts 90					1A7G
1A85	Pentode R.F. Amplifier	8-pin O.	5BF	1.2	0.05	R.F. Amplifier	90	0	90	0.8	3.5	275000	1100	—	—	—		1A85
1B7G	Pentagrid Converter	6-pin O.	7Z	1.4	0.1	Osc.-Mixer	150	-1.5	150	2.0	6.8	125000	1350	—	—	—		1B7G
							90	0	45	1.3	1.5	350000	Grid No. 1 resistor 200,000 ohms					
1B8GT	Diode Triode Tetrode	8-pin O.	8AW	1.4	0.1	Triode Amplifier Tetrode Amplifier	90	0	—	—	0.15	240000	275	—	—	—		1B8GT
							90	-6.0	90	1.4	6.3	—	1150	—	14000	210		
1C5G	Pentode Power Amplifier	7-pin O.	6X	1.4	0.1	Class-A ₁ Amplifier	90	-7.5 ³	90	1.6	7.5	115000	1550	165	8000	240		1C5G
1D8GT	Diode Triode Pentode	8-pin O.	8AJ	1.4	0.1	Triode Amplifier Pentode Amplifier	90	0	—	—	1.1	43500	575	95	—	—		1D8GT
							90	-9.0	90	1.0	5.0	200000	925	—	—	—		

Max. a.c. voltage per plate — 117. Max. output current — 0.5 ma.

433

TABLE VIII—1.5-VOLT FILAMENT DRY-CELL TUBES—Continued

Type	Name	Base ²	Socket Connections ¹	Filament		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Milliwatts	Type
				Volts	Amps.												
1E4G	Triode Amplifier	8-pin O.	5S ¹²	1.4	0.05	Class-A Amplifier	90 90	0 -3.0	—	—	4.5 1.5	11000 17000	1325 825	14.5 14	—	—	1E4G
1G4G	Triode Amplifier	7-pin O.	5S	1.4	0.05	Class-A Amplifier	90	-6.0	—	—	2.3	10700	825	8.8	—	—	1G4G
1G6G	Twin Triode	6-pin O.	7AB	1.4	0.1	Class-A Amplifier Class-B Amplifier	90 90	0 —	—	—	1.7 ³	34 volts input per grid		—	12000	675	1G6G
1H5G	Diode High- μ Triode	7-pin O.	5Z	1.4	0.05	Class-A Amplifier	90	0	—	—	0.14	240000	275	65	—	—	1H5G
1L4 ¹³	R. F. Pentode Amplifier	7-pin B. ¹⁰	6AR	1.4	0.05	Class-A Amplifier	90	0	90	2.0	4.5	350000	1025	—	—	—	1L4
1LA4	Pentode Power Amplifier	8-pin L.	5AD	1.4	0.05	Class-A Amplifier	Characteristics same as 1A5G										1LA4
1LA6	Pentagrid Converter	8-pin L.	7AK	1.4	0.05	Osc.-Mixer	90	0	45	0.6	0.55	Anode Grid Volts 90					1LA6
1LB4	Pentode Power Amplifier	8-pin L.	5AD	1.4	0.05	Class-A Amplifier	90	-9	90	1.0	5.0	200000	925	—	12000	200	1LB4
1LB6GL	Heptode Converter	8-pin L.	8AX	1.4	0.05	Osc.-Mixer	90	0	67.5	2.2	0.4	Grid No. 4—67.5 v., No. 5—0 v.					1LB6GL
1LC5	Triple-Grid Variable- μ	8-pin L.	7AO	1.4	0.05	R.F. Amplifier	90	0	45	0.2	1.15	1500000	775	—	—	—	1LC5
1LC6	Pentagrid Converter	8-pin L.	7AK	1.4	0.05	Osc.-Mixer	90	0	35 ⁹	0.7	0.75	Anode Grid Volts 45					1LC6
1LD5	Diode Pentode	7-pin L.	6AX	1.4	0.05	Class-A Amplifier	90	0	45	0.1	0.6	950000	600	—	—	—	1LD5
1LE3	Triode Amplifier	8-pin L.	4AA	1.4	0.05	Class-A Amplifier	90 90	0 -3	—	—	4.5 1.3	11200 19000	1300 760	14.5	—	—	1LE3
1LH4	Diode High- μ Triode	8-pin L.	5AG	1.4	0.05	Class-A Amplifier	90	0	—	—	0.15	240000	275	65	—	—	1LH4
1LN5	Triple-Grid Amplifier	8-pin L.	7AO	1.4	0.05	Class-A Amplifier	90	0	90	0.3	1.2	1500000	750	—	—	—	1LN5
1N5G	Pentode R.F. Amplifier	7-pin O.	5Y	1.4	0.05	Class-A Amplifier	90	0	90	0.3	1.2	1500000	750	1160	—	—	1N5G
1N6G	Diode-Power-Pentode	6-pin O.	7AM	1.4	0.05	Class-A Amplifier	90	-4.5	90	0.6	3.1	300000	800	—	25000	100	1N6G
1P5G	Triple-Grid Pentode	5-pin O.	5Y	1.4	0.05	R.F. Amplifier	90	0	90	0.7	2.3	800000	800	640	—	—	1P5G
1Q5G	Tetrode Power Amplifier	5-pin O.	6AF	1.4	0.1	Class-A Amplifier	85 90	-5.0 -4.5	85 90	1.2 1.6	7.2 9.5	70000 75000	1950 2100	—	9000 8000	250 270	1Q5G
1R4/ 1294	U.h.f. Diode	8-pin L.	4AH	1.4	0.15	Rectifier	Max. r.m.s. voltage per plate—30										1R4/ 1294
1R5	Pentagrid Converter	7-pin B. ¹⁰	7AT	1.4	0.05	Osc.-Mixer	90	0	67.5	3.0	1.7	500000	300	Grid No. 1 100000 ohms			1R5
1S4	Pentagrid Power Amplifier	7-pin B. ¹⁰	7AV	1.4	0.1	Class-A Amplifier	90	-7.0	67.5	1.4	7.4	100000	1575	—	8000	270	1S4
1S5	Diode Pentode	7-pin B. ¹⁰	6AU	1.4	0.05	Class-A Amplifier	67.5	0	67.5	0.4	1.6	600000	625	—	—	—	1S5
1SA6GT	R.F. Pentode	8-pin O.	6CA	1.4	0.05	Resistor-Coupled Amp.	90	0	90	Screen resistor 3 meg., grid 10 meg.					1 meg.	50 ¹³	1SA6GT
1SB6GT	Diode Pentode	7-pin O.	6CB	1.4	0.05	R.F. Amplifier	90	0	67.5	0.68	2.45	800000	970	—	—	—	1SB6GT
1T4 ¹⁵	Triple-Grid Variable- μ	7-pin B. ¹⁰	6AR	1.4	0.05	Class-A Amplifier	90	0	45	0.65	2.0	800000	750	—	—	—	1T4
1T5GT	Beam Power Amplifier	7-pin O.	6AF	1.4	0.05	Class-A Amplifier	90	-6.0	90	1.4	6.5	—	1150	—	14000	170	1T5GT
3B7/ 1291	U.h.f. Twin Triode	8-pin L.	7BE	1.4	0.22	Class-A Amplifier	90	0	—	—	5.2	11350	1850	21	—	—	3B7/ 1291
1293	U.h.f. Triode	8-pin L.	Fig. 2 ¹¹	1.4	0.11	Class-A Amplifier	90	0	—	—	4.7	10750	1300	14	—	—	1293
3D6/ 1299	U.h.f. Tetrode	8-pin L.	6BB	1.4	0.22	Class-A Amplifier	135	-6	90	0.7	5.7	—	2200	—	13000	0.5	3D6/ 1299
CK501 ¹⁸	Pentode Voltage Amplifier	None ⁶	— ¹⁶	1.25	0.033	Class-A Amplifier	30 45	0 -1.25	30 45	0.06 0.055	0.3 0.28	1000000 1500000	325 300	—	—	—	CK501
CK502 ¹⁸	Pentode Output Amplifier	None ⁶	— ¹⁶	1.25	0.033	Class-A Amplifier	30	0	30	0.13	0.55	500000	400	—	60000	3	CK502
CK503 ¹⁸	Pentode Output Amplifier	None ⁶	— ¹⁶	1.25	0.033	Class-A Amplifier	30	0	30	0.33	1.5	150000	600	—	20000	6 ⁷	CK503
CK504 ¹⁸	Pentode Output Amplifier	None ⁶	— ¹⁶	1.25	0.033	Class-A Amplifier	30	-1.25	30	0.09	0.4	500000	350	—	60000	3 ⁷	CK504
CK505 ¹⁸	Pentode Voltage Amplifier	None ⁶	— ¹⁶	0.625 ¹¹	0.03	Class-A Amplifier	30 45	0 -1.25	30 45	0.07 0.08	0.17 0.2	1100000 2000000	140 150	—	—	—	CK505

TABLE VIII—1.5-VOLT FILAMENT DRY-CELL TUBES—Continued

Type	Name	Base ²	Socket Connections ¹	Filament		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resist Ohms	Power Output Milliwatts	Type
				Volts	Amps.												
CK506 ¹⁵	Pentode Output Amplifier	None ⁶	— ¹⁶	1.25	0.05	Class-A ₁ Amplifier	45	-4.5	45	0.4	1.25	120000	500	—	30000	25	CK506
CK507 ¹⁵	Pentode Output Amplifier	None ⁶	— ¹⁶	1.25	0.05	Class-A ₁ Amplifier	45	-2.5	45	0.21	0.6	360000	500	—	50000	12	CK507
CK509 ¹⁵	Triode Voltage Amplifier	None ⁶	— ¹⁶	0.625 ¹¹	0.03	Class-A Amplifier	45	0	—	—	0.15	150000	160	16	1000000	—	CK509
CK510 ¹⁵	Dual Space-Charge Tetrode	None ⁶	— ¹⁶	0.625 ¹¹	0.05	Class-A Preamplifier	45	0	0.2 ¹²	200 μ c	60 μ c	500000	65	32.5	—	—	CK510
HY113	Triode Amplifier	5-pin P. ⁴	5K ⁸	1.4	0.07	Class-A Amplifier	45	-4.5	—	—	0.4	25000	250	6.3	40000	6.5	HY113
HY123	Triode Amplifier	5-pin P. ⁴	5K	1.4	0.07	Class-A Amplifier	45	-1.5	22.5	0.008	0.03	5200000	58	300	—	—	HY123
HY115	Pentode Voltage Amplifier	5-pin P. ⁴	5K	1.4	0.07	Class-A Amplifier	90	-1.5	45	0.1	0.48	1300000	270	370	—	—	HY115
HY145	Pentode Voltage Amplifier	5-pin P. ⁴	5K	1.4	0.07	Class-A Amplifier	45	-3.0	45	0.2	0.9	825000	310	255	50000	11.5	HY145
HY155	Pentode Power Amplifier	5-pin P. ⁴	5K	1.4	0.07	Class-A Amplifier	90	-7.5	90	0.5	2.6	420000	450	190	28000	90	HY155
RK42	Triode Amplifier	4-pin S.	4D	1.5	0.6	Class-A Amplifier	Characteristics same as Type 30—Table VI										RK42
RK43	Twin Triode Amplifier	6-pin S.	6C	1.5	0.12	Twin Triode Amplifier	135	-3	—	—	4.5	14500	900	13	—	—	RK43

¹ Refer to Receiving Tube Diagrams.

² M. — medium; S. — small; O. — octal; L. — Ioktal.

³ Series bias is recommended.

⁴ Obtained from 90-volt supply through 70,000-ohm dropping resistor.

⁵ Per tube. Values to left of diagonal line for no-signal condition; values to right are with signal.

⁶ Special miniature peanut base.

⁷ With 5-megohm grid resistor and 0.02- μ fd. grid coupling condenser.

⁸ No screen connection.

⁹ Through series resistor. Screen voltage must be at least 10 volts lower than oscillator anode.

¹⁰ Special 7-pin "button" base, miniature type.

¹¹ Two tubes connected in series for 1.4-volt operation.

¹² Internal shield connected to pin 1.

¹³ Voltage gain.

¹⁴ No external shield needed.

¹⁵ Tinned wire leads extend from bottom of tube. Connections are labeled on tube.

¹⁶ Space-charge grid resistance megohms — returned to positive of plate supply voltage.

¹⁷ Hearing aid tubes. AX suffix added.

¹⁸ See Supplementary Base Diagrams.

TABLE IX — HIGH-VOLTAGE HEATER TUBES

Type	Name	Base ³	Socket Connections ¹	Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
12A5	Pentode Power Amplifier	7-pin M.	7F	12.6	0.3	Class-A ₁ Amplifier	100	-15	100	3/6.5	17/19	50000	1700	—	4500	0.8	12A5
				6.3	0.6		180	-25	180	8/14	45/48	35000	2400	—	3300	3.4	
12A6	Beam Power Amplifier	7-pin O.	7AC	12.6	0.15	Class-A Amplifier	250	-12.5	250	3.5	30	70000	3000	—	7500	3.4	12A6
12A7	Rectifier-Amplifier ⁵	7-pin M.	7K	12.6	0.3	Class-A Amplifier	135	-13.5	135	2.5	9.0	102000	975	100	13500	0.55	12A7
12A8GT	Pentagrid Converter	8-pin O.	8A	12.6	0.15	Osc.-Mixer	Characteristics same as 6A8—Table I										12A8GT
12AH7GT	Twin Triode	8-pin O.	8BE	12.6	0.15	Converter and Amplifier	Characteristics same as 6AH7GT—Table II										12AH7GT
12B6M ³	Diode Triode	6-pin O.	6Y	12.6	0.15	Class-A Amplifier	250	-2.0	—	—	0.9	91000	1100	100	—	—	12B6M
12B7ML	Pentode Amplifier	8-pin O.	8V	12.6	0.15	Class-A Amplifier	250	-3.0	100	2.6	9.2	800000	2000	—	—	—	12B7ML
12B8GT	Triode-Pentode	8-pin O.	8T	12.6	0.3	Class-A Triode Class-A Pentode	100	-1	—	—	0.6	73000	1500	110	—	—	12B8GT
							100	-3	100	2	8	170000	2100	360	—	—	
12C8	Duplex-Diode Pentode	8-pin O.	8E	12.6	0.15	Class-A Amplifier	Characteristics same as 6B8—Table I										12C8
12E5GT	Triode Amplifier	6-pin O.	6Q	12.6	0.15	Class-A Amplifier	250	-13.5	—	—	50	—	1450	13.8	—	—	12E5GT
12F5GT	Triode Amplifier	5-pin O.	5M	12.6	0.15	Class-A Amplifier	Characteristics same as 6F5—Table I										12F5GT
12G7G	Duplex-Diode Triode	7-pin O.	7V	12.6	0.15	Class-A Amplifier	250	-3.0	—	—	—	58000	1200	70	—	—	12G7G
12H6	Twin Diode	7-pin O.	6Q	12.6	0.15	Rectifier	Characteristics same as 6H6—Table I										12H6
12J5GT	Triode Amplifier	6-pin O.	6Q	12.6	0.15	Class-A Amplifier	Characteristics same as 6J5—Table I										12J5GT
12J7GT	Pentode Voltage Amplifier	7-pin O.	7R	12.6	0.15	Class-A Amplifier	Characteristics same as 6J7—Table I										12J7GT
12K7GT	Remote Cut-off Pentode	7-pin O.	7R	12.6	0.15	R.F. Amplifier	Characteristics same as 6K7—Table I										12K7GT
12K8	Triode Hexode Converter	8-pin O.	8K	12.6	0.15	Osc.-Mixer	Characteristics same as 6K8—Table I										12K8
12L8GT	Twin Pentode	8-pin O.	8BU	12.6	0.15	Class-A ₁ Amplifier ¹³	180	-9.0	180	2.8	13.0	160000	2150	—	10000	1.0	12L8GT
12Q7GT	Duplex-Diode Triode	7-pin O.	7V	12.6	0.15	Class-C Amplifier	Characteristics same as 6Q7—Table I										12Q7GT
12SA7	Pentagrid Converter	8-pin O.	8R	12.6	0.15	Osc.-Mixer	Characteristics same as 6SA7—Table I										12SA7
12SC7	Twin Triode	8-pin O.	8S	12.6	0.15	Class-A Amplifier	Characteristics same as 6SC7—Table I										12SC7

TABLE IX—HIGH-VOLTAGE HEATER TUBES—Continued

Type	Name	Base ²	Socket Connections ¹	Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
12SF5	High- μ Triode	6-pin O.	6AB	12.6	0.15	Class-A Amplifier											12SF5
12SF7	Diode Variable- μ Pentode	8-pin O.	7AZ	12.6	0.15	Class-A Amplifier											12SF7
12SG7	Triple-Grid Variable- μ	8-pin O.	8BC	12.6	0.15	Class-A Amplifier											12SG7
12SH7	H-F Amplifier Pentode	8-pin O.	8BK	12.6	0.15	H-F Amplifier											12SH7
12SJ7	Pentode Voltage Amplifier	8-pin O.	8N	12.6	0.15	Class-A Amplifier											12SJ7
12SK7	Remote Cut-off Pentode	8-pin O.	8N	12.6	0.15	R.F. Amplifier											12SK7
12SL7GT	Twin Triode	8-pin O.	8BD	12.6	0.15	Class-A Amplifier											12SL7GT
12SN7GT	Twin Triode	8-pin O.	8BD	12.6	0.3	Class-A Amplifier											12SN7GT
12SQ7	Duplex-Diode Triode	8-pin O.	8Q	12.6	0.15	Class-A Amplifier											12SQ7
12SR7	Duplex-Diode Triode	8-pin O.	8Q	12.6	0.15	Class-A Amplifier											12SR7
14A4	Triode Amplifier	8-pin L.	5AC	14 ¹	0.16	Class-A Amplifier											14A4
14A5	Beam Power Amplifier	8-pin L.	6AA	14 ¹	0.16	Class-A ₁ Amplifier	250	-12.5	250	3.5 5.5 30 32	70000	3000			7500	2.8	14A5
14A7/12B7	Triple-Grid Variable- μ	8-pin L.	8V	14 ¹	0.16	Class-A Amplifier	250	-3.0	100		2.6	9.2	800000	2000			14A7/12B7
14AF7	Twin Triode	8-pin L.	8AC	14	0.16	Class-A Amplifier	250	-10			9	7600	2100	16			14AF7
14B6	Duplex-Diode Triode	8-pin L.	8W	14 ¹	0.16	Class-A Amplifier											14B6
14B8	Pentagrid Converter	8-pin L.	8X	14 ¹	0.16	Osc.-Mixer											14B8
14C5	Beam Power Amplifier	8-pin L.	6AA	14 ¹	0.24	Class-A Amplifier											14C5
14C7	Triple-Grid Amplifier	8-pin L.	8V	14 ¹	0.16	Class-A Amplifier	250	-3.0	100	0.7	2.2	1000000	1575				14C7
14E6	Duplex-Diode Triode	8-pin L.	8W	14 ¹	0.16	Class-A Amplifier											14E6
14E7	Duplex-Diode Pentode	8-pin L.	8AE	14 ¹	0.16	Class-A Amplifier											14E7
14F7	Twin Triode	8-pin L.	8AC	14 ¹	0.16	Class-A Amplifier											14F7
14H7	Triple-Grid Semi-Variable- μ	8-pin L.	8V	14 ¹	0.16	Class-A Amplifier	250	-2.5	150	3.5	9.5	800000	3800				14H7
14J7	Triode-Hexode Converter	8-pin L.	8AR	14 ¹	0.16	Osc.-Mixer											14J7
14N7	Twin Triode	8-pin L.	8AC	14 ¹	0.32	Class-A Amplifier											14N7
14Q7	Heptode Pentagrid Converter	8-pin L.	8AL	14 ¹	0.16	Osc.-Mixer											14Q7
14R7	Duplex-Diode Pentode	8-pin L.	8AE	14 ¹	0.16	Class-A Amplifier											14R7
14S7	Triode Heptode	8-pin L.	8BL	14 ¹	0.16	Osc.-Mixer	250	-2.0	100	3	1.8	1250000	525				14S7
14V7	H.F. Pentode	8-pin L.	8V	14 ¹	0.24	Class-A Amplifier	300	-2.0	150	3.9	9.6	300000	5800				14V7
14W7	Pentode	8-pin L.	8BJ	14 ¹	0.24	Class-A Amplifier	300	-2.2	150	3.9	10	300000	5800				14W7
18	Pentode	6-pin M.	6B	14 ¹	0.30	Class-A Amplifier											18
20J8GM ¹	Triode Heptode Converter	8-pin O.	8H	20	0.15	Osc.-Mixer	250	-3.0	100	3.4	1.5						20J8GM ¹
21A7	Triode Hexode Converter	8-pin L.	8AR	21	0.16	Osc.-Mixer	250	-3.0	100	2.8	1.3		275				21A7
25A6	Pentode Power Amplifier	7-pin O.	7S	25	0.3	Class-A Amplifier	150	-3.0		Triode	3.5		1900	32			25A6
25A7G	Rectifier-Amplifier ⁵	8-pin O.	8F	25	0.3	Class-A Amplifier	135	-20.0	135	8	37	35000	2450	85	4000	2.0	25A7G
25AC5G	Triode Power Amplifier	6-pin O.	6Q	25	0.3	Class-A Amplifier	100	-15.0	100	4	20.5	50000	1800	90	4500	0.77	25AC5G
25B5	Direct-Coupled Triodes	6-pin S.	6D	25	0.3	Class-A Amplifier	110	-15.0			45	3800	58	2000	2.0	25B5	
25B6G	Pentode Power Amplifier	7-pin O.	7S	25	0.3	Class-A Amplifier	165							58	2000	2.0	25B6G
25B8GT	Triode Pentode	8-pin O.	8T	25	0.15	Class-A Amplifier	110	0	110	7	45	11400	2200	25	2000	2.0	25B8GT
25C6G	Beam Power Amplifier	7-pin O.	7AC	25	0.3	Class-A ₁ Amplifier	95	-15.0	95	4	45		4000		2000	1.75	25C6G
25D8GT	Diode Triode Pentode	8-pin O.	8AF	25	0.15	Triode Amplifier Pentode Amplifier	135	-13.5	135	3.5 11.5	58 60	9300	7000		2000	3.6	25D8GT
25L6	Beam Power Amplifier	7-pin O.	7AC	25	0.3	Class-A ₁ Amplifier	100	-1.0			0.5	91000	1100	100			25L6
25N6G	Direct-Coupled Triodes	7-pin O.	7W	25	0.3	Class-A Amplifier	100	-3.0	100	2.7	8.5	200000	1900				25N6G
26A7GT	Twin Beam-Power Audio Amplifier	8-pin O.	8BU	26.5	0.6	Class-A Amplifier ¹³ Class-AB Amplifier ⁹	110	-8.0	110	3.5/10.5	45/48	10000	8000	80	2000	2.2	26A7GT
							26.5	-4.5	26.5	2/5.5	20/20.5	2500	5500	25	2000	2.0	26A7GT
							26.5	-7.0	26.5	2/8.5	19/30				2500 ¹¹	0.5	26A7GT

TABLE IX — HIGH-VOLTAGE HEATER TUBES — Continued

Type	Name	Base ²	Socket Connections ¹	Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Trans-conductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
				Volts	Amps.												
32L7GT	Diode-Beam Tetrode ⁵	8-pin O.	8F	32.5	0.3	Class-A Amplifier	110	- 7.5	110	3	40	15000	6000	—	2500	1.5	32L7GT
35A5	Beam Power Amplifier	8-pin L.	6AA	35	0.15	Class-A ₁ Amplifier	110	- 7.5	110	3/7	40/41	14000	5800	—	2500	1.5	35A5
35L6G	Beam Power Amplifier	7-pin O.	7AC	35	0.15	Class-A ₁ Amplifier	110	- 7.5	110	3/7	40/41	13800	5800	—	2500	1.5	35L6G
43	Pentode Power Amplifier	6-pin M.	6B	25	0.3	Class-A Amplifier	95	-15.0	95	4.0	20.0	45000	2000	90	4500	0.90	43
48	Tetrode Power Amplifier	6-pin M.	6A	30	0.4	Class-A Amplifier	96	-19.0	96	9.0	52.0	—	3800	—	1500	2.0	48
50A5	Beam Power Amplifier	8-pin L.	6AA	50	0.15	Class-A ₁ Amplifier	110	- 7.5	110	4/11	49/50	10000	8200	—	2000	2.2	50A5
50C6G	Beam Power Amplifier	7-pin O.	7AC	50	0.15	Class-A ₁ Amplifier	135	-13.5	135	3.5 11.5	58 60	9300	7000	—	2000	3.6	50C6GT
50L6GT	Beam Power Amplifier	7-pin O.	7AC	50	0.15	Class-A Amplifier	110	- 7.5	110	4/11	49/50	—	8200	82	2000	2.2	50L6GT
70A7GT	Diode-Beam Tetrode ⁵	8-pin O.	8AB ⁷	70	0.15	Class-A Amplifier	110	- 7.5	110	3.0	40	—	5800	80	2500	1.5	70A7GT
70L7GT	Diode-Beam Tetrode ⁵	8-pin O.	8AA	70	0.15	Class-A ₁ Amplifier	110	- 7.5	110	3/6	40 43	15000	7500	—	2000	1.8	70L7GT
117L7GT/ 117M7GT	Rectifier-Amplifier ⁶	8-pin O.	8AO	117	0.09	Class-A Amplifier	105	- 5.2	105	4/5.5	43	17000	5300	—	4000	0.85	117L7GT/ 117M7GT
117N7GT	Rectifier-Amplifier ⁶	8-pin O.	8AV	117	0.09	Class-A Amplifier	100	- 6.0	100	5.0	51	16000	7000	—	3000	1.2	117N7GT
117P7GT	Rectifier-Amplifier ⁶	8-pin O.	8AV	117	0.09	Class-A Amplifier	105	- 5.2	105	4/5.5	43	17000	5300	—	4000	0.85	117P7GT
1284	U.h.f. Pentode	8-pin O.	Fig. 4 ⁶	12.6	0.15	Class-A Amplifier	250	- 3.0	100	2.5	9.0	800000	2000	—	—	—	1284
1629	Electron-Ray Tube	7-pin O.	6RA	12.6	0.15	Indicator Tube	Characteristics same as 6E5—Table IV										1629
1631	Beam Power Amplifier	7-pin O.	7AC	12.6	0.45	Class-A Amplifier	Characteristics same as 6L6—Table I										1631
1632	Beam Power Amplifier	7-pin O.	7AC	12.6	0.6	Class-A Amplifier	Characteristics same as 25L6										1632
1633	Twin Triode	8-pin O.	8BD	25	0.15	Class-A Amplifier	Characteristics same as 6SN7GT—Table II										1633
1634	Twin Triode	8-pin O.	8S	12.6	0.15	Class-A Amplifier	Characteristics same as 6SC7—Table I										1634
1644	Twin Pentode	8-pin O.	Fig. 7 ⁶	12.6	0.15	Class-A Amplifier	180	- 9.0	180	2.8/4.6	13	160000	2150	—	10000	1.0	1644
XXD	Twin Triode	8-pin L.	8AC	12.6	0.15	Class-A Amplifier	250	- 10	—	—	9.0	—	2100	16	—	—	XXD
28D7	Double Beam Power Amplifier	8-pin L.	8BS	28.0	0.4	Class-A ₂ Amplifier	28	390 ¹⁰	28 ⁹	0.7 ⁹	9.0 ⁹	—	—	—	4000 ⁸	0.08 ⁸	28D7
							180 ¹⁰	28 ⁹	1.2 ⁹	18.5 ⁹	—	—	—	—	6000 ¹¹	0.175 ⁹	

¹ Refer to Receiving Tube Diagrams.
² M. — medium; S. — small; O. — octal; L. — loktal.
³ Metal-sprayed glass envelope.
⁴ Maximum rating, corresponding to 130-volt line condition; normal rating is 12.6 v. for 117-v. line.

⁵ For rectifier data, see Table XIII.
⁶ See Supplementary Base Diagrams.
⁷ 6.3-volt pilot lamp must be connected between pins 6 and 7.

⁸ Per section (except heater) — resistance coupled.
⁹ P. P. operation — values for both sections, resistance coupled.
¹⁰ Cathode resistor — ohms.
¹¹ Plate to plate.
¹² Type Y has micanol base.
¹³ Each unit.

TABLE X — SPECIAL RECEIVING TUBES

Type	Name	Base ²	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Trans-conductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type
					Volts	Amps.												
00-A	Triode Detector	4-pin M.	4D	Fil.	5.0	0.25	Grid Leak Detector	45	—	—	—	1.5	30000	666	20	—	—	00-A
01-A	Triode Detector Amplifier	4-pin M.	4D	Fil.	5.0	0.25	Class-A Amplifier	135	- 9.0	—	—	3.0	10000	800	8.0	—	—	01-A
3A4	Power Amplifier Pentode	7-pin B.	7BB	Fil. ⁶	1.4	0.2	Class-A Amplifier	135	- 7.5	90	2.6	14.8	90000	1900	—	8000	0.6	3A4
					2.8	0.1		150	- 8.4	90	2.2	13.3	100000	1900	—	8000	0.7	
3A5	H.F. Twin Triode	7-pin B.	7BC	Fil. ⁶	1.4	0.22	Class-A Amplifier	90	- 2.5	—	—	3.7	8300	1800	15	—	—	3A5
3A8GT	Diode Triode Pentode	8-pin O.	8AS	Fil. ⁶	1.4	0.1	Class-A Triode	90	0	—	—	0.15	240000	275	65	—	—	3A8GT
					2.8	0.05	Class-A Pentode	90	0	90	0.3	1.2	600000	750	—	—		
3B5GT	Beam Power Amplifier	7-pin O.	7AP	Fil. ⁶	1.4	0.1	Class-A Amplifier	67.5	- 7.0	67.5	0.6	8.0	100000	1650	—	5000	0.2	3B5GT
					2.8	0.05					0.5	6.7		1500			0.18	
3C5GT	Power Output Pentode	7-pin O.	7AQ	Fil. ⁶	1.4	0.1	Class-A Amplifier	90	- 9.0	90	1.4	6.0	—	1550	—	8000	0.24	3C5GT
					2.8	0.05								1450			10000	

TABLE X — SPECIAL RECEIVING TUBES — Continued

Type	Name	Base ¹	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
					Volts	Amps.													
3LE4	Power Amplifier Pentode	8-pin L.	6BA	Fil.	2.8	0.05	Class-A Amplifier	90	- 9.0	90	1.8	9.0	110000	1600	—	6000	0.30	3LE4	
3LF4	Power Amplifier Tetrode	8-pin L.	6BB	Fil. ⁶	1.4 2.8	0.1 0.05	Class-A Amplifier	90	- 4.5	90	1.3 1.0	9.5 8.0	75000 80000	2200 2000	—	8000 7000	0.27 0.23	3LF4	
3Q4	Power Amplifier Pentode	7-pin B. ⁹	7BA	Fil. ⁶	1.4 2.8	0.1 0.05	Class-A Amplifier	90	- 4.5	90	2.1 1.7	9.5 7.7	100000 120000	2150 2000	—	10000	0.27 0.24	3Q4	
3Q5GT	Beam Power Amplifier	7-pin O.	7AP	Fil. ⁶	1.4 2.8	0.1 0.05	Class-A Amplifier	90	- 4.5	90	1.6 1.0	9.5 7.5	—	2100 1800	—	8000	0.27 0.25	3Q5GT	
3S4	Power Amplifier Pentode	7-pin B. ⁹	7BA	Fil. ⁶	1.4 2.8	0.1 0.05	Class-A Amplifier	90	- 7.0	67.5	1.4 1.1	7.4 6.1	100000	1575 1425	—	8000	0.27 0.235	3S4	
10 ²⁴	Triode Power Amplifier	4-pin M.	4D	Fil.	7.5	1.25	Class-A Amplifier	425	-39.0	—	—	18.0	5000	1600	8.0	10200	1.6	10	
11 12	Triode Detector Amplifier	4-pin M.	4D	Fil.	1.1	0.25	Class-A Amplifier	135	-10.5	—	—	3.0	15000	440	6.6	—	—	11 12	
20	Triode Power Amplifier	4-pin S.	4D	Fil.	3.3	0.132	Class-A Amplifier	135	-22.5	—	—	6.5	6300	525	3.3	6500	0.11	20	
22	Tetrode R.F. Amplifier	4-pin M.	4K	Fil.	3.3	0.132	R.F. Amplifier	135	- 1.5	67.5	1.3	3.7	325000	500	160	—	—	22	
26	Triode Amplifier	4-pin M.	4D	Fil.	1.5	1.05	Class-A Amplifier	180	-14.5	—	—	6.2	7300	1150	8.3	—	—	26	
40	Triode Voltage Amplifier	4-pin M.	4D	Fil.	5.0	0.25	Class-A Amplifier	180	- 3.0	—	—	0.2	150000	200	30	—	—	40	
4A6G	Twin Triode Amplifier	8-pin O.	8L	Fil. ⁶	4 ³ 2 ³	0.06 0.12	Class-A Amplifier ⁴ Class-B Amplifier	90 90	- 1.5 0	—	—	2.2 4.6 ³	13300	1500	20	—	8000	1.0	4A6G
50	Triode Power Amplifier	4-pin M.	4D	Fil.	7.5	1.25	Class-A Amplifier	450	-84.0	—	—	55.0	1800	2100	3.8	4350	4.6	50	
6AG5 ²²	Pentode R.F. Amplifier	7-pin B. ⁹	7BD	Htr.	6.3	0.3	Class-A Amplifier	250 100	200 ¹⁵ 100 ¹⁴	150 100	2.0 1.6	7.0 5.5	800000 300000	5000 4750	—	—	—	6AG5	
6AJ5	U.H.F. Pentode	7-pin B.	Fig. 32	Htr.	6.3	0.175	R.F. Amplifier Class-AB Amplifier	28 180	200 ¹⁶ —	28 7.5	1.2 75	3.0 —	90000	2750	250	—	28000	1.0	6AJ5
6AK5 ²²	H.F. Pentode	7-pin B. ⁹	7BD	Htr.	6.3	0.175	R.F. Amplifier	180 150 120	200 ¹⁴ 330 ¹⁶ 200 ¹⁵	120 140 220	2.4 2.2 2.5	7.7 7.0 7.5	690000 420000 340000	5100 4300 5000	3500 1800 1700	—	—	6AK5	
6AK6	Power Amplifier Pentode	7-pin B. ⁹	7BK	Htr.	6.3	0.15	Class-A Amplifier	180	- 9.0	180	2.5	15.0	200000	2300	—	10000	1.1	6AK6	
6AL5	U.H.F. Twin Diode ²³	7-pin B. ⁹	6BT	Htr.	6.3	0.3	Detector	Max. r.m.s. voltage — 150. Max. d.c. output current — 10 ma. ²⁵										6AL5	
6AQ6	Duodiode Hi-mu Triode	7-pin B. ⁹	7BT	Htr.	6.3	0.15	Class-A Triode	250 100	- 3.0 - 1.0	—	—	1.0 0.8	58000 61000	1200 1150	70 70	—	—	6AQ6	
6C4	Triode Amplifier	7-pin B. ⁹	6BG	Htr.	6.3	0.15	Class-A Amplifier	250	- 8.5	—	—	10.5	7700	2200	17	—	—	6C4	
6F4	Acorn Triode	Acorn	7BR	Htr.	6.3	0.225	Class-A ₁ Amplifier	80	150 ¹⁵	—	—	13.0	2900	5800	17	—	—	6F4	
6J4	U.H.F. Grounded-Grid R.F. Amplifier	7-pin B. ⁹	7BQ	Htr.	6.3	0.4	Grounded-Grid Class-A Amplifier	150 100	100 ¹⁴ 100 ¹⁴	—	—	15.0 10.0	4500 5000	12000 11000	55 55	—	—	6J4	
6J6 ²⁸	Twin Triode	7-pin B. ⁹	7BF	Htr.	6.3	0.45	Class-A Amplifier Mixer, Oscillator	100	50 ¹⁴	—	—	8.5	7100	5300	38	—	—	6J6	
6N4 ³⁰	U.H.F. Triode Amp.	7-pin B. ⁹	—	Htr.	6.3	0.2	Class-A R.F. Amplifier	180	- 3.5	—	—	12.0	—	6000	32	—	—	6N4	
71-A	Triode Power Amplifier	4-pin M.	4D	Fil.	5.0	0.25	Class-A Amplifier	180	-43.0	—	—	20.0	1750	1700	3.0	4800	0.79	71-A	
99 ²³	Triode Detector Amplifier	4-pin S.	4D	Fil.	3.3	0.063	Class-A Amplifier	90	- 4.5	—	—	2.5	15500	425	6.6	—	—	99	
112A	Triode Detector Amplifier	4-pin M.	4D	Fil.	5.0	0.25	Class-A Amplifier	180	-13.5	—	—	7.7	4700	1800	8.5	—	—	112A	
182B/ 482B	Triode Amplifier	4-pin M.	4D	Fil.	5.0	1.25	Class-A Amplifier	250	-35.0	—	—	18.0	—	1500	5.0	—	—	182B/ 482B	
183/ 483	Power Triode	4-pin M.	4D	Fil.	5.0	1.25	Class-A Amplifier	250	-60.0	—	—	25.0	18000	1800	3.2	4500	2.0	183/ 483	
485	Triode	5-pin S.	5A	Htr.	3.0	1.3	Class-A Amplifier	180	- 9.0	—	—	6.0	9300	1350	12.5	—	—	485	
864	Triode Amplifier	4-pin S.	4D	Fil.	1.1	0.25	Class-A Amplifier	90	- 4.5	—	—	2.9	13500	610	8.2	—	—	864	
954 ⁷	Pentode Detector, Amplifier	Special	5BB	Htr.	6.3	0.15	Class-A Amplifier Bias Detector	250 250	- 3.0 - 6.0	100 100	0.7	2.0	1.5 megohms	1400	2000	—	—	—	954
955 ⁷	Triode Detector, Amplifier, Oscillator	Special	5BC	Htr.	6.3	0.15	Class-A Amplifier	250	- 7.0	—	—	6.3	11400	2200	25	—	—	955	
							Class-A Amplifier	90	- 2.5	—	—	2.5	14700	1700	25	—	—	—	

TABLE X—SPECIAL RECEIVING TUBES—Continued

Type	Name	Base ²	Socket Connections ¹	Cathode	Fil. or Heater		Use	Plate Supply Volts	Grid Bias	Screen Volts	Screen Current Ma.	Plate Current Ma.	Plate Resistance, Ohms	Transconductance Micromhos	Amp. Factor	Load Resistance Ohms	Power Output Watts	Type	
					Volts	Amps.													
956 ⁷	Triple-Grid Variable- μ R.F. Amplifier	Special	5BB	Htr.	6.3	0.15	R.F. Amplifier Mixer	250	- 3.0	100	2.7	6.7	700000	1800	1440	—	—	—	956
957 ⁷	Triode Det., Amp., Osc.	Special	5BD	Fil.	1.25	0.05	Class-A Amplifier	250	-10.0	100	—	—	Oscillator peak volts— 7 min.				—	—	957
958 ⁷ 958-A	Triode A.F. Amp., Osc.	Special	5BD	Fil.	1.25	0.1	Class-A Amplifier	135	- 5.0	—	—	2.0	20800	650	13.5	—	—	—	958 958-A
959 ⁷	Pentode Det., Amplifier	Special	5BE	Fil.	1.25	0.05	Class-A Amplifier	135	- 7.5	—	—	—	10000	1200	12	—	—	—	959
7E5/1201	U.H.F. Triode	8-pin L.	8BN	Htr.	6.3	0.15	Class-A Amplifier	145	- 3.0	67.5	0.4	1.7	800000	600	480	—	—	—	7E5/1201
7C4/1203	U.H.F. Diode	8-pin L.	4AH	Htr.	6.3	0.15	Rectifier	180	- 3	—	—	5.5	12000	—	36	—	—	—	7C4/1203
1204	U.H.F. Pentode	8-pin L.	Fig. 5 ¹¹	Htr.	6.3	0.15	Class-A Amplifier	250		2	100	0.6	1.75	800000	1200	—	—	—	1204
1609	Pentode Amplifier	5-pin S.	5B	Fil.	1.1	0.25	Class-A Amplifier	135	- 1.5	67.5	0.65	2.5	400000	725	300	—	—	—	1609
9001	Triple-Grid Detector, Amplifier	7-pin B. ⁸	7PM	Htr.	6.3	0.15	Class-A Amplifier Mixer	250	- 3.0	100	0.7	2.0	Over 1 meg.	1400	—	—	—	—	9001
9002	Triode Det., Amp., Osc.	7-pin B. ⁸	7TM	Htr.	6.3	0.15	Class-A Amplifier	250	- 5.0	100	—	—	Osc. peak voltage 4 volts	550	—	—	—	—	9002
9003	Triple-Grid Variable- μ R.F. Amplifier	7-pin B. ⁸	7PM	Htr.	6.3	0.15	Class-A Amplifier Mixer	250	- 7.0	—	—	6.3	11400	9200	25	—	—	—	9003
9004 ⁷	U.H.F. Diode	Special	Fig. 15 ¹¹	Htr.	6.3	0.15	Detector	90	- 2.5	—	—	2.5	14700	1700	25	—	—	—	9004
9005 ⁷	U.H.F. Diode	Special	Fig. 16 ¹¹	Htr.	3.6	0.165	Detector	250	- 3.0	100	2.7	6.7	700000	1800	—	—	—	—	9005
9006	U.H.F. Diode	7-pin B. ⁸	6BH	Htr.	6.3	0.15	Detector	250	- 10.0	100	—	—	Osc. peak voltage 9 volts	600	—	—	—	—	9006
EF-50	High Frequency Pentode Amplifier	9-Pin L.	Fig. 14 ¹¹	Htr.	6.3	0.3	I.F.-R.F. Amplifier	250		150 ¹²	250	3.1	10	600000	6300	—	—	—	EF-50
GL-2C44 GL-464A	U.H.F. Triode ²⁹	6-pin O.	Fig. 17 ¹¹	Htr.	6.3	0.75	Class-A Amplifier and Modulator	250	100 ¹³	—	—	25.0	—	7000	—	—	—	—	GL-2C44 GL-464A
GL-446A GL-446B ²²	U.H.F. Triode ²⁹	6-pin O.	Fig. 19 ¹¹	Htr.	6.3	0.75	Oscillator, Amplifier or Converter	250	200 ¹⁴	—	—	15.0	—	4500	45	—	—	—	GL-446A GL-446B
559 GL-559	U.H.F. Diode ²⁹	6-pin O.	Fig. 18 ¹¹	Htr.	6.3	0.75	Detector or transmission line switch	5.0	—	—	—	24.0	—	—	—	—	—	—	559 GL-559
M54	Tetrode Power Amplifier	None ⁹	—	Fil.	0.625 ¹⁰	0.04	Class-A Amplifier	30	0	30	0.06	0.5	130000	200	26	35000	0.005	—	M54
M64	Tetrode Voltage Amplifier	None ⁹	—	Fil.	0.625 ¹⁰	0.02	Class-A Amplifier	30	0	—	—	0.03	200000	110	25	—	—	—	M64
M74	Tetrode Voltage Amplifier	None ⁹	—	Fil.	0.625 ¹⁰	0.02	Class-A Amplifier	30	0	7.0	0.01	0.02	500000	125	70	—	—	—	M74
XXB	Twin Triode Frequency Converter	7-pin L.	Fig. 9 ¹¹	Fil. ^{8, 21}	2.8 /1.4 3.2 ¹¹ /1.6	0.05 /0.10 —	Frequency Converter ¹⁷	90 ¹²	0	—	—	4.5 ¹⁹ 4.5 ²⁰	11200 ¹⁹ 11200 ²⁰	1300 ¹⁹ 1300 ²⁰	14.5 ¹²	—	—	—	XXB
XXFM	Twin-Diode Triode	8-pin L.	Fig. 10 ¹¹	Htr.	6.3	0.3	Special Detector Amplifier	250 ¹³ 100 ¹³ 100 ¹⁴	- 1 0 —	— — —	— — —	1.9 1.2 4 ¹⁵	1900 ¹⁹ 1900 ²⁰ —	760 ¹⁹ 760 ²⁰ —	100 85 —	— — —	— — —	— — —	XXFM

¹ Refer to Receiving Tube Diagrams.

² M.—medium; S.—small; O.—octal; L.—loktal.

³ Cathode terminal is mid-point of filament; use series connection with 4 volts, parallel with 2 volts.

⁴ Triodes connected in parallel. ⁵ Idling current, both plates.

⁶ Filament mid-point tap permits series or parallel connection.

⁷ "Acorn" type; miniature unbase tubes for ultrahigh frequencies.

⁸ Special 7-pin "button" base, miniature type.

⁹ No base; tinned wire leads. Dimensions 0.36" x 1.10".

¹⁰ Intended for series-parallel operation on 1.4-volt dry cell.

¹¹ See Supplementary Base Diagrams.

¹² Both Sections. ¹³ Amplifier plate.

¹⁴ Diode plates (A.C. max. volts per plate).

¹⁵ Max. D.C. output. ¹⁶ Cathode resistor ohms.

¹⁷ Section No. 2 recommended for h.f.o.

¹⁸ Dry battery operation.

¹⁹ Section No. 1.

²⁰ Section No. 2.

²¹ Series operation; pin 8 is negative & pin 9 positive. Parallel operation, pins 1 & 8 tied together for positive.

²² Highest frequency oscillator. Use 10,000 to 20,000 ohm grid-leak in this service.

²³ Same as X99. Type V99 is same, but socket connections are 4E.

²⁴ Type 210-T has ceramic base. ²⁵ Resonant frequency 700 Mc.

²⁶ Per plate. ²⁷ Useful up to 400 Mc. ²⁸ Useful up to 600 Mc.

²⁹ "Lighthouse" tube. Has special ring contacts.

³⁰ Useful up to 500 Mc.

TABLE XI—CONTROL AND REGULATOR TUBES

Type	Name	Base ¹	Socket Connections ²	Cathode	Fil. or Heater		Use	Peak Anode Voltage	Max. Anode Current ²	Minimum Starting Voltage	Operating Voltage	Operating Current ³	Grid Resistor	Tube Voltage Drop	Type
					Volts	Amps.									
0A2	Voltage Regulator	7-pin B. ²¹	Fig. 25 ²²	Cold	—	—	Voltage Regulator	—	—	185	150	5-30 ⁴	—	—	0A2
0B2	Voltage Regulator	7-pin B. ²¹	Fig. 25 ²²	Cold	—	—	Voltage Regulator	—	—	133	108	5-30 ⁴	—	—	0B2
0A4G	Gas Triode Starter-Anode Type	6-pin O.	4V	Cold	—	—	Cold-Cathode Starter-Anode Relay Tube	With 105-120-volt a.c. anode supply, peak starter-anode a.c. voltage is 70, peak r.f. voltage 55. Peak D.C. ma = 100. Average D.C. ma = 25							0A4G
1C21	Gas Triode Glow-Discharge Type	6-pin O.	4V	Cold	—	—	Relay Tube	125-145	25	66 ⁵	—	—	—	73	1C21
2A4G	Gas Triode Grid Type	7-pin O.	5S	Fil.	2.5 ¹⁶	2.5	Voltage Regulator	200	0.1 ¹³	180 ¹⁷	—	—	—	55 ¹⁵	2A4G
2B4	Gas Triode Grid Type	8-pin O.	6Q	Htr.	6.3	0.6	Control Tube	300	300	—	—	1.0	10000 ¹⁸	15	2B4
6Q5G	Gas Triode Grid Type	5-pin M.	5A	Htr.	2.5	1.4	Sweep Circuit Oscillator	300	300	—	—	—	100000 ¹⁹	19	6Q5G
2D21	Gas Tetrode	7-pin B. ²¹	7BN	Htr.	6.3	0.6	Grid-Controlled Rectifier Relay Tube	650	500	—	650	100	0.1-10 ¹⁸	8	2D21
3C23	Gas and Mercury Vapor Grid Type	4-pin M.	3G	Fil. ¹⁹	2.5	7.0	Grid-Controlled Rectifier	400	—	—	500	1500	1.0 ²⁰	15	3C23
17	Mercury Vapor Triode	4-pin M.	3G	Fil.	2.5	5.0	Grid-Controlled Rectifier	1000	6000	—	100	1500	4.5 ²¹	15	17
874	Voltage Regulator	4-pin M.	4S	—	—	—	Grid-Controlled Rectifier	7500 ²²	2000	—	500	200-3000	—	—	874
876	Current Regulator	Mogul	—	—	—	—	Grid-Controlled Rectifier	2500	—	5 ¹¹	1000	250	—	10-24	876
884	Gas Triode Grid Type	6-pin O.	6Q	Htr.	6.3	0.6	Sweep Circuit Oscillator	300	300	—	—	2	25000 ⁴	—	884
885	Gas Triode Grid Type	5-pin S.	5A	Htr.	2.5	1.4	Grid-Controlled Rectifier	350	300	—	75	25000 ⁴	—	—	885
886	Current Regulator	Mogul	—	—	—	—	Same as Type 884	Characteristics same as Type 884							886
967	Mercury Vapor Triode	4-pin M.	3G	Fil.	2.5	5.0	Current Regulator ³	—	—	—	40-60	2.05	—	—	967
991	Voltage Regulator	Bayonet ¹⁴	—	—	—	—	Grid-Controlled Rectifier	2500	500	-5 ¹¹	—	—	—	10-24	991
2050	Gas Tetrode	8-pin O.	8BA	Htr.	6.3	0.6	Voltage Regulator	—	—	87	55-60	2.0	—	—	2050
2051	Gas Tetrode	8-pin O.	8BA	Htr.	6.3	0.6	Grid-Controlled Rectifier	650	500	—	—	100	0.1-10 ¹⁸	8	2050
2523N1/128AS	Gas Triode Grid Type	5-pin M.	5A	Htr.	2.5	1.75	Grid-Controlled Rectifier	350	375	—	—	75	0.1-10 ¹⁸	14	2051
KY21	Gas Triode Grid Type	4-pin M.	—	Fil.	2.5	10.0	Relay Tube	400	300	—	—	1.0	300 ¹⁵	13	2523N1/128AS
RK62	Gas Triode Grid Type	4-pin S.	4D	Fil.	1.4	0.05	Grid-Controlled Rectifier	—	—	—	3000	500	—	—	KY21
RM208	Permatron	4-pin M.	—	Fil.	2.5	5.0	Relay Tube ⁴	45	1.5	—	30-45	0.1-1.5	—	15	RK62
RM209	Permatron	4-pin M.	—	Fil.	5.0	10.0	Controlled Rectifier ⁷	7500 ⁵	1000	—	—	—	—	15	RM208
0A3/VR75	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Controlled Rectifier ⁷	7500 ⁵	5000	—	—	—	—	15	RM209
0B3/VR90	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	105	75	5-40 ⁹	—	—	0A3/VR75
0C3/VR105	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	125	90	5-40 ⁹	—	—	0B3/VR90
0D3/VR150	Voltage Regulator	6-pin O.	4AJ	Cold	—	—	Voltage Regulator	—	—	135	105	5-40 ⁹	—	—	0C3/VR105
KY866	Mercury Vapor Triode	4-pin M.	Fig. 8 ²²	Fil.	2.5	5.0	Voltage Regulator	—	—	185	150	5-40 ⁹	—	—	0D3/VR150
							Grid-Controlled Rectifier	10000	1000	0-150	—	—	—	—	KY866

¹ M. — medium; S. — small; O. — octal; B. — button-base miniature.
² Refer to Receiving Tube Diagrams.
³ Not less than 1000 ohms per grid volt; 500,000 ohms max.
⁴ For use in series with power transformer primary.
⁵ For use as self-quenching super-regenerative detector with high-resistance relay (5000-10000 ohms) in anode circuit.
⁷ For use as grid-controlled rectifier or with external magnetic

control. RM-208 has characteristics of 866, RM-209 of 872.
⁸ When under control peak inverse ratings is reduced to 2500.
⁹ Sufficient resistance must be used in series with tube to limit current to maximum current rating.
¹⁰ Refer to Transmitting Tube Diagrams.
¹¹ At 1000 anode volts.
¹² At 350 anode volts and 0 Grid No. 2 volts.
¹³ At 650 anode volts and 0 Grid No. 2 volts.

¹⁴ Candelabra type, double contact.
¹⁵ Grid.
¹⁶ Filament voltage should be applied 2 seconds before using.
¹⁷ Grid tied to plate.
¹⁸ Heating time 15 seconds.
¹⁹ Special 7-pin button-base miniature.
²⁰ Refer to supplementary base diagrams.
²¹ Minimum.
²² Peak inverse voltage.

TABLE XII—CATHODE-RAY TUBES AND KINESCOPIES

Type	Name	Socket Connections ¹	Heater		Use	Size	Anode No. 2 Voltage	Anode No. 1 Voltage	Cut-Off Grid Voltage ²	Grid No. 2 Voltage	Signal-Swing Voltage	Max. Input Voltage ³	Screen Input Power ⁴	Deflection Sensitivity ⁵		Anode No. 3 Voltage	Pattern Color ⁶	Type
			Volts	Amps.										D ₁ D ₂	D ₃ D ₄			
2AP1	Electrostatic Cathode-Ray	11B	6.3	0.6	Oscillograph Television	2"	1000	250	- 60	—	—	660	—	0.11	0.13	—	Green	2AP1
							500	125	- 30	—	—			0.22	0.26			
3AP1/ 906-P1 ¹⁵	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	1500	430	- 50	—	—	550	10	0.22	0.23	—	Green Blue White	3AP1/ 906-P1
							1000	285	- 33	—	—			0.33	0.35			
							600	170	- 20	—	—			0.55	0.58			
3BP1- 4-11	Electrostatic Cathode-Ray	14A	6.3	0.6	Oscillograph	3"	2000	575	- 60	—	—	550	—	0.13	0.17	—	Green	3BP1- 4-11
							1500	430	- 45	—	—			0.17	0.23			
3EP1/ 1806-P1	Electrostatic Cathode-Ray	11A	6.3	0.6	Oscillograph Television	3"	2000	575	- 60	—	—	550	—	0.115	0.154	—	Green	3EP1/ 1806-P1
							1500	430	- 45	—	—			0.153	0.205			
3GP1 ¹⁵	Electrostatic Cathode-Ray	11A	6.3	0.6	Oscillograph	3"	1500	350	- 50	—	—	550	—	0.21	0.24	—	White Green Blue	3GP1
							1000	234	- 33	—	—			0.32	0.36			
3JP1- 2-4-11	Electrostatic Cathode-Ray	14B	6.3	0.6	Oscillograph	3"	2000	575	- 60	—	—	550	—	0.13	0.17	4000	Green Blue White	3JP1- 2-4-11
							1500	430	- 45	—	—			0.17	0.23	3000		
5AP1/ 1805-P1 5AP4/ 1805-P4	Electrostatic Picture Tube	11A	6.3	0.6	Oscillograph Television	5"	2000	575	- 35	—	—	500	10	0.17	0.21	—	Green	5AP1/ 1805-P1 5AP4/ 1805-P4
							1500	430	- 27	—	—			0.23	0.28			
5BP1/ ¹⁶ 1802-P1	Electrostatic Picture Tube	11A	6.3	0.6	Oscillograph	5"	2000	450	- 40	—	—	500	10	0.3	0.33	—	Green White Blue	5BP1/ 1802-P1
							1500	337	- 30	—	—			0.4	0.45			
5CP1 ¹⁶	Electrostatic Cathode-Ray	14B	6.3	0.6	Oscillograph Television	5"	2000	575	- 60	—	—	550	—	0.28	0.32	4000	White Green Blue	5CP1
							1500	430	- 45	—	—			0.37	0.43	3000		
							2000	575	- 60	—	—			0.36	0.41	2000		
5FP1 -2-4-11	Electromagnetic Cathode-Ray	5AN	6.3	0.6	Oscillograph Television	5"	7000	250	- 45	—	—	—	—	—	—	—	Green White Blue	5FP1 -2-4-11
							4000	250	- 45	—	—			—	—			
5HP1 5HP4	Electrostatic Cathode-Ray	11A	6.3	0.6	Oscillograph	5"	2000	425	- 40	—	—	500	—	0.3	0.33	—	Green White	5HP1 5HP4
							1500	310	- 30	—	—			0.4	0.44			
5JP1 ¹⁶	Electrostatic Cathode-Ray	11E	6.3	0.6	Oscillograph	5"	2000	520	- 75	—	—	500	—	0.25	0.28	4000	White Green Blue	5JP1
							1500	390	- 56	—	—			0.33	0.37	3000		
5LP1 ¹⁶	Electrostatic Cathode-Ray	11F	6.3	0.6	Oscillograph Television	5"	2000	500	- 60	—	—	500	—	0.25	0.28	4000	White Green Blue	5LP1
							1500	375	- 45	—	—			0.33	0.37	3000		
							1000	250	- 30	—	—			0.49	0.56	2000		
5MP1 ¹⁵	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	5"	1500	375	- 50	—	—	660	—	0.39	0.42	—	White Green Blue	5MP1
							1000	250	- 33	—	—			0.58	0.64			
5RP1 -2-4-11	Electrostatic Cathode-Ray	Fig. 34	6.3	0.6	Oscillograph	5"	3000	—	- 90	—	—	1200	—	0.12	0.12	15000	Green White Blue	5RP1 -2-4-11
							2000	575	- 60	—	—			0.18	0.18	10000		
7AP4	Electromagnetic Picture Tube	5AJ	2.5	2.1	Television	7"	3500	1000	-67.5	—	—	—	2.5	—	—	White	7AP4	
7BP1 -2-4-11	Electromagnetic Cathode-Ray	5AN	6.3	0.6	Oscillograph Television	7"	7000	250	- 45	—	—	—	—	—	—	—	White Green Blue	7BP1 -2-4-11
							4000	250	- 45	—	—			—	—			

TABLE XII—CATHODE-RAY TUBES AND KINESCOPES—Continued

Type	Name	Socket Connections ¹	Heater		Use	Size	Anode No. 2 Voltage	Anode No. 1 Voltage	Cut-Off Grid Voltage ²	Grid No. 2 Voltage	Signal-Swing Voltage	Max. Input Voltage ³	Screen Input Power ⁴	Deflection Sensitivity ⁵		Anode No. 3 Voltage	Pattern Color ⁶	Type			
			Volts	Amps.										D ₁ D ₂	D ₂ D ₃						
7CP1/1811-P1	Electromagnetic Cathode-Ray	6AZ	6.3	0.6	Oscillograph	7"	7000	1470	-45	250	—	—	—	—	—	—	Green	7CP1/1811-P1			
							4000	840	-45	250	—	—	—	—	—	—					
9AP4/1804-P4	Electromagnetic Picture Tube	6AL	2.5	2.1	Television	9"	7000	1425	-40	250	25	—	10	—	—	—	White	9AP4/1804-P4			
							6000	1225	-38	—	—	—	—	—	—	—					
9CP4	Electromagnetic Picture Tube	4AF	2.5	2.1	Television	9"	7000	—	-110	—	25	—	10	—	—	—	White	9CP4			
9JP1/1809-P1	Electrostatic-Magnetic Cathode-Ray	8BR	2.5	2.1	Oscillograph	9"	5000	1570	-90	—	—	3000	—	0.136	—	—	Green	9JP1/1809-P1			
							2500	785	-45	—	—	—	—	0.272	—	—					
12AP4/1803-P4	Electromagnetic Picture Tube	6AL	2.5	2.1	Television	12"	7000	1460	-75	250	25	—	10	—	—	—	White	12AP4/1803-P4			
							6000	1240	—	—	—	—	—	—	—	—					
12CP4	Electromagnetic Picture Tube	4AF	2.5	2.1	Television	12"	7000	—	-110	—	25	—	10	—	—	—	White	12CP4			
12DP4	Electromagnetic Cathode-Ray	5AN	6.3	0.6	Television	12"	7000	250	-45	—	—	—	—	—	—	—	White	12DP4			
							4000	250	-45	—	—	—	—	—	—	—					
902	Electrostatic Cathode-Ray	Fig. 1 ¹¹	6.3	0.6	Oscillograph	2"	600	150	-60	—	—	350	5	0.19	0.22	—	Green	902			
903 ¹⁰	Electrostatic Cathode-Ray	6AL	2.5	2.1	Oscillograph	9"	7000	1360	-120	250	—	—	10	—	—	—	Green	903			
904	Electrostatic-Magnetic Cathode-Ray	Fig. 3 ¹¹	2.5	2.1	Oscillograph	5"	4600	970	-75	250	—	4000	10	0.09	—	—	Green	904			
905	Electrostatic Cathode-Ray	Fig. 6 ¹¹	2.5	2.1	Oscillograph	5"	2000	450	-35	—	—	1000	10	0.19	0.23	—	Green	905			
907	Electrostatic Cathode-Ray	Fig. 6 ¹¹	2.5	2.1	Oscillograph	5"	Characteristics same as Type 905										—	—	—	Blue	907
908	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	Characteristics same as Type 3AP1/906P1										—	—	—	Blue	908
909 ¹⁰	Electrostatic Cathode-Ray	Fig. 6 ¹¹	2.5	2.1	Oscillograph	5"	Characteristics same as Type 905										—	—	—	Blue	909
910 ¹⁰	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	Characteristics same as Type 3AP1/906P1										—	—	—	Blue	910
911 ¹⁰	Electrostatic Cathode-Ray	7AN	2.5	2.1	Oscillograph	3"	Characteristics same as Type 3AP1/906P1 ⁷										—	—	—	Green	911
912	Electrostatic Cathode-Ray	Fig. 8 ¹¹	2.5	2.1	Oscillograph	5"	10000	2000	-66	250	—	7000	10	0.041	0.051	—	—	Green	912		
913	Electrostatic Cathode-Ray	Fig. 1 ¹¹	6.3	0.6	Oscillograph	1"	500	100	-65	—	—	250	5	0.07	0.10	—	—	Green	913		
914	Electrostatic Cathode-Ray	Fig. 12 ¹¹	2.5	2.1	Oscillograph	9"	7000	1450	-50	250	—	3000	10	0.073	0.093	—	—	Green	914		
1800 ¹⁰	Electromagnetic Kinescope	6AL	2.5	2.1	Television	9"	6000	1250	-75	250	25	—	10	—	—	—	—	Yellow	1800		
1801 ¹⁰	Electromagnetic Kinescope	Fig. 13 ¹¹	2.5	2.1	Television	5"	3000	450	-35	—	20	—	10	—	—	—	—	Yellow	1801		
2001	Electrostatic Cathode-Ray	Fig. 2 ¹¹	6.3	0.6	Oscillograph	1"	Characteristics essentially same as 913										—	—	—	Green	2001
2002	Electrostatic Cathode-Ray	Fig. 1 ¹¹	6.3	0.6	Oscillograph	2"	600	120	—	—	—	—	—	0.16	0.17	—	—	Green	2002		
2005	Electrostatic Cathode-Ray	Fig. 1 ^{11,15}	2.5	2.1	Television	5"	2000	1000	-35	200	—	—	10	0.5	0.56	—	—	—	2005		
24-XH	Electrostatic Cathode-Ray	Fig. 1 ¹¹	6.3	0.6	Oscilloscope	2"	600	120	-60	—	—	—	10	0.14	0.16	—	—	Blue	24-XH		

¹ Refer to Receiving Tube Diagrams.

² For current cut-off. In terms of average center values; should be adjustable to \pm 50 per cent to take care of individual tubes. Control grid should never be allowed to go positive.

³ Between Anode No. 2 and any deflecting plate.

⁴ In mw./sq. cm., max.

⁵ In mm./volt d.c.

⁶ Phosphorescent material used in screen determines persistence

as well as color. P1 is phosphor of medium persistence, P2 long, P3 also medium but especially suited for television, P4 same as P3 but white, and P5 short persistence for oscillographic use. P11 long, higher photographic and visual efficiency.

⁷ The 911 is identical to 906 except for the gun material, which is

designed to be especially free from magnetization effects.

⁸ Cathode connected to pin 7.

¹⁰ Obsolete type.

¹¹ See Supplementary Base Diagrams.

¹⁵ Also available in P4, P5 and P11.

¹⁶ Also available in P2, P4, P5 and P11.

TABLE XIII—RECTIFIERS—RECEIVING AND TRANSMITTING

See also Table XI—Control and Regulator Tubes

Type No.	Name	Base ¹	Socket Connections ¹	Cathode	Fil. or Heater		Max. A.C. Voltage Per Plate	D.C. Output Current Ma.	Max. Inverse Peak Voltage	Peak Plate Current Ma.	Type ⁷
					Volts	Amps.					
BA	Full-Wave Rectifier	4-pin M.	4J	Cold	—	—	350	350	Tube drop 80 v.	—	G
BH	Half-Wave Rectifier	4-pin M.	4J	Cold	—	—	350	125	Tube drop 90 v.	—	G
BR	Half-Wave Rectifier	4-pin M.	4J	Cold	—	—	300	50	Tube drop 60 v.	—	G
CE-220	Half-Wave Rectifier	4-pin-M.	4P	Fil.	2.5	3.0	—	20	20000	100	V
OZ4	Full-Wave Rectifier	6-pin O.	4R	Cold	—	—	350	30-75	1250	200	G
1 ⁵	Half-Wave Rectifier	4-pin S.	4G	Htr.	6.3	0.3	350	50	1000	400	M
1-V ⁴	Half-Wave Rectifier	4-pin S.	4G	Htr.	6.3	0.3	350	50	—	—	V
1B48	Half-Wave Rectifier	7-pin B.	—	Cold	—	—	800	6	2700	50	G
2V3G	Half-Wave Rectifier	6-pin O.	6BA	Fil.	2.5	5.0	—	2.0	16500	12	V
2W3	Half-Wave Rectifier	5-pin O.	4X	Fil.	2.5	1.5	350	55	—	—	V
2X2/879	Half-Wave Rectifier	4-pin M.	4AB	Fil.	2.5	1.75	4500 ¹¹	7.5	—	—	V
2Y2	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	1.75	4400 ¹¹	5.0	—	—	V
2Z2/G84	Half-Wave Rectifier	4-pin M.	4B	Fil.	2.5	1.5	350	50	—	—	V
3B24	Half-Wave Rectifier	4-pin M.	T-4A ⁴	Fil. ²¹	5.0 2.5	3.0 3.0	—	60 30	20000 20000	300 150	V
3B25	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	500	4500	2000	G
3B26 ²⁷	Half-Wave Rectifier	8-pin O.	Fig. 31	Htr.	2.5	4.75	—	20	15000	8000	V
DR-3B27	Half-Wave Rectifier	4-pin M.	4B	Fil.	2.5	5.0	3000	250	8500	1000	V
5R4GY	Full-Wave Rectifier	5-pin M.	5T	Fil.	5.0	2.0	900 ¹⁶ 950 ¹⁸	150 ¹⁰ 175 ¹⁸	2800	650	V
5T4 ³	Full-Wave Rectifier	5-pin O.	5T	Fil.	5.0	3.0	450	250	1250	800	V
5U4G	Full-Wave Rectifier	8-pin O.	5T	Fil.	5.0	3.0	Same as Type 5Z3				V
5V4G	Full-Wave Rectifier	8-pin O.	5L	Htr.	5.0	2.0	Same as Type 83V				V
5W4	Full-Wave Rectifier	5-pin O.	5T	Fil.	5.0	1.5	350	110	1000	—	V
5X3	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	2.0	1275	30	—	—	V
5X4G	Full-Wave Rectifier	8-pin O.	5Q	Fil.	5.0	3.0	Same as 5Z3				V
5Y3G	Full-Wave Rectifier	5-pin O.	5T	Fil.	5.0	2.0	Same as Type 80				V
5Y4G	Full-Wave Rectifier	8-pin O.	5Q	Fil.	5.0	2.0	Same as Type 80				V
5Z3	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	3.0	500	250	1400	—	V
5Z4 ⁴	Full-Wave Rectifier	5-pin O.	5L	Htr.	5.0	2.0	400	125	1100	—	V
6W5G	Full-Wave Rectifier	6-pin O.	6S	Htr.	6.3	0.9	350	100	1250	350	V
6X5 ⁵	Full-Wave Rectifier	6-pin O.	6S	Htr.	6.3	0.5	350	75	—	—	V
6Y5	Full-Wave Rectifier	6-pin S.	6J	Htr.	6.3	0.8	350	50	—	—	V
6Z3	Half-Wave Rectifier	4-pin M.	4G	Fil.	6.3	0.3	350	50	—	—	V
6Z5	Full-Wave Rectifier	6-pin S.	6K	Htr.	6.3	0.6	230	60	—	—	V
6Z5YG	Full-Wave Rectifier	6-pin O.	6S	Htr.	6.3	0.3	350	35	1000	150	V
7Y4	Full-Wave Rectifier	8-pin L.	5AB	Htr.	7.0 ¹²	0.53	350	60	—	—	V
7Z4	Full-Wave Rectifier	8-pin L.	5AB	Htr.	7.0 ¹²	0.96	450 ⁸ 325 ¹⁰	100	1250	300	V
12A7	Rectifier-Pentode ¹⁴	7-pin S.	7K	Htr.	12.6	0.3	125	30	—	—	V
12Z3	Half-Wave Rectifier	4-pin S.	4G	Htr.	12.6	0.3	250	60	—	—	V
12Z5	Voltage Doubler	7-pin M.	7L	Htr.	12.6	0.3	225	60	—	—	V
14Y4	Full-Wave Rectifier	8-pin L.	5AB	Htr.	14 ¹²	0.32	450 ⁸ 325 ¹⁰	70	1250	210	V
14Z3	Half-Wave Rectifier	4-pin S.	4G	Htr.	14 ¹²	0.3	250	60	—	—	V
25A7G	Rectifier-Pentode ¹⁴	8-pin O.	8F	Htr.	25	0.3	125	75	—	—	V
25X6GT	Voltage Doubler	7-pin O.	7Q	Htr.	25	0.15	125	60	—	—	V
25Y4GT	Half-Wave Rectifier	6-pin O.	5AA	Htr.	25	0.15	125	75	—	—	V
25Y5	Voltage Doubler	6-pin S.	6E	Htr.	25	0.3	250	85	—	—	V
25Z3	Half-Wave Rectifier	4-pin S.	4G	Htr.	25	0.3	250	50	—	—	V
25Z4	Half-Wave Rectifier	6-pin O.	5AA	Htr.	25	0.3	125	125	—	—	V
25Z5	Rectifier-Doubler	6-pin S.	6E	Htr.	25	0.3	125	100	—	500	V
25Z6	Rectifier-Doubler	7-pin O.	7Q	Htr.	25	0.3	125	100	—	500	V
28Z5	Full-Wave Rectifier	8-pin L.	5AB	Htr.	28	0.24	450 ¹⁸ 325 ¹⁰	100	—	300	V
32L7GT	Rectifier-Tetrode ¹⁴	8-pin O.	8F	Htr.	32.5	0.3	125	60	—	—	V
35Y4	Half-Wave Rectifier	8-pin O.	5AL	Htr.	35 ⁸	0.15	235	60 100 ¹⁹	700	600	V
35Z3 ²³	Half-Wave Rectifier	8-pin L.	4Z	Htr.	35	0.15	250 ¹³	100	700	600	V
35Z4GT	Half-Wave Rectifier	6-pin O.	5AA	Htr.	35	0.15	250	100	—	—	V
35Z5G	Half-Wave Rectifier	6-pin O.	6AD	Htr.	35 ⁸	0.15	125	60 100 ¹⁹	—	—	V
35Z6G	Voltage Doubler	6-pin O.	7Q	Htr.	35	0.3	125	110	—	500	V
40Z5GT	Half-Wave Rectifier	6-pin O.	6AD	Htr.	40 ⁸	0.15	125	60 100 ¹⁹	—	—	V
45Z3	Half-Wave Rectifier	7-pin B.	5AM	Htr.	45	0.075	117	65	350	390	V
45Z5GT	Half-Wave Rectifier	6-pin O.	6AD	Htr.	45 ⁸	0.15	125	60 100 ¹⁹	—	—	V
50Y6GT	Full-Wave Rectifier	7-pin O.	7Q	Htr.	50	0.15	125	85	—	—	V
50Z6G	Voltage Doubler	7-pin O.	7Q	Htr.	50	0.3	125	150	—	—	V
50Z7G	Voltage Doubler	8-pin O.	8AN	Htr.	50	0.15	117	65	—	—	V

TABLE XIII—RECTIFIERS—RECEIVING AND TRANSMITTING—Continued

See also Table XI—Conerol and Regulator Tubes

Type No.	Name	Base ²	Socket Connections ¹	Cathode	Fil. or Heater		Max. A.C. Voltage Per Plate	D.C. Output Current Ma.	Max. Inverse Peak Voltage	Peak Plate Current Ma.	Type ⁷
					Volts	Amps.					
70A7GT	Rectifier-Tetrode ¹⁴	8-pin O.	8AB	Htr.	70	0.15	125	60	—	—	V
70L7GT	Rectifier-Tetrode ¹⁴	8-pin O.	8AA	Htr.	70	0.15	117	70	—	350	V
72	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	3.0	—	30	20000	150	V
73	Half-Wave Rectifier	8-pin O.	4Y	Fil.	2.5	4.5	—	20	13000	3000	V
80	Full-Wave Rectifier	4-pin M	4C	Fil.	5.0	2.0	350 ¹⁰ 500 ¹⁸	125 125	1400	375	V
81	Half-Wave Rectifier	4-pin M.	4B	Fil.	7.5	1.25	700	85	—	—	V
82	Full-Wave Rectifier	4-pin M.	4C	Fil.	2.5	3.0	500	125	1400	400	M
83	Full-Wave Rectifier	4-pin M.	4C	Fil.	5.0	3.0	500	250	1400	800	M
83-V	Full-Wave Rectifier	4-pin M.	4AD	Htr.	5.0	2.0	400	200	1100	—	V
84/6Z4	Full-Wave Rectifier	5-pin S.	5D	Htr.	6.3	0.5	350	60	1000	—	V
117L7GT/ 117M7GT	Rectifier-Tetrode ¹⁴	8-pin O.	8AO	Htr.	117	0.09	117	75	—	—	V
117N7GT	Rectifier-Tetrode ¹⁴	8-pin O.	8AV	Htr.	117	0.09	117	75	350	450	V
117P7GT	Rectifier-Tetrode ¹⁴	8-pin O.	8AV	Htr.	117	0.09	117	75	350	450	V
117Z4GT	Half-Wave Rectifier	6-pin O.	5AA	Htr.	117	0.04	117	90	350	—	V
117Z6GT	Voltage Doubler	7-pin O.	7Q	Htr.	117	0.075	235	60	700	360	V
217-A	Half-Wave Rectifier	4-pin J.	T-3A ⁴	Fil.	10	3.25	—	—	3500	600	V
217-C	Half-Wave Rectifier	4-pin J.	T-3A ⁴	Fil.	10	3.25	—	—	7500	600	V
Z225 ¹⁷	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	250 ¹⁰	10000	1000	M
HK253	Half-Wave Rectifier	4-pin J.	T-3A ⁴	Fil.	5.0	10	—	350	10000	1500	V
705A RK-705A ²⁰	Half-Wave Rectifier	4-pin W	T-3 AA	Fil. ²¹	2.5 ²⁸ 5.0	5.0 5.0	— —	50 100	35000 35000	375 750	V
816	Half-Wave Rectifier	4-pin S.	4P	Fil.	2.5	2.0	1750	125	5000	500	M
836	Half-Wave Rectifier	4-pin M.	4P	Htr.	2.5	5.0	—	—	5000	1000	V
866A/866	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	250 ¹⁰	10000	1000	M
866B	Half-Wave Rectifier	4-pin M.	4P	Fil.	5.0	5.0	—	—	8500	1000	M
866Jr.	Half-Wave Rectifier	4-pin M.	4B	Fil.	2.5	2.5	1250	250 ⁹	—	—	M
HY866Jr.	Half-Wave Rectifier	4-pin M.	4P	Fil. ²²	2.5	2.5	1750	250 ⁹	5000	—	M
RK866	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	250 ¹⁰	10000	1000	M
871 ²⁴	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	2.0	1750	250	5000	500	M
878 ¹¹	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	7100	5	20000	—	V
879 ¹¹	Half-Wave Rectifier	4-pin S.	4P	Fil.	2.5	1.75	2650	7.5	7500	100	V
872A/872	Half-Wave Rectifier	4-pin J.	T-3A ⁴	Fil.	5.0	7.5	—	1250	10000	5000	M
975A	Half-Wave Rectifier	4-pin J.	T-3A ⁴	Fil.	5.0	10.0	—	1500	15000	6000	M
OZ4A/ 1003	Full-Wave Rectifier	8-pin O.	4R	Cold ²⁵	—	—	—	110	880	—	G
1005/ CK1005	Full-Wave Rectifier	8-pin O.	T-9F	Fil.	6.3	0.1	—	70	450	—	G
1006 CK1006	Full-Wave Rectifier	4-pin M.	4C	Fil.	1.75	2.25	—	200	1600	—	G
CK1007	Full-Wave Rectifier	8-pin O.	T-9G	Fil.	1.0	1.2	—	110	980	—	G
CK1009 BA	Full-Wave Rectifier	4-pin M.	—	Cold ²⁵	—	—	—	350	1000	—	G
1616	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	130	6000	800	V
1641/ RK60	Full-Wave Rectifier	4-pin M.	T-4AG	Fil.	5.0	3.0	—	50 250	4500 2500	—	V
8008	Half-Wave Rectifier	4-pin ¹⁶	Fig. 11 ¹⁵	Fil.	5.0	7.5	—	1250	10000	5000	M
8013A ²⁵	Half-Wave Rectifier	4-pin M.	4P	Fil.	2.5	5.0	—	20	40000	150	V
8016	Half-Wave Rectifier	6-pin O.	4Y	Fil.	1.25	0.2	—	2.0	10000	7.5	V
8020	Half-Wave Rectifier	4-pin M.	4P	Fil.	5.0 5.8	5.5 6.5	10000 12500	1.0 100	40000 40000	750 750	V
RK19	Full-Wave Rectifier	4-pin M.	T-3A ⁴	Htr.	7.5	2.5	1250	200 ¹⁰	3500	600	V
RK21	Half-Wave Rectifier	4-pin M.	4P	Htr.	2.5	4.0	1250	200 ¹⁰	3500	600	V
RK22	Full-Wave Rectifier	4-pin M.	T-4AG ⁴	Htr.	2.5	8.0	1250	200 ¹⁰	3500	600	V

¹ Refer to Receiving Tube Diagrams.

² M. — medium; S. — small; O. — octal; L. — loktal; J. — jumbo; B. — button; W. — wafer.

³ Metal tube series.

⁴ Refer to Transmitting Tube Diagrams.

⁵ Types 1 and 1-V interchangeable.

⁶ With input choke of at least 20 henrys.

⁷ M. — Mercury-vapor type; V. — high-vacuum type; G. — gaseous type.

⁸ Tapped for pilot lamps.

⁹ Per pair with choke input.

¹⁰ Condenser input.

¹¹ For use with cathode-ray tubes.

¹² Maximum rating, corresponding to 130-volt line condition; normal rating is 12.6 v. for 117-v. line.

¹³ With 100 ohms min. resistance in series with plate; without series resistor, maximum r.m.s. plate rating is 117 volts.

¹⁴ For other data, see Table IX.

¹⁵ See Supplementary Base Diagrams.

¹⁶ Same as 872A/872 except for heavy-duty push-type base. Filament connected to pins 2 and 3, plate to top cap.

¹⁷ Same as 872A/872 except for small envelope.

¹⁸ Choke input.

¹⁹ Without panel lamp.

²⁰ Ceramic base.

²¹ Center tapped.

²² Formerly heater type.

²³ Formerly type LT.

²⁴ Obsolete.

²⁵ Formerly 8013.

²⁶ Using only one-half of filament.

²⁷ In clipper service series resistor limiting instantaneous peak ma. required.

²⁸ Ionic heated cathode.

TABLE XIV — TRIODE TRANSMITTING TUBES

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacities (μfd.)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.										
958-A****	0.6	1.25	0.1	135	7	1.0	12	0.6	2.6	0.8	Special	5BD	Class-C Amp.-Oscillator	135	- 20	7	1.0	0.035	0.6	958-A
RK24**	1.5	2.0	0.12	180	20	6.0	8.0	3.5	5.5	3.0	4-pin S.	4D	Class-C Amp.-Oscillator	180	- 45	16.5	6.0	0.5	2.0	RK24
6J6****	1.5	6.3	0.45	300	30	16	32	2.2	1.6	0.4	7-pin B.	7BF ¹⁵	Class-C Amp. (Telegraphy)	150	- 10	30	16	0.35	3.5	6J6
9002***	1.6	6.3	0.15	250	8	2	25	1.2	1.4	1.1	7-pin B.	7TM	Class-C Amp.-Oscillator	180	- 35	7	1.5	—	0.5	9002
955***	1.6	6.3	0.15	180	8	2	25	1.0	1.4	0.6	Acorn	5BC	Class-C Amp. Oscillator	180	- 35	7	1.5	—	0.5	955
HY114B***	1.8	1.4	0.155	180	12	3.0	13	1.0	1.3	1.0	5-pin O.	T-8AC	Class-C Amp.-Oscillator	180	- 30	12	2.0	0.2	1.4 ¹¹	HY114B
													Class-C Amp. Plate-Mod.	180	- 35	12	2.5	0.3	1.4 ¹¹	
3A5 ⁷	2.0	1.4 2.8	0.22 0.11	135	30	5.0	15	0.9	3.2	1.0	7-pin B.	7BC ¹⁵	Class-C Amp.-Oscillator	135	- 20	30	5.0	0.2	2.0 ²¹	3A5
6F4****	2.0	6.3	0.225	150	20	8	17	2.0	1.9	0.6	Acorn	7BR	Class-C Amp.-Oscillator	150	- 15 550 ¹⁹ 2000 ¹⁹	20	7.5	0.2	1.8 ²⁰	6F4
HY24* ⁵	2.0	2.0	0.13	180	20	4.5	9.3	2.7	5.4	2.3	4-pin S.	4D	Class-C Amp. (Telegraphy)	180	- 45	20	4.5	0.2	2.7	HY24
													Class-C Amp. (Telephony)	180	- 45	20	4.5	0.3	2.5	
RK33* ^{4,7}	2.5	2.0	0.12	250	20	6.0	10.5	3-2	3-2	2.5	7-pin S.	T-7DA	Class-C Amp.-Oscillator	250	- 60	20	6.0	0.54	3.5	RK33
6N4	3.0	6.3	0.2	180	12	—	32	—	—	—	7-pin B.	—	Class-C Amp. Oscillator	180	—	—	—	—	—	6N4
2C22 7193	3.5	6.3	0.3	500	—	—	20	2.2 ¹⁴	3.6	0.7	8-pin O.	4AM ¹⁵	Class-C Amp. (Telegraphy)	—	—	—	—	—	—	2C22/7193
HY615*** HY-E1148	3.5	6.3	0.175	300	20	4.0	20	1.4	1.6	1.2	5-pin O.	T-8AG	Class-C Amp.-Oscillator	300	- 35	20	2.0	0.4	4.0 ¹¹	HY615
													Class-C Amp. Plate-Mod.	300	- 35	20	3.0	0.8	3.5 ¹¹	HY-E1148
HY6J5GTX*	3.5	6.3	0.3	250	20	4.0	20	3.8	2.7	3.0	6-pin O.	T-8AD	Class-C Amp. (Telegraphy)	250	- 30	20	2.0	0.2	3	HY6J5GTX
													Class-C Amp. (Telephony)	250	- 30	20	2.5	0.4	3	
GL-446A**** GL-446B****	3.75	6.3	0.75	400 ²³	20	—	45	2.2	1.6	0.02	6-pin O.	Fig. 19	Class-C Amp.-Oscillator	250	10000 ¹⁹ 20000 ¹⁹	25 ²³	—	—	—	GL-446 GL-446B
GL-2C44**** GL-461A****	5.0	6.3	0.75	500 ²³	40 ²³	—	—	2.7	2.0	0.1	6-pin O.	Fig. 17	Class-C Amp.-Oscillator	250	—	—	—	—	—	GL-2C44 GL-461A
6C4	5.0	6.3	0.15	300	25	8.0	17	1.8	1.6	1.3	7-pin B.	6BG ¹⁵	Class-C Amp.-Oscillator	300	- 27	25	7.0	0.35	5.5	6C4
1626	5.0	12.6	0.25	250	25	8.0	5.0	3.2	4.4	3.4	8-pin O.	T-8AD	Class-C Amp.-Oscillator	250	- 70	25	5.0	0.5	4.0	1626
2C21/RK33	5 ⁷	6.3	0.6	250	40 ⁷	12 ⁷	—	1.6	1.6	2.0	7-pin S.	T-7DA	Class-C Amp.-Oscillator	250	- 60	40 ⁷	12 ⁷	1.0 ⁷	7 ⁷	2C21/RK33
2C40***	6.5	6.3	0.75	500	25	—	36	2.1	1.3	0.05	6-pin O.	Fig. 19	Class-C Amp.-Oscillator	250	- 5	20	0.3	—	0.075	2C40
2C43	—	6.3	0.9	500	40	—	48	2.9	1.7	0.05	6-pin O.	Fig. 19	Class-C Amp.-Oscillator	470 ²⁸	—	38 ²⁸	—	—	9 ²⁸	2C43
2C26A***	10	6.3	1.10	3500 ²¹	—	—	16.3	2.6	2.8	1.1	8-pin O.	4BB	Pulse Oscillator	400	- 15	16	—	—	—	2C26A
2C45	10	7.0	1.18	250	40	0	3.6	5.0	7.7	3.0	4-pin M.	4D	Class-A Modulator	250	- 40	29	0	0	1.0	2C45
2C34 RK34****	10 ⁷	6.3	0.8	300	80	20	13	3.4	2.4	0.5	7-pin M.	T-7DC	Class-C Amp.-Oscillator	300	- 36	80	20	1.8	16	2C34 RK34
205D	14	4.5	1.6	400	50	10	7.2	5.2	4.8	3.3	4-pin M.	4D	Class-C Amp.-Oscillator	400	- 112	45	10	1.5	10	205D
													Class-C Amp. (Plate-Mod.)	350	- 144	35	10	1.7	7.1	
2C25	15	7.0	1.18	450	60	15	8.0	6.0	8.9	3.0	4-pin M.	4D	Class-C Amp.-Oscillator	450	- 100	65	15	3.2	19	2C25
													Class-C Amp. Plate-Mod.	350	- 100	50	12	2.2	12	

TABLE XIV — TRIODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{mf.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.										
10Y	15	7.5	1.25	450	65	15	8	4.1	7.0	3.0	4-pin M.	4D	Class-C Amp.-Oscillator	450	-100	65	15	3.2	19	10Y
													Class-C Amp. Plate-Mod.	350	-100	50	12	2.2	12	
843	15	2.5	2.5	450	40	7.5	7.7	4.0	4.5	4.0	5-pin M.	5A	Class-C Amp.-Oscillator	450	-140	30	5.0	1.0	7.5	843
													Class-C Amp. (Plate-Mod.)	350	-150	30	7.0	1.6	5.0	
RK59 ⁷	15	6.3	1.0	500	90	25	25	5.0	9.0	1.0	4-pin M.	T-4D	Class-C Amp.-Oscillator	500	-60	90	14	1.3	32	RK59
HY75 ⁸	15	6.3	2.5	450	80	20	10	1.6	3.8	0.6	5-pin O.	T-8AC	Class-C Amp.-Oscillator	450	-50	80	12	—	21 ¹¹	HY75
													Class-C Amp. Plate-Mod.	450	-60	80	12	—	16 ¹¹	
1602	15	7.5	1.25	450	60	15	8.0	4.0	7.0	3.0	4-pin M.	4D	Class-C Amp. (Telephony)	450	-115	55	15	3.3	13	1602
													Class-C Amp. (Telephony)	350	-135	45	15	3.5	8.0	
841	15	7.5	1.25	450	60	20	30	4.0	7.0	3.0	4-pin M.	4D	Class-C Amp. (Telephony)	450	-34	50	15	1.8	15	841
													Class-C Amp. (Telephony)	350	-47	50	15	2.0	11	
10 RK10 ⁴	15	7.5	1.25	450	65	15	8.0	3.0	8.0	4.0	4-pin M.	4D	Class-C Amp. (Telephony)	450	-100	65	15	3.2	19	10
													Class-C Amp. (Telephony)	350	-100	50	12	2.2	12	RK10
RK100 ⁴	15	6.3	0.9	150	250	100	40	23	19	3.0	6-pin M.	T-6B	Class-C Oscillator ¹⁰	110	—	80	8.0	—	3.5	RK100
													Class-C Amplifier ¹⁰	110	—	185	40	2.1	12	
1608	20	2.5	2.5	425	95	25	20	8.5	9.0	3.0	4-pin M.	4D	Class-C Amp. (Telephony)	425	-90	95	20	3.0	27	1608
													Class-C Amp. (Telephony)	350	-80	85	20	3.0	18	
310	20	7.5	1.25	600	70	15	8.0	4.0	7.0	2.2	4-pin M.	4D	Class-C Amp. (Telephony)	600	-150	65	15	4.0	25	310
													Class-C Amp. (Telephony)	500	-190	55	15	4.5	18	
801-A/801 [*]	20	7.5	1.25	600	70	15	8.0	4.5	6.0	1.5	4-pin M.	4D	Class-C Amp. (Telephony)	600	-150	65	15	4.0	25	801-A/801
													Class-C Amp. (Telephony)	500	-190	55	15	4.5	18	
HY801-A [*]	20	7.5	1.25	600	70	15	8.0	4.5	6.0	1.5	4-pin M.	4D	Class-C Amp. (Telephony)	600	-200	70	15	4.0	30	HY801-A
													Class-C Amp. (Telephony)	500	-200	60	15	4.5	22	
T20 ⁶	20	7.5	1.75	750	85	25	20	4.9	5.1	0.7	4-pin M.	3G	Class-C Amp. (Telephony)	750	-85	85	18	3.6	44	T20
													Class-C Amp. Plate-Mod.	750	-140	70	15	3.6	38	
TZ20 ⁶	20	7.5	1.75	750	85	30	62	5.3	5.0	0.6	4-pin M.	3G	Class-C Amp. (Telephony)	750	-40	85	28	3.75	44	TZ20
													Class-C Amp. Plate-Mod.	750	-100	70	23	4.8	38	
15E	20	5.5	4.2	10000 ²³	—	—	25	1.4	1.15	0.3	None	T-4AF	Oscillator at 400 Mc. ²²	10000	4500 ¹³	3	1	—	10000 ²⁵	15E
														2000	-130	63	18	4.0	100	
25T	25	6.3	3.0	2000	75	25	24	2.7	1.5	0.3	4-pin M.	3G	Class-C Amp.-Oscillator	1500	-95	67	13	2.2	75	25T
														1000	-70	72	9	1.3	47	
														2000	-170	63	17	4.5	100	
3C24* 24G	25	6.3	3.0	2000	75	25	23	1.7	1.5	0.3	4-pin S.	2D	Class-C Amp.-Oscillator	1500	-110	67	15	3.1	75	3C24 24G
														1000	-80	72	15	2.6	47	
														750	-120	105	21	3.2	55	
RK11 ⁴	25	6.3	3.0	750	105	35	20	7.0	7.0	0.9	4-pin M.	3G	Class-C Amp. (Telephony)	600	-120	85	24	3.7	38	RK11
														750	-100	105	35	5.2	55	
RK12 [*]	25	6.3	3.0	750	105	40	100	7.0	7.0	0.9	4-pin M.	3G	Class-C Amp. Plate-Mod.	600	-100	85	27	3.8	38	RK12
														2000	-140	56	18	4.0	90	
HK24 [*]	25	6.3	3.0	2000	75	30	25	2.5	1.7	0.4	4-pin S.	3G	Class-C Amp. Plate-Mod.	1500	-145	50	25	5.5	60	HK24
														750	-45	75	15	2.0	42	
HY25 [*]	25	7.5	2.25	800	75	25	55	4.2	4.6	1.0	4-pin M.	3G	Class-C Amp. (Telephony)	700	-45	75	17	5.0	39	HY25

TABLE XIV — TRIODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{fd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.										
8025	30	6.3	1.92	1000	65	20	18	2.7	2.8	0.35	4-pin M.	4AQ	Class-C Amp. (Grid. Mod.)	1000	-135	50	4 ¹⁷	3.5 ¹⁷	20	8025
	20				65								20	1.4 ¹⁷	22					
	30				80								20	1.6 ¹⁷	35					
Twin 30* ^{5,7}	30	6.0	4.0	1500	85	25	32	1.9	2.0	0.3	4-pin M.	T-4DB	Class-C Amp. (Telegraphy)	1500	-100	150 ⁸	40 ⁸	15	225	Twin 30
HY30Z *	30	6.3	2.25	850	90	25	87	6.0	4.9	1.0	4-pin M.	T-4BE	Class-C Amp. Plate-Mod.	1250	-100	135 ⁸	40 ⁸	15	125	HY30Z
													Class-C Amp.-Oscillator	850	-75	90	25	2.5	58	
HY31Z * HY1231Z* ^{5,7}	30	6.3	3.5	500	150	30	45	5.0	5.5	1.9	4-pin M.	T-4D	Class-C Amp. (Telegraphy)	500	-45	150	25	2.5	56	HY31Z HY1231Z
		12.6	1.7										Class-C Amp. (Telephony)	400	-100	150	30	3.5	45	
316A ****	30	2.0	3.65	450	80	12	6.5	1.2	1.6	0.8	None ⁹	—	Class-C Amp. (Telephony)	450	—	80	12	—	7.5	316A
													Class-C Amp. Plate-Mod.	400	—	80	12	—	6.5	
809 * ⁶	30	6.3	2.5	1000	125	—	50	5.7	6.7	0.9	4-pin M.	3G ¹⁵	Class-C Amp. (Telegraphy)	1000	-75	100	25	3.8	75	809
1623 * ⁶	30	6.3	2.5	1000	100	25	20	5.7	6.7	0.9	4-pin M.	3G ¹⁵	Class-C Amp. Plate-Mod.	750	-60	100	32	4.3	55	1623
													Class-C Amp.-Oscillator	1000	-90	100	20	3.1	75	
53A	35	5.0	12.5	15000	—	—	35	3.6	1.9	0.4	None	T-4B	Class-C Amp. Plate-Mod.	750	-125	100	20	4.0	55	53A
													Oscillator at 300 Mc.	Approximately 50 watts output						
RK30 * ⁴	35	7.5	3.25	1250	80	25	15	2.75	2.5	2.75	4-pin M.	T-4BC	Class-C Amp. (Telegraphy)	1250	-180	90	18	5.2	85	RK30
													Class-C Amp. Plate-Mod.	1000	-200	80	15	4.5	60	
800 *	35	7.5	3.25	1250	80	25	15	2.75	2.5	2.75	4-pin M.	T-4BC	Class-C Amp. (Telegraphy)	1250	-175	70	15	4.0	65	800
													Class-C Amp. Plate-Mod.	1000	-200	70	15	4.0	50	
1628****	40	3.5	3.25	1000	60	15	23	2.0	2.0	0.4	None ⁹	T-4BB	Class-C Amp.-Oscillator	1000	-65	50	15	1.7	35	1628
													Class-C Amp. Plate-Mod.	800	-100	40	11	1.6	22	
8012 **** GL-8012-A****	40 ¹⁴	6.3	2.0	1000	80	20	18	2.7	2.8	0.35	None ⁹	T-4BB	Grid-Modulated Amp.	1000	-120	50	3.5	5.0	20	8012 GL-8012-A
								2.7	2.5	0.4			Class-C Amp.-Oscillator	1000	-90	50	14	1.6	35	
RK18 * ¹	40	7.5	3.0	1250	100	40	18	6.0	4.8	1.8	4-pin M.	3G ¹⁵	Class-C Amp. Plate-Mod.	800	-105	40	10.5	1.4	22	RK18
													Class-C Amp. (Telegraphy)	1250	-160	100	12	2.8	95	
RK31	40	7.5	3.0	1250	100	35	170	7.0	1.0	2.0	4-pin M.	3G ¹⁵	Class-C Amp. Plate-Mod.	1000	-135	50	4.0	3.5	20	RK31
													Class-C Amp. (Telegraphy)	1250	-80	100	30	3.0	90	
HY40 *	40	7.5	2.25	1000	125	25	25	6.1	5.6	1.0	4-pin M.	3G ¹⁵	Class-C Amp. Plate-Mod.	1000	-80	100	28	3.5	70	HY40
													Class-C Amp. (Telegraphy)	1000	-90	125	20	5.0	94	
HY40Z *	40	7.5	2.6	1000	125	30	80	6.2	6.3	0.8	4-pin M.	3G ¹⁵	Class-C Amp. Plate-Mod.	850	-90	125	15	3.5	82	HY40Z
													Grid-Modulated Amp.	1000	—	125	—	—	20 ¹⁵	
T40 * ⁶	40	7.5	2.5	1500	150	40	25	4.5	4.8	0.8	4-pin M.	3G ¹⁵	Class-C Amp. (Telegraphy)	1000	-27	125	25	5.0	94	T40
													Class-C Amp. Plate-Mod.	850	-30	100	30	7.0	82	
TZ40 * ⁶	40	7.5	2.5	1500	150	45	62	4.8	5.0	0.8	4-pin M.	3G ¹⁵	Grid-Modulated Amp.	1000	—	60	—	—	20 ¹⁵	TZ40
													Class-C Amp.-Oscillator	1500	-140	150	28	9.0	158	
													Class-C Amp. Plate-Mod.	1250	-115	115	20	5.25	104	
													Class-C Amp.-Oscillator	1500	-90	150	38	10	165	
													Class-C Amp. Plate-Mod.	1250	-100	125	30	7.5	116	

TABLE XIV — TRIODE TRANSMITTING TUBES — Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{mf.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type	
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.											
HY57 *	40	6.3	2.25	850	110	25	50	4.9	5.1	1.7	4-pin M.	3G ¹⁵	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	850 700 850	- 48 - 45 —	110 90 70	15 17 —	2.5 5.0 —	70 47 20 ¹²	HY57	
756 *	40	7.5	2.0	850	110	25	8.0	3.0	7.0	2.7	4-pin M.	4D	Class-C Amplifier	850	—	110	25	—	—	756	
830 *	40	10	2.15	750	110	18	8.0	4.9	9.9	2.2	4-pin M.	4D	Class-C Amplifier Grid-Modulated Amp.	750 1000	- 180 - 200	110 50	18 2.0	7.0 3.0	55 15	830	
35T 35TG	50	5.0	4.0	2000	150	50	39	4.1	1.8	0.3	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate Mod.	2000 1500	- 135 - 120	125 100	45 30	13 5.0	200 120	35T 35TG	
8010-R ****	50	6.3	2.4	1350	150	20	30	2.3	1.5	0.97	Special	—	Grid Modulated Amp. Class-C Amplifier	2000	- 400	60	3.0	3.0	50	8010-R	
RK32 **	50	7.5	3.25	1250	100	25	11	2.5	3.4	0.7	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1250 1000	- 225 - 310	100 100	14 21	4.8 8.7	90 70	RK32	
RK35 *	50	7.5	4.0	1500	125	20	9.0	3.5	2.7	0.4	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1500 1250 1500	- 250 - 250 - 180	115 100 37	15 14 —	5.0 4.6 2.0	120 93 25	RK35	
RK37 *	50	7.5	4.0	1500	125	35	28	3.5	3.2	0.2	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1500 1250 1500	- 130 - 150 - 50	115 100 50	30 23 —	7.0 5.6 2.4	122 90 26	RK37	
UH50 *	50	7.5	3.25	1250	125	25	10.6	2.2	2.6	0.3	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1250 1250 1250	- 225 - 325 - 200	125 125 60	20 10 2.0	7.5 11.5 3.0	115 115 25	UH50	
UH51 *	50	5.0	6.5	2000	175	25	10.6	2.2	2.3	0.3	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	2000 1500 1500	- 500 - 400 - 400	150 165 85	20 15 2.0	15 200 8.0	225 200 65	UH51	
HK54 *	50	5.0	5.0	3000	150	30	27	1.9	1.9	0.2	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	3000 2500 2000	- 290 - 250 - 150	100 100 39	25 8.0 1.5	10 210 3.0	250 210 28	HK54	
HK154 *	50	5.0	6.5	1500	175	30	6.7	4.3	5.9	1.1	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1500 1250 1500	- 590 - 460 - 450	167 170 52	20 20 —	15 12 5.0	200 162 28	HK154	
HK158 *	50	12.6	2.5	2000	200	40	25	4.7	4.6	1.0	4-pin M.	2D	Class-C Amp.-Oscillator Class-C Amp. Plate-Mod.	2000 2000	- 150 - 140	125 105	25 25	6.0 5.0	200 170	HK158	
WE304A * 304B *	50	7.5	3.25	1250	100	25	11	2.0	2.5	0.7	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1250 1000	- 200 - 180	100 100	— —	— —	85 65	WE304A 304B	
356A *	50	5.0	5.0	1500	120	35	50	2.25	2.75	1.0	Special	T-4BD	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1250	- 60 - 100	100 100	— 35	— —	100 85	100 85	356A
808	50	7.5	4.0	1500	150	35	47	5.3	2.8	0.15	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1250	- 200 - 225	125 100	30 32	9.5 10.5	140 105	808	
834 *	50	7.5	3.1	1250	100	20	10.5	2.2	2.6	0.6	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1250 1000	- 225 - 310	90 90	15 17.5	4.5 6.5	75 58	834	
841A *	50	10	2.0	1250	150	30	14.6	3.5	9.0	2.5	4-pin M.	3G	Class-C Amplifier	—	—	—	—	—	85	841A	
841SW	50	10	2.0	1000	150	30	14.6	—	9.0	—	4-pin M.	3G	Class-C Amplifier	—	—	—	—	—	85	841SW	

448

TABLE TRANSMITTING TUBES — Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{fd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.										
T55 **	55	7.5	3.0	1500	150	40	20	5.0	3.9	1.2	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1500	-170 -195	150 125	18 15	6.0 5.0	170 145	T55
811 **	55	6.3	4.0	1500	150	50	160	5.5	5.5	0.6	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1250	-113 -125	150 125	35 50	8.0 11	170 120	811
812 **	55	6.3	4.5	1500	150	35	29	5.3	5.3	0.8	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1250	-175 -125	150 125	25 25	6.5 6.0	170 120	812
RK51 *	60	7.5	3.75	1500	150	40	20	6.0	6.0	2.5	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1500 1250 1500	-250 -200 -130	150 105 60	31 17 0.4	10 4.5 2.3	170 96 128	RK51
RK52 *	60	7.5	3.75	1500	130	50	170	6.6	12	2.2	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1250	-120 -120	130 115	40 47	7.0 8.5	135 102	RK52
T-60 HF60	60	10	2.5	1600	150	—	20	—	5.2	—	4-pin M.	2D	Class-C Amp.-Oscillator	1600	-150	—	—	—	100	T-60 HF60
826 ***	60	7.5	4.0	1000	125	40	31	3.7	2.9	1.4	Special	T-9A	Class-C Amp.-Oscillator Class-C Amp. Plate-Mod. Class-B Amp. (Telephony) Grid-Modulated Amp.	1000 800 1000 1000	-70 -98 -50 -125	125 94 65 65	35 35 8.5 9.5	5.8 6.2 3.7 8.2	86 53 25 22	826
830B 930B	60	10	2.0	1000	150	30	25	5.0	11	1.8	4-pin M.	3G	Class-C Amp.-Oscillator Class-C Amp. Plate-Mod. Class-B Amp. (Telephony) Class-C Amp. (Telegraphy)	1000 800 1000 1000	-110 -150 -35 -75	140 95 85 175	30 20 6.0 20	7.0 5.0 6.0 7.5	90 50 26 131	830B 930B
HY51A * HY51B *	65	7.5 10	3.5 2.25	1000	175	25	25	6.5	7.0	1.1	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1000 1000 1000	-75 -67.5 —	175 130 100	20 15 —	7.5 7.5 —	104 104 33 ¹²	HY51A HY51B
HY51Z *	65	7.5	3.5	1000	175	35	85	7.9	7.2	0.9	4-pin M.	T-4BE	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1000 1000 1000	-22.5 -30 —	175 150 100	35 35 —	10 10 —	131 104 33 ¹²	HY51Z
UH35 **	70	5.0	4.0	1500	150	35	30	1.4	1.6	0.2	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1500	-170 -120	150 100	30 30	7.0 5.0	170 120	UH35
V70 V70B	70	10	2.5	1500	140	25	14	5.0	9.0	2.3	4-pin J. 4-pin M.	T-3AB 3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1250	-215 -250	130 130	6.0 6.0	3.0 3.0	140 120	V70 V70B
V70A V70C	70	10	2.5	1500	140	20	25	5.0	9.5	2.0	4-pin J. 4-pin M.	T-3AB 3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1000 800	-110 -150	140 95	30 20	7.0 5.0	90 50	V70A V70C
V70D	70	10	3.0	1500	165	40	20	4.5	4.5	1.75	4-pin M.	3G	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod.	1500 1000	-200 -140	130 165	20 30	6.0 7.0	140 120	V70D
50T *	75	5.0	6.0	3000	100	30	12	2.0	2.0	0.4	4-pin M.	2D	Class-C Amplifier	3000	-600	100	25	—	250	50T
75TH 75TL	75	5.0	6.25	3000	225	40 35	20 12	2.7 2.6	2.3 2.4	0.3 0.4	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. (Telegraphy)	2000 2000	-200 -300	150 150	32 21	10 8	225 225	75TH 75TL
HF75 *	75	10	3.25	2000	120	—	12.5	—	2.0	—	4-pin M.	2D	Class-C Osc.-Amp.	2000	—	120	—	—	150	HF75
TW75 *	75	7.5	4.15	2000	175	60	20	3.35	1.5	0.7	4-pin M.	2D	Class-C Amp.-Oscillator Class-C Amp. Plate-Mod. Class-C Amp. (Telegraphy)	2000 2000 1500	-175 -260 -200	150 125 150	37 32 18	12.7 13.2 6.0	225 198 170	TW75
T-100 HF100	75	10	2.0	1500	150	30	23	3.5	4.5	1.4	4-pin M.	2D	Class-C Amp. (Telegraphy) Class-C Amp. Plate-Mod. Grid-Modulated Amp.	1500 1250 1500	-200 -250 -280	150 110 72	18 21 1.5	6.0 8.0 6.0	170 105 42	T-100 HF100

TABLE XIV — TRIODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{mfd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.										
111H	75	10	2.25	1500	160	—	23	—	4.6	—	4-pin M.	2D	Class-C Osc.-Amp.	1500	—	160	—	—	175	111H
ZB120	75	10	2.0	1250	160	40	90	5.3	5.2	3.2	4-pin J.	4E	Class-C Amp. (Telegraphy)	1250	-135	160	23	5.5	145	ZB120
													Class-C Amp. Plate-Mod.	1000	-150	120	21	5.0	95	
													Grid-Modulated Amp.	1250	—	95	8.0	1.5	45	
327B	75	10.5	10.6	15000	—	—	30	3.4	2.45	0.3	None	T-4D	—	—	—	—	—	—	—	327B
242A	85	10	3.25	1250	150	50	12.5	6.5	13	4.0	4-pin J.	4E	Class-C Amp. (Telegraphy)	1250	-500	150	—	—	125	242A
284D	85	10	3.25	1250	150	100	4.8	6.0	8.3	5.6	4-pin J.	4E	Class-C Amp. Plate-Mod.	1000	-450	150	50	—	100	284D
8005 ^{*4}	85	10	3.25	1500	200	45	20	6.4	5.0	1.0	4-pin M.	T-4BB	Class-C Amp.-Oscillator	1500	-130	200	32	7.5	220	8005
													Class-C Amp. Plate-Mod.	1250	-195	190	28	9.0	170	
													Class-B Amp. (Telephony)	1500	-80	83	1.0	5.0	45	
RK36 ^{*4}	100	5.0	8.0	3000	165	35	14	4.5	5.0	1.0	4-pin M.	2D	Class-C Amp. (Telegraphy)	2000	-360	150	30	15	200	RK36
													Class-C Amp. (Telephony)	2000	-360	150	30	15	200	
													Grid-Modulated Amp.	2000	-270	72	1.0	3.5	42	
RK38 ^{*4}	100	5.0	8.0	3000	165	40	—	4.6	4.3	0.9	4-pin M.	2D	Class-B Amp. (Telephony)	2000	-180	75	3.0	10	50	RK38
													Class-C Amp. (Telegraphy)	2000	-200	160	30	10	225	
													Class-C Amp. (Telephony)	2000	-200	160	30	10	225	
100TH	100	5.0	6.3	3000	225	60	40	2.9	2.0	0.4	4-pin M.	2D	Grid-Modulated Amp.	2000	-150	80	2.0	5.5	60	100TH
													Class-B Amp. (Telephony)	2000	-100	75	2.0	7.0	55	
													Class-C Amp. (Telegraphy)	3000	-200	165	51	18	400	
100TL	100	5.0	6.3	3000	225	50	14	2.3	2.0	0.4	4-pin M.	2D	Class-C Amp. Plate-Mod.	3000	-210	167	45	18	400	100TL
													Class-B Amp. (Telephony)	3000	-70	50	2.0	5.0	50	
													Grid-Modulated Amp.	3000	-400	70	3.0	7.0	100	
VT127A	100	5.0	10.4	16000	—	—	15.5	2.7	2.3	0.35	None	T-4B	Class-C Amp. (Telegraphy)	3000	-400	165	30	20	400	VT127A
227A	100	10.5	10.7	15000	—	—	31	3.0	2.2	0.30	None	T-4B	Class-C Amp. Plate-Mod.	3000	-600	167	35	18	400	
327A	100	10.5	10.7	15000	—	—	31	3.4	2.3	0.35	None	T-4D	Class-B Amp. (Telephony)	3000	-280	50	1.0	5.0	50	
HK254	100	5.0	7.5	4000	200	40	25	3.3	3.4	1.1	4-pin J.	T-3AC	Grid-Modulated Amp.	3000	-560	60	2.0	7.0	90	HK254
													Class-C Amp. (Telegraphy)	4000	-380	120	35	20	475	
													Class-C Amp. Plate-Mod.	3000	-290	135	40	23	320	
RK58 ⁵	100	10	3.25	1250	175	70	—	—	—	—	—	T-3AB	Class-B Amp. (Telephony)	3000	-125	51	2.0	3.0	54	RK58
													Grid-Modulated Amp.	3000	—	51	3.0	4.0	58	
													Class-C Amp. (Telegraphy)	1250	-90	150	30	6.0	130	
HF120	100	10	3.25	1250	175	—	12	—	—	—	—	—	Class-C Amp. Plate-Mod.	1000	-135	150	50	16	100	HF120
HF125	100	10	3.25	1500	175	—	25	—	—	—	—	—	Class-B Amp. (Telephony)	1250	—	106	15	6.0	42.5	
													Class-C Amp.-Oscillator	1250	—	175	—	—	150	
													Class-C Amp.-Oscillator	1500	—	175	—	—	200	HF125

XIV — TRIODE TR

TABLE XIV — TRIODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{mfd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.										
HF140	100	10	3.25	1250	175	—	12	—	12.5	—	4-pin J.	—	Class-C Amp.—Oscillator	1250	—	175	—	—	150	HF140
203A 303A	100	10	3.25	1250	175	60	25	6.5	14.5	5.5	4-pin J.	4E	Class-C Amp. (Telegraphy)	1250	-125	150	25	7.0	130	203A 303A
													Class-B Amp. (Telephony)	1000	-135	150	50	14	100	
203H	100	10	3.25	1500	175	60	25	6.5	11.5	1.5	4-pin J.	T-3AB	Class-C Amp. (Telegraphy)	1250	-45	105	3.0	3.0	42.5	203H
													Class-B Amp. (Telephony)	1500	-200	170	12	3.8	200	
211 311 835	100	10	3.25	1250	175	50	12	6.0 6.0	14.5 9.25	5.5 5.0	4-pin J.	4E	Class-C Amp. (Telephony)	1250	-160	167	19	5.0	160	211 311 835
													Class-B Amp. (Telephony)	1500	-48	100	3.0	2.0	52	
242B 342B	100	10	3.25	1250	150	50	12.5	7.0	13.6	6.0	4-pin J.	4E	Class-C Amp. (Telegraphy)	1250	-225	150	18	7.0	130	242B 342B
													Class-C Amp. Plate-Mod.	1000	-160	150	50	—	100	
242C	100	10	3.25	1250	150	50	12.5	6.1	13.0	4.7	4-pin J.	4E	Class-B Amp. (Telephony)	1250	-80	120	—	—	50	242C
													Class-C Amp. (Telegraphy)	1250	-175	150	—	—	130	
261A 361A	100	10	3.25	1250	150	50	12	6.5	9.0	4.0	4-pin J.	4E	Class-C Amp. Plate-Mod.	1000	-160	150	50	—	100	261A 361A
													Class-B Amp. (Telephony)	1250	-100	125	—	—	50	
276A 376A	100	10	3.0	1250	125	50	12	6.0	9.0	4.0	4-pin J.	4E	Class-C Amp. (Telegraphy)	1250	-175	125	—	—	100	276A 376A
													Class-C Amp. Plate-Mod.	1000	-160	125	50	—	85	
284B	100	10	3.25	1250	150	100	5.0	4.2	7.4	5.3	4-pin J.	T-3AB	Class-B Amp. (Telephony)	1250	-100	125	—	—	50	284B
													Class-C Amp. (Telegraphy)	1250	-500	150	—	—	125	
295A	100	10	3.25	1250	175	50	25	6.5	14.5	5.5	4-pin J.	4E	Class-C Amp. Plate-Mod.	1000	-125	150	50	—	100	295A
													Class-B Amp. (Telephony)	1250	-75	105	—	—	42.5	
838 938	100	10	3.25	1250	175	70	—	6.5	8.0	5.0	4-pin J.	4E	Class-C Amp. (Telegraphy)	1250	-90	150	30	6.0	130	838 938
													Class-C Amp. (Telephony)	1000	-135	150	60	16	100	
852	100	10	3.25	3000	150	40	12	1.9	2.6	1.0	4-pin M.	2D	Class-B Amp. (Telephony)	1250	0	106	15	6.0	42.5	852
													Class-C Amp. (Telegraphy)	3000	-600	85	15	12	165	
8003	100	10	3.25	1500	250	50	12	5.8	11.7	3.4	4-pin J.	T-3AB	Class-C Amp. (Telephony)	2000	-500	67	30	2.3	75	8003
													Class-B Amp. (Telephony)	3000	-250	43	0	7.0	40	
3C22****	125	6.3	2.0	1000	150	70	40	4.9	2.4	0.05	6-pin O.	Fig. 30	Class-C Amp.—Oscillator	1350	-180	245	35	11	250	3C22
													Class-C Amp. Plate-Mod.	1100	-250	200	40	15	167	
F-123-A DR-123C	125	10	4.0	2000	300	75	14.5	6.5	8.5	3.3	4-pin J.	Fig. 26	Class-B Amp. (Telephony)	1350	-110	110	1.5	8	50	F-123-A DR-123C
													Class-C Amp. (Telegraphy)	1500	-250	250	30	11	300	
													Class-C Amp. Plate-Mod.	1500	-290	160	25	10	200	
													Class-B Amp. (Telephony)	1500	-100	120	1	6	65.5	

TABLE XIV — IRIODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{mf.d.}$)			Base 1	Socket Connections 2	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts 3	Approx. Carrier Output Power Watts	Type	
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.											
RK57/ /805	125	10	3.25	1500	210	70	—	6.5	8.0	5.0	4-pin J.	T-3AB	Class-C Amp. (Telegraphy)	1500	-105	200	40	8.5	215	RK57/ /805	
													Class-C Amp. (Telephony)	1250	-160	160	60	16	140		
T125 *	125	10	4.5	2500	250	60	25	6.3	6.0	1.3	4-pin J.	T-3AC	Class-B Amp. (Telephony)	1500	-10	115	15	7.5	57.5	T125	
													Class-C Amp. (Telegraphy)	2500	-200	240	31	11	475		
HF130	125	10	3.25	1250	210	—	12.5	—	9.0	—	4-pin J.	—	Class-C Amp. Plate-Mod.	2000	-215	200	28	10	320	HF130	
HF150	125	10	3.25	1500	210	—	12.5	—	7.2	—	4-pin J.	—	Class-C Amp. Oscillator	1250	-210	—	—	—	170	HF150	
HF175	125	10	4.0	2000	250	—	18	—	6.3	—	4-pin J.	—	Class-C Amp. Oscillator	1500	—	210	—	—	200	HF175	
GL146	125	10	3.25	1500	200	60	75	7.2	9.2	3.9	4-pin GL	T-4BG	Class-C Amp. Oscillator	2000	—	250	—	—	300	GL146	
													Class-C Amp. Plate-Mod.	1000	-200	160	40	—	100		
GL152	125	10	3.25	1500	200	60	25	7.0	8.8	4.0	4-pin GL	T-4BG	Class-B Amp. (Telephony)	1250	0	132	—	—	55	GL152	
													Class-C Amp. Oscillator	1250	-150	180	30	—	150		
805	125	10	3.25	1500	210	70	40	60	8.5	6.5	10.5	4-pin J.	T-3AB	Class-C Amp. Plate-Mod.	1000	-200	160	40	—	100	805
														Class-B Amp. (Telephony)	1250	0	132	—	—	55	
150T ⁴	150	5.0	10	3000	200	50	13	3.0	3.5	0.5	4-pin J.	T-3AC	Class-C Amp. (Telephony)	1500	-105	200	40	8.5	215	150T	
													Class-C Amp. Plate-Mod.	1250	-160	160	60	16	140		
152TH	150	5 10 ¹³	12.51	3000	450	85	20	5.7	4.5	0.8	Special	4BC	Class-C Amp. (Telegraphy)	3000	-600	200	35	—	450	152TH	
152TL	150	5 10 ¹³	6.25	3000	450	75	12	4.5	4.4	0.7			Class-C Amp. (Telephony)	3000	-300	250	70	27	600		
TW150	150	10	4.1	3000	200	60	35	3.9	2.0	0.8	4-pin J.	T-3AC	Class-C Amp. Oscillator	3000	-400	250	40	20	600	TW150	
													Class-C Amp. Plate-Mod.	3000	-170	200	45	17	470		
HK252-L**	150	5 10 ¹³	13 6.5	3000	500	75	10	7.0	5.0	0.4	Special	T-4BF	Class-C Amp. Oscillator	3000	-400	250	30	15	610	HK252-L	
													Class-C Amp. Plate-Mod.	2500	-350	250	35	16	500		
HF200 HV18	150	10-11	3.4	2500	200	50	18	5.2	5.8	1.2	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	2500	-300	200	18	8.0	380	HF200 HV18	
													Class-C Amp. Plate-Mod.	2000	-350	160	20	9.0	250		
HD203A	150	10	4.0	2000	250	60	25	—	12	—	4-pin J.	T-3AB	Class-B Amp. (Telephony)	2500	-140	90	—	4.0	80	HD203A	
HF250	150	10.5	4.0	2500	200	—	18	—	5.8	—	4-pin J.	T-3AC	Class-C Amplifier	—	—	—	—	—	375	HF250	
HK354	150	5.0	10	4000	300	50	14	4.5	3.8	1.1	4-pin J.	T-3AC	Class-C Amp. Oscillator	2500	—	200	—	—	375	HK354	
													Class-C Amp. Plate-Mod.	4000	-690	245	50	48	830		
HK354C	150	5.0	10	4000	300	50	14	4.5	3.8	1.1	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	3000	-550	210	50	35	525	HK354C	
													Class-B Amp. (Telephony)	3000	-205	78	2.0	10	82		
HK354D	150	5.0	10	4000	300	55	22	4.5	3.8	1.1	4-pin J.	T-3AC	Grid-Modulated Amp.	3000	-400	78	3.0	12	85	HK354D	
													Class-C Amp. (Telegraphy)	3500	-490	240	50	38	690		
HK354E	150	5.0	10	4000	300	60	35	4.5	3.8	1.1	4-pin J.	T-3AC	Class-C Amp. Plate-Mod.	3500	-425	210	55	36	525	HK354E	
													Class-C Amp. (Telegraphy)	3500	-448	240	60	45	690		
HK354F	150	5.0	10	4000	300	75	50	4.5	3.8	1.1	4-pin J.	T-3AC	Class-C Amp. Plate-Mod.	3000	-437	210	60	45	525	HK354F	
													Class-C Amp. (Telegraphy)	3500	-368	250	75	50	720		
810 ⁶ 1627 ¹	150	10	4.5	2250	275	70	36	8.7	4.8	12	4-pin J.	T-3AC	Class-C Amp. Plate-Mod.	3000	-312	210	75	45	525	810 1627	
													Class-C Amp. (Telegraphy)	2250	-160	275	40	12	475		
													Class-C Amp. (Telephony)	1800	-200	250	50	17	335		
													Class-B Amp. (Telephony)	2250	-70	100	2.0	4.0	75		
													Grid-Modulated Amp.	2250	-140	100	2.0	4.0	75		

TABLE XIV — TRIODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances ($\mu\text{fd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ³	Approx. Carrier Output Power Watts	Type
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.										
8000 ⁴	150	10	4.5	2250	275	40	16.5	5.0	6.4	3.3	4-pin J.	T-3AC	Class-C Amp.-Oscillator	2250	-210	275	25	9.0	475	8000
													Class-C Amp. Plate-Mod.	1800	-320	250	20	8.8	335	
													Class-B Amp. (Telephony)	2250	-145	100	0	5.4	75	
													Grid-Modulated Amp.	2250	-265	100	0	2.5	75	
RK63 RK63A	200	5.0 6.3	10 14	3000	250	60	37	2.7	3.3	1.1	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	3000	-200	233	45	17	525	RK63 RK63A
													Class-C Amp. Plate-Mod.	2500	-200	205	50	19	405	
													Class-B Amp. (Telephony)	3000	-150	100	1.0	12	100	
													Grid-Modulated Amp.	3000	-250	100	7.0	12.5	100	
T200	200	10	5.75	2500	350	80	16	9.5	7.9	1.6	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	2500	-280	350	54	25	685	T200
													Class-C Amp. Plate-Mod.	2000	-260	300	54	23	460	
F-127-A	200	10	2.0	3000	325	70	38	13	4	13	4-pin J.	Fig. 26	Class-C Amp. (Telegraphy)	3000	-250	250	47	18	600	F-127-A
													Class-C Amp. Plate-Mod.	2500	-300	200	58	25.2	420	
822 822S	200	10	4.0	2500	300	60	30	8.5	13.5	2.1	4-pin J. 4-pin J.	T-3AB T-3AC	Class-C Amp. (Telegraphy)	2500	-190	300	51	17	600	822 822S
													Class-C Amp. Plate-Mod.	2000	-75	250	43	13.7	405	
HF300	200	11-12	4.0	3000	275	60	23	6.0	6.5	1.4	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	3000	-400	250	28	16	600	HF300
													Class-C Amp. Plate-Mod.	2000	-300	250	36	17	385	
													Class-B Amp. (Telephony)	2500	-100	120	0.5	6.0	105	
													Class-C Amp. (Telegraphy)	2500	-240	300	30	10	575	
T814 HV12	200	10	4.0	2500	200	60	12	8.5	12.8	1.7	4-pin J.	T-3AB	Class-C Amp. Plate-Mod.	2000	-370	300	40	20	485	T814 HV12
													Class-C Amp. (Telegraphy)	2500	-175	300	50	15	585	
T822 HV27	200	10	4.0	2500	300	60	27	8.5	13.5	2.1	4-pin J.	T-3AB	Class-C Amp. Plate-Mod.	2000	-195	250	45	15	400	T822 HV27
													Class-B Amp. (Telephony)	2500	-95	195	5.0	8.0	110	
													Class-C Amp. (Telegraphy)	3300	-600	300	40	34	780	
													Class-C Amp. Plate-Mod.	3000	-670	195	27	24	460	
806 ⁴	225	5.0	10	3300	300	50	12.6	6.1	4.2	1.1	4-pin J.	T-3AC	Class-B Amp. (Telephony)	3300	-280	102	—	10.3	115	806
250TH	250	5.0	10.5	4000	350	100	37	5.0	2.9	0.7	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	2000	-120	350	100	34	750	250TH
													Class-C Amp. Plate-Mod.	3000	-210	330	75	42	750	
													Class-B Amp. (Telephony)	3000	-80	195	4.0	15	125	
													Grid-Modulated Amp.	3000	-160	125	4.0	20	125	
250TL	250	5.0	10.5	4000	350	50	14	3.7	3.1	0.7	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	3000	-350	335	45	29	750	250TL
													Class-C Amp. Plate-Mod.	3000	-350	335	45	29	750	
													Class-B Amp. (Telephony)	3000	-225	125	2.0	15	125	
													Grid-Modulated Amp.	3000	-450	125	2.0	15	125	
GL159	250	10	9.6	2000	400	100	20	11	17.6	5.0	4-pin GL	T-4BG	Class-C Amp.-Oscillator	2000	-200	400	17	6.0	620	GL159
													Class-C Amp. Plate-Mod.	1500	-240	400	23	9.0	450	
													Class-B Amp. (Telephony)	2000	-90	190	—	2.5	130	
													Class-C Amp.-Oscillator	2000	-100	400	42	10	620	
GL169	250	10	9.6	2000	400	100	85	11.5	19	4.7	4-pin GL	T-4BG	Class-C Amp. Plate-Mod.	1500	-100	400	45	10	450	GL169
													Class-B Amp. (Telephony)	2000	-10	190	—	3.5	130	
													Class-C Amp. (Telegraphy)	2500	-200	250	30	15	450	
													Class-C Amp. Plate-Mod.	2000	-250	250	35	20	350	
204A 304A	250	11	3.85	2500	275	80	23	12.5	15	2.3	Special	T-1A	Class-B Amp. (Telephony)	2500	-70	160	—	15	100	204A 304A
													Class-C Amp. (Telegraphy)	2500	-200	250	30	15	450	

TABLE XIV — TRIODE TRANSMITTING TUBES — Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Plate Current Ma.	Max. D.C. Grid Current Ma.	Amp. Factor	Interelectrode Capacitances (μμfd.)			Base	Socket Connections	Typical Operation	Plate Voltage	Grid Voltage	Plate Current Ma.	D.C. Grid Current Ma.	Approx. Grid Driving Power Watts ²	Approx. Carrier Output Power Watts	Type									
		Volts	Amps.					Grid to Fil.	Grid to Plate	Plate to Fil.																			
308B	250	14	4.0	2250	325	75	8.0	13.6	17.4	9.3	4-pin W.E.	T-2A	Class-C Amplifier	3500 2000	-600 -300	300 500	60	— —	800 800	308B									
HK454H ^{5,6}	250	5.0	11	5000	375	85	30	4.6	3.4	1.4	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	1750	-400	300	—	—	350	HK454H									
HK454-L ^{5,6}	250	5.0	11	5000	375	60	12	4.6	3.4	1.4	4-pin J.	T-3AC	Class-C Amp. Plate-Mod.	1250	-320	300	75	—	950	HK454-L									
219E	275	14	4.0	3000	350	75	16	14.9	18.8	8.6	4-pin W.E.	T-2A	Class-C Amplifier	3500	-275	270	60	28	760	219E									
241B												T-2AA	Class-C Amplifier	3500	-450	270	45	30	760	241B									
312E												T-2AA	Class-C Amplifier	3500	-450	270	45	30	760	312E									
300T ⁴	300	8.0	11.5	3500	350	75	16	4.0	4.0	0.6	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	2000	-225	300	—	—	400	300T									
HK304-L ⁸	300	5 10 ¹²	26 13	3000	1000	150	10	12	9.0	0.8	Special	T-4BF	Class-C Amp. Plate-Mod.	1500	-200	300	75	—	300	HK304-L									
													Class-B Amp. (Telephony)	2000	-120	300	—	—	200										
527	300	5.5	135.0	20000	—	—	38	19.0	12.0	1.4	Special	T-4B	Oscillator at 200 Mc.	Approximately 250 watts output					527										
HK654	300	7.5	15	4000	600	100	22	6.2	5.5	1.5	4-pin J.	T-3AC	Class-C Amp. (Telegraphy)	2000	-380	500	75	57	720	HK654									
304TH	300	5 10 ¹³	25 12.5	3000	900	170	20	13.5	10.2	0.7	Special	T-4BF	Class-C Amplifier	1500	-125	667	115	25	700	304TH									
304TL											Special	T-4BF	Class-C Amplifier	1500	-250	665	90	33	700	304TL									
833A	300	10	10	3000	500	100	35	12.3	6.3	8.5	Special	T-1AB	Class-C Amp. (Telephony)	2500	-300	335	75	30	635	833A									
270A	350	10	4.0	3000	375	75	16	18	21	2.0	Special	T-1A	Class-C Amp. Plate-Mod.	2250	-300	300	80	—	450	270A									
849 ⁴	400	11	5.0	2500	350	125	19	17	33.5	3.0	Special	T-1A	Class-C Amp. (Telephony)	2000	-300	300	30	14	425	849									
831 ⁴	400	11	10	3500	350	75	14.5	3.8	4.0	1.4	Special	T-1AA	Class-C Amp. (Telephony)	3000	-500	200	60	50	360	831									

1 S. — small; M. — medium; J. — jumbo; O. — octal.
 2 Refer to Transmitting Tube Diagrams.
 3 See Chapter Five for discussion of grid driving power.
 4 Obsolete type.
 5 Instant-heating filament for mobile use.
 6 Intermittent commercial and amateur service ratings.
 7 Twin triode. Values, except interelement capacities, are for both sections, in push-pull.
 8 The 805 has a variable high-μ grid.
 9 All wire leads. Ratings at 500 Mc.
 10 Gaseous discharge tube for use on 110-volt d.c.
 11 Output at 112 Mc.

12 Calculated at 33 per cent efficiency for 100 per cent modulation.
 13 Multiple-unit tube with dual filaments which can be connected in series or parallel.
 14 Forced-air cooling is recommended at ratings above 75 per cent of maximum.
 15 See Receiving Tube Base Diagrams.
 16 Input resonant frequency approximately 335 Mc.
 17 Subject to wide variation. 18 Cathode resistor in ohms.
 19 Grid-leak resistor in ohms.
 20 Approximately 45 milliwatts output at 1200 Mc. (With 100 volts and 2000-ohm grid resistor).

21 At 40 Mc. 22 At 150 Mc. 23 Absolute maximum.
 24 Max. peak volts, plate pulsed. 25 Pulse power output.
 26 Duty cycle = 0.5. 27 Duty cycle = 0.1.
 28 Values are for two tubes.

Frequency limits:
 * May be used at full ratings on 56-60 Mc. band and lower.
 ** May be used at full ratings on 112-Mc. band and lower.
 *** May be used at full ratings on 224-Mc. band and lower.
 **** May be used at full rating above 300 Mc.

TABLE XV—TETRODE AND PENTODE TRANSMITTING TUBES

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Screen Voltage	Max. Screen Dissipation Watts	Interelectrode Capacitances ($\mu\text{fd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Screen Resistor Ohms	Approx. Grid Driving Power Watts ⁴	Approx. Carrier Output Power Watts	Type	
		Volts	Amps.				Grid to Fil.	Grid to Plate	Plate to Fil.															
3A4	2.0	1.4 2.8	0.2 0.1	150	135	0.9	4.8	0.2	4.2	7-pin B.	7BB ¹¹	Class-C Amp.-Oscillator	150	135	0	-26	18.3	6.5	0.13	2300	—	1.2	3A4	
HY63* ^{6c}	3.0	2.5	0.125	200	100	0.6	8.0	0.1	8.0	7-pin O.	T-8DB	Class-C Amp.-Osc.	200	100	—	-22.5	20	4.0	2.0	—	0.1	3.0	HY63	
		1.25	0.225									Class-C Amp. Plate-Mod.	180	100	—	-35	15	3.0	2.0	—	0.2	2.0		
RK64* ⁵	6.0	6.3	0.5	400	100	3.0	10	0.4	9.0	5-pin M.	T-5BB	Class-C Amp. (Telegraphy)	400	100	30	-30	35	10	3.0	—	0.18	10	RK64	
												Class-C Amp. Plate-Mod.	300	—	30	-30	26	8.0	4.0	30000	0.2	6.0		
1610	6.0	2.5	1.75	400	200	2.0	8.6	1.2	13	5-pin M.	T-5CA	Class-C Amp.-Oscillator	400	150	—	-50	22.5	7.0	1.5	—	0.1	5.0	1610	
												Class-C Amp. (Telegraphy)	400	300	—	-40	62	12	1.6	—	0.1	12.5		
RK56*	8.0	6.3	0.55	300	300	4.5	10	0.2	9.0	5-pin M.	T-5BB	Class-C Amp. Plate-Mod.	950	200	—	-40	50	10	1.6	2800	0.28	8.5	RK56	
												Class-C Amp. (Telegraphy)	500	200	45	-90	55	38	4.0	—	0.5	22		
RK23	10	2.5	2.0	500	250	8	10	0.2	10	7-pin M.	T-7C	Class-C Amp. (Telephony)	400	150	0	-90	43	30	6.0	8300	0.8	13.5	RK23	
RK25		6.3	0.9									Suppressor-Modulated Amp.	500	200	-45	-90	31	39	4.0	—	0.5	6.0	RK25	
RK25B ⁴												Class-C Amp. (Telegraphy)	350	200	—	-35	50	10	3.5	20000	0.22	9		
1613	10	6.3	0.7	350	275	2.5	8.5	0.5	11.5	7-pin O.	75 ¹⁴	Class-C Amp. Plate-Mod.	275	200	—	-35	42	10	2.8	10000	0.16	6.0	1613	
												Class-C Amp. (Telegraphy)	350	200	—	-35	50	10	3.5	—	0.22	9.0		
6F6	11	6.3	0.7	375	285	3.75	6.5	0.2	13	7-pin O.	7AC ¹⁴	Class-C Amp.-Oscillator	275	200	—	-35	42	10	2.8	—	0.16	6.0	6F6	
6F6G							8.0	0.5	6.5			Class-C Amp. Plate-Mod.	275	200	—	-35	42	10	2.8	—	0.16	6.0	6F6G	
												Class-C Amp. (Telegraphy)	500	200	40	-70	80	15	4.0	20000	0.4	28		
837	12	12.6	0.7	500	300	8	16	0.2 ¹⁴	10	7-pin M.	T-7C	Class-C Amp. (Telephony)	400	140	40	-40	45	20	5.0	13000	0.3	11	837	
RK44 ⁵												Suppressor-Modulated Amp.	500	—	65	-20	30	23	3.5	14000	0.1	5.0		
												Class-C Amp. (Telegraphy)	600	250	40	-120	55	16	2.4	22000	0.30	23	RK44	
802 ⁷	13	6.3	0.9	600	250	6.0	12	0.15 ¹¹	8.5	7-pin M.	T-7C	Class-C Amp. Plate-Mod.	500	245	40	-40	40	15	1.5	16300	0.10	12	802	
												Suppressor-Mod. Amp.	600	250	-45	-100	30	24	5.0	14500	0.6	6.3		
												Class-C Amp.-Osc.	300	200	—	-45	60	7.5	2.5	—	0.3	12		
HY6V6-GTX*	13	6.3	0.5	350	225	2.5	9.5	0.7	9.5	7-pin O.	7AC ¹¹	Class-C Amp. Plate-Mod.	250	200	—	-45	60	6.0	2.0	15000	0.4	10	HY6V6-GTX	
												Class-C Amp. (Telegraphy)	425	200	—	-62.5	60	8.5	3.0	—	0.3	18		
HY60*	-15	6.3	0.5	425	225	2.5	10	0.2	8.5	5-pin M.	T-5BB	Class-C Amp. Plate-Mod.	325	200	—	-45	60	7.0	2.5	—	0.2	14	HY60	
												Class-C Amp.-Osc.	450	250	—	-45	75	15	3.0	—	0.5	24		
HY65* ⁵	15	6.3	0.85	450	250	4.0	9.1	0.18	7.2	7-pin O.	T-8DB	Class-C Amp. Plate-Mod.	350	200	—	-45	63	12	3.0	—	0.5	16	HY65	
												Class-C Amp.-Oscillator	450	250	—	-70	75	15	3.5	—	0.4	20		
2E25	15	6.0 ^c	0.8	450	250	4.0	8.5	0.18	6.0	8-pin O.	Fig. 24	Class-C Amp. Plate-Mod.	400	200	—	-45	60	12	3.0	—	0.4	16	2E25	
306A	15	2.75	2.0	300	300	6.0	13	0.35	13	5-pin M.	T-5CB	Class-C Amp. (Telephony)	300	180	—	-50	36	15	3.0	8000	—	7.0	306A	
307A	15	5.5	1.0	500	250	6.0	15	0.55	12	5-pin M.	T-5C	Class-C Amp. (Telegraphy)	500	250	0	-35	60	13	1.4	20000	—	20	307A	
RK-75												Suppressor-Modulated Amp.	500	200	-50	-35	40	20	1.5	14000	—	6.0		
832** ¹⁰	15	6.3 12.6	1.6 0.8	500	250	5.0	7.5	0.05 ¹¹	3.8	Special	7BP	Class-C Amp. (Telegraphy)	500	200	—	-65	72	14	2.6	21000	0.18	26	832	
												Class-C Amp. (Telephony)	425	200	—	-60	52	16	2.4	14000	0.15	16		
832A** ¹⁰	15	6.3 12.6	1.6 0.8	750	250	5.0	7.5	0.05 ¹¹	3.8	Special	7BP	Class-C Amp. (Telegraphy)	750	200	—	-65	48	15	2.8	36500	0.19	26	832A	
												Class-C Amp. (Telephony)	600	200	—	-65	36	16	2.6	25000	0.16	17		
844 ⁴	15	2.5	2.5	500	180	3.0	9.5	0.15	7.5	5-pin M.	T-5BB	Class-C Amp. (Telegraphy)	500	175	—	-125	25	—	5.0	—	—	9.0	844	
												Class-C Amp. (Telephony)	500	150	—	-100	20	—	—	—	—	4.0		
												Class-C Amp. (Telegraphy)	750	125	—	-80	40	—	5.5	—	—	1.0	16	
865	15	7.5	2.0	750	175	3.0	8.5	0.1 ¹¹	8.0	4-pin M.	T-4C	Class-C Amp. (Telephony)	500	125	—	-120	40	—	9.0	—	—	2.5	10	865

TABLE XV—TETRODE AND PENTODE TRANSMITTING TUBES—Continued

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Screen Voltage	Max. Screen Dissipation Watts	Interelectrode Capacitances ($\mu\text{mfd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Screen Resistor Ohms	Approx. Grid Driving Power Watts ⁴	Approx. Carrier Output Power Watts	Type	
		Volts	Amps.				Grid to Fil.	Grid to Plate	Plate to Fil.															
1619	15	2.5	2.0	400	300	3.5	10.5	0.35	12.5	7-pin O.	7AC ¹⁴	Class-C Amp. (Telegraphy)	400	300	—	- 55	75	10.5	5.0	9500	0.36	19.5	1619	
254A	20	5.0	3.25	750	175	5.0	4.6	0.1	9.4	4-pin M.	T-4C	Class-C Amp. Plate-Mod.	325	285	—	- 50	62	7.5	2.8	5000	0.18	13		
6L6	21	6.3	0.9	375	300	3.5	10	0.4	12	7-pin O.	7AC ¹⁴	Class-C Amp.-Oscillator	375	200	—	- 35	88	9.0	3.5	—	—	—	25	254A
6L6G							11.5	0.9	9.5			Class-C Amp. Plate-Mod. ⁸	325	—	- 70	65	—	—	—	—	—	—	—	—
6L6GX	21	6.3	0.9	500	300	3.5	11	1.5	7.0	7-pin O.	7AC	Class-C Amp. (Telegraphy)	500	250	—	- 50	90	9.0	2.0	—	0.25	30	6L6GX	
HY6L6-GTX*	21	6.3	0.9	500	300	3.5	11	0.5	7.0	7-pin O.	7AC	Class-C Amp. Plate-Mod.	325	225	—	- 45	90	9.0	3.0	—	0.25	20		
												Class-C Amp.-Osc.	500	250	—	- 50	90	9.0	2.0	—	0.5	30		
T21*	21	6.3	0.9	400	300	3.5	13	0.7	12	6-pin M.	T-6B	Class-C Amp. (Telegraphy)	400	250	—	- 50	95	8.0	3.0	—	0.2	25	T21	
RK49	21	6.3	0.9	400	300	3.5	11.5	1.4	10.6	6-pin M.	T-6B	Class-C Amp. Plate-Mod.	350	200	—	- 45	65	17	5.0	—	0.35	14		
												Class-C Amp. (Telegraphy)	400	250	—	- 50	95	8.0	3.0	—	0.2	25		
1614*	21	6.3	0.9	375	300	3.5	10	0.4	12.5	7-pin O.	7AC	Class-C Amp. (Telephony)	300	200	—	- 45	60	15	5.0	6700	0.34	12	RK49	
RK41* ⁶ RK39*	25	2.5 6.3	2.4 0.9	600	300	3.5	13	0.2	10	5-pin M.	T-5BB	Class-C Amp. (Telegraphy)	375	250	—	- 40	80	10	2.0	12500	0.1	21		
												Class-C Amp. Plate-Mod.	325	—	—	- 40	70	8.0	2.0	10000	0.1	15		
HY61/ 807*	25	6.3	0.9	600	300	3.5	11	0.2	7.0	5-pin M.	T-5BB	Class-C Amp. (Telephony)	600	250	—	- 50	93	10	3.0	—	0.38	36	RK41 RK39	
815** ^{7 10}	25	6.3	1.6	500	200	4.0	13.3	0.2 ¹¹	8.5	8-pin O.	T-8FA ¹²	Class-C Amp. (Telephony)	475	250	—	- 50	100	9.0	3.0	39000	0.22	40		
												Class-C Amp. (Telephony)	600	250	—	- 50	83	9.0	3.5	25000	0.2	27		
254B	25	7.5	3.25	750	150	5.0	11.2	0.085	5.4	4-pin M.	T-4C	Class-C Amp.-Oscillator	500	200	—	- 45	150	17	2.5	—	0.13	56	815	
1624*	25	2.5	2.0	600	300	3.5	11	0.25	7.5	5-pin M.	T-5DC	Class-C Amp. Plate-Mod.	400	175	—	- 45	150	15	3.0	—	0.16	45		
												Class-C Amplifier	750	150	—	-135	75	—	—	—	—	—	—	—
RK66*	30	6.3	1.5	600	300	3.5	12	0.25	10.5	5-pin M.	T-5C	Class-C Amp. (Telegraphy)	600	300	—	- 60	90	10	5.0	30000	0.43	35	1624	
807* ⁷ 1625* ⁷	30	6.3 12.6	0.9 0.45	750	300	3.5	11	0.2 ¹¹	7.0	5-pin M. 7-pin M.	T-5BB Fig. 29	Class-C Amp. Plate-Mod.	500	275	—	- 50	75	9.0	3.3	25000	0.25	24		
												Class-C Amp. (Telephony)	600	300	—	- 60	90	11	5.0	—	0.5	40		
2E22	30	6.3	1.5	750	250	10	13	0.2	8.0	5-pin M.	5J ¹⁴	Class-C Amp. Plate-Mod.	500	—	—	- 50	75	8.0	3.2	25000	0.23	25	RK66	
RK20 ⁵ RK20A RK46 ⁴	40	7.5 7.5 12.6	3.0 3.25 2.5	1250	300	15	14	0.01	12	5-pin M.	T-5C	Class-C Amp. (Telephony)	750	250	—	- 50	100	8.0	3.0	—	0.22	50		
												Class-C Amp. (Telephony)	600	275	—	- 90	100	6.5	4.0	—	0.4	42.5		
HY69* ⁶	40	6.3	1.5	600	300	5.0	15.4	0.23	6.5	5-pin M.	T-5D	Class-C Amp.-Oscillator	750	250	-60	- 60	100	16	—	—	—	—	48	
												Suppressor Mod. Amp.	750	250	-90	- 90	55	29	—	—	—	16.5		
829 ^{5**10}	40	6.3 12.6	2.25 1.12	500	225	40	14.5	0.1 ¹¹	7.0	Special	7BP ¹⁴	Class-C Amp. (Telegraphy)	1250	300	45	-100	92	36	11.5	—	1.6	84		
												Class-C Amp. (Telephony)	1000	300	0	-100	75	30	10	23000	1.3	52		
829	40	6.3 12.6	2.25 1.12	500	225	40	14.5	0.1 ¹¹	7.0	Special	7BP ¹⁴	Suppressor-Modulated Amp.	1250	300	-45	-100	48	44	11.5	—	1.5	21		
												Grid-Modulated Amp.	1250	300	45	-142	40	7.0	1.8	—	1.5	20		
829	40	6.3 12.6	2.25 1.12	500	225	40	14.5	0.1 ¹¹	7.0	Special	7BP ¹⁴	Class-C Amp.-Oscillator	600	250	—	- 60	100	12.5	4.0	30000	0.25	42		
												Class-C Amp. Plate-Mod.	600	250	—	- 60	100	12.5	5.0	30000	0.35	42		
829	40	6.3 12.6	2.25 1.12	500	225	40	14.5	0.1 ¹¹	7.0	Special	7BP ¹⁴	Modulated Doubler	600	200	—	-300	90	11.5	6.0	35000	2.8	27		
												Class-C Amp. (Telegraphy)	500	200	—	- 45	240	32	12	9300	0.7	83		
829	40	6.3 12.6	2.25 1.12	500	225	40	14.5	0.1 ¹¹	7.0	Special	7BP ¹⁴	Class-C Amp. Plate-Mod.	425	200	—	- 60	212	35	11	6400	0.8	63		
												Grid-Modulated Amp.	500	200	—	- 38	120	10	2.0	—	0.5	23		

TABLE XV — TETRODE AND PENTODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Screen Voltage	Max. Screen Dissipation Watts	Interelectrode Capacitances ($\mu\text{fd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Screen ³ Resistor Ohms	Approx. Grid Driving Power Watts ⁴	Approx. Carrier Output Power Watts	Type	
		Volts	Amps.				Grid to Fil.	Grid to Plate	Plate to Fil.															
829A ⁵⁺¹⁰	40	6.3	2.25	750	240	7.0	14.4	0.1 ¹¹	7.0	Special	7BP ¹⁴	Class-C Amp.-Oscillator	750	200	—	-55	160	30	12	18300	0.8	87	829A	
		12.6	1.12									600	200	—	-70	150	30	12	13300	0.9	70			
		750	200									—	-55	80	5.0	0	—	0.7	24					
829B ^{**10} 3E29 ^{**10}	40	12.6	1.125	750	225	6	14.5	0.1	7.0	Special	7BP ¹⁴	Class-C Amp. (Grid Mod.)	750	200	—	-55	80	5	0	—	0.7	24	829B 3E29	
		6.3	2.25	600	225	7						150	30	12.0	13300	0.9	70							
HY1269 ^{*6}	40	6.3	3.5	750	300	5.0	16.0	0.25	7.5	5-pin M.	T-5DB ¹³	Class-C Amp. (Plate-Mod.)	600	200	—	-70	150	30	12.0	18300	0.8	87	HY1269	
		12.6	1.75									750	225	7	100	12.5	4	—	0.25	63				
RK47	50	10	3.25	1250	300	10	13	0.12	10	5-pin M.	T-5D	Class-C Amp. Plate-Mod.	600	250	—	-70	100	12.5	5	35000	0.5	42	RK47	
												Grid-Modulated Amp.	750	300	—	—	80	—	—	—	—	20		
												Class-C Amp. (Telephony)	1250	300	—	-70	138	14	7.0	—	1.0	120		
312A	50	10	2.8	1250	500	20	15.5	0.15	12.3	6-pin M.	T-6C	Class-C Amp. Plate-Mod.	900	300	—	-150	120	17.5	6.0	—	1.4	87	312A	
												Grid-Modulated Amp.	1250	300	—	-30	60	2.0	0.9	—	4.0	25		
												Class-C Amp. (Telephony)	1250	300	20	-55	100	36	5.5	—	0.7	90		
804 ⁷	50	7.5	3.0	1500	300	15	16	0.01 ¹¹	14.5	5-pin M.	T-5C	Class-C Amp. Plate-Mod.	1000	—	40	-40	95	35	7.0	22000	1.0	65	804	
												Suppressor-Mod. Amp.	1250	—	-85	-50	50	42	5.0	22000	0.55	23		
												Class-C Amp. (Telephony)	1500	300	45	-100	100	35	7.0	34000	1.95	110		
305A	60	10	3.1	1000	200	6	10.5	0.14	5.4	4-pin M.	T-4CE	Class-C Amp. Plate-Mod.	1250	250	50	-90	75	20	6.0	50000	0.75	65	305A	
												Grid-Modulated Amp.	1500	300	45	-130	50	13.5	3.7	—	1.3	28		
												Suppressor-Mod. Amp.	1500	300	-50	-115	50	32	7.0	—	0.95	28		
HY67	65	6.3	4.5	1250	300	10	—	0.19	14.5	5-pin M.	T-5DB	Class-C Amp. (Telephony)	1000	200	—	-200	125	—	—	—	—	—	85	HY67
		12.6	2.25									800	200	—	-270	125	—	—	—	70				
		Class-C Amp. (Telephony)	1250									300	—	-80	175	22.5	10	—	1.5	152				
814 ⁷	65	10	3.25	1500	300	10	13.5	0.1 ¹¹	13.5	5-pin M.	T-5D	Class-C Amp. Plate-Mod.	1000	300	—	-150	145	17.5	14	—	2.0	101	814	
												Grid-Modulated Amp.	1250	300	—	—	78	—	—	—	—	32.5		
												Class-C Amp. (Telephony)	1500	300	—	-90	150	24	10	50000	1.5	160		
282A	70	10	3.0	1000	250	5.0	12.2	0.2	6.8	4-pin M.	T-4C	Class-C Amp. (Telephony)	1250	300	—	-150	145	20	10	48000	3.2	130	282A	
												Class-C Amp. Plate-Mod.	1500	250	—	-120	60	3.0	2.5	—	4.2	35		
												Class-C Amp. (Telephony)	1000	150	—	-160	100	—	—	—	—	33		
4E27/ 8001	75	5.0	7.5	4000	750	30	12	0.06	6.5	7-pin J.	T-7CB	Class-C Amp. Plate-Mod.	750	150	—	-180	100	—	50	—	—	50	4E27/ 8001	
												Class-C Amp. (Telephony)	2000	750	—	-200	150	18	0.7	300000	0.2	230		
												Suppressor-Mod. Amp.	2000	600	60	-200	100	8	0.6	240000	0.1	200		
HK257* HK257B**	75	5.0	7.5	4000	500	25	13.8	0.04	6.7	7-pin J.	T-7CB	Class-C Amp. (Telephony)	2000	500	-300	-130	55	45	3.0	—	—	0.4	35	HK257 HK257B
												Class-C Amp. Plate-Mod.	2000	500	60	-200	150	11	6.0	—	1.4	230		
												Suppressor-Modulated Amp.	1800	400	60	-130	135	11	8.0	—	1.7	178		
828 ⁷	80	10	3.25	2000	750	23	13.5	0.05 ¹¹	14.5	5-pin M.	T-5C	Class-C Amp. Plate-Mod.	2000	500	-300	-130	55	27	3.0	—	—	0.4	35	828
												Class-C Amp. (Telephony)	1500	400	75	-100	180	28	12	40000	2.2	200		
												Class-C Amp. Plate-Mod.	1250	400	75	-140	160	28	12	30000	2.7	150		
RK28 ⁵	100	10	5.0	2000	400	35	15	0.02	15	5-pin J.	T-5C	Grid-Modulated Amp.	1500	400	75	-150	80	4.0	1.3	—	—	1.3	41	RK28
												Class-C Amp. (Telephony)	2000	400	45	-100	150	55	13	21000	2.0	210		
												Class-C Amp. (Telephony)	1500	400	45	-100	135	52	13	21000	2.0	155		
RK28 ⁵	100	10	5.0	2000	400	35	15	0.02	15	5-pin J.	T-5C	Suppressor-Modulated Amp.	2000	400	-45	-100	85	65	13	—	—	1.8	60	RK28
												Grid-Modulated Amplifier	2000	400	45	-140	80	20	4.0	—	0.9	75		

TABLE XV — TETRODE AND PENTODE TRANSMITTING TUBES — *Continued*

Type	Max. Plate Dissipation Watts	Cathode		Max. Plate Voltage	Max. Screen Voltage	Max. Screen Dissipation Watts	Interelectrode Capacitances ($\mu\text{mfd.}$)			Base ¹	Socket Connections ²	Typical Operation	Plate Voltage	Screen Voltage	Suppressor Voltage	Grid Voltage	Plate Current Ma.	Screen Current Ma.	Grid Current Ma.	Screen Resistor Ohms	Approx. Grid Driving Power Watts ⁴	Approx. Carrier Output Power Watts	Type
		Volts	Amps.				Grid to Fil.	Grid to Plate	Plate to Fil.														
RK48 RK48A	100	10	5.0	2000	400	22	17	0.13	13	5-pin J.	T-5D	Class-C Amp. (Telegraphy)	2000	400	—	-100	180	40	6.5	—	1.0	250	RK48 RK48A
												Class-C Amp. (Telephony)	1500	400	—	-100	148	50	6.5	22000	1.0	165	
												Grid-Modulated Amplifier	1500	400	—	-145	77	10	1.5	—	1.6	40	
813	100	10	5.0	2000	400	22	16.3	0.2 ¹¹	14	7-pin J.	Fig. 28	Class-C Amp. (Telegraphy)	2000	400	—	-90	180	15	3.0	107000	0.5	260	813
												Class-C Amp. (Telephony)	1600	400	—	-130	150	20	6.0	21600	1.2	175	
												Grid-Modulated Amplifier	2000	400	—	-120	75	3.0	—	—	50		
850	100	10	3.25	1250	175	10	17	0.25 ¹¹	25	4-pin J.	T-3B	Class-C Amp. (Telegraphy)	1250	175	—	-150	160	—	35	—	10	130	850
												Class-C Amp. (Telephony)	1000	140	—	-100	125	—	40	—	65		
												Grid-Modulated Amplifier	1250	175	—	-13	110	—	—	—	40		
860	100	10	3.25	3000	500	10	7.75	0.08 ¹¹	7.5	4-pin M.	T-4CB	Class-C Amp.-Oscillator	3000	300	—	-150	85	25	15	—	7.0	165	860
												Class-C Amp. Plate-Mod.	2000	220	—	-200	85	25	38	100000	17	105	
4-125A**	125	5.0	6.2	3000	400	20	10.3	0.03	3.0	Special	Fig. 27	Class-C Amp. (Telegraphy)	3000	350	—	-150	167	30	9	—	2.5	375	4-125A
												Class-C Amp. Plate Mod.	2500	350	—	-330	150	30	13	—	6	300	
RK28A	125	10	5.0	2000	400	35	15	0.02	15	5-pin J.	T-5C	Class-C Amp. (Telegraphy)	2000	400	45	-100	170	60	10	—	1.6	250	RK28A
												Class-C Amp. Plate-Mod.	1500	400	45	-100	135	54	10	18500	1.6	150	
												Grid-Modulated Amp.	2000	400	45	-55	80	18	2.0	—	0.5	60	
												Suppressor-Mod. Amp.	2000	—	-45	-115	90	52	11.5	30000	1.5	60	
												Class-C Amp. (Telegraphy)	2000	500	40	-90	160	45	12	—	2.0	210	
803	125	10	5.0	2000	600	30	17.5	0.15 ¹¹	29	5-pin J.	T-5C	Class-C Amp. (Telephony)	1600	500	100	-80	150	20	4.0	20000	4.0	155	803
												Suppressor-Modulated Amp.	2000	—	-110	-100	80	48	15	35000	2.5	53	
												Grid-Modulated Amplifier	2000	600	40	-80	80	20	4.0	—	2.0	53	
RK65	215	5.0	14	3000	500	35	10.5	0.24	4.75	4-pin J.	T-3BC	Class-C Amp. (Telegraphy)	3000	400	—	-100	240	70	24	—	6.0	510	RK65
												Class-C (Plate & Screen Mod.)	2500	—	—	-150	200	70	22	30000	6.3	380	
4-250A*	250	5.0	14.5	4000	600	50	12.7	0.06	4.5	Special	Fig. 27	Class-C Amp. (Telegraphy)	4000	500	—	-250	250	22	13	—	4.1	750	4-250A
												Class-C Amp. (Telephony)	2500	500	—	-100	325	70	22	—	3.7	562	
861	400	11	10	3500	750	35	14.5	0.1 ¹¹	10.5	Special	T-1B	Class-C Amp. (Telegraphy)	3500	500	—	-250	300	40	40	—	30	700	861
												Class-C Amp. (Telephony)	3000	375	—	-200	200	—	55	70000	35	400	

458

¹S. — small; M. — medium; O. — octal; J. — jumbo.

²See Transmitting Tube Base Diagrams.

³In plate-and-screen modulated Class-C amplifiers, connect screen-dropping resistor direct to r.f. B+ to mod., and bypass for r.f. only. This does not apply to the 828.

⁴See Chapter 4-8 for discussion of grid driving power.

⁵Obsolete type. ⁶Instant-heating filament for mobile operation.

⁷Intermittent commercial and amateur service ratings.

⁸Triode connection — screen-grid tied to plate.

⁹Calculated on basis of 33% efficiency at 100% modulation.

¹⁰Dual tube. Values for both sections, in push-pull.

¹¹With external shielding.

¹²Terminals 3 and 6 must be connected together.

¹³Early tubes of this type do not have center-tapped filament.

¹⁴See Receiving Tube Base Diagrams.

¹⁵Only for Class-C Telegraphy up to 120 Mc.

Frequency limits:

* May be used at full ratings on 56-60 Mc. band and lower.

** May be used at full ratings on 112-Mc. band and lower.

*** May be used at full ratings on 224-Mc. band and lower.

**** May be used at full ratings above 300 Mc.

TABLE XVI—MAGNETRON AND VELOCITY-MODULATED TUBES

Type	Max. Plate or Collector Dissipation Watts	Cathode		Base	Socket Connections	Typical Operation	Plate or Collector Voltage	Grid No. 4 Voltage	Grid No. 3 Voltage	Grid No. 2 Voltage	Grid No. 1 Voltage	Grid No. 4 Current Ma.	Grid No. 3 Current Ma.	Grid No. 2 Current Ma.	Plate or Collector Current Ma.	Stabilizing Electrode Voltage	Stabilizing Electrode Current Ma.	Magnetic Field Gauss	Carrier Output Watts	Type	
		Volts	Amps.																		
2J25-1	4.0	1.8	2.0	4-pin M.	4AP	Magnetron Oscillator ¹	1000	—	—	—	—	—	—	—	—	4	650	10	1300	1.0	2J25
2J25 ^{2, 6}	50	6.3	0.75	Special	T-9C	Class-C Amp. (Grid-Mod.)	1500	800	3600	3600	-33	1.0	0.3	0.5	25	—	—	—	—	9.0	825
410-R ³	—	6.3	—	8-pin O.	T-9D	Class-C Amp. (Telephony)	1500	800	3600	3600	-40	2.0	0.5	1.0	45	—	—	—	—	35	—
						Oscillator-Amplifier or Frequency Multiplier	2500 ⁴	—	—	—	—	—	—	—	—	—	—	—	—	20	410-R

¹ Transit-time split-plate type magnetron with internal circuit (approximate wavelength 10 cm.)
² Inductive-output amplifier (recommended for frequencies above 300 Mc.).

³ Klystron with integral resonators (recommended for frequencies above 1000 Mc.).
⁴ Collector anode voltage should be applied before applying grid voltage.

⁵ Grid no. 2 (smoother grid) is electrically connected to collector anode.
⁶ Focusing electromagnet (double lens) should be operated at approximately 1000 ampere turns.

TABLE XVII—TELEVISION TRANSMITTING TUBES

Type	Name	Socket Connections ¹	Heater		Use	Collector Voltage	Pattern Electrode Voltage	Anode No. 2 Voltage	Anode No. 1 Voltage	Cut-off Grid Voltage ²	Signal Plate Voltage	Collector Current μ a. ³	Beam Current μ a.	Pattern Electrode Current ⁴	Signal ⁵ Plate Input	Beam ⁶ Resolution Capability	Signal Output Volts	Type
			Volts	Amps.														
1840	Orthicon	M	6.3	0.6	Direct and film pick-up	—	—	300 ⁷	300	-40	—	—	1.0	—	—	—	0.03-0.15	1840
1847	Iconoscope	Fig. 1	6.3	0.6	Direct pick-up	600	—	600	150	-120	—	—	—	—	—	—	—	1847
1848	Iconoscope	Fig. 25	6.3	0.6	Direct pick-up	1200	—	1000 ⁷	300	-40	—	0.1	0.25	—	—	—	0.015-0.075	1848
1849	Iconoscope	Fig. 21	6.3	0.6	Film pick-up	1000	—	1000	360	-25	—	0.1	—	—	—	—	—	1849
1850	Iconoscope	Fig. 21	6.3	0.6	Direct pick-up	—	—	—	—	—	—	—	—	—	—	—	—	1850
														Same as 1849				
1050-A	Iconoscope	Fig. 35	6.3	0.6	Direct and film pick-up	1000 ¹¹	—	300 ¹⁰	1000 ⁹	-50	1000	0.2 ¹¹	—	—	—	—	—	1850-A
1898	Monoscope	Fig. 20	2.5	2.1	Test pattern	—	950	1000	300	-60	—	—	2.0	2.0	—	—	—	1898
1899	Monoscope	Fig. 22	2.5	2.1	Test pattern	1700	1500	1500	390	-60	—	—	4.0	2.5	—	500	—	1899
2203	Monotron	Fig. 23	2.5	2.1	Test pattern	—	—	1000	400	-20	-150	—	—	—	5	300	0.1	2203

¹ Refer to Cathode Ray Tube Socket Connections.
² Adjust bias for minimum (most negative) value for satisfactory signal. Maximum resistance in grid circuit should not exceed 1 megohm.

³ Collector current measurements made with mosaic not illuminated.
⁴ Peak-to-peak signal value in μ a.
⁵ In mw. sq. cm. max.

⁶ With full scanning.
⁷ Accelerating electrode (Grid No. 2) voltage same as Anode No. 2 voltage.
⁸ Obsolete.
⁹ Grid No. 2. ¹⁰ Grid No. 3. ¹¹ Grid No. 4.

Radio Operating

THE efficient and successful operation of a radio station is, in itself, an exacting accomplishment. It is a task that requires skill and specialized training. For this reason, by federal regulation as well as by international treaty it is rigidly stipulated that no radio station, amateur or otherwise, may transmit except under the supervision of a licensed operator having qualifications appropriate to the class of station. To acquire such qualifications requires training in the various specialized practices employed.

The basic object of most radio communication is the transmission of intelligence from one point to another, accurately and in as short a time as possible. For efficiency in communication, each class of radio service has set up operating methods and procedure which provide the most expeditious handling of radio traffic. Skilled operators should not only be expert in transmitting and receiving code or voice signals, but also should be thoroughly familiar with the uniform practices observed in the particular class of service concerned. The material following, although generally that of the amateur service, is typical of the basic operating procedure employed in nearly all services with necessary modifications.

☞ Memorizing the Code

Apart from the technical and regulatory phases of the examination, the most important requirement for obtaining an amateur operator's license is ability to send and receive the Continental (International Morse) code at the rate of 13 words per minute. Aside from this consideration, a knowledge of the code is especially desirable during wartime; it is not putting it too strongly to say that everyone should know the code and be able to use it.

The serious student of code — sending, receiving, operating practices, copying on the typewriter, etc. — would be best advised to purchase a copy of the ARRL booklet, *Learning the Radiotelegraph Code* (price, 25 cents, postpaid), and, in fact, anyone desirous of learning the code is advised to do so via the modern and effective method outlined in this booklet. However, the following suggestions will suffice to enable one to acquire the rudiments of code ability.

The first step is to *memorize* the code. This is no task at all if you simply make up your mind to apply yourself to the job and get it over as quickly as possible. The complete Continental alphabet, including the most-used punctuation

marks and numerals, is shown in the table of Fig. 2201. All of the characters shown should be learned, starting with the basic alphabet and then going on to the numerals and punctuation marks. Take a few at a time. As progress is made it is helpful to review at intervals all the letters learned up to that time.

One suggestion: Learn to think of the letters in terms of *sound* rather than their appearance as printed dot-and-dash combinations. This is an important point; in fact, successful mastery of the code can be acquired only if one thinks always in terms of the sound of a letter, right from the start. Think of A as the sound "didah" — not as a printed "dot-dash." The sound "dit" is pronounced as "it" with a "d" before it. The sound "dah" is pronounced with "ah" as in "father." The sound "dah" is always stressed or accented — not in a different tone of voice, but slightly drawn out and the least bit louder. The sound "dit" is pronounced as rapidly and sharply as possible; for purposes of easy combination, as a prefix, it is often shortened to "di." When combinations of the sounds appear as one letter, say them smoothly but rapidly, remembering to make the sound "di" staccato, and allowing equal stress to fall on every dah. There should never be a space or hesitation between dits and dahs of the same letter.

If someone can be found to "send" to you, either by whistling or by means of a buzzer or code oscillator, the best way is to enlist his cooperation and learn the code by listening to it. It is best to have someone do this who is familiar with the code and who can be depended on to send the characters correctly.

Learning the code is like learning a new language, and the sooner you learn to understand the language without the necessity for mental "translation" the easier it will be for you to attain speed and proficiency. You don't think of the spoken letter U, for example, as being composed of two separate and distinct sounds — yet actually it is made up of the pure sounds "ee" and "oo," spoken in rapid succession. You learned the letter U as a sound unit itself. Similarly, you should learn code letters as individual sounds themselves, and not as combinations of other sounds.

Don't think about speed at first; the first requirement is to learn every character to the point where you can recognize each of them without hesitation. Concentrate on any difficult letters until they become as familiar as the rest.

A	● —	didah
B	— ● ● ●	dahdididit
C	— ● ● ● ●	dahdidahdit
D	— ● ● ●	dahdidit
E	●	dit
F	● ● — ●	dididahdit
G	— — ● ●	dahdahdit
H	● ● ● ●	didididit
I	● ●	didit
J	● — — — —	didahdahdah
K	— ● ● —	dahdidah
L	● ● ● ●	didahdidit
M	— — —	dahdah
N	— ●	dahdit
O	— — — —	dahdahdah
P	● — — ● ●	didahdahdit
Q	— — ● ● —	dahdahdidah
R	● ● — ●	didahdit
S	● ● ●	dididit
T	—	dah
U	● ● ● —	dididah
V	● ● ● ● —	didididah
W	● — — —	didahdah
X	— ● ● — —	dahdididah
Y	— ● — — —	dahdidahdah
Z	— — ● ● ●	dahdahdidit

1	● — — — — —	didahdahdahdah
2	● ● — — — —	dididahdahdah
3	● ● ● — — —	didididahdah
4	● ● ● ● — —	dididididah
5	● ● ● ● ●	dididididit
6	— ● ● ● ● ●	dahdidididit
7	— — ● ● ● ●	dahdahdididit
8	— — — ● ● ●	dahdahdahdidit
9	— — — — ● ●	dahdahdahdahdit
0	— — — — — ●	dahdahdahdahdah

Period	● — ● — ● — ● —
Comma	— — — ● — — — —
Question mark	● ● — — ● ● ● ●
Error	● ● ● ● ● ● ● ●
Double dash	— — ● ● ● —
Wait	● — ● ● ● ●
End of message	● — ● — ● — ● —
Invitation to transmit	— — ● ●
End of work	● ● ● — ● ●

Fig. 2201—The Continental (International Morse) Code.

Acquiring Speed by Buzzer Practice

When the code is thoroughly memorized, you can start to develop speed in receiving code transmission. Perhaps the best way to do this is to have two people learn the code together and send to each other by means of a buzzer-and-key outfit. An advantage of this system is that it develops sending ability, too, for the person doing the receiving will be quick to criticize uneven or indistinct sending. If possible it is a good idea to obtain the assistance of an experienced operator for the first few sessions, so that you will learn how well-sent characters should sound.

Either the buzzer set shown in Figs. 2202 and 2203 or one of the audio oscillators described will give satisfactory results as a practice set. The oscillator more closely simulates actual radio signals.

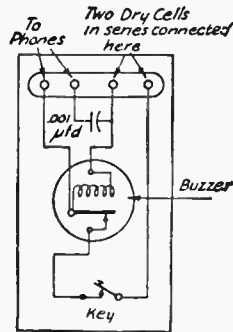


Fig. 2202—Wiring diagram of a buzzer code-practice set. The headphones are connected across the coils of the buzzer, with a condenser in series. The size of this condenser determines the strength of the signal in the 'phones. If the value shown gives an excessively loud signal, it may be reduced to 500 μfd. or even 250 μfd.

The battery-operated audio oscillator in Figs. 2204 and 2205 is easy to construct and gives effective performance. If nothing is heard in the headphones when the key is depressed, reverse the leads going to either transformer winding (do not reverse both windings).

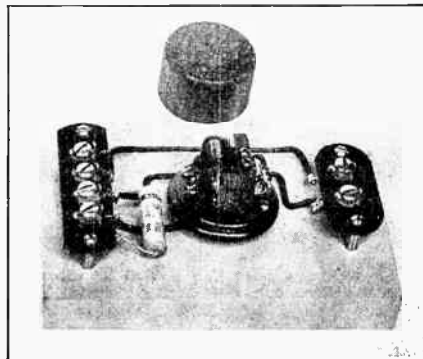


Fig. 2203—The cover of the buzzer unit has been removed in this view of the buzzer code-practice set.

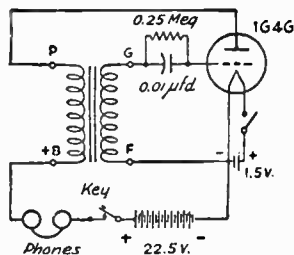


Fig. 2204 — Wiring diagram of a simple vacuum-tube audio-frequency oscillator for use as a code-practice set.

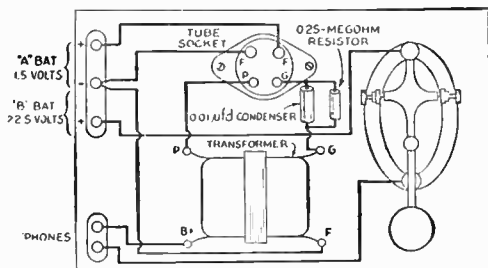


Fig. 2205 — Layout of the audio-oscillator code-practice set. All parts may be mounted on a wooden baseboard, approximately 5 × 7 inches in size.

The a.c.-d.c. oscillator in Fig. 2206 utilizes a combination diode-pentode tube, the pentode section being used as a vacuum-tube oscillator. This set operates directly from the 115-volt a.c. or d.c. power line and must be installed and handled so that electrical shock will be impossible. The set should be enclosed in a protective cabinet or box. If a metal chassis is used, the components *must* be insulated from the chassis.

The headphone circuit is insulated from the power line, as shown in Fig. 2206, but care is required to prevent contact with ground or power line while touching the key.

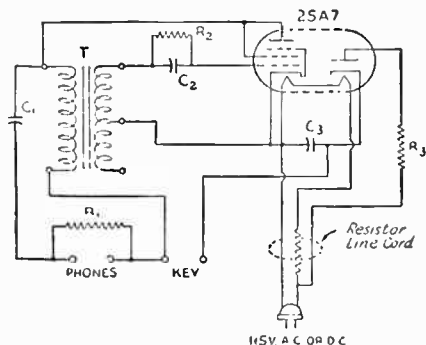


Fig. 2206 — A.c.-d.c. vacuum-tube audio oscillator.

C_1 — 100- μ fd, midget mica.

C_2 — 250- μ fd, midget mica.

C_3 — 8- μ fd, 200-volt electrolytic.

R_1 — 0.5 megohm, $\frac{1}{2}$ -watt. (A lower value, or a variable resistor, may be used to reduce volume.)

R_2 — 1 megohm, $\frac{1}{2}$ -watt.

R_3 — 50 ohms, 1-watt.

T — 3:1-ratio midget push-pull audio transformer.

Line cord resistor — 310 ohms. (A 300-ohm, 50-watt wire-wound fixed resistor may be used instead.)

After the practice set has been built, and another operator's help secured, practice sending turn and turn about to each other. Send single letters at first, the listener learning to recognize each character quickly, without hesitation. Following this, start slow sending of complete words and sentences, always trying to have the material sent at just a little faster rate than you can copy easily; this speeds up your mind. Write down each letter you recognize. Do *not* try to write down the dots and dashes; write down the letters. Don't stop to compare the sounds of different letters, or think too long about a letter or word that has been missed. Go right on to the next one, or each "miss" will cause you to lose several characters you might otherwise have gotten. If you exercise a little patience you will soon be getting every character, and in a surprisingly short time will be receiving at a good rate of speed. When you can receive 13 words a minute (65 letters a minute), have the sender transmit code groups rather than English text. This will prevent you from recognizing a word "on the way" and filling it in before you've really listened to the letters themselves.

After you have acquired a reasonable degree of proficiency, concentrate on the less common characters, as well as the numerals and punctuation marks. These prove the downfall of many applicants taking the code examination under the handicap of nervous stress.

Using a Key

The correct way to grasp the key is important. The knob of the key should be about eighteen inches from the edge of the operating table and about on a line with the operator's right shoulder, allowing room for the elbow to rest on the table. A table about thirty inches in height is best. The spring tension of the key varies with different operators. A fairly heavy spring at the start is desirable. The back adjustment of the key should be changed until there is a vertical movement of about one-sixteenth inch at the knob. After an operator has mastered the use of the hand key the tension should be changed and can be reduced to the minimum spring tension that will cause the key to open immediately when the pressure is released. More spring tension than necessary causes the expenditure of unnecessary energy. The contacts should be spaced by the rear screw on the key only and not by allowing play in the side screws, which are provided merely for aligning the contact points. These side screws should be screwed up to a setting which prevents appreciable side play but not adjusted so tightly that binding is caused. The gap between the contacts should always be at least a thirty-second of an inch, since a too-finely spaced contact will cultivate a nervous style of sending which is highly undesirable. On the other hand too-wide spacing (much over one-sixteenth inch) may result in unduly heavy or "muddy" sending.

Do not hold the key tightly. Let the hand rest lightly on the key. The thumb should be against the left side of the key. The first and second fingers should be bent a little. They should hold the middle and right sides of the knob, respectively. The fingers are partly on top and partly over the side of the knob. The other two fingers should be free of the key. Fig. 2207 shows the correct way to hold a key.

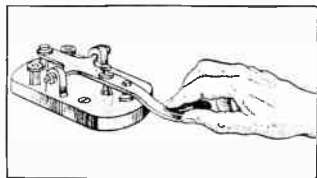


Fig. 2207—This sketch illustrates the correct position of the hand and fingers for good sending with a telegraph key.

A wrist motion should be used in sending. The whole arm should not be used. One should not send "nervously" but with a steady flexing of the wrist. The grasp on the key should be firm, but not tight, or jerky sending will result. None of the muscles should be tense but they should all be under control. The arm should rest lightly on the operating table with the wrist held above the table. An up-and-down motion without any sideways action is best. The fingers should never leave the key knob.

Good sending may seem easier than receiving, but don't be deceived. A beginner should not attempt to send fast. Keep your transmitting speed down to the receiving speed, and bend your efforts to sending well. Do not try to speed things up too soon. A slow, even rate of sending is the mark of a good operator. Speed will come with time alone. Leave special types of keys alone until you have mastered the knack of handling the standard key. Because radio transmissions are seldom free from interference, a "heavier" style of sending is best to develop for radio work. A rugged, heavy key will help in developing this characteristic.

☞ Radiotelegraph Operation

The radiotelegraph code is used for record communication. Aside from his ability to copy at high speeds, a good operator is noted for his neatness and accuracy of copy. It is evident that a radio operator should copy exactly what is sent, and if there is any doubt about a letter or word he should query the transmitting operator about it.

General procedure—(1) Calls should be made by transmitting not more than three times the call signal of the station called, and DE, followed by one's own call signal sent not more than three times, thus: VE2BE VE2BE VE2BE DE W1AW W1AW W1AW. In amateur practice this form is repeated completely once or twice. The call signal of the calling station must be inserted at frequent intervals for identification purposes. Repeating the call signal of the called station five times and sign-

ing not more than twice has proved excellent practice in connection with break-in operation (the receiver being kept tuned to the frequency of the called station). The use of a break-in system is highly recommended to save time and reduce unnecessary interference.

(2) Answering a call: Call three times (or less); send DE; sign three times (or less); and after contact is established decrease the use of the call signals of both stations to once or twice. Example:

W1GNF DE W1AW GE OM GA K (meaning, "Good evening, old man, go ahead").

(3) Ending signals and sign off: The proper use of AR, K and VA ending signals is as follows: AR (end of transmission) shall be used at the end of messages during communication; and also at the end of a call, indicating when so used that communication is not yet established. In the case of CQ calls, the international regulations recommend that K shall follow. K (invitation to transmit) shall also be used at the end of each transmission when answering or working another station, carrying the significance of "go ahead." VA (or SK) shall be used by each station only when signing off, this followed by the call of the station being worked and your own call sent once for identification purposes. Examples:

(AR) — W1KQY DE W1CTI AR (showing that W1CTI has not yet gotten in touch with W1KQY but has called and is now listening for his reply). Used after the signature between messages, it indicates the end of one message. There may be a slight pause before starting the second of the series of messages. The courteous and thoughtful operator allows time for the receiving operator to enter the time on the message and put another blank in readiness for the traffic to come. If K is added, it means that the operator wishes his first message acknowledged before going on with the second message. If no K is heard, preparations should be made to continue copying.

(K) — W1JEQ DE W6AJM R K. (This arrangement is very often used for the acknowledgment of a transmission. When anyone overhears this he knows at once that the two stations are in touch, communicating with each other, that W1JEQ's transmission was all understood by W6AJM, and that W6AJM is telling W1JEQ to go ahead with more of what he has to say.) W9KJY DE W7NH NR 23 R K. (Evidently W9KJY is sending messages to W7NH. The contact is good. The message was all received correctly. W7NH tells W9KJY to "go ahead" with more.)

(VA) — R NM NW CUL VY 73 AR VA W6TI DE W7WY. (W7WY says, "I understand OK, no more now, see you later, very best regards, I am through with you for now and will listen for whomsoever wishes to call. W7WY 'signing off' with W6TI.")

☞ Radiotelephone Operation

Procedure to be used in radiotelephone operation follows the foregoing general principles closely. The operator makes little use of the special abbreviations available for code work, of course, since he may directly speak out their full meaning. Radiotelephony is used principally for command and control purposes, such as communication between ground stations and aircraft, where recorded message traffic is at a minimum. Transmissions consist mostly of short bursts with little variety in

form or content, and each operator must become familiar with procedure methods adopted by the particular service.

FOR RADIOTELEPHONE

A list can be obtained from the local Western Union office and posted beside the telephone to use when telephoning messages containing initials and difficult words. Such code words prevent errors due to phonetic similarity. Also all voice operated stations should use a *standard* list as needed to identify call signals or unfamiliar expressions. A.R.R.L. Official Phone Stations have adopted the following word list:

A — ADAMS	N — NEW YORK
B — BOSTON	O — OCEAN
C — CHICAGO	P — PETER
D — DENVER	Q — QUEEN
E — EDWARD	R — ROBERT
F — FRANK	S — SUGAR
G — GEORGE	T — THOMAS
H — HENRY	U — UNION
I — IDA	V — VICTOR
J — JOHN	W — WILLIAM
K — KING	X — X-RAY
L — LINCOLN	Y — YOUNG
M — MARY	Z — ZERO

Example: W1EH . . . W 1 EDWARD HENRY.

Names of states and countries have been used for identifying letters in amateur radiotelephone work. It is recommended by A.R.R.L. that use of Q code and special abbreviations be minimized in voice work insofar as possible, and the full expression (with conciseness) be substituted.

Unusual words should be avoided in the interest of accuracy if possible when drafting messages. When they unavoidably turn up difficult words may be repeated, or *repeated and spelled*. The operator says "I will repeat" when thus retransmitting a difficult word or expression.

The speed of radiotelephone transmission (with perfect accuracy) depends almost entirely upon the skill of the two operators involved. One must learn to speak at a rate allowing perfect understanding as well as permitting the receiving operator to copy down the message text, if that is necessary. Because of the similarity of many English speech sounds, the use of alphabetical word lists has been found necessary. All voice-operated stations should use a *standard* list as needed to identify call signals or unfamiliar expressions.

Message handling — Each service — commercial, military, amateur — prescribes its own message form, but all are generally similar to the example here given. A message is broadly divided into four parts: (1) the pre-

amble; (2) the address; (3) the text; (4) the signature. The preamble contains the following:

- a) Number (of this message).
- b) Station of origin.
- c) Check (number of words in text).
- d) Place of origin.
- e) Time filed.
- f) Date.

Therefore, it might look like this:

NR 34 WLTK JH 13

CHICAGO ILL 450 PM MAY 12 1942

CAPT WM MONTGOMERY

MUNITIONS BLDG

WASHINGTON DC BT

SIXTH CORPS AREA HAS 68

MEN AVAILABLE FOR ACTIVE DUTY

FIXED SERVICE REGARDS BT

HUNTER WLTK

• R-S-T SYSTEM OF SIGNAL REPORTS

The R-S-T system is an abbreviated method of indicating the main characteristics of a re-

READABILITY

- 1 — Unreadable
- 2 — Barely readable, occasional words distinguishable
- 3 — Readable with considerable difficulty
- 4 — Readable with practically no difficulty
- 5 — Perfectly readable

SIGNAL STRENGTH

- 1 — Faint — signals barely perceptible
- 2 — Very weak signals
- 3 — Weak signals
- 4 — Fair signals
- 5 — Fairly good signals
- 6 — Good signals
- 7 — Moderately strong signals
- 8 — Strong signals
- 9 — Extremely strong signals

TONE

- 1 — Extremely rough hissing note
- 2 — Very rough a.c. note, no trace of musicality
- 3 — Rough, low-pitched a.c. note, slightly musical
- 4 — Rather rough a.c. note, moderately musical
- 5 — Musically modulated note
- 6 — Modulated note, slight trace of whistle
- 7 — Near d.c. note, smooth ripple
- 8 — Good d.c. note, just a trace of ripple
- 9 — Purest d.c. note

(If the note appears to be crystal controlled simply add an X after the appropriate number.)

ceived signal, the Readability, Signal Strength, and Tone. The letters R-S-T determine the order of sending the report. In asking for this form of report, one transmits RST? or simply QRK?

Such a signal report as "RST 387X" (abbreviated to 387X) will be interpreted as "Your signals are readable with considerable difficulty; good signals (strength); near d.c. note, smooth ripple; crystal characteristic noticed." Unless it is desired to comment in regard to a crystal characteristic of the signal, a single three-numerical group will constitute a complete report on an amateur signal. The R-S-T system is the standard ARRL method of reporting. Various report combinations are based on the table.

This is obviously the 34th message (of that day or that month, as the policy of the station prescribes) from station WLTN. The "JH 13" is the "sine" of the operator plus the number of words in the message text. All operators designate themselves with a personal sine to be used on message traffic and on the air; in most cases it consists of the operator's initials. The signal BT (double-dash) is used to separate the text from address and signature.

Several radiograms may be transmitted in series (QSG. . . .) with the consent of the station which is to receive them. As a general rule long radiograms should be transmitted in sections of approximately fifty words, each ending with . . . — — . . . (?), meaning, "Have you received the message correctly thus far?"

If the first part of a message is received but substantially all of the latter portions lost, the request for the missing parts is simply RPT TXT AND SIG, meaning, "Repeat text and signature." PBL and ADR may be used similarly for the preamble and address of a message. RPT ALL or RPT MSG should not be sent unless nearly all of the message is lost. When a few word-groups in conversation or message handling have been missed, a selection of one or more of the following abbreviations are used to ask for a repeat on the parts in doubt.

Abbreviation	Meaning
?AA	Repeat all after
?AB	Repeat all before
?AL	Repeat all that has been sent
?BN . . . AND	Repeat all between . . . and . . .
?WA	Repeat the word after
?WB	Repeat the word before

The good operator will ask only for what fills are needed, separating different requests for repetition by using the break sign or double dash (— . . . —) between these parts. There is seldom any excuse for repeating a whole message just to get a few lost words.

Another interrogation method is sometimes used, the question signal (. . . — — . . .) being sent between the last word received correctly and the first word (or first few words) received after the interruption.

As an example of what procedure would be followed in the transmission of a commercial message, let us assume that a passenger aboard the S.S. *Coastwise* wishes to notify a friend of his arrival. Station WKCZ aboard the ship would call a shore station (WSC) and the following would ensue:

WSC WSC WSC DE WKCZ WKCZ WKCZ P AR K

WKCZ WKCZ WKCZ DE WSC ANS 700 K

WSC WSC WSC DE WKCZ P 1 CK12 SS COASTWISE 0827 MAY 10 BT MISS JANET SHANNON 18 LAMBERT STREET BOSTON BT ARRIVE PIER 18 TONIGHT LOVE BT JOHN AR K

WKCZ DE WSC R 1 K

WSC DE WKCZ QRU SK

WKCZ DE WSC R SK

If the receiving operator missed the number of the pier of arrival, he would send:

PIER ?? TONIGHT OR ?WA PIER.

whereupon the transmitting operator would say:

PIER 18 TONIGHT

and then would stand by for an acknowledgment of receipt (R).

The service message — When one station has a message to transmit to another concerning the handling of a previous message, the message is titled a "service" and is indicated by "SVC" in the preamble when sent. Such a message may refer to non-delivery, delayed transmission, errors, or to any phase of message handling activity. Words may be abbreviated in the text of the service message to conserve time. Do not abbreviate to the point where misunderstanding may arise.

Provisions in the Communications Act of 1934 make it a misdemeanor to give out information of any sort to any person except the addressee of a message or his authorized agent. When for some reason a message cannot be delivered, a service message should be sent to the station of origin containing information to that effect.

Land-line check — The land-line or "text" count, consisting of count only of the words in the body or text of the message, is probably now most widely used. (The "cable" count covers all words in the address and signature, as well, probably accounting for its unpopularity.) When in the case of a few exceptions to the basic rule in land-line checking, certain words in the address, signature or preamble are counted, they are known as extra words and all such are so designated in the check right after the total number of words.

The check includes:

- 1) All words, figures and letters in the body, and
- 2) the following extra words:
 - (a) Signature except the first, when there

are more than one (a title with signature does not count extra, but an address following a signature does).

(b) Words "report delivery," or "rush" in the check.

(c) Alternate names and/or street addresses, and such extras as "personal" or "attention."

Dictionary words in most languages count as one word irrespective of length of the word. In counting figures, a group of five digits or less counts as one word. Bars of division and decimal points may constitute one or more of the digits in such a group. It is recommended that, where feasible, words be substituted for figures to reduce the possibility of error in transmission. Detailed examples of word counting are about as difficult in one system of count as another.

Net Operation

In field work many military communications units operate in "net" fashion, wherein one station (at the headquarters of the unit) is designated as net-control station (NCS) to direct the business of the net. The operation of all stations in the same net is on one single frequency, so that any one operator may hear any other station(s) without retuning his receiver. "Break-in" is advantageously employed here — the receiver is kept running during transmissions, so that nearly simultaneous two-way communication is possible.

Briefly, the procedure in net operation is as follows: The NCS calls the net together at a pre-announced time and using a predetermined call. Immediately, station members of the net reply in alphabetical (or some other predetermined) order, reporting on the NCS's signal strength and stating what traffic is on hand and for whom. The NCS acknowledges, meanwhile keeping an account of all traffic on hand, by stations. He then directs the transfer of messages from one station to another, giving preference to any urgent traffic so indicated at roll call. When all traffic has been distributed and it is apparent there is no further business, the NCS will close the net, in most cases maintaining watch on the net frequency for any special traffic which might appear.

Keeping a Log

FCC regulations require nearly every radio-communication station to keep a complete operating record or "log," including such data as times and dates of transmissions, stations

contacted, message traffic handled, input power to the transmitter, frequency used, and signature or "sine" of the operator in charge.

Log-keeping procedure differs with each class of communications service. A typical page from an amateur radio station log, prepared on the standard ARRL form, is shown below and is illustrative of the form and data required.

AMATEUR RADIO STATION LOG									
Date of this log: 100		Frequency: 3705 AC		Approximate location:		Remarks (Use check marks or initials)			
TIME	STATION CONTACTED	MODE	CLASS OF SERVICE	POWER USED	FREQUENCY USED	REMARKS (Use check marks or initials)	REMARKS (Use check marks or initials)	REMARKS (Use check marks or initials)	REMARKS (Use check marks or initials)
5:45 PM	W6T M	X	X	5.5 W	5.517	6:05 PM	None again!		
6:00	W6SEP	X	X	5.5 W			No. air.		
6:10	W6RHH	X	X	5.5 W			Hi! How three that you check!		
6:57	W6F M	X	X	5.5 W	5.517		Business, C. G.		
7:20	C. G.								
7:22	W6BPP	X	X	3.4 W	5.517	7:55	In early for 8:00 signature		
7:55	W6BPP	X	X						
7:57 AM	W6AFD	X	X				Start		
7:58	W6GGO	X	X				Check about 10:00		
8:07	C. G.								
8:21	W6F M	X	X	5.5 W	5.517	8:58	W6BPP at his home		
8:40	C. G.						Swirl! Swirl!		
6:10 PM	C. G.								
6:15	W6F M	X	X	5.5 W			6:25 PM found time to		
6:32	W6RHH	X	X				at 7:00		
7:00	W6T M	X	X						

Time Systems

While most continental-commercial telegraph and radio circuits use local standard (or war) time in log-keeping and message-handling, international radiocommunication stations and the military services now use a 24-hour system of time-keeping. One is Greenwich Civil Time, a 24-hour clock system used in international radiocommunication work. All figures are based on the time in Greenwich, England, the city of 0° meridian fame. 0000 represents midnight in Greenwich; 0600 represents 6 A.M. there; 1200 is noon; 1800 is 6 P.M.; 2400 is again midnight and the same as 0000 of the following day. The figures must be corrected to each individual time zone. The Central War Time zone is five hours behind Greenwich, so that 0630 GCT (6:30 A.M. in Greenwich) would represent 1:30 A.M. CWT, for example. As an example of reverse translation, 9:30 A.M. CWT would be designated in the log as 1430 GCT. EWT is four hours behind GCT; MWT, six hours; PWT, seven.

At present the military services use simply a 24-hour clock, based on local time, without correcting to Greenwich or any other longitude. Then 6 A.M. CWT becomes 0600; 6 A.M. EWT is 0600, and so on. The principal advantage of this system is an elimination of the necessity for the use of P.M. or A.M. abbreviations.

"Q CODE"

IN THE REGULATIONS accompanying the existing International Radiotelegraph Convention, there is a very useful internationally agreed code designed to meet the major needs in international radio communication. This code

is given in the following table. The abbreviations themselves have the meanings shown in the "answer" column. When an abbreviation is followed by an interrogation mark (?), it assumes the meaning shown in the "question" column.

Abbreviation	Question	Answer
ORA	What is the name of your station?	The name of my station is
ORB	How far approximately are you from my station?	The approximate distance between our stations is nautical miles (or kilometers).
QRC	What company (or Government Administration) settles the accounts for your station?	The accounts for my station are settled by the company (or by the Government Administration of).
QRD	Where are you bound and where are you from?	I am bound for from
QRC	Will you tell me my exact frequency (wave-length) in ke/s (or m)?	Your exact frequency (wave-length) is ke/s (or m).
QRU	Does my frequency (wave-length) vary?	Your frequency (wave-length) varies.
QRV	Is my note good?	Your note varies.
QRJ	Do you receive me badly? Are my signals weak?	I cannot receive you. Your signals are too weak.
QRK	What is the legibility of my signals (1 to 5)?	The legibility of your signals is (1 to 5).
QRL	Are you busy?	I am busy (or I am busy with). Please do not interfere.
QRM	Are you being interfered with?	I am being interfered with.
QRN	Are you troubled by atmospherics?	I am troubled by atmospherics.
QRO	Shall I increase power?	Increase power.
QRP	Shall I decrease power?	Decrease power.
QRO	Shall I send faster?	Send faster (..... words per minute).
QRS	Shall I send more slowly?	Send more slowly (..... words per minute).
QRT	Shall I stop sending?	Stop sending.
QRU	Have you anything for me?	I have nothing for you.
QRV	Are you ready?	I am ready.
QRW	Shall I tell that you are calling him on ke/s (or m)?	Please tell that I am calling him on ke/s (or m).
QRX	Shall I wait? When will you call me again?	Wait (or wait until I have finished communicating with). I will call you at o'clock (or immediately).
QRY	What is my turn?	Your turn is No. (or according to any other method of arranging it).
QRZ	Who is calling me?	You are being called by
QSA	What is the strength of my signals (1 to 5)?	The strength of your signals is (1 to 5).
QSB	Does the strength of my signals vary?	The strength of your signals varies.
QSD	Is my keying correct; are my signals distinct?	Your keying is incorrect; your signals are bad.
QSC	Shall I send telegrams (or one telegram) at a time?	Send telegrams (or one telegram) at a time.
QSJ	What is the charge per word for including your internal telegraph charge?	The charge per word for is francs, including my internal telegraph charge.
QSK	Shall I continue with the transmission of all my traffic? I can hear you through my signals.	Continue with the transmission of all your traffic, I will interrupt you if necessary.
QSL	Can you give me acknowledgment of receipt?	I give you acknowledgment of receipt.
QSM	Shall I repeat the last telegram I sent you?	Repeat the last telegram you have sent me.
QSO	Can you communicate with direct (or through the medium of)?	I can communicate with direct (or through the medium of).
QSP	Will you retransmit to free of charge?	I will retransmit to free of charge.
QSR	Has the distress call received from been cleared?	The distress call received from has been cleared by
QSU	Shall I send (or reply) on ke/s (or m) and/or on waves of Type A1, A2, A3, or B?	Send (or reply) on ke/s (or m) and/or on waves of Type A1, A2, A3, or B.
QSV	Shall I send a series of VVV	Send a series of VVV
QSW	Will you send on ke/s (or m) and/or on waves of Type A1, A2, A3, or B?	I am going to send (or I will send) on ke/s (or m) and/or on waves of Type A1, A2, A3, or B.
QSX	Will you listen for (call sign) on ke/s (or m)?	I am listening for (call sign) on ke/s (or m).
QSY	Shall I change to transmission on ke/s (or m) without changing the type of wave? or Shall I change to transmission on another wave?	Change to transmission on ke/s (or m) without changing the type of wave or Change to transmission on another wave.
QSZ	Shall I send each word or group twice?	Send each word or group twice.
QTA	Shall I cancel telegram No. as if it had not been sent?	Cancel telegram No. as if it had not been sent.
QTB	Do you agree with my number of words?	I do not agree with your number of words; I will repeat the first letter of each word and the first figure of each number.
QTC	How many telegrams have you to send?	I have telegrams for you (or for).

Abbreviation	Question	Answer
QTE	What is my true bearing in relation to you? or What is my true bearing in relation to (call sign)? What is the true bearing of (call sign) in relation to (call sign)?	Your true bearing in relation to me is degrees or Your true bearing in relation to (call sign) is degrees at (time) or The true bearing of (call sign) in relation to (call sign) is degrees at (time).
QTF	Will you give me the position of my station according to the bearings taken by the direction-finding stations which you control?	The position of your station according to the bearings taken by the direction-finding stations which I control is latitude longitude.
QTG	Will you send your call sign for fifty seconds followed by a dash of ten seconds on kc/s (or m) in order that I may take your bearing?	I will send my call sign for fifty seconds followed by a dash of ten seconds on kc/s (or m) in order that you may take my bearing.
QTH	What is your position in latitude and longitude (or by any other way of showing it)?	My position is latitude longitude (or by any other way of showing it).
QTI	What is your true course?	My true course is degrees.
QTJ	What is your speed?	My speed is knots (or kilometers) per hour.
QTM	Send radioelectric signals and submarine sound signals to enable me to fix my bearing and my distance.	I will send radioelectric signals and submarine sound signals to enable you to fix your bearing and your distance.
QTO	Have you left dock (or port)?	I have just left dock (or port).
QTP	Are you going to enter dock (or port)?	I am going to enter dock (or port).
QTQ	Can you communicate with my station by means of the International Code of Signals?	I am going to communicate with your station by means of the International Code of Signals.
QTR	What is the exact time?	The exact time is
QTU	What are the hours during which your station is open?	My station is open from to
QUA	Have you news of (call sign of the mobile station)?	Here is news of (call sign of the mobile station).
QUB	Can you give me in this order, information concerning: visibility, height of clouds, ground wind for (place of observation)?	Here is the information requested
QUC	What is the last message received by you from (call sign of the mobile station)?	The last message received by me from (call sign of the mobile station) is
QUD	Have you received the urgency signal sent by (call sign of the mobile station)?	I have received the urgency signal sent by (call sign of the mobile station) at (time).
QUF	Have you received the distress signal sent by (call sign of the mobile station)?	I have received the distress signal sent by (call sign of the mobile station) at (time).
QUG	Are you being forced to alight in the sea (or to land)?	I am forced to alight (or land) at (place).
QUH	Will you indicate the present barometric pressure at sea level?	The present barometric pressure at sea level is (units).
QUJ	Will you indicate the true course for me to follow, with no wind, to make for you?	The true course for you to follow, with no wind, to make for me is degrees at (time).
QUK	Can you tell me the condition of the sea observed at (place or coördinates)?	The sea at (place or coördinates) is
QUL	Can you tell me the swell observed at (place or coördinates)?	The swell at (place or coördinates) is
QUM	Is the distress traffic ended?	The distress traffic is ended.

Special abbreviations adopted by the ARRL:

- QST** General call preceding a message addressed to all amateurs and ARRL Members. This is in effect "CQ ARRL."
- QRR** Official ARRL "land SOS." A distress call for use by stations in emergency zones only.

Scales Used in Expressing Signal Strength and Readability

(See QRK and QSA in the Q Code)

Strength	Readability
QSA1 Barely perceptible.	QRK1 Unreadable.
QSA2 Weak.	QRK2 Readable now and then.
QSA3 Fairly good.	QRK3 Readable with difficulty.
QSA4 Good.	QRK4 Readable.
QSA5 Very good.	QRK5 Perfectly readable.

Index

	PAGE
"A" Battery	40
A.C.	30-37
A.C.-D.C. Converters	187
A.C.-D.C. Power Supplies	183
A.C. Generators	30
A.C. Instruments	36
A.C. Spectrum	33
AT-Cut Crystals	58
Abbreviations, Radio and Electrical	413
Abbreviations, Radiotelegraph	463-468
Absorption	189
Absorption Frequency Meters	400-402
Absorption Modulation	120-121
Acorn Tubes	90, 153
Adjacent-Channel Selectivity	143
Air-Core Transformers	37
Air-Gap Crystal Holder	96
Air Masses	191-192
Alignment, Receiver	169-172, 174
Alternating Current	30-37
Alternating Current, Ohm's Law for	33-36
Alternating Current Spectrum	33
Alternator	30
Amateur Bands	12
Amateur Operator and Station Licenses	12
Amateur Radio	9-12
Amateur Regulations	12
American Radio Relay League:	
Foundation	11
Headquarters	12
Hiram Percy Maxim Memorial	12
Joining the League	12
Ammeters	29-30, 36-37
Ampere	17
Ampere-Hour Capacity	20
Ampere Turns	22
Amplification	142
Amplification Factor	61
Amplification, Vacuum-Tube	61, 63-74
Amplifier Classifications	71-72
Amplifiers (see basic classification, e.g., "Receivers," "Transmitters" and "Radiotelephony")	
Amplitude	30
Amplitude-Modulated Signal Generators	410
Amplitude Modulation	117-119
Anchor, Guy Wire	377-378
Angle, Amplifier Operating	104, 112
Angle of Radiation	191, 194-196
Angular Velocity	31
Anode	18
Antenna Systems:	
Alford Loop Antenna	223
Angle of Radiation	191, 194-196
Bazooka Line Balancer	224
Beam Antennas	214-216
Bent Antennas	214
Billboard Array	225
Broad-Band Antennas	224-225
Broadside Arrays	216-218
Capacity Ground	222
Capacity-Loaded Antenna	223
Coaxial Vertical Radiator	223-224
Collinear Arrays	216-218
Combination Arrays	222
Compact Antennas	213-214
Conductor Size	195
Cone Antennas	225
Construction	375-384
Corner Reflector Antennas	226
Counterpoise	222-223
Coupling to Receiver	146
Coupling to Transmitter	199-202
Current Distribution	194-209
Cylindrical Antennas	224
Directive Antennas	214-222
Directivity	194
Director	216
Doublet	194
Driven Elements	216-219
Dummy Antennas	109
Emergency	392-394
End-Effect	194
End-Fire Arrays	216-218
Extended Double Zepp	219

	PAGE
Feed Systems:	
Balance to Ground	198
Characteristic Impedance	50, 199
Coaxial Lines	198, 206
Concentric Lines	195, 206
Current Feed	197-198
Delta Matching Transformer	206-207
Direct Excitation	197
Feeder Connections	381
Harmonic Resonance	49
Impedance	50
Impedance Transformer	51-52
Length	199, 203-204, 219
Linear Transformers	207-209
Losses	198-199
Non-Resonant Lines	199, 204-209
Open-Wire Line	198, 202
"Q" Section	207
Reactance	51
Resistance	51
Resonant Lines	199, 202-204
Single-Wire Feed	198, 205
Standing-Wave Ratio	50-51
Stub Matching	206-208
Tuned Transmission Lines	202-204
Twisted-Pair Line	198, 206
Untuned Transmission Lines	199, 204-209
Voltage Feed	198
Folded-Dipole Antennas	225
Folded Doublet	225
Free-Space Pattern	195
Ground Connection	222
Ground Effect	195-199
Ground-Plane Antenna	224
Grounded Antennas	222-223
Guys	378
Half-Wave	194-195
Halyards	378
Hertz Antenna	194
Horn Radiators	226
Impedance	194, 195, 196, 210
Inductance-Loaded Antenna	223
Installation	375-384
"J" Antenna	223, 393
Lazy-H Antenna	218
Length	194, 207, 220, 222
Lightning Protection	384
Loaded Antennas	223
Long-Wire Antennas	209-211, 214-216
Loop Antennas	224-224
Mareoni (Grounded) Antennas	222-223
Masts	375-377
Measurements	411-412
Mobile	382, 393
Multi-Band Antennas	211-214
Parabolic Reflectors	225-226
Parasitic Elements	220-222
Patterns, Radiation	197, 211
Phased Arrays	216-219
Plane Reflector Antennas	225-226
Plane Sheet Reflectors	225
Polarization	188, 194, 196
Power Gain	194, 210
Pulleys	378
Radiation Characteristics	195
Radiation Resistance	49
Receiving	226
Reflection, Ground	195
Reflector	220
Resonant-Loop Antennas	223
Restricted Space	213-214
Rhombic or Diamond Antennas	215-216
Rotary-Beam Antennas	220-223, 379
Sleeves, Line Matching	224
Standing Waves	48-49
Switching	384
Tilt Angle	215
Top-Loaded Antennas	223
Transmission Lines	199-209, 379
Tuners, Construction of:	
Low-Power Rack-Mounted Antenna Tuner	264
Medium-Power Antenna Tuner	271
Pi-Section Antenna Coupler	274
Wide-Range Antenna Coupler	280
Turnstile Antenna	224

	PAGE		PAGE
"V" Antennas	214	Catcher	92
Very-High Frequency (see "Very-High Frequencies")		Cathode	18, 60, 73-74
Voltage Distribution	194-195, 209-210	Cathode Bias Calculation	73-74
Wide-Band Antennas	224-225	Cathode By-Pass	73
Zepp Antenna	202	Cathode Circuits	74
Anti-Nodes	49	Cathode Coupler	78
Are-Back	176	Cathode Follower	78
Arms, Bridge-Circuit	48	Cathode Keying	139
Arrays, Antenna	214-222	Cathode Modulation	119, 122-123
Atoms	15	Cathode-Ray Oscilloscopes	85-86, 130-132, 427-428
Atmospheric Bending	188	Cathode-Ray Tubes	85-86
Atmospheric Refraction	188	Cathode Resistor	73
Attraction	14, 21	Cavity Resonators	55-56
Audio Frequencies	33	Cell	18-19
Audio-Frequency Amplifiers	142, 149-151	Cement, Coil	235
Audio-Frequency Measurement	407-410	Center-Tap, Filament	73
Audio Image	161	Center-Tap Full-Wave Rectifier	176
Audio Limiting	129, 166	Center-Tap Keying	139
Audio Oscillators	462	Center-Tap Modulation	122-123
Aurora Skip	199	Channel	118
Autodyne Reception	112	Characteristic Curves	60
Automatic Volume Control	163-164	Characteristic Impedance	59-51, 199
Autotransformer	41	Characteristics of Vacuum Tubes (Tables)	419-459
Average Current Value	31	Charges, Electrical	14
Axes, Cathode-Ray Tube	85	Charging Batteries	20
"B" Battery	60	Charts and Tables:	
Back-Wave	137	Abbreviations, Radiotelegraph	465
Baffle Shield	46	Amateur Frequency Bands	12
Balanced Transmission Line	198	Antenna and Feeder Lengths	205, 212, 214, 215, 226
Band Changing	153	Antenna Gain	217, 220
Band-Pass Filters	46-47	Band-Width, Typical I.F.	161
Bandspread	153	Battery Service Hours	387
Band-Switching	153	Cathode-Modulation Performance Curves	123
Band-Width	160	Characteristic Impedance	199
Batteries	18-21, 186-187, 385	Coil-Winding Data	107
Battery Service Hours (Table)	387	Color Code for Radio Parts	414
Bazooka Balances	224	Condenser Color Code	414
Beam Antennas (see "Antenna Systems")		Conductivity of Metals	416
Beam Tubes	77	Continental Code	461
Beat Frequencies	59	Copper Wire Table	418
Beat-Frequency Signal Generators	410	Dielectric Constants	417
Beat Note	142	Drill Sizes	231
Beat Oscillator	155, 163	Dynamotors (Types and Data)	388
Bent Antennas	214	Gain of Directive Antennas	217, 220
Bias	62, 76, 77, 79, 105, 121-122, 124	Gas-Driven Generators (Types and Data)	389
Bias Calculation	76, 105	Inductance, Capacity and Frequency Charts	415-416
Bias Modulation	121-122	Inductance-Design Charts for V.H.F. Coils	416
Bias Supplies	181-182, 203	Line-of-Sight V.H.F. Range	193
Biological Hours	225	Message Form	464
Billboard Array	227	Modulator Data	313-314
Birdies	155, 171, 172	Phonetic Code	464
Blesser	177	Q Code	467-468
Blocked-Grid Keying	139	R-S-T System	464
Blocked-Grid Limiter	88	Radiation Angles	196
Blocking	148	Radiation Patterns	199, 211
Blocking Oscillator	87	Radiation Resistance	196, 210
Body Capacity	101, 146-147	Reactance Chart	416
Brake-Field Oscillators	92	Reactance Table	416
Break-In	138	Receiving-Tube Classification Chart	419
Bridge Circuits	48	Resistor Color Code	414
Bridge Rectifiers	176	Rhombic Antenna Design	215, 216
Broad-Band Amplifier	71	Schematic Symbols	Frontispiece
Broad-Band Antennas	224-225	Signal Strength and Readability Scales	464
Broadside Arrays	216, 217-218	Surge Impedance	199, 212
Buffer Amplifier	94	Tank Circuit Capacity	231
Buffer Condenser	185	Tap Sizes	231
Buncher	91	Tools	237
Bus Wire	232	Transmission Lines, Signaling	199
Butterfly Circuits	57	Transmission Lines as Reactive Circuit Elements	51
Button, Microphone	125-126	Transmission Lines as Resonant Circuit Elements	52
Buzzer Code-Practice Set	461	V-Antenna Design Chart	215
By-Pass Condensers	59, 151	Vacuum-Tube Characteristics	419-459
C	16	Vacuum-Tube Classification Chart, Receiving	419
C/I Ratios	38, 43, 106	Vacuum-Tube Index	419-459
CR and CL Time Constants	29	Vacuum-Tube Socket Diagrams	420-425
CT-Cut Crystals	58	Vibrator Power Supplies (Types and Data)	388
C, W, Reception	142, 147, 167-168	Wire Table	418
Canadian General Manager	11	Word Lists for Accurate Transmission	464
Capacitive Coupling	44, 100	Chassis Layout	230
Capacitive Reactance	34	Chirp, Keying	140
Capacity	15-16	Choke Coil	59
Capacity Coupling	44, 100	Choke-Coupled Modulator	120
Capacity, Distributed	36	Choke, Filter	177, 178-179
Capacity Feed-Back	80	Choke-Input Filter	177, 178-179
Capacity, Grid-Cathode	63	Choke, Swinging	179
Capacity, Grid-Plate	63	Circuit-Diagram Schematic Symbols	Frontispiece
Capacity Ground	222	Circuit, Electric	13-14
Capacity, Inductance and Frequency Charts	415	Circuits, Bridge	48, 417, 424-425
Capacity, Inter-electrode	63	Circuits, Butterfly	57
Capacity-Loaded Antenna	223	Circuits, Cathode	74
Capacity, Plate-Cathode	63	Circuits, Coaxial-Line	49-50, 115-116, 198, 206
Capacity-Resistance Time Constant	29	Circuits, Colpitts	80
Carbon Microphone	125-126	Circuits, Coupled	43-48
Carrier	94, 127	Circuits, Hartley	80
Cascade Amplifiers	65	Circuits, High-Q	113
		Circuits, Lag	140
		Circuits, Linear	48-53, 113-114
		Circuits, Pot Tank	57

	PAGE
Circuits, Lumped-Constant.....	57
Circuits, Parallel-Resonant.....	42
Circuits, Power-Amplifier.....	70
Circuits, Radio-Frequency Power Amplifier.....	100-104
Circuits, Receiver (see "Receivers")	
Circuits, Resonant.....	40-43, 45
Circuits, Resonant Line.....	49, 52-53
Circuits, Resonator.....	57
Circuits, Series.....	28-29, 40
Circuits, Sweep.....	86-87
Circuits, Transmitter (see "Transmitters")	
Circuits, Tuned.....	40-43, 45
Circuits, Ultrasonic.....	80
Circuits, Voltage-Multiplying.....	183
Class-A, -AB, -B, and -C Amplifiers.....	71-72
Class-B Modulators.....	124-125
Class-B Modulator Data.....	313-314
Checks, Keying.....	137, 139-140
Closed Circuit.....	14
Cloud-Layer Inversion.....	192
Coaxial-Line Circuits.....	49, 50, 115-116, 206
Coaxial-Transmission Lines.....	52, 206
Coaxial Vertical Radiators.....	223-224
Code (Continental) and Code Practice.....	460-463
Code Practice Sets.....	460-463
Code, "Q".....	467-468
Coefficient of Coupling.....	44
Coefficient, Temperature.....	58
Coil (see "Inductance")	
Coil Cement.....	233
Coil, Field.....	151
Coil, Voice.....	150
Coils, Winding.....	233
Collector Electrode.....	91
Collinear Arrays.....	216, 217-218
Color Codes, RMA.....	414
Colpitts Circuit.....	80
Combined A.C. and D.C.....	59
Combined Phonetic Alphabet.....	464
Combination Arrays.....	232
Communications Department, ARRL.....	11, 460-468
Compact Antennas.....	213-214
Compensation, High-Frequency.....	78
Compensation, Low-Frequency.....	78
Complex Waves.....	59
Concentric-Line Circuits (see Coaxial-Line Circuits)	
Concentric Transmission Line (see Coaxial-Transmission Lines)	
Condenser.....	16
Condenser, Band-Setting.....	153
Condenser Color Code.....	414
Condenser Coupling.....	44
Condenser-Input Filter.....	177-178
Condenser Microphones.....	126
Condenser Series and Parallel Connections.....	28, 29
Condenser Reactance.....	34
Condensers, Bandspread.....	153
Condensers, Buffer.....	185
Condensers, By-Pass.....	59
Condensers, Electrolytic.....	177
Condensers, Neutralizing.....	103
Condensers, Voltage Rating.....	107, 177
Conductance.....	26
Conduction.....	13, 15-18
Conduction, Electrolytic.....	17-18
Conduction, Gaseous.....	17
Conduction, Thermionic.....	18
Conductivity.....	13, 26
Conductivity of Metals.....	416
Conductors.....	13
Conical Horn.....	226
Conical Antennas.....	225
Constant, Time.....	29, 164
Constants, I.C.....	43
Construction Practice.....	227-233
Continental Code.....	461
Control Circuits, Station.....	303-304
Control Grid.....	60
Controlled-Rectifier Keying.....	138
Conversion Efficiency.....	156
Converters, A.C.-D.C.....	187
Converters, Frequency.....	155, 156-158
Converters, V.I.F.....	157, 329-332
Copper Wire Table.....	418
Core.....	25, 37
Corner Reflector Antenna.....	226, 383
Coulomb.....	13
Counterpoise.....	222-223
Counting Messages.....	463
Coupled Circuits.....	43-48
Coupling.....	25
Coupling, Antenna to Receiver.....	146
Coupling, Antenna to Transmitter.....	199-202
Coupling, Choke.....	120
Coupling Condenser.....	14, 100
Coupling, Critical.....	46
Coupling, Inductive.....	44-45
Coupling, Interstage.....	99-100

	PAGE
Coupling, Link.....	44, 100, 203
Coupling to Transmission Lines.....	199-202
Coupling Transformer.....	119, 128
Crackle Finish.....	230
Critical Angle.....	191
Critical Coupling.....	46
Critical Frequency.....	189
Critical Inductance.....	178
Crystals, Piezoelectric.....	57-58
Crystal-Controlled Transmitter Construction (see "Transmitters" and "Very-High Frequencies")	
Crystal, Failure to Oscillate.....	58
Crystal Filters.....	162, 168
Crystal Headphones.....	150
Crystal Microphones.....	126
Crystal Mountings.....	96
Crystal Oscillators.....	81, 97-99
Current, Alternating.....	30-37
Current, Direct.....	25
Current Feed for Antennas.....	197-198
Current Flow.....	13, 16-21
Current in A.C. Circuits.....	30
Current-Intensity Modulation.....	91
Current Lag and Lead.....	30-37
Current Measurement.....	29-30, 36, 405-407
Curve Tracing Oscilloscope.....	407
Curves, Tube Characteristics.....	60-65
Cutting Sheet Metal.....	230
Cutting Threads.....	232
Cut-Off Frequency.....	46
Cut-Off Limiter.....	89
Cut-Off, Plate Current.....	63
Cycle.....	30
Cyclic Variations.....	190
Cylindrical Antennas.....	224
Cylindrical Grid.....	91
D.C.....	25
D.C. Instruments.....	29, 405-407
D'Arsonval Crystals.....	58
D'Arsonval Movement.....	29
Damping.....	42
Dead Spots.....	147-148
Decibel.....	71
Decoupling.....	128
Decoupling Circuit.....	77
Decrement.....	42
Deflection Plates.....	84
Deflection Sensitivity.....	84
Degeneration.....	69
Degenerative Oscillator.....	81
Delayed A.V.C.....	164
Delivering Messages.....	463
Delta Matching Transformer.....	206-207
Demodulation.....	142
Depolarizer.....	19
Detection.....	142, 143-149
Deviation Ratio.....	134
Diagrams, Schematic Symbols for.....	<i>Frontispiece</i>
Diamond Antenna.....	215
Dielectric.....	13
Dielectric Constant.....	16
Dielectric Constants (Table).....	417
Dies.....	232
Difference of Potential.....	15
Differentiating Circuits.....	88-89
Diffraction.....	188, 190
Diode Detectors.....	143-144
Diode Voltmeters.....	422-423
Diodes.....	60
Dipole, Folded.....	225
Direct Coupling.....	44
Direct Current.....	25
Direct Feed for Antennas.....	197
Direct-Ray Transmission.....	188, 192
Direction of Current Flow.....	18
Directional Antennas (see "Antenna Systems")	
Directive Antennas.....	214-222
Directivity, Antenna.....	194
Director, Antenna.....	216
Directors, ARRL.....	11
Disassociation.....	18
Discriminator.....	173-174
Dissipation, Plate.....	63
Dissipation, Power.....	32-33
Distortion.....	64-65
Distributed Capacity and Inductance.....	36
Dividers, Voltage.....	28, 183
Divisions, ARRL.....	11
Door Knob Tube.....	90
Double-Lead Tubes.....	90
Doublet, Frequency.....	94
Double Resonance.....	110
Double Superheterodyne.....	156
Doublet Antenna.....	196
Downward Modulation.....	133
Drift, Frequency.....	58, 79
Drift Space.....	92

	PAGE
Drill Sizes (Table).....	231
Drilling Holes.....	230
Driven Elements.....	216-219
Driver.....	99, 121
Driver Coupling.....	124
Driver Power.....	70, 105, 121, 124
Drop Voltage.....	28, 42, 175
Dry Batteries.....	186, 385
Dry Cell.....	19
Dummy Antennas.....	109
Duplex-Diode Triodes and Pentodes.....	79
Duplex Power Supplies.....	184
Dynamic Characteristics.....	62
Dynamic Instability.....	80
Dynamic Inversion.....	192
Dynamic Loudspeakers.....	150-151
Dynamic Microphones.....	126-127
Dynamotors.....	387
Dynamotors (Table).....	388
Dynatron Oscillator.....	81-82
E	
E-Layer.....	15
E-Layer.....	189
ET-Cut Crystals.....	58
Eddy Current.....	39, 46
Effective Current Value.....	31
Efficiency, Amplifier.....	104
Efficiency, Frequency Conversion.....	156
Efficiency, Transformer.....	38
Electric Charges.....	14-16
Electric Circuit.....	13-14
Electrical Length.....	210
Electricity.....	13
Electricity, Static.....	14-16
Electrodes.....	17
Electrolyte.....	18
Electrolytic Condensers.....	177
Electrolytic Conduction.....	17-18
Electromagnetic Deflection.....	83, 84
Electromagnetic Radiation.....	48-49
Electromagnetism.....	21-25
Electromotive Force (E.M.F.).....	15
Electron Orbits.....	18, 93
Electrons.....	13
Electron-Coupled Oscillator.....	80, 431
Electron Flow.....	13, 60
Electron Gun.....	83-84
Electronic Conduction.....	60
Electronic Keying Circuits.....	87
Electronic Keys.....	141
Electronic Switching.....	87
Electron Transit Time.....	90
Electron Transit-Time Oscillator.....	92
Electronic Voltage Regulation.....	180-181
Electrostatic Coupling.....	44
Electrostatic Deflection.....	84
Electrostatic Field.....	14
Electrostatic Induction.....	14-15
Electrostatic Shield.....	109-110
Element, Antenna.....	218
Elliptical Trace.....	409
Emergency Apparatus.....	385-394
Emergency Power Supply.....	186-187
Emission, Electron.....	18
Emission, Secondary.....	75, 76
End Effect.....	194
End-Fire Arrays.....	216, 218, 220
Energy.....	15, 25, 26
Energy Relationships.....	38
Energy Transfer.....	43-44
Envelope, Modulation.....	130
Equi-Potential Cathode.....	75
Excitation.....	79, 107-108
Exciter.....	94
Exciter Units (see "Transmitters").....	
Executive Committee, ARRL.....	11
Extended Double Zepp Antenna.....	219
Extinction Voltage.....	85
F	
F-Layers.....	189-190
FT-Cut Crystals.....	58
Fading.....	191
Farad.....	15
Faraday Shield.....	109-110
Federal Communications Commission, Regulations.....	12
Feed, Series and Parallel.....	81
Feed-Back.....	68, 69, 80
Feeders and Feed Systems (see "Antenna Systems").....	
Feeding Crystal-Oscillator Stages.....	295
Fidelity.....	125, 143, 160
Field Coil.....	150
Field Intensity Meters.....	411-412
Field, Electrostatic.....	14-15
Field, Magnetic.....	21-24
Field-Strength Meters.....	411-412
Filament.....	18, 75-77
Filament Supply.....	175
Fills and Repeats.....	463

	PAGE
Filter, Crystal.....	162, 168
Filters.....	46-47, 162, 177-179
Filters, R.F.....	139
Final Amplifier.....	94
Firing Voltage.....	85
First Detector.....	155
Five Meters (see "Very-High Frequencies").....	
Flat-Plane Reflector.....	225
Flat Response.....	125
Flow, Current.....	13, 16-21
Fluorescent Screen.....	84
Flux Density, Magnetic.....	22-23
Fly-Back.....	85
Flywheel Effect.....	42
Focusing Electrode.....	83
Folded Dipole.....	225
Force, Electromotive.....	15
Force, Lines of.....	14, 21
Formulas.....	
A.C. Average, Effective and Peak Values.....	31
Amplification Factor.....	61, 64
Antenna Length.....	194, 210, 219, 222
Bias-Supply Bleeder.....	181
Bridge Balance.....	48
Capacitive Reactance.....	34
Capacity of Condenser.....	413
Cathode Bias.....	73
Characteristic Impedance.....	50, 51, 207, 456
Coefficient of Coupling.....	44
Combined A.C. and D.C.....	59
Complex Wave.....	59
Conductance.....	26, 28
Coupling-Transformer Turns Ratio.....	124
Critical Inductance.....	178
Crystal Frequency-Thickens Ratio.....	58
Decibel.....	71
Delta Matching Transformer Design.....	207
Electromotive Force, Induced.....	25
Filter Design.....	47, 178
Frequency.....	40
Grid Impedance.....	105
Grid Leak Bias.....	74
Impedance.....	35, 36, 50
Impedance Matching.....	39, 119, 209
Impedance Ratios.....	39
Inductance Calculation.....	413
Inductance of Transmission Lines.....	198
Inductive Reactance.....	31
LC Time Constant.....	29, 43
Modulation Impedance.....	119
Modulation Percentage.....	118, 130
Modulator Transformers, Turns Ratio.....	124
Mutual Conductance.....	62
Ohm's Law (A.C.).....	33-37
Ohm's Law (D.C.).....	26-27
Output Voltage.....	64, 124, 179
Parallel Impedance.....	42
Plate Efficiency.....	70
Plate Resistance.....	62
Pot-Tank Design.....	57
Power.....	25
Power Factor.....	36
Power Output.....	109
Power-Supply Output Voltage.....	179
Power-Supply Transformer Voltage.....	179
Q.....	41-43
Q Antenna.....	207
RC Time Constant.....	29
Radiation Field.....	400
Reactance.....	34, 35, 36
Resistance, Equivalent Series.....	43
Resonance.....	41
Resonant Impedance.....	44
Rhombic Antenna.....	216
Ripple.....	178
Standing-End Impedance of Transmission Lines.....	199
Series, Parallel and Series-Parallel Capacities.....	28, 29, 35
Series, Parallel and Series-Parallel Inductance.....	28, 35
Series, Parallel and Series-Parallel Resistances.....	27-28, 35
Shunts, Meter.....	424
Standing-Wave Ratio.....	51
Surge Impedance.....	50, 207
Temperature Coefficient of Resistance.....	27
Time Constant.....	29
Transformer Volt-Ampere Rating.....	180
Transmission-Line Constants.....	199
Transmission-Line Length.....	199
Transmission-Line Spacing.....	199, 207
Turns Ratio.....	37
V.H.F. Transmission Range.....	193
Voltage Dividers.....	28, 183
Voltage, Induced.....	25
Voltage Regulation.....	175
Voltage-Regulator Limiting Resistor.....	180
Wave-length.....	48
Wave-length-Frequency Conversion.....	48, 411
Work.....	25
Franklin Oscillator.....	81

	PAGE
Free-Space Pattern, Antenna	195
Frequencies	33
Frequencies, Amateur, Characteristics of	12
Frequency	30, 48
Frequency Allocations, Amateur	11
Frequency Compensation	78
Frequency Converters	155, 156-158
Frequency Deviation	134
Frequency Divider	65
Frequency Distortion	83
Frequency Doubler	112
Frequency Drift	58-59, 79-80
Frequency Inductance and Capacity Charts	415-416
Frequency Measurement	
Absorption Frequency Meters	400-402
Calibrated Receiver	401
Calibrated Receiver with Auxiliary Oscillator	396
Comparison Methods	402
Frequency Standards	396-398
Heterodyne Frequency Meters	398-399
Locher Wires	403
V.H.F. Wavemeter	402
WWV Schedules	397
Frequency Meters	400-406
Frequency Modulation	
Constructional	
Modulator-Oscillator Unit	347-348
5-Mc. F.M. Transmitter	345-346, 348-349
5-Mc. F.M. L.F. Amplifier	333-336
Deviation Ratio	134
Discriminator	173-174
Limiter	172-173
Methods	117, 135-136
Principles	117, 134-136, 172-174
Reactance Modulator	135
Reception	172-174
Signal Generators	434
Frequency Multipliers	94, 112
Frequency Response	65, 125
Frequency Stability	79-80, 138
Frequency Standards	396-399
Frequency-Thickness Ratio of Crystals	58
Frequency-Wavelength Conversion	48
Fronts	191-192
Full-Wave Rectifiers	176
Fundamental Frequency	48
GT-Cut Crystals	58
Gain Control	128, 151
Galvanometers	30
Ganged Tuning	153
Gaseous Conduction	17
Gaseous Regulator Tubes	180
Gauges, Metal	466
Gauss	23
Generators	187, 387
General-Coverage Tuning	153-154
Generator, A.F. Signal	410
Generator, A.M. Signal	410
Generator, F.M. Signal	410
Generator, Sweep	407
Generators, Gas-Driven (Table)	389
Godley, Paul	10
Government Licenses	12
Grid	60
Grid Bias	62, 76, 79, 105
Grid-Bias Modulation	119, 121-122
Grid-Cathode Capacity	63
Grid Control	60-61
Grid-Control Rectifiers	75, 139
Grid Current	61
Grid Driving Power	64
Grid Emission	110
Grid Excitation	63-64
Grid Impedance	105-106
Grid Keying	139
Grid Leak Calculation	74
Grid-Leak Detectors	144-145
Grid Losses	79
Grid Neutralization	101, 102
Grid-Plate Capacity	63
Grid-Plate Oscillator	98
Grid-Plate Transconductance	62
Grid, Screen	75
Grid, Suppressor	76
Grid Swing	71
Grid Voltage	105
Ground	59
Ground Connection	222
Ground Effect	195-197
Ground, Imperfect	196
Ground-Plane Antenna	224
Ground Potential	59
Ground Waves	188, 192-193
Grounded Antennas	222-223
Grounded-Grid Amplifier	75
Grounded-Plate Amplifier	75
Grounds	59

	PAGE
Gun, Electron	83-84
Guys, Antenna	377
Hairpin Coupling Loop	113
Half-Wave	48
Half-Wave Antenna	194-195
Half-Wave Rectifiers	176
Halyards, Antenna	378
Hand Capacity	101
Harmonic	49
Harmonic Antenna	49
Harmonic Distortion	64-65
Harmonic Frequencies	49
Harmonic Generation	98-99, 112
Harmonic Operation of Antennas	49, 209-211
Harmonic Reduction	202
Harmonic Resonance	49
Harmonic Suppression	109, 202
Hartley Circuit	80
Hash	185
Headphone Impedance	149
Headphones	150
Headquarters, ARRL	11
Headset Amplifier	149
Headsets	150
Heater	73
Heating Effect	27
Henry	25
Hertz Antenna	194
Heterodyne Frequency Meters	397-400
Heterodyne Reception	142
High-C Circuit	43
High Frequencies	33
High-Frequency Compensation	78
High-Frequency Oscillator (Receiver)	155, 158-159
High-Frequency Relaxation Oscillator	82
High-Pass Filters	46-47
High-Q Circuits	113
High-Vacuum Rectifiers	175
Hiram Percy Maxim Memorial	11
Hiss Noise	152, 165
History of Amateur Radio	9-12
Holes, Drilling and Cutting	230
Hollow Wave Guides	54-55
High-Speed Sweep Circuits	86-87
Hook-Up Wire	232
Horn Radiators	226
Hum	129, 133, 147
Hydrometer	20
I	16-17
Icososcopes (Table)	441
Image, A.F.	161
Image, R.F.	155
Image Ratio	155, 165
Image Suppression	165
Impedance	34-35, 39, 42
Impedance, Antenna	50, 194, 195, 196, 210
Impedance-Coupled Amplifiers	66-67
Impedance, Grid	105-106
Impedance Matching	39, 51
Impedance Ratio, Transformer	39
Impedance, Resonant	42
Impedance, Surge	50
Impedance, Tank	95, 104-105, 106
Impedance Transformer	51
Impulse Noise	166
Incomplete Neutralization	104
Indicators, Tuning	164-165
Induced Voltage	23
Inductance	24-25
Inductance, Capacity and Frequency Charts	415-416
Inductance-Design Charts for V.H.F. Coils	416
Inductance, Distributed	36
Inductance, Mutual	25
Inductances in Series and Parallel	28
Inductance Winding Charts	107
Induction	14-15
Induction, Magnetic	22
Induction, Self	24
Inductive Capacity	16
Inductive Coupling	44
Inductive Neutralization	102
Inductive-Output Tube	90-91
Inductive Reactance	34
Inductively Coupled Circuits	44-45
Infinite Impedance Detector	145-146
Input Capacity, Tube	68
Input Choke	177, 178-179
Input Loading	152
Input Resistance, Tube	68, 152
Instability	79-80, 172
Instantaneous Current Value	31
Instantaneous Plate Current	175
Instruments	
A.C.	36
Ammeters	30, 36
Audio-Frequency Signal Generator	410

	PAGE		PAGE
D.C.	30, 405-406	Lazy H. Antenna	218
Field-Intensity Meters	402, 411	Lead, Current	31-32
Frequency Meters	395-404	Lead Storage Battery	19-20
Frequency Standards	396-400	Leakage Inductance	38
Galvanometer	30	Leakage Reactance	38-39
Lecher-Wire Systems	103	<i>Learning the Radioteletype Code</i>	460
Metering	302	Lecher Wires	403-404
Microammeter	30	Lenz's Law	23-24
Milliammeter	30	<i>License Manual, The Radio Amateur's</i>	12
Monitors	404	Licenses, Amateur	12
Multimeters	406	Lightning Protection	384
Multi-Range V-O-M	406, 107	Limiter	88
Ohmmeters	406	Limiter, F.M.	172-173
Oscilloscopes	407, 110	Limiting, Audio	166
R.F.	400, 403	Limiting (Noise) Circuits	165-167
Signal Generators	410	Limiting Resistor	180
Sweep Generator	408	Line-of-Sight Transmission	193
Test Oscillators	410	Line Voltage Adjustment	186, 304
Voltmeters	30	Linear Amplifiers	72
Wattmeter	30	Linear Antenna Transformers	51, 207-209
Insulators	14	Linear Circuits	48-53, 113-114
Integrating Circuit	88, 89	Linear Sweep	85, 407
Inter-electrode Capacities	63	Linear Transformers	207-209
Intermediate Frequency	155, 159, 163	Linearity	118, 119, 123, 132, 135, 143
Intermediate Frequency Amplifiers	142, 159, 163	Lines of Force	14, 21
Intermediate Frequency Noise Silencer	167	Lines, Resonant	51, 52-53
Intermediate-Frequency Transformers	160, 161	Lines, Two-Conductor	52-53
Intermodulation	117	Link Coupling	44, 100, 201
Internal Resistance	19	Lissajous's Figures	417
International Amateur Radio Union	10	Load	13, 39, 43, 175
Interpolation, Frequency	395	Loaded Antennas	223
Interruption Frequency	148, 149	Load Impedance	59, 104-105
Interstage Coupling	99, 100	Local Oscillator (Receiver)	155, 158-159
Interstage Transformers, I.F.	160, 161	Load Resistance	175
Inverse Peak Voltage	175	Locking	82, 83
Inversion, Cloud-Layer	192	Locking-In	148
Inversion, Dynamic	192	Log Books	466
Inversion, Nocturnal	192	Long-Wire Antennas	209-211, 214-216
Inversion, Phase	129	Loop Antennas	223
Inversion, Subsidence	192	Loops	49
Inversion, Temperature	192	Loose Coupling	46
Inverted Amplifier	78, 104	Losses, Antenna	200-201
Ionization	17, 189	Loudspeakers	150-151
Ionosphere	189, 191	Low-C Circuit	43
Ionospheric Waves	188, 189, 191	Low Frequencies	33
Ions	17	Low-Frequency Compensation	78
Iron-Core Transformers	39	Low-Frequency Parasitics	110
Iron-Vane Meters	36	Low-Level Modulators	125
		Low-Pass Filters	46-47
"J" Antenna	223, 393	Low-Power Transmitters (see "Transmitters")	
Joule	25	Lumped-Constant Circuits	57, 118
Key Chirps	140	MT-Cut Crystals	58
Key Clicks	137, 140	Magic-Eye (Electron-Ray) Tubes	164-165
Key, Electronic	141	Magnet, Permanent and Temporary	22
Key, How to Use	462	Magnetic Attraction and Repulsion	21-22
Keying:		Magnetic Circuit	22-23
Back Wave	137	Magnetic Feed-Back	80
Break-In	138	Magnetic Field	21
Electronic Keys	141	Magnetic Headphones	150
Key-Click Reduction	139, 140	Magnetic Induction	22
Methods:		Magnetic Storms	190
Blocked Grid	139	Magnetism	21-25
Cathode or Center-Tap	139	Magnetizing Current	38
Grid-Controlled Rectifier	139	Magnetomotive Force	22
Plate	138	Magnetron Oscillators	92-93
Power-Supply	138	<i>Manual, The Radio Amateur's License</i>	12
Primary	139	Marconi (Grounded) Antennas	222-223
Screen Grid	138	Masts	376-380
Suppressor Grid	139	Matching Impedances	39, 51
Tube Keyer	140, 300	Materials	228
Waveform	137	Maximum Current Value	31
Monitoring	141	Maximum Usable Frequency	180
Oscillator Keying	140	Measurements:	
Parasitic Clicks	140	Antenna	411-412
Keying Circuits, Electronic	87	Current	29-30, 36-37, 405-407
Kilocycle	30	Frequency	393-404
Kilohm	28	Modulation	125-127, 136, 407
Kilovolt	28	Power	29-30, 405
Kilowatt	28	Resistance	405
Kilowatt-Hour	28	Voltage	29-30, 405-407
Kinescopes (Table)	41	WVY Schedules	397
Klystron Amplifier	91, 92	Measuring Instruments	29-30, 36-37, 396-412
Klystron Oscillator	91, 92	Mezocycle	30
		Micohm	26
L	24	Memorizing the Code	460-461
LC Constants	43	Mercury Vapor Rectifiers	79
L/C Ratios	43, 79, 107	Message Handling	464-465
L/C Time Constant	49	Metal, Cleaning and Finishing	232
L-Section Filters	47	Meters (see "Instruments")	
Lag Circuits	140	Mho	26
Lag, Current	31-32	Micrometers	30
Lag, Keying	137	Micrometers	26
Laminations	39	Micromeg and Micromicrofarad	15
Land Line Check	465	Microhony	25
Lapse Rate	192	Microhm	62
Laws Concerning Amateur Operation	11	Microphones	117, 125-127
Layer Height	190	Microvolt	26

	PAGE
Microwatt	26
Microwave Oscillators	372-374
Milliammeters	30
Milliamperes	26
Millihenry	25
Millivolt	26
Milliwatt	26
Mixers	155
Mixers, Signal Generator	410
Mobile Antennas	382, 393
Mode	55
Modes of Propagation	55
Modulation:	
Adjustments and Testing	130, 131, 407
Amplitude Modulation	117, 119
Capability	118
Cathode Modulation	122, 123
Characteristic	118
Envelope	130, 131
Frequency Modulation	117, 134, 136
Grid-Bias Modulation	121, 122
Impedance	119, 123
Linearity	118, 119, 123, 132, 135, 143
Measurements	125-127, 136, 107
Methods	117-123, 135, 136
Monitoring	131
Percentage	118, 130, 131
Plate Modulation	119, 121
Power	118, 119, 121
Suppressor Modulation	122
Test Equipment	407
Waveform	131
Modulator Data	313, 314
Modulators	124, 125, 305-315, 373, 374, 392
Molecular Friction	14
Molecules	13
Monitors	131, 141, 404
Monoscopes (Table)	411
Motorboating	128, 172
Mounting Crystals	96
Moving-Coil Meters	36
Moving Iron-Vane Meters	29, 30, 36
Mu	61
Multi-Band Antennas	211, 214
Multi-Element Tubes	74, 77
Multi-Hop Transmission	191
Multimeters	406
Multi-Purpose Tubes	74, 77
Multiplicers, Frequency	91, 112
Multiplicers, Voltmeter	30, 406
Multi-Segment Anode Magnetron	93
Multi-Stage Bias Supplies	182
Multivibrator	83, 306, 307
Mush	172
Mutual Conductance	62
Mutual Inductance	25
N.T.-Cut Crystals	58
Naval Reserve	10
Negative Charges	13, 14
Negative Feed-Back	69
Negative Resistance	79
Negative-Resistance Magnetron Oscillator	92
Negative-Resistance Oscillators	81-82
Negative Transconductance	82
Net Operation	466
Neutralization	101, 104
Neutralizing Condensers	101, 103
Nocturnal Inversion	192
Noises	49
Noise	129, 133, 152, 165, 166
Noise Ratio	143, 152, 165
Noise Reduction	165-167, 390
Non-Resonant Lines	51, 199, 204-209
Non-Synchronous Vibrators	185
Nucleus	13
Numbering Messages	462
Ohm	26
Ohm's Law	26
Ohm's Law for A.C.	33, 37
Ohmmeters	406
Open Circuit	14
Open-Wire Line	198, 202
Operating Angle, Amplifier	104, 112
Operating Point	62
Operating Procedure, General	460, 468
Operator's License, Amateur	12
Orbital-Beam Tube	90
Originating Messages	462
Oscillating Detector	146, 149
Oscillation	42, 74, 79-83, 110-112, 171
Oscillator Keying	140
Oscillators	79-83, 90-93, 95-99, 113-116, 158-159, 163
Oscillators, Test	410
Oscilloscope Amplifiers	407, 409
Oscilloscopes	85, 130-134, 407-410
Output Capacity, Tube	63

Output Limiting	129
Output Power	69, 79, 109
Output Transformer	70
Output Voltage	69, 124, 178, 179
Oxide-Coated Cathode	73
Over excitation	125
Overmodulation	118
Overmodulation Indicators	135, 407
P	25
Padding Condensers	154
Parabolic Reflectors	225
Parallel Amplifiers	70
Parallel Antenna Tuning	200
Parallel Capacities	29
Parallel Circuits	28-29, 35, 42
Parallel-Conductor Line	51
Parallel Feed	81
Parallel Inductance	35, 42
Parallel Impedances	28
Parallel-Line Oscillators	114
Parallel Resistances	27-28
Parallel Resonance	42
Parallel Tuning	200
Parasitic Elements	220-222
Parasitic Oscillations	110-112
Pass Band	47
Patterns, Oscilloscope	130, 132, 408
Patterns, Radiation	197, 211
Peak Current Value	31
Peak Plate Current	175
Peak Voltage Rating	106
Peaking	88-89
Pentagrid Converters	156-157
Pentode Amplifiers	77, 78, 100
Pentode Crystal Oscillators	97
Pentode Relaxation Oscillator	82
Pentodes	76
Per Cent Conductivity	26
Percentage of Modulation	118, 130-131
Per-Cent Ripple	177
Period	30
Permanent Magnet	22
Permeability	23
Persistence, Screen	84
Phase	31, 32
Phase Angle	31
Phase Difference	31
Phase Inversion	129
Phase Modulation	117
Phase Relations, Amplifiers	67-68
Phase Reversal	68
Phase Shift	435
Phase-Shift Network	82
Phase-Shift Oscillator	82
Phased Antennas	216-219
Phasing Control	162
Phone (see "Radiotelephony")	
Phonetic Alphabet	464
Pick-Up Coil	199
Pi-Section Antenna Couplers	200
Pi-Section Filters	47, 200
Pierce Oscillator	98
Piezoelectricity	58
Piezoelectric Crystals	58, 96
Piezoelectric Microphone	126
Plane Reflector Antennas	227-228
Plane Sheet Reflectors	227
Plate	18, 60
Plate-Cathode Capacity	63
Plate Current	60
Plate Current Shift	132-133
Plate Detectors	145
Plate Dissipation	63
Plate Efficiency	70, 79
Plate Keying	138
Plate Load Resistance	61-62
Plate Modulation	119-121
Plate Neutralization	101-102
Plate Resistance	61-62
Plate Supply	175, 183, 184
Plate Transformer	179-180
Plate Tuning, Power Amplifier	108-109
Plate Voltage	60
Plate Voltage Calculation	77
Plates, Deflection	83-84
Polarity	14, 16
Polarization	16, 18, 188, 194, 196
Pole	14, 22
Portable Equipment	385-394
High-Frequency	390
H.F. Antennas	392-393
Low Frequency	391
L.F. Antennas	394
Simple Modulator	392
Positive Charges	13, 14
Positive Feed-Back	68
Positive-Grid Oscillators	92

	PAGE		PAGE
Pot Oscillator	113	Radio-Frequency Power-Amplifier Circuits	100-104
Pot Tank Circuits	57	Radio-Frequency Power Amplifiers (see "Transmitters")	
Potential Difference	15, 16	Radio-Frequency Power Generation	94-116
Potentiometers	28	Radio-Frequency Resistance	41
Power	25	Radio-Frequency Shielding	145
Power Amplification	69-70	Radio Reception	142
Power Amplifiers, Receiver	149-150	Radiotelegraph Operating Procedure	463
Power Factor	36	Radiotelephony:	
Power Gain, Antenna	194-210	Adjustments and Testing	130-134
Power Measurement	30, 405-407	Class-B Modulators	124-125
Power Output	69, 79, 109	Class-B Modulators (Table)	313-314
Power Sensitivity	70	Constructional:	
Power-Supply Keying	138-139	6-Watt P.P. 2A3 Speech-Amplifier and Driver	
Power Supplies:		with Volume Compression	309
A.C.-D.C.	183-184	10-Watt Class-B 6A6 Modulator	305
A.C.-D.C. Converters	187, 388	20-Watt 6L6 Speech Amplifier/Modulator	307
Battery Service Hours (Table)	188	40-Watt 6L6 Speech Amplifier/Modulator	308
Bias Supplies	279	F.M. Modulator-Oscillators	347-348
Combination A.C.-Storage Battery Supplies	385-386	High-Power Modulators	310-311
Constructional:		Measurements	125-127, 136, 395
100-Volt Bias Supply	279	Microphones	125-127
300-Volt 75-Ma.	262	Modulation	117-125, 134-136
300-Volt 100-Ma. Vibrator Storage-Battery		Monitors	404
Supply	386	Operating Procedure	460
450-Volt 130-Ma. Plate Supply	257	Principles	117-136
780-620-Volt 260-Ma. Plate Supply	263	Reception	168
1000-400-Volt 125-150-Ma. Dual Supply	309	Resistance-Coupled Speech Amplifier Data	115, 311-312
1250-1050-830-Volt 250-Ma. Plate Supply	271	Speech Amplifiers	127-129
1500-1250-Volt 425-Ma. Plate Supply	279	Radio Transmission	188
2180-2025-Volt 450-Ma. Plate Supply	287	Radio Waves	9-110, 188
Design Data	175	Range, V.H.F.	193
Dry Batteries	186, 385	Range vs. Height	193
Dynamotors	187	Ratio Arms	48
Dynamotors (Table)	388	Ratio, Impedance	39
Emergency Power Supply	186, 385-390	Ratio, Turns	37
Filament Supply	175	Ray, Direct and Reflected	188
Genomotors	187	Reactance	33-34, 51
Generators, Gas-Driven (Table)	389	Reactance, Capacitive	34
Noise Elimination	390	Reactance, Inductive	34
Plate Supply	175, 183, 184	Reactance, Leakage	38
Portable	186-187	Readability Scale	464
Principles	175, 187	Receivers:	
Storage Batteries	19-20, 186-187, 389	Antennas for	226
Transformers, Rewinding for Vibrator Supplies	389	Constructional:	
Vibrapak	187	2-Tube 2-Stage Regenerative	234-238
Vibrators	185-186, 187, 386	2-Tube Superheterodyne (6K8-6C8G)	238-241
Vibrator Supplies (Table)	388	3-Tube Wide-Range Superheterodyne	241-244
Preselection	165	7-Tube Regenerative S.S. Superheterodyne	245-248
Preselectors (see "Receivers")		12-Tube Crystal Filter	248-252
Primary	37, 45	Panoramic	252-255
Primary Cells	19	(See also "Very-High Frequencies — Receivers")	
Primary Coil	37	Measurements	395
Primary Keying	139	Principles and Design	142-174
Procedure, Operating	462-465	Test Equipment	395
Propagation, Wave	188-193	Receiving-Tube Classification Chart	419
Protective Bias	181	Rectification	60
Pulleys, Antenna	378	Rectifier Circuits	175
Pulling	156	Rectifiers	60, 79, 175-176
Pulsating Current	59	Rectifiers (Table)	443-444
Pulse Transmission	12, 88	Reflected Impedance	39
Pure D.C.	175	Reflected Load	39
Push-Back Wire	232	Reflected Waves	48-49
Push-Pull Amplifiers	70-71	Reflection of Radio Waves	188, 189, 195
Push-Pull Negative-Resistance Oscillator	82	Reflector	221
Push-Pull Neutralization	102	Reflector Electrode	91
Push-Push Doubler	112	Refraction of Radio Waves	190
Push-Pull Parallel-Line Oscillators	115	Regeneration	68, 162, 165
Pyramidal Horn	226	Regeneration Control	146
Q	32, 42-43, 46, 95, 113	Regenerative Detectors	146
Q Antenna	207	Regenerative I.F.	162
Q Code	467-468	Regenerative Receivers	142
QRK Scale	468	Regulation, Voltage	175, 181
QRR	468	Regulations, Amateur	11
QSA Scale	468	Regulator Tubes	180
"Q"-Section Transformer	208	Regulator, Voltage	175
QST	468	Relative Polarity	15
QST	11	Relaxation Oscillator	82-83
Quarter Wave	49	Relay, Keying	138
Quartz Crystals (see "Crystals")		Reluctance	23
Quench Frequency	148-149	Repulsion	14, 21
R	26	Repulsion-Type A.C. Meters	36
R.M.S. Current Value	31	Resistance	13, 26-28, 33
Rack Construction	300-301	Resistance-Capacity Filter	47
Radiation	9, 49	Resistance-Capacity Oscillators	82
Radiation Angle	191-194, 196	Resistance-Capacity Time Constant	20
Radiation Characteristics	195	Resistance-Coupled Amplifier Data (Chart)	128, 307-308
Radiation Field	196	Resistance-Coupled Amplifiers	65-66
Radiation Patterns	195, 197, 211	Resistance-Coupled Audio Amplifiers	128
Radiation Resistance	49, 195, 210	Resistance Coupling	44, 128
Radiator (see "Antennas")		Resistance Measurement	405
Radio Amateur's License Manual, The	12	Resistance, Negative	81
Radio Communication	9-12	Resistance, Radiation	49
Radio Frequency	33	Resistance, R.F.	41
Radio-Frequency Amplification	100-104	Resistance, Tube Input	152
Radio-Frequency Amplifiers (Receivers)	142, 151-153	Resistances in Series and Parallel	27-28
Radio-Frequency Choke Coil	59	Resistor	27

	PAGE		PAGE
Resistor Color Code	414	Solar Cycle	190
Resonance	41, 179	Soldering	233
Resonance Curve	143	Space Charge	60
Resonance, Harmonic	49	Space Wave	188
Resonance of Transmission Lines, Computing	457	Spectrum, A.C.	33
Resonance, Sharpness of	41	Spectrum, Triangular	134
Resonant Circuits	40-43, 45-46	Speech Amplifiers	127-129, 136
Resonant Frequency	40	Speech Amplifier Design Charts	128
Resonant Impedance	42, 457	Speech Waves	119
Resonant-Line Circuits	52-53	Sporadic-E Layer Ionization	190
Resonant Transmission Lines	199, 202-204	Spreaders, Antenna	198, 387
Resonator Circuits	55-56	Spurious Responses	155, 168-169
Response Frequency	65, 125	Spurious Sidebands	119, 133
Restricted Space Antennas	213-214	Square Wave	88
Retarding Field	81, 91, 92	Squeezing	159, 172
Retarding-Field Oscillators	91, 92	Squeezing Oscillator	82
Return Trace	85	Stability, Frequency	79-80, 138
Reversal, Phase	68	Stability, Receiver	145, 172
R.F. Instruments	395-400	Stabilization, Voltage	180-181, 182
Rhombic Antenna	217-218	Stage Gain	127
Ribbon Microphones	126	Standards, Frequency	414-416
Ripple Voltage	177, 178	Standing Waves	50-51
Rochelle Salts Crystals	58	Standing-Wave Ratio	51
Root-Mean-Square Value	31	Starting Voltage	180
Rotary Antennas	220-222, 379-381	Static Characteristics	62-63
S Meters	164-165	Static Charge	13
S Scale	464	Static Electricity	14-16
Saturation, Magnetic	23	Station Control Circuits	303-304
Saturation Point	60	Storage Batteries	19-20, 156-187, 389
Sawtooth Sweep	408	Straight Amplifier	94
Sawtooth Wave	85, 88	Striking Voltage	86
Schematic Symbols	<i>Frontispiece</i>	Subs, Antenna Matching	207
Screen Grid	75	Subsidence Inversion	192
Screen-Grid Amplifiers	120	Subspot Cycle	190
Screen-Grid Keying	138	Superheterodyne	142
Screen-Grid Tubes	75	Superegneration	148
Screens, Fluorescent	84	Superegnerative Detectors	142, 148-149
Screen Voltage, Calculation	77	Superegnerative Receivers	142, 316
Seasonal Effects	190	Suppression, Harmonic	98
Second Detector	155, 163, 166	Suppressor Grid	62
Secondary	37-38	Suppressor-Grid Keying	139
Secondary Cells	19-20	Suppressor-Grid Modulation	121
Secondary Coil	37	Suppressor, Noise	166-167
Secondary Emission	75-76	Surface Wave	190, 194
Section Communications Managers	11	Surge Impedance	51-52, 209
Sectoral Horn	228	Sweep Circuits	86-87, 407
Selective Fading	193	Sweep Generator	407
Selectivity	41, 143, 161	Sweep Waveforms	408
Selectivity Control	162	Swing Grid	61
Self-Bias	73	Swinging Choke	178
Self-Controlled Oscillators	95-96	Switching, Antenna	384
Self-Induction	24	Switching, Control Systems	303-304
Self-Oscillation	79	Symbols, Schematic	<i>Frontispiece</i>
Self-Quenching	148	Symbols, Vacuum Tube	420
Sending Code	462	Synchronization	83, 86
Sensitivity, Microphone	125	Synchronous Vibrators	187
Sensitivity, Receiver	142, 143	T-Section Filters	48
Separation, Pulse	89	Tables (see "Charts and Tables")	
Separators, Battery	20	Talking Level, Microphone	125
Series Antenna Tuning	202	Tank Circuit	79, 95, 106
Series Capacities	29	Tank Circuit Q	95, 106
Series Circuits	28-29, 40	Tank Constants	106-107
Series Feed	81	Taps	232
Series Inductances	28	Tapped Circuit	41
Series Resistances	28	Temperature Coefficient of Crystals	58
Series Resonance	40	Temperature Coefficient of Resistance	27
Service Message	465	Temperature Inversion	194
Sharpness of Resonance	41	Temporary Magnet	22
Sheet Metal Working	230	Terminal Strips	232
Shield Grid	75	Termination, Line	51-52
Sharp Cut-Off Tubes	76	Tertiary Winding	161
Shielding	46, 109-110, 151	Test Equipment	395-404
Shields, Baffle	46	Test Oscillators	400-404
Shields, Electrostatic	109-110	Tetrode Amplifiers	100
Short-Wave Receivers (see "Receivers")		Tetrode Crystal Oscillators	97
Short Noise	165	Tetrodes	74
Shunts, Meter	30, 402, 406	Thermal Agitation	152
Sidebands	118-119, 133, 135, 160	Thermionic Conduction	18
Signal	62	Thermionic Emission	18
Signal-Generators	410	Thermocouple Ammeters	38
Signal-Handling Capability	143	Thickness of Crystals	58
Signal to Image Ratio	155	Thoriated-Tungsten Cathodes	76
Signal-Noise Ratio	143, 152, 165	Threads, Cutting	232
Signal-Strength Indicators	164-165	Three-Mesh Phase-Shift Oscillator	82
Signal-Strength Scale	462	Threshold Control	167
Silencers, Noise	166-167	Thump Filters	140
Sine Curve	30	Tickler	80
Sine Wave	30	Tight Coupling	45
Single-Signal Effect	161	Time Base	85-86, 408
Single-Signal Reception	161	Time-Base Circuit, 60-Cycle	408
Single-Wire Feed	198, 204-205	Time Constant	29-30, 164
Skin Effect	41	Time Systems	466
Skip Distance	191	Tone Control	150
Skip Zone	191	Tools	227
Sky Wave	188, 190	Top-Loaded Antennas	223
Smoothing Choke	179	Trace, Cathode-Ray	85-86
Socket Connections (Diagrams)	420-425	Tracking	154, 159

	PAGE
Trans-Atlantic Tests	10
Transceivers	340
Transconductance, Grid-Plate	62
Transconductance, Negative	82
Transformer Color Codes	414
Transformer-Coupled Amplifiers	67
Transformer Coupling	44-45, 119, 128
Transformer, Delta-Matching	206-207
Transformer Design	179-180
Transformer Efficiency	38
Transformer Primary	37
Transformer, "Q"-Section	207
Transformer Secondary	37
Transformerless Power Supplies	183
Transformers	37-40
Transformers, I.F.	160-161
Transformers, Linear-Circuit	54-55, 208-209
Transformers, Plate	179-180
Transformers, Rewinding for Vibrator Supplies	385
Transformers, Triple-Tuned	161
Transitron	82
Transit Time	90
Transit-Time Magnetron Oscillator	93
Transmission Lines	54, 198, 209, 382
Transmission Lines as Circuit Elements	52
Transmission Line Coupling	199-202
Transmission-Line Resonators	456-457
Transmitters:	
Antenna Coupling	198
Antenna Switching	384
Antenna Tuners (see "Antennas")	
Constructional:	
Complete Transmitter Assemblies:	
15-Watt 6L6 All-Band	256
75-Watt Multi-Band With 807 Final	264
75-Watt All-Band With 807 Final	260
90-Watt C.W. With P.P. 6L6s	265, 266
100-Watt 5-Band With 1623 Final	267, 268
200-Watt Four-Band	270
300-Watt Compact Transmitter	274
450-Watt Band-Switching Transmitter	280
450-Watt Variable-Frequency Gang-Tuned	299
Exciters or Low-Power Transmitters:	
Variable-Frequency Exciters	287-294
15-Watt Output 6L6 Bread-Board	256-257
50-Watt Output 6L6-807 Plug-In Coil	257-259
50-Watt Output 6C5-6N7 Band-Switching	260-262
60-Watt Output 6L6-6L6s P.P.	265
75-Watt Output 6L6-HY65-1623	267-268
150-Watt Output	270
Power Amplifiers:	
450-Watt Input Push-Pull	272-276
450-Watt Band-Switching Push-Pull	276-278
450-Watt Gang-Tuned Push-Pull	296
300-500-Watt Single-Ended	281-283
800-Watt Push-Pull Tetrode	283
1-Kw. Push-Pull	285
(See also "Very-High Frequencies - Transmitters")	
Control Circuits	303-304
Keying (see "Keying")	
Measurements	395
Metering	392
Modulation (see "Modulation" and Radiotelephony")	
Power Supply (see "Power Supplies")	
Principles and Design	91-116
Rack Construction	300-301
Vacuum-Tube Keyer	301
Transverse Electric Mode	55
Transverse Magnetic Mode	55
Trapezoidal Pattern	131-132
Trapezoid Wave	88
Triangular Spectrum	131
Trigger Circuits	87
Triggering Voltage	85
Trimmer Condenser	154
Triodes	60-63
Triode Amplifiers	100
Triode Crystal Oscillators	97
Triple-Tuned Transformers	161
Tri-Tot Oscillator	98
Troposphere Propagation	191-192
Tropospheric Waves	188
Trouble Shooting (Receivers)	169-172
Trough Line	49
Tube Classification Charts	419
Tube Keyer	140, 297
Tube Noise	152
Tube Ratings	63, 425
Tubes (see "Vacuum Tubes")	
Tuned Circuits	40-43, 52
Tuned-Grid Tuned-Plate Circuit	81
Tuned R.F. Receiver	142
Tuned Transmission Lines	202-201
Tungsten Cathodes	164-165
Tuning Indicators	147, 153-154, 168, 174
Tuning Receivers	147, 153-154, 168, 174

	PAGE
Tuning Transmitters	96, 97, 98-99, 107-110
Turns Ratio	37
Two-Terminal Oscillators	82
Turnstile Antenna	224
Twisted Pair Feed	198, 206
Two-Conductor Lines	48-49, 202
Ultrahigh Frequencies	33
(See also "Very-High Frequencies")	
Ultrasonic Circuit	80
Untuned Transmission Lines	204-209
Upward Modulation	133
Using a Key	462
"V." Antennas	214-216
Vacuum Tubes	18, 60-93
Vacuum-Tube Classification Chart, Receiving	419
Vacuum-Tube Index	426-439
Vacuum-Tube Socket Connections	420-425
Vacuum-Tube Symbols	420
Vacuum-Tube Tables:	
Cathode-Ray Tubes	441-442
Control and Regulator Tubes	440
Receiving	426-439
Rectifiers	443-444
Transmitting	445-458
Vacuum-Tube Voltmeters	30, 422-423
Variable-a Tubes	76
Variable Selectivity	161, 162
Velocity, Angular	31
Velocity Microphone	126
Velocity-Modulated Tubes	91
Velocity Modulation	48
Velocity of Radio Waves	48
Very-High Frequencies:	
Antenna Systems:	
Coaxial Antenna	223-224
Constructional	223-226, 383, 384
Corner Reflector Antenna	226, 383
Directive Arrays	214-222
Field-Strength Meters	404
Folded Dipole	225
"J" Antenna	223, 392
Loop Antennas	223
Mobile Antennas	382, 393
Polarization	188, 191, 196
Propagation	188, 193
Radiation Patterns	197, 211
Transmission Lines	198-200, 379, 381
Turnstile Antennas	224
Constructional:	
Receivers:	
144-Mc. Simple Superregenerative	317-318
144-Mc. Superregenerative Superhetro	321-326
144-Mc. Superregen. Built-In Speaker	319-320
144-Mc. P.R.F. Superregenerative	322-324
144-Mc. Vacuum Tube Superhetro	327-329
50- and 144-Mc. Converter	329-332
P.M. I.F. Amplifier	333-336
Transmitters:	
Complete 144-Mc. Mobile Station	363-366
Simple 144-Mc. Transceiver	360-361
144-Mc. Handie-Talkie	361-362
Transmitters:	
A.M. F.M. 50-Mc. Transmitter	338-340
Double-Beam Tetrode Amplifier	357-359
F.M. Modulator-Oscillator	347-348
H.C. 114-Mc. Oscillator	353-354
High Power Linear Oscillator	368-369
"Lighthouse" Tube Oscillator	369-371
Low-Power 50-Mc. F.M. Transmitter	345-346
Parallel Line P.P. Oscillator	367
Simple 220-Mc. Transmitter	368-369
Stabilized 144-Mc. Transmitter	354-356
10-Watt 50-Mc. Transmitter	343-345
12-Watt 50-Mc. Mobile	349-351
50-144-Mc. Driver Amplifier	341-343
140-150-Mc. Oscillator	372-374
144-Mc. Oscillator (6C4)	351-352
Very Low Frequency	33
Vibratack	187
Vibrator Power Supplies	185, 187, 385
Vibrator Power Supplies (Table)	388
Video	12
Virtual Height	189
Visual Alignment	170-171
Visual Alignment Signal Generator	409
Voice Coil	150
Volt	15
Volt-Amperes	36
Voltage Amplification	64, 149
Voltage Amplifier Data	307-308
Voltage Dividers	28, 183
Voltage Drop	28, 42, 175
Voltage Feed for Antennas	198
Voltage Measurement	29-30, 406
Voltage Multiplier Circuits	183
Voltage, Plate Calculation	76-77

	PAGE
Voltage Ratio, Transformer	37
Voltage Regulation	175, 180, 181
Voltage, Ripple	177, 178
Voltage Rise	42
Voltage, Screen Calculation	77
Voltage-Stabilized Power Supplies	180-181, 182
Voltmeters	29-30, 106
Volume Control	128, 163-164
W1AW-WLMK, ARRL Hq. Station	11
W1NF	11
W1MK	11
WAC Certificates	11
Watt	25-26
Watt-Hour	26
Watt-Second	26
Wattmeter	30
Wave Angle	191
Wave Envelope Pattern	130-132
Wave Guides	54-56
Wave, Ground	188, 192-193
Wave Propagation	188-193
Wave Sine	30
Wave, Sky	188
Waveform	30, 130-132, 137
Wavelength	48
Wavelength-Frequency Conversion	48
Wavelength Performance	190

	PAGE
Wavelengths, Amateur	11
Wavemeter (see "Frequency Meters")	9-10
Waves, Radio	37, 61, 85, 88, 105, 117-121, 125, 162
Waveshape	88-89
Waveshaping Circuits	48
Wheatstone Bridge	78
Wide-Band Amplifier	224-225
Wide-Band Antennas	233
Winding Coils	418
Wire Table	232-233
Wired Wireless (see "Carrier-Current Communication")	Frontispiece
Wiring Apparatus	462
Wiring Diagrams, Symbols for	177
World Lists for Accurate Transmission	227-233
Working Voltage	397
Workshop Practice	33-34
WWV Schedules	58
X	58
X-Cut Crystals	58
Y-Cut Crystals	58
Z	34-35
Zero Bias	148
Zero-Bias Limiter	88
Zepp Feed for Antennas	202

Notes



The Catalog Section



In the following pages is a catalog-
file of products of the principal manu-
facturers who serve the short-wave
field. Appearance in these pages is
by invitation—space has been sold
only to those dependable firms whose
established integrity and whose prod-
ucts have met with the approval of
the American Radio Relay League.


INDEX OF MANUFACTURERS

★ CATALOG SECTION ★

The Radio Amateur's Handbook

	Page		Page
Aerovox Corporation.....	145	Industrial Transformer Co.....	173
Allied Radio Corporation.....	144	Instructograph Company, The.....	68
Altec-Lansing Corporation.....	78	International Resistance Co.....	108
American Lava Corporation.....	137	Jensen Radio Mfg. Co.....	63
American Phenolic Corporation.....	27	Johnson Co., E. F.....	142-143
American Radio Relay League, Inc.	1, 2, 125-136, 138	Jones Co., Howard B.....	152
American Television & Radio Co.....	176	James Knights Company, The.....	95
American Transformer Company.....	94	Lewis Electronics.....	90
Amperex Electronic Products.....	56, 57	Mallory & Co., Inc., P. R.....	58
Andrew Company.....	33	Marion Electrical Instrument Co.....	62
Astatic Corporation, The.....	65	Maryland Engineering Co.....	174
Barker & Williamson.....	47	McElroy Mfg. Co.....	21-26
Birnbach Radio Company, Inc.....	119	McElroy, Ted.....	110-111
Bliley Electric Company.....	43-46	Measurements Corporation.....	76
Brach Mfg. Corp., L. S.....	75	Micro-Switch Corporation.....	54
Browning Laboratories, Inc.....	48	Millen Mfg. Co., Inc., James.....	102-103
Burgess Battery Company.....	74	National Company, Inc.....	3-20
Cambridge Thermionic Corporation.....	114	Newark Electric Company.....	150-151
Cameradio Co.....	104	Ohmite Mfg. Co.....	66-67
Candler System.....	82	Par-Metal Products Corp.....	64
Cardwell Mfg. Corp., Allen D.....	70	Plymold Corporation, The.....	146
Centralab.....	86, 87	Premax Products.....	55
Cinaudagraph-Aireon Mfg. Corp.....	166-167	Radio Corporation of America.....	116-117
Clarostat Mfg. Company, Inc.....	115	Radio Manufacturing Engineers, Inc.....	98-100
Collins Radio Company, The.....	49-51	Radio Shack Corporation, The.....	77
Concord Radio Corporation.....	96	Raytheon Manufacturing Co.....	147
Cornell-Dubilier Electric Corp.....	28-29	Sangamo Electric Co.....	59
Crystal Products Inc.....	124	Shure Brothers.....	53
Crystal Research Laboratories, Inc.....	162-163	Sigma Instruments.....	165
Deutschmann, Corp., Tobe.....	52	Silver, McMurdo Co.....	168
DuMont Laboratories Inc., Allen B.....	170-171	Sola Electric Company.....	112
DX Radio Products Co.....	153	Solar Mfg. Co.....	32
Echophone Radio Company.....	60-61	Sprague Electric Co.....	42, 91
Eitel-McCullough, Inc.....	30-31	Standard Electrical Products Co.....	120
Electric Soldering Iron Co.....	84	Standard Transformer Corp.....	101
Electro-Voice Corporation.....	139	Stupakoff Ceramic & Mfg. Co.....	149
Electronic Laboratories, Inc.....	81	Sun Radio & Electronics Co.....	161
Freed Transformer Company.....	164	Superior Electric Co.....	140
General Electric Company.....	105-107, 113	Sylvania Electric.....	92-93
Gothard Manufacturing Co.....	165	Taylor Tubes.....	122
Gould-Moody Co., The.....	88	Telegraph Apparatus Co.....	118
Hall, R. C. & L. F.....	172	Terminal Radio Co.....	157
Hallcrafters Company, The.....	177-208	Thordarson Electric Mfg. Co.....	85
Hammarlund Manufacturing Co. Inc., The.....	34-41	Trimm, Inc.....	80
Harrison Radio Corporation.....	121	Turner Company, The.....	97
Harvey Radio Company.....	89	Ungar Electric Tools, Inc.....	160
Harvey-Wells Electronics, Inc.....	158-159	United Transformer Corp.....	69
Heintz & Kaufman, Ltd.....	109	Valpey Crystal Co.....	71
Henry Mfg.....	141	Vibroplex Company, The.....	79
Henry Radio Shops.....	83	Weller Mfg. Co.....	156
Hewlett-Packard Co.....	154-155	Wholesale Radio Laboratories.....	148
Howard Radio Company.....	123	Wiley & Sons, John.....	175
Hytron Radio & Electronics Corporation.....	72-73		

NATIONAL RADIO PRODUCTS 1946

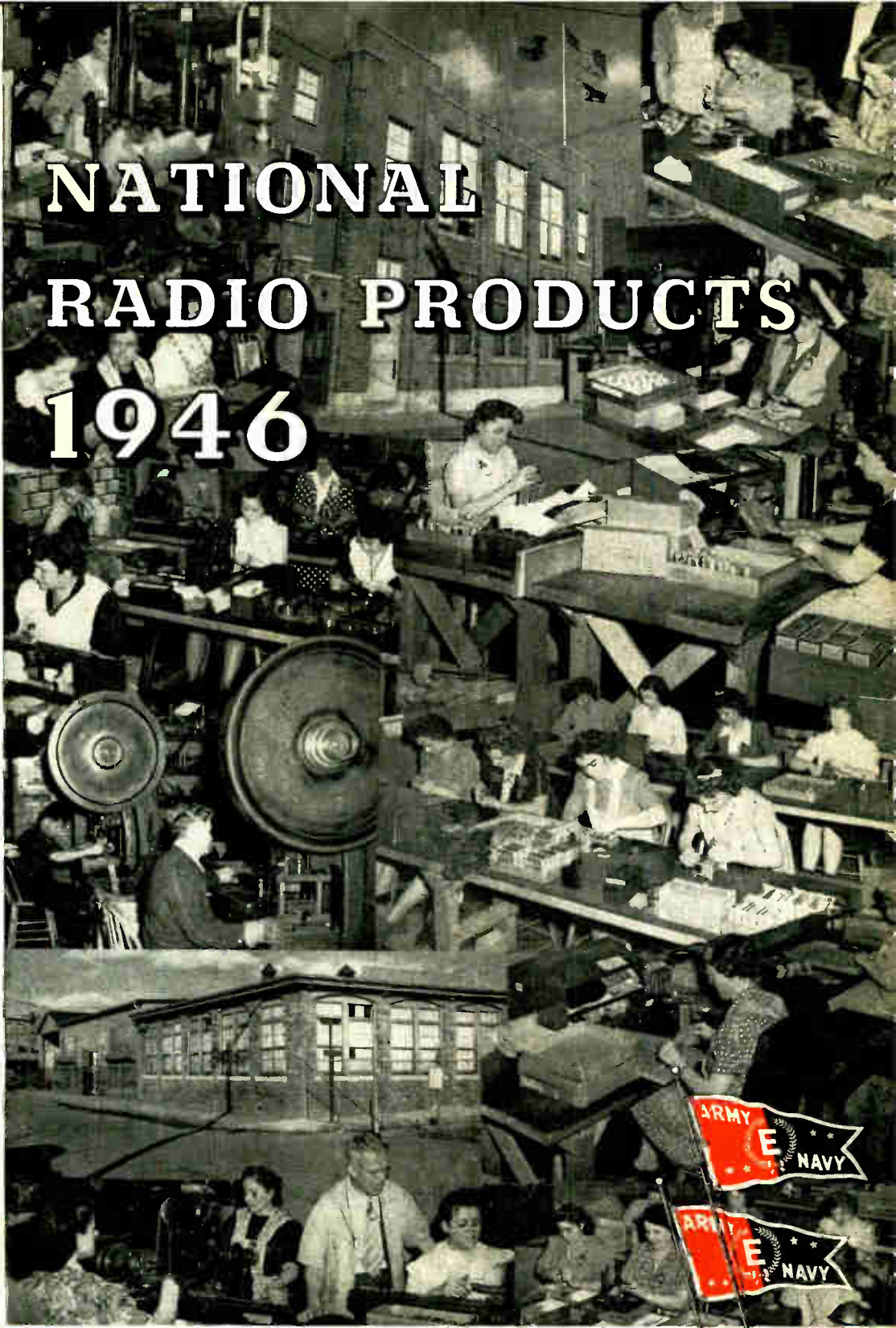

 **NATIONAL COMPANY, INC.**

MALDEN, MASSACHUSETTS, U.S.A.

World Radio History

MALDEN
MELROSE
★★★★

NATIONAL DIALS



The four-inch N Dial has an engine divided scale and vernier. The vernier is flush with the scale. The planetary drive has a ratio of 5 to 1, and is contained within the body of the dial. 2, 3, 4 or 5 scale. Fits 1/4" shaft. Specify scale.

N Dial List \$



"Velvet Vernier" Dial, Type B, has a compact variable ratio 6 to 1 minimum, 20 to 1 maximum drive that is smooth and trouble free. An illuminator is available. The case is black bakelite. 1 or 5 scale. 4" diam. Fits 1/4" shaft. Specify scale.

B Dial List \$
Illuminator, extra List \$

The original "Velvet Vernier" mechanism is now available in a metal skirted dial 3" in diameter. The planetary drive has a ratio of 5 to 1. It is available with 2, 3, 4, 5 or 6 scale and fits 1/4" shaft

AM Dial List \$



The BM Dial is a smaller version of the B Dial (described in the opposite column) for use where space is limited. The drive ratio is fixed. Although small in size, the BM Dial has the same smooth action as the larger units. 1 or 5 scale. 3" diam. Fits 1/4" shaft. Specify scale.


BM Dial List \$



INEXPENSIVE DIALS



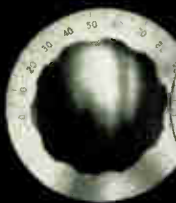TYPE R
List \$
1 5/8" Dia.
Etched Nickel
Silver



TYPE O
List \$
3 1/2" Dia.



TYPE K
List \$
3 1/2" Dia.

TYPE L
List \$
5" Dia.

TYPE M
List \$
5" Dia.

R Dial scale 3 only but marked 10-0; O, K, L, M scale 2. All fit 1/4" shafts.

FOR INDIVIDUAL CALIBRATING



For experimenters who "build their own" and des direct calibration. Fine for Freq. Monitors and ECC

- Dial bezel size 5" x 7 1/4"
- Five blank scales for direct calibration
- Employs Velvet Vernier Drive ● Easy to mount

TYPE ACN List \$

KNOB

HRK (Fits 1/4" shaft)
Black bakelite knob 2 3/8" diam.

List \$



HRP-P (Fits 1/4" shaft) List \$
Black bakelite knob 1 1/4" long and 1/2" wide. Equipped with pointer.

HRP List \$
The Type HRP knob has no pointer, but is otherwise the same as the knob above.

DIAL SCALES			
Scale	Divisions	Rotation	Direction of Condenser Rotation for Increase of dial reading
1	0-100.0	180°	Either
2	0-100	180°	Counter Clockwise
3	100.0	180°	Clockwise
4	150.0	97°	Clockwise
5	200.0	36°	Clockwise
6	0-150	270°	Counter Clockwise

ACCESSORIES

ODL List \$
A locking device which clamps the rim of O, K, L and M Dials. Brass, nickel plated.


ODD List \$
Vernier drive for O, K, L, M or other plain dials.

SB (Fits 1/4" shaft) List \$
A nickel plated brass bushing 1/2" diam.

RSL (Fits 1/4" shaft) List \$
Rotor Shaft Lock for TMA, TMC and similar condensers.



NATIONAL PRECISION CONDENSERS

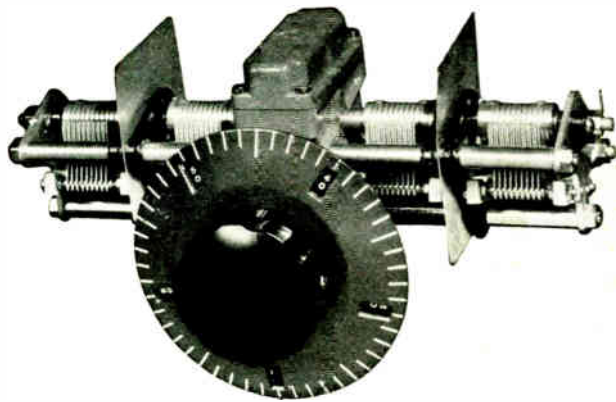

The Micrometer dial reads direct to one part in 500. Division lines are approximately $\frac{1}{4}$ " apart. The dial revolves ten times in covering the tuning range, and the numbers visible through the small windows change every revolution to give consecutive numbering by tens from 0 to 500. The condenser is of extremely rigid construction, with four bearings on the rotor shaft. The drive, at the mid-point of the rotor, is through an enclosed preloaded worm gear with 20 to 1 ratio. Each rotor is

individually insulated from the frame, and each has its own individual rotor contact. Stator insulation is Steatite. Plate shape is straight-line frequency when the frequency range is 2:1.


PW Condensers are available in 2, 3 or 4 sections, in either 160 or 225 mmf per section. Larger capacities cannot be supplied.

A single-section PW condenser with grounded rotor is supplied in capacities of 150, 200, 350 and 500 mmf, single spaced, and capacities up to 125 mmf, double spaced.

PW condensers are all with rotor shaft parallel to the panel.

- | | | | | | |
|-------|--------------------------|---------|-------|-----------------------------------|---------|
| PW-1R | Single section right | List \$ | PW-3R | Double section right; single left | List \$ |
| PW-1L | Single section left | List \$ | | | |
| PW-2R | Double section right | List \$ | PW-3L | Double section left; single right | List \$ |
| PW-2L | Double section left | List \$ | | | |
| PW-2S | Single section each side | List \$ | PW-4 | Double section each side | List \$ |

NPW MODELS with micrometer dial

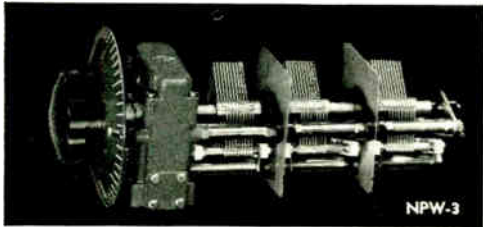


NPW-3. Three sections, each 225 mmf.
List \$

NPW-X. Three sections, each 25 mmf.
List \$

Both condensers are similar to PW models, except that rotor shaft is perpendicular to panel.

GEAR DRIVE UNITS with micrometer dial

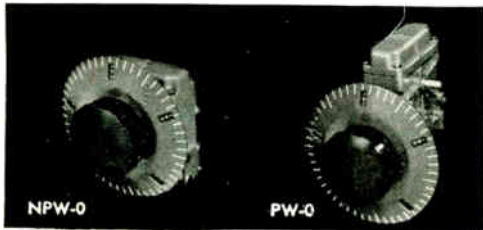

NPW-O List \$

Uses parts similar to the NPW condenser. Drive shaft perpendicular to panel. One TX-9 coupling supplied.


PW-O List \$

Uses parts similar to the PW condenser. Drive shaft parallel to panel. Two TX-9 couplings supplied.


MICROMETER DIAL

PW-D List \$

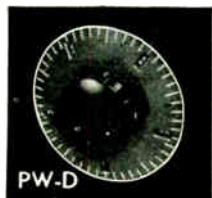Identical with the dials used on the condensers and drives above. It revolves ten times in covering the complete range and as there is no gear reduction unit furnished, the driven shaft will revolve ten times, also. The PW-D dial fits a shaft $\frac{3}{16}$ " in diameter.



NATIONAL RECEIVING CONDENSERS

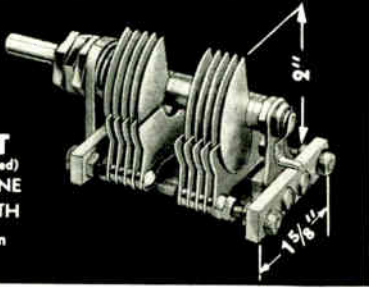


TYPE ST
(Type STD Illustrated)
STRAIGHT-LINE
WAVELENGTH
180° Rotation

Capacity	Minimum Capacity	No. of Plates	Air Gap	Length	Catalog Symbol	List	
SINGLE BEARING MODELS							
15 Mmf.	3 Mmf.	3	.018"	1 3/16"	STHS- 15	\$	
25	3.25	4	.018"	1 3/16"	STHS- 25		
50	3.5	7	.018"	1 3/16"	STHS- 50		
DOUBLE BEARING MODELS							
35 Mmf.	6 Mmf.	8	.026"	2 1/4"	ST- 35	\$	
50	7	11	.026"	2 1/4"	ST- 50		
75	8	15	.026"	2 1/4"	ST- 75		
100	9	20	.026"	2 1/4"	ST-100		
140	10	27	.026"	2 3/4"	ST-140		
150	10.5	29	.026"	2 3/4"	ST-150		
200	12.0	27	.018"	2 1/4"	STH-200		
250	13.5	32	.018"	2 3/4"	STH-250		
300	15.0	39	.018"	2 3/4"	STH-300		
335	17.0	43	.018"	2 3/4"	STH-335		
SPLIT STATOR DOUBLE BEARING MODELS							
50-50	5-5	11-11	.026"	2 3/4"	STD- 50		\$
100-100	5.5-5.5	14-14	.018"	2 3/4"	STDH-100		

NOTE — Type SS Condensers, having straight-line-capacity plates but otherwise similar to the Type ST, are available. Capacities and Prices same as Type ST.

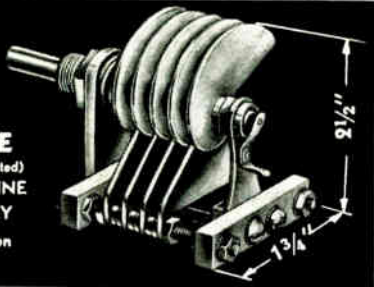The ST Type condenser has Straight-Line Wavelength plates. All double-bearing models have the front bearing insulated to prevent noise. On special order a shaft extension at each end is available, for ganging. On double-bearing single shaft models, the rotor contact is through a constant impedance pigtail. Isolantite insulation.



TYPE SE
(Type SEU Illustrated)
STRAIGHT-LINE
FREQUENCY
270° Rotation

Capacity	Minimum Capacity	No. of Plates	Air Gap	Length	Catalog Symbol	List
15 Mmf.	7 Mmf.	6	.055"	2 1/2"	SEU- 15	\$
20	7.5	8	.055"	2 1/2"	SEU- 20	
25	8	9	.055"	2 1/2"	SEU- 25	
50	9	11	.026"	2 1/2"	SE- 50	\$
75	10	15	.026"	2 1/2"	SE- 75	
100	11.5	20	.026"	2 1/2"	SE-100	
150	13	29	.026"	2 3/4"	SE-150	
200	12	27	.018"	2 1/4"	SEH-200	
250	14	32	.018"	2 3/4"	SEH-250	\$
300	16	39	.018"	2 3/4"	SEH-300	
335	17	43	.018"	2 3/4"	SEH-335	

TYPE SE — All models have two rotor bearings, the front bearing being insulated to prevent noise. A shaft extension at each end, for ganging, is available on special order. On models with single shaft extension, the rotor contact is through a constant impedance pigtail. The SEU models (illustrated) are suitable for high voltages as their plates are thick polished aluminum with rounded edges. Other SE condensers do not have polished edges on the plates. Isolantite insulation.



TYPE EM
STRAIGHT-LINE
CAPACITY
180° Rotation

Capacity	Minimum Capacity	No. of Plates	Length	Catalog Symbol	List
350 Mmf.	12 Mmf.	20	2 3/4"	EM-350	\$
500	16	29	4 3/8"	EM-500	
1000	22	56	6 3/4"	EM-1000	

TYPE EM — A general purpose condenser available in large sizes and having Straight-Line capacity plates. They are similar in construction to the TMC Transmitting condenser, and have high efficiency and rugged frames. Insulation is Isolantite, and Peak Voltage Rating is 1000 volts.

NATIONAL MINIATURE CONDENSERS

PSR — See table —

Type PSR condensers are small, compact, low-loss units with silver plating on conducting parts. Their soldered construction makes them particularly suitable for applications where vibration is present. Adjustment is made with a screw driver. Steatite base.

PSE — See table —

Type PSE condensers are similar to Type PSR, but are provided with a 1/4" diameter shaft extension at each end.

PSL — See table —

Type PSL condensers are similar to Type PSR, but are provided with a rotor shaft lock, so that the rotor can be clamped at any setting.

MSR, MSE, MSL —

See table — Condensers of the MS series are similar in appearance to the PS series described above, but they differ in making use of plates which are like those of the UM condenser. This and other small changes result in a more robust and rigid assembly. Other details of the MSR, MSE, and MSL are the same as the PSR, PSE, and PSL respectively.



Capacity	Catalog Symbol			List
25 mmf.	PSR-25	PSE-25	PSL-25	\$
50	PSR-50	PSE-50	PSL-50	
75	PSR-75	PSE-75	PSL-75	
100	PSR-100	PSE-100	PSL-100	
140	PSR-140	PSE-140	PSL-140	

Capacity	Catalog Symbol			List
25 mmf.	MSR-25	MSE-25	MSL-25	\$
50	MSR-50	MSE-50	MSL-50	
75	MSR-75	MSE-75	MSL-75	
100	MSR-100	MSE-100	MSL-100	

Capacity	Minimum Capacity	No. of Plates	Air Gap	Catalog Symbol	List
15 mmf.	1.5	6	.017"	UM-15	\$
35	2.5	12	.017"	UM-35	
50	3	16	.017"	UM-50	
75	3.5	22	.017"	UM-75	
100	4.5	28	.017"	UM-100	
140	5.5	34	.017"	UM-140	
25	3.4	14	.042"	UMA-25	

BALANCED STATOR MODEL					
25	2	4-4-4	.017"	UMB-25	\$

M-30 List \$

Type M-30 is a small adjustable mica condenser with a maximum capacity of 30 mmf. Dimensions 1 3/16" x 9/16" x 1/2". Isolantite base.

W-75, 75 mmf. List \$

W-100, 100 mmf. List \$

Small padding condensers having very low temperature coefficient. Mounted in an aluminum shield 1 1/4" in diameter. The UM CONDENSER is designed for ultra high frequency use and is small enough for convenient mounting in PB-10 and RO shield cans. They are particularly useful for tuning receivers, transmitters, and exciters. Shaft extensions at each end of the rotor permit easy ganging when used with one of our flexible couplings. The UMB-25 Condenser is a balanced stator model, two stators act on a single rotor. The UM can be mounted by the angle foot supplied or by bolts and spacers. See table for sizes.

Dimensions: Base 1" x 2 1/4", Mounting hole: 5/8" x 1 3/32", Axial length 2 1/8" overall.

Plates: Straight line capacity, 180° rotation.

NATIONAL NEUTRALIZING CONDENSERS

NC-600U List \$

With standoff insulator

NC-600 List \$

Without insulator

For neutralizing low power beam tubes requiring from .5 to 4 mmf., and 1500 max. total volts such as the 6L6. The NC-600U is supplied with a GS-10 standoff insulator screwed on one end, which may be removed for pigtail mounting.

STN List \$

The Type STN has a maximum capacity of 18 mmf. (3000 V), making it suitable for such tubes as the 10 and 45. It is supplied with two standoff insulators.

NC-800 List \$

The NC-800 disk-type neutralizing condenser is suitable for the RCA-800, 35T, HK-54 and similar tubes. It is equipped with a micrometer thimble and clamp. The chart below gives capacity and air gap for different settings.

NC-75 List \$

For 75T, 808, 811, 812 & similar tubes.



NC-150 List \$

For HK354, RK36, 300T, 852, etc.


NC-500 List \$

For WE-251, 450TH, 450TL, 750TL, etc.

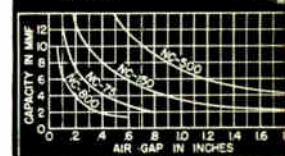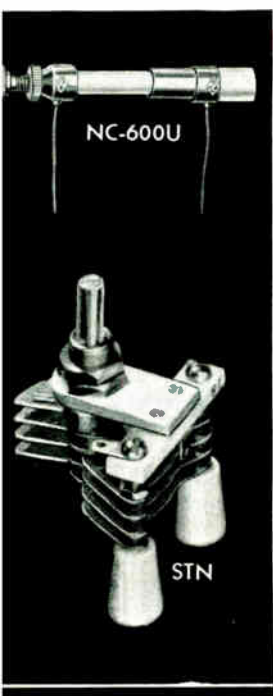These larger disk type neutralizing condensers are for the higher powered tubes. Disks are aluminum, insulation steatite.




NATIONAL TRANSMITTING CONDENSERS

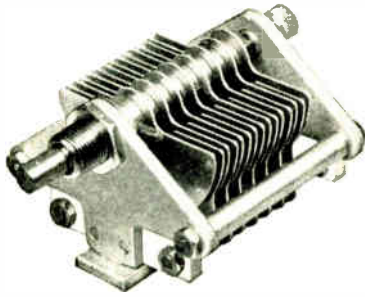

TYPE TMS

is a condenser designed for transmitter use in low power stages. It is compact, rigid, and dependable. Provision has been made for mounting either on the panel, on the chassis, or on two stand-off insulators. Insulation is Isolantite. Voltage ratings listed are conservative.

Capacity	Minimum Capacity	Length	Air Gap	Peak Voltage	No. of Plates	Catalog Symbol	List Price
SINGLE STATOR MODELS							
100 Mmf.	9.5	3"	.026"	1000v.	9	TMS-100	
150	11	3"	.026"	1000v.	14	TMS-150	
250	13.5	3"	.026"	1000v.	22	TMS-250	
300	15	3"	.026"	1000v.	27	TMS-300	
35	8	3"	.065"	2000v.	7	TMSA-35	
50	11	3"	.065"	2000v.	11	TMSA-50	
DOUBLE STATOR MODELS							
50-50 Mmf.	6-6	3"	.026"	1000v.	5-5	TMS-50D	
100-100	7-7	3"	.026"	1000v.	9-9	TMS-100D	
50-50	10.5-10.5	3"	.065"	2000v.	11-11	TMSA-50D	

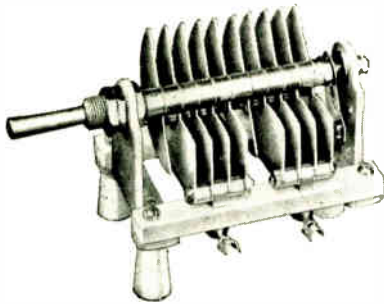

TYPE TMH


features very compact construction, excellent power factor, and aluminum plates .040" thick with polished edges. It mounts on the panel or on removable stand-off insulators. Isolantite insulators have long leakage path. Stand-offs included in listed price.

Capacity	Minimum Capacity	Length	Air Gap	Peak Voltage	No. of Plates	Catalog Symbol	List
SINGLE STATOR MODELS							
50 Mmf.	9	3 $\frac{3}{4}$ "	.085"	3500v.	15	TMH-50	
75	11	3 $\frac{3}{4}$ "	.085"	3500v.	19	TMH-75	
100	12.5	5 $\frac{1}{8}$ "	.085"	3500v.	25	TMH-100	
150	18	6 $\frac{1}{2}$ "	.085"	3500v.	37	TMH-150	
35	11	5 $\frac{1}{8}$ "	.180"	6500v.	17	TMH-35A	
DOUBLE STATOR MODELS							
35-35 Mmf.	6-6	3 $\frac{3}{4}$ "	.085"	3500v.	9-9	TMH-35D	
50-50	8-8	5 $\frac{1}{8}$ "	.085"	3500v.	13-13	TMH-50D	
75-75	11-11	6 $\frac{1}{2}$ "	.085"	3500v.	19-19	TMH-75D	

NATIONAL TRANSMITTING CONDENSERS

TYPE TMK

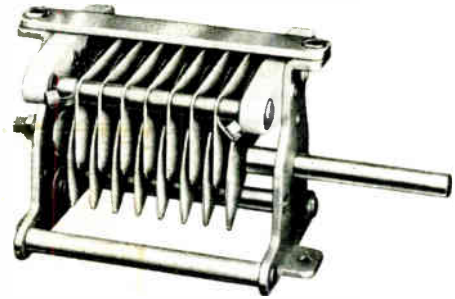
is a new condenser for exciters and low power transmitters. Special provision has been made for mounting AR-16 coils in a swivel plug-in mount on either the top or rear of the condenser, (see page 10). For panel or stand-off mounting. Isolantite insulation.



Capacity	Minimum Capacity	Length	Air Gap	Peak Voltage	No. of Plates	Catalog Symbol	List Price
SINGLE STATOR MODELS							
35 Mmf.	7.5	2 ⁷ / ₈ "	.047"	1500v.	7	TMK-35	
50	8	2 ³ / ₈ "	.047"	1500v.	9	TMK-50	
75	9	2 ¹ / ₂ "	.047"	1500v.	13	TMK-75	
100	10	3"	.047"	1500v.	17	TMK-100	
150	10.5	3 ⁵ / ₈ "	.047"	1500v.	25	TMK-150	
200	11	4 ¹ / ₄ "	.047"	1500v.	33	TMK-200	
250	11.5	4 ⁷ / ₈ "	.047"	1500v.	41	TMK-250	
DOUBLE STATOR MODELS							
35-35 Mmf.	7.5-7.5	3"	.047"	1500v.	7-7	TMK-35D	
50-50	8-8	3 ⁵ / ₈ "	.047"	1500v.	9-9	TMK-50D	
100-100	10-10	4 ¹ / ₄ "	.047"	1500v.	17-17	TMK-100D	
Swivel Mounting Hardware for AR 16 Coils						SMH	


TYPE TMC

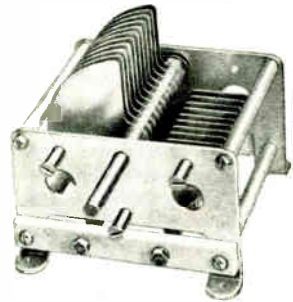is designed for use in the power stages of transmitters where peak voltages do not exceed 3000. The frame is extremely rigid and arranged for mounting on panel, chassis or stand-off insulators. The plates are aluminum with buffed edges. Insulation is Isolantite. The stator in the split stator models is supported at both ends.



Capacity	Minimum Capacity	Length	Air Gap	Peak Voltage	No. of Plates	Catalog Symbol	List Price
SINGLE STATOR MODELS							
50 Mmf.	10	3"	.077"	3000v.	7	TMC-50	
100	13	3 ¹ / ₂ "	.077"	3000v.	13	TMC-100	
150	17	4 ⁵ / ₈ "	.077"	3000v.	21	TMC-150	
250	23	6"	.077"	3000v.	32	TMC-250	
300	25	6 ³ / ₄ "	.077"	3000v.	39	TMC-300	
DOUBLE STATOR MODELS							
50-50 Mmf.	9-9	4 ⁵ / ₈ "	.077"	3000v.	7-7	TMC-50D	
100-100	11-11	6 ³ / ₄ "	.077"	3000v.	13-13	TMC-100D	
200-200	18.5-18.5	9 ¹ / ₄ "	.077"	3000v.	25-25	TMC-200D	


NATIONAL TRANSMITTING CONDENSERS

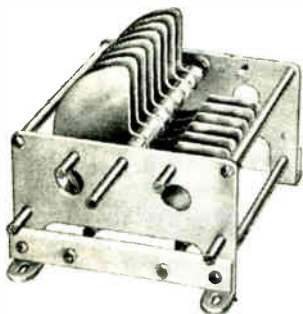

TYPE TMA

is a larger model of the popular TMC. The frame is extremely rigid and arranged for mounting on panel, chassis or stand-off insulators. The plates are of heavy aluminum with rounded and buffed edges. Insulation is Isolantite, located outside of the concentrated field.

Capacity	Minimum Capacity	Length	Air Gap	Peak Voltage	No. of Plates	Catalog Symbol	List Price
SINGLE STATOR MODELS							
300 Mmf.	19.5	4 $\frac{3}{8}$ "	.077"	3000v.	23	TMA-300	
50	15	4 $\frac{1}{2}$ "	.171"	6000v.	7	TMA-50A	
100	19.5	6 $\frac{1}{8}$ "	.171"	6000v.	15	TMA-100A	
150	22.5	6 $\frac{1}{2}$ "	.171"	6000v.	21	TMA-150A	
230	33	9 $\frac{1}{4}$ "	.171"	6000v.	33	TMA-230A	
100	30	9 $\frac{1}{4}$ "	.265"	9000v.	23	TMA-100B	
150	40.5	12 $\frac{1}{2}$ "	.265"	9000v.	33	TMA-150B	
50	21	7 $\frac{1}{8}$ "	.359"	12000v.	13	TMA-50C	
100	37.5	12 $\frac{1}{8}$ "	.359"	12000v.	25	TMA-100C	
DOUBLE STATOR MODELS							
200-200 Mmf.	15-15	6 $\frac{3}{8}$ "	.077"	3000v.	16-16	TMA-200D	
50-50	12.5-12.5	6 $\frac{1}{8}$ "	.171"	6000v.	8-8	TMA-50DA	
100-100	17-17	9 $\frac{1}{8}$ "	.171"	6000v.	14-14	TMA-100DA	
60-60	19.5-19.5	12 $\frac{1}{8}$ "	.265"	9000v.	15-15	TMA-60DB	
40-40	18-18	12 $\frac{1}{8}$ "	.359"	12000v.	11-11	TMA-40DC	

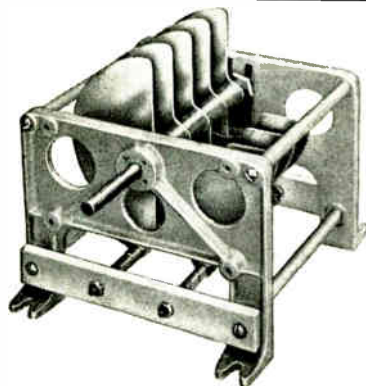


TYPE TML

condenser is a 1 KW job throughout. Isolantite insulators, specially treated against moisture absorption, prevent flashovers. A large self-cleaning rotor contact provides high current capacity. Thick capacitor plates, with accurately rounded and polished edges, provide high voltage ratings. Sturdy cast aluminum end frames and dural tie bars permit an unusually rigid structure. Precision end bearings insure smooth turning and permanent alignment of the rotor. End frames are arranged for panel, chassis or stand-off mountings.

Capacity	Minimum Capacity	Length	Air Gap	Peak Voltage	No. of Plates	Catalog Symbol	List Price
SINGLE STATOR MODELS							
75 Mmf.	25	18 $\frac{1}{8}$ "	.719"	20,000v.	17	TML-75E	
150	60	18 $\frac{1}{2}$ "	.469"	15,000v.	27	TML-150D	
100	45	13 $\frac{3}{8}$ "	.469"	15,000v.	19	TML-100D	
50	22	8 $\frac{1}{2}$ "	.469"	15,000v.	9	TML-50D	
245	54	18 $\frac{1}{8}$ "	.344"	10,000v.	35	TML-245B+	
150	45	13 $\frac{3}{8}$ "	.344"	10,000v.	21	TML-150B+	
100	32	10 $\frac{3}{8}$ "	.344"	10,000v.	15	TML-100B+	
75	23.5	8 $\frac{1}{2}$ "	.344"	10,000v.	11	TML-75B+	
500	55	18 $\frac{1}{2}$ "	.219"	7,500v.	49	TML-500A+	
350	45	13 $\frac{3}{8}$ "	.219"	7,500v.	33	TML-350A+	
250	35	10 $\frac{3}{8}$ "	.219"	7,500v.	25	TML-250A+	
DOUBLE STATOR MODELS							
30-30 Mmf.	12-12	18 $\frac{1}{8}$ "	.719"	20,000v.	7-7	TML-30DE	
60-60	26-26	18 $\frac{1}{2}$ "	.469"	15,000v.	11-11	TML-60DD	
100-100	27-27	18 $\frac{1}{2}$ "	.344"	10,000v.	15-15	TML-100DB+	
60-60	20-20	13 $\frac{3}{8}$ "	.344"	10,000v.	9-9	TML-60DB+	
200-200	30-30	18 $\frac{1}{2}$ "	.219"	7,500v.	21-21	TML-200DA+	
100-100	17-17	10 $\frac{3}{8}$ "	.219"	7,500v.	11-11	TML-100DA+	

NATIONAL RF CHOKES

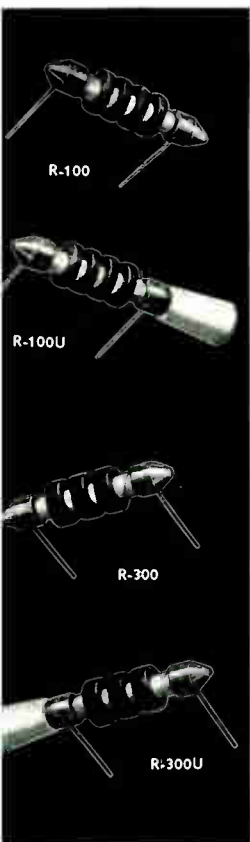

R-100 List \$

Without standoff insulator

R-100U List \$

With standoff insulator

R.F. chokes R-100 and R-100U are identical electrically, but the latter is provided with a removable standoff insulator screwed on one end. Both have Isolantite insulation and both have a continuous universal winding in four sections. Inductance $2\frac{1}{2}$ m.h.; distributed capacity 1 mmf.; DC resistance 50 ohms; current rating 125 ma.

R-300 List \$

Without insulator

R-300U List \$

With insulator

R.F. chokes R-300 and R-300U are similar in size to R-100U but have higher current capacity. The R-300U is provided with a removable stand-off insulator screwed on one end. Inductance 1 m.h.; distributed capacity 1 mf.; DC resistance 10 ohms; current rating 300 ma.

R.F. chokes are available in a variety of inductance values, ranging from 6 microhenries to 10 millihenries, in addition to those shown above. Various mounting arrangements are also available. Full information will be furnished on request.

R-152 List \$

For the 80 and 160 meter bands. Inductance 4 m.h., DC resistance 10 ohms, DC current 600 ma. Coils honey-comb wound on Isolantite core.

R-154 List \$

R-154U List \$

For the 20, 40 and 80 meter bands. Inductance 1 m.h., DC resistance 6 ohms. DC current 600 ma. Coils honey-comb wound on Isolantite core. The R-154U does not have the third mounting foot and the small insulator, but is otherwise the same as R-154. See illustration.


R-175 List \$

The R-175 Choke is suitable for parallel-feed as well as series-feed in transmitters with plate supply up to 3000 volts modulated or 4000 volts unmodulated. Unlike conventional chokes, the reactance of the R-175 is high throughout the 10 and 20 meter bands as well as the 40, 80 and 160 meter bands. Inductance $225 \mu\text{h}$, distributed capacity 0.6 mmf., DC resistance 6 ohms, DC current 800 ma., voltage breakdown to base 12,500 volts.



National has manufactured a great many sizes and styles of chokes not shown above, during the war. A complete line of chokes will be available in the near future but full technical data had not been prepared at the time this edition of the A.R.R.L. Handbook went to press. Complete information will be found in later catalogs or can be obtained by writing us direct.

NATIONAL SHAFT COUPLINGS

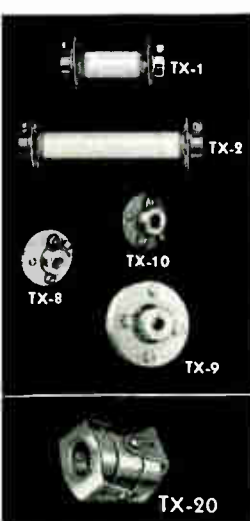

TX-1, Leakage path 1" List \$

TX-2, Leakage path $2\frac{1}{2}$ " List \$

Flexible couplings with glazed Isolantite insulation which fit $\frac{1}{4}$ " shafts.

TX-8 List \$

A non-flexible rigid coupling with Isolantite insulation. 1" diam. Fits $\frac{1}{4}$ " shaft.

TX-9 List \$

This small insulated flexible coupling provides high electrical efficiency when used to isolate circuits. Insulation is Steatite. $1\frac{1}{8}$ " diam. Fits $\frac{1}{4}$ " shaft.

TX-20 List \$

A small insulated flexible coupling of the Hooke's joint type

which will accommodate angular misalignment up to five degrees as well as $\frac{1}{64}$ " transverse misalignment between the shafts.

TX-10 List \$

A very compact insulated coupling free from backlash. Insulation is canvas Bakelite. $1\frac{1}{8}$ " diam. Fits $\frac{1}{4}$ " shaft.


TX-11 List \$

The flexible shaft of this coupling connects shafts at angles up to 90 degrees, and eliminates misalignment problems. Fits $\frac{1}{4}$ " shafts. Length $4\frac{1}{4}$ ".

TX-12, Length $4\frac{5}{8}$ " List \$

TX-13, Length $7\frac{1}{8}$ " List \$

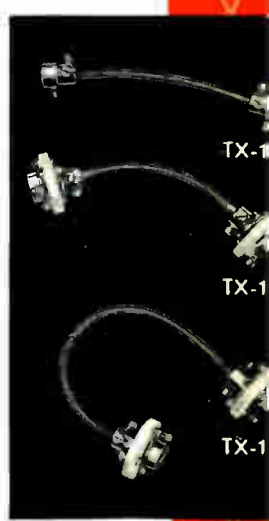These couplings use flexible shafting like the TX-11 above, but are also provided with Isolantite insulators at each end.





XR-14A

XR-10A

PB-15

XB-15

TRANSMITTER COIL FORMS

The Transmitter Coil Forms and Mounting are designed as a group, and mount conveniently on the bars of a TMA condenser. The larger coil form, Type XR-14A, has a winding diameter of 5", a winding length of 3 3/4" (30 turns total) and is intended for the 80 meter band. The smaller form, Type XR-10A, has a winding length of 3 3/4" and a winding diameter of 2 1/2" (26 turns total). It is intended for the 20 and 40 meter bands.


Either coil form fits the PB-15 plug. For higher frequencies, the plug may be used with a self-supporting coil of copper tubing. The XB-15 Socket may be mounted on breadboards or chassis, as well as on the TMA Condenser.

SINGLE UNITS

- XR-10A, Coil Form only List \$
- XR-14A, Coil Form only List \$
- PB-15, Plug only List \$
- XB-15, Socket only List \$

ASSEMBLIES

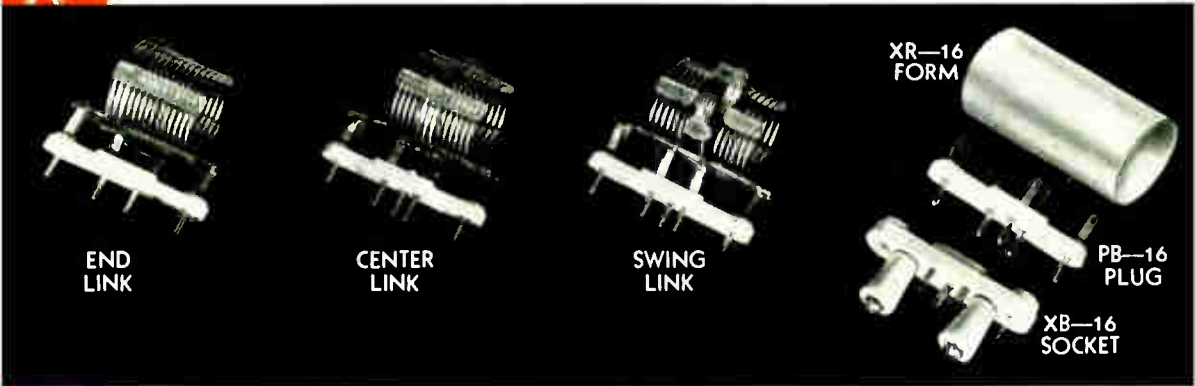- UR-10A, Assembly (including small Coil Form, Plug and Socket) List \$
- UR-14A, Assembly (including large Coil Form, Plug and Socket) List \$



END LINK

CENTER LINK

SWING LINK

XR-16 FORM

PB-16 PLUG

XB-16 SOCKET

EXCITER COILS AND FORMS — TYPE AR-16 (Air Spaced)

These air-spaced coils are suitable for use in stages where the plate input does not exceed 50 watts and are available in the sizes tabulated below. Capacities listed will resonate the coils at the low frequency end of the band and include all stray circuit capacities. All have separate link coupling coils and all fit the PB-16 Plug and XB-16 Socket.

The XR-16 Coil Form also fits the PB-16 Plug and XB-16 Socket. It has a winding diameter of 1 1/4" and a winding length of 1 3/4".


- XR-16, Coil Form only List \$
- PB-16, Plug-in Base only List \$
- XB-16, Plug-in Socket only List \$
- AR-16, Coils — Any type (see table). Include PB-16 Plug as illustrated Each, List \$

Exciter coil on TMK condenser


Band	End Link	Cap Mmf	Center Link	Cap Mmf	Swinging Link	Cap Mmf
5 meter	AR16-5E	20	AR16-5C	20		
10 meter	AR16-10E	20	AR16-10C	20	AR16-10S	25
20 meter	AR16-20E	26	AR16-20C	26	AR16-20S	40
40 meter	AR16-40E	33	AR16-40C	33	AR16-40S	55
80 meter	AR16-80E	37	AR16-80C	37	AR16-80S	60
160 meter	AR16-160E	65	AR16-160C	65		

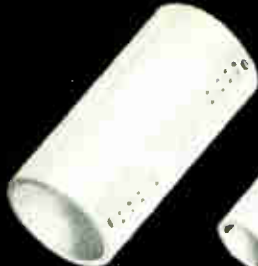When final allocation of the amateur bands has been made the exciter coils will be redesigned to provide coverage.






XR-13

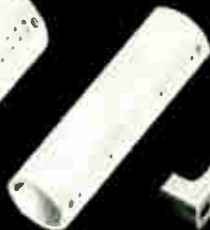


XR-13A



PB-5

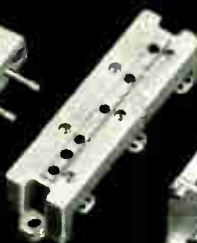

XB-5

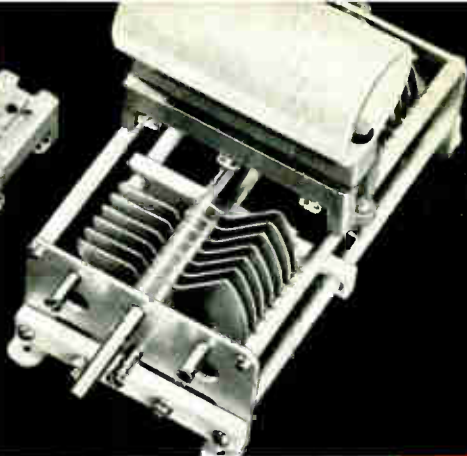

BUFFER COIL FORMS

National Buffer Coil Forms are designed to mount directly on the tie bars of a TMC condenser using the PB-5 Plug and XB-5 Socket. Plug and Socket are of molded R-39.

The two coil forms are of Isolantite, left unglazed to provide a tooth for coil dope. The larger form, Type XR-13, is 1 3/4" in diameter and has a winding length of 2 3/4". The smaller form, Type XR-13A, is 1" in diameter and provides a winding length of 2 3/4". Both forms have holes for mounting and for leads.

SINGLE UNITS

- XR-13, Coil Form only List \$
- XR-13A, Coil Form only List \$
- PB-5, Plug only List \$
- XB-5, Socket only List \$

ASSEMBLIES

- UR-13A, Assembly (including small Coil Form, Plug and Socket) List \$
- UR-13, Assembly (including large Coil Form, Plug and Socket) List \$

FIXED-TUNED EXCITER TANK



PLUG-IN BASE AND SHIELD



SPP-9



SPP-3



12



24



8

FIXED TUNED EXCITER TANK

Similar in general construction to National I.F. transformers, this unit has two 25 mmf., 2000 volt air condensers and an unwound XR-2 coil form.

- FXT, without plug-in base List \$
- FXTB-5, with 5 prong base List \$
- FXTB-6, with 6 prong base List \$

PLUG-IN BASE AND SHIELD

The low-loss R-39 base is ideal for mounting condensers and coils when it is desirable to have them shielded and easily removable. Shield can is 2" x 2 3/8" x 4 1/8".

- PB-10-5, (5 Prong Base & Shield) List \$
- PB-10-6, (6 Prong Base & Shield) List \$
- PB-10A-5, (5 Prong Base only) List \$
- PB-10A-6, (6 Prong Base only) List \$

SAFETY GRID AND PLATE CAPS

National Safety Grid and Plate Caps have a ceramic body which offers protection against accidental contact with high voltage caps on tubes.

- SPP-9 List \$
- Ceramic insulation. Fits 9'16" diameter.
- SPP-3 List \$
- Ceramic insulation. Fits 3/8" diameter.


GRID AND PLATE GRIPS

National Grid and Plate Grips provide a secure and positive contact with the tube cap and yet are released easily by a slight pressure on the ear.

- Type 12, for 9/16" Caps List \$
- Type 24, for 3/8" Caps List \$
- Type 8, for 1/4" Caps List \$



NATIONAL PARTS

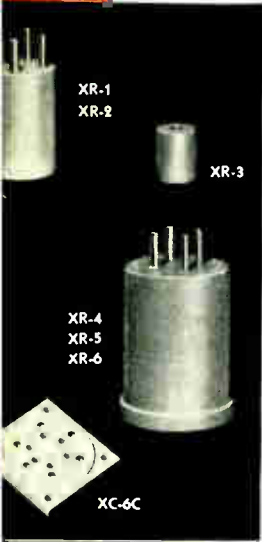

COIL FORMS
XR-1, Four prong, List \$
XR-2, without prongs List \$

Molded of R-39, permitting them to be grooved and drilled. Coil form diameter 1", length 1 1/2".

XR-3 List \$
 Molded of R-39. Diameter 3/16", length 3/4". Without prongs.

XR-4, Four prong, List \$
XR-5, Five prong, List \$
XR-6, Six prong, List \$


Molded of R-39, permitting them to be grooved and drilled. Coil form diameter 1 1/8", length 2 1/4". A special socket is required for the six-prong form.

XC6C, Special six-prong socket for XR-6 Coil Form, List \$



IMPEDANCE COUPLER
S-101 List \$

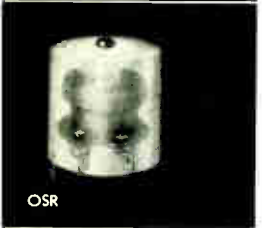A plate choke, coupling condenser and grid leak sealed in one case, for coupling the output of a regenerative detector to an audio stage. Used in SW-3U.



OSCILLATOR COIL
OSR List \$

A shielded oscillator coil which tunes to 100 KC with .00041 Mfd. Two separate inductances, closely coupled. Excellent for interruption-frequency oscillator in super-regenerative receivers.



H. F. COIL FORMS

Symbol	Outside Diameter	Length	List
PRC-1	3/16"	3/8"	\$
PRC-2	1/8"	1/2"	
PRC-3	3/8"	3/4"	
PRD-1	1/2"	1/2"	\$
PRD-2	1/2"	1"	
PRE-1	3/16"	3/4"	\$
PRE-2	3/16"	1"	
PRE-3	3/16"	2"	
PRF-1	3/4"	3/4"	\$
PRF-2	3/4"	1 1/4"	

COIL SHIELDS
RZ, coil shield List \$
 1 3/8" square x 4" high.
RS, coil shield List \$
 1 1/16" x 1 7/8" x 3 1/2" high.
RO, coil shield List \$
 2" x 2 3/8" x 4 1/8" high.
B-30, coil shield List \$
 3" dia. x 3 3/4" high without mounting base.



National coil shields are formed from a single piece of pure aluminum. They are mechanically strong and have ample thickness to mount small parts on the walls.

The RZ, RS and RO coil shields are supplied with two threaded studs extending downward from the open end for attaching to the chassis. The B-30 coil shield is supplied with an aluminum base which not only provides a convenient mounting, but also completes the coil enclosure.

JACK SHIELD
JS-1, Jack shield List \$
 For shielding small standard jacks mounted behind a panel, or on the ends of extension cords.

NATIONAL CABINETS

The National Cabinets listed below are the same as those used in National Receivers, except that they are supplied in blank form. They are made of heavy gauge steel, and the paint is unusually well bonded to the metal. Sub-bases and bottom covers are included in the price.

Type	Width	Height	Depth	List Price
Type C-SW3	9 3/4"	7"	9"	
Type C-NC100	17 1/4"	8 3/4"	11 1/4"	
Type C-HRO	16 3/4"	8 3/4"	10"	
Type C-One-Ten	11"	7"	7 1/4"	
Type C-SRR	7 1/2"	7"	7 1/2"	





CHART FRAME

The National Chart Frame is blanked from one piece of metal, and includes a celluloid sheet to cover the chart. Size $2\frac{1}{4}'' \times 3\frac{1}{4}''$, with sides $\frac{1}{4}''$ wide.

Type CFA List \$

COIL DOPE

CD-1, $\frac{1}{4}$ pint can List \$
Liquid Polystyrene Cement — is ideal for windings as it will not spoil the properties of the best coil form.

TOUCH-UP PAINT

A high quality air-drying paint that may be applied with a brush. It is especially suited to touching up places on radio equipment where the paint may have become marred through abrasion.

CP-1, gray List \$
CP-2, black List \$

SPEAKER CABINETS

NDC-8 for 8'' speaker List \$
NDC-10 for 10'' speaker List \$
NDC-2 for 10'' speaker List \$

These metal speaker cabinets are acoustically correct. They are lined with acoustic felt, and are of welded construction to eliminate rattles. Finish is black wrinkle on NDC-8 and NDC-10. NDC-2 is finished in two-tone gray to match the NC-200 TG receiver.

National Oscilloscopes have power supply and input controls built in. A panel switch permits use of the built-in 60-cycle sweep or external audio sweep for securing the familiar trapezoid pattern for modulation measurements.

CRM, less tubes List \$
1'' screen, using RCA-913 and 6X5 rectifier. Table model, $4\frac{1}{8}'' \times 6\frac{1}{8}'' \times 8''$.

CRR, less tubes List \$
9'' screen, using RCA-902 and 6X5 rectifier. Relay rack mounting.

I. F. TRANSFORMERS

IFC, Transformer, air core List \$
IFCO, Oscillator, air core List \$

Air dielectric condensers isolated from each other by an aluminum shield. Litz wound coils on a moisture proofed ceramic base. Shield can $4\frac{1}{8}'' \times 2\frac{3}{8}'' \times 2''$. Available for either 175 KC or 450-550 KC. Specify frequency.

IFD, Diode Transformer, air core List \$

Tuned primary and untuned, closely-coupled secondary for full-wave diode rectifiers. For noise silencing circuits, etc. 450-550 KC. air core only.

IFE, Transformer List \$
Same as IFC but iron core, 450-550 KC only.

IFG, IF Transformer List \$
IFH, Discriminator List \$

High frequency IF transformers, similar in construction to the IFC above. They are intended for FM receivers and others requiring a high IF frequency. Frequency is 3 MC. When definite assignment of the bands has been made these transformers will be available in a frequency which gives the minimum images in the FM and television bands.

IFJ, with variable coupling List \$
IFK, with fixed coupling List \$

15 MC IF transformers suitable for ultra high frequency superheterodynes. They are made in two models, with and without variable coupling

National TRF units are designed as a single channel high fidelity TRF receiver for reception in the broadcast band. Each RF transformer is similar in construction to the IFC transformer above and is tuned both primary and secondary. The coupling is adjustable to include 10 KC with less than 1 db variation in the audio range. Sensitivity is adjustable from 5 microvolts to 1 volt. Three models cover ranges of 540-875, 740-1230, and 1100-1700 KC.

DLT, RF Transformer, set of four required. List, each \$

IFC

IFD

IFK

DLT
SET OF
FOUR
REQUIRED

CHART FRAME

COIL DOPE

TOUCH-UP PAINT

DC-8
DC-10

DC-2

NATIONAL OSCILLOSCOPES




CRM



CRR


NATIONAL LOW-LOSS SOCKETS AND INSULATORS

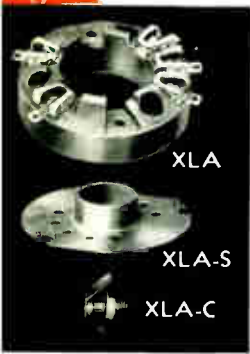

XL A List \$
 A low-loss socket for the 6F4 and 950 series acorn tubes for frequencies as high as 600 MC. Conventional by-pass condensers may be compactly mounted between the contact terminals and the chassis. Low contact resistance, short and direct leads and low and constant inductance are features of the design.

XL A-S List \$
 An internal shield fitting the XL A socket and suitable for tubes such as the 956.

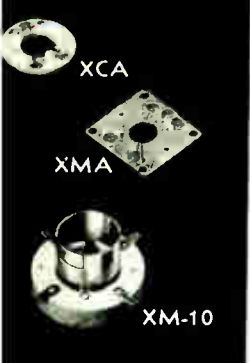
XL A-C List \$
 This miniature by-pass condenser may be mounted inside the socket, directly below the contact.



XC A List \$
 A low-loss socket for acorn triodes.

XMA List \$
 For pentode acorn tubes, this socket has built-in by-pass condensers. The base is a copper plate.

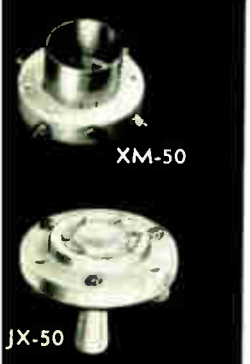XM-10 List \$
 A heavy duty metal shell socket for tubes having the UX base.



XM-50 List \$
 A heavy duty metal shell socket for tubes having the Jumbo 4-pin base ("fifty waiters").

JX-50 List \$
 Without Standoff Insulators

JX-50S List \$
 With Standoff Insulators
 A low-loss wafer socket for the 813 and other tubes having the Giant 7-pin base.



HX-100 List \$
HX-100S List \$
 A low-loss wafer socket suitable for the EIMAC-4-125-A, 4-250-A and other tubes using the Giant 5-pin base.

- GS-1, 1/4" x 1 1/8" List \$
- GS-2, 1/4" x 2 3/8" List \$
- GS-3, 1/4" x 2 1/8" List \$
- GS-4, 3/4" x 4 1/8" List \$
- GS-4A, 3/4" x 6 7/8" List \$

Cylindrical low-loss steatite standoff insulators with nickel plated caps and bases.

GSJ, (not illustrated) List \$
 A special nickel plated jack top threaded to fit the 3/4" diameter insulators GS-3, GS-4 & GS-4A.

- GS-5, 1 1/4" List, each \$
- GS-6, 2" List, each \$
- GS-7, 3" List, each \$
- GS-10, 3/4", package of 10 List \$

These cone type standoff insulators are of low-loss steatite. They have a tapped hole at each end for mounting.

- GS-8, with terminal List \$
- GS-9, with jack List \$

These low-loss steatite standoff insulators are also useful as lead-through bushings.




XC Series Sockets

- XC-4
- XC-5
- XC-6
- XC-7S
- XC-7L
- XC-8

- List \$
- List \$
- List \$
- List \$
- List \$
- List \$

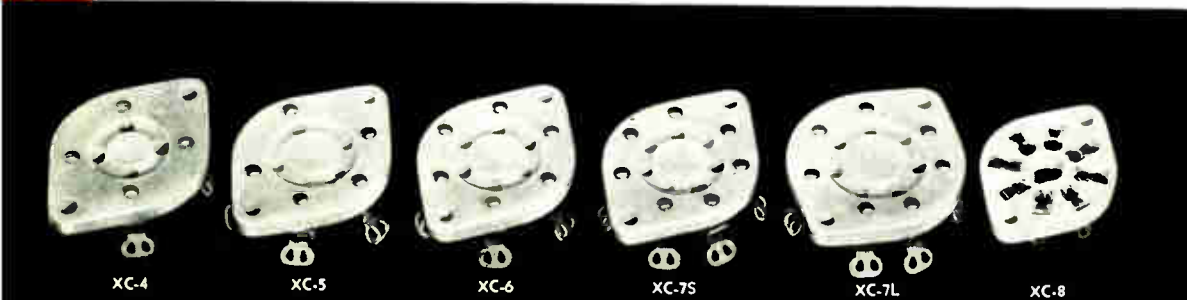
National wafer sockets have exceptionally good contacts with high current capacity together with low loss Isolantite insulation. All types have a locating groove to make tube insertion easy.



NATIONAL LOW-LOSS SOCKETS AND INSULATORS



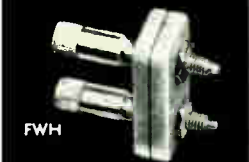
FWG List \$
A Victron terminal strip for high frequency use. The binding posts take banana plugs at the top, and grip wires through hole at the bottom, simultaneously, if desired.




FWH List \$
The insulators of this terminal assembly are molded R-39 and have serrated bosses that allow the thinnest panel to be gripped firmly, and yet have ample shoulders. Binding posts same as FWG above.



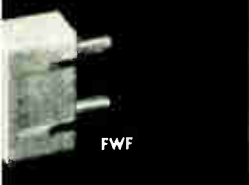FWJ List \$
This assembly uses the same insulators as the FWH above, but has jacks. When used with the FWF plug (below), there is no exposed metal when the plug is in place.



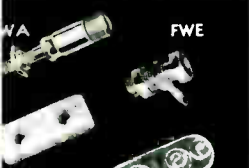FWF List \$
This molded R-39 plug has two banana plugs on $\frac{3}{4}$ " centers and fits FWH or FWJ above. Leads may be brought out through the top or side.



FWA, Post List, each \$
Brass Nickel Plated
FWE, Jack List, each \$
Brass Nickel Plated



FWC, Insulator List, per pair \$
R-39 Insulation
FWB, Insulator List, each \$
Polystyrene insulation

CIR Series Sockets

Any Type List \$

Type CIR Sockets feature low-loss isolantite or steatite insulation, a contact that grips the tube prong for its entire length, and a metal ring for six position mounting.

AA-3 List \$
A low-loss steatite spreader for 6 inch line spacing. (600 ohms impedance with No. 12 wire.)

AA-5 List \$
A low-loss steatite aircraft-type strain insulator.

AA-6 List \$
A general purpose strain insulator of low-loss steatite.

XS-6 List, each \$
A low-loss isolantite bushing for $\frac{1}{2}$ " holes.

XP-6 List, box of ten \$
Same as above but Victron.

TPB List, per dozen \$
A threaded polystyrene bushing with removable .093 conductor moulded in, $\frac{1}{4}$ " diam., 32 thread.

XS-7, ($\frac{3}{8}$ " Hole) List \$

XS-8, ($\frac{1}{2}$ " Hole) List \$

Steatite bushings. Prices include male and female bushings with metal fittings.

XS-1, (1" Hole) List \$

XS-2, (1 $\frac{1}{2}$ " Hole) List \$

Prices listed are per pair, including metal fittings. Insulation steatite.

XS-3, (2 $\frac{3}{4}$ " Hole) List \$






XS-4, (3 $\frac{3}{4}$ " Hole) List \$

Prices are per pair, including metal fittings. These low-loss steatite bowls are ideal for lead-in purposes at high voltages.

XS-5, Without Fittings List, each \$

XS-5F, With Fittings List, per pair \$

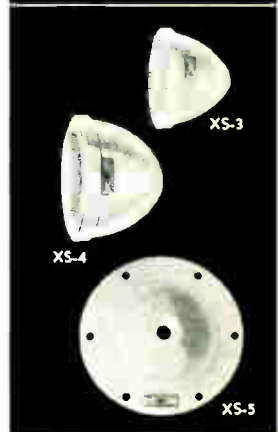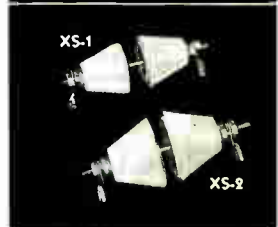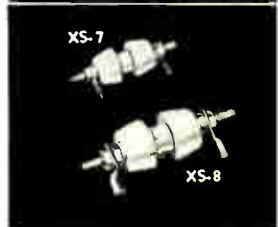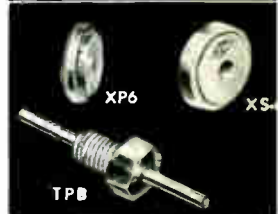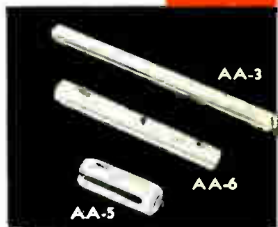These big low-loss bowls have an extremely long leakage path and a 5 $\frac{1}{4}$ " flange for bolting in place. Insulation steatite.



CIR-4

CIR-5

CIR-6

CIR-7S

CIR-7L

CIR-8

CIR-8E

NATIONAL NC-2-40C

NATIONAL NC-2-40CS


The NC-2-40C is a twelve-tube superheterodyne covering a continuous frequency range of 490 to 30,000 KC. The NC-2-40CS is identical but covers from 200 to 400 KC and from 1000 to 30,000 KC.

The circuit employed on all bands consists of one stage of radio frequency amplification, a separate first detector and stabilized high frequency oscillator, two intermediate frequency stages, an infinite impedance second detector, a self-balancing phase inverter and audio amplifier, and an 8-watt push-pull audio output stage.

Auxiliary circuits include a crystal filter with exceptionally wide selectivity range for use on both CW and phone, a series valve noise limiter, AVC, beat oscillator, tone control, and signal strength meter. The power supply is built in.

These receivers have a number of new features of recent design. A new high frequency oscillator design of extreme stability eliminates detuning effects of RF gain control and motorboating or fluttering which occurs in some receivers when tuning in strong signals. A line voltage shift from 100 to 120 volts produces less than 1000 cycles at ten meters.

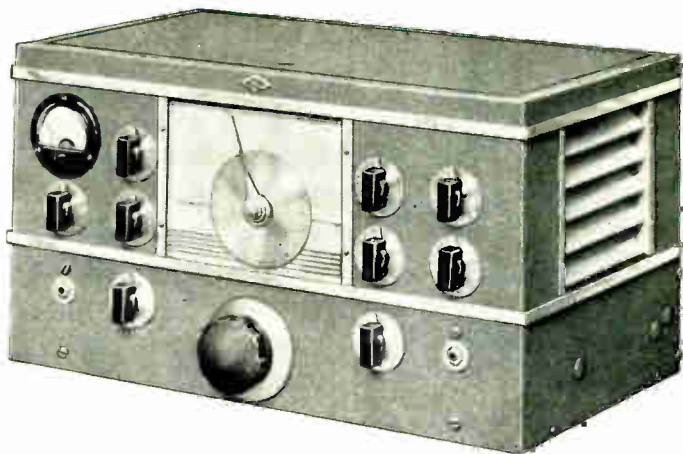Sensitivity is particularly high, an input signal of 1 microvolt providing 1 watt of audio output, and full sensitivity is maintained up to the highest frequencies. Signal-to-image ratio is better than 30 db at ten meters. The AVC is flat within 2 db for signals from 10 to 100,000 microvolts. Moulded polystyrene



coil forms are used in both RF and IF circuits and padding and tuning condensers are of the air-dielectric type.

There are six calibrated coil ranges, controlled by a knob on the front panel which moves the desired coils into position below the tuning condenser and plugs them into the circuit. No coil switch is used. The tuning control has a ratio of 60 to 1 approximately, and is designed to have enough fly-wheel effect to facilitate spinning the knob for quick changes in frequency.

All models of the NC-2-40 are suitable for either AC or battery operation, having both a built-in AC power supply and a special detachable cable and plug for battery connection. Removal of the speaker plug disconnects both plate and screen circuits of the audio power stage thus providing maximum battery economy. The B supply filter and the standby switch are wired to the battery terminals, so that the filter is available for vibrator or dynamotor B supplies.

The ten-inch speaker is housed in a separate cabinet specially designed to harmonize with the trim lines of the receiver. The undistorted output is 8 watts.

- NC-2-40C, Table model, receiver only List \$
- NC-2-40CS, Table model, receiver only List \$
- NC2-TS, Table model 10" PM speaker to match receiver List \$

NATIONAL NC-46

The NC-46 receiver is a ten tube superheterodyne combining capable performance with low price. Features include a series valve noise limiter with automatic threshold control, CW oscillator, separate RF and AF gain controls, and amplified and delayed AVC. Power supplies are self contained and operate on 105 to 130 volts AC or DC. An audio output of 3 watts is provided by push-pull 25L6's.

A straight-line-frequency condenser is used in conjunction with a separate band spread condenser. This combination plus the full vision dial calibrated in frequency for each range covered and a separate linear scale for the band spread condenser, makes accurate tuning easy. Both condensers have inertia type drive. A coil switch with silver plated contacts selects the four ranges from 550 KC to 30 MC. Provision is made for either headphone or speaker.

Like all receivers which have no preselector stage, the NC-46 is not entirely free from images. However, where price is an important considera-



tion, the NC-46 will be found a very satisfactory receiver.

NC-46 — Receiver only, complete with tubes, coils covering from 550 KC to 30 MC for 105-130 volts AC or DC operation — gray finish.

List \$

NC-46TS — Loud Speaker in table mounting cabinet to match above receiver.

List \$

RRA — Relay Rack Adapters designed for mounting these receivers in a standard relay rack.

List \$



RACK MODEL

HRO-5TA table model, receiver only, complete with four sets of coils having bandspread on amateur bands as well as general coverage (1.7-4.0, 3.5-7.3, 7.0-14.4, 14.0-30.0 MC). **List \$**

HRO-5RA rack model, other details same as for HRO-5TA above. **List \$**

COILS

HRO Type E, Range 900-2050 kc **List \$**

HRO Type F, Range 480-960 kc **List \$**

HRO Type G, Range 180-430 kc **List \$**

HRO Type H, Range 100-200 kc **List \$**

HRO Type J, Range 50-100 kc **List \$**

HRO Type A, Range 14.0-30.0 mc **List \$**

HRO Type B, Range 7.0-14.4 mc **List \$**

HRO Type C, Range 3.5-7.3 mc **List \$**

HRO Type D, Range 1.7-4.0 mc **List \$**

MCS Table model cabinet, 8" PM dynamic speaker and matching transformer. **List \$**

697 Table power unit; 115 volt 60 cycle input; 6.3 volt heater and 230 volt, 75 ma. output, with tube. **List \$**

See General Catalogue for relay rack mounting, coil containers and accessories

NATIONAL HRO

The HRO Receiver is a high-gain super-heterodyne designed for communication service. Two preselector stages give remarkable image suppression, weak signal response and high signal-to-noise ratio. Air-dielectric tuning capacitors account, in part, for the high degree of operating stability. A crystal filter with both variable selectivity and phasing controls

makes possible adjustment of selectivity over a wide range. Heterodynes and interfering c.w. signals may be "phased out" (attenuated) by correct setting of the phasing control. A signal strength meter, connected in a vacuum tube bridge circuit, is calibrated in S units from 1 to 9 and in db above S9 from 0 to 40. Also included are automatic and manual volume control, a beat oscillator, a headphone jack and a B+ stand-by switch. Power supply is a separate unit. The standard models, HRO-5TA and HRO-5RA, are supplied with four sets of coils covering all frequencies from 1.7 to 30 MC and have bandspread on the 10, 20, 40 and 80 meter amateur bands.

All models of the HRO are supplied with 6.3 volt heater type metal tubes. Table models and accessories are finished in black wrinkle enamel.

A technical bulletin covering completely all details will be supplied upon request.



NATIONAL SCR-4

List \$

The SCR-4 is an extremely compact crystal controlled receiver for single channel reception. It is mounted on a 5 1/4" panel and uses 13 tubes. Two stages of tuned RF amplification are followed by a separately excited converter with crystal controlled oscillator, three stages of IF amplification, a detector and two audio stages. The power supply is self-contained. Auxiliary circuits include amplified and delayed AVC, CW oscillator, noise limiter, CONS and signal strength meter. Signal-to-noise ratio averages 6 db for 1 microvolt. The AVC is

NATIONAL } SCR-4 SCR-4A

flat within 6 db for inputs from 1 microvolt to 1 volt. Being crystal controlled, frequency stability is excellent. The IF channel has a wide-band characteristic to allow for slight transmitter drift.

As the SCR-4 receiver is intended for communication work, the audio channel has been made flat only from 100-3000 cycles, with increasing attenuation of higher frequencies, thus providing good intelligibility with maximum reduction of unwanted signals and noise.

NATIONAL SCR-4A

List \$

The SCR-4A receiver is similar to the SCR-4 but has no beat oscillator and no signal strength meter. Both receivers are available for use at fixed frequencies between 100 KC and 40 MC.




1-10 Receiver and 6 sets of coils without tubes, speaker or power supply. List \$

5886 Power Supply for above receiver, with tube. List \$

NATIONAL ONE-TEN

The One-Ten Receiver fulfills the need for an adequate receiver to cover the field between one and ten meters.

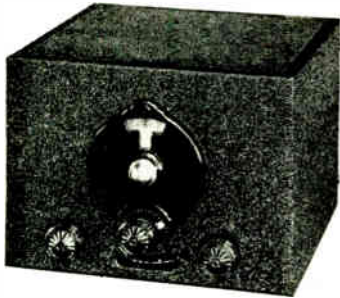A four-tube circuit is used, composed of one tuned R.F. stage, a self-quenching super-regenerative detector, transformer coupled to a first stage of audio which is resistance coupled to the power output stage. Tubes required: 954-R.F.; 955-Detector; 6C5-1st Audio, 6F6-2nd Audio.



NATIONAL SW-3

The SW-3U Receiver employs a circuit consisting of one R.F. stage transformer coupled to a regenerative detector and one stage of impedance coupled audio. This circuit provides maximum sensitivity and flexibility with the smallest number of tubes and the least auxiliary

equipment. The single tuning dial operates a precisely adjusted two gang condenser; the regeneration control is smooth and noiseless, with no backlash or fringe howl; the volume control is calibrated from one to nine in steps corresponding to the R scale.

ONE UNIVERSAL MODEL — The circuit of the SW-3U is arranged for either battery or AC operation without coil substitution or circuit change. Battery operation utilizes two 1N5-G and one 1A5-G tubes. AC operation utilizes two 6J7-G and one 6C5-G tubes. Type 5886 AB power supply is recommended.

SW-3U, Universal model, without coils, phones tubes or power supply. List \$

5886-AB, Power Supply, 115 V., 60 cycle, with 80 Rectifier

List \$

General Coverage Coils

Cat. No.	Range — Meters	List Per Pair \$
30	9 to 15	\$
31	13.5 to 25	
32	23 to 41	
33	40 to 70	
34	65 to 115	
35	115 to 200	
36	200 to 360	
37	350 to 550	
38	500 to 850	
39	850 to 1200	
40	1200 to 1500	
41	1500 to 2000	
42	2000 to 3000	

Band Spread Coils

30A	— 10 meter	\$
31A	— 20 meter	
33A	— 40 meter	
34A	— 80 meter	
35A	— 160 meter	



NATIONAL POWER SUPPLIES

National Power Supplies are specially designed for high frequency receivers, and include efficient filters for RF disturbances as well as for hum frequencies. The various types for operation from an AC line are listed under the receivers with which they are used.

High voltage power supplies can be supplied for National Receivers for operation from batteries. These units are of the vibrator type.

686, Table model (165 V., 50 MA.), for operation from 6.3 volts DC, with vibrator. List \$

NATIONAL



COMPANY

61 SHERMAN STREET, MALDEN, MASS., U. S. A.

McELROY "400" SERIES

COMPLETE AUTOMATIC RADIO AND TELEGRAPH TRANSMITTING AND RECEIVING ASSEMBLIES AND ASSOCIATED EQUIPMENT

While this new McElroy equipment is basically designed for speeds up to 400 words per minute, the high speed transmitters and recorders have been given long tests in our plant at speeds of 700 words per minute. In each piece of equipment will be found features which incorporate the experience of Mr. McElroy as an operator together with suggestions from commercial operators with RCAC, Press Wireless, Mackay, and the communications men of the Armed Forces and Merchant Marine.


Inasmuch as all equipment is regular stock production, it is possible to make prompt shipment on all orders in any quantity. Illustrated catalog and technical manuals are available in all the commonly used languages.



McElroy


MANUFACTURING CORPORATION
82 BROOKLINE AVENUE BOSTON, MASSACHUSETTS

McELROY Complete Transmitting Assembly

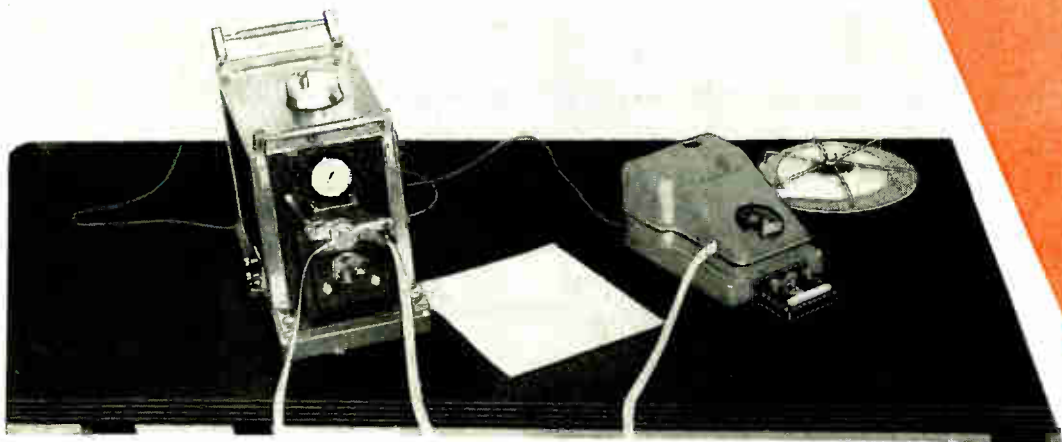

At the left — the Keying Head, complete with Polarized Relay, and together with the Universal Drive combine to form the transmitter unit . . . XTR-400 at \$435.00. At the right — the Wheatstone Code Tape Perforator, PFR-400, at the new low price of \$95.00. Stain-proof Operator's Table, 2½' x 5', at \$165.00. Operator's Chair, \$15.00.

McELROY Complete Receiving Assembly

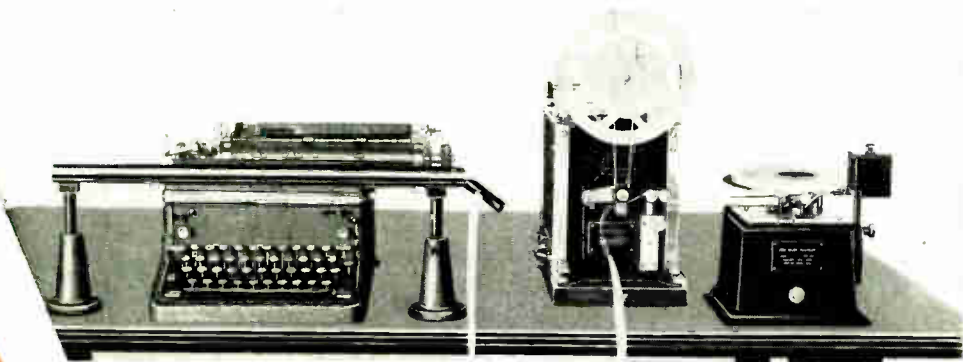


In the center — the Tape Pulling Head and the Universal Drive combine to form the Receiver Unit . . . ATP-400 at \$240.00 (Universal Drive \$195.00 plus Tape Pulling Head, \$45.00). In traffic operation, the tape is drawn through the Ink Recorder (extreme right) by one Receiver Unit running at high speed to the right of the typewriter, and then across the Reversible Tape Bridge by another Tape Puller running at one-man speed to the left.



McElroy

MANUFACTURING CORPORATION
82 BROOKLINE AVENUE BOSTON, MASSACHUSETTS

Clean Contacts! High Speeds!

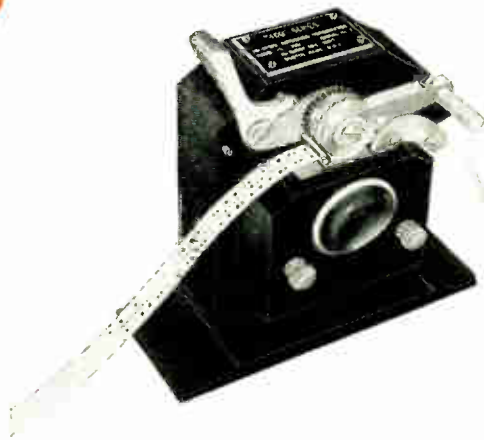

McELROY

KEYING HEAD

MODEL HED-400

Complete with Built-in


Polarized Relay

An ingenious McElroy design places the studs that pull the transmitting tape on the feed drum, not on the Star Wheel, used in other types of auto heads in the contact case. With the old style heads, the contact case functioned as a dust bin . . . the tape swept the floor, carried the dirt up, dropped it into the Star Wheel opening, and fouled the contacts. The McElroy design, which has no Star Wheel in the contact case, assures clean contacts, and less headaches for you. The speed of this new Keying Head, when used with the Universal Drive, ranges from 10 to 300 words per minute. Priced for immediate delivery at \$240.00.

McELROY Universal Drive — Model MSD-400

Permits Rapid Interchangeability of Keying Head and Tape Pulling Head

Before the new Universal Drive was designed, there had to be two different motor assemblies on traffic positions; one to drive the keying head, and the other to pull the receiving slip. Now, with the Universal Drive, the Keying Head and the Tape-Pulling Head are interchangeable. You'll save money on maintenance and on spares, too. Using an old-fashioned installation with two tape pullers, two transmitting bases, and one spare for each, you had a total of six units. With the new Universal Drive, you get 100% more protection with six units, an equal amount with five. Priced for immediate delivery at \$195.00. Universal Drive DTP-400, at the same price, uses AC or DC.

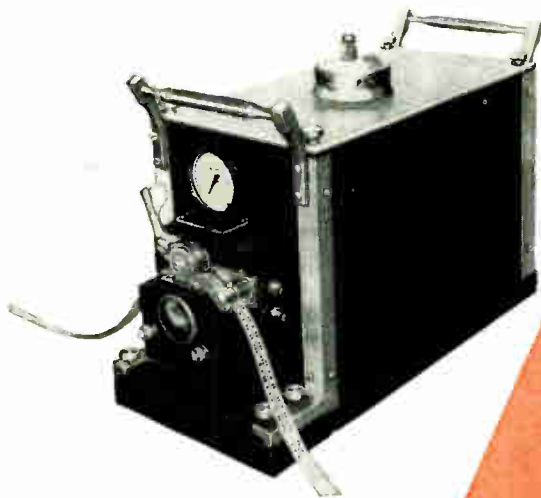

Note that in the illustration, the Keying Head is mounted in position on the Universal Drive . . . this is the same position required by the interchangeable Tape-Pulling Head TP11-400.

McElroy

MANUFACTURING CORPORATION

82 BROOKLINE AVENUE

BOSTON, MASSACHUSETTS

Sensationally Low Priced!



McELROY WHEATSTONE CODE TAPE PERFORATOR PFR-400

Designed to modernize small stations — at sea, ashore and on the air — where, previously the difficulty in keeping the old keyboard perforators in adjustment did not allow automatic operation. Anyone can easily master this instrument, as long as he can read code by sight from a chart. The PFR-400 requires no specially skilled staff for its maintenance . . . adjustments can be made with a screwdriver and a pair of pliers. For 110-120 volts AC or DC. Very low priced for immediate delivery at \$95.00.



McELROY TAPE-PULLING HEAD TPH-400

Has an original arrangement that stops the tape re-wind when the tape pressure wheel is raised. If you've seen tape run wild when you tried to stop it for examination, you'll appreciate the value of this McElroy feature. Another novel adjustment admits the tape at any angle from the right, which makes for smoother flow, prevents breakage, and permits the tape to come from any level on the receiving table — straight from the recorder at high speed, through the bridge at one-man speed, or even from the floor. Priced for immediate delivery at \$45.00.



McElroy

MANUFACTURING CORPORATION
82 BROOKLINE AVENUE BOSTON, MASSACHUSETTS

Another McElroy Improvement!



New...

INK RECORDER REC-400

Although smaller and lighter than previous models, it is capable of speeds up to 700 words per minute, and will operate at high efficiency over longer periods of time. The tape holder, which is part of this equipment, may be attached to either the right or back of the case, whichever is best suited to your receiving table layout. Operates from either AC or DC by snapping a toggle. Priced for immediate delivery at \$195.00.

McELROY Recorder Amplifier MRD-400

Designed to drive the Ink Recorder at speeds up to 300 words per minute (special prices quoted for speeds up to 700 words per minute). No special arrangements are required in any recorder when changing over to this new Recorder Amplifier. Supplied in either a cabinet or rack mounting. It moves the signal coil by push-pull instead of the old-style "push-flip" method by which the pen arm was slapped down to the zero line mechanically by springs. Immediate delivery \$195.00.



McElroy

MANUFACTURING CORPORATION
82 BROOKLINE AVENUE BOSTON, MASSACHUSETTS



McELROY Phototube Keyer PTK-400

Now Priced Within Reach of All

The Phototube Keyer, invented by Ted McElroy more than ten years ago, and widely imitated, has been simplified and made more rugged. Like the Wheatstone Code Tape Perforator, this unit is priced so drastically low that it is now available for schools and clubs throughout the world, as well as for individual amateur and professional operators. The operator may build his own tape pulling arrangement with a phonograph motor, or use the ATP-400 unit. The PTK-400 scans $\frac{3}{8}$ " recorded tape photoelectrically and delivers a tone code signal to from 1 to 50 headphones for operator training, and runs at either low or extremely high speeds. Each practice roll, complete with a 16 mm. metal movie reel, costs \$2.00; at 20 w.p.m., it provides an hour's unattended transmission. . . . A special set of ten rolls, recorded by McElroy, comprises a complete course of instruction for \$20.00. The PTK-400 is priced for immediate delivery at \$45.00.

Special Note on the McELROY "400" SERIES

Except where otherwise noted, all equipment is made for 110-120 volt, 60-cycle operation. For 220-230 volt, 50 cycle operation, add \$15.00.

SHIPPING DATA

Prices quoted are FOB Boston. All equipment is packed to reach destination in operating condition, whether domestic shipment or export. No extra charge on this packing. Equipment meets specifications as to fungus proof, salt spray, rustproof.

McElroy engineers never copy, never imitate. We create, design, build . . . we are never satisfied with mediocrity.

McElroy MANUFACTURING CORPORATION
82 BROOKLINE AVENUE BOSTON, MASSACHUSETTS





SYNTHETICS FOR ELECTRONICS

CONNECTORS

STEATITE SOCKETS

SYNTHETICS FOR ELECTRONICS

A-N FITTINGS

COAXIAL CABLES

**The Line That Reaches
'Round the World**



A-N CONNECTORS

PREFOCUSED LAMP RECEPTACLES

MICROPHONE CONNECTORS

● Among other radio experts, "hams" now welcome the return of the Amphenol line from honorable service on far-flung battlefronts around the world. Amphenol components — greatly improved by wartime experience and augmented in number, style and type — are currently available for civilian applications. Simplifying buying, this wider selection of high-quality, tested items can be procured from one manufacturer.

To know these popular Amphenol products better — write today for the new Condensed Catalog No. 72.

AMERICAN PHENOLIC CORPORATION
In Canada • Amphenol Limited • Toronto

CHICAGO 50, ILL.

**U. H. F. CABLES AND CONNECTORS • CONDUIT • CABLE ASSEMBLIES
CONNECTORS (A-N, U. H. F., BRITISH) • RADIO PARTS • PLASTICS FOR INDUSTRY**


WIRELESS

1910-1946

Welcome back to the air waves, friends! Hams, it's like old times to hear your calls again. Remember when you first began to make "wireless" history? That's when C-D built the first capacitors. You were an inspiration then . . . as you are today.

While your CQ's have been silent, many of you have made radio history in war . . . have ceased to be "amateurs" in the old sense. You have acquired a professional concept of how radio parts must perform. That's as it should be.

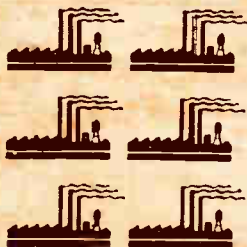We anticipated your demands for more in capacitors, too . . . and we are prepared to continue to uphold your faith in C-D's. We value the confidence you have shown in them for thirty-six years. Cornell-Dubilier Electric Corporation, New Bedford, Mass. Other Plants: So. Plainfield, New Jersey; Worcester, Brookline, Mass. and Providence, R. I.



SIX MODERN PLANTS

The C-D Capacitors you buy today are products of one of our six great plants, centrally located to speed deliveries to your dealer. He can supply you quickly with any C-D type you require.



MANUFACTURING SKILL

C-D quality has kept up despite our tremendous growth and quantity production. Our skilled craftsmen, many of whom have been with us five to twenty years, are outstanding technicians. They make C-D Capacitors to precision standards.

CORNELL-DUBILIER

CORNELL-DUBILIER CAPACITORS *for every radio need*



**TYPE
9**

Moulded mica capacitor for r.f. by-pass, grid and plate blocking in low power transmitters and amplifiers. Strong, well-insulated, moisture-resistant, with short, heavy terminals, minimum r.f. and contact resistance. Stable in capacity and high insulation resistance.



**TYPE
TJU**

Dykanol transmitting filter capacitor, compact, lightweight, safety-rated, furnished with universal mounting clamp, well-insulated terminals, fire-proof, and attractively priced. Hermetically sealed against any climatic conditions, in sturdy steel container, aluminum-painted, non-corrosive, can be mounted in any position. Extra high dielectric strength. Conservative D.C. rating — triple tested. Wide range of voltage ratings.



**TYPE
6**

Medium power mica transmitter capacitor for r.f. applications where size and weight must be minimized. Patented series stack mica construction. Permanent non-magnetic clamps. Vacuum-impregnated — results in low loss, high insulation — no air voids. Low loss filter reduces stray losses. Suited to grid, plate, coupling, tank and by-pass uses.



**TYPE
59**

Mica transmitting capacitor — improved design — extremely adaptable, dependable under the most severe operating conditions. In low-loss, white glazed ceramic cases, with low-resistance, wide path terminals. Can be mounted individually or in groups in series or parallel combinations. For grid, plate blocking, coupling, tank and by-pass applications in high power transmitters.

SEND FOR CATALOG 195 also "The C-D Capacitor," a monthly digest of developments in radio, articles, engineering data, helpful facts . . . yours free for the asking.

Copyright Map Courtesy Rand McNally & Co., Chicago



CAPACITORS

World Radio History

MICA • DYKANOL • PAPER • ELECTROLYTIC

PERFORMANCE

EIMAC TRANSMITTING TUBES

EIMAC TUBE TYPES	ELECTRICAL							MECHANICAL				MAX. RATINGS				PRICE		
	FIL. VOLTS	FIL. AMPS.	AMP. FACTOR	GRID-PLATE, UIUF	INPUT, UIUF	OUTPUT, UIUF	TRANSCONDUCTANCE, UMHRS	BASE	BASING	MAX. LENGTH, INCHES	MAX. DIAMETER, INCHES	FIL. VOLTAGE	PL. CURRENT, MA.	SCREEN VOLTAGE	SCREEN DISSIPATION, WATTS		GRID DISSIPATION, WATTS	PL. DISSIPATION, WATTS
3-25A3 (25T)	6.3	3.0	29	1.6	2.4	0.4	2500	M8-071	3G	4.38	1.43	2000	75	...	7	25	\$ 6.00	
3-25D3 25TG	6.3	3.0	25	1.6	1.8	0.2	2500	M8-071	3G	4.38	1.43	2000	75	...	8	25	9.00	
3-50A4 35T	5.0	4.0	30	1.9	4.0	0.2	2850	M8-078	3G	5.5	1.81	2000	160	...	15	50	6.00	
3-50D4 35TG	5.0	4.0	30	1.9	1.9	0.2	2850	M8-078	2M	5.75	1.81	2000	150	...	15	50	6.75	
3-50G2 UH50	7.5	3.25	13	2.4	2.2	0.4	...	M8-078	2M	7.0	2.69	1250	125	...	13	50	12.50	
3-75A3 75TH	5.0	6.5	20	2.3	3.5	0.25	4150	M8-078	2M	7.25	2.81	3000	225	...	16	75	9.00	
3-75A2 75TL	5.0	6.5	11	2.3	2.2	0.4	3350	M8-078	2M	7.25	2.81	3000	225	...	13	75	9.00	
3X100A11 2C39*	6.3	1.1	...	1.95	6.5	0.30	21,000	2.75	1.26	1000	100†	...	3	100	30.00	
3-100A4 100TH	5.0	6.2	4.0	2.0	2.9	0.4	5500	M8-078	2M	7.75	3.18	3000	225	...	20	100	13.50	
3-100A2 100TL	5.0	6.5	12	2.3	2.0	0.4	2300	M8-078	2M	7.75	3.19	3000	225	...	15	100	13.50	
3-150A3 (152TH)	5 or 10	13 or 6.5	20	4.7	7.0	0.5	8300	5000B	4BC	7.63	2.56	3000	450	...	30	150	20.00	
3-150A2 (152TL)	5 or 10	13 or 6.5	11	5.0	4.8	0.8	7150	5000B	4BC	7.63	2.56	3000	500	...	25	150	20.00	
3X150A3 (3C37)*	6.3	2.4	...	3.50	4.25	0.60	8000	3.10	1.50	1000	150	45.00	
3-250A4 (250TH)	5.0	10.5	37	2.9	5.0	0.7	6650	5001B	2N	10.13	3.81	4000	350	...	40	250	24.50	
3-250A2 (250TL)	5.0	10.5	13	3.5	3.0	0.5	2650	5001B	2N	10.13	3.81	4000	350	...	35	250	24.50	
3-300A3 (304TH)	5 or 10	26 or 13	20	9.4	14.0	1.0	16,700	5000B	4BC	7.63	3.56	3000	900	...	60	300	50.00	
3-300A2 (304TL)	5 or 10	26 or 13	11	10.0	10.0	1.5	16,700	5000B	4BC	7.63	3.56	3000	1000	...	50	300	50.00	
3-450A4 (450TH)	7.5	12.0	38	4.7	8.1	0.8	6650	5002B	4AQ	12.63	5.13	6000	500	...	80	450	60.00	
3-450A2 (450TL)	7.5	12.0	19	5.0	6.6	0.9	6060	5002B	4AQ	12.63	5.13	6000	500	...	65	450	60.00	
3-750A2 (750TL)	7.5	21.0	15	4.5	6.0	0.8	3500	5003B	4BD	17.0	7.13	6000	1000	...	100	750	135.00	
3-1000A4 (1000T)	7.5	18.0	30	4.0	6.0	0.6	9050	5004B	4AQ	12.63	5.13	8000	750	...	80	1000	100.00	
3-1500A3 (1500T)	7.5	26.0	24	7.0	9.0	1.3	10,000	5005B	4BD	17.0	7.13	6000	1250	...	125	1500	185.00	
3-2000A3 (2000T)	10.0	26.0	20	9.0	13.0	1.5	11,000	5006B	4BD	17.75	8.13	6000	1750	...	150	2000	225.00	
3X2500A3*	7.5	4.0	20	2.0	4.8	1.2	20,000	9.0	4.25	5000	2000	...	125	2500	135.00	
4-125A	5.0	6.2	6.2	0.03	10.3	3.0	2450	5008B	...	5.69	2.72	3000	225	400	30	5	125	20.00
4-250A	5.0	14.5	...	0.06	12.7	4.5	4000	5098B	...	6.38	3.56	4000	350	600	50	5	250	30.00
4X500A*	5.0	12.2	...	0.05	11.1	3.75	5200	4.32	2.57	4000	300	450	30	5	500	80.00

TRIODES

TETRODES

*External Anode requiring forced-air-cooling. †Cathode Current.

CAUTION: Check serial numbers on Eimac tubes before you buy. Be sure you're getting the right ones. Look for latest serial numbers.

the Only Criterion

On merit and on merit alone, Eimac tubes have achieved a position of leadership throughout the world. Their outstanding performance characteristics have set and maintained an extremely high standard for more than a decade.

Standing behind Eimac tubes are a prewar performance record second to none and a wartime achievement record of the highest order both in production and development. Today Eimac stands at the threshold of the great new era of electronics with a family of electron vacuum tubes embodying all the original Eimac concepts in addition to highly advanced techniques and developments gained by the concentrated efforts of the past five years.

In the final analysis, performance is the only criterion. It's what the tubes do in your application that really counts. Below is a brief listing of the basic data on many Eimac tubes. Eimac stands ready to provide additional information or assistance without cost or obligation. Please let us hear from you.

EIMAC RECTIFIERS


	MV RECTIFIERS		HIGH VACUUM RECTIFIERS			
	RX21A (RX-21)	KY21A (KY-21) Grid Control	2-100A (100-R)	2-150A (152-R)	2-150D (152-RA)	2-250A (250-R)
1. Filament Voltage.....	2.5	2.5	5.0	5.0	5.0	5.0
2. Filament Current.....	10 amperes	10 amperes	6.5	13.0	13.0	10.5
3. Peak Inverse Voltage.....	11,000	11,000	40,000	30,000	30,000	60,000
4. Peak Plate Current.....	3 amperes	3 amperes
5. Average Plate Current.....	.75 amperes	.75 amperes	.100 amperes	.150 amperes	.150 amperes	.250 amperes
Price.....	\$7.50	\$10.00	\$13.50	\$15.00	\$15.00	\$20.00

EIMAC VACUUM CAPACITORS



Type.....	VC6-20	VC12-20	VC25-20	VC50-20	VC6-32	VC12-32	VC25-32	VC50-32
Capacity.....	6-mmfd	12-mmfd	25-mmfd	50-mmfd	6 mmfd	12-mmfd	25 mmfd	50 mmfd
Rating.....	20-KV	20-KV	20-KV	20-KV	32-KV	32-KV	32-KV	32-KV
RFPeak.....								
Price.....	\$10.00	\$11.30	\$14.00	\$16.70	\$12.00	\$13.30	\$16.00	\$18.70

EIMAC VACUUM SWITCHES

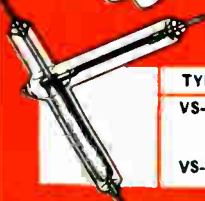

TYPE	GENERAL DATA	PRICE
VS-1....	Single pole double throw switch within a high vacuum making it adaptable for high voltage switching. The contact spacing is .015". In spite of the close spacing this switch will handle R. F. potentials as high as 20-KV. In D. C. switching circuits the contacts will handle approximately 1.5 amperes at 5 KV.	\$6.00
VS-2....	Same as above except for slightly longer glass tubulation.....	\$6.00

EIMAC DIFFUSION PUMP



HV-1 DIFFUSION PUMP	PRICES ON APPLICATION
EIMAC PUMP OIL	

FOLLOW THE LEADERS TO





TYPE 11

SMALL, LOW-COST, SOLA CONSTANT VOLTAGE TRANSFORMERS FOR CHASSIS MOUNTING

Reliable communications equipment must have stabilized voltage—and the right place to provide for it is in the equipment itself. These three types of SOLA Constant Voltage Transformers have been specifically designed for "built-in" applications. They are low in cost and their use will often permit the elimination of other components. For complete information consult Bulletin 34CV-102, available on request.



TYPE 12



TYPE 1

	Catalog Number	Output Capacity in VA	Input Volts	Output Volts	Dimensions in Inches					Approx. Shipping Weight	List Price Each
					A	B	C	E	F		
TYPE 1	30488	15	95-125	6.0	5 ¹¹ / ₁₆	2 ⁵ / ₈	3 ¹ / ₁₆	5 ¹ / ₁₆		6	\$15.00
	30492	15	95-125	6.3	5 ¹¹ / ₁₆	2 ⁵ / ₈	3 ¹ / ₁₆	5 ¹ / ₁₆		6	15.00
	30498	15	95-125	115.0	5 ¹¹ / ₁₆	2 ⁵ / ₈	3 ¹ / ₁₆	5 ¹ / ₁₆		6	15.00
TYPE 11	30785	17	95-125	6.3	5 ¹¹ / ₁₆	3 ²¹ / ₃₂	2 ¹⁹ / ₃₂	3	2	5 ¹ / ₂	20.00
	30955	17	95-125	115.0	5 ¹¹ / ₁₆	3 ²¹ / ₃₂	2 ¹⁹ / ₃₂	3	2	5 ¹ / ₂	20.00
TYPE 12	301002	15	95-125	6.3	5 ¹ / ₁₆	3 ¹ / ₂	2 ¹ / ₄	3	1 ¹ / ₂	2 ¹ / ₂	18.50
	301003	15	95-125	115.0	5 ¹ / ₁₆	3 ¹ / ₂	2 ¹ / ₄	3	1 ¹ / ₂	2 ¹ / ₂	18.50

*Condenser supplied as separate unit.

DIMENSIONS:
 A: Overall Length
 B: Overall Width
 C: Overall Height
 E & F: Mounting Dimensions
 Prices subject to change without notice.

VOLTAGE FLUCTUATIONS UP TO 30%

STABILIZED WITHIN ± 1% OF RATED VALUE




FOR COMMUNICATIONS EQUIPMENT NOW IN SERVICE

Where provision for constant voltage protection has not been made within the equipment itself, these standard SOLA Constant Voltage Transformers can be easily installed. They require no supervision or maintenance, are instantaneous in operation and they protect both themselves and the equipment against short-circuit. Other capacities ranging from 10VA to 15KVA fully described in Bulletin 34CV-102, available on request.



TYPE 2

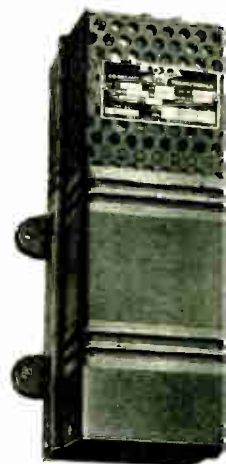

TYPE 3

	Catalog Number	Output Capacity in VA	Input Volts	Output Volts	Dimensions in Inches					Approx. Shipping Weight	List Price Each
					A	B	C	E	F		
TYPE 2	30804	30	95-125	115.0	8 ⁹ / ₁₆	4 ³ / ₁₆	4 ³ / ₈	7 ¹¹ / ₁₆	2 ³ / ₈	12	\$17.00
	30805	60	95-125	115.0	8 ¹³ / ₁₆	4 ⁷ / ₁₆	4 ³ / ₈	8 ¹ / ₁₆	2 ³ / ₈	13	24.00
	30806	120	95-125	115.0	9 ¹¹ / ₁₆	4 ⁷ / ₁₆	4 ³ / ₈	8 ¹ / ₁₆	2 ³ / ₈	17	32.00
TYPE 3	30807	250	95-125	115.0	11 ⁵ / ₈	6 ¹³ / ₁₆	5 ³ / ₈	3 ¹ / ₂	6 ¹ / ₂	30	52.00
	30M807	250	190-250	115.0	11 ⁵ / ₈	6 ¹³ / ₁₆	5 ³ / ₈	3 ¹ / ₂	6 ¹ / ₂	30	52.00
	30808	500	95-125	115.0	14 ¹ / ₂	6 ¹³ / ₁₆	5 ³ / ₈	5	6 ¹ / ₂	40	75.00
	30M808	500	190-250	115.0	14 ¹ / ₂	6 ¹³ / ₁₆	5 ³ / ₈	5	6 ¹ / ₂	40	75.00

Constant Voltage SOLA Transformers

This new Folded Unipole Antenna for commercial use weighs only 15 pounds. Its "Slide Trombone" calibration eliminates old-fashioned pruning. Comparative tests show it out-performs other antennas at several times the price.

HIGH GAIN DIRECTIVE ANTENNAS

for Amateur Use


In vital military and emergency communications all over the world, the name ANDREW means sound engineering plus skill and ingenuity in meeting specific antenna design problems.

NOW FOR AMATEURS

This engineering skill and know-how with commercial antennas is being applied to the production of ham antennas, including both vertically polarized directive arrays and horizontally polarized rotatable systems.


Andrew Co. pioneered in the development of UHF antennas, coaxial transmission lines and accessories.

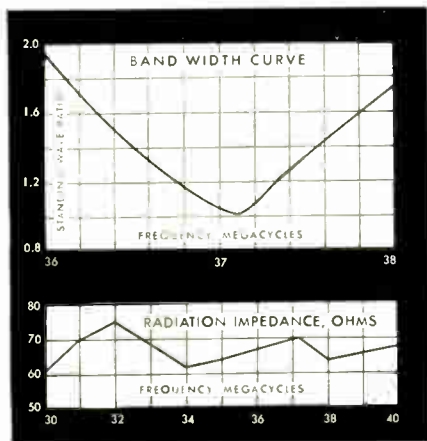Andrew Co. specializes in the solution of antenna problems — in the designing, engineering and building of antenna equipment.



ANDREW CO.

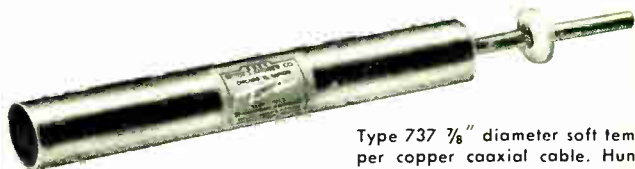363 EAST 75TH STREET
CHICAGO 19, ILLINOIS



Type 737 $\frac{7}{8}$ " diameter soft temper copper coaxial cable. Hundreds of miles of this Andrew cable are now in use with police and military transmitters.

AMATEUR • COMMERCIAL • MILITARY

COMMUNICATIONS RECEIVERS

Prepare now to fit Hammarlund communications receivers into your postwar program. This new line of receiving equipment will include highly specialized single band VHF and UHF models for commercial and amateur use, several models of the well known "Super-Pro", and a new "HQ-129-X" amateur receiver, selling at \$129.00, net to the amateur. The "HQ-129-X" is basically the same as the original "HQ-120-X", but has several improvements and modifications.



New "HQ-129-X"



"Super-Pro"




ESTABLISHED 1910

... 35 YEARS OF

RESEARCH
KNOW HOW
EXPERIENCE



Single Band UHF

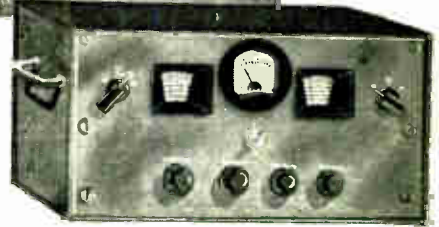

Amateur VHF



Single Band VHF



Wide Range VHF



An entire new group of VHF and UHF receivers for point to point, relay, facsimile, and other services in those ranges.


HAMMARLUND

THE HAMMARLUND MFG. CO., INC., 460 W. 34TH ST., NEW YORK 1, N.Y.
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT

35

RADIO TRANSMITTERS

FOR EVERY SERVICE

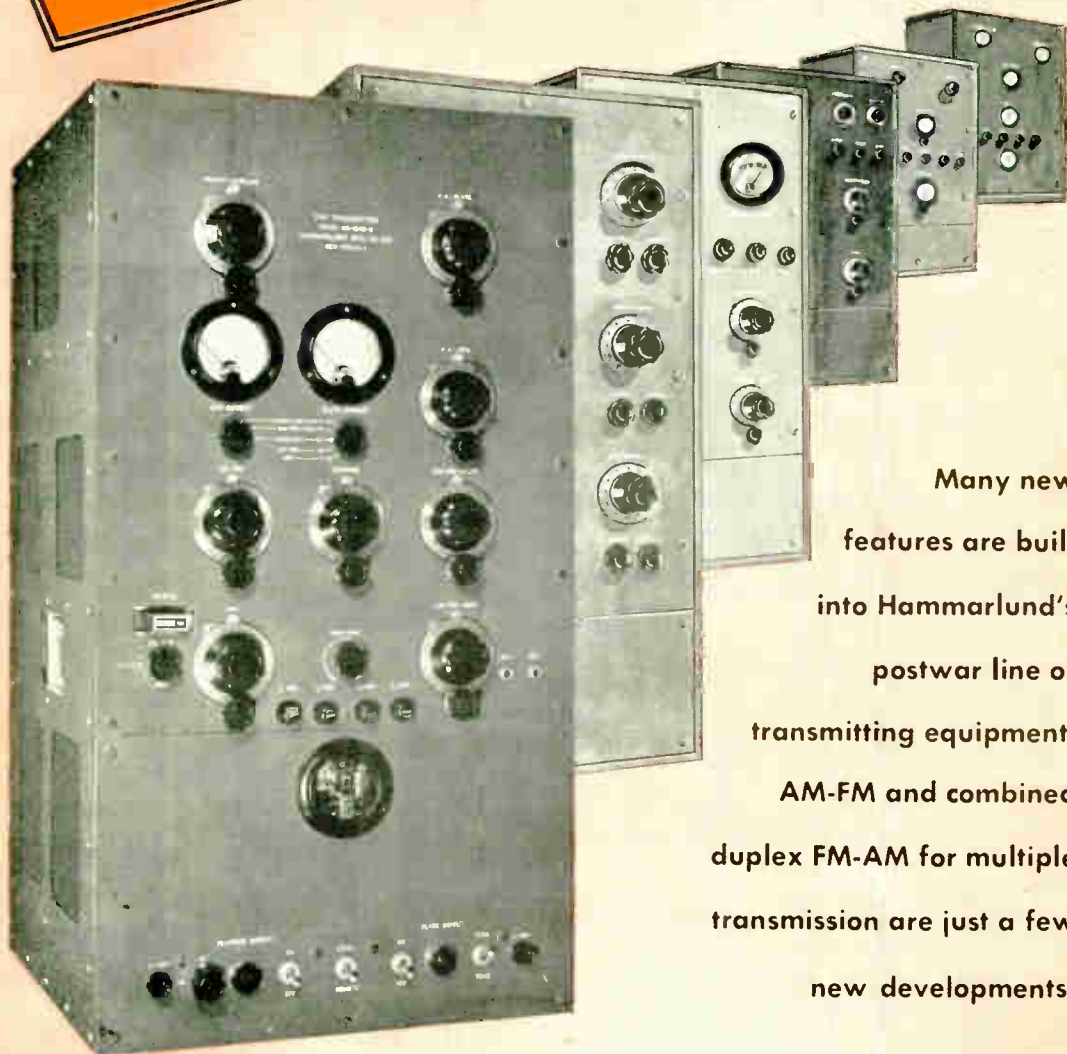

Many new features are built into Hammarlund's postwar line of transmitting equipment.

AM-FM and combined duplex FM-AM for multiple transmission are just a few new developments.

A full line of quality transmitters up to 1-KW for Forestry; Police; Point-to-Point; Aviation; facsimile; with either FM, AM or narrow band FM telegraphy.



... 35 YEARS OF

RESEARCH

KNOW HOW

EXPERIENCE



Amateurs as well as professionals will find outstanding values in this advanced line of 50-1000 Watt transmitters which includes high-stability VFO's, exciters, and modulation units.

Variable Frequency Oscillators; Exciters; complete transmitters with Phone—CW—FM—AM. Write today for latest data in transmitter design.


HAMMARLUND

THE HAMMARLUND MFG. CO., INC., 460 W. 34TH ST., NEW YORK 1, N.Y.
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT


World Radio History




Multi-Frequency Control

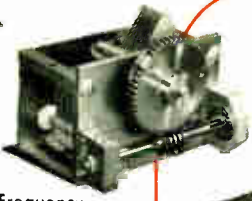


Precision Frequency Control Unit

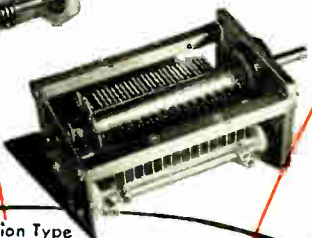

Aviation Type

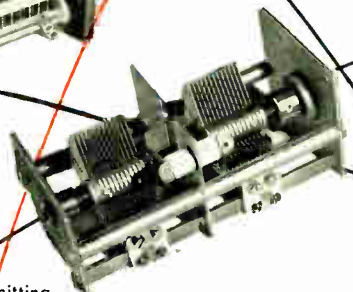

Mobile Transmitting

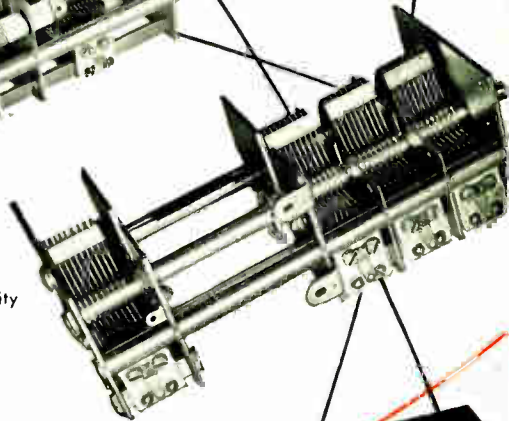

High Stability Receiving

TRANSMITTING

35 YEARS OF RESEARCH • KNOW HOW • EXPERIENCE

RECEIVING

COMMERCIAL


AMATEUR

HAMMARLUND


PRECISION

VARIABLE CAPACITORS

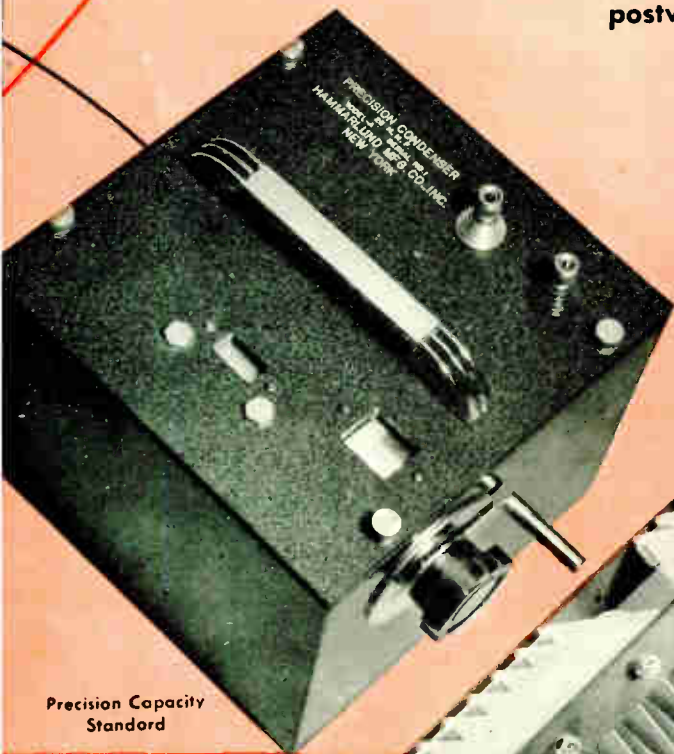The finest line of precision capacitors for every purpose—commercial, amateur, laboratory. Specify Hammarlund in your postwar equipment. They wear well and reduce servicing.



Precision Capacity Standard

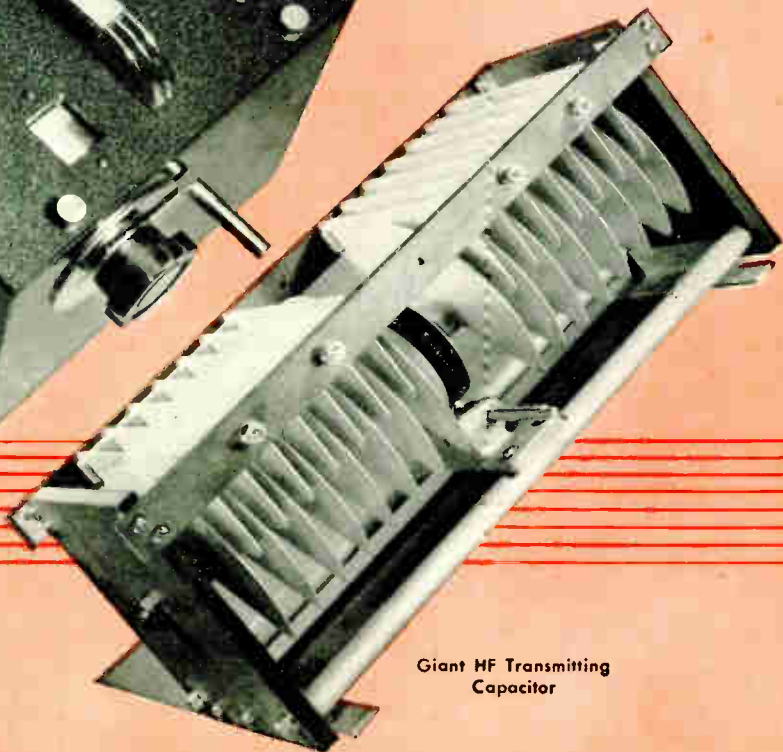

Giant HF Transmitting Capacitor



ESTABLISHED 1910


NEW "HQ-129-X" AMATEUR RECEIVER

\$129⁰⁰
NET

This is an Improvement Over the "HQ-120-X" and Will Meet Every Amateur Requirement at a Much Lower Cost

The new "HQ-129X" meets the most critical demands of amateur and professional operators. This modern amateur receiver is an adaptation of the original "HQ-120-X" and has all the basic performance characteristics of the original model with a number of improvements and modifications. It covers a continuous range of from 31 to .54 MC (9.7 to 555 meters) in six bands, taking in all of the important amateur, communications and broadcast channels. The "HQ-129-X" should not be confused with ordinary low-cost beginner type amateur receivers. Every wave range is individual. Each has its own individual coil and tuning condenser of proper value for maximum efficiency. These are a few of its features:

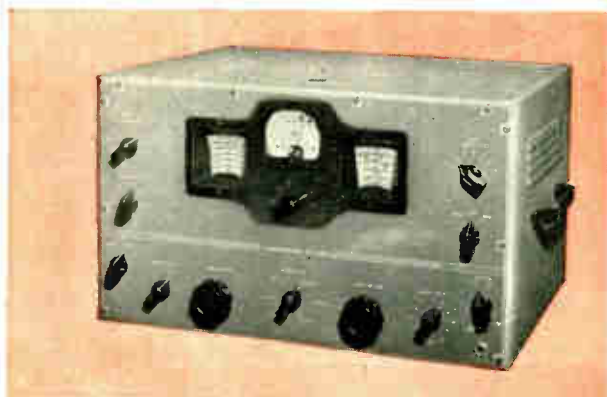variable band-width crystal filter for phone and CW—antenna compensator for matching antennas—improved noise limiter—beat oscillator—calibrated S-meter—AVC—310 degrees of band spread. Amateur net price, complete less speaker—\$129.00. Speaker in metal cabinet—\$10.50, net.



"SUPER-PRO"

Amateur
Commercial
Receiver

PRICES SUBJECT TO CHANGE
WITHOUT NOTICE

Through a long war record of outstanding service, the "Super-Pro" has become the standard of measurement of all types of commercial communications receivers. The "Super-Pro" has variable selectivity crystal filter and variable IF band width, providing an over-all selectivity range of from less than 100 cycles to approximately 16 KC, an improved noise limiter, two stages of tuned RF for maximum image suppression, high-gain, high-quality audio amplifier with output of approximately 8 Watts, new and improved S-meter for accurate measurement of relative signal strength, full band spread on all bands, beat oscillator, "Send-Receive" switch, relay connections, connections for phona-pickup, better than 1 Micravolt sensitivity. Amateur net price, complete with speaker but without speaker cabinet:



SP-210-X 15-560 meters
SP-210-SX 7.5-240 meters
SPC-10" Speaker Cabinet
to match receiver

Amateur net
\$279.00
\$279.00

5.10



THE COMMUNICATIONS LINE OF EXTRA VALUE

Keep up to date. Get your name on our technical mailing list — Write today!

Be sure to send your name and address to receive technical bulletins and information on postwar products, including commercial and amateur transmitters, receivers, and components, covering all frequencies from 555 KC to over 500 MC. Write today, stating your preference as to "amateur" or "commercial," so that we can place your name on our mailing list for new and interesting technical data.



ESTABLISHED 1910

HAMMARLUND

THE HAMMARLUND MFG. CO., INC., 460 W. 34TH ST., NEW YORK 1, N.Y.
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT


ONE STANDARD TYPE

does the job...

NEW type end seal for extra humidity protection.

WOUND WITH
CERAMIC
INSULATED
WIRE
1000°C.
HEAT-PROOF!

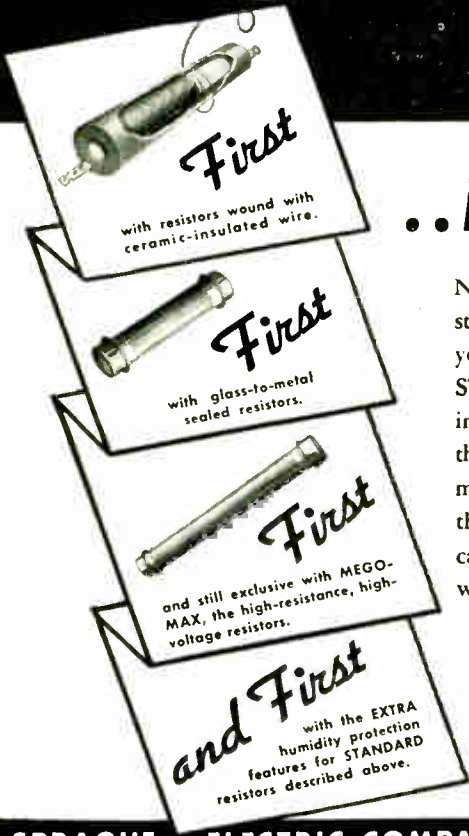NEW glazed ceramic shell to withstand thermal shock, humidity and corrosive conditions.



..in ANY climate!

No more "special orders" to obtain suitable resistors to withstand the extreme thermal and humidity conditions to which your product may be subjected in many parts of the world! STANDARD Sprague Koolohm Wire-Wound Resistors now incorporate these extra protection features — and this means that you can count on STANDARD Sprague Koolohms for maximum dependability in ANY climate, ANYwhere on the face of the globe. Write for new catalog of Sprague Koolohm wire-wound types for every requirement.




SPRAGUE KOOLOHM

TRADEMARK REGISTERED U.S. PAT. OFF.

WIRE-WOUND RESISTORS

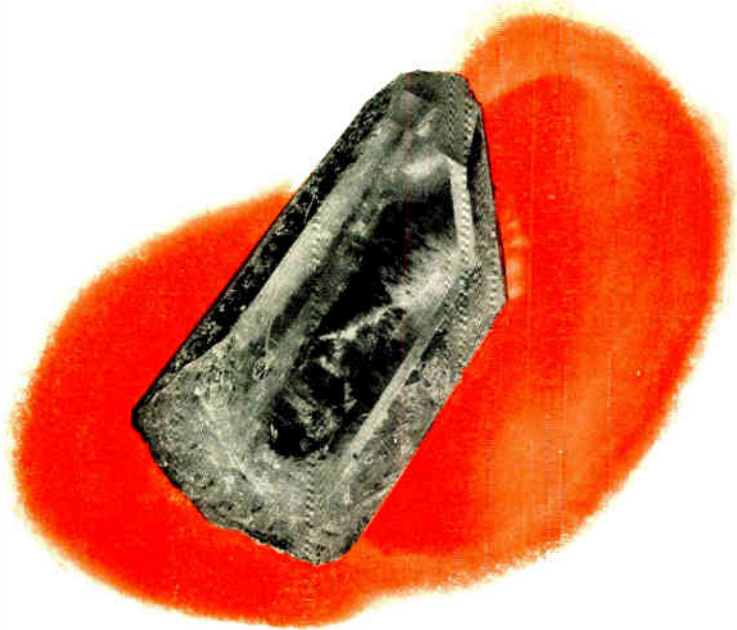SPRAGUE ELECTRIC COMPANY, Resistor Division, North Adams, Mass.



Here all similarity ends...

from this point on, it's craftsmanship!

For over 15 years the Bliley organization has devoted its talent exclusively to the production of quartz crystals. From this long experience have come many of the "firsts" that have contributed substantially to the rapid growth and development of world-wide communications.

On the following pages are listed the standard Bliley acid etched* crystal units that have proved their worth under the most exacting conditions. With these units it is possible to cover the entire frequency spectrum in which frequency control with quartz crystals is practicable.

The best crystal unit for your particular application can easily be determined by consideration of the operating conditions. All details, such as oscillator circuit, grid drive to following stage, frequency tolerance, ambient temperature range, vibration and humidity must be analyzed to obtain completely satisfactory performance. Faster service is assured when this information accompanies your inquiry.

Make it a habit to consult Bliley engineers on all frequency control problems. Your product will benefit from this background of creative experience.

*Acid etching quartz crystals to frequency is a patented Bliley process.



Bliley
CRYSTALS

Be sure your name is on Bliley's list to receive announcements of new developments

BLILEY ELECTRIC COMPANY • UNION STATION BUILDING, ERIE, PA.

Bliley CRYSTALS



TYPE BC10
350-5000kc.

Precision holder employs micrometer screw control of upper crystal electrode for frequency adjustment after installation. For use in fixed equipment such as broadcast monitors and frequency standards.



TYPE BC46R
70-200kc.

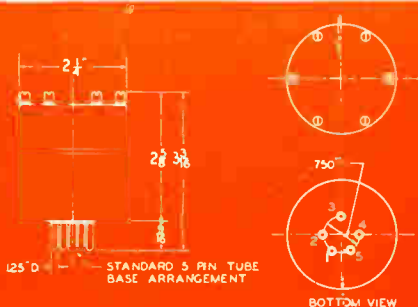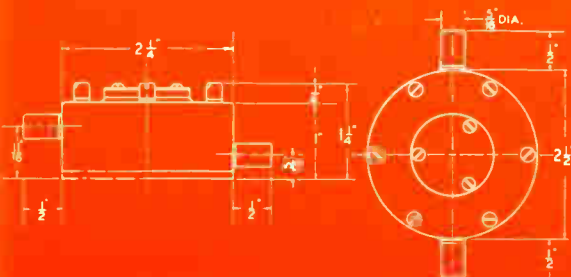Constant temperature oven combined with special crystal assembly. Provides exceptional frequency stability. Heater current 1 amp. at 10V.—a.c. or d.c. Recommended for frequency standards and precision test equipment.





TYPE BC46T
200-5000kc.

Combined BC10 crystal assembly and constant temperature oven. Heater current 1 amp. at 10V.—a.c. or d.c. Exceptional frequency stability. Fully approved by FCC for automatic frequency control in U.S.A. broadcast stations.



TYPE CF6
455kc.

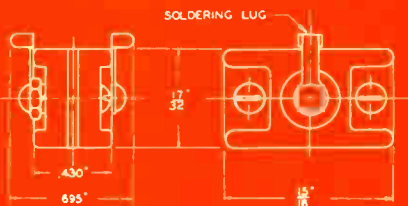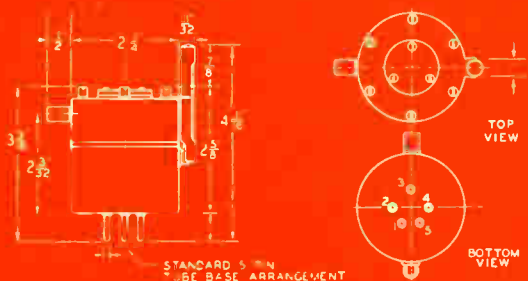Single signal filter crystal unit. Exceptionally low holder capacity permits sharp signal discrimination in filter network of general communications receivers. Frequency 455kc. free from spurious responses within ± 7 kc.





TYPE CF3
455kc.

Single signal filter crystal unit. Frequency 455kc., ± 5 kc.—free from spurious responses within ± 7 kc. of fundamental. Designed for intermediate frequency filter in general communications receivers.



TYPE FM6
70-400kc.

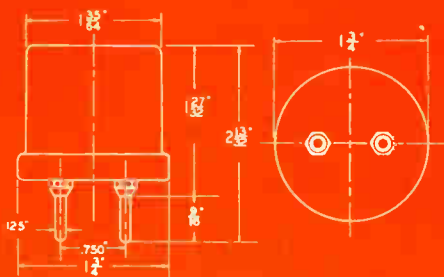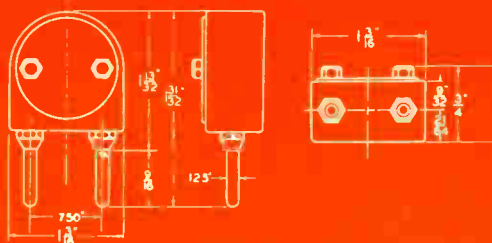
Plated crystal rigidly clamped between resonant pins provides exceptional electrical and mechanical stability. Captive gasket seals case effectively for any service. For all applications requiring an accurate source of low frequency in this range.





TYPE MC85
400-1500kc.

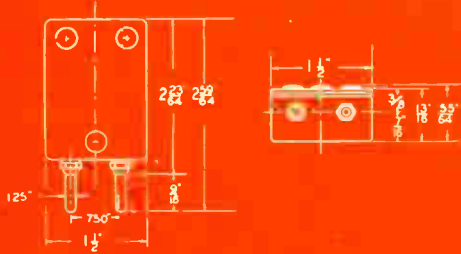
Utilizes fixed air-gap assembly with unclamped crystal. Glass spacers maintain relative position of electrodes. Holder accommodates quartz plate $1" \times 1"$ for maximum activity with medium power tubes and circuits.



TYPE MC7
1700-11,000kc.




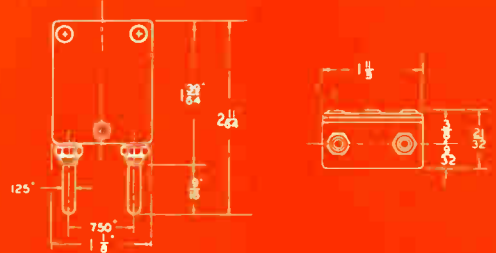Gasket sealed holder with pressure air-gap crystal assembly. Ideal for multi-channel applications. Accommodates quartz plate up to $.7" \times .9"$ for adequate activity in medium power circuits. Used widely in marine radio-telephone equipment.





TYPE MC9
3000-11,000kc.

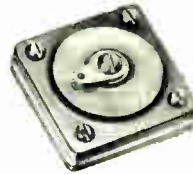Compact holder for multichannel portable equipment where space is a factor. Gasket sealed against moisture and humidity. Suggested for all vehicular and air-borne equipment having low power oscillator tubes and circuits.



TYPE SMC100
100 and 1000kc.

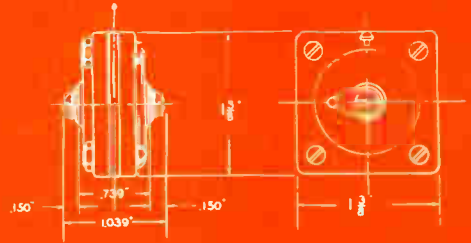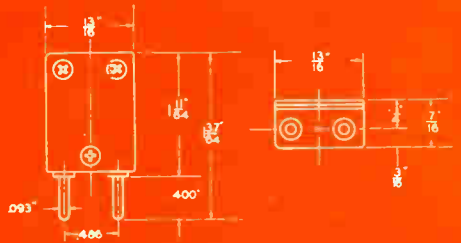Dual frequency crystal provides either 100kc. or 1000kc. source. In recommended circuit 1000kc. is within $\pm .05\%$ and 100kc. can be adjusted to zero beat. Excellent for alignment of radio receivers.





TYPE MS433
1000kc.

High precision crystal assembly sealed in metal tube envelope. Frequency within ± 15 cycles at 20°C . when used in recommended oscillator. Will maintain frequency within 60 cycles between 0°C . and 50°C . Designed for use in frequency meters.



TYPE M03
2000-11,000kc.

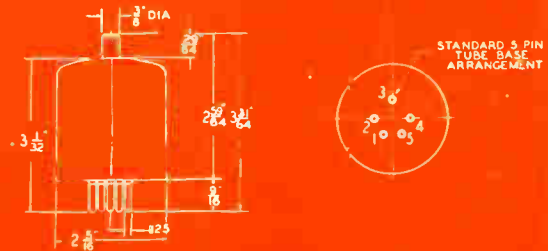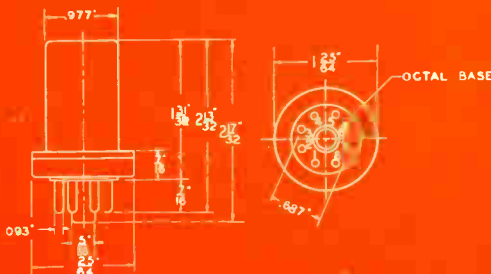Constant temperature crystal oven combined with crystal assembly. Heater current 1 amp. at 6.3V. Compact unit provides temperature stability for maintenance of close tolerances in point to point communication.







TYPE BH5
4500-9500kc.

Midget holder with aluminum plated crystal mounted between spring contacts on wire supports. Hermetically sealed metal case protects assembly. Recommended for use only with low power oscillator tubes and circuits where space is at a premium.




TYPE SR6
1700-11,000kc.

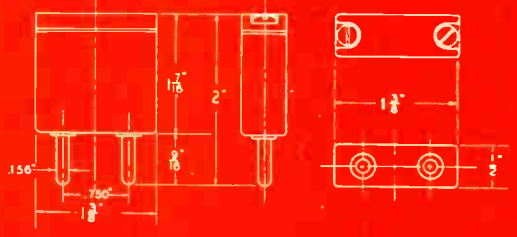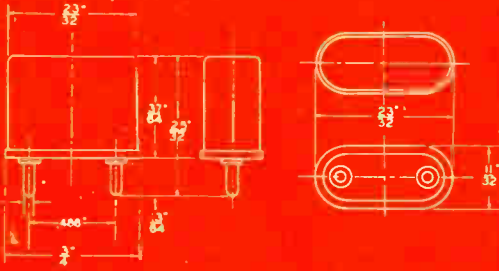Pressure air-gap crystal assembly in gasket sealed phenolic case. Accommodates .750" x .750" quartz plate for adequate activity with medium power tubes and circuits, particularly low frequency range. Suggested for all mobile applications.





TYPE SR7
1700-11,000kc.

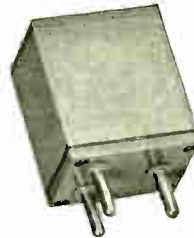Heavy duty holder equipped with banana plug connections. Pressure air-gap crystal assembly provides excellent mechanical stability. Fully protected by gasket seals at all case openings. Recommended for marine use and similar applications.



TYPE AR5W
400-11,000kc.

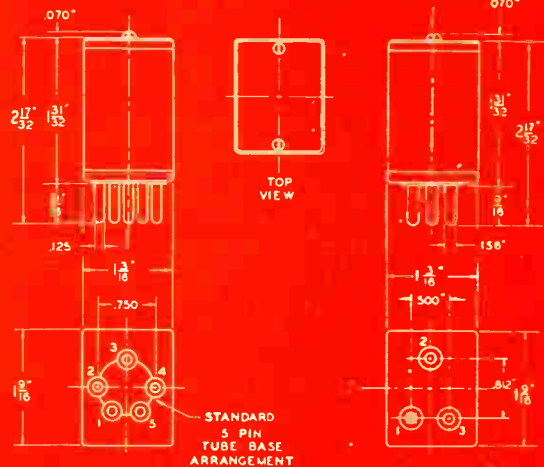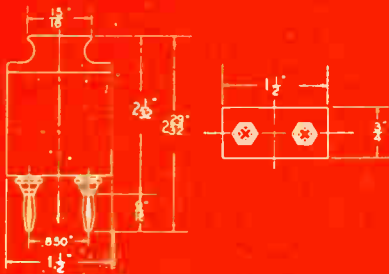Compact unit supplied with 2 crystals for transceiver equipment where both transmitter and receiver are crystal controlled. Excellent mechanical and electrical stability over wide range of service conditions. Single crystal, specify type AR4W.



B & W



Durable, light-weight Air-Wound Inductors—all shapes, types, and sizes—for every radio amateur and industrial requirement.



INDUCTOR COIL *Headquarters*

BARKER & WILLIAMSON • 235 FAIRFIELD AVENUE • UPPER DARBY, PA

World Radio History

No matter what the Frequency
BE SURE YOU'RE ON IT!

The postwar Browning Frequency Meter, like pre-war and wartime models, will assure you of meeting FCC requirements.

Like its popular predecessors, it will be a boon to amateur, police, aircraft and other mobile services.

Continued, whole-hearted devotion of all Browning resources and facilities to war service demands prevents any "unveiling" of the new Browning Frequency Meter at this time.

When it does come, it will reflect the expressed desires of many who have written us about it. It will be exactly what you want.

You'll be glad you waited for it!



BROWNING
LABORATORIES, INCORPORATED
WINCHESTER, MASSACHUSETTS



For Quality Leadership in

1

AM and FM communications equipment.

2

**AM and FM broadcast transmitters, remote amplifiers,
and studio accessories.**

3


Amateur Radio Equipment.

THE COLLINS RADIO COMPANY

Cedar Rapids, Iowa

11 West 42nd St., New York 18, N. Y.

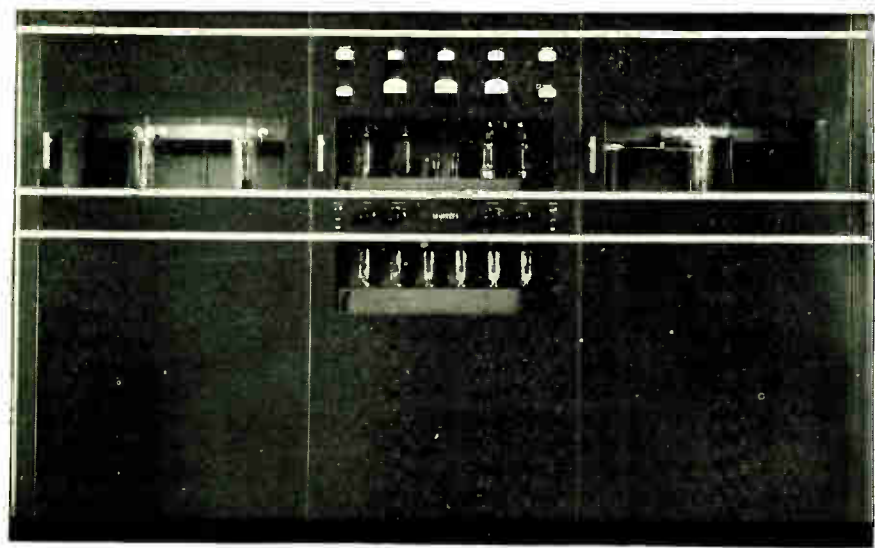Collins equipment is sold in Canada by Collins-Fisher, Ltd., Montreal.



The Collins 21A 5 KW AIR COOLED BROADCAST TRANSMITTER

Broadcast Transmitters and Accessories

featuring high fidelity, and increased safety factors through use of oversize components



1. 21A, 5 kw, automatic reduction to 1 kw.
2. 20T, 1 kw, automatic reduction to 500w.
3. 300G, 250w, automatic reduction to 100w.
4. 12Y remote amplifier, 1 channel, a.c. or d.c.
5. 12Z remote amplifier, 4 channel, a.c./d.c.
6. Three types of studio consoles.
7. Program, limiting, and line amplifiers and monitors.


FM COMMUNICATION AND BROADCAST TRANSMITTERS

1. 250 watt and 25 watt fixed and mobile communication transmitters, 30-162 Mc. range.
2. FM communication receivers for specific applications.
3. Complete line of FM broadcast equipment, including both transmitting and studio equipment.

AMATEUR RADIO EQUIPMENT

In prewar years, Collins came to be known as headquarters for highest quality amateur equipment. Continuing that tradition, our new contributions to ham radio will have the added experience and knowledge gained by supplying radio equipment for war time usage. Look to Collins for a versatile transmitter that is complete in every respect, and for a receiver of higher performance under the exacting conditions of ham radio.

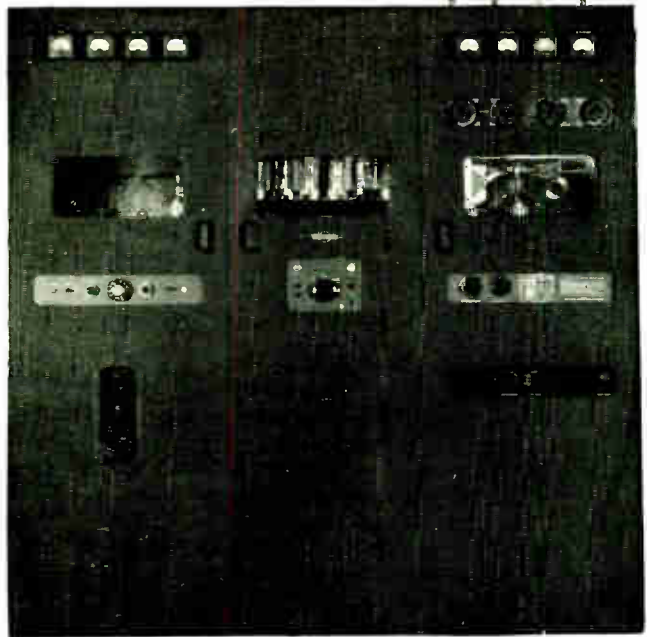
The Collins 231D
3-5 KW
AUTOTUNE
COMMUNICATION
EQUIPMENT



Collins Communication Equipment

1. 231D, 10 channel, 3-5 kw, 2-18.1 Mc Autotune Transmitter.
2. 16F, 10 channel, 300-500 watts, 2-20 Mc Autotune Transmitter.
3. 32RA, 4 channel, band switching, 50-75 watts, 1.5-15 Mc Transmitter.
4. 51J, Communication Receiver, 1.5-36.5 Mc.

The Collins Autotune

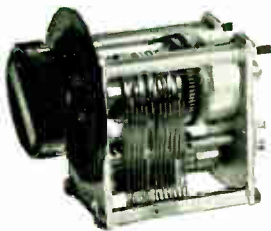

The Collins Autotune is an electrically controlled means of mechanically repositioning adjustable rotary elements. Any combination of such components can be returned to any one of a number of preselected positions. By means of the Collins Autotune system, radio transmitters and receivers can be completely retuned in a matter of a very few seconds.



..... IN RADIO COMMUNICATION IT'S

Capacitors FOR THE AMATEUR



Whether you're building new gear for your ham shack — or whether you're rebuilding the old — you'll find TOBE capacitors fit in wherever you need convenience and dependability

From the smallest mica or oil-paper by-pass unit to the largest Xmitting filter block, TOBE gives you convenience in diversified styles, mountings, and terminal arrangements — plus the ability to stand up under every operating condition.

Ask your jobber for TOBE capacitors and write directly to our capacitor division for recommendations on capacitor uses.



• FIELD OFFICES IN NEW YORK CITY • CHICAGO • DETROIT • GLENDALE, CALIFORNIA •



—Your Microphone is here

As outstanding manufacturers of Microphones for war—Shure offers a complete Microphone line. You will find the proper Microphone for every need above. A complete description of any model will be furnished upon request.

- | | |
|-------------------------------------|---------------------------|
| A. Super-Cardioid Broadcast Dynamic | G. Lapel Microphone |
| B. Unidyne Cardioid Dynamic | H. Military Carbon |
| C. Uniplex Cardioid Crystal | I. Throat Microphone |
| D. Stratoliner Dynamic | J. Carbon Hand Microphone |
| E. Laboratory Non-Directional | K. Mask Microphone |
| F. "Economy" Crystal | L. Stethophone |
| M. Vibration Pick-up | |

Crystal Microphones licensed under patents of The Brush Development Company

SHURE BROTHERS

Designers and Manufacturers of Microphones and Acoustic Devices

225 West Huron Street, Chicago 10, Illinois • Cable Address: SHUREMICRO

MICRO SWITCH

Division of First Industrial Corporation
Home Office and Plant: Freeport, Illinois

43 East Ohio Street
Chicago 1, Illinois

101 Park Avenue
New York 17, New York

BRANCH
OFFICES:

4900 Euclid Avenue
Cleveland 3, Ohio

1709 West 8th Street
Los Angeles 14, California

126 Newbury Street
Boston 16, Massachusetts

The Precise, Small, Lightweight, Sensitive Switch for Radio Applications

Micro Switch precision snap-action switches have proven invaluable for applications that call for switching substantial amounts of power by a unit operating in a small space. Micro Switch products are important electrical switching units for electrical mechanisms that make change, package products, control temperatures, heat water, bottle fluids, limit machine tools, record airplane flights, control electronic tubes and perform thousands of other diversified electrical control functions.

MICRO SWITCH Products Meet These Requirements

Small Size . . . No larger than your thumb, the basic, plastic enclosed switch measures $\frac{1}{16}$ " x $\frac{1}{32}$ " x $1\frac{1}{16}$ ", (shown in hand, below).

Light Weight . . . With pin-type plunger, the plastic enclosed switch weighs less than one ounce.

Long Life . . . Patented three-bladed beryllium copper spring gives millions of accurate repeat operations.

Small Operating Force . . . Force required to operate the switch may be as little as one ounce . . . or as much as 60 ounces.

Small Operating Movement . . . Movement of the operating plunger may be as little as .0004" . . . or as much as $\frac{1}{4}$ ".

Good Electrical Capacity . . . Switch is Underwriters' listed and rated at 1200 V. A. at 125 to 460 volts a.c.



KEEP ON BUYING BONDS!

© 1945 First Industrial Corporation




MICRO-SWITCH Actuators To Meet Every Requirement


Here are a few typical Micro Switch Actuators which makes these switches useable under a wide variety of special mounting and operating conditions.

Micro Switch Type "MC2711" Auxiliary Actuator for panel mounting. To provide extra overtravel in excess of that obtainable with plastic enclosed switches.

Panel Mount
Actuator
(Short Plunger)

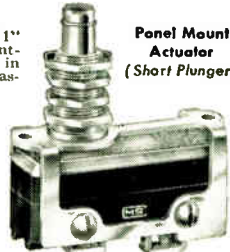


Panel Mount
Actuator
(Long
Plunger)

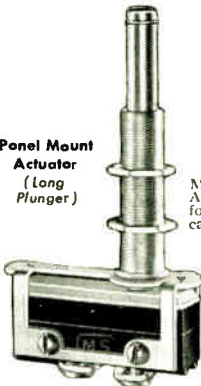


Micro Switch Type "MC7711" Auxiliary Actuator with long plunger overtravel for use with mechanisms whose motion cannot be controlled accurately.

Roller Lever Actuator

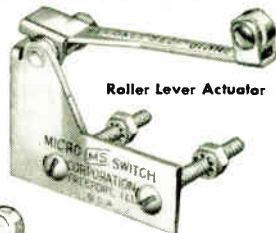

Type "A" Adjustable Actuator

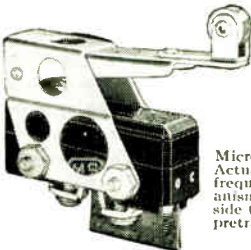

Micro Switch Type "JR" Roller Lever Actuator for use with Basic Switches. This gives long overtravel and light operating force characteristics and protection against wear from side thrust and slide operation.

Micro Switch Type "A" Auxiliary Actuator for use where the operation frequency is high and where the mechanism operating the actuator imparts side thrust. Allows for adjustment of pretravel and operating point.




SEND FOR THIS CATALOG

For full information on Micro Switch products . . . switches, housings and actuators . . . you are invited to send for Micro Switch Handbook-Catalog No. 60.

Ready For Peace

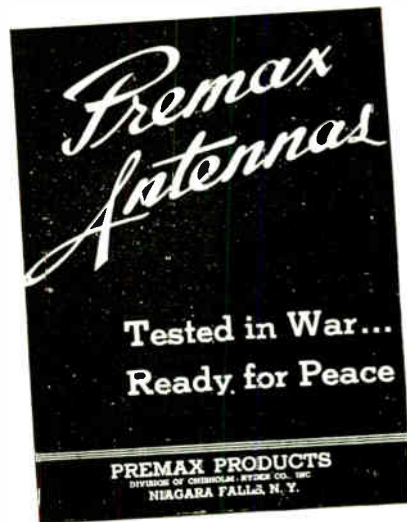After performing exceptional service in the Armed Services of the Allied Nations throughout World War II, Premax Antennas have turned to peacetime manufacture.



Premax Antennas and Mountings

Premax Tubular Metal Antennas are now available for commercial and mobile installations as well as for amateurs who realize the necessity of having the best equipment available.

There are standard designs in steel, monel, aluminum and stainless steel... all on accepted types that have been proven in wartime service under the most trying conditions.

For mobile units, the Premax Police Antennas and Mountings have a wide acceptance.

When planning your post-war equipment, it will pay you well to investigate Premax Antennas and Mountings.

Premax Products
Division of Chisholm-Ryder Co., Inc.
4622 Highland Ave. Niagara Falls, N. Y.



AMPEREX

A Scientific Laboratory Geared
for Large-Scale Production
of Water and Air Cooled

TRANSMITTING and RECTIFYING TUBES

AMPEREX TRANSMITTING TUBES

WATER-COOLED TYPES

TYPE NO.	FILAMENT		Mu	Gm	Capacitance Grid to Plate	*PLATE			*Nominal Output Watts	Max. Freq. MC.	
	Volts	Amps.				Max. Volts	Max. Amps.	Max. Dissipation Watts		At Max. Plate Input	At 50% Max. Plate Input
207	22.0	52.0	20.0	6500	27.0	15000	2.00	10000	C20000	1.6	20
220C	21.5	41.0	35.0	5000	22.0	15000	1.00	10000	BR2500	3.0	30
228A	21.5	41.0	17.0	6500	23.4	6000	.75	3000	BR1000	1.5	20
232C	20.0	72.0	40.0	8000	22.0	20000	2.00	20000	BR8500	1.5	20
233	24.0	70.0	52.0	16500	25.0	15000	4.00	25000	C35000	7.5	30
342A	20.0	67.0	40.0	6820	27.0	18000	1.40	25000	BR8500	4.0	16
343A	21.5	57.5	40.0	6750	23.5	15000	.70	10000	BR3500	4.0	8
520B	22.0	34.0	17.0	5000	27.0	10000	1.20	5000	C5000	2
846	11.0	51.0	40.0	2800	9.0	7500	1.00	1600	C2500	50	150
858	22.0	52.0	42.0	4500	18.0	20000	2.00	20000	C20000	1.6	40
859	11.0†	71.0	36.0	8000	15.0	20000	3.50	20000	C35000	1.5	40
889	11.0	195.0	21.0	8000	17.5	7500	2.00	5000	C10000	50	150
891**	11.0†	60.0	8.0	4200	27.0	15000	2.00	5000	B22000	1.6	20
892**	11.0†	60.0	50.0	7000	32.0	10000	1.00	6600	CP6000	1.6	20

† Single or two-phase filament (two units); voltage is per unit. ** Single or two-phase filament excitation.

FORCED-AIR COOLED TYPES

TYPE NO.	FILAMENT		Mu	Gm	Capacitance Grid to Plate	*PLATE			*Nominal Output Watts	Max. Freq. MC.	
	Volts	Amps.				Max. Volts	Max. Amps.	Max. Dissipation Watts		At Max. Plate Input	At 50% Max. Plate Input
220R†	21.5	41.0	35.0	5000	22.0	12500	1.00	6000	BR2500	4.0	30
232R†	20.0	72.0	40.0	8000	22.0	12500	2.00	7500	CP10000	3.0	20
233R†	24.0	70.0	52.0	16500	26.5	12000	4.00	10000	C15000	7.5	30
235R	14.5	39.0	14.0	16500	9.0	4000	1.25	1500	C2000	90	200
343R†	21.5	57.5	40.0	6750	23.5	7500	1.50	5000	CP5000	4.0	30
889R	11.0	125.0	21.0	8000	19.0	6000	1.00	3000	CP4000	25	100
891R†	11.0†	60.0	8.0	4200	28.0	10000	2.00	4500	B10000	1.6	20
892R†	11.0†	60.0	50.0	7000	32.0	8500	1.00	4000	CP5000	1.6	20
HF3000°	21.5	40.5	16.0	6500	10.0	10000	1.35	3000	C7500	20	50
Z83200°	21.5	40.5	85.0	5000	10.0	10000	1.50	2000	B8000	20	50

† Single or two-phase filament (two units); voltage is per unit. ° All glass radiation and air-cooled transmitting tubes.
 □ \$30.00 credit will be allowed against purchase of new tube if radiator and crate are returned in good condition.
 † \$75.00 credit will be allowed against purchase of new tubes if radiator and crate are returned in good condition. * Ratings given are typical of the class of service in which the tube is most commonly used. See next page for alphabetical designations.

TYPE NO.	FILAMENT		Mu	Gm	Capacitance Grid to Plate	* PLATE			*Nominal Output Watts	Max. Freq. MC.	
	Volts	Amps.				Max. Volts	Max. Ma.	Max. Dissipation Watts		At Max. Plate Input	At 50% Max. Plate Input
AB-150	10.0	3.25	5.3	3400	9.5	1500	100	AB150
HF-60	10.0	2.50	20.0	5000	5.2	1600	150	60	C100	30	100
HF-75	10.0	3.25	12.5	4000	2.0	2000	120	75	C150	75	200
HF-100	10.0	2.50	23.0	4200	4.5	1500	150	75	C150	30	150
HF-120	10.0	3.25	12.0	4500	10.5	1250	175	100	C150	20	80
HF-125	10.0	3.25	25.0	4500	11.5	1500	175	100	C200	30	90
HF-130	10.0	3.25	12.5	4300	9.0	1250	210	125	C170	20	90
HF-140	10.0	3.25	12.0	4500	12.5	1250	175	100	C150	15	60
HF-150	10.0	3.25	12.5	4300	7.2	1500	210	125	C200	30	100
HF-175	10.0	4.00	18.0	5000	6.3	2000	250	125	C300	25	100
HF-200	10.5	4.00	18.0	5000	5.8	2500	200	150	C350	20	100
HF-250	10.5	4.00	18.0	5000	5.8	3000	200	150	C375	20	100
HF-300	11.0	4.00	23.0	5600	6.5	3000	275	200	C600	20	100
ZB-120	10.0	2.50	30.0	5000	5.2	1500	160	75	B300	30	90
111H	10.0	2.50	23.0	4200	4.6	1500	160	75	C175	25	50
203A	10.0	3.25	25.0	4500	13.5	1250	175	100	C150	15	80
203H	10.0	3.25	25.0	4500	11.5	1500	175	100	C200	30	90
204A	11.0	3.85	23.0	4000	15.0	2500	275	250	C500	3	30
211	10.0	3.25	12.0	4500	12.5	1250	175	100	C150	15	80
211C	10.0	3.25	12.5	4300	9.0	1250	210	125	C175	20	90
211H	10.0	3.25	12.5	4300	7.2	1500	210	125	C200	30	100
212E	14.0	6.00	16.0	8000	19.0	2000	350	275	BR75	1.5	3.0
241B	14.0	6.00	16.0	8500	18.8	2000	350	275	C400	7.5	20
242A	10.0	3.25	12.5	3600	13.0	1250	150	85	A20	6	25
242B	10.0	3.25	12.5	3600	13.0	1250	150	100	A20	6	25
242C	10.0	3.25	12.5	3600	13.0	1250	150	100	A20	6	25
251A	10.0	16.00	10.5	3800	8.0	3000	600	1000	C1200	30	60
261A	10.0	3.25	12.0	4000	9.0	1250	210	125	C175	30	50
270A	10.0	9.75	16.0	5700	21.0	3000	375	350	C700	7.5	20
276A	10.0	3.25	12.0	4000	9.0	1250	210	125	C175	30	50
279A	10.0	21.00	10.0	5000	18.0	3000	800	1200	BR500	20	40
304B	7.5	3.25	11.0	2000	2.5	1250	100	50	C85	100	350
308B	14.0	6.00	8.0	7500	17.4	2250	325	250	A50	1.5	3
801	7.5	1.25	8.0	1600	6.0	600	70	42	C25	60	120
805	10.0	3.25	50.0	4800	6.0	1500	210	125	B400	30	80
810	10.0	4.50	35.0	5000	4.8	2000	250	125	C375	30	100
813	10.0	5.00	0.2	2000	180	100	C250	30	60
830	10.0	2.50	8.0	2000	9.9	750	130	40	C60	6	50
830B	10.0	2.50	25.0	3080	11.0	1000	150	60	B175	15	65
833A	10.0	10.00	35.0	8000	6.3	3000	500	300	C1000	30	100
834	7.5	3.25	11.0	2000	2.5	1250	100	50	C75	100	350
838	10.0	3.25	50.0	4800	8.0	1250	175	100	B275	30	120
841	7.5	1.25	30.0	750	7.0	425	60	15	B25	6	50
842	7.5	1.50	3.0	1250	7.0	425	12	A3
845	10.0	3.25	5.3	3400	11.5	1250	75	A25
849	11.0	5.00	19.0	6000	33.0	3000	350	300	B1225	3	30
849A	11.0	7.70	19.0	7600	11.5	4000	500	500	B1900	3	30
849H	11.0	7.70	19.0	7600	11.5	3500	500	500	C1180	20	40
851	11.0	15.50	20.5	15000	47.0	2500	1000	750	C1700	3	15
852	10.0	3.25	12.0	1200	2.6	3000	150	100	C165	30	120

Ratings given are typical of the class of service in which the tube is most commonly used.

The letter preceding each rating identifies the particular class of service as follows:

— power output per tube as Class A power amplifier and modulator

AB—power output per pair of tubes as Class AB power amplifier and modulator

B — power output per tube as Class B power amplifier and modulator

BR—power output per pair of tubes as Class B Radio Frequency power amplifier

C — power output per tube as Class C power amplifier or oscillator

CP—power output per tube as Class C plate modulated power amplifier

AMPEREX RECTIFYING TUBES

MERCURY VAPOR RECTIFIERS

TYPE NO.	FILAMENT		Peak Inverse Volts	Approx. Ave. Plate Amps.	Peak Plate Amps.
	Volts	Amps.			
249B	2.5	7.50	7500	0.50	1.5
258B	2.5	7.50	7500	0.50	1.5
266B	5.0	42.00	22000	7.00	20.0
267B	5.0	6.75	10000	1.25	5.0
315A	5.0	10.00	15000	1.50	6.0
575A	5.0	10.00	15000	1.50	6.0
857B	5.0	40.00	22000	10.00	40.0
866	2.5	5.00	7500	0.25	1.0
866A	2.5	5.00	10000	0.25	1.0
869B	5.0	20.00	20000	2.50	10.0
872A	5.0	6.75	10000	1.25	5.0

WATER-COOLED VACUUM RECTIFIERS

TYPE NO.	FILAMENT		Peak Inverse Volts	Ave. Emission Amps.	Peak Plate Amps.
	Volts	Amps.			
222A	21.5	41.00	25000	7.0	5.5
237A	20.0	61.00	50000	10.0	8.0

RADIATION COOLED HIGH VACUUM RECTIFIERS

TYPE NO.	FILAMENT		Peak Inverse Volts	Approx. Peak Plate Rate Amps.	Peak Rate Amps.
	Volts	Amps.			
217C	10	3.25	7500	0.150	0.600
221A	5	10	25000	0.300	1.5
404	20	35	120000	0.400	1.5
8020	5	6	40000	0.100	0.750

AMPEREX


ELECTRONIC PRODUCTS

25 Washington St. • Brooklyn 1, N. Y.

* Actual value will depend on wave-form resulting on load and filter circuit.

P. R. MALLORY & CO. Inc.
MALLORY

Approved Precision Products

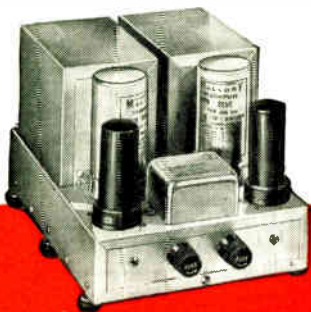

The Vibrapack line includes models for input voltages of 6, 12, and 32 volts DC and nominal output voltages from 125 to 400. Models available with switch for four output voltages in 25-volt stages. Hermetically sealed vibrators. High efficiency—low battery drain.

Vibrapacks* Provide Dependable Plate Power for Portable Equipment

Mallory Vibrapacks provide economical, efficient and dependable plate power for operating radio receivers, transmitters, PA systems, direction finders and other electronic equipment on vehicles, farms, portable equipment, or wherever commercial AC power is unavailable.

Write for Form E-555 for detail information



Mallory Transmitting Capacitors

Built with adequate safety factor for long life. Round and square can styles. Available in 20 stock sizes, working voltages from 600 to 6,000.



Vitreous Enamel Resistors

Mallory fixed and adjustable power resistors provide maximum efficiency in operation with excellent temperature and humidity characteristics. Available in rated capacities from 10 to 200 watts, resistances from 1 to 100,000 ohms.

Ham Band Switches

Ceramic insulation provides low losses at high frequencies. The Mallory Ham Band Switch is rated for use in transmitter plate circuits using up to 1,000 volts DC with power up to 100 watts, inclusive.



OTHER MALLORY PRODUCTS INCLUDE:

Attenuators
 Battery Chargers
 Capacitors, Dry Electrolytic
 Capacitors, Paper

Ham Band Switches
 Jacks
 Jack Switches
 Knobs
 "L" Pad Attenuators
 Noise Filters

Plugs
 Potentiometers
 Push Button Switches
 Rectifiers, Dry Disc Resistors
 Rheostats

"T" Pad Attenuators
 Variohn* Resistors
 Vibrators
 Vitreous Resistors
 Volume Controls
 *Reg. U.S. Pat. Off.

All Mallory standard parts available from Mallory Distributors

Write for Catalog

FOR IMPROVED PERFORMANCE USE MALLORY APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

EXCELLENCE

IS BUILT INTO

Sangamo MICA CAPACITORS

★ The many processes that are required in producing SANGAMO MICA CAPACITORS involve numerous critical operations. Some of these are MICA SPLITTING, MICA GAUGING, MICA PUNCHING, MICA INSPECTION, and CAPACITOR STACKING.

★ To achieve EXCELLENCE, a well planned, effective quality control is maintained every step of the way. Skilled operators have the most modern mechanical equipment with which to work. This, together with competent supervision, has enabled SANGAMO to play an important part in meeting the heavy and exacting requirements of wartime America.

★ The complete line of SANGAMO MICA CAPACITORS merits every confidence of the most exacting user of Capacitors.



SANGAMO ELECTRIC COMPANY **SPRINGFIELD ILLINOIS**





MODEL EC-1A

ECHOPHONE COMMERCIAL

*A real communications receiver
at a sensationally low price*

The 1946 Echophone, Model EC-1A is a 6-tube AC/DC communications receiver of outstanding value. With electrical bandspread throughout its frequency range of .55 to 30 megacycles, BFO for CW reception, and a new automatic noise limiter to sup-

press interference from automobile ignition, etc., the EC-1A provides genuine communications receiver performance in the lowest price range. Standard 115-volt AC or DC operation; also available for 220 to 250-volt operation.

FEATURES

1. Frequency coverage, .55 to 30 mc, complete in three bands.
2. Electrical bandspread on all bands with dial indicator.
3. Dial calibrated in megacycles with all important service bands identified.
4. Beat frequency oscillator for CW reception.
5. Automatic noise limiter.
6. Self-contained PM dynamic speaker.
7. Headphones or speaker selected by panel switch, headphones completely isolated by means of phone circuit transformer.
8. AC/DC operation 115 volts or 220 to 250 volts available with external line cord.
9. Good selectivity combined with exceptional sensitivity.
10. Modern 6-tube superheterodyne circuit.

SPECIFICATIONS

Tube Lineup:

1—12SA7 Mixer; 1—12SK7 I.F. Amplifier; 1—12SQ7 Second Detector, First Audio Amplifier and AVC; 1—35L6GT Second Audio Amplifier; 1—12SQ7 Beat Frequency Oscillator and Automatic Noise Limiter; 1—35Z5GT Rectifier.

Controls:

TUNING, BAND SPREAD, VOLUME, BAND SELECTOR, CW/AM, NOISE LIMITER, PHONES/SPEAKER, STAND BY. (BFO pitch adjustment conveniently located on rear of chassis.)

External Connections:

(On rear of chassis.) Power line cord,

phone tip jacks, antenna (doublet or single wire and ground).

Physical Characteristics:

The EC-1A is housed in a metal cabinet attractively finished in machine tool gray wrinkle lacquer. The cadmium plated steel chassis is substantially constructed. The PM dynamic speaker is mounted in the top of the cabinet and is protected by special sound projecting louvers instead of the ordinary grill.

Dimensions:



8" high, 11 $\frac{1}{4}$ " wide, 8 $\frac{1}{8}$ " deep; overall. Act. wt., 11 lbs. Ship. wt., 22 lbs. Model EC-1A Amateur Net Price, \$29.50.

ECHOPHONE

ECHOPHONE DIVISION • THE HALLICRAFTERS CO. • 2611 INDIANA AVE., CHICAGO 16, U.S.A.

"SEALED LIKE A

VACUUM TUBE"

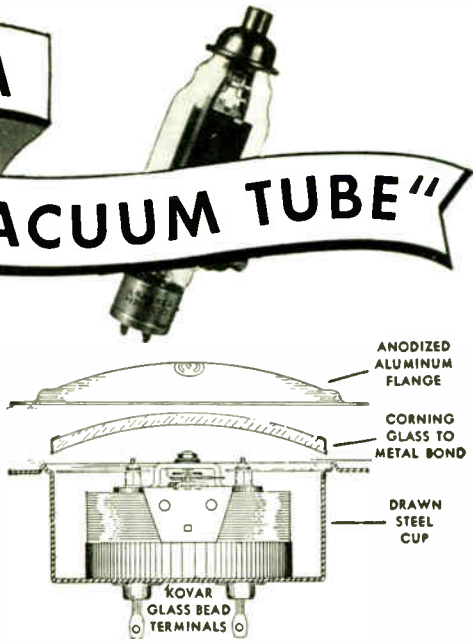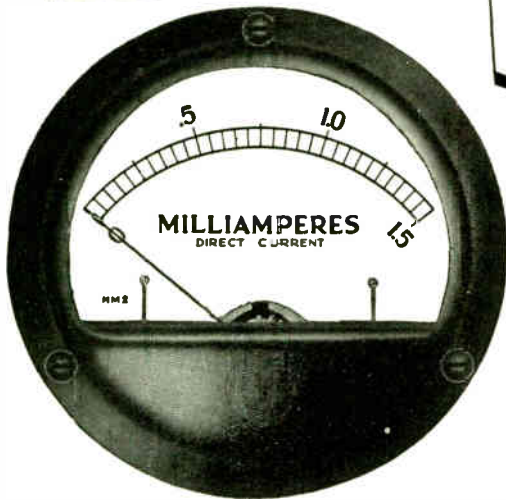

Marion Glass-to-Metal Truly Hermetically Sealed 2½" and 3½" Electrical Indicating Instruments

By building the mechanism into a one-piece, drawn steel cup, and then sealing the glass cover to the metal rim, perfect hermetic sealing has been achieved with a minimum number of seals. *Marion "hermetics" are positively interchangeable, and cost no more than standard unsealed instruments.* Not only do we offer these instruments in standard ranges, but we also specialize in supplying them with special and unusual characteristics for new and unusual applications.

- There are no rubber gaskets, no cement seals.
- Can be immersed in boiling brine solution for weeks without deterioration of seals.
- Windows are of double thickness *tempered* glass processed for solder sealing, and are highly resistant to shock.
- Instruments are completely dehydrated and are filled with dry air at sea level pressure.
- A newly designed crowned crystal permits greater scale length, reduces shadows, and makes for better visibility.
- Magnetic shielding permits interchangeability on any type of panel without affecting calibration; can be supplied silver plated for extra R.F. shielding.
- Silver clad beryllium copper hair springs reduce zero shift at all temperatures.
- Standard Kovar glass bead type terminals with solder lugs.
- Special phosphate finish on cases meets two-hundred-hour salt spray test.
- Window sealing process developed and perfected in cooperation with engineers of the Corning Glass Co.
- Instruments manufactured in accordance with AWS Spec. C-39.2 1944 *plus* hermetic sealing.

TYPE HM 2 DIRECTLY INTERCHANGEABLE WITH AWS TYPE MR 24 AND 25
TYPE HM 3 DIRECTLY INTERCHANGEABLE WITH AWS TYPE MR 34 AND 35

Available in all DC ranges. Write for booklet.



MARION ELECTRICAL INSTRUMENT CO.
 MANCHESTER, NEW HAMPSHIRE

EXPORT DIVISION 458 BROADWAY • NEW YORK 13, N. Y., U. S. A.
 CABLE ADDRESS: MORHANEX

**HORN TYPE
LOUD SPEAKERS**

**Jensen
Technical
Monograph**

25c

**WHAT ABOUT
Horn
LOUD SPEAKERS?**



What effect do horn formula, flare and length have on low frequency "cut off?" In the most commonly used frequencies which horn is most directional—one with large or one with small mouth? What are the advantages of the reflex type horn? How is a 500-watt "bull horn" constructed? What are the advantages of the new Hypex,* originated by JENSEN, over the exponential type horn?

"HORN TYPE LOUD SPEAKERS"—JENSEN Monograph No. 5.—the latest number in the JENSEN Monograph series and now available, discusses simply and clearly these and many other questions pertinent to the study of electroacoustics. By means of photographs, diagrams and graphs it reviews the principles, performance characteristics and applications of horn type loud speakers and illustrates modern reproducers employing horns.

Get your copy of this or any others of the series today from your JENSEN jobber or dealer or from the JENSEN Technical Service Department. Price each 25c.

Specialists in Design and Manufacture of Fine Acoustic Equipment



Jensen

FREE to merit in the Armed Services, and to Technical Schools, Colleges and Libraries.

Jensen RADIO MANUFACTURING COMPANY
5635 South Laramie Avenue, Chicago 38, Ill.

Send me the Monographs checked:

- (1) "Loud Speaker Frequency-Response Measurements"
- (2) "Impedance Matching and Power Distribution"
- (3) "Frequency Range in Music Reproduction"
- (4) "The Effective Reproduction of Speech"
- (5) "Horn Type Loud Speakers"

Send 25c
for each
book ordered.

Name _____

Address _____

City _____ Zone _____ State _____



*Trade Mark Registered; U. S. Patent No. 2,330,262


METAL HOUSINGS

for
**COMMUNICATION
APPARATUS**

Custom-quality is a characteristic of skillful workmanship—the result of years of specialization.

Par-Metal Products have this quality—plus the virtues of ruggedness and economy as well.

Write for Catalogue No. 41-A.

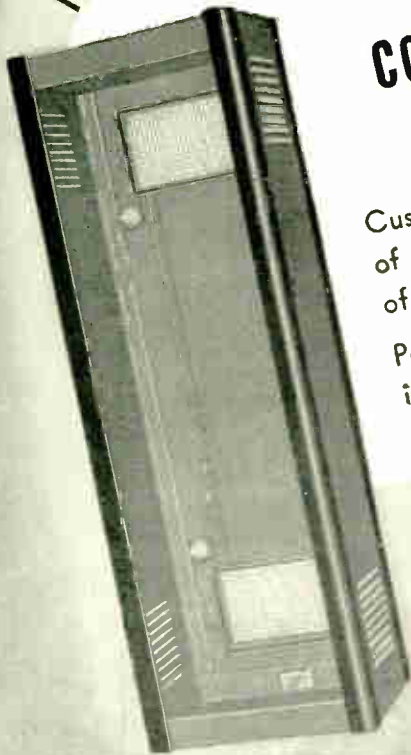

• CABINETS • CHASSIS
• PANELS • RACKS

PAR-METAL PRODUCTS CORPORATION

32-62—49th STREET . . . LONG ISLAND CITY, N. Y.

Export Dept. 100 Varick St., N. Y. C.



K-2
Crystal

D-104
Crystal

T-3
Crystal

WR
Crystal

PICKUP CARTRIDGE

FP SERIES
PICKUP


GDN SERIES
Dynamic

The Astatic Corporation
CONNEAUT, OHIO.

ASTATIC

ASTATIC CRYSTAL DEVICES
MANUFACTURED UNDER BRUSH
DEVELOPMENT CO. PATENTS

RADIO SUPPLIES AND SATELLITES

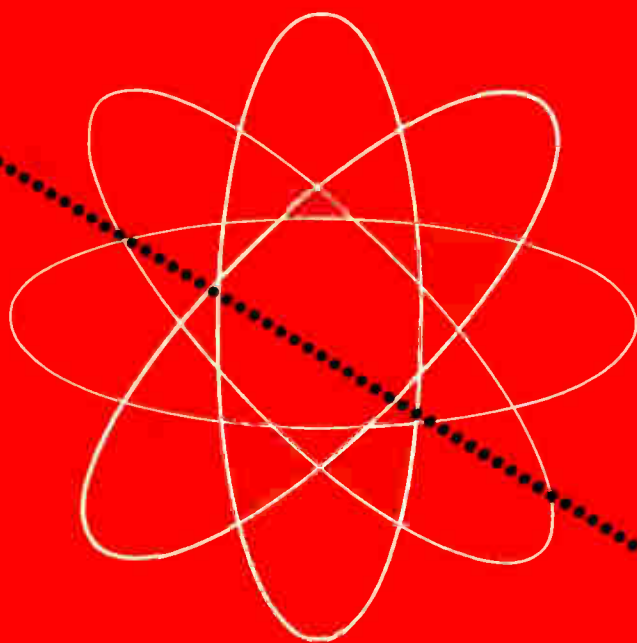

ELECTRONIC EQUIPMENT

Available — through
hallicrafters, agent for RFC

head phones • test equipment • component parts
• marine transmitters and receivers • code practice
equipment • sound detecting equipment •
vehicular operation police and command sets •
radio beacons and airborne landing equipment

*Write or wire for lists of available equipment
Specify types of equipment in which you are interested*

hallicrafters RADIO

Agent for RFC under contract SIA-3-24. Address: Hallicrafters,
RFC Dept. 010, 5025 West 65th Street, Chicago 38, Illinois
MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT

Learn Code the EASY Way

Beginners, Amateurs and Experts alike recommend the INSTRUCTOGRAPH, to learn code and increase speed.

Learning the INSTRUCTOGRAPH way will give you a decided advantage in qualifying for Amateur or Commercial examinations, and to increase your words per minute to the standard of an expert. The Government uses a machine in giving examinations.

Motor with adjustable speed and spacing of characters on tapes permit a speed range of from 3 to 40 words per minute. A large variety of tapes are available — elementary, words, messages, plain language and coded groups. Also an "Airways" series for those interested in Aviation.

MAY BE PURCHASED OR RENTED

The INSTRUCTOGRAPH is made in several models to suit your purse and all may be purchased on convenient monthly payments if desired. These machines may also be rented on very reasonable terms and if when renting should you decide to buy the equipment the first three months rental may be applied in full on the purchase price.

ACQUIRING THE CODE

It is a well-known fact that practice and practice alone constitutes ninety per cent of the entire effort necessary to "Acquire the Code," or, in other words, learn telegraphy either wire or wireless. The Instructograph supplies this ninety per cent. It takes the place of an expert operator in teaching the student. It will send slowly at first, and gradually faster and faster, until one is just naturally copying the fastest sending without conscious effort.

BOOK OF INSTRUCTIONS

Other than the practice afforded by the Instructograph, all that is required is well directed practice instruction, and that is just what the Instructograph's "Book of Instructions" does. It supplies the remaining ten per cent necessary to acquire the code. It directs one how to practice to the best advantage, and how to take advantage of the few "short cuts" known to experienced operators, that so materially assists in acquiring the code in the quickest possible time. Therefore, the Instructograph, the tapes, and the book of instructions is everything needed to acquire the code as well as it is possible to acquire it.

MACHINES FOR RENT OR SALE



The Instructograph

ACCOMPLISHES THESE PURPOSES:

- FIRST:** *It teaches you to receive telegraph symbols, words and messages.*
- SECOND:** *It teaches you to send perfectly.*
- THIRD:** *It increases your speed of sending and receiving after you have learned the code.*


With the Instructograph it is not necessary to impose on your friends. It is always ready and waiting for you. You are also free from Q.R.M., experienced in listening through your receiver. This machine is just as valuable to the licensed amateur for increasing his speed as to the beginner who wishes to obtain his amateur license.

Postal Card WILL BRING FULL PARTICULARS IMMEDIATELY

THE INSTRUCTOGRAPH CO.

4705 SHERIDAN ROAD

CHICAGO, ILLINOIS

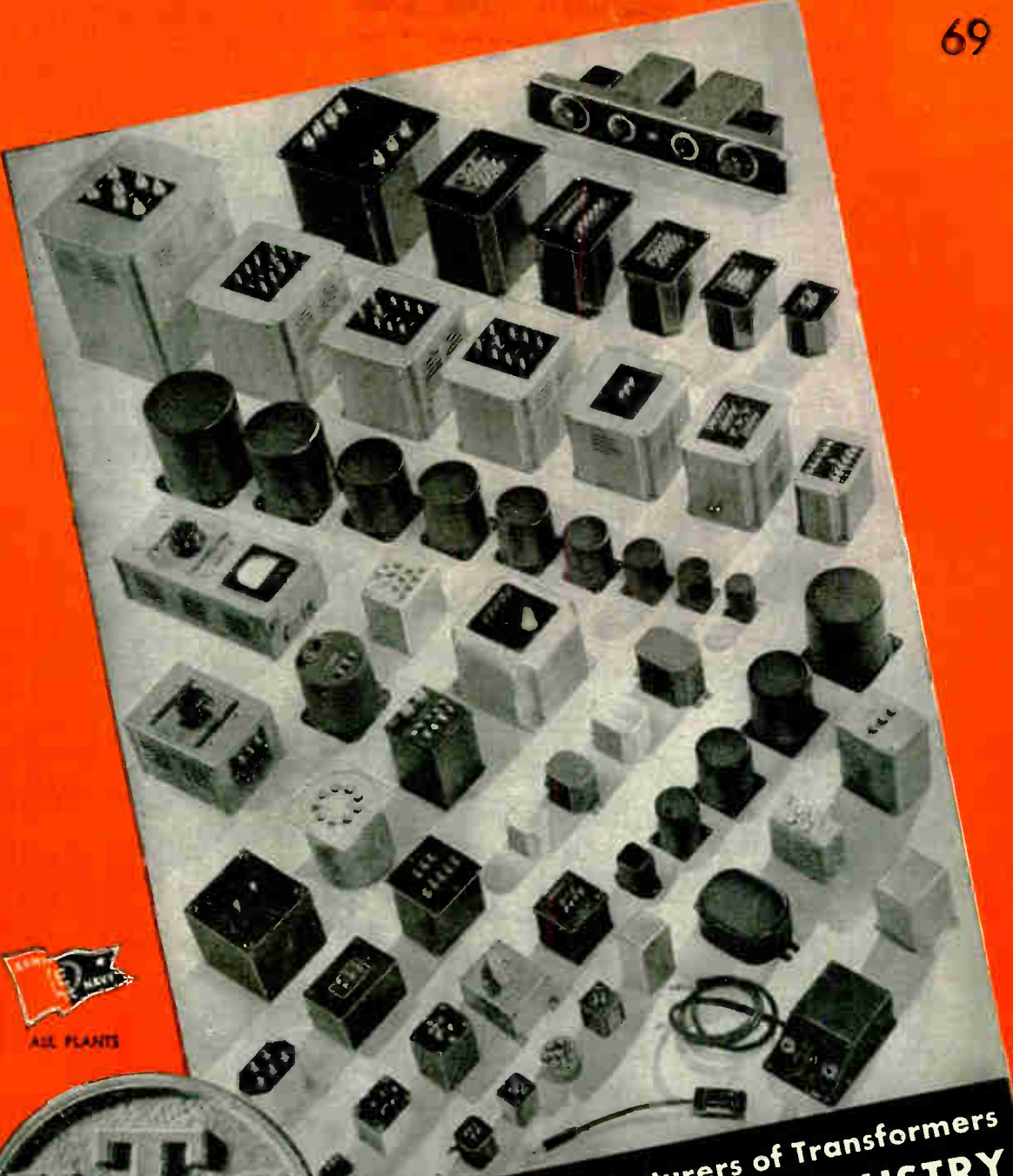

Foremost Manufacturers of Transformers
to the **ELECTRONIC INDUSTRY**

United Transformer Corp.

150 VARICK STREET

NEW YORK 13, N. Y.

EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y., CABLE: "ARLAN"

... interesting, attractive pages from a book every ham and electronic engineer will want to own . . .

TRIM-AIR MIDGET CAPACITORS

Single and Dual . . .



GENERAL SPECIFICATIONS

TYPE: . . .
RANGE: . . .
CAPACITANCE: . . .

TYPE	MIN. CAPACITANCE	MAX. CAPACITANCE	MIN. VOLTAGE	MAX. VOLTAGE
100	100	100	100	100
200	200	200	200	200
300	300	300	300	300
400	400	400	400	400
500	500	500	500	500
600	600	600	600	600
700	700	700	700	700
800	800	800	800	800
900	900	900	900	900

TYPE	MIN. CAPACITANCE	MAX. CAPACITANCE	MIN. VOLTAGE	MAX. VOLTAGE
100	100	100	100	100
200	200	200	200	200
300	300	300	300	300
400	400	400	400	400
500	500	500	500	500
600	600	600	600	600
700	700	700	700	700
800	800	800	800	800
900	900	900	900	900

TYPE	MIN. CAPACITANCE	MAX. CAPACITANCE	MIN. VOLTAGE	MAX. VOLTAGE
100	100	100	100	100
200	200	200	200	200
300	300	300	300	300
400	400	400	400	400
500	500	500	500	500
600	600	600	600	600
700	700	700	700	700
800	800	800	800	800
900	900	900	900	900



CARDWELL QUALITY PRODUCTS: STANDARD OF COMPARISON

THE VALUABLE NEW CARDWELL CATALOG No. 46

containing 24 pages of descriptions, charts and photos of Cardwell Variable and Fixed Air Dielectric Condensers and Cardwell Flexible and Rigid Couplings and Electronic Accessories

for almost* every application . . .

*We say almost every application because no one can anticipate every conceivable need of the postwar capacitor consumer. Cardwell is, however, prepared as never before to put war tempered facilities and engineers to work on what may be paramount, yet unfilled, needs in the amateur and electronic fields.


That is why we urge you to send for the new Cardwell Catalog No. 46, and tell us what you would like to see added. With your help, we shall try to turn out a complete line of instruments, embodying the fine design and craftsmanship that has always been associated with the Cardwell name. Your copy sent free upon request.



THE ALLEN D. CARDWELL MANUFACTURING CORP.

Main Office: 81 PROSPECT ST., BROOKLYN 1, N. Y.

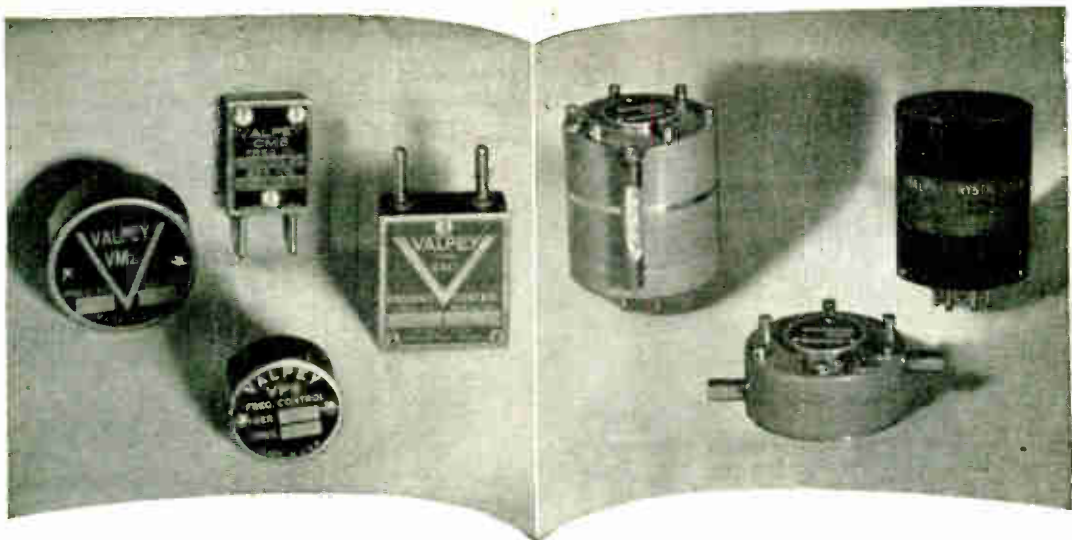Factories: BROOKLYN, N. Y. • PLAINVILLE, CONN.



RELIABLE PERFORMANCE

Is Only One of the Many Reasons Why...

Valpey Crystals

Met the Exact Specifications of Our Armed Forces

With peace there comes again those products of industry such as radio, television, airplanes, refrigerators, washing machines, etc., which never really were luxuries so much as necessities. We are now prepared again

to help build precision parts and accessories for such products required by the electronics industry, as well as help design and produce many complex, new ones that have emerged from war. Plan NOW with—VALPEY.

QUARTZ CRYSTALS for All Frequency
Control Applications

QUARTZ CRYSTAL MOUNTINGS
TEMPERATURE CONTROL OVENS
QUARTZ PRISMS, LENSES and
Special Optical Pieces

WRITE FOR "CRYSTONICS" INFORMATION

VALPEY CRYSTAL CORP.

"Craftsmanship in Crystals since 1931"

HOLLISTON, MASS.



HYTRON TUBES



Whether you are interested in the low or high frequencies — c.w. or 'phone — high or medium mu triodes — the popular beam tetrodes — pentodes — rectifiers — acorns — miniatures — or gaseous voltage regulators — there are Hytron tubes just right for your new rig.

TRIODES You find a wide range of plate dissipation, filament and plate potentials, and amplification factors. Standard replacements, such as the 801A 801, are included, as well as carefully engineered triodes with graphite anodes, dual grid stem leads, filament heat radiators, low-loss lava insulation, and low-loss bases. The twin triodes, 3A5, HY31Z, and HY1231Z, offer special application economies.

V-H-F TRIODES The HY75, HY114B, and HY615 with their familiar grid and plate top caps are automatically associated with Hytron. Suitable for transmitting or receiving, they are extremely popular for efficient v-h-f portable and mobile equipment. The 955 acorn and 9002 miniature are also widely known.

PENTODE The 837 is a popular transmitting pentode with 12.6-volt filament and 12-watt plate dissipation. It is particularly suited for suppressor grid modulation.

R.F. BEAM TETRODES Instant-heating or cathode types for 6 or 12 volt AC or DC filament supplies are offered in a generous variety of plate voltages and plate dissipations. Ideal for mobile use where battery power must be conserved during standby, are the instant-heating 2E25, HY69, and HY1269. Low driving power requirements, freedom from neutralization and ease of band switching on frequencies up to 60 megacycles (100 mc. for the 2E25) — are attractive features of all these beam tetrodes.

ACORN AND MINIATURE PENTODES The 954, 9001, and 6AK5 assure top receiver performance on those higher frequencies.

RECTIFIERS Mercury vapor types are supplemented by the 1616 for applications where filament and plate potentials must be applied simultaneously. The v-h-f 6AL5 has many interesting possibilities: rectifier, detector and avc, clipper, limiter, and fm frequency discriminator.

VOLTAGE REGULATORS Literally millions of the Hytron OC3 VR105 and OD3 VR150 have been sold. They are economical, simple to use, and sure-fire in maintaining steady potentials. The OC3 and OD3 may be used in series for regulating a 250-volt supply. New Hytron miniatures, OA2 and OB2, are compact and closely approximate in performance the standard regulators.

And that's not all! Hytron's wartime experience is bringing you many new tubes — particularly in the u-h-f field — tubes engineered for your exacting needs. Watch for them.

For better reception, it's also I
radio receiving tubes — c



Ever wonder just how tubes are put together? Hytron has a 17 by 21 inch sheet for you which shows the step-by-step assembly of a typical Hytron tube.



HYTRON RADIO AND ELECT

YOUR NEW RIG

HYTRON TRANSMITTING AND SPECIAL PURPOSE TUBES

Description	Type No.	Filament Ratings		Type	Max. Plate Volts	Max. Plate Ma.	Max. Plate Dis.
		Volts	Amps.				
LOW	3A5	1.4	0.22	Oxide	150	30*	2*
	6J5GTX	2.8	0.11				
	10Y	6.3	0.3	Cath.	330	20	3.5
	HY24	7.5	1.25	Thor.	450	65	15
	HY40	2	0.13	Oxide	180	20	2
MEDIUM	HY51A	7.5	2.25	Thor.	1000	125	40
	HY51B	7.5	3.55	Thor.	1000	175	65
	HY51B	10	2.25	Thor.	1000	175	65
MEDIUM	801A/801	7.5	1.25	Thor.	600	70	20
	841	7.5	1.25	Thor.	450	60	15
	864	1.1	0.25	Oxide	135	5	—
HIGH-MU	1626	12.6	0.25	Cath.	250	25	5
	HY30Z	6.3	2.25	Thor.	850	90	30
	HY31Z	6	2.55	Thor.	500	150*	30*
HIGH-MU	HY40Z	7.5	2.6	Thor.	1000	125	40
	HY51Z	7.5	3.55	Thor.	1000	175	65
	HY1231Z	6	3.2	Thor.	500	150*	30*
HIGH-MU	12	1.6					
	2C26A	6.3	1.15	Cath.	3500	NOTE	10
	HY75	6.3	2.6	Thor.	450	80	15
HIGH-MU	HY114B	1.4	0.155	Oxide	180	12	1.8
	HY615	6.3	0.175	Cath.	300	20	3.5
	955	6.3	0.15	Cath.	200	8	1.8
	E114B	6.3	0.175	Cath.	300	20	3.5
	9002	6.3	0.15	Cath.	200	8	1.8
HIGH-MU	2E25	6	0.8	Thor.	450	75	15
	6AR6	6.3	1.2	Cath.	630	60	10
	6L6GX	6.3	0.9	Cath.	500	115	21
	6V6GTX	6.3	0.45	Cath.	350	60	13
	HY60	6.3	0.5	Cath.	425	60	15
	HY61/807	6.3	0.9	Cath.	600	120	25
	HY65#	6	0.8	Thor.	450	75	15
	HY67	6	4.5	Thor.	1250	175	65
	HY69	12	2.25	Thor.	600	100	30
	HY1269	6	3.2	Thor.	750	120	30
HIGH-MU	1625	12.6	0.45	Cath.	600	120	25
	837	12.6	0.7	Cath.	500	80	12
	6AK5	6.3	0.175	Cath.	Sharp cut-off pentode		
HIGH-MU	954	6.3	0.15	Cath.	Sharp cut-off pentode		
	9001	6.3	0.15	Cath.	Sharp cut-off pentode		
HIGH-MU	Type No.	Filament Volts	Filament Amps.	Type	Peak Plate Ma.	Max. D.C. Ma.†	Inv. Peak Pot.
	HY866 Jr.	2.5	2.5	Mer.	500	250	5000
	866A/866	2.5	5.0	Mer.	1000	500	10000
	1616	2.5	5.0	Vac.	800	260	6000
	6AL5	6.3	0.3	Vac.	60	20	460
HIGH-MU	Type No.	Average Operating Voltage	Operating Ma. Min. Max.	Av. Volts Reg.	Min. Starting Voltage		
	OA2	150	5 30	2	185		
	OB2	108	5 30	1	133		
	OC3/VR105	108	5 40	2	133		
	OD3/VR150	150	5 40	3.5	185		

*Both sections of twin triode. †Discontinued; 2E25 supersedes and replaces. ‡Current for full wave.

NOTE: Not recommended for C.W. Consult Hytron Commercial Engineering Dept. for data.



WRITE TODAY for your copy of the Hytron transmitting and special purpose tube catalogue. You should have it for planning your new gear.



oldest manufacturer specializing in
of the popular BANTAM GT.

ONICS CORP., SALEM, MASS.

World Radio History

BURGESS BATTERIES

for every purpose

RECOGNIZED BY THEIR STRIPES • REMEMBERED FOR THEIR SERVICE



No. 4FA

No. 530B

No. F4BP

No. 4FA LITTLE SIX—1½ volts—replaces one round No. 6 cell. Radio “A” type; is recommended for the filament lighting of vacuum tubes. Size, 4¼” x 2⁹/₁₆” x 2⁹/₁₆”. Weight, 1 lb. 5 oz.

No. 530B—45 volt “B” battery equipped with insulated junior knobs. Taps at —, +22½, +45 volts. Size, 5⁷/₈” x 4³/₁₆” x 2⁹/₁₆”. Weight, each—2 lbs. 15 oz.

No. F4BP—A 6 volt, heavy-duty portable battery, designed for Burgess X109 headlight. Contains four F cells connected in series. Screw terminals and brass knurled nuts. Size, 2²¹/₃₂” x 2²¹/₃₂” x 4⁷/₃₂”. Weight, 1 lb. 6 oz.

No. 230B—A 45 volt super-service, standard size radio “B”. Designed for receivers with plate current drain of 10 to 15 milliamperes. Size, 7¹/₈” x 8” x 2⁷/₈”. Weight, 7 lbs. 6 oz.

No. Z30N—45 volt “B” battery. Improved small size. Adapted to radio, portable receivers and transmitters. Screw terminals. Size, 3” x 1⁷/₈” x 4³¹/₃₂”. Weight, 1 lb. 4 oz.

No. 2F2H—A 3 volt radio “A” battery used with portable radios, amplifiers, and special instruments. Size, 2⁵/₈” x 2⁵/₈” x 4³/₈”. Weight, 1 lb. 6 oz.

No. W30BPX—45 volts. Extremely small and light in weight. Very suitable for personal transceivers used by amateur clubs and radio stations. Equipped with insulated junior knobs. Size, 1⁷/₃₂” x 2²¹/₃₂” x 4¹/₁₆”. Weight, 10 oz.

No. Z30N

No. 2F2H

No. W30BPX



VOTED FIRST CHOICE
IN NATIONAL POLL OF ELECTRONIC ENGINEERS

2 out of 3! That's the way electronic engineers voted for Burgess Batteries in a recent survey. Use the brand the experts choose...**BUY BURGESS!**

Fresh Stocks at Your Local Burgess Distributor

BURGESS BATTERY COMPANY
FREEPORT • ILLINOIS

WORLD'S LARGEST and OLDEST MANUFACTURERS OF

Antenna Systems

AND RADIO-ELECTRICAL PRODUCTS



NEW
PLANT
AND
OFFICES

40

YEARS' DEPENDABILITY

BRACH

ESTABLISHED

1906

ANTENNAS

and MOUNTINGS

FOR

AUTOMOBILE, F.M.,

TELEVISION, POLICE,

and MARINE

COLLAPSIBLE . . . SECTIONAL . . . DIRECTION FINDING . . . RADAR
AND CO-AXIAL TYPE. ALL SIZES, LENGTHS and MATERIALS

OTHER BRACH PRODUCTS INCLUDE: LIGHTNING PROTECTIVE DEVICES • JUNCTION
BOXES • POT HEADS • GAS RELAYS • ARRESTER HOUSINGS • PROTECTIVE
PANELS • TERMINALS & HOUSINGS • HIGH TENSION DETECTORS • SOLDER-
ALL & FLUX • SOLDERLESS BEE TERMINAL BLOCKS "LOCK A WIRE TO A WIRE"

TEST-O-LITE, quickly locates trouble in Circuits 100-550 A.C. or D.C.

L. S. BRACH MFG. CORP.

75

NEW PLANT & OFFICE: 200 CENTRAL AVE., NEWARK, N. J.

World Radio History


Laboratory Standards



MODEL 78-B STANDARD SIGNAL GENERATOR
Two Frequency Bands between 15 and 250 megacycles



MODEL 84
U.H.F. STANDARD SIGNAL GENERATOR
300 to 1000 megacycles, AM and Pulse Modulation

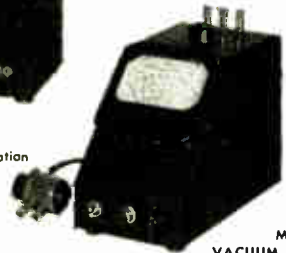

MODEL 62
VACUUM TUBE VOLTMETER
0 to 100 volts AC, DC and R.F.



MODEL 71 SQUARE WAVE GENERATOR
5 to 100,000 cycles
Rise Rate 400 volts per microsecond




MODEL 58 U.H.F. RADIO NOISE
AND FIELD STRENGTH METER
15 to 150 megacycles



MODEL 65-B
STANDARD SIGNAL GENERATOR
75 to 30,000 kilocycles
M.O.P.A., 100% Modulation



MODEL 79-B PULSE GENERATOR
50 to 100,000 cycles
0.5 to 40 microsecond pulse width

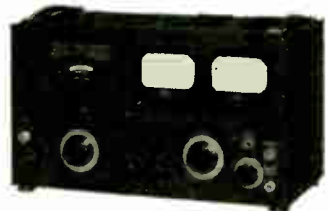


MODEL 80
STANDARD SIGNAL GENERATOR
2 to 400 megacycles
AM and Pulse Modulation

Standards are only as reliable as the reputation of their maker.

M E A S U R E M E N T S C O R P O R A T I O N
B O O N T O N · N E W J E R S E Y

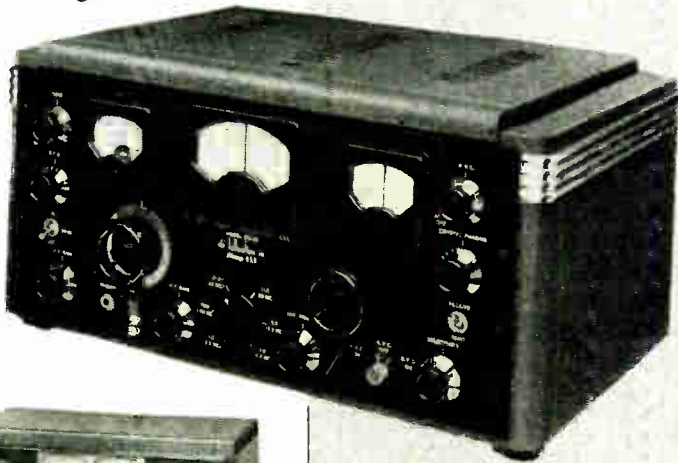Order Your
COMMUNICATION RECEIVER
from the **RADIO SHACK**




Ask about these
 Famous Receivers
 NATIONAL
 HALLICRAFTERS
 HAMMARLUND
 RME
 ECHOPHONE



Now is the time to choose that new "Super-duper" receiver for your post-war ham shack . . . and here's the place to get it, for the Radio Shack has available modern communications receivers, made by leading manufacturers and embodying the latest design features for efficiency and smooth handling.

And you can use your receiver while you are paying for it . . . the Radio Shack time-payment plan requires only a small down payment. Get back in the game with new gear . . . write today for price and time-payment schedule of your post-war receiver.

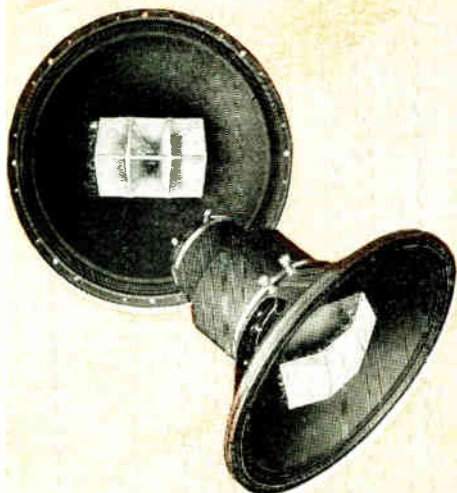The **RADIO SHACK**
 ★ 167 WASHINGTON ST. ★
 BOSTON, MASS., U.S.A.



ALTEC LANSING

Manufacturers of the Speaker

which Revolutionizes the

Methods of Sound Reproduction

● The new Altec Lansing multi-cellular Duplex speaker provides broadcasters, manufacturers and audiences with high quality sound in a frequency range of from 40 to 15,000 cycles plus.

Altec Lansing's complete line of audio frequency components provide the primary standards of comparison for laboratory and design engineering...in addition to high quality sound for commercial reproduction.

ALTEC LANSING COMPONENTS

The Duplex Speaker • Two Way Theatre Sound Systems • Public Address Systems
High Frequency Horns • Low Frequency Horns • General Purpose Speakers • Power Supply Units • Amplifiers • Transformers
Power Chokes • Dividing Networks
Inter Modulation Equipment

A Complete Sound Engineering Service

SEND FOR BULLETINS

ALTEC

LANSING CORPORATION

1210 TAFT BLDG., HOLLYWOOD 28, CALIF.
250 WEST 57 STREET, NEW YORK 19, N. Y.
IN CANADA: NORTHERN ELECTRIC CO.

WORLD FAMOUS RADIO TELEGRAPH KEYS

The Choice of
Good Operators
Everywhere

VIBROPLEX

Reg. Trade Marks: Vibroplex, Lightning Bug, Bug




The "BUG"
Trade Mark
Identifies
the Genuine
Vibroplex

Accept no
substitute


"ORIGINAL" DeLuxe Model WITH PATENTED JEWEL MOVEMENT

The aristocrat of all Vibroplex keys. It's the PATENTED JEWEL MOVEMENT feature exclusive with DeLuxe Vibroplex keys, that has so completely eliminated tiresome sending effort that it has made sending easier than you ever dreamed sending could be. The jewels used in DeLuxe Vibroplex keys are the same as placed in the finest made watches and precision instruments providing watch-like precision, feather-touch action, lifetime service and ease of operation unapproachable by any other key. Chromium finished base. Bright machined parts. Colorful red switch knob, finger and thumb piece. DIE CUT contacts and main spring. 3/16th contacts. Circuit closer, cord and wedge, \$19.50. Standard finish, \$15.95

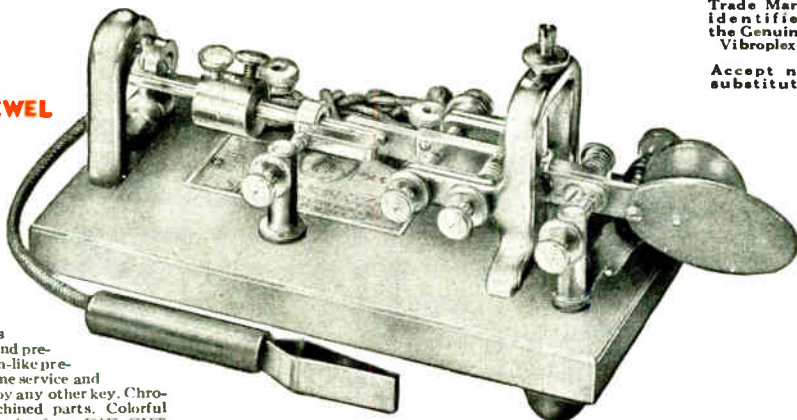


HANDY "BLUE RACER" MODEL

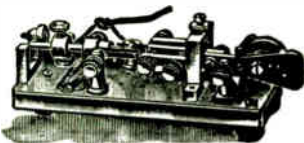Patterned after the "Original" Vibroplex and capable of the same high class sending performance that has made that key world famous. Smaller, handier, a space saver. Easy to operate. Standard black crackle base. Bright machined parts. DIE CUT contacts and main spring. 3/16th contacts. Circuit closer, cord and wedge, \$15.95. DeLuxe finish with PATENTED JEWEL MOVEMENT, \$19.50



"LIGHTNING BUG" MODEL

One of the latest and most popular Vibroplex keys. Easy working... smooth action... uniformly accurate and dependable. Responds to the touch of the average operator as well as the expert. Many advanced and exclusive features. Standard black crackle base. Bright machined parts. DIE CUT contacts and main spring. 3/16th contacts. Circuit closer, cord and wedge, \$13.95. DeLuxe finish with PATENTED JEWEL MOVEMENT, \$17.50

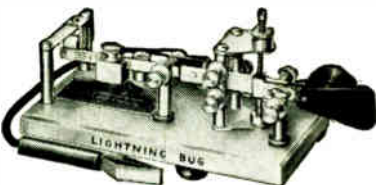

CARRYING CASE

Keeps out dust, dirt and moisture. Prolongs life of key. Heavily reinforced. Flexible leather handle, \$3.50

Vibroplex Semi-automatic Radio Telegraph keys are famous the world over for clear, fast, easy sending. Under the most exacting operating conditions on land, sea and air Vibroplex keys have measured up to the highest standards of sending proficiency and operating dependability and are the choice of tens of thousands of the world's finest operators. Every Vibroplex key is scientifically designed... precision machined... improved in every possible detail. You'll be proud to own and delighted to use a Vibroplex key.

THE "CHAMPION"

A smart, efficient, full-size semi-automatic key for radio use only. Easy to learn and operate. Ideal for beginners. Black crackle base. Chrome-plated parts. 3/16th contacts, \$9.95



NEW 1945
ENLARGED
EDITION OF
PHILLIPS
CODE


It's definitely new, completely standard, strictly up-to-date. In addition to changes and additions to previous editions, it contains Radio Code Signals, International Morse, American Morse, Russian, Greek, Arabic, Turkish and Japanese Morse Codes, World Time Chart, United States Time Chart, Commercial "Z" Code, Aeronautical "Q" Code, Miscellaneous abbreviations used on International wire, submarine cable and radio-telegraph circuits. Postpaid \$1.50

Remit by money order or registered mail. Write for FREE illustrated catalog of Standard and DeLuxe Vibroplex keys.

THE VIBROPLEX CO., Inc.
833 Broadway, New York 3, N. Y.

J. E. Albright, President


TRIMM HEADSETS

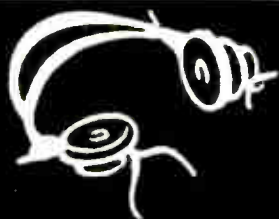

FIRST IN WAR...



FIRST IN PEACE...

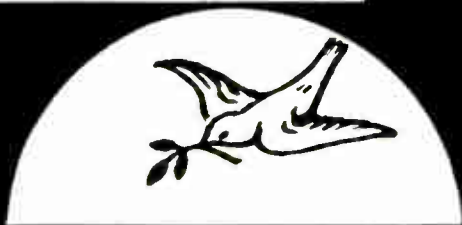

FIRST IN QUALITY AND SERVICE
ALL OVER THE WORLD!

TRIMM INC.

1770 BERTEAU AVE.

CHICAGO, ILL., U.S.A.

YOUR JOBBER HAS BEEN SUPPLYING
TRIMM QUALITY HEADSETS FOR 23 YEARS
HE CAN SUPPLY YOU TODAY

E-L Power Supplies

FOR PORTABLE AND MOBILE OPERATION

**Maximum Efficiency!
Low Battery Drain! Low Noise Level!
Long Life!**

If you're planning a portable or mobile set-up—or any other layout for which standard 110 v AC is unavailable—E-L Power Supplies will provide the necessary voltages most efficiently and economically. In addition, they are excellent for mobile public address systems.

A complete line of E-L Converters (DC-DC) and Inverters (DC-AC) is available for radio amateurs. E-L Converters and Inverters are of the vibrator type, offering the highest efficiencies, longest service life, and very low battery drain. They are especially filtered to meet amateurs' circuit requirements, resulting in an exceptionally low noise level.

E-L Converters and Inverters have been proven completely dependable during the war where they came through the toughest battle conditions with flying colors.

Contact your local distributor for these efficient, reliable units.

E-L Converters. E-L Converters are offered in a full line of models to provide high DC voltages from 6, 12 and 24 volts DC, in output wattages ranging from 19 to 200 watts. They are compact in design and ruggedly built to withstand the toughest service. Typical of the E-L Converter line are the three models illustrated here.



Model 601

Input Voltage: 6 Volts DC

Output Voltages:

225 Volts DC at 50 ma.

250 Volts DC at 65 ma.

275 Volts DC at 80 ma.

300 Volts DC at 100 ma.

Size: 4 3/4" x 4" x 6"

Weight: 6 lbs.

Model 605

Input Voltage: 6 Volts DC

Output Voltages:

150 Volts DC at 35 ma.

200 Volts DC at 40 ma.

250 Volts DC at 50 ma.

275 Volts DC at 65 ma.

Size: 5 1/2" x 3 1/4" x 6"

Weight: 5 1/2 lbs.



Model 619

Size: 9 3/4" x 5 3/4" x 6"

Weight: 14 1/2 lbs.



Input Voltages: 6 Volts DC and 115 Volts AC

Output Voltages: 300 Volts DC at 100 ma.; 6.3 Volts AC at 4.75 amps.

E-L Inverters. A complete line of E-L Inverters is also available to permit operation of 115 VAC equipment from 6, 12, 32, 110 and 220 volts DC. Output wattages range from 5 to 1000 watts. The Inverters also are engineered and manufactured for long, dependable service under all conditions. The two models shown here are typical of these efficient E-L units.

Model 303

Input: 6 Volts DC

Output: 115 Volts AC

Size: 7 1/8" x 4 1/4" x 5 1/4"

Weight: 6 lbs.



Model 307

Input: 6 Volts DC

Output: 115 Volts AC

Size: 10 3/4" x 7 1/2" x 8 1/4"

Weight: 23 1/2 lbs.



Contact your local distributor

COPYRIGHT 1945 ELECTRONIC LABORATORIES, INC.

Electronic



LABORATORIES, INC.

INDIANAPOLIS, INDIANA

TRANSFORMERS AND VIBRATOR POWER EQUIPMENT FOR LIGHTING, COMMUNICATIONS, ELECTRIC AND ELECTRONIC APPLICATIONS



RADIO and CODE OPERATORS

GET CODE SENDING and RECEIVING Speed

the WAY CHAMPIONS DO



WALTER H. CANDLER
Originator of the famous Candler System and founder of the Candler Code Speed Training.

You can now improve your present speed and proficiency in code sending and receiving with the famous Candler System, which trains you to meet all speed requirements of amateur and commercial licensed operators. You can learn code right from the beginning as you will be using it as an operator with the Candler System Training, and you will master it in half the usual time required.

SPEED UP WITHOUT TENSION OR NERVOUSNESS

You can take Candler Training wherever you may be. It qualifies you for higher rating and a better paying job. If you are seeking a license you will be able to qualify quickly. You will learn how to free yourself of all fear, tension or jitteriness and thereby apply your talents to speed and accuracy. Candler System Training has provided a background for some of the highest paid operators in the field. It is so surprisingly easy and inexpensive. It takes more than memorizing the code and merely sending and receiving to become a skilled radio operator. Ask any good operator. He will tell you CANDLER teaches you quickly, thoroughly, the technique of fast, accurate telegraphing, and trains you to meet all requirements. Why not let the internationally famous Candler System give you the speed, accuracy and technique to eliminate all worry and code problems.

★ COURSES FOR BEGINNERS and OPERATORS

THE SCIENTIFIC CODE COURSE is a complete radio-code course for beginners. It teaches all the necessary fundamentals scientifically.

THE HIGH SPEED TELEGRAPHING COURSE is for operators who want to increase their w.p.m. and improve their proficiency.

THE TELEGRAPH TOUCH TYPEWRITING COURSE is specially prepared for those who want to become expert in the use of the typewriter for copying code.

NO EXPENSIVE PRACTICE EQUIPMENT NEEDED

Learning Code or Improving Speed and Accuracy are Mental Processes that require Special Training, which vast experience in developing high-speed operators enables CANDLER to give you simply, thoroughly, interestingly. Practice without understanding these laws and fundamentals governing speed and skill is always hard, and wastes much valuable time. CANDLER shows you the EASY, BETTER WAY to SPEED, SKILL and CODE PROFICIENCY, quickly.

CANDLER SYSTEM

BOX 928 — DEPT. 10-A-6, DENVER 1, COLORADO

CANDLER SYSTEM COMPANY, 121 KINGSWAY, LONDON, W. C. 2, ENGLAND



World Champion T. R. McELROY

Official Champion Radio Operator. Speed 75.2 w.p.m., won at Asheville Code Tournament July 2, 1939, says: "My skill and speed are the result of the exclusive, scientific training Walter Candler gave me. Practice is necessary, but without proper training to develop Concentration, Coordination and a keen Perceptive Sense, practice is of little value. One likely will practice the wrong way."



SEND TODAY FOR THIS FREE Book of Facts

It gives you the story of CANDLER CODE CHAMPIONS, and many inside tips that will help you. It is FREE. A postcard will bring it to you. No obligation.



THE HENRY RADIO CREED:



1. To have the world's most complete stock of Hallicrafters, National, Hammarlund, RME, and other amateur receivers, transmitters, and parts at lowest wholesale prices. To help you get the best equipment for your use. To see that you are 100% satisfied.
2. To take your communications receiver in trade for a liberal allowance. Tell us what you want and what you have to trade.
3. To sell to you on terms financed by Bob Henry. No third party. No red tape. Less interest. You save time and money.

I intend to give you the best service, the best terms (financed by me), the best trade-in allowance; to help you in every possible way; to advise you in getting the best equipment for your use; to see that you are always 100% satisfied.

Write, wire or phone for any amateur equipment in this Handbook or in any catalog or advertisement at lowest price shown. Write for latest manufacturers' bulletins on any equipment you are especially interested in. Write for any information. Your inquiries welcomed.

For your convenience — two stores. A store in Butler, Missouri, managed by Bob Henry, W9ARA, and John Henry, W9XCO. A store in Los Angeles 25, California, managed by Ted Henry, W6LOU. Write, wire, phone or visit either store.

73,

Bob Henry
W9ARA

HENRY RADIO SHOPS


211-215 NORTH MAIN STREET
BUTLER, MISSOURI

2331-35 WESTWOOD BOULEVARD
LOS ANGELES 25, CALIF.

"WORLD'S LARGEST DISTRIBUTOR OF SHORT WAVE RECEIVERS"

ESICO

REG. U. S. PAT. OFF.

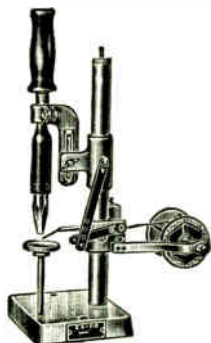

SOLDERING IRONS





are widely used in industrial plants throughout the country. They are designed to withstand the strain of continuous service required of factory tools.

SPOT SOLDERING MACHINE

designed for treadle operation for advancement of iron and solder leaving operator's hands free for handling of product.

SOLDERING IRON TEMPERATURE CONTROLS

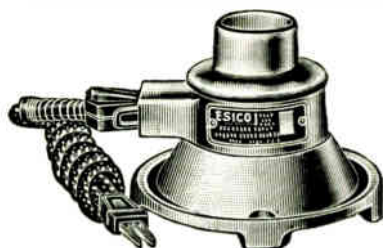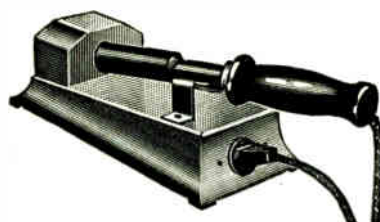prevent overheating of soldering irons between soldering operations. Irons do not deteriorate when being used. The idle period causes oxidation and shortens life.



SOLDER POTS


ruggedly constructed pots of various sizes designed for continuous operation and so constructed that they are easily and quickly serviced, should elements have to be replaced.

Write for Catalog

ELECTRIC SOLDERING IRON CO., INC.

2546 West Elm Street

DEEP RIVER, CONNECTICUT

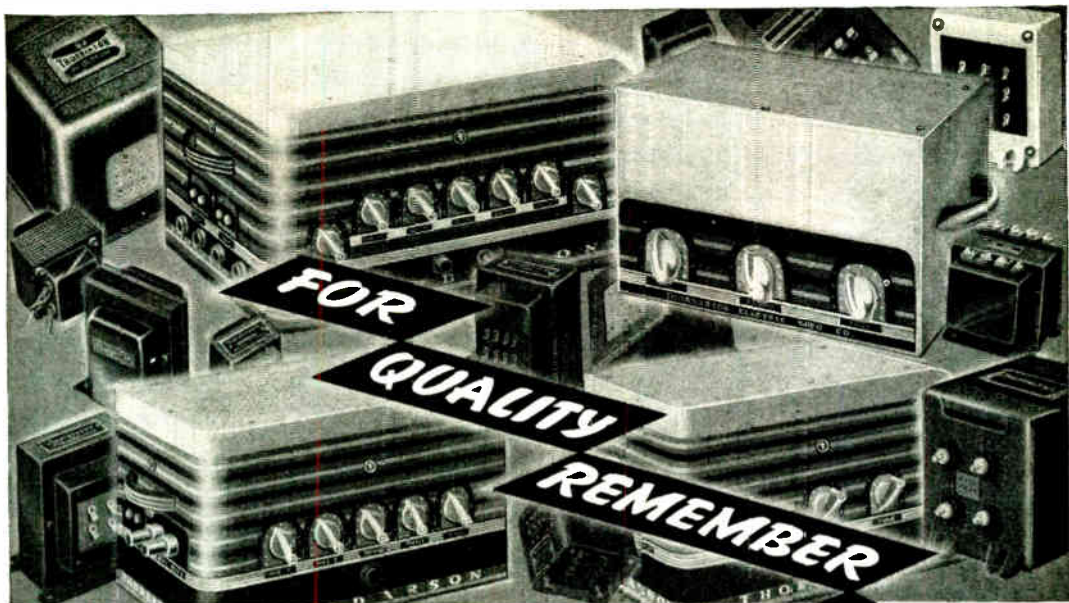

THORDARSON

**Transformer Specialists since 1895
Originators of Tru-Fidelity Amplifiers**

Every *Thordarson* product is precision engineered and built entirely of quality materials to insure the utmost in overall performance.

Extensive metallurgical research has produced the superior coil and core materials used throughout *Thordarson* transformers. In addition, we have transformers that are Tropex impregnated for protection against moisture, salt air and humidity.

Thordarson Tru-Fidelity amplifiers feature: advanced tone compensation, conservative ratings, ventilation for continuous operation, low hum level, multiple input channels and maximum flexibility of controls.

Leading manufacturers in the electronics industry use large quantities of *Thordarson* products for most exacting requirements. Soon many new applications and developments, rising out of *Thordarson* wartime production, will be available for your requirements.

Remember Thordarson . . . over 50 years of precision manufacturing experience . . . for quality products.

500 WEST HURON ST., CHICAGO, ILL.



ORIGINATORS OF TRUE-FIDELITY AMPLIFIERS



Cent

Ceramics

The experience earned in producing millions of Ceramic parts for the industry is at your disposal.

Centralab is equipped to furnish coil forms up to 5 inches in diameter and pressed pieces to approximately 6 inches square. Write for bulletin 720.

Centralab
CR
 Division of GLOBE-UNION INC., Milwaukee

Centralab

Parts by Centralab

- Variable Resistors
- High Frequency and High Voltage Selector Switches
- Fixed and Variable Ceramic Capacitors
- Steatite Insulators



 Division of GLOBE-UNION INC., Milwaukee



Improved!

Now better than ever...
**Gould-Moody "Black Seal" Aluminum
Instantaneous Recording Blanks**

Technological advancements, brought about by our wartime assignments, now provide the critical engineer with "Black Seal" blanks of improved cutting and reproduction qualities, plus more satisfactory playback life.

Gould-Moody "Black Seal" blanks are made of the finest nomeplate aluminum, coated with an exclusive compound, and free from all abrasive materials. They are guaranteed not to dry out, age, harden or deteriorate. Continued high fidelity is assured through many months of playbacks. The true tonal qualities, long life and great economy of Gould-Moody "Black Seal" blanks place them head-and-shoulders above competition. The proof of their value is in their performance. Order as a trial a sample case, and see for yourself.


You can get Gould-Moody
"Black Seal" Aluminum
Instantaneous Recording
Blanks without delay.

**Old Aluminum Blanks recoated with the
famous "Black Seal" formula on short notice**

THE GOULD-MOODY COMPANY

RECORDING BLANK DIVISION

395 BROADWAY, NEW YORK 13, N. Y.

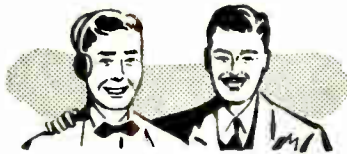

Veteran Hams and Industrial Purchasing Agents recognize and respect the name

HARVEY

because, since the infancy of radio, we have supplied them with the latest in

RADIO AND ELECTRONIC COMPONENTS

hot off the production lines of America's leading manufacturers.

HARVEY invites your continued patronage and welcomes the friendship of those of you who are setting up new ham rigs.

If you cannot visit our conveniently located headquarters at 103 West 43rd St., New York City (one block east of Times Square), to see long-promised postwar products...

WRITE . . . WIRE . . . OR PHONE . . .

HARVEY

- **Orders filled promptly!**
- **Sound technical advice, upon request!**
- **Prompt deliveries anywhere in the U. S. A.!**



SOME OF THE MANUFACTURERS WHOSE PRODUCTS WE DISTRIBUTE

ABBOTT INSTRUMENT, INC.
 AEROVOX CORPORATION
 ALLIANCE MANUFACTURING CO.
 ALTEC LANSING
 AMERICAN PHENOLIC CORP.
 AMERICAN RADIO HARDWARE CO.
 AMERICAN TELEVISION & RADIO CO.
 AMPERITE COMPANY
 AMPEREX ELECTRONIC CORPORATION
 ASTATIC MICROPHONE LABORATORY
 ATLAS SOUND CORP.
 AUDAK COMPANY
 AUDIO DEVICES CO.

BARKER & WILLIAMSON
 BELDEN MFG. CO.
 BIRNBACH RADIO CO.
 BLILEY ELECTRIC CO.
 BOGEN COMPANY, DAVID
 BRUSH DEVELOPMENT CO
 BUD RADIO COMPANY

CARDWELL MFG. CO.
 CENTRALAB
 CLAROSTAT
 CORNELL-DUBILIER
 CORNING GLASS WORKS
 COTO COIL

DAVEN ATTENUATORS
 DIAL PLATES
 DRAKE ELECTRIC WORKS
 DUMONT LABORATORIES, INC., ALLEN B.

EASTERN MIKE-STAND CO.
 EBY CO., HUGH H.
 EITEL McCULLOUGH (EIMAC)
 ELECTRONIC LABORATORIES

GENERAL INDUSTRIES CO.
 GORDON SPECIALTIES CO.

HALLICRAFTERS, INC.
 HAMMARLUND MFG. CO.
 HEINZ-KAUFMAN (GAMMATRON)
 HICKOCK ELECTRIC
 HYTRON CORPORATION

INSULINE CORP. (ICA)
 INTERNATIONAL RESISTANCE CO. (IRC)

JANETTE MFG. CO.
 JENSEN RADIO MFG. CO.
 JOHNSON CO., E. F.
 JONES, HOWARD B.

KENYON TRANSFORMER CO.
 KRAEUTER & CO., INC.

LENZ ELECTRIC MFG. CO.
 LITTELFUSE LABORATORIES

MEISSNER MFG. CO.
 MILLEN MFG. CO.
 MILLER CO., J. W.
 MUELLER ELECTRIC CO.

NATIONAL COMPANY
 NATIONAL UNION RADIO CORPORATION
 OHMITE MFG. CO.

PAR-METAL PRODUCTS CORP.
 PHILCO
 PIONEER GENEMOTOR CORP.
 PRECISION APPARATUS CO.
 PRESTO RECORDING CORP.

RADIO MFG. ENGINEERS (RME)
 RAYTHEON PRODUCTION CORP.
 RCA MANUFACTURING CO.

SANGAMO ELECTRIC CO.
 SHURE BROTHERS
 SIGNAL ELECTRIC MFG. CO.
 SIMPSON ELECTRIC MFG. CO.
 STANDARD ELECTRIC PRODUCTS CO.
 (STACO)
 STANDARD-TRANSFORMER CORP.
 (STANCOR)

STROMBERG-CARLSON
 STRUTHERS DRUM, INC. (DUNCO)
 SUPREME INSTRUMENTS CORP.

TAYLOR TUBES, INC.
 THORDARSON ELECTRIC MFG. CO.
 TRIMM HEADPHONES
 TRIPIETT ELECTR. INSTRUMENT CO.
 TURNER COMPANY



UNITED TRANSFORMER CO. (UTC)
 UNIVERSITY LABORATORIES
 UTAH RADIO PRODUCTS CO.

WARD-LEONARD ELECTRIC CO.
 WESTON ELECTR. INSTRUMENT CO.
 WORTNER PRODUCTS CO.

Government Surplus
TUBES *and*
RECTIFIERS
Immediately Available!

We have been appointed a sales agent by the Reconstruction Finance Corporation of government surplus tubes. Many types of transmitting, cathode ray and rectifier tubes immediately available. All tubes tested to government specifications and rigidly inspected. Highest quality — not rejects!

Trade discounts to dealers on case lots

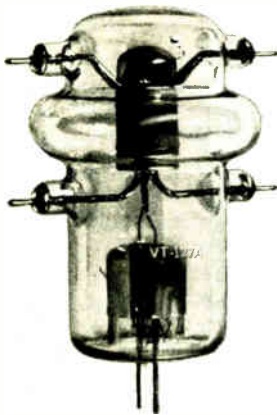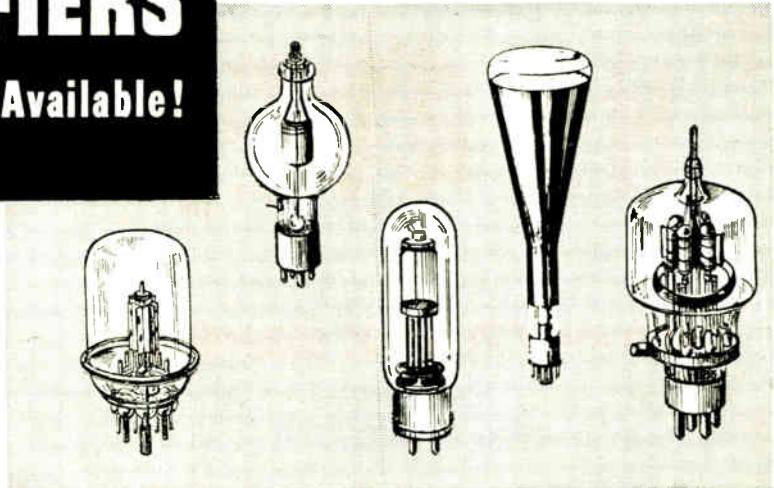

VT127A, above, with dual plate and grid leads. Filament V-5, 10-A. Capable of operating in many of the HF post-war amateur bands. Formerly used by Gov't. in radar — average cost over \$20, now offered at . . . 7.50

Write for complete list of tubes and prices!

All immediately available, including:

826 (HF triode) • VT127A (HF triode)
304TL • 872A (MV rectifier)

Cathode Ray Tubes:

5AP1 • 5BP4 • 3AP1


★

USED TUBES — a limited supply of used tubes in the larger sizes, at 40% discount. All tested and in good operating condition. Following types available:

250TH - 250TL - 750TL - 803 - 805
807 - 813 - 815 - 100TH - 450TH - 829
830B - 832 - 851 - 860 - 845 - 849

Lewis ★ **ELECTRONICS**
 LOS GATOS · CALIFORNIA

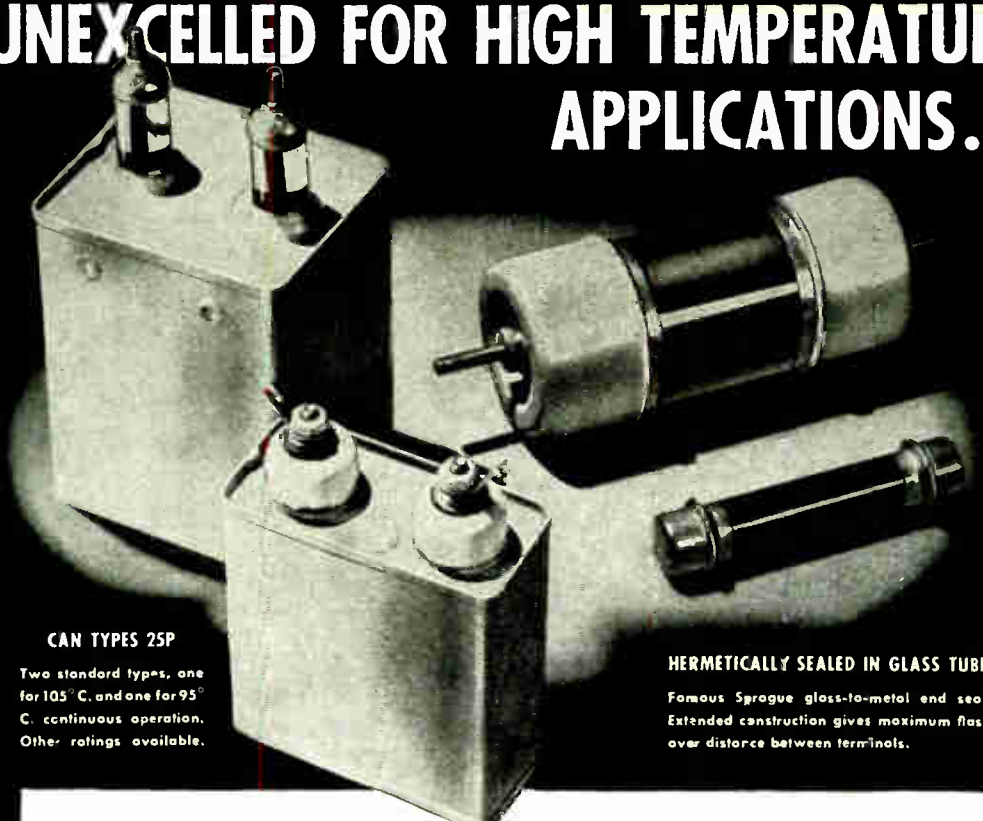UNEXCELLED FOR HIGH TEMPERATURE APPLICATIONS...



CAN TYPES 25P

Two standard types, one for 105° C. and one for 95° C. continuous operation. Other ratings available.

HERMETICALLY SEALED IN GLASS TUBES

Famous Sprague glass-to-metal end seals. Extended construction gives maximum flash-over distance between terminals.

...ideal for higher ratings in smaller sizes at lower temperatures

Sprague Capacitors impregnated with the exclusive VITAMIN Q impregnant make possible the use of much smaller units—with a substantial safety margin—on numerous high-voltage, high temperature applications ranging from transmitting to television. Where high temperature is not a factor, their unique characteristics assure materially higher capacity ratings for a given size.

Type 25 P VITAMIN Q Capacitors operate satisfactorily at thousands of volts at ambient

temperature as high as 115° C. Insulation resistance at room temperature is *more than 20,000 megohms per microfarad*. Throughout the temperature range of +115° C. to -40° C. they retain all virtues of conventional oil-impregnated capacitors.

WRITE FOR NEW CATALOG

Sprague Catalog 20—just off press—brings you details on VITAMIN Q Capacitors in both can and glass tube types as well as dozens of other paper dielectric types for today's exacting uses.



SPRAGUE ELECTRIC COMPANY • North Adams, Mass.

SPRAGUE

VITAMIN "Q" CAPACITORS



TRADE MARK REG. U. S. PAT. OFF.



FOR YOUR NEWEST RIG-

- Sylvania Electric makes the tubes you want.

Now that you're back on the air, you'll need the kind of electronic equipment that will help you keep up with the many advances made in the field of communications. Now's the time to prepare for the increase in television transmitting stations all over the nation . . . higher frequencies, FM.

You'll welcome the news, then, that cathode ray tubes are now available through Sylvania distributors, retailers or radio servicemen. Our constant research in this field, combined with wide experience in large-scale production to meet war needs, has placed us in a position to manufacture cathode ray tubes to a much higher stand-




ard than it has ever been possible before.

And concerning higher frequencies, the Sylvania Lock-In Radio Tube was built to handle high and ultra-high frequencies—yet be more than perfectly suitable for sets working with the “regular” bands.

Yes, Sylvania Electric makes the tubes you want—dependable, precision-built tubes of every description. And each tube you buy is backed by over 40 years of the kind of research and development that have made Sylvania Radio Tubes the perfect electronic units they are today.

SYLVANIA ELECTRIC

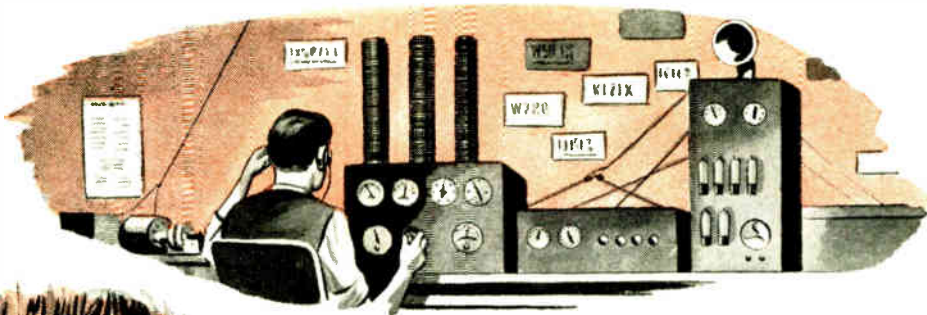Makers of Radio Tubes; Cathode Ray Tubes; Electronic Devices;
Fluorescent Lamps, Fixtures, Wiring Devices; Electric Light Bulbs



AMERTRAN...


Old Timer's Favorite



● Old time hams have fond memories of AmerTran and many radio and radar operators found the AmerTran name on their most dependable components during the recent war. Now, AmerTran, associated for more than forty years with quality transformers, returns to amateur radio.

Many improvements will be found in the new, complete, line of audio and power transformers now being offered.

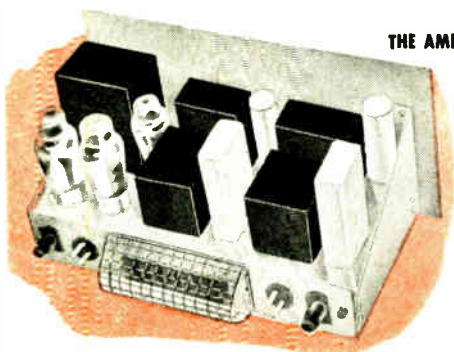THE AMERICAN TRANSFORMER COMPANY, 178 Emmet St., Newark 5, N. J.




Pioneer Manufacturers of Transformers, Reactors and Rectifiers for Electronics and Power Transmission



Crystals

FOR THE CRITICAL

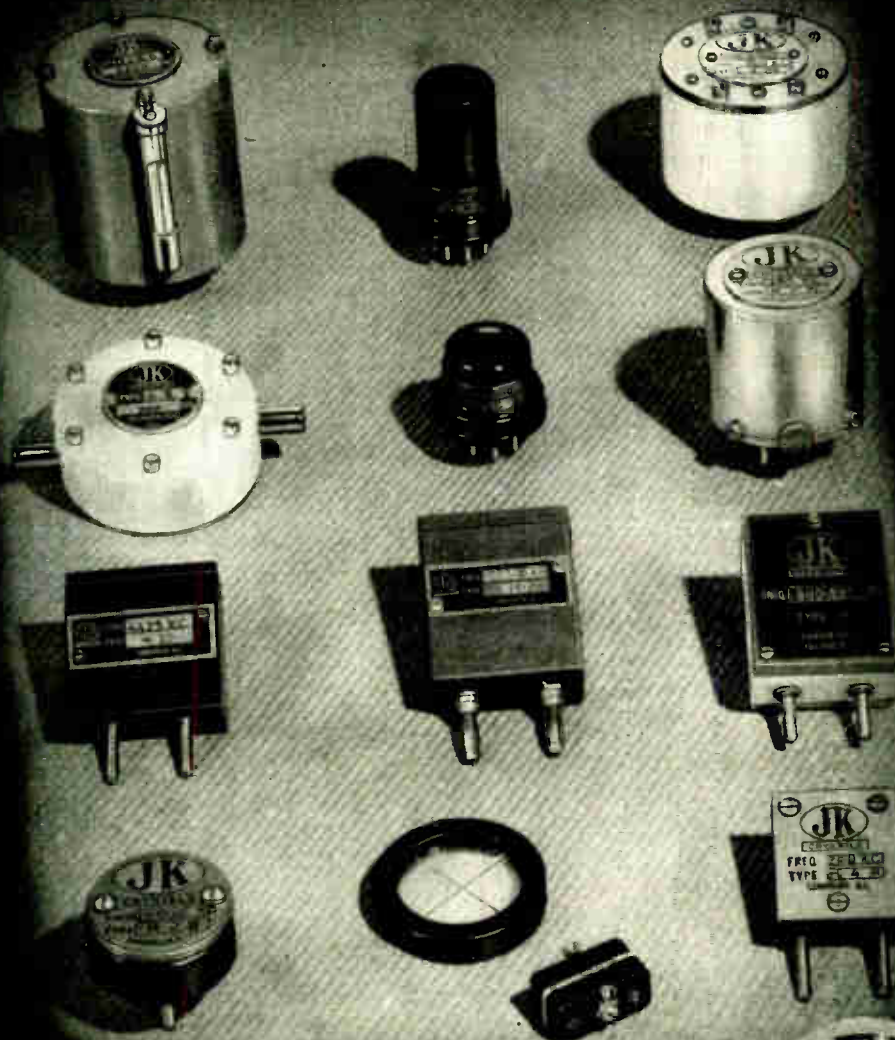

The **JAMES KNIGHTS Co.**
SANDWICH, ILLINOIS
Sixty Miles Southwest of Chicago





TO BUILD

TO REPAIR

TO TEST

ORDER YOUR EQUIPMENT

FROM CONCORD

(LAFAYETTE RADIO CORPORATION)

Used by Amateurs for 25 years as Headquarters for RADIO PARTS and ELECTRONIC EQUIPMENT

Once again CONCORD invites the radio amateur to avail himself of the exceptional service which has made us the dependable source of radio parts and electronic equipment for almost 25 years. Look to CONCORD

to supply you quickly with the items you want. Our business is to carry them in stock for you on your call. Our quality is dependable. Our stocks are huge and complete. Our service is fast.

Order Today for Shipment Tomorrow from CHICAGO or ATLANTA

ALL STANDARD LINES

As Few or as Many as You Need

CONCORD is famous for carrying in stock for immediate shipment hundreds of nationally known lines of amateur radio parts and equipment. Below is a partial list:

- Aerovox, Amphenol, Ampere, Amperite,
- Astatic, B & W, Biley, Brush, Burgess,
- Cardwell, Centralab, Clarostat,
- Cornell-Dubilier, Dumont, Echophone,
- Eimac, General Electric, Hallcrafters,
- Hammatlund, Heintz & Kaufman, Hickok,
- IRC, Janette, Jensen, Johnson, Mallory,
- McElroy, Meissner, Millen, National,
- Ohmite, Pioneer, Presto, Racon, RCA,
- Readrite, Shure, Simpson, Solar, Sprague,
- Stancor, Supreme, Thordarson, Trimm,
- Triplett, Turner, UTC, Universal,
- Utah, Vibroplex, Weston, Worner

Two convenient shipping-warehouses serve you with utmost speed. Send your order to the one nearest you.

Complete Catalog FREE

In addition to all standard brands of quality items, this Catalog and Buying Guide contains items not available at any price during the war, it offers many new post-war developments, it shows the last word in modern radio parts and electronic equipment. Many of the recent advances in the science of radio communication are included. You'll find this Catalog a priceless reference guide and a valuable addition to your library. Mail the coupon below for a copy. It's absolutely FREE.

CONCORD

RADIO CORPORATION
(Lafayette Radio Corporation)

CHICAGO 7, ILL. • ATLANTA 3, GA.
901 W. Jackson Boulevard 265 Peachtree Street

CONCORD RADIO CORP., Dept. RAH
901 W. Jackson Blvd., Chicago 7, Ill.

Gentlemen: Send me at once a FREE copy of your latest Catalog and Buying Guide, listing standard lines of Radio Parts and Electronic Equipment.

Name.....

Address.....

City..... Zone..... State.....

TURNER

Microphones

Faithfully Reproduce
Your Complete Messages

These famous microphones, priced within the range of every amateur, amplify all vibrations received by the diaphragm without adding any of the harmonics to assure clear, sharp communications without distortion. You can rely on Turner under all climatic and acoustic conditions.



**211
DYNAMIC**

No. 211 is a Rugged Dynamic utilizing a new type magnet structure and acoustic network. The high frequency range has been extended and the extreme lows have been raised 2 to 4 decibels to compensate for overall deficiencies in loud speaker systems. Unique diaphragm structure results in extremely low harmonic and phase distortion without sacrificing high output level. Tilting head, balanced line output connection. Chrome or gunmetal finish.



**33D Dynamic
33X Crystal**

The full satin chrome finish of 33D Dynamic adds class to any rig. 90° tilting head gives semi- or non-directional pick-up. Output level -54DB. Range 40-9,000 cycles. Ruggedly built for recorder or P.A. work. Built in transformer free from hum pick-up. Available in 200 or 500 ohms or high impedance. 33X Crystal same appearance as 33D. Level -52DB. Range 30-10,000 cycles.

**22X
22D**



22X Crystal is tops in performance. Reproduces clean and sharp. Smart engineering cuts feedback to minimum.

Tilting head and removable 7-foot cable set. Built-in wind-gag permits outdoor operation. Crystal impregnated against moisture. Automatic barometric compensator. Chrome type finish. Level -52 DB. Range 30-7,000 cycles.

22D Dynamic is identical in appearance with 22X but has high level dynamic cartridge. Dependable indoors or out. Output -54 DB. Range 30-8,000 cycles. 200 or 500 ohms or high impedance.

NEW TURNER CHALLENGERS

Plus Performance at Low Cost



Model CD

Dynamic, same style and finish as CX, with removable 7 foot cable set. In 200-250 ohms, 500 ohms or high impedance. Level -52 DB. Range 50-7,000 cycles.

Model CX

Crystal, in rich brushed chrome finish, with 7 foot removable cable set using Amphenol connectors. Level -52 DB. Range 50-7,000 cycles.



Model BX

Crystal mike for recording, P.A. and ham work. Bronze enamel finish. Level -52 DB. Range 50-6,000 cycles. An excellent unit. With 7 foot cable.

Model BD

Dynamic, same finish as BX. Works indoors or out. Level -52 DB. Range 50-6,000 cycles. 200-250 ohms, 500 ohms or high impedance with 7 foot cable.



Han-D

Hang it, hold it, use it on desk or floor stands. Han-D does the job of several mikes. Available as 9X Crystal, in brushed chrome finish, Level -48DB, or 9D Dynamic in brushed chrome or gunmetal. Level -50DB, 200 or 500 ohms or high impedance.

FREE Turner Microphone Catalog with complete information and prices on Turner Microphones. Write for your free copy.


Crystals Licensed Under Patents of The Brush Development Co.

THE TURNER CO.

CEDAR RAPIDS, IOWA

The NEW RME

45 RECEIVER

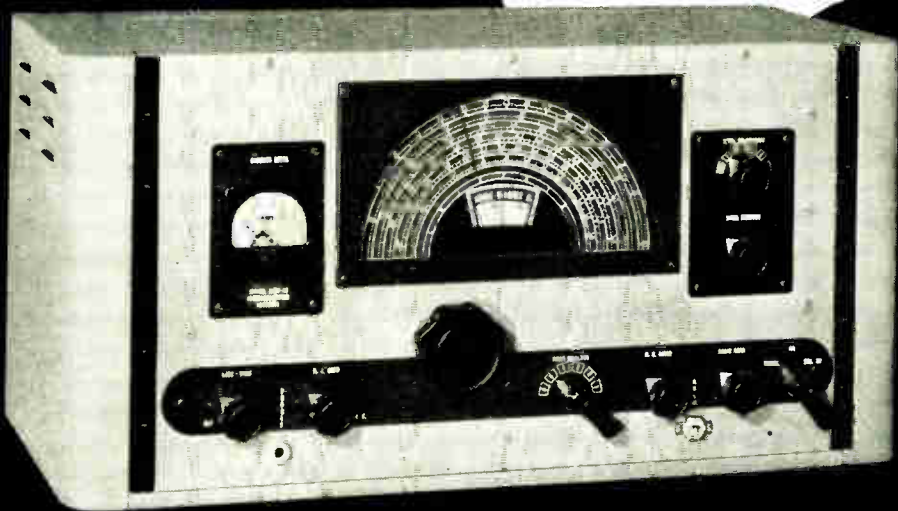

PERFORMANCE BACKED BY PRECISION



THE XC-2 PLUG-IN UNIT

A unit for fixed frequency operation of RME communications receivers. A crystal ground to a frequency either 455KC higher or lower than the frequency of the signal to be received, is an integral part of the XC-2. The XC-2 is inexpensive, easily adapted and very effective in locations where fixed frequency operation of a general coverage receiver is desired.

Every control is conveniently located, all scales are illuminated and distinctive, the chassis is mounted on a relay rack panel, and the cabinet is attractively designed in a two-tone finish.

The RME • 45 is the type of receiver by which radio amateurs the world over judge dependability and performance; **PRIDE OF OWNERSHIP MUST BE BUILT INTO EVERY SET**—that has been our creed in the past twelve years.

The RME • 45 is truly your postwar receiver dream come true! It has been so engineered that it delivers peak performance on all frequencies 550 to 33,000 KC. Loctal tubes, short leads, temperature compensating padders, triple spaced condensers and advances made while producing for the armed forces — all these details have collaborated to give you the "finest" and most stable reception you have ever listened to.

There is bandsread aplenty for the most exacting ham or

INDIVIDUAL EQUIPMENT BULLETINS
WITH PRICES AVAILABLE ON ALL
RME UNITS.

98

SINCE 1933



RME

FINE COMMUNICATIONS EQUIPMENT

RADIO MFG. ENGINEERS, INC.

Provia 6, Illinois U. S. A.

World Radio History

commercial operator. The 20 meter band, 14,000 to 14,400 KC., for instance, covers 20 divisions on the translucent dial—equivalent to 72 degrees on a five-inch diameter disc.

The appearance of the RME-45 is consistent with its performance. The receiver is housed in a new streamlined two-toned cabinet and supplied with a matched acoustically designed speaker housing.


These and a multitude of additional features make the new RME-45 the receiver you have long been waiting for!

Features

Streamline Two-Tone Cabinet
Acoustically Designed Speaker Housing
Relay Rack Mounting Panel
Six Bands, 550 to 33,000 KC
Automatic Noise Limiter
Relay Control and Break-In Terminals
Signal Level Meter
Variable Crystal Filter
Bandspread Equivalent To 75 Linear Inches For Every 180° Sweep Of Main Pointer

R. M. E. S P E A K E R

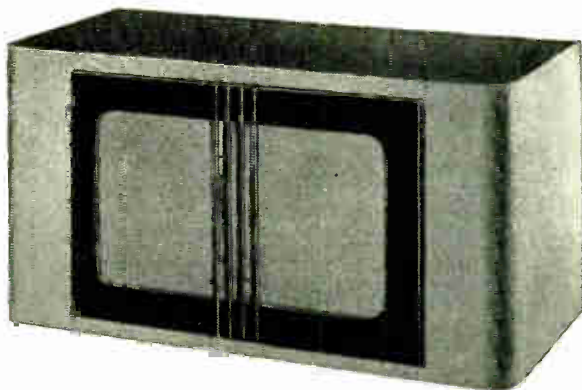A new housing to match the new receiver. Built in a sturdy design, open in the rear, the eight-inch electrodynamic speaker in every way gives true and balanced performance, no matter whether used for CW, voice or music!



VHF-152 CONVERTER

During pre-war days, thousands of hams were introduced to the five meter band through the use of the DM 36, High Frequency Converter.

This instrument gave exceptional performance, at low cost, on the 5 and 10 meter bands when used with a good communications receiver.

To make VHF operation really practical and worthwhile for the new FCC allocations, an entirely new version of the DM 36 is now introduced covering 28 to 30 MC, 50 to 54 MC and the new 144 to 148 MC band. At modest cost, the VHF 152 far exceeds any present day method offered for working these frequencies. Your RME-45 is an excellent receiver to use with the VHF-152. RME has always pioneered with the finest first!



The new VHF-152, with the addition of a good communications receiver, will give you the best in all band amateur reception.

THE LF 90 FREQUENCY CONVERTER (90 TO 600 KC)

In combination with a good communications receiver, the LF-90 permits reception of such frequencies as aircraft beacons, air navigation, ship, coastal stations, and others operating in this low range.

Small in size, the LF-90 has its individual power supply, standard 115V, 60 cycle.



A new radio controlled unit, serving as a standby operator for your radio station, and known as the AUTOMATIC ANNOUNCER was recently introduced by RME. As a "radio operated switch," contacts control the lighting of a signal light or the ringing of a bell, or both. The unit gives a visual as well as an audible indication of incoming radio signals. In no way are the normal functions of a communications receiver affected when the SPD-33 is connected to it. The unit is designed for standard relay rack mounting, panel height being 3½ inches and depth 12 inches.



AUTOMATIC ANNOUNCER SPD - 33

FOR PRIVATE PILOTS—THE NEW RME RECEIVER—TRANSMITTER

Here is the really practical receiver transmitter unit for which private pilots have been waiting. Light in weight, carefully designed for proper light ship installation, and built to rigid RME specifications and quality, and nominal in cost, this new unit is already making a hit with its performance.

Receiver specifications:

180 to 420KC —For Range Stations.

550 to 1500KC—For Standard Broadcast Stations.

278 KC —For Tower Frequency Position.

Transmitter has normal ten mile range.

Both units obtain their power from small dry cells.

AT-12



Optional units:
6 volt and
12 volt input
with external
vibro-
pack.



THE DB 20 PRESSELECTOR

Thousands of DB20's were used by our Navy during the war to give tremendous increase in both gain and selectivity when used with a good communications receiver. Over-all gain of from 20 to 25 db is achieved throughout the tuning range of 550 to 33,000 KC, covered in six bands. The unit gives true production—optimum gain with best possible signal to noise ratio.

Other features include antenna change-over switch, stability and excellent reverse attenuation characteristics.

INDIVIDUAL EQUIPMENT BULLETINS
WITH PRICES AVAILABLE ON ALL
RME UNITS.





RME

FINE COMMUNICATIONS EQUIPMENT

RADIO MFG. ENGINEERS, INC.

Peoria 6, Illinois U. S. A.

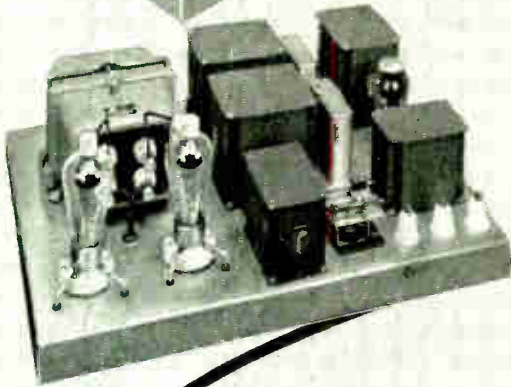
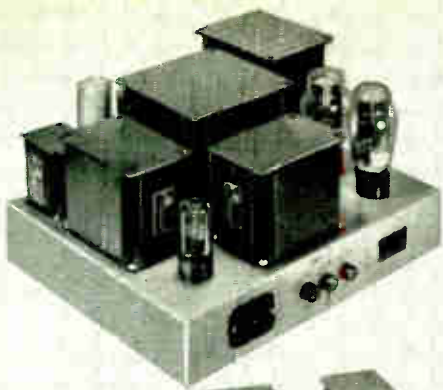


The Symbol of
QUALITY, VALUE AND GUARANTEED PERFORMANCE
in Amplifier Kits . . . Transmitter Kits and Component Parts

THESE time-tested STANCOR Kits for Amateurs are designed for simplicity, efficiency and usefulness. Backed by the recognized and respected STANCOR guarantee against defects in material and workmanship, they render complete satisfaction. Full data furnished on each unit . . . description, diagram, illustration . . . for proper assembly, wiring and operation. "Standardized" punched chassis simplifies set-up . . . accommodates variety of equipment without structural change. STANCOR units make possible maximum performance with minimum labor and expense. See your Jobber or write for full details.



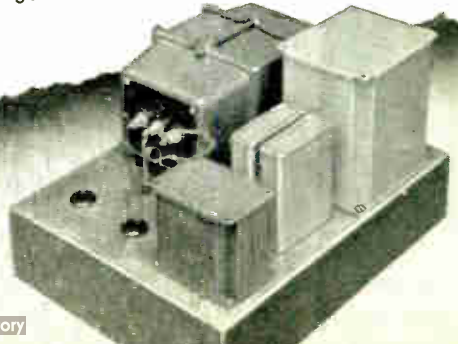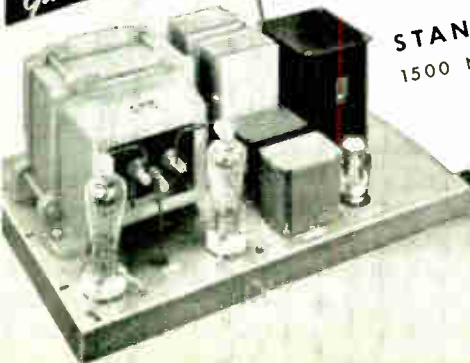STANCOR
STANDARD TRANSFORMER CORPORATION
1500 NORTH HALSTED STREET • CHICAGO 22, ILLINOIS





MILLEN MODERN PARTS

MILLEN RADIO PRODUCTS are well designed MODERN PARTS for MODERN CIRCUITS, attractively packaged, moderately priced, and fully guaranteed. They have been designed with a view toward ease and practical application as well as efficient performance. For instance, the terminals are located so as to provide shortest possible leads, mounting feet are designed for easy insertion of screws and socket contacts, so that the solder won't run down inside them and make impossible the insertion of the tube, etc. Thus our slogan, "Designed for Application." Our general catalog is available for the asking either from your favorite parts supply house or direct from the factory.



11000, 12000, 13000, 14000 SERIES CONDENSERS .077" air gaps for 3000 volt peak rating

MILLEN TYPE					
Code	Capacity per Side		Air Gap	Voltage Rating	Net Price
	Min.	Max.			
11035	36	4.6	.077"	3000	\$6.90
11050	51	6.5	.077"	3000	7.14
11070	74	9.5	.077"	3000	7.80
13035	35	4.9	.077"	3000	4.56
13050	19.5	6.3	.077"	3000	5.20
13070	71	7.3	.077"	3000	5.88
12000	204	10.7	.077"	3000	7.80
11000	90.5	12.0	.171	6000	12.00
14050	50		.171	6000	7.20
14060	60		.265	9000	12.00

CONVENTIONAL SINGLE SECTION TYPE

Code	Capacity per section		Air Gap	Finish on Plates	Net Price
	Min.	Max.			
12935	9	37	.176"	Polished	\$4.32
12936	9	37	.176	Plain	3.90
12536	6	43	.077"	Plain	2.10
12551	7	55	.077"	Plain	2.70
12576	9	76	.077"	Plain	3.00
12510	12	101	.077"	Plain	3.60
12515	18	151	.077"	Plain	4.50

CONVENTIONAL DOUBLE SECTION TYPE

Code	Capacity per section		Air Gap	Finish on Plates	Net Price
	Min.	Max.			
12035	6	43	.077"	Polished	\$4.32
12036	6	43	.077"	Plain	3.90
12050	7	55	.077"	Polished	4.10
12051	7	55	.077"	Plain	4.32
12075	9	76	.077"	Plain	5.61
12076	9	76	.077"	Plain	5.40

Code	Description	Net Price
10000	Worm Drive Unit	\$1.50
10001	Drum Meter Dial-0-100	1.85
10007	1 1/2" Nickel Silver Inst. Dial-0-100	1.50
10008	3/4" Nickel Silver Inst. Dial-0-100	1.00
10050	Dial Lock	.15
10060	Shaft Lock for 1/2" Shafts	.36
10061	Shaft Lock	.36
10065	Ventur Drive Unit	.36
10067	Shaft Bearing	.21
15001	Neutral Condenser 0.7 4.3	.90
15002	Neutral Condenser 0.5 13.5	1.05
15003	Neutral Condenser 1.5 8.5	.90
15005	Neutral Condenser 3.1 11.6	2.00
13006	Neutral Condenser 2.8 9.1	3.00
20015	Steatite Ultra Midget 15 mmfd 5Z	.75
20035	Steatite Ultra Midget 35 mmfd 5Z	1.00
20050	Steatite Ultra Midget 50 mmfd 5Z	1.20
20100	Steatite Ultra Midget 100 mmfd 5Z	1.50
20920	Steatite Ultra Midget 20 mmfd D8	1.20
20935	Steatite Ultra Midget 35 mmfd D8	1.40
21050	Steatite Ultra Midget 50 mmfd 5Z	1.75
21100	Steatite Ultra Midget 100 mmfd 5Z	1.90
21140	Steatite Ultra Midget 140 mmfd 5Z	2.10
21935	Steatite Ultra Midget 35 mmfd D8	1.90
22075	Steatite Midget 75 mmfd 5Z	1.32
22100	Steatite Midget 100 mmfd 5Z	1.38
22140	Steatite Midget 140 mmfd 5Z	1.62
22915	Steatite Midget 15 mmfd D8	1.20
22935	Steatite Midget 35 mmfd D8	1.30
22950	Steatite Midget 50 mmfd D8	1.50
23075	Steatite Dual Midget 75 mmfd per section 5Z	2.60
23100	Steatite Dual Midget 100 mmfd per section 5Z	2.50
23925	Steatite Dual Midget 25 mmfd per section D8	2.25
23950	Steatite Dual Midget 50 mmfd per section D8	2.50
24100	100 mmfd per section, Single spaced	2.75
24935	35 mmfd per section, Double spaced	2.75
25130	93 130 Air Padder	1.50
26025	3.2 25 Air Padder	.96
26040	4-50 Air Padder	1.08
26075	4.3 76 Air Padder	1.20
26100	5-97 Air Padder	1.32
26920	4.5-20 Air Padder	1.40
26935	5.5 36 Air Padder	1.50
28030	30 mmfd Mica Padder	.15
30001	Standoff, 1/2 x 1 1/4, Quartz	.15
30002	Standoff, 3/4 x 2 1/4, Quartz	.21
30003	Standoff, 1 x 2 1/4, Quartz	.55
30004	Standoff, 3/4 x 1 1/4, Quartz	.65

JAMES MILLEN



MFG. CO., INC.

MAIN OFFICE

AND FACTORY

102

MALDEN, MASSACHUSETTS, U.S.A.

World Radio History



DESIGNED for APPLICATION

Code	Description	Net Price
31001	Standoff, 1/2 x 1, Isolantite	\$.20
31002	Standoff, 1/2 x 2 1/2, Isolantite	.27
31003	Standoff, 1/2 x 2, Isolantite	.30
31004	Standoff, 1/2 x 3 1/2, Isolantite	.42
31011	Cone, 1/2 x 1/2, Steatite	.21
31012	Cone, 1 x 1, Steatite	.27
31013	Cone, 1 1/2 x 1, Steatite	.27
31014	Cone, 2 x 1, Steatite	.42
31015	Cone, 3 x 1 1/2, Steatite	.45
32100	Steatite Bushing for 3/8" hole	.30
32101	Steatite Bushing for 1/2" hole	.35
32102	Steatite Bushing for 5/8" hole	.40
32103	Steatite Bushing for 1" hole	.45
32150	Isolantite Thru-bushing, for 1" hole	.05
32201	Steatite Bushing and Hardware	.75
32303	Steatite Bushing and Hardware	3.60
32500	Isolantite Bushing	1.80
33002	Crystal Socket	.25
33004	4 Prom Socket	.24
33005	5 Prom Socket	.24
33006	6 Prom Socket	.24
33007	7 Prom, Large, Socket	.24
33008	8 Prom, Octal, Socket	.24
33087	Base Clamp for 807 etc.	.30
33102	Crystal Socket	.40
33105	Acorn Socket, QuartzQ	.90
33202	Crystal Socket	.40
33888	Aluminum Shield for 33008	.18
33991	Socket for 907 etc.	.45
34010	Shielded 10 MH receiving	.75
34100	Univer at 2.5 MH	.36
34101	Univer at 2.5 MH, less Standoff	.30
34102	Commercial type 2.5 MH	.36
34110	Univer at air core Transmitting	1.00
34151	Transmitting Choke	1.50
34210	General Purpose RFC 10 MH	.60
34225	General Purpose RFC 25 MH	.75
34240	General Purpose RFC 40 MH	.75
34285	General Purpose RFC 85 MH	1.25
34800	Intermittent Frequency Oscillator Coil	1.20
36001	Ceramic Plate Cap, 9/16" for 866 etc.	.21
36002	Ceramic Plate Cap, 1/2" for 807 etc.	.21
37001	Black Bakelite Safety Terminal	.40
37104	Four Terminal, Black Bakelite	.60
37202	Steatite Plates, Pr.	.30
37211	Bracket	.15
37222	Terminal Posts, Pr	.40
37302	Two Terminal, Steatite	.60
37303	Three Terminal, Steatite	.70
37304	Four Terminal, Steatite	.80
37305	Five Terminal, Steatite	.90
37405	Six Terminal, Steatite	1.00
37501	Low Loss Mica Bakelite Safety Terminal	.65
38001	Isolantite 3/16" O.D. Beads (Pk of 50)	.30
38500	100 Beads, 5/16" dia., QuartzQ	.60
39001	Truly Flexible Isolantite	.36
39002	Conventional	.36
39003	Solid Glass, N.P.	.21
39005	Universal Joint, Non-Insulated	.36
39006	Slide Action	.36
40205	Midnet Plug	.24
40305	Intermediate size plug	.15
41205	Midnet Socket	.30
41305	Intercalate size socket	.45
43001	Quart-Q blank form and plug	.90
43011		.90
43021	Midnet coils for each	.90
43041	band Mounted on No. 40205	.90

Code	Description	Net Price
43081	plug, No. 1 at end of code means	\$.90
43161	center link, No. 2, end link	.90
44000	QuartzQ form 1 1/2" dia. x 3 1/2"	.75
44001	QuartzQ blank form and plug	1.20
44005		1.50
44010		1.50
44020		1.50
44030	"100 watt" coils	1.50
44080	for each band, Mounted on	1.90
44160	No. 40305 plug	2.10
44500	Swinging link and socket	1.75
45000	Coll Form, 1" dia, no p., low loss mica	1.50
	base Phenolic	.21
45004	Coll Form, 1 1/2" dia, 4 p., low loss mica	.30
45005	Coll Form, 1 1/2" dia, 5 p., low loss mica	.30
	base Phenolic	.45
45500	Coll Form, 3/4" dia., Steatite	.45
46100	Coll Form, 1 1/2" dia, no p., QuartzQ	.10
47001	Coll Form, 1/2" dia., QuartzQ	.15
47002	Coll Form, 3/4" dia., QuartzQ	.35
47003	Coll Form, 1/2" dia., QuartzQ	.45
47004	Coll Form, 3/4" dia., QuartzQ	.45
53001	Sheet, 3/8 x 5/8 x 1/2, QuartzQ	.45
58000	Coll Dope, 2 oz., QuartzQ	.30
77083	"83" Hash Filter 250MA	1.00
77866	"866" Hash Filter 500MA	1.25 pr.
77872	"872" Hash Filter	1.40 pr.
79020	1 1/2" Band Wave Trap	.90
79040	7mc Band Wave Trap	.90
79080	3.5mc Band Wave Trap	.90
79160	1.7mc Band Wave Trap	.90
<i>Air Trimmed</i>		
60454	456 Diode Air Core	1.50
60455	456 Interstage (1) Air Core	4.50
60456	456 Interstage (2) Air Core	4.50
60501	5000 Interstage (2) Air Core	1.50
60502	5000 Diode Air Core	1.50
60503	5000 FM Interstage Air Core	4.50
60504	5000 FM Disc Air Core	1.50
62161	1600 Interstage Iron Core	4.50
62162	1600 Diode Iron Core	1.50
62451	456 Diode Iron Core	4.50
62456	456 Interstage Iron Core	4.50
63163	1600 RFC Air Core	4.50
63156	456 RFC Air Core	4.50
63503	5000 RFC Air Core	1.50
<i>Mica Trimmed</i>		
67454	456 Diode Iron Core	1.25
67456	456 Interstage Iron Core	1.25
67503	5000 FM Interstage Air Core	1.50
67504	5000 FM Disc Air Core	1.50
<i>Permeability Tuned</i>		
64154	456 Diode (2)	1.50
64116	456 Interstage (2)	1.50
65156	456 RFC	1.50
90500	Complete set of four Wavemeters in case	12.00
90605	Range 2.8 to 9.7 mc Wavemeter	3.00
90606	Range 9.0 to 28 mc Wavemeter	3.00
90607	Range 26 to 65 mc Wavemeter	3.00
90608	Range 50 to 110 Wavemeter	3.00
90721	Retrol	4.00


JAMES MILLEN MFG. CO., INC.
 MAIN OFFICE AND FACTORY
 MALDEN, MASSACHUSETTS, U.S.A.

103

World Radio History

HEADQUARTERS

For the Biggest Names in Amateur Radio

CAMERADIO

SINCE



1919

PIONEERS IN RADIO AND ELECTRONICS

The news that "Hams" may again take the airways finds us ready as always to serve every need for parts and supplies made by the biggest names in Radio.

Ours is an organization that grew up with radio—that kept pace with its progress from Crystal Sets to Television. Our stocks are large and complete. We have the technical "know-how" and the trade-knowledge of what is available and when!


And we've always had "Ham" operators in our organization to help you with your technical problems. Men who do understand your language.

If you are considering new design, improvement or addition to your old "Rig"—try CAMERADIO first!

QUALITY MERCHANDISE • PROMPT SERVICE

CAMERADIO CO., 963 LIBERTY AVE., PITTSBURGH 22, PA.

*For
better results
use*

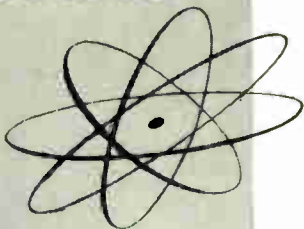

TEST EQUIPMENT




**Oscilloscope
CRO-3A**

This new cathode-ray oscilloscope is ideal for accurate and rapid service work. It is entirely portable and is designed for Frequency Modulation, Amplitude Modulation and Television service work. It can be used for the study of wave shapes and transients, measurement of modulation, adjustment of radio receivers and transmitters, the determination of peak voltages, and the tracing of electronic tube characteristics. All controls are conveniently located on the front panel. Welded steel case.



Signal Generator SG-3A Intended primarily for the accurate adjustment of receivers and the measurement of receiver sensitivity, this signal generator will also find application in radio equipment manufacturing for production and design testing. The SG-3A may also be used for the standardization of receiver performance.

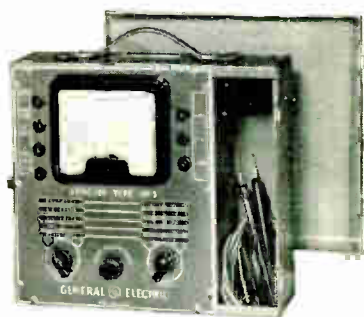It is a quality instrument which permits directly calibrated readings of Radio Frequency Output. The clearly marked dial and convenient arrangement of controls assures easy, accurate operation.



Unimeter UM-3 A portable, all-around, utility instrument for service work. A large-faced, clearly calibrated dial permits quick, accurate reading. All functions are separated to minimize any possibility of applying high voltage when preparing for current or resistance measurements. Easy identification is provided for in reading by printing scales in red and black, with values most used on the upper part of the dial. The case is of welded steel finish, in Federal wrinkle gray. Weight—approximately 10 lbs.

*Commercial quality
for amateur
station testing!*

For complete information, write to
Electronics Department, Specialty Division,
General Electric Company, Syracuse, N. Y.

17 / D7

GENERAL ELECTRIC



World's History


For better amateur rigs

INSIST UPON COMPONENTS




Safety door interlock switch

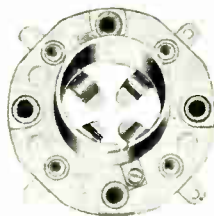An inexpensive and dependable safety switch used to interrupt the control circuits where doors, windows or covers are opened when power is on.



Electronic tube sockets

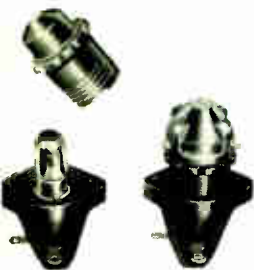Rugged and dependable these sockets have spring-like contacts at the bottom and sides which insure constant electrical connections. A complete line for receiver, transmitter and industrial tubes including a line of split type water jackets.



Indicator lamps

A "ready-to-mount" assembly for use on electric equipment panels. Vibration proof, opaque, "lock-on" cap, with or without "dimmer" feature. Choice of five color caps; also clear neon bulb type.



P. M. speakers

Introducing the new line of G-E Speakers using the new alnico No. 5 magnet material throughout. Unsurpassed in fidelity, dependability and durability. The speakers range in size from 4 inches to 12 inches. They have been completely redesigned for postwar applications.



Snap-slide fastener

A reliable and secure fastener that will not release its grip when subjected to vibration.




Thermocell crystals

The General Electric G-30 and G-31 Thermocell Crystals are designed for the ultimate in useful crystal stability—compact, dependable and quick heating. Many other types of quartz crystals and holders are available including high frequency rectifier types.



"IF" transformers

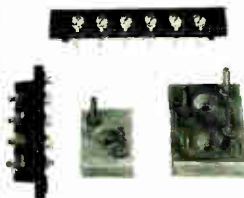Top tuned with trimmer—rugged and compact construction—low cost.



Terminal Strips

Specially designed textolite and plastic terminal strips adaptable for permanent or temporary lead connections where many wires are used. Neat, compact and efficient. Several types are now available.



Air Trimmers

Stability from 2 to 32 mmf. no reverse loops insure smooth tuning over entire range where stability is required in high frequency oscillator and discriminator circuits.



Insulated Couplings

A mechanical link that separates electrically the shaft and chassis. They allow greater flexibility in the accuracy of mounting dimensions for shafts. Insulating portion may be textolite, plastic or steatite.



Tube Clamps

An adjustable tube clamp designed to fit most of the generally used electronic tubes. Field tests have proved its superiority to withstand shock and vibration tests.



Thermoplastic cement

Ideal for cementing loud-speaker cones into metal housings, making laminated sheet metal for radio. Fast air drying, cementing either on one or both sides. No moist surfaces.

*A complete
line for
every purpose!*

For complete information, write to
Electronics Department, Specialty Division,
General Electric Company, Syracuse, N. Y.

146-03

GENERAL  **ELECTRIC**

World's history



Preferred for Performance

FOR TWO DECADES



Since the inception of modern broadcasting IRC resistors have been the overwhelming choice of discriminating amateurs. Scientifically designed and engineered to highest quality standards, IRC units "belong" in the finest rigs and can be depended upon to function with complete satisfaction.

IMPROVED NEW TYPES

While continuous laboratory research to constantly improve both design and characteristics of IRC products is no new venture with us, war requirements greatly accelerated the pace and today many new types of resistances are available which might not have reached marketing stage for months to come. Among these are the Type BTS ($\frac{1}{2}$ watt) and Type BTA (1 watt) resistors. Both are smaller than their older counterparts and have other definite advantages.

SERVICE CATALOG No. 50

Most of the resistor items you'll need frequently will be found pictured and described in detail in IRC's new Service Catalog No. 50. All units listed are "in stock" on your favorite IRC jobber's shelves or can be obtained for you by him almost overnight. If you do not have your copy of the IRC Service Catalog No. 50, stop in at your IRC Distributor's today or drop a line to Dept. RL-6.

INTERNATIONAL RESISTANCE CO.

401 N. Broad Street, Philadelphia 8, Pa.

In Canada: International Resistance Co., LTD., Toronto

IRC makes more types of resistance units, in more shapes, for more applications, than any other manufacturer in the world.



GAMMATRON TUBES



This complete line, covering a power range of 50 to 5,000 watts, embodies 19 years of pioneering and experience in the design and manufacture of tantalum tubes. Special plate, grid, and filament design, and new metal-to-glass seals, give Gammatrons remarkable VHF performance. Other features: ability to withstand high plate voltages, complete protection against tube failure due to overloading, and long, efficient operating life. The Gammatron engineers responsible for these developments will be glad to help you with your special problems.

24G
PLATE DISS.
25 W.



257B
PLATE DISS.
75 W.



454
PLATE DISS.
250 W.



HEINTZ-KAUFMAN
TUBES
DURHAM SAN FRANCISCO LTD. CALIFORNIA U.S.A.

TYPE NO.	24	24G	54	254	257B*	304L	304H	354C	354E	454L	454H	654	854L	854H	1054L	1554	2054A	3054
MAX. POWER OUTPUT: Class 'C' R.F.	90	90	250	500	230	1220	1220	615	615	900	900	1400	1800	1820	3000	3600	2000	5300
PLATE DISSIPATION: Watts	25	25	50	100	75	300	300	150	150	250	250	300	450	450	750	1000	1200	1500
AVERAGE AMPLIFICATION FACTOR	25	25	27	25		10	19	14	35	14	30	22	14	30	13.5	14.5	10	20
MAX. RATINGS: Plate Volts Plate M.A. Grid M.A.	2000 75 25	2000 75 25	3000 150 30	4000 225 40	4000 150 25	3000 1000 150	3000 1000 150	4000 300 60	4000 300 70	5000 375 60	5000 375 85	4000 600 100	6000 600 80	6000 600 110	6000 1000 125	5000 1000 250	3000 800 200	5000 2000 500
MAX. FREQUENCY, Mc.: Power Amplifier	200	300	200	175	150	175	175	50	50	150	150	50	125	125	100	30	20	30
INTERELECTRODE CAP: C _{g-p} u.u.f. C _{g-f} u.u.f. C _{p-f} u.u.f.	1.7 2.5 0.4	1.6 1.8 0.2	1.8 2.1 0.5	3.6 3.3 1.0	0.08 10.5 In 4.6 Ou	9 12 0.8	10.5 14 1.0	3.8 4.5 1.1	3.8 4.5 1.1	3.4 4.6 1.4	3.4 4.6 1.4	5.5 6.2 1.5	5 6 0.5	4 8 0.5	5 8 0.8	11 15.5 1.2	18 15 7	15 25 2.5
FILAMENT: Volts Amperes	6.3 3	6.3 3	5.0 5	5.0 7.5	5.0 7.5	5.10 26-13	5.10 26-13	5 10	5 10	5 11	5 11	7.5 15	7.5 12	7.5 12	7.5 21	11 17.5	10 22	14 45
PHYSICAL: Length, Inches Diameter, Inches Weight, Oz. Base	4 1/2 1 3/8 1 1/2 Small UX	4 1/2 1 3/8 1 1/2 Small UX	5 1/4 2 2 1/2 Std. UX	7 2 3/4 6 1/2 Std. 50 Watt	5 1/4 2 1/4 6 Giant 7 Pin	7 3/4 3 1/2 9 John-son #213	7 3/4 3 1/2 9 John-son #213	9 3 3/4 6 1/2 Std. 50 Watt	9 3 3/4 6 1/2 Std. 50 Watt	10 3 3/4 7 Std. 50 Watt	10 3 3/4 7 Std. 50 Watt	10 3/4 3 3/4 14 Std. 50 Watt	12 1/4 5 14 Std. 50 Watt	12 1/4 5 14 Std. 50 Watt	16 1/4 7 42 John-son #214	18 6 56 HK 255	21 1/4 6 66 W.E. Ca.	30 3/4 9 200 HK 255
*Beam Pentode.																		

WRITE FOR FULL DATA ON ALL **GAMMATRONS**

Ted McElroy

THE WORLD'S MOST ENTHUSIASTIC DISTRIBUTOR OF HALLICRAFTERS EQUIPMENT

Wherever we Yanks travel throughout the world, we get kidded about "world's largest", "world's best", etc. So I figure to be typically Yankee, and grab for myself the title as the world's most enthusiastic distributor of the fine transmitting and receiving equipment produced by the world's largest builder of communications equipment.

I know Hallicrafters. I've known the sets ever since Bill Halligan started making them about ten years ago. And I learned lots more about them during the past few years when they did such a remarkable job for our Armed Forces. And I'm awfully happy to tell you that I have the privilege of supplying these Hallicrafter receivers and transmitters to operators everywhere.

Now I've got to tell you something. All through this lousy war, while my boys and girls joined the Army and Navy and Marine Corps and Merchant Marine, I got itchier and itchier. Too old (so "they" said) for the Army and Navy, I finally was lucky enough to get back into harness as a seagoing radio operator. While I was away, Frank Bascomb ran the factory, and did a good job. So good, that I'm going to let him keep running it. Naturally, I'll continue the design on high speed transmitters and recorders, etc., but actually I'm going to devote myself to a job that'll enable me to be in closer touch with more operators throughout the world.

So strongly do I feel about this job that I'm planning to run the show 100% by myself. I can't write advertising like a regular advertising man. But I ain't selling radios to advertising men, I'm selling them to guys like myself — radio operators.

Radio is my life. When I tell anyone, whether an operator or one of those short wave guys, or fellows out of the Armed Services — when I tell you I'm going to give you the finest equipment with the best personal attention to every letter, inquiry or order — then you can be sure that you're going to get it. No matter where you live — here in the U.S., or Canada, Mexico, Central and South America — anywhere in the world — I'll see to it that your set reaches you in perfect operation — AND FAST.

Supposing you want a swell little set like the EC-1-A, or the Champion, or the Super Defiant. All you have to do is just to let me know, and I'll see to it that you get what you want when you want it. Yes, and I'm providing for time payments and trade-ins, etc.

I'd like you also to know that I'm getting in lots and lots of other fine products — things all you fellows need and can use. So, keep in touch with me, will you? I'm promising you the best kind of merchandise, the best kind of values, and the best kind of service.

73





Ted McElroy looks over the SX28 with Panoramic Adapter, as Bill Halligan, President of Hallicrafters, describes the units.

Joe Thompson, Hallicrafters sales, congratulates Ted McElroy on the signing of the franchise to become "the world's most enthusiastic distributor of Hallicrafters".



*Available for Immediate Delivery!
No Priority Needed!*


*Extremely low-cost Hallicrafter sponsored time payment plan.
Send me your order now, and I'll ship your set the same day.*

Ted McElroy

82 BROOKLINE AVENUE • BOSTON, MASSACHUSETTS

SOLAR capacitors

**EXCEL IN
QUALITY !**

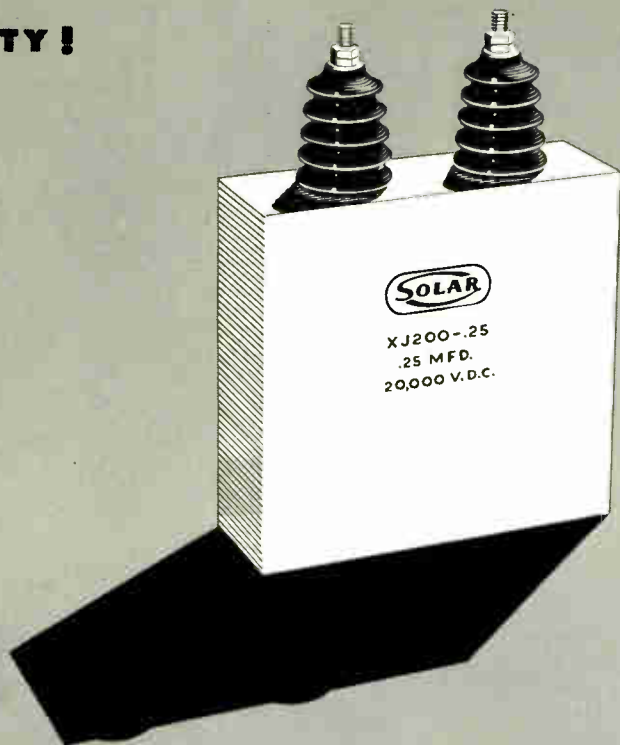

THE size varies but the *quality* of Solar Capacitors is constant. From the famous tiny "Minicap" dry electrolytic capacitor to the big Solar Type XJ high voltage filter capacitor shown, all Solar Capacitors are guaranteed "Reliable in Every Climate." That they live up to that guarantee is evident in the acceptance Solar enjoys throughout the world. Type XJ Capacitors range in D. C. voltage ratings from 6,000 to 25,000. **Solar Capacitor Sales Corporation**, 285 Madison Avenue, New York 17, N. Y.



WPI IN V. BAYBURN
PLANT
A TOTAL OF TEN
ARMY-NAVY EXCELLENCE AWARDS



Most popular transmitting tube



TYPE GL-807 Beam Power Amplifier

High-vacuum, 4-electrode, beam-power-amplifier tube, with heater-type filament. Filament voltage and current, 6.3 v and 0.90 amp. Max plate ratings (CCS) are: voltage 600 v, current 0.10 amp; input 60 w, dissipation 25 w. Max plate ratings (ICAS) are: voltage 750 v, current 0.10 amp; input 75 w, dissipation 30 w. Frequency at max ratings 60 megacycles; at reduced ratings 125 megacycles. Gm. 6,000.

WELL-KNOWN to amateurs, this versatile Type GL-807 G-E tube is used also in commercial broadcasting, communications, and police radio work. The tube is em-

ployed as a power amplifier in smaller sets; large transmitters use it for service in their low power stages.

Continuous improvement has enabled Type GL-807 to meet the ever more rigid requirements of the armed forces. Especially is this true of the screen current limits, which now are lower than before. As a result, the tube's usefulness and application-range are fur-

ther broadened in its field.

Ratings above give evidence of Type GL-807's adaptability. Here is a leading member of the improved G-E family of tubes for amateur use on which post-war "ham" broadcasting will be solidly based! See your nearest G-E distributor for complete performance data, or write to *Electronics Department, General Electric Company, Schenectady 5, New York.*

When you get back on the air, General Electric will have a complete line of tubes for you.

GENERAL ELECTRIC

161-D13-6880

TRANSMITTING, RECEIVING, INDUSTRIAL, SPECIAL PURPOSE
TUBES • VACUUM SWITCHES AND CAPACITORS



1. C.T.C. TURRET TERMINAL LUGS. Heavily silver plated brass lugs. A short cut to speedy assembly. Firmly anchored to terminal boards by simple swaging operation. Lugs heat quickly, assuring neat, positive wiring. Two soldering spaces. Stocked to fit $1/32''$, $1/16''$, $3/32''$, $1/8''$, $3/16''$ and $1/4''$ terminal board thicknesses. Also available with single soldering space.

2. C.T.C. SPLIT TERMINAL LUGS are being enthusiastically received by manufacturers of transformers and other potted units that require soldering after potting. A $.050''$ hole through the lugs makes them ideal for this type of application. Perfect for terminal boards, too, because wiring can be done from top or bottom of the board without drilling. Made of brass, heavily silver plated, to fit $3/32''$ terminal boards.

3. C.T.C. DOUBLE END TERMINAL LUGS. Twin terminal posts in a single swaging operation. Perfect electrical contact because both posts are part of the same lug. Neat, positive wiring from either top or bottom. These heavily silver plated brass lugs are stocked to fit $3/32''$ terminal boards.

4. C.T.C. ALL-SET TERMINAL BOARDS are proving a time-saver in the laboratory and on the assembly line. Just select proper width board and go to work.

All-Set Terminal Boards are made in 4 widths — $1/2''$; $2''$ and $3/16''$ linen bakelite in 4 widths — $1/2''$; $2''$ (lug row spacing $1\ 1/2''$); $2\ 1/2''$ (lug row spacing $2''$) and $3''$ (lug row spacing $2\ 1/2''$). Fit all standard resistors and condensers. Boards may be broken in fifths by bending on scribed line or used full length. Available in sets of any of the 4 widths or in any single width in lots of 6 or multiples of 6.

5. C.T.C. HAND PRESSURE SWAGER for quick, firm, uniform swaging of terminal lugs to terminal boards. Adjustable to fit all thicknesses of boards. Lugs are put in board *right side up* and may be swaged as far as $1\ 7/8''$ from edge. Adjustable pressure assures uniform swage. Unit pictured swages all C.T.C. standard Turret Lugs. Can be furnished with additional anvils and punches to fit C.T.C. Double End and Split Lugs.

6. C.T.C. MATHEMATICALLY DIMENSIONED CRYSTALS. A new C.T.C. development, mathematical dimensioning achieves greater accuracy. It assures consistent performance—guarantees frequency stability, high activity and long life in every C.T.C. Crystal.

WRITE FOR C.T.C. CATALOG NO. 100

It contains complete information on these and other C.T.C. radio and electronic components you should know about. It's yours for the asking.

CAMBRIDGE THERMIONIC CORPORATION
455 CONCORD AVENUE • CAMBRIDGE 38, MASSACHUSETTS

C T C

Constant impedance output attenuators for control of individual loud-speakers.



Let **CLAROSTAT**

Solve

your

RESISTANCE PROBLEM

Wire-wound rheostats and potentiometers in widest range of resistances, tapers, taps, etc.

Above: Composition-element control
Below: Wire-wound power rheostat.

Greenohms - rugged power resistors - 4 to 500 watts, fixed adjustable.

Plug-in tube type resistors and ballasts.

★ Just as Clarostat stood 100% behind the radio-electronics war effort, so Clarostat is now 100% behind you in your peacetime activities. ★ With vastly expanded production facilities; with skilled personnel second to none; with rare experience in meeting the critical design and production requirements of the war, Clarostat can and is offering you extraordinary collaboration in the realization of the greatest era of "ham" radio and electronic experimentation. ★ The Clarostat line is exceptionally complete — especially with the new items. ★ "Let Clarostat solve your resistance problems" with . . .

Resistors . . .

All types, both standard and special. Metal-clad strip resistors. Bakelite-molded strip resistors. Voltage dividers. Flexible resistors including Glasohms or glass-insulated power resistors and low-wattage heating elements. Greenohms - the tougher green-colored cement-coated power resistors found in quality assemblies.

Controls . . .

Composition element Clarostat controls with the stabilized element, establishing new standards for this type. 250 ohms to 5 megohms. Wire-wound rheostats and potentiometers. 1/2 to 100,000 ohms. Choice of tapers, taps, shafts, switches. Single or multiple units in tandem. Power rheostats in 25 and 50 watt sizes - the toughest

things in their class. Also padders, faders, mixers and other controls. Also output attenuators, constant impedance, for control of individual loud-speakers. The most intricate resistance devices designed and made to meet extraordinary requirements.

Resistance Devices . . .

Tube-type plug-in resistors for AC-DC sets, ballasts, line-voltage regulators, voltage-dropping power cords, etc.

Ask Our Jobber . . .

If your resistance or control requirements are conventional, ask your jobber for standard Clarostat units. Otherwise, write us direct.

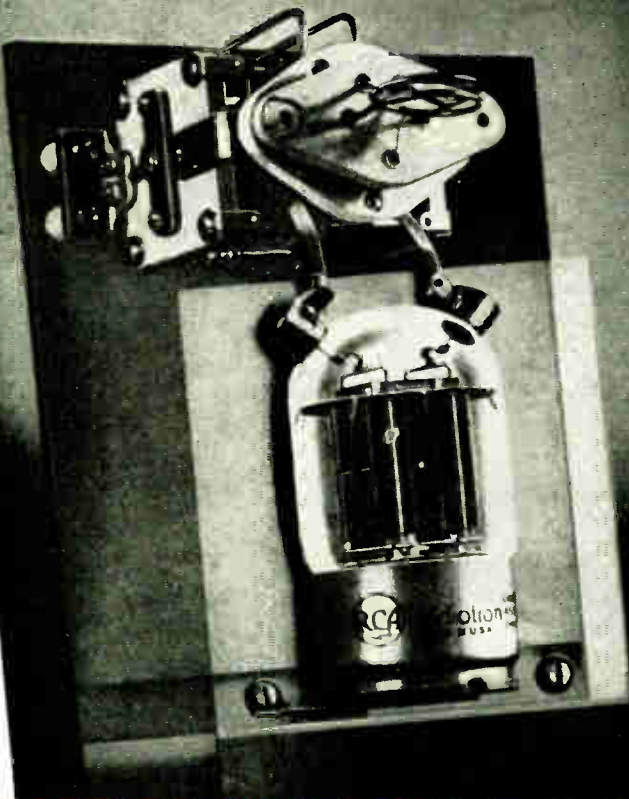

CLAROSTAT

Controls and Resistors

CLAROSTAT MFG. CO., Inc. - 285-7 N. 6th St., Brooklyn, N. Y.

GET THIS AUTHORITY

RCA GUIDE for TRANSMITTING TUBES

For
**ENGINEERS
EXPERIMENTERS**

Includes
SPECIAL CHART FOR
TRANSMITTING TUBES
(Air- and Water-Cooled),
PHOTOTUBES, CATHODE-
RAY AND SPECIAL TUBES
Price 35 Cents

HARRISON, N.J., U.S.A.

MAIL THIS COUPON TODAY

Section 62-79Q, Commercial Engineering Department
Radio Corporation of America
Harrison, N. J.

Please send me a copy of the RCA GUIDE FOR TRANSMITTING
TUBES. I am enclosing 35¢.

Name

Address

City Zone State

62-6486-78

**TO BE SURE YOU GET YOUR COPY
OF RCA GUIDE FOR TRANSMITTING
TUBES—AT THE POPULAR PREWAR PRICE
OF ONLY 35¢ — CLIP AND MAIL
THIS CONVENIENT ORDER FORM TODAY!**

GUIDE TO TRANSMITTING— TUBE SELECTION AND APPLICATION

Contains helpful information on ratings, circuits, basing, and applications of RCA transmitting tubes

NO HAM LIBRARY is complete without the RCA GUIDE FOR TRANSMITTING TUBES. You need this convenient, practical book because it contains just the information you require on up-to-the-minute tubes and circuits.

Originally published in 1939 as the "RCA Ham Guide," this book has gone through several editions and has been eagerly purchased by thousands of hams.

Only a few thousand copies of the present revised edition have been printed. The supply is limited—get your copy early!

Here is a summary of the contents of this invaluable book:

- Photographs, basing diagrams, circuits, complete technical data, and prices of all RCA transmitting tubes of interest to amateurs
- Tested, economical transmitter circuits designed by radio's foremost engineers
- Complete instructions for building a u-h-f transmitter and other types of equipment
- Condensed tables giving essential characteristics of RCA transmitting tubes, cathode-ray tubes, phototubes, thyratrons, voltage-regulator tubes, rectifier tubes, and special amplifiers

Here, in 72 pages crammed with vital information, you have one of the most popular books ever published on transmitting tubes—backed by all the years of engineering and application know-how of the RCA organization.

CONTENTS

Technical data, prices, application information on transmitting tubes, filter design curves.

Tables giving data, prices, and ratings of transmitting tubes, rectifiers, cathode-ray tubes, phototubes, voltage regulators, special amplifiers, and relay tubes.

General tube and transmitter data—including choice of tube types, grid-bias considerations, inductance and capacitance for tuned circuits, neutralizing, tuning Class C r-f amplifiers, how tube ratings are determined, interpretation of tube ratings, circuits, mathematical calculations, and other vital information.

How To Build—

- A variable-frequency oscillator with an r-f power output of 10 to 25 watts over a frequency range from 1.75 to 30 mc.
- The RCA "economy" transmitter with 70-watt c-w output over frequency range from 3.7 to 7.5 mc.
- The RCA-815 u-h-f transmitter with 30 to 45 watts phone output over frequency range from 15 to 120 mc.
- The RCA single-control 360-watt transmitter (360 watts input on c-w and 240 watts input on phone) over frequency range from 1.9 to 7.5 mc.
- The RCA 5-band plate-modulated transmitter with 450 watts input on c-w and 310 watts input on phone over frequency range from 1.7 to 30 mc.

THE FOUNTAINHEAD OF MODERN TUBE DEVELOPMENT IS RCA

DO YOU HAVE THESE OTHER RCA PUBLICATIONS?

Designed to Keep You Up To The Minute in Technical Information.

RCA HB3 TUBE HANDBOOK—An invaluable loose-leaf, engineering reference book on all RCA tubes—transmitting, receiving, cathode-ray, and special types. Kept up to date with periodic revisions. Sold on subscription basis—write for descriptive folder and order form.

RCA RC-14 RECEIVING-TUBE MANUAL—Data on 340 different RCA receiving-tube types, 256 pages containing application data, circuits, charts, and simplified tube theory. Net price \$0.25.

RCA PHOTOTUBES BOOKLET—A clear exposition of phototube theory, including data on 15 types, curves, and circuits for light-operated relays, light measurement, and sound reproduction. Free upon request.

RCA RADIOTRON DESIGNER'S HANDBOOK—Fundamental principles of practical circuit design, prepared especially for the radio-set designer. Valuable to amateurs interested in the subject. Illustrated, and contains reference charts, tables, and miscellaneous data. Stiff cover. 356 pages. Net price \$1.00.

RCA POWER AND SPECIAL-TUBES BOOKLET (TT-100)—An illustrated catalog of air- and water-cooled transmitting tubes, rectifiers, television tubes, phototubes, oscillograph tubes, thyratrons, voltage regulators, and special amplifier tubes. Free upon request.

RCA RECEIVING TUBES AND ALL-EO SPECIAL-PURPOSE TYPES BOOKLET (1275-B)—Characteristics and socket connections of 327 receiving types and 38 allied types. Free upon request.

All of these publications are available from RCA tube distributors, or direct from Radio Corporation of America. Write Commercial Engineering Department, Section 62-79Q, Harrison, N. J.




RADIO CORPORATION OF AMERICA

TUBE DIVISION • HARRISON, N. J.

**ADJUSTABLE
RESONATOR**

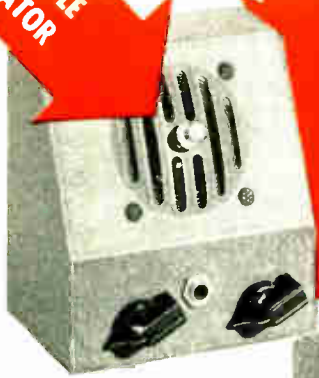T.A.C. ANNOUNCES THE NEW CODE PRACTICE OSCILLATONES WITH ADJUSTABLE RESONATOR for Greater Volume . . . Better Tone



Here is the last word in code practice Oscillatones. New Adjustable Resonator (optional) increases volume five times. Tone frequency variable from 600 to 1500 cycles. Volume controllable from 0 to FULL ON. "PM" DYNAMIC speaker may be disconnected during headphone operation if desired. Up to 300 headphones may be used. Has phone jack for headphones. Optional built-in key. Absolutely safe. No shocks. Clean cut, chirpless keying. Operates on 110 V. AC or DC. Uses 117N7GT tube. Gray crackle finish metal case.

Designed by
**THE WORLD'S
CHAMPION
RADIO
TELEGRAPHER**

MS 710 has all features described but less resonator and less built-in key. Amateur net price

9.00

MS 710R with resonator but less built-in key. Amateur net price

10.50

MS 710P with built-in key but less resonator. Amateur net price

11.50

MS 710PR DeLuxe Master Oscillatone with all features including resonator and built-in key. Amateur net price...

13.00


NOW IN STOCK AT ALL LEADING RADIO DISTRIBUTORS

LEG CLAMP HAND KEY



Made to Signal Corps specifications. Spring metal band fits thigh of leg comfortably. Folds for compact packing. With 5 ft. rubber covered cord and plug. Model J-45; Amateur Net Price..... **5.10**


PROFESSIONAL SPEED KEY

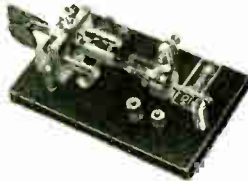

Fully adjustable. Model CP 510. Amateur Net Price..... **6.75**

Designed by World's Champion Radio Telegrapher. Gray wrinkle finish and polished chrome. Silver contact points.

DELUXE SPEED KEY

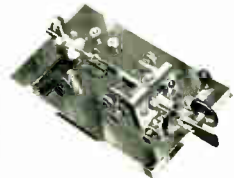

Nine points of adjustment. Model CP 810; Amateur Net Price..... **9.75**

Finest tube available. Chrome finished base and super-structure. Selected blue steel springs for uniform performance. Silver contacts.

MODEL 200 HAND KEY



circuit closing switch. Model 200; Amateur Net Price..... **2.25**

Built to professional standards. Coin silver contacts. Accurately machined bearing screws. Black crackle finish metal base with

STANDARD HAND KEY



Made to Signal Corps specifications. Solid lever. Model J-37; Amateur Net Price..... **1.80**

coin silver contacts. Silver plated Bakelite base. Very smooth operation.

DELUXE HAND KEY



Circuit closing switch. Model 300; Amateur Net Price..... **3.45**

Finished in polished chrome and nickel. 3/16" diameter contacts adjustable for tension, spacing and bearing position.

TELEGRAPH Apparatus Co.


412 SOUTH GREEN ST.

World Radio History

CHICAGO 7, ILLINOIS

Engineered

FOR **DEPENDABLE PERFORMANCE**

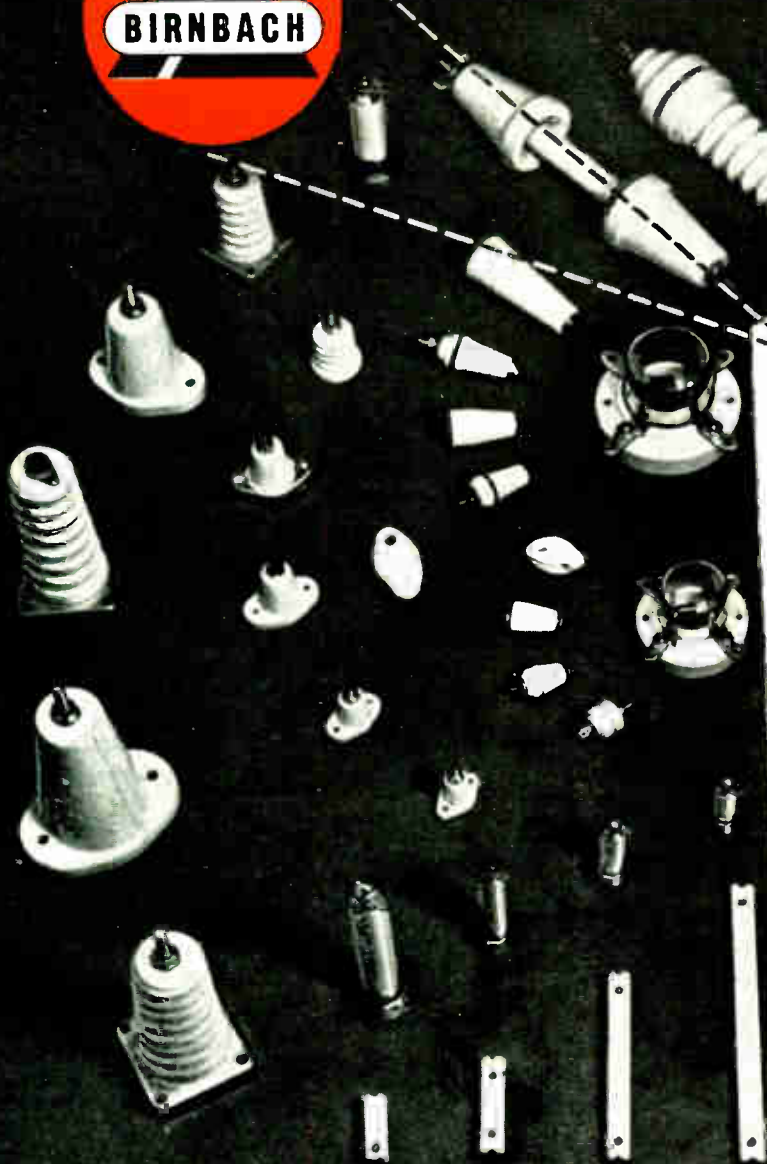

Quality
Since 1923

... Birnbach has won top recognition by specializing exclusively in the engineering, design and manufacture of

**CERAMIC—PORCELAIN
& STEATITE INSULATORS**

also in the manufacture
of **RADIO HARDWARE**
and **ANTENNAS**

We also carry a complete
line of **WIRES,**
CABLES & HOOK-UP
WIRES

Birnbach products continue to win
top honors for uniformly dependable
performance.



Send for your copy
of our Catalog H-46

BIRNBACH RD 470W

BIRNBACH NO 471W

BIRNBACH RADIO CO., Inc.
145 HUDSON ST. NEW YORK, N. Y., U. S. A.

QUALITY

STACO


RELAYS




No. MR-11 • Miniature relay, 3/16" fine silver SPDT contacts, 110-volt AC coil, \$1.59 net. MR-7 is 6-volt AC model of some price.



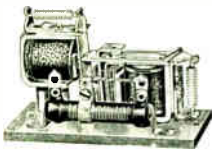
No. MRD-2 • Miniature relay 2500-ohm coil operates on 12 ma., 3/16" fine silver DPDT contacts, \$2.70 net. MRD-5 for 7.5-ma. operation and MRD-6 for 6-volt DC are \$3.60 and \$2.70 respectively. MRD-11 for 110-volt AC and MRD-7 for 6-volt AC are each \$3.00.



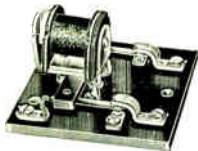No. OA-2 • Overload relay, adjustable for 250-500 ma., operating and reset coils are 110-volt AC, 3/16" fine silver SPDT contacts \$4.50 net. OA-5 is 110-volt AC model for 500-1000 ma. range. Other models for 6-volt DC and 6-volt AC and for either range are all priced at \$4.50 net.



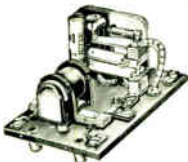
No. ABA • Antenna change-over relay, 3/16" fine silver DPDT contacts, 110-volt AC coil, \$3.00 net. Type ABD for 6-volt DC operation, \$3.00. Types AMA (110-volt AC) and AMD (6-volt DC) Mycolex insulated are \$4.00 net. Other R.F. Relays, SPST and DPST are available at from \$2.10 to \$3.00.



No. TD-11 • Time delay relay, room temperature compensator, adjustable delay from 5 seconds to 1 minute, 110-volt AC operation, \$6.45 net. Model TD-4 for 15 seconds to 45 seconds delay and less compensator, \$4.50 net.



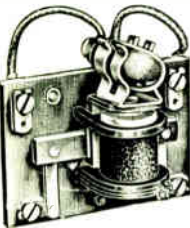No. CMA-10G • Sensitive power relay, will control 1 HP on 115-volt AC or 1/2 HP on 230-volt AC, 10,000-ohm coil, will operate on 6 ma. DC, SPDT Snap action contacts. \$3.25 net. Other SPDT models from \$3.73 to \$5.25. DPDT models from \$6.00 to \$7.50.



No. MSA • Mercury switch relay, will handle 1/4 HP motor or its equivalent, in addition to the SPST mercury contacts there is a SPST (double break) 3/16" fine silver contact set, 110-volt AC coil, \$3.75 net. Models MSA-6 (6-volt AC) and MSD-6 (6-volt DC) are also available at \$3.75.

No. MR-2 • Miniature relay, 2500-ohm coil, operates on 6 ma., SPDT contacts are 3/16" fine silver, \$1.50 net. MR-5 (5000-ohm) and MR-6 (6-volt DC) are \$2.10 and \$1.50 respectively.

No. LEA • Latching relay, electrical reset, 110-volt AC coils, 3/16" fine silver SPDT contacts, \$3.75 net. LEA-6 for 6-volt AC and LED for 6-volt DC are also \$3.75 each.



No. KBA • Keying relay, high speed operating, 3/16" SPST (double break) fine silver contacts, 110-volt AC coil, \$2.10 net. Models KBD for 6-volt DC and KBA-6 for 6-volt AC are available at the same price.

No. BBA • Break-in relay, four-pole (DPDT, SPST (normally open) and SPST (normally closed), 3/16" fine silver contacts, 110-volt AC coil, \$4.20 net. Type BBD for 6-volt DC operation is \$4.20. Types BMA (110-volt AC) and BMD (6-volt DC) Mycolex insulated are \$6.00 net.

No. T63F • Communication relay, one break and one make contact sets, 3/16" fine silver contacts, 6300-ohm coil operates on 1/10 watts, \$3.30 net. T10G—10,000-ohm coil—\$3.30, T40F—4000-ohm coil—\$3.15, T10F—1000-ohm coil—\$2.85, T25E—250-ohm coil—\$2.55.

No. PMA-1 • Power relay, will control 1 HP motor on 115-volt AC or 1/2 HP on 230-volt AC, 110-volt AC coil, SPDT snap action contacts, \$4.05 net. Models PMC-1 (6-volt AC) and PMD-1 (6-volt DC) are available at \$4.05 DPDT models of above, PMA-2 (110-volt AC), PMC-2 (6-volt AC) and PMD-2 (6-volt DC) are each \$6.00.

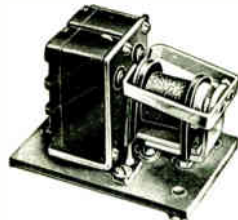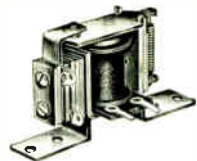No. SR-50C • Sensitive electronic relay, 12-milliwatt operation, will control 150-watt non-inductive load, SPDT fine silver contacts, 5000-ohm coil, pickup at 1.55 ma., \$5.00 net. Relays with coil resistances of 50, 100, 250, 500, 1000, and 2000 ohms are available and priced at \$4.50.



See Your Jobber or Write for New Catalog

STANDARD ELECTRICAL PRODUCTS CO.

404 LINDEN AVENUE

• • •

DAYTON 3, OHIO

W9HA AND W9KFD ARE ALWAYS READY TO HELP ON HAM PROBLEMS, SEND THEM IN

SINCE 1925



HEADQUARTERS FOR HAMS

Factory Distributors

- ABBOTT
- ADVANCE
- ALABAMA
- ALLIANCE
- ALPHA
- AMERICAN
- AMPHENOL
- AMRECO
- ARL
- ATL
- AMPEREX
- AMPERITY
- ASTATIC
- ATLANTIC
- B & W
- BELOIT
- BELL
- BERNARD
- BOLEY
- BOGUS
- BOUSH
- BUD
- BURGESS
- CARDWELL
- CENTRAL
- CHALODGRAPH
- COMPTON
- CORNELL
- CROWE
- DEAKE
- DUNLOP
- DUNCO
- EMPHON
- EMAC
- ESCO
- ELECTRONIC
- ERIC
- GAMMATRON
- GC
- GE
- GENERAL
- GUARDIAN
- HALLCRAFTER
- HAMMARLUND
- HICKOK
- HOWARD
- ICA
- IRC
- JACKSON



YES—for more than twenty years Amateurs in all parts of the world have relied on us for all their equipment. As authorized Factory Distributors for all leading manufacturers, we carry only the best and the newest Receivers, Transmitters, Parts, etc.


Our years of experience, our tremendous stock, and, above all, our sincere desire to render friendly and helpful service make Harrison your most satisfactory source for all your requirements.

Your orders are welcomed. They will be quickly filled at the very lowest Amateur prices.

May we serve you?

73 de
BILL HARRISON, W2AVA

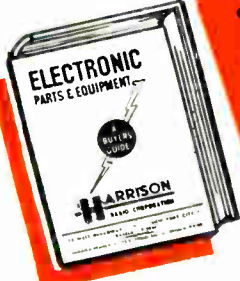A postcard will put you on the list to receive mailings of "Harrison Has It"—our bulletins of New Items, Hard-to-get Gear, and "Harrison Specials"—those famous money-saving values! Send it now. *Just write "H H I!"



Do you have "Electronic Parts and Equipment"—the NEW 800 page Buyers Guide? You can obtain one without charge—write today.

- JANETTE
- JENSEN
- J. JOHNSON
- JONES
- KENYON
- KRAUTER
- LECTROHM
- LITTELFUSE
- MARSHNER
- MILLER
- MILLER
- MULLER
- NATIONAL
- OHMITE
- FARNITAL
- PIGNEER
- PRECISION
- PREMAX
- PRESTO
- PYREX
- RADIART
- RCP
- RME
- RAYTHEON
- RCA
- SANGAMO
- SHURE
- SIGNAL
- SIMPSON
- SPEED-X
- SPRAGUE
- STANCOR
- SUPREME
- SYLVANIA
- TAYLOR
- THORNDARSON
- TRIPLEX
- TRIPLETT
- TUNNER
- UNITED
- UTC
- UNIVERSAL
- UNIVERSITY
- UTAH
- VIRE O'LEK
- WARD LEONARD
- WESTINGHOUSE
- WESTON



HARRISON RADIO CORPORATION

12 WEST BROADWAY • NEW YORK CITY 7
BARCLAY 7-9854

JAMAICA BRANCH — 172-31 Hillside Ave. — REPUBLIC 9-4102

Taylor Tubes

100% for Amateurs!



Frank J. Hajek, Pres.
W9ECA

For Amateurs — by Amateurs — that expresses Taylor Tubes basic policy in a nutshell. Since our beginning, our main efforts have been to develop tubes that would give “More Watts Per Dollar” to Amateur Radio Operators. Of course, we do have countless tubes in Broadcast and Police Radio Transmitters and in many industrial and medical units, but our main efforts have been, and always will be, “good old ham radio.” Taylor Tubes pioneered new standards of tube values with such tubes as the 866 Jr., 866A, T-20—TZ-20, T-40—TZ-40, T-55, T-200 and others. Taylor Tubes inaugurated a generous replacement policy and was first to give Hams a complete transmitter manual. You can count on continued leadership by Taylor Tubes.

FREE FOR THE ASKING!

New Taylor Tube Manual gives full information on all Taylor Tubes and has 32 pages of valuable technical data. Get one at your Radio Parts Distributor or write to us.



Rex L. Munger, Sales Mgr.
W9LIP

“MORE WATTS PER DOLLAR”

Taylor HEAVY **CUSTOM BUILT** DUTY **Tubes**

TAYLOR TUBES INC., 2312-18 WABANSIA AVE., CHICAGO 47, ILL.

HOWARD

... a Great Name in

Radio Communications

**... a Symbol of Dependability
with Amateurs Everywhere!**

Superlative quality, advanced engineering and efficient performance — that rare combination of all that is best in radio, reaches the summit of satisfaction in communication products bearing the Howard Radio name.

You can be sure that Howard products for the future will in every way reflect the same skills and craftsmanship that have for years made them favorites with Amateurs throughout the entire world.

HOWARD RADIO COMPANY

1731-35 BELMONT AVE • CHICAGO 13, ILL.

America's Oldest Radio Manufacturer

Handy for Hams!

QUARTZ CRYSTAL AMATEUR KIT*

3 CRYSTAL BLANKS (TC — made to Army Air Corps Specifications) approximately 2 parts Drift, Operative 7,000, 14,000, and 28,000 kc.

1 BAG ABRASIVE for grinding crystals to desired frequency together with folder of instructions for most efficient method of grinding crystals.

2 HOLDERS complete with both regular electrodes and springs and two additional sets of electrodes.

*Additional crystals, holders and electrodes
may be secured*

Complete ONLY \$100
Postpaid

★ Quality guaranteed by a Company that has made more than 2,000,000 crystals for the Armed Forces. We are able to make this offer only because this is surplus material.



PRODUCTS COMPANY

USE THIS ORDER BLANK BEFORE SUPPLY IS EXHAUSTED

CRYSTAL PRODUCTS, INC.
1519 McGee, Kansas City, Mo.

Send me..... Quartz Crystal Amateur Kits as advertised, Postpaid. Cash Enclosed. C.O.D.

NAME.....

ADDRESS.....

CITY..... STATE.....

QST BINDERS

Those who take pride in the appearance of their lay-out and wish to keep their reference file of **QST's** in a presentable manner, appreciate the **QST** binder. It is stiff-covered, finished in beautiful and practical fabrikoid. Cleverly designed to take each issue as received and hold it firmly without mutilation, it permits removal of any desired issue without disturbing the rest of the file. It accommodates 12 copies of **QST**. Opens flat at any page of any issue.

With each Binder is furnished a sheet of gold and black gummed labels for years 1927 through 1947. The proper one can be cut from the sheet and pasted in the space provided for it on the back of the binder. The back copies of **QST** contain the record of development of modern amateur technique. They are invaluable as technical references.

Back copies are generally available—list will be sent upon request.


Binder Price

\$1.50 each
postpaid

Available only in U. S.
and Possessions




The standard elementary guide for the prospective amateur. Features equipment which, although simple in construction, conforms in every detail to present practices. The apparatus is of a thoroughly practical type capable of giving long and satisfactory service—while at the same time it can be built at a minimum of expense. The design is such that a high degree of flexibility is secured, making the various units fit into the more elaborate station layouts which inevitably result as the amateur progresses. Complete operating instructions and references to sources of detailed information on licensing procedure are given.

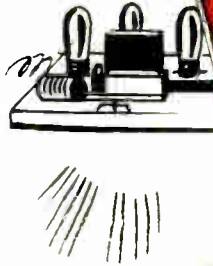

25c

Postpaid Anywhere



This booklet is designed to train students to handle code skillfully and with precision, both in sending and in receiving. Employing a novel system of code-learning based on the accepted method of sound conception, it is particularly excellent for the student who does not have the continuous help of an experienced operator or access to a code machine. It is similarly helpful home-study material for members of code classes. Adequate practice material is included for classwork as well as for home-study. There are also helpful data on high-speed operation, typewriter copy, general operating information—and an entire chapter on tone sources for code practice, including the description of a complete code instruction table with practice oscillator.

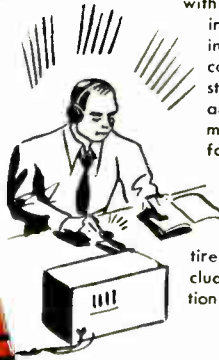

25c

Postpaid Anywhere

To obtain an amateur operator's license you must pass a government examination. The License Manual tells how to do that—tells what you must do and how to do it. It makes a simple and comparatively easy task of what otherwise might seem difficult. In addition to a large amount of general information, it contains questions and answers such as are asked in the government examinations. If you know the answers to the questions in this book, you can pass the examination without trouble.

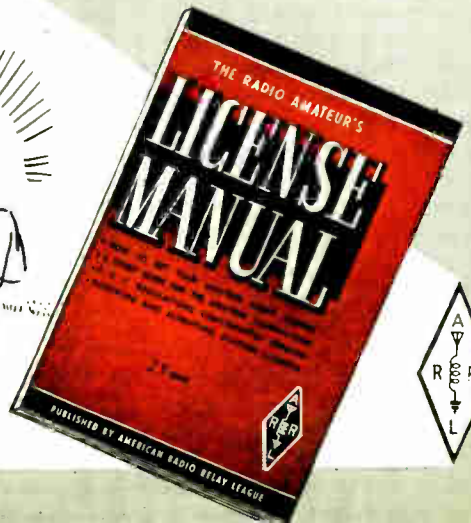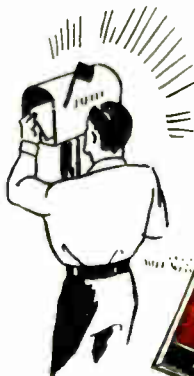


25c


Postpaid Anywhere

THE OFFICIAL MAGAZINE OF THE AMERICAN RADIO RELAY LEAGUE

QST faithfully and adequately reports each month the rapid development which makes Amateur Radio so intriguing. Edited in the sole interests of the members of The American Radio Relay League, who are its owners, **QST** treats of equipment and practices and construction and design, and the romance which is part of Amateur Radio, in a direct and analytical style which has made **QST** famous all over the world. It is essential to the well-being of any radio amateur. **QST** goes to every member of The American Radio Relay League and membership costs \$2.50 per year in the United States and Possessions. All other countries \$3.00 per year. Elsewhere in this book will be found an application blank for A.R.R.L. membership.

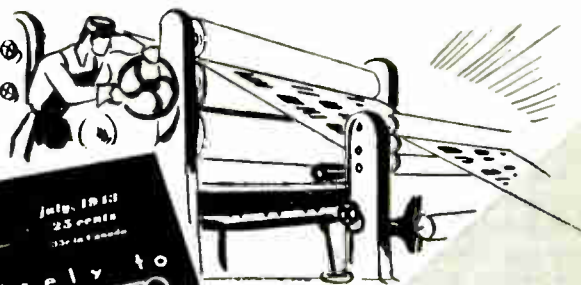For thirtyone years (and thereby the oldest American radio magazine) **QST** has been the "bible" of Amateur Radio.





In keeping with its policy of providing all services within its power, The American Radio Relay League makes available to amateurs and would-be amateurs literature properly prepared to present in the best form all available information pertaining to amateur radio. The fact that its offices are the national and international headquarters of radio amateurs, makes League publications authoritative, complete, up-to-the-minute; written from a thoroughly practical amateur's point-of-view. These publications are frequently revised and augmented to keep abreast of the fast-changing field. At this time they will be found particularly adaptable for radio training purposes. All are printed in the familiar *QST* format which permits thorough but economical presentation of the information. Most of the publications and supplies described in the following pages are handled by your dealer for your convenience.

**THE AMERICAN RADIO
RELAY LEAGUE, INC.**

WEST HARTFORD 7
CONNECTICUT




Amateurs are noted for their ingenuity in overcoming by clever means the minor and major obstacles they meet in their pursuit of their chosen hobby. An amateur must be resourceful and a good tinkerer. He must be able to make a small amount of money do a great deal for him. He must frequently be able to utilize the contents of the junk box rather than buy new equipment. Hints and Kinks is a compilation of hundreds of good ideas which amateurs have found helpful. It will return its cost many times in money savings—and it will save hours of time.

50c

Postpaid

A comprehensive manual of antenna design and construction, by the headquarters staff of the American Radio Relay League. Eighteen chapters, profusely illustrated. Both the theory and the practice of all types of antennas used by the amateur, from simple doublets to multi-element rotaries, including long wires, rhomboids, vees, phased systems, v.h.f. systems, etc. Feed systems and their adjustment. Construction of masts, lines and rotating mechanisms. The most comprehensive and reliable information ever published on the subject.

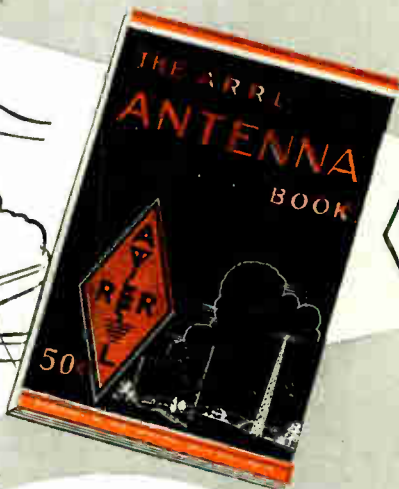

50c

Postpaid

The Story of Amateur Radio, by Clinton B. DeSoto—a detailed, accurate presentation in full book length of all the elements that have served to develop the most unique institution of its kind in the history of the world. A book of history but not a history-book, TWO HUNDRED METERS AND DOWN: The Story of Amateur Radio tells in spirited, dramatic fashion the entire chain of significant events in the development of the art.


Approximately 200 pages, 90,000 words, with durable imitation leather-red paper cover

\$1.00
Postpaid

Deluxe edition bound in blue cloth

\$2.00
Postpaid



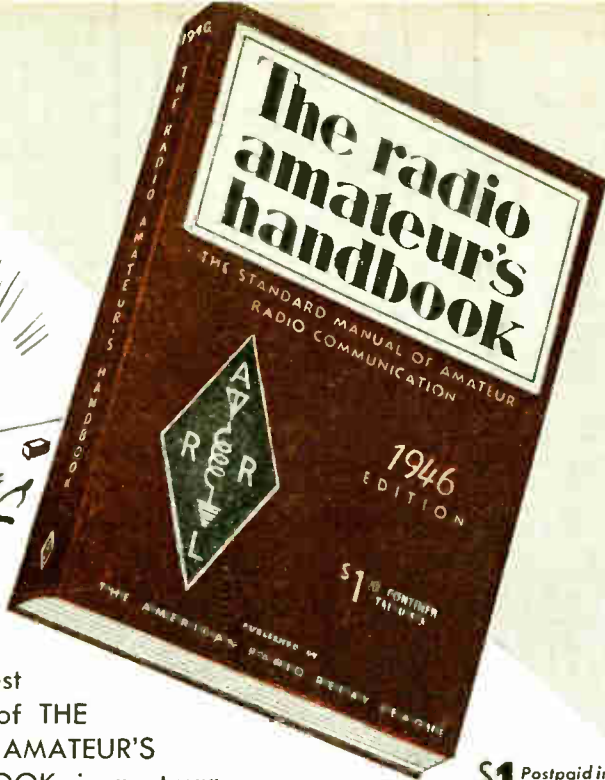


The latest edition of THE RADIO AMATEUR'S HANDBOOK is postwar in content, containing 688 pages of the kind of information which has made the HANDBOOK world-famous. To maintain the high standard of practical usefulness set by previous editions, a new treatment of the constructional sections of the HANDBOOK has been accomplished. The theory and design sections cover every subject encountered in practical radio communication. Completely sectionalized by topics with abundant cross-referencing, and fully indexed. The HANDBOOK continues to be the world's most valuable and widely-used radio book.



\$1 Postpaid in Continental U. S. A.
 \$1.50 Postpaid Elsewhere
 Buckram Bound \$2.00

50c

Postpaid Anywhere

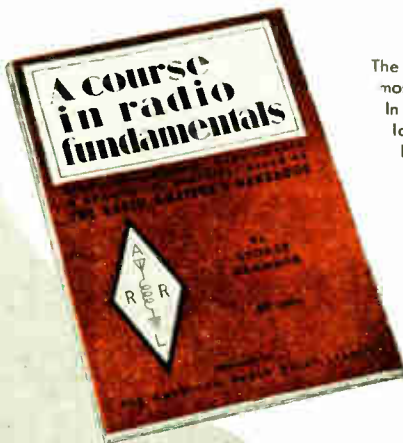

The objective in preparing this course was to accent those principles most frequently applied in actual radio communication. "A Course In Radio Fundamentals" is a study guide, examination book and laboratory manual. Its text is based on the "Radio Amateur's Handbook." Either the special edition prepared during the war for training purposes or the Standard Edition may be used. References contained in the "Course" are in both editions. As a text, this book greatly smooths the way for the student of the technicalities of radio. It contains interesting study assignments, experiments and examination questions for either class or individual instruction. It describes in detail 40 experiments with simple apparatus giving a complete practical knowledge of radio theory and design.

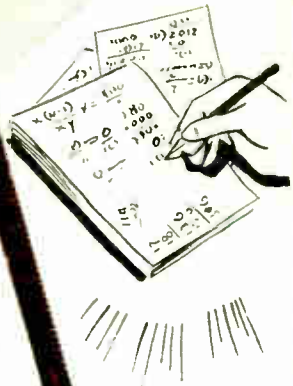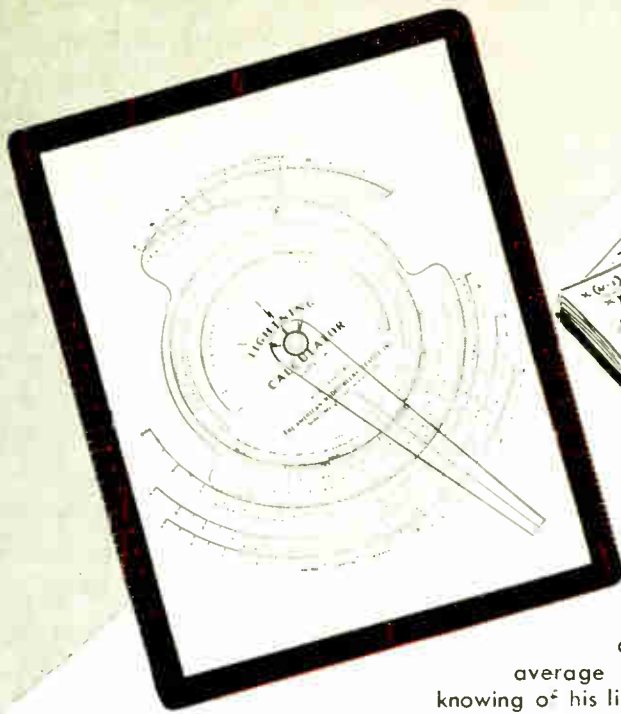

Aware of the practical bent of the average amateur and knowing of his limited time, the

League, under license of the designer,

W. P. Koehel, has made available these calculators

to obviate the tedious and sometimes difficult mathematical work involved in the design and construction of radio equipment. The lightning

calculators are ingenious devices for rapid, certain and simple solution of the various mathematical problems which arise in radio and allied work.

They make it possible to read direct answers without struggling with formulas and computations. They are tremendous time-savers for amateurs, engineers, servicemen and experimenters. Their accuracy is more than adequate for the solution of practical problems, and is well within the limits of measurement by ordinary means. Each calculator has on its reverse side detailed instructions for its use; the greatest mathematical ability required is that of dividing or multiplying simple numbers. They are printed in several colors. You will find lightning calculators the most useful gadgets you ever owned.

RADIO CALCULATOR

TYPE A

This calculator is useful for the problems that confront the amateur every time he builds a new rig or rebuilds an old one or winds a coil or designs a circuit. It has two scales for physical dimensions of coils from one-half inch to five and one-half inches in diameter and from one-quarter to ten inches in length; a frequency scale from 400 kilocycles through 150 megacycles; a wavelength scale from two to 600 meters; a capacity scale from 3 to 1,000 micro-microfarads; two inductance scales with a range of from one microhenry through 1,500; a turns-per-inch scale to cover enameled or single silk covered wire from 12 to 35 gauge, double silk or cotton covered from 0 to 36 and double cotton covered from 2 to 36. Using these scales in the simple manner outlined in the instructions on the back of the calculator, it is possible to solve problems involving frequency in kilocycles, wavelength in meters, inductance in microhenrys and capacity in microfarads, for practically all problems that the amateur will have in designing—from high-powered transmitters down to simple receivers. Gives the direct reading answers for these problems with accuracy well within the tolerances of practical construction.

\$1.00
Postpaid

OHM'S LAW CALCULATOR

TYPE B

This calculator has four scales:


- A power scale from 10 microwatts through 10 kilowatts.
- A resistance scale from 01 ohm through 100 megohms.
- A current scale from 1 microampere through 100 amperes.
- A voltage scale from 10 microvolts through 10 kilovolts.

With this concentrated collection of scale, calculations may be made involving voltage, current, and resistance, and can be made with a single setting of a dial. The power or voltage or current or resistance in any circuit can be found easily if any two are known. This is a newly-designed Type B Calculator which is more accurate and simpler to use than the justly-famous original model. It will be found useful for many calculations which must be made frequently but which are often confusing if done by ordinary methods. All answers will be accurate within the tolerances of commercial equipment.

\$1.00
Postpaid


STATION OPERATING

Sup

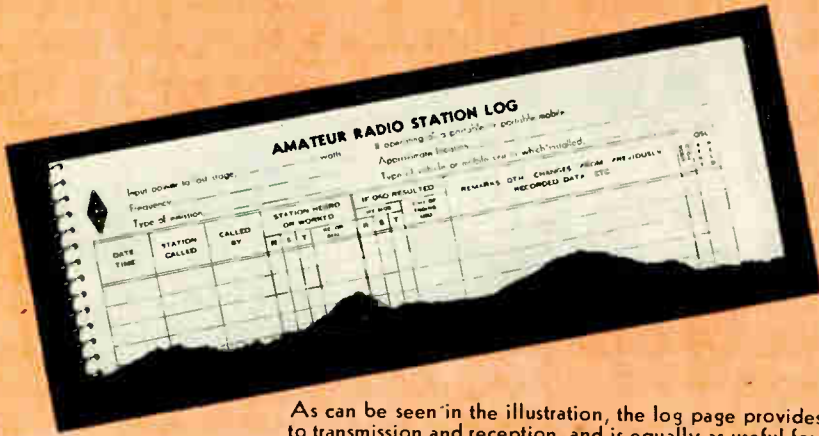

LOG BOOK

As can be seen in the illustration, the log page provides space for all facts pertaining to transmission and reception, and is equally as useful for portable or mobile operation as it is for fixed. The log pages with an equal number of blank pages for notes, six pages of general log information (prefixes, etc.) and a sheet of graph paper are spiral bound, permitting the book to be folded back flat at any page, requiring only the page size of 8½ x 11 on the operating table. In addition, a number sheet, with A.R.R.L. Numbered Texts printed on back, for traffic handlers, is included with each book. \$5.00 per book or 3 books for \$11.

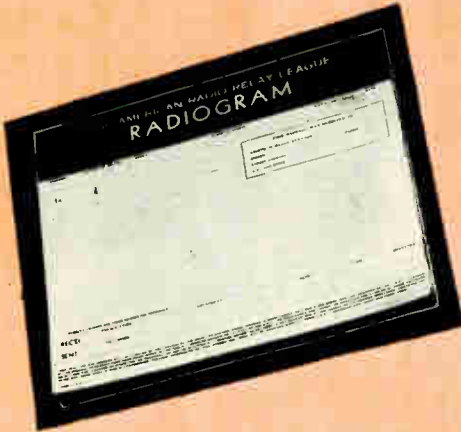

OFFICIAL RADIOGRAM FORMS

The radiogram blank is designed to comply with the proper order of transmission. All blocks for fill-in are properly spaced for use in typewriter. It has a heading that you will like. Radiogram blanks, 8½ x 7¼, lithographed in green ink, and padded 100 blanks to the pad, 25c per pad, postpaid.

MESSAGE DELIVERY CARDS

Radiogram delivery cards embody the same design as the radiogram blank and are available in two styles — on stamped government postcard, 2c each; unstamped, 1c each.



The operating supplies shown on this page have been designed by the A.R.R.L. Communications Department.

STATIONERY

Members' stationery is standard 8½ x 11 bond paper which every member should be proud to use for his radio correspondence. Lithographed on 8½ x 11 paper.

100 Sheets, **50c** 250 Sheets, **\$1.00**

500 Sheets, **\$1.75**

POSTPAID



In the January, 1920 issue of *QST* there appeared an editorial requesting suggestions for the design of an A.R.R.L. emblem — a device whereby every amateur could know his brother amateur when they met, an insignia he could wear proudly wherever he went. There was need for such a device. The post-war boom of amateur radio brought thousands of new amateurs on the air, many of whom were neighbors but did not know each other. In the July, 1920 issue the design was announced — the familiar diamond that greets you everywhere in Ham Radio — adopted by the Board of Directors at its annual meeting. It met with universal acceptance and use. For years it has been the unchallenged emblem of amateur radio, found wherever amateurs gathered, a symbol of the traditional greatness of that which we call Amateur Spirit — treasured, revered, idealized.

THE LEAGUE EMBLEM, with both gold border and lettering, and with black enamel background, is available in either pin (with safety clasp) or screw-back button type.

In addition, there are special colors for Communications Department appointees.

- Red enameled background for the SCM.
- Blue enameled background for the ORS or OPS.

THE EMBLEM CUT: A mounted printing electro-type, ⅜" high, for use by members on amateur printed matter, letterheads, cards, etc.

50c EACH,
POSTPAID



Stationery and Emblems are available only to A.R.R.L. Members

The American Radio Relay League

THE American Radio Relay League, Inc., is a non-commercial association of radio amateurs, bonded for the promotion of interest in amateur radio communication and experimentation, for the relaying of messages by radio, for the advancement of the radio art and of the public welfare, for the representation of the radio amateur in legislative matters, and for the maintenance of fraternalism and a high standard of conduct.

It is an incorporated association without capital stock, chartered under the laws of Connecticut. Its affairs are governed by a Board of Directors, elected every two years by the general membership. The officers are elected or appointed by the Directors. The League is non-commercial and no one commercially engaged in the manufacture, sale or rental of radio apparatus is eligible to membership on its board.

"Of, by and for the amateur," it numbers within its ranks practically every worth-while amateur in the nation and has a history of glorious achievement as the standard-bearer in amateur affairs.

Inquiries regarding membership are solicited. A bona fide interest in amateur radio is the only essential qualification; ownership of a transmitting station and knowledge of the code are not prerequisite.

Membership Application Blank ➔

Application for Membership

AMERICAN RADIO RELAY LEAGUE

Administrative Headquarters: West Hartford 7, Conn., U. S. A.



..... 194

AMERICAN RADIO RELAY LEAGUE,
West Hartford, Conn., U. S. A.

Being genuinely interested in Amateur Radio, I hereby apply for membership in the American Radio Relay League, and enclose \$2.50 (\$3.00 in foreign countries) in payment of one year's dues,* \$1.25 of which is for a subscription to QST for the same period. Please begin my subscription with the..... issue.

The call of my station is

The class of my operator's license is

I belong to the following radio societies

.....

Send my Certificate of Membership or Membership Card (indicate which) to the address below:

Name:

.....

.....

A bona fide interest in amateur radio is the only essential requirement but full voting membership is granted only to licensed radio amateurs of the United States and Canada. Therefore, if you have a license, please be sure to indicate it above.

[*The dues are \$2.50 per year in the United States and Possessions. All other countries \$3.00 per year.]

To Manufacturers of Products Used in Short-Wave Radio Communication

THE RADIO AMATEUR'S HANDBOOK is the world's standard reference on the technique of high-frequency radio communication. Now in its twenty-third annual edition, it is used universally by radio engineers as well as the thousands of amateurs and experimenters for whom it is published. Year after year, each succeeding edition has sold more widely than its predecessor, until the Handbook now has a world-wide annual distribution in excess of two hundred thousand copies of its English and Spanish editions. To manufacturers whose integrity is established and whose products meet the approval of the American Radio Relay League technical staff, we offer use of space in the Handbook's Catalog-Advertising Section. Testimony to its effectiveness is the large volume of advertising which the Handbook carries each year. It is truly the standard guide for amateur, commercial and government buyers of short-wave radio equipment. Particularly valuable as a medium through which complete data on products can be made easily available to the whole radio engineering and experimenting field, it offers a surprisingly inexpensive method of producing and distributing a creditable catalog, accomplishes its production in the easiest possible manner, and provides adequate distribution and permanent availability impossible to attain by any other means. We solicit inquiries from qualified manufacturers who wish full data for their examination when catalog and advertising plans are under consideration.


ADVERTISING DEPARTMENT . . .

American Radio Relay League

WEST HARTFORD 7, CONNECTICUT



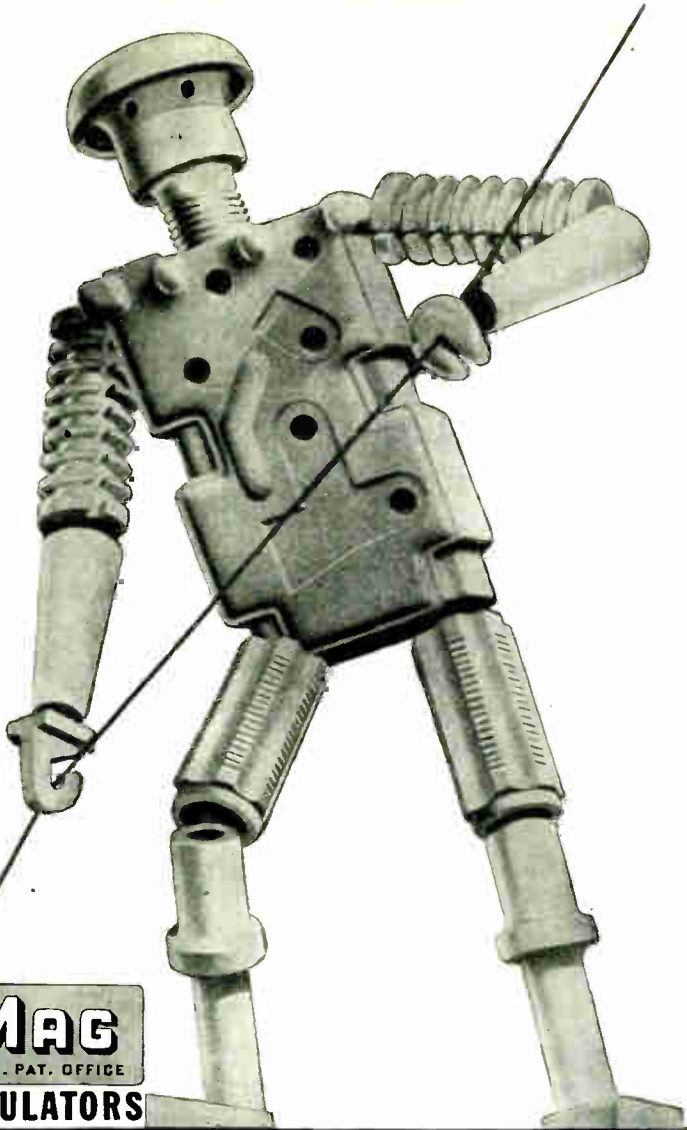*ALCO has been awarded
for the fifth time the
Army-Navy "E" Award
for continued excellence
in quantity and quality
of essential war production.*



ALSiMAG
TRADE MARK REG. U. S. PAT. OFFICE
CERAMIC INSULATORS

Side by side with the brilliant achievements in radio communications has been the development of ALSIMAG Steatite bodies of extremely low dielectric loss, together with high mechanical strength and rigidity—assuring constancy under any operation condition.

AMERICAN LAVA CORPORATION
CHATTANOOGA 5, TENNESSEE

43RD YEAR OF CERAMIC LEADERSHIP

THE AMATEUR'S BOOKSHELF

A balanced selection of good technical books, additional to the ARRL publications, should be on every amateur's bookshelf. We have arranged, for the convenience of our readers, to handle through the ARRL Book Department those works which we believe to be most useful. Make your selection from the following, add to it from time to time, and acquire the habit of study for improvement. *Prices quoted include postage.* Please remit with order.

Theory and Principles

BASIC RADIO PRINCIPLES, by M. G. Sufferin. Elementary radio principles, circuits and components described in simple practical language, without mathematics. 271 pages, illustrated. 1943.....\$3.00

BASIC ELECTRICITY FOR COMMUNICATIONS, by W. H. Timbie. A practical treatment of the electrical principles which underlie communications, circuits and practice. 603 pages, illustrated. 1943.....\$3.50

PRINCIPLES OF RADIO, by Keith Henney. A medium-level text covering both electrical and radio fundamentals, particularly written for home study. 549 pages, illustrated. 4th edition, 1942.....\$3.50

BASIC RADIO, by J. Barton Haag. A complete treatment of the circuits used in radio, television and electronics apparatus, including up-to-date applications. 380 pages, illustrated. 1942.....\$3.25

FUNDAMENTALS OF RADIO COMMUNICATIONS, by A. R. Frey. A more advanced treatment requiring previous background. Authoritative, clearly written, well organized. 393 pages, illustrated. 1944.....\$4.00

INTRODUCTION TO MICROWAVES, by Simon Rama. A non-mathematical description of concepts necessary to an understanding of microwave phenomena. 138 pages, illustrated. 1945.....\$1.75

Engineering and Reference

RADIO ENGINEERS' HANDBOOK, by F. E. Terman. Broad scope and detailed treatment make this book serve both as text and reference handbook. 1019 pages, illustrated. 1943.....\$6.00

RADIO ENGINEERING HANDBOOK, Keith Henney, Editor. An authoritative handbook for engineers, with technical data on all fields and aspects of radio, contributed by 23 specialists. 945 pages, illustrated. 1941.....\$5.00

ULTRA-HIGH-FREQUENCY RADIO ENGINEERING, by W. I. Emery. Written for engineering students, this book provides an excellent transition treatment for amateurs. 295 pages, illustrated. 1944.....\$3.25

COMMUNICATION CIRCUITS, by Ware and Reed. From low-frequency transmission line and network theory, this volume leads the student into wave guides and advanced u.h.f. techniques. 330 pages, illustrated. 2nd edition, 1944.....\$3.50

PRINCIPLES OF ELECTRON TUBES, by H. J. Reich. A condensed but complete treatment of the theory, characteristics and applications of electron tubes. 398 pages. 1941...\$3.50

COMMUNICATION ENGINEERING, by W. I. Everitt. Complete treatment of network theory, including mathematical analysis of radio circuits and tube operation. 727 pages, 411 illustrations. 1937.....\$5.00

HYPER AND ULTRA-HIGH FREQUENCY ENGINEERING, by Sarbacher and Edson. A digest of published literature covering all phases of technique from 30 Mc. to 10,000 Mc. 644 pages, illustrated. 1943....\$5.50

FIELDS AND WAVES IN MODERN RADIO, by Rama and Whinney. An extensive theoretical treatment of field and wave theory, requiring a knowledge of engineering mathematics. Revealing and impartant. 502 pages, illustrated. 1944.....\$5.00

RADIO ENGINEERING, by F. E. Terman. A comprehensive treatment covering all phases of radio communication. An all-around book for students and engineers. 813 pages, illustrated. 2nd edition, 1937.....\$5.50

FREQUENCY MODULATION, by August Hund. An advanced engineering text on f.m., presenting both theory and practice. 375 pages, illustrated. 1942.....\$4.00

PRINCIPLES OF TELEVISION ENGINEERING, by D. G. Fink. Information on the fundamental processes of television technique, with design data and descriptions of modern equipment. 541 pages, illustrated. 1940.....\$5.00

MICROWAVE TRANSMISSION, by J. C. Slater. A comprehensive treatment of principles and techniques employed in the region between 300 and 3000 Mc. For the advanced student or engineer. 309 pages, illustrated. 1942.....\$3.50

Experiments and Measurements

MEASUREMENTS IN RADIO ENGINEERING, by F. E. Terman. A comprehensive engineering treatment of the measurement problems encountered in engineering practice, with emphasis on basic principles. 400 pages, illustrated. 1935.....\$4.00

RADIO FREQUENCY ELECTRICAL MEASUREMENTS, by H. A. Brown. A laboratory course in r.f. measurements for communications students. Contains practical information on methods. 384 pages, illustrated. Second edition, 1938.....\$4.00

EXPERIMENTS IN ELECTRONICS AND COMMUNICATION ENGINEERING, by Schulz and Anderson. A laboratory text describing 108 experiments covering all aspects of radio and electronic fields. 380 pages. 1943.....\$3.00

Commercial Equipment and Operating

HOW TO PASS RADIO LICENSE EXAMINATIONS, by C. E. Drew. Gives answers and explanations for the paraphrased questions in the FCC study guide, covering all six elements of the commercial examination. 320 pages, illustrated. 2nd edition, 1944...\$3.00

PRACTICAL RADIO COMMUNICATION, by Nilsen and Harnung. Covers basic principles and technical requirements in the commercial fields—broadcasting, police, aviation and marine communication. 927 pages, illustrated. 2nd edition, 1943.....\$6.00

THE RADIO MANUAL, by G. E. Sterling. An excellent practical handbook, invaluable to the commercial and broadcast operator and engineer. Covers principles, methods and apparatus of all phases of radio. 666 pages, illustrated. 2nd edition, 1938.....\$6.00

Miscellaneous

MATHEMATICS ESSENTIAL TO ELECTRICITY AND RADIO, by Caake and Orleans. Provides the essentials of algebra, geometry and trigonometry needed to solve everyday

problems, with practical examples. 418 pages, illustrated. 1943.....\$3.00

PRINCIPLES AND PRACTICE OF RADIO SERVICING, by H. J. Hicks. Receiver circuit

fundamentals and their application to general service practice. Covers modern testing equipment and business principles in servicing. 391 pages, illustrated. 1943.....\$3.50

THE AMERICAN RADIO RELAY LEAGUE, INC. • WEST HARTFORD 7, CONNECTICUT

Microphones Engineered by

Electro-Voice

Answer Everyday Sound Problems



Maximum Intelligibility Under Extreme Noise

Hand-Held, close-talking single button carbon *DIFFERENTIAL microphone for all speech transmission in any noisy, windy, wet or extremely hot or cold locations. Cancels out background noise. Articulation is at least 97% under quiet conditions, and 88% under a 115 db noise field.

Model 205-S. List Price \$25

*Patent No. 2,350,010



Higher Articulation with Less Fatigue

Moving coil, hand-held Dynamic microphone for high fidelity speech transmission. Uniform response, free from peaks, in the useful frequencies gives higher articulation, provides more usable power level, and is less fatiguing to the listener. For outdoor or indoor use.

Model 600-D. Dynamic. List. \$27.50

Model 210-S. Carbon. List. \$17.50



Poly-Directional with Adjustable Polar Pattern

The versatile high fidelity Cardak is readily adjustable to reduce any combination of reflected sound. Cuts reverberation or random noise pick-up... minimizes acoustic feedback. For broadcasting, recording, public address, communications.

Model 725—Cardak I. List. \$55

Model 730—Cardak II. List. \$75



General-Purpose Dynamic for Voice and Music

Widely used because of its dependable all-around performance. Excellent frequency response for both indoor and outdoor speech and music pick-up. Rugged, small size, light weight. High output. Suitable for public address, dispatching, paging, recording and remote broadcast.

Model 630-C. List Price \$30




Velocity High Fidelity Bi-Directional Sound Pick-Up

Wide, flat frequency response, bi-directional polar pattern, high fidelity characteristics, wide-angle front pick-up, and pick-up range make it ideal for solo, orchestra, or chorus, for single speaker or groups. For indoor P.A., broadcasting, recording.

Model V-1-C. List Price \$30

Model V-2. List Price \$37.50

Model V-3. List Price \$50

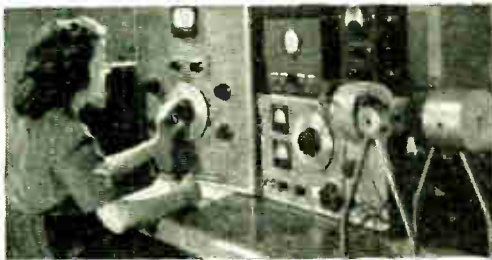

Corner of E-V "Lab"

One of our Quality-Control units used in testing close-talking microphones. Harmonic distortion, frequency response, positional response (for carbons) level, etc., are carefully analyzed. Calibration is effected by Bell Laboratory standards and our own reciprocity checks.



SEND FOR COMPLETE CATALOG

Gives valuable data on Electro-Voice Microphones for communications, public address, broadcasting and recording. Includes helpful Reference Level Conversion Chart.

Authorized Distributors Everywhere



No finer choice than

Electro-Voice

M I C R O P H O N E S

GUARANTEE

The E-V models shown here are guaranteed forever against defects in workmanship and material.


ELECTRO-VOICE, INC., 1239 South Bend Ave., South Bend 24, Indiana * Export Division: 13 East 40th St., New York 16, N. Y., U. S. A.—Cables: Arlab

POWERSTAT FOR R9 PERFORMANCE

EVERY
"COMPLETE"
TRANSMITTER SHOULD
HAVE A POWERSTAT
VARIABLE VOLTAGE TRANSFORMER



TYPE 20

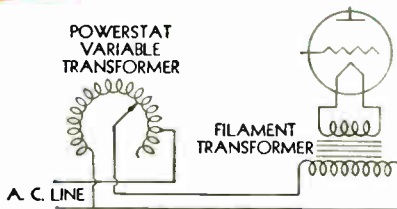

FILAMENT VOLTAGE CONTROL



TYPE 116

Peak operating efficiency of your transmitter can only be obtained by maximum performance of its power supply. The POWERSTAT is a Variable Voltage Transformer designed to deliver any output voltage from zero to line voltage or above without circuit interruption.

This POWERSTAT in the primary of your plate, grid, or filament power supply will enable you to...Tune up the rig at low powers eliminating danger of tank condenser arc overs, tube overloads and meter burnouts...QSO at any power level up to maximum...Smoothly adjust bias voltage for maximum efficiency without shutting down...Set filament voltage to rated value protecting emission characteristics with resulting increase in tube life...Boost your line voltage if low or reduce it if too high.

POWERSTAT Variable Transformer type 20 (for panel mounting) rated:
Input: 115 volts, 50/60 cycles

Output: 0 - 135 volts, 3.0 amperes max.

POWERSTAT Variable Transformer type 116U (for panel mounting) rated:

Input: 115 volts, 50/60 cycles

Output: 0 - 135 volts, 7.5 amperes max.

POWERSTAT Variable Transformer type 116

This unit is electrically the same as type 116U but equipped with cord and plug, on-off switch, output receptacle and enclosure. Ideal for experimental use in the shack.

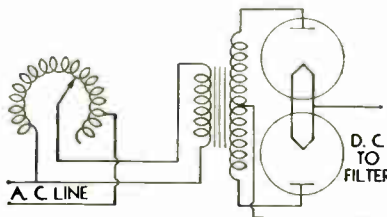


PLATE VOLTAGE CONTROL



TYPE 116U

Send for Bulletin LA

SUPERIOR ELECTRIC COMPANY
12 LAUREL STREET · BRISTOL · CONNECTICUT

STOCKED BY LEADING DISTRIBUTORS IN THE UNITED STATES AND CANADA

The WESTLINE CRYSTAL



ACTUAL SIZE

*P*erfected through four years of war production, the Westline crystal is as fine as modern technology can produce.

Every blank is precisely orientated by X-ray and polaroid, assuring a low drift crystal. Drift is less than 1 cycle/mc/°F. Each is dimensioned to produce highest activity. Each is finished to exact frequency and specially treated to prevent its changing frequency or activity with use.

Amateur crystals are available in the 40, 80, and 160 meter bands or to multiply into any higher frequency amateur band. The price is \$3.50 complete with holder,* supplied within 1 kc of frequency you specify with frequency stamped to nearest 100 cycles. Holder plugs into either 8 prong or 5 prong socket. Holder dimensions are $1\frac{1}{8}''$ x $13/16''$ x $7/16''$. Each crystal carries an unconditional money back guarantee. Send your orders for whatever crystals you want, specifying frequency. Shipment will be made the day order is received — shipment C.O.D. if you wish.

We can promptly supply commercial and special crystals of any type in any quantities. Tell us what you want — ask us to quote prices.

Bob Henry offers his record of seventeen years service to amateur radio as your guarantee of 100% satisfaction.


Send your orders and inquiries to Henry Radio, Butler, Missouri, or to Henry Radio, Los Angeles 25, California.

*Price subject to change without notice.

HENRY RADIO

BUTLER, MO., and LOS ANGELES 25, CALIF.

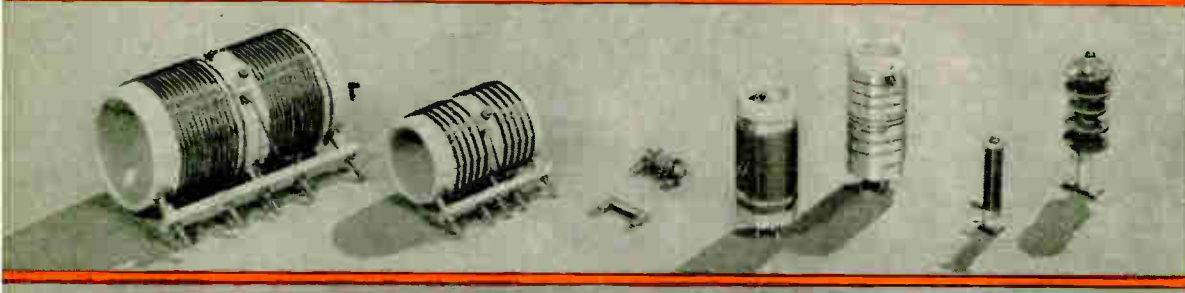“WORLD’S LARGEST DISTRIBUTOR OF SHORT WAVE RECEIVERS”



BROADCAST EQUIPMENT
 Illustrated at left is a JOHNSON Directional Antenna Phasing Unit, an Antenna Coupling Unit and a Variable Pressure Condenser.

These are representative of the popular JOHNSON products widely used by Commercial Broadcast stations.

Write if you need specific information

JOHNSON variable condensers are rigidly constructed and engineered to meet exacting requirements of amateur, commercial broadcast and industrial applications. They are the choice of amateurs who demand the highest quality and latest in condenser design.

In JOHNSON condensers there are many superior features, which help assure top performance of equipment in which they are employed.

There is a JOHNSON condenser for every stage of the amateur transmitter from oscillator through the final amplifier.

JOHNSON tube sockets have been known for more than twenty years as a top line. New sockets are being added continually to the JOHNSON line, keeping it always up to date.

JOHNSON's superior mechanical and electrical design never fails to meet the rigid requirements of present day radio-electronic circuits and equipment.

The complete line of JOHNSON sockets meet every amateur tube socket requirement. JOHNSON standard and "special" sockets are also supplied for a wide variety of commercial broadcast and industrial applications.

JOHNSON insulators are designed to obtain great mechanical strength and high breakdown voltages.

Materials used in the manufacture of JOHNSON insulators are selected after laboratory tests prove conclusively that they meet all of JOHNSON's rigid specifications.

The JOHNSON line includes stand-off cone, thru-panel, antennas, feeder and strain insulators. There's a JOHNSON insulator for every amateur need and you will be more than satisfied with the performance of JOHNSON insulators.

JOHNSON inductors and chokes are available in popular standard types for amateur radio requirements and special types are available to meet any broadcast or industrial application.

The famous JOHNSON rotating coil and tube socket, "HI Q", inductors are designed for optimum LC ratios on all bands. A special highly glazed low-loss electrical porcelain is used for the coil forms, which are ribbed to assure minimum contact between the wire and insulating form.

JOHNSON RF chokes are uniformly flat in response and are equally effective over the entire range for which they are designed.

JOHNSON Hardware Items are manufactured from high grade materials and quality workmanship.

The JOHNSON line includes the following items: couplings, tube caps, plugs and jacks, inductor clips, soldering terminals, tube locking clamps, panel bearing, flexible shafts, fuse clips, handle indicators, cable connectors, pilot and dial lights.

JOHNSON parts can be obtained from radio-electronic parts Jobbers, or write directly for further information about JOHNSON components and assemblies.

Send for the
latest JOHNSON
Catalog —
Dept. P

E. F. Johnson Co.
Waseca, Minn.

JOHNSON


a famous name in Radio



ORDER YOUR NEW Communications Receiver NOW from ALLIED *For Earliest Delivery*


**Available on Time-Payments
Trade-ins Accepted**

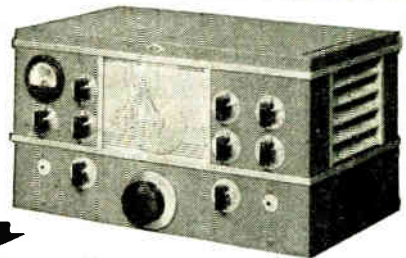BE ONE OF THE FIRST to own and enjoy one of these celebrated receivers. All models cover amateur, short-wave, and broadcast bands. War-proved features plus latest engineering developments. Allied is a leader in the distribution of communications receivers. Orders are filled in turn. Place your order now.




NATIONAL NC-2-40C

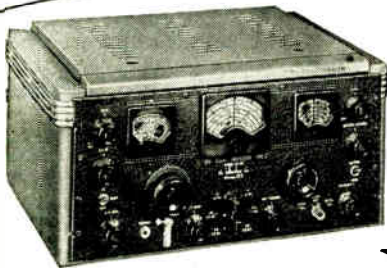490 kc. to 30 Mc. range in 6 bands. Accurate single dial control. Temperature compensation. Automatic voltage stabilization. Adjustable series-valve-noise limiter. Flexible crystal filter. Phonograph or high level microphone pick-up jack. Net..... **\$225**
Speaker in matching cabinet, net..... **\$15.00**



HALLCRAFTERS SX-28A

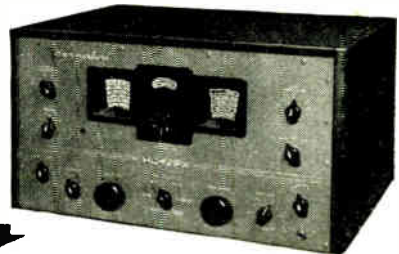550 kc. to 42 Mc. continuous in 6 bands. Accurately calibrated tuning dial. Separate calibrated bandspread dial. Two r.f. stages. Lamb type 3 stage adjustable noise limiter. 6 position i.f. and crystal filter selectivity switch. Oscillator temperature compensated. Net..... **\$223**
PM23 Speaker, net..... **\$15.00**



HAMMARLUND HQ-129X

Full range .54 to 31 Mc. accurately calibrated. 4 calibrated Ham bands and 1 arbitrary scale. Variable selectivity crystal filter. Low drift beat oscillator for code and locating stations. Antenna compensator. Voltage regulation. Compensated oscillator to reduce drift during warm-up. Automatic noise limiter. Net..... **\$129**
Speaker, net..... **\$10.50**

Other well-known receivers such as:

Hollicrofters SX-25	\$ 94.50
Hollicrofters S-20R	\$ 60.00
Hollicrofters S-39	\$110.00
Hollicrofters S-36A	\$115.00
Hollicrofters S-36A	\$ 15.00
PM23 Speaker	\$ 29.50
Echophone EC-1A	

Net, F.O.B. Chicago
(All prices subject to possible change)

ALLIED RADIO

Everything in Radio & Electronics
833 W. Jackson Blvd. • Chicago, Ill.

ALLIED RADIO CORP., L. M. Dezettel W95FW
833 W. Jackson Blvd., Dept. 10-46
Chicago 7, Illinois.

Date.....

- Please ship..... Model.....
- Enclosed \$..... Full Payment Part Payment
(Balance C.O.D.)
- Send literature on Receivers and Time Payment Plan.
- Send Allied Catalog of Radio Parts and Equipment.

Name.....

Address.....

City..... Zone..... State.....

A real choice of capacitor types

FOR STILL BETTER "RIGS"...



Unsealed case paper capacitors in widest range of containers, terminals, mountings, capacities, voltages, combinations. These capacitors give your "rig" that professional touch, while providing the super duper performance and life you want.



Dependable high-frequency jobs can best be handled with these heavy-duty Aerovox mica capacitors. Available in bakelite metal and ceramic cases, including the stack mounting units. Current rating data at various frequencies can prove invaluable in your engineering.



For ultra-high-frequency work, there are Aerovox low-loss capacitors such as Type 1360 here shown. Aluminum can. Mica disc-insulated terminal. Ratings up to 10,000 test volts effective. .00000 to .000125 mfd. There's also Type 1885 with ceramic-insulated terminal and cast aluminum case. Refined sulphur dielectric.



Aerovox molded-in bakelite mica capacitors are available in voltage ratings up to 10,000 test. Also in widest range of mountings, terminals, meter mounting brackets, with ceramic mounting washers, etc. Aerovox selection certainly is at its best in these molded-in bakelite mica capacitors.



To build on a solid foundation when you select Aerovox Type UC rectangular can oil capacitor. Although mass-produced at the lowest cost, these quality units are built for tough going and longest service. Choice of mountings. Voltage ratings from 600 to 7500 D.C.W. High voltage leak proof terminals.



They're available again those heavy-duty metal can Aerovox electrolytics. Widest selection of cans, mountings, terminals, capacities, voltages, combinations. Positively the outstanding choice today. And where compactness and lowest cost are prime requisites, there are the midjet-can "Dandees" and Type PBS cardboard-case units.



Do you want to make your own capacitor banks or combinations? Type UC unsealed paper sections are the answer. These compact paper sections are thoroughly impregnated and sealed in varnished-paper jackets, and have long pigtail leads. Mount them and case them as you wish. Here's the most paper capacitance for the money.



The war made Aerovox more space-conscious than ever. Type UC miniature oil-filled transmitting capacitor is typical. Single pillar terminal. Rounded case. Ring mounting 3000 v. There's also Type 2 with two pillar terminals and knob cover 2000 to 7500 v. D.C.W. Here's high-voltage insurance in minimum bulk and at popular prices.

● The Aerovox line offers you a greater selection of capacitor types than ever before. Yes, capacitors that were special before—those extra-heavy-duty types you envied in commercial X-mitting "rigs"—and definitely too high-priced for your pocketbook—are now available to you and at within-reach prices.

The latest Aerovox catalog contains many new

as well as earlier types. And for your extra-special requirements, your Aerovox jobber can tell you what's available beyond the listings in the General catalog.

Consult your Aerovox jobber. He can tell you what types to use for that "rig." Ask for our latest catalog. Also ask for a free subscription to the Aerovox Research Worker. Or write us direct.

Buy branded merchandise! And look for the yellow label!



FOR RADIO-ELECTRONIC AND INDUSTRIAL APPLICATIONS

AEROVOX CORPORATION, NEW BEDFORD, MASS., U.S.A.

SALES OFFICES IN ALL PRINCIPAL CITIES • Export: 13 E. 40th St., New York 16 N.Y.

Cable: "AERLAB" • In Canada: AEROVOX CANADA LTD., HAMILTON, ONT.

Now it can be **SOLD...**

The Plytube 50 ft. "HAM-MAST"

The Plytube HAM-MAST is the answer to the need of amateurs and experimenters for a strong, light-weight compact mast that can be used for portable or permanent installations. It is designed for U.H.F. or V.H.F. antennas and with slight modification can be adapted for F.M. and Television reception.

This is the same type high quality mast that was used during the war, by the thousands, in Army, Navy and Coast Guard installations. Complete with erection kit for only \$98.50.

The mast is made up of four sections which telescope into a bundle 14' 3" long. Each mast is supplied with two sets of guy wires, with four anchors, a base plate with four spikes, and an erection kit consisting of a boom, boom shoe, top collar, rope vangs, block and tackle and boom anchor.

SPEEDY ERECTION — Two men can erect the Plytube "Ham-Mast" in 15 minutes.

WEATHER PROOF — Withstands wind velocities of 100 m.p.h., extreme temperatures and weather conditions.

PORTABLE — Demountable, compact and light weight (mast 29 lbs. — fittings 41 lbs. — erection kit 15 lbs.)

LOW MAINTENANCE COST — No painting required.

NON-METALLIC — Made of exterior grade plywood — no interference.


Complete with
erection kit
F. O. B.
LAWRENCE
MASS.

\$98.50

Prices subject to O.P.A. approval

Top:
Mast in place — easily and
securely erected.

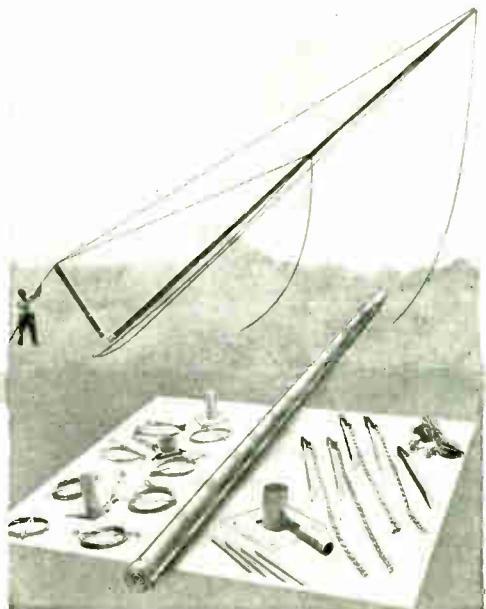Bottom:
Assembly of Nested Mast and
fittings ready for erection



© 1945 PLYMOLD CORPORATION, Lawrence, Mass.

PLYMOLD CORP.

Manufacturers of Plytube

Lawrence • Mass.


146

Stay on the air with

RAYTHEON Tubes

Amateurs like to work their rigs hard—overload power tubes to get more output. Raytheon tubes stand up under such conditions—because they're built to operate well beyond their minimum performance standards, as described by ratings or Army-Navy specifications.

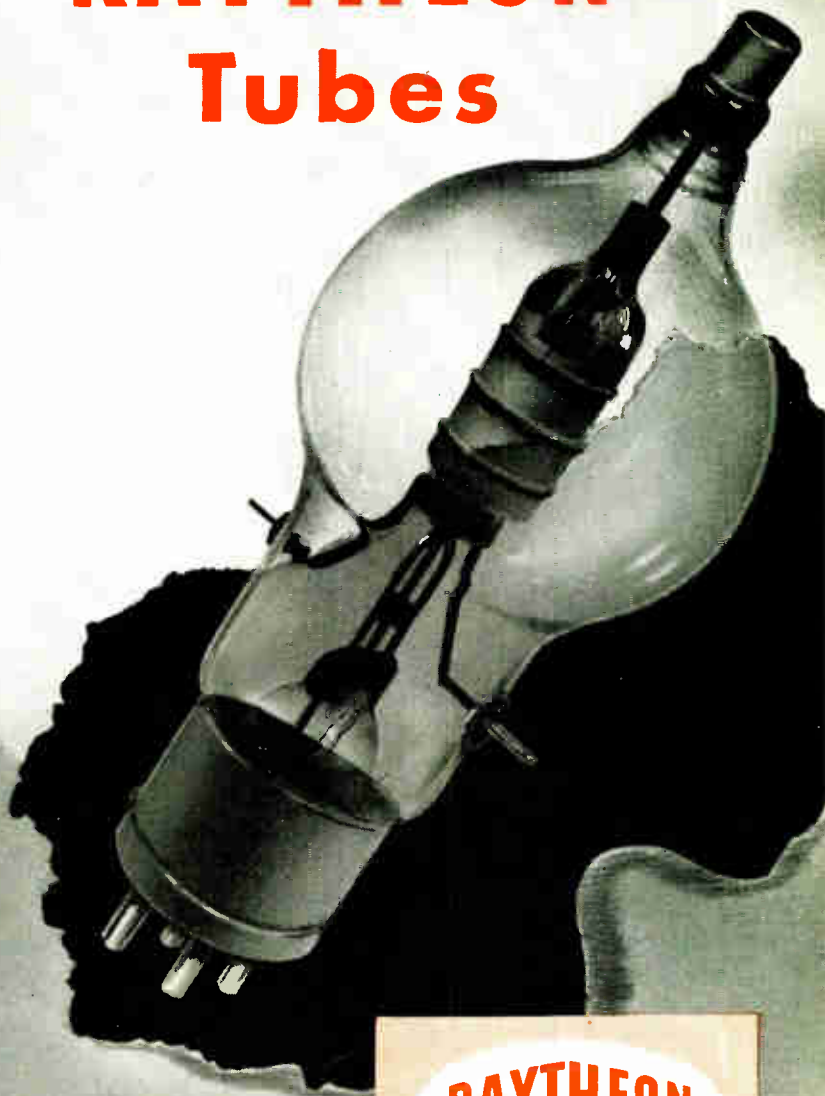Remember the first power pentodes? They were built by Raytheon. And now Raytheon is ready to go back to work for amateurs . . . providing you with tubes of new design, built to keep you on the air.



RAYTHEON

MANUFACTURING COMPANY
WALTHAM 54, MASS.

AMATEUR RADIO DIVISION

Excellence in Electronics

Are YOU ready to go on the air?


WRL TRANSMITTER KITS

Leo has the transmitter kit you want at the price you want to pay . . . 15, 35, 70, 150 watts. Also units custom built to your specifications.

QUALITY RECEIVERS

The best in receivers from all manufacturers, at OPA prices . . . ready for quick delivery to you. Use your present receiver for trade-in or as a down payment on a new set.

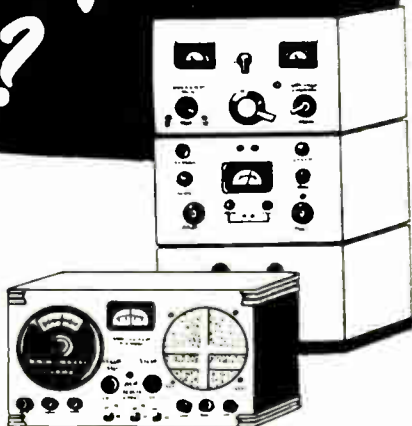Liberal trade-in allowance. Convenient terms — always the lowest in the country.



Exclusive at Leo's! . . .

Our latest Flyer . . . packed with the latest in radio parts . . . the kind you've been looking for **FREE**

Handy Tube-Base Calculator that tells you in a jiffy tube characteristics which enable you to substitute available tubes for those you can't get **25c**

Giant Radio Reference Map with time and amateur zones, standard and short wave stations, and other valuable information. Printed in colors. Size 3½ x 4½ feet **Only 15c**



Everything FOR THE HAM

Today, as always, our stock of parts, receivers, transmitters, and general electronic equipment is the most complete you'll find. Amateurs and radiomen the nation over appreciate our quick, personalized service. Write Leo, W9GFQ, today and be the FIRST with the LATEST. We invite inquiries for special equipment of all kinds.

We specialize in Hallicrafters equipment. Available now for immediate shipment.

For Quick Service On Everything In Radio

TRY LEO!




Address Leo, W9GFQ, Dept. H-46

WHOLESALE RADIO LABORATORIES

744 West Broadway, Council Bluffs, Iowa

Stupakoff Ceramic Insulators

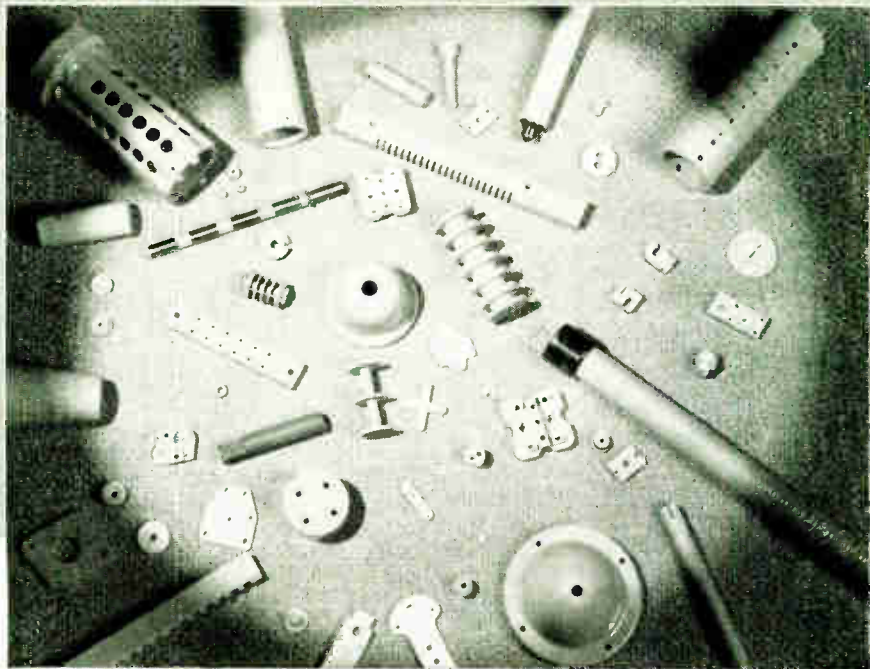FOR ALL FREQUENCIES—ALL VOLTAGES—ALL TEMPERATURES



Stupakoff Hermetic Seals



KOVAR* The ideal alloy for sealing to glass.

•
GLASS TO METAL
HERMETIC SEALS

TRADE MARK 337962 REGISTERED IN U. S. PATENT OFFICE

STUPAKOFF CERAMIC AND MANUFACTURING CO., LATROBE, PA.

World Radio History

Two big NEWARK stores well stocked to serve your needs and staffed by people who know and can help solve your problems.

LATEST MODELS WELL-KNOWN RECEIVERS

LATEST MODEL RECEIVERS NOW AVAILABLE HAMMARLUND HALLICRAFTERS



- HQ-129X (with tubes) \$129.00
- ASPC-210X 318.00
- ASP-210SX 318.00

*Available for rack mounting
at same prices*



- SX-28A Super Skyrider with crystal, less speaker \$223.00
- S-20R Sky Champion with built-in speaker 60.00
- S-22R Skyrider Marine with built-in speaker 74.50
- SX-25 Super Defiant with crystal, less speaker 94.50
- S-39 Sky Ranger portable, AC DC and battery 110.00
- SX-36 FM AM receiver 415.00
- S-37 V.H.F. FM AM receiver 591.75
- PM-23 10" PM speaker in cabinet for use with SX-25, SX-28A 15.00

NATIONAL



NC-2-40C and speaker \$240.00

RME



RME-45 and speaker \$166.00

GET YOUR NAME ON OUR MAILING LIST

Be first to get announcements of merchandise available, special bargains, etc., etc. Send name and address on post card. State whether amateur, engineer school, industrial or serviceman. Address orders and inquiries to Dept. H at NEWARK store nearest you.

**ALL PRICES SUBJECT TO
CHANGE WITHOUT NOTICE**

NEW YORK
Newark ELECTRIC Company
CHICAGO

115-117 W. 45th St.
NEW YORK 19
BRYant 9-4735
(Adolph Gross)

"Dependable Service
Is the Foundation
of Our Business"

323 W. Madison St.
CHICAGO 6
DEArborn 0083
(Sam Poncher)

HAMS... here are all the things you've been waiting for in NEWARK'S two big stores. Order from the store nearest you for fast service.

SHOP NEWARK FOR BIG BARGAINS

THORDARSON TRANSFORMERS

(Power Transformers and Chokes)

T-45556 or T-92R21 leads out of side. 778 v. C.T. at 200 MA. 115 v. 60 Cycle 6.3 v. C.T. at 5A. 5 v. at 30 amp. 9 lbs..... \$5.29

T-13C30 8H. 150 MA. 200 ohm 1600 v. Insulation 2 1/4 lbs..... 1.41

T-4557 or T-74C29 leads out of side. 15H. 150 MA. 200 ohm 2000 v. Insulation 5 1/4 lbs..... 2.82

Western Electric Micro Ammeters

Bakelite case fits 3 3/4" hole. Radium dial 150-0-150. Can be used with 0-200 micro and amp scale listed below. Excellent as a 5,000 ohm-pervolt meter or null, sound level and galvanometer indicator. Instructions included.



No priority required... \$7.50
0-200 paper scale for above..... \$1.5

GENERAL ELECTRIC METERS

0-500 D.C. MA. 2" round Bakelite case..... \$3.50
0-8 RF ammeter, 2" round Bakelite case..... 4.00

The famous Newark bargain oil-filled, oil-impregnated

FILTER CONDENSERS

FULLY GUARANTEED AT RATED VOLTAGES



Capacity	Working Voltage	Height	Width	Depth	Wt.	Price
1 mfd.	1500 V. D.C.	2 3/8	1 1/4	1	4 oz.	\$.79
5 mfd.	2000 V. D.C.	4	3 1/4	1 1/4	1 lb.	
8 mfd.	2000 V. D.C.	4 1/2	3 1/4	2 1/2	1 oz.	2.15
.25 mfd.	2000 V. D.C.	3 1/4	1 3/4	1	2 1/2 lb.	2.75
10 mfd.	Special porcelain Insulators 3000 V. D.C.	4 7/8	3 3/4	3 1/4	6 oz.	.69
15 mfd.	3000 V. D.C.	4 3/4	4 3/8	3 7/8	3 lb.	4.75
6 mfd.	3000 V. D.C.	6 3/4	6 1/2	3	8 oz.	5.25
8 mfd.	3000 V. D.C.	7 3/8	6 1/2	3 1/2	5 lb.	3.25
2 mfd. and 4 mfd.	600 V. metal can	4 7/8	2 1/2	1 1/4	with mounting feet width included mounting feet 7 lb. 4 oz.	3.95
					1 1/2 oz.	.80

GET YOUR NAME ON OUR MAILING LIST

Be first to get announcements of merchandise available, special bargains, etc., etc. Send name and address on post card. State whether amateur, engineer, school, industrial or serviceman. Address orders and inquiries to Dept. H at NEWARK store nearest you.

ALL PRICES SUBJECT TO
CHANGE WITHOUT NOTICE

NEW YORK
Newark ELECTRIC Company
CHICAGO

115-117 W. 45th St.
NEW YORK 19
BRyant 9-4735
(Adolph Gross)

"Dependable Service
Is the Foundation
of Our Business"

323 W. Madison St.
CHICAGO 6
OEArborn 0083
(Sam Poncher)

JONES

ELECTRICAL CONNECTING DEVICES

PLUGS · SOCKETS · TERMINAL STRIPS

FOR EVERY ELECTRONIC NEED



P-306-FHT



S-306-AB

300 SERIES PLUGS AND SOCKETS

A high quality line of small Plugs and Sockets adaptable to a thousand uses. Made in 2 to 33 contacts and designed for 45 volts at 5 amperes. All Plugs and Sockets are Polarized. Knife switch socket contacts are of Phosphor Bronze, cadmium plated. Bar type plug contacts are of Brass, cadmium plated. Body of molded Bakelite.



P-2406-FHT

2400 SERIES PLUGS AND SOCKETS

Fulfill practically every requirement in Public Address, Radio and kindred fields. Designed for highest electrical and mechanical efficiency. Made in 2, 4, 6, 8, 10 and 12 contacts. Designed for 110 volts at 10 amperes. All Plugs and Sockets are Polarized. Knife switch socket contacts are of Phosphor Bronze, cadmium plated. Bar type plug contacts are Hard Brass, cadmium plated. Body of molded Bakelite. Steel Caps have baked black crackle enamel finish.



S-2406-SB

500 SERIES PLUGS AND SOCKETS

(NOT ILLUSTRATED)

Heavy Duty Series designed for 5,000 volts at 25 amperes. Made in 2 to 12 contacts. Polarized. Molded Bakelite body. Parkerized Steel Brackets and Caps. Send for No. 500 catalog now.



P-101-1/4"



S-101

SHIELDED PLUGS AND SOCKETS

Low loss plugs and sockets suitable for high frequency circuits. Ideal for antenna connections, photo-cell work, microphone connections, etc. Can be furnished with $\frac{1}{4}$ ", $.290$ ", $\frac{5}{16}$ ", $\frac{3}{8}$ " or $\frac{1}{2}$ " ferrule for cable entrance. Knurled nut securely fastens units together. All metal parts are of brass, suitably plated to meet Navy specifications. No. 101 Series.



Barrier Terminal Strip

TERMINAL STRIPS

Barrier type Terminal Strips as illustrated are most popular and not only improve electrical connections, but add to the appearance. Made in 6 series to cover every requirement. Hundreds of standard types of Terminal Strips available. Also fuse mounts.

Carried in stock by all leading jobbers. Send today for catalog No. 14 showing complete line of products.

HOWARD B. JONES COMPANY

2460 W. GEORGE ST. CHICAGO 18

DX RADIO PRODUCTS ¹⁵³


do a Better Job!



DX RADIO PRODUCTS CO.

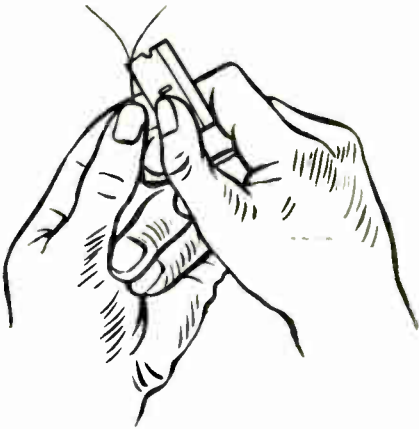GENERAL OFFICES 1200 N. CLAREMONT AVE., CHICAGO 22, ILL., U.S.A.





SPLIT-HAIR ACCURACY IS IN DEMAND TODAY

What little "rule-of-thumb" thinking there was in the electronic and radio fields five years ago has been swept away by war's scientific demands.

Accurate test and measurement equipment is a vitally necessary part of the future, not only of commercial and industrial electronic applications, but in every "ham" radio as well.

Brief, technical specifications of most *-hp-* instruments are shown on these pages.

Write for your copy of the *-hp-* catalog which gives much valuable information about electronic AF measurements and the instruments with which to make them. No obligation.



945

HEWLETT-PACKARD COMPANY


BOX 945 • STATION A • PALO ALTO, CALIFORNIA

INSTRUMENT	FUNCTION	FREQUENCY	CALIBRATION
200-A	Resistance-Tuned Audio Oscillator	35 cps to 35 kc	Dial Scale—35-350 cps Calibration Points—48 Ranges—3 (1.10, 100 times dial calibration)
200-B	Resistance-Tuned Audio Oscillator	20 cps to 20 kc	Dial Scale—20-200 cps Calibration Points—41 Ranges—3 (1.10, 100 times dial calibration)
200-C	Resistance-Tuned Audio Oscillator	20 cps to 200 kc	Dial Scale—20-200 cps Calibration Points—41 Ranges—4 (1.10, 100, 1000 times dial calibration)
200-D	Resistance-Tuned Audio Oscillator	7 cps to 70 kc	Dial Scale—7-70 cps Calibration Points—78 Ranges—4 (1.10, 100, 1000 times dial calibration)
202-D	Resistance-Tuned Audio Oscillator	2 cps to 70 kc	Dial Scale—7-70 cps Calibration Points—78 Ranges—4 (1.10, 100, 1000 times dial calibration) Dial Scale A—2-50 cps Calibration Points—
200-I	Resistance-Tuned Spread Scale Audio Oscillator	6 cps to 6 kc	Dial Scale A—5-20 cps Calibration Points—78 Dial Scale B—20-60 cps Calibration Points—78 Ranges—3 (1.10, 100 times dial calibration)
206-A	Resistance-Tuned Audio Signal Generator	20 cps to 20 kc	Dial Scale—20-200 cps Calibration Points—80 Ranges—3 (1.10, 100 times dial calibration)
206-AG	Resistance-Tuned Audio Signal Generator with 49 db Voltmeter	20 cps to 20 kc	Dial Scale—20-200 cps Calibration Points—78 Ranges—3 (1.10, 100 times dial calibration)
206-AH	Resistance-Tuned Signal Generator	1 kc to 100 kc	Dial Scale—1-10 kc Calibration Points—130 Ranges—2 (1.10 times dial calibration)

INSTRUMENT	FUNCTION	FREQUENCY	ACCURACY
100-A	Low Frequency Standard	Output—100 kc, 10 kc, 1 kc, 100 cps	±0.01% over room temperature variation of 35° C
100-B	Low Frequency Standard	Output—100 kc, 10 kc, 1 kc, 100 cps	±0.001% from ±10° C to ±50° C
210-A	Square Wave Generator	Input—20 cps to 100 kc	square within ±1% from 20 cps to 10 kc
300-A	Harmonic Wave Analyzer	Measurement Range—30 cps to 16 kc	Frequency—±3% Voltage overall—±5%
320-A	Distortion Analyzer	Measures at—400 cps and 5 kc	Less than ±5% (at distortions of 30% or more)
320-B	Distortion Analyzer	Measures at—50 cps, 100 cps, 400 cps, 1 kc, 5 kc, and 7.5 kc	Less than ±5% (at distortions of 30% or more)
325-B	Noise and Distortion Analyzer	Measures at—30 cps, 50 cps, 100 cps, 400 cps, 1 kc, 5 kc, 7.5 kc, 15 kc	Voltmeter Overall—±2% Distortion—Less than ±2% (at distortion of 30% or more)
350-A	Attenuator	Max. input—100 kc	Each Resistor—±0.5% Response—Accumulative Error at 100 kc approx 1 db in 50 db
400-A	Vacuum Tube Voltmeter	Measurement Range—10 cps to 1 mc	10 cps to 100 kc—±3% 100 kc to 1 mc—±5%
500-A	Electronic Frequency Meter	Measurement Range—5 cps to 50 kc in 10 ranges	±2% of full scale
505-A	Electronic Tachometer	An Electronic Frequency Meter and a Tachometer Assembly calibrated to measure speeds up to 3,000,000 RPM.	



400A—Vacuum Tube Voltmeter

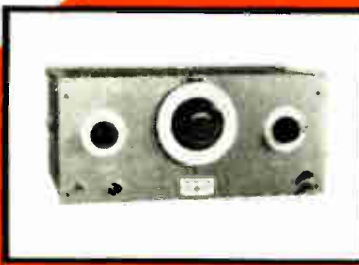

200C—Resistance-Tuned Audio Oscillator



500A—Electronic Frequency Meter

INSTRUMENTS FOR SPEED AND ACCURACY

FREQUENCY RESPONSE	STABILITY	ACCURACY OF CALIBRATION	POWER OUTPUT INTO RATED LOAD	LOAD IMPEDANCE	DISTORTION AT RATED OUTPUT	HUM LEVEL BELOW RATED OUTPUT	POWER REQUIREMENTS	SIZE
1 decibel, 20 cps to 15 kc	±2%	±2%	1 watt	600 ohms	less than 1%	60 db	115 volts 50-60 cyc 60 watts	Length, 16 ins. Height, 8 ins. Depth, 9 ins. Weight, 32 lbs.
1 decibel, 20 cps to 15 kc	±2%	±2%	1 watt	500 ohms	less than 1%	60 db	115 volts 50-60 cyc 60 watts	Length, 16 ins. Height, 8 ins. Depth, 9 ins. Weight, 32 lbs.
1 decibel, 20 cps to 150 kc	±2%	±2%	100 milliwatts	1000 ohms	less than 1% 20 cps to 20 kc	60 db	115 volts 50-60 cyc 60 watts	Length, 16 ins. Height, 8 ins. Depth, 9 ins. Weight, 32 lbs.
1 decibel, 7 cps to 70 kc	±2%	±2%	100 milliwatts	1000 ohms	less than 1% 10 cps to 20 kc	60 db	115 volts 50-60 cyc 60 watts	Length, 17 ins. Height, 8 1/2 ins. Depth, 11 ins. Weight, 32 lbs.
1 decibel, 7 cps to 70 kc 2 decibels, 2 cps to 7 cps	±2%	±2%	100 milliwatts	1000 ohms	less than 2% 7 cps to 70 kc	60 db	115 volts 50-60 cyc 60 watts	Length, 17 ins. Height, 8 1/2 ins. Depth, 11 ins. Weight, 32 lbs.
1 decibel, 6 cps to 6 kc	±2% or ±1% with Standardization	±2%	100 milliwatts	1000 ohms	less than 1% 10 cps to 6 kc	60 db	115 volts 50-60 cyc 60 watts	Length, 17 ins. Height, 8 1/2 ins. Depth, 11 ins. Weight, 28 lbs.
down 2.0 decibels at 20 cps down 1.0 decibel at 20 kc at full output	±2% or ±1% with Standardization	±2%	5 watts	50, 200, 500, 5000 ohms (all ct)	less than 1% 30 cps to 20 kc at rated output	60 db below output or 90 db below zero level, whichever is larger	115 volts 50-60 cyc 125 watts	Length, 21 1/2 ins. Height, 11 1/4 ins. Depth, 14 1/2 ins. Weight, 73 lbs.
down 2.0 decibels at 20 cps down 1.0 db at 20 kc at full output. Voltage within ±0.2 db of 400 cps ref. from 20 cps to 20 kc	±2% or ±1% with Standardization	±2%	5 watts	Generator: 50, 200, 500, 5000 ohms (all ct) Voltmeter: 5000 ohms input impedance	less than 1% 30 cps to 20 kc at rated output	60 db below output or 90 db below zero level, whichever is larger	115 volts 50-60 cyc 125 watts	Length, 21 1/2 ins. Height, 11 1/4 ins. Depth, 14 1/2 ins. Weight, 73 lbs.
from 10 kc ref. 1 kc to 100 kc at full output	±1% after 1/2 hour warm-up	±2%	5 watts	50, 200, 500, 5000 ohms (all ct)	less than 1% at 1 watt 3% at 5 watts	65 db below output or 90 db below zero level, whichever is larger	115 volts 50-60 cyc 125 watts	Length, 21 1/2 ins. Height, 11 1/4 ins. Depth, 14 1/2 ins. Weight, 63 lbs.
VOLTAGE		IMPEDANCE		MISCELLANEOUS CHARACTERISTICS			POWER REQUIREMENTS	SIZE
Output—5 volts into 1000 ohms		Load—Not less than 1000 ohms		Wave Shape—Sinusoidal— total distortion not more than 4% on open circuit			115 volts 50-60 cyc 100 watts	Length, 21 1/2 ins. Height, 11 1/4 ins. Depth, 14 1/2 ins. Weight, 63 lbs.
Output—5 volts into 1000 ohms		Load—not less than 1000 ohms		Wave Shape—Sinusoidal— total distortion not more than 4% on open circuit			115 volts 50-60 cyc 105 watts	Length, 21 1/2 ins. Height, 11 1/4 ins. Depth, 14 1/2 ins. Weight, 63 lbs.
Input—min. 2; max. 200 —60 v peak to peak on open circuit		Input—25,000 ohms Internal—Each side, 500 ohms to ground		Wave Shape—Square (1 microsecond to 90% of maximum) Attenuator—70 db in 5 db steps			115 volts 50-60 cyc 85 watts	Length, 16 ins. Height, 8 ins. Depth, 9 ins. Weight, 30 lbs.
Input—1 mv to 500 v		Input—200,000 ohms		Variable Selectivity at 40 db down from resonance { max. selectivity is 30 cps } { min. selectivity is 145 cps } Dial Calibration Points—62			115 volts 50-60 cyc 105 watts	Length, 21 1/2 ins. Height, 24 ins. Depth, 14 1/2 ins. Weight, 78 lbs.
Max. Input—100 v		Analyzer Input—20,000 ohms Detector Input—Should be not less than 100,000 ohms		Max. Attenuation: Fundamental—more than 60 db (-1%) Second and higher harmonics—less than 5% Filters—Tuned to nominal frequencies within ±5% (non-adjustable) Attenuator—70 db in 1 db steps				Length, 13 ins. Height, 9 ins. Depth, 8 ins. Weight, 16 lbs.
Max. Input—100 v		Analyzer Input—20,000 ohms Detector Input—Should be not less than 100,000 ohms		Max. Attenuation: Fundamental—more than 60 db (-1%) Second and higher harmonics—less than 5% Filters—Tuned to nominal frequencies within ±5% (non-adjustable) Attenuator—70 db in 1 db steps				Length, 13 ins. Height, 9 ins. Depth, 8 ins. Weight, 17 1/2 lbs.
Voltmeter Measurement Range—.01 v to 300 v in 3 ranges Precision—min. input 1 v for .1% distortion line—min. input .003 volts for full scale		Amplifier Input— 200,000 ohms shunted by approx. 24 mmfd Voltmeter Input 1 megohm (min.) shunted by approx. 32 mmfd		Max. Attenuation: Fundamental—more than 60 db (-1%) Second and higher harmonics—less than 5% Filters—Tuned to nominal frequencies within ±5% (adjustable -1%) Voltmeter—Average Reading (calibrated in rms volts and in db above a 1 mw, 600 ohm level)			115 volts 50-60 cyc 65 watts	Length, 21 1/2 ins. Height, 11 1/4 ins. Depth, 14 1/2 ins. Weight, 56 lbs.
Maximum Input—50 v		Input—500 ohms—one side grounded Output—500 ohms—one side grounded		Attenuation—110 db in 1 db steps				Length, 8 ins. Height, 5 ins. Depth, 4 1/2 ins. Weight, 4 lbs.
Measurement Range—.01 v to 300 v in 3 ranges		Input—1 megohm (min.) shunted by approx. 16 mmfd		Voltmeter—Average Reading (calibrated in rms volts and in db above a 1 mw, 600 ohm level)			115 volts 50-60 cyc 40 watts	Length, 7 1/2 ins. Height, 5 1/2 ins. Depth, 10 1/2 ins. Weight, 15 lbs.
Input—0.5 v to 200 v		Input—50,000 ohms		Separate External Attachments— 1. Photocell Input (jack provided) 2. Esterline-Angus 1 mil, 1400 ohm Automatic Recorder (jack provided)			115 volts 60-60 cyc 65 watts	Length, 17 1/2 ins. Height, 8 1/2 ins. Depth, 11 ins. Weight, 28 lbs.




205AG—Audio Signal Generator

100A—Secondary Frequency Standard

325B—Noise and Distortion Analyzer

NEW SOLDIERING GUN

SPEED IRON* READY FOR USE IN 5 SECONDS

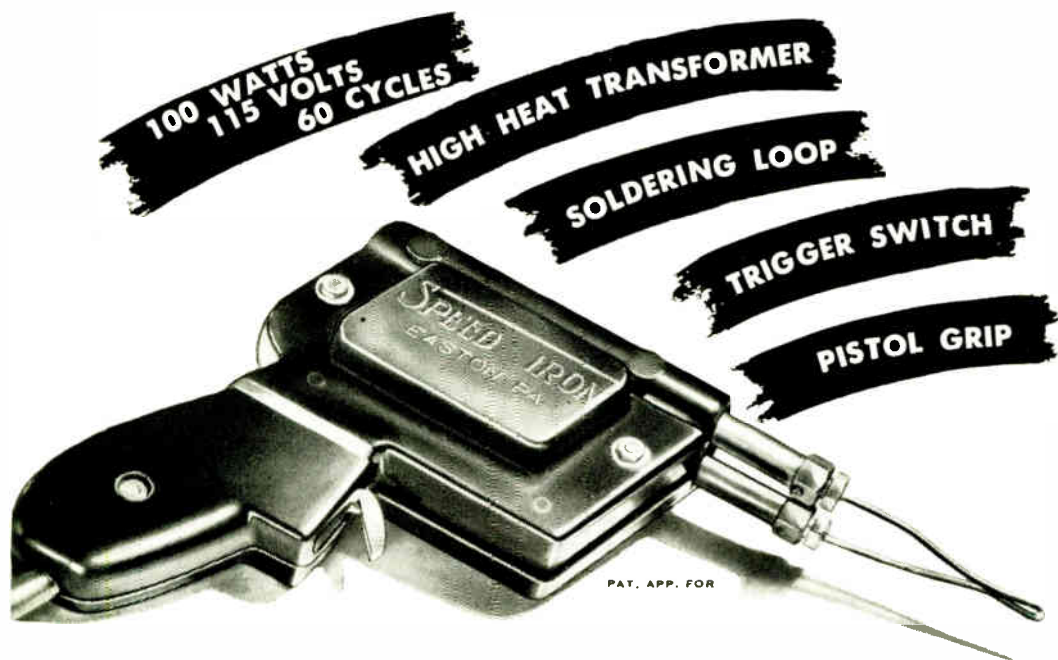

NEEDED BY AMATEURS, EXPERIMENTERS, SERVICE MEN

WITH the new Speed Iron you will solder faster and better than you ever have before. You can make a soldered electrical connection or change it easier than you ever imagined possible.

Heat is provided by a heavy current at low voltage from the compact built-in transformer. Current flows through the copper loop soldering—generates heat in the tip. Loop and tip come up to temperature because current flows through them. The trigger switch gives soldering heat in 5 seconds—when

you need it. The pistol grip handle and good distribution of weight makes it easy to hold. The compact dimensions enable you to get in close to the job. The loop soldering tip gets in the tough spots and still lets you see what you are soldering.

This new up-to-date soldering tool—the Speed Iron—is needed by every radio amateur, experimenter, and service man if he wants to have the best and latest equipment. See your radio parts distributor or order direct.

*T. M. REG. U. S. PAT. OFF.

WELLER MFG. CO.

DEPT. R.A.H.

EASTON, PA.

YOUR **BEST** SOURCE OF **ALL** RADIO AND ELECTRONIC **EQUIPMENT**

From the producing factories, from warehouse stocks and from little known sources, **TERMINAL** draws a steady flow of equipment. Our large, complete stock is your full assurance that we are your best source of supply.

For quick and intelligent service, turn to **TERMINAL**

FACTORIES



LITTLE KNOWN SOURCES




WAREHOUSES

Always Large Stocks of

- | | |
|-----------------|-----------------|
| Condensers | Fuses |
| Relays | Soldering irons |
| Insulators | Resistors |
| Tubes | Reactors |
| Microphones | Key |
| Sound equipment | Transformers |
| Coils | Clips |
| Wire and cable | Switches |
| Crystals | Vibrators |
| Batteries | Etc., etc. |
| Headphones | |

These and Other Famous Brands Always in Stock

- | | |
|------------------|-----------------|
| Aerovox | Mallicroft |
| Allied Relays | Hammarlund |
| Amphenol | IRC |
| ATF | Jensen |
| Amperex | Janet |
| Autoc | Kenyon |
| Audiotek | Littelfair |
| B. & W. | Philco |
| Borden | Phonetics |
| Burleigh | Miller |
| Chiley | Miller |
| Boyd | Muller |
| Bad | National |
| Bequest | Chassis |
| Canxon | Ray-Metal |
| Candwell | Primo |
| Centralco | Raytheon |
| Circuit Concepts | PCA |
| Conrad Dubilier | Shur |
| Drake | Spice-X |
| Dunco | Yayor |
| Echophone | Thorn |
| Emac | System |
| Essex | Supert |
| Electrovox | RTC |
| Genetron | Waltair Roulard |
| Guardar | Wetzel |

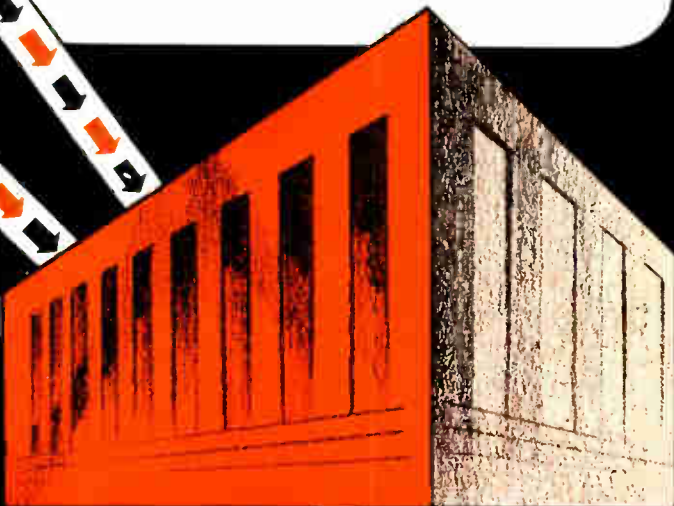

RADIO AMATEURS

Buy your ham equipment over the counter or by mail.

If It's Radio . . . We Have It!

TERMINAL

RADIO CORP.

85 Cortlandt Street, New York 7, N. Y. Tel. WOrth 2-4416


Hundreds of new developments have been born due to wartime development. In order to be sure that you are best posted write to us and be placed on our mailing list. We will mail catalogs and brochures as fast as they are printed.

THE HARVEY-WELLS


with a distinguished record for war




POLICE

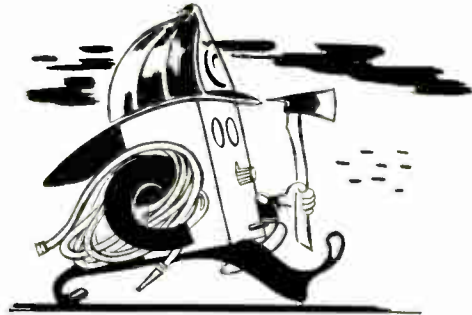


FIRE

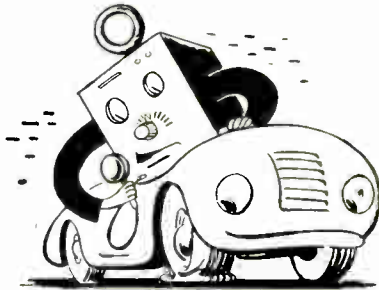

CARS

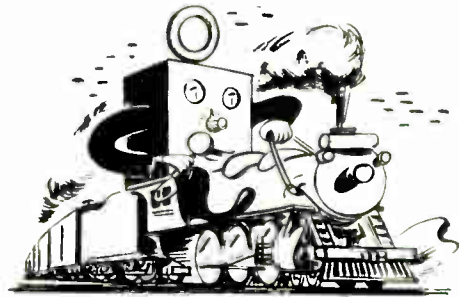


RAILROADS

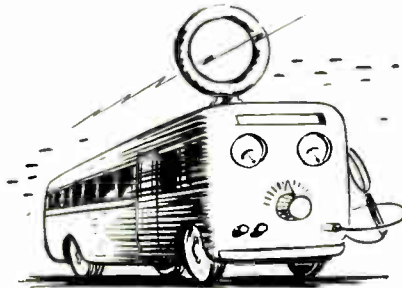

BUSES



TAXIS

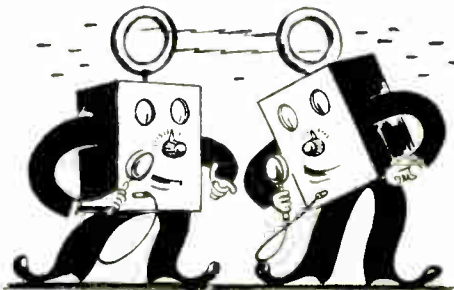

WALKIE-TALKIE

**With the
CIVILIAN
GROUND
FORCES**

COMMUNICATIONS CORPS

is ready to serve for peace


With the SEA and AIR FORCES of PEACE!



YACHTING



FISHING

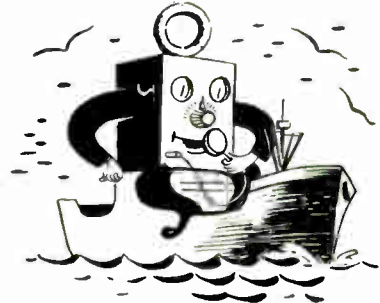


SHIPPING



PERSONAL PLANES



AIRPORTS

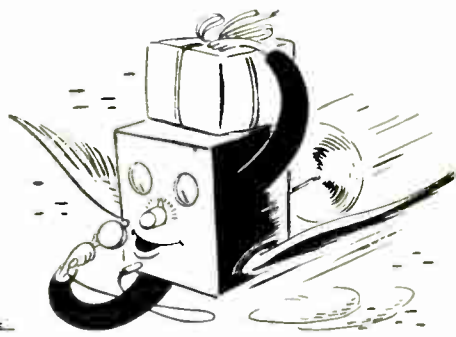

AIR TRANSPORT

The cartoonist's facile pen has vividly pictured the fields which Harvey-Wells hopes to serve when production hits its full peacetime stride.

The same skillful manufacturing techniques and highly specialized engineering which operated so successfully in war will produce Harvey-Wells communications equipment of distinctive merit for tomorrow's needs.

These specialized facilities, together with the Harvey-Wells design engineering organization, are available to you today. If you have a communications problem requiring the most competent handling, we urge you to get in touch with us at once.

Harvey-Wells
ELECTRONICS
SOUTHBRIDGE, MASSACHUSETTS



Every TECHNICIAN NEEDS THIS ALL-PURPOSE SOLDERING PENCIL

No. 536 • Pyramid
Tip, made from Tellurium.

RADIO AMATEUR'S HANDBOOK lists soldering equipment as one of the radio technician's indispensable tools. And out of the crucible of war came the Electrical Industry's, newest, trimmest, slimmest soldering tool . . . the Ungar light-as-a-feather Soldering Pencil—available in **FOUR INTERCHANGEABLE TIPS** . . . each designed to solve a particular problem, which makes it a "MUST" for the amateur now that peacetime activity is here.

For speedy precision on intricate, hard-to-reach jobs, you can't beat this ruggedly built Ungar Soldering Pencil! Takes plenty of punishment . . . weighs only 3.6 ounces . . . perfectly balanced; length 7 inches . . . heats in 90 seconds . . . draws only 17 watts and handles with fountain pen ease. No. 776 Handle-Cord set with No. 536 tip sells for considerably less than \$2. Please order only from your Electronics Distributor.


No. 776 • Handle-Cord Set. Plastic, 6 ft. cord. For all tips.

No. 537 • PencilTip, made from Elkaloy A, tip 1/8" dia.

No. 539 • Extra Hot, made from Tellurium.

No. 538 • Chisel Tip, made from Elkaloy A, tip 1/8" dia.

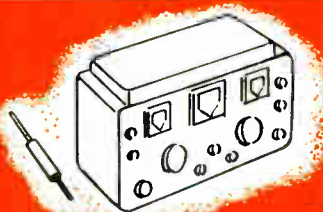Ungar Electric Tools, Inc.
Formerly Harry A. Ungar, Inc.
LOS ANGELES 54, CALIF.



**FROM A TINY RESISTOR
TO A COMPLETE RIG**

**YOU CAN
GET IT AT**

SUN

**AN ESTABLISHED *fact*
*since 1922***

We started serving the "ham" over 23 years ago, when radio was just a novelty. As the years rolled by, we grew with radio's natural development. Many times we literally "pushed the walls back" to make room for the thousands upon thousands of parts, as fast as they were introduced. Today we occupy 6,000 square feet of space and carry over 10,000 different items. We maintain expert technical and sales staffs. A huge stock of standard, nationally advertised products and a thoroughly trained shipping staff that means... FAST—PROMPT—SERVICE. Small wonder we are called—America's Most Complete Source of Supply.

SUN RADIO & ELECTRONICS CO., INC.

122 DUANE ST., NEW YORK CITY 7 • Tel. BArcly 7-1840

When buying crystals insist on

Specialists in Special Crystals

1 OIL BATH INSPECTION

2 COMSCOPE ORIENTATION

3 X-RAY ORIENTATION

4 ELECTRICAL AXES TEST

5 PRECISION SAWING

6 X-RAY ANGULAR CHECK

7 FLAW INSPECTION

8 BLANK STAMPING

9 DICING BLANKS

10 SURFACE GRINDING

11 BLANK ETCHING

12 FINAL LAPPING

13 BLANK EDGING

14 CRYSTAL FINISHING

15 STANDARD CALIBRATION

16 CRYSTAL PLATING

17 WAFER ETCHING

18 REMOVAL OF REJECTS

19 HOLDER LACQUERING

20 ALTITUDE TEST

NEW E NEW

R. PAUL
SALE

COMPLETE FACILITIES

In addition to finished crystals, Crystalab also engineers semi-finished or finished blanks in any quantity desired. Furthermore, inasmuch as we specialize in special crystals, Crystalab can mount any crystal in any holder, standard or custom-made.

Crystalab makes oscillating crystals from 50 kilocycles up to harmonic crystals in the 50 megacycle range . . . supersonic crystals from 20 kilocycles to 14 megacycles . . . filter crystals from 100 to 1,000 KC.

24 HOUR SERVICE

Orders for standard type crystals for Aircraft, Police or other emergency use will be filled within twenty-four hours from the time they are received.

CRYSTAL RESEARCH LABOR

World Radio History

Crystalab

C R Y S T A L S

There are no finer crystals made

The same top-notch engineering and processing skill which won for Crystalab a pre-eminent place as a prime contractor of military crystals is now being made available to amateur crystal users. Crystal Research Laboratories, engineers of Selectronic crystals, continues and increases its research in order to produce better crystals. When you buy a Crystalab crystal, whether it's finished to cycle accuracy or a blank that you bring to frequency yourself, you are assured that you have bought the finest crystal that engineering skill can devise — at the lowest cost for quality.

Coming soon!



AMATEUR CRYSTAL KIT

Soon, Crystalab will have at your radio dealers the crystal kit you want. This kit, consisting of just what you Amateurs have asked for, in the recent Crystalab contest, is being engineered for Amateurs, manufactured for Amateurs, and priced for Amateurs. It represents the height of engineering skill, at the lowest cost for quality. Ask to see the Crystalab Amateur Crystal Kit at your dealers today.

Ask your dealer!

Free

8 PAGE

Catalogue

Write Dept. Q.T. for comprehensive catalogue "Selectronic Crystals" and facilities booklet "Crystalab solves Problem".

ORIES, INC.

**29 ALLYN STREET
HARTFORD 3, CONN.**

World Radio History



They **LOOK** *like*
other transformers

BUT— the difference is in
performance — exceptional
FREED performance.

Built into every transformer are the specialized engineering techniques in design and production that mark the name **FREED**. Soundly constructed to withstand long and severe usage, **FREED** transformers are completely dependable for every application in all fields of communications and electronics.

FREED specialized engineering, which pioneered shock proof construction, hermetic sealing and many more outstanding improvements, is available to help solve your transformer problems. Why not take advantage of it?

Wave Filters
Audio Systems
Carrier System Components
Phase Shift Devices
Special Bridge Circuits
Supersonic Frequency
Components
Supersonic Frequency
Systems



FREED TRANSFORMER Co.

72 H SPRING STREET, NEW YORK 12, N.Y.

SPECIAL PILOT LIGHT OFFER

REASON FOR THIS OFFER

This offer is being made to acquaint you with the high standard, precision manufacture of Gothard Pilot Lights and to actually place in your hands *proof* of Gothards "fixed position terminals" which cannot twist or short, and other exclusive features found only in Gothard Lights.

THIS COUPON AND 25¢ presented to your jobber or dealer gives you a 50¢ No. 403 Gothard Pilot Light as illustrated below, and catalog showing complete line.

GOTHARD MANUFACTURING COMPANY

2124 Clear Lake Ave.

Springfield, Illinois

Name _____

Street _____


City _____

HAVE YOU THIS NEW— GOTHARD CATALOG?




It's different!

It's an engineering handbook!

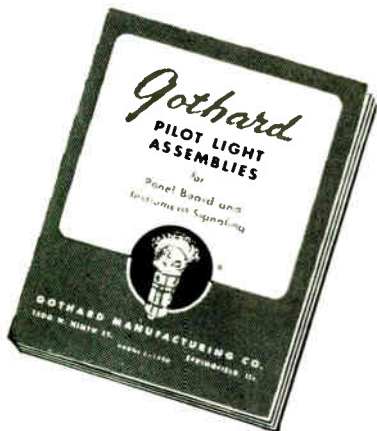Here's what it tells you — and it's free for the asking



Pilot Lights of every conceivable type are illustrated, together with blueprints giving essential dimensions. The correct lamp bulb to use with each type is illustrated and Mazda numbers listed. Pilot Light list prices range from 10¢ to \$3.00 per unit; a type for every purpose. Gothard engineers have made many improvements in construction details. Hot tin dipped, fixed position terminals are used on all miniature socket assemblies. Brackets have reinforcing ribs. All parts heavily plated.

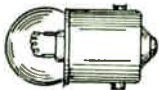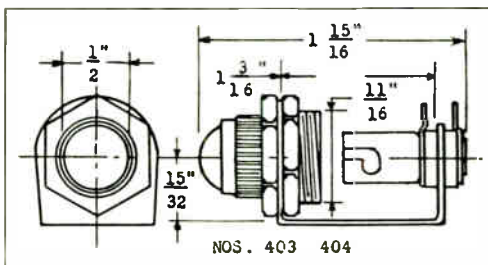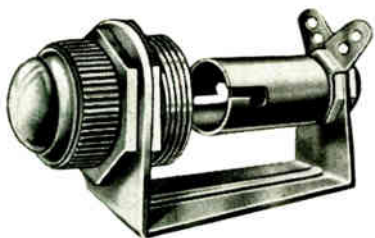

Mazda No. 51 6-8 volt

Mazda No. 53 12-16 volt

Mazda No. 356 28 volt



Mazda No. 44 6-8 volt

Mazda No. 1815 12-16 volt

Mazda No. 313 28 volt

No. 403—Faceted Jewel List \$0.50
No. 404—Plain Jewel List \$0.50

Bulbs not included

Gothard

MANUFACTURING COMPANY

2124 Clear Lake Ave.

Springfield, Illinois

Canadian Distributor: William F. Kelly Company, 1207 Bay Street, Toronto 5, Ontario
Export Division: 25 Warren Street, New York 7, N. Y. Cables: Simontrice, New York

It's Aireon

The Speaker of Tomorrow **TODAY!**

Famous Cinaudagraph Speakers, known the world over for tone, stamina, engineering perfection and design are once more in peacetime production. P.M. models of all sizes now utilize Alnico 5, the miracle metal that gives you 4 times the performance without size or weight increase. Constant research for improvements, highest standards of production and inspection plus use of only the finest materials—these are the extra features you get when you select a Cinaudagraph Speaker to do a job in a better way.



Cinaudagraph Speakers

A SUBSIDIARY OF Aireon

W6EX

W6LFD

W6JW

*It takes "Hams" to Know
what tubes are best for "Hams"*

W6BZ

W6FKG

W6MTD

W6LXA

W6LZL

Lewis **ELECTRONICS, Subsidiary of Aireon**
MANUFACTURING CORP., HAS THE TUBES YOU WANT

FOR DESCRIPTIVE CATALOGUES WRITE **Aireon**, KANSAS CITY, KANS.

for Your

FUTURE IN RADIO



50-WATT RADIO STATION


The Aireon Type RS-1 radio station is a complete, self-contained, simple-to-operate unit specifically designed to meet the requirements of airports, airlines, and similar types of communication systems. It includes two transmitter channels, two receiver channels, and remote control equipment, all ready for installation—it's ready to plug into the socket. The transmitter is rated at 50 watts output; channels available in 200 to 400 kilocycles, 2.00 to 8.00 megacycle, and 118 to 132 megacycle bands.

- Experienced Operators Unnecessary
- Designed for Any Climate

FIXED TUNED RECEIVER



AIREON Type 578-A Receiver

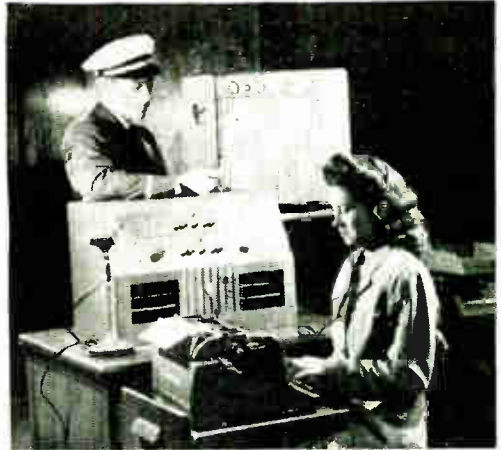

Type RS-1 50-Watt Radio Station

The Type 578-A Receiver is a single channel fixed tuned crystal controlled receiver of exceptional sensitivity and selectivity. This receiver covers frequency range from 2.5 to 16 mc; its sensitivity is better than 1 microvolt. The 578-A Receiver is well suited for remote locations where unattended operation is necessary.

★ FM EMERGENCY EQUIPMENT

FM Emergency Equipment by AIREON covers 30 to 42 megacycle and 156 to 162 megacycle range. It is produced in both portable and stationary units. Designed and engineered specifically for Police Depts., Fire Depts., Taxis, Bus and Truck lines, and many other types of mobile and stationary installations.

★ RAILROAD RADIO

Far in advance of the electronic field, AIREON is completely prepared to supply ANY RADIO COMMUNICATION EQUIPMENT A RAILROAD MAY DESIRE. Numerous AIREON products are engineered specifically for railroad use.

Type AA9-E



• CRYSTALS FOR EVERY RADIO NEED •

The Type AA9-E Crystal is made from selected Brazilian quartz, operates over a frequency range of 1,500 to 10,000 kc, and is designed to meet the most severe C.A.A. tests.

Type 604-A is designed for compact commercial aircraft transmitters. It has a frequency range from 2,000 to 10,000 kc and will withstand any conditions prevalent in air-borne equipment.

Type 604-A



Aireon

MANUFACTURING
CORPORATION

KANSAS CITY
SAN FRANCISCO
SLATER, MO.
OKLAHOMA CITY

BURBANK
CHICAGO
NEW YORK
GREENWICH, CONN.
MEXICO CITY, D. F.

SILVER



"VOMAX"

Measures **EVERY** Voltage

The secret of the overwhelming demand for "VOMAX" is just that simple. With it you can measure every voltage in radio receiver design and servicing.

"VOMAX" handles a wide range of d.c. and a.c. voltages at meter resistance so astronomically high that you can measure directly and accurately every such voltage. It goes far beyond conventional volt-ohm-ma-meters. For "VOMAX" will measure every a.f., i.f. and r.f. voltage from 20 cycles right up to beyond 100 megacycles.

This remarkable post-war instrument gives you vitally important visual dynamic signal tracing. Read the briefed specifications at left

practically a complete service station by itself . . . see how "VOMAX" makes you the master, no longer the victim, of tough service jobs. Imagine the time you'll save, the increased efficiency, the multiplication of your profits when you put "VOMAX" to work and can at last measure every voltage.

Requiring no priority and despite heavy demand, your favorite jobber can arrange quick delivery . . . if you act fast.

**NET PRICE \$59.85
ONLY**

AMATEUR PARTS & KITS

Born out of the war are many more money-saving new SILVER developments. As an up-to-the-minute amateur you'll want to know all about the new 904 resistance-capacitance bridge . . . new 1.6 thru 30mcs. "all-band" 5 to 500 watt transmitting inductors . . . u.h.f. tuners "harnessing" 112 thru 470 mcs. . . the new SILVER am/fm receiver/kit covering 1.6 thru 150 mcs. . . new "progressive" 5 to 500 watt xmitter/kit . . . 1.6 thru 500 mcs. absorption frequency meter.

1. Brand new post-war design . . . positively not a "warmed-over" pre-war model.
2. More than an "electronic" voltmeter, **VOMAX is a true vacuum tube voltmeter** in every voltage, resistance, db. function.
3. Complete signal tracing from 20 cycles through over 100 megacycles by withdrawable r.f. diode probe.
4. 3 through 1200 volts d.c. full scale in 6 ranges at 50, and in 6 added ranges to 3000 volts at 125 megohms input resistance.
5. 3 through 1200 volts a.c. full scale in 6 ranges at honest effective circuit loading of 6.6 megohms and 8 mmfd.
6. 0.2 through 2000 megohms in six easily read ranges.
7. -10 through +50 db. (0 db. = 1 mw. in 600 ohms) in 3 ranges.
8. 1.2 ma through 12 amperes full scale in 6 d.c. ranges.
9. **Absolutely stable** - one zero adjustment sets all ranges. No probe shorting to set a meaningless zero which shifts as soon as probes are separated. Grid current errors completely eliminated.
10. Honest, factual accuracy: $\pm 3\%$ on d.c.; $\pm 5\%$ on a.c.; 20 ω through 100 megacycles; $\pm 2\%$ of full scale, $\pm 1\%$ of indicated resistance value.
11. Only five color-differentiated scales on $4\frac{1}{4}$ " D'Arsonval meter for 51 ranges (including d.c. volts polarity reversal) eliminate confusion.
12. Meter 100% protected against overload burnout on volts, ohms db.
13. Substantial leather carrying handle. Size only $12\frac{3}{4}$ " x $7\frac{3}{4}$ " x $5\frac{1}{4}$ "

SEND FOR FREE CATALOG
SEE YOUR JOBBER

OVER 34 YEARS OF RADIO ENGINEERING ACHIEVEMENT

McMurdo Silver Company

1240 MAIN STREET, HARTFORD 3, CONNECTICUT

SIGMA


Specialists in Precision Relay Engineering and Manufacture

SIGMA RELAYS achieve a peak in the difficult combination of extreme ruggedness with exceptional sensitivity


SIGMA RELAYS give precise operation on low levels of input power (down to .0005 watts) while maintaining exceptional resistance to vibration and other conditions of physical environment. These relays are particularly suited for applications such as:

**Accurate Switching
High Speed Keying**

**Operation from Vacuum Tube Output
Operation on Close Differential**

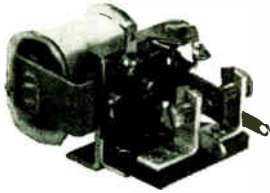

TYPE 4F
1 3/8" x 1 3/8" x 1 1/2"
Weight: 2 3/16" oz.

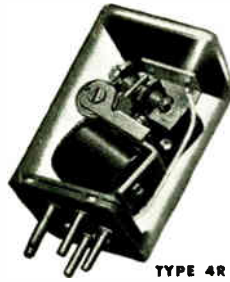


TYPE 4R
1 1/2" x 1 1/2" x 2 3/4"
5 Pin Plug-in Base



TYPE 4A
2 3/8" Diam. x 2" High
5 Pin Plug-in Base


The 4 Series is recommended for: High Speed (down to 1 millisecond)—Keying (up to 200 operations per second)—Sensitivity (aircraft performance on 30–50 milliwatts input, 10 milliwatts in less severe environment)—Economy—Compactness—Moderately Severe Environment (temperature, humidity and vibration).

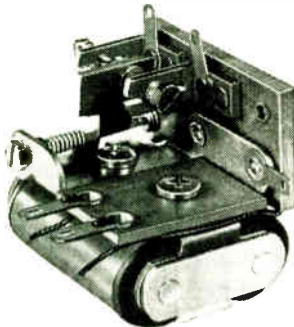

TYPE 5F
1 3/8" x 1 3/8" x 1 3/8"



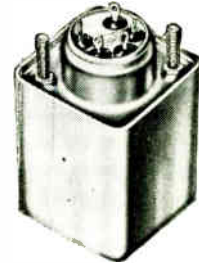TYPE 5R
1 1/2" x 1 1/2" x 2 1/4"
5 Pin Plug-in Base



TYPE RJB2
Hermetically Sealed Enclosure, available for both the 4 and 5 series

The 5 Series is best suited for: Extreme Sensitivity (input power as little as 1/2 milliwatt, aircraft performance on 5 milliwatts)—Severe Environment (withstands temperatures -40° to +90° C, vibration of 11 g's or more, shock of 500 g's).

- Sigma Relays are not ordinarily sold as stock items, but upon definite recommendations as to the solution of particular problems. However, small quantities are available as quickly as stock items, because all components are in stock and production is on the "short order" line.
- SIGMA shares the responsibility for the proper operation of all Sigma relays . . . in other words, Sigma Instruments establishes the proper relay specifications in accordance with your problem requirements, then guarantees that the relays will perform with complete satisfaction. Sigma Relays are available with coil resistances up to 18,000 Ohms.

• **For A.C.**—Both the Series 4 and 5 are available with a built-in full-wave rectifier giving D.C. sensitivity on A.C. input. The Series 5 is available for time-delay operation.

Sigma Instruments, inc.
Sensitive **RELAYS**
78 CEYLON STREET BOSTON 21, MASS.

DuMONT

OSCILLOGRAPH

CATHODE-RAY TUBES

Hundreds of thousands of DuMont cathode-ray tubes of many types served in oscillographs, radar and other wartime equipment. Of the many available types, the three types herewith have been chosen as the most popular for ham and experimental purposes.



**DuMONT
TYPE 3AP**

Designed for oscillographic and other applications where simplicity of equipment is paramount. Small bright spot obtained at

low accelerating voltage and without anced deflection.

MECHANICAL CHARACTERISTICS:

Overall length	11 1/2"	± 3/8"
Maximum diameter	3"	± 1/16"
Base	Medium 7-pin	
Basing	RMA Basing Designation 7AN	

TYPICAL OPERATION:

Heater Voltage	2.5	2.5 volts
Anode No. 2 Voltage (E ₁₂)	1000	1500 volts
Anode No. 1 Voltage (E ₁₁) for focus when E ₁₁ is 75% of cutoff value	286	430 volts ± 20%
Grid Voltage (E ₁₁) for beam cutoff	-33	-50 volts ± 50%
Deflection Factor:		
D ₁ D ₂	76	114 d.c. volts/inch ± 20%
D ₁ D ₁	73	109 d.c. volts/inch ± 20%



**DuMONT
TYPE 3GP**

Designed for oscillographic and other applications where small spot size, brilliant

trace and minimum of defocusing with deflection are required.

MECHANICAL CHARACTERISTICS:

Overall Length	11 1/2"	± 3/8"
Maximum diameter	3"	± 1/16"
Base	Medium Magnal	
Basing	RMA Basing Designation 11A	

TYPICAL OPERATION:

Heater Voltage	6.3	6.3 volts
Anode No. 2 Voltage (E ₁₂)	1000	1500 volts
Anode No. 1 Voltage (E ₁₁) for focus when E ₁₁ is 75% of cutoff value	234	350 volts ± 20%
Grid Voltage (E ₁₁) for beam cutoff	-33	-50 volts ± 50%
Deflection Factor:		
D ₁ D ₂	80	120 d.c. volts/inch ± 20%
D ₁ D ₁	70	105 d.c. volts/inch ± 20%



**DuMONT
TYPE 5CP**

Designed for oscillographic and television applications. Intensifier principle used to provide maximum deflection sensitivity for given final accelerating voltage. A standard

Army-Navy diheptal base provides a quite insulation between electrodes. In television applications, a P4 screen is available.

MECHANICAL CHARACTERISTICS:

Overall Length	16 3/4"	± 3/8"
Maximum Diameter	5 1/8"	± 3/32"
Base	Medium 12-pin Diheptal	
Basing	RMA Basing Designation 14B	

TYPICAL OPERATION:

Heater Voltage	6.3	6.3	6.3 volts
Anode No. 3 Voltage (E ₁₃)	1500	3000	4000 volts
Anode No. 2 Voltage (E ₁₂)	1500	1500	2000 volts
Anode No. 1 Voltage (E ₁₁) for focus when E ₁₁ is 75% of cutoff value	431	431	575 volts ± 20%
Grid Voltage (E ₁₁) for beam cutoff	-45	-45	-60 volts ± 50%
Deflection Factor:			
D ₁ D ₂	55	69	92 d.c. volts/inch ± 20%
D ₁ D ₁	48	59	79 d.c. volts/inch ± 20%

Descriptive literature on DuMont Oscillographs and Tubes, sent on request.

MEANS BOTH

CATHODE-RAY OSCILLOGRAPHS

Tens of thousands of DuMont oscillographs helped win the war. An even greater number will help win the peace. And now, in keeping with the specific needs and the pocketbooks of hams and experimenters, DuMont engineers recommend these two popular instruments in addition to the Type 208B which is too well known to require description or praise here:

DuMONT TYPE 164E



In the radio field a DuMont oscillograph is a "must" for seeing performance at any point in the circuit. See the output voltage; see resonance and frequency response curves; see measurements of hum; see

oscillation and regeneration in I.F. stages; see distortion and trace it to its origin; see proper neutralization in your transmitter; see modulation.

OPERATING LIMITS . . .

Deflection sensitivity (with maximum amplification):

Vertical	0.80 r.m.s. volts/inch
Horizontal	0.65 r.m.s. volts/inch

Deflection sensitivity direct connection to cathode-ray tube plates.....30 r.m.s. volts/inch

Input Characteristics:

Vertical amplifier 1 megohm. Horizontal amplifier 0.8 megohm.
Voltage gain, vertical amplifier 43 times; horizontal amplifier 55 times.

Frequency range of amplifiers	5 to 100,000 "sinusoidal" c.p.s.
Frequency range of timing axis	15 to 30,000 "sawtooth" c.p.s.
Maximum allowable a.c. voltage input to amplifiers	250 v.
Maximum allowable d.c. voltage input to amplifiers	400 v.

Type 164E operates on either 115 or 230 volts a.c., 40-60 cycles. Furnished in metal cabinet equipped with carrying handle,

measuring 11 $\frac{5}{8}$ " h. x 7 $\frac{3}{8}$ " w. x 14" d.
Weight: 20 lbs.

DuMONT TYPE 224A



Utilizes a Type 3GP1 tube operating with accelerating potential of 1,000 volts. Bright, well-defined trace. Four free deflection plates permit push-pull deflection and minimize distortion. Wide-band amplifiers

make this instrument highly desirable for experimentation and service work in FM and television. Z-axis terminal on front panel for intensity modulation of beam.

AMPLIFIER FREQUENCY RESPONSE:

Y-axis, sine wave frequency response uniform within 3 db. from 20 cycles to 2 megacycles.
X-axis.....uniform within 3 db. from 10 cycles to 100 KC.

DEFLECTION FACTOR WITH AMPLIFIER:

Y-axis terminals	0.1 volt r.m.s./inch deflection
Y-axis with probe	0.4 volt r.m.s./inch deflection
X-axis terminals	0.7 volt r.m.s./inch deflection

TO DEFLECTION PLATES:

Y-axis	25 volts r.m.s./inch deflection
X-axis	28 volts r.m.s./inch deflection
Z-axis	Intensity modulation 15 volts peak is sufficient to bring beam from just-extinguished condition to normal brilliance,

LINEAR TIME-BASE:

Frequency range	15 to 30,000 c.p.s.
Direction of sweep	Left to right
Synchronizing signal sources	Internal (Y-signal); Line Frequency, external.
Synchronizing Polarity	Either polarity of synchronizing signal.

Type 224A operates on 115 volts a.c., 50-60 cycles. Metal cabinet with removable pro-

TECTIVE COVER. Carrying handle 14 $\frac{1}{8}$ " h. x 8 $\frac{3}{8}$ " w. x 15 $\frac{1}{8}$ " d. Weight: 49 lbs.

DUMONT

Precision Electronics & Television

ALLEN B. DUMONT LABORATORIES, INC., PASSAIC, NEW JERSEY • CABLE ADDRESS: ALBEEDU, PASSAIC, N. J., U. S. A.



R. C. (Dick) Hall
W5EIB

R. C. & L. F. HALL

"THE HAM SHACK"

"The Ham Shack" is a busy place these days. Ham gear from hundreds of manufacturers is pouring into our Receiving Department and onto our shelves (when it



L. F. (Lillian) Hall
W5EUG

gets by the Shipping Department) . . . We have continued to serve our many friends through the War Years and the fact that the Harris County War Emergency Radio Service stations generally had modern tubes and components is an indication of our success.

"Across the Operating Table"

was the name of our Amateur Bulletin, as many of you will recall. There will soon be a new "Across the Operating Table" and you can sit across the table from us for our informal little "ragchews" by dropping us your name and address—a postal will do.

Equipment with Our Name on It Is Worth More

but costs just the same as anywhere else. For example, if you buy a communications receiver from us, you not only get the same receiver you would get anywhere else but you also have the benefit of our service, which includes:

- (1) We take care of the factory guarantee.
- (2) We give you a "Guaranteed Trade-In Allowance" on equipment purchased from us.
- (3) Easy terms are available if desired.
- (4) Liberal trade-in allowance on used equipment.
- (5) Technical advice to assist you in your selection.
- (6) A large stock for your personal inspection if you can drop in to see us.

OUR PARTS SERVICE includes:

- (1) Technical advice on the selection of components, which gives you the most for your money. We are constantly experimenting with new products for your benefit.
- (2) Easy payment plan on large purchases of parts.

GET ON OUR MAILING LIST . . . whether you live just around the corner or two thousand miles away and try our service. You will see why we are called "Specialists in Amateur Equipment & Supplies."

A FEW OF THE MANUFACTURERS
WHOSE PRODUCTS WE DISTRIBUTE

Aerovox Corporation
 American Phenolic Corp.
 American Radio Hardware Co.
 American Radio Relay League, Inc.
 Alliance Manufacturing Co.
 The Astatic Corporation
 Atlas Sound Corp.
 Barker & Williamson
 Belden Mfg. Co.
 Birnbach Radio Co.
 Bitley Electric Co.
 Browning Laboratories, Inc.
 Brush Development Co.
 Bud Radio Company
 The Allen D. Cardwell Mfg. Co.
 Centralab
 Cinsudagraph Speakers, Inc.
 Drake Electric Works
 Dumont Laboratories, Inc., Allen B.
 Eastern Mike-Stand Co.
 Echophone Radio Co.
 Eitel-McCullough, Inc. (Eimac)
 Electronic Laboratories
 Electro-Voice Corporation
 General Cement Mfg. Co.
 General Electric Co.
 General Industries Co.
 Gordon Specialties Co.
 Gotthard Mfg. Co.
 The Hallicrafters Co.
 The Hammarlund Mfg. Co., Inc.
 Hytron Radio & Electronics Corporation
 Heints and Kaufman (Gammatron)
 The Instructograph Co.
 Insuline Corp.
 Jensen Radio Mfg. Co.
 Johnson Co., E. F.
 Jones, Howard B.
 Kaar Engineering Co.
 Leach Relay Co.
 Littelfuse Laboratories
 Les Logan Co.
 McElroy, T. R.
 McGraw-Hill Book Co., Inc.
 John Meck Industries, Inc.
 Meissner Mfg. Co.
 James Millen Mfg. Co. Inc.
 Mueller Electric Co.
 National Company
 Ohmite Mfg. Co.
 Peerless Electrical Products Co.
 Pioneer Genemotor Corp.
 Precision Apparatus Co.
 Premax Products
 Radio Mfg. Engineers, Inc. (RME)
 Radio Corporation of America
 Sangamo Electric Co.
 Setchell-Carlson, Inc.
 McMurdo Silver Co.
 Standard Transformer Corp.
 Taylor Tubes, Inc.
 Thordarson Electric Mfg. Co.
 Trimm, Inc.
 Triplett Electrical Instrument Co.
 The Turner Company
 Harry A. Ungar, Inc.
 United Electronics Co.
 University Laboratories
 Utah Radio Products Co.
 Vibraloc Mfg. Co.
 John Wiley & Sons, Inc.

"THE HAM SHACK" (R. C. & L. F. Hall)

P. O. Box 2434, Zone 1, Dept. A • 1015-17 Caroline Street, Houston 2, Texas

Telephone • Capitol 9731

Quality

FOR EFFICIENCY

DESIGNED

TRANSFORMERS



There Are ITC TRANSFORMERS To Meet YOUR Specifications

Power, voltstats, voltage regulating, step-up, step-down, plate, audio, input, interstage, output, modulation driver, Microphone, line, mixing transformers, audio, reactors. . . .

Our expert Engineering staff and years of experience in developing and manufacturing transformers have established an unexcelled reputation for Dependability and Quality.

Insist on an "ITC TRANSFORMER"



Write for Catalog H-46

INDUSTRIAL TRANSFORMER CORP.
2540 BELMONT AVENUE, NEW YORK, N. Y.

Out of the War Comes the MECO TUBULAR PLASTIC PLYWOOD SECTIONAL MAST

AN amazing development, used for radio antenna masts and for aircraft landing and launching gear.

Now available for commercial and amateur radio use—light, easily handled, amazing strength, low in cost. Will withstand horizontal and vertical loads at the head as great as 10,000 pounds. In sizes from 3" to 8" diameter, heights from 12 to 125 feet, in 12 ft. sections.

Stays every 25 ft. of height are corkscrew anchored. Hinged base and erecting boom are part of installation, making it easy to raise or lower at any time.

Secret lies in the sectional tubular construction, of alternate layers of wood veneer and fabric, convolutely wound and bonded with waterproof phenol-resin. Weatherproof, strong, light, resistant to corrosion, mold, rot or insects.

12 ft. sections easy to handle, positive coupling.

READ THESE 8 ADVANTAGES

1. Non-metallic — does not interfere with radiation pattern of U.H.F. antennas.
2. Strong, light, weather-proof.
3. Easy to erect.
4. Readily removed to new site.
5. Short sections, easy to transport.
6. Good looking, clean, modern.
7. Low-cost.
8. Minimum maintenance.

SEND FOR DATA

write

MARYLAND ENGINEERING CO.

PIKESVILLE

BALTIMORE 8, MARYLAND


FREE!


MECO MAST

Maryland Engineering Co.
PIKESVILLE
BALTIMORE 8, MARYLAND

ERECTING BOOM

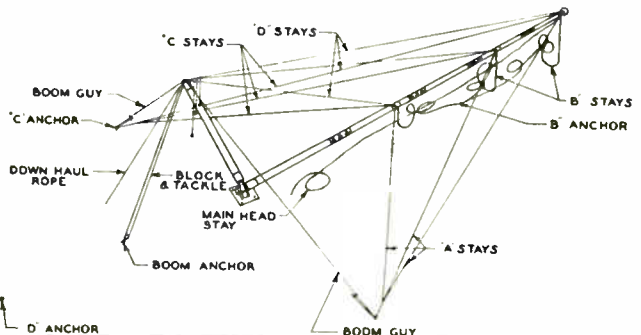Erecting boom and hinged base make erecting and dismantling easy, quick, economical.



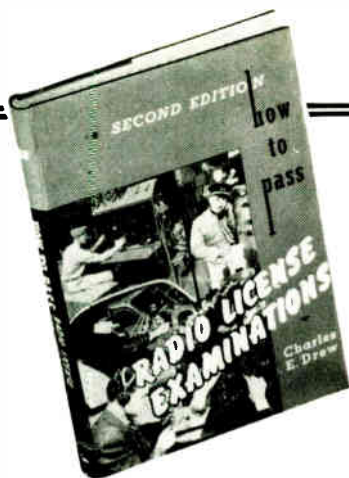

DREW'S HOW TO PASS RADIO LICENSE EXAMINATIONS

For Amateur Radio Operators, Radiotelephone and Telegraph Operators

COVERS

Broadcasting, Marine, Aeronautical, or any field of Radio Transmission and Reception

If you are an amateur and want to win your "ticket" this is the book for you. It will help you pass your radio license examinations.

For you who want to win your mark in the radio profession, this edition covers every type of radio activity whether it is marine, aeronautical, police or amateur broadcasting. Presented in easy-to-follow question-and-answer form.

Second Edition, 1944

320 Pages

\$3.00

CONTENTS

- I. Basic Radio Laws
- II. Basic Theory and Practice
- III. Radiotelephone
- IV. Advanced Radiotelephone
- V. Radiotelegraph
- VI. Advanced Radiotelegraphy

has helped thousands prepare to get their "ticket"!

Read what these important publications say about the revised Second Edition of this "bible" for radio operators, radiotelephone and telegraph men.

RADIO NEWS: "In this new and revised second edition, Mr. Drew has presented much valuable information for the benefit of those preparing to take the FCC radio license examinations. The author has avoided the inclusion of extraneous and nonessential information and has presented a clear-cut picture of the type of question which is asked of examinees."

ELECTRONICS: "The new edition, like its predecessor, provides a valuable and efficient means of refreshing theoretical knowledge in preparation for the examinations."

PROCEEDINGS OF THE I. R. E.: "As a whole, this work appears to be superior to previous publications of this type. Notably, one finds greater accuracy in the choice and expression of formulas, and more care in specifying the case to which the formula is applicable and the units in which the factors are expressed where basic units are not employed. Also the author has included discussions and notes immediately following the answers with a view to enabling the reader to understand the manner in which fundamental principles were applied in arriving at the aforesaid answer. This will aid the reader in handling successfully examination questions based on the same general principles but worded in a somewhat different manner."

RADIO CRAFT: "The new edition of this standard book has been awaited by communications students for some seasons. It fulfills all their expectations. Thoroughly revised to meet the new (since the first edition) type of government examinations, it retains the same clear and to-the-point style that distinguished the older issues."

BULLETIN OF THE WESTERN SOCIETY OF ENGINEERS: "Anyone contemplating taking a radio license examination will find material in this book invaluable for study or for review."

PROFESSIONAL ENGINEER: "Just the book for those seeking radio operator license . . . contains extracts from radio laws and a number of very useful tables, and it can be recommended not only to those who wish to acquire a commercial radio operator's license, but to those interested in radio communications as well."

10-DAY FREE TRIAL

JOHN WILEY & SONS, Inc., 440 Fourth Avenue, New York 16, N. Y.

ON APPROVAL COUPON

JOHN WILEY & SONS, Inc.
440 Fourth Ave., New York 16, N. Y.

Please send me a copy of Drew's HOW TO PASS RADIO LICENSE EXAMINATIONS on ten days' approval. At the end of that time, if I decide to keep the book, I will remit \$3.00 plus postage; otherwise I will return the book postpaid.

Name

Address


City and State

Employed by

ARRL-1946

ATR

NEW MODELS Built to Military Standards

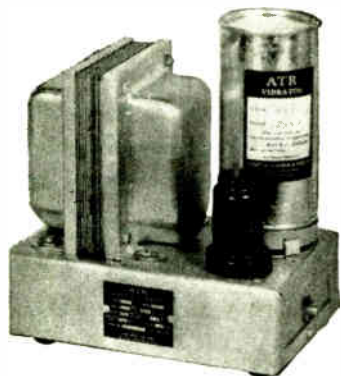

Illustrating ATR Vibrator Pack complete without audio filter, Style A

• **ATR** HEAVY DUTY

VIBRATOR PACKS


For Inverting Low Voltage D. C.
to High Voltage D. C.

For Operation of Portable Receivers and Transmitters, Aircraft Apparatus, Battle Announce Systems, Amplifiers, and Scientific Apparatus.

• **ATR** STANDARD AND HEAVY DUTY

INVERTERS

For Inverting D. C. to A. C.

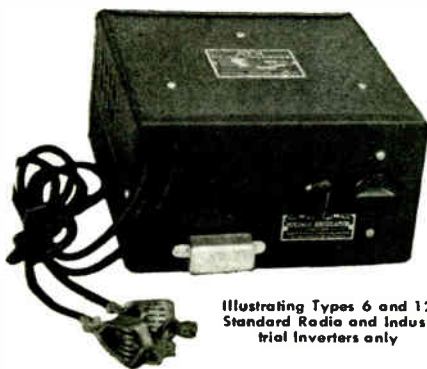

Illustrating Types 6 and 12 Standard Radio and Industrial Inverters only

Specially Designed for Operating Electrical Equipment including A. C. Radios, Battle Announce Systems, Television Sets, Amplifiers, Intercall Systems, and Radio Test Equipment from D. C. Voltages in Vehicles, Ships, Trains, Planes, and in D. C. Districts.

Write for Catalog No. 244 illustrating the ATR Complete Line of Vibrators, Vibrator-Operated and Rectifier Power Supplies


AMERICAN TELEVISION & RADIO CO.

Manufacturers of Quality Products Since 1931

ST. PAUL, MINNESOTA, U. S. A.

Hallcrafters

radio equipment
that covers the
SPECTRUM

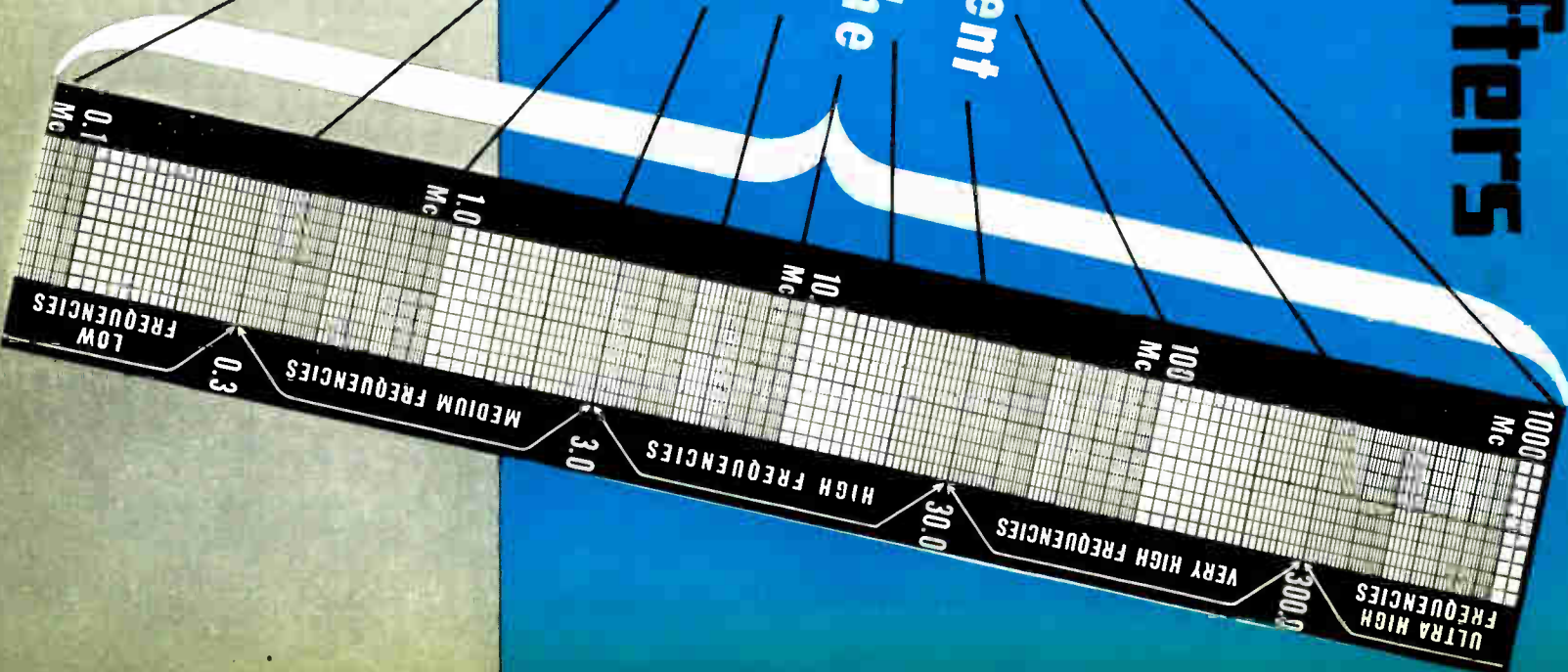

A MESSAG

hallicrafters

FOR AMATEURS

FIRST, LAST AND ALWAYS

hallicrafters RADIO

178

FROM BILL HALLIGAN



With this edition of the American Relay League Handbook, amateur radio finds itself on the threshold of an entire new era. At this time Hallicrafters wants to reaffirm its original position of being primarily devoted to the development of radio equipment specifically designed for amateur use. "Amateurs, first, last and always..." is a brief but powerful summary of postwar production plans at Hallicrafters.

The amateurs have always been far out in front in the swift technological progress that has marked the growth of radio science in the 20th century. In the exciting years ahead very high and ultra high frequency communications, frequency modulation, facsimile reproduction and television will be among the many new phases of the art to be explored and utilized by amateur operators. Hallicrafters engineers backed by years of pioneering experience in high frequency work are now turning their attention to these new fields.

Throughout all of this forward development the company will keep pace with the character and spirit of amateur growth. Dyed in the wool amateurs high up in the management of the company, amateurs on the engineering staff and thousands of amateur friends of the company reporting back to us about how Hallicrafters equipment served in the war all combine to give us a "board of directors" that keeps us close to the amateur ideal.

In the following section are details of a long and distinguished line of Hallicrafters receivers and transmitters. High spots include the famous Super Skyrider - the SX-28A, considered by many amateurs the greatest communications receiver ever designed; the Super Defiant and the Sky Champion, highly versatile, high frequency receivers representing top values in the medium and lower priced brackets. Here are sets like the S-36A, five years ahead of time in anticipation of the extension of FM up into the higher frequencies. Here is the renowned HT-4E transmitter, the heart of the famous SCR-299, back from the wars ready to resume its position in your ideal ham shack. And here are many more models, designed by engineers who know and can answer the insistent demands of the amateurs for better and better radio.

Bill Halligan
W9WZE



THE SUPER


The new Hallicrafters Model SX-28A is a further refinement of the famous Model SX-28 that achieved such popularity with amateur and professional operators prior to Pearl Harbor. Embodying circuit refinements and constructional modifications necessitated by the arduous conditions of military service the new SX-28A offers the maximum in communications receiver performance to the discriminating buyer.

The traditional sensitivity and selectivity of the Model SX-28 have been

further improved in this new Super Sky-Rider by the use of "micro-set" permeability-tuned inductances in the r.f. section. The inductances, trimmer capacitors, and associated components for each r.f. stage are mounted on small individual sub-chassis and may be removed as a unit for easy servicing.

Thousands of these fine receivers have seen service with the armed forces in all parts of the world and have maintained Hallicrafters' reputation for outstanding quality and performance under the most difficult conditions.

hallicrafters RADIO

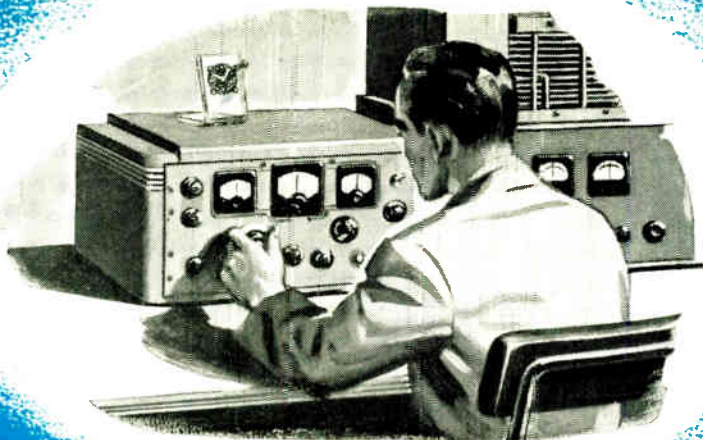

KYRIDER MODEL SX-28A

550 kc. to 42 Mc. Continuous in Six Bands

FEATURES

1. Frequency range 550 kc. to 42 Mc. continuous in 6 bands.
2. Main tuning dial accurately calibrated in megacycles.
3. Separate calibrated bandspread dial.
4. Two stages of radio frequency amplification.
5. Beat frequency oscillator, pitch variable from front panel.
6. Combination a.v.c.-b.f.o. switch.
7. Send-receive switch.
8. Lamb type 3-stage adjustable noise silencer.
9. Separate r.f. and a.f. gain controls.
10. Provision for battery or external power supply operation.
11. Push-pull 8-watt output stage.
12. Variable tone control, band-pass audio filter and bass boost switch.
13. Provision for break-in operation.
14. 500 or 5000 ohm output.
15. Six position i.f. and crystal filter selectivity switch.
16. Crystal phasing control.
17. "S" meter calibrated in S units and db. above S9.
18. Oscillator compensated for frequency drift.
19. Antenna compensator mounted on panel.
20. Separate a.v.c. amplifier.
21. "Unit-style" r.f. sections for easy servicing.
22. "Micro-set" type coils in r.f. section permeability tuned.
23. Dial lock on main tuning dial.
24. Inertia flywheel tuning and pre-loaded gear drive on main and bandspread dials.
25. Phonograph input jack.

THE INSIDE STORY OF THE FAMOUS

The frequency range of the SX-28A extends from 550 kc. to 42 Mc. and is covered in six bands with suitable overlap at the band ends. In addition to the main tuning dial which is accurately calibrated in megacycles, there is a calibrated band-spread dial covering the frequency ranges of 3.5 to 4 Mc., 7 to 7.3 Mc., 14 to 14.4 Mc. and 28 to 30 Mc. Both dials are provided with flywheel inertia tuning.

One stage of r.f. amplification is used on frequencies below 3 Mc. and two stages on the higher frequency bands. These pre-selector stages using the new high-Q "micro-set" inductances assure a good signal-to-noise ratio and a high degree of selectivity. The Model SX-28A has an image ratio of 40 to 1 at 30 Mc.—350 to 1 at 14 Mc., and a proportionately increasing ratio as the frequency is decreased.

The two stage i.f. amplifier is designed to retain its adjustment under conditions of extreme change in temperature and humidity. The i.f. transformers are permeability tuned and are provided with small extra windings which can be connected to increase the coupling between circuits. These windings are used in conjunction with the crystal filter to furnish six different degrees of selectivity. Control is by means of a six-position panel switch. Any desired i.f. selectivity from wide-band high fidelity to razor-sharp c.w. reception is instantly

available. In the medium and broad crystal positions the i.f. circuits function as a band-pass filter rather than as the more common broadly peaked resonant circuit and provide fully intelligible reception of radio telephone signals while holding interference and atmospheric to a minimum.

The SX-28A incorporates a double a.v.c. system. A.v.c. voltage for the r.f. and mixer tubes is taken from the broadly tuned carrier after it has passed through only three tuned i.f. circuits. A.v.c. for the i.f. stages, however, is taken from the carrier after it has passed through six tuned i.f. circuits. This arrangement provides a reduction in between-station noise and a more sharply defined aural tuning action. The "S" or signal intensity meter operates in conjunction with the a.v.c. and is calibrated in S units of approximately six db. each and in decibels above S9. A three position panel switch is provided for the control of a.v.c., "S" meter, and b.f.o. circuits.

Other features which contribute to the fine performance of the SX-28A are a Lamb three-stage noise silencer with panel adjustment; push-pull 6V6GT output stage with band-pass filter, bass boost, and tone control; antenna compensator; separate a.f. and r.f. volume controls; and panel stand-by switch. All controls and switches are conveniently arranged on the panel.



MODEL PM-23 SPEAKER

This Mallcrafters-Jensen speaker is designed for use with the larger Mallcrafters receivers. Of the permanent magnet type the Model PM-23 has a ten-inch cone and is mounted with its coupling transformer in a steel cabinet finished in gray wrinkle lacquer to match the receiver. Speaker opening is concealed by attractive metal grill. Transformer matches 5000 ohm output of receiver.

WEIGHT: packed for shipment, 22 pounds.



X-28A

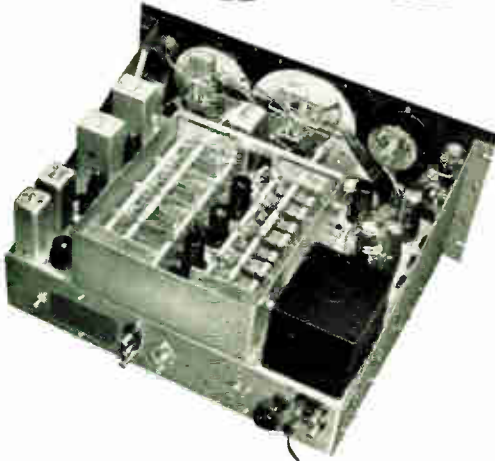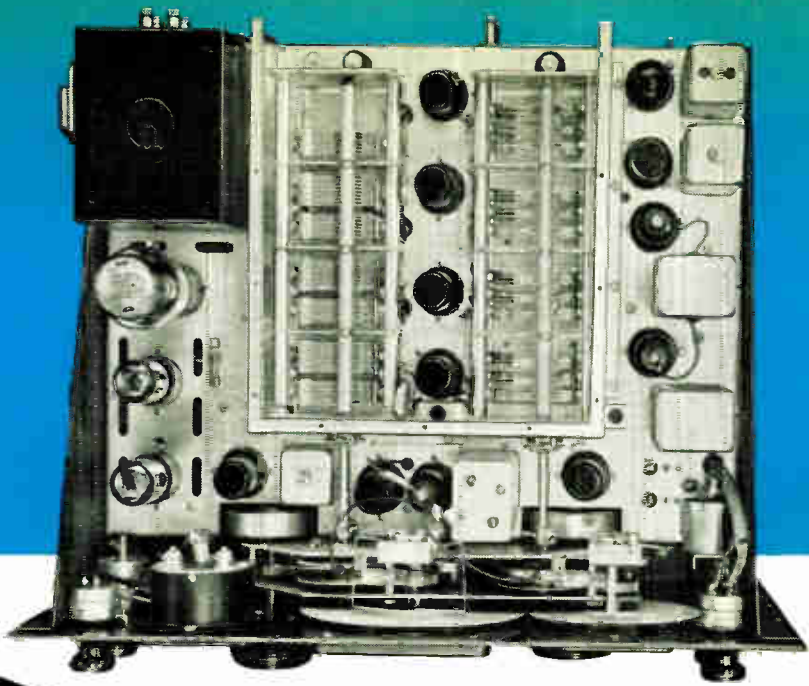

CONTROLS:

TONE and AC. ON/OFF; B.F.O. (pitch control); BASS IN/OUT; A.F. GAIN; MAIN TUNING; R.F. GAIN; BAND SWITCH; ANT. TRIMMER; BANDSPREAD TUNING; A.V.C. and B.F.O. ON/OFF; SELECTIVITY; SEND/RECEIVE; CRYSTAL PHASING; A.N.L.; "S" meter adjustment on rear of chassis.

EXTERNAL CONNECTIONS:

Antenna-ground terminals arranged for single wire or doublet; speaker terminals for either 500 or 5000 ohm output; line cord ana plug; line fuse; special socket, normally shorted by octal plug, provides for battery or external power supply operation and stand-by connection to transmitter; phonograph in-

put jack. All connections are mounted on rear of chassis except headphone jack on panel.

PHYSICAL CHARACTERISTICS:

All components of the Super-Skyrider, Model SX-28A are mounted on a rugged steel chassis. Copper plated steel panel has etched black leatherette finish. Panel and chassis are joined by heavy side members. Cabinet is finished in gray wrinkle lacquer with chromium trim. Openings provided for cooling and ventilation.

DIMENSIONS:

Cabinet is 20½" long by 10" high by 14¾" deep. Panel is 19" long by 8¾" high. Clearance needed for relay rack mounting, 17⅞" long by 8¾" high by 14¾" deep.

WEIGHT:

Model SX-28A—75 pounds.
Packed for shipment—87 pounds.

FIFTEEN TUBES:

1-6AB7	1st r.f. Amplifier
1-6SK7	2nd r.f. Amplifier
1-6SA7	Mixer
1-6SA7	H.f. Oscillator
1-6I7	1st i.f. Amplifier Noise Limiter
1-6SK7	2nd i.f. Amplifier
1-6B8	A.v.c. Amplifier
1-6B8	2nd Detector and S Meter Tube
1-6AB7	Noise Amplifier
1-6H6	Noise Rectifier
1-6J5	Beat Oscillator
1-6SC7	1st Audio Amplifier
2-6V6GT	Push-Pull Output Amplifiers
1-5Z3	Rectifier

hallicrafters RADIO





THE SUPER DEFIANT

*Every worthwhile feature
at a moderate price . . .*

The SUPER DEFIANT has long been one of Hallicrafters most popular models. Incorporating every important feature for superb communications receiver performance, the Model SX-25 has achieved true economy without compromising quality.

The outbreak of war with its sudden demand for military communications receivers found Hallicrafters already in mass production of the Model SX-25 for amateur use. Production was immediately stepped up and tremendous quantities of these receivers were put into military communications work. Many minor modifications and improvements in quality of components to meet rigid military requirements were made but the basic design remains unchanged. The rugged construction, fine workmanship, and superb performance which proved so valuable in military service will continue to feature the Hallicrafters Model SX-25.

hallicrafters RADIO

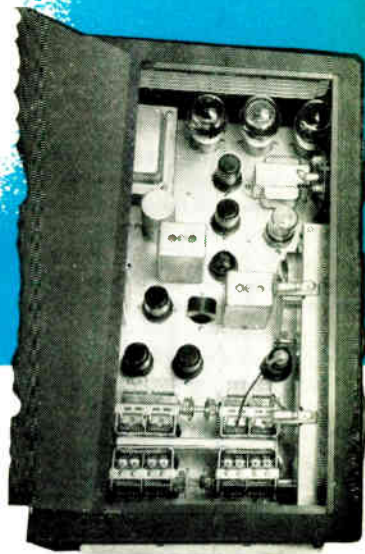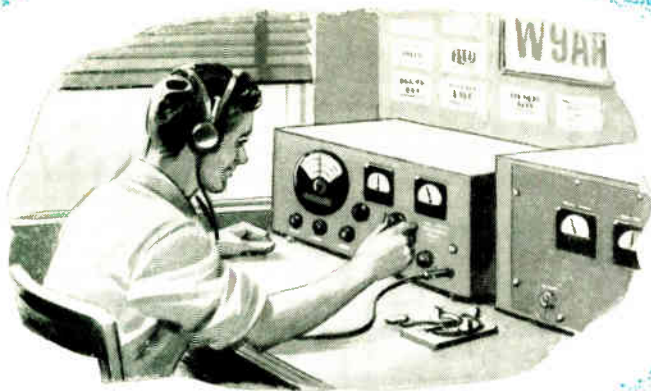

MODEL SX-25

FEATURES

1. Frequency range 545 kc. to 42 Mc., continuous in 4 bands.
2. Main tuning dial accurately calibrated in megacycles.
3. Separate calibrated bandspread dial.
4. Two stages of radio frequency amplification.
5. Beat frequency oscillator, pitch variable from front panel.
6. A.v.c. switch.
7. B.f.o. switch.
8. Send-receive switch.
9. Automatic noise limiter.
10. Separate r.f. and a.f. gain controls.
11. Provision for battery or external power supply operation.
12. Push-pull 8-watt output stage.
13. High-low tone switch.
14. Provision for break-in operation.
15. 500 or 5000 ohm output.
16. Six position i.f. and crystal selectivity switch.
17. Crystal phasing control.
18. "S" meter calibrated in S units and db. above S9.
19. Oscillator compensated for frequency drift.
20. Inertia flywheel tuning on bandspread dial.

CONTROLS:

R.F. GAIN; BAND SWITCH; SELECTIVITY; MAIN TUNING; TONE HIGH-LOW; XTAL PHASING; BANDSPREAD; A.N.L. ON/OFF; A.F. GAIN; PITCH CONTROL; B.F.O. ON/OFF; SEND-REC.; "S" meter adjustment on rear of chassis.

EXTERNAL CONNECTIONS:

Antenna terminals arranged for doublet or single wire antenna. Speaker output for either 500 or 5000 ohms. Standby terminals for external control of receiver in conjunction with transmitter. Line card and plug. Special socket, normally shorted by octal plug, for use of external power supply or batteries. All connections are mounted on rear of chassis except headphone jack on panel.

PHYSICAL CHARACTERISTICS:

The SUPER-DEFIANT, Model SX-25 is mounted in a steel cabinet finished in gray wrinkle lacquer. Ornamental metal grills in either end provide ventilation. Chassis is cadmium plated steel.

DIMENSIONS:

Receiver cabinet only—19½" long by 9½" high by 11⅞" deep.

WEIGHT:

Model SX-25—38 pounds.
Packed for shipment—46 pounds.

TWELVE TUBES:

1-6SK7	1st r.f. Amplifier
1-6SK7	2nd r.f. Amplifier
1-6K8	1st Detector-Mixer, h.f. Oscillator
1-6SK7	1st i.f. Amplifier
1-6SK7	2nd i.f. Amplifier
1-6SQ7	2nd Detector, a.v.c. 1st Audio Amplifier
1-6SQ7	Phase Inverter
2-6F6	Push-pull Audio Output Stage
1-6H6	Automatic Noise Limiter
1-6J5GT	Beat Frequency Oscillator
1-80	Rectifier

Compact • Reliable


TOP PERFORMANCE IN THE LOW PRICE FIELD

The Hallicrafters SKY CHAMPION, Model S-20R is probably the greatest value ever offered in communications receivers. Its simplicity of design, excellent workmanship, and sturdy construction insure long, satisfactory service and make traditional Hallicrafters performance available to the purchaser of an economical receiver.

In common with its larger brothers, the Model S-20R has a distinguished war record, and like them, it has been strengthened and improved to cope with military requirements. Large quantities have been produced for the armed forces and have been used for training and communications purposes where performance was important; but the use of a complicated receiver was not justified. It is a compact, reliable receiver offering top performance in the low price field.

FEATURES

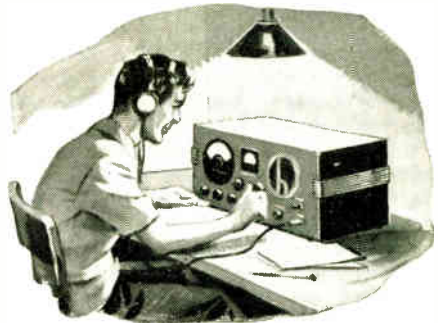1. Frequency range 550 kc. to 43 Mc., continuous in four bands.
2. Main tuning dial accurately calibrated in megacycles.
3. Separate electrical bandspread dial.
4. Beat frequency oscillator, pitch variable from front panel.
5. A.v.c. switch.
6. B.f.o. switch.
7. Send-receive switch.
8. Automatic noise limiter.
9. Separate r.f. and a.f. gain controls.
10. Provision for battery or external power supply operation.
11. 2½-watt output stage.
12. Three-position tone control.
13. Provision for break-in operation.
14. Provision for external S meter.
15. Inertia flywheel tuning on bandspread dial.
16. Internal rubber shock mounted 5" dynamic speaker.



CONTROLS:

R.F. GAIN; BAND SWITCH; AUDIO GAIN; MAIN TUNING; A.V.C. ON/OFF; B.F.O. ON/OFF; BAND-SPREAD TUNING; A.N.L. ON/OFF; TONE A.C. OFF/HIGH/MED./LOW; PITCH CONTROL; SEND-REC.

EXTERNAL CONNECTIONS:

Antenna terminals for doublet or single wire antenna. Line cord and plug. Special socket for operation from external power supply. All connections except headphone jack are mounted on rear of chassis.

PHYSICAL CHARACTERISTICS:

Components of the Model S-20R are mounted on a strong cadmium-plated steel chassis. Cabinet is of steel finished in machine tool gray enamel with chrome trim. Internal five-inch dynamic speaker is held in rubber stock mounts.

DIMENSIONS:

Cabinet only—18½" long by 8½" high by 9¾" deep.

WEIGHT:


Packed for shipment—32 pounds.

NINE TUBES:

1—6SK7	R.f. Amplifier
1—6K8	1st Detector-Mixer, h.f. Oscillator
1—6SK7	1st i.f. Amplifier
1—6SK7	2nd i.f. Amplifier
1—6SQ7	2nd Detector, a.v.c. and 1st Audio Amplifier
1—6F6G	2nd Audio Amplifier
1—6H6	Automatic Noise Limiter
1—6J5GT	Beat Frequency Oscillator
1—80	Rectifier

THE SKY CHAMPION MODEL S-20R



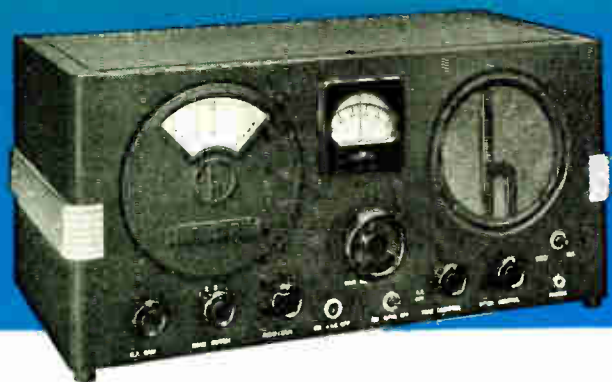

THE SKYRIDER MARINE MODEL S-22R

AN EFFICIENT MARINE RECEIVER AT A MODERATE PRICE

The Hallicrafters Model S-22R is specifically designed for marine service covering frequencies from 110 kc. to 18 Mc. Maximum convenience is assured through the use of a directly calibrated main tuning dial and the division of bands so that calling and working frequencies lie in the same band. An efficient mechanical bandspread with separate dial provides for easy logging. Excellent image rejection on the higher frequencies is achieved by the use of a 1600 kc. i.f. amplifier.

Special precautions have been taken to protect the Model S-22R against the hazards of salt sea atmosphere. Mica trimmer condensers are treated to maintain their adjustment, transformers are impregnated, and the chassis is nickel plated.

Many boats are provided with 110 volts d.c. and the SkyRider Marine is designed for a.c./d.c. operation. This feature makes the Model S-22R valuable for use ashore where a high performance receiver to operate from a d.c. line is desired.



FEATURES

1. Frequency range 110 kc. to 18 Mc. in four bands.
2. Main tuning dial accurately calibrated in megacycles.
3. Mechanical bandspread with separate dial.
4. Beat frequency oscillator, pitch variable from front panel.
5. A.v.c. switch.
6. B.f.a. switch.
7. Send-receive switch.
8. Separate r.f. and a.f. gain controls.
9. Variable tone control.
10. Inertia flywheel tuning.
11. A.c./d.c. operation.
12. 1600 kc. i.f. for maximum image rejection.
13. Internal rubber shock mounted 5" PM speaker.

CONTROLS:

R.F. GAIN; BAND SWITCH; AUDIO GAIN; A.V.C. ON/OFF; MAIN TUNING; B.F.O. ON/OFF; TONE CONTROL; PITCH CONTROL; SEND-REC.

EXTERNAL CONNECTIONS:

Antenna terminals arranged for doublet or single wire. Line cord and plug. Phone jack on panel.

PHYSICAL CHARACTERISTICS:

The Model S-22R is mounted in a steel cabinet finished in black wrinkle lacquer with chrome trim. Steel chassis is nickel-plated. Five-inch PM dynamic speaker is built in.

DIMENSIONS:

Cabinet only—18½" long by 8½" high by 9⅞" deep.

WEIGHT:

Packed for shipment—31 pounds.

EIGHT TUBES:

- 1—6SK7 R.f. Amplifier
- 1—6K8 1st Detector-Mixer, h.f. Oscillator
- 1—6SK7 1st i.f. Amplifier
- 1—6SK7 2nd i.f. Amplifier
- 1—6SQ7 2nd Detector, a.v.c., 1st a.f. Amplifier
- 1—25L6 2nd a.f. Amplifier
- 1—6J5 Beat Frequency Oscillator
- 1—25Z5 Rectifier



MODEL S-36A

FM • AM • CW


The new Hallicrafters a.m./f.m. receiver, Model S-36A, is designed for maximum performance on the very high frequencies. Using acorn tubes in the r.f. amplifier, first detector and high frequency oscillator circuits, the S-36A provides continuous frequency coverage from 27.8 to 143 megacycles. Either a limiter and discriminator for f.m. or a third i.f. amplifier, diode detector and noise limiter for a.m. may be switched into the circuit from the front

panel. A beat frequency oscillator is provided for the reception of c.w. telegraph signals. The S-36A incorporates a new 3-watt audio system with a response curve which is essentially flat from 40 to 15,000 cycles. All components are of the highest quality and the entire receiver is designed for service in any climate. Combining f.m., a.m., and c.w. telegraph reception in one superb unit, the S-36A provides the utmost in very-high-frequency reception.

hallicrafters RADIO

VHF VERSATILITY

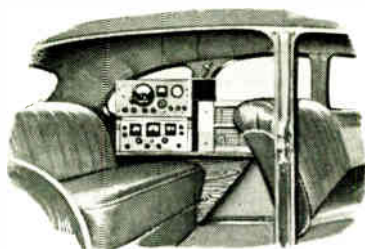Outstanding for Sensitivity—Stability—High Fidelity



FEATURES

1. Frequency range 27.8 Mc. to 143 Mc. continuous in three bands.
2. Main tuning dial accurately calibrated in megacycles.
3. Mechanical bandspread dial.
4. R.f. stage with acorn tube.
5. Beat frequency oscillator, pitch variable from panel.
6. A.v.c. switch.
7. B.f.o. switch.
- B. Send-receive switch.

9. Automatic noise limiter.
10. Separate r.f. and a.f. gain controls.
11. Push-pull high fidelity output stage.
12. 4-position tone control with bass boost.
13. Provision for break-in operation.
14. 500 or 5000 ohm output plus special balanced 600 ohm line.
15. Sharp-broad selectivity switch.
16. Dual purpose S and tuning meter.
17. Oscillator compensated for frequency drift.
18. Antenna compensator mounted on panel.
19. R.f. assembly easily removed for servicing.
20. Inertia flywheel tuning.
21. Hermetically sealed transformers and reactors.
22. All paper condensers oil impregnated and hermetically sealed.
23. Moisture proofed wiring.
24. F.m./o.m. switch.
25. Switch on chassis permits operation on 115 or 230 volts a.c.
26. Line fuse on panel.
27. Improved gear drive in dust proof housing.
28. "S" meter adjustable from front panel.

CONTROLS:

R.F. GAIN; A.V.C. ON/OFF; BAND SWITCH; ANTENNA; SEND-RECEIVE; SELECTIVITY; TONE; A.N.L. ON/OFF; TUNING; PITCH CONTROL; METER ADJUSTMENT; B.F.O. ON/OFF; A.M./F.M.; A.F. GAIN.

EXTERNAL CONNECTIONS:

Input terminals for single wire and doublet antennas. 500 ohm, balanced 600 ohm, and 5000 ohm terminals for speaker. Line cord and plug. Octal socket on rear of chassis permits operation from external power source such as batteries and makes provision for remote stand-by switch. This socket is normally shorted by octal plug. Line fuse is mounted on front panel.

PHYSICAL CHARACTERISTICS:

All components of the S-36A are mounted on a heavy steel chassis which is provided with special end plates for ease of maintenance. High frequency r.f. section is built in a separate chassis which may easily be removed for servicing. Cabinet is of steel finished in black wrinkle lacquer. Military type shock mounting is available if desired.

DIMENSIONS:

Model S-36A—19 $\frac{1}{4}$ " wide by 9 $\frac{1}{2}$ " high by 15 $\frac{3}{4}$ " deep.


Model S-36A with military type shock mounting—21 $\frac{1}{2}$ " wide by 11 $\frac{1}{4}$ " high by 15 $\frac{3}{4}$ " deep.


WEIGHT:

Packed for shipment—95 pounds.

FIFTEEN TUBES:

1—956	(Acorn) Radio Frequency Amplifier
1—954	(Acorn) Converter-Mixer
1—6AC7 or 1852	First i.f. Amplifier
1—6AB7 or 1853	Second i.f. Amplifier
1—6SK7	Third i.f. Amplifier
1—6H6	A.m. Detector and Automatic Noise Limiter
1—6AC7 or 1852	F.m. Limiter
1—6H6	F.m. Discriminator
1—6SL7GT	Audio Amplifier
1—VR150	Voltage Regulator
2—6V6GT	Power Audio Amplifier
1—5U4G	Rectifier
1—6J5	Beat Frequency Oscillator
1—955	(Acorn) High Frequency Oscillator

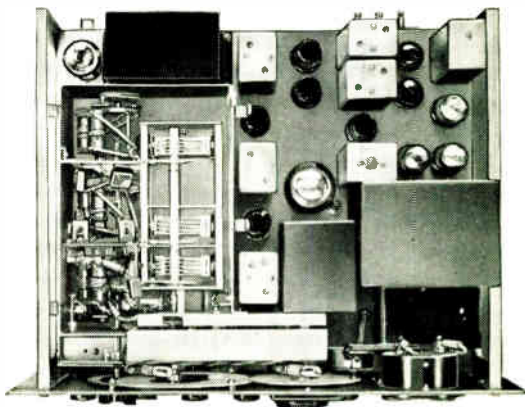

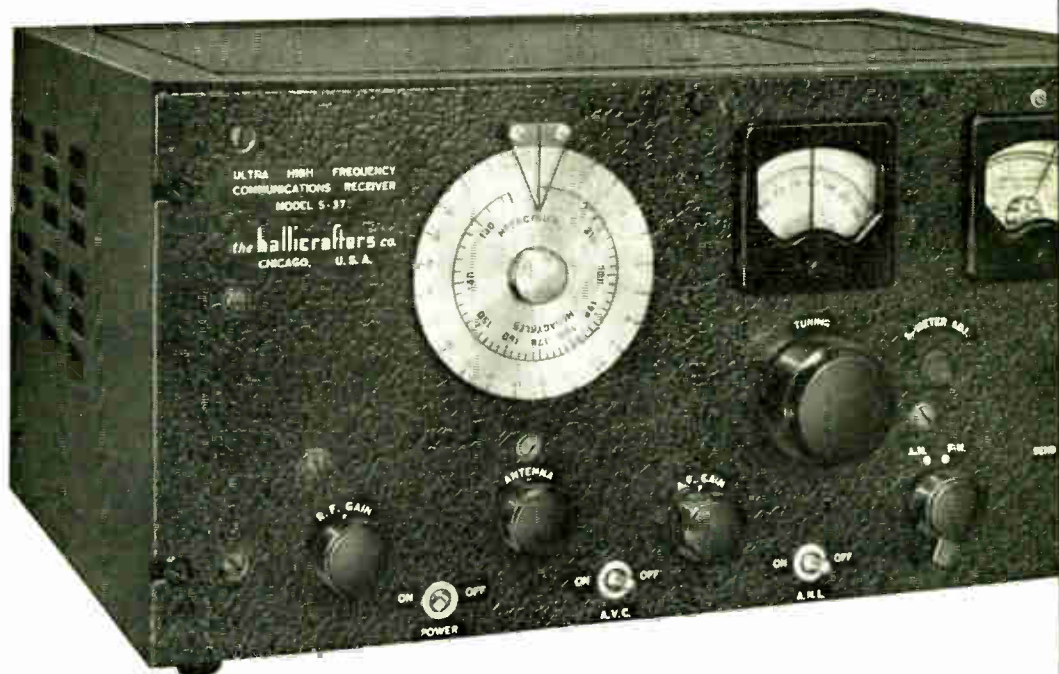


The Highest Frequency Range of Any General Coverage Commercial Type Receiver

The new Model S-37 has been designed to fill the need for very-high-frequency receiving equipment with the performance characteristics of Hallicrafters' top communications receivers and a frequency range extending above 200 Mc. Basically similar to the Model S-36A this new receiver incorporates the latest developments in


v.h.f. circuit design and provides sensitivity and selectivity in the range from 130 to 210 Mc. that is in every way comparable to the performance of fine communications receivers on the standard frequencies.

A new pre-loaded gear drive with separate bandsread dial provides ease of tuning and the entire range of the receiver is covered without band switching. Two r.f. stages are used and, in conjunction with an intermediate frequency of 18 Mc., assure an amazingly high ratio of image rejection. Hermetically sealed transformers and capacitors make the Model S-37 suitable for use in any climate.

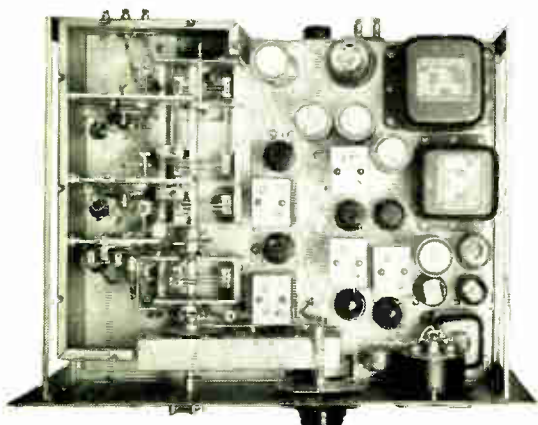This new receiver again emphasizes Hallicrafters' pre-eminence in the commercial production of v.h.f. equipment.



MODEL S-37 (FM · AM)

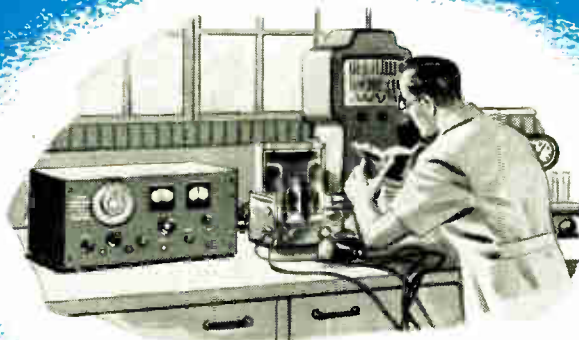

FEATURES

1. Frequency range continuous from 130 Mc. to 210 Mc.
2. Main tuning dial accurately calibrated in megacycles.
3. Mechanical bondspread dial.
4. Two r.f. stages with ocrn tubes.
5. A.v.c. switch.
6. Send-receive switch.
7. Automatic noise limiter.
8. Separate r.f. and a.f. gain controls.
9. Variable tone control.
10. Provision for break-in operation.
11. 500 or 5000 ohm output.
12. Dual purpose S and tuning meter.
13. Oscillator compensated for frequency drift.
14. Antenna compensator mounted on panel.
15. R.f. assembly easily removed for servicing.
16. Inertia flywheel tuning.
17. Hermetically sealed transformers and reactors.
18. All paper condensers oil impregnated and hermetically sealed.
19. Moisture-proof wiring.
20. F.m./a.m. switch.
21. Provision for operation on 115 or 230 volts a.c.
22. Line fuse on rear of chassis.
23. Improved gear drive in dust proof housing.
24. "S" meter adjustable from front of panel.
25. 18 Mc. i.f. for maximum image rejection.

CONTROLS:

R.F. GAIN; POWER ON/OFF; ANTENNA; A.V.C. ON/OFF; A.F. GAIN; A.N.L. ON/OFF; TUNING; S-METER ADJ.; AM/FM; SEND/REC; TONE.

EXTERNAL CONNECTIONS:

Input terminals for single wire and doublet antennas. 500 ohm, and 5000 ohm terminals for speaker. Line cord and plug. Octal socket on rear of chassis permits operation from external power source such as batteries and makes provision for remote stand-by switch. This socket is normally shorted by octal plug. Line fuse is mounted on rear of chassis.

PHYSICAL CHARACTERISTICS:

All components of the S-37 are mounted on a heavy steel chassis which is provided with special end plates for ease of maintenance. High frequency r.f. section is built in a separate chassis which may easily be removed for servicing. Cabinet is of steel finished in block wrinkle lacquer. Military type shock mounting is available if desired.

DIMENSIONS:

Model S-37—19¼" wide by 9½" high by 14-13/16" deep.

WEIGHT: Packed for shipment—95 pounds.

FOURTEEN TUBES:

- 2—954 (Acorn) Radio Frequency Amplifiers
- 1—954 (Acorn) Converter-Mixer
- 1—6AC7 or 1852 First i.f. Amplifier
- 1—6AB7 or 1853 Second i.f. Amplifier
- 1—6SK7 Third i.f. Amplifier
- 1—6H6 A.M. Detector and Automatic Noise Limiter
- 1—6AC7 or 1852 F.M. Limiter
- 1—6H6 F.M. Discriminator
- 1—6SC7 Audio Amplifier
- 1—VR150 Voltage Regulator
- 1—6V6GT Power Audio Amplifier
- 1—5U4G Rectifier
- 1—955 (Acorn) High Frequency Oscillator

hallicrafters RADIO

THE SKY RANGER

FINE



The new SKY RANGER is a 9-tube communications receiver which combines the utmost in convenience with a high order of performance.

Incorporating electrical bandspread, b.f.o. for c.w. reception, automatic noise limiter, and the standard controls found on good communications receivers, the light weight, high sensitivity and collapsible built-in antenna of the Sky Ranger make it an ideal portable receiver. It may be operated on either 115 volts a.c. or d.c. or on its own self-contained batteries. Frequency coverage is continuous from 540 kc. to 30.5 Mc. in 4 bands.

hallicrafters RADIO

MODEL S-39

PORTABLE COMMUNICATIONS RECEIVER MADE

FEATURES

1. Operates from its own self contained batteries or 115 volts a.c. or d.c.
2. Frequency range 540 kc. to 30.5 Mc. continuous in four bands.
3. Main tuning dial accurately calibrated in megacycles.
4. Separate bandspread dial.
5. R.f. stage used on all bands.
6. Beat frequency oscillator.
7. A.v.c. switch.
8. B.f.o. switch.
9. Send-receive switch.
10. Automatic noise limiter.
11. Separate r.f. and a.f. gain controls.
12. Collapsible built-in antenna.
13. Moisture-proof wiring.
14. Components impregnated for use in tropical climates.
15. Neon on/off indicator to prevent waste of batteries.
16. Permeability tuned r.f. and i.f. stages.
17. Plug-in type filter capacitors.
18. Completely rainproofed for outdoor use.

CONTROLS:

MAIN TUNING; BANDSPREAD TUNING; A.F. GAIN; R.F. GAIN; BAND SWITCH; POWER SWITCH; A.N.L. ON/OFF; A.V.C. ON/OFF; STANDBY ON/OFF; B.F.O. ON/OFF.

EXTERNAL CONNECTIONS:

Socket and plug are provided to connect doublet or single wire antenna. A.c./d.c. power cord is carried in a closed compartment at rear of set. Phone jack permits use of headphones and shuts off loud speaker automatically.

PHYSICAL CHARACTERISTICS:

The S-39 is housed in a strong steel cabinet finished in olive drab wrinkle lacquer. All components are mounted on a pressed steel chassis and the entire receiver is designed for hard service. Particular care

has been taken to make all components easily accessible for servicing.

DIMENSIONS:

Cabinet alone—7¼" high by 8¾" wide by 13½" deep.


Over all: 8½" high by 8¾" wide by 15¼" deep.

WEIGHT:


Model S-39—28 pounds, with batteries.

NINE TUBES:

1—1T4	R.f. Amplifier
1—1R5	Mixer
1—1P5GT	First i.f. Amplifier
1—1P5GT	Second i.f. Amplifier
1—1H5GT	Second Detector, First Audio Amplifier and a.v.c.
1—1H5GT	Beat Frequency Oscillator, Automatic Noise Limiter
1—3Q5GT	Second Audio Amplifier
1—3Z5GT	Rectifier

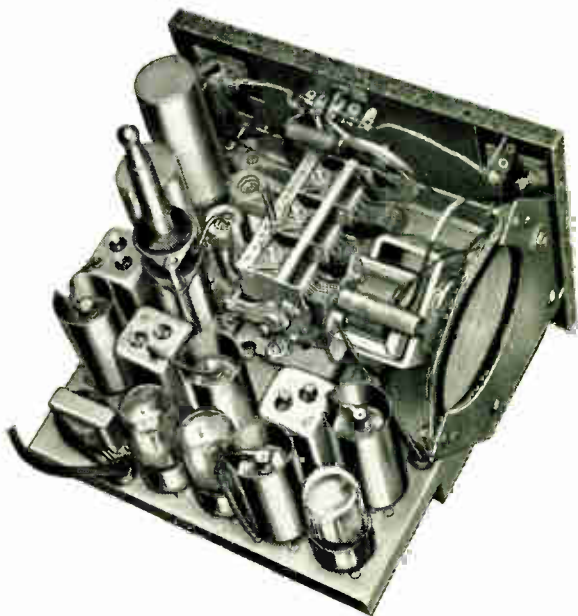


FM CONVERTERS . . .

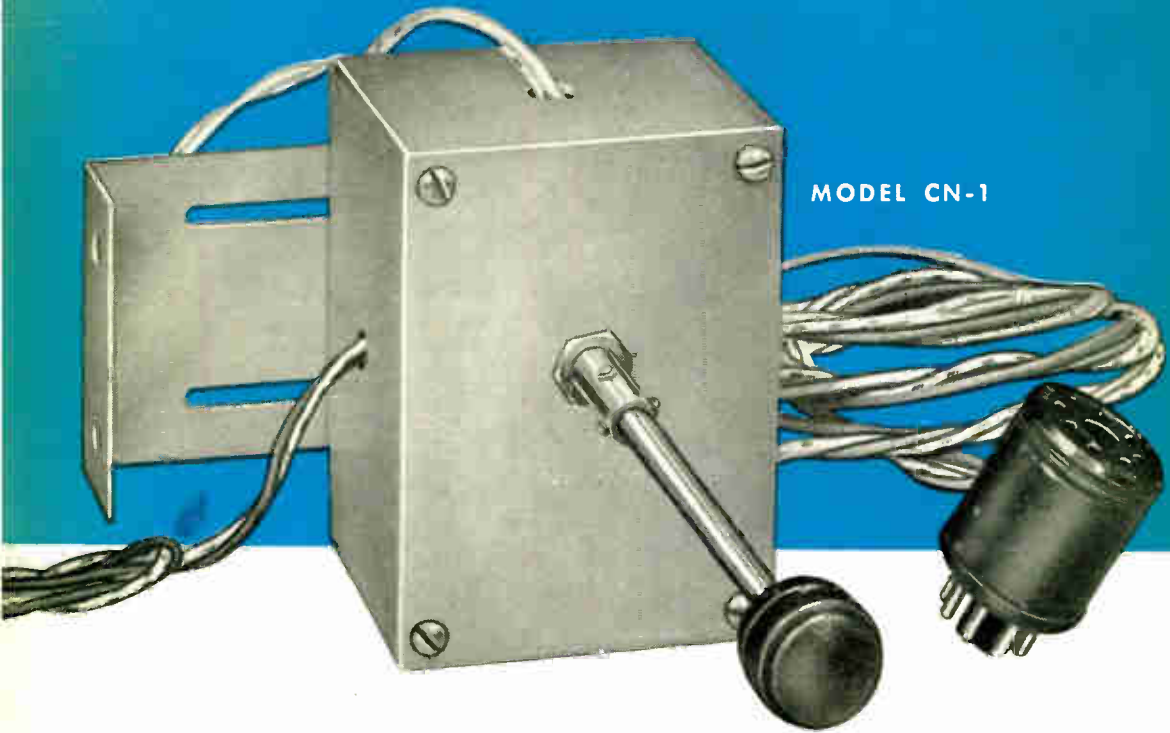

MODEL CN-1

Hallicrafters single tube converter Model CN-1 is housed in a small case suitable for mounting inside console type FM receiver as shown in inset at right. It is provided with universal mounting bracket, power take off plug and cable which is inserted under one of the final amplifier tubes of the receiver. Requires single hole in receiver panel to accommodate the four-position control switch. This switch selects any one of the three operating ranges or disconnects the converter, thus permitting normal operation of the receiver. All tuning is done with the regular receiver dial.

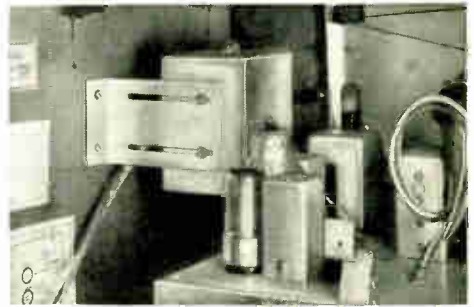

This model is recommended for use in areas having normally high signal strength. Uses a single type 7N7 dual triode as mixer-h.f. oscillator. Compact, inexpensive and easy to install.


hallicrafters RADIO

to make present FM sets work at 88-108 Mc.

Hallicrafters FM converters will prevent obsolescence of present FM receivers covering the 42-50 Mc. band when all FM broadcasting is transferred to the new band of 88-108 Mc. Operating on the principle of the double super heterodyne they are designed to feed into the antenna input circuit of any FM receiver.

To meet the requirements of widely different operating conditions three models are offered — a one-tube unit which can be installed inside the cabinet of practically any FM receiver, and three- and five-tube models, housed in attractive wood cabinets. These larger models incorporate their own power supplies and provide greater sensitivity and selectivity.

The three-tube and five-tube converters, Models CN-3 and CN-5, shown at right, are intended for use where maximum sensitivity and selectivity are required. In these models the receiver is set at 42 Mc. and tuning is done with the converter dial. Separate oscillator and mixer tubes are used. In addition the five-tube model has two tuned r.f. stages. Power supply for use on 115 volt 60 cycle current is incorporated.

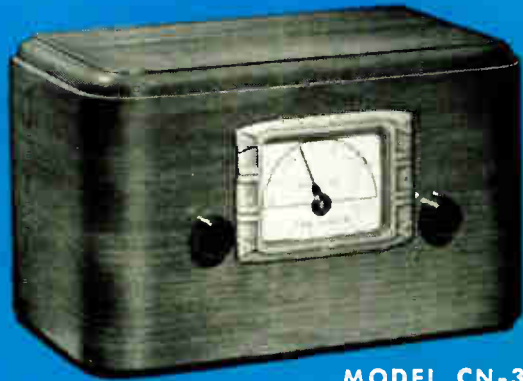

MODEL CN-3



MODEL CN-5



MODEL S-35

Panoramic receiver

The Hallicrafters PANORAMIC RECEIVER, Model S-35 is one of the newest and most interesting applications of the cathode-ray tube. This equipment, a special adapter mounted complete with an SX-28A receiver, makes possible the visual monitoring of whole sections of the frequency spectrum up to 100 kc. in width. All stations on the air in the portion of the spectrum being monitored are visible on the screen of the S-35. The station which is audible in the speaker or headphones always appears in the center of the oscilloscope screen. As the receiver is tuned the entire picture shifts across the screen.

The panoramic adapter unit consists of a chassis and panel of approximately the same dimensions as the SX-28A. Only one electrical connection is made between the adapter and the SX-28A and it does not interfere in any way with the normal operation of the receiver


NOTE: All of the following are in addition to the normal equipment of the standard Model SX-28A receiver.

CONTROLS:

R.F. GAIN; SWEEP WIDTH; A.V.C.; VERTICAL (gain); HORIZONTAL (gain); POWER ON/OFF.

EXTERNAL CONNECTIONS:

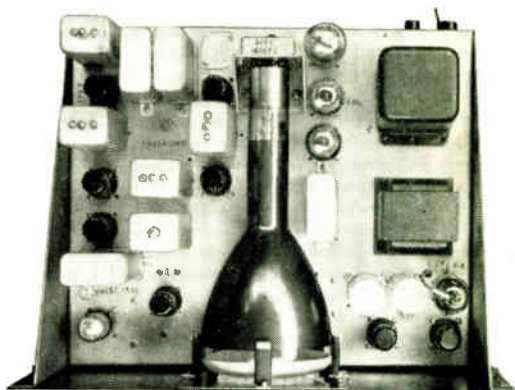Line cord and plug. Input lead from mixer stage of SX-28A.



PHYSICAL CHARACTERISTICS:

Panoramic adapter components are mounted on a steel chassis. Panel is of same dimensions as the SX-28A. Panel has etched black leatherette finish. Panel and chassis are joined by rugged end braces, and adapter unit and SX-28A are mounted together in sturdy metal cabinet finished in gray wrinkle lacquer.

DIMENSIONS:


Cabinet only, 20½" wide by 18⅝" high by 18" deep.

WEIGHT:

Model S-35—105 pounds.
Packed for shipment—166 pounds.

FOURTEEN TUBES:

- | | |
|-----------|-------------------------------------|
| 1—6SG7 | 455 kc. Input Amplifier |
| 1—6SA7 | 1st Detector |
| 1—6SK7 | 100 kc. i.f. Amplifier |
| 1—6SQ7 | 2nd Detector and Vertical Amplifier |
| 1—6SN7GT | Sawtooth Oscillator |
| 1—6SJ7 | Return Trace Blanking Tube |
| 1—6AC7 | Reactance Modulator |
| 1—6J5 | R.f. Oscillator |
| 1—6SC7 | Horizontal Amplifier |
| 1—2X2/879 | High Voltage Rectifier |
| 1—80 | Low Voltage Rectifier |
| 1—VR105 | Voltage Regulator |
| 1—VR150 | Voltage Regulator |
| 1—5AP1 | Cathode-ray Tube |

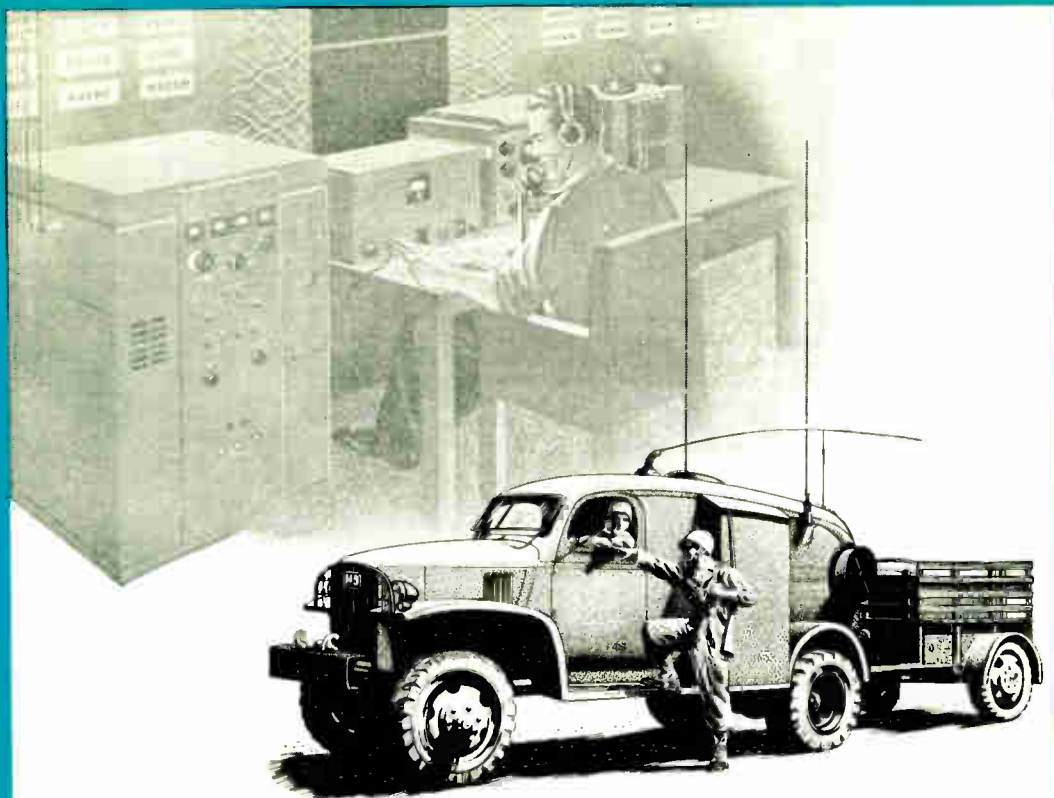

**Home from the wars
. . . . ready for peace**

MODEL HT-4E *"The Voice of Victory"*

hallicrafters RADIO

MODEL HT-4E

Telephone and Telegraph Transmitter



Hallicrafters' Model HT-4E transmitter has the most distinguished war record of any piece of radio communications equipment. First produced several years before Pearl Harbor and designed to meet the requirements of the most exacting amateur operators, the Model HT-4 was selected as the transmitter for the SCR-299 mobile radio station. This famous Signal Corps unit, built by Hallicrafters, has been acclaimed by high military authorities as "the best piece of radio equipment in any army."

The performance of this superb transmitter on every battle front and under the most adverse conditions has become one of the great legends of the war. Originally intended for use as a mobile unit over ranges of a few hundred miles, the SCR-299 so far surpassed expectations that it was soon operating in long distance service over thousands of miles. Commanding officers in the field diverted many of them to use as fixed headquarters stations. SCR-299's were set up as permanent broadcast transmitters in the far corners of the earth, and, dismounted from their trucks, they have been flown into the most remote outposts,

there to establish vital communications. All of these outstanding accomplishments were made possible by the sterling performance and rugged construction of the HT-4 and its successors.

Radio operators who were acquainted with the pre-war Model HT-4 are not surprised at its wartime achievements but they will be more than pleased with the many refinements and conveniences now available in the new Model HT-4E. Like other Hallicrafters products, this transmitter has undergone a continuous series of modifications and improvements to cope with the hazards of war and most of these refinements will prove as valuable to the amateur operator as they have to the Signal Corps. Among these wartime changes are: adoption of vacuum padding capacitors for low frequency operation, redesign of exciter tuning units to permit v.f.o. as well as crystal-controlled operation, addition of guide channels to make the insertion of tuning units easy and positive, addition of a remote control relay to switch from phone to c.w. and vice-versa, use of a side-tone oscillator in the speech amplifier to permit


monitoring of c.w. transmissions, addition of locking rings to hold tubes firmly in position, slight redesign of cabinet for greater rigidity, and many others.

Refined and strengthened, battle tested under every conceivable hardship, and built by the thousands for service on every continent, the Hallicrafters HT-4E is ready for the reopening of amateur radio.

With the return of peace, this high-power transmitter again takes its place in the leading amateur stations and will once more be heard around the world. The proud owner of a new Hallicrafters HT-4E can rest secure in the knowledge that he has "the best piece of radio equipment" in any amateur station.

FEATURES

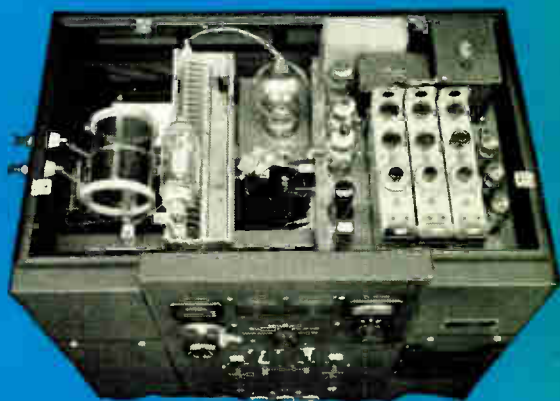1. Coils available for frequency range 1.5 Mc. to 18 Mc.
2. Power output 450 watts c.w., 325 watts phone (continuous operation).
3. Oscillator and buffer stages may be pre-tuned for any three operating frequencies and selected by a panel switch.
4. High level class B modulation
5. Plug-in pre-tuned r.f. exciter units.
6. Transmitter may be remotely controlled and keyed from speech amplifier.
7. Crystal or v.f.o. operation.
8. All operating controls on front panel.
9. Phone-c.w. operation controlled by single switch.
10. Break-in operation provided for.
11. Metering of all exciter stages and power amplifier grid current through meter switching.
12. All components plainly identified.
13. Voltage regulated oscillator power supply.
14. Optimum LC ratio on all bands due to plug-in vacuum padding condenser.
15. Heavy duty components used throughout.
16. Compact, unit style construction for maximum efficiency.
17. Filament voltage adjustment.
18. Modulator bias adjustment.
19. Filament power switch.
20. Exciter power switch.
21. Plate power switch.
22. High voltage protect switch.
23. Overload reset button.
24. Phone-c.w. switch.
25. Four power supplies.
26. Dual overload relays in high voltage supply.
27. Phone-c.w. relay.
28. Plate power relay.
29. Filament voltmeter on power amplifier.
30. Power amplifier plate current meter.
31. All fuses on front panel.
32. Dial lock on power amplifier tuning.
33. Guides for easy insertion of r.f. exciter units.
34. Tuning chart pocket on panel.
35. Overmodulation limiter on speech amplifier.
36. Modulator plate meter in speech unit for monitoring.
37. Sidetone oscillator (keying monitor).



hallicrafters RADIO

199

CONTROLS:

PLATE TUNING; EXCITATION METER SWITCH; BAND SWITCH; CW/PHONE; OVERLOAD RESET; FILAMENT POWER; EXCITER PLATE POWER; HIGH VOLTAGE PROTECT; PLATE POWER; FILAMENT VOLTAGE MODULATOR BIAS. On speech amplifier; GAIN; MOD. LIMITER; SIDETONE ON/OFF; TRANS. ON TRANS. OFF.

Note: Three tuning units may be plugged into exciter unit at one time. Each unit has controls for OSCILLATOR, DOUB., and INT. AMP. These are pre-tuned and the desired channel is selected by the BANDSWITCH.

METERS:

P.A. PLATE; EXCITATION METER; FIL. VOLTAGE; MODULATOR PLATE METER (on speech amplifier.)

EXTERNAL CONNECTIONS:

A.c. plug and cord, antenna terminals, socket for speech amplifier input and power; key and microphone inputs on speech amplifier panel.

PHYSICAL CHARACTERISTICS:

All components of the HT-4E are mounted on heavy steel chassis, finished in gray lacquer. Cabinet is of

heavy gauge steel, finished in black wrinkle. Speech amplifier is in its own table model cabinet, finished in black wrinkle.

DIMENSIONS:

Model HT-4E overall: 32 $\frac{3}{8}$ " wide by 39 $\frac{7}{8}$ " high by 21 $\frac{3}{8}$ " deep.



WEIGHTS:

Model HT-4E: 412 pounds.
Packed for shipment, 500 pounds.

TWENTY-THREE TUBES:

1—6V6GT	Crystal or v.f.o. Oscillator
1—6L6	Intermediate Amplifier
2—807	Buffer Amplifiers
1—250TH	R.f. Power Amplifier
3—VR150	Voltage Regulators
2—5Z3	Rectifiers
2—100TH	Class B Modulators
2—2A3	Class B Drivers
2—866	High Voltage Rectifiers
1—6SQ7	Microphone Amplifier
1—6J5	Speech Amplifier
1—6SN7GT	Phase Inverter
1—6SN7GT	Push-pull Output
1—6SR7	Modulation Limiter
1—6SN7GT	Sidetone Generator
1—80	Speech Amplifier Power Supply Rectifier

**SPEECH AMPLIFIER
MODEL HT-5E**

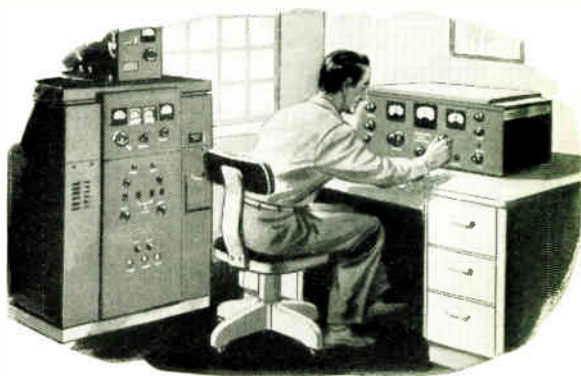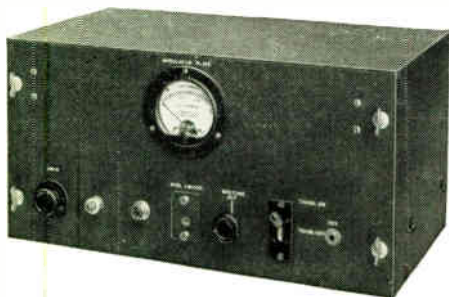

"With the return of peace, this high-power transmitter again takes its place in the leading amateur stations and will once more be heard around the world. The proud owner of a new Hallicrafters HT-4E can rest secure in the knowledge that he has 'the best piece of radio equipment' in any amateur station."

hallicrafters RADIO

ANTENNA TUNING UNITS

The antenna tuning units shown on this page were designed for use with the Model HT-4E transmitter. With these two units the transmitter can be matched to any type or size of antenna with the maximum possible transfer of energy.

MODEL AT-2 ANTENNA TUNING UNIT

Designed for use with a two wire transmission line, this unit employs the well known pi-section network. Has heavy duty capacitors and ceramic insulated plug-in inductances and is equipped with an antenna changeover relay to permit the use of one antenna for transmitting and receiving.

DIMENSIONS:

Model AT-2 overall: 22 $\frac{3}{8}$ " wide by 9" high by 19 $\frac{1}{4}$ " deep.

WEIGHT:

Model AT-2: 33 pounds.
Packed for shipment: 39 pounds.

MODEL AT-3 ANTENNA TUNING UNIT

This unit which was used in recent versions of the SCR-299 represents an outstanding achievement in high-frequency design. Covering all frequencies between 1.5 and 18 Mc. without the use of plug-in inductances, the Model AT-3 will tune any single wire antenna from a fifteen foot whip to a long wire. This unit is ceramic insulated to withstand the high r.f. voltages which are generated when antennas are operated far below their fundamental frequencies and will prove invaluable to the operator who is compelled to use an antenna of inadequate size.

DIMENSIONS:


Model AT-3 overall: 10 $\frac{1}{4}$ " wide by 14 $\frac{1}{4}$ " high by 24" deep.

WEIGHT:

Model AT-3: 48 pounds.
Packed for shipment: 56 pounds.



AT-2

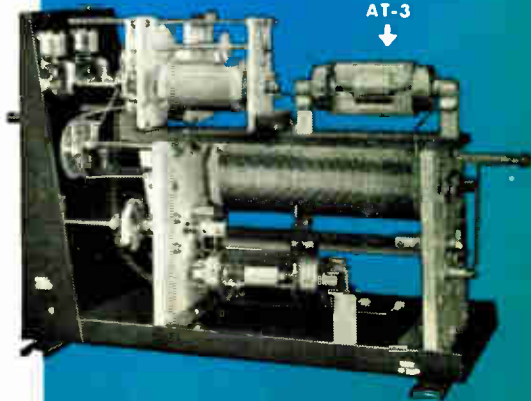
 ↑
AT-3
↓




MODEL HT-9

TELEPHONE AND TELEGRAPH TRANSMITTER

Hallicrafters' Model HT-9 is an ideal medium power transmitter. Designed for maximum flexibility and convenience, it is completely self-contained, requiring only a microphone or key, antenna, and source of 115-volt a.c. power to go on the air.


Five individual plug-in tuning units and crystals may be accommodated in the exciter section simultaneously. Band switching is easily accomplished by changing one coil in the final amplifier and selecting the desired exciter frequency by means of a panel switch. Exciter units are pre-tuned and the only additional operation needed is a slight adjustment of the final tank tuning capacitor.

Separate meters are provided for the power amplifier plate and grid circuits and a third meter may be switched into either the exciter or modulator cathode circuit. All controls are conveniently arranged on the panel and a safety interlock switch is

provided for protection against accidental shock when the cabinet is open.

FEATURES

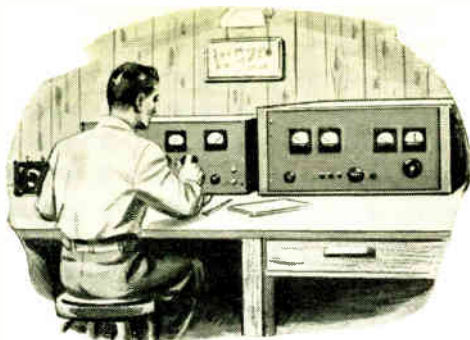1. Frequency range 1500 kc. to 18 Mc. and amateur 28 Mc. band.
2. Power output 100 watts on c.w., 75 watts on phone.
3. Five operating frequencies may be pre-set in the oscillator and buffer doubler stages and selected at will by means of the bandswitch.
4. 100 percent modulation with low distortion.
5. All operating controls on front panel.
6. Metering of cathode current of exciter or modulator, power amplifier grid, and power amplifier plate.
7. Input for any medium level, high impedance microphone.
8. Carrier hum more than 40 db. below 100% modulation.
9. Frequency response flat within 3 db. from 100 to 5000 cycles.
10. Antenna coil will match any resistive load from 10 to 600 ohms.
11. Line fuses mounted on rear of chassis.
12. Convenient table mounting.
13. Rugged construction and oversize components assure dependable operation.



CONTROLS:

AUDIO GAIN, (speech amplifier) OFF; CATHODE CURRENT EXC.-MOD.; PLATE PWR. ON OFF; FIL. PWR. ON/OFF; C.W.-PHONE; BAND SWITCH; TRANSMIT-STANDBY; PLATE TUNING.

METERS:

CATHODE CURRENT; P.A. GRID; P.A. PLATE.

EXTERNAL CONNECTIONS:

Antenna terminals. Terminal strip for key, antenna relay, and remote control of receiver. Line cord and plug. Two line fuses. Microphone input connector (on left end of cabinet). All connections except microphone are located on rear of chassis.

PHYSICAL CHARACTERISTICS:

The Model HT-9 is constructed on a heavy cadmium plated steel chassis. Cabinet is of steel finished in black wrinkle lacquer and is provided with heavy rubber mounting feet. Ventilating openings in top and sides assure adequate cooling. Interlock switch under lid cuts high voltage supply when cabinet is opened.

DIMENSIONS:

Model HT-9, overall clearance: 29 $\frac{1}{8}$ " wide by 12 $\frac{1}{2}$ " high by 20 $\frac{1}{2}$ " deep.

WEIGHT:

Model HT-9 transmitter: 120 pounds.
Packed for shipment. 160 pounds.


TUNING UNITS:

Final amplifier coils and exciter tuning units are available for the 3.5, 7, 14 and 28 Mc. amateur

bands. General coverage coils and units for all frequencies between 1.5 and 18 Mc. may be obtained on special order.

FOURTEEN TUBES:

1-6L6	Crystal Oscillator (used above 8 Mc. only)
1-6L6	Crystal Oscillator or Doubler
1-814	Final r.f. Amplifier
1-6SJ7	1st Speech Amplifier
1-6J5	2nd Speech Amplifier
4-6L6	Push-pull Parallel Modulator Stage
2-5Z3	Rectifiers
1-80	Rectifier
2-866	Rectifiers

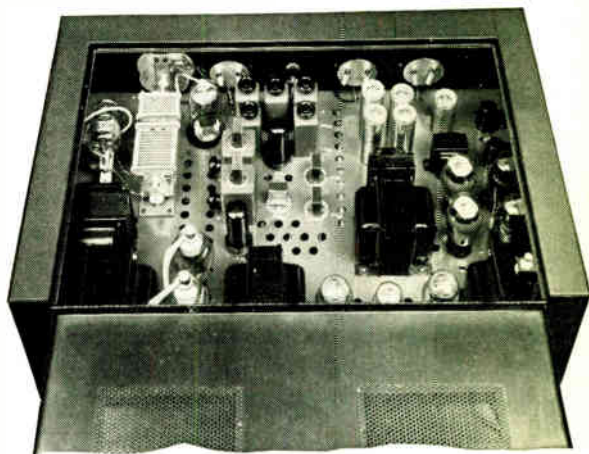

hallicrafters RADIO

MODEL HT-6

Telephone and Telegraph Transmitter

Filling a long felt need for a low cost high performance transmitter, the HT-6 offers most of the desirable features found in Hallicrafters' larger units. Complete sets of coils and crystals for any three bands may be plugged in, pre-tuned, and selected at will by means of a panel switch. All operating controls are conveniently arranged on the front panel. Metering of all circuits is provided by a switch which places the meter in the proper circuit. E.c.o. operation is available at any point in the amateur bands if desired.

A high quality audio system assures complete modulation, and is designed for use with any medium level microphone. Sockets on rear of chassis permit emergency operation from external power supplies.

FEATURES

1. Frequency range amateur bands from 3.5 Mc. to 60 Mc. General coverage, 1.5 to 54 Mc. on special order.
2. Normal power output 25 watts, phone or c.w.
3. Three operating frequencies may be pre-set in the transmitter and selected by means of the bandswitch.
4. 100 percent modulation with low distortion.
5. All operating controls on front panel.
6. Metering of all circuits through use of multi-range meter and switch.
7. Input for any medium level, high impedance microphone.

8. Carrier hum more than 40 db. below 100% modulation.
9. Frequency response flat within 3 db. between 125 and 5000 cycles.
10. Antenna coil to match all common resistive loads.
11. Line fuse mounted on rear of chassis.
12. Convenient table mounting.

CONTROLS:

AUDIO GAIN; METER SWITCH; CW/PLATE OFF/PHONE SWITCH; BAND SWITCH; PLATE CIRCUIT TUNING; ON/OFF; TRANSMIT/STANDBY.

EXTERNAL CONNECTIONS:

Antenna terminals. Line cord and plug. Microphone input socket. Remote control socket. Two external power supply sockets.

PHYSICAL CHARACTERISTICS:

All components of the HT-6 are mounted on a rugged gray lacquered steel chassis, and housed in an attractive steel cabinet finished in machine tool gray.

DIMENSIONS:

Model HT-9—20" wide by 9" high by 15" deep.

SHIPPING WEIGHT:

67 pounds.

TUNING UNITS:

Final amplifier coils and exciter tuning units are available for the 3.5, 7, 14, 28 and 50 Mc. amateur bands.

NINE TUBES:

- | | |
|--------|-------------------------------|
| 1-6J5 | Oscillator (50 Mc. band only) |
| 1-6L6 | Crystal or e.c.o. Oscillator |
| 1-807 | Power Amplifier |
| 1-6SQ7 | Speech Amplifier |
| 1-6SC7 | Phase Inverter |
| 2-6L6G | Modulators |
| 2-5Z3 | Rectifiers |



hallicrafters RADIO



THE ENSIGN MODEL HT-11

MARINE RADIOTELEPHONE

Safety - Convenience - Economy

The Hallicrafters ENSIGN, Model HT-11 marine radiotelephone provides the safety and convenience of radio communication at a price within the reach of all boat owners. Comprising a 12-watt crystal-controlled transmitter and a five-tube superheterodyne receiver mounted in a single small cabinet, the ENSIGN provides instantaneous ship-to-shore and ship-to-ship radiotelephone communication and excellent broadcast reception. Small enough to find room in boats of any size, the Model HT-11 is designed for complete reliability combined with utmost simplicity of operation.

TRANSMITTER FEATURES

1. Instant selection of any 3 transmitter frequencies, crystal-controlled.
2. Twelve watts output.
3. Transmitter may be used in the range 2000 kc. to 3000 kc.
4. Can be used with any length antenna.
5. Convenient "push to talk" operation.
6. Separate economical low drain power supply.
7. Rust and corrosion protected throughout.
8. Small size for ease of installation.
9. Can be supplied for use with any power source.
10. Panel mounted chart for recording of operating frequencies.

RECEIVER FEATURES

1. Two bands; broadcast 550 kc. to 1700 kc. and marine 2000 kc. to 3000 kc.
2. Receiver output may be switched to speaker or handset.
3. Built in moisture resistant PM speaker.
4. Illuminated, easily read tuning dial.

CONTROLS:

SPEAKER-PHONES; TRANSMITTER FREQUENCY; RECEIVER TUNING; BAND-SWITCH; VOLUME; TRANS. FILS. ON/OFF. Push-to-talk button on hand-set.

EXTERNAL CONNECTIONS:

Antenna terminal on top of cabinet. Power cable plugs into receptacle at left end of cabinet.

PHYSICAL CHARACTERISTICS:

Both transmitter and receiver components are mounted on a single nickel-plated chassis. Cabinet is finished in gray wrinkle lacquer. Speaker grill and controls are on front of cabinet and handset is permanently connected and carried in cradle at left end of cabinet.

POWER SUPPLY:

Power supplies are available for the following voltages: 6 volts d.c.; 12 volts d.c.; 32 volts d.c.; 115 volts d.c.; 115 volts a.c.

Power supplies are mounted separately and are connected to the Model HT-11 by a cable.

DIMENSIONS:

Cabinet only, 14 $\frac{1}{8}$ " wide by 9 $\frac{1}{4}$ " high by 9 $\frac{1}{4}$ " deep. Overall including handset on cradle 16 $\frac{1}{2}$ " wide by 10 $\frac{1}{8}$ " high by 10" deep.

D.c. Power Supply with Cover, 13" wide by 9 $\frac{1}{2}$ " high by 8 $\frac{3}{8}$ " deep.

A.c. Power Supply with Cover, 9 $\frac{1}{4}$ " wide by 7 $\frac{3}{8}$ " high by 7 $\frac{3}{8}$ " deep.

WEIGHT:

Model HT-11—31 pounds.

D.c. power supply—21 pounds.

A.c. power supply—21 pounds.

Add 3 pounds to any of above for shipping weight.

NINE TUBES:

Receiver:

- | | |
|--------|--|
| 1-6SK7 | R.f. Amplifier |
| 1-6K8 | 1st Detector, Mixer, h.f. Oscillator |
| 1-6SK7 | I.f. Amplifier |
| 1-6SQ7 | 2nd Detector, a.v.c., 1st a.f. Amplifier |
| 1-6K6G | 2nd a.f. Amplifier |

Transmitter

- | | |
|-------|-------------------------------|
| 1-6V6 | Crystal-controlled Oscillator |
| 1-807 | R.f. Amplifier Output Stage |
| 2-6V6 | Push-pull Modulator Stage |

THE COMMODORE

MODEL HT-14

Marine Radiotelephone



Dependable communications on the high seas

The new Hallicrafters COMMODORE, Model HT-14 Marine Radiotelephone incorporates every feature experience has shown desirable for ship-to-shore and ship-to-ship telephone service. A commercial adaptation of the famous Hallicrafters-built SCR-543, the HT-14 basic design has been literally "battle tested." With 6 crystal-controlled channels selected simultaneously in both transmitter and receiver and an output of 45 watts capable of 100 percent amplitude modulation, the HT-14 is an ideal medium power marine radiotelephone.

TRANSMITTER FEATURES

1. Instant selection of any 6 operating frequencies, crystal-controlled in both transmitter and receiver.
2. 45 watts output.
3. Frequency range, 1680 to 4450 kc.
4. Any antenna from 15 feet to a long wire may be used.
5. "Push-to-talk" switch on handset.
6. All components rust and corrosion resistant.
7. Metering of antenna current, final amplifier grid and plate, and modulator plate provided.
8. Entire unit easily removable for servicing.

9. May be operated from 115 volts a.c., 12, 32 or 115 volts d.c.
10. Chart mounted on panel for recording of operating frequencies.
11. All operating adjustments may be made at front of unit.

RECEIVER FEATURES

1. Two ranges; 1680 kc. to 2750 kc. and 2750 to 4450 kc., either crystal controlled or manually tuned.
2. Crystal receiver frequencies switched simultaneously with those of the transmitter.
3. Iron core, high-Q inductances used in the r.f., detector, and oscillator circuits provide maximum gain.
4. Exceptionally flat automatic volume control.
5. Newly developed diode noise limiter and audio filter circuit.
6. Receiver output may be used on handset or speaker.
7. 5" PM speaker with moisture resistant cone.

CONTROLS:

OPERATING CHANNEL SWITCH (6 positions); TRANSMITTER ANTENNA TUNING; RECEIVER TUNING; RECEIVER BAND SWITCH; A.F. GAIN; NOISE CONTROL; STATIC FILTER ON/OFF; SPEAKER ON/OFF; METER SWITCH; RECEIVER POWER ON/OFF; TRANSMITTER POWER ON/OFF; SEND-RECEIVE SWITCH (located on hand set, thumb operated).

METERS:

Antenna current ammeter is of the thermo-couple type and is flush mounted on the upper panel. Range, 0 to 2½ amperes. A dual range d.c. milliammeter 0-15-300 m.a. is mounted on the lower panel and can be connected to read final amplifier plate current, final amplifier grid current, and modulator plate current.

CONNECTIONS:

The antenna connector is mounted on a stand-off insulator on top of cabinet. Handset plugs into a receptacle at lower left corner of cabinet. The cable to the power supply unit plugs into a socket at lower right corner of cabinet. The power supply has a line cord for connection to the 115-volt a.c. supply line. The steel cabinet should be connected to a good ground.

ANTENNA REQUIREMENTS:

The Model HT-14 Radiotelephone is designed to operate with any antenna from a 15-foot whip to a long wire. For maximum transmitting range, the antenna should be large and as high above water as possible. With single-masted boats, an insulated forestay makes a satisfactory antenna. On boats having two masts, the antenna should be supported between the mast-heads and may consist of one or more wires.

INSTALLATION:

A universal type of shock mounting is furnished with the HT-14 permitting installation either on a bulk-head or table. Special screw type fasteners hold the HT-14 to the shock mounting and permit its easy removal for servicing.

PHYSICAL CHARACTERISTICS:

The HT-14 Radiotelephone is mounted in a steel cabinet. The cabinet is divided into 2 sections which are held together by heavy clamps. The upper section contains the radio frequency components of both transmitter and receiver. The lower section holds the speech amplifier and modulator. The loud speaker is mounted in the center of the lower panel and the handset is hung in a bracket at the left. All operating controls and switches are conveniently placed. The power supply unit is mounted in a separate cabinet.

POWER SUPPLY:

Power supply combinations for use on four different voltages are available. The 115-volt a.c. power supply unit is mounted in a separate cabinet. The 32-volt (or 110-volt) d.c. models include a 32-volt (or 110-volt) d.c. rotary converter which supplies power to the 115-volt a.c. power supply unit. The 12-volt d.c. model includes a 12-volt dynamotor type power supply unit, instead of the 115-volt a.c. power supply unit, in a cabinet of the same dimensions.

DIMENSIONS (overall):

Main cabinet. 23" high by 21" wide by 16¼" deep. Power supply cabinet. 9¾" high by 16" wide by 15" deep.

These measurements include protruding parts.

Note: Shock mounts add 2¾" to height or depth according to type of installation.

WEIGHTS:

Main cabinet—110 lbs.

115-volt a.c. Power Supply—67 lbs.

Combined shipping weight—275 lbs.

For d.c. operated models, add 55 lbs. to shipping weight.

TWENTY TUBES:

Transmitter

1—6L6G	Crystal Oscillator
2—807	R.f. Amplifier
1—12J5GT	Speech Amplifier
4—6L6G	Modulator

Receiver

1—6SK7-GT G	R.f. Amplifier
1—6SA7-GT G	First Detector
1—6SK7-GT G	I.f. Amplifier
1—6H6-GT G	2nd Detector, a.v.c. and Noise Limiter
1—6SK7GT G	First Audio Amplifier
1—6K6-GT G	Second Audio Amplifier
1—6J5-GT G	High Frequency Oscillator



Power Supply

1—80	Rectifier (for receiver)
4—5Z3	Rectifiers (for transmitter)



Ned Hockensmith

DESIGN

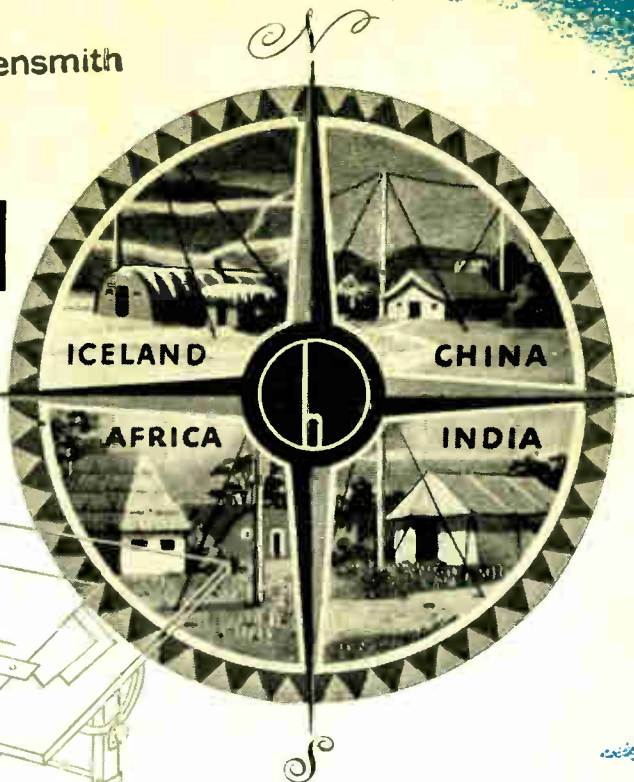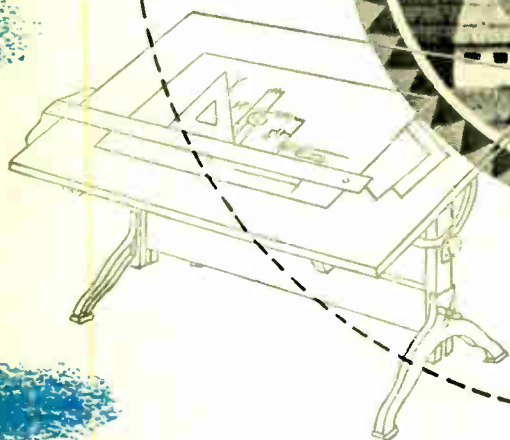

by remote control

The design of radio equipment that is offered by Hallicrafters is determined largely by thousands of hams who, from their remote control locations all over the world, have sent in advice and suggestions on new radio ideas to Hallicrafters engineering department.

Thousands and thousands of Hallicrafters pieces of high frequency radio equipment were used in the armed services. In a high percentage of cases this equipment was used by operators with practical amateur experience. From these qualified experts Hallicrafters has received hundreds of letters telling how Hallicrafters-built equipment stood up under the most vicious battle conditions. Even now Hallicrafters receives regularly many valuable suggestions from hams in the field and at home. From this rich deposit of "design by remote control" Hallicrafters equipment is developed—built to meet ham requirements, designed by the world's most exacting users—the radio amateurs.



hallicrafters RADIO

THE HALLICRAFTERS CO. MANUFACTURERS OF RADIO AND ELECTRONICS EQUIPMENT, CHICAGO 16, U. S. A.

Ned Hockensmith

