

electronics today

APRIL 1978

INTERNATIONAL

45p

200 W AMPLIFIER PROJECT



— FREE TANDY CATALOGUE —

MOST BRITISH SALES ONLY

PET HOME COMPUTER WHITE LINE FOLLOWER CASINGS SURVEY



... NEWS ... PROJECTS ... MICROPROCESSORS ... AUDIO ...


INTERNATIONAL POWERSLAVE 200 watt AMPLIFIER

POWERTRAN

COMPLETE KIT AS FEATURED IN THIS ISSUE OF E.T.I.

Super-Fi performance for studio / monitoring / hi-fi use with the inherent reliability and ruggedness for the most demanding group / disco applications.

- Features
- ★ over 200W rms continuous from each of 2 totally independent DC coupled amplifiers — over 800W peak power
 - ★ highly original fully complementary high linearity o/p stage utilizing the inherent symmetry of no less than 4 differential pairs!
 - ★ ultra low feedback (an incredibly low 14dB overall!) together with super high slewing rate (20 / μ S) banish ricochet effects and TID!
 - ★ distortion only 0.03% at FULL power 1KHz rising to only 0.07% at 10KHz (how many high power amplifier producers dare to quote at this frequency?)
 - ★ independent stabilized power supplies driven by custom designed TOROIDAL transformers
 - ★ inherent reliability — monster heat sinks for cool running at the hottest venues — electronic open and short circuit protection — 4 rugged power transistors/amplifier — each 250W rating
 - ★ professional quality — metal oxide resistors, cermet adjusters, fibre glass boards, sturdy 19" rack mounting cabinet complete with sleeve and feet for free standing work too
 - ★ easy to build — plenty of working space with ready access to all components, minimal wiring, extensive instructions suitable for both experienced constructors and newcomers to electronics — can be purchased one channel at a time
 - ★ value for money — quality and performance comparable with ready-built amplifiers costing over £600!

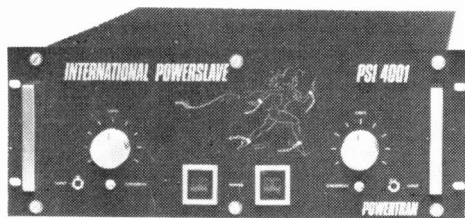

PSI4001 SLAVE MODEL

OVER 800W
PEAK POWER!



PSI4002 STUDIO MODEL

Pack	Price
1. Fibre glass printed circuit board for power amp	£4.20
2. Set of capacitors, metal oxide resistors, thermistor, cermet pre-sets for power amp	£6.40
3. Set of semiconductors for power amp with mounting hardware, cooling tabs	£27.60
4. Pair of monster black drilled heat sinks, transistor mounting bracket	£6.90
5. Toroidal transformer: Primary 0-117V-234V, Secondaries 42-0-42V, 0-15V, 0-15V, Electrostatic screen	£19.20
6. Set of all parts for stabilised power supply including fibre glass printed circuit board, mounting bracket, semiconductors, resistors, capacitors, etc.	£20.50
7A. Set of all parts for buffer/overdrive unit including fibre glass printed circuit board, semiconductors, resistors, capacitors, controls — required for PSI 4001 only	£3.80
7B. Set of parts for peak power meter including professional quality meter, fibre glass printed circuit board, components, control — required for PSI 4002 only	£11.50
8. Set of all miscellaneous parts including sockets, illum. mains switches, fuse holders, fuses, cut-outs, cable, etc.	£12.10
9. Cabinet including chassis, anodised silver on black panels, fixing parts, etc. Please state whether Slave of Studio model required	£27.50
10. Handbook £0.50 or free on request when ordering any of above packs. 2 each of packs 1-7 (A or B), 1 each 8, 9 and 10 are required for complete 200 + 200W professional amplifier.	
Total cost of individually purchased packs	PSI 4001 £216.80 PSI 4002 £232.20

Transistors used in this kit

2N5401	£0.40
2N5832	£0.40
2N6052	£2.80
2N6059	£2.40
BC182L	£0.10
BC212L	£0.12
BD419	£0.70
BD420	£0.75
BF460	£0.60
BF463	£0.65
BRF41	£0.30
BRF81	£0.30
MJ15003	£3.80
MJ15004	£4.10

SPECIAL OFFER PRICE for

Complete PSI4001 Kit
£205.00 + VAT

Complete PSI4002 Kit
£220.00 + VAT

MANY MORE KITS ALSO AVAILABLE — ASK FOR OUR FREE CATALOGUE

Amplifiers (20-200W), Tuners, Cassette Deck, Quadraphonics, etc., etc.



De Luxe Linsley-Hood 75w Amplifier

20 + 20w AMPLIFIER COMPLETE KIT ONLY

Based on P.W. TEXAN **£33.10 + VAT**

30w VERSION (T30+30) ONLY **£38.40 + VAT**

75 + 75w AMPLIFIER
COMPLETE KIT ONLY **£99.30 + VAT**

T20 + 20 AMPLIFIER



PRICE STABILITY: Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until May 30th, 1978 if ETI April, 1978 issue is mentioned with your order. Errors and VAT rate changes excluded.

U.K. ORDERS: Subject to 12½% surcharge for VAT (i.e. add ½ to the price). No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only), add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect your kit from the factory, call at Sales Counter (at rear of factory) Open 9 a.m. - 4.30 p.m. Monday - Thursday.

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!


POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

electronics today

APRIL 1978 VOL 7 NO 4 INTERNATIONAL

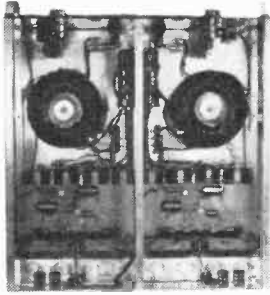

Powerful stuff P.43

FEATURES


COMMODORE PET COMPUTER	13	How house-trained?
OP AMPS PART 3	29	Tim Orr explains
DIGITAL ELECTRONICS PART 7	38	The way into digital mysteries
READER SURVEY	46	We need your help
PROJECT CASINGS SURVEY	67	Now where do you put it?
TECH-TIPS	77	Three pages of your ideas

PROJECTS

WHITE LINE FOLLOWER	23	Put some 'go' into models
GAS MONITOR	32	Sniff out trouble
200W AUDIO AMPLIFIER	43	Power <i>and</i> quality!
RAIN ALARM	62	Don't be a drip!

NEWS

NEWS DIGEST	7	Who does what and where
DATA SHEET	57	Gas sensor examined
MICROFILE	73	Board with keys?
ELECTRONICS TOMORROW	83	Motorola have ...

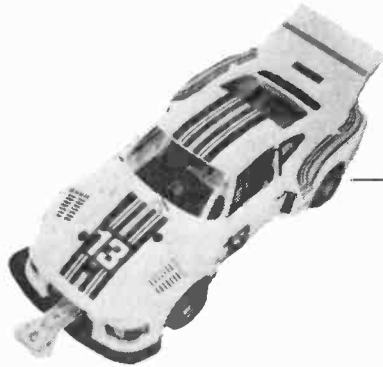

Porsche show P.23

INFORMATION

ETIPRINTS	9	PCBs the easy way
SUBSCRIPTIONS	11	Don't miss an issue
ETI BOOK SERVICE	37	Something for all
SPECIALS FROM ETI	45	A few leaves from our pages
ETI MAY PREVIEW	56	Next!
PANEL TRANSFERS	75	Stuck up? Why not?



Not a drop P.62

OFFERS

CBM 5R39	20	Count on this
ETI CLOCK	20	Time to get one
CHESS CHALLENGER	21	Check this price

INTERNATIONAL EDITIONS

AUSTRALIA	Collyn Rivers Publisher Les Bell Acting Editor
HOLLAND	Anton Kriegsman Editor-in-chief
CANADA	Steve Braidwood Editor Graham Wideman Assistant Editor
GERMANY	Udo Wittig Editor



ABC

EDITORIAL AND ADVERTISEMENT OFFICE

25-27 Oxford Street, London, W1R 1RF. Telephone 01-434 1781/2 Telex 8811896

Halvor W. Moorshead	Editor
Ron Harris B.Sc	Assistant Editor
Gary Evans	Projects Editor
John Koblanski	Project Development
Jim Perry	Specials Editor
William King	Editorial Assistant
Paul Edwards	Technical Drawings
Margaret Hewitt	Administration
Andrew Scott	Office Manager
Kim Hamlin, Tim Salmon, Brenda Goodwin	Reader Services
Mark Strathern (Manager), Tom Moloney	Advertising


PUBLISHED BY Modmags Ltd., 25-27 Oxford Street, London W1R 1RF
 DISTRIBUTED BY Argus Distribution Ltd. (British Isles)
 Gordon & Gotch Ltd. (Overseas)
 PRINTED BY QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

THE MOST COMPREHENSIVE RANGE OF TUNER MODULES EVER DISPLAYED

HF 7948 FRONT END

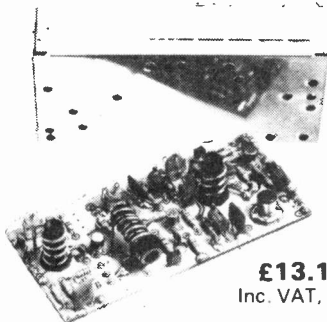

£13.12
Inc. VAT, P&P


TECHNICAL CHARACTERISTICS:

Output terminal for digital frequency meter;
Antenna impedance - 75 to 300 Ohms;
Frequency ranges 87.5 to 104 MHz or to 108 MHz; Sensitivity - 0.9 μ V 26dB signal to noise ratio \pm 75 kHz deviation; Intermodulation 80dB Image rejection - 60dB; Tuning voltage - 1V to 11V; Total gain - 33dB; Intermediate frequency - 10.7 MHz; Power supply voltage +15V; Power consumption 15mA; Dimensions 104 x 50 mm.

TECHNOLOGY:

Double sided epoxy printed circuit board with plated through holes; Dual gate effect transistors; Silvered coils.

FI 2846 IF AMP AND DECODER

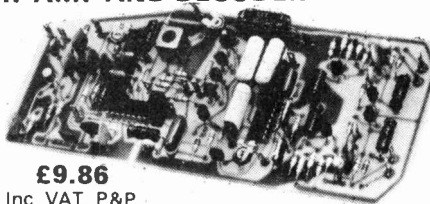

£9.86
Inc. VAT, P&P


TECHNICAL CHARACTERISTICS:

Intermediate frequency - 10.7MHz; IF Bandwidth - 280kHz; Signal to noise ratio 70dB with 1mV input; Distortion - mono 0.1%, stereo 0.3%; Sensitivity - 30 μ V up to the 3dB limit; Channel separation - 40dB at 1kHz; Pass band - 20 to 15,000Hz; Rejection at 38 kHz greater than 55dB; Am rejection - 45dB; De-emphasis - 50 to 75 μ s. Pilot capture at 19kHz +4%; Channel matching within less than 0.3dB; Output impedance - 100 Ohms; Output voltage - 500mV; Phase locked loop stereo decoder; Output for LED VU-meter; Null indicator; Outputs for AGC AFC and inter-station muting; Consumption - 55mA LEDs extinguished, 100mA LEDs illuminated; Power supply - 15V; Dimensions 195 x 76mm.

CIRCUIT TECHNOLOGY:

Epoxy printed circuit board; Monolithic integrated circuits, ceramic filter.

ALS 1500 STABILISED POWER SUPPLY

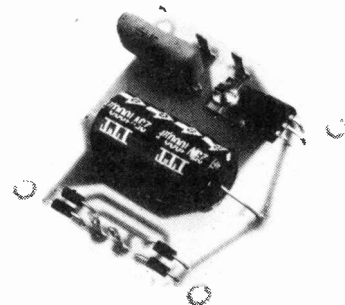

£2.53
Inc. VAT, P&P

TECHNICAL CHARACTERISTICS:


Output voltage - 15V; Max. output current - 500mA; Thermal coefficient less than 1mV/ $^{\circ}$ C; 15V power supply for modules HF 7948 and FI 2846; Supply protected against short circuit (power and current protection); Dimensions - 65 x 55mm.

TECHNOLOGY:


Double sided epoxy circuit board; Monolithic integrated circuit.

OPTOELECTRONIC OPTIONS

£8.06
Inc. VAT, P&P

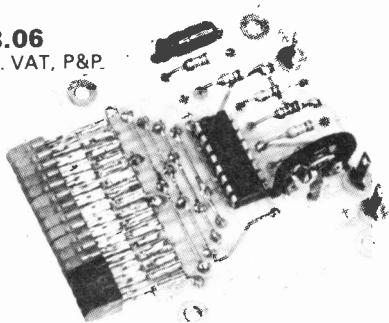


LED VU-METER
Station strength indicator

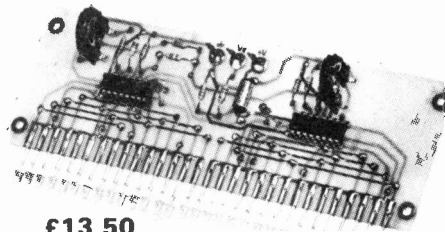


£13.50
Inc. VAT, P&P

ILLUMINATED POINTER
Station finder

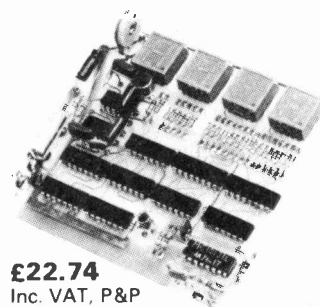


£22.74
Inc. VAT, P&P

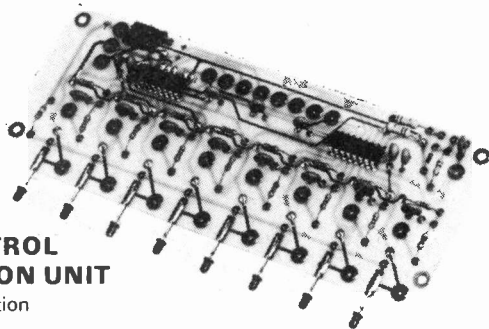FREQUENCY METER
Digital display of received station frequency



£8.77
Inc. VAT, P&P

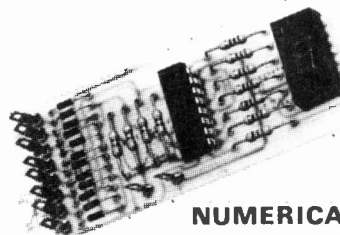**TOUCH CONTROL
PRE-SELECTION UNIT**
LED channel indication



£4.35
Inc. VAT, P&P

NUMERICAL DISPLAY
Pre-selected channel number

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT
Telephone: (0227) 63218 Telex: 965780

NEW SEASON'S COMPONENTS

BRIDGE RECTIFIERS

SILICON 1 amp	Order No.	Price
Type	BR1/50	£0.20
50V RMS	BR1/100	£0.22
100V RMS	BR1/200	£0.25
200V RMS	BR1/400	£0.36
400V RMS		
SILICON 2 amp	Order No.	Price
Type	BR2/50	£0.45
50V RMS	BR2/100	£0.48
100V RMS	BR2/200	£0.52
200V RMS	BR2/400	£0.58
400V RMS	BR2/1000	£0.68
1000V RMS		

BOOKS BY BABANI

Purchase books to the value of £5.00 from the list below and choose any 60p pak from this page FREE.

BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60p†
	Handbook of Tested Transistor Circuits	40p†
BP3	Engineers and Machinists Reference Tables	40p†
BP6	Radio & Electronic Colour Codes and Data Chart	
BP7		15p†
BP10	Modern Crystal and Transistor Set Circuits for Beginners	35p†
BP14	Second Book of Transistor Equivalents	95p†
BP15	Constructors Manual of Electronic Circuits for the Home	50p†
BP16	Handbook of Electronic Circuits for the Amateur Photographer	60p†
BP18	Boys and Beginners Book of Practical Radio and Electronics	60p†
BP22	79 Electronic Novelty Circuits	75p†
BP23	First Book of Practical Electronic Projects	75p†
BP24	52 Projects Using IC741 (or equivalents)	75p†
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85p†
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p†
BP29	Major Solid State Audio Hi-Fi Construction Projects	85p†
BP32	How to Build Your Own Metal & Treasure Locators	85p†
BP34	Practical Repair & Renovation of Colour TVs	95p†
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	95p†
BP36	50 Circuits Using Germanium, Silicon & Zener Diodes	75p†
BP37	50 Projects Using Relays, SCR's and TRIACS	1.10†
BP39	50 (FET) Field Effect Transistor Projects	1.25†
129	Universal Gram-motor Speed Indicator	8p†
160	Coil Design and Construction Manual	75p†
161	Radio, TV and Electronics Data Book	60p†
196	AF-RF Reactance -- Frequency Chart for Constructors	
202	Handbook of Integrated Circuits (ICs) Equivalents and Substitutes	75p†
205	First Book of Hi-Fi Loudspeaker Enclosures	75p†
213	Electronic Circuits for Model Railways	85p†
214	Audio Enthusiasts Handbook	85p†
216	Electronic Gadgets and Games	85p†
217	Solid State Power Supply Handbook	85p†
219	Solid State Novelty Projects	85p†
220	Build Your Own Solid State Hi-Fi and Audio Accessories	85p†
222	Solid State Short Wave Receivers for Beginners	95p†
223	50 Projects Using IC CA3130	95p†
224	50 CMOS IC Projects	95p†
225	A Practical Introduction to Digital IC's	95p†
226	How to Build Advanced Short Wave Receivers	1.20†
RCC	Resistor Colour Code Disc Calculator	10p†

BOOKS BY NEWNES

No. 229	Beginners Guide to Electronics	Price £2.25†
No. 230	Beginners Guide to Television	Price £2.25†
No. 231	Beginners Guide to Transistors	Price £2.25†
No. 233	Beginners Guide to Radio	Price £2.75†
No. 234	Beginners Guide to Colour Television	Price £2.25†
No. 235	Electronic Diagrams	Price £1.80†
No. 236	Electronic Components	Price £1.08†
No. 237	Printed Circuit Assembly	Price £1.08†
No. 238	Transistor Pocket Book	Price £3.90†
No. 225	110 Thyristor Projects Using SCRs & Triacs	Price £2.50†
No. 227	110 COS/MOS Digital IC Projects For the Home Constructor	Price £2.25†
No. 226	110 Operational Amplifier Projects for the Home Constructor	Price £2.50†
No. 242	Electronics Pocket Book	Price £3.75†
No. 239	30 Photoelectric Circuits & Systems	Price £1.80†

CASES

ALUMINIUM BOXES: Made from bright all., folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/4in	2 1/4in	1 1/2in	62p†
160	4in	4in	1 1/2in	62p†
161	4in	2 1/4in	1 1/2in	62p†
162	5 1/4in	4in	1 1/2in	74p†
163	4in	2 1/2in	2in	64p†
164	3in	2in	1in	44p†
165	7in	5in	2 1/2in	£1.04†
166	8in	6in	3in	£1.32†
167	6in	4in	2in	86p†

INSTRUMENT CASES. In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/4in	2in	£1.40†
156	11in	6in	3in	£1.80†
157	6in	4 1/4in	1 3/4in	£1.25†
158	6in	5 1/4in	2 1/2in	£1.60†

SPECIAL OFFER!

AGFA CASSETTES

STEREOCROM

307 C60 RRP £2.03	Our price £1.60
308 C90 RRP £2.54	Our price £1.80
309 C120 RRP £3.49	Our price £2.60

SFD - Super Ferro Dynamic

310 C60 RRP £1.48	Our price £1.00
311 C90 RRP £1.89	Our price £1.50
312 C120 RRP £2.62	Our price £2.00

DIODES SIL G.P.

300mW 40 PIV (min) SUB-MIN FULLY TESTED

Ideal for Organ builders

30 for 50p, 100 for £1.50, 500 for £5, 1,000 for £9

INTEGRATED CIRCUITS

CMOS

Type	Price	Type	Price	Type	Price
CD4000	£0.15	CD4022	£0.90	CD4046	£1.30
CD4001	£0.18	CD4023	£0.20	CD4047	£1.10
CD4002	£0.18	CD4024	£0.80	CD4049	£0.55
CD4006	£0.98	CD4025	£0.20	CD4050	£0.55
CD4007	£0.18	CD4026	£1.70	CD4054	£1.10
CD4008	£0.98	CD4027	£0.60	CD4055	£1.40
CD4009	£0.58	CD4028	£0.98	CD4056	£1.35
CD4010	£0.58	CD4029	£1.15	CD4069	£0.40
CD4011	£0.20	CD4030	£0.55	CD4070	£0.40
CD4012	£0.20	CD4031	£2.20	CD4071	£0.23
CD4013	£0.52	CD4035	£1.30	CD4072	£0.23
CD4015	£0.98	CD4037	£0.90	CD4081	£0.20
CD4016	£0.50	CD4040	£0.95	CD4082	£0.23
CD4017	£0.98	CD4041	£0.82	CD4510	£1.30
CD4018	£1.00	CD4042	£0.82	CD4511	£1.60
CD4019	£0.55	CD4043	£0.98	CD4516	£1.40
CD4020	£1.10	CD4044	£0.94	CD4518	£1.25
CD4021	£0.98	CD4045	£1.40	CD4520	£1.25

LINEAR

Type	Price	Type	Price	Type	Price
CA3011	£1.05†	LM381	£1.85†	UA710C	£0.40†
CA3014	£1.70†	LM3900N	£0.65†	72710	£0.30†
CA3018	£0.75†	MC1303L	£1.48†	UA711C	£0.32†
CA3020	£1.70†	MC1304P	£0.95†	72711	£0.32†
CA3028	£1.02†	MC1310P	£0.95†	UA723C	£0.45†
CA3035	£1.70†	MC1312PQ	£1.20†	72723	£0.45†
CA3036	£1.35†			UA741C	£0.24†
CA3024	£1.50†	MC1330P	£1.90†	72741	£0.24†
CA3043	£1.85†	MC1350	£1.20†	741P	£0.20†
CA3046	£0.80†	MC1351P	£1.20†	UA747C	£0.70†
CA3052	£1.60†	MC1352P	£1.40†	72747	£0.79†
CA3054	£1.35†	MC1456B	£1.40†	UA748	£0.35†
CA3075	£1.50†	MC1466L	£4.50†	72748	£0.35†
CA3081	£1.50†	MC1469R	£2.95†	748P	£0.35†
CA3089	£2.10†	MC1496B	£0.98†	SN76013N	£1.75†
CA3090	£4.25†				
CA3123	£1.90†	NE536	£3.50†	SN76023N	£1.75†
CA3130	£0.93†	NE515A	£3.50†		
CA3140	£0.90†	NE540	£1.50†	SN76110	£1.50†
LM301	£0.39†	NE550	£0.95†	SN76115	£1.90†
LM304	£1.80†	NE555	£0.32†	SN76660	£0.75†
LM308	£1.40†	NE556	£0.82†	SL414A	£1.95†
LM309K	£1.50†	NE561	£3.95†	TAA550B	£0.35†
LM320-5v	£1.50†	NE562B	£3.95†	TAA621A	£2.00†
		NE565A	£1.75†	TAA661A	£1.85†
LM320-12v	£1.50†	NE566	£1.50†	TAD100	£1.30†
		NE567	£1.80†	TBA540Q	£2.20†
LM320-15v	£1.50†	UA702C	£0.46†	TBA541B	£2.25†
		72702	£0.46†	TBA500	£0.80†
LM320-24v	£1.50†	UA703A	£0.25†	TBA810S	£1.05†
		UA709C	£0.25†	TBA820	£0.80†
LM380-14v	£1.50†	72709	£0.46†	TBA920Q	£3.40†
		709P	£0.25†	TCA270S	£2.20†

PANEL METERS

4" RANGE			2 1/2" RANGE		
Value	No.	Price	Value	No.	Price
0-50U	1302	£6.70	0-50UA	1307	£5.50
0-100UA	1303	£6.70	0-100UA	1308	£5.50
0-500UA	1304	£6.70	0-500UA	1309	£5.50
0-1MA	1305	£8.40	0-1MA	1310	£5.50
0-50V	1306	£8.40	0-50V	1311	£5.50

MR2P TYPE			MIN. LEVEL METER		
Value	No.	Price	Value	No.	Price
0-50UA	1313	£5.40	Size 23 x 22 x 26mm		
0-1MA	1315	£5.40	Sensitivity 200UA		
			No.		
			1320		£2.80

BALANCE/TUNING			VU METER		
Value	No.	Price	Value	No.	Price
Size 45 x 22 x 34mm			Size 40 x 40 x 29mm		
Sensitivity 100/0/100UA			Sensitivity 130UA		
No.			No.		
1319		£2.00	1321		£2.00

MINIATURE BALANCE/TUNING METER			MINI MULTI-METER		
Value	No.	Price	Value	No.	Price
Size 23 x 22 x 26mm			Size 60 x 24 x 30mm		
Sensitivity 100/0/100MA			Sensitivity 1000 ohms/V		
No.			AC VOLTS 0-10, 50, 250, 1000		
1318		£1.95	DC VOLTS 0-10, 50, 250, 1000		
			DC CURRENT 0-1-100mA		
			Resistance 0-150K ohms		
			No.		
			1322		£7.50

TRANSFORMERS

MINIATURE MAINS Primary 240V			MINIATURE MAINS Primary 240V		
No.	Type	Price	No.	Secondary	Price
2024	MT280 0-6V, 0-6V RMS	£1.50†	2021	6V-0-6V 100mA	90p†
2025	MT150 0-12V, 0-12V RMS	£1.50†	2022	9V-0-9V 100mA	90p†
			2023	12V-0-12V 100mA	95p†

1 AMP MAINS Primary 240V			STANDARD MAINS Primary 240V		
No.	Secondary	Price	No.	Secondary	Price
2026	6V-0-6V 1 amp	£2.50	2027	9V-0-9V 1 amp	£2.00
2027	9V-0-9V 1 amp	£2.00	2028	12V-0-12V 1 amp	£2.60†
2028	12V-0-12V 1 amp	£2.60†	2029	15V-0-15V 1 amp	£2.75†
2029	15V-0-15V 1 amp	£2.75†	2030	30V-0-30V 1 amp	£3.45†
2030	30V-0-30V 1 amp	£3.45†			

G.P. SWITCHING TRANS.		
No.	Rating	Price
2031	1/2 amp	£5.50†
2032	1 amp	£6.60†
2033	2 amp	£8.40†

G.P. SWITCHING TRANS.

TO18 SIM TO 2N706/8

BSY27/28/95A. All usable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2906, BCY 70


20 for 50p, 50 for £1, 100 for £1.80, 500 for £8, 1,000 for £14.

When ordering please state NPN or PNP

JUST OUT - NEW EDITION BI-PAK CATALOGUE



Send for

2+3=?

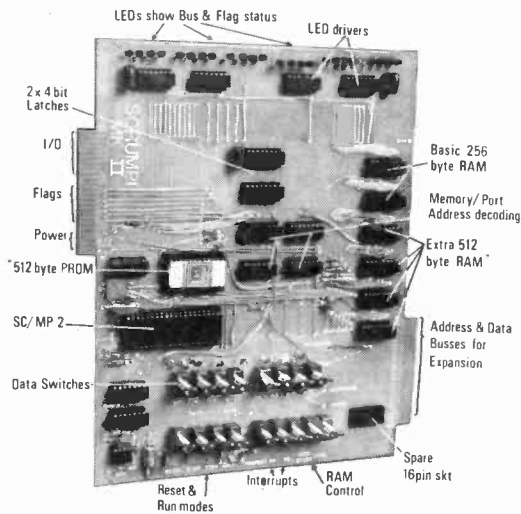

All component & sockets included in Basic kit except those marked * (Full kit only).

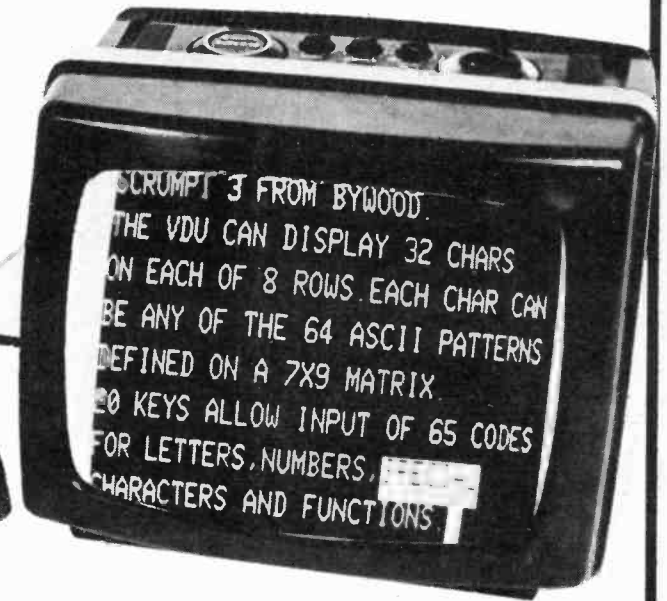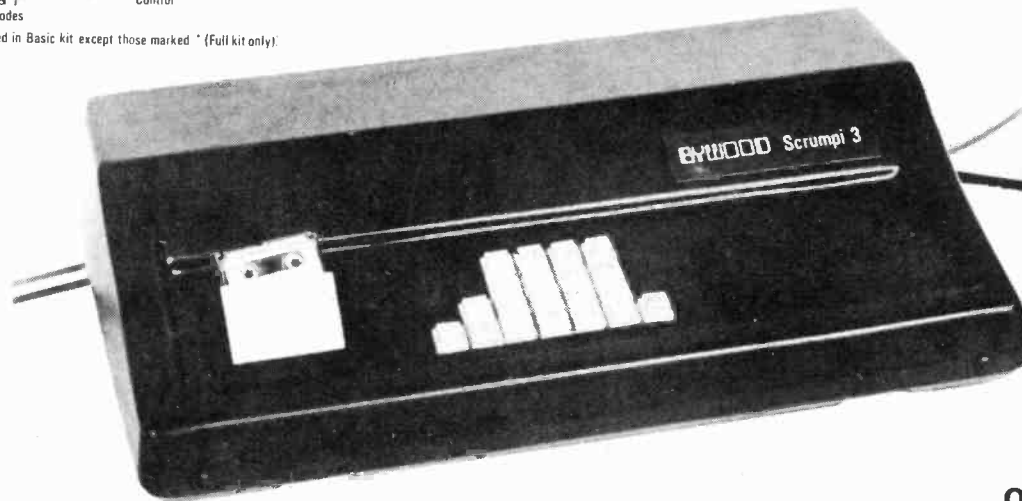Both SCRUMPI 2 and SCRUMPI 3 are powerful MPU kits in their own rights . . . Together they make one of the most powerful MPU Hardware/Software development systems available. Please write for details of combined kit/upgrade offer.



Quantity discounts are available to OEM users, Distributors, Retailers and Training Establishments.

SCRUMPI 2 is a single board MPU system based on the SC/MP2 microprocessor chip. Switches allow Single-step/Halt/Run modes with PROM or RAM bootstraps, RAM protect and interruption. Basic kit includes all IC sockets, all ancilliary components, SC/MP2, drivers, decoders, latches and 256 bytes of RAM. Full kit includes additional 512 byte PROM & 512 byte RAM.

SCRUMPI 2B £55.56 + VAT

SCRUMPI 2F £74.07 + VAT

SCRUMPI 3 is a single board MPU system based on the SC/MP2 microprocessor chip and including Keyboard, VDU interface, UART, two 8 bit parts, 128 byte RAM, 1K PROM and sockets for additional 1K PROM & 1K RAM.

SCRUMPI 3 Basic kit **£154.92**, with case & PSU **£189.75**.

BYWOOD

BYWOOD ELECTRONICS
68 Ebbens Road
Hemel Hempstead
Herts HP3 9ORC
Tel 0442 62757

news digest.

strike me


Straight out of Star Wars is a 'Strike Sight' computer from Ferranti.

The further away from the target a tactical aircraft can release a bomb load the greater chance the pilot has of returning safely. In particular, when releasing bombs equal to thousands of tons of TNT, unless the load can be released from an aircraft flying at very high altitudes (most tactical aircraft are not built for this), the only way is to release the load at some distance from the target.

The strike sight computer enables the pilot to do just that. The computer receives signals from and transmits signals to the range and doppler radars, the master reference gyro, and the altimeter. It guides the pilot on the approach to the target. At a specific time from the target the pilot selects whether to release the bomb or to abort the attack and pull out. At a precise interval thereafter, having selected to make the attack, the pull out begins and the computer takes over — the bomb is released automatically.

The only direct decision required by the pilot is whether or not to release the bomb. When he has made the selection the computer computes the release times and the pull-up process is initiated.

level out

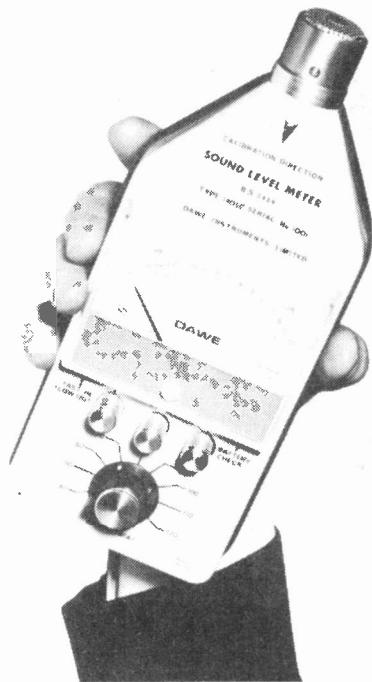


Pictured here is the Dawe Sound Level Meter 1405C. This device has a very wide dynamic range, from 34 to 130dB — from a whisper to well above the loudest shouting. Dawe Instruments Ltd, Concord Road, Western Avenue, London W3 05D.

getting a buzz


Wired like an ordinary plug and looking not much larger, the BUZZ PLUG may be fitted as a direct replacement for a standard plug.

The slightly thicker top actually contains some newly designed microcircuitry which continuously monitors the mains supply. In the event of a power failure (due to accidental switch-off, power cut, blown fuse) the plug produces a loud instantaneous warning which will persist until some action is taken.

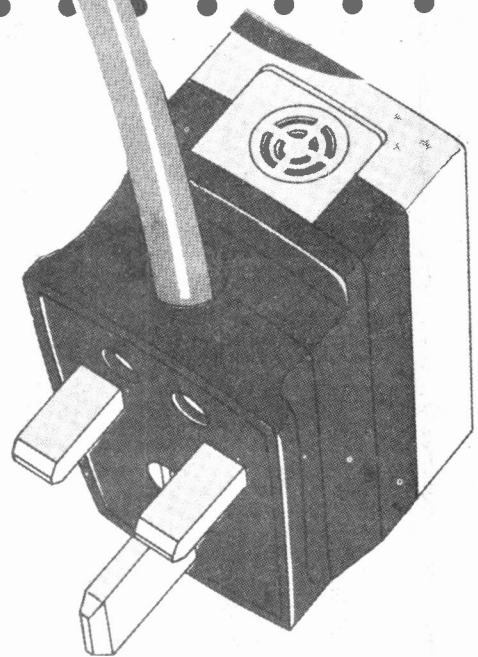The plug is powered by a single inexpensive battery which will give up to 60 hours warning. Typical applications include use with freezers, fridges, incubators and equipment which must run constantly or would require recalibration. Abbatal is the manufacturer, and further information is available from Ian Jones on Basingstoke (0256) 56417.



all yer mpus in one chip

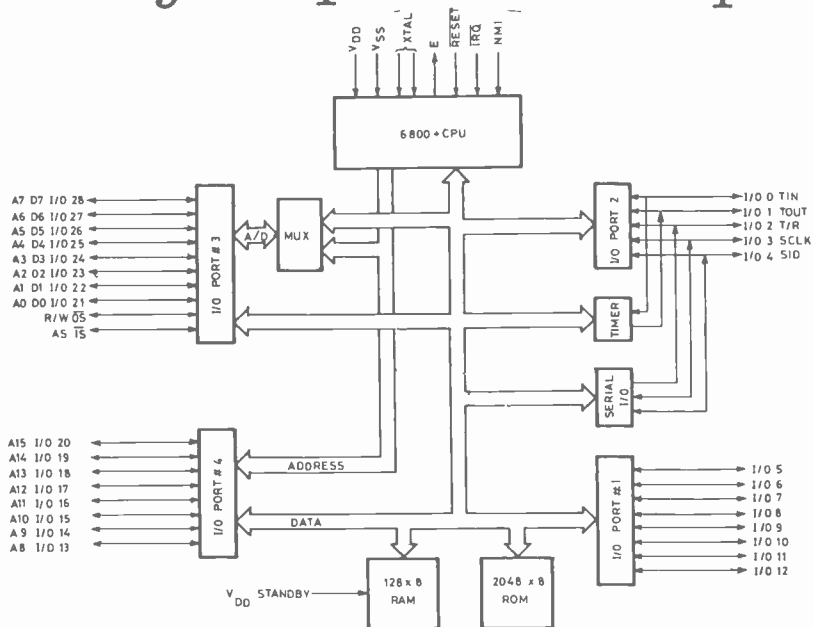

Motorola, manufacturers of the 6800 MPU has announced the introduction of a new one chip microprocessor in May. The chip, the MC6801 includes 2K-bytes of ROM, 128 bytes of RAM, a 16-bit timer, clock, serial output and 31 input/output lines.

The MC6801 is not a cut-down low end microprocessor but a very large scale integration MPU with an equivalent of 40,000 devices on the chip. The 6801 implements the full 6800 instruction set with the execution time of many key instructions reduced.

right hook

In a historic ruling, the US Supreme Court has confirmed that private individuals have the right to buy or make their own telephone equipment and connect it to the US telephone network.

Under the ruling it will be legal to hook

up as many devices as the user wishes — computer controlled systems, 'phone diverters, memory diallers, picturephones etc, etc. The only restriction is that the various bits must meet the relevant FCC requirements.


LINES FROM OUR VAST STOCK Please add post 35p per order
 THESE ARE ALL SPECIAL OFFERS BELOW MANUFACTURERS' PRICES ALL NEW STOCK, FULLY
 GUARANTEED All prices inclusive of VAT
 EXPORT ENQUIRIES INVITED ON ALL ITEMS

DIGITAL 24 HOUR CLOCK

USED IN BRAUN
DIGITAL CLOCKS

WITH
BUILT-IN
ALARM

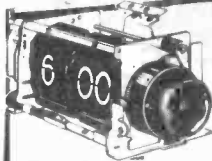- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS ● SIZE 6 3/8 x 2 3/8 x 2 3/4



MECHANISM

£6.00 + VAT 48p
P&P 25p
THREE FOR £16.50
+ VAT £1.32 POST FREE

Six button selector switch with built in 100K pots. Self cancelling buttons. Ideal for use with varicap tuned FM sets and TVs 120x64x55mm £2. 10 for £15. 100 for £125.

BOYMAR 9 digit calculator display with P.C. connector 0.1" digits. common cathode with red bezel £1.25. 10 for £10.

TEXAS 19 gold plated 'snap' key contacts on gold plated P.C. Board — all kinds of useful applications Size 70x80x2mm Height. 65p. 10 for £5. 100 for £40.

OSMOR change over reed relay with 12V coil. Approx. 20mA operating current. 59x17x13mm 50p. 10 for £4. 100 for £30.

Small mains transformers with 240V pri. 12V @ 100mA 60x40x42mm 95p. 10 for £7.50. 100 for £85. Valve type 40. 1 Output TX 61x15x42mm 75p. 10 for £6. Output TX EL64 80x53x34mm 95p. 10 for £8.

Clocking oscillator: PYE DYNAMICS thick film 1MHz 5V supply 19x25x6mm 85p. 10 for £7.

FAIRCHILD FND 10 0.15" 7 segment display. Common Cathode 50p. 10 for £4.50. 100 for £30.

6+6 WATT STEREO 24/28v 8ohm
Input 50/60 M/V. Into 500K
Tone Controls on P/C £4.95
Size 15.5 x 14 x 4.5 cm
WITH CIRCUIT

10+10 WATT STEREO PA8/25
Input 300 M/V. Into 100K cs
Size 18 x 7.3 x 4.8 cm
24 volt £5.95
4 ohm WITH CIRCUIT

FREE
VALVE
TRANSISTOR
CATALOGUE
AND EQUIPMENT
SENT STAMPED
(12 1/2p U.K.)
ADDRESSED ENVELOPE
(min 9 1/2" x 6 1/2")
FOR YOUR COPY NOW

Built 5 watt power amplifier Gould-Advance. 4-8 ohms output, up to 24V supply 500mV into 2K input. Complete with instructions. 11.5x6x3cm £3.00. 10 for £22.50.

Suitable power supply for above, in kit form. £2.20.

HDNEYWELL Proximity Detector Integral Amplifier 8V DC £2.50 ea. 10 for £22.

AUDIBLE TRANSISTORISED WARNING DEVICE 6-12 volts. Size 30mm x 10mm Polarised 50p ea. 10 for £4. 100 for £35.

SUPPLY PANEL containing 6 high quality 0.1µF 10% 1KV poly capacitors. 102x19x75mm 35p. 10 for £2.50.

ALMA push-button reed switches, push to make High reliability. 18x27x18mm 35p. 25 for £7. 100 for £25. 1000 for £225.

BURROUGHS 9 digit Panaplex calculator display. 7 segment 0.15" digits. neon type. with red bezel socket and instructions. £3.50. 10 for £30. 100 for £250.

TV sound converter through your FM tuner module. Complete with instructions £5.50.
 I.C. Audio Power by TOSHIBA 35 WATT module. 8 ohms o/p 200mV into 47K for full output 0.3% distortion (max). 60V power supply required. £8.50. 10 for £75.

10.7MHz crystal filters. Size 35x25x20mm 25KHz band width for NBFM £7. 10 for £60.

TEXAS 4+5 Digit C. Cathode Display with 16 pin DIL Base 0.2" digits.
 Pair £1.50. 10 pairs £12.50. 100 pairs £100.

2 1/2" 40 ohm speaker 250 M.Watt — Ideal for that small space 75p. 10 for £6. 100 for £50.

3 DIGIT 7 SEGMENT DISPLAYS. C. cathode pack of 2 with data (one or more segments are missing) 60p pack. 10 packs for £5.

TBA 120A 75p. 10 for £7. 100 for £55.

SOLDER at half price, 5 packs of 2 metres 18 gauge Servisol £1.20. 20 packs £10.

AVO meter movements for a military version of the Avo 8. Precision 37.5 micro Amp 50 µA with integral shunt movement. Electronic voltmeter circuit available on request. £8.50.

28 pin calendar/clock chip type MK501 7BB for use with common cathode LED display (with circuit) £4.49.

PACKS OF SEMI CONDUCTOR DEVICES	ALL NEW TESTED, CODED, GUARANTEED	
	Ten Packs	Hundred Packs
10-BC171A Plastic BC107 type	75p	£6 £50
TTL 8-Gates 7420, 7430, 7451	60p	£5 £40
TTL 6-Gates and Complex Mixed	75p	£6 £50
15-1 1/2 Watt Zeners 3.9-91 volt mixed	89p	£7.50 £65
10-10 watt Zeners mixed voltages	95p	£8.50 £75
10-400 M/W Zeners 3.3-33 volts	65p	£5.50 £45
50 — Germanium & Silicon Diodes	55p	£5 £40

5012 12 digit calculator chip. 4 functions. with circuits and data £2.50.

VITALITY 12V 0.15 amp. MES Bulbs. 100 for £5. 1000 for £40.

BECKMAN 500KHz triggerable clocking oscillator for use with calculator chips etc. 5V supply 25x10x12mm £1. 10 for £8. 100 for £65.

Re-settable thermostatic switch. A push button on-off switch which automatically drops out when the ambient temperature exceeds 72 C 47x29x46mm 75p. 10 for £6.50.

FT243 crystal packs. 10 crystals of mixed frequencies between 5800 and 8500 KHz (Our choice of frequencies) Ideal for re-grinding.
 £1.50 per pack. 10 packs £10. 100 packs £85.

Diode. 10X packs of 10 crystals 250 kc/s 50 mcr/s £1 pack. 12 packs £10. 100 packs £70.

Calculator chip CT5002 12 digit four functions for common cathode multiplex displays ONLY £1.95 complete with circuit.

1 MHz HC6U quartz crystals. For frequency meters, clocks, frequency references etc. 17x19x7mm £3.

TAPE HEADS 1/4 track Record Marriot. XRPS36 £5. XES11 erase £1.25. XRPS 18, £3.50.

T4/RF LONG-MEDIUM & F/M TUNER WITH MC1310 DECODER * 5-BUTTON SELECTOR SWITCHES * INPUT SELECTORS FOR GRAM AND TAPE * Supplied complete with FRONT-END TUNER AND FERRITE AERIAL * SIMPLE INTERCONNECTIONS * Size 19x13cm.
 THIS QUALITY AMPLIFIER £10.95 WITH CIRCUIT

POWER UNIT KIT FOR ABOVE MODELS 25/28 VOLTS £2.95.

MULLARD TUNER MODULES with data
 LP1171 combined AM/FM IF strip—£4 LP1179 FM front end with AM tuning gear, used with LP1171—£4 LP1171 and 79 pair—£6.50. LP1157 complete AM strip—£2.05. Ferrite Aerial — 95p with circuits


Henry's
RADIO

All mail to: Henry's Radio 404 Edgware Rd, London W2

LONDON W2, 404 6 Edgware Road, Tel: 01-723 1008

news

hammer fet-ish

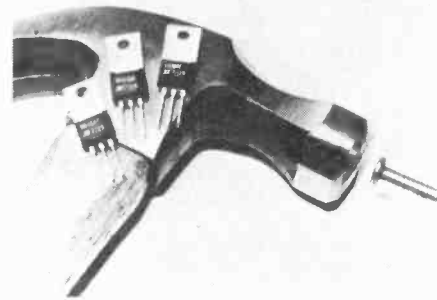

A new range of low cost VMOS power FETs in plastic have been introduced by Siliconix. These devices are aimed at replacing conventional bipolar transistors in a great many applications. This development in VMOS technology has cut the price of such devices by a third enabling them to compete directly with bipolar devices.

The direct interfacing with most logic families makes VMOS ideal for use in computer peripherals, micro- and mini-computer

systems, process control, etc. In addition to the many existing applications, VMOS should open up many new areas in telephone switching, analogue switching, and unlike conventional FETs or bipolar devices, VMOS transistors are inherently linear and ideally suited to use in linear power amplifiers from audio right through to VHF.

Siliconix Ltd.,
 Llanllienwen Close
 Morriston,
 SWANSEA SA6 6NE

digital dialling

Unilever have recently had a new computer controlled telephone system installed in their Rotterdam headquarters. The system comprises a Philips computer controlled exchange with electronic switching and the latest pushbutton keyphones installed throughout the building. Now each phone has its own 'switchboard' capability and supports many new facilities such as short code dialling, automatic call back and 3-way conversations.

The new system should make telephoning quicker, easier and more effective (in 1976 the phone bill came to over £200,000 — more than £200 per person!).

A similar system will be installed in their London offices in the future.

bbc get it taped

The BBC and 3M have collaborated to develop a new tape recording system claimed to provide 90 dB noise figure. The system will accommodate 32 tracks on one-inch tape at an undisclosed tape speed.

digest...

lcd giving a hand

A Scottish company, Murrell Dynamics, has designed an LCD watch with an analogue-type 'dial'. The main problem which Murrell has overcome is reducing the number of connections required to address the segments which comprise the 'hands'.

The 100 mm diameter prototype (which Murrell claims can readily be reduced to 25 mm) utilises two concentric rings of 60 radial lines — the inner ones are addressed uniquely for the hours indication, the two rings together for minutes, and the outer one for seconds.

hp in the day

Hewlett-Packard have announced red and yellow seven-segment displays which can be viewed in direct sunlight or in ambient lighting as bright as 10,000 foot-candles.

planer sailing

Planer instruments have introduced a new hand-held digital voltmeter using a 3½ digit display with 11mm high digits. The device has an input

sensitivity of 10M and four ranges from 0.1999 volts to 199.9 volts. Price is around £50. Planer Products Ltd, Windmill Road, Sunbury-on-Thames, Middlesex.



ETIPRINTS

In case you have missed out on ETIPRINTS thus far, they are a complete PCB pattern already to rub down in seconds. The patterns are produced from our original artwork so that the results they produce are nice and sharp.

We think that ETIPRINTS are such a good idea that we have patented the system (Patent numbers 1445171 and 1445172).

ETIPRINTS 005 is now available, and joins 001-004 as part of the regular system.

Details of ordering the ETIPRINTS are shown below.



Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ORDER TODAY

Send cheque or P.O (payable to ETI Magazine) to:
ETIPRINT
ETI MAGAZINE,
25/27, OXFORD STREET, LONDON. W.1.R. 1RF.

75p

Inc. VAT and P & P.

Please indicate clearly the ETI PRINTS you require. Those available at present are:

- 001 With patterns for skeet, clock board A, and the compander from Nov 77 plus the spirit level, three-channel tone control, and the digital thermometer from Oct 77.
- 002 With patterns for the burglar alarm from Jan 78 plus clock board B and the rev monitor from Dec 77.
- 003 With patterns for hammer throw and race track from Jan 78 plus the freezer alarm from Dec 77.
- 004 With patterns for the ultrasonic transmitter-receiver, metronome, 1B metal locator and porch light from Feb. '78 plus 51 w stereo amplifier Mk. 2 from Jan. '77.
- 005 March 77 issue projects, including howlround suppressor, RMS voltmeter, LCD panel meter

Readers please note that in earlier ads the contents of 002 and 003 were reversed. Would you please indicate when ordering from which issue the patterns you require were taken.

The latest kit innovation!

from **Sparkrite**

the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM

Introductory
SPECIAL OFFER
£2 off kit



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1-3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light systems function light, and security changeover switch. All kits fit vehicles with coil distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE: Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing.

Electronics Design Associates, Dept. E112
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

Inc VAT and PP	QUANTITY REQ'D
X4 KIT £14.95 £12.95	
TACHS PULSE SLAVE UNIT £3.35	
ACCESS OR BARCLAYCARD NO	

I enclose cheque PO's for
£
Cheque No _____
Send SAE if brochure only required

... news

gambling on

By Gerald Chevin
Videocraft Ltd.

WINTER CONSUMER ELECTRONICS
SHOW 5th-8th January 1978

The WCES at its new Las Vegas home, utilised 350 000 square feet and boasted over 550 exhibitors, with products ranging from Television through to Automobile sound. The new East Hall at the Las Vegas Convention Centre housed 350 exhibitors, the remaining 200 occupied the Pavilion Exhibition Hall and Grand Ballroom of the adjacent Las Vegas Hilton.

On the American VCR/VTR front, we have an alignment of manufacturers, opting for either the Sony Betamax or the V.H.S. (video home systems) format.

The sales forecasts estimated for 1977 by RCA is approximately 250 000 Video machines. This gives some indication of the kind of market penetration that the Video revolution is beginning to generate.

A number of Television large screen projectors are also on show, judging by the number of enthusiastic onlookers a very attractive unit the "Network 2000" from Magna-Vision, selling for less than £1,200 and including such features as Digital TV Channel read-out and cordless remote control, could be an indication of a new trend in large screen TV.

New Video games were not introduced at this winter show, but plenty of new programme cartridges, some with strange sounding onomatopiac titles like "Zzz ap," "Scribbling," "Acey-Deucey," "Bingo Math," "Indy 500" and "Draw Poker" to name a few were introduced by Atari, Bally and Coleco. Fairchild have introduced five more Video Carts.

These will interest anybody with a Videoplay TV Game, as the Video Carts, are totally compatible with the European version of the Fairchild game.

Microprocessor orientated games, included the GAMMONMASTER II Backgammon Computer (which is now available in the U.K.). COMPU-CHESS, at £100. A hand held game with six different levels of skill. One and Two are utilised for teaching purposes. Players familiar with the game, use levels three to five, but due to the number of algorithms, at level five, it could take the game nearly seven hours to reply to your move, and at level six, could take nearly two days!! For only £190, "BORIS" is available, whose features include programmable starting position, handicapping, autoqueening, en passant, editing, castling, timer and an eight digit alphanumeric read-out that flashes "congratulations" should you defeat it.


Parker Bros (who brought us Monopoly) are now micro-orientated with their code name sector. Two opponents command destroyers, trying to destroy a computer controlled submarine, which may be at any of the 4800 locations. Digital read-out of speed, depth, headings, and range are included. Collisions may throw the players off course, and if one misses the submarine, it then adopts a secret course.

Apart from most of the now familiar statistical scientific and programmable calculators, calculator alarms and calculator watches, the main interest in this sec-


digest...

new development

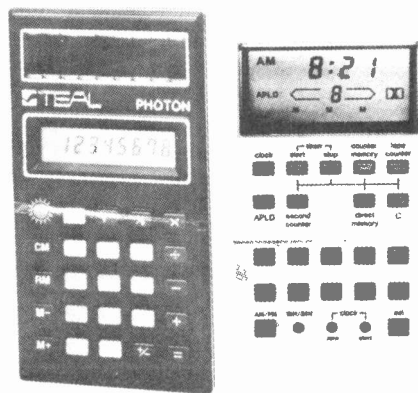tion was the photon by teal. It's features do not include an on-off switch, batteries, or a charger unit. It operates on pure Solar power, even under "LLL" low light levels.



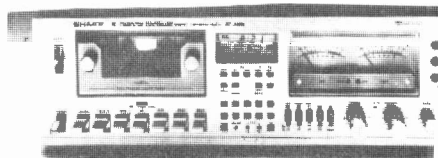Audio-wise, we saw a nice combination between the Micro processor and cassette deck by Sharp/Optonica. Some of it's features include *auto programme locate* which



can skip ahead or backwards, up to 19 songs, and automatically play your choice. *Counter memory* will stop or play at your own number selection on the counter. An LCD display indicates the function in use, or real time, which may also be used to turn the machine on and off. Approximate price £250.

Fisher offer on their model CR 4025 a cordless pause control with accompanying LED indicator on the deck. Price approximately \$250.

Blank tape is also a potential money spinning market. Not just the audio cassette field, but the video boom means a prime market place for both types of video cassette formats. One Company who likes to show its products to the full intermagnetics, emphasise their mechanical qualities by utilising transparent housings.

Radio sets has taken a turn for the better. With improved audio (maybe even soon stereo A.M.!) and arrays of digital read-outs for almost everything. Even "Star Wars" R2 D2 and CP30 are now available as radios.

Finally a brief look at the up and coming Autosound industry, which is expected to top the billion dollar mark in '78.

We now have a 150 watt per channel power amplifier from AUDIOMOBILE INC. A seven channel stereo graphic equaliser from PYRAMID INDUSTRIES coupled with a multitude of goodies like digital read-outs, ultra small, heavy sounding loudspeakers and a claim most manufacturers make that performance levels are comparable to home audio systems.

The best quote from the show by Nolan Bushnell, the Chairman of Atari TV Games; "Only after you've experienced the sheer joy of slaughtering your best friend, will you know the true meaning of fun."



Gaps?



38 555 CIRCUITS



Gaps?

It can be a nuisance can't it, going from newsagent to newsagent? "Sorry squire, don't have it - next one should be out soon."

Although ETI is monthly, it's very rare to find it available after the first week. If it is available, the newsagent's going to be sure to cut his order for the next issue - but we're glad to say it doesn't happen very often.

Do yourself, your newagent and us a favour. Place a regular order for ETI; your newsagent will almost certainly be delighted. If not, you can take out a postal subscription so there's nothing for you to remember - we'll do it for you.

For a subscription, send us £7.00 (£8.00 overseas) and tell us which issue you want to start with. Please make your payment (in sterling please for overseas readers) to ETI Subscriptions and keep it separate from any other services you want at the same time.

ETI Subscription Service,
Electronics Today International,
25-27 Oxford Street, London W1R 1RF.



Get a great deal from

Marshall's

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome.

A. MARSHALL (LONDON) LTD. DEPT. E.T.I.
LONDON — 40-42 Cricklewood Broadway, NW2 3ET
Tel. 01-452 0161. Telex 21492

LONDON — 325 Edgware Road, W2 Tel. 01-723 4242/3

GLASGOW — 85 West Regent Street, G2 2QD
Tel. 041-332 4133

BRISTOL — 1 Straits Parade, Fishponds Rd., BS16 2LX
Tel. 0272 654201

CATALOGUE NEW 1978 CATALOGUE

Our New 40 Page Spring '78 Catalogue is now available price 35p callers and 45p Post paid.

Top 400 Semiconductors from the largest range in the UK.
Express M.O. service by return post.

All prices are exclusive of VAT

All orders received are despatched same day on stock items

Prices correct at 3rd Feb., 1978, please add VAT to your order, postage & packing 40p

2N696	0.35	2N3703	0.15	2N6126	0.45	8C159	0.16	80116	1.20	8F885	0.35	TA521	1.00
2N697	0.30	2N3704	0.15	40361	0.50	8C160	0.35	80131	0.51	8F887	0.30	TA522	1.00
2N698	0.62	2N3705	0.15	40362	0.55	8C161	0.35	80132	0.54	8F888	0.30	TA550	0.60
2N699	0.55	2N3706	0.16	40363	1.30	8C167	0.12	80135	0.37	8F889	1.25	TA560	1.75
2N706	0.28	2N3707	0.18	40406	0.60	8C168	0.12	80136	0.37	8F890	0.25	TA570	2.30
2N706A	0.28	2N3708	0.13	40407	0.52	8C169	0.12	80137	0.38	8F891	0.25	TA6118	1.85
2N708	0.28	2N3709	0.15	40408	0.75	8C170	0.18	80138	0.38	8F892	0.30	TA621	1.15
2N709	0.50	2N3710	0.16	40409	0.75	8C171	0.16	80139	0.40	8F893	0.34	TA661A	1.50
2N710	0.27	2N3711	0.16	40410	0.75	8C172	0.14	80140	0.40	8F894	1.20	TA661B	1.50
2N718A	0.50	2N3712	1.20	40411	2.85	8C177	0.20	80239	0.40	8F895	0.50	TA670	3.91
2N720A	0.80	2N3713	2.30	40594	0.80	8C178	0.20	80240	0.45	8F896	0.25	TA680A	1.50
2N914	0.35	2N3714	2.45	40595	0.90	8C179	0.23	80241	0.45	8F897	0.32	TA680B	1.50
2N918	0.30	2N3715	2.55	40673	0.75	8C182	0.11	80242	0.50	8F898	1.40	TA690	1.95
2N919	0.38	2N3716	3.00	40126	0.45	8C182L	0.14	80243	0.60	8F899	1.80	TA695	1.60
2N929	0.25	2N3717	1.95	40127	0.45	8C183	0.14	80244	0.65	8F900	2.42	TA695A	1.75
2N930	0.26	2N3722	2.00	40128	0.45	8C183L	0.14	80245	0.65	8F901	1.52	TA7400	2.21
2N113L	0.30	2N3773	2.90	40151V	0.40	8C184	0.12	80246	0.66	8F902	1.15	TA7400A	2.30
2N1132	0.37	2N3789	2.80	40152U	0.50	8C184L	0.14	80529	0.45	8F903	1.88	TA7400B	2.30
2N1013	0.30	2N3790	3.10	40153	0.55	8C207	0.16	80530	0.50	8F904	1.00	TA7400C	2.30
2N1711	0.30	2N3791	3.10	40153K	0.55	8C206	0.16	80530	0.50	8F905	1.70	TA7400D	2.30
2N1893	0.38	2N3792	3.50	40176	0.50	8C212	0.14	8F115	0.38	8F906	1.35	TA7400E	2.30
2N2102	0.98	2N3794	0.62	8F124	0.65	8C212L	0.17	8F121	0.35	8F907	1.85	TA7400F	2.30
2N2218	0.33	2N3819	0.36	40178K	0.60	8C213	0.14	8F123	0.55	8F908	1.35	TA7400G	2.30
2N2218A	0.37	2N3820	0.38	40188K	0.60	8C213L	0.16	8F152	0.25	8F909	0.58	TA7400H	2.30
2N2219	0.35	2N3823	0.80	40161	1.00	8C214	0.16	8F153	0.25	8F910	0.40	TA7400I	2.30
2N2219A	0.36	2N3830A	0.21	40162	1.00	8C214L	0.17	8F154	0.25	8F911	0.60	TA7400J	2.30
2N2220	0.35	2N3906	0.22	4F106	0.55	8C237	0.14	8F159	0.35	8F912	0.45	TA7400K	2.30
2N2221	0.25	2N4036	0.67	4F105	0.75	8C238	0.12	8F160	0.30	8F913	0.65	TA7400L	2.30
2N2221A	0.26	2N4037	0.55	4F124	0.65	8C239	0.15	8F161	0.30	8F914	0.85	TA7400M	2.30
2N2222	0.25	2N4058	0.20	4F125	0.65	8C251	0.15	8F165	0.40	8F915	0.95	TA7400N	2.30
2N2222A	0.25	2N4059	0.15	4F126	0.65	8C252	0.22	8F167	0.35	8F916	1.10	TA7400O	2.30
2N2368	0.20	2N4060	0.20	4F139	0.65	8C257A	0.17	8F173	0.35	8F917	0.40	TA7400P	2.30
2N2369	0.27	2N4061	0.17	4F186	0.50	8C258A	0.17	8F177	0.25	8F918	0.45	TA7400Q	2.30
2N2369A	0.25	2N4062	0.18	4F187	0.50	8C258B	0.18	8F178	0.25	8F919	0.49	TA7400R	2.30
2N2646	0.75	2N4126	0.17	4F239	0.65	8C258A	0.17	8F179	0.30	8F920	0.25	TA7400S	2.30
2N2647	1.40	2N4289	0.20	4F240	1.14	8C262B	0.24	8F180	0.35	8F921	0.25	TA7400T	2.30
2N2904	0.36	2N4519	0.65	4F279	0.80	8C263C	0.30	8F181	0.35	8F922	0.40	TA7400U	2.30
2N2904A	0.37	2N4820	0.75	4F280	0.85	8C300	0.40	8F182	0.35	8F923	0.25	TA7400V	2.30
2N2905	0.37	2N4821	0.50	8C107	0.15	8C301	0.40	8F183	0.40	8F924	0.30	TA7400W	2.30
2N2905A	0.38	2N4822	0.55	8C108	0.15	8C302	0.40	8F184	0.38	8F925	0.50	TA7400X	2.30
2N2906	0.28	2N4823	0.70	8C109	0.15	8C307	0.15	8F185	0.35	8F926	0.30	TA7400Y	2.30
2N2906A	0.35	2N4824	0.60	8C113	0.20	8C308	0.15	8F194	0.15	8F927	0.55	TA7400Z	2.30
2N2907	0.25	2N4825	0.70	8C115	0.20	8C309C	0.15	8F195	0.15	8F928	0.60	TA7400AA	2.30
2N2907A	0.25	2N4826	0.75	8C116	0.19	8C317	0.14	8F196	0.15	8F929	0.95	TA7400AB	2.30
2N2924	0.18	2N4827	0.90	8C118A	0.20	8C318	0.13	8F197	0.17	8F930	0.60	TA7400AC	2.30
2N2925	0.17	2N4828	0.34	8C117	0.20	8C319	0.18	8F198	0.18	8F931	0.49	TA7400AD	2.30
2N3019	0.55	2N4829	0.40	8C118	0.20	8C328	0.19	8F200	0.35	8F932	0.25	TA7400AE	2.30
2N3053	0.26	2N4829A	0.40	8C119	0.30	8C337	0.19	8F225J	0.25	8F933A	0.50	TA7400AF	2.30
2N3054	0.60	2N4829B	0.40	8C121	0.45	8C338	0.21	8F244	0.35	8F934	0.66	TA7400AG	2.30
2N3055	0.70	2N4829C	0.40	8C132	0.30	8C547	0.12	8F245	0.40	8F935	0.55	TA7400AH	2.30
2N3390	0.20	2N4847	0.15	8C135	0.20	8C548	0.12	8F246	0.75	8F936	0.75	TA7400AI	2.30
2N3391	0.20	2N4848	0.15	8C135	0.20	8C549	0.13	8F254	0.24	8F937	0.25	TA7400AJ	2.30
2N3391A	0.20	2N4849	0.19	8C136	0.19	8C530	1.00	8F255	0.24	8F938A	1.10	TA7400AK	2.30
2N3392	0.16	2N4857	0.32	8C137	0.20	8C531	1.00	8F257	0.37	8F939	0.90	TA7400AL	2.30
2N3393	0.15	2N4858	0.33	8C140	0.35	8C532	1.00	8F258	0.45	8F940A	1.20	TA7400AM	2.30
2N3394	0.15	2N4859	0.29	8C141	0.40	8C533	1.00	8F259	0.49	8F941C	2.50	TA7400AN	2.30
2N3439	0.84	2N4864	0.34	8C142	0.30	8C534	1.00	8F259A	0.50	8F942A	2.80	TA7400AO	2.30
2N3440	0.84	2N4866	0.38	8C143	0.30	8C535	1.00	8F261	0.60	8F943A	2.60	TA7400AP	2.30
2N3441	0.61	2N6027	0.60	8C147	0.12	8C542	0.60	8F262	0.74	8F944	0.90	TA7400AQ	2.30
2N3442	1.35	2N6101	0.45	8C148	0.12	8C548	0.25	8F262A	1.38	8F945A	0.80	TA7400AR	2.30
2N3638	0.16	2N6107	0.42	8C149	0.14	8C559	0.25	8F261	0.30	8F946C	1.00	TA7400AS	2.30
2N3638A	0.16	2N6109	0.50	8C153	0.27	8C570	0.25	8F269	0.35	8F947C	0.65	TA7400AT	2.30
2N3639	0.38	2N6121	0.38	8C154	0.27	8C571	0.26	8F229	0.35	8F948C	0.92	TA7400AU	2.30
2N3641	0.20	2N6122	0.41	8C157	0.14	8C572	0.24	8F230	0.35	8F949C	0.43	TA7400AV	2.30
2N3702	0.13	2N6123	0.43	8C158	0.14	80115	0.80	8F284	0.35	8F950	0.35	TA7400AW	2.30

INTEGRATED CIRCUITS

CA3020	2.00	LM748-8	0.55	TA521	1.00
CA3020A	2.29	LM748A	0.55	TA522	1.00
CA3028B	1.29	LM1800	1.76	TA550	0.60
CA3028A	1.01	LM1808	1.92	TA560	1.75
CA3030	2.42	LM330	1.00	TA570	2.30
CA3030A	2.00	LM330N	0.85	TA6118	1.85
CA3045	1.40	LM3302N	1.40	TA621	1.15
CA3046	0.89	LM3401	0.70	TA661A	1.50
CA3048	2.23	LM3900	0.75	TA661B	1.50
CA3049	1.80	LM3905	1.60	TA670	3.91
CA3050	2.42	LM3930	1.50	TA680A	1.50
CA3053	1.62	MC1003	1.75	TA680B	1.50
CA3080	0.75	MC1303	1.03	TA690	1.95
CA3080A	1.88	MC1304	1.40	TA695	1.60
CA3086	0.60	MC1305	1.40	TA695A	1.75
CA3088	1.70	MC1310	1.91	TA7400	2.30
CA3090	2.52	MC1327	1.54	TA7400A	2.30
CA3090	4.00	MC1330	1.00	TA7400B	2.30
CA3093	0.98	MC1350	0.90	TA7400C	2.30
LM301A	0.67	MC1351	1.20	TA7400D	2.30
LM301A	0.40	MC1352	1.10	TA7400E	2.30
LM304	2.45	MC1458	0.91	TA7400F	2.30
LM308	0.65	MC555	1.10	TA7400G	2.30
LM308A	1.82	MC555	1.10	TA7400H	2.30
LM308B	0.85	MC565	1.30	TA7400I	2.30
LM308C	1.85	MC565	1.65	TA7400J	2.30
LM317K	3.00	MC567	1.80	TA7400K	2.30
LM318	2.26	SA550	2.50	TA7400L	2.30
LM319	6.48	SA570	2.50	TA7400M	2.30
LM322K	1.40	SA929	1.25	TA7400N	2.30
LM348N	1.50	76001N	3.30	TA7400O	2.30
LM360N	2.75	76003N	2.20		

THE CBM PET ~ IS IT HOUSE TRAINED?

Gary Evans, in conjunction with Graham Wideman and Mark Czerwinski of our Canadian offices, takes a look inside the machine that might do for 1978 what the TV game did for 1977.

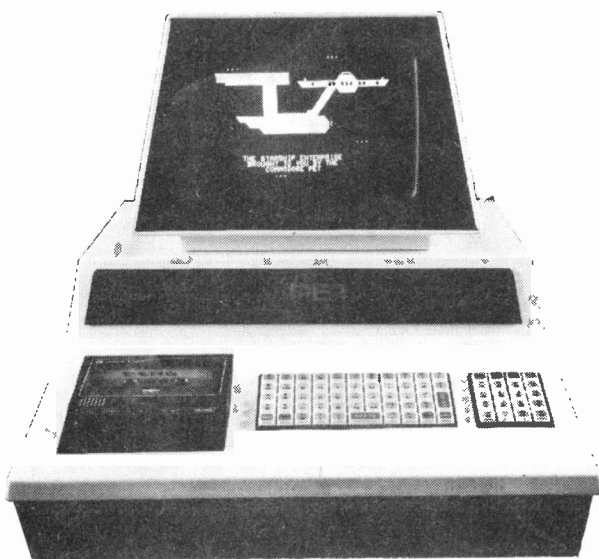


Fig. 1. The version of PET that is as far as we know the version that will be available in the UK.

WE FIRST SAW the Commodore PET as long ago as last April and reported on the fact in the July 1977 Microfile. It's taken until now for the final prototype we saw then to be translated into a production model, investments in production facilities completed and at last we have seen the official UK launch of the long awaited machine.

We have been dying to get our hands on a PET for some time and between our Canadian and British offices have now managed to put in some time on various PETS. Before getting down to a detailed description of the hardware just a few words about what will be available, at what price, when and from whom.

Commodore have set up a new division specifically to market PET and associated products (notably KIM 1 A 6502 development kit). Commodore Systems plan to mount a direct marketing operation to retail PET. They hope to locate suitable London showrooms very shortly.

The model available in Britain will initially be assembled in Germany and will feature 8K or user RAM (the 4K version sold in the States is not to be made available in the UK) and will retail for £695 (inclusive).

At the launch in early February Commodore Systems were quoting delivery times of about thirty days but expected these to lengthen to perhaps sixty days as demand increased. It might be worth mentioning however that the backlog of orders in the states has meant waits of up to one hundred and twenty days. The thirty or even sixty days quoted by Commodore Systems might be a little optimistic until production reaches target levels. ▶

The Machine Itself

The machine shown in Fig. 1. is as close to the final production version as makes no odds.

What you get for your money is what you see (CRT, cassette mechanism, calculator style keyboard) all packaged in a neatly styled case, plus the inards (6502 MPU, 12K or REM containing all that is necessary to operate the hardware plus a fast BASIC interpreter, 8K or RAM plus other assorted bits shown in Fig. 2.)

How did we like it

There is no doubt that this package of micro-pieces is well thought out, and designed with the idea that the user needs to know very little about computers to get "into" the PET. Remember the increased popularity of tape recording when cassettes came out? Make it simpler to use, easier for the human being. Same philosophy at work here, and that is what will sell it. Needless to say in spite of the fact we had very little documentation, we were highly impressed.

First of all there is no wiring up to do. When you plug in and switch on the PET, after only a couple of seconds it's ready for action. No BASIC to load from tape, it's already in there. This is one great headache reliever if the program you've written bombs out and writes all over memory in selected vital (of course) locations. No waiting for a 20 minute BASIC reload. 14K of built-in software is worth ten times its weight in silicon.

So after "power up" you can start programming, (more about that under SOFTWARE) or load from a cassette the software you want. Presumably in the future, tapes for various useful software packages will be widely available, so you will infrequently *need* to write your own, but it's lots of fun so you'll actually want to.

Taped

Upon entering the LOAD instruction, the machine tells you to stick the tape in and press the "PLAY" button. Here's where a compromise has been made. Although the PET can switch the transport motor on and off, it tells you to do the muscle work. Commodore have saved money by using a standard (cheap) cassette recorder, which is sensible for the consumer market they are aiming at.

The cassette feature worked quite well, although a couple of demonstration tapes did not load properly (we suspect over-worn tapes due to heavy use). One feature we would have liked, (which could not have been included without a large extra cost) would be a fast forward search. Without it the machine took a long time to find a program if the tape was started at the beginning and the program happened to be near the end. For this reason it seems most economical (time wise) to only use C30 cassettes (these are thicker and stronger anyway) and then record only one or two programs near the start of each side, unless programs are recorded in some long sequence in which they are to be used, or for storage of little used data etc.

BASIC

Commodore claims that their full floating point BASIC is the fastest yet implemented on a microcomputer. Here are the statements and features included.

Standard Dartmouth BASIC Statements: LET, READ, PRINT, DATA, IF, THEN, FOR, NEXT, DIM, END, GOTO

Extended BASIC Statements: RESTORE, REM, GET, GOSUB, DEF, RETURN, STOP, STEP, INPUT, FN, ON . . . GOTO, ON . . . GOSUB

Scientific Functions: .SGN, INT, ABS, SQR, RND, SIN, COS, TAN, ATN, LOG, EXP, PI

Logical Operators: AND, OR, NOT

Operation Commands: RUN, NEW, CLR, LIST, CONT, FRE

Formatting Functions: TAB, POS, SPC

Machine Level Statements: PEEK, POKE; Allow the user to examine and store at specific memory locations. USR, SYS; Link BASIC to machine language subroutines with parameter passing or developmental subsystems. WAIT; Monitors status of a memory location such as an I/O port until specified bits are set.

String Functions: LEFT\$, RIGHT\$, MID\$; Returns substrings (of specified length and position) of string acted upon. CHR\$, ASC; CHR\$ returns a character, given a numeric code. ASC returns a numeric code corresponding to a character. LEN; Returns the length of a string. VAL, STR\$; Convert decimal values to numeric strings and vice-versa.

Extended I/O Statements: OPEN, CLOSE; Control association of a logical file number to a physical device and, optionally, a file name on the device. SAVE, LOAD, VERIFY; Store and retrieve a program, with optional file name, on a physical device. Load allows for program overlay, VERIFY compares contents of memory to stored program. PRINT#, INPUT#, GET#; Allow communication with logical device numbers other than keyboard or screen. GET# inputs one character. CMD; Permits communication with multiple devices simultaneously.

Variables

TYPES: Real, Integer (%), String (\$)
NAMES: Variable names are uniquely given as a letter or a letter followed by a letter or digit.

Special Variables

TI, TI\$: Time of day. ST: Status word for I/O operations.

Key features

Another cost saver is the keyboard, being of calculator type construction and feel. All our reviewers disliked the feel (no feedback, you have to look at the screen to see your entry). On the other hand these reviewers were all

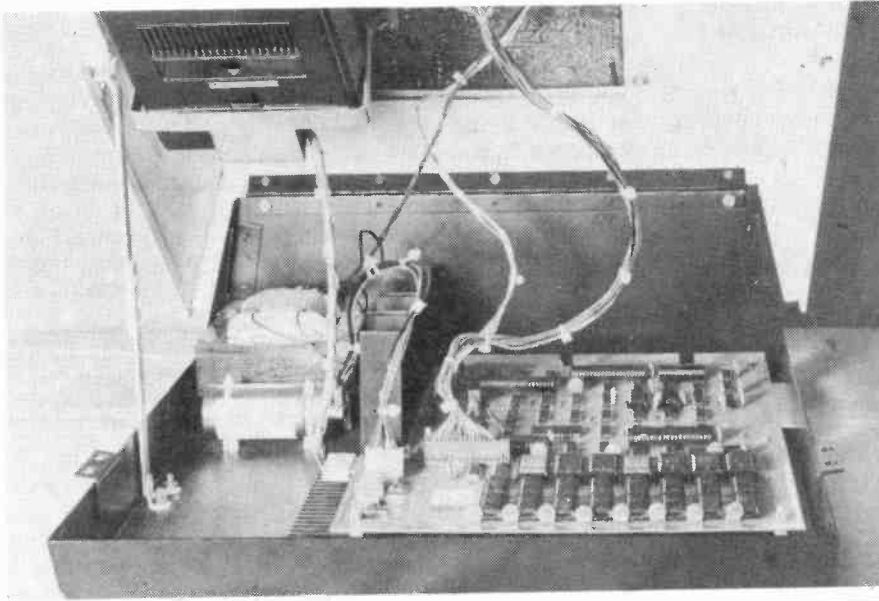


Fig. 2. Our first sight of the insides. It's a real pleasure to open up and discover a "prop" already in place to hold up the top. Notice neat cabling and connecting plugs, making for cheap efficient assembly and service.

Fig. 3. Here we've detached some of the parts from their mountings so we didn't have to draw a block diagram. Video monitor board is above.


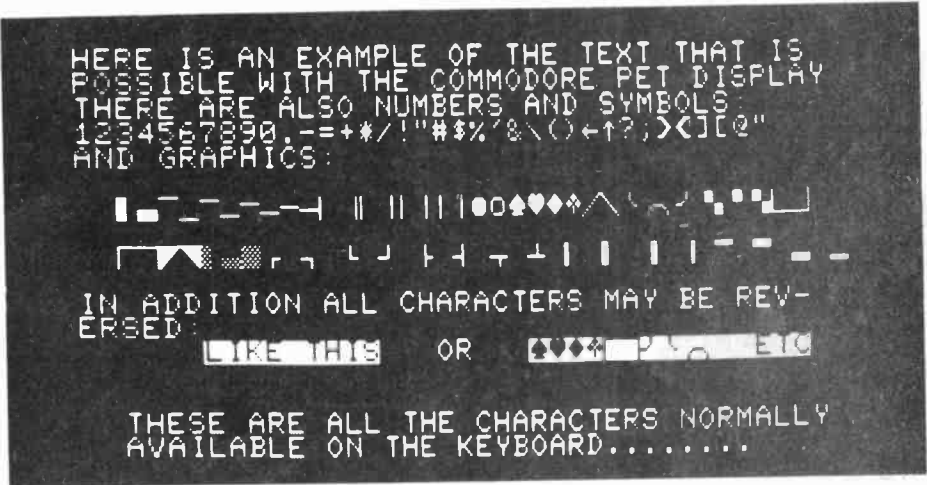


Fig. 4. The two PET keyboards. We found it quite handy to have a separate numeric pad.

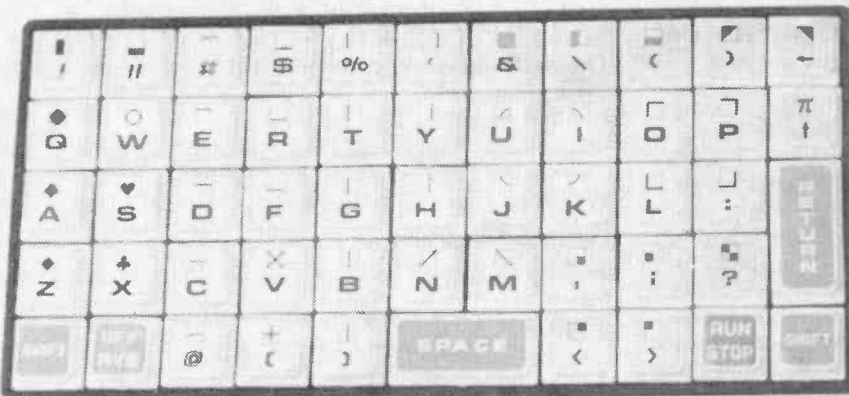

unfair.

The keyboard arrangement has all the rows of keys lined up instead of offset as in a normal keyboard, which would appear to be a big disadvantage to experienced typists. However, one is unlikely to enter vast quantities

of text, and this turned out to be less annoying than anticipated.

To solve all these problems, it would be a simple matter to replace the main keyboard with a "proper" one. Since there are electronics inside, it would simply

be a question of configuring the switches the same way. How long will it be until some one comes out with a PET soup-up kit, come on, we've started counting . . .!

The video monitor appears to be quite standard, Fig. 4 is a view in the back. The 9 inch CRT provided is with high resolution for the twenty-five lines of forty characters. A brightness control is located at the rear.

Electronics

For the electronics enthusiasts (well, you're reading this magazine aren't you?) we've got Fig. 2. Most of the important features are shown on this photo, from which a basic idea of the system configuration can be gleaned. All the big chips are plugged into sockets, something nice to see, especially for ROMs. (When's APL coming???)

The keyboard is accessed via a sixteen line Peripheral Interface Adapter (6520 like a 6820 for Motorola fans) which we expect uses eight outputs and eight inputs for decoding sixty-four keys, and then also a couple of the PIA "handshaking" lines for the rest of the work. In other words most of the keyboard decoding is done by software.

The cassette recorder as previously mentioned is a customised standard one, with a new PCB inside full of electronics suitable for data recording. In fact two cassette interfaces are included (second cassette recorder available later) with input, output, and motor on/off lines. This uses six lines of the sixteen on the second 6520 PIA (we assume) leaving ten lines, eight for parallel I/O and two serial, at TTL levels. Both cassettes record at 1 000 baud, but using built in software any program is recorded twice in series for reliability, cutting the effective rate of 500 baud. Thus an 8K program takes about two and a half minutes to load.

In addition, the PET is probably the first popular micro-computer to use the IEEE 488 bus for instrumentation communications, making it compatible with many existing and future digital instruments, printers etc.

A final note of the hardware. Unlike some of the early hobby computer equipment the inside of this machine looks like it's built for business, and for the manufacturer to stay in business. Constructed with quality electronics, and chassis and PCB arrangement for easy assembly and service.

Software

As stated before, one of the beauties of the PET is its built in ROM — full of software. The 14K includes 8K BASIC, 4K Operating System, 1K Machine Language and 1K Diagnostic routine, according to Commodore's literature.

First there's 8K of "extended" BASIC. The correct term is "BASIC interpreter". In simple terms an interpreter is a machine language program which takes your BASIC program as data, "translates" it to machine language subroutines and then executes it. This process actually occurs in a line-by-line translate-execute manner. The term "extended" refers to the fact that many statements are included that are omitted in some versions of BASIC. Using BASIC means that programming can be conducted in a civilized manner, using statements that are almost readable in English, with base ten numbers. The machine does the work of converting to machine language and eight bit binary arithmetic. As

encouragement to skeptics we've included a description of the language and how (easy it is) to use it.

Commodore claim that their BASIC is significantly faster than anybody else's which we cannot attest to, but for general use the PET performed admirably as compared to the reasonably typical IBM 360 and 370 interactive, multi-user systems that the reviewers were familiar with. (But we do like APL 1/2).

The cassette I/O, keyboard, video, and other functions are handled by the 8K operating system. These together with the BASIC are provided in seven 2K x 8 ROMs.

Lacking documentation, we can only guess at the other two ROM items provided. The diagnostic routine we assume verifies the operation of the hardware, and uses a LED mounted on the main board as an indicator for this task.

The 1K machine language we guess refers to an assembly language ("machine language" is what the MPU uses, "assembler" is one step higher, using mnemonics for each instruction, and is generally more readable and useable). There is also a mention of next year's "assembler device", to be plugged into the expansion port for "machine language" (?) programming. The advantage of machine or assembler language programming is increased efficiency of programs over those "interpreted" from BASIC. This could be critical in case of a routine which runs several thousands times in a loop, or for a frequently used function.

Basic Basic (interactive)

One can think of the PET as operating in one of two modes: "calculator mode" in which the operator asks the machine to execute and give the results of one statement; and "programmed mode" in which the programmer enters a series of statements, then has the machine execute the entire set at one go. The second mode requires a little more structure for "administrative" purposes.

Calculator Mode

Known by this name because it is the process of getting a quick answer from a small formula, (similar to calculators), or telling the machine to do one thing.

Example: PRINT 3+4

The machine works out 3+4 and "prints" the result on the screen.

Another example: LOAD FRED

This causes the machine to obtain a program called "FRED" from the cassette, including giving you instructions about what buttons to push on the recorder.

Program mode

Problem: Figure out the sum of the integers zero to ten.

Program: 10 J% = 0
20 FOR 1% = 1 TO 10
30 J% = J% + 1%
40 NEXT
50 PRINT J%
60 END

The numbers down the side are line numbers which can be any integers, and they keep the lines in order. We have chosen multiples of ten as it makes for easy editing at a later date by inserting line numbers in between if necessary. The variables are J% and 1%. The % signs identify them as integers.

Graphics

We suspect some pretty creative, intelligent people sat down and worked out the graphics character set on this machine. Figure 4 shows the keyboard and all the characters you can key in.

The display system is based upon 8x8 dot units, which may contain 5x7 dot upper case letters, or assorted symbols which are so designed to provide very versatile diagram and graphing capabilities. Because the 8x8 blocks fit together both horizontally and vertically, it means that adjacent lines of text look a little crammed together, but this can be avoided by judicious line spacing if necessary.

The "cursor" is a flashing "element" or character that can be moved about the screen, and it normally indicates the next space to be typed in. After typing in that space the cursor moves to the next adjacent spot and so forth. "RETURN" causes the cursor to move to the first position on the next line, just as a carriage return does on a typewriter. Additional cursor control is provided to move it quickly up, down or sideways. The cursor is useful also for editing and correcting programs already written on screen, with the facility for inserting and deleting characters. When the cursor attempts to move below the bottom of the "page", the screen "scrolls up". That is to say each line moves up one, with the top line disappearing.

In addition to the normal characters, each may be "reversed", that is appear as black on white, which can be used to advantage on some occasions.

Finally, here's our big surprise! If you're been counting keyboard characters, there are a lot less than the 256 possible with the character generator used in PET. Quite by accident we found a whole set of lower case letters! Very interesting. We're not quite sure what does it but check the pictures for yourself. That still doesn't add up to 256 characters, so there may be yet more we don't know about. In fact keyboards on early prototypes showed a set of graphic symbols that included assorted Greek letters, could they be inside as well? We don't know, but it all depends on what's in the character generator. We wonder if Commodore has lower case letters planned as a future "add-on option?" For that matter you could always burn your own PROM . . .

Add-ons

Well that's the basic PET Commodore Systems to introduce a number of peripherals specifically designed for PET during this year. These include a 24K memory unit (thought to be dynamic) with its own power supply, a printer and floppy. The fact that PET has the IEE-488 bus and ready access to other data lines means that, with luck, we should see a wide range of add ons at reasonable prices from a wide variety of sources. Many pets (lower case for the furry kind) are bought in an initial burst of enthusiasm but are soon abandoned as some new copy comes along. More recently this fate has befallen many a TV game.

This phenomena is far less likely to apply to a versatile beast like PET but the User's Club Commodore Systems are to set up should go a long way to keeping interest in PET alive well beyond the initial purchase.

The club open to users and, for want of a better phrase, non-users, alike for an annual fee of ten pounds.

The club will produce a newsletter and provide a means of exchanging news, information and software on PET type subjects on an international scale.

Commodore Systems, although themselves running, the club, hope that the driving force will be the many PET users throughout the world.

What more can we say?

It looks like computers are starting their march into the homes of the masses, which sounds very science-fiction and scary to some. We hope that the familiarity with computers this may bring to the man/woman/child in the street will reverse the widespread fear of THE COMPUTER as an enemy. Perhaps man will once again feel master over objects. There was after all a time when the automobile was regarded as an evil fire breathing monster, until everybody got one.

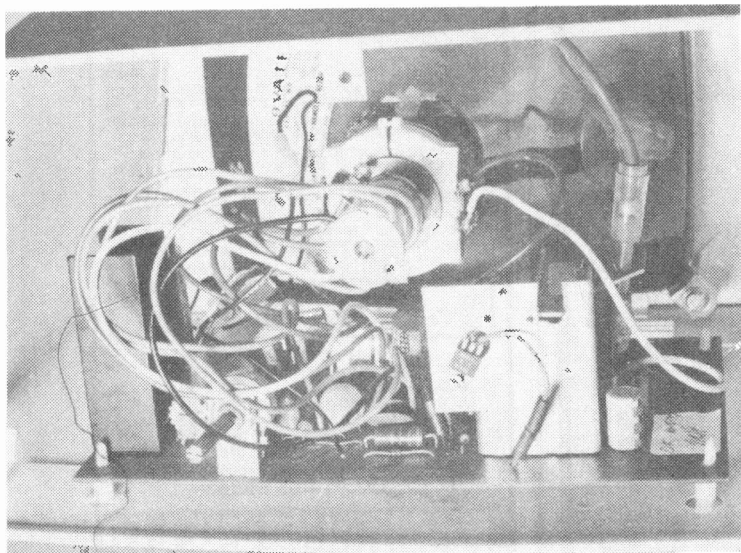


Fig. 5. Peeking in the back of the video monitor (left) reveals a fairly standard set of works.

```

....ETI'S REVIEWERS DISCOVERED THAT
BY EXECUTING THE STATEMENT:
POKE 59500,72
you can have lower case letters
INSTEAD of graphics. You can't have
both on screen at once, but can
alternate them in one program.
    
```

what a bind

Losing copies of ETI (your favourite magazine) can be very annoying. Why not take yourself off the ropes and bind them up neatly?

Half our orders for binders are repeats: we think that says a lot for their quality. At £3.00 all inc. you get a great deal of peace of mind too!

ETI Binders


25-27 Oxford Street

London W1R 1RF

FOR THE EXECUTIVE THE MIND READER

Your electronic computerised secretary that never needs a hair-do

the new 36 24 36

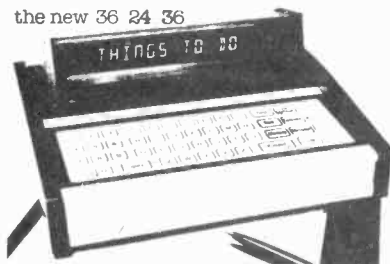

Memory system combined with stopwatch, calendar and clock.

Use as if a sophisticated diary to display programmed information on a daily basis.

Sorry, it doesn't make coffee!

£299

Prices include VAT and P&P. Send your Company Order, Cheque or phone your card no. to:

TEMPUS
Dept. ETI

19/21 Fitzroy Street, Cambridge
Tel. 0223 312866

AN AMAZING ^{NEW} WATCH BARGAIN

A 12-FUNCTION LCD
CHRONOGRAPH FOR THE PRICE
OF AN ORDINARY
LCD WATCH



6 digit, hours, minutes, seconds, 4 year callender, day, date, month, chrono time 1/100th sec. 2 event timing, non interrupt between chromo & real time, backlight, water resistant. Full 12 months guarantee.

**ONLY
£24.95**

Inc. VAT, P&P

Cheques and P.O. payable to:

VIDEOTIME PRODUCTS

The video & time products people

**56 QUEENS RD.
BASINGSTOKE
HANTS. RG21 1RE
TEL. (0256) 56417**



New TEXAS 58 & 59

The new Texas 58
480 program steps
60 memories
Looping increment
6 levels subroutines
Insert delete, prog
review
Master module,
recharger included
Only £79.95
+85p P&P

	Our Price
●58 480 program steps up to 60 memories	£79.95
●59 Card programmable 960 steps 100 memories	£208.95
●57 50 step programmable	£42.95
PC 100A print cradle for use with 58 52 56 58	£175.95
●51 Fu fully sci 3 mem	£33.95
●41 financial	£27.95
CBM	
●Pr 100 72 steps programmable	£37.95
●N60 Navigator	POA
●SR61 Statistician	POA
●4/5590R 92 steps pre-programmable sci	£29.95
4148 full sci	£19.95
SINCLAIR	
●New Cambridge programmable	£14.95
Set of libraries	£4.95
HEWLETT PACKARD A1	
●HP 29C, New	£139.90
●HP 19C, Cont. Mem Key Prog Printer	£236.52
●HP 25 Prog	£85.32
●HP 27 10 mem Sci Fin Stat	£129.06
●HP 67 Card Prog 224 steps	£312.12
●HP 97 Prog with Print	£547.56
●HP 19C Print out	£118.74
●Free recharger: Full range of HP Texas and Accessories available	
CASIO	
CQ1 Time stopwatch calc alarm set alarm	
diff times and 4 diff tones	£29.95
●FAT card programmable	£129.95
●FX201 Programmable	£44.95
●FX202 Prog with facility for keeping prog when off	£67.95
FX120 Full sci	£17.95
LC820 LCD in wallet	£17.95

●Rechargeable Free

We also stock a range of desk printouts ordinary calcs, specialist calcs, cassette, cassette radios, stereo, etc. Tell us your requirements and we will supply.

MAIL ORDER ONLY

TRITRON
57 Bridge Lane, London NW11

HAVE YOU DONE IT LATELY!



Full Catalogue 25p

Please enclose
20p P&P with order

B24—RP stereo cassette
glass/ferrite record/
playback **£9.84**

B12—01 mono cass.
playbk. **£1.60**

B24—01 stereo cass.
playbk. **£2.80**

A28—05 stereo 8tk car-
tridge **£1.80**

E12—09 stereo/mono
cass, erase **£1.80**

5/7 Church St, Crewkerne, Som. Tel. (0460) 74321

ELECTRONIC CALCULATORS SCIENTIFIC

*TEXAS PC100A (Printing Unit for SR52/SR56/T159/T158)	£161.22
HP & TEXAS Libraries Accessories avail	POA
*TEXAS T1-59 (Card Progs. 960 steps of 100 Mem.)	£205.00
*TEXAS T1-58 (Key Progs., 480 steps or 60 Mem)	£74.00
*TEXAS SR51 II (3 Mem./Stat Sci.)	£29.95
*TEXAS T157 (Key Progr. 8 Mem. up to 150 Key-strokes)	£36.50
*TEXAS T1 45 (new updated version of T140)	£22.40
*CBM 4148R (Scient. Exp. 10 dig.)	£20.75
*CBM 4190R (Scient. Pre-prog. 14-dig/EXP)	£26.30
*CBM Maths (M55) Nav (N60) Stat (S61)	£54.00
*CBM PR100 (100 Mem. 72 step prog.)	£35.00
*CBM S61 (stat plus sci 6 mem M and S div. chi sq DIS. LIN Regn., etc.)	
*HP 19C (continuous mem. key prog. printer)	£183.00
*HP 25A (key prog. 49 steps)	£74.50
*HP27 (10 mem sci/fin./stat. 8 digit+exp)	£104.00
*HP 67 (card prog. 224 steps 26 mem)	£260.00
*HP 97 (card prog. 224 steps print 26 mem)	£432.00
All HP range available. Prices on request	
CASIO 120 (new 8 dig +ex mem st. div. polar/rec. 0 6 levels fractions)	£22.40
CASIO /CO1 (Cal. Dig. Alarm Clock)	£27.69
CASIO /CO2 (Cal. Dig. Alarm Clock)	£31.50
*CASIO FX201P (sci. 11 mem. 127 step prog)	
*"FORTAN SYSTEM"	£46.25
*CASIO PROFX1 (as above but card prog)	£99.00
FREE Mains charger included	

SPECIAL OFFER

Texas T159 with PC100A **£356**

SPECIFICATION LISTS ON REQUEST
(Send S.A. Envelope)

GOODS FULLY GUARANTEED. PRICES EXCLUDE VAT (ADD 8%) BUT INC. P&P CHEQUE WITH ORDER

Company, Hospital and Government orders accepted by phone

EXPORT ORDERS ACCEPTED
Barclaycard, Access order accepted by phone

Tel: 01-455 9855

MOUNTAINDENE LTD
22 Cowper Street, London, EC2
(Near Old St. Station) Tel. 01-455 9855

DIODES/ZENERS				SOCKETS/BRIDGES				TRANSISTORS, LEDS, etc.				
1N914	100v	10mA	.05	8-pin	pcb	.25	ww	.45	2N2222	NPN	(Plastic .10)	.15
1N4005	600v	1A	.08	14-pin	pcb	.25	ww	.40	2N2907	PNP		.15
1N4007	1000v	1A	.15	16-pin	pcb	.25	ww	.40	2N3906	PNP		.10
1N4148	75v	10mA	.05	18-pin	pcb	.25	ww	.75	2N3054	NPN		.35
1N753A	6.2v	z	.25	22-pin	pcb	.45	ww	1.25	2N3055	NPN	15A 60v	.50
1N758A	10v	z	.25	24-pin	pcb	.35	ww	1.10	T1P125	PNP	Darlington	.35
1N759A	12v	z	.25	28-pin	pcb	.35	ww	1.45	LED Green, Red, Clear			.15
1N4733	5.1v	z	.25	40-pin	pcb	.50	ww	1.25	D.L.747	7 seg 5/8" high com-anode		1.95
1N5243	13v	z	.25	Molex pins	.01	To-3 Sockets		.45	XAN72	7 seg com-anode		1.50
1N5244B	14v	z	.25	2 Amp Bridge		100-prv		1.20	FND 359	Red 7 seg com-cathode		1.25
1N5245B	15v	z	.25	25 Amp Bridge		200-prv		1.95				

C MOS		- T T L -									
4000	.15	7400	.15	7473	.25	74176	1.25	74H72	.55	74S133	.45
4001	.20	7401	.15	7474	.35	74180	.85	74H101	.75	74S140	.75
4002	.20	7402	.20	7475	.35	74181	2.25	74H103	.75	74S151	.35
4004	3.95	7403	.20	7476	.30	74182	.95	74H106	.95	74S153	.35
4006	1.20	7404	.15	7480	.55	74190	1.75			74S157	.80
4007	.35	7405	.25	7481	.75	74191	1.35	74L00	.35	74S158	.35
4008	.95	7406	.35	7483	.95	74192	1.65	74L02	.35	74S194	1.05
4009	.30	7407	.55	7485	.95	74193	.85	74L03	.30	74S257 (8123)	.25
4010	.45	7408	.25	7486	.30	74194	1.25	74L04	.35		
4011	.20	7409	.15	7489	1.35	74195	.95	74L10	.35	74LS00	.35
4012	.20	7410	.10	7490	.55	74196	1.25	74L20	.35	74LS01	.35
4013	.40	7411	.25	7491	.95	74197	1.25	74L30	.45	74LS02	.35
4014	1.10	7412	.30	7492	.95	74198	2.35	74L47	1.95	74LS04	.35
4015	.95	7413	.45	7493	.40	74221	1.00	74L51	.45	74LS05	.45
4016	.35	7414	1.10	7494	1.25	74367	.85	74L55	.65	74LS08	.35
4017	1.10	7416	.25	7495	.60			74L72	.45	74LS09	.35
4018	1.10	7417	.40	7496	.80	75108A	.35	74L73	.40	74LS10	.35
4019	.60	7420	.15	74100	1.85	75110	.35	74L74	.45	74LS11	.35
4020	.85	7426	.30	74107	.35	75491	.50	74L75	.55	74LS20	.35
4021	1.35	7427	.45	74121	.35	75492	.50	74L93	.55	74LS21	.25
4022	.95	7430	.15	74122	.55			74L123	.55	74LS22	.25
4023	.25	7432	.30	74123	.55	74H00	.25			74LS32	.40
4024	.75	7437	.35	74125	.45	74H01	.25	74S00	.55	74LS37	.35
4025	.35	7438	.35	74126	.35	74H04	.25	74S02	.55	74LS40	.45
4026	1.95	7440	.25	74132	1.35	74H05	.25	74S03	.30	74LS42	1.10
4027	.50	7441	1.15	74141	1.00	74H08	.35	74S04	.35	74LS51	.50
4028	.95	7442	.45	74150	.85	74H10	.35	74S05	.35	74LS74	.65
4030	.35	7443	.85	74151	.75	74H11	.25	74S08	.35	74LS86	.65
4033	1.50	7444	.45	74153	.95	74H15	.30	74S10	.35	74LS90	.95
4034	2.45	7445	.65	74154	1.05	74H20	.30	74S11	.35	74LS93	.95
4035	1.25	7446	.95	74156	.95	74H21	.25	74S20	.35	74LS107	.85
4040	1.35	7447	.95	74157	.65	74H22	.40	74S40	.25	74LS123	1.00
4041	.69	7448	.70	74161	.85	74H30	.25	74S50	.25	74LS151	.95
4042	.95	7450	.25	74163	.95	74H40	.25	74S51	.45	74LS153	1.20
4043	.95	7451	.25	74164	.60	74H50	.25	74S64	.25	74LS157	.85
4044	.95	7453	.20	74165	1.50	74H51	.25	74S74	.40	74LS164	1.90
4046	1.75	7454	.25	74166	1.35	74H52	.15	74S112	.90	74LS367	.85
4049	.70	7460	.40	74175	.80	74H53J	.25	74S114	1.30	74LS368	.85
4050	.50	7470	.45			74H55	.25				
4066	.95	7472	.40								
4069	.40										
4071	.35										
4081	.70										
4082	.45										

9000 SERIES	
9301	.85
9309	.35
9322	.85
95H03	.55
9601	.75
9602	.50

MEMORY CLOCKS	
74S188 (8223)	3.00
1702A	6.95
MM5314	3.00
MM5316	3.50
2102-1	1.75
2102L-1	1.95
TR 1602B/ TMS 6011	6.95
8080AD	15.00
8T13	1.50
8T23	1.50
8T24	2.00
2107B-4	4.95

LINEARS, REGULATORS, etc.							
8266	.35	LM320K5 (7905)	1.65	LM340T24	.95	LM723	.50
MCT2	.95	LM320K12	1.65	LM340K12	2.15	LM725	1.75
8038	3.95	LM320T5	1.65	LM340K15	1.25	LM739	1.50
LM201	.75	LM320T12	1.65	LM340K18	1.25	LM741 (8-14)	.25
LM301	.25	LM320T15	1.65	LM340K24	.95	LM747	1.10
LM308 (Mini)	.75	LM339	.95	LM373	2.95	LM1307	1.25
LM309H	.65	7805 (340T5)	.95	LM380	.95	LM1458	.95
LM309K (340K-5)	.85	LM340T12	1.00	LM709 (8,14 PIN)	.25	LM3900	.50
LM310	1.15	LM340T15	1.00	LM711	.45	LM75451	.65
LM311D (Mini)	.75	LM340T18	1.00			NE555	.50
LM318 (Mini)	.65					NE556	.95
						NE565	.95
						NE566	1.75
						NE567	1.35

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd., San Diego, CA 92111 U.S.A.
No Minimum

All prices in U.S. dollars. Please add postage to cover method of shipping. Orders over \$100 (U.S.) will be shipped air no charge. Payment should be submitted with order in U.S. dollars. All IC's Prime/Guaranteed. All orders shipped same day received.

Phone (714) 278-4394 **BARCLAYCARD/VISA/ACCESS/AMERICAN EXPRESS**

SPECIAL DISCOUNTS	
Total Order	Deduct
\$35 - \$99	5%
\$100 - \$300	10%
\$301 - \$1000	15%
\$1000 - Up	20%

ETI MARKET

CBM 5R39



£14.95
ALL INC.

We've said this before, but you asked for it. Last time the 5R39 proved very successful, and orders were being received long after the offer period expired. Since then there has been a steady 'lobby' to bring back the beast — and so we have finally capitulated!

In case you missed it then (WHY?) the 5R39 is a fully rechargeable scientific calculator with all the facilities required for serious work. Its unusual keyboard layout makes it ideal for everyday use too, and with no batteries to buy (charger INCLUDED in price) it's irresistible!

FEATURES: sin, cos, tan and inverse, change sign, exchange register, x^2 , y^x , $\log e$, $\log 10$, \sqrt{x} , \sqrt{y} , rectangular and polar coordinates, e^x , 10^x , standard deviation and mean value, two memories, summation to memory, $1/x$, parenthesis, full arithmetic functions. Algebraic logic is employed.

TO CALCULATOR OFFER
ETI MAGAZINE
25-27 OXFORD STREET
LONDON W1R 1RF

Offer closes April 30th

Name

Address


ETI ALARM CLOCK

£14.50

THE LONG-RUNNING OFFER ON A DIGITAL ALARM CLOCK HAS BEEN ONE OF OUR MOST SUCCESSFUL EVER! OUR PRICE INCLUDES VAT AND POST & PACKING.

Our clock shows the time 18mm high on bright Fluor Gas Discharge displays (there is a brightness control on the back). The dot on the left of the display shows AM/PM and the flashing (1Hz) colon shows if the alarm and clock are working. A beeper alarm sounds until the clock is tipped forwards. Then the 'snore' facility can give you 5 minutes sleep, before the alarm sounds again, and then another 5 minutes, etc., until you switch the alarm off. The clock also features a mains-failure indicator, and is 12hr. — the alarm being 24 hour.

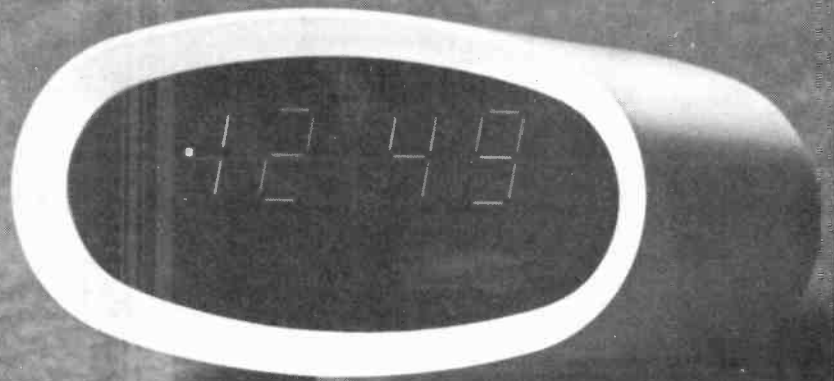We have a large number of units in stock for this offer but please allow 28 days for delivery.



CLOCK OFFER
ETI MAGAZINE
25-27 OXFORD STREET
LONDON W1R 1RF

I enclose cheque/£O. for £14.50 (payable to ETI) for an Alarm Clock. Please write your name and address on the back of your cheque to speed processing of your order.

NAME


ADDRESS

Those not wishing to cut their magazine may order on their own notepad.

Full size is 5in. across by 3 1/2in. deep.

PLACE CHESS CHALLENGER

£99.95 INC

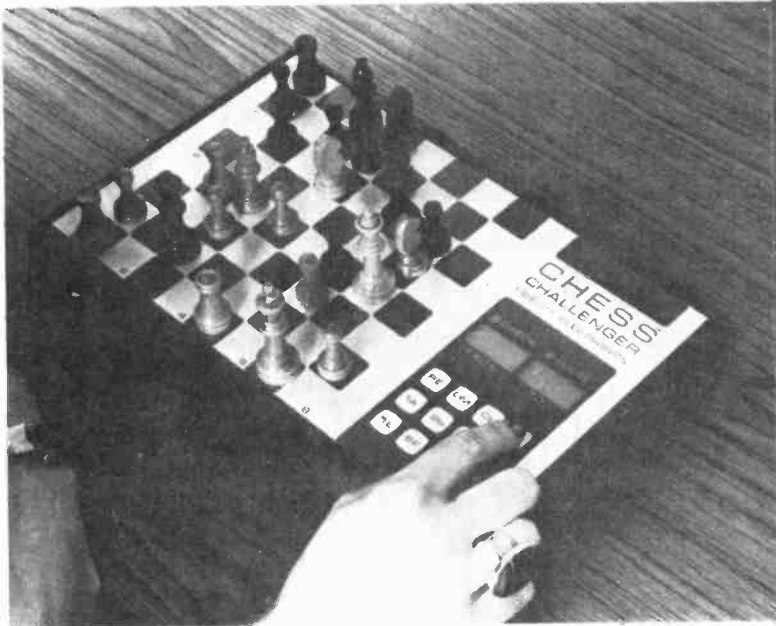

Play the Chess Challenger with anything less than a clear mind and it will beat you. Embarrassing but true. You punch in your move on the keyboard next to the board, and the reply appears on four LED displays. We ran this a while back at £115, but have now managed to knock down the price AGAIN, and present it to you at what is definitely our final offer!

Ideal for the chess tyro to improve his game, or for the more experienced player to get some practice in.

To: Chess Challenger Offer
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please find enclosed by payment of £99.95

Name

Address

Offer subject to availability
Allow 28 days for delivery

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safelogs

Miniature & Sub Miniature

Volts	Milli-amps	Ref. No.	Price £	P&P
3-0-3	200	238	1.95	55
0-6.0-6	1A 1A	212	2.60	55
9-0-9	100	13	1.85	40
0-9.0-9	330 330	235	1.95	40
0-8-9.0-8-9	500 500	207	2.35	55
0-8-9.0-8-9	1A 1A	208	3.50	55
0-15.0-15	200 200	236	1.95	40
0-20.0-20	300 300	214	2.35	70
20-12.0-12.20	700(DC)	221	3.10	70
0-15-20.0-15-20	1A 1A	206	4.20	85
0-15-27.0-15-27	500 500	203	3.65	70
0-15-27.0-15-27	1A 1A	204	4.75	85

12 AND/OR 24 VOLT

Pri. 220-240 Volts				
Amps	24V	Ref.	Price £	P&P
0.5	0.25	111	1.95	55
1.0	0.5	213	2.30	70
2	1	71	2.90	70
4	2	18	3.75	70
6	3	70	5.35	85
8	4	108	6.25	100
10	5	72	6.95	100
12	6	116	7.85	100
16	8	17	9.25	110
20	10	115	12.75	130
30	15	187	16.60	130
60	30	226	22.90	160

30 VOLT (Pri. 220-240V)

Sec. 0-12-15-20-24-30V				
Amps	Ref. No.	Price £	P&P	
0.5	112	2.45	70	
1.0	79	3.05	70	
2.0	3	4.80	85	
3.0	20	5.80	100	
4.0	21	6.85	100	
5.0	51	7.75	100	
6.0	117	9.50	100	
8.00	88	11.35	130	
10.0	89	12.00	130	

CATALOGUE 30p

Please add VAT at 8%
Barclaycard and Access facilities
available
Trade and Education Welcome

50 VOLT (Pri. 220-240V)

Sec. 0-19-25-33-40-50V				
Amps	Ref. No.	Price £	P&P	
0.5	102	3.20	70	
1.0	103	4.20	85	
2.0	104	6.10	100	
3.0	105	7.85	100	
4.0	106	9.80	110	
6.0	107	14.95	130	
8.0	118	15.75	150	
10.0	119	20.50	200	

60 VOLT (Pri. 220-240V)

Sec. 0-24-30-40-48-60V				
Amps	Ref. No.	Price £	P&P	
0.5	124	3.40	70	
1.0	126	4.65	85	
2.0	127	6.50	100	
3.0	125	9.15	110	
4.0	123	11.25	130	
5.0	40	11.80	130	
6.0	120	14.75	140	

AUTO TRANSFORMERS

Input/Output Tapped 0-115-210-240V

VA (Watts)	Ref. No.	Price £	P&P
20	113	2.25	70
75	64	3.50	70
150	4	5.35	85

Input/Output Tapped 0-115-210-220-240V

300	66	7.15	100
500	67	10.75	130
1000	84	17.00	140

Also 1500/2000/3000VA

MAINS ISOLATING (Centre Tapped & Screened)

Pri. 120/240 Sec. 120/240V

VA (Watts)	Ref. No.	Price £	P&P
60	149	5.75	85
100	150	6.40	100
200	151	10.00	110
250	152	11.95	130
350	153	14.45	140
1000	156	35.00	300

BAYDIS 54a Mortimer Street
Herne Bay, Kent
Herne Bay G458B

Complete digital clock kits

TEAK or PERSPEX CASE



Non alarm **£12.50**

Alarm **£15.50**

NON-ALARM

Complete Kit including case	£12.50
Ready built	£14.50
Module Kit excluding case	£9.50
Ready Built	£10.00

Features:

- 4 LED digits 1/2" high, red
- 12-hour display with AM/PM indication
- Mains frequency accuracy
- Easy-to-build: all components included
- Beautiful real wood case or Perspex; White, Black, Red, Blue, Green
- Flashes to indicate power cuts

ALARM

- Pulsed Alarm tone. Automatic Brightness control. 9 minute Snooze. Simple setting
- Complete Kit including case **£15.50**
- Ready Built **£17.00**
- Module Kit excluding case **£13.00**
- Ready Built **£13.50**

TIMER FACILITY: Stopwatch use up to 9 min. 59 secs. extra 50p

EXCELLENT VALUE

GUARANTEED

- National Semi. 5 Function LCD Watch. Backlight **£15.95**
- NOV5 850 Calculator £3.78. Adaptor £2.70.

DISPLAYS: FND 500 1/2" LED **£1.19** each, 6 for **£6.48**.
NSB 5430 1/2" red LED stick of 4 **£4.32** 5LT02 1/2" green phosphor stick of 4 **£5.40**

CLOCK CHIPS: 50253N Alarm 12/24 hr 4/6 digit	£5.67
50362N Calendar clock £7.75	MM5385N 12 hr. 4 digit Alarm £4.32
6 Decade Up/Down Counters: 50395/6/7	£9.45
MICROPROCESSOR: Z80 CPU	£22.68
Z80 CTC £15.70	1702A UV Erasable PROM £11.35
Z80 PIO £15.70	2102NA 1K Static RAM £2.70
UV PROM Eraser £103.00 + £5.00 p&p	4KX1 16 pin Dyn. RAM £7.05

RECHARGEABLE BATTERY SET. Super Value **£8.10**

Includes: 4 AA (1.2v) Nickel Cadmium batteries (separately £1.08 each)
3/6/9v switched Universal Mains Adaptor with 4 plug connector
for most calculators (separately £3.78) plus battery holder

ALPHA CLOCK KITS 1/2" Green Display, Perspex Case
Alarm **£15.50** Non-Alarm **£12.50**

Send payment with order. SAE for details



BARON
SOUTHVIEW HOUSE
6 GOWER ROAD
ROYSTON, HERTS.
Phone: Royston (0763) 43695



TEMPUS Specialists in electronic timekeeping

NEW FROM CASIO


A wide selection of the world's most advanced timepieces and superb Japanese quality.

INTRODUCTORY OFFER

Free with your new MQ-2. Spare batteries worth £1.30 (on request, with order).

NEW CASIO MQ-2

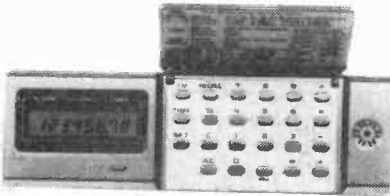Clock, plus Two Alarms, Alarm-Timer, Time Memory, Calendar, and Calculator.



24-hour Alarm and Alarm-Timer (with count-down). Time and Date calculations. LCD display. Around 18 months battery life. ± 15 seconds/month accuracy $\frac{3}{4} \times 4\% \times 1\frac{1}{2}''$ 1.6oz.


£34.95 including batteries and case. RRP £39.95.

NEW LOWER PRICE CASIO AQ810

Pocket Watch. Calculator
Two Way Timer
Alarm (24 hr.). 3000 hrs batteries
 $\frac{1}{4} \times 2\frac{3}{4} \times 4\frac{1}{4}''$.

£16.95 including batteries and wallet.

NEW OPTIM TRAVEL/ALARM CLOCK

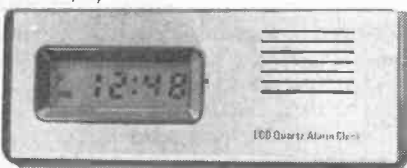

Portable. Battery powered. LCD display. Constantly displays hours, minutes, am and pm. Nightlight. STOPWATCH facility. 4 minute alarm with cancel switch (24 hr.). Brushed aluminium/black finish. $5 \times 1 \times 1\frac{3}{4}''$.

£19.90 including case

NEW LOW PRICES Fairchild Timaband

Mains digital alarm clocks

C500	C590
Black or	£22.95
White	C6110
£12.95	£13.95



Send 25p for our illustrated catalogue. Prices include VAT and P&P. Send your cheque, PO or phone card no. to:

TEMPUS

Dept. ET1, 19/21 Fitzroy Street, Cambridge. Tel. 0223 312866



31QR-17B
Probably the best value for money available today

£26.95
RRP £30.95

7+2 functions. Stopwatch. 8.4mm thick



31QS-12B
The best looking watch at a sensible price we have seen

£39.95
RRP £49.95

Stopwatch. Dual Time Zone. 7.7mm thick

38CS-14B CHRONOGRAPH

Up to 25 functions including 1st-2nd place times

£49.95
RRP £64.95

Six digit. 1/100 second. 7.9mm thick



CASIO watches have a constant LCD display of hours, minutes, seconds, am/pm with day, date and month on demand. With night light, automatic 28, 30, 31 day calendar, mineral glass face and all stainless steel cases, they are water resistant to 100 feet. One battery lasts approximately 12 months. Accurate to less than ± 15 seconds/month

WATCH BATTERIES 65p

Ray-O-Vac, long life. Fresh stock

D.I.Y. KIT 25p

(with battery order). Case opening tool, fits most watches. Plastic tweezers, chart, instructions.

BUILD THE TREASURE TRACER MK III



METAL LOCATOR

AS SEEN ON BBC-1 & BBC-2 TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit. 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components sited printed on.
- Complete after sales service.
- Weighs only 22oz.; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil

£15.95
Plus £1.20 P&P
Plus £1.37 VAT (8%)

Built, tested and Guaranteed

£20.95
Plus £1.20 P&P
Plus £1.77 VAT (8%)

MINIKITS ELECTRONICS,
6d Cleveland Road, South Woodford,
LONDON E18 2AN
(Mail order only)

WHITE LINE FOLLOWER

ETI's Project Team present here a project for either the modeller who wishes to go electronic, or the electronic enthusiast who wants an excuse for crawling around the carpet all weekend . . .



THE IDEA OF A SLOT CAR that doesn't need a slot is not new — in fact, sophisticated systems based on inductive loops have been used in large factories for some years. This project is at the other end of the complexity scale, and uses a simple light / photocell combination to follow a white line. The electronics involved make up a simple feedback control system — as soon as one photocell sees more light than the other, the differential amplifier applies a correcting voltage to the steering servomotor and so the model steers itself back on to the line.

We are not sure whether to class this project as a toy or as a serious experimental project. Certainly, the basic project makes a great toy, but there is tremendous scope for experimenting and 'tuning' the control circuitry. Like all control systems, this one displays a characteristic called 'damping' — if the system is overdamped, the car will steer sluggishly and will have difficulty following anything, except the smoothest curves. If the control circuitry is under-damped, the car

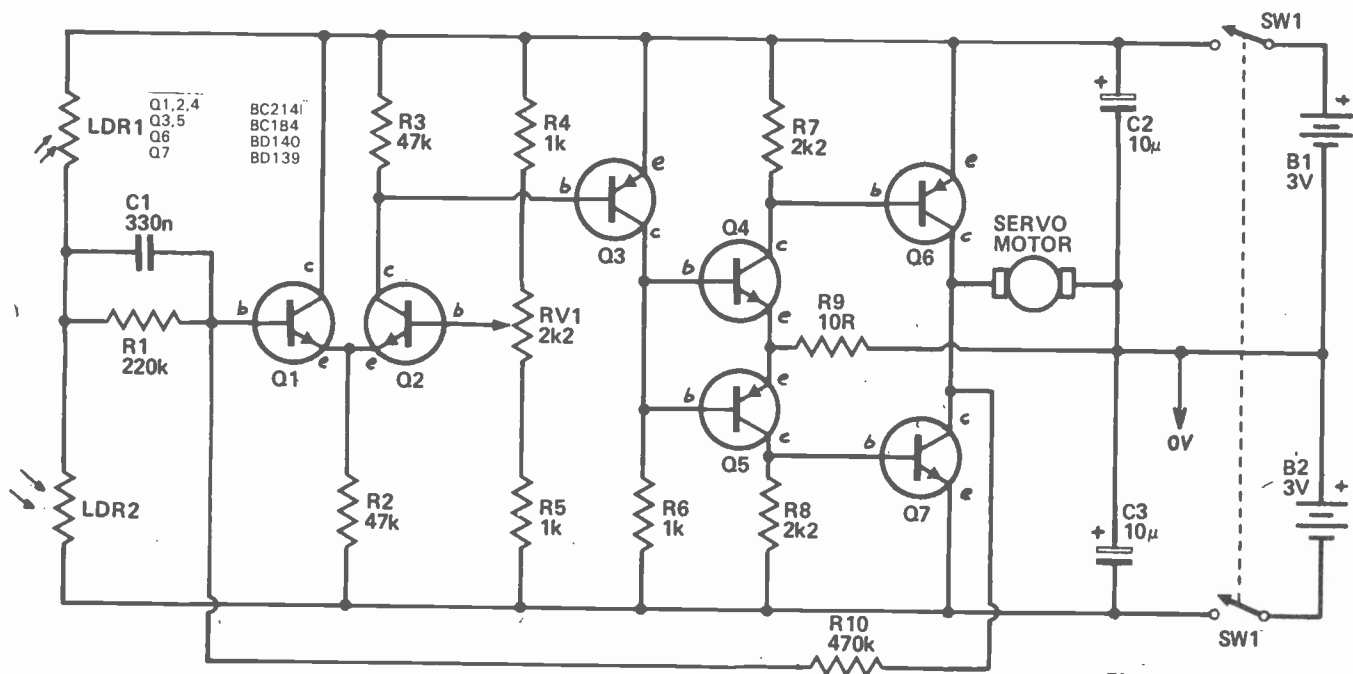


Figure 1. (Above) Circuit diagram of the white line follower unit.

HOW IT WORKS

The sensor used to look for the white line is a pair of light dependent resistors (LDRs) which are aimed at either side of the line so that each sees half white half dark. The line is illuminated by a bulb to ensure that the LDRs have a relatively low resistance. If the car is moved off the centre line one LDR will see more 'white' and its resistance will fall. The two LDRs are connected in series across the supply voltage and so the voltage at the junction will vary as the car moves in relation to the line.

This voltage is compared with that set on RV1 by Q1 and Q2, the error signal driving the servo motor in the correct direction to try to eliminate the error. Negative feedback is provided by R10 to reduce the 'open loop gain', and dynamic feedback is provided by C1 which is used to reduce overshoot.

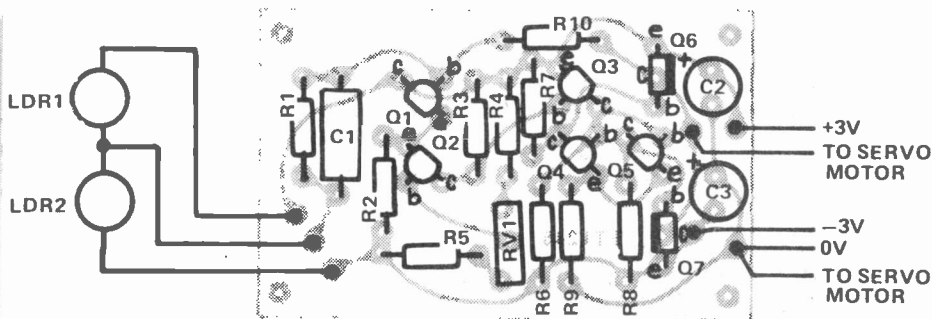


Figure 2. Component overlay. See text for details of mounting the board and servo motors within the model.

will oscillate from side to side on curves — this may also be set-off by small deviations on the straights.

The ideal situation is to have a 'critically damped' system, which has just the right combination of characteristics to respond quickly on curves without oversteering. This can be achieved by theoretical analysis, using techniques like Nyquist's Criterion, but it's more fun to tune by trial and error. The damping is a factor of the photocell spacing, the amplifier gain and the servomotor characteristics.

You can have a lot of fun racing these cars, especially since there is quite a bit of scope for tinkering and tuning them. The layout of your race track should include both smooth and tight curves — you may have problems with figure-8's that cross at anything but right angles. And of course you can time races with your ETI stopwatch!

Construction

The mechanical side of constructing the car we must leave to the individual reader. As we were more

interested in the electronics side of the project we tended to take short cuts as far as the mechanics go. The car we used was a Tamiya Porsche 935 Turbo, a model specifically designed for radio control applications but ideal for our application. No doubt the model enthusiasts amongst you will know of many other models that would prove suitable.

We cheated with the steering mechanism as well by using a commercial servo motor stripped of its electronics to provide control of ▶

PARTS LIST

RESISTORS

R1	220k
R2,3	47k
R4,5,6	1k
R7,8	2k2
R9	10R
R10	470k

LIGHT DEPENDENT RESISTORS

LDR1,2	ORP12
--------	-------

POTENTIOMETER

RV1	2k2 min vert
-----	--------------

CAPACITORS

C1	330 μ Polyester
C2,3	10 μ 10 V Electrolytic

SEMICONDUCTORS

Q1,2,4	BC214
Q3,5	BC184
Q6	BD140
Q7	BD139


MISCELLANEOUS

PCB as pattern, 3V bulb, 2-pole on/off switch, servo motor and car (see text)


On the right the Porsche with its lid off. The PCB is mounted behind the drive motor, which is sitting between the rear wheels. The servo is sited between the front wheels, and the board upon which we put the LDRs and bulb can be seen on the front of the chassis.

BUYLINES

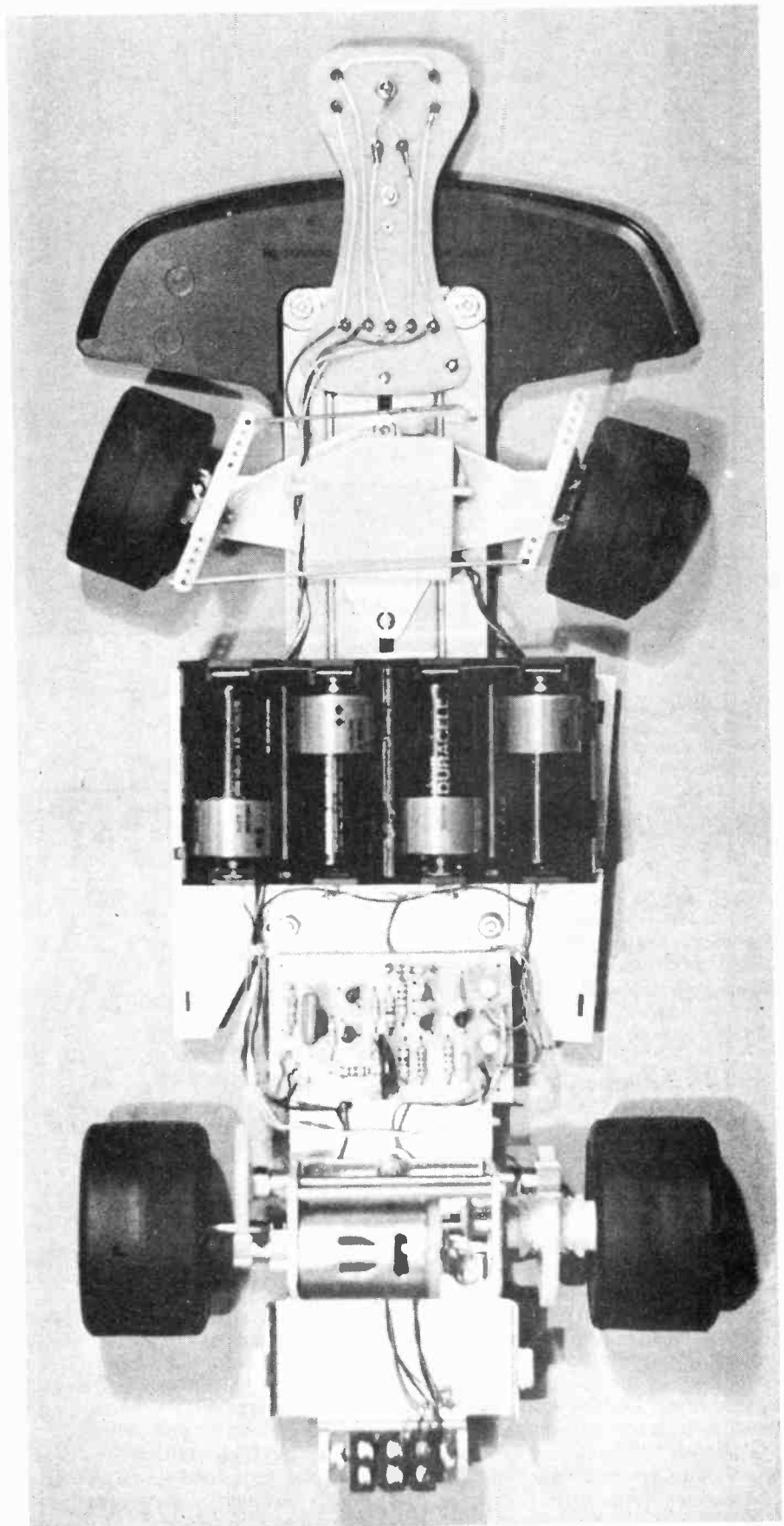
Purchasing the electronic components should prove straightforward. The mechanical parts are, as we say in the main text, a matter for the individual constructor.



PROJECT: Line Follower

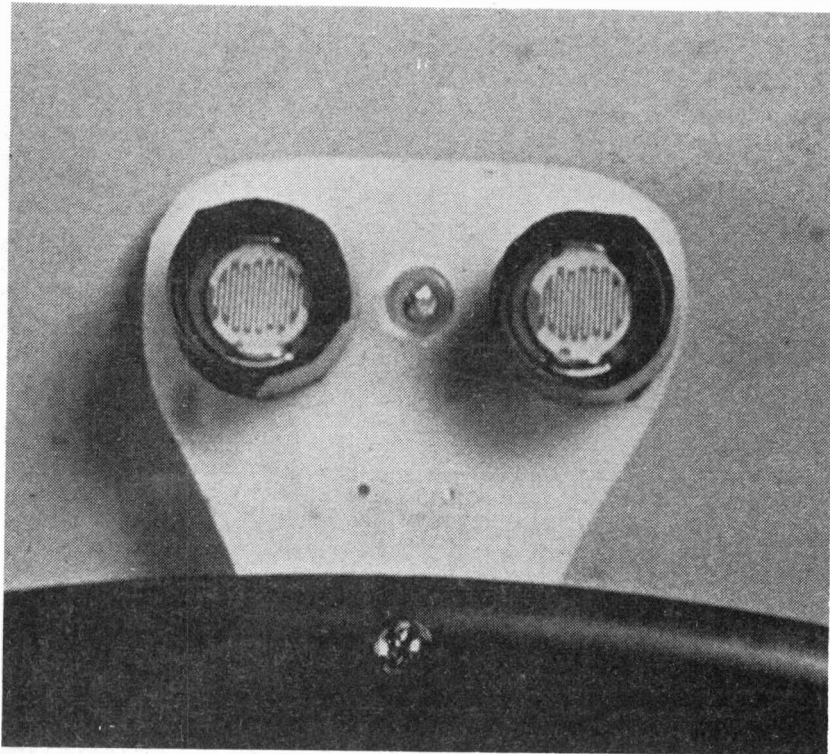

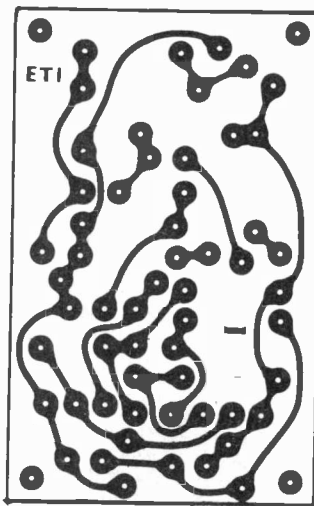Above: the eyes of the animal. The bulb lies right between the LDRs. On the right: the foil pattern for the white line follower circuit, shown full size.



the steering. Again for those with a mechanical bent, a standard model motor (one that will operate reliably on 1.5V) driving the front wheels via suitable links is probably the best bet.

Ideally the sensors should be mounted in front of the wheels and should move with them so that when the wheels turn to the right the sensor does likewise and visa versa (another test of mechanical ingenuity).

The LDRs were housed in short lengths (about 10 mm) of cardboard tube to act as a shield and were spaced about 15mm apart (we used a 12 mm wide line) with the bulb mounted between them.

Electrically the components can be built onto the PC board described which can be mounted somewhere in the car. We used separate batteries for the electronics and ran the bulb off the main batteries, to keep the electronics supply more constant.

Experimenting

Using different motors/gear ratios some changes to the electronics will probably be found necessary. These would mainly involve C1, R1 and R10. Increasing R10 or reducing R1 increases the DC gain, while increasing C1 increases the dynamic damping to reduce overshoot. Track width may also be experimented with as well as LDR spacing.

ETI

THE NORTH'S PREMIER AMATEUR RADIO & ELECTRONICS EVENT!

Northern
Radio Societies Association

RADIO & ELECTRONICS EXHIBITION

BELLE VUE—
MANCHESTER

SUNDAY, 2nd
APRIL, 1978

Doors open at 11 a.m.

- ★ INTER-CLUB QUIZ
- ★ CONSTRUCTION CONTEST
- ★ RSGB BOOKSTALL
- ★ GRAND RAFFLE
- ★ AMATEUR COMPUTER CLUB STAND
- ★ RADIO SOCIETIES STANDS
- ★ CLUB STAND TROPHY
- ★ HOME OFFICE & RAYNET EXHIBITS
- ★ TRADE STANDS FEATURING RADIO EQUIPMENT, MICRO-PROCESSORS, PERSONAL COMPUTERS AND COMPONENTS
- ★ AMPLE CAR PARKS AND LEISURE FACILITIES FOR THE FAMILY INCLUDING FUNFAIR!

Talk-in for FM mobiles via GB3NRS and G8NRS/A on 145 MHz chs. S22 SO & R6 and on 433 MHz chs. SU8 SU20 RB4 & RB14.

ENTER AT REAR OF BELLE VUE, OPPOSITE MAIN CAR PARK—OFF HYDE ROAD, A57.

NOW—A VDU BOARD

WITHOUT KEYBOARD AND NO DISPLAY

A double-sided board with plated through holes 12½" x 8" (4 Eurocard size). 960 Characters in a 40x24 line format. 64 ASCII characters. Flashing cursor. 32 control functions available. Adjustable baud rate. Provision for a keyboard. Serial input and output. Requires + 5V and - 12V and any modified television or video monitor. Board is crystal controlled to give a rock steady display. Supplied in kit form (All components supplied) **£95**. P&P £1.75. Assembled and tested **£125**. P&P £1.75.

<p>MARCONI VALVE VOLTMETER TF428B NOW £12.50 ea.</p>	<p>FURZEHILL EX-MINISTRY AUDIO GENERATOR 0-20KHZ Sinewave output. Metered. 600 Ohms. Size 16x10x9" deep. Standard mains now at £15 each</p>	<p>EX-MINISTRY MARCONI 0-6 WATTS Multi Range. Multi Impedance POWER METERS. £25 each</p>	<p>ITT-CREED Punches and Prints on 7/8" paper. Complete with Power Supply. Solid State. Size 15x11¾x22" deep £32.50.</p>
<p>★ I.C. BOARD PACK 50 I.C.s and other useful components for £1 P&P 75p</p>	<p>★ SEMICONDUCTOR PACK Guaranteed full spec. devices make up this pack. (No large quantities warrant individual advertising) 50 devices for £1 P&P 40p Highly Recommended</p>	<p>MARCONI R.F. POWER METER Type TF 1152A/1 (CT419) 2 ranges 10 watts fsd and 25 watts fsd. 50 ohms £75 each</p>	<p>TRIPODS WITH PAN AND TILT HEAD will take 56lb load £22.50</p>
<p>TRANSFORMERS — All 240V 50HZ INPUTS Type A170 17V 250MA 7 5 0 7 5V 250MA 0-20V 5 Amps 0.4V5 Amps 0.11 5V Amps £2 each. P&P £1.25. Type C 19.0-19V 250MA. 8-0 8V 250MA 0-7 5V Amps 0-1 4V 5 Amps £1.25 each P&P £1.25. All brand new APT Surplus.</p>	<p style="text-align: center;">PICK-A-PACK— 50 PENCE A POUND</p> <p>From Our Pick-A-Pack area weight up your own components. No restrictions on what you take.</p>		<p>TELEPHONES. Post Office style 745. Black or two-tone £6.50 ea. Modern style 706. Black or two-tone grey £4.50 ea. P&P £1 each. Old black style £1.50 ea. P&P £1. *HANDSETS only 706 style £1.75 ea. Older style £1 P&P 75p. TELEPHONE EXCHANGES. Eg. 15-way automatic (exchange only) from £95. MODERN FANS. 4¼ x 4½ x 1½" 110 volts. Superbly quiet. 6 blades £4.50 ea. P&P 75p. PAPST Fan 240V available at £7.50 ea. P&P 75p. TUBES. All Brand New Boxed Electrostatic deflection. Type GEC 924F 3½" dia. (Replacement for Telequipment D33 & Solartron 1016 scopès) £25 ea. P&P £1.50. Type GEC 924E 3½" dia (Replacement for Solartron 1015 scope) £17.50 ea. P&P £1.50. *1000F Feed thru Capacitors 10 for 30p. P&P 15p. HIVAC Miniature NEONS. App 60V Brand New 10 off 20p P&P extra. GRATICULES 12x14cm high quality plastic 15 ea. P&P 10p. MARCONI TF1041B Valve Voltmeter £25 ea. MARCONI TF338B Attenuator 600 ohms £12 ea. PHILIPS Cassettes Model 2200. Play only £9 ea. P&P £1.50. PROGRAMMABLE TIMER 5 decade (Photography) £8 ea.</p>
<p>*POT PACK. All Brand New Modern Single and Ganged. Our choice 7 for 25p. P&P 48p. Ex-ministry OSCILLOSCOPE. CT436. Double beam. DC 6MHZ £120 each. SOLARTRON CD 1212 SB 40 meg £100. DB 24 meg twice £135. Many other types available. MARCONI SIGNAL GENERATORS. Freq. range 10-470MHZ Type TF80 1B3/S £160 each. MARCONI TF142F DISTORTION FACTOR METER giving percentage distortion on a directly calibrated dial and includes any spurious components up to 30kHz £29.50 each. MARCONI PORTABLE FREQUENCY METER TF 1026/11 100 to 160MHZ. Very fine condition £25. TF1026/4M 2.4 GHz £35 each.</p>	<p>PHOTOMULTIPLIER Type 931A £4 ea. P&P 75p. Other types available. *POTENTIOMETERS — All 5p ea. P&P extra. Metal bodies AB Linear. PCB Mount Brand new. 250K ganged. 100K ganged concentric shafts. *BEEHIVE TRIMMERS 3 30pt Brand New 10 off 40p P&P 15p. 100 off £3.50 P&P 75p. 500 off £15 P&P £1.25. 1,000 off £25 P&P £1.50. LARGE RANGE OF ELECTROSTATIC VOLT-METERS. From 0.300V 2 £3, or 250KV Max. General guide 5KV 3½. £5. Thereafter £1 per KV. P&P 75p. DON'T FORGET YOUR MANUALS. S.A.E. with requirements. TUBE Type DB7 36 — Replacement for Teleequipments S31 £11 ea. P&P £1.50. E.H.T. TRANSFORMERS 20KV 2KVA £70 ea. 240KV SINGLE PHASE 20KVA Output 2x2 5KV £85. 240V SINGLE PHASE. 1KVA Output 40KV 25MA £175. Many other EHT Transformers and EHT Capacitors available.</p>		<p>MULLARD & BRIMAR OSCILLOSCOPE TUBES BRAND NEW BOXED—ALL RECTANGULAR D14-121 Green 50MHZ Y 4 4.2V CM £45 ea. As above but P7 Phosphor £35 ea. D13-46GM P7 £35 ea. D13-51GH Green £65 ea. D10-210GH/32 £40 ea. Carriage all tubes £1.75 ea.</p>
<p>TRANSISTORS/DIODES/RECTIFIERS, ETC. Guaranteed all full spec. devices. Manufacturers Markings. At 5p each. BC147, 2N3707, BC172B, BC261; BC251B, BC348B, BC171A/B, BC413; D10, BC182, BC212; BAX13, 1N937; BA102BE, BZX83, 2N4047, TIS61, 2N5040 At 10p each BFX85, 1N4733A, SN7451N; BYX10-1, 5KV 0.36A. TIP30 — 20p ea. TIP34A — 50p ea. BD538 — 40p ea. Heavy Duty Bridge Rectifier — 20p ea. TBA810S — 75p ea. CA3123E — £1 ea. BDY55 — £1 ea. TIP318 — 12p ea. 2N3055 — 40p ea. 2N5879 with 2N5881 Motorola 150W Comp pair 2 ea. BD535/BD538 Comp pair — 75p ea. BYZ10 10p ea. LM733CN 20p ea. TBA560CQ £2 ea. 1N4436T-TO3 Flat mount 10A 200piv £1 ea. *Linear Amp 709 — 25p ea. High Speed Voltage Comparator 710 — 15p ea. P&P Extra on all items. Finned heat sink — single TO3 — size 4¼in x 3in x 1¼in 50p ea. P&P 75p.</p>	<p>EX-DYNAMCO Oscilloscopes INVERTORS 30V Input 6KV Output. Size 2" x 4½" x 1½". Complete with circuit £10 ea. P&P £1.</p>		<p>SOLID STATE TIMEBASES By LARGE BRITISH MANUFACTURERS These are a Plug-in Modular Timebase covering 0-2 microseconds per cm to 5 secs per cm in 23 steps. Tunnel Diode triggering. 8 Front Panel Controls. 37 Transistors/FETs — all plug-in Silver anodised front panel. Size 4x5½x10½" deep. Guaranteed absolutely brand new in original manufacturer's packaging. Complete with extremely comprehensive copy of manual £17.50 ea. P&P £2.</p>
<p>FRESH MINISTRY RELEASE Solartron CT316 oscilloscope DC — 6 megs. Size 8½" x 11" x 20" Sorry £37.50 this time</p>	<p style="text-align: center;">NEW INTAKE OF TEKTRONIX 545A</p> <p>Oscilloscope with CA plug-in (Dual Beam — 24 megs) £220 each</p>		<p>COSSOR OSCILLOSCOPE CAMERAS Brand New Boxed with 4 film packs & Manual £12 ea. Carriage £2.75.</p>
<p style="text-align: center;">BACK IN STOCK — CREED 7B TELEPRINTERS</p> <p style="text-align: center;">THE CHEAPEST WAY OF GETTING A FULL ALPHA/NUMERIC PRINTOUT FROM YOUR MICRO</p> <p>Large Ministry purchases enables us to offer these at £25 each In good working condition. Requires 110 Volts DC. Requires ASC11/BAUDET convertor for coupling to your microprocessor. These units are Processor tested before dispatch. Circuits included. Adequately packed to guarantee safe arrival for £3.25.</p>			
<p>TELETYPE ASR 33 from £450. TELETYPE KSR33 £275. NON-STANDARD KSR33 eg basic ASC11-20MA loop — but small print 0 to 9 above standard 0 to 9, some of the symbols having been relocated. £250.</p>			
<p>TELETYPE 35 RO Cased £95. TELETYPE 35 RO with 20MA interface. Few only £120 ea.</p>			
<p>LITTON SYSTEM — Must go — £375 or offer.</p>			

Minimum Mail Order £2. Excess postage refunded. Unless stated — please add **£2.75** carriage to all units
VALUE ADDED TAX not included in prices — Goods marked with * 12½ % VAT, otherwise 8 %
Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order.
Open 9 a.m. to 5.30 p.m. Mon. to Sat.



CHILTMEAD LTD




7/9 ARTHUR ROAD, READING, BERKS (near Tech. College, King's Road). Tel. Reading 582605.

SERVICE TRADING CO

WHY PAY MORE?!

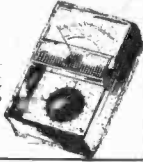MULTI RANGE METERS Type MF15A A.C./D.C. volts 10. 50 250 500 1000. Ma 0.5 0-10 0-100. Sensitivity 2000V. 24 range, diameter 133 x 93 x 46mm. Price **£6.50** plus 50p P&P (**£7.56** inc. VAT & P)



TRIAC.

Raytheon tag symmetrical Triac. Type Tag 250/500v. 10 amp 500 p.w. Glass passivated plastic triac. Swiss precision product for long term reliability. **£1.25** P&P 10p (**£1.46** inc. VAT & P) (inclusive of date and application sheet). Suitable Diac **22p**.

0 to 60 MINUTES CLOCKWORK TIMER.

Double pole 15 amp 230AC. Contacts (no dial). **£1.50**, P&P 30p (**£1.94** inc. VAT & P).

MERCURY SWITCH

Size 27mm x 5mm. 10 for **£5.00** (inc. VAT **£5.72**) Min quantity 10.



CONTACTOR

Mfg. by Hendry Relays. type C2839 220/250 AC ops. Contact 4C/O at 20 amp at 440 volts AC. Price **£6.00** P&P 75p (**£7.29** inc. VAT & P)




230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete with 5 blade 6 1/2" aluminium fan. New reduced price **£3.00** P&P 65p (**£3.94** inc. VAT & P).



21-WAY SELECTOR SWITCH with reset coil

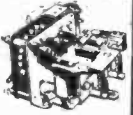The ingenious electro mechanical device can be switched up to 21 positions and can be reset from any position by engaging the reset coil. 230/240V. A.C. operation. Unit is mounted on strong chassis. Complete with cover. Price **£5.50** P&P 75p (**£6.75** inc. VAT & P).



VORTEX BLOWER AND VACUUM UNIT


Dynamically balanced to fully enclosed 9" rotor with max. air delivery of 1.5 cubic metres per min. Max static pressure 600mm WG. Suction or blow from 2 side-by-side 37mm I.D. circular apertures fitted to base of unit. Powerful continuously rated 115v a.c. motor mounted on alloy base with fixing facilities. Dimensions: Length 22cm x width 25cm x height 25cm.



These units are ex-equipment but have had minimum use. Fully tested prior to despatch. Price **£12** + **£1.50** P&P (**£14.58** inc. VAT & P). Suitable transformer for 230/240v a.c. **£6** + **£1** P&P (**£7.56** inc. VAT & P).

CENTRIFUGAL BLOWER

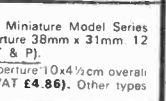
Mfg. by Smiths Industries 230/240v a.c. Miniature Model Series SE7200. Size 95mm x 82mm x 82mm. Aperture 38mm x 31mm. 12 c/f m. **£2.75**, Post 50p (**£3.51** inc. VAT & P).
Suff. type FB 1906 022 220/240v a.c. Aperture 10x4 1/2 cm overall size 16x14cm Price **£3.75** p&P 75p (inc. VAT **£4.86**). Other types available phone for details.



NI-CAD BATTERIES

	Height (mm)	Width (mm)	Length (mm)
23 AH 1.2v Plastic Case	14	214	79
35 AH 1.2v Metal	16.50	219	75
40 AH 1.2v Plastic Case	18	275	80

Postage 30p per unit

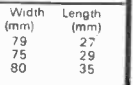

UNISELECTOR SWITCH

4 bank, 25 way 75 ohm coil. 36-48v O.C. operation. Ex. new equipment. **£4.25**, P&P 75p. Total price inc. VAT **£5.40**.




MINIATURE UNISELECTOR

12v 11 way 4 bank (3 non-bridging, 1 homing). **£2.50** P&P 35p (**£3.08** inc. VAT & P).




MICRO SWITCHES

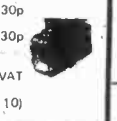As illustrated but fitted with 1" Lever. 10 for **£2.00** P&P 30p (**£2.48** inc. VAT & P).
Sub-miniature Burgess type v 41 1. 10 for **£2.50** P&P 30p (**£3.02** inc. VAT & P).
50 for **£10.00** post paid (**£10.80** inc. VAT & P)
Type 3 J15M 906T 10 for **£2.50** post paid (**£2.70** inc. VAT & P).
Unimax USA. 10 for **£4.00** plus 50p P&P (min. order 10) (**£4.86** inc. VAT & P).



NEW HEAVY DUTY SOLENOID

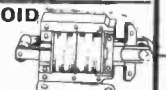Mfg. by Magnetic Devices 240v AC. Operation approx. 20lb. pull at 1.25". Price **£7.00** P&P 75p (**£8.37** inc. VAT & P).
Similar to above approx. 10lb pull **£3.50** P&P 60p (**£4.43** inc. VAT & P).



230-250 VOLT A.C. SOLENOID

Similar in appearance to illustration. Approximately 1 1/2 lb. pull. Size of feet 1 3/4" x 13/16". Price **£1.00** Post 25p (**£1.35** inc. VAT & P).



24 VOLT D.C. SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25 lb. pull at 1 in travel. 2 solenoids of approx. 7 lb. pull at 1/2 in travel. 6 solenoids of approx. 4 oz. pull at 1/2 in travel. Plus 1 24V D.C. 1 heavy duty 1 make relay. Price **£3.00** Post **£1.00** (**£4.32** inc. VAT & P).



ABSOLUTE BARGAIN

240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring 1/2 in. b.s.p. inlet outlet. Precision made. British mfg. PRICE **£2.75** Post 50p (**£3.57** inc. VAT & P).



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 v. A.C. 50/60

OUTPUT VARIABLE 0/260V. A.C.

BRAND NEW. All types.

200W (1 Amp) fitted A/C

volt meter **£12.50**

0.5 KVA (Max. 2 1/2 Amp) **£15.00**

1 KVA (Max. 5 Amp) **£19.50**

2 KVA (Max. 10 Amp) **£32.00**

3 KVA (Max. 15 Amp) **£39.50**

4 KVA (Max. 20 Amp) **£60.00**



Carriage extra

LT TRANSFORMERS

0-12v/24v at 1 amp. **£2.50** p&P 50p (**£3.24** inc. VAT & P)

0-15v at 1 amp + 0-15v at 1 amp (30v 1 amp) **£2.50** p&P **£3.24** inc. VAT & P

25-0-25v at 2 1/2 amp. **£4.50** p&P 75p (**£5.67** inc. VAT & P)

0-12v/24v. 10 amp. **£12.35** p&P **£1.50** (**£14.96** inc. VAT & P)

0-4v/6v/24v/32v at 12 amp. **£13.00** p&P **£1.50** (**£15.66** inc. VAT & P)

0-12v at 20 amp. or 0-24v at 10 amp. **£12.00** p&P **£1.50** (**£15.01** inc. VAT & P)

0-6v/12v/17v/18v/20v at 20 amp. **£14.00** p&P **£1.50** (**£16.74** inc. VAT & P)

0-6v/12v at 20 amp. **£11.85** p&P **£1.00** (**£13.88** inc. VAT & P)

Other types in stock. phone in enquiries

300 V.A. ISOLATING TRANSFORMER

115/230 screened primary, two separate or 115v for 115 or 230v. Secondary two 115v at 150 V.A. each for 115 or 230v output. Can be used in series or parallel connections. Fully transformer. Length 13.5cm. width 11cm. weight 15lbs. Special price **£6.00**, carr. **£1.00** (**£7.56** inc. VAT & P).

COMPRESSOR, precision built by Emerson USA

Horizontally opposed twin head diaphragm type producing 20lbs. Plus P.S.I. per head 3.5 plus C.F.M. Output virtually pulse free. Powered by 110v A.C. motor size 30x23x15cm weight 7 kilos. Price **£20** p&P **£2.00** inc. VAT **£23.76**. Suitable transformer for 230/240v a.c. **£8.00** p&P **£1.00** inc. VAT **£9.72**.

STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT MK. IV

Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s. Designed for large rooms, halls, etc. Light output greater than many (so called 4 Joule) strobes. Mini 12in. 8 watt **£2.50**, Post 25p. (**£2.97** inc. VAT & P). 9in. 6 watt **£2.00** Post 25p (**£2.43** inc. VAT & P). 6in. 4 watt **£1.75** Post 25p (**£2.16** inc. VAT & P). Complete ballast unit. Either 6", 9" or 12" tube 230V. A.C. op. **£3.50** plus P&P 40p (**£4.21** inc. VAT & P). Also available for 12V. D.C. op. **£3.50** plus P&P 40p (**£4.21** inc. VAT & P).

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 watt **£7.75** (callers only). 2ft. 20 watt **£5.50**, Post 80p. (For use in stan bi-pin fittings). Mini 12in. 8 watt **£2.50**, Post 25p. (**£2.97** inc. VAT & P). 9in. 6 watt **£2.00** Post 25p (**£2.43** inc. VAT & P). 6in. 4 watt **£1.75** Post 25p (**£2.16** inc. VAT & P). Complete ballast unit. Either 6", 9" or 12" tube 230V. A.C. op. **£3.50** plus P&P 40p (**£4.21** inc. VAT & P). Also available for 12V. D.C. op. **£3.50** plus P&P 40p (**£4.21** inc. VAT & P).

XENON FLASH GUN TUBES

Range of Xenon tubes available from stock. S.A.E. for full details

RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries.

230/240V A.C. Relays: Arrow. 2 c/o. 15 amp **£1.50** (**£1.84** inc. VAT & P).

T.E.C. open type 3 c/o. 10 amp **£1.10** (**£1.40** inc. VAT & P). Mag Devices 2 c/o. 20 amp **£1.50** (**£1.84** inc. VAT & P). Omron or Keyswitch 1 c/o. 7 amp **£1.00** (**£1.30** inc. VAT & P).

D.C. Relays: Open type 9/12V 3 c/o 7 amp **£1.00** (**£1.30** inc. VAT & P). Sealed 12V 1 c/o 7 amp **£1.10** (**£1.40** inc. VAT & P). Sealed 12V 2 c/o 7 amp octal base. **£1.25** (**£1.56** inc. VAT & P). Sealed 12V 3 c/o 7 amp 11-pin. **£1.35** (**£1.67** inc. VAT & P). 24V Sealed 3 c/o 7 amp 11-pin **£1.35** (**£1.67** inc. VAT & P) (amps = Contact rating). P&P on any Relay 20p.

Other types available - phone for details.

RESET COUNTER

230 volts AC 3 digits mfg. Vaeder Root type LL/144L **£1.75** P&P 25p (**£2.16** inc. VAT & P).
7 fig 24v d.c. non set **£1.50** P&P 25p (**£1.89** inc. VAT & P).
6 fig 24v d.c. resettable **£3.00** P&P 25p (**£3.51** inc. VAT & P).




BIG INCH

Tiny precision built 3 rpm USA motor size only 1 x 1 100 volt AC op. supplied with resistor for 230 volt AC price **£2.37** 20p 4 for **£5.40** post paid.



INSULATION TESTERS (NEW)

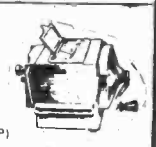Test to I.E.E. spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L 8 in. W 4 in. H 6 in., weight 6 lb. 500 VOLTS 500 megohms **£49.00** Post 80p (**£57.78** inc. VAT & P)
1000 VOLTS 1000 megohms **£46.00** Post 80p (**£60.26** inc. VAT & P)
SAE for leaflet.



VAT AT CURRENT RATE MUST BE ADDED TO ALL ORDERS
FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED
ACCOUNT CUSTOMERS MIN. ORDER **£10.00**

GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

115 lb. ins. 110 volt. 50Hz. 2.8 amp. single phase. split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled. In-line gearbox. Length 250mm. Dia. 135mm. Spindle Dia. 15.5mm Length 145mm. Ex-equipment tested **£12.00** Post **£1.50** (**£14.58** inc. VAT & P). Suitable transformer 230/240 volt **£8.00** Post 75p (**£9.45** inc. VAT & P).



BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 38 amp. This U.S.A. motor is offered in with transformer for 230/240v AC. input Price type **£8.25** Post 75p (**£9.75** inc. VAT & P). or less transformer **£3.75** Post 65p (**£4.75** inc. VAT & P). (Type 3) 71 r.p.m. 230 volt A.C. Continuously rated. Non reversible **£8.50** Post 75p (**£9.83** inc. VAT & P).



FRACMO

30rpm 50lbs. inch 240VAC reversible 0.7 amp sharp length 35mm dia. 10mm. weight 6 kilos 600 grams Price **£15.00** P&P 1.50 (**£17.82**).



PARVALUX GEARED MOTOR

type SD18 24v AC reversible 3u rpm 50lbs inch Price **£15.00** P&P 1.50 **£17.82** inc. VAT



A.E.G. WATER PUMP

200/240v a.c. motor. 2850 rpm. 480w approx. 1/2 hp. driving a centrifugal pump with 1 1/2" inlet and outlet delivering approx. 40 gals per min at 10ft head. Ideal for pumping or circulating any non corrosive light viscosity liquid. Dozens of uses in industrial labs. etc. Note this pump is not self-priming. Price **£15** + 75p P&P (**£17.01** inc. VAT & P).



CITENCO 19 RPM

FHP motor type C 7333/15 220/240v a.c. 19 rpm reversible motor. torque 14.5 kg. Gear ratio 144:1 Brand new incl. capacitor. our price **£14.25** + **£1.25** P&P (**£16.20** inc. VAT & P).



REVERSIBLE MOTOR 230V A.C.

General Electric 230v A.C. 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor O/A size 110mm x 95mm Spindle 5/16" dia. 20mm long. Ex-equipment tested. **£3.00** Post 50p (**£3.78** inc. VAT & P).



METERS 90mm Diameter

D. Amperes type 0-2A U.S.A. 0-20A 0-50A 0-100A A.C. Amperes type 0-12 U.S.A. 0-50A DC Volts type 0-50V 0-150V 0-300V All at **£3.50** P&P 50p. **£4.32** inc. VAT



'VENNER TYPE' ERD TIME SWITCH

200/250V A.C. 2 on/2 off every 24 hrs. at any manually pre-set time. 36 hour spring reserve and day omitting device. Built to highest Electricity Board specification. Price **£7.75** P&P 75p (**£9.18**).




SANGAMO WESTON TIME SWITCH

115v 25/1 20/2 230/240v a.c. 2 on/2 off every 24 hours. 20 amp contacts with overvoltage switch dimmer 4 x 3" price **£6.00** P&P 50p **£7.02** inc. VAT & P. Also available with solar timer.



A.E.G. TIME SWITCH

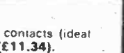200/250V A.C. 1 on/1 off every 24 hrs. 80 amp contacts (ideal storage heater). spring reserve. Price **£10.00** P&P 50p (**£11.34**).




A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders. Lights. Electric Blankets etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price **£2.25**. Post 40p. (Total inc. VAT & Post **£2.87**).



POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
25 WATT 10 25 100 150 250 500 1k 1.5k ohm **£2.40** Post 20p (**£2.81** inc. VAT & P). 50 WATT 100 500 1k ohm **£2.90** Post 25p (**£3.40** inc. VAT & P). 100 WATT 1/5 10/25 100/250 500/1k 1.5k/2.5k/5k ohm **£5.50**. Post 35p (**£6.32** inc. VAT & P).
Black Silver Skirted knob calibrated in Nos. 1-9. 1/2 in. dia brass bush. Ideal for above Rheostats. 24p ea.

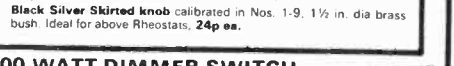

600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600w of lighting except fluorescent at mains voltage. Complete with simple instructions. **£3.95** Post 25p (**£4.53** inc. VAT & P). 1000 watt model **£5.60** Post 25p (**£6.32** inc. VAT & P). 2000 watt model **£9.75** Post 40p (**£10.96** inc. VAT & P).





OP-AMPS PART 3

Continuing along Tim Orr's circuit strewn path through op-amps

Simple Musical Chime Generator

The circuit shown is that of a multiple feedback band-pass filter. The preset is used to add some positive feedback and so further increase the Q factor. The principle of operation is as follows. A short click (pulse), is applied to the filter and this makes it ring with a frequency which is its natural resonance frequency. The oscillations die away exponentially with respect to time and in doing so closely resemble many naturally occurring percussive or plucked sounds. The higher the Q the longer the decay time constant. High frequency resonances resemble chimes, whereas lower frequencies sound like claves or bongos. By arranging several of these circuits, all with different tuning, to be driven by pulses from a rhythm generator an interesting pattern of sounds can be produced. There may be some stability problems when high Q or high frequency operation is involved. To achieve better performance, an op-amp with a greater bandwidth than the 741 should be used. Alternatively, a different structure, such as a state variable filter could be used. Qs of up to 500 can be obtained with this latter circuit.

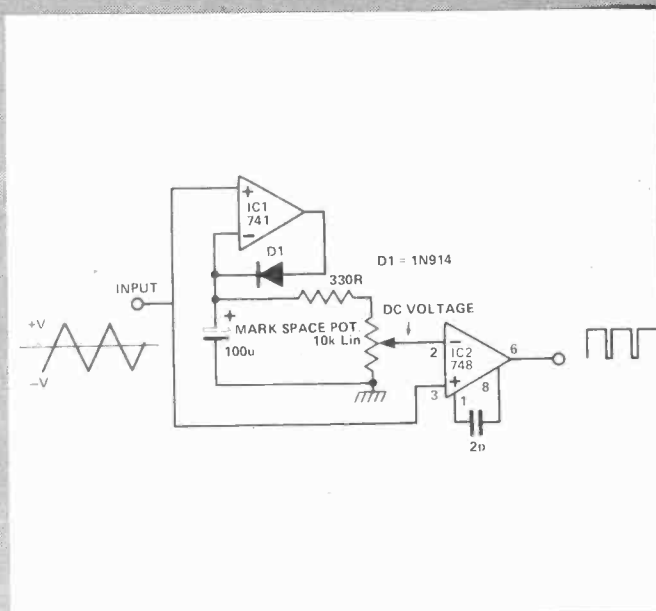
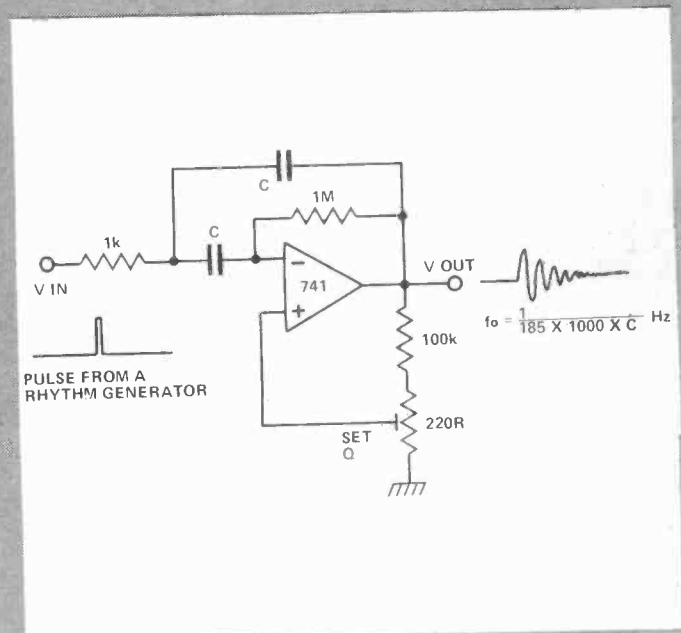


Variable Markspace Squarewave Generator with Automatic Level Adjustment

By putting a triangle wave into one input of a comparator and a manually controlled DC level into the other, it is possible to generate a variable ratio mark/ space square wave. However, if the amplitude of the triangle varies then so will the markspace ratio. Alternatively, if you want the manual control to produce a very thin waveform at one end of its travel, then you will probably need a preset and a very stable triangle amplitude. However, this circuit solves these problems. The DC voltage is generated by a peak voltage follower, IC1, driven by the triangle itself. Thus the circuit tracks the peak voltage level. Secondly, only 97% of this voltage is ever fed to the comparator, IC2, and so at the end of the markspace pot, a 60:1 ratio square wave is generated. At the other end of the pot the ratio is 1:1. A 748 is used as the comparator because it has more bandwidth than the 741. As the frequency of the triangle increases, it may be necessary to use an even faster op-amp for IC2 or even a comparator.

Simple Triangle to Sinewave Converter

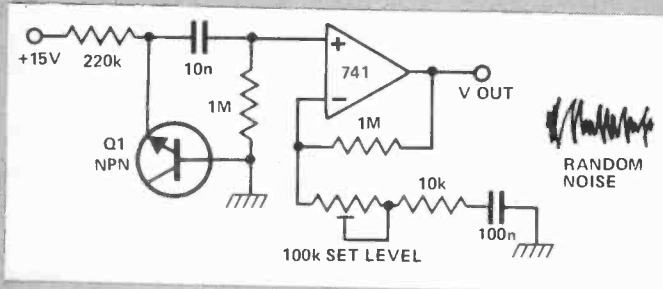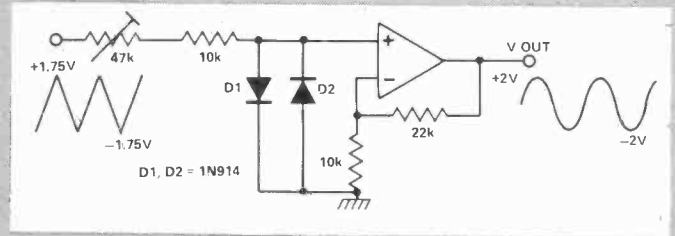A simple way of converting a triangle to a sinewave is shown. The logarithmic characteristic of the diodes is used to approximate to that of a sine curve. The distortion to be expected is of the order of 5%. However, the distortion may be tolerable if the sinewave is only used to generate audio tones.





Noise Generator

The zener breakdown of a transistor junction is used in many circuits as a noise generator. The breakdown mechanism is random and so generates a small noise voltage. Also this voltage has a high source impedance. By using the op-amp as a high input impedance, high AC gain amplifier, a low impedance, large signal noise source is obtained. The preset is used to set the noise level by varying the gain from 40 to 20 dB.

Logarithmic Voltage to Voltage Converter

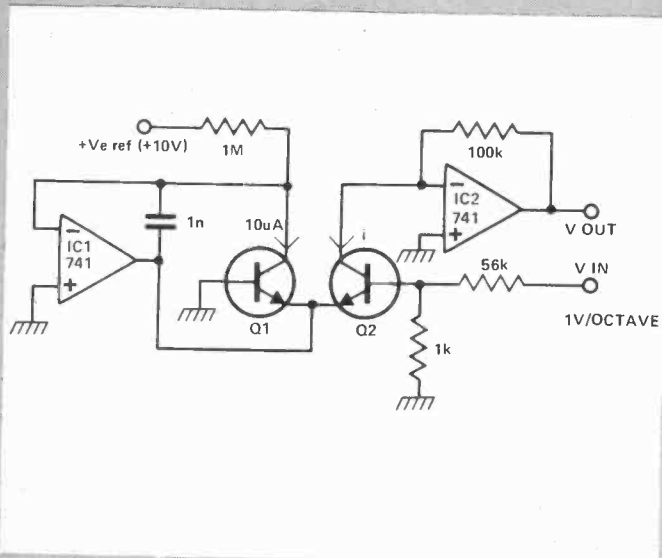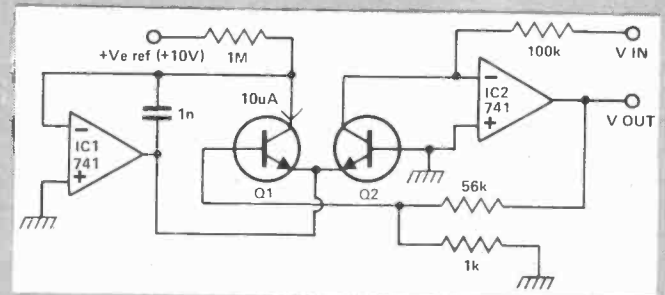The output voltage is logarithmically proportional to the input voltage. The difference between this circuit and the previous is that the exponentiator is in the feedback loop of the op-amp and hence the mathematical function has been inverted. The circuit is useful for performing true logarithmic compression or for converting linear inputs into dBs.



Exponential Voltage to Current/Voltage Converter



The circuit shown converts a linear input voltage into an exponential current or voltage. This type of circuit is used in music synthesizers to change linear control voltages into musical intervals. That is, if the circuit were used to control an oscillator, input increments of 1 V would change the pitch by one octave. The exponential characteristics of a transistor are employed to generate the correct transfer function. Q1 and Q2 are a matched pairs of transistors, preferably a transistor dual. IC1 maintains Q1 at a constant current. Thus, the op-amp serves only to bias the emitter of the second transistor Q2 into a suitable operating region. The purpose of Q1 is to generate this bias voltage. The base emitter junction of a transistor has a high temperature coefficient ($-1.9 \text{ mV}/^\circ\text{C}$) and so the reason for using a matched pair is to use the first transistor, Q1, to provide temperature compensation for the second.

Musical Envelope Generator and Modulator

A gate voltage is applied to initiate the proceedings. When the gate voltage is in the ON state, Q1 is turned on, and so the capacitor C is charged up via the attack pot in series with the 1K resistor. By varying this pot, the attack time constant can be manipulated. A fast attack gives a percussive sound, a slow attack the affect of 'backward' sounds. When the gate voltage returns to its off state, Q2 is turned on and the capacitor is then discharged via the decay pot and the other 1K resistor, to ground. Thus the decay time constant of the envelope is also variable.

This envelope is buffered by IC1, a high impedance voltage follower and applied to Q3 which is being used as a transistor chopper. A musical tone in the form of a squarewave is connected to the base of Q3. This turns the transistor on or off and thus the envelope is chopped up at regular intervals, the intervals being determined by the pitch of the squarewave.

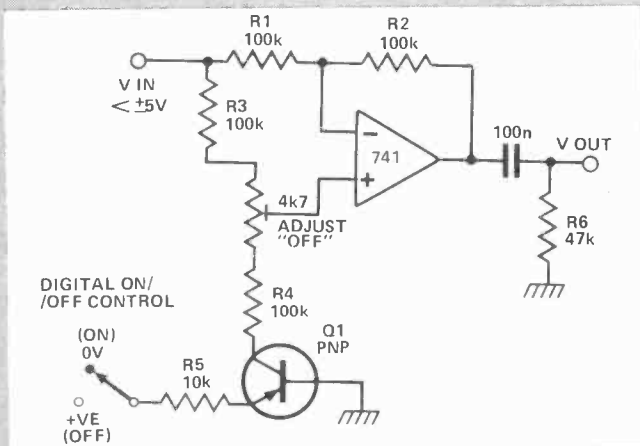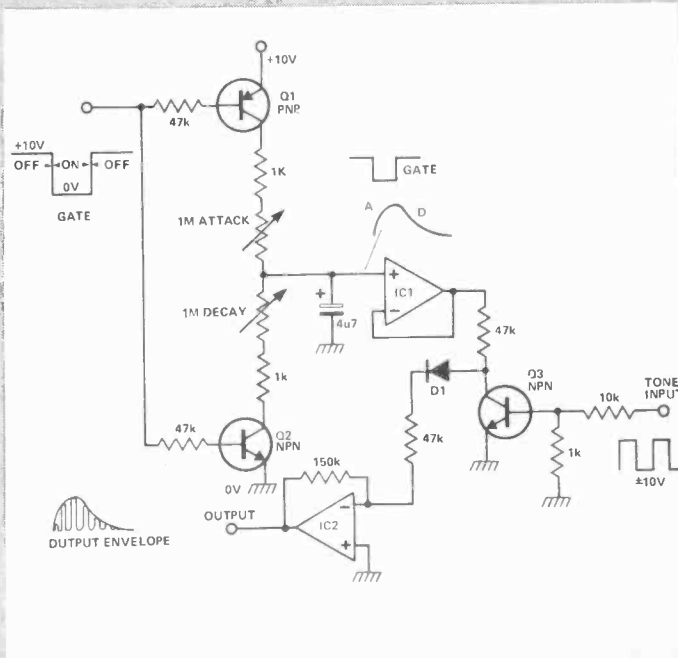The resultant waveform has the amplitude of the envelope and the harmonic structure of the squarewave. IC2 is used as a virtual earth amplifier to buffer the signal and D1 ensures that the envelope dies away at the end of a note.




Transistor Used To Turn An Op Amp On Or Off

When transistor Q1 is switched off, the circuit behaves as a voltage follower. By applying a positive voltage to the emitter of Q1 via a 10K resistor, the transistor is made to turn on and go into saturation. Thus the lower end of R4 is shorted to ground. The circuit has now changed into that of a differential amplifier (see fig. 7), but where the difference is always 0v. Now as long as the resistor ratios in the two branches around the op amp are in the same ratio then there should be zero output. A 4K7 preset is used to null out any ratio errors so that the 'OFF' attenuation is more than 60dB. The high common mode rejection ratio of a 741 enables this large attenuation to be obtained.

Fast Symmetrical Zener Clamping

The problem with using two zeners, back to back in series to get symmetrical clamping are one, the knee of the zener characteristics is rather sloppy. Two; charge storage in the zeners causes speed problems and Three; the zeners will have slightly different knee voltages and so the symmetry will not be all that good. The circuit overcomes these problems. By putting the zener inside a diode bridge then the same zener voltage is always experienced. The voltage errors due to the diodes are much smaller than those due to the zener. Also the charge storage of the bridge is much less. Lastly by biasing the zener on all the time, the knee appears to be much sharper.

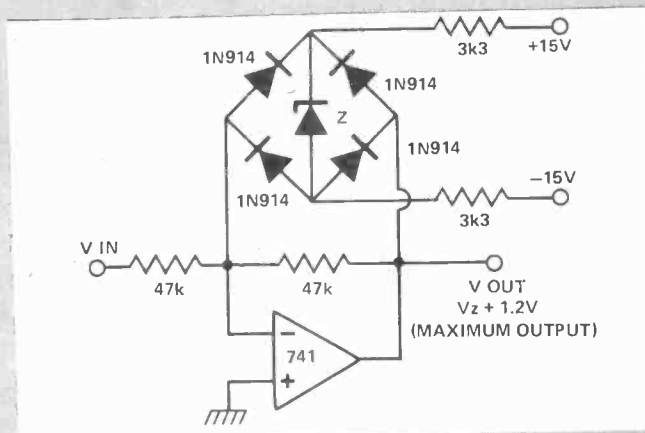

To be continued

GAS MONITOR

ETI Project Team present a machine which nose when you're fuming, and which can be suitably alarming. Particularly useful to boat owners, and of value to all needing to keep an eye on the gases.

PETROL VAPOUR, closed space and electrical sparks are not ideal companions. Many a boat has been destroyed when the owner has switched on the ignition without realising there had been a petrol leak and the vapour content in the engine compartment is at a dangerous level. Unfortunately the circumstances also lead to injury and loss of life. Therefore any system which can prevent this is of great value.

This unit is designed to meet this requirement and uses a semiconductor gas detector (TGS cell) to monitor the atmosphere in the engine compartment and either prevent the engine being started or shut it down if a high vapour concentration occurs during operation.

Construction

This is relatively easy if the printed circuit board is used and the wiring diagrams are followed. Some precautions should be taken if the unit is to be used in a boat to prevent corrosion. The rear side of the board should be coated with a cellulose spray (dope, nail polish, etc.) and the box, while having to be near the control panel, should be shielded from direct spray. Although we have used a separate box the unit can be mounted behind the control panel if desired.

A small heatsink (about 25 mm square aluminium) should be bolted on to IC 1 to keep it cool.

The relay should be capable of handling up to 5A and should have a 12V coil with a resistance of over 100 ohms.

Obviously the sensor must be mounted in the engine compartment and while it must be in free air it must also be protected against mechanical damage.



Installation and Adjustment

The sensor should be mounted in a position where vapour may be expected and should be mechanically protected against damage. The

connection to the sensor should be via a four core cable (on long runs use a shielded cable).

Note that the sensor is symmetrical in layout and also the fact that it will fit into a standard seven pin miniature valve socket.

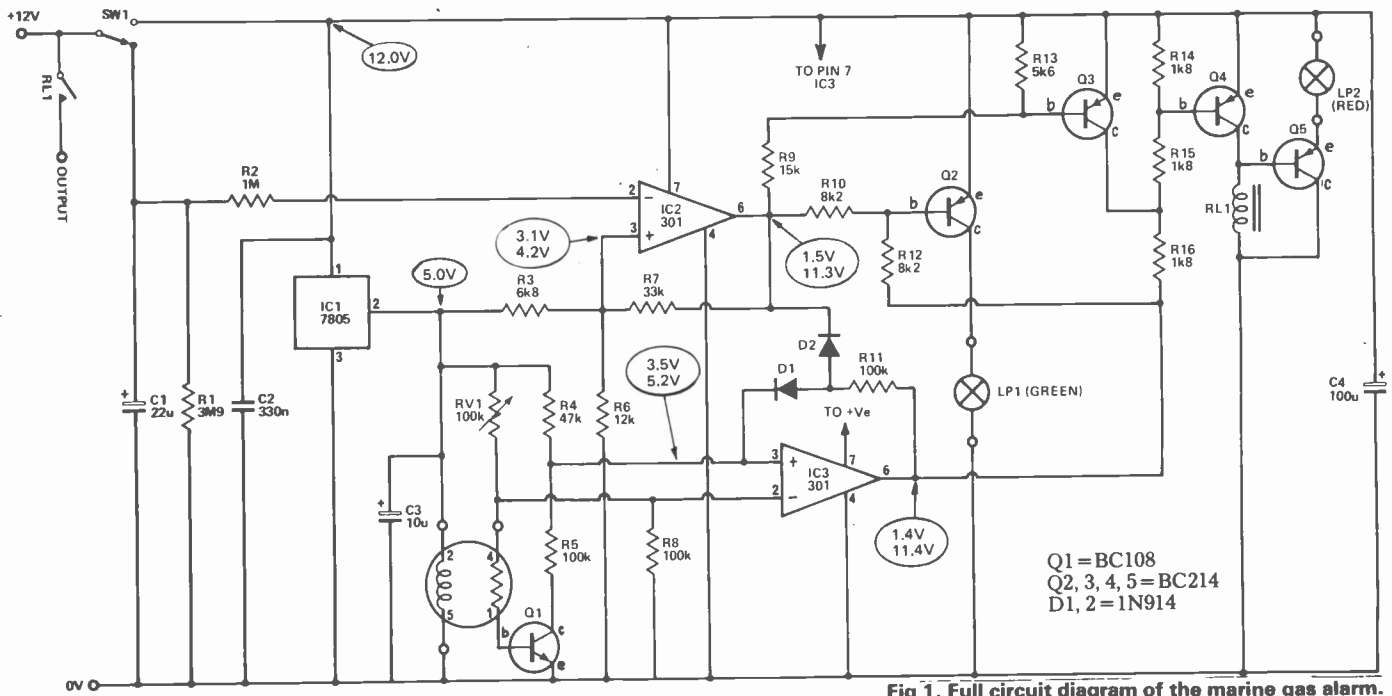


Fig 1. Full circuit diagram of the marine gas alarm.

HOW IT WORKS

This project is designed primarily to monitor the concentration of volatile gases inside the bilge of petrol-engined boats. The circuit provides an electrical cutout which prevents the engine from being started if fumes are present and also will remove all electrical power if fumes become present at any time.

The unit acts as a master switch and due to its warm up requirements, a two minute delay occurs on switch on. Two indicator lights indicate either "safe" or "fail" condition and in the initial warm up period both lights are on. The initial timing is performed by C1 and IC2. With the main switch off there is +12 V across C1. When it is switched on the

capacitor is allowed to discharge through R1. IC2 compares the voltage on C1 with that on pin 3 (about 3 V). During this period the output of IC2 will be about +2 V.

IC1 is a 5 V regulator and supplies the power for the heater of the sensor. The sensor's resistant element is in series with RV1 and this voltage is compared to the voltage set by R4/R5.

The transistor Q1 gives a fail safe operation and if the sensor is not connected this transistor will be off giving +5 V on pin 3 of IC3. Resistor R8 ensures that the voltage on pin 2 will always be slightly less than +5 V.

If vapour is present the sensor resistance will be low and the output of IC3 will be high. During the first two minutes the diodes D1 and D2 prevent the feedback loop (R11) operating. After two minutes if the output goes high the reference voltage on pin 3 of IC3 will go above 5 V and therefore the IC will latch in that position.

The relay is operated by Q4 and for it to close the output of IC3 must be low (no vapour) and also the output of IC2 must be high (more than two minutes after switch on). If the unit does switch off, or prevents initial switch on, it must be switched off and then on again (after clearing the fumes) and the two minute delay operates again.

The only adjustment is the sensitivity control and this is set by bringing a small container of petrol near the sensor and ensuring it operates. The adjustment should be as sensitive as possible without giving false operation.

Other Applications

By suitable choice of sensor from the TGS range (see data sheet this issue) the basic electronics, with perhaps a few modifications, can be used for a number of other applications — for example switching on an extractor fan if the carbon monoxide level in a garage reaches a dangerous level. No doubt numerous other applications for this project will occur to you.

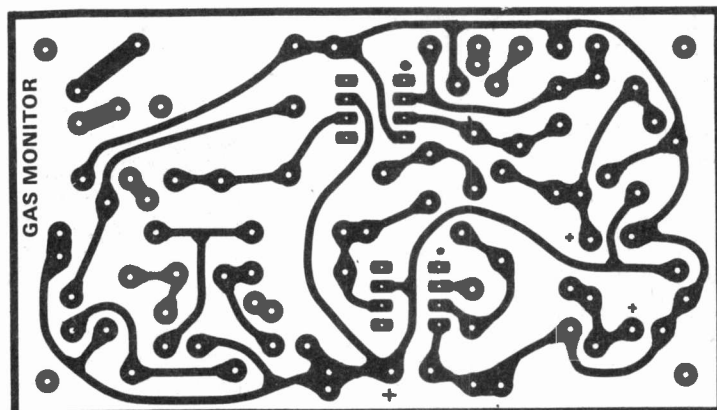


Fig 2. PCB pattern foil side shown full size (52 x 92 mm).

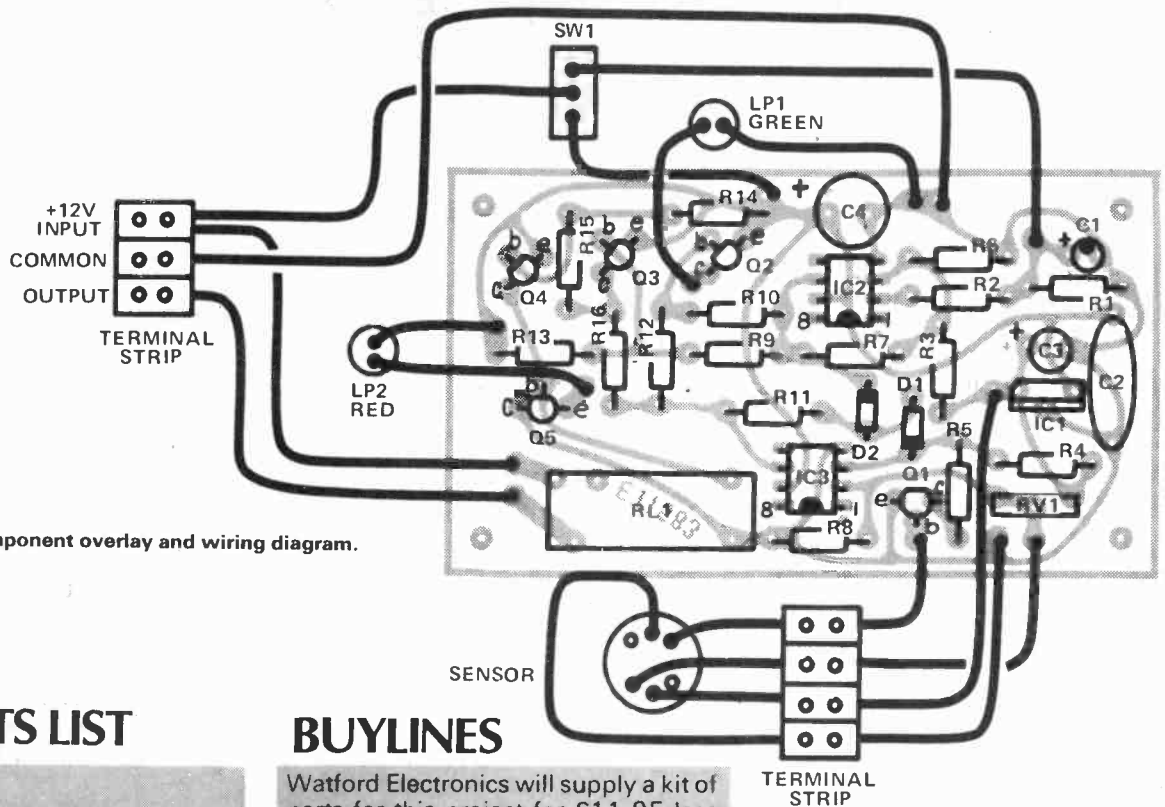


Fig 3. Project component overlay and wiring diagram.

PARTS LIST

RESISTORS

R1	3M9
R2	1M
R3	6k8
R4	47k
R5,8,11	100k
R6	12k
R7	33k
R9	15k
R10,12	8k2
R13	5k6
R14,15,16	1k8

POTENTIOMETERS

RV1	100k vert. preset
-----	-------------------

CAPACITORS

C1	22u 16V Tantalum
C2	330n Polyester
C3	10u 16V Electrolytic
C4	100u 25V Electrolytic

SEMICONDUCTORS

IC1	7805
IC2,3	LM301A
Q1	BC548
Q2,3,4,5	BC214

SENSOR

TGS	812 or 813
-----	------------

LAMPS

LP1,2	12V 100mA
-------	-----------


MISCELLANEOUS

Relay to suit application (min res 100R).
PCB as pattern, box etc.

BUYLINES

Watford Electronics will supply a kit of parts for this project for £11.95 less box which should be selected to suit the constructor's particular application, i.e. the expense of a die cast box would not be warranted unless the device needs to be waterproof.

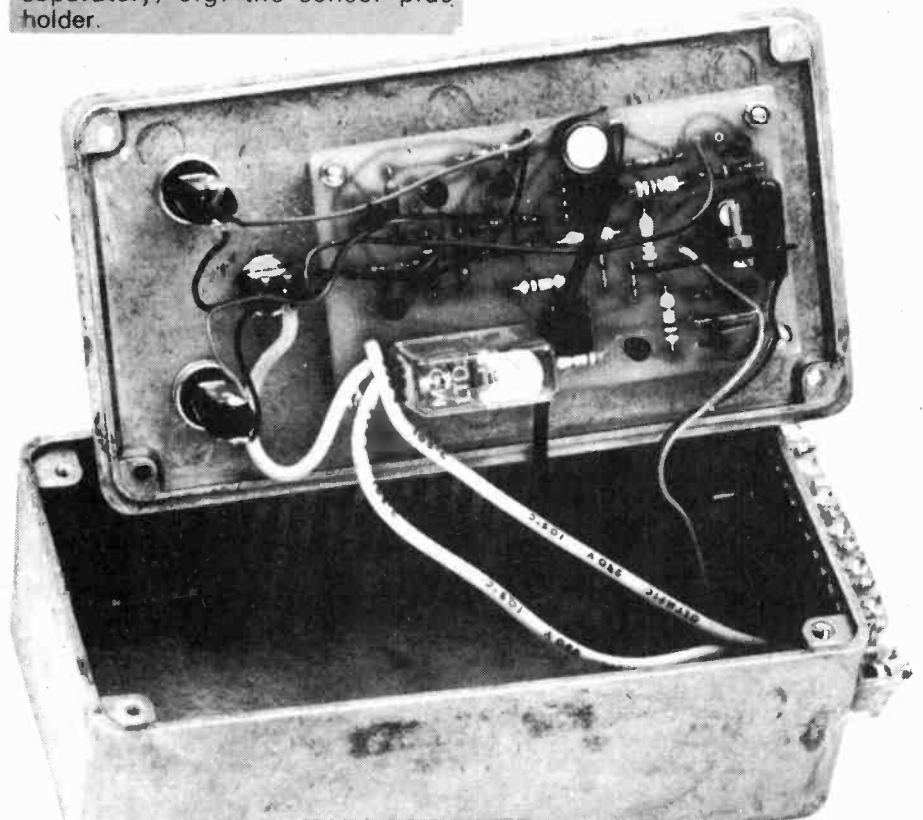
Watford will also supply all parts separately, e.g. the sensor plus holder.



The TANK BATTLE T.V. GAME

AY-3-8710
NOW AVAILABLE

- ★ Hide behind barricades and avoid being hit
- ★ dodge the enemy's mines
- ★ force your opponent into deserting the battlefield
- ★ three forward and reverse tank speeds
- ★ tank firing range is two-thirds of the battlefield
- ★ on-screen scoring
- ★ 32 rotational angles
- ★ shells travel in an authentic curved trajectory
- ★ sound direct from the TV
- ★ realistic battle sounds derived from a synthesiser
- ★ tanks move and fire in all directions
- ★ black and white kit available NOW
- ★ budget-priced colour add-on unit available shortly

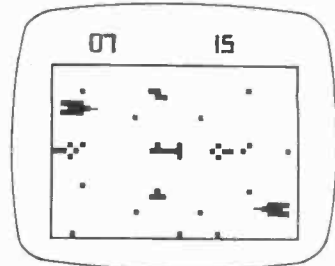

TANK BATTLE PRINTED CIRCUIT BOARD Application and assembly notes £3.90


TANK BATTLE AY-3-8710 I.C. and application drawing £14.90 (Normal Retail Price £21.50)

TANK BATTLE BASIC KIT (Just add controls and cases) £27.50

TANK BATTLE CASES with printed facia plate and hand controls £4.95

TANK BATTLE COMPLETE KIT Including mains power unit and case - no extras needed £37.90

STUNT CYCLE AY-3-8760-1

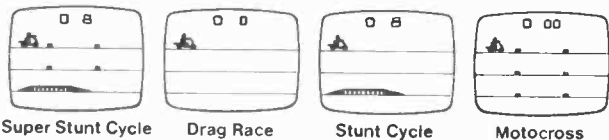


Super Stunt Cycle

Drag Race

Stunt Cycle

Motocross

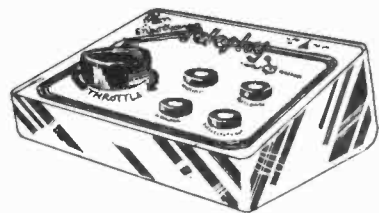VERY EASY ASSEMBLY
Suitable for first timers



- ★ Realistic stunt-cycle sounds come directly from the TV
- ★ Realistic crash effects and penalty points
- ★ Four competitive games with amateur and professional modes
- ★ On-screen scoring
- ★ Up to 36 buses can be jumped
- ★ Throttle has the 'feel' of a motorbike: too much and you will skid and crash, too little and you will not get over the buses or obstacles

DEMONSTRATIONS AT OUR SHOP HAVE PROVED THIS TO BE THE MOST COMPULSIVE TV GAME EVER MADE!

STUNT CYCLE I.C. AY-3-8760-1 £12.90

STUNT CYCLE PRINTED CIRCUIT BOARD, application and assembly notes £2.50

STUNT CYCLE BASIC KIT (Just add controls and case) £21.90

STUNT CYCLE CASE with printed facia panel £2.50

STUNT CYCLE COMPLETE KIT including mains power unit and case *no extras needed* £28.50

TEN-GAME PADDLE II AY-3-8600

- ★ X-Y axis bat movement
- ★ sound direct from TV
- ★ automatic ball speed-up


★ small or large bats for one or both players for handicapping
SPECIAL NOTICE to customers who have already purchased this game - two extra games now available - send a s.a.e. for free switching diagram

PADDLE II basic b+w kit (just add controls and case) £15.00

PADDLE II basic colour kit (just add controls and case) £20.90

JOYSTICK CONTROLS suitable for AY-3-8600 and AY-3-8550 i.c.'s £3.50 pair (or one only for £1.90)

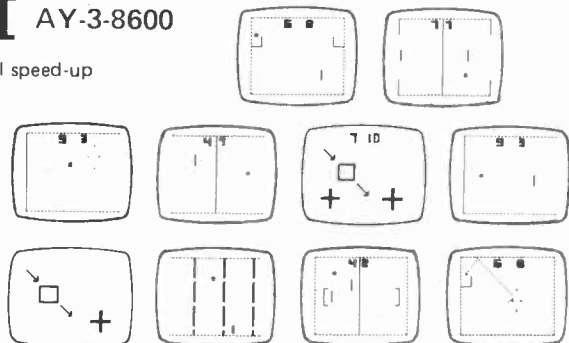MAINS ADAPTOR UNIT for TV games (9v 100mA) £3.25



WHILE STOCKS LAST AY-3-8500 i.c.'s £3.90

CASES FOR PADDLE GAMES

(less facia plates) £4.50 per set

Colour Converter for AY-3-8500 and AY-3-8550 games

£8.50 complete

SOUND MODULATORS £2.90 VISION MODULATORS £2.90
(or buy both for just £5.50) suitable for TV games

BARGAIN OF THE MONTH

SIX-GAME AY-3-8500 COLOUR

Basic Kit (just add controls and case)

Football, Tennis, Squash and Practice

2 Rifle games - Rifle not supplied

£12.90

All prices include VAT. For orders under £10 add 20p p&p. Cheques and postal orders to be made payable to TELEPLAY, or telephone your order quoting your Barclaycard or Access number



IF YOU CAN BUY ANY OF OUR PRODUCTS CHEAPER ELSEWHERE, WE WILL REFUND THE DIFFERENCE.



TELETEXT DECODERS—prices on application

WANTED!

TV game applications engineer

teleplay (formerly TELECRAFT)

14 Station Road, New Barnet, Herts EN5 1QW Tel: 01-440 7033/01-441 2922

CALCULATORS

ADVANCED APPLICATIONS FOR POCKET CALCULATORS
J. Gilbert £4.20

COMPUTER & MICROPROCESSORS

MICROPROCESSORS AND MICROCOMPUTERS
B. Sowick £18.00

BUILD YOUR OWN WORKING ROBOT
D. Herseman £3.35

DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS
N. M. Morris £3.50

INTRODUCTION TO DIGITAL FILTERING
Bogner £9.40

MICROPROCESSOR/MICROPROGRAMMING HANDBOOK
B. Ward £4.10

TRANSISTOR TABELLE
Includes physical dimensions & their pin assignments £4.10

MICROPROCESSORS
D. C. McGlynn £8.40

INTRODUCTION TO MICROPROCESSORS
Aspinall £5.35

MODERN GUIDE TO DIGITAL LOGIC
Processors - Memories and Interfaces £4.30

LOGIC DESIGN PROJECTS USING STANDARD ICs
J. Wakerly £5.10

PRACTICAL DIGITAL DESIGN USING ICs
J. Greenfield £12.50

COMMUNICATION

COMMUNICATION SYSTEMS INTRD TO SIGNALS & NOISE
B. Carlson £7.50

DIGITAL SIGNAL PROCESSING, THEORY & APPLICATIONS
L. R. Rabiner £23.80

ELECTRONIC COMMUNICATION SYSTEMS
G. Kennedy £8.50

FREQUENCY SYNTHESIS, THEORY & DESIGN
Mannasewitsch £20.40

PRINCIPLES OF COMMUNICATION SYSTEMS
H. Taub £8.10

COOKBOOKS

TV TYPEWRITERS COOKBOOK £7.40

CMOS COOKBOOK £8.00

TTL COOKBOOK £7.55

ACTIVE FILTERS £11.00

IC TIMER COOKBOOK £7.50

IC OP-AMP COOKBOOK £9.40

ELECTRONICS

BEGINNERS GUIDE TO ELECTRONICS
Squires £2.65

BEGINNERS GUIDE TO TRANSISTORS
Reddihough £2.55

APPLICATIONS OF OPERATIONAL AMPLIFIERS
Graeme (Burr Brown) £8.30

BASIC MATHS COURSES FOR ELECTRONICS
H. Jacobowitz £1.85

BUILD IT BOOK OF MINIATURE TEST INSTRUMENTS
R. Haviland £3.55

DESIGNING WITH TTL INTEGRATED CIRCUITS
Texas Instruments £9.05

DESIGNING WITH OPERATIONAL AMPLIFIERS
Burr Brown £13.75

ELECTRONIC ENGINEERS REFERENCE BOOK
4th Edition
L. W. Turner £27.70

SOLID STATE CIRCUIT GUIDE BOOK
B. Ward £2.25

TRANSISTOR CIRCUIT DESIGN
Texas £9.35

ELECTRONIC COMPONENTS
M. A. Colwell £2.45

ELECTRONIC DIAGRAMS
M. A. Colwell £2.45

ELECTRONIC FAULT DIAGNOSIS
I. R. Sinclair £3.20

ELECTRONIC MEASUREMENT SIMPLIFIED
C. Hallmark £2.20

ELECTRONICS AND PHOTOGRAPHY
R. Brown £2.30

ELECTRONICS SELF TAUGHT
Ashe £4.40

ESSENTIAL FORMULAE FOR ELECTRICAL AND ELECTRICAL ENGINEERS
N. M. Morris £1.65

EXPERIMENTS WITH OPERATIONAL AMPLIFIERS
Clayton £3.40

FIRE AND THEFT SECURITY SYSTEMS
B. Wales £2.00

HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS
B. Brown £1.95

HOW TO BUILD PROXIMITY DETECTORS AND METAL LOCATORS
J. Shields £3.85

HOW TO USE IC CIRCUIT LOGIC ELEMENTS
J. Streeter £3.65

INTEGRATED ELECTRONICS
J. Milman £7.70

HOW TO BUILD ELECTRONIC KITS
Capel £2.10

LINEAR INTEGRATED CIRCUIT APPLICATIONS
G. Clayton £5.00

FUNCTION CIRCUITS DESIGN & APPLICATIONS
Burr Brown £15.95

110 ELECTRONIC ALARM PROJECTS
R. M. Marston £3.45

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR
R. M. Marston £2.95

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR
R. M. Marston £2.95

110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR
R. M. Marston £3.20

110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR
R. M. Marston £3.25

110 THYRISTOR PROJECTS USING SCRs
R. M. Marston £2.95

MICROELECTRONICS
Hallmark £3.90

MODERN ELECTRONIC MATHS
Clifford £6.70

MOS DIGITAL ICs
G. Flynn £4.60

OPERATIONAL AMPLIFIERS DESIGN AND APPLICATIONS
G. Tobey (Burr Brown) £7.40

OP-AMP CIRCUIT DESIGN & APPLICATIONS
I. Carr £4.00

HANDBOOK OF IC CIRCUIT PROJECTS
Ashe £2.30

INDEXED GUIDE TO MODERN ELECTRONIC CIRCUITS
Goodman £2.30

BEGINNERS GUIDE TO INTEGRATED CIRCUITS
Sinclair £3.15

PRACTICAL ELECTRONIC PROJECT BUILDING
Ainslie and Colwell £2.45

PRACTICAL SOLID STATE D.C. SUPPLIES
T. D. Towers £6.20

PRACTICAL TRIAC/SCR PROJECTS FOR THE EXPERIMENTER
R. Fox £2.25

PRINCIPLES OF TRANSISTOR CIRCUITS
S. Amos £4.75

PRINTED CIRCUIT ASSEMBLY
Hughes & Colwell £2.45

RAPID SERVICING OF TRANSISTOR EQUIPMENT
G. King £2.95

SEMICONDUCTOR CIRCUIT ELEMENTS
T. D. Towers £6.40

UNDERSTANDING ELECTRONIC CIRCUITS
R. Sinclair £4.10

UNDERSTANDING ELECTRONIC COMPONENTS
R. Sinclair £4.10

UNDERSTANDING CMOS INTEGRATED CIRCUITS
R. Melan £3.90

SEMICONDUCTOR DATA

INTERNATIONAL TRANSISTOR SELECTOR
T. D. Towers £5.25

INTERNATIONAL FET SELECTOR
T. D. Towers £4.35

POPULAR VALVE/TRANSISTOR SUBSTITUTION GUIDE
£2.25

RADIO VALVE AND SEMICONDUCTOR DATA
A. M. Ball £2.60

MASTER TRANSISTOR/INTEGRATED CIRCUIT SUBSTITUTION HANDBOOK
£5.60

RADIO, TELEVISION AND AUDIO

AUDIO HANDBOOK
G. King £6.50

BEGINNERS GUIDE TO AUDIO
L. R. Sinclair £3.20

CASSETTE TAPE RECORDERS
J. Earl £5.25

FOUNDATIONS OF WIRELESS AND ELECTRONICS
M. Q. Scroggie £4.45

COLOUR TELEVISION THEORY
Hudson £6.20

WORLD RADIO TV HANDBOOK NEW 1978
(A complete Directory of Radio, TV Stations) £7.50

RADIO, TV AND AUDIO TECHNICAL REFERENCE BOOK
Amos £24.85

SOLID STATE COLOUR TV CIRCUITS
G. R. Wilding £6.35

TV TECHNICIANS BENCH MANUAL (new edition)
Wilding £5.10

HI-FI LOUDSPEAKERS AND ENCLOSURES
Cohen £8.20

BEGINNERS GUIDE TO RADIO
King £3.15

TAPE RECORDER SERVICING MANUAL
VOL I 1968-70 Gardner £8.50
VOL II 1971-74 Gardner £8.50

HOW TO BUILD SPEAKER ENCLOSURES
Badmaeff £3.10

FM RADIO SERVICING HANDBOOK
King £4.80

BEGINNERS GUIDE TO AUDIO
Sinclair £3.10

MASTER HI-FI INSTALLATION
King £2.80

TEST EQUIPMENT & OSCILLOSCOPES

BASIC ELECTRONIC TEST PROCEDURES
I. M. Gottlieb £2.45

THE OSCILLOSCOPE IN USE
Ian Sinclair £3.10

PRACTICAL TEST EQUIPMENT YOU CAN BUILD
W. Green £2.25

TEST INSTRUMENTS FOR ELECTRONICS
M. Clifford £2.40

WORKING WITH THE OSCILLOSCOPE
A. Saunders £1.95

SERVICING WITH THE OSCILLOSCOPE
G. King £5.60

RADIO TELEVISION AND AUDIO TEST INSTRUMENTS
King £5.90

HOW TO ORDER

Please note that our prices include postage and packaging. Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to:
ETI Book Service
P.O. Box 79
Maidenhead
Berks.

DIGITAL ELECTRONICS

THE 7490 DECADE COUNTER is a single-chip counter containing four flip-flops and various gates, which are arranged so that frequency division and decimal counting can be carried out. To make the counter more versatile, one flip-flop is separately connected so that it can be independently used as a scale-of-two counter, and the remaining three flip-flops are gates so that they act as a scale-of-five. The two sections of the counter can be connected together in different ways, either as a divide-by-ten circuit, or as a decimal counter with BCD outputs.

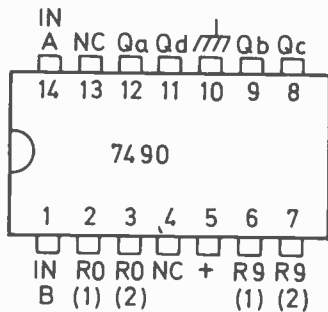


Figure 1. Pinout of 7490 Decade counter.

Twos Into Tens

BCD — meaning Binary-Coded-Decimal — is a form of binary code which is particularly useful if decimal numbers have to be displayed. In a BCD count, each figure of a decimal number is represented by its binary equivalent, so that the number 85 (decimal) becomes 1000 0101, binary 8 and binary 5. Although more convenient, because each BCD counter can then drive a display unit, this form is longer than a pure binary number (binary 85 = 1010101, only seven figures), and BCD numbers are not so simple to add and subtract as pure binary numbers.

BCD in Practice

Connect the power supplies to the 7490 with pin 10 to earth and pin 5 to +5 V. Pins 2 and 7 should also be


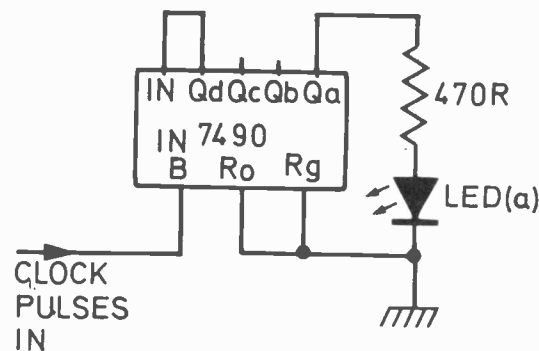


Figure 2. Connections for frequency division by ten — note that the symbol does not show the true pin positions.

Figure 3. Connections for BCD counting, with reset switch. The reset pin must be kept at logic zero for counting, and taken to logic 1 for reset, so that an inverter must be used along with the push-button switch.

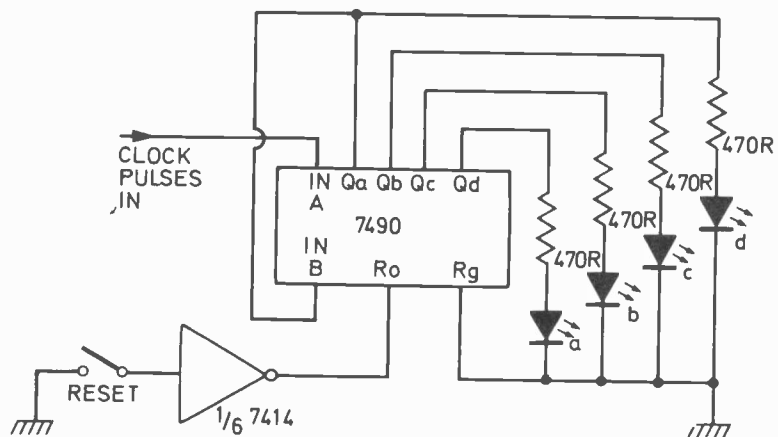

earthed for most of the experimental work in this section, although we may use pin 2 later for resetting to zero. Now connect LEDs and their limiting resistors, using the spare pads on the board, to Qa on pin 12 and Qd on pin 11. Connect the clock pulse from the slow oscillator to input A (pin 14) and by watching the clock LED and the LED connected to pin 12 (Qa), note the action of this section of the counter.

Switch off, transfer the clock pulse input to input B on pin 1, and switch on again, watching the clock LED and the Qd LED on pin 11. Note that the counter will operate only if the reset pins are earthed. There are two pairs of reset pins, each pair being inputs to an AND gate which operates the reset. Pins 2 and 3 are the reset to zero pins, and earthing either of them enables

the counter. If both are allowed to float to logic 1, or are taken to logic 1, the counter resets to zero. Pins 6 and 7 also act through an AND gate, but with both high the reset is to BCD 9 (1001) rather than to zero.

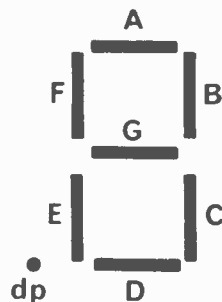


Figure 5. Arrangement of segments in a seven-segment display. The decimal point, which may be on the other side of the figure, is always energised separately, often from a range switch.

BY EXPERIMENT PART 7

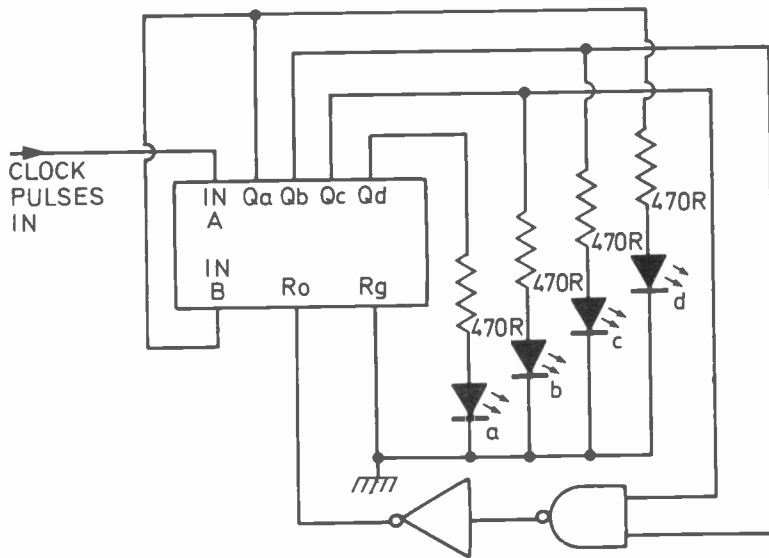


Figure 4. A terminated count. At some stage in the count, the gate will force the counter to reset. When does this happen?

Number/ Character	a	b	c	d	e	f	g
0	x	x	x	x	x	x	-
1	-	x	x	-	-	-	-
2	x	x	-	x	x	-	x
3	x	x	x	x	-	-	x
4	-	x	x	-	-	x	x
5	x	-	x	x	-	x	x
6	-	-	x	x	x	x	x
7	x	x	x	-	-	-	-
8	x	x	x	x	x	x	x
9	x	x	x	-	-	x	x
[-](10)	x	-	-	x	x	x	-
] (11)	x	x	x	x	-	-	-
⌋(12)	-	x	-	-	-	x	x
⌈(13)	x	x	-	x	-	x	x
⌊(14)	-	-	x	x	x	x	x
Blank (15)	-	-	-	-	-	-	-

x - lit
- - unlit

	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
1	1	0	0	0	1	0	0	1	1	1	1
2	0	1	0	0	0	0	1	0	0	1	0
3	1	1	0	0	0	0	0	0	1	1	0
4	0	0	1	0	1	0	0	1	1	0	0
5	1	0	1	0	0	1	0	0	1	0	0
6	0	1	1	0	1	1	0	0	0	0	0
7	1	1	1	0	0	0	0	1	1	1	1
8	0	0	0	1	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	1	1	0	0

Figure 6 (left) Truth table for figure and character displays.
Figure 7 (above). Truth table for a common-anode display, figures only.

To use the 7490 as a frequency divider (Fig. 2), we connect Qd (pin 11) to INa (pin 14) and take the clock pulse to INb (pin 1). The output will appear at Qa, on pin 12, and the state of this output is monitored by an LED already. Connect up the clock pulse from the slow oscillator on the board, and by counting pulses, confirm that the correct division ratio is being obtained.

For a BCD count, the connections must be changed around (Fig. 3). We now need LED indicators on the Qb (pin 9) and Qc (pin 8) outputs as well

as on Qa (pin 12) and Qd (pin 11), and the cross-connections are different, with Qa connected to input B and the clock input taken to input A on pin 14. Label the LEDs as A, B, C, and D, and switch on, noting the values at each stage of the count. Use de-bounced switch as a clock supply if the oscillator is too fast to follow. Note that in the circuit of Fig. 3 a reset switch has been used; because we are using push-to-make switches, an inverter must be used as shown.

Because the 7490 is on a single chip it may be convenient to adapt it

for counts of less than 10, rather than use separate flip-flops. This is made easier by the arrangement of the reset lines, connected through AND gates. Ignoring the reset-to-nine pins, we can arrange for pin 2 to be driven by a gate whose output must be zero during the count, rising to 1 at the end of the count. Pin 3 must be kept high, or the count will not be interrupted.

Try the circuit of Fig. 4 — can you work out what the count figure will be? Connect up and try the circuit out.

Displays

Though several other forms of display exist, the most convenient type for use with TTL circuits is the seven-segment LED display. The type used for this board, the BI-PAK DL747 (Jumbo) is one of the largest displays of this type available at the time of writing, and has been selected from the point of view of easy reading at a distance. If any other type is substituted, care will have to be taken with the pin connections, since there are several pinout standards for this type of display.

As the name suggests, the seven-segment display consists of seven LEDs made in one chip in the arrangement of a figure-of-eight, as shown in Fig. 5. The letters allocated to the strips are also shown (fortunately these are standardised).

Looking at the arrangement of the segments, we can draw up a table of the segments that will have to be activated (ON) for each number we want to display. Fig. 6 shows such a

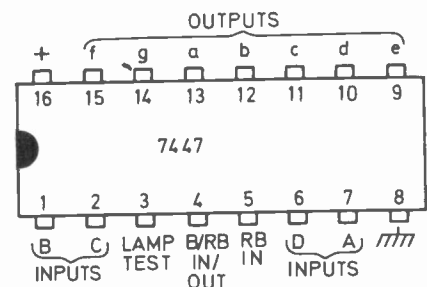


Figure 8. Pinout of 7447 BCD to 7-segment decoder-driver.

table for the numbers 0 to 9, and also some of the other characters which can be obtained. We now have to translate this ON/OFF table into terms of logic 1 and 0.

The next step depends on the type of display that is being used — common cathode or common anode. As the name suggests, the common cathode display has all of the LED cathodes connected together to logic 0, and each anode must be taken to logic 1 to be illuminated. To prevent excessive current flowing — because the normal forward voltage across the LED is less than the +5 V of the logic circuits — we must wire a limiting resistor in the connection to each anode. We cannot use one single resistor in the cathode lead, as this would cause the brightness of the display to alter according to the number of segments lit.

The other possibility is to connect the anodes of the LEDs together and take the cathodes out to separate pins. In this common-anode type of display, the segments will be lit when their respective cathodes are at logic zero, and once again limiting resistors must be used between each cathode and the TTL driving stage.

The type of display specified for this board is a common anode type, with several of the pins on the display connected to the common anode. Only one of these pins need be connected to the 5V line.

Decoders

To obtain a decimal readout from the BCD output of the 7490 counter, a decoder stage is needed with the truth table shown in Fig. 7.

The type used here is the 7447 BCD-to-seven segment decoder/-driver, which has output stages of transistor collectors with no loads. In this way, the combination of LED and limiting resistor acts as load for the collectors of the output transistors in the 7447.

Care should be taken that the outputs of a 7447 are never connected directly to the +5 V line, as excessive currents could flow if the decoder were operated.

In use, the segment output pins of the 7447 are connected through the limiting resistors to the segment pins of the display. The values of the limiting resistors used will determine the brightness of the display. For the 7447 display we can use 150 R res-

istors, but 470R resistors have been specified on our board to ensure long life and to cut down current consumption. If other displays are used, 470R should also be suitable — in general the small displays need less current, and so larger values of limiting resistors should be used than with larger displays. If a common cathode display, such as the MAN-3 types, had been used, the 7448 decoder would have been needed.

Now connect up the display and the decoder on your board, noting the connection diagram of Fig. 9. In the

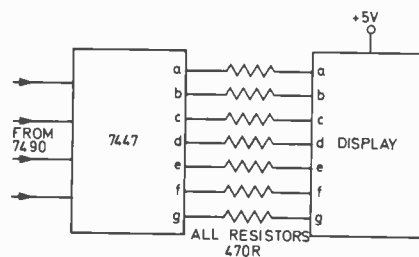


Figure 9. Connection of 7447 to display — not that the arrangement on the board is tidy as the diagram would suggest!

prototype boards, the very small resistors used for limiting could be passed under the body of the display, so avoiding long paths around it. The +5 V supply is taken to pin 16 of the 7447, and earth is taken pin 8. The outputs of the 7447, all on the side facing the display, and marked on the circuit diagram with small letters, are taken through the 470R limiters to the correspondingly lettered pins of the display. The inputs indicated by the capital letters A, B, C and D on pins 1, 2, 7 and 6 of the 7447 are for the BCD input from a 7490 and should be connected to the appropriate Q outputs from the 7490 counter.

Testing and Blanking


Note that pin 3 of the 7447 is labelled "lamp test." Taking this pin to logic 0 illuminates all segments of the display irrespective of what stage the count has reached, and is a useful check on the operation of the display. For example, an operator can check that a steady display of is not just with two segments faulty.

Pins 4 and 5 on the 7447 are for blanking, used mainly when the display is one of a set, to suppress zeros occurring before the first significant figures and after the last one. When pin 4 is low, the display is blanked out, though counting is unaffected.

To be continued

ETI

WIRELESS INTERCOM

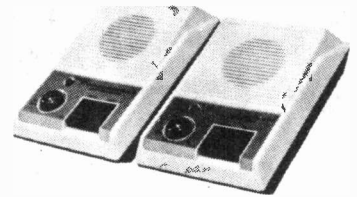

Just plug each unit into house mains, up to 1/2 mile. Distance depending on conditions. No other wires needed or batteries required. Excellent for offices, warehouses, homes, etc. Identical units, volume control on/off switch, pilot light, talk and lock buttons.

£33.95 + 85p P&P

MICRO CASSETTE

The MICRO CASSETTE. Tape down your thoughts, notes, work, etc. Uses the Philips Micro Cassette.

Dimensions:
14.5 cm. long
6.6 cm. wide
2.8 cm. deep
Wt. 320 gram.
2 hr. battery life

Output jack for earpiece

Speaker output 80MW

FANTASTIC VALUE £29.95

+ 65p P&P

SUPERB 2-WAY

1/6 WALKIE TALKIES

HV1 100 M Watt
Range up to 3km
approx. 100mv call
buzzer, compact
volume control
Only £37.95 per pair

HV100 1 Watt
Range up to 8km
approx. 1 watt 3 channel
int circuit FET
volume control call
buzzer case earphone
Only £85.50 per pair

HV 2500 2.5 Watt
Range 12 km approx.
2.5 watt 2 channel
superhet squelch
volume control call
buzzer, carr. case,
earphone rechargeable.
Only £165.00 per pair

CB 155 5 Watt

Range 16 km approx. 5 watt 3 channel 2 fitted crystal controlled super heterodyne with tuned RF variable squelch noise limited and AGC. Can be used public address Bat check meter and incoming signal check. Carr case earphone. Rechargeable call buzzer.
Only £225.50

All prices include VAT, add 85p P&P

Full 12 months guarantee

All sets 30% longer range at sea. These sets are solidly made to the highest standard for export and Yachtsman.


Send cheque and postal order to

TRITRON

57 Bridge Lane, London, NW11

01-458 4755

(Mail Order)

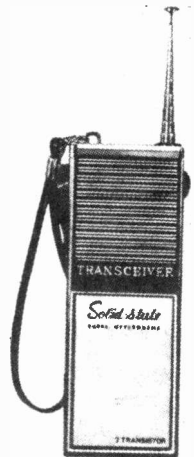

AUDIO AND TEST EQUIPMENT CENTRE


BRAND NEW STOCKS — NO RECONS.

Only regular stocks listed — other makes and models available. SCOPEX — LEVELL — SINCLAIR — AVO — GOULD ADVANCED — FLUKE — NEW LINEAR LAWTRONICS — PLUS IMPORTED TYPES

Telephone your order with Barclaycard and Access



4D10A

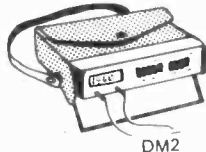

DM2



SWR

LONDON'S TEST GEAR CENTRE


OPEN 6 DAYS A WEEK 9 am — 6 pm

SCOPES

B1010 10MHz Batt / Mains portable with carry case. Probe. Batt. Charger	220.00
M515 15 MHz Version of above	260.00
455 Scope x 6MHz single beam	129.50
OS245A Gould Adv. 10MHz Dual beam	225.00
4D10A. Scope x 10MHz Dual beam	149.00
PROBES. x1/x10 12.95. x10 9.95. x1 7.95	205.00

DIGITAL MULTIMETERS

PDM35 Sinclair Pocket 3 1/2 digit	31.95
DM2 Sinclair Battery Portable 3 1/2 digit (Mains adaptor 3.95. DM2 carrycase 6.48)	52.90
LM3A 3 Digit Miniature with large LED displays	75.50
LM3.5A 3 1/2 Digit Recharge Batts. and charger	88.50
LM40A 4 Digit	151.20
BETA 3 1/2 digit LCD (Mains)	149.00
LM300 3-digit Miniature battery Op	79.50
LM350 3 1/2 digit with LCD displays	93.50

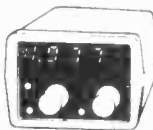

LM3.5A

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts. DC current. Resistance Ranges all with mirror scales except T11/T12/T12/TM3A (TM3 AC volts only), some with AC current etc.

TM11 Incredible 120 Range Electronic Multi-meter	130.00
TM3A 83mm Scale AC Microvoltmeter	105.00
TM3B 127 Scale 3MHz > 4 Megohm	117.50
360TR 100k/volt 23 Rangs (plus transistor checker) Large scale	32.50
PROE 20k/volt 26 Range. Large scale	29.95
7081 50k/volt 36 Range Multi-meter	22.50
TMk500 30k/volt 22 Range Multi-meter (plus Continuity Buzzer)	19.95
680R 20k/volt 52 Range Pocket Multi-meter	27.27
7200 20k/volt 22 Range Double Multi-meter	16.95
Micro80 20k/volt 26 Range Pocket Multi-meter	16.15
IT1-2 20k/volt 16 Range Popular Multi-meter	10.95
LT22 20k/volt 19 Range Pocket Multi-meter with carry case	14.50
T12 5k/volt 13 Range Pocket Multi-meter	7.95
T1/LT101 1k/volt 12 Range Pocket Multi-meter	6.95
K200 FET Multi-meter 3R Ranges 3MHz	72.80
GT101. 20K/Volt 23 Ranges/Transmission Checker / Continuity Checker	19.95

Large range of replacement tests leads in stock

GENERAL EQUIPMENT

SWR50 SWR / Power 1kW	19.50
100MHz Probe x 10 State BNC	9.95
100MHz Probe x1-x10 or 4mm	12.95
TE20D 500MHz RF Gen	49.50
LP30 30MHz Low Pass Filter	4.95
CX3A 150Watt 3-way AC Switch	7.50
DC25kV 100 Meg. HV Probe	11.95
9 Value CAP Subs Box	2.95
FX2000 Xtal Marker	11.95
LC1 Univ. Logic Checker	26.00
CT1 Continuity Checker	21.00
MOD63 Signal Injector	7.50
TT169 in Circuit TR Checker	44.75
LB1 Transistor / Diode Checker	21.50
3101 Clamp Meter 0/1K ohm 0/150/300/600 AC Volts 0/300 Amp	29.50
C3042 SWR & FS Meter	9.95
SWR50 SWR Power Meter	19.95
MS319 2x100 Watt Audio Watt Meter	17.50
500V Megohmmeter 500 Megohms	48.00
1000V Megohmmeter 100 Megohms	55.00
2 1/2 Amp Variable Transformer	18.00
5 Amp Variable Transformer	29.00
10 Amp Variable Transformer	40.00
TM12 Multi-ranger Transistor / Diode checker Adjustable Volts etc	130.00
100 Range Capacitance Decade	48.80
1 ohm - 11 Meg Resistance Decade	48.80

LEVELL OSCILLATORS / GENERATORS

TG152 Series RC Oscillators Sine / Square output 3Hz-300KHz	69.95
TG152D (with meter)	89.95
TG200 Series RC Oscillators Sine / Square output 1Hz-1MHz	93.85
TG200D (with meter)	112.50
TG200 Dmp (Meter & Fine control)	117.50

All models battery operated and portable

CAPACITANCE BRIDGES

100A. Portable analogue read	32.40
300A. 1pI — 2000 mfd Auto Ranging Digital Readout	253.80

ALL PRICES INCLUDE VAT Correct at time of preparation.

EXPORT — E & O E

QUANTITY DISCOUNTS.

Ask for New FREE TRANSISTOR/IC/VALVE CATALOGUE



TM11



TMK500



FM7 7 Digit 60MHz Rech. Batt. Freq. counter £140
SC5 Extends FM7 to 512 MHz 72.50



TM3

CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724-3564. OPEN 9-6, MON-SAT.

ELECTRONIC COMPONENTS AND EQUIPMENT

FREE CATALOGUE

SEND STAMPED (12" x 4" UK) ADDRESSED ENVELOPE (MIN. 5" x 8") FOR YOUR COPY NOW

Intersil 3 1/2 DIGIT PANEL METER

LED KIT




BUILD A WORKING DPM IN 1/2 HOUR WITH THESE COMPLETE EVALUATION KITS

Test this new part for yourself with Intersil's low cost prototyping kit, complete with A/D converter and LED display. Kit provides all materials, including PC board, for a functioning digital panel meter.

Order P/N ICL7107EV

£15.05

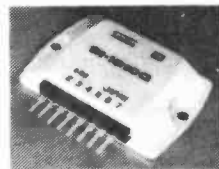


HYBRID AUDIO

POWER AMPLIFIERS

- Multi-purpose linear amplifiers for commercial and industrial applications.
- Less than 0.5% harmonic distortion at full power.
- 1/2 dB response from 20 to 100,000 Hz.
- Single or split (dual) power supply.
- Rugged, compact and lightweight packages.
- Built-in current limiting for SI-1030G, SI-1050G and efficient heat radiating construction.

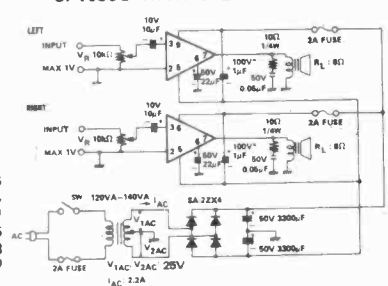TYPICAL CONNECTIONS SI-1050G WITH SPLIT SUPPLY



SANKEN Series SI-1000G amplifiers are self-contained power hybrid amplifiers designed for Hi-Fi, stereo, musical instruments, public address systems and other audio applications. The amplifiers have quasi-complementary class B output. The circuit employs flip chip transistors with high reliability and passivated chip power transistors with excellent secondary breakdown strength. Built-in current limiting is provided for SI-1030G, SI-1050G and all devices can be operated from a single or split supply.

SI-1010G (10W output)	£ 4.76
SI-1020G (20W output)	£ 8.34
Socket for above	.70
SI-1030G (30W output)	£ 12.85
SI-1050G (50W output)	£ 16.58
Socket for above	.70

1/4 WATT 5% CARBON FILM

RESISTOR KIT

COMPLETE WITH STORAGE BIN. Each KIT contains 20 each of 42 different values of 1/4W Carbon Film Resistors from 68 ohm to 4.7 megohm

Order P/N RS-14-25

£14.40

RASTR8 ELECTRONICS LTD.

275-281 King Street · Hammersmith · London W6 9NF

Tel. 01-748 3143/2960

Telex 24443

CLOCKS

A fine range of Electronic Digital Clocks

- ★ Unik Time Led Alarm Clock **£9.95**
- ★ Cassia LCD Battery Alarm Clock (see Kramer advert for picture) **£19.95**
- ★ Beta LCD Battery Alarm Clock with stop watch facilities **£16.95**
- ★ Casio LCD Calculator with Alarm Clock, Stop Watch, etc. **£19.95**
- ★ ETI Alarm Clock offer, available from Metac **£13.50**

WATCHES

The largest range of exclusive Electronic Watches anywhere

- | | Our Price |
|--|---------------|
| ★ Solar Watch, superb, 6 function LCD, with Seiko Module. Batteries are re-charged by daylight | £44.00 |
| ★ Casio 6 digit, LCD Chronograph | £26.95 |
| ★ Lambda 6 digit, 10 function, LCD Chronograph | £28.50 |
| ★ CBM 4 digit, 5 function, LCD with very large clear display | £21.50 |
| ★ Texas & Fairchild, Tritium, LCD 5F man's S/S | £26.00 |
| ★ Unik LCD 6 digit, 5 function, S/S bracelet | £21.50 |
| ★ Unik LCD 6 digit, 5 function, leatherette strap | £14.50 |
| ★ Ladies Watches (Timeband, CBM, National, etc.) | |
| 4 digit, 5 function, LCD Auto cal, back light, leatherette | £16.00 |
| leather | £23.00 |
| silver | £26.00 |
| gold | £29.00 |

SPECIAL OFFER

Man's 4 digit 5 function LCD, slim with metal bracelet **£12.95**
All watches, clocks and calculators carry the full manufacturer's guarantee and are supplied with a 10-day money back assurance.

BATTERIES


Metac carry a full range of watch batteries **70p each**

CALCULATORS

- Casio**
- AQ810 LCD Alarm Calculator **£19.95**
(2 timers, Alarm Clock: 5 functions plus memory, pocket size) 2,000 hrs. batts.
 - CQ1 Desk Calc, Clock, Stop Watch, green display **£29.95**
 - MQ2 Pocket Watch (size of Combe Case) LCD 5F Calc.: 2 alarms, Timer-alarm, 6 function Watch, Auto Cal., 12 months batt. life. Superb silver case **£34.95**
 - LC822 LCD Pocket Calc 5F plus mem, 2,000 hrs. batt. **£10.95**
 - LC87 LCD Pocket Calc., credit card size, 3/16in thick, 2,000 hrs. batt. life, 5F plus mem plus leather case **£16.95**

THE METAC DIGITAL CLOCKS

★ COMPLETE KIT ★

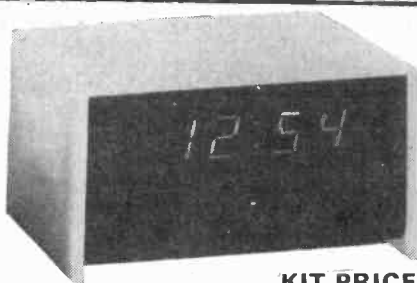

- Pleasant green display · 12/24 Hour readout
- Silent Synchronous Accuracy · Fully electronic
- Pulsating colon · Push-button setting
- Building time 1 Hr. · Attractive acrylic case
- Easy-to-follow instructions · Size 10.5 x 5.7 x 8 cm
- Ready drilled PCB to accept components

KIT PRICE
£9.75

+ 78p VAT
MODEL 100

METAC CLOCK KITS

are also available from:
Henry's, 404 Edgware Road, London, W2
Marshall's, 85 West Regent St., Glasgow
Watford Electronics, 33 Cardiff Rd., Watford, Herts.

C-SCOPE TOP QUALITY METAL DETECTORS

Plus accessory items. **PRICES £29.65 to £81.00**
Now available from our Uxbridge & Daventry shops
Officially franchised C-Scope distributors

GIVE YOURSELF A TREAT

Why not pay us a visit and see for yourself the full range of top-quality watches, clocks, treasure tracers, electronic ignition, TV games and battery eliminators.

EXPORT ENQUIRIES WELCOME

Metac-Electronics & Time Centres

MAIL-ORDER

DEPT. PB
HIGH STREET
DAVENTRY
NORTHANTS

SERVICE CENTRE

METAC
SERVICE CENTRE
MIDDLE MARCH
INDUSTRIAL EST.
DAVENTRY
NORTHANTS

SHOP

DAVENTRY

67 HIGH STREET
DAVENTRY
NORTHANTS
Tel. (032 72) 76545

SHOP

UXBRIDGE

NEW ARCADE
HIGH STREET
UXBRIDGE
MIDDX
(0895) 56961

LONDON

327 EDGWARE RD.
LONDON, W2
Tel. 01-723 4753

10 mins. walk Marble Arch, close to Henry's, Lasky's, Marshall's, etc., etc.



METAC STOCK LIST

RESISTORS

½W 5% carbon film
1Ω to 10 MΩ
E24 series
Price 2p each

PRE-SETS VARIABLE RESISTORS

100 ohm	10p
4K7 ohm	10p
47K ohm	10p
10K ohm	10p
100K ohm	10p
1M ohm	10p

ZENER DIODES

	10 volts
2.7 volts	10
3.0	12
3.3	15
3.6	20
7.5	30
8.2	68
	72

Price 10p each

DISPLAYS

2" LED Lamp	16p
1" LED Lamp	13p
DL707 Comm. Anode 3"	70p
DL704 Comm. Cath. 3"	80p
HP Comm. Anode 3"	90p
Comm. Anode 5"	£1.15
Futaba 5LTo1 Display	£4.96

Diodes IN 4001 1 amp 70V **5p**

Bridge Rect W04 1 amp 400V **30p**

Transistors, NPN Plastic 180V 8W **10p**

Mercury Gravity Switch **50p**

Switches

Push-button on/off **22p**
Push-button on/off reed **60p**
Slide switch on/off/on **25p**
Slide switch on/off **25p**

Battery Eliminator, 9V 100MA **£3.25**
(Suitable Calculators, TV Games, etc.)

Watch Batteries, all types **70p**

Sockets

40 pin DIL **50p**
28 pin DIL **35p**
24 pin DIL **30p**
16 pin DIL **18p**
14 pin DIL **15p**
8 pin DIL **10p**

Transformers, various values
Many other electronic components in stock at our shops

Dual Opto-Isolators, MCT6 **£2.00**

CMOS

CD4000 0.17	CD4024 0.80	CD4048 0.58	CD4081 0.23
CD4001 0.18	CD4025 0.23	CD4049 0.58	CD4082 0.23
CD4002 0.17	CD4026 1.78	CD4050 0.58	CD4085 0.74
CD4006 1.20	CD4027 0.58	CD4051 0.94	CD4086 0.74
CD4007 1.00	CD4028 0.92	CD4052 0.94	CD4089 1.60
CD4008 0.18	CD4029 1.18	CD4053 0.94	CD4093 1.94
CD4009 0.58	CD4030 0.58	CD4054 1.20	CD4094 0.92
CD4010 0.58	CD4031 2.30	CD4055 1.36	CD4095 1.08
CD4011 0.20	CD4032 1.44	CD4056 1.36	CD4096 1.08
CD4012 0.23	CD4033 1.02	CD4059 4.93	CD4097 3.85
CD4013 1.04	CD4034 1.97	CD4060 1.15	CD4098 1.13
CD4014 0.58	CD4035 1.22	CD4063 1.13	CD4099 1.90
CD4015 1.04	CD4036 3.29	CD4066 0.63	CD4502 1.24
CD4016 0.58	CD4037 0.98	CD4067 3.85	CD4510 1.41
CD4017 1.04	CD4038 1.10	CD4068 0.23	CD4511 1.72
CD4018 1.03	CD4039 3.20	CD4069 0.23	CD4514 2.84
CD4019 1.28	CD4040 1.11	CD4070 0.51	CD4515 3.24
CD4020 1.04	CD4041 0.86	CD4071 0.23	CD4516 1.40
CD4021 1.04	CD4042 0.86	CD4072 0.23	CD4518 1.24
CD4022 0.94	CD4043 1.01	CD4073 0.23	CD4520 1.19
CD4023 0.23	CD4044 1.45	CD4075 0.23	CD4527 1.64
	CD4045 0.96	CD4076 1.34	CD4532 1.39
	CD4046 1.37	CD4077 0.45	CD4555 0.90
	CD4047 1.04	CD4078 0.23	CD4556 0.90

TV GAMES

- ★ 4-game black & white **£12.95**
- ★ 5-game colour, 4 players & mains adaptor **£34.50**
- ★ 6-game colour with gun **£26.00**
- ★ Battery eliminators **£3.25**



SPEC.
BATTERY OPERATED WITH MAINS ADAPTOR SOCKET.
SOUND. 2 BAT SIZES. 2 BALL SPEEDS. 2 BALL ANGLES.
GAMES: TENNIS, FOOTBALL, SKEET & TARGET ON GUN GAMES.

TV GAMES

All games have superb plastic case. Are fully guaranteed, and are beautifully packed in a presentation carton.


Mail order customers please include 90p P&P

Shops open 9 to 5.30 daily

Barclay and Access welcome
Send card number with order

SHOP

200W AUDIO AMPLIFIER

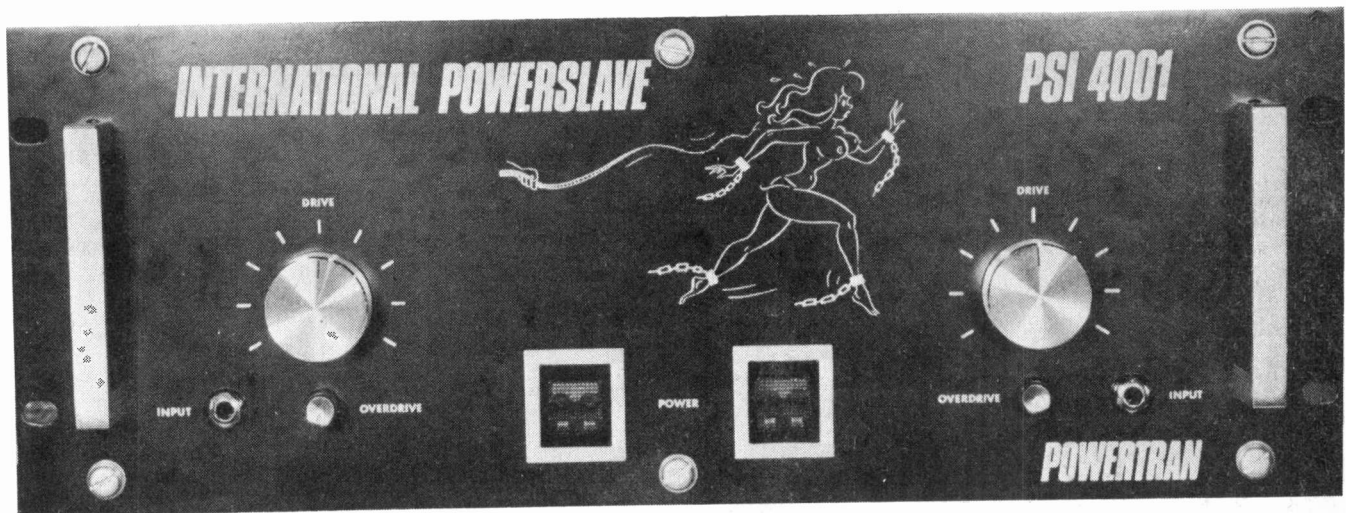

NO LITTLE TIME AGO we published a project for a 100 W guitar amplifier. It has since proved to be our popular project *ever*, and shows no signs of lying down to die in a respectable manner.

The main complaint about this machine has been that it is not powerful *enough* — something which our burst eardrums have repeatedly failed to grasp. In an attempt to please all the people all the time (as usual) we decided to re-do a design completely, uprating the spec to 200W, and generally improving the quality as far as we could to make the amplifier suitable for high quality domestic usage.


The subjective quality of the design is such that it will not be out of place in the highest of hi-fi set-ups, and its power enables it to drive the more inefficient monitors which seem to dominate such spheres.

SPECIFICATION

Output power	200 W	
Input sensitivity (for rated output)	.775 mV (0 dB)	
Distortion at 200 W	1 kHz	0.031 %
	10 kHz	0.073 %
	1 kHz	0.025 %
20 W	10 kHz	0.060 %
	1 kHz	0.027 %
2 W	10 kHz	0.042 %
Signal to noise ratio (CCIR weighted)	-101 dB	
Frequency response (-3dB)	10.2 Hz — 70.0 kHz	
Slewing rate	20 V/u sec	

NOTE:

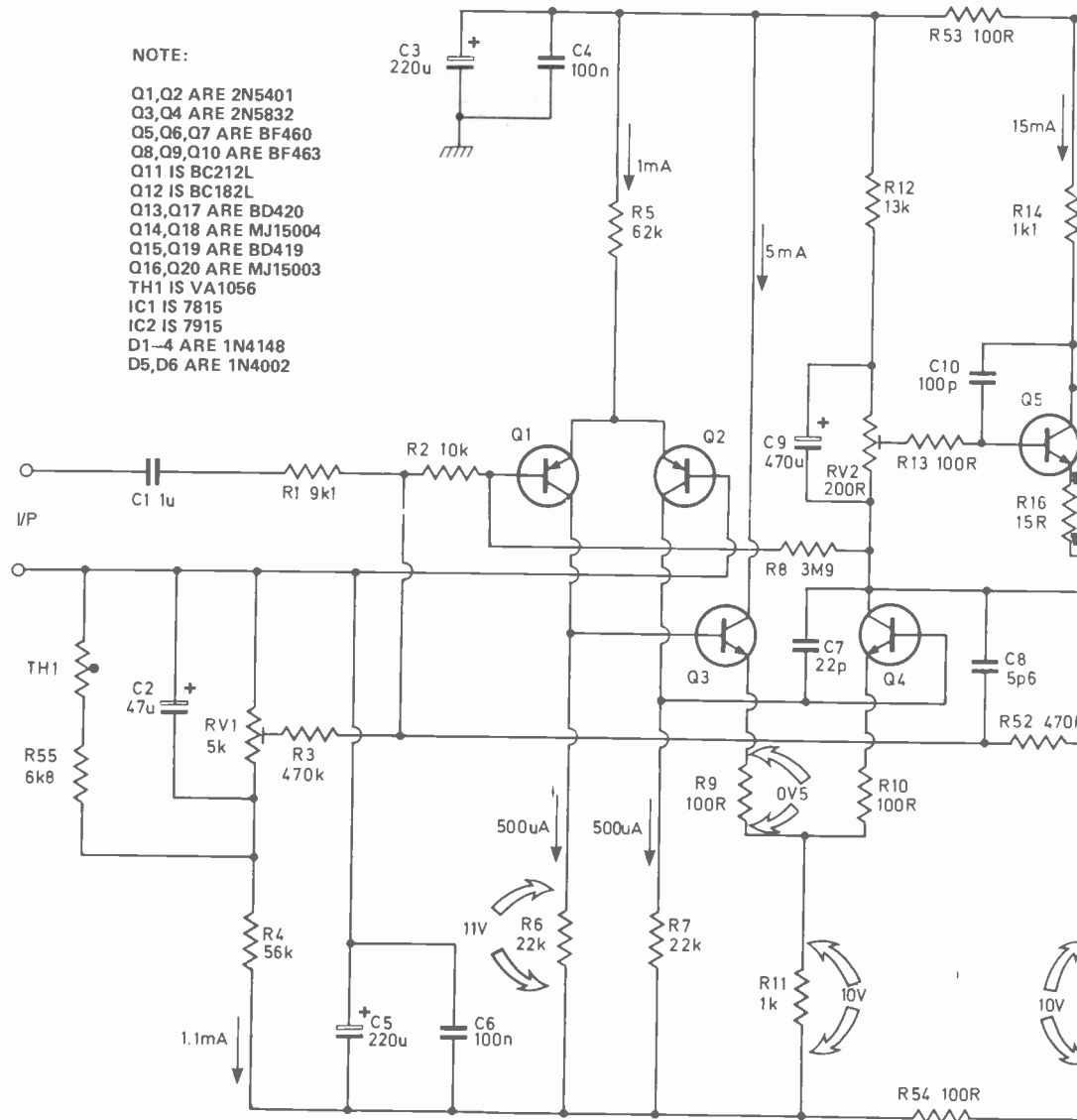- Q1,Q2 ARE 2N5401
- Q3,Q4 ARE 2N5832
- Q5,Q6,Q7 ARE BF460
- Q8,Q9,Q10 ARE BF463
- Q11 IS BC212L
- Q12 IS BC182L
- Q13,Q17 ARE BD420
- Q14,Q18 ARE MJ15004
- Q15,Q19 ARE BD419
- Q16,Q20 ARE MJ15003
- TH1 IS VA1056
- IC1 IS 7815
- IC2 IS 7915
- D1-4 ARE 1N4148
- D5,D6 ARE 1N4002



HOW IT WORKS

USE OF DIFF. PAIRS

Extensive use is made in the design of the 'long-tailed' or differential pair. The basic voltage amplification stage is shown in Fig.2. The symmetrical operation of the long-tailed pairs run with equal current in each arm affords the stage low distortion. Differential operation also possesses high linearity, as any non-linearity in V_{be} for either transistors is compensated for by the other.

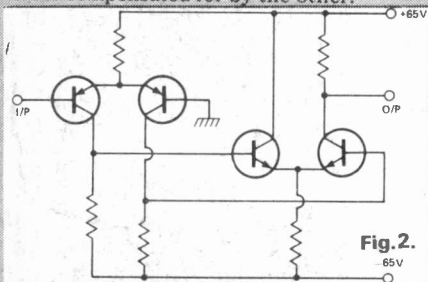


Fig. 2.

It is normal to operate differential pairs with a constant-current source in the tail, i.e.

Q8, D2 and R22-24 supply Q9 and Q10, and Q7, D1 and R18-20 supply Q5 and Q6. However, at the input of the amp (Q1 and Q2), only very small changes in tail current occur due to the small voltage swings, and a fairly 'large' value resistor, i.e. R5 will suffice. Similarly for R11 and Q3 and Q4. In the output driver stages very large voltage swings will be present and thus a current source is essential to correct operation.

OPERATION

For the purposes of operation the amplifier can be considered in four blocks: Two low gain, low distortion voltage amplification stages formed by Q1 and Q2 and by Q3 and Q4 output drivers Q5 and Q6 with Q9 and Q10 and finally the fully complementary output stages which consist of paralleled darlings. Discrete devices are employed for their better operating characteristics and speed 2MHz. Q15 and Q16 are paralleled with Q19 and Q20 to form in effect a single output 'transistor'. Q13, Q14, Q17 and Q18 constitute

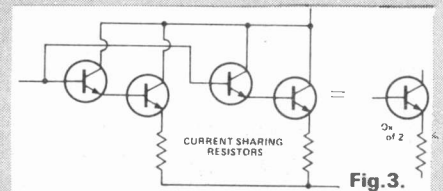


Fig. 3.

an identical configuration for the other half of the cycle. Fig.3 shows how the four may be combined into 'Qx'.

OUTPUT TRANSISTORS

The output types themselves are 250 watt devices, since for reliability the load line of these transistors must lie within the "safe operating" area (Fig 4). This is simply achieved with a pure resistive load, but not with the reactive component of a loudspeaker added. For a 4R load instantaneous dissipation in this design has a max of 144W, but with a reactive load dissipation can rise to 288 W. For these reasons lower power



ETI SPECIALS

TOP PROJECTS No. 1 + No. 2

A massive 180 page book containing all the projects originally described in our first two Top Projects Books -- originally published in October 1974 and June 1975 -- which are now out of print.

Projects include Master Mixer 100W Guitar Amp, Low Power Laser, Printimer, Transistor Tester, Mixer Preamp, Logic Probe, Simple Amp, Ni-Cad Battery Charger, Loudhailer, Scope Calibrator, Electronic Ignition, Automatic Car Theft Alarm, Turn Indicator Canceller, Brake Light Warning, LM380 Circuits, Temperature Alarm, Aerial Matcher, UHF TV Preamp, Metal Locator, Four Input Mixer, Super Stereo, IC Power Supply, Rumble Filter, IC Tester, Ignition Timing Light, 50W Stereo Amp PLUS MANY MORE

£2.50 + 25p P&P

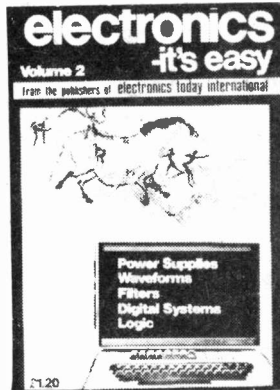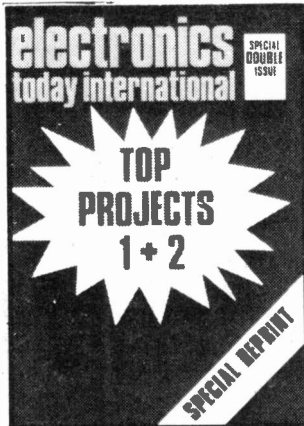

ELECTRONICS — IT'S EASY


Our successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series, (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics. Each volume costs.

£1.20 + 25p P&P

TOP PROJECTS No. 4

Published October, 1976. This includes Sweet-Sixteen Stereo Amp, Waa-Waa, Audio Level Meter, Expander-Compressor, Car Anti-Theft Alarm, Headlight Reminder, Dual-Tracking Power Supply, Audio Millivoltmeter, Thermocouple Meter, Intruder Alarm, Touch Switch, Push-Button Dimmer, Exposure Meter, Photo Timer, Electronic Dice, High Power Beacon, Temperature Controller, Electronic One-armed Bandit, plus many more.

£1.00 + 25p P&P

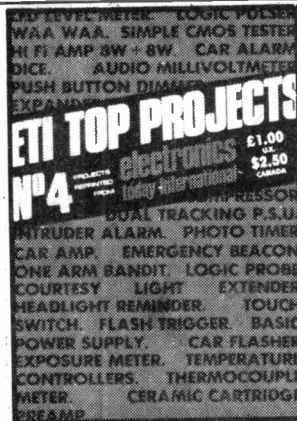

TRANSDUCERS IN MEASUREMENT AND CONTROL

by PETER H SYDENHAM
M.Sc., Ph.D., M. Inst. M.C., F.I.I.C.A.

TRANSDUCERS IN MEASUREMENT AND CONTROL

This book is rather an unusual reprint from the pages of ETI. The series appeared a couple of years ago in the magazine, and was so highly thought of by the University of New England that they have re-published the series splendidly for use as a standard textbook. Written by Peter Sydenham, M.E., Ph.D., M. Inst. M.C., F.I.I.C.A., this publication covers practically every type of transducer and deals with equipment and techniques not covered in any other book. Enquiries from educational authorities, universities and colleges for bulk supply of this publication are welcomed. These should be addressed to H. W. Moorshead, Editor.

£3.00 + 25p P&P

TOP PROJECTS No. 5


Twenty-two complete projects including, 5W Stereo Amp, Stage Mixer, Disco Mixer, Touch Organ, Audio Limiter, Infra-Red Intruder Alarm, Model Train Controller, Reaction Tester, Headphone Radio STD Timer, Double Dice, G.P. Power Supply, Logic Tester, Power Meter, Digital Voltmeter, Universal Timer, Breakdown Beacon, 1-2 Hour Timer, Heart Rate Monitor, IB Metal Locator and Temperature Meter.

£1.00 + 25p P&P



electronics tomorrow 75p

A SPECIAL EDITION FROM ETI MAGAZINE

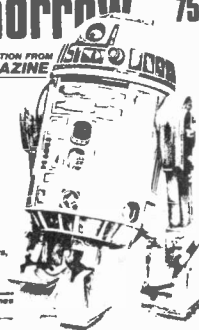

ELECTRONICS TOMORROW

This is our latest special, and one which even we consider very special! Comprised entirely of new material, the edition covers such diverse subjects as Star Wars and hi-fi! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, Audio, Calculators and Video. How can you not read it?

75p + 25p P&P

ETI CIRCUITS No.1

\$5.00 £1.50 \$2.50

ETI CIRCUITS No. 1

Contains nearly 250 circuits largely taken from the best of our Tech-Tips. Great care has been taken to index each circuit for rapid selection. An additional section at the back gives plenty of reference data including transistor specs and equivalents.

Sales of this publication have been excellent -- hardly surprising when the circuits cost less than 1p each!

£1.50 + 25p P&P

HOW TO ORDER

Postage and packing also refers to overseas. Send remittance in sterling only.

ETI Specials
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please mark the back of your cheque or PO with your name and address.

ETI 4600 SYNTHESISER

A complete reprint of our superb synthesiser design, published with Maplin Electronics (who also supply the parts). This reprint will also be of interest to those not specifically wanting to build the unit as the circuitry is highly original and is in fact patented by ETI!

£1.50 + 25p P&P

ELECTRONICS TODAY



READER SURVEY

Dear Reader,

Can you spare a few minutes to help ETI?

Pages 47 and 48 take the form of a reader survey/questionnaire. We want as many readers as possible to fill in and return these to us. As a token of our appreciation we will be giving away 60 ETI T shirts, the lucky readers will be picked at random on the 10th of April. The only reason we ask for your name and address is to send out the T shirts, if you don't want a T shirt and would prefer to remain anonymous please still fill in and return the page —without your name or address.

We have done several surveys in the past, the most recent being in 5% of the July 1977 issue. Since this we have made several changes in the magazine's format and organization, a lot of the changes being catalysed by careful analysis of the returned questionnaires. Yes, we really do care about what you, the reader, thinks!

Thanks for your help,
May the EMF be with you.



50p OFF

ANYTHING YOU BUY VALUED
£1.00 OR OVER
AT YOUR TANDY STORE

Complete this coupon and
bring it with you to your
TANDY store — NOW!

SOUNDS GREAT FOR '78
TANDY

NAME _____
ADDRESS _____

_____ POST CODE _____

is entitled to 50p off any purchase valued at £1.00 or over. Only valid for one transaction per person. Must be presented in person—no orders by post.
Offer available 1st April—31st May 1978.

Please Note: For commercial reasons the Tandy catalogue is only being inserted in most copies of the magazine for U.K. distribution, and the 50p off coupon is only valid at U.K. Tandy Shops.

THIS ISSUE RECENT

1. Please tick your interest in each of these features:

	Readership			Rating (if read)		
	Read Fully	Scanned Over	Not Read	Good	Average	Poor
200W AMPLIFIER	✓			✓		
<u>WHITE LINE FOLLOWER</u>	✓			✓		
RAIN ALARM		✓			✓	
GAS MONITOR		✓			✓	
<u>PET REVIEW</u>	✓				✓	
CASING SURVEY	✓			✓		-
OP-AMPS PART 3			✓			-
DIGITAL ELECTRONICS			✓			
<u>TECH TIPS</u>		✓			✓	
DATA SHEET		✓				
MICROFILE						
ELECTRONICS TOMORROW						
NEWS DIGEST						
AUDIOPHILE						-
LETTERS PAGE						
<u>SYSTEM 68</u>						

2. a) Please underline any features above that you find particularly interesting.
 b) Please circle any features you find poor or uninteresting.
 c) Please mark an asterisk (*) next to the single best feature from your point of view.
3. a) Do you consider yourself a regular reader? YES/NO
 b) If yes, for how long? Last six months / 1 year / 2 years / 3 years / Longer
 c) If a reader for one year or more, how do you rate recent issues of E.T.I. (Say those of the past three months, compared to those of a year ago?)
 Much better / Slightly better / Same / Slightly worse / Much worse
 d) How long do you keep your copies of E.T.I.? 1 month / 3 months / 6 months / 1 year / Longer
 e) How long have you been interested in electronics?
 Last six months / 1 year / 2 years / 3 years / Longer
 f) How did you become a reader of E.T.I.? Friend's copy / Impulse purchase / Advertisement / Other (please specify)
 saw a circuit I wished to build. O.
 g) How many other people read your copy? O.

4. a) Have you ever built a project from E.T.I.? YES/NO
 b) If yes, how many have you built in the last year?
 c) Please give details of those built in the last year (including those originally featured in the magazine over a year ago).

- d) What are your main areas of interest?
 MP3s / Audio / Video / RF / Gadgets / Other (please specify)
 e) What would you like to see as a project?
 f) In general do projects work first time? YES/NO

5. Do you own, hope to own, or have access to the following (please tick).

	Own	Year acquired	Hope to own	Access to
Good Multimeter				
Cheap Multimeter				
Oscilloscope				
G.P. Power Supply	✓			
A.F. Signal Gen				
R.F. Signal Gen				

6. a) What proportion of E.T.I.'s advertising do you normally read?
 Over 75% / 50-75% / 25-50% / Below 25% / None
 b) Would you like more advertising (as long as the editorial pages are not cut back to accommodate it): YES/NO
7. Offers.
 a) We run quite a lot of offers in E.T.I. Do you consider them a good idea? YES/NO
 b) How do you rate these recent offers?

	Purchased	Good	O.K.	Uninterested
L.C.D. Calculator	X			
Smoke Detector	X	X	✓	X
M.P.U. Doorbell	X	✓	X	X
Chess Challenger	X			

- c) What would you like to see as an offer?
 more offers on components for projects
 (preferably those which are difficult to obtain)
 eg. IC's SCR's LDR's Transistors etc.

8. The Competition.

	READ				OPINION			RATING
	Regularly	Often	Never	Used to Read	Good	OK	Poor	
Practical Electronics								
Practical Wireless			✓					
Wireless World								
Everyday Electronics	✓				✓			9
Elektor			✓					
Radio Constructor			✓					
Television			✓					
ETI	✓							10

On an arbitrary 1-20 scale with E.T.I. rating 10, please rate your opinion of our competitors. Please mark an asterisk (*) next to any magazines you subscribe to.

9. a) Do you read E.T.I. as an extension of your job? **YES/NO**
- b) Are you employed in the electronics (or closely related) field?
YES/NO/Not in Full time employment
- c) If yes to 9b, in what capacity (please tick) *see 12 a (i)*
- Management Maintenance Clerical
- R & D Buying Technician
- Production Sales Other
- d) Are you a student or studying full time? **YES/NO**
- e) If a student, do you hope to get work in the electronics or closely related fields?
YES/NO
- f) Have you ever considered taking a course in electronics? **YES/NO**
10. a) Have you read the Electronics Tomorrow special? **YES/NO**
- b) If yes how do you rate it? **Poor/OK/Good/V. Good**
- c) Did you see the February issue? **YES/NO**
- d) If yes, did you like the colour sections? **YES/NO**
- e) Would you like us to do more colour issues? **YES/NO**
- f) Do you like the free catalogues? **YES/NO**
- g) Would you like more catalogues? **YES/NO**
11. a) Have you ever purchased goods by mail order from E.T.I.? **YES/NO**
- b) Approximately how much do you personally spend on electronics annually?
 £ *No idea*
- c) Do you usually purchase by mail order or personal visit? **Mail/Visit**

12. Personal information. If you find it offensive to answer please ignore this question.

- a) Educational.
- i) What was your age last birthday? *14*
- ii) Highest educational level achieved (please tick)
 For Scottish readers and those educated outside U.K. please tick equivalents
- CSE A level Degree
- O level HNC etc. Other
- b) Income.
- i) Are you paid (please delete) *Weekly/Monthly/Other*
- ii) Basic Income p.w./p.a.
- Average overtime, commission, bonus, etc p.w./p.a.
- Other income (including that from second job) p.w./p.a.
- iii) Do you have any of these credit cards (please tick)
- Barclaycard/Visa Access American Express
- c) Sex. **Male/Female/Other (please specify)**

13. What is your interest in microprocessors? **Very High/High/Fair/Little**
14. What do you like about E.T.I.?
15. What do you dislike about E.T.I.?
16. Have you any suggestions for improvements?
17. Other comments

Please enclose a separate sheet if not enough space for your comments.

Name	<i>N. Crook</i>
Address	<i>19 Greenlands Rd. Stones, Midx TW5 4R</i>
If you win a T shirt, what size do you want? Small/Medium/Large	

THANK YOU FOR YOUR TIME,
 PLEASE MAIL TO:
 ETI SURVEY,
 25/27 OXFORD STREET,
 LONDON W1R 1RF

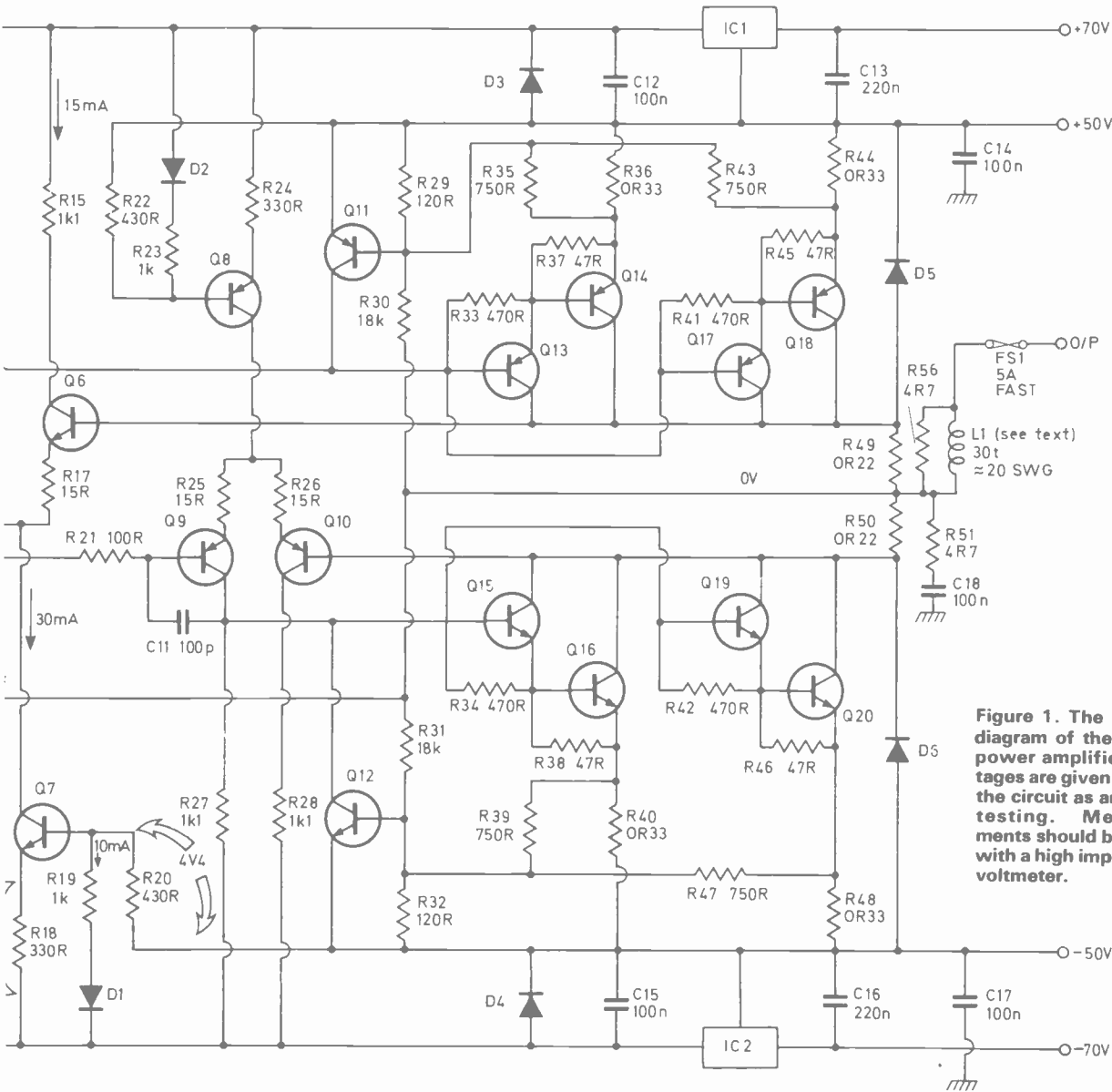


Figure 1. The Circuit diagram of the 200W power amplifier. Voltages are given around the circuit as an aid to testing. Measurements should be made with a high impedance voltmeter.

RKS-Main Amp

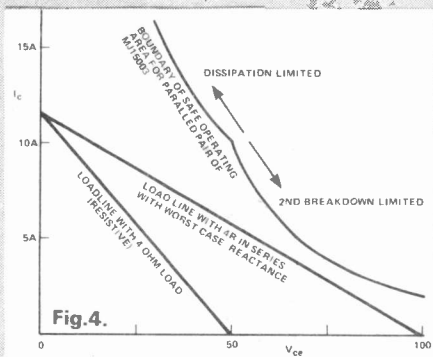


Fig. 4. devices are not recommended for use, unless more are paralleled to share the load.

Because the amp employs low overall feedback (14 dB) the bias current for Q1 is not obtained via the feedback resistor R52 since this would result in a large DC offset at the output. An independent supply is provided, consisting of RV1, R55 and R4. Temperature compensation is provided by TH1.

QUIESCENT CURRENT

With the employment of long-tailed pairs, setting of quiescent current in the output 'switches' QX is somewhat different to a 'normal' design. The function is affected by RV2, which varies the DC between Q5 and Q6 bases. Q5 base will follow the base of Q6 by differential pair action, and similarly Q9 and Q10 this means that the voltage across R49 and R50, which is proportional to I_q will be 'referred back' to RV2. Temperature effects can be removed by keeping Q5 and Q6 as well as Q9 and Q10 at the same temperature, and to ensure this pair is thermally connected to a (different) heat sink.

Regulators IC1 and IC2 are employed to stabilize the 50-volt rails with respect to the 65-volt rail for the constant current sources supplying driver stages Q5 and Q6 and Q9 and Q10.

Diodes D3 and D4 protect IC1 and IC2 from any reverse voltages that might be present at switch on.

OUTPUT PROTECTION

Conventional short circuit protection is employed, using load-line limiting, i.e., refer-


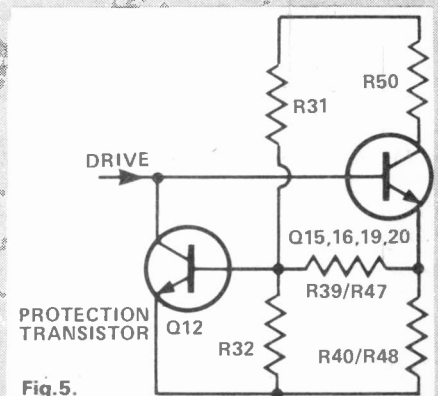



Fig. 5.

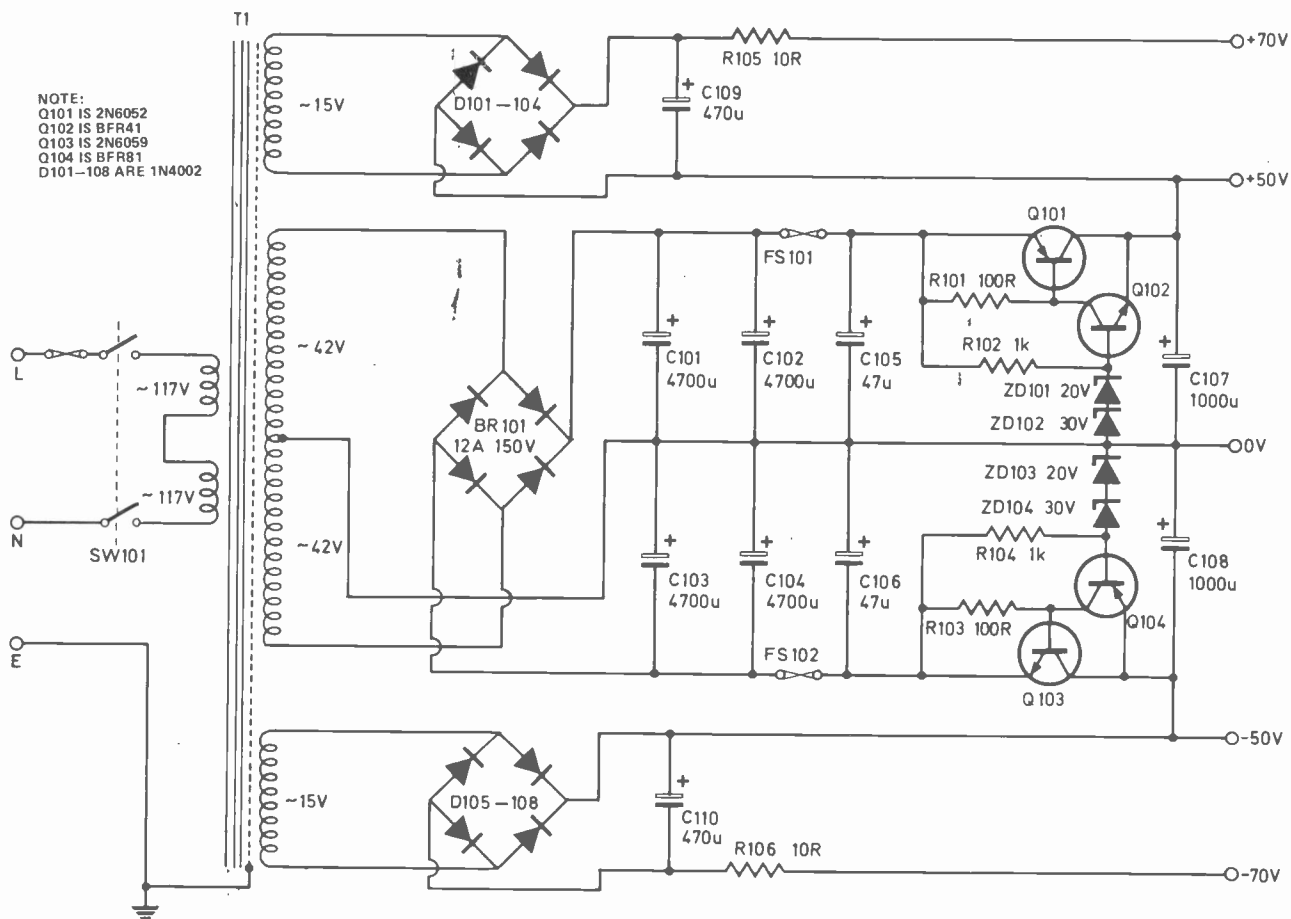ring to Fig 5. The current through R31 will voltage limit the output, and the current through the parallel combination imposes a current limiting function. If either limit is exceeded, Q12 switches on and closes down the drive signal.



NOTE:
 Q101 IS 2N6052
 Q102 IS BFR41
 Q103 IS 2N6059
 Q104 IS BFR81
 D101-108 ARE 1N4002

Figure 6. (Above) Circuit diagram for the PSU. Note that the transformer is a special unit wound for the 200W amplifier by Powertran Electronics. Figure 7. (Below) The circuit diagram for the buffer to increase the input impedance of the unit, and provide variable input sensitivity if required.

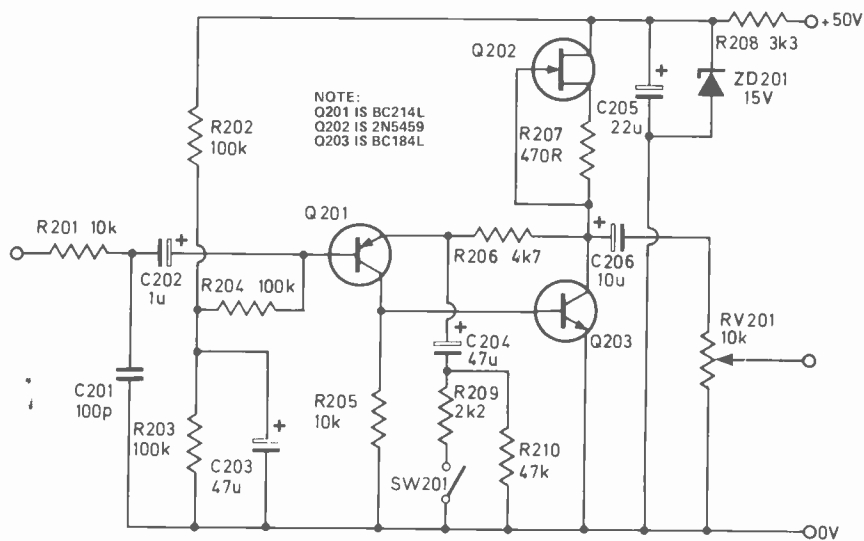


NOTE:
 Q201 IS BC214L
 Q202 IS 2N5459
 Q203 IS BC184L

HOW IT WORKS ~Buffer & PSU

THE power supply is a conventional series pass circuit. The basic circuit elements are shown below. The circuit is essentially an emitter follower, the voltage at the base of the transistor being some 0V6 below that set by the zener in the base. The final circuit shown in Fig. 6 shows that Q101 forms the pass element in the +50V rail while Q103 forms the complementary device in the negative rail. Q102 and Q104 provide increased drive to the pass elements.

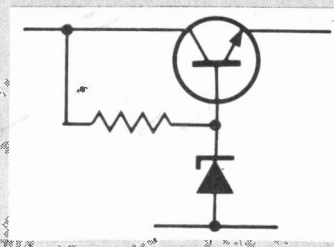
The $\pm 70V$ rails are derived from a simple bridge rectifier circuits.



THE BUFFER

The buffer is a straightforward circuit formed by Q201-203. The buffer provides an high input impedance and allows for two gains, with RV201 at maximum, +0dB with SW201 open and +10dB with R209 in circuit. Changing the value of R209 to 470R will give a 20dB boost when SW1 is operated.

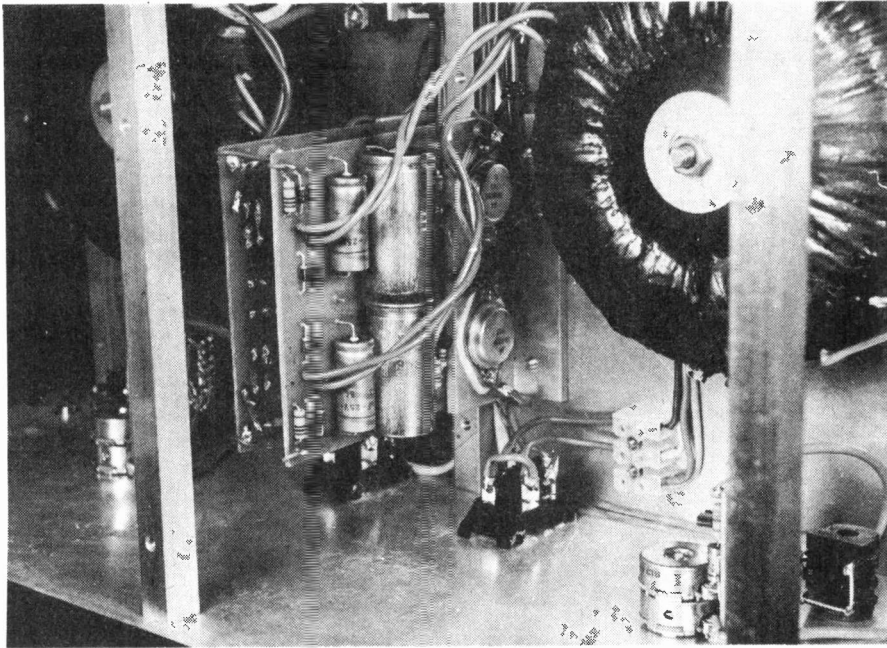The buffer is powered from the +50V rail with ZD201 included to provide a 15V rail.



The PSU can be seen above. The layout of all the major components can be seen with the buffer (in close up below) just appearing at bottom right.

In addition the bodies of diodes D1 and D2 should be in contact with the heat sink of the appropriate group transistors.

The coil L1 is formed by winding thirty turns of self-fluxing polyurethane covered wire (about 26 SWG) around resistor R56 (4R7), soldering the wire to the leadouts at either end of the resistor.

The interwiring of the various completed units should be undertaken by referring to the overlays and the various views of the amplifier chassis designed to show the layout that should be adopted in the completed unit.

Testing

Test of the amplifier should commence with satisfying yourself that the power supply is operating correctly before connecting it to the main amplifier. The voltages shown in Table 1 should be present upon switching on the mains.

TABLE 1

C102+ to 0 V	62 V
C103- to 0 V	-62 V
C109- to C109+	22 V
C110- to C110+	22 V

If all is well switch off and — please — discharge the four hefty capacitors via a resistor before doing anything further or else you will be in danger of having a lot of energy make its way to earth via you.


Next connect a 1k5 1W resistor between Q101c and 0V and a similar resistor between Q103c and 0V. Switch on and hopefully the voltages will be shown in Table 2.


TABLE 2

Q101c to 0 V	+50 V
Q103c to 0 V	-50 V
PSU pin 101 to 0 V	+72 V
PSU pin 106 to 0 V	-72 V


Again if OK, switch off and discharge those Cs.

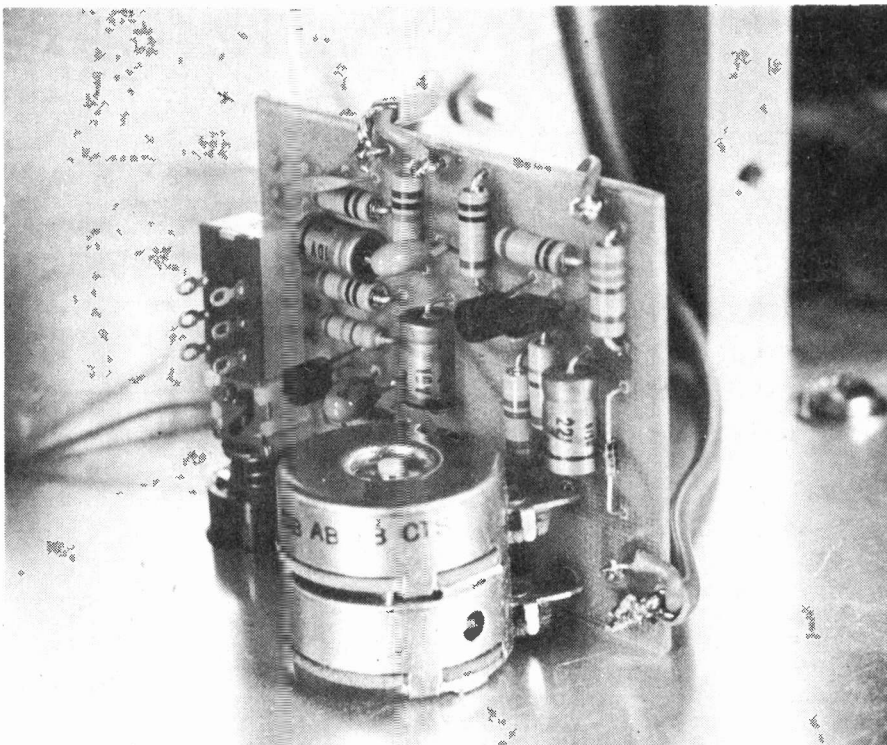Next replace the 5A PSU fuses with a 12V 2W4 light bulb in series with a 47R ½W resistor. This



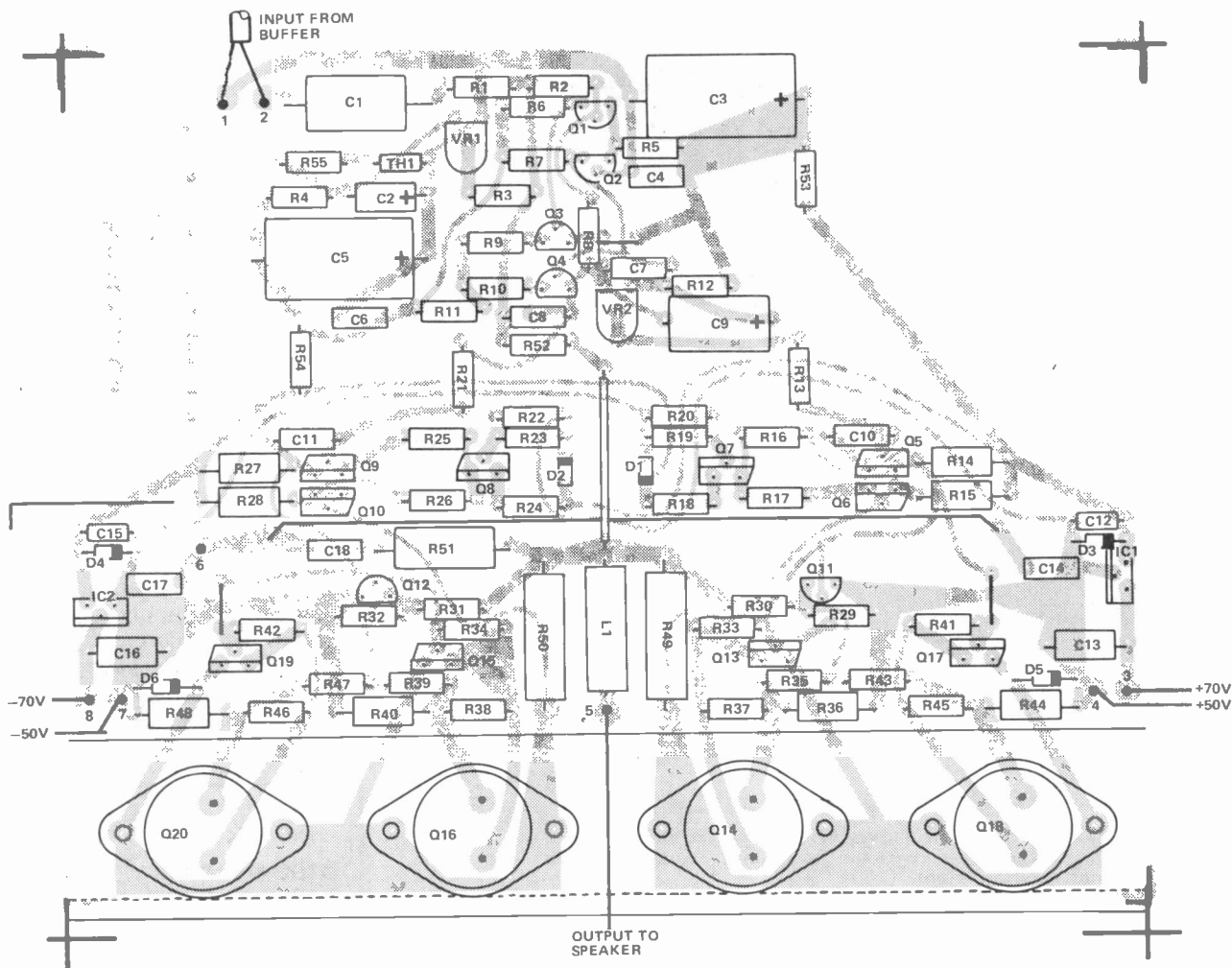

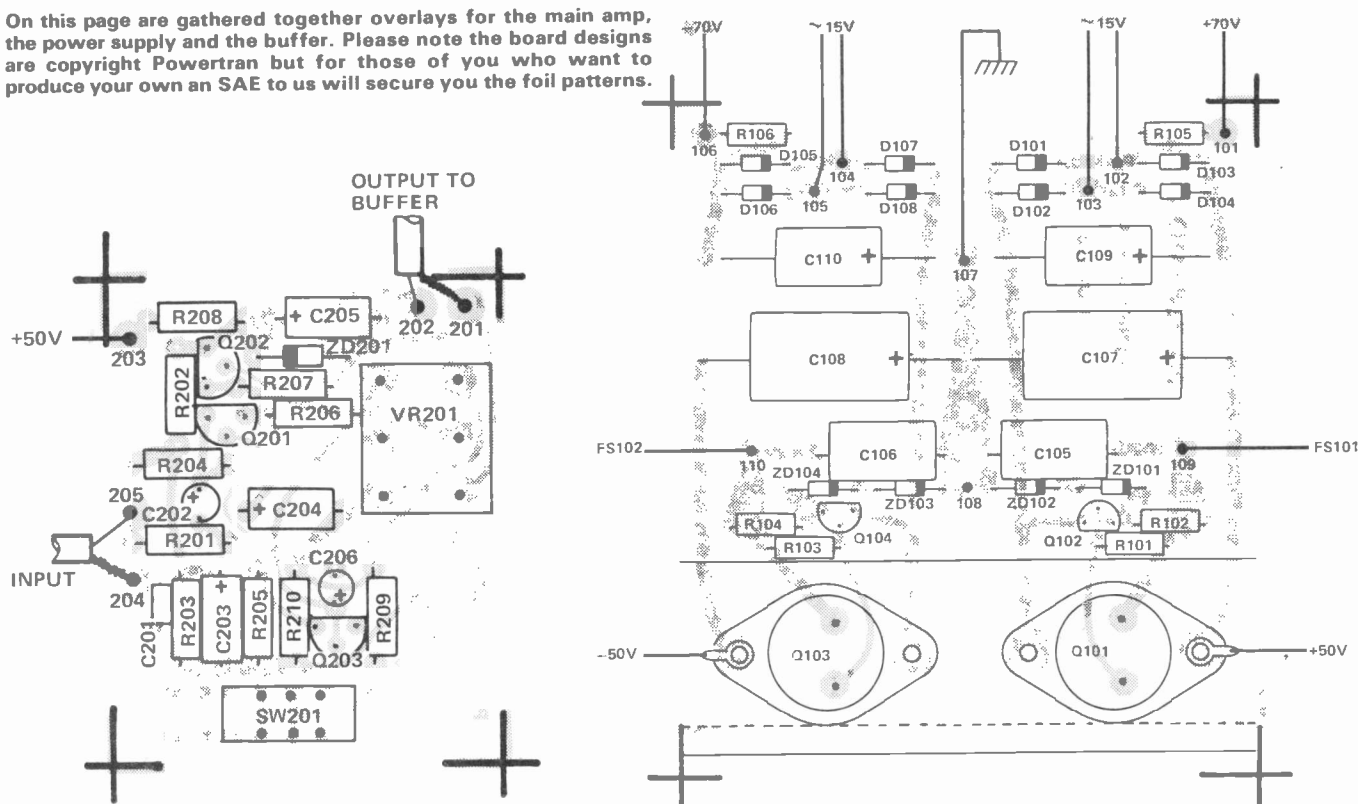On this page are gathered together overlays for the main amp, the power supply and the buffer. Please note the board designs are copyright Powertran but for those of you who want to produce your own an SAE to us will secure you the foil patterns.



PARTS LIST~Buffer & PSU

POWER SUPPLY PARTS LIST		BUFFER	
RESISTORS (allows 2% metal oxide unless stated).		RESISTORS (All 2% OW5 metal oxide unless stated).	
R101, 103	100R	R201, 205	10k
R102, 104	1k	R202, 203, 204	100k
R105, 106	10R	R206	4k7
CAPACITORS		R207	470 R
C101, 102, 103	4700u 63 V electrolytic	R208	3k3
104		R209	2k2
C105, 106	47u 63 V electrolytic	R210	47k
C107, 108	1000u 63 V electrolytic	POTENTIOMETERS	
C109, 110	470u 25 V electrolytic	RV20 1	10k
SEMICONDUCTORS		CAPACITORS	
Q101	2N6052	C201	100p polystrene
Q102	BFR 41	C202	1u 16 V tantalum
Q103	2N 6059	C203, 204	47u 10 V electrolytic
Q104	BFR 81	C205	22u 25 V electrolytic
D101-108	1N4002	C206	10u 16 V tantalum
BR1	12A 150 V bridge	SEMICONDUCTORS	
ZD 101, 103	20 V 400 mW	Q201	BC214L
ZD 102, 104	30 V 400 mW	Q202	2N5459
TRANSFORMER		Q203	BC184L
T1	see text	ZD1	15 V 400 mW
MISCELLANEOUS PCB as pattern, fuses.		MISCELLANEOUS PCB as pattern.	

Construction

With a project of this type, while attempting to keep construction as straightforward as possible, the sheer physical size of many of the components precludes mounting them on a PCB. This inevitably leads to more constructional work and hence to a greater scope for error. Care taken during assembly and careful checking at each stage can save time and (plenty of) money later on. With this in mind please read this section thoroughly and study the photographs of the finished unit before starting constructional work.

The first stage in building up the amplifier is to mount all the passive components and links on the three PCBs according to the appropriate overlay. Needless to say all soldering must be of the highest standard and checks should be made to ensure that there are no solder bridges present.

Power And Its Place

The four power transistors associated with the amplifier and the two required for the power supply are mounted on cooling brackets as shown in our photographs. Care should be taken to ensure that there are no burrs around the holes in the heat sink that might damage the mica washers that must be fitted to all six transistors. In order to aid heat flow from the transistors silicon grease should be smeared on both sides of these mica washers.

Note that solder tags are required to connect to the cases of the two PSV transistors but not on the main amp's devices where connection is made via the PCB.

Bracketed Cooling


The thermal cutout is also fitted to the cooling bracket on which the amplifier's output devices are mounted.

As can be seen in the photos of the amplifier board the following groups of transistors are thermally connected

Q5 Q6 and Q7
Q8, Q9 and Q10
Q13 and Q17
Q15 and Q19

PARTS LIST~Main Amp.

200 W AMP PARTS LIST		CAPACITORS	
RESISTORS (all 2% OW5 Metal Oxide unless stated)		RESISTORS (all 2% OW5 Metal Oxide unless stated)	
R1	9k1	C1	1u polyester
R2	10k	C2	47u 10 V electrolytic
R3, 52	470k	C3, 5	220 63 V electrolytic
R4	56k	C4, 6, 12, 14, 15, 17, 18	100n polyester
R5	62k	C7	22p 160 V polystrene
R6, 7	22k	C8	5p6 63 V polystrene
R8	3M9	C9	470u 6V3 electrolytic
R9, 10, 13, 21, 53, 54	100R	C10, 11	100p 160 V polystrene
R11, 19, 23	1k	C13, 16	220n poltester
R12	13k	SEMICONDUCTORS	
R14, 15, 27, 28	1k1 1W Carbon Film	Q1, 2	2N5401
R16, 17	15R	Q3, 4	2N5382
R18, 24	330R	Q5, 6, 7	BF460
R20, 22	430R	Q8, 9, 10	BF463
R25, 26	15R	Q11	BC212L
R29, 32	120R	Q12	BC182L
R30, 31	18k	Q13, 17	BD420
R33, 34, 41, 42	470R	Q14, 18	MJ15004
R35, 39, 43, 47	750R	Q15, 19	BD419
R36, 40, 44, 48	OR33 2W5 Wire Wound	Q16, 20	MJ15003
R37, 38, 45, 46	47R	INDUCTOR	
R49, 50	OR22 5W Wire Wound	IC1	7815
R51	4R7	IC2	7915
R55	6k8	D1-4	1N4148
R56	4R7 2WG Wire Wound	D5, 6	1N4002
POTENTIOMETERS		MISCELLANEOUS PCB as pattern, thermal fuse, mica washers, connecting wire, etc.	
RV1	5k Cermet		
RV2	200R Cermet		
THERMISTOR			
TH1	VA1056		

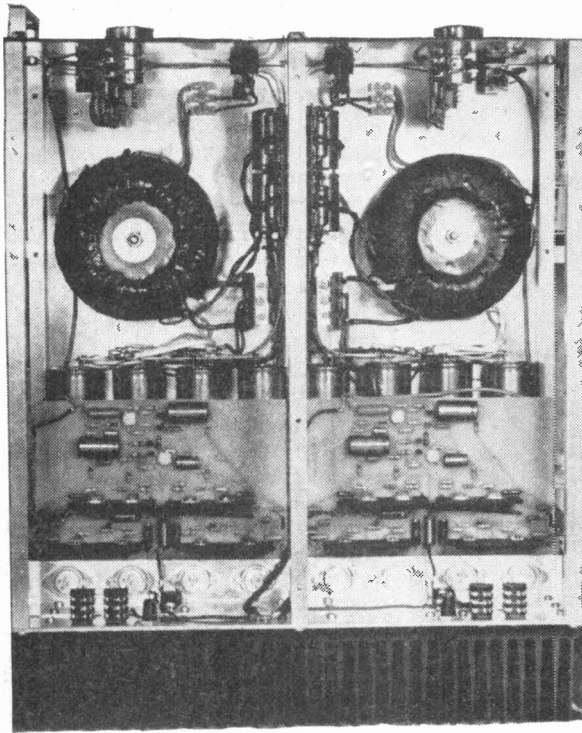

Below can be seen the main circuitry. The heatsinking arrangements of the various output devices can be seen as well as the mounting of C101-C104. Above — an overall view of the amplifier.



The photograph above shows a version of the amplifier built with power level meters. The circuitry required to provide this facility is shown below.


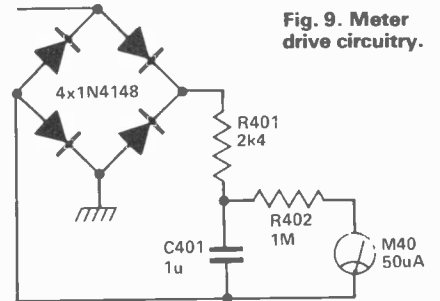


Fig. 9. Meter drive circuitry.

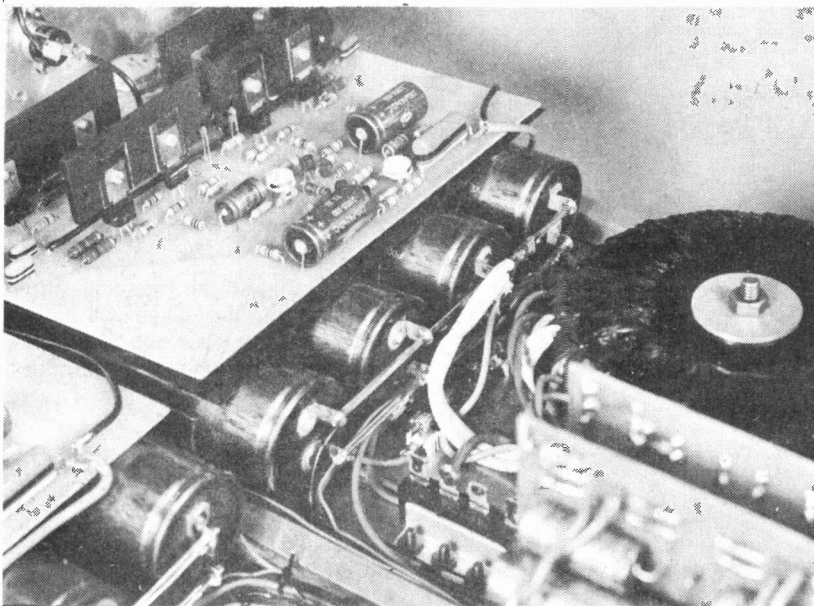

BUYLINES

Powertran are to provide a complete kit of parts for this project. For prices and further details see their advert on the inside front cover.

provides a convenient method of monitoring and limiting the current drawn by the amplifier. Note that if the main amplifier is working correctly you will see an initial surge of light from the bulb which should then die away.

Before connecting power to the amplifier set RV1 to its centre position RV2 fully clockwise and RV201 fully anti-clockwise.

Switch on and check that the voltage between 0V and the R56 and R51 junction is near zero. RV1 should be adjusted until this voltage is exactly zero.

Next RV2 should be rotated until the lamps in the power supply lines start to brighten.

If everything is still going according to plan, replace the power supply fuses and adjust RV2 until the voltage between Q14c and Q16c is 20mV. Resetting the output to zero volts with RV1 completes setting up.

Leave the amp on for about half an hour and recheck all voltages, making any necessary adjustments connect a speaker to the output and 'test drive' the amp for about an hour. A final check of all voltages and your amplifier is ready to go into service.

ETI

SEMICONDUCTOR OFFERS ALL FULL SPEC.

BC212, BC182, BC237, BF197, BC159, BCY71, all 8p each, RCA 2015 TO3 Power Transistor (Sim to 2N3055) 35p, ACY18 18p BF200 20p Motorola MRD 3051 Photo Transistors 35p, N. Channel F.E.T.s, similar to 2N3819 18p, Mosfet Sim to 40673 35p, 3N140 Mosfets 50p, M203 Dual Matched Pairs Mosfets Single Gate per F.E.T. 40p, SL301 Dual Matched Pair SIL N.P.N. Power Transistors FT 300MHz 30p, Intel 1024 bit MOS Rams 95p, Mullard 68113 Triple Varicap Diode 35p, MC1310 Stereo Decoder I.C.s £1.20, TBA800 I.C. Amps 90p CD4051 CMOS 50p, 741 8-pin D.I.L. 23p, MM5316 Clock Chips £3.50 500v 600mA Bridge Rect. (ex. equip.) 25p, 1N4002 100v 1A Diodes 4p, 14005 800v 1A Diodes 7p, E.H.T. SIL Rec 15Kv 2.5mA, 15mm x 5mm 85p, 7812 12v 1A Plastic V. Rees 95p, Min. Nixies ITT 58705i 13 x 6mm Fig Size 85, Nixies ITT GN/9A 13 x 8mm 65p, 0.2" or 0.125" Red LEDs 12p each, MAN3A 3mm LED Displays 50p, Murata 40KHz transducers 15mm diam, £2.95 pair, 300 volts 2 amps (TOS) Thyristors 30p.

MICROPHONES. Grundig Electret Inserts with built-in F.E.T. Preamp £1.50, Crystal Mike Inserts 37mm 50p, Electret Condenser Mikes 1KQ Imp. with std. Jack Plug £2.85, Cassette Condenser Mikes with 2.5 and 3.5 Jack Plugs £2.85, Standard Cassette Mikes 200 ohm Imped. with 2.5 and 3.5 Jack Plugs £1.20, P.A. Mikes Mobile Type 50KQ, Thumb Switch, £4.20

MORSE KEYS—Plastic Type 95p, Hi-speed Type, all metal, £2.25, Hi Imp Phones 2KQ £1.95, SWR/Power Meter type SWR50, SWR 1, 3:1, Power 0-1kW., 3.5-150MHz., 52 ohms Imped., £12.75, SWR ANOF.S. Meter, 3-150MHz., 50 ohms Imped., £9.50, Marker Gen., 300KHz steps to 60MHz., supplied with Xtal for this coverage, £7.90.

CRYSTALS. 300KHz HC6U 40p, 4.43MHz C.T.V. Xtals 45p, 0-1" Edge Connectors, 64 way 65p, 32 way 40p

RELAYS. Min. sealed Relays, all 4 pole changeover, 36Q (6v DC) 45p, 700Q (24v DC) 55p, Min. 220v AC Sealed Relay 2 pole C/O 45p, 240v AC Sealed Relay 3 pole C/O 5 amp Contacts 11-pin base 80p, 12 volt 4 pole N/O Reed Relay 20p, 30 turn dial mechanism with locking arm, aluminium finish dial scaled 0-100, window 0-29, 32mm diam, 6.3mm spindle new £1.75.

MOTORS. 1.5 to 6v DC Model 20p, 12v DC 5 pole 35p, 115v AC min. 3 R.P.M., with Gearbox 30p, 240v AC Synch Motor 1/6th R.P.M. 65p, 240v AC Synch. Motor 1/24th R.P.M. 65p.

BOXES. Black A.B.S. Plastic with brass inserts and lid, 75 x 56 x 35mm 40p, 95 x 71 x 35mm 49p, 115 x 95 x 16mm 57p, Grey Potting Boxes with lugs, 23 x 48 x 23mm 11p, 38 x 52 x 25mm 13p, 60 x 80 x 42mm 28p.

TRANSFORMERS. -6.0-6v 100mA, 9.0-9v 75mA, 12.0-12v 50mA 75p each, 12.0-12v 100mA 95p, 1 1 Triac Xenon Pulse Transformer 30p.

CONDENSER MIKES. EM506 Condenser Mikes, Uni-directional, F.E.T. Amp. Dual Imped. 50K/600 ohms, 30-18KHz., on/off switch, £11.00, Miniature Tie Pin Condenser Mike, 1K Imp., omni-directional, uses hearing aid battery (supplied) £4.95.

STEREO HEADPHONES. 8 ohms, padded earpieces and headband, with curly lead, 30-18KHz only £3.00.

SWITCHES—Min. Toggle, SPST 8 x 5 x 7mm 30p, DPDT 8 x 7 x 7mm 60p, DPDT Centre Off 12 x 11 x 9mm 75p, 4P 2W Sliders 20p, DPDT C/O Sliders 20p, SPST 10 amp Rockers 12p, R.S. Single Pole C/O Push Buttons 45p, Roller Micro Switches 15p, Min. Micro Switches 13 x 10 x 4mm 20p, G.P.O. Keyswitch Assy. 3 Switches 2:3 way, 1-2 way Multipole 35p, Min. Push to make or push to break Switches 16 x 6mm 15p, Plessey Winkler Stud Switches, 2 bank, 1 pole 30 way adj. stop, 75p, Solder Sucker, Plunger type, eye protection, replaceable nozzle, high suction £4.95, Reed switches 28mm norm. open, 6p each

TAPE HEADS—Jap. Cassette Mono 99p, Cassette Stereo £3.00, BSR MN1330 1/2 Track Dual Impedance Rec./Playback 50p, BSR SR99D 1/2 Track Stereo Rec./Playback £1.95, TD10 Assemblies, two heads, 1/2 Track Rec./Playback Staggered Stereo with built-in erase per head £1.20, Tape Head Demag 240v AC £1.95.

BUZZERS—GPO Type 6-12v 20p, Min. Solid State Buzzers 6.9-12 or 24v 15mA 75p, U.H.F. TV Transistorised Push Button Tuners (not Varicap), new and boxed, £2.50

POT CORES—Adj. Vinkor 250-370 Micro H 20p, 260 or 500 Milli Henry Cores 10p each

METERS—Stereo Tuning Meters 100µA per movement £2.75, Grundig Batt. Level Meter 1mA 40 x 40mm £1.10, Min. Level Meter 200µA x 25 x 15mm 75p, Ferranti 600v AC Meter £3.95

BOARDS. 465KHz I.F. Panels, 61F.T.s 30p Board with 14 12v N/O Reed Relays £2.40 Board with 6v C/O Reed Relay £1.20, Contact cooled set reel, 12v/50mA — 15p, Cannon 50 way gold inlay plugs and sockets, free plug — new £1.50 pair

AEROSOLS—Servisol Switch Cleaner + Lubricant 8ozs 55p, Freezer 8ozs 50p, Gear Cleaner + Tar Remover 14ozs, 85p

SOLENOIDS—240v AC 45p, 12v DC H. Duty 75p

POSTAGE 30p UNLESS OTHERWISE SHOWN (EXCESS POSTAGE REFUNDED WITH ORDER) OVERSEAS POST AT COST VAT INCLUDED IN ALL PRICES

S A E FOR LISTS

ORDER ADDRESS

PROGRESSIVE RADIO
31 CHEAPSIDE, LIVERPOOL 2
051-236 0982

SENSATIONAL NEWS!

Hi-Fi Stereo at prices everyone can afford

Hi-Fi Stereo Speakers

our price **£4.95**

Specially matched 8" x 6" high performance drivers with all necessary leads for DIN connection.



Hi-Fi Stereo BSR Autchanger

is records for single play, cue & pause control. Leads supplied for DIN specification for turntable chassis.


our price **£12.95**



Hi-Fi Stereo Tuner Amplifier chassis

30 Watts rated power output, 100pF input, output sockets for headphones, 100pF sockets for private wide, 5p, deep, 21" high, messengers, plugs and leads.

our price **£29.95**



Hi-Fi Stereo Cassette deck

ask for literature to view your own Hi-Fi Stereo tapes, test plug-in, Records direct, Automatic recording adjustment, recording every time.

our price **£39.95**




* All prices include VAT POSTAGE & PACKING. Send cheque/P.O. Today for immediate delivery. Goods fully guaranteed for 12 months. Easy payment terms available on request.

CALLERS WELCOME — ACCESS & BARCLAY CARD ORDERS ACCEPTED
100 Chase Side, Southgate, London N14 5PL — Tel: 01-882 1644

NOW! THE WORLD'S SLIMMEST CALCULATOR

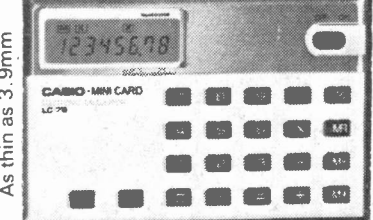The new DINKY calculator with the super slender style from KRAMER & Co. ONLY £16.90.



As thin as 3.9mm

Weights only 39g (including batteries), nearer in size to a business card than to the common calculator. Its features are: 8 digit LCD, also shows function command signs to help you operate it easily. Perfect percentage — regular, ratio, add-on, discount mark-up, profit, increase/decrease. Battery lasts for a long 1,000 continuous hours.

Comes in special leatherette card case.

Enquiries to: **Price £16.90**
KRAMER & CO.
9 OCTOBER PLACE
HOLDERS HILL ROAD, LONDON
NW4 1EJ
Telex 888941. Attn. KRAMER K7
Telephone: 01-203 2473
EXPORT ORDERS WELCOME
MAIL ORDER ONLY

APRIL FOOL

APRIL ONLY
DM958 10p. DM936 10p.
2N2192, 25 £1. 74H00 15p.
TBA810S + Data 50p. TIP 31 35p.
2N3055 40p. 3.5 MM JACK SKT
Chassis MNT 5 for 30p. FPE 100
GaAs Intra Red Emitter + Data 35p.
Westinghouse Hybrid Rectifier/
Voltage Regulators 12-18.5v 2A +
Data £3.50. BF1956P, T1L209
(Red) 9p. 2 Led (Red) 10p. Ocp70
10p. WO4 (400v 1 amp Bridge)
18p. 75450 30p. 741 (8DiI) 17p.
All above P/P 10p.

POCKET PAGER

Miniature crystal controlled FM RX Single Superhet around 30MHZ 450KHZ IF contains various tone detectors. Ideal for modification to 27MHZ Radio Control OR 28MHZ Amateur Band. Many complete with built in 2.5v DEAC + circuit of similar type £3.95. P/P 25p.

A1, A2, A3 Boards still available.

L.B. Electronics
43 Westacott, Hayes
Middlesex UB4 8AH

electronics today


international

What to look for in the May issue: On sale April 8th

ROBOT ISSUE

To many people robots are in the realm of fantasy, forming part of the visionary world of science-fiction. Sci-Fi authors paint scenarios about possible future existences; Dr Peter Sydenham, Electronics Today International special correspondent, and one time robot builder himself, presents the factual side of robots.

Features discuss what robots are, their purpose and structure. An exclusive interview with Britain's robot expert, Professor Thring of Queen Mary College, London, will provoke thought about the future. Dr Mike Larcombe, Head of the Warwick University Robot Laboratory, will explain the state of the art of robot brainpower and combines with Dr Sydenham to provide a guide to constructing professional-quality robots.

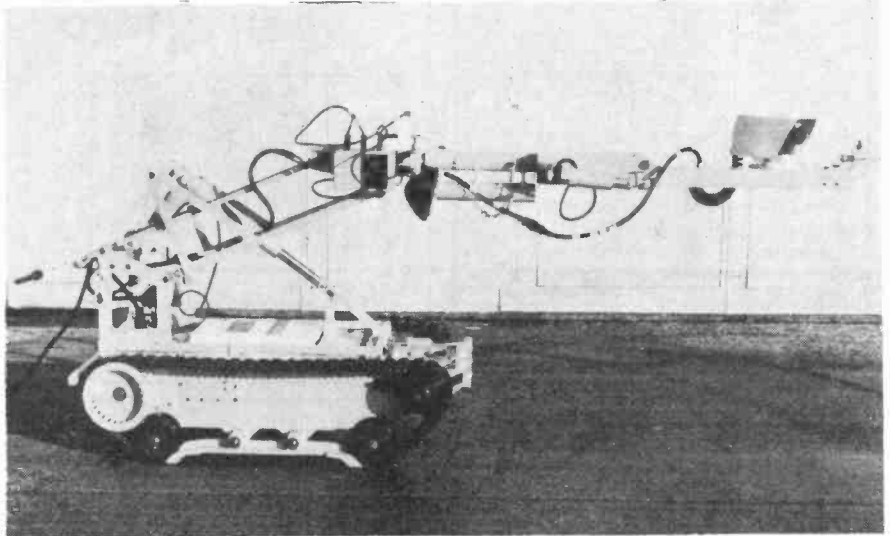

C.C.D. PHASER

In the beginning there was tape phasing, and it was good — but cumbersome. Then ETI said, 'Let us use new technology,' and it was good — and compact. Next month we publish a state-of-the-art phaser/flanger using the Mullard TDA1022 delay line, which is a charge coupled device. So if you want really good effects, don't miss the May edition of ETI!

MK2 ELECTRONIC IGNITION

The Mk 1 was originally published in September 1973, and many thousands have been successfully built since then. Stirling Sound have taken the design a step further, refining the component values and designing a PCB (instead of the tagboards). So if you missed it first time round, you can investigate the Mk 2 with added vitamin B and marilbone jelly!

SPOCK RADIO

"Most illogical! How did primitive Earthlings design such a machine?" Beam down next month for the answer.



T159 Review

The Texas T159 is one of the latest pocket card programmables to challenge the calculator market. With its phenomenal programming power — up to 960 program steps memory position, software in plug-in pre-programmed modules and pocketability, this calculator will undoubtedly set the pace for the next few years. Next month we shall be looking critically at the T159 and bringing you all the facts.

HELPING HAND PROJECT

Quite a while ago, we ran a competition in conjunction with the Royal National Institution for the Deaf — next month we publish the winning entry. Although designed as an integrated system, we think the separate units will find applications in other areas besides remote warning for the deaf.

Articles mentioned here are in an advanced state of preparation but circumstances may affect the final contents.

data sheet

TGS 812/813 GAS SENSOR

FIGARO

THE TGS 812/813 are semiconductor gas sensors suitable for general purpose combustible gas detection.

The sensor consists of a ceramic tube onto which is deposited a layer of the semiconductor (mainly tin dioxide) and the electrodes.

In fresh air the resistance of the semiconductor is constant, but as the concentration of the detectable gases increases and comes into contact with the sensor's surface, the resistance of the semiconductor changes.

In order to increase the response time of the device, the sensor is heated to a temperature between 200 and 400°C by a heated coil in the ceramic tube.

The sensitivity characteristics of the TGS sensors are altered by changes in atmospheric temperature and humidity. The detection principle of the sensor is based on chemical absorption and desorption of gases on the sensor's surface, and because these reactions are temperature dependent and water vapour can be considered a gas, the effects of temperature and humidity changes cannot be eliminated from the sensor. These effects can, however, be reduced by suitable circuit design (see Fig 7).

The TGS812/813 sensors are available from:
Watford Electronics
 33-35 Cardiff Road Watford Herts.

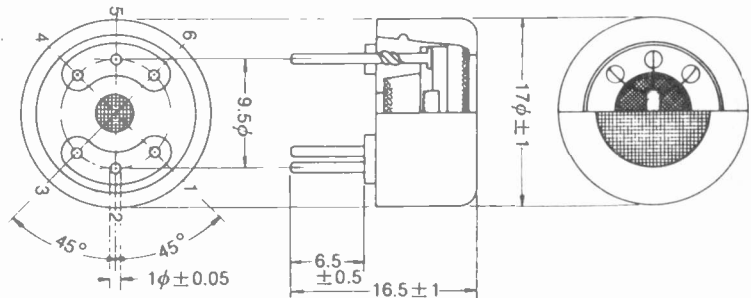
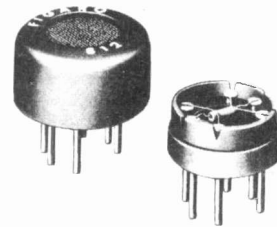
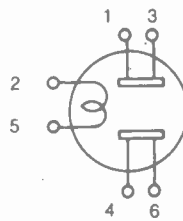
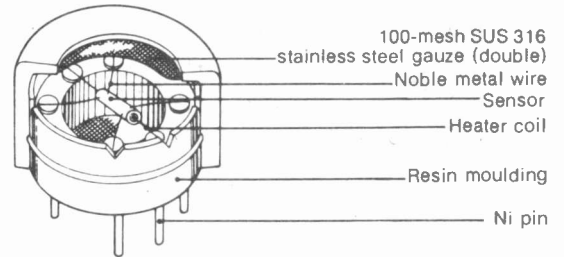


Fig 1. Mechanical structure of types 812 & 813 sensors, in mm.

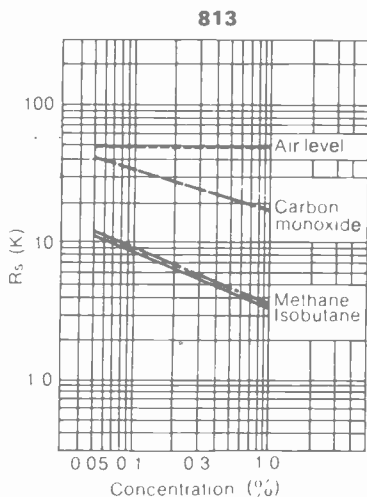
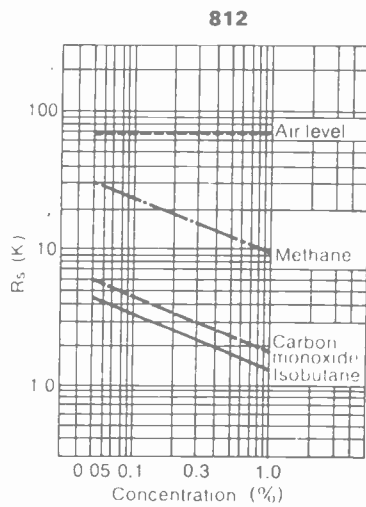


Fig 2. Sensor resistance (R_s) changes with different concentrations of gas.

TYPE NO.	TGS 812/813
TEST CONDITION	
(A) Circuit Voltage (VC)	10V (A.C. or D.C.)
(B) Heater Voltage (VH)	5.0V (A.C. or D.C.)
Heater Power	
Dissipation (PH)	Approx. 650mW.
(C) Load Resistance (RL)	4K
WARM-UP TIME	Approx. 2 min.
HEATER RESISTANCE (RH)	38±3
SENSOR RESISTANCE (Rs)	1~10K in Isobutane 1000ppm/air
RATIO OF RESISTANCE	$\frac{R_s \text{ in Isobutane } 3000\text{ppm/air}}{R_s \text{ in Isobutane } 1000\text{ppm/air}} = 0.63 \pm 0.05$

Fig 3. Sensor characteristics.

Sensor type	Electrical ratings	Applications and Features
812	V _{CC} : (Max.)24V V _H : 5.0V	General purpose combustible gas detection. Carbon Monoxide detection. High CO sensitivity enables most types of smoke to be detected.
813	V _{CC} : (Max.)24V V _H : 5.0V	General purpose combustible gas detection. Methane detection. High CH ₄ sensitivity makes it suitable for Natural Gas detectors.

Fig 4. Differences in sensitivities between 812 & 813.

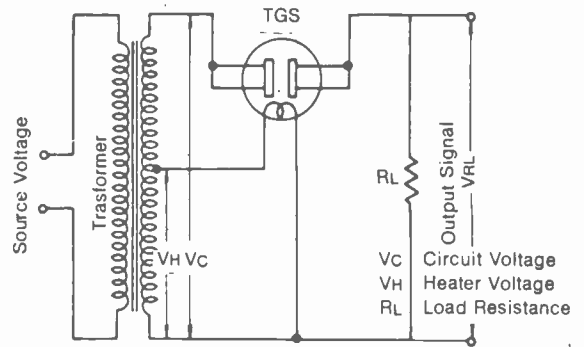


Fig 5. Basic test and measuring circuit.

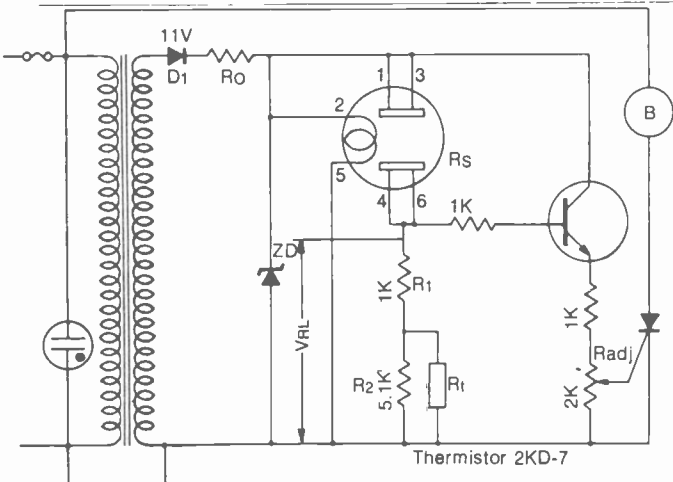


Fig 6. Circuit for use as a gas leak detector.

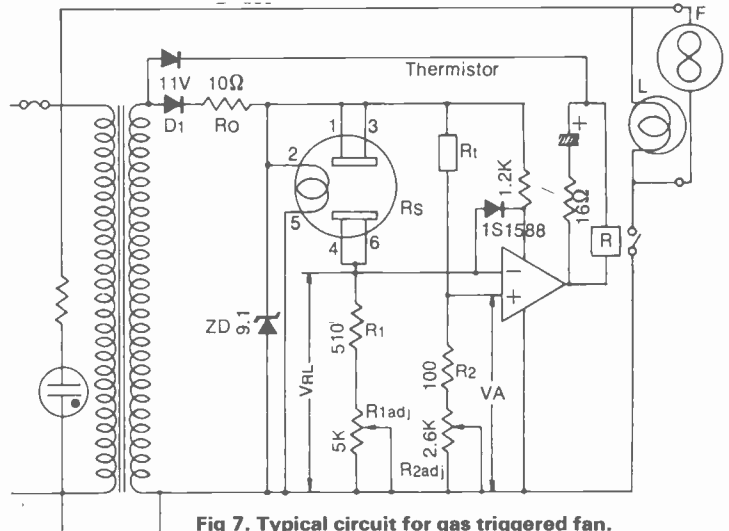


Fig 7. Typical circuit for gas triggered fan.

INTRODUCING OUR NEW AND EXCITING TV GAME TRIO

Easy to build TV Games — no test equipment required

STUNT RIDER

4 GAMES based on

- AY-3-8760 **ONLY***
- B & W Kit **£20.90**
- Colour Kit **£26.90**
- AY-3-8760 **£12.70**

NEW

SUPER TELESPORTS

10 GAMES based on

- AY-3-8600 **ONLY***
- B & W Kit **£14.90**
- Colour Kit **£20.90**
- AY-3-8600 **£9.50**


NEW

TANK BATTLES

Based on AY-3-8710


- ONLY***
- B & W Kit **£21.50**
- Colour Kit **£27.50**
- AY-3-8710 **£12.90**

NEW

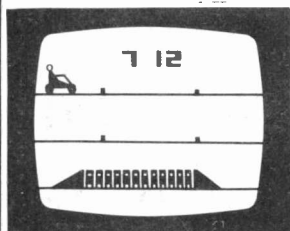


* Super Stunt (illustrated), Bus Stunt, Moto-cross, Drag Race.

- * On Screen Scoring and Timing.
- * Realistic throttle and crash sounds through TV speaker.
- * Amateur or professional selection mode.
- * Simple potentiometer throttle control.
- * Single 9v supply.

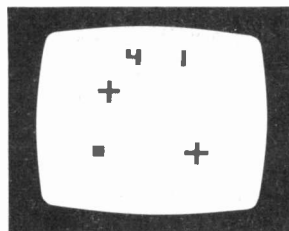

* Shoot 2-no rifle required! (illustrated). Shoot 1, Football, Hockey, Solo, Basketball, Gridball, Tennis, Squash, Basketball Practice.

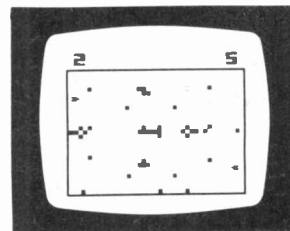- * On screen scoring coded to player.
- * Triple sounds through TV speaker.
- * Auto ball speed-up mode.
- * Controlled by joystick and fire/serve button.
- * Single 9v supply.



* Battle as Professional or Territorial Soldier.

- * On screen scoring coded to tanks.
- * Tanks controlled by toggle switches or joystick and fire button.
- * Realistic tank, shell burst and explosion sounds through TV speaker.
- * Three speed tank control.
- * Exploding mines and terrain barriers.
- * Guided missile shells
- * Single 9v supply.

All kits include full instructions LS I, PCB, pre-tuned UHF and sound modulators, etc., fully guaranteed. Cases and controls not included. UHF and Sound Modulators, pre-tuned, **£5.50** (pair). Joysticks for AY-3-8600 **£3.50** (pair). Joysticks for AY-3-8710 (TBA) colour encoder module, pre-tuned **£6.60**. Regulated mains adaptor **£3.50**.

* All prices include VAT and P&P

TUNE IN TO A BARGAIN TODAY. Send cheque or P.O. to:

VIDEOTIME PRODUCTS

the video and time products people

Trade enquiries welcome

**56 QUEENS ROAD
BASINGSTOKE, HANTS
RG21 1RE
TEL. (0256) 56417**

E.T.I. I.B. METAL LOCATOR Mk 2

Save Time and Money by buying KIT

The Kit includes:
Resistor PAK
Capacitor PAK
Semiconductor PAK

Screened Cable, Wire for Coils, Fibre Glass Printed Circuit Boards, Case, Meter, Solder, Speaker Jack Sockets, Knobs, etc., in fact everything except Marley Pipe and Hand Grip.

Save £1.50 on cost of components bought separately and solve your supply problem at the same time.

Price inclusive of VAT £18.50


P&P 40p

R. F. EQUIPMENT SPARES LTD

3 Lacy Close, Wimborne, Dorset

Tel: (0202) 885854

LOOK! HERE IT IS!

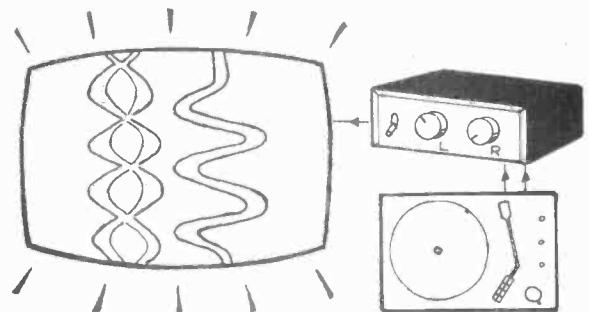

THE AMAZING VIDEOGRAPH ©

- Displays sound waves in full colour.
- Automatic background colour change.
- Superb home / disco entertainment — Also useful for stereo waveform analysis, etc.
- Output direct to TV aerial socket.

● COMPLETE KIT ONLY **£18.95** ● CASE AND CONTROLS IF REQUIRED **£6.95**

COLOUR MODULATOR FOR ALL TV GAMES **£6.95**

The only design to offer:

- 3 separate inputs R, G and B.
- SWITCHABLE background colours.
- Easy connection to any game.

PCB and Parts for AY-3-8500/8550 Game **£3.95**

J. M. STUART-BRUGES

137 BILLERICAY ROAD, HERONGATE, BRENTWOOD
ESSEX CM13 3SD. TEL. 0277 810244



HOME MICROCOMPUTER

**NORTHERN SEMINAR
MANCHESTER
APRIL 1 **£5.50****

After the enormous success of the Wembley Seminar Lynx have been persuaded that there are sufficient Northerners waiting to attend their own show. All day. Microprocessor lectures and presentation of the Nascom I. Only 350 seats.

**Z80 QUERTY KEYBOARD
MONITOR PROGRAM
VDU INTERFACE (TV)
2K R.A.M. CASSETTE INTERFACE
P.C.B. TELETYPE INTERFACE**

EXPANDABLE SYSTEM

NASCOM I **£197.50
+ VAT**

LYNX ELECTRONICS (LONDON) LTD.


**92 BROAD STREET, CHESHAM, BUCKS
02405 75151**

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11¼" x 8¼" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems.

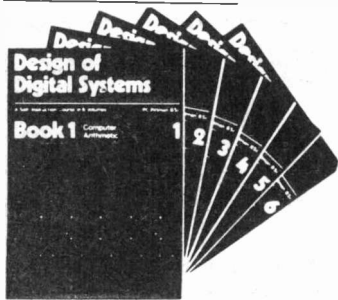

£7.10

plus 90p packing and surface post anywhere in the world

Overseas customers should send for Proforma invoice.

VAT zero rated

Also available — a more elementary course assuming no prior knowledge except simple arithmetic.

Digital Computer Logic and Electronics.

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4.60

plus 90p P&P

Offer Order both courses for the bargain price £11.10 plus 90p P&P A saving of £1.50

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

NEW from Cambridge Learning Enterprises: **THE ALGORITHM WRITER'S GUIDE** use, design and layout; vital for computing, training, wall charts, etc.

£2.95

plus 45p P&P

Guarantee. If you are not entirely satisfied your money will be refunded. Cambridge Learning Enterprises, Rivermill Lodge, St. Ives, Huntingdon, Cambs. Proprietors: Drayridge Ltd. Regd. Office as above. Reg. No. 1328762.

To: Cambridge Learning Enterprises, Unit 15 Freepost Rivermill Lodge, St. Ives, Huntingdon, Cambs. PE14 4BR.
Please send me . . . set(s) of Design of Digital Systems at £8.00 each, P&P included.
or . . . set(s) of Digital Computer Logic and Electronics at £5.50 each, p & p included
or . . . combined set(s) at £12.00 each, p & p included
or . . . The Algorithm Writer's Guide at £3.40 each, p & p included

Name


Address

*Delete as applicable

No need to use a stamp — just print FREEPOST on the envelope.

ETI 11

THE DYNAMIC DUO

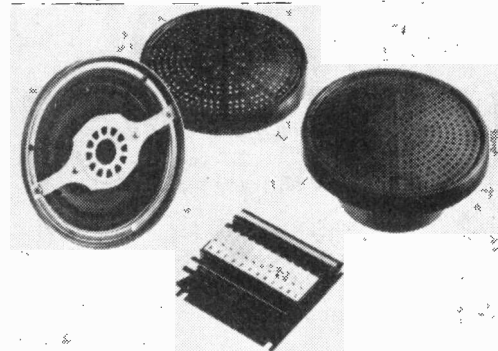

The C15/15 is a unique Power Amplifier providing Stereo 15 watts per channel or 30 watts Mono and can be used with any car radio/tape unit. It is simply wired in series with the existing speaking leads and in conjunction with our speakers S15 produces a system of incredible performance.

A novel feature is that the amplifier is automatically switched on or off by sensing the power line of the radio/tape unit, hence alleviating the need for an on/off switch.

The amplifier is sealed into an integral heatsink and is terminated by screw connectors making installation a very easy process.

The S15 has been specially designed for car use and produces performance equal to domestic speakers yet retaining high power handling and compact size.

C15/15

- 15 watts per channel into 4Ω
- Distortion 0.2% at 1kHz at 15 watts
- Frequency Response 50Hz-30kHz
- Input Impedance 8Ω nominal
- Input Sensitivity 2 volts R.M.S. for 15 watts output
- Power Line 10-18 volts
- Open and Short Circuit Protection
- Thermal Protection
- Size 4 x 4 x 1 inches

C15/15 Price £17.74 + £2.21 VAT P&P free

Data on S15

- 6" Diameter
- 5¼" Air Suspension
- 2" Active Tweeter
- 20oz Ceramic Magnet
- 15 watts R.M.S. Handling
- 50Hz-15kHz Frequency Response
- 4Ω Impedance

S15 Price per pair £17.74 + £2.21 VAT P&P free

TWO YEARS GUARANTEE ON ALL OF OUR PRODUCTS

Please supply
Total Purchase Price

I enclose cheque Postal Order Money Order
Please debit my Access Account Barclaycard Account

Account Number

Name & Address

Signature



Crossland House,
Nackington,
Canterbury, Kent
Tel (0227) 63218

COMPU/TIME offers
COMPU/TIME A
CT 100
Real Darn Clever
Enhancement to users of
IMSAI/ALTAIR
Microprocessors

\$100 BUS COMPATIBLE

TIME & CALENDAR

COMPU/TIME CT100 \$199 Kit \$245 Assembled
 COMPU only CT101 \$149 Kit \$189 Assembled
 TIME only T102 \$165 Kit \$205 Assembled
 COMPU/TIME PC Board only \$ 80

MM16 EPROM

- Utilizing up to 16 2708 EPROMS
- S-100 Bus Computer Systems
- Memory capacity of 8K or 16K bytes by DIP
- 8K boundary addressing by DIP Switch
- 0 to 4 wait cycles by DIP Switch
- Data output address inputs line fully buffered
- High grade glass epoxy with plated-thru holes
- Epoxy solder masked

\$99.00

FCS 8000A — 3 1/2 Digit — 8" Display
 NEW! 25 Pin Version with color & amp/pm indicator
 • Connects almost any one for one with 3817, 3817A or D. (3817 available at \$5.00 each)
 • Typical segment current 8mA except color, 10 hrs @ 5 c and 10 min, @ 8 d which are 16 mA
 • MAXIMUM FORWARD CURRENT — 25 mA

SPECIAL \$4.95 EA.

1 Forward voltage drop
 15 volts

Vector

SLIT-N-WRAP WIRE WRAP TOOL

- Slits and opens insulation exposing bare wire.
- No pre-cutting or pre-stripping.
- Comes complete with two 100ft spools. No. 28 AWG wire

Model P130 \$24.50

Channel F — additional cartridges — \$17.95 ea.

- 0811 — Tic Tac / Shooting Gallery
- 0815 — Spacewar (2 players)
- 0818 — Quadra-doodle / Doodle
- 0819 — Drag Strip (1 or 2 players)
- 0812 — Desert Fox / Shooting Gallery
- 0820 — Maze (2 players)
- 0822 — Baseball (2 players)

Plugboards 8800V

Universal Microcomputer Processor plugboard, use with S-100 bus complete with heat sink & hardware 5.3 x 10 x 1/16

\$19.95

CHANNEL F — **FRANCHISE VIDEO ENTERTAINMENT SYSTEM**

- Freeze Action • Speed Option
- Automatic time and scorekeeping
- Battery-free AC operation
- Dual controls with 8-way action
- Built-in Pro Hockey and Tennis games
- Easy hook-up on any B/W or Color TV
- Factory warranty

\$129.95

D-SUB CONNECTORS

NO. PINS	PART NO	PRICE	COVER PRICE
9	DE 9P	1.49	1.25
9	DE 9S	2.15	
15	DA 15P	2.11	1.50
15	DA 15S	3.10	
25	DB 25P	3.00	1.50
25	DB 25S	4.00	
37	DE 37P	4.14	2.00
37	DE 37S	6.00	
50	DD 50P	5.40	2.25
50	DD 50S	8.00	

EDGE CONNECTORS

NO. PINS	TYPE	PRICE
20	DUAL 10 PIN	GOLD \$ 5.00
30	DUAL 15 PIN	GOLD 7.75
44	DUAL 22 PIN	GOLD 1.95
44	DUAL 22 PIN	GOLD 2.50
80	DUAL 40 PIN	GOLD 4.95
86	DUAL 43 PIN	GOLD (8000) 5.00
100	DUAL 50 PIN	GOLD (IMSAI/ALTAIR) 4.25
100	DUAL 50 PIN	GOLD (IMSAI/ALTAIR) 4.95
100	DUAL 50 PIN	GOLD (IMSAI/ALTAIR) 3.50
100	DUAL 50 PIN	TIN (1" SPACING) 3.25

ALTAIR/IMSAI CARD GUIDES 25¢ EACH

CLOCK CHIPS

MM5309 6 Digit, BCD Outputs, Reset PIN \$9.95
 MM5311 6 Digit, BCD Outputs, 12 or 24 Hour 4.95
 MM5312 4 Digit, BCD Outputs, 1 PPS Output 4.95
 MM5314 6 Digit, 12 or 24 Hour, 50 or 60 Hz 4.95
 MM5316 4 Digit, Alarm, 1 PPS Output 6.95
 MM5318 Video Clock Chip, For Use With (MM5814) \$9.95
 CT7001 6 Digit, Calendar Alarm, 12 or 24 Hour 5.95

IC SOCKETS

PIN	Lo Profile-Solder Tin				PIN	Wire Wrap			
	1 24	25 99	100 999	1K & up		1 24	25 99	100 999	1K
(8)	15	14	13	12	14	34	33	31	29
(14)	25	20	16	14	16	36	34	32	30
(16)	25	20	16	14	18	38	36	34	32
(20)	28	27	26	20	22	40	38	36	34
(22)	34	33	30	239	28	42	40	38	36
(28)	36	35	34	28	24	44	42	40	38
(34)	36	35	34	289	36	46	44	42	40
(36)	44	43	42	367	36	46	44	42	40
(40)	60	58	57	493	40	56	54	52	50

7400 TTL Series

7400	18	7441	75	7496	80	74160	130
7401	20	7442	76	7497	82	74161	130
7402	20	7443	120	74100	125	74162	130
7403	20	7445	105	74107	40	74163	140
7404	20	7446	105	74108	40	74164	150
7405	25	7447	85	74110	80	74165	140
7406	35	7448	95	74116	200	74166	150
7407	35	7450	70	74120	70	74167	150
7408	25	7451	20	74121	55	74170	200
7409	25	7453	20	74122	45	74172	9.75
7410	30	7454	20	74123	90	74173	100
7411	25	7460	20	74125	55	74174	1.10
7412	40	7470	40	74126	60	74175	1.20
7413	75	7472	74	74128	65	74176	1.50
7416	35	7473	40	74132	1.50	74177	90
7417	40	7474	40	74136	1.80	74180	1.00
7420	20	7475	70	74141	1.15	74181	2.00
7422	75	7476	40	74142	4.00	74182	90
7425	30	7479	200	74144	4.00	74184	2.00
7426	30	7480	60	74145	1.10	74185	2.00
7427	35	7482	1.50	74147	2.50	74186	12.00
7428	40	7483	85	74148	7.75	74190	1.40
7429	40	7485	1.10	74150	1.00	74191	1.25
7430	25	7486	40	74151	1.10	74192	1.10
7432	30	7489	2.75	74153	1.10	74193	1.10
7433	40	7490	55	74154	1.10	74194	1.20
7437	30	7491	1.10	74155	1.10	74195	1.00
7438	35	7492	60	74156	1.10	74196	1.10
7439	36	7493	60	74157	1.20	74197	1.30
7440	20	7494	85	74158	7.75	74198	1.50
		7495	90	74159	3.60	74199	1.75

74LS00

74LS00	29	74LS130	125	74LS192	275
74LS01	29	74LS131	125	74LS193	275
74LS02	29	74LS132	125	74LS194	275
74LS03	29	74LS133	125	74LS195	187
74LS04	29	74LS134	125	74LS196	187
74LS05	29	74LS135	125	74LS197	187
74LS10	29	74LS136	125	74LS201	200
74LS12	29	74LS137	125	74LS202	200
74LS13	29	74LS138	125	74LS203	200
74LS14	110	74LS139	125	74LS204	200
74LS15	40	74LS140	125	74LS205	200
74LS16	69	74LS141	125	74LS206	200
74LS17	69	74LS142	125	74LS207	200
74LS18	69	74LS143	125	74LS208	200
74LS19	69	74LS144	125	74LS209	200
74LS20	69	74LS145	125	74LS210	200
74LS21	40	74LS146	125	74LS211	200
74LS22	40	74LS147	125	74LS212	200
74LS23	40	74LS148	125	74LS213	200
74LS24	40	74LS149	125	74LS214	200
74LS25	40	74LS150	125	74LS215	200
74LS26	39	74LS151	125	74LS216	200
74LS27	39	74LS152	125	74LS217	200
74LS28	39	74LS153	125	74LS218	200
74LS29	39	74LS154	125	74LS219	200
74LS30	29	74LS155	125	74LS220	200
74LS31	29	74LS156	125	74LS221	200
74LS32	29	74LS157	125	74LS222	200
74LS33	29	74LS158	125	74LS223	200
74LS34	29	74LS159	125	74LS224	200
74LS35	29	74LS160	125	74LS225	200
74LS36	29	74LS161	125	74LS226	200
74LS37	29	74LS162	125	74LS227	200
74LS38	29	74LS163	125	74LS228	200
74LS39	29	74LS164	125	74LS229	200
74LS40	29	74LS165	125	74LS230	200
74LS41	29	74LS166	125	74LS231	200
74LS42	29	74LS167	125	74LS232	200
74LS43	29	74LS168	125	74LS233	200
74LS44	29	74LS169	125	74LS234	200
74LS45	29	74LS170	125	74LS235	200
74LS46	29	74LS171	125	74LS236	200
74LS47	29	74LS172	125	74LS237	200
74LS48	168	74LS173	125	74LS238	200
74LS49	29	74LS174	125	74LS239	200
74LS50	29	74LS175	125	74LS240	200
74LS51	29	74LS176	125	74LS241	200
74LS52	29	74LS177	125	74LS242	200
74LS53	29	74LS178	125	74LS243	200
74LS54	29	74LS179	125	74LS244	200
74LS55	29	74LS180	125	74LS245	200

CMOS

34001	40	4050	61	4517	850	MM74C129N	139
4000	25	4051	110	4518	105	MM74C130N	139
4001	25	4052	110	4519	90	MM74C131N	139
4002	25	4053	110	4520	185	MM74C132N	139
4004	350	4060	325	4521	25	MM74C133N	139
4006	40	4061	700	4522	175	MM74C134N	139
4007	25	4063	250	4527	300	MM74C135N	139
4008	125	4066	35	4528	175	MM74C136N	139
4010	48	4067	600	4583	145	MM74C137N	139
4011	25	4068	35	4584	75	MM74C138N	139
4012	25	4070	85			MM74C139N	139
4013	60	4071	35			MM74C140N	139
4014	125	4072	35	MM74C00N	38	MM74C00N	84
4015	125	4073	35	MM74C01N	38	MM74C01N	84
4016	59	4075	35	MM74C02N	38	MM74C02N	84
4017	125	4076	185	MM74C03N	38	MM74C03N	84
4018	125	4077	47	MM74C04N	38	MM74C04N	84
4019	70	4078	35	MM74C05N	38	MM74C05N	84
4020	125	4081	35	MM74C06N	38	MM74C06N	84
4021	125	4082	35	MM74C07N	38	MM74C07N	84
4022	125	4085	135	MM74C08N	38	MM74C08N	84
4023	35	4086	300	MM74C09N	38	MM74C09N	84
4024	100	4089	300	MM74C10N	38	MM74C10N	84
4025	35	4093	75	MM74C11N	38	MM74C11N	84
4026	225	4098	250	MM74C12N	84	MM74C12N	565
4027	50	4100	175	MM74C13N	84	MM74C13N	565
4028	125	4161	175	MM74C14N	200	MM74C14N	1200
4029	150	4162	175	MM74C15N	200	MM74C15N	1200
4030	60	4163	175	MM74C16N	99	MM74C16N	1200
4032	160	4174	175	MM74C17N	675	MM74C17N	1200
4033	200	4175	160	MM74C18N	132	MM74C18N	1200
4034	350	4184	180	MM74C19N	389	MM74C19N	1200
4035	160	4501	175	MM74C20N	189	MM74C20N	84
4038	160	4502	175	MM74C21N	189	MM74C21N	84
4040	150	4503	175	MM74C22N	189	MM74C22N	84
4041	48	4506	70	MM74C23N	189	MM74C23N	84
4042	125	4507	100	MM74C24N	567	MM74C24N	84
4043	120	4508	400	MM74C25N	340	MM74C25N	84
4044	25	4510	175	MM74C26N	171	MM74C26N	84
4045	250	4511	200	MM74C27N	257	MM74C27N	84
4046	150	4512	150	MM74C28N	189	MM74C28N	84
4047	250	4514	475	MM74C29N	161	MM74C29N	84
4048	100	4515	475	MM74C30N	161	MM74C30N	84
4049	61	4516	175	MM74C31N	161	MM74C31N	84

LINEAR

LM300A	170	LM702H	79	LM211N	139
LM301AH	35	LM703LN	45	LM2900N	139

Avoid the horrors of heavenly H₂O with our Project Teams

RAIN ALARM

MARCH WINDS AND APRIL showers bring forth May flowers — not exactly poetry, more accurate reporting of activity on the weather and horticulture fronts at this time of year. Additionally the bit about April showers is likely to bring forth more than the odd May bud if one of these periods of intermittent precipitation disrupts a busy housewife's washday by relegating her almost dry laundry to the ranks of the wet behind the eiderdown brigade.

It May Rain!

It's here that the good guys of the ETI project team come to the rescue with their Rain Alarm. This little fellow might well upstage any canine companion as a housewife's best friend, at least on washday, by giving a warning at the first sign of rain, giving plenty of time to get the washing in before it gets too wet.

The rain alarm should be placed out in the open and a length of two core wire run between it and an eight ohm speaker. We used an old

intercom sub-station to provide a home for our speaker but a car extension speaker or indeed any suitably boxed eight ohm device would be fine.

Any rain falling on the sensor track, formed as part of the PCB (neat innit?), will set off the alarm and produce a distinctive, intermittent bleep-bleep.

Construction

Construction is straightforward if the PCB layout shown is used and in the case of this project we would recommend that the PCB is used, as this adds to the attractiveness of the project.

Assemble the components according to the overlay, ensuring that the tantalum capacitor is connected the right way round. If you do not use a socket for IC1, solder pins seven and fourteen before the others (this allows the device's internal protection circuitry to function).

In our prototype we used a value of 4M7 for R1 which acts as a sensitivity adjustment. This value leads to a 'hair trigger' alarm and the value could well be reduced according to the level of sensitivity required.


When construction is complete and the alarm has been tested the area of the PCB that holds the components should be covered with some suitable non-conducting potting compound — epoxy resin should do — to render it waterproof.

Power To Your

Power consumption of the unit is so low when the alarm is not triggered that it was not thought necessary to provide an on/off switch.

While this unit is not as effective as a device to control the weather — still working on that one — it should at least prevent some of those washday blues.

ETI

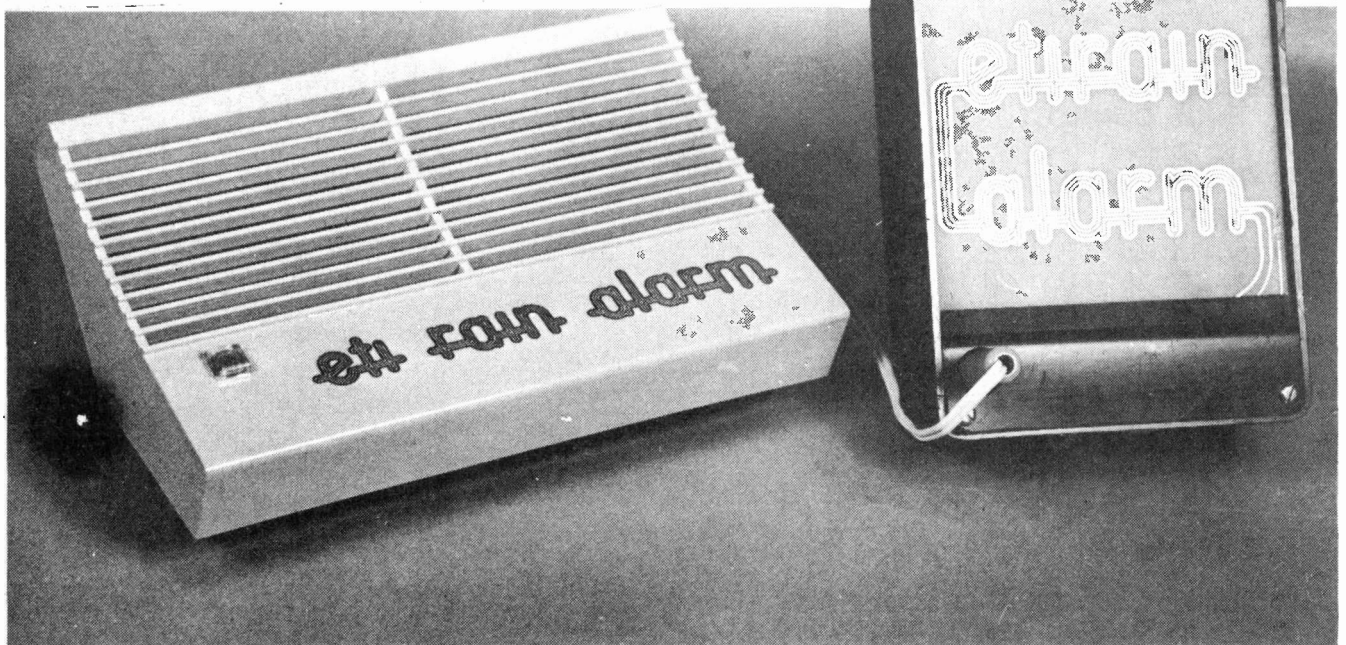


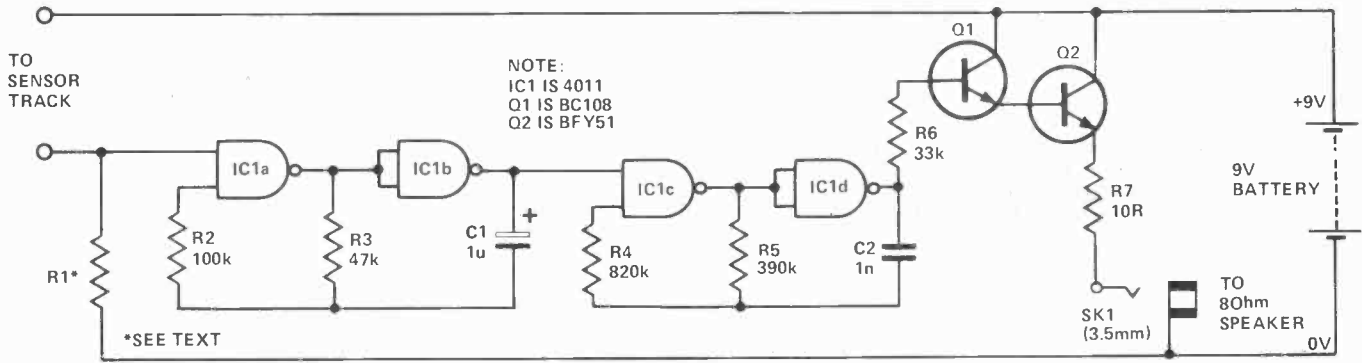


Fig. 1. Circuit diagram of Rain Alarm.

HOW IT WORKS

THE rain alarm is formed by two gated CMOS oscillators and an audio output stage.

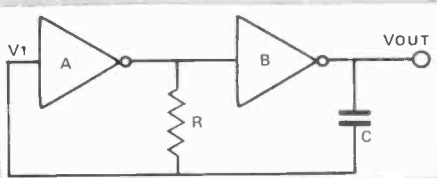The basic CMOS oscillator is shown in Fig. 2. Upon switch on, with C discharged, the output of inverter B will be low, the input to A low and its output high. Capacitor C will now commence to charge towards supply, the voltage level at A's output, via resistor R.




We can consider a CMOS gate to be a comparator that will change output state when the level of voltage at its input reaches a specified value, the transfer voltage (V_{tr}), usually about half supply. Thus as the voltage on C increases due to the charge current being supplied by R there will come a point when the voltage on the input of A will pass its transfer voltage and the output of B to go high.

At this point the charge on C corresponds to a voltage level of approximately half supply.

As the inverters A and B change states the end of C that was held at 0 volts is now at

supply and the end of C that was connected to supply via R is now returned to 0 volts via the same resistor.

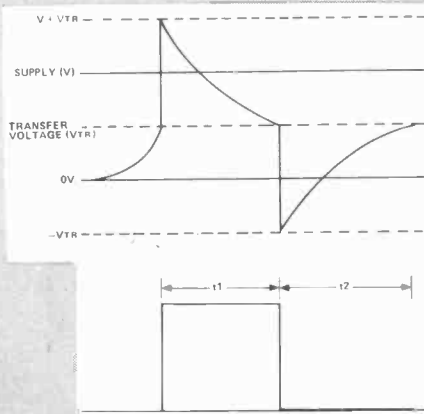These changes together with the charge stored on C mean that the potential across C is now supply plus the transfer voltage of gate A. This is shown in Fig. 3.



Capacitor C will now discharge via R until once again the transfer voltage of A is reached whereupon the outputs of the inverters will assume their original states.

The conditions are not quite the same as at

switch on because, as can be seen in Fig. 3, the Potential across C is now a negative value equal to A's transfer voltage.

From this point C charges via R again to repeat the cycle.

The output is shown in Fig. 3 where $t_1 = t_2 = 1.1 RC$ (the time taken for C to charge (discharge) via R to two-thirds of the maximum value of voltage across it).

In practice, due to the protection networks associated with modern CMOS devices, it is necessary to include a resistor in series with the input of A in order to ensure that the voltages across C are allowed to reach the values shown in Fig. X.

The final circuit diagram (Fig. 1) of the Rain Alarm shows that the inverters are in fact formed from the four NAND gates of a 4011 package. In each oscillator, while one gate is configured as a straightforward inverter, the other has one input that can act as a control input, oscillator action being inhibited if this input is held low.

The first oscillator (IC1a and IC1b) has this input tied low via a high value resistor (R1) that acts as a sensitivity control. Thus this oscillator will be disabled until the control input is taken high. Any moisture bridging the sensor track will so enable the output which is square wave at about 10 Hz. This in turn will gate on and off the 500 Hz oscillator formed by IC1c and IC1d.

This latter oscillator drives the loud-speaker via R6, the Darlington pair formed by Q1 and Q2 and resistor R7.

PARTS LIST

RESISTORS (all 1/4W 5%)

R1	See text
R2	100k
R3	47k
R4	820k
R5	390k
R6	33k
R7	10R

CAPACITORS


C1	1u0 16 V tantalum
C2	1n0 polyester

SEMICONDUCTORS

IC1	4011
Q1	BC 108
Q2	BFY 51


MISCELLANEOUS
PCB as pattern, 3.5mm jack socket, 8R speaker, battery.

Fig. 2. Overlay of the section of the Rain Alarm PCB that holds the components.

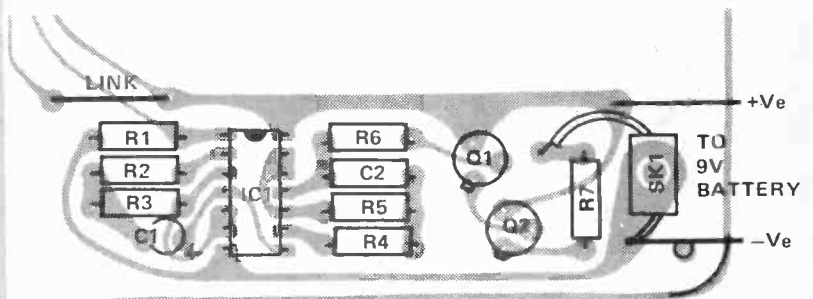

BUYLINES

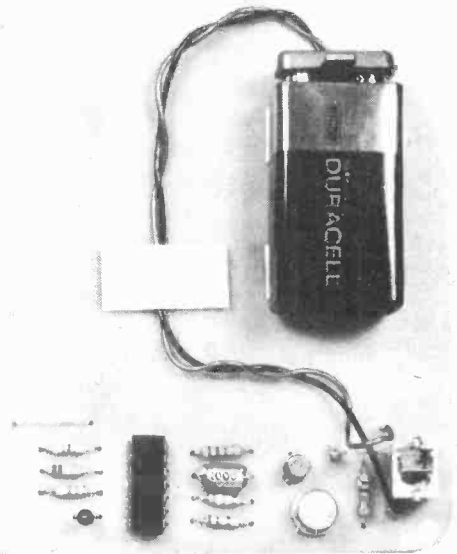The PCB will be available from any of the usual suppliers that advertise in ETI. C1 must be a low voltage tantalum but this component should be widely available. All of the other components are likewise obtainable from most electronic retailers.



WIREWRAP

PRECUT WIRE

Why buy wire on rolls?

PRECUT & STRIPPED WIRE IS:

- **Fast** - No more cutting & stripping by hand
- **Reliable** - Good, clean, uniform strip
- **Economical** - Cheaper than using bulk wire

Precut Wire

100 pcs of 3' at \$5.82 - 3¢/ft.
100 pcs of 6' at 1.06 - 2¢/ft.
Wire Kit 1 at \$6.95 - 2.1¢/ft.

Bulk Wire

50 ft. roll at \$1.99 - 4¢/ft.
100 ft. roll at 2.95 - 3¢/ft.

* 30 Kynar stripped 1" on each end. Lengths are overall Colors: Red, Blue, Green, Yellow, Black, Orange, White. Wire packaged in plastic bags. Add 25¢/length for tubes.

	100	500	1000	5000
2 1/2 in.	78	2.40	4.30/K	3.89/K
3 in.	82	2.50	4.71/K	4.22/K
3 1/2 in.	86	2.80	5.12/K	4.55/K
4 in.	90	3.00	5.52/K	4.88/K
4 1/2 in.	94	3.21	5.93/K	5.21/K
5 in.	98	3.42	6.34/K	5.52/K
5 1/2 in.	1.02	3.65	6.75/K	5.86/K
6 in.	1.06	3.85	7.16/K	6.19/K
6 1/2 in.	1.15	4.05	7.57/K	6.52/K
7 in.	1.20	4.25	7.98/K	6.85/K
7 1/2 in.	1.25	4.45	8.39/K	7.18/K
8 in.	1.29	4.65	8.80/K	7.53/K
8 1/2 in.	1.32	4.85	9.21/K	7.84/K
9 in.	1.36	5.05	9.62/K	8.17/K
9 1/2 in.	1.40	5.25	10.03/K	8.50/K
10 in.	1.45	5.51	10.44/K	8.83/K
Addl. in.	10	.41	.82/K	.66/K

WIRE KITS

# 1	\$6.95	# 2	\$19.95
250 3"	100 4 1/2"	250 2 1/2"	250 4 1/2"
250 3 1/2"	100 5"	500 3"	250 5"
100 4"	100 6"	500 3 1/2"	100 6 1/2"
		500 4"	1 250 ft. Roll Bulk

Choose One Color or Assortment

WIRE WRAP SOCKETS

	1-9	10-24	25-99	100-249	250-999	1K-5K
8 pin	.41	.38	.35	.31	.29	.27
14 pin	.42	.39	.36	.32	.29	.27
18 pin	.45	.43	.39	.35	.32	.30
18 pin	.63	.58	.54	.47	.44	.41
20 pin	.54	.78	.71	.63	.59	.54
22 pin	1.30	1.20	1.10	.95	.90	.84
24 pin	.91	.84	.78	.68	.64	.59
28 pin	1.25	1.15	1.08	.95	.89	.82
40 pin	1.65	1.55	1.42	1.25	1.15	1.09

Gold 3-level Closed Entry Sockets
End & Side Stackable All prices include gold
Tin sockets and 2-level sockets available

WIRE WRAP TOOLS



\$34.95

HOBBY WRAP

Model BW 630

With Free Wire Kit 1
(\$6.95 Value)

Batteries & Charger \$11.00
WSU 30 Hand Wrap-Unwrap Strip Tool 5.95
WSU 30M. for Modified Wrap 6.95
BT 30 Extra Bit 2.95

INTERCONNECT CABLES

Ribbon cable connectors for connecting boards to front panels, or board to board.


	SINGLE ENDED			DOUBLE ENDED		
	14 pin	16 pin	24 pin	14 pin	16 pin	24 pin
6"	1.24	1.34	2.05	2.24	2.45	3.37
12"	1.33	1.44	2.24	2.33	2.55	3.92
24"	1.52	1.65	2.63	2.52	2.76	4.31
48"	1.91	2.05	3.40	2.91	3.17	5.08

Ordering Information:

- Orders under \$25, add \$2
 - Include 10% for shipping
 - Payable by cashiers check in U.S. Funds
 - Visa and Master Charge Accepted
 - Send 2 Int'l. Postal Reply Coupon for Catalog
- Dealer Inquiries Invited

PAGE DIGITAL ELECTRONICS

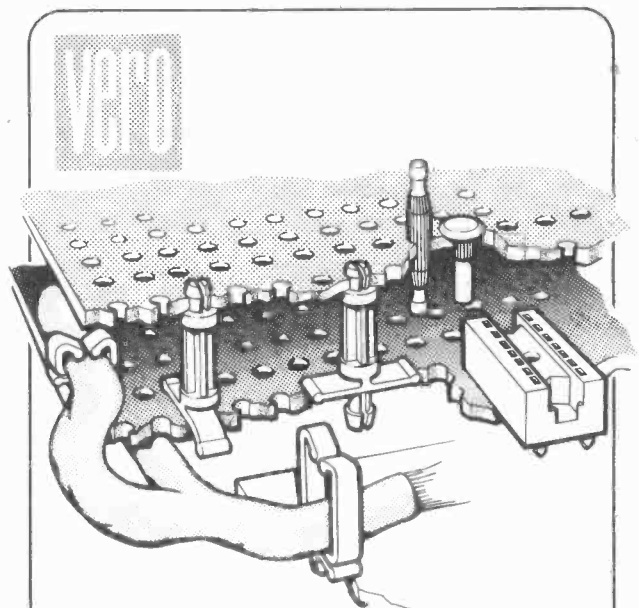135 E. Chestnut Street 4A
Monrovia, California 91016
Phone (213) 357-5005



Our new 1978 catalogue lists circuit board accessories for all your projects — DIP sockets, pins, standoffs, cable clips, hand tools. And we've got circuit boards, module systems, cases and boxes — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.

Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

MK14—the only low-cost keyboard-addressable microprocessor!



The new Science of Cambridge MK14 Standard Microprocessor kit

**Just
£39.95**
(+ £3.20 VAT, and p&p)

The MK14 National Semiconductor Scamp-based Microprocessor Kit gives you the power and performance of a professional keyboard-addressable unit—for less than half the normal price! For less than £44.00 you can have your own microprocessor. One with a specification that makes it perfect for the engineer who needs to keep up to date with digital systems, or for use in school science departments. It's ideal for hobbyists and amateur electronics enthusiasts, too.

But the MK14 isn't just a training aid. It's been designed for practical performance, so you can use it as a working component of, even the heart of, larger electronic systems and equipment.

MK14 Specification

- * Hexadecimal keyboard
- * 8-digit LED display
- * 512 x 8 Prom, containing monitor program and interface instructions
- * 256 bytes of RAM
- * 4MHz crystal
- * 5V Stabiliser
- * Single 6V power supply
- * Space available for extra RAM and RAM I/O

Free Manual

Every MK14 Microprocessor kit includes a free Operation Manual. It contains operational instructions and examples for training applications, and numerous programs including math routines, timing, general purpose sequencing, games, etc.

Designed for fast, easy assembly

Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 14 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings.

The MK14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the step-by-step illustrated instructions provided.

Tomorrow's technology—today!

"It is not unreasonable to assume that within the next five years...there will be hardly any companies engaged in electronics that are not using microprocessors in one area or another."

Phil Pittman, Wireless World, Nov. 1977

The low-cost computing power of the microprocessor is already being used to replace other forms of digital, analogue, electro-mechanical, even purely mechanical forms of control systems.

The Science of Cambridge MK14 Standard Microprocessor Kit allows you to learn more about this exciting and rapidly advancing area of technology. It allows you to use your own microprocessor in practical applications of your own design. And it allows you to do it at a fraction of the price you'd have to pay elsewhere.

Getting your MK14 Kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,
6 Kings Parade,
Cambridge,
Cambs., CB2 1SN.
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me an MK14 Standard Microprocessor Kit. I enclose cheque/money order/PO for £43.55 (£39.95 + 8% VAT and 40p p&p).

Name _____

Address (please print) _____

Allow 21 days for delivery.

Science of Cambridge

ETI

More power per £ from Stirling Sound

READY BUILT



OR BASIC MODULES

4 CHANNEL MIXER/CONTROL UNIT & POWER SUPPLY

By designing and manufacturing in our own Essex factory and selling direct to YOU the customer, we believe we have produced just about the best value ever in mixer/control equipment. You can buy the Disco 2 Unit assembled, tested and ready to connect up and use at once, or build your own unit using Stirling Sound Basic Modules. Either way you stand to save — and look at the advantages you get — sensibly arranged controls (on the built unit), proper DJ/PA facilities and RELIABILITY.

- INPUTS — Left deck, right deck, mic. and aux.
- INPUT IMPEDANCE — 47K ohms
- POWER SOURCE — 220-240V. A.C. Mains
- CONTROLS — Mains on-off, master volume, base ± 15 db, treble

± 15 db, L and R mixing, L and R motor switches, selector switch for P.F.L. (Pre-Fade Listening), headphone volume m/c, vol., aux. vol., LED indicators on main and decks on/off switches.

- HEADPHONE AMPLIFIER — Powerful 2 watts into 8 ohms, separate vol. control.
- TERMINATIONS — Five $\frac{1}{4}$ " jack sockets — 2 input, 2 output, headphones.
- SIZE — $23\frac{1}{4}$ " x $3\frac{3}{4}$ " x $2\frac{1}{2}$ " max. depth to rear (plus separate power unit) Panel in matt black with controls sensibly grouped for easy handling

Suggested Stirling Sound power amps with heat sinks and power supply units — 140PH £18.160PH £22.1100PH £26.75.

Built, tested and guaranteed.

£39.95

POST FREE in U.K. and INC V.A.T.

Kit of basic modules less power pack, 5 jack sockets, and 3 mains switches, but with front panel

£21.00

POST FREE in U.K. and INC V.A.T.

READY BUILT OR D.I.Y. MODULES

READY BUILT

(Prices inc. V.A.T. but NOT cost of carriage)

SDUND-LIGHT UNITS

- SSTL3/250B — 3 channels, 250w each **£22.95**
- SSTL3/1000B — 3 channels, 1000w each **£25.95**

INTEGRATED POWER AMPS

- In strongly made metal cases, complete
- POWER AMP 40 — 40w. r.m.s./4 ohms, 2 ch. mixer **£43.00**

POWER AMP 60 — 60w. r.m.s./4 ohms, 2 ch. mixer **£48.00**

POWER AMP 100 — 100w. r.m.s./4 ohms, 4 ch. mixer **£85.00**

100w. SLAVE AMP **£50.00**

LOUDSPEAKERS

Disco 25 — 25w. r.m.s. in cabinet, 20' lead **£23.95**

Disco 50 — 50w. r.m.s. in cabinet, 20' lead **£39.95**

Disco 100 — 100w. r.m.s. in cabinet, 20' lead **£55.95**

Ampower 50 — 50w. amp & speaker in cabinet **£60.00**

Ampower 100 — 100w. amp & speaker in cabinet **£80.00**

Complete Disco with Disco 2 console and

Ampower 50 **£155.00**

ditto with Disco 2 console & two Ampower 50s **£210.00**

ditto with Disco 2 console & one Ampower 100 **£175.00**

ditto with Disco 2 console & two Ampower 100s **£250.00**

Carriage in U.K. please add for SSTL Unit £1; for Power Amps 40 & 60 £1.50; for Power Amp 100 & 100w. Slave Amp or Disco 25 or 50 £2.00 Ampower 50 and 100, Disco Console or Disco 100 £5.00. Complete Discos, £10.

EVERYTHING RIGOROUSLY TESTED AND GUARANTEED

BASIC MODULES

For constructors wishing to build systems to their own requirements. As their description implies, these

modules will require control knobs, pots in some cases, etc. Each module is supplied assembled on its own PCB

SSB4 Phase splitter (for two SS 105s) **£2.75**

SS104/2 Two channel mixer stage **£3.75**

SS104/4 Four channel mixer stage **£7.00**

SS.DTM

Output control stage Master vol. 30dB variation on both treble and bass; 3mV in for 2V out. 18V working voltage

£6.75

SSTL3/250 Sound/light, 3 ch., 250w. ea **£9.25**

SSTL3/1000 Sound/light, 3 ch., 1000w. ea **£11.50**

POWER AMPS.

Ready assembled on P.C.B.s, tested and guaranteed. Easy to connect. With instructions. Output ratings ± 1 dB.

- SS.103 1 C. amp. 3 watts R.M.S. using 20V/8 Ω or 14V/4 Ω . Input 100mV **£2.85**
- SS.103-3 Stereo version of above, 2 I.C.s. **£5.00**
- SS.105 5 watts R.M.S. into 3 Ω using 13.5V. Sensitivity — 30mV. THD — 0.3%. $3\frac{1}{4}$ " x 2 " x 1 " **£3.95**
- SS.110 10 watts R.M.S. into 4 Ω using 24V. Sensitivity — 60mV. THD — 0.3%. $3\frac{1}{4}$ " x 2 " x 1 " **£4.65**
- SS.120 20 watts R.M.S. into 4 Ω using 34V. Sensitivity — 80mV. THD — 0.3%. $3\frac{1}{4}$ " x 2 " x 1 " **£5.15**
- SS.125 25 watts R.M.S. into 8 Ω using 50V. Sensitivity — 140mV. Distortion — Less than 0.05% into 8 Ω S/N better than 70dB **£7.25**
- SS.140 40 watts R.M.S. into 4 Ω using 45V. Sensitivity — 300mV. Distortion typically 0.1%. 5 " x $3\frac{1}{2}$ " x $1\frac{1}{4}$ " **£6.50**
- SS.160 64 watts R.M.S. into 4 Ω using 50V. Sensitivity — 350mV. Distortion typically 0.1%. 5 " x $3\frac{1}{4}$ " x $1\frac{1}{4}$ " **£8.50**
- SS.1100 100 watts R.M.S. into 4 Ω using 70V/2A. Input sensitivity — 500mV. Distortion at half-power, typically 0.1%. 5 " x $3\frac{1}{2}$ " x $1\frac{1}{4}$ " **£10.50**
- HS.160 Multi-finned heatsink for SS.140 or SS.160 **75p**
- HS.1100 Ditto for SS.1100 **£1.50**

POWER SUPPLIES

Every Stirling Sound Power Unit is tested and guaranteed under working conditions before despatch. All units except SS.312 include a stabilised low voltage take-off point (13-15V) for pre-amp, tone control, radio tuner, etc. Outputs quoted are minimal unloaded ratings.

SS.312 12V/1A **£6.60**

SS.318 18V/1A **£6.95**

SS.324 24V/1A **£7.65**

SS.334 34V/2A **£8.75**

SS.345 45V/2A **£10.75**

SS.350 50V/2A **£11.75**

SS.360 60V/2A **£12.75**

SS.370 70V/2A **£14.75**

SS.310/50 Stabilised power supply unit with variable output from 10V to 50V/2A. Short circuit protected **£17.75**

SS.300 Power stabilising unit variable from 10 to 50V/BA for adding to unstabilised supply units **£5.50**

CONTROL/PRE-AMPS.

UNIT ONE

Combined stereo pre-amp & active tone control unit 50mV in for 200mV out 10 16V operation Bass ± 15 dB; Treble ± 15 dB; Balance control; Volume control. Ceramic P.U., radio or tape inputs. WITH FREE CONTROL PANEL FASCIA **£9.00**

UNIT TWO

Controls as UNIT ONE but for magnetic cartridge input. 5mV in for 200mV out. R.I.A.A. corrected. WITH FREE CONTROL PANEL FASCIA **£12.43**

CONTROL PANEL FASCIA

For above **50p**

SS.100

Basic active stereo tone control module to provide ± 15 dB on bass at 30Hz and on treble at 10KHz **£3.00**

SS.101

Stereo pre-amp suitable for ceramics, tape, radio, etc **£2.75**

SS.102

Stereo pre-amp for mag. pick-ups **£4.45**

STIRLING SOUND PRODUCTS ARE MADE IN OUR OWN ESSEX FACTORY AND SOLD DIRECT TO YOU, THE CUSTOMER. SEND NOW FOR FREE CATALOGUE SHEETS.

WHEN ORDERING. All goods sent post free in U.K. (except certain heavy ready built items) and ALL INCLUDE V.A.T. Prices subject to alteration without notice. Credit facilities available. E. & O.E. S.A.E. with enquiries, please. ACCESS OR BARCLAYCARD — JUST LET US KNOW YOUR No.

MAIL ORDERS

Dept. ET13, 37 VANGUARD WAY, SHOE BURNNESS, ESSEX. Telephone: (03708) 5543.

SHOP & SHOWROOMS

220-224 West Road, Westcliff-on-Sea, Telephone: Southend (0702) 351048.

Stirling Sound

To STIRLING SOUND, 37 VANGUARD WAY, SHOE BURNNESS, ESSEX.

Please send (or as list attached) for which I enclose £


NAME

ADDRESS

ET13

PROJECT CASINGS SURVEY

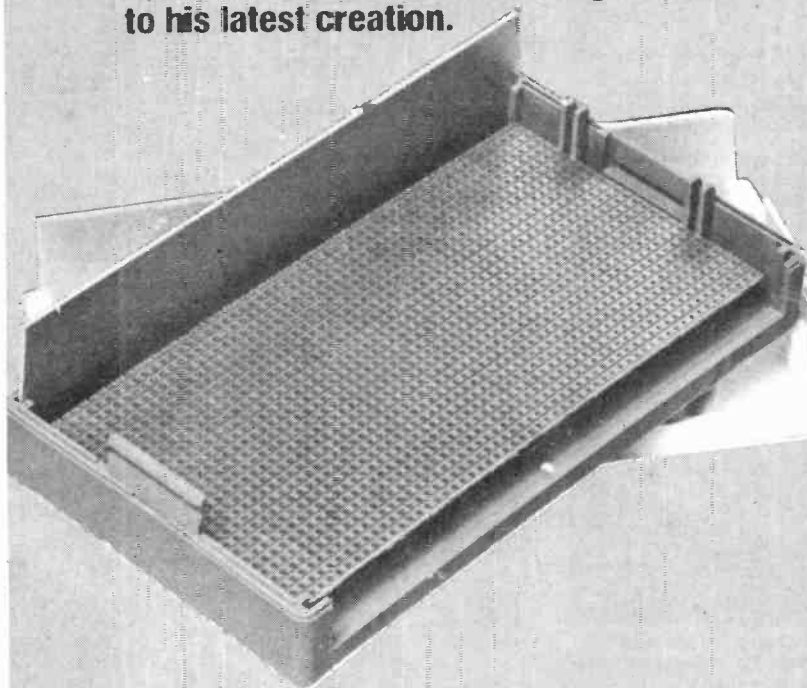Built a project recently and don't know where to put it? William King has been looking at some of the vast range of project cases available to the amateur constructor to enable him to add the finishing touches to his latest creation.



UNLESS YOU ONLY go in for the assembly of commercial electronic kits which come complete with a ready drilled case and all the nuts, bolts and washers required to produce a project with an almost professional finish, you may never have realised that amateur "electronics" is more than just soldering neatly and knowing the difference between a pretty "C280" series capacitor and a liquorice allsort, but that a little "metal bashing" is also required.

Casing The Joints

Electronics can often be a very uninteresting subject and a PCB full of the latest chips is not going to be as interesting to a friend (with little or no electronic knowledge) as would be a (say) simple electronic dice built in a nice neat plastic box. Although some people seem to believe that so long as their latest high power electronic rat exterminator works it doesn't matter if it is housed in a tobacco tin held together with insulating tape and chewing gum. Needless to say this is not the attitude we expect from ETI readers.

A little extra money spent on a few basic tools (small drill and assorted bits, files, nuts, bolts, washers) is really essential (making holes in plastic boxes with your soldering iron is not a good idea). This coupled with a little time spent selecting a case, can turn a mediocre run-of-the-mill project into an impressive piece of electronic sophistication that you won't feel embarrassed to have lying around when the friends/relatives drop in unexpectedly.

Although there are many different cases in a multitude of shapes and sizes, the daunting prospect of choosing a suitable case is eased by the parameters governed by the project itself — is screening required? Will it take a PP9 battery, will it fit in your pocket?


Once a box has been chosen the work begins. The first essential is a layout of all the controls, sockets cable exits and any other holes which need to be made. Careful attention should be made to details such as not mounting audio switches near mains switches to avoid hum pick up.

Once satisfied that the panel has been designed to be both aesthetic and functional, drilling can begin. This successfully completed leaves only one more stage before the project can be fitted into its housing, this is inscribing legends for the controls.


This can be done in a variety of ways (typed labels glued on, dymo type labelling strips . . .) but the method which gives the most professional appearance is rub down lettering transfers (a set of transfers suitable for panel marking, including potentiometer scales (rotary and slider) is available from ETI — see the advert in this issue.

If using transfers it is best to either use a clear varnish spray or self adhesive plastic film to prevent the lettering from rubbing off with use.

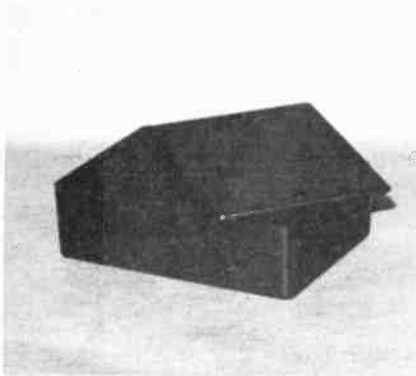
All that remains then is to secure the project in its case, stand back and admire . . .



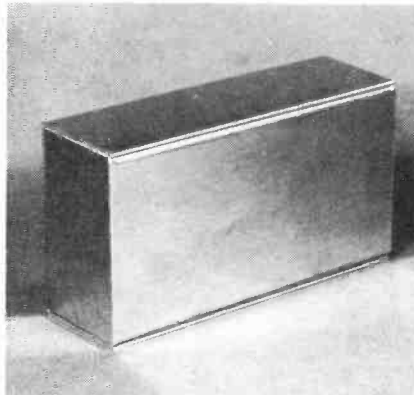
All-plastic 'Gemini' box and lid in black, grey or white. 110x70x30 at 71p. Supplier B.



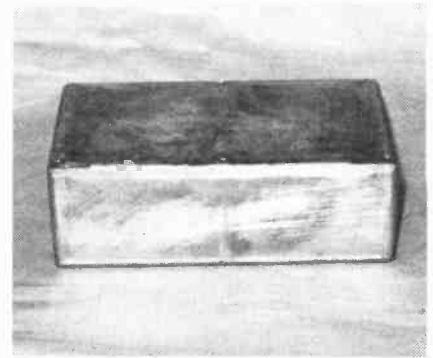
Aluminium plate box in two parts. 6 sizes available. Supplier B.



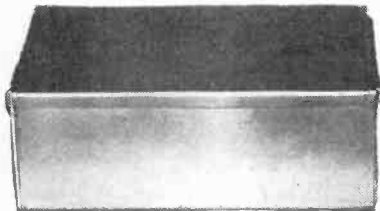
'Eddystone' die-cast aluminium boxes in 1.5mm thick walls. 8 sizes available from 89x38x32 to 222x146x108. Prices from £1.13. Suppliers B & C.



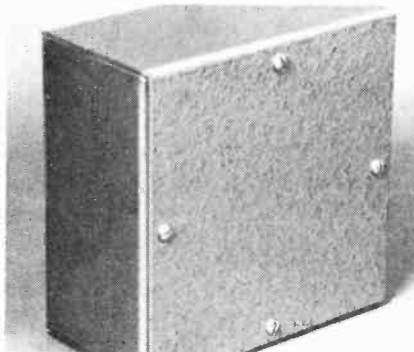
Folded aluminium boxes with lid and screws. 20 sizes from 76x51x25 to 304x203x76. Prices from 49p to £2.27. Supplier B



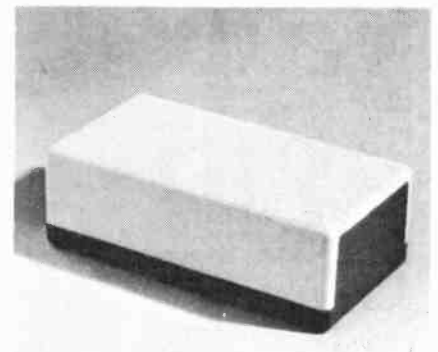
16 SWG aluminium, silver hammer finish cubical boxes. Type N in 3 sizes from 102x102x51 to 203x152x51. Prices from £1.90. Supplier A.



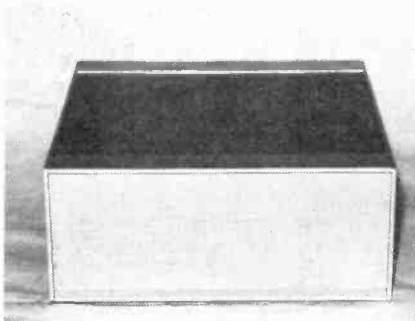
65 series plastic two-piece rectangular cases in white/grey. Sizes from 100x50x25 at £1.80. Supplier G.



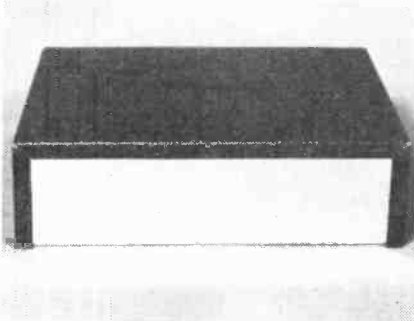
'Classic' instrument case. Satin-finished anodised aluminium with textured vinyl-coated steel top & bottom plates. 6 sizes from 216x127x63. Price from £7.94. Supplier B.



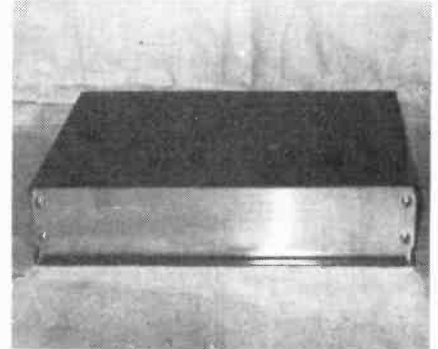
Aluminium two part construction case (type PJ) with front and rear vinyl covered. 7 sizes available from 127x63x57 to 305x158x133. Prices from 65p. Supplier B.



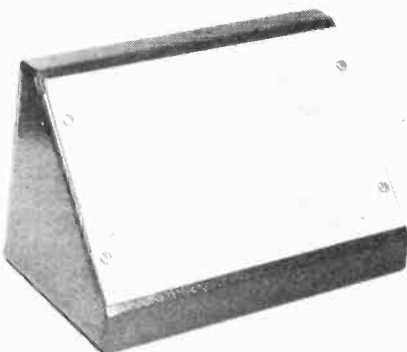'Opal range', steel cases with aluminium panels, in 3 sizes from 65x58x210 to 65x160x210 with price from £9.67. Supplier B.




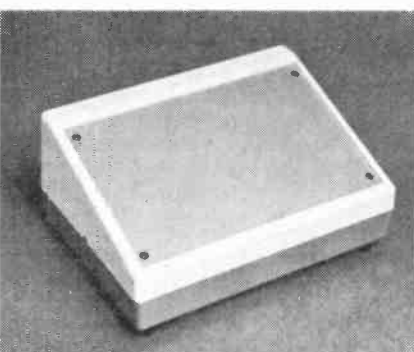Steel cases with 45° sloping aluminium panels available in 3 sizes, from 150x95x95 with 150x100 front panel. Price from £2.10. Supplier E.



Two colour plastic case with sloping aluminium panel with mounting points for EUROCARD board. Size 171x121x75. Type 75-1798K at £4.53. Supplier G.

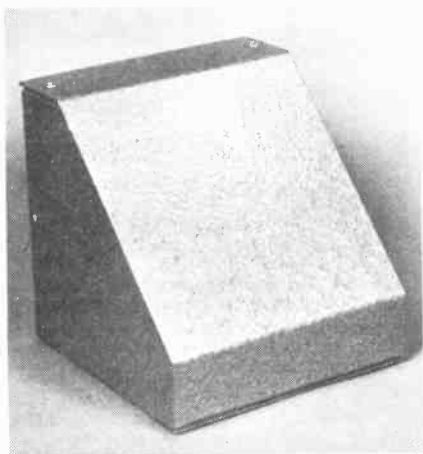
A key to the supplier codes is printed at the end. All dimensions are in millimetres. Prices include VAT but not postage and packing and should be used as a guide only.




16 SWG aluminium, silver hammer finish. 3-piece construction. Type U case in 8 sizes from 76x76x76 to 381x229x229 from £1.50. Supplier A.



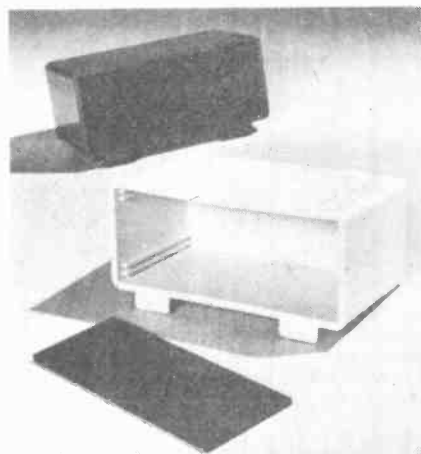
Flip-top polypropylene boxes with aluminium alloy panel in black or yellow. Two sizes 130x75x34 and 196x127x51 at approx £2.05 and £2.70. Supplier G.



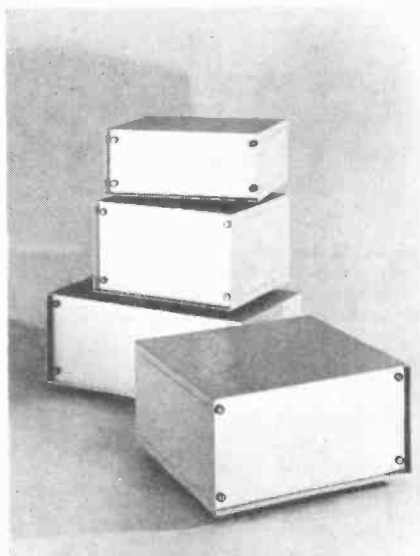
"Time box" for digital clocks in antistatic ABS. Slots for two PCBs available in white, red, orange or blue. Price £2.22. Supplier C.



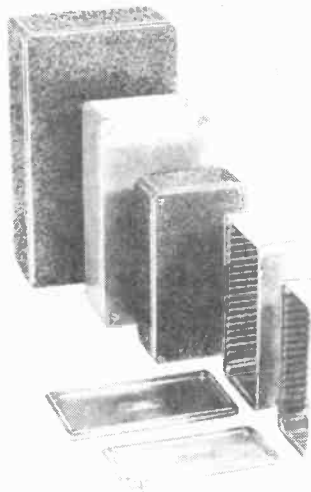
Veropak 49 series cases made of heavy gauge PVC clad steel in 5 sizes from 277 x 113 x 219 with prices from £9.70. Supplier G.



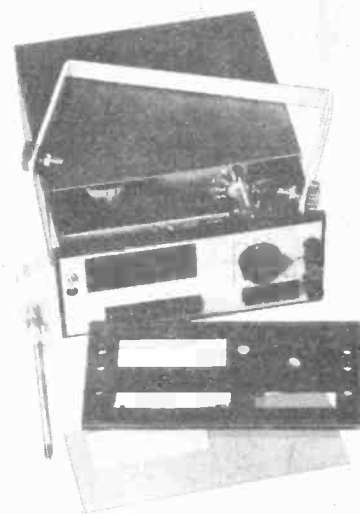5000 series boxes in die-cast aluminium in 5 sizes with slotted guides for 1.5mm PCBs. Sizes from 100x50x25 with natural or hammertone. Price from £1.05.



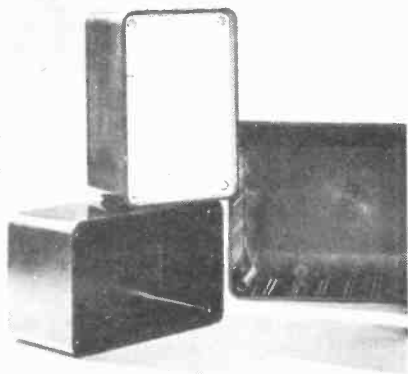
Amatek PDS instrument case system in PVC-coated aluminium with ready drilled front panel. Accepts push button switches, digital displays, meters. Size 178x80x152. Price £9.18. Supplier D.




Miniature "Minos" cases in black or white ABS with aluminium panel. Guides for PCBs. 4 sizes from 65 x 100 x 50 to 130 x 200 x 54 at prices from 52p. Supplier C.



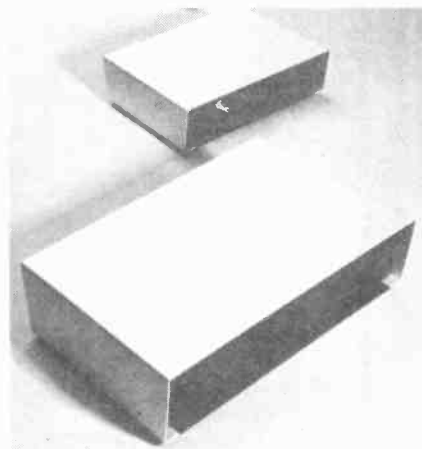
Two vacuum formed cases in black ABS with aluminium panel supplied, for mounting keyboards. Sizes 220 x 276 (about £8) and 550 x 340 (price TBA). Supplier G.



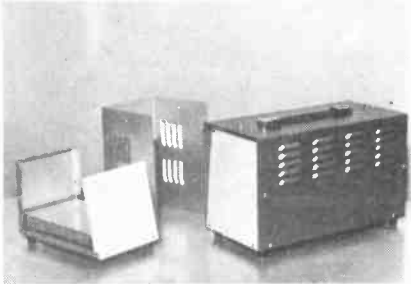
"G range" cases with sloping visor, in 3 sizes with slide on cover. 3 sizes from 44x134x123 from £4.86. Supplier G.



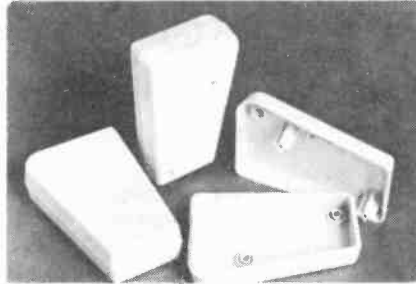Hammered finished 20 SWG zinc-coated mild steel cases in two colours and 4 sizes, from 101x101x155 to 177x152x307. Supplier E.



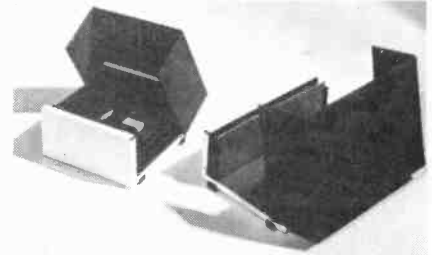
Hand held plastic control boxes approx. 61x94x27 type 75-1799E, in white high impact ABS. Price approx 70p. Supplier G.




Samos miniature cases in 7 sizes. Two part construction, holds up to 4 PCBs with special PCB feet. Sizes from 50x50x100 to 75x200x125. Prices from £1.47. Supplier C.



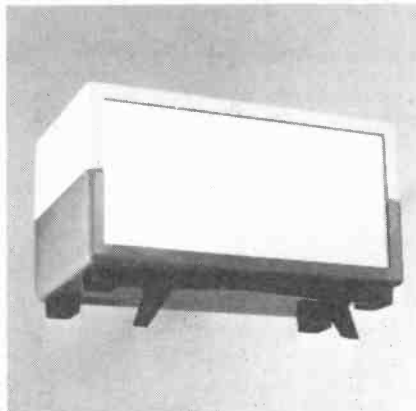
Alfa range plastic cases in 3 sizes. Aluminium panel front & rear. Sizes from 173x130x35 to 173x130x70 with prices from £3.46. Supplier B.



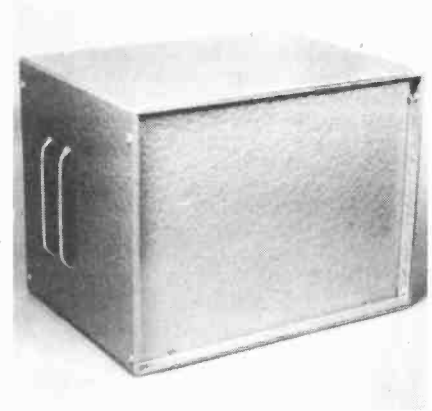
A range of cases in two colours. Plastic with aluminium front & rear panels with provision for tilt leg. Sizes from 85x40x154 at £2.76. Supplier G.



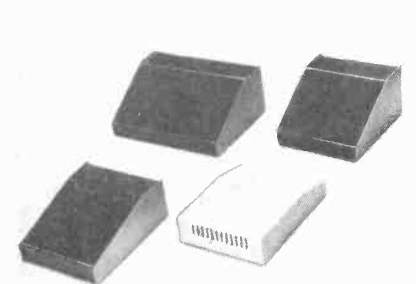
16 SWG aluminium case, silver hammer finish (type W). 4 sizes from 203x152x152 to 381x228x203 with prices from £4.55. Supplier A.



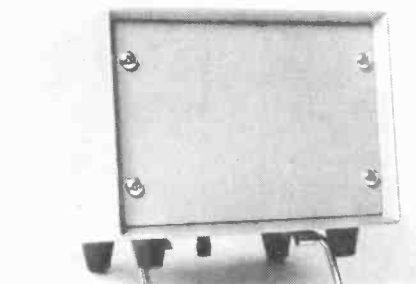
7000 series consoles of all-metal or ABS/metal construction with sizes from 102x28x140 to 356x33x287. Prices from £10.18. Supplier F.



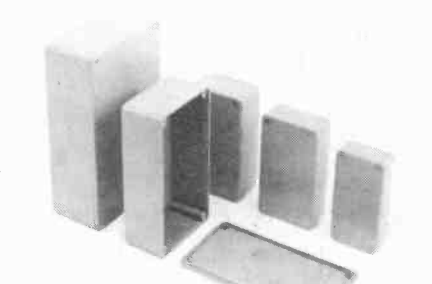
Minicases in mild zinc coated steel sheets with hammertone finish. Sizes from 165x114x114. Supplier E.



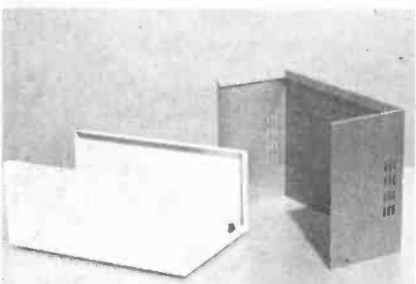
2000 range of boxes in ABS moulded in four colours with slotted guides for 1.5mm PCBs. 5 sizes from 100x50x25 from £1.03. Supplier F.



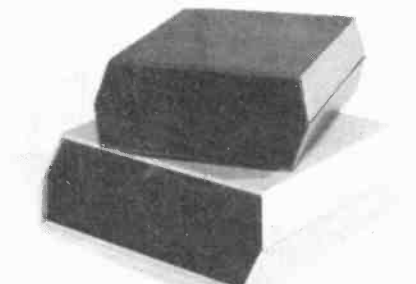Zinc-coated mild steel case with vents in blue/light grey. Available in 8 sizes from 127x69x101 with price from £2.64. Supplier E.



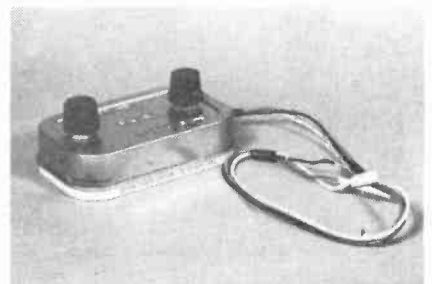"Nuova" enclosures in anti-static abs. Transparent red front panel is inclined at 70°. Contains pillars for PCBs. Four colours and three sizes available, from 120x50x90 at £1.72. Supplier C.



One size boxes in tin-plated steel popular with some constructors. Boxes come with free contents which should be burnt before use. Price varies.

SUPPLIER CODES

A

H. L. Smith & Co Ltd
278-289 Edgware Road
London W2 1BE

D

Amatek
22 Bardsley Lane
Greenwich, London SE10

G

Vero Electronics Ltd
Industrial Estate
Chandlers Ford
Hampshire SO5 3ZR

B

Watford Electronics
33 Cardiff Road
Watford, Herts.

E

Olson Electronics Ltd
5-7 Long Street,
London E2 8HJ


C

West Hyde Developments
Unit 9, Park Street Industrial
Estate
Aylesbury, Bucks.

F

Boss Industrial Mouldings
2 Herne Hill Road
London SE24 0AU

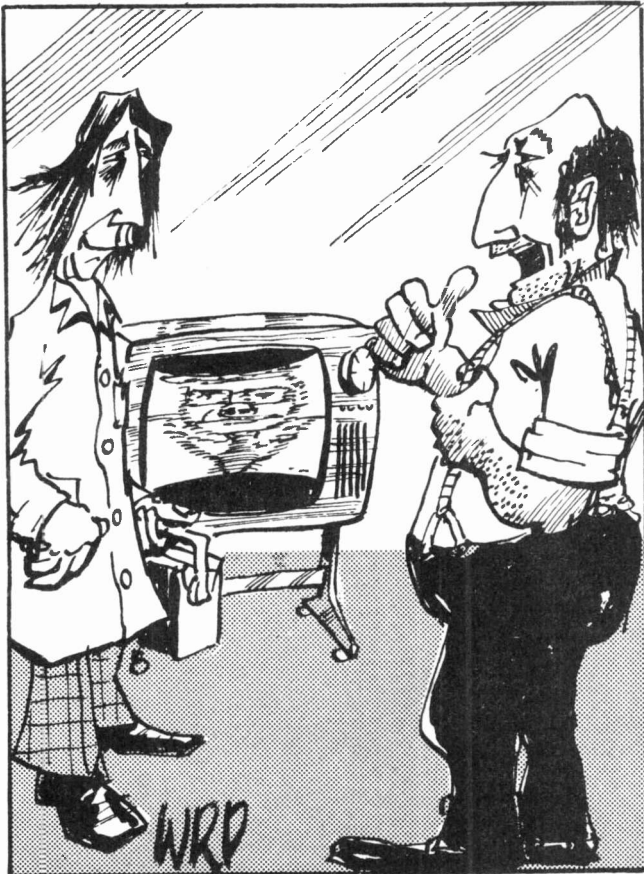We would like to thank the suppliers for providing photographs and details of their products, and in particular Watford Electronics who rendered us valuable assistance during the compilation of this article.



If it gets much worse the wife'll begin to notice!



That young devil Jenkins is on about lowering the modulus of elasticity of air . . . is he sending me up again Stan?!!

"STOP PRESS" NEW LOW PRICES

CHROMASONIC electronics

56 Fortis Green Road
Muswell Hill London N10 3HN
Telephone 01-883 3705

TRANSFORMERS 6-0-6V 100mA 1.00* 0-0-9V 75mA 1.00* 12-0-12V 100mA 1.15* 0-8-17V 1A 2.15* 0-8-17V 2A 3.25* 0-8-17V 4A 4.35* 20-0-20V+ 1A 3.25* 24-0-24V 500mA 2.15* 0-19-25-33-40-50V+ 1A 3.25* 0-19-25-33-40-50V+ 1A 3.85* 0-19-25-33-40-50V+ 2A 5.45* 0-12-15-20-24-30V+ 1A 3.25* 0-12-15-20-24-30V+ 2A 4.35* Please add an extra 50p to items marked +			DIODES BA114 15p BY105 25p OA91 10p BA115 25p BY126 12p OA200 10p BA145 20p BY127 12p OA202 10p BA148 20p BY133 25p IN914 5p BA155 15p BY182 1.85 IN4003 7p BA156 15p BY250 30p IN4007 8p BAX16 12p OA47 12p IN4148 5p BB105B 50p OA79 12p IN5401 15p BY103 25p OA90 10p IN5407 25p			LIGHT EMITTING DIODES 9-125" (inc. clip) 1+ 10+ 100+ TIL209 Red 15p 13p 11p* TIL212 Yellow(H.B.) 27p 22p 17p* TIL216 Red(H.B.) 27p 22p 17p* TIL232 Green(H.B.) 27p 22p 17p* 8-2" (inc. Clip) TIL220 Red 15p 13p 11p* TIL224 Yellow(H.B.) 30p 26p 20p* TIL228 Red(H.B.) 30p 26p 20p* TIL234 Green(H.B.) 30p 26p 20p* (H.B.)—High Brightness.			POLYESTER CAPACITORS Mullard C281 Series 250Vw 0-01µf 5p 0-088µf 8p 0-47µf 12p 0-015µf 5p 0-10µf 8p 0-68µf 17p 0-022µf 5p 0-15µf 8p 1-0µf 25p 0-033µf 5p 0-22µf 8p 1-5µf 34p 0-047µf 5p 0-33µf 8p 2-2µf 40p Mullard C281 Series 400Vw 0-01µf 10p 0-088µf 15p 0-47µf 33p 0-015µf 10p 0-10µf 15p 0-68µf 35p 0-022µf 10p 0-15µf 18p 0-033µf 12p 0-22µf 25p 0-047µf 15p 0-33µf 30p		
HEATSINKS TO 92 7p* TO 5 (5F) 8p* TV 2 25p* TO 18-(18F) 11p* TV 3 25p* U1 (TBA900) 10p* TV 4 25p* U2 (TBA810AS) 21p* TV 5 24p* U3 (TDA2020) 52p* TV 16 33p* AY 14 51p* CH 106 31p* 1-18 E-17 94p* 3-15 E-18 1.49p* 3-15 E-19 1.68p* (For 1xTDA2020) (For 2xTDA2020) Transistor Covers TO66 and TO3 12p*			ZENERS BZY88 400mw 2-7v-33v 10p 1ZS 1w 3.6v-100v 20p			I.C. SOCKETS 8 pin 10p* 16 pin 14p* 28 pin 30p* 14 pin 12p* 24 pin 26p* 40 pin 44p* I.C. pins 100 54p* 1,000 £3.78*			CERAMIC CAPACITORS Mullard 632 Series 1-8pf 10pf 56pf 390pf 1500pf 2-2pf 12pf 82pf 470pf 1800pf 3-7pf 15pf 82pf 560pf 2200pf 2-7pf 18pf 100pf 680pf 2700pf 3-9pf 22pf 120pf 820pf 3300pf 4-7pf 27pf 150pf 1000pf 3900pf 5-8pf 33pf 180pf 1200pf 4700pf 6-8pf 39pf 220pf 1500pf 5600pf 8-2pf 47pf 270pf 2000pf 7500pf 330pf 8p each Mullard 623 Series 0-01uf 0-022uf		
PLUGS AND SOCKETS DIN Connectors Pins Plugs Sockets Line Couplers 2 14p 10p 18p 3 14p 10p 18p 4 14p 10p 18p 5 (180) 14p 10p 18p 5 (240) 14p 10p 18p 6 14p 10p 18p 7 14p 10p 18p			T.T.L. Just a selection. Send for full list 7400 10p* 7430 16p* 7474 27p* 74121 27p* 7401 16p* 7441 30p* 7475 40p* 74123 49p* 7402 16p* 7442 32p* 7476 30p* 74141 65p* 7403 16p* 7443 30p* 7477 30p* 74145 82p* 7404 17p* 7447 50p* 7478 27p* 74151 49p* 7408 19p* 7448 65p* 7479 2-32* 74154 85p* 7410 16p* 7451 16p* 7490 30p* 74174 72p* 7413 27p* 7470 27p* 7492 41p* 74192 86p* 7420 16p* 7472 22p* 7493 41p* 74193 86p* 7427 28p* 7473 27p* 74107 27p* 74196 79p*			C. Mos 4000 18p* 4014 1-00* 4024 70p* 4051 86p* 4001 18p* 4015 97p* 4025 19p* 4052 86p* 4002 18p* 4016 53p* 4026 1-78* 4060 1-16* 4006 1-08* 4017 97p* 4027 30p* 4068 22p* 4007 19p* 4018 97p* 4028 87p* 4070 22p* 4009 82p* 4019 98p* 4029 1-18* 4071 22p* 4010 82p* 4020 1-08* 4040 1-88* 4081 22p* 4011 18p* 4021 97p* 4042 83p* 4082 22p* 4012 21p* 4022 88p* 4049 58p* 4510 1-24* 4013 58p* 4023 19p* 4050 33p* 4511 1-54*			POLYSTYRENE CAPACITORS 10pf 100pf 1000pf 10,000pf (0-01uf) 12pf 120pf 1200pf 15pf 150pf 1500pf 22pf 220pf 2200pf 33pf 330pf 3300pf 47pf 470pf 4700pf 8p each 56pf 560pf 5600pf 82pf 820pf 8200pf		
JACK CONNECTORS Type Plastic Plugs Chrome Sockets 2.5mm 15p 25p 12p 3.5mm 15p 25p 12p Mono — 30p 20p Stereo — 37p			LINEAR INTEGRATED CIRCUITS uA703 (TO99) £1-00 LM370N £2-75 SL415A £2-47 uA709 (8 pin DIL) 41p LM371N £2-75 SL440A £2-38* uA709 (14 pin DIL) 41p LM372N £1-75 SN75491N 85p* uA709 (TO99) 50p LM373N £2-99 SN75492N £1-15* uA710 (8 pin DIL) 50p LM373T £1-95 SN76001N £1-40 uA710 (14 pin DIL) 55p LM3800-8 £1-06 SN76003N £2-45 uA710 (TO99) 80p LM380N 90p SN76013N £1-80 uA711 (14 pin DIL) 80p LM381N £1-75 SN76023N £1-80 uA711 (TO99) 98p LM382N £1-35 SN76033N £2-45 uA741 (8 pin DIL) 25p LM3900N 65p SN76544N £1-55 uA741 (14 pin DIL) 42p LM3905N £1-50 SN76532N £1-55 uA741 (TO99) 45p LM3909N 70p* SN76552N 65p uA747 (14 pin DIL) 90p MC1303/LM1303N £1-10 uA748 (8 pin DIL) 42p MC1310P £1-80 uA748 (14 pin DIL) 60p MC1312P £2-15 uA748 (TO99) 65p MC1314P £3-50 uA753 (8 pin DIL) £1-95 MC1315P £6-10 AY-1-0212 £8-50 MC1327P/TDA1327 £2-50 AY-1-5051 £1-85 MC1330P £1-50 AY-5-1224A £3-99* MC1335P £1-00 AY-5-3507 £3-99* MC1351P £1-00 AY-5-4007 £7-99* MC1352P/TDA1352 £1-20 CA3045 80p TD A1352 £1-20 CA3046 80p MC1357P/TDA1357 £1-20 CA3053 80p AC128 11p £1-78 CA3075 £2-90 MC1375P £1-50 CA3080 80p MC1455CG £2-50 CA3081 £1-50 MC1495L £4-90 CA3082 £1-50 MC3302P £1-85 CA3089/TDA1200 £2-30 MC36030A £1-90 CA3090Q £4-25 NE540L £2-40 CA3123E/LM1820 £1-50 NE546 £2-15 CA3097E £1-75 NE555 35p* CA3130S 90p* NE556 90p* CA3140S 90p NE560 90p* CA3160S £1-60 NE561 £4-40 CA3600E £1-75 NE562 £7-40 LM301A/N (8 pin) 40p NE563 £4-40 LM301AT (TO99) 50p NE565 £1-85 LM308N (8 pin) 90p NE566 £1-05 LM308T (TO99) £1-40 NE567 £1-85 LM339N £1-00 ZLA414A £1-90			SILVER MICA CAPACITORS 2-2pf 10p 88pf 10p 500pf 15p 3-3pf 10p 75pf 10p 560pf 15p 5pf 10p 32pf 10p 1800pf 15p 10pf 10p 100pf 10p 820pf 15p 18pf 10p 120pf 10p 1000pf 20p 20pf 10p 150pf 10p 1500pf 20p 22pf 10p 180pf 10p 1800pf 20p 25pf 10p 200pf 10p 2200pf 20p 27pf 10p 220pf 10p 2700pf 30p 30pf 10p 250pf 10p 3600pf 30p 33pf 10p 270pf 10p 4700pf 30p 39pf 10p 300pf 15p 5000pf 30p 47pf 10p 330pf 15p 6800pf 40p 50pf 10p 390pf 15p 8200pf 40p 56pf 10p 470pf 15p 0-01µf 40p					
PHONO Connectors Plugs Sockets Plastic Moulded 10p 1 way 8p 3 way 12p Chrome Screened 15p 2 way 12p 4 way 14p			CO-AXIAL Connectors Plug Surface Socket Coupler 18p 16p 43p			SWITCHES D.P.D.T. toggle .50p* S.P.S.T. toggle .30p* D.P.D.T. Slide .18p* D.P.D.T. Slide Miniature .15p* Push to Make Miniature .18p*			MYLAR CAPACITORS 1000pf 8p 0-04µf 8p 2000pf 5p 0-047µf 8p 2200pf 5p 0-05µf 8p 4700pf 5p 0-088µf 8p 5000pf 5p 0-1µf 10p 0-01µf 7p 0-2µf 10p 0-02µf 8p 0-22µf 15p 0-022µf 7p -0-03µf 8p		
RESISTORS Type Range 1/2 watt 5% Carbon film E12 Series 10R-1M 2p each 1/2 watt 5% Carbon film E24 Series 3-3R-10M 2p ea. 1 watt 5% Carbon film E12 Series 10R-1M 5p each			POTENTIOMETERS 5K 250K Lin and Log less Switch (inc. IK Lin) .27p 10K 500K Lin and Log Dual less Switch .75p 25K 1M Lin and Log with Switch .60p 50K 2M 10K, 100K, 500K, 1M Dual log with Switch .75p 100K 10K Log + 10K Antidiv less Switch .75p			TANTALUM BEAD CAPACITORS 0-1µf 35v 15p 10µf 25v 20p 0-22µf 35v 15p 15µf 35v 22p 0-47µf 35v 15p 22µf 16v 22p 1-0µf 35v 15p 47µf 16v 25p 2-2µf 35v 15p 100µf 3v 22p 4-7µf 35v 15p 0.01µf 6.3v 35p 10µf 16v 17p 100µf 0v 24p					
PRESETS 100R 5K 250K -1 watt 250R 10K 500K Horizontal 500R 25K 1M 1K 50K 2-5M Vertical 2-5K 100K 5M 7p each			REGULATORS 723 Variable 45p* 78L05AWC 5V 85p* 78L12AWC 12V 85p* 78L15AWC 15V 85p* 7805KC 5V 2-17* 7812KC 12V 2-17* 7815KC 15V 2-17* 7805UC 5V 1-25* 7812UC 12V 1-25* 7815UC 15V 1-25* 7818UC 18V 1-25* 7824UC 24V 1-25* LM005T1 5V 1-50* LM005T2 5V 1-50* LM037T1 12V 1-50* LM037T2 12V 1-50* LM037T3 12V 1-50* LM037T4 12V 1-50* LM037T100 12V 1-50*			TRANSISTORS AC126 20p* BC558 15p MPF104 40p 2N1302 45p* AC127 20p BC559 15p MPF105 40p 2N1304 45p* AC128 20p BC547 15p MPS A05 25p 2N1305 38p* AC176 20p BC548 15p MPS A06 25p 2N1306 45p* AC187K 35p BC549 15p MPS A55 30p 2N1308 30p* AC188K 35p BCY70 10p MPS A56 30p 2N1309 45p* AD181 45p BCY71 10p MPS A50 50p 2N1711 25p AD182 45p BCY72 10p MPS U06 55p 2N1893 35p BC107 18p BC108 10p BC109 10p BC110 10p BC111 10p BC453 10p BC454					

microfile.....

Gary Evans tip toes through the micros

THE MICROPROCESSOR WAS a boon to those people who like organising conferences. Here was a device about which many people felt a keen "need to know."

News of conferences/seminars/lectures came thick and fast, one could have flitted from one event to the next without drawing breath.

A lot of these activities were aimed at the professional but a fair few were designed to appeal to the amateur. With the initial deluge behind us now it is interesting to note that not only are there fewer events but that the nature of those that take place, at least those aimed at the amateur, is changing.

In the early days the subject matter was almost solely concerned with details of the internal architecture of the MPU, max speeds of operation, PSU requirements etc. However, most amateurs, from the word go, thought of the MPU in terms of home computer systems. In this light, a lot of the details presented at these conferences were, essentially, boring. After all, whilst the LSI technology that gave birth to the MPU was essential if any low cost computer was to be envisaged, in essence, a good PSU is just as important to the operation of the overall system and we didn't see many talks on the detailed operation of power supplies — interesting as they might have been.

The realisation that what most people are interested in is personal computing means that today we are seeing more and more conferences dealing with this aspect of things.

Early February saw Microsystems 78, a three day event with one day devoted to Personal Computing.

With Dr Chris Evans (must be O.K. with a name like that — Chris I mean) in the chair, delegates were treated to a day of talks on all aspects of personal computing — talk of accumulators accumulating and stacks stacking was not to be heard.

Later in the year we have the second of the DIY Computer Shows organised by Online (more of that later) and no doubt there are many other events of this nature in the pipe line.

Initial PCW

Early February also saw a new magazine on the market. Personal Computing World is a welcome addition to the ranks of titles that appear on our newsagents shelves every month. Dealing, as it does, almost exclusively with personal computing it should act as some sort of focus for this new hobby — something we need.

While we at ETI hope we have been, and intend to remain with for instance our personal computing supplement in June, involved with personal computing — after all the American magazine Popular Electronics has a regular computing section in spite of the Plethora of computing mags — we acknowledge that with the greater space available to them, PCW fill a long felt need in these Islands.

We wish PCW luck.

For further information on the magazine contact:

PCW
62A Westbourne Grove London
W2

It should however be available from your local newsagent.

Video Writer


The COSMAC VIP (Video Interface Processor) pictured is a new computer kit from RCA.

Featuring the CDP 1802 MPU the VIP is specifically designed to allow easy generation of TV graphics and games. The VIP offers a versatile 4K operating system with facilities for storing and retrieving programs developed in the system's 2K RAM on cassette tape.

Using an interpretive language known as CHIP-8, 2 byte instructions entered via the VIP's hex keyboard, allow patterns to be generated on the screen, the generation of random bytes, the sounding of tones and allow subroutine nesting.

Expansion is possible and the hobbyist manual contains detailed information on use with music synthesizers, relays, printers and ASCII keyboards as well as program listings for twenty video games.

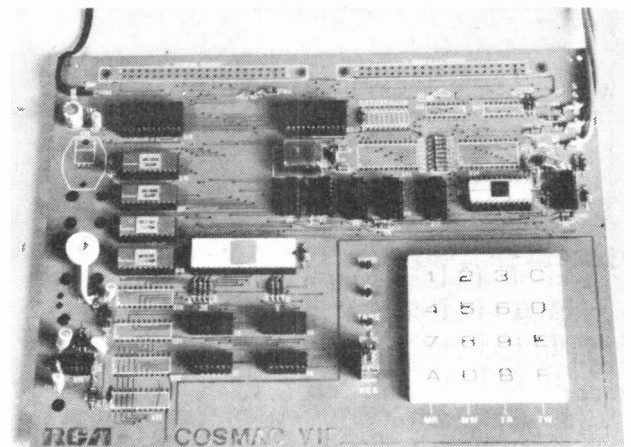At present available only in a NSTC monochrome standard soon a PAL interface chip and programmable sound capability will be available. Further details from: RCA Solid State-Europe Sunbury-On-Thames Middlesex TW16 7HW



Be Rat-ional

If I hear the words Womp Rat once more I think I shall become an intergalactic hermit.


The response to my offer to provide a BASIC listing of a game program last month has been overwhelming.

I thought that I might, if lucky, get a few requests for the game and so did not bother to ask for an SAE. The result — to avoid being lynched by an overworked reader services department — I had to address a good few envelopes myself. A short Microfile this month because writer's cramp has set in.

It was impossible to give personal replies to the letters — no Microfile if I had, no eating or sleeping either — but please anybody who offered us game programs of any sort — take this as a blanket request to send them in to me at ETI.

ETI

Gould Advance Instruments— Professional quality at a realistic price.

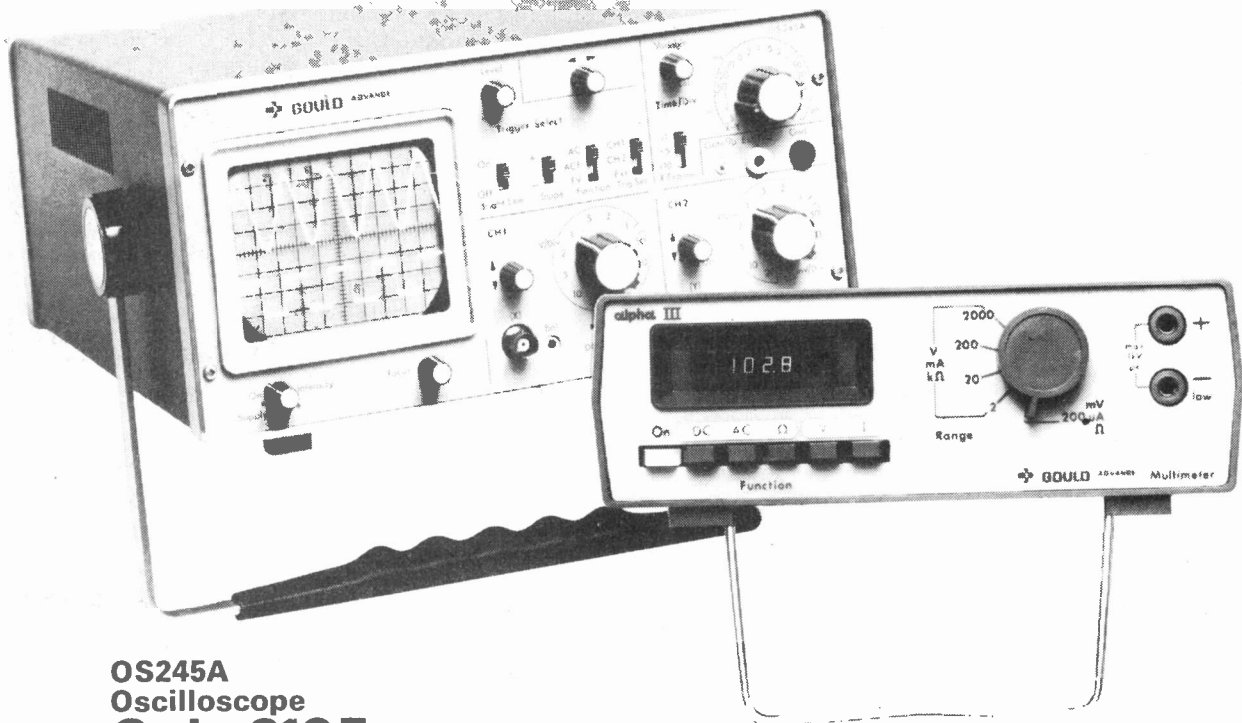

**OS245A
Oscilloscope
Only £195** (excluding VAT)

**Alpha III Digital
Multimeter** **Only £89** (excluding VAT)

OS245A Oscilloscope

Fault-finding, circuit testing or servicing – an oscilloscope is indispensable. It saves time, prevents costly mistakes, and enables you to tackle bigger, better projects.

Now, Gould Advance offer you this professional-quality, dual-trace instrument, at a price which brings it within reach of the amateur enthusiast.

Just look at these great Gould Advance features – then compare the OS245A for value!

- *DC-10MHz bandwidth
- *Dual trace
- *Clear controls, simple operation
- *Fully guaranteed for 2 years
- *5mV/div. sensitivity
- *Time-base speeds to 100 ns/div.
- *4" CRT with 8 × 10 div.

Gould Instruments Division,
Roebuck Road, HAINAULT, Essex IG6 3UE.
Telephone: 01-500 1000 Telex: 263785.
Registered Number 263834 England.

Alpha III Digital Multimeter

With a choice of 25 ranges and basic accuracy of $\pm 0.2\%$, the Alpha III is a professional's multimeter, yet it is versatile enough to cover every amateur application.

And although it is offered at such a modest price, it shares the advanced design features of the more expensive Gould Advance instruments – in particular, the purpose-built chip, incorporating all analogue and digital circuitry.

- *2,000 scale length (100mV resolution)
- *Tough, attractive moulded case
- *Bright red LED display
- *25 ranges
- *Fully guaranteed for 2 years



TO Bob Wheeler, Gould Instruments Division,
Roebuck Road, HAINAULT, Essex IG6 3UE.
Essex IG6 3UE.

PLEASE SEND ME:—

AN OS245A OSCILLOSCOPE at *
£214.00 (inc. p&p and VAT)

AN Alpha III DIGITAL MULTIMETER at *
£99.00 (inc. p&p and VAT)

I enclose *
CHEQUE * POSTAL ORDER * CASH *

for the amount of £ _____

Or please charge my Access *
Barclaycard *

Account for the amount of £ _____

MY ACCOUNT NUMBER IS

Signature _____ (I am over 18)

Surname _____

Initials _____ (Mr/Mrs/Miss)

Address _____

Postal Code _____

*Tick which appropriate Block Capitals Please

Note: This offer applies to the U.K. and Ireland only.

videocraft


Half price Teletext

You can now buy Texas **Tifax** module Teletext decoder complete with matching cable connected keyboard, power supply, interface board and complete instructions for installation in most common television receivers for only £180 +VAT and £2.50 postage, packing and insurance.

Since the interface is connected directly to the television's video output circuitry, picture quality is excellent with pure colours — much more so than is possible from decoders which feed the aerial socket.

Due to the compact nature of the **Tifax** module, installation within most receiver cabinets is no problem. Facilities include seven colours, upper and lower case alphanumeric, graphics, time coded display, and newsflash and subtitle inserted in TV picture.

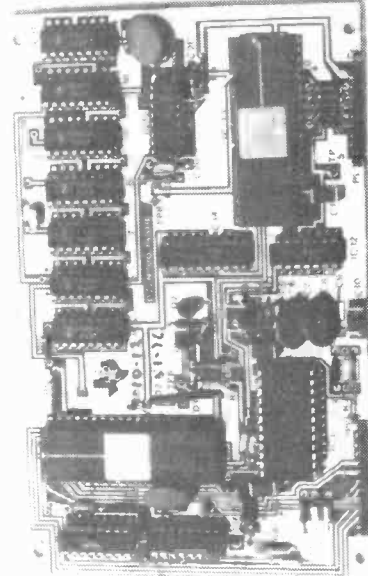To enable us to supply the correct interface board and instructions, we must know your television set make and model and, if possible, chassis type.



videocraft

29-31 Goswell Road
London EC1.

01-251 0391/2/3
Telex: 896953

WE'RE OUT TO FINISH YOU OFF!

Rapitape #
eti PANEL TRANSFERS


MOD MAGS 1977 no 1

GOOD AND PROPER!

... or at least your projects. If there is one thing which is impossible to do at home is lettering front panels to professional standards. At least until now. If you cast your eyes right a while you'll see our new panel transfers sheet, which has been carefully designed to allow you to do exactly that.

The transfers are easily rubbed down, and the two sheet set contains a mass of lettering and —uniquely—control scales for both rotary and slider puts.

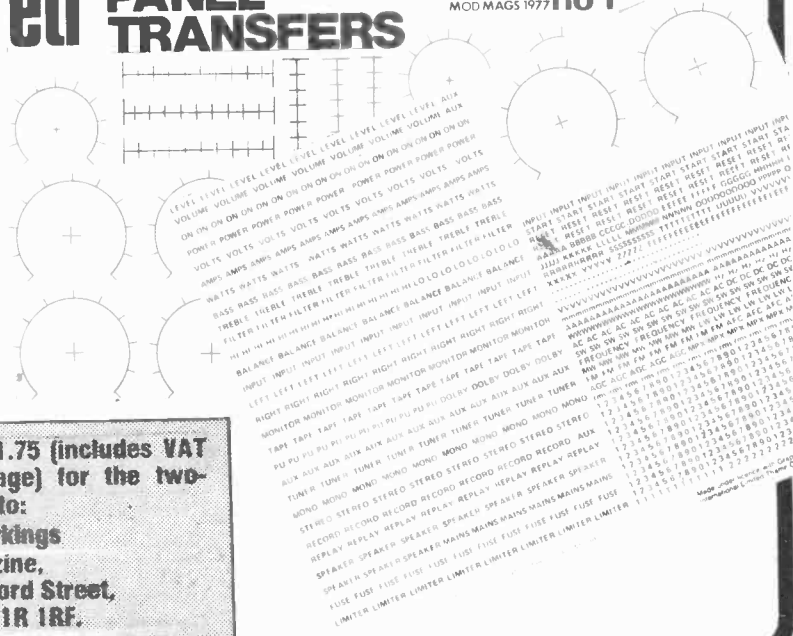Each sheet measures 180mm X 240mm and comes packed flat in a stiff cardboard envelope for protection. There should be enough for dozens of projects here - and the longer you wait the worse they'll look!



Send £1.75 (includes VAT and postage) for the two-sheet set to:
Panel Markings
ETI Magazine,
25-27 Oxford Street,
London W1R 1RF.

AIRAMCO LTD. OPENING SALE

741 op Amp MDIP	20
380 2W Audio Amp DIP	80*
381N Low Noise Dual pre amp DIP	1.45*
555 Timer mDIP	29
556A Dual 555 Timer DIP	85
8038 Volt Controlled Sig Gen DIP 14	3.50

AY51013A UART	5.25
2102 1024 x 1 RAM	1.55
1702A 256 x 8 EPROM	6.25
2708A 1024 x 8 EPROM	10.90
8080A CPU	9.90
8008A CPU	9.90

MM5312 12 Clock 4 digit, MPX, BCD, 7 seg 12/24 hr. 50/60 Hz. 24 pin	5.05
MM5314 Clock 6 digit MPX. 12/24 hr. 50/60 Hz. 24 pin	3.99
MM5316 Clock 5 digit + Alarm. 12/24 hr. 50/60 Hz. 40 pin	6.99
16 pin Skt	16
24 pin Skt	35

Discounts for quantities over 100 . . . P.O.A.
Trade enquiries and orders welcome. Add
12 1/2 % VAT to items marked*



Add 8% VAT to all orders
P&P Add 40p
Mail order only
Facilities for
Access and
Barclaycard




24 Ansaphone ordering service with access or
Barclaycard NO.

AIRAMCO LTD.
30 Witches Linn
Ardrossan, Ayrshire
0294 65530

JAYEN

FG-1

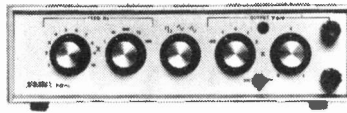

BUILD THIS ADVANCED DESIGN FUNCTION GENERATOR

★ Designed around 8038 Waveform
Generator I.C.

★ DC Coupled Amplifier

★ 1 Hz to 100 kHz

★ Sine, Triangle and Square Wave output

JAYEN Developments, 25 Westgate, Louth, Lincs LN11 9YQ.

Please send a JAYEN FG-1 PC board complete with
instructions, photo annotated Front Panel and Component
Shopping List at £3.85 incl VAT and P&P

Name _____

Address _____

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in
£2.50 with all symbols for direct
application to P.C. board. Individual
sheets 25p each. (1) Mixed Symbols (2)
Lines 0.05 (3) Pads (4) Fish Plates and
Connectors (5) 4 Lead and 3 Lead and
Pads (6) DILS (7) BENDS 90° and 130°
(8) 8-10-12 T.O.5. Cans (9) Edge
Connectors 0.15 (10) Edge Connectors
0.1 (11) Lines 0.02 (12) Bends 0.02 (13)
Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over
250 symbols, signs and words. Also
available in reverse for perspex, etc.
Choice of colours, red, blue, black, or
white. Size of sheet 12in x 9in. Price £1.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours
red, blue, black or white. Each sheet
12in. x 9in contains capitals, lower case
and numerals 1/8in kit or 1/4in kit. £1
complete. State size.

All orders dispatched promptly.
All post and VAT paid

Ex U.K. add 50p for air mail
Shop and Trade enquiries welcome
Special Transfers made to order

E. R. NICHOLLS
P.C.B. TRANSFERS
DEPT. PE/10
46 LOWFIELD ROAD
STOCKPORT, CHES.061-480 2179

1N4148 Diodes by ITT/TEXAS
100 for £1.50

TEXAS TIS 88A VHF FET 10 for £2.30
100 for £20.00

7410	10 for £1.00	Special offer
7412	10 for £1.50	
7420	10 for £1.00	
7430	10 for £1.00	LEDs 0.125"
7432	10 for £2.00	or
7442	10 for £3.50	
7474	10 for £2.00	0.2" red
7476	10 for £2.50	
7483	10 for £7.00	100 for
7493	10 for £2.50	
7496	10 for £4.50	£9.00
74107	10 for £2.00	
74121	10 for £2.50	1000 for
74153	10 for £4.00	
74161	10 for £8.00	£60.00

Ring for devices not listed

555 10 for £2.80 | 741 10 for £2.00

MULLARD 0.01 uf C280 100 for £2.50

1200µ F 63v 2 for £1.00	BTY87	
2200 63v 2 for £1.50	100R	£1.00
3300 63v 2 for £1.60	100V 8.5A	each

BD607/608 Comp Power £1.50 pair

RCA, SCR TO3 case 100v 12.5A
£2.00 each

2102/4L RAM	4 for £6.00
@ £1.60 each	8 for £11.60

BF257 10 for £1.50

Prices include Post and VAT

XEROZA RADIO

306 ST PAUL'S ROAD
HIGHBURY CORNER, LONDON N1
TEL: 01-226 1489

Save on Calculators

TEXAS	
T15040 (print, display, 10 digits, mem, printing calc)	£85.95
PC100A (Print Cradle for T1 prog. calculators)	£174.12
SR51-11 (3 memories/stats. engineering notation)	£32.35
T145 Scientific Green Display 15 sets of 0's	£24.00
T133 (15 bracket levels £15.00, RK3 (Rech Kit)	£5.44
T157 (Key Prog. 150 Prog. steps 8 Mem)	£39.42
T159 (80 Prog. steps/50 mem)	£79.92
T159 (960 Prog. steps/100 mem)	POA
Software for T159 & 58 (each) (four available)	£25.00
T1 Programmer	£50.40

CASIO	
*PROFXI (Mag. card prog. 11 memories 127 steps)	POA
*FX201P (Key programmable, 127 steps, 11 memories)	£49.95
FX2200 (6 + 2, scientific/fraction, LCD, 1000 hours)	£19.95
FX120 (10 dig full sci + 6 brkts + Polar/rect coordinates Permutations + combinations)	£19.95
J3 (12 Digit with Delta%)	£24.95
FX31 (29 sci / fractions inc. degree, rad and grad)	£13.95
FX3000 (L.C.D. full sci + 2 brkts + rect / polar + %)	£25.95
ST-1 (4-way Stopwatch function & %)	£24.95
MO1 (L.C.D. Clock, Calendar, Stopwatch & Calc.)	£34.95
MO2 (L.C.D. Clock, two Alarms, Calendar, Calc.)	£34.95
CO1 (Clock + Calculator + Stopwatch)	£29.89
CO2 (Larger Clock, Calculator, Stopwatch)	SAE
AO810 (L.C.D. Calc., Timer Clock, Alarm)	£19.95
Casio 31C5 10b L.C.D. watch	£59.95
*Free mains adaptor CO1 or CO2 ADAPTOR	£3.00

HEWLETT PACKARD	
HP 19C (cont mem., prog., sci. printer)	£203.32
H.P. 21 (8 + 2 Scientific, R.P.N.)	£52.95
H.P. 22 Business/Management Calculator	£80.64
H.P. 25 (45 prog. steps, 8 mems, engineering notation)	£80.64
H.P. 25C (Continuous memory programmable scientific)	£106.95
H.P. 29C (new combo H.P. 27 + H.P. 25C)	£123.83
H.P. 67 (Mag card programmable, 224 steps)	£287.04
H.P. 97 (Mag card prog. with LED display & Printer)	£437.06

CBM	
4130R (90 functions 10 + 2)	£28.40
PRO100 (B + key prog. 72 steps, 10 memories)	£37.80
M55 (Maths) S61 (Stats) N 60 (Navigator)	£68.50
LC5KI (L.C.D., 5,000hr bat life)	£11.38
LC43SR Scientific 1,000hrs	£21.95

SINCLAIR MICROVISION TV in stock
SHARP EL8 130, LCD musical calc. - great, no keys
EL8029 L.C.D. Folding Pen type Calculator with clip
CT550 L.C.D. Clock Calc. 24 time zones (Alarm)
Basic Chess Challenger at £99.95 (20,000 moves)
Master Chess Challenger POA (60,000 moves)
Gamma Master II (Computer backgammon) £175.

NEW FROM SINCLAIR
A 36 Step
Programmable
Scientific **ONLY**
£13.92
inc. VAT

Full algebraic functions plus 1 x 1/2, x/., sin, cos, tan, arc, rads/degrees in and ex.
PLUS 36 STEPS OF PROGRAMMING WITH CONDITIONAL BRANCHING
AC Adaptor £2.95
Full set Program Library only £4.92 + 54p P&P if bought separately

ELECTRONIC STOPWATCH CALCULATOR

Specifications
STOPWATCH
Measuring capacity:
9 hours 59 minutes 59.9 seconds
(after 10 hours, it reverts to 0 again)
Timing unit:
1/10th of a second
Types of measurement:
Normal time
Net time
Two kinds of Lap times
Read-out
Digital display of hours, minutes, seconds, fraction of a second.
CALCULATOR
Operation:
Four basic functions, chain and mixed operations, constant calculation for four functions, automatic accumulation in four functions, direct access to the memory, percentage calculations including add-ons/discounts and mark-ups, square roots, powers, reciprocals, time calculations, and various kinds of practical calculations.
Capacity:
Four basic functions 8 digits
Accumulation into the memory 8 digits
Square root 7 digits
Time calculation Max 2 digits (hour, 2 digits (minute and second); 1 digit (fraction of a second))

12 FUNCTION CHRONOGRAPH LCD

Hours, mins, secs day
month, chrono stopwatch
Backlight, mineral glass
water resist, chrono timing
to 1/100th. Lap time to
max of 59 59 99 (but
function still continued)
Stainless steel bracelet and
case.
ONE OF THE MOST
ACCURATE LCD
WATCHES ON SALE IN
THE UK

NE6290/18

£38.00 inc. VAT, P&P

The New MO2, the tiny alarm clock, timer, calculator with day, date, year, valid 'till past 2000 A.D. a.m./p.m. hour, minute, 2 alarm clock settings. Time zone memory and full function calculator with % all in a tiny 3/4" x 4 3/4" x 1 3/4" case with 18 month (approx) battery life for only £34.90.

WE SUPPLY ALL SIEKO WATCHES
We accept govt./company purchase orders on all goods

KRAMER & CO
9 October Place, Holders Hill Road, London NW14 1EJ.
Telex: 888941. ATTN. KRAMER, K7. Tel. 01-203 2473
MAIL ORDER ONLY, S.A.E. for data sheets
Export enquiries welcome

tech tips

Proper Identification for T.V. Game Chip

E. Parr

Many of the T.V. game circuits, whether ready built or as a magazine project, use the popular GI 8500 chip. The standard circuit gives white players, ball and court on a black background. The circuit described below gives a grey background, one white and one black player and a white ball and court. This is aesthetically more pleasing and has the advantage of making the squash game less confusing.

The modifications are shown below. The output on Q2 emitter spends the majority of the time at a "grey" level, and this "grey" voltage is defined at the junction of R6 and R7.



The three signals from the 8500 requiring a white output are Ball (pin 6), left player (pin 10) and the score and field (pin 24). These are "Or'ed" together by Q1 to produce a white level defined by the ratio of R1-R3 and R4. The white level on Q1 takes the output on Q1 to white via diode D4.

The one black signal is the right bat (pin 9). This is buffered by two stages of a CMOS 4011 chip, and turns on Q4. This takes the output to a black voltage defined by R6, R7, R8. If a white and black signal occur together

(as happens when the bats cross in squash) the white from Q1 will predominate.

The sync output from pin 16 is inverted and turns on Q3 pulling the output down to sync level, 0V.

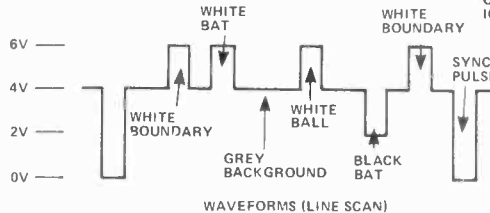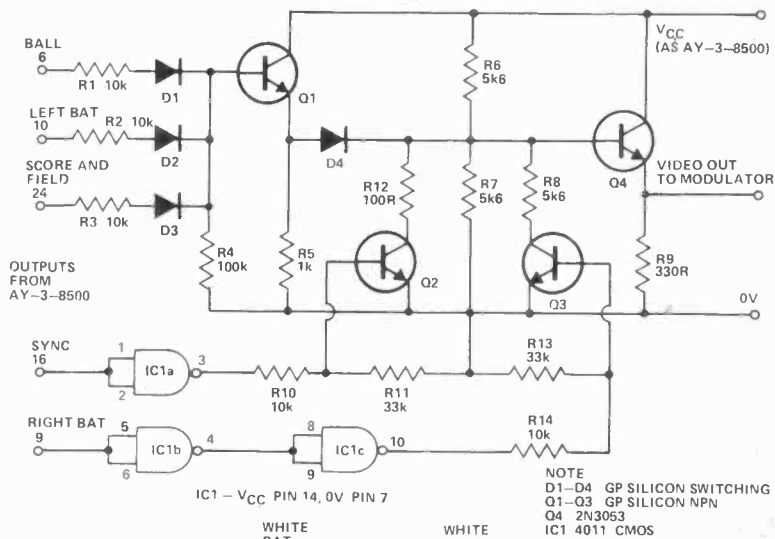
With the values shown and a supply of 9V the open circuit output voltages are White 6V, Grey 4V, Black 2V and sync bottom 0V. The output is positive going video.



Pot Shot

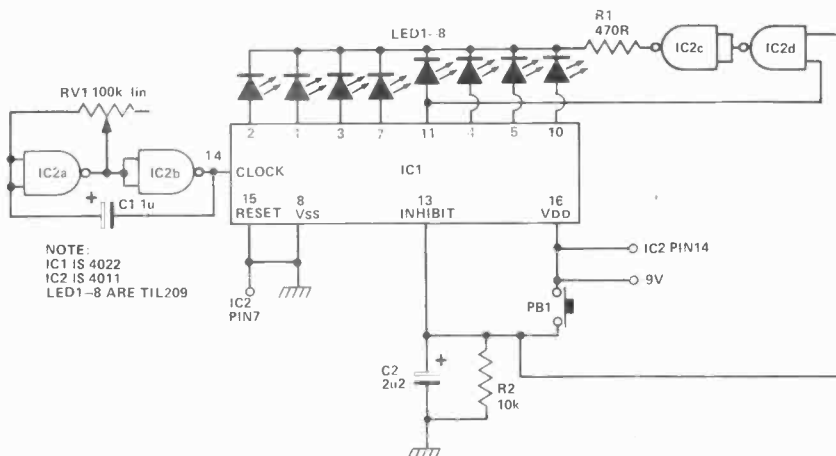A. Kenny

This is a circuit for a game of the shooting gallery variety. IC2a and b form an astable multivibrator clocking IC1 which causes LEDs 1-8 to flash in turn LED 5 is the "target" LED and the object of the game is to depress PB1 just as LED 5 comes on. If this is done, the whole display is blanked for a few seconds signifying a hit. Otherwise, the LED which was lit remains lit. When the push button is released, C2 discharges through R2 taking 8 pin 13 low again and the LEDs will start to flash again.



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

*** SAVE ON TIME—No delays in waiting for parts to come or shops to open!**

*** SAVE ON MONEY — Bulk buying means lowest prices — just compare with others!**

*** HAVE THE RIGHT PART — No guesswork or substitution necessary!**

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors. 5% 10 of each value 22pF to 1000pF. Total 210. **£3.35.**

K002. Extended range. 22pF to 0.1µF. 330 values. **£4.90.**

K003. Polyester capacitors. 10 each of these values. 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for **£4.75**

K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for **£3.75**

K005. Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 series 5% 160V. Total 370 for **£12.30**

K006 Tantalum bead capacitors. 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tants for **£14.20**

K007 Electrolytic capacitors 25V working. Small physical size. 10 each of these popular values: 1.2, 2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.50**

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for **£5.90**

K009. Extended mylar pack. Contains all values from 1000pF to 0.47µF total 290 capacitors to **£11.25.**

K021 Miniature carbon film 5% resistors, CR25 or similar. 10 of each value from 10R to 1M. E12 series. Total 610 resistors, **£6.00**

K022 Extended range, total 850 resistors from 1R to 10M **£8.30**

K043 Zener diodes, 400mW 5%. BZY88 etc. 10 of each value from 27V to 36V, E24 series. Total 280 for **£15.30**

K042 As above but 5 of each value **£8.70**

VEROBOARD

Our packs of vero offcuts are one of our biggest sellers — and no wonder, they are amazing value! Each pack contains 7 or 8 pieces to make up a total area of 100 sq. ins. All packs are the same price, **£1.30 each** and are available as follows:

Pack A, all 0.1" pitch
Pack B, all 0.15" pitch
Pack C, mixed 0.1 & 0.15"
Pack D, all 0.1" plain
Also available by weight: 1lb **£3.95** 10lbs **£32.50**

Regular size vero:
17x3¾x0.1" **£2.00**, 10 strips **£15**
17x3¾x0.15 **£1.76**; 0.1" plain **£1.63** *

DIP Breadboard, size 6.15x4.5", can accommodate 20 x 14 pin IC's **£2.35**

VQ Board, size 148 x 75mm 0.1" pitch. Copper strips in rows of 4 to facilitate construction with IC's. Layout sheet provided **85p**

VERO PINS AND TOOL

Spot face cutter for 0.1 or 0.15 pitch **75p**
0.1" pins single sided **30p/100**
0.1" pins double sided **35p/100**
0.15" pins single sided **30p/100**
0.15" pins double sided **35p/100**

VEROCASES

Plastic top and bottom, ally panels front and back.

1237	154x85x40	£2.53
1238	154x85x60	£2.79
1239	154x85x80	£3.32
3007	180x120x40	£3.30
3008	180x120x65	£3.50
3009	180x120x90	£3.74
1410	205x140x40	£3.51
1411	205x140x75	£4.05
1412	205x140x110	£5.12

VERO PLASTIC BOXES

Professional quality two tone grey polystyrene with threaded inserts for mounting PC boards

2518	120x65x40	£2.17
2520	150x80x50	£2.45
2522	188x110x60	£3.23

SLOPING FRONT BOXES

1798 171x121x75/37.5 **£4.19**
2523 220x174x100/53 **£6.90**

Potting box, 71x49x24mm black or white **40p**

Hand controller box 94x61x23mm White **64p**

SEMICONDUCTORS

Diodes. 1N4001 2 5p; 4004/5 7p; 4006 8p; 4007 9p; 1250V 1A, 10p; 1250V 1.5A, 12p; 50V 3A 10p; 100V 3A, 12p; 400V 3A, 15p; 200V 10A stud, 40p; 400V 10A stud, 48p.

400mW Zeners 2V 7 to 36V, 10p each. 1.3W Zeners 3V3-200V, 20p.
10 watt zeners from 4V3 to 200V **93p**.
OA81, 5p; OA91, 8p; 1N4148, 4p.

Bridge Rectifiers

50V 1A 25p; 200V 1A 32p; 400V 1A 36p; 100V 2A 48p; 400V 2A 58p; 100V 4A 65p; 400V 4A 80p; 100V 6A 74p; 400V 6A 98p.

SCR's

0.8A	60V	T092	35p
1A	400V	T05	60p
4A	200V	T0220	52p
4A	400V	T0220	70p
6A	200V	T0220	56p
6A	400V	T0220	75p
6A	400V	T066	80p
10A	100V	T0220	82p
10A	200V	T0220	87p
10A	400V	T0220	120p
10A	600V	T0220	148p

Triacs

6A	400V	T0220	98p
8A	600V	T0220	135p
15A	200V	Stud	135p
15A	400V	Stud	220p

TRANSISTORS

AC127	18p	BC548	10p	8RY56	40p
AC128	18p	BC549	10p	0CP71	120p
AC176	18p	BCY70	15p	TIP41A	56p
AC187	20p	BCY71	15p	TIP42A	66p
AC188	20p	BCY72	14p	TIP2955	86p
AD149	70p	BD131	38p	TIP3055	42p
AD161	40p	BD132	40p	TIS43	35p
AD162	40p	BD133	48p	2N2646	60p
AF279	75p	BD137	40p	2N2905	21p
BC107	12p	BD138	40p	2N2926	12p
BC108	10p	BD139	42p	2N3053	28p
BC108C	12p	BD140	44p	2N3054	28p
BC109	12p	BF173	20p	2N3055	50p
BC109C	15p	BF181	30p	2N3442	130p
BC147	10p	BF194	10p	2N3702	10p
BC148	10p	BF195	10p	2N3703	10p
BC149	10p	BF196	10p	2N3704	10p
BC157	10p	BF197	12p	2N3705	10p
BC158	10p	BF200	28p	2N3706	10p
BC159	10p	BF199	24p	2N3708	10p
BC182	12p	BF179	26p	2N3710	10p
BC183	12p	BF179	26p	2N3819	28p
BC184	12p	BF179	26p	2N3904	15p
BC212	14p	BF184	22p	2N3906	15p
BC213	14p	BF188	22p	2N6027	55p
BC214	14p	BF190	18p	2N6028	60p
BC441	32p	BFY51	18p	40673	65p
BC461	32p	BFY52	18p		
BC547	10p	8RY39	40p		

All prices quoted except Bulk Buyers Corner** include VAT. Just add 25p UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export / Wholesale enquiries welcome. Wholesale list now

available for bona fide traders. Surplus components always wanted.

Our retail shops at **21 Deptford Broadway, London, SE8 (01-692 2009)** and **38 Lower Addiscombe Road, Croydon (01-688 2950)** stock some of the advertised goods for personal callers only. Ring them for details.

1977/8 CATALOGUE

48 BIG pages packed with over 4,000 items, many of them illustrated. Discount vouchers worth 50p. PRICE **30p + 15p** post. (Overseas send **60p** surface or **£1** airmail.) Also included is our current Bargain List. Send SAE for bargain list alone.

SIRENS

Use in cars, houses, anywhere that a powerful noise will frighten off would-be intruders. Uses 4 HP7 batts. Overall size 100 x 72 x 60mm. Only **£1.70**.

COMPONENT PACKS

200 miniature resistors, ¼, ½, 1W **£1.00**
400 assorted resistors, ¼, ½, 1W **£1.30**
200 poly, mica, ceramic capacitors **£1.20**
100 Mullanid C280 polyesters, 0.01-1µF **£1.00**
150 wirewound resistors, 2-10W **£1.60**.
200 PC resistors, ¼ and ½W **60p**.
20 assorted pots, inc. sliders **£1.70**.
200 transistors, mostly unmarked, inc. power devices. About 75% useable **£1.35**.

COMPUTER PANELS

A dozen boards with top grade components — transistors, inc. power types, zeners, trim pots, IC's, resistors and capacitors. Hundreds of parts for just **2.75**.

PC ETCHING KIT MkIII

This latest version of our popular kit now contains 200 sq. ins copper clad board, 2 miniature drill bits, 1lb Ferric Chloride, DALO etch resist pen, abrasive cleaner, etching dish and full instructions. **£3.90**.

VOLTAGE REGULATORS

78L12	T092	12V	150mA	75p
723	14dl	2-37V	150mA	50p
MC1469A	T066	2½-37	500mA	150p
78M05	T05	5V	500mA	85p
78M12	T05	12V	500mA	85p
1405	T0126	5V	500mA	85p
1412	T0126	12V	500mA	95p
7715	T0220	15V	750mA	120p
7805	T0220	5V	1A	150p
7812	T0220	12V	1A	150p
LM309K	T03	5V	1.2A	150p
LM323	T03	5V	3A	650p

POWER SUPPLY UNIT



A102 standard mains input. Outputs 3, 6, 7½, or 9V DC @ 400mA max. 3 switches, on/off, polarity reversing and voltage change. Regulated to supply exact marked voltage from no load up to full current. Size 127x76x57mm. Price **£5.95**

★ ★ ★ BULK BUYERS CORNERS ★ ★ ★

All prices per 100; all goods full spec. Send sae for current list containing hundreds of bulk offers.


1N4001	£3.20	BC157/8/9	£6.00
1N4002	£3.80	BC183	£5.00
1N4003	£4.40	BC213	£8.00
1N4004	£5.00	BFY51	£12.00
1N4005	£5.60	2N3053	£16.00
1N4006	£6.20	2N3055	£34.00
1N4007	£6.80	741 8DIL	£18.00
1N4148	£2.30	555	£28.00
AC127	£12.00	LM301	£16.00
AC128	£12.00		
AC176	£13.00	74 series TTL less 25%	
AC187	£14.00	for 100+ of any one type (+VAT). Tant bead caps — less 30% for 100+ of one value.	
AC188	£14.00		
BC107	£7.00		
BC108	£7.00		
BC109	£7.00		
BC147/8/9	£6.00		

★ **SPECIALS** ★
1,000 off 8 pin DIL
741C op-amp by Texas
90p/100 **£6.20/**
1,000. No mixing
Special 100 each value
1R-10M (8500) **£65**;
1,000 each value **£550**;
50V min ceramic plate
caps, 22pF to 1000pF
5% **£2** per 100.
£1.75/1,000. No
mixing.
1500uF 18V PC mntg
elects. 18 x 32mm
£4/100, **£35/1000**
12.5uF 25V 12 x 7mm
£1/100, **£7/1,000**
50uF 350V 27 x 38mm
£18/100.

Add VAT to bulk prices

Speed Controller

J. Harris

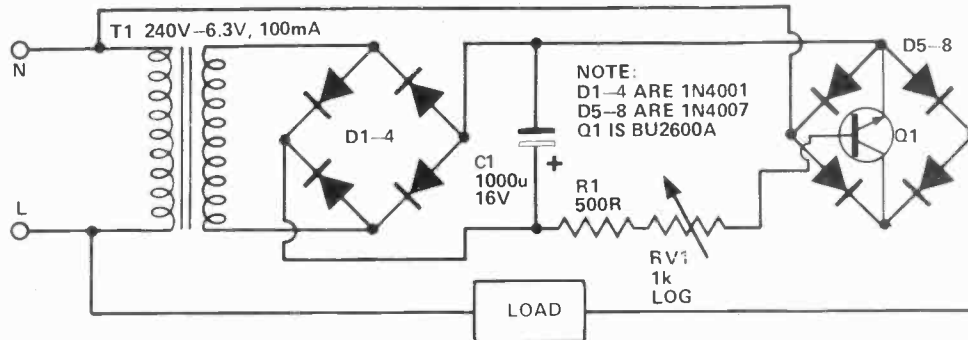

Some AC motors judder badly at low speeds when controlled by triacs, using phase control. This circuit gives very smooth operation with no RFI.

Q1 acts as a 'variable resistor' in the mains supply, with diodes D5-8 ensuring unidirectional current flow through the transistor.

Bias to the transistor is supplied by the mains transformer and controlled by RV1. Q1 must be able to withstand peak mains voltage ($\sim 350V$).


Increasing Regulator Outputs

D. Self

It is often necessary to arrange an integrated circuit 3-terminal voltage regulator to give a higher output voltage than that set by the regulator alone. The normal way of doing this is to connect the "common" terminal to the mid-point of a potential divider hung between the regulated output and ground. The regulator voltage now appears across the top divider resistor; hence, if for example equal divider resistors are used, the output voltage is twice that maintained by the regulator between its common terminal and output.

The problem with this method is that most IC regulators (eg the 78-series) have a small quiescent current (approx 10mA) flowing out of the common terminal to ground. The magnitude of this current is not closely controlled, and hence the total output voltage becomes somewhat unpredictable due to this extra current flowing in the bottom half of the divider. Low divider resistor values help, but there are likely to be the complications of heat dissipation and inefficiency.

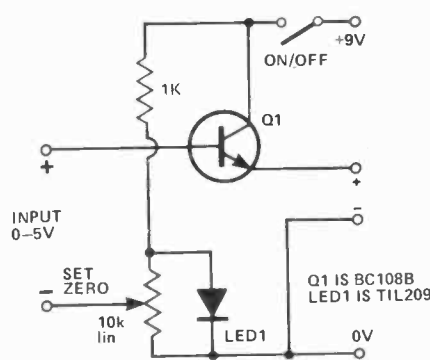The circuit above avoids the problem by using transistor Q1 to generate a low impedance at the regulator common terminal by emitter-follower action, while trans-




More Ohms Per Volt

R. Soar

This circuit is designed to improve the performance of a low cost 1k/volt multimeter on the 0.5V DC range.

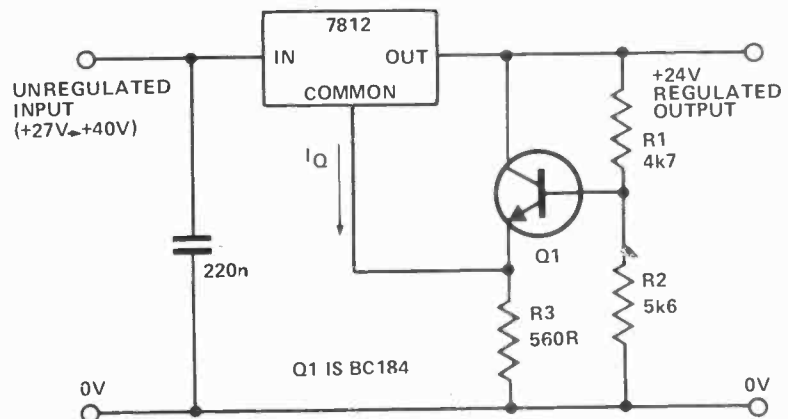The BC108 emitter follower provides an impedance transformation with a gain of 250 or more, so that the effective input impedance of the multimeter is now 250k/volt. The LED provides a fixed reference voltage for the set zero control, which compensates for the voltage drop across the transistor.



ferring the voltage derived from a relatively high-resistance divider network. The value of R3 is not critical, but must be low enough to accept the

highest likely quiescent current without causing Q1 to turn off.


The circuit shows a practical 24 Volt supply using a 7812 regulator.

SEND FOR SINTEL FREE CATALOGUE

SINTEL

RESEARCH MACHINES COMPUTER SYSTEMS
 AVAILABLE THROUGH SINTEL
RESEARCH MACHINES 2802 with 2k ROM Monitor, 4k bytes RAM £398.00
RESEARCH MACHINES 3802 Part-Assembled, 2k ROM Monitor, 4k RAM £539.00
RESEARCH MACHINES 3802 Ready-Built, 2k ROM Monitor, with Keyboard, with 16k RAM £1081; with 32k RAM £1448; with 48k RAM £1895
 Supporting Software available, including 8k Extended BASIC £24.50
 PRICES exclusive of VAT. CARRIAGE at Cost.
 PLEASE CONTACT SINTEL FOR FULL INFORMATION ON THESE AND OTHER SYSTEMS

SINTEL CLOCK KITS



RED DIGIT DESK CLOCK

CODE	PRICE
ACK	£28.80
111-222	£15.50
GCK	£12.95
CCK	£41.90
AUT-CK	£18.85
XTK	£5.46

6 Red Digit **ALARM CLOCK** w.205mm h.40mm d.140mm
 4 Red Digit **DESK CLOCK** w.154mm h.40mm d.85mm
 4 Green Digit **DESK CLOCK** w.154mm h.40mm d.85mm
 6 Red Digit **CAR CLOCK WITH TIMER** w.205mm h.40mm d.140mm
 4 Red Digit **CAR CLOCK** w.154mm h.40mm d.85mm
 50Hz **CRYSTAL TIMEBASE KIT**

CMOS

CD4020	1.28	CD4040	1.11	CD4066	0.63	CD4096	1.08
CD4021	1.04	CD4041	0.86	CD4067	3.85	CD4097	3.85
CD4022	0.94	CD4042	0.86	CD4068	0.23	CD4098	1.13
CD4000	0.17	CD4023	0.23	CD4043	1.01	CD4069	0.23
CD4001	0.18	CD4024	0.80	CD4044	0.96	CD4070	0.51
CD4002	0.17	CD4025	0.23	CD4045	1.45	CD4071	0.23
CD4006	1.20	CD4026	1.78	CD4046	1.37	CD4072	0.23
CD4007	0.18	CD4027	0.58	CD4047	1.04	CD4073	0.23
CD4008	1.00	CD4028	0.92	CD4048	0.58	CD4075	0.23
CD4009	0.58	CD4029	1.18	CD4049	0.58	CD4076	1.34
CD4010	0.58	CD4030	0.58	CD4050	0.58	CD4077	0.45
CD4011	0.20	CD4031	2.30	CD4051	0.94	CD4078	0.23
CD4012	0.23	CD4032	1.02	CD4052	0.94	CD4079	0.23
CD4013	0.58	CD4033	1.44	CD4053	0.94	CD4082	0.23
CD4014	1.04	CD4034	1.97	CD4054	1.20	CD4085	0.74
CD4015	1.04	CD4035	1.22	CD4055	1.36	CD4086	0.74
CD4016	0.58	CD4036	3.29	CD4056	1.36	CD4089	1.60
CD4017	1.04	CD4037	0.98	CD4059	4.93	CD4093	0.92
CD4018	1.03	CD4038	1.10	CD4060	1.15	CD4094	1.94
CD4019	0.58	CD4039	3.20	CD4063	1.13	CD4095	1.08

A RANGE OF SINTEL INDUSTRIAL MODULE KITS
 Latched Counter modules are now available from SINTEL, using both CMOS and TTL ICs. These kits will give you a very compact unit at less than the cost of the components bought separately and will save you considerable design, purchasing, building and de-bugging time. Each kit has a set of red LED displays, two PCBs and the appropriate number of TTL or CMOS ICs, plus brackets, etc., resistors, capacitors, single in-line plug and sockets and instructions.

KITS FOR LATCHED COUNTER MODULES

	TTL		CMOS	
	Part No	Price	Part No	Price
2 digit	526-412	£10.52	548-470	£10.42
4 digit	657-412	£17.98	191-470	£18.11
6 digit	721-412	£25.66	869-470	£25.85

For our full range of Counter PCB sets and Display PCBs — send for FREE CATALOGUE

COMPONENTS

MICROPROCES-	SOLDERCON	DISPLAYS	MEMORIES
SORS	PINS	TYPE	2102A-6 2.05
MC68002 190.00	100 0.50	FM0500 C.C. 1.30	2112A-4 2.90
MC6800 15.97	1000 4.00	TYPE	
MC6820 8.02	3000 10.50	TIL321 C.A. 1.49	VEROCASES
Z80 CPU 2.5MHz		SLT01 4.90	751410J 3.36
Z80 CPU 4MHz			7514110 4.10
Z80 CTC 36.98	CLOCK CHIPS		751237J 2.50
Z80 P10 12.80	AY51202 3.10	CRYSTALS	7512380 3.00
Z80 P10 12.80	AY51224 3.50	32.768KHz 3.50	751239X 3.50
	NK50253 5.60	5.12MHz 3.60	

DATABOOKS

Intel Memory Design Handbook	£5.20
Intel 8080 Microcomputer Systems User's Manual	£5.25
Intel 8085 Microcomputer System User's Manual	£5.15
Motorola Booklets From the Computer to the Microprocessor	£1.80
Motorola CMOS Databook (Vol. 5 Series B)	£3.50
Motorola M6800 Microprocessor Applications Manual	£12.95
Motorola M6800 Programming Manual	£5.35
National SC/MP Introkrit User's Manual	£0.75
National SC/MP Technical Description	£1.80
National Semiconductor TTL Databook	£2.10
RCA CMOS and Linear IC Databook	£5.45
Texas Instruments Pin Configuration Guide: A very useful set of gloss cards showing top and bottom pin-out views of 7400 ICs plus many others (T 1. Memories, Op-Amps, etc.)	£2.95
Z80 Assembly Language Programming Manual	£7.50
Zilog Z80 CPU Technical Manual	£5.60
Zilog Z80 CTC Product Specifications	£0.80
Zilog Z80-P10 Technical Manual	£3.30
DATASHEETS at 75p each on IM6100, 6800, SC/MP, CDP1802, 2650, TMS5501, TMS8080, 9131, Z80, P, Intel 8085. Also free data on some components.	
BEST OF BYTE Volume 1, 380 pages	£11.95

Our Offices are at 209 Cowley Road, Oxford, but please do not use this as a postal address.
ALL PRICES VALID UNTIL 30th APRIL, 1978
OFFICIAL ORDERS ARE WELCOME from Companies, Govt. Depts, Natn. Inds., Univs., Polys.
ORDERS: C.W.O. add VAT @ 8% + 35p p&p. TELEPHONE and CREDIT (Invoice) ORDERS add VAT @ 8% + 80p p&p minimum charge (the balance will be charged at cost). Please see FAST SERVICE. EXPORT ORDERS welcome, no VAT but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For Export postage rates on heavy items — contact us first.

ORDERS TO: SINTEL, PO BOX 75A, OXFORD
 Tel. 0865 49791

FAST SERVICE We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon-Fri) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.



Wilmslow Audio

THE firm for speakers!

Send 15p stamp for the world's best catalogue of Speakers, Drive Units, Kits, Crossovers, etc., and discount price list

- ATC ● AUDAX ● BAKER ● BOWERS & WILKINS
- CASTLE ● CELESTION ● CHARTWELL ●
- COLES ● DALESFORD ● DECCA ● EMI ● EAGLE
- ELAC ● FANE ● GAUSS ● GOODMANS ●
- HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN
- WATTS ● KEF ● LEAK ● LOWTHER ●
- McKENZIE ● MONITOR AUDIO ● PEERLESS ●
- RADFORD ● RAM ● RICHARD ALLAN ● SEAS ●
- TANNOY ● VIDEOTONE ● WHARFEDAILE

WILMSLOW AUDIO Dept. ETI


SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE, SK9 1HF

Discount HiFi, etc., at 5 Swan Street and 10 Swan Street

TEL: WILMSLOW 29599 FOR SPEAKERS
 WILMSLOW 26213 FOR HIFI

TECHNALOGICS PROUDLY PRESENT
 THE "LOGISCAN Mk. II"
 COLOUR TELETEXT DECODER

WITH "NEW FACILITIES"

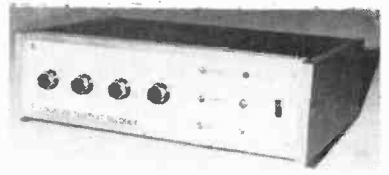

YOU CAN NOW BUY A TELETEXT DECODER TO THE LATEST BBC/IBA/BREMA JOINT SPEC. (NB. Many other decoders are not full spec. display).

THE LOGISCAN Mk. II OFFERS THESE EXTRAS:

- ★ Double/Single Height
- ★ Conceal/Reveal Switch
- ★ Discrete Graphics
- ★ Graphics Hold/Release
- ★ Auto Newsflash
- ★ Flash/Steady Display
- ★ 6800 MPU Compatible
- ★ Background Colour Fix
- ★ Unfix (revert to black)
- ★ Contiguous Graphics (Instant Colour Changes)
- ★ Roll Mode
- ★ Sub-title Inserts
- ★ DMA Capability

★ Kit is complete with case, psu ★ Header Switch ★ Freeze switch

FULL TECHNICAL BACK UP SERVICE

- 12 months' guarantee on all parts — subject to correct assembly and use.
- Board fault finding service (boards unpluggable for easy dispatch) Interface included
- Technical advice on installation.

We are also glad to announce that our decoders are available installed in either 26" or 22" colour televisions for just over £500 and are available for view or purchase from Colourvision, Smith-down Road, Liverpool L18.


KIT £205 + 12 1/2% BUILT £265 + 12 1/2%
 Details large S.A.E. Mail Order

TECHNALOGICS
 8 EGERTON STREET
 LIVERPOOL L8 7LY

Car Voltage Regulator

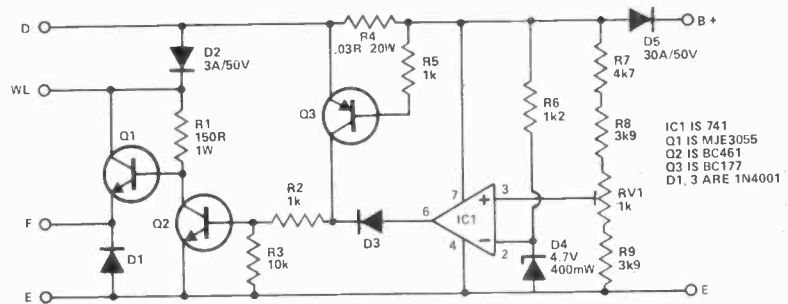C. Gibbons

This circuit provides solid state control of battery charging. The field winding of the dynamo is initially energized via the ignition light as in a conventional system. Current flowing down the WL lead passes through Q1 to the F lead then to the field coil. Once the engine has started, current from the dynamo passes through D2 to Q1. The ignition light goes out because the WL lead rises in voltage to that of the battery. Current also passes through D5 to the battery. The battery voltage is sensed by IC1, which is wired as a comparator, once the voltage of the non inverting input, rises above that of the inverting input (Held at 4.6 volts by D4) the output goes high. Current then flows through D3 and R2 to the base of Q2 turning it on. This then pulls down the base of Q1 turning it off and cutting off the current to the field winding. The output from the dynamo then drops bringing down the battery voltage. This holds the battery voltage con-



stant. The battery voltage is adjusted by RV1 to approximately 13.5 volts.

Under cold weather starting the battery voltage drops very low. Once the engine has started the internal resistance of the battery is also very low, which would draw excessive current from the dynamo causing possible damage. To limit the current R4 is inserted in the main power lead from the dynamo, the resistance of R4 is chosen so that at maximum current


(Typically 20 amps) 0.6 volts is developed across it, this then turns on Q3. When Q3 turns on current flows from the power rail through R2 to the base of Q2 turning it on, which in turn, turns off Q1 and cuts off current to the field winding. The output from the dynamo then drops.

No changes have to be made to the existing wiring. The circuit can be housed in an old regulator box, Q1, Q2 and D5 should be mounted on a heat sink.

Organ Modification

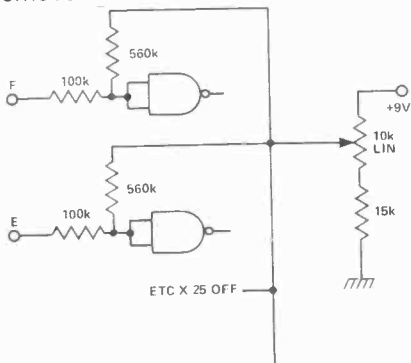I. Cole

One of the problems with the ETI Touch Organ (December 76) is that peoples skin resistance varies enormously and with the 4M7 pull up resistors as specified, when a person with moist skin touches the keyboard the note is sustained for several seconds even when the finger is removed.




This modification provides a solution in the form of a sensitivity control.

The pull up resistors are removed and replaced by 560k resistors stood vertically on the board. The free ends of the resistors were then joined with a piece of rigid wire and connected to the wiper of the "sensitivity" pot.

Low Current Touch Switch

D. Ian

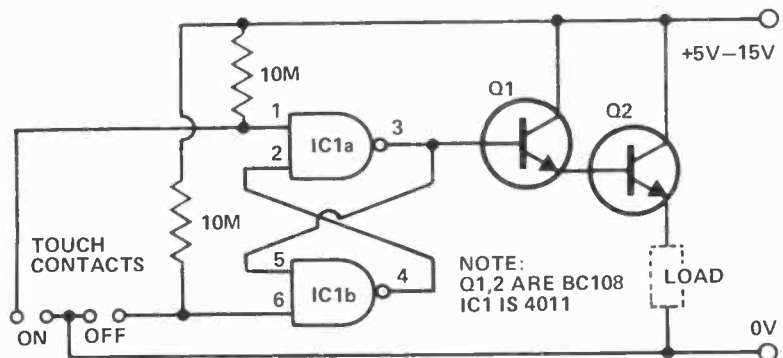

The cost of many CMOS ICs is now lower than a mechanical on/off switch. Using only one half of a 4011, plus a couple of general purpose transistors, a touch operated switch can be constructed which is ideal for many battery powered projects.

Assuming that the inputs to the remaining half of the 4011 are tied low, the current drawn in the off state

is almost negligible and battery life is hardly affected.

Touching the 'on' contacts with a finger brings pin 3 high, turning on the darlington pair and supplying power to the load (transistor radio etc). Q1 must be a high gain transistor, and Q2 chosen for the current required by the load circuit.

electronics tomorrow.....

by John Miller-Kirkpatrick

6800 Update

RECENTLY RECEIVED from a Motorola distributor is an M6800 series shortform catalogue entitled 'Micro-processor News — September 1977'. This catalogue lists Motorola's MPU products ranging from integrated circuits to EXORcisers and Polyvalent Development System components.

In the area of chips Motorola have announced some interesting new goodies. Their 1024 x 4 MCM6614, static RAMs come in 200, 300 and 450ns versions. Motorola's 128 x 8 bit static RAM, the MCM6810 is now also offered in 250, 360 or 450 ns versions. On the subject of memories there is the MCM68708 10 24 x 8 EPROM (basically a 2708) and the pre-announcement of the 2716 product, the MCM68716.

New Interfaces

Motorola have not been any slower than other MPU manufacturers in getting onto the LSI interface chip bandwagon. LSI technology allows many functions to be integrated on one chip to give high density, low cost interfaces to I/O devices which would otherwise require multi-TTL chip solutions. An example is the MC6843 Floppy Disk Controller which performs the complex interface between an M6800 system and a range of Floppy Disk drives.

The MC6845 is Motorola's CRT controller chip which performs the 6800 to CRT interface with so many programmable options that one set of options is bound to fit your requirements. It features programmable dots per character, lines per character, characters per row, rows per screen, sync generation and cursor generation. It even features an on-chip light pen register to allow the use of presumably some form of photo diode or transistor to recognise a particular character location on the CRT. This would allow the use of a non-keyboard entry device for a low cost MPU system. If the MPU is programmed to display its complete character set at the bottom of the screen whenever it expects a keyboard entry then the light pen can be used to choose the input character from those displayed — System 68 VDU revisited?

Continuing through the catalogue we pass the various auxiliary circuits which include a GPIA General



New Total Development System M68 TDS from Motorola.

Purpose Interface Adaptor, Modems, DMA Controller, Bus transceivers and a thing called a 'Triple Bi-directional Bus Extender/Switch' (TB-DBES?) or MC6881/3449. After this it becomes simple to understand the new two-chip M6800 (MC6802 + MC6846) and the two-board computer (MEK D2 kit).

By now you are prepared for the Polyvalent Development System (PDS) which fills the gap between low-cost and on-a-board microcomputers, and the sophisticated aids for designing microprocessor systems. As its name suggests the PDS is really a family of sub-systems that can be selected to provide the required options and can then be used to analyse the system. This is Motorola's description of their PDS, which looks to me like a rich man's System 68. One version of the PDS is called the Autonomous Development System (you guessed it — ADS for short) which includes the PDS master board interfaced to a keyboard and 5 inch CRT monitor, the kit with monitor is the M68ADS1 or M68ADW1 without the CRT. I am not sure that I could recommend these kits as cost effective MPU tools at over £900 if System 68 costs about £300! But congratulations to Motorola for seeing the problem of high-cost TTYs and trying to overcome the problem.

On page 16 of the catalogue you are introduced to the MC68CIM1 (CIM stands for Audio-Cassette Interface Module). This is used to interface any ordinary audio-cassette recorder with any of the PDS configurations (SAC, MEB, ADS). The data is recorded on the cassette according to the Kansas City Standard (CUTS), in the playback mode the clock is recovered from the signal and used to clock the receiving ACIA in the PDS, this feature copes with cassette speed variations of up to 30% without producing errors. The MC68CIM1 is a module consisting of several chips on a PCB (isn't it about time someone produced a single chip CUTS interface to plug on to any 8 bit data bus?), if anybody knows of one please let us know.

ETI

BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors, EX-equipment panels, etc. covered in valuable components. No time to sort. Must sell by weight 7lbs—£4.95, 14lbs—£7.95, 28lbs—£12.00, 56lbs—£20.00, 112lbs—£30.00

BARGAIN PACKS

Handy Packs

- 4 aluminium boxes 128 x 44 x 38mm, ideal for signal injectors, etc. £1.00
- Self-fluxing enamelled copper wire 18 and 22 swg on 2oz. reels 2 for £1.10
- 100 miniature reed switches, ideal for burglar alarms, model railways, etc. £3.30
- 15 2-pole reed relays on board operate at 12 volts £2.45
- 6 6-pole 12 volt reed relays on board £2.45
- High quality computer panels smothered in top-grade components:
 - 5lbs. £4.75
 - 10lbs. £8.95
- New U.H.F. transistor TV tuners, 4 push-button type £2.50
- Rotary type with slow motion drive £2.50
- Set of 4 black and chrome knobs for P/B tuners above 60p
- Aluminium TV coax plugs 10 for £1.00
- 20mm anti-surge fuses.
 - 800mA 1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A. Your selection 12 for £1.00
 - 100 for £7.00
- Ultrasonic transceiver units, each contains transmit, and receive transducers (3/8" Diam), transistor circuit board, range control, connection chart and tamper-proof switch contained in small aluminium case with grille. Brand new and boxed £5.25 ea.

Miniature mains transformers, fully shrouded, ex new equipment. 240V in 6-0-6v out at 100 mA. Complete with mains lead and plug on input and short leads on output £1.20

Miniature edgewise panel meters 200µA F.S.D. £1.20

Component Bargains

300 mixed resistors 1/2 & 1/4 watt £1.50

300 modern mixed caps most types £3.30

100 mixed polyester caps £2.20

100 mixed modern miniature ceramic plate caps £1.80

Semiconductor Bargains

100 new and marked silicon and germanium transistors including BC148, BF194, BC183, etc. £3.95

200 new and marked transistors including 2N3055, AC128, 8FY50, BD131, etc. £6.95

100 mixed diodes IN4148, etc. £1.20

100 mixed diodes including zener, power and bridge types £3.30

200 unmarked mixed transistors, lots of interesting types including power. Send 60p for samples £4.50

25 new and marked integrated circuits including 555, 741, 7400, 7490, TBA 800, CD4001, etc. £4.70

BR 101 full spec. 5 for £1.00

ITT 25kV ctv eht triplers for Decca 'Bradford' chassis brand new £2.50 for 10

DELUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad f/g board, 1lb. ferric chloride, 1 dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions — only £5.30.

REFILL PACKS FOR ABOVE

- 150 sq. ins. fibre glass board £2.00
- Dalo pen 90p
- 1lb. ferric chloride to mil spec £1.95
- 5lbs. ferric chloride to mil spec £5.00
- Instruction sheet 20p

30p P & P. ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY DEPT., ETI, 149a BROOKMILL ROAD, DEPTFORD, LONDON, SE8

Callers by appointment only

TV GAMES

Fully assembled, attractively cased TV games — black and white £14.95. Colour £28.95. AY-3-8500 £5.95 (only £4.80 for 10 off). AY-3-8550 £9.95. AY-3-8600 £11.95. Black and white TV games kits: Standard model £9.50. Economy model £4.95. Colour TV games kits: Standard £17.00. Economy £12.45. Colour Generator kit, adds colour to most black and white games £7.50. Rifle kit £4.95. Send see for giant, free data.



NEW COMPONENT SERVICE

Resistors 5% carbon E12 10 to 10M. 1/4W 1 1/2p. 1W 3p. Preset pots subminiature 0.1W 100 to 4M7 9p. Potentiometers 1/4W 4K7 to 2M2 log or lin. Single 30p, dual 95p. Polystyrene capacitors E12 63V 22pF to 8200pF 3 1/2p. Ceramic capacitors 50V E6 22pF to 47000pF 3p. Polyester capacitors 250V E6 0.1 to 1mf 5 1/2p, 15, 22, 33mf 7p, 47mf 11p. Electrolytics 50V 47 1, 2mf 5p, 25V 5, 10mf 5p, 18V 22, 33, 47mf 6p, 100mf 7p, 220, 330 9p, 470 11p, 1000mf 16p. Zener diodes 400mW E24 3V3 to 33V 8 1/2p.

MAINS TRANSFORMERS

6-0-6V 100mA 94p. 9-0-9V 75mA 94p. 12-0-12V 50mA 94p. 13V 1 1/2A £1.10. 6.3V 1 1/2A £1.89. 6-0-6V 1 1/2A £2.35. 9-0-9V 1A £1.99. 12-0-12V 1A £2.49. 15-0-15V 1A £2.79. 30-0-30V 1A £3.59. 20V 2 1/2A £1.99. 9-0-9V 2A £2.60.

PRINTED CIRCUIT MATERIALS

PC etching kits — economy £1.70. Standard £3.82. 50 sq ins pcb 40p. 1 lb FeCl3 £1.05. Etch resist pena. Economy 45p. Dalo 83p. Small drill bit 20p. Laminate cutter 75p.

S-DECS AND T-DECS*


S-DeC £2.23. T-DeC £3.98. u-DeCA £3.97. u-DeCB £6.67. 16 diode adaptors — plan 89p. With socket £1.91. New S-dekit £4.95.

SINCLAIR PRODUCTS*

Cambridge Scientific programmable calculator £13.95. Prog. library £4.95. Mains adaptor £3.20. Cambridge Scientific £8.45. Oxford Scientific £10.60. PDM35 digital multimeter £25.95. Adaptor £3.24.

BI-PAK AUDIO MODULES

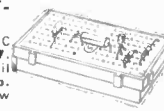S450 Tuner £21.95. AL60 £4.86. PA100 £14.95. MK60 audio kit £36.45. Stereo £6. £17.95. SPM80 £3.75. BMT80 £5.95. Send for free data.



JC12, JC20, JC40 AMPLIFIERS

A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 Watts £1.95. JC20 10 Watts £2.95. JC40 20 Watts £4.20. Send see for free data.



FERRANTI ZN414

IC radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send see for free data.

BATTERY ELIMINATOR BARGAINS

TV games power unit stabilized 7.7V 100mA £3.25. 3-way models with switched output and 4-way multi-jack — 3/4 1/2 6V 100mA £2.92. 6/7 1/2 9V 150mA £3.30. 100mA radio models with press stud connectors. 9V £2.85. 6V £2.85. 4 1/2V £2.85. 9V+9V £4.50. 6V+6V £4.50. 4 1/2V+4 1/2V £4.50. Cassette recorder mains unit 7 1/2V 100mA with 5 pin din plug £2.85. Fully stabilised model switched output of 3/6 7/2 9V 400mA stabilised £6.40. Car connector 12V DC input. Output 9V 300mA £1.80. Output 7 1/2V 300mA £1.80.

BATTERY ELIMINATOR KITS

Send see for free leaflet on range.

100mA radio types with press stud battery terminals. 4 1/2V £1.80. 6V £1.80. 9V £1.80. 4 1/2V+4 1/2V £2.50. 6V+6V £2.50. 9V+9V £2.50.

Cassette type 7 1/2V 100mA with din plug £1.80. Transistor stabilised 8-way type for low hum. 3/4 1/2 6V 7 1/2 9V 150mA £3.20. 1 Amp model £6.40. Heavy duty 13-way types 4 1/2 6 7 7 1/2 8 1/2 11 13 14 17 21 25 28 34 42V. 1 Amp £4.85. 2 Amp £7.95.

Car Converter kit. Input 12V DC output 6/7 1/2 9V DC 1A transistor stabilised £1.95. Stabilised power kits 3-18V 100mA £3.60. 3-30V 1A £9.95. 3-60V 1A £10.95. 3-60V 2A £13.95.

BULK BUY OFFERS

Minimum purchase of one item £10. SN76023N 79p. ZN414 84p. 4.43MHz crystals 65p. 741 8 diode 22p. NE555 8 diode 36p. Dalo pens 58p. 2N3055 53p. BD131 30p. BC107 7p. BC109 7p. BC212 8p. 1N4002 42p. Bridge rectifiers 200V piv — 1A 26p, 2A 33p. Electrolytics axial 200mF 40V 36p.

CUT PRICE TELETEXT

Labgear CM7026 ready to use, attractively cased complete unit which just plugs straight into the aerial socket of the set, giving full colour and requiring no modification to the TV. Remote control page selection £323.

Texas Instruments Tifex Module for the experienced 'do-it-yourself' man £120.

SWANLEY ELECTRONICS

DEPT. ETI, PO BOX 68, 32 GOLDSEL RD., SWANLEY, KENT BR8 8TQ

Mail order only. Please add 30p to total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked * and 11% on others. Official credit orders welcome.

24 HR. CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1kW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC. 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCB and full instructions £13.75

Special white box (56 x 131 x 71mm) with red acrylic window — undrilled £2.20 ready drilled for kit £2.50

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated touch plates. Complete with easy to follow instructions.

TS300K TOUCHSWITCH and DIMMER combined. ONE touchplate to switch light on or off. Brightness controlled by small knob. £5.20

TS300K — TOUCHSWITCH. TWO touch plates. One for ON, one for OFF. £4.00

TS300K — AUTOMATIC TOUCHSWITCH. ONE touch plate. Touch for ON and light stays on for preset time (variable from 2 secs to 3 1/2 mins). Ideal for stairs and hall £4.00

LD300K — 300W LIGHT DIMMER KIT. Replaces conventional light switches. £2.80

AY-5-1230 Clock Appliance Timer I.C. £4.85

LM3911 Thermometer/Temperature Control I.C. (with data) £1.00

NE555 Timer I.C. 8 pin diode 36p (3 for £1.00)

741 Op. Amp I.C. 8 pin diode 24p (5 for £1.00)

TRIAC BARGAINS

400V Plastic isolated tab 3A 63p

6 5A with trigger** 80p

8 5A** 79p

12A 84p

16A 105p

20A 165p

25A 190p

DIAC 21p

C106D 5A/400V SCR 50p

CMOS LOW PRICES

4000 18p 4012 18p 4023 18p 4077 45p

4001 18p 4013 51p 4025 18p 4501 20p

4002 18p 4015 91p 4040 97p 4510 150p

4007 18p 4016 51p 4049 50p 4516 150p

4011 18p 4017 91p 4050 50p 4519 56p

MINI MAINS TRANSFORMERS

6-0 6V 100mA 85p*

12-0 12V 100mA 95p*

OPTO ELECTRONICS

0.2" Red L.E.D. 10p

0.2" Green L.E.D. 21p

0.2" Yellow L.E.D. 25p

DL727 Dual 0.5" Display £1.50

C280 Polyester Capacitors 250V d.c. (values in uF). 01 4p; 022, .033, 047, 068 5p; 0.1 6p; 15 7p; 22 8p; 33 11p; 47 12p; 68 17p; 1.0 20p; 2.2 36p

RESISTORS. 33W 5% 22ohm to 10Mohm 1 1/2p

Push Button, push to make 20p

QUANTITY DISCOUNTS ON REQUEST

Add 8% (1 1/2%) V.A.T. plus 25p P&P. MAIL ORDER ONLY TO:

T.K. ELECTRONICS (ETI)

106 STUDLEY GRANGE ROAD, LONDON, W7 2LX

TRAMPUS



BARGAIN MONTH! POST FREE £5+

FREE 1978 CATALOGUE SALE LIST. MANY SURPLUS & CLEARANCE LINES. SEND S.A.E. DO YOURSELF A FAVOUR A SEMICONDUCTOR POWER HOUSE

TRAMPUS ELECTRONICS LTD. 58-60 GROVE ROAD, WINDSOR, BERKS. SL4 1HS. Telephone Windsor (07535) 54525

Fast service on ex stock product. Normally 24 hour turn around. Quality devices to manufacturers specifications. No minimum order charge except Barclaycard or Access by post or telephone £5 minimum. Send C.W.O. Post Free over £5. except invoiced or Credit Card orders. Otherwise add 20p post & packing. Add 8% VAT to items marked *. 12 1/2% VAT to unmarked items

LEDS 1/2 & 0.2 Dia

RED No Clip 9p*

Color LEDs all 12p*

DISPLAY 16p*

03 DL704. 2 & 707 2 59p*

0.6" DL742 2 £1.50*

TGS Gas Detectors £5*

CAPACITORS Ceramic 22pF to 0.5 5p

Electrolytic 1uF to 200 uF 7p

1000uF/25V 20p

Tantalums Only 15p ea

RESISTORS 1/4 W 25p

Presets 10p. Pots 25p

VERO 0.1 Matrix 59p*

2 1/2" x 3 1/2" 42p*. 3 1/2" x 5" 59p*

3 1/2" x 7 1/2" £2.50. 2 1/2" x 5" 50p*

On Board 6 1/4" £2.50*

Dalo PCB Pen 65p*

Nylon Board Copper 60p*

Tab FEC etch 1/2kg £1*

RS Bleeper 12V £1.50*

KNBS. Cheap 10p*

RELAY. Multi pole 12V £1*

Silicon grease satch £1*

Digital Clock IC £2

BULK BUY BARGAINS

FULL SPEC. PAKS. ALL £1 ea

PAK A 12xRED LEDES £1*

PAK B 5x741 8 Pin £1*

PAK C 4x2N 3055 90w £1*

PAK D 12xBC109 £1*

PAK E 13xBC182 £1*

PAK F 13x2N 3704 £1*

PAK G 7xBFY51 £1*

PAK H 7x2N3819E £1*

PAK J 6x2N 3053 £1*

PAL K 40xIN 4148 £1*

PAK M 4xPair NPN £1*

PNP 2A £1*

PAK N 50xOAB1/91 £1*

PAK P 20xPlastic 109 £1*

PAK R 14xBC107 £1*

PAK S 14xBC108 £1*

PAK T 10xNPN 2A 60V £1*

PAK U 4x1A 50V SCR £1*

PAK V 40x5MFD 10V £1*

PAK W 20 Electrolytics £1*

PAK X 4xLM301/14 £1*

PAK Y 20x2N3702 Type PNP £1*

NEW PAK X 4x555 £2*

REDUCED LINES ICs & TRANSISTORS

BC107	3p	OP12	50p*
BC108	8p	TIP 2955	65p*
BC109	8p	TIP 3055	55p*
BC109C	15p	2N 3055	45p*
BC177/8/9	20p	2N 3702/4	8p*
BC182/3/4	7p	2N 3819E	18p*
BD123/4	7p	2N 3820	38p*
BCY101/2	20p	2N 2546	50p*
80131/132	39p	2N 5457	50p*
MJ2955	£1.50*	Matching	+20p
MJE2955	£1*	MS BUSH	9p
MJE 3055	55p*	9s ADD	10p*

ZENERS 400MW 9p

DIODES: IN4148 914 5p

LINEARS

301/14 Pin	23p*	ICs	
308 0PA	£1*	7812	£1*
555	29p	7815	75p*
741/8	21p	7813	£1.49
747	89p	LM309IC	£1*
748/14	25p	LM380	89p
748/8	39p*	LM390	£1.55
748/5	£1*	LM3900	69p
7805	£1*	MC1310	£1
		ZN114 RX	75p

7400 TTL 12p

7401	8p	7490	33p*
7405	8p	74121	27p*
7413	27p	74123	50p*
7420	8p	74157	50p*
7430	5p	CMOS etc.	
7445	50p*	4001	18p*
7447	79p*	4011	18p*

FREE: 1978 CATALOGUE SALE LIST. SEND S.A.E. BARGAIN OFFERS!

THIS MONTH'S SNIPS. LIMITED STOCKS

Tuner Module Brand New Expensive ex music centre £22.50

MW/LW FM MPX Push Button £3.69

Tuning Gang Air spaced 0.360 39pft Hair Price £1 ea

B. BAMBER ELECTRONICS

DEPT. ETI, 5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE
Tel. ELY (0353) 860185 (Tues. to Sat.)

CASH WITH ORDER. (MINIMUM ORDER £2.00)

PLEASE ADD VAT AS SHOWN
POST PAID (UK ONLY), SAE WITH ENQUIRIES
CALLERS WELCOME BY APPOINTMENT ONLY

ALL BELOW — ADD 8% VAT

MAINS TRANSFORMERS, TYPE 15/300 240V input, 15V at 300mA output, £1.50 each
MAINS TRANSFORMERS, TYPE 45/100, 240, 220, 110, 20, 0V input, 45V at 100mA output, £1.50 each
MECHANICAL COUNTERS, 4 digit Resettable, 60p each
REVOLUTION COUNTERS, 000-999, 1 rev of spindle=10, 4mm spindle, 2 hole fixing, alloy body, good quality, 40p each
4-DIGIT P.O. TYPE PULSE COUNTERS, 24V DC, 500ohm coil. Size approx. 1" x 1" face, 4" deep, 25p each
SLOW-MOTION MOTORS, 120V 50Hz 1RPM. Size approx. 2" dia. 1 1/2" deep, with 1/8" spindle, 60p each, or 2 for £1.00
1 1/2 V DC MOTORS (Ideal for model makers, quite powerful), 50p each
6BW6 VALVES (BRAND NEW), 85p each, or 2 for £1.50
SUB-MINIATURE ROTARY SWITCHES, 4 x 5-way make contacts. Size approx. 3/8" dia. 1" deep, 3/16" spindle, 50p each
300p BEEHIVE TRIMMERS, Brand new, 4 for 50p
Min. 5p AIR SPACE TRIMMERS, approx. 1/8" square, 3 for 50p
Min. 5p COMPRESSION TRIMMERS, 1/2" x 5/16", 4 for 50p
SMITHS CLOCK MOTORS, 200-250V 50Hz 2 watts, 1 rev every 2 mins. 3 hole fixing, 1/8" spindle, £1.00 each

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES

Aluminium Boxes with Lids

AB10	5 1/4 x 4 1/2	60p
AB13	6 x 4 x 2	80p
AB14	7 x 5 x 2 1/2	£1.00
AB15	8 x 6 x 3	£1.30
AB16	10 x 7 x 3	£1.50
AB17	10 x 4 x 3	£1.30
AB25	6 x 4 x 3	£1.00

Vinyl Coated Instrument Cases with White Lower Sections Very smart finish

WB1	5 x 2 1/2 x 2 1/4	60p
WB2	6 x 4 1/2 x 1 1/4	£1.10
WB3	8 x 5 x 2	£1.60
WB4	9 x 5 1/2 x 2 1/2	£1.80
WB5	11 x 6 1/4 x 3	£2.00
WB6	11 x 7 1/2 x 3 1/2	£2.25
WB7	12 x 6 x 5 1/2	£2.60
WB853	8 x 5 1/2 x 3 1/2	£2.00

ALL BELOW — ADD 8% VAT

FULL RANGE OF BERNARDS/BABINI ELECTRONICS BOOK IN STOCK S.A.E FOR LIST

LARGE ELECTROLYTIC PACKS. Contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces, £3.00 per pack (+ 12 1/2% VAT)
MIXED COMPONENT PACKS. Containing resistors, capacitors, switches, pots, etc. All new, and hundreds of items, £2.00 per pack, while stocks last
PLUGS AND SOCKETS
BNC PLUGS (ex equip.), five for £1.50
N-TYPE PLUGS, 50ohm 60p each, 3 for £1.50
Greenpreer (GE300015) Chassis Lead Terminations (These are the units which bolt on to the chassis, the lead is secured by screw cap, and the inner of the core passes through the chassis.) 30p each, 4 for £1.00
PL250 Plugs (PTFE), brand new, packed with reducers, 75p each
SO239 Sockets (PTFE), brand new (4-hole fixing type), 60p each

VALVES
OOV03/20A (ex equipment) £3.00
OOV03/10 (ex equipment) 75p or 2 for £1.20
6BH6 (ex equipment), 2 for 50p
All the above valves are untested, except for heaters, and no guarantee of percentage of emission is given. Sorry, no returns.
MULLARD 85A2 85V STABILISER VALVES (brand new), 70p each or 2 for £1.20
6BW6 brand new 85p each or 2 for £1.50

TRANSISTORS
BFY51 Transistors, 4 for 60p
BYX38/300 Stud Rectifiers, 300V at 2.5A, for 60p
BOY72 Transistors, 4 for 50p
BSX20 (VHF osc/mult.), 3 for 50p
BC107 (metal can) 4 for 50p
BC108 (metal can) 4 for 50p
PBC108 (plastic BC108), 5 for 50p
BF152 (UHF amp/mixed), 3 for 50p
2N3819 Fet, 3 for 60p
BC148 NPN SILICON, 4 for 50p
BC158 PNP SILICON, 4 for 50p
BAY31 Signal Diodes, 10 for 35p
741C RCA OP Amps 4 for £1.00
SCRs 400V at 3A, stud type, 2 for £1.00
TIP2955 Silicon PNP power transistor, 60V at 15A, 90 Watts, Flat pack type, 2 for £1.50
GERMANIUM DIODES, approx 30 for 30p
1N4148 (1N914) diodes 10 for 25p

ALL BELOW — ADD 8% VAT

RED LEDs (Min. type), 5 for 70p
VIDICON SCAN COILS (Transistor type; but no data), complete with vidicon base, £6.50 each. Brand new
DIECAST BOXES: We still stock these but, owing to frequent price rises from our suppliers, and costly postal charges, it has been found impossible to publish up-to-date prices on these items. Please ring or write (with SAE) for latest mail order prices.
AEI CS108/R MICROWAVE DIODES, up to X-Band, max. noise figure 8.5dB at 9.375GHz, 80p each

PUSH-BUTTON TELEPHONES
A ten digit push-button intercom telephone with handset, finished in smart grey plastic. XSA equipment, but good condition. Only £2.50 each

SPIRALUX Tools for Electronics enthusiast... SAE for list

4MHz XTAL PACKS (10 assorted xtals between 4MHz and 5MHz). Our selection only £1.00 pack
ALU-SOL ALUMINIUM SOLDER (made by Multi-core), solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16SWG with Multicore flux with instructions, approx. 1m coil, 40p pack. Large reel £2.75

SOLDER SUCKERS (Plunger Type)
Standard Model, £5.50
Skirted Model, £6.00
Spare Nozzles, £6.00 each
MULTICORE SOLDER
1/8kg (1 lb.) 60/40 20 SWG on plastic reel, £3.00
WELLER WP600 Mains operated temperature control, soldering iron, £15.00
SPARE TIPS (for WP600). Two types available. TYPE CC7 (W600) Standard. TYPE AA7 (W600). Finer tip, £1.15 each
Slider Switches, 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p

A RANGE OF DRAPER TOOLS FOR THE ELECTRONICS ENTHUSIAST
(GOOD QUALITY, FULLY GUARANTEED)
MAINS TESTER SCREWDRIVERS, 100 to 500V. Standard size 50p. Large 70p.
RADIO PLIERS, 5 1/4" £1.60, 6 1/4" £1.80.
DIAGONAL SIDE CUTTERS, 6 1/4" £1.90
SMALL SIDE CUTTERS, LJ2 Standard £3.70
LJ7 (with wire holding device), £4.10
FLAT NOSE TOP CUTTERS, LJ1 £4.10
COMBINATION PLIERS, 6 1/4" £1.75, 7" £1.80

ALL BELOW — ADD 8% VAT

TIN SNIPS, 7", £2.25
SLIM OPEN ENDED SPANNER SETS, 0+3, 1+2, 2+4, 3+5, 4+6, 6+8BA SIZES, £1.15
MIDGET OPEN ENDED SPANNER SETS
0+1, 2+2, 3+5, 4+6, 6+8BA SIZES, £2.85 set of 5
4+4.5, 5+5.5, 6+6, 6+7, 8+9, 10+11 MM SIZES, £3.60 set of 6
MINIATURE WATCHMAKERS SCREWDRIVER SETS, £1.50 set of 5
MINIATURE FILE SETS, set of 6 £1.90. Set of 10 £3.25 (Round, flat, etc.)
TAP AND DIE SETS (18-piece) contain 1 each of 0, 2, 4, 6, 8 BA SIZES IN Dies, Plug taps, Taper Taps + American Type tap wrench, T-type tap wrench, Die Holder, £11.60
TUBULAR HACKSAW FRAMES (with Blade), £2.75
OSMOR REED RELAY COILS (for reed relays up to 1/4" dia. not supplied), 12V, 500ohm coil, 2 for 50p

PLASTIC PROJECT BOXES, with screws on lids (in black ABS) with brass inserts
Type NB1 approx. 3" x 2 1/4" x 1 1/2" 40p each
Type NB2 approx. 3 1/4" x 2 1/4" x 1 1/2" 50p
Type NB3 approx. 4 1/2" x 3 1/4" x 1 1/2" 60p each
Slider Switches 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p

ALL BELOW — ADD 12 1/2 % VAT

VARICAP TUNERS, Multitard type, ELC1043/05. Brand new £4.40
TV Plugs (metal type), 4 for 50p
TV Sockets (metal type), 4 for 50p
Line connectors (back-to-back skt.), 4 for 50p
3-pin Din Plugs, 4 for 50p
Din 3-pin Line sockets, 15p each
Din Speaker Skts, 2-pin, 4 for 30p
Dublier Electrolytics, 50µF 450V, 2 for 50p
Dublier Electrolytics, 100µF 275V, 2 for 50p
Plessey Electrolytics, 470µF 63V, 3 for 50p
TCC Electrolytics, 1000µF 30V, 3 for 60p
Dublier Electrolytics 5000µF 35V, 50p each
Dublier Electrolytics, 5000µF 50V, 60p each
ITT Electrolytics, 6800µF 25V, high grade, screw terminals, with mounting clips, 50p each
Resistor PKs, approx 300 pieces 1/2 to 2 watt types, mixed values, our selection, £1.00 each

A RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. SAE FOR LIST.

THE WORLD'S FINEST FM TUNER MODULES OK?

We've said it before, and we'll say it again; We offer the Largest and the Best range of FM Tuner modules in the UK, Europe and we believe in the World. (Please advise us if you know differently.) We gasp when we read the unsupported claims of other 'suppliers', describing things like deviation muting, which we have been offering in our 7030 FM IF system for ages. Long before most others gave it a thought. To read some adverts, you might imagine somebody had just discovered the wheel. Furthermore, we believe good signal processing is more important than rows of pretty lights and numbers, don't you?

ALL NEW CATALOGUE

To celebrate our new range of ICs, components, coils, filters, FM and AM modules etc., we are presenting an entirely new catalogue, which is free if you send an A4 SAE (15p stamp on it pse), and the front page from one of our old catalogues. This offer ceases on May 31st 1978, when the normal price of 45p will apply. The new catalogue contains radio and wireless features centred on our new developments with Sprague, Telefunken and RCA, with the TDA1083 MW/LW/FM/Audio all-in-one IC system, the TDA1062 4 stage IC tunerhead, the CA3189E IF system, the Hitachi HA11219 FM noise blanking system and other radical new technology announced in the past few months. We are certain this will be of great value and interest to anyone concerned with radio and RF design.

The rest of our new range includes resistors, capacitors and many items that now complete our range for the electronics enthusiast and designer. We naturally carry the very latest in radio semiconductors, and are pleased to report many new developments in the past six months, that are now readily available, with technical backup, from Ambit. But quite apart from our technical capability, we think you will find our prices attractive, and our product always first quality.

Examples from the range of components, modules etc.:
Resistors 1/4 watt types in E12 series, 1 ohm to 10M ohms (Mullard/Iskra/piher) 15p/10 Minimum order 10 per value please. Minimum resistor-only order £1.50
Ceramic plate and disc capacitors: only miniature and compact types eg. 10nF: 35p/10
CA3189E: RCA's new IF system, £2.75 inc. detector coil and 22uH choke
TDA1083: Sprague/Telefunken AM/FM/Audio IC. 800mW output max £2.55
TDA1062: Telefunken FM tunerhead IC, good for 200MHz, £2.75
Modules as previously advertised, plus these new ones: EF5803, 93189, EF5400, MPX decoder: 91196B: The superior HA1196 now with a 2W monitor amplifier, and optional adjacent or alternate channel notching facility, as well as a 55kHz low pass filter, pilot tone filters etc. £16.45
New from TOKO: CFM2 series 4 section ladder filters for 455kHz 6 & 12kHz versions £1.35 each, CFM2 2 section mechanical filters for 455kHz, same size as CFS series filters! Plus others.....



ambit INTERNATIONAL
2 GRESHAM ROAD BRENTWOOD ESSEX

ELECTRONICS TODAY INTERNATIONAL — APRIL 1978

The EF5400, a 4 stage varicap tunerhead, tuning 88-108MHz with a bias swing of just 2.8 volts DC. A single IC provides all functions, including PIN diode AGC drive, balanced mixer, RF amplifier. All this and edge connection too! £9.75 built.



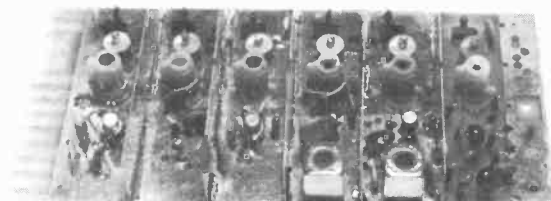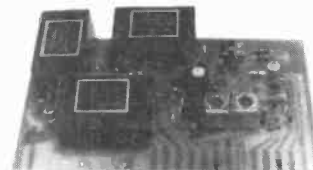Always in the leading group, here is Ambit's 73189 IF system, optional 2 or 3 pole linear phase IF filters, 2xMOSFET IF AGC stage, with the CA3189E. £16.25 built and aligned.




The EF5803 here is shown less the tinplate shielding can normally supplied
The EF5803: the ultimate? 2x low noise MOSFET RF stages with AGC, MOSFET mixer, very loose stage coupling for super high Q. Amplified local osc output. Used in conjunction with the 73189 system, provides 35dB S/N with a 0.63uV PD input. And all these modules are British Made. EF5803: £19.75.

Prices exclude VAT. Postage 25p per order. Catalogue (see text) 45p. Telephone (0277)216029. Parking outside the front of our building.

SECOND GENERATION INDUCTION BALANCE METAL DETECTOR

DESIGNED SPECIALLY
FOR THE HOME
CONSTRUCTOR

EASY
TO
BUILD

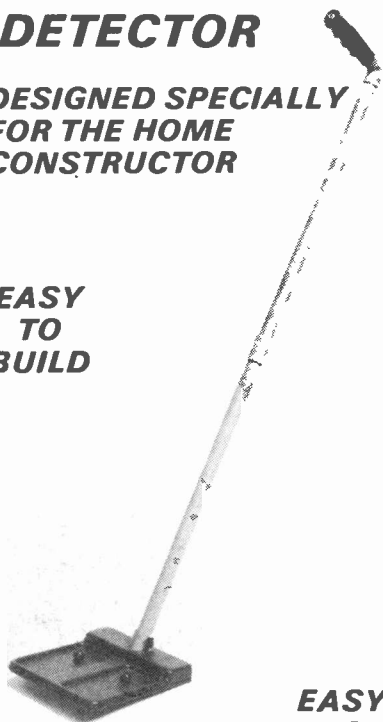

EASY
TO
USE

- A second generation Induction Balance system with improved Variable-Tone detection.
 - Designed by professionals for easy assembly by amateurs but with very good performance.
 - The search coils are fully assembled and adjusted for you.
 - Coils pre-assembled and tested wedge shaped search field
- Uses include:
- ★ Treasure hunting — it's amazing what you can find in the garden or on the beach.
 - ★ Finding lost metallic items.
 - ★ Locating waterpipes and cables under floorboards on in walls.
 - ★ Checking old timber for nails before cutting, etc., etc., etc., etc.

KIT - COMPLETE WITH PRE-ASSEMBLED SEARCH COILS

£16.50

Plus £1-00p+p Plus £1-32 VAT

ASSEMBLED & TESTED

£22.50

Plus £1-00p+p Plus £1-80 VAT

Communication Measurement Ltd
15 MALLINSON OVAL, HARROGATE, YORKS.


GREENBANK CUT PRICE CMOS

Cut prices for Amateur users and Export only. Note: Industrial Users — No % discount available on these prices, instead use franchised distributors standard prices, list available on request. Mostly Motorola, RCA

4000	15p	4050	52p	40107	60p	4514	£2.65
4001	17p	5051	75p	40108	£3.30	4515	£2.99
4002	17p	5052	75p	40109	£1.02	4516	£1.06
4006	£1.05	4053	75p	40181	£3.30	4517	£3.82
4007	18p	4054	£1.20	40182	£1.40	4518	£1.02
4008	92p	4055	£1.34	40182	£1.40	4519	51p
4009	50p	4056	£1.34	40183 TMA	£1.40	4520	£1.06
4010	50p	4057	£25.70			4521	£1.06
4011	19p	4059	£4.80	40194	£1.10	4522	£1.06
4012	18p	4060	£1.15	40257	£1.40	4524	N/S
4013	55p	4061	£15.87	4160	£1.06	4526	£1.06
4014	99p	4062T	£10.00	4161	£1.06	4527	£1.52
4015	95p	4063	£1.09	4162	£1.06	4528	99p
4016	52p	4064	N/S	4163	£1.06	4529	£1.14
4017	99p	4065	N/S	4174	£1.06	4530	85p
4018	99p	4066	57p	4175	95p	4531	£1.45
4019	60p	4067	£3.80	4194	£1.17	4532	£1.27
4020	£1.02	4068	22p	4408	£6.59	4534	£5.13
4021	94p	4069	22p	4409	£6.59	4536	£3.69
4022	96p	4070	22p	4410	£5.75	4537L	£13.23
4023	20p	4071	21p	4411	£3.58	4538	£1.25
4024	76p	4072	21p	4412N	£17.14	4539	91p
4025	19p	4073	21p	4412L	£12.82	4541	£1.14
4026	£1.80	4075	23p	4415V	£7.50	4543	£1.90
4027	35p	4076	£1.05	4415F	N/S	4549	£3.69
4028	81p	4077	22p	4419	£2.66	4552	£10.55
4029	£1.08	4078	21p	4422	£5.00	4553	£3.87
4030	58p	4081	22p	4431	TBA	4554	£1.19
4031	£2.30	4082	21p	4433	£11.32	4555	78p
4032	£1.00	4085	74p	4435	£7.93	4556	78p
4033	£1.45	4086	73p	4440L	£11.58	4557	£3.86
4034	£1.96	4089	£1.50	4450	£2.67	4558	£1.14
4035	£1.20	4093	63p	4461	£2.67	4559	£3.69
4036	£2.45	4094	£1.90	4452	TBA	4560	£1.84
4037	£1.00	4095	£1.05	4480FP	£6.54	4561	65p
4038	£1.06	4096	£1.05	4480VP	£4.92	4562	£5.33
4039	£2.45	4097	£3.72	4700	£1.75	4566	£1.59
4040	£1.05	4098	£1.10	4501	17p	4568	£2.38
4041	85p	4099	£1.90	4502	81p	4569	£2.57
4042	81p	40061	N/S	4503	75p	4572	25p
4043	94p	40100	2.50	4505	£5.71	4580	£5.74
4044	90p	40101	£1.61	4505	51p	4581	£2.62
4045	£1.45	40102	£2.12	4507	35p	4582	98p
4046	£1.30	40103	£2.12	4508	2.48	4583	76p
4047	99p	40104	£1.00	4510	£1.29	4584	£1.50
4048	58p	40105	£1.06	4511	£1.38	4585	£1.01
4049	52p	40106	71p	4512	81p		

74C00 Series (National)

74C00	26p	74C86	60p	74C173	£1.21	74C810	£7.20
74C02	26p	74C89	£4.65	74C174	£1.21	74C814	£1.90
74C04	26p	74C90	92p	74C192	£1.40	74C818	£2.80
74C08	26p	74C93	92p	74C193	£1.40	74C820	£11.83
74C10	26p	74C95	1.31	74C195	£1.31	74C821	£11.83
74C14	£1.51	74C107	£1.31	74C200	£7.20	74C825	£8.28
74C20	26p	74C150	£4.17	74C221	£1.50	74C826	£8.28
74C30	26p	74C151	£2.63	74C301	74p	74C827	£8.28
74C32	26p	74C154	£3.83	74C302	74p	74C828	£8.28
74C42	£1.20	74C157	£2.36	74C303	74p	80C35	£1.20
74C48	£2.37	74C160	£1.40	74C304	74p	80C36	92p
74C73	74p	74C161	£1.40	74C305	£7.71	80C37	97p
74C74	63p	78C182	£1.40	74C306	74p	80C38	92p
74C76	74p	74C163	£1.40	74C307	74p	88C29	£8.21
74C83	£1.97	74C164	£1.31	74C308	2.63	88C30	£8.21
74C85	£1.97	74C186	£1.31	74C309	£1.74		

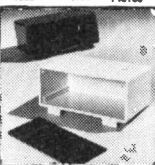

TIMEBOX. Digital Clock Case, 56 x 131 x 71.5 mm with red acrylic window. Choice of case colour, white, red, orange, blue. £2.20.

LED DISPLAYS FND 500/507 Jumbo 0.1" 7-segment £1.30 FND 357 0.35" c.a. 7-segment £1.40	QUARTZ CRYSTALS 32.768 KHz (Motorola) £4.50 32.768 KHz (Equivalent) £2.05 100 KHz/200 KHz £2.05 1 MHz/2 MHz/2.097 MHz/3.268 MHz/1.843 MHz £3.23 4.194 MHz/5.0 MHz/5.12 MHz/10.0 MHz £3.62 4.43 MHz £1.50 (Enquire for other frequencies)
"E" LED DISPLAYS. Class II devices, but fully guaranteed by us for 'even' segment brilliance, etc. — money back or exchange if not satisfied. DL-704 0.3in cc 85p DL-707E 0.3in cc 85p DL-728E 2 x 0.5in cc £2.00 DL-727E 2 x 0.5in cc £2.00 DL-750E 0.6in cc £1.80 DL-747E 6in ca £1.80	TIMER ICs NE 555/556 36p/72p
LIQUID CRYSTAL DISPLAY 4 x 0.5in digital 40 pin DIL £9.83	OP-AMPS CA 3130 (COS/MOS) 94p CA 3140 (BI MOS) 95p 741 Mindip 22p
CMOS CLOCK CHIP 1½ volt battery operated to suit our LCD. 40 pin DIL 11440 £11.58	DIL SOCKETS B/14/16 pin 10p/12p/13p
CLOCK CHIPS AY-5-1224A £3.50 MK 50253 £5.50 MK 50362/50366 £6.95	SOLDERCON PINS 100 50p 1000 £3.50
SIX DECADE COUNTER MK 50395/6/7 £9.95 (Quantity prices available)	"VEROBOARD" 0.1" Pitch with copper strips 2½" x 1" (pack of five) 52p 2½" x 3¼" 36p 2½" x 5" 43p 2½" x 17" £1.34 3¼" x 3¼" 43p 3¼" x 5" 48p 3¼" x 17" £1.75 4.7" x 17.9" £2.22
SC/MP MICROPROCESSOR ISP-8A 500D (PMOS) £12.00 ISP-8A 600N (NMOS) 5v £10.00	0.1" Plain board (no strips) 28p 3¼" x 2½" 45p 3¼" x 5" £1.28 3¼" x 17.9" £1.50/£5.00 V-Q DIP board 89p DIP breadboard £2.10 Spot face cutter 69p Pin insertion tool 89p
MEMORIES, SWEET MEMORIES (RAMS) 2101/2N £3.00 2102/2N £3.00 2111/2N £3.00 2112/2N £3.00	

CATALOGUE. Free on request. Terms CWO. Add VAT to all prices at 8%. Post, etc. UK 25p (+ 2p = 27p) per order. Export add 75p (Europe), £2.50 elsewhere, no VAT. Polys, universities, govt. depts., etc., can telephone their orders for immediate despatch.

GREENBANK ELECTRONICS (Dept. T4E)
92 New Chester Road, New Ferry
Wirral, Merseyside L62 5AG
England. Tel. 051-645 3391

NOW IT IS HERE



The new liquid crystal display with Alarm!

£59.95
inc VAT & PP

This beautifully finished watch in stainless steel with adjustable stainless steel bracelet and the time is constantly on display

TIME!

Shows hours minutes seconds

DATE!

Shows date month & day of the week in Alpha numeric

ALARM!

The alarm is simple to operate and set and easy to check, once set and activated it bleeps penetratingly for 15 seconds.

REMINDER!

If you want a reminder just press before 15 seconds are up and it will go off again in 5 minutes to call you. This you can keep doing till you want to get up!

CALENDAR!

Automatic calendar for 29, 30, 31 day month.

BACK LIGHT!

For night viewing

There is nothing quite like it on the market and at £59.95 inc VAT it is fantastic value. Full 12 months manufacturers guarantee.

We also offer you 14 days free trial and if you are not entirely delighted just return it and we will return your money.



LCD SOLAR STOP- WATCH

£59.95
inc. VAT and P.P.

THE solar watch is an electronic marvel, the solar cells take their energy from light therefore you never need change batteries, it just goes on and on. **AN ASTOUNDING WATCH!** Space age technology has brought this marvel to you at a price you can afford.

TIME!

Shows hours, minutes, seconds.

CALENDAR!

Shows month and date alpha numeric, and automatic calendar for 29, 30, 31 day month.

STOP WATCH!

Hours, minutes, 10th second.

BACK LITE!

for night viewing so you can see display in the dark. Made from stainless steel with adjustable matching st/st. bracelet.

5 YEARS GUARANTEED! Manufacturer guaranteed and we also offer you 14 days free trial period.

Just return it if you are not entirely satisfied, and we will refund you your money.

Just send cheque or postal order for **£59.95** to:

TRITON

57 Bridge Lane, London, NW11
01-458 4755

Style may vary slightly from picture.
(MAIL ORDER ONLY)

15 - 240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV, Ceramic Pick-up 30mV, Tuner 100mV, Microphone 10mV, Auxiliary 3-100mV, input impedance 47k Ω at 1kHz

OUTPUTS: Tape 100mV, Main output 500mV R.M.S.


ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz, Bass \pm at 100Hz

DISTORTION: 0.1% at 1kHz, Signal/Noise Ratio 68dB

OVERLOAD: 38dB on Magnetic Pick-up, **SUPPLY VOLTAGE** \pm 16-50V

Price £5.22 + 65p VAT P&P free

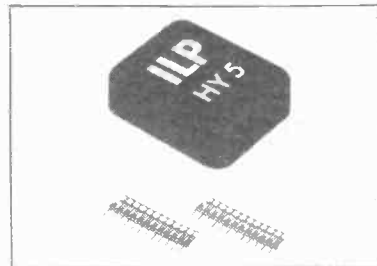HY5 mounting board B1 48p + 6p VAT P&P free.



HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of 1 C, heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build


SPECIFICATIONS:

OUTPUT POWER: 15W R.M.S. into 8 Ω , **DISTORTION:** 0.1% at 15W

INPUT SENSITIVITY: 500mV, **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB

SUPPLY VOLTAGE \pm 18V

Price £5.22 + 65p VAT P&P free.

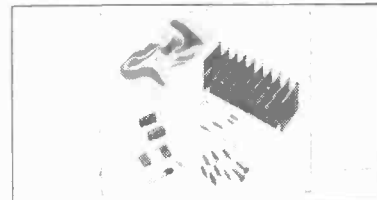

HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS: **INPUT SENSITIVITY:** 500mV

OUTPUT POWER: 25W RMS in 8 Ω **LOAD IMPEDANCE:** 4-16 Ω , **DISTORTION:** 0.04% at 25W at 1kHz

SIGNAL/NOISE RATIO: 75dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB

SUPPLY VOLTAGE \pm 25V, **SIZE:** 105.50 x 25mm

Price £6.82 + 85p VAT P&P free



HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

SPECIFICATIONS:


INPUT SENSITIVITY: 500mV

OUTPUT POWER: 60W RMS into 8 Ω , **LOAD IMPEDANCE:** 4-16 Ω , **DISTORTION:** 0.04% at 60W at 1kHz

SIGNAL/NOISE RATIO: 90dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB, **SUPPLY VOLTAGE** \pm 35V

Size: 114 x 50 x 85mm

Price £15.84 + £1.27 VAT P&P free.

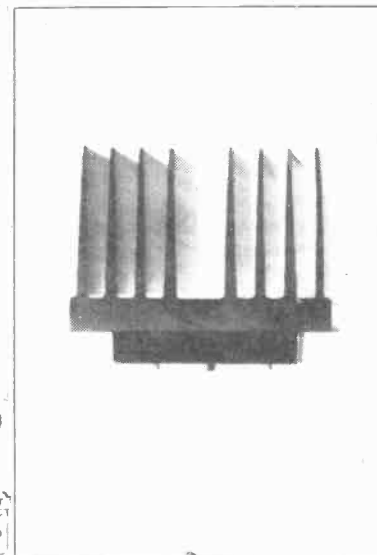

HY200 120 Watts into 8 Ω

The HY200, now improved to give an output of 120 Watts, has been designed to stand the most rugged conditions, such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Loadline protection — Integral Heatsink — No external components

APPLICATIONS: Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address

SPECIFICATIONS:

INPUT SENSITIVITY: 500mV

OUTPUT POWER: 120W RMS into 8 Ω , **LOAD IMPEDANCE:** 4-16 Ω , **DISTORTION:** 0.05% at 100W at 1kHz

SIGNAL/NOISE RATIO: 96dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB, **SUPPLY VOLTAGE** \pm 45V

SIZE: 114 x 100 x 85mm

Price £23.32 + £1.87 VAT P&P free.

HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components

APPLICATIONS: Public address — Disco — Power slave — Industrial


SPECIFICATIONS:

OUTPUT POWER: 240W RMS into 4 Ω , **LOAD IMPEDANCE:** 4-16 Ω , **DISTORTION:** 0.1% at 240W at 1kHz

SIGNAL/NOISE RATIO: 94dB, **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB, **SUPPLY VOLTAGE** \pm 45V

INPUT SENSITIVITY: 500mV, **SIZE:** 114 x 100 x 85mm

Price £32.17 + £2.57 VAT P&P free.

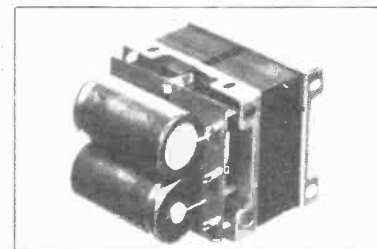

POWER SUPPLIES

PSU36 suitable for two HY30's £5.22 plus 65p VAT P/P free
 PSU50 suitable for two HY50's £6.82 plus 85p VAT P/P free
 PSU70 suitable for 2 HY120's £13.75 plus £1.10 VAT P/P free
 PSU90 suitable for one HY200 £12.65 plus £1.01 VAT P/P free
 PSU180 suitable for two HY200's or one HY400 £23.10 plus £1.85 VAT P/P free.

B1 48p plus 6p VAT

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd
 Crossland House
 Nackington, Canterbury
 Kent CT4 7AD
 Tel (0227) 63218

Please Supply _____
 Total Purchase Price _____
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number _____
 Name & Address _____
 Signature _____

MINI-ADS & CLASSIFIED

SECURITY PRODUCTS

Designed for the Do-It-Yourself market. Easily installed. Full instructions supplied. As supplied to the trade.

- Magnet and Reed switch Flush 65p
- Surface 70p
- Pressure Mats Large £1.20
- Stair 80p
- Bells and Sirens from £5.00
- Bell Covers — Metal - Plastic coated £5.00
- Window Foil self adhesive £2.20
- Foil Blocks 15p
- Door Loops complete 70p
- Key Switches top grade £2.50
- Control panels from £18.75
- Radar, Infra-Red, and many other items available. Send for details.

Please add 12½% VAT + £1 P&P

STRATHAND SECURITY

44 St Andrews Sq
Glasgow G1 5PL
041-552 6731 or 2

PRINTED CIRCUITS and HARDWARE


Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components. Full range of ETI printed circuit boards, normally ex-stock, same day despatch at competitive prices. P.C. Boards to individual designs. Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES MASONS ROAD STRATFORD-ON-AVON WARWICKS. Tel. 4879

LOW COST BOXES

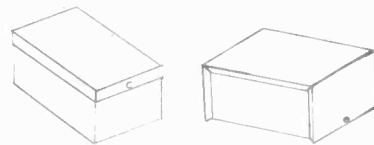

AND INSTRUMENT CASES

Aluminium box with lid and screws	2 Section case. Black pvc coated top and aluminium base	L	W	H	Price
3x2x1					42p
4x3x1½					49p
4x3x2		6x4½x2			£1.25
6x4x2		6x4x3½			£1.37
6x4x3		8x5½x2½			£1.50
8x6x2		10x6½x3			£1.95
8x6x3					1.08p

all prices incl. p&p

Sheet aluminium standard and cut to size, self-tapping screws, nuts bolts and washers. Pamphlet on our full range of cases supplied with every order or send a stamped self addressed envelope to **HARRISON BROS., P.O. Box 55, Westcliff-on-Sea, Essex.** Manufacturing service of sheet metal parts for trade; send drawing and s.s.a.e. for quotation.

ETI P.C.B.'s

Buy it with Access

Available for all ETI projects from day one of ETI, phone your order

SPECIAL OFFER—Single sided Pax PCB mat, four off, 4¾" x 6½", 99p all up

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD · Tel: 01-891 1923

P.C.B.'s

Standard or 'FR-Glaxep' fibreglass P.C.B.'s for ETI projects supplied tinned and drilled.

E.T.I. 541	68p	3 Channel tone control	63p
E.T.I. 549	77p	Digital Therm	
S68 VDUa (Mod)	255p		112p
S68 VDUb (Mod)	249p	Clock A	97p
S68 Mainframe	81p	Clock B	197p
PSU	226p	Compana	152p
S68 CPU	193p	Rev Monitor	89p
S68 TTY		Freezer alarm	46p

PLUS Special Offers now valid till Mar. '78.

Item 1: Full set S68 pcbs (VDU a & b, PSU, CPU) only £6.75 per set.

Item 2: ETI 804 TV Game, £1.00 each


Item 3: ETI 480 + 480 PSU, £1.90 per pair

All prices shown include VAT. Add 20p post & packing

P.C.B.s also available for this month's ETI projects. Send SAE for full list of available boards

TAMTRONIK LIMITED 217 TOLL END ROAD, TIPTON, WEST MIDLANDS DY4 0HW Telephone 021-557 9144

BARGAIN FOR ELECTRONIC HANDYMAN

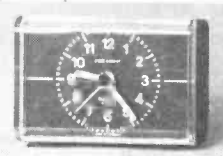

Size 95 x 65mm

1977/78 model 4MHz quartz alarm, made in the Black Forest by Kienzle. Offered as new, unused, but with slightly marked cases.

Ideal for personal use or electronic experimentation.

Recommended retail price £18.95.

Offered at £9.50 inc. VAT with normal movement guarantee while stocks last.

Prescott Clock & Watch Co. Ltd.
Prescott House, Humber Road
London NW2 6ER, England
Telephone: 01-452 9871



NEW GENTS LED GOLD PLATED BRACELET WATCHES

Swiss 10 micron gold plated case.
Hughes 786,432 Hz
5-Function module.
Mineral crystal glass.
Battery access hatches

Exceptional offer only to readers of E.T.I.

Not to be confused with many electronic so-called bargains.

Retail value £69.95 but very slight marks on the bracelets and some cases enables us to offer a limited quantity at £19.95 inc. VAT.

To be sold boxed, unused, in good working order but without guarantee; suitable for your own wear or electronic experimentation.

Offered subject to being unsold.

PRESCOTT CLOCK & WATCH CO. LTD.
Prescott House, Humber Road
London NW2 6ER, England
Telephone 01-452 9871

HI-FI BARGAINS

Special low prices for repair yourself (RY) Units

	Full Price	RY Price*
20W stereo Hi-fidelity Amp	£52.00	£26 P&P £1.50
Hi-fi stereo cassette Deck	£51.00	£36 P&P £1
25W stereo amp, plus turntable in case	£123.00	£60 P&P £2.50
10W tuner amp plus auto-change in case	£125.00	£60 P&P £2.50
70W speaker system full hi-fi spec. (carries full guarantee)	£195.00 pr	£95 pr. P&P £3

Range of repaired Videotone speakers at keen prices fully guaranteed. Send for list.

ALL PRICES INCLUDE VAT

The repair yourself (RY) items are brand new and complete with only minor faults. Full spares are available at low prices and there is a better than 75% chance of the unit being perfect.

These are incredible bargains to the enthusiast with limited funds.

ELBAR INDUSTRIES
7 Cheriton Avenue, Bromley, Kent
Telephone: 01-690 1916

BARGAIN BUYS. 1702A EROMS, £3.50 each + 15p post and packing. LM309K 5V Regulators. 85p each + 15p post and packing. DID's VDU's, to clear, £110. One VDU with logic fault, £60. Carr. by arrangement. Manual available. Dane Services, 2 Lupin Close, Hinckley, Leics, LE10 2UJ.

VALVES — RADIO, T.V., INDUSTRIAL, AND PROJECTOR LAMPS. 1930 to 1978. 4,000 types in stock. Many obsolete. List 30p. Postal export service. Access & Barclaycard. We wish to purchase new and boxed valves, also projector lamps. Cox Radio (Sussex) Ltd., Dept. ETI, The Parade, East Wittering, Sussex. West Wittering 2023 (STD Code 024366).

0.5" LED DIGITAL CLOCK Module (MA1012) £5.50. Postage 15p. Just add transformer and switches. Panel with buzzer and switches £1 extra. Has repeater alarm/snooze/sleep/radio timer features. SAE free details. Mr Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

THIS SECTION IS A PRE-PAYMENT SERVICE ONLY

MINI-ADS: 3 1/4" x 2 1/8", 1-3 £31, 4-11 £29, 12 or more £28 per insertion. CLASSIFIED DISPLAY: 15p per word. Minimum 25 words. No P.O. Box Numbers can be accepted without full address. Enquiries to: Advertising Department, 01-437 5982. 25-27 Oxford Street, London W1R 1RF.

WATCH BATTERIES SUPPLIED for 60p each + 15p P&P. All types available. Please indicate battery type. Hayes Audio, 44 North Crescent, London N3.

Z80 MICROPROCESSOR FAMILY: Z80CPU £20.00, Z80P10 £13.50, Z80CTC £13.50. All include Post/Packing U.K. only. Crowan & Wald Ltd., Manor Mill, Crowan, Praze, Camborne, Cornwall.

NEW QUALITY STEREO AMP CHASSIS. 60w (RMS). Protected 3Ω min. 0.03% THD, 12/30V Wkg. 20 trans., din socks, controls: Select, V/C, etc. Boxed, data, £9.95 (inc.). K. Lawrence, 1 Regent Road, Ilkley, W. Yorks.

ICL LINE PRINTER ASCII coded TTL input. Full documentation £50. Three MCM 6810 static rams £10. Expertise in 6800 Microcomputer Building, trouble shooting, programming. 01-960 2042.

PLATINUM, GOLD, SILVER, etc. etc. etc. Top London prices.
DOUG HOLDEN
Shore Road, Perth
Tel. 24137 or 24544

FREE CATALOGUE/ORDER FORM

SEND S.A.E

Send stamped addressed envelope for catalogue/order form and up to four priced lists of components for ETI projects from January, 1978. Examples from Ace Range.

741 ONLY 30p	555 ONLY 50p	TIL209 ONLY 15p	IN4001 ONLY 5p
----------------------------------	----------------------------------	-------------------------------------	------------------------------------

All prices include VAT. P&P FREE over £2.

Name _____
Address _____

Get an ACE up your sleeve!

ACE MAILTRONIX LTD
Dept. ETI Footstall Street
Wakefield, W. Yorkshire WF1 5JR

POLYPROPYLENE TRAYS

Ideal for use as storage trays for small components or as PCB etching trays. 8 3/4" x 5" x 2" deep, orange colour. 10 off 25p each, 100 off 20p each, 500 off 15p each, 1000 off 12p each, 5000 10p each.

**174B High Street, Skelmersdale
Lancashire WN8 8AF**

PLEASE MENTION ETI WHEN REPLYING TO ADVERTS

ADVERTISEMENT INDEX

Ace	89	ILP	4, 60, 87	R.F. Equipment	59
Airamco	76	Integrated Circuits		Science of Cambridge	65
Ambit	85	Unlimited	19	Service Trading Co Ltd	28
Arrow Electronics	90	Jade Computer Products		Sintel	80
Audio Electronics	41	35, 61	Sentinel Supply	84
Bamber	85	Jayen	76	Sterling Sound	66
Baron	21	Kramer	55, 76	Stevenson C.N.	90
Baydis	21	L.B. Electronics	55	Stuart-Bruges	59
Bi-pak	5	Lewis Radio	55	Swanley	84
Bywood	6	Lynx Electronics	59	Technalogics	80
Cambridge Learning	60	Maplin	92	Technomatic	82
Chiltmead	27	Marshall's	12	Teleplay	36
Chromasonics	72	Metac	42	Tempus	18, 22
Communications		Minikits	22	T.K. Electronics	84
Measurement	86	Monolith	18	Trampus	84
Crimson Elektrik	90	Mountaine	18	Tritron	18, 40, 86
E.D.A.	10	Nicholls E.R.	76	Vero	64
Electrovalue	82	Northern Radio Society	26	Videocraft	75
Gould Advance	74	Page Digital Electronics	64	Videotime	18, 58
Greenbank	86	Powertran	2	Watford	91
Greenweld	78	Progressive Radio	55	Wilmslow Audio	80
Henry's Radio	8, 82, 90	Rastra Electronics	41	Xeroza Radio	76

LEADER Electronic Kits

Digital Clock Kits

Available in 24 hour version (Kit No. LCK101) or 12 hour version (Kit No. LCK201)
0.5" High brightness Red LED display, Teak case with Optical grade red perspex front, Fast & slow reset, 240V 50 Hz. Modular construction, Full instruction booklet.

Rec. Retail **£13.99** inc. VAT/P&P (Ex. VAT **£12.95**)



Bench Power Supply LPU102

Variable voltage power supply kit with 5 - 30V DC, at 1 Amp. Featuring unique Fairchild regulator chip, (as featured in E.T. Magazine), Fully drilled & painted case/chassis, Meter, all parts, Full instruction booklet

Rec. Retail **£18.75** inc. VAT/P&P (Ex. VAT **£17.36**)



Laboratory Power Supply LPU103

Excellent power supply design featuring exceptional regulation, Zero to 30 volt and Zero to 1 Amp variable output with variable limiting in two ranges 0 - 100mA & 0 - 1A. Output meter reads both current & voltage. System can stand up to 2 hours in full short circuit condition. Fully punched, plated & painted case/chassis, front panel decal, Building manual/circuits etc.


Rec. Retail **£29.99** inc. VAT/P&P (Ex. VAT **£27.77**)



Test Bench Oscillator LTO104

Sine wave test oscillator featuring, Output variable 0 - 1 volt between 15 Hz to 30 kHz in four ranges 600 Ohm output impedance, Max. 1% distortion at 1 kHz. Fully portable, (uses 2 x PP3 batteries - extra)

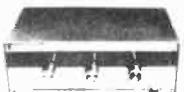Rec. Retail **£7.99** inc. VAT/P&P (Ex. VAT **£7.40**)



"LEADER" Electronic kits enable even the inexperienced constructor to produce equipment of excellent appearance through our policy of providing Comprehensive manual of building instructions, Fully finished cases/chassis including all necessary drilling, punching, plating, painting, Screen printed front panel decals with all lettering etc. Matching instrument knobs. And most of all - ALL PARTS to the last nut & bolt.

"LEADER" Electronic kits are distributed by Arrow Electronics Limited, Leader House, Copfold Road, Brentwood, Essex. Tel: 0277 219435 Telex 99443

NEW LOW PRICES!

Due to massive purchases, in many cases direct from the manufacturer we are now able to offer TTL and CMOS at considerably reduced prices. We stress that all devices are brand new and full specification from leading manufacturers only (Texas, National, ITT, Fairchild, etc.). Quantity discount regardless of mix 25+ 10%, 100+ 15%, 1000+ 20%.

TTL	12p	13p	45p	60p	75p	85p	90p	100p	110p	130p	150p	180p	200p	220p	250p	300p	350p	400p	450p	500p	550p	600p	650p	700p	750p	800p	850p	900p	950p	1000p						
7400	7451	74125	74185	4028	70p																															
7401	7453	74126	74186	4029	80p																															
7402	7454	74128	74188	4030	90p																															
7403	7460	74132	74190	4033	110p																															
7404	7470	74141	74191	4035	110p																															
7405	7472	74142	74192	4040	90p																															
7406	7473	74143	74193	4041	80p																															
7407	7474	74144	74194	4042	75p																															
7408	7475	74145	74195	4043	85p																															
7409	7476	74147	74196	4044	85p																															
7410	7480	74148	74197	4049	45p																															
7411	7481	74150	74198	4050	45p																															
7412	7482	74151	74199	4051	88p																															
7413	7483	74153	CMOS	4052	88p																															
7414	7484	74154	60p	4053	88p																															
7416	7485	74155	63p	4055	100p																															
7417	7486	74156	63p	4060	100p																															
7420	7489	74157	63p	4066	50p																															
7421	7490	74159	170p	4068	25p																															
7422	7491	65p	80p	4069	20p																															
7423	7492	45p	80p	4070	20p																															
7425	7493	35p	80p	4071	20p																															
7426	7494	80p	80p	4072	20p																															
7427	7495	55p	90p	4073	20p																															
7428	7496	62p	90p	4075	20p																															
7430	7497	240p	100p	4076	110p																															
7432	74100	95p	270p	4078	22p																															
7433	74104	40p	170p	4081	19p																															
7437	74105	40p	400p	4082	20p																															
7438	74107	28p	120p	4083	20p																															
7440	74109	45p	90p	4084	20p																															
7441	74110	46p	70p	4085	20p																															
7442	74111	70p	90p	4086	110p																															
7443	74116	160p	90p	4087	100p																															
7444	74118	82p	120p	4088	95p																															
7445	74119	130p	110p	4089	110p																															
7446	74120	82p	92p	4090	100p																															
7447	74121	26p	195p	4092	110p																															
7448	74122	40p	75p	4093	95p																															
7450	74123	55p	120p	4098	105p																															

555 27p 741 20p LM380 76p

Prices VAT inclusive. Please add 20p for carriage. Send large SAE for our more detailed list containing semiconductors, resistors, capacitors, etc. Overseas postage at cost.

C. N. STEVENSON (ET6)

22 Tiverton Drive, London SE9 2BY, England

NASCOM 1 Microcomputer for the Hobbyist

THE ONLY COMPLETE MICROCOMPUTER
AVAILABLE TO THE HOME CONSTRUCTOR

FEATURES:

- ★ Supplied in Kit Form for Self-Assembly
- ★ Full documentation supplied
- ★ Includes Printed Circuit Board
- ★ Full Keyboard included
- ★ Interfaces to Keyboard, Cassette Recorder & T.V.
- ★ 2K x 8 RAM
- ★ 1K x 8 Eprom Monitor Program
- ★ Powerful Z80 CPU, Mostek
- ★ 16 line x 48 Character Display Interface to standard, unmodified T.V. set
- ★ On board expansion to 2K x 8 Eprom
- ★ On Board Expansion Facility for Additional 16 Lines I/O
- ★ Total expansion to 256 Input Ports and 256 Output Ports

SOFTWARE FEATURES:

- ★ 1K x 8 Nasbug Program in Eprom
- ★ Provides 8 Basic Operator Commands including single step
- ★ Expandable Software System via additional user Programs in Ram of Eprom

Manuals
Separately
£3.50

Complete Kit's

£197.50
+VAT 8%
POST £2.50

Sole Appointed
London
Stockists


After: sales service available

HENRY'S
RADIO

All mail to: Henry's Radio 404 Edgware Rd, London W2

LONDON W2. 404 6 Edgware Road. Tel: 01-723 1008

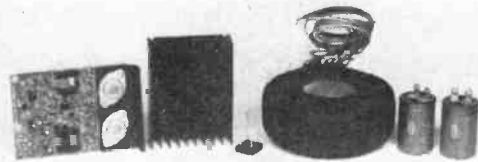TWO NEW SUPERMODULES 170W INTO 4 OR 8 OHMS



By popular demand we have designed higher powered versions of our well known modules. The CE 1704 which gives 170W into 4 ohms and the CE 1708 which gives 170W into 8 ohms are physically similar to the original types and have the same combination of compatible performance features which makes CRIMSON amplification audibly superior to the competition and the only choice if you have an ear for music. We have also produced suitable power supplies which again use our superb TOROIDAL TRANSFORMERS, only 50mm high, with a 120-240 primary and single bolt fixing. Write of phone for more information and biased opinions.

	Home	Europe	T.H.D.	Typically < 0.2% any power, 1kHz, 8 ohms
POWER AMPLIFIER MODULES				
CE 608 60W/8 ohms 35-0-35V	£16.30	£16.60		

WATFORD ELECTRONICS

33 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDERS, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 30p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. SEND S.A.E. FOR OUR FREE LIST.

VAT

Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12 1/2%.

We stock thousands more items. Send a large S.A.E. for our Free Stock List. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in μ F)
400V: 0.01 0.015 0.022 0.033 0.047 0.068 0.1 0.15 0.22 0.33 0.47 0.68 1 1.5 2.2 3.3 4.7 6.8 10 15 22 33 47 68 100 150 220 330 470 500 680 1000 1500 2200 3300 4700 5000
150V: 0.033 0.047 0.068 0.1 0.15 0.22 0.33 0.47 0.68 1 1.5 2.2 3.3 4.7 6.8 10 15 22 33 47 68 100 150 220 330 470 500 680 1000 1500 2200 3300 4700 5000
DUBILIER: 1000V: 0.01 0.015 0.022 0.033 0.047 0.068 0.1 0.15 0.22 0.33 0.47 0.68 1 1.5 2.2 3.3 4.7 6.8 10 15 22 33 47 68 100 150 220 330 470 500 680 1000 1500 2200 3300 4700 5000

POLYESTER RADIAL LEAD: Values in μ F. 250V
0.01 0.015 0.022 0.033 0.047 0.068 0.1 0.15 0.22 0.33 0.47 0.68 1 1.5 2.2 3.3 4.7 6.8 10 15 22 33 47 68 100 150 220 330 470 500 680 1000 1500 2200 3300 4700 5000
FEED THROUGH CAPACITORS: 1000pf 350V 8p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F)
63V: 0.47 1.0 1.5 2.2 2.5 3.3 4.7 6.8 8 10 15 22 27 33 39 47 50 56 63 75 82 91 100 120 150 200 250 300 330 360 400 450 500 560 630 750 820 910 1000 1200 1500 2000 2500 3000 3300 3600 4000 4500 5000
75V: 1.0 1.5 2.2 2.5 3.3 4.7 6.8 8 10 15 22 27 33 39 47 50 56 63 75 82 91 100 120 150 200 250 300 330 360 400 450 500 560 630 750 820 910 1000 1200 1500 2000 2500 3000 3300 3600 4000 4500 5000
100V: 1.5 2.2 2.5 3.3 4.7 6.8 8 10 15 22 27 33 39 47 50 56 63 75 82 91 100 120 150 200 250 300 330 360 400 450 500 560 630 750 820 910 1000 1200 1500 2000 2500 3000 3300 3600 4000 4500 5000
250V: 2.2 3.3 4.7 6.8 8 10 15 22 27 33 39 47 50 56 63 75 82 91 100 120 150 200 250 300 330 360 400 450 500 560 630 750 820 910 1000 1200 1500 2000 2500 3000 3300 3600 4000 4500 5000
TAG-END TYPE: 70V: 2000 98p; 470V: 121p; 50V: 10.000 255p; 300V 75p; 40V: 4000 70p; 250V: 65p; 25V: 4700 48p; 2000 37p; 470V: 2000+5000 95p; 325V: 200+100+50+100 190p.

TANTALUM BEAD CAPACITORS: 35V: 0.1 μ F 0.22 0.33 0.47 0.68 1.0 2.2 3.3 4.7 6.8 10 15 22 33 47 68 100 150 220 330 470 500 680 1000 1500 2200 3300 4700 5000
20V: 1.5 16V: 10 μ F 13p each 22 25p. 47 μ F 100 40p each. 10V: 22 μ F 33 47 6V: 47 68 100 3V: 68 100 μ F 20p each

MYLAR FILM CAPACITORS: 100V: 0.001 0.002 0.005 0.01 μ F 5p 0.015 0.02 0.04 0.05 0.056 μ F 6p 0.1 μ F 0.15 0.2 7p. 50V: 0.47 μ F 10p

CERAMIC CAPACITORS 50V: Range: 0.5pF to 10.000pF 3p 0.015 μ F 0.022 μ F 0.033 μ F 4p 0.1 μ F 4p 0.1 μ F 6p

SILVER MIC: Values in pF: 3.3 4.7 6.8 10 12 18 22 33 47 50 68 75 82 85 100 120 150 220 9p each 250 300 330 360 390 600 820 16p each 1000 1800 2000 2200 20p each

CERAMIC TRIMMER CAPACITORS: 2 7/8 4 15pF 6 25pF 8 30pF 20p

MINIATURE TRIMMERS: 2.5 5pF 3 10pF 10 40pF 22p 2.5 5pF 5.45pF 60pF 88pF 30p

COMPRESSION TRIMMERS: 3.40pF 10.80pF 25 190pF 25p 100 500pF 1250pF 45p

JACK PLUGS: Screened chrome 2.5mm 12p 3.5mm 15p MONO 23p STEREO 31p

SOCKETS: Plastic body 8p 8p 8p 13p 15p moulded with break contacts 20p 18p 24p

DIN: 2 PIN Loudspeaker 13p 3 PIN 5 Audio 8p 20p

CO-AXIAL (TV): 14p 14p 14p

PHONO: assorted colours 9p 5p single 8p double 15p Metal screened 10p 3-way

BANANA: 4mm 10p 2mm 10p 1mm 8p

ETI 583 GAS MONITOR
All parts available
Gas Sensors TGS109, 308, 812 & 813 385p*
Sockets for above 20p*



RHYTHM GENERATOR
Build this PE (Jan. '78) Easybuild Low Cost Rhythm Generator. We are the sole suppliers of the complete Kit including the case, pre-drilled printed front panel and the Printed Circuit Boards send see for leaflet.
Complete Kit price incl. VAT **£49.95** only Plus P&P £1
For ready built Units add **£15.00.**

DIGITAL PANEL METER
Intersil Evaluation Kit **£21.52*** plus 30p p&p
All parts as per ETI **£23.85*** plus 30p p&p
ICL7106 **£9.75***
LCD3901 **£9.95***

TTL 74*

7400	14	7480	50	74162	116	4021	99	702	75	
401	14	481	97	74163	116	4022	99	709C 14 pin	35	
7402	16	482	82	74164	121	4024	76	741CA 8 pin	22	
403	16	483	95	74165	130	4025	19	747C	70	
404	20	484	95	74166	141	4026	180	748C	36	
405	22	485	110	74167	198	4027	55	753	150	
406	38	486	36	74170	248	4028	90	8038CC*	355	
407	38	489	30	74172	625	4029	100	AY 10212	90	
7408	20	490	36	74173	175	4030	58	AY 15050	241	
409	20	491	80	74174	113	4033	145	AY 15051	125	
410	15	492	53	74175	90	4034	196	AY 16721	6195	
411	24	493	35	74176	120	4040	105	AY 38500*	450	
412	23	494	85	74177	116	4042	81	AY 38505*	750	
413	37	495	70	74180	142	4043	96	AY 38600*	85	
414	74	496	82	74181	299	4044	95	AY 51234*	295	
416	35	497	262	74182	127	4045	145	AY 51230*	490	
417	39	4100	125	74183	225	4046	130	AY 51317A	630	
420	16	4104	62	74185	146	4047	99	CA3014*	137	
421	33	4105	62	74188	650	4048	58	CA3018*	82	
422	24	4107	33	74190	140	4049	52	CA3020	170	
423	32	4109	54	74191	140	4050	52	CA3023	170	
425	30	4110	54	74192	140	4054	120	CA3028A*	95	
426	36	4111	70	74193	140	4055	134	CA3035	140	
427	36	4116	198	74194	140	4056	134	CA3036	180	
428	38	4118	90	74195	110	4060	115	CA3043	190	
430	16	4120	115	74196	118	4067	380	CA3046	406	
432	32	4121	28	74197	118	4068	CA3048	200	ROM2513*	700
433	40	4122	48	74198	248	4069E	22	CA3075	175	
437	30	4123	70	74199	110	4070	32	CA3080E	80	
438	33	4125	65	74191	75	4072	21	CA3081	190	
440	17	4126	60	74192	80	4075BE	23	CA3089E	210	
442	68	4127	73	CMOS*		4076	129	CA3090AQ	330	
443	115	4136	56			4078	21	CA3130*	200	
444	112	4141	72	4000	15	4081	22	CA3140	95	
445	94	4142	280	4001	17	4082	21	ICL160*	950	
446	94	4143	314	4002	17	4082	120	ICM7200*	1150	
7447	82	4144	314	4003	11	4083	11	LM3004	170	
7448	74	4145	85	4007	18	4510	13	LM301A	39	
7450	17	4147	175	4009	58	4511	168	LM318	195	
451	17	4148	143	4010	58	4512	98	LM324	98	
453	17	4150	118	4011	19	4516	125	LM339	55	
454	17	4151	75	4012	18	4518	102	LM348	120	
7457	17	4153	82	4013	11	4519	99	LM379	38	
460	30	4154	140	4015	93	4520	108	LM380A	98	
472	28	4155	82	4016	52	4528	99	LM382	170	
473	32	4157	80	4017	99	4532	127	LM387	125	
474	32	4159	225	4018	99	4539	110	LM3900	65	
475	42	4160	116	4019	60	4553	449	LM3909N	70	
476	30	4161	116	4020	102	4558	101	LM3911	125	

LINEAR ICs


M252AA*	570
M252AB*	795
MC1303	45
MC1304P	260
MC1310P	185
MC1312PQ	185
MC14433L	1250
MC1458P*	90
MC1469	101
MC1710CG	79
MC3360P	89
MCFC6040*	97
MK50253*	550
MK50362*	550
MM2101	210
MM2112 2A*	298
NE518A	210
NE555*	36
NE560B*	90
NE560*	325
NE561*	410
NE562*	410
NE565A*	185
NE566*	180
NE567V*	187
NE57*	450
RA2102 2A*	210
SGM2513*	700
SG3402*	255
SN7233N	125
SN76003N	240
SN76013	240
SN76023	140
SN76033N	200
SN76115	215
SN76227N	175
TA6621A*	228
TA6661A	155
LM3004	170
LM301A	39
LM318	195
LM324	98
LM339	55
LM348	120
LM379	38
LM380A	98
LM382	170
LM387	125
LM3900	65
LM3909N	70
LM3911	125
ZN14	110

TRANSISTORS

AC117	3	BC161A	11	BF194	10	OC42	40	Z1X501	15	ZN3615*	135
AC125*	19	BC169C	12	BF195	10	OC44*	65	Z1X502	19	ZN3663	26
AC126*	19	BC170	18	BF196	12	OC45*	35	Z1X503	19	ZN3702	10
AC127*	18	BC171	11	BF197	15	OC46*	35	Z1X504	25	ZN3703	11
AC128*	18	BC172	10	BF198	18	OC47*	35	Z1X531	28	ZN3704	10
AC129*	18	BC173	10	BF199	30	OC70*	30	Z1X550	25	ZN3705	11
AC141*	24	BC174	18	BF200	30	OC71*	30	Z1X551	25	ZN3706	10
AC142*	24	BC175	16	BF201	30	OC72*	30	Z1X552	25	ZN3707	10
AC143*	24	BC176	16	BF202	30	OC73*	30	Z1X553	25	ZN3708	10
AC144*	24	BC177	16	BF203	30	OC74*	30	Z1X554	25	ZN3709	11
AC145*	24	BC178	18	BF204	30	OC75*	30	Z1X555	25	ZN3710	11
AC146*	24	BC179	18	BF205	30	OC76*	30	Z1X556	25	ZN3711	11
AC147*	24	BC180	18	BF206	30	OC77*	30	Z1X557	25	ZN3712	11
AC148*	24	BC181	18	BF207	30	OC78*	30	Z1X558	25	ZN3713	11
AC149*	24	BC182	18	BF208	30	OC79*	30	Z1X559	25	ZN3714	11
AC150*	24	BC183	18	BF209	30	OC80*	30	Z1X560	25	ZN3715	11
AC151*	24	BC184	18	BF210	30	OC81*	30	Z1X561	25	ZN3716	11
AC152*	24	BC185	18	BF211	30	OC82*	30	Z1X562	25	ZN3717	11
AC153*	24	BC186	18	BF212	30	OC83*	30	Z1X563	25	ZN3718	11
AC154*	24	BC187	18	BF213	30	OC84*	30	Z1X564	25	ZN3719	11
AC155*	24	BC188	18	BF214	30	OC85*	30	Z1X565	25	ZN3720	11
AC156*	24	BC189	18	BF215	30	OC86*	30	Z1X566	25	ZN3721	11
AC157*	24	BC190	18	BF216	30	OC87*	30	Z1X567	25	ZN3722	11
AC158*	24	BC191	18	BF217	30	OC88*	30	Z1X568	25		


MAPLIN

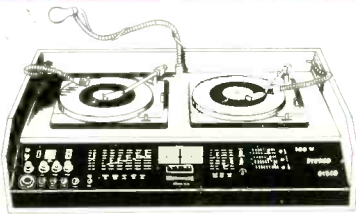everything for the modern D.I.Y. electronics enthusiast and more.




100W RMS STEREO DISCO

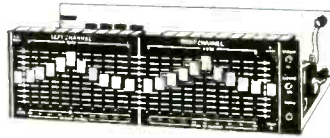A genuine 100W RMS per channel (both channels driven) stereo disco with auto fade on microphone, VU meters, full monitoring and cueing facilities and a very high quality light show. Complete construction booklet MES41 price 25p. Cabinet comes complete with lid and carrying handles.



10 CHANNEL STEREO GRAPHIC EQUALISER

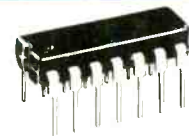A new design with no difficult coils to wind, but a specification that puts it in the top-flight hi-fi class. All this for around £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 25p. (All prices include V.A.T. and p.&p.)



INTEGRATED CIRCUITS

Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applications circuits and projects to build. Post the coupon now!




VERY LOW-DISTORTION AUDIO OSCILLATOR

The very low distortion sine wave (±0.01%) output is suitable for testing very high quality hi-fi audio equipment. Also includes square wave output. Range 20Hz to 26kHz. Output 0V to 1V in three continuously variable steps. Total cost around £2*. Full construction details in our catalogue. Send the coupon below, now! (All prices include V.A.T. and p.&p.)




TOUCH-SENSITIVE PIANO

The revolutionary new IC AY-1-1320 first seen on 'Tomorrow's World' is not available. Complete kit of IC's to build a 60-note piano (18 x IC's) order as HQ534 price £36.86. Preliminary circuit details in our October newsletter. Complete design, pcb's attractive veneered wooden cabinet available soon. It's the most realistic-sounding electronic piano we've ever heard and includes simulated damping, loud and soft pedals. Full details in our newsletters. (All prices include V.A.T. and p.&p.)

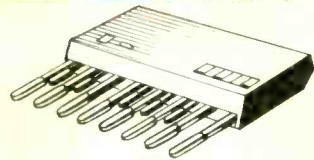


PEDAL UNIT

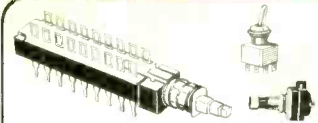A completely self-contained pedal unit. 13-note, 2-Octave range, 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue - post the coupon below, now!




SWITCHES

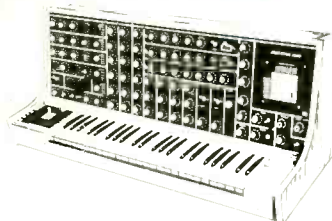We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches - there are dozens to choose from, but it's only a tiny part of our fantastic range.



SYNTHESISER

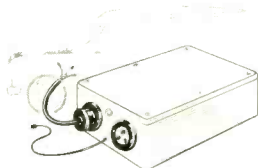The International 4600 Synthesiser. A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart leak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request. Full construction details in our construction book £1.50. (All prices include V.A.T. and p.&p.)



ELECTRONIC IGNITION SYSTEM

A high performance electronic ignition system that saves fuel, cuts points wear, gives strong spark and easy start even with very low battery, improves engine power at high revs. Change back to conventional system in seconds. Total cost around £14. Full construction details in our catalogue. Send the coupon below, now! (All prices include V.A.T. and p.&p.)



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).



POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME _____

ADDRESS _____

IT'S A FANTASTIC BESTSELLER!
216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!
DON'T MISS OUT! SEND 60p NOW!

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 715157