


electronics today

DECEMBER 1978

INTERNATIONAL

45p

FIVE CHANNEL LIGHT SHOW

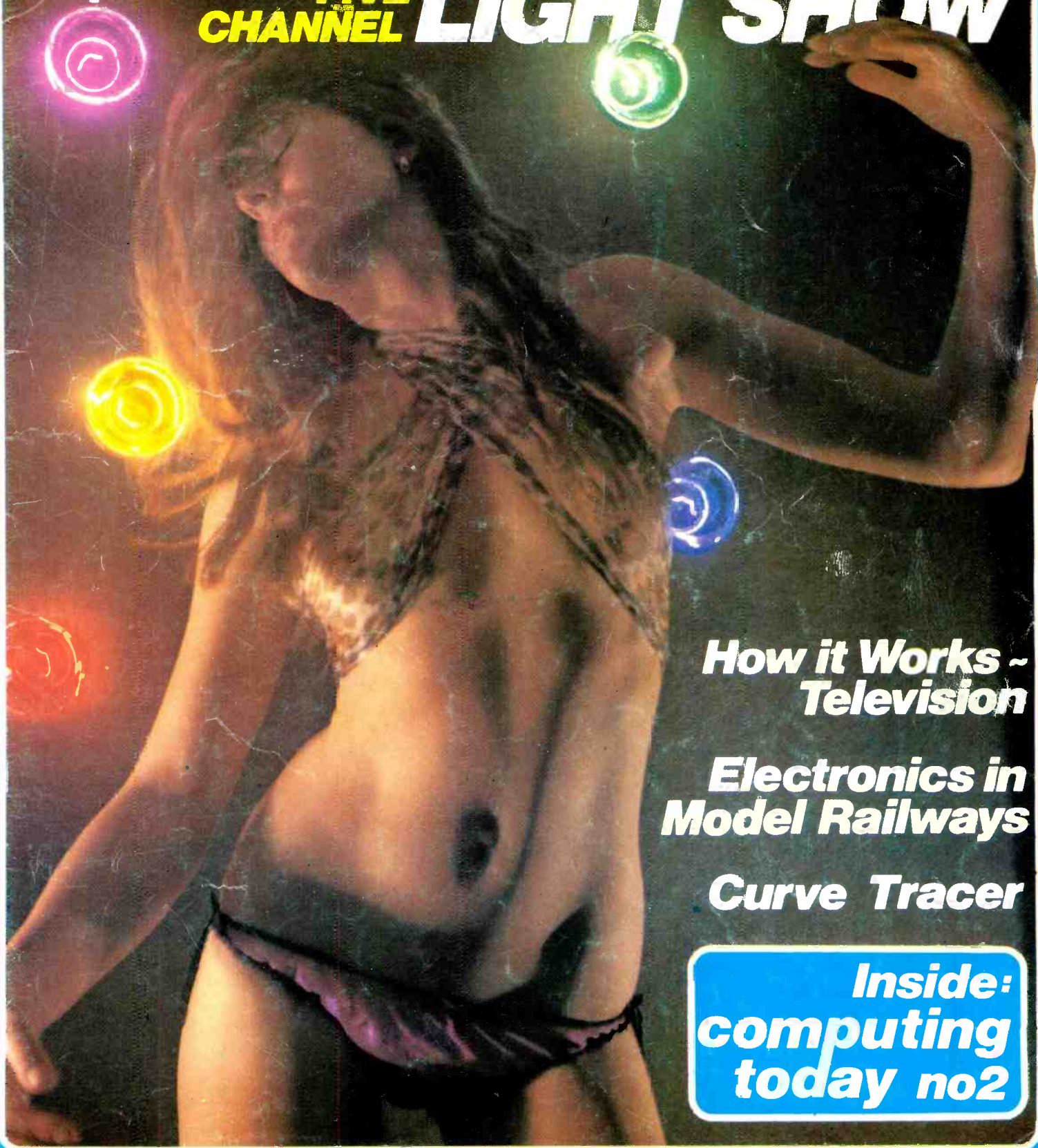

**How it Works -
Television**

**Electronics in
Model Railways**

Curve Tracer

**Inside:
computing
today no2**

... NEWS . . . PROJECTS . . . MICROPROCESSORS . . . AUDIO . . .

TRANSCENDENT 2000

SINGLE BOARD SYNTHESIZER


LIVE PERFORMANCE SYNTHESIZER DESIGNED BY CONSULTANT TIM ORR (FORMERLY SYNTHESIZER DESIGNER FOR EMS LIMITED) AND FEATURED AS A CONSTRUCTIONAL ARTICLE IN ELECTRONICS TODAY INTERNATIONAL.

The TRANSCENDENT 2000 is a 3 octave instrument transposable 2 octaves up or down giving an effective 7 octave range. There is portamento, pitch bending, a VCO with shape and pitch modulation, a VCF with both low and high pass outputs and a separate dynamic sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibre glass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready built units selling for between £500 and £700!

**COMPLETE KIT
ONLY
£172.00 + VAT!**

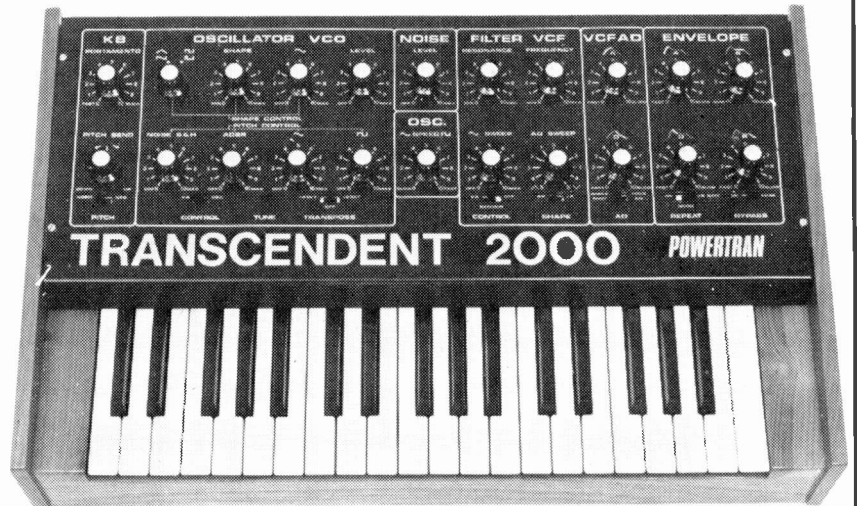Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!



Cabinet size 24.6" x 15.7" x 4.8" (rear) 3.4" (front)

THIS MONTH'S FRONT COVER FEATURE!



**COMPLETE KIT
ONLY
£49.50 + VAT!**

PSI 4002 STUDIO MODEL



cabinet size 17.2" x 17.2" x 6.7"

COMPLETE KIT ONLY £196.90 + VAT

The kits shown on this page are also available as separate packs (e.g. PCB component sets, hardware sets etc). Prices are given in our FREE CATALOGUE

200 + 200 watt AMPLIFIER

As featured in Electronics Today International

400W rms continuous — 800W peak!

0.03% THD at FULL power!

PLUS all the following features too!

- ★ Each channel totally independent with its own stabilised power supply driven by custom designed TOROIDAL transformers!
- ★ Inherent reliability — monster heat sinks for cool running at the hottest venues — electronic open and short circuit protection!
- ★ Ultra low feedback (an incredible low 14dB overall!), super high slewing rate (20V/μs) 200W rms continuous to 4 ohm from EACH channel, input sensitivity 0.775V (0dB)
- ★ Professional quality components — sturdy 19" rack mounting chassis complete with sleeve and feet for free standing work too
- ★ Easy to build — plenty of working space with ready access to all components, minimal wiring — extensive instruction suitable for both experience constructors and newcomers to electronics
- ★ Value for money — quality and performance comparable with ready-built amplifiers costing over £600!

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3NM

ANDOVER
(STD 0264) 64455

PRICE STABILITY: Order with confidence irrespective of any price changes we will honour all prices in this advertisement until January 31st, 1979 if ETI December 1978 issue is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subject to 12 1/2% surcharge for VAT* (i.e. add 1/6 to the price). No charge is made for carriage *or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.


SALES COUNTER: If you prefer to collect your kit from the factory — call at Sales Counter (at rear of factory). Open 9 a.m. - 4.30 p.m. Monday-Thursday.

electronics today

DECEMBER 1978 VOL 7 NO 12 INTERNATIONAL



Leave a trace p.73

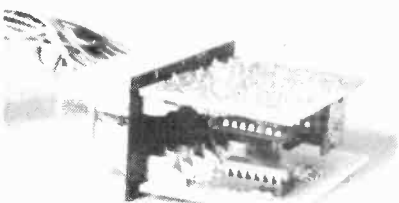

Keep your wheels p.16



A project for a fling p.44

FEATURES


NEWS DIGEST	7	Latest on the latest
HOW IT WORKS — TELEVISION	21	A new series on circuits
ELECTRONICS IN MODEL RAILWAYS	36	Tips for the living room express drivers!
INDEX 78	53	A listing of all we've done since April 77
IONOSPHERE	61	An atmospheric article!
DATA SHEET	69	Amplify at speed
MICROFILE	77	Micro-men take note
AUDIOPHILE	88	Strathern speak to us, and Sony arm us!
TECH TIPS	93	All your own work

PROJECTS

CAR ALARM	16	Hang on to what's yours!
WINE TEMPERATURE METER	31	Don't make them the grapes of wrath!
LIGHT SHOW CONTROLLER	44	Five channels to run a disco through
CURVE TRACER	73	Not 36-24-36 — but useful nonetheless
AUTOCHORD PART 2	80	Full construction details

INFORMATION

SUBSCRIPTIONS	8	Make it easy on yourself
BINDERS	9	Take care of us!
BACK NUMBERS	11	Wot we got and wot we ain't
ETIPRINTS	29	The only boarding card you need
ETI BOOK SERVICE	43	Good sound stuff all in fine print
COME AND JOIN US	51	ETI needs you — well 3 of you anyway!
MARKETPLACE	57	Timely offers!
ETI JANUARY PREVIEWED	59	On its way to you
SPECIALS	67	All our wares on show
HOBBY ELECTRONICS	87	Coming up up in number two

<p>INTERNATIONAL EDITIONS</p> <p>AUSTRALIA Collyn Rivers Publisher Les Bell Acting Editor</p> <p>Holland Anten Kriegsman Editor-in-Chief</p> <p>CANADA Steve Braidwood Editor Graham Wideman Assistant Editor</p> <p>GERMANY Udo Wittig Editor</p> 	<p>EDITORIAL AND ADVERTISEMENT OFFICE 25-27 Oxford Street, London W1R 1RF. Telephone 01-434 1781/2. Telex 8811896</p>	
	<p>Halvor W. Moorshead Editor</p> <p>Ron Harris B.Sc Assistant Editor</p> <p>Gary Evans Project Editor</p> <p>Jim Perry Specials Editor</p> <p>Phil Cohen B.Sc Editorial Assistant</p> <p>Pete Howells Production Editor</p> <p>Paul Edwards Technical Illustrator</p> <p>John Koblanski Project Design</p> <p>Steve Ramsahadeo Project Development</p> <p>Margaret Hewitt Administration</p> <p>Andrew Scott Office Manager</p> <p>Kim Hamlin, Brenda Goodwin Reader Services</p> <p>Tim Salmon, Val Tregidgo Advertising Manager</p> <p>Mark Strathern Provincial Advertising Manager</p> <p>David Sinfield Advertising Assistants</p> <p>Tom Moloney, Joy Cheshire</p>	
	<p>PUBLISHED BY Modmags Ltd., 25-27 Oxford Street, London W1R 1RF</p> <p>DISTRIBUTED BY Argus Distribution Ltd. (British Isles)</p> <p>Gordon & Gotch Ltd (Overseas)</p> <p>PRINTED BY Q8 Limited, Colchester</p>	

Electronics Today International is normally published on the first Friday of the month prior to the cover date

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.

BOOKS AND COMPONENTS

BOOKS BY BABANI

Purchase books to the value of £5.00 from the list below and choose any 60p paK from this page FREE.

BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60pt
BP6	Engineers and Machinists Reference Tables	40pt
BP7	Radio & Electronic Colour Codes and Data	15pt
BP10	Modern Crystal and Transistor Set Circuits for beginners	35pt
BP15	Constructors Manual of Electronic Circuits for the Home	50pt
BP22	79 Electronic Novelty Circuits	75pt
BP23	First book of Practical Electronic Projects	75pt
BP24	52 Projects Using IC741 (or equivalents)	75pt
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85pt
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60pt
BP29	Major Solid State Audio Hi-Fi Construction Projects	85pt
BP32	How to Build Your Own Metal & Treasure Locators	85pt
BP34	Practical Repair & Renovation of Colour TVs	95pt
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	95pt
BP36	50 Circuits Using Germanium, Silicon & Zener Diodes	75pt
BP37	50 Projects Using Relays, SCRs and TRIACS	£1.10†
BP39	50 (FET) Field Effect Transistor Projects	£1.25†
BP43	How to Make Walkie Talkies	£1.25†
BP44	I.C. 555 Timer Projects	£1.45†
BP47	Mobile Discotheque Handbook	£1.35†
BP129	Universal Gram-motor Speed Indicator	10pt
BP160	Coil Design and Construction Manual	75pt
BP196	AF-RF Reactance — Frequency Chart for Constructors	15pt
BP202	Handbook of Integrated Circuits (ICs) Equivalents and Substitutes	75pt
BP205	First Book of Hi-Fi Loudspeaker Enclosures	75pt
BP213	Electronic Circuits for Model Railways	85pt
BP214	Audio Enthusiasts Handbook	85pt
BP216	Electronic Gadgets and Games	85pt
BP217	Solid State Power Supply Handbook	85pt
BP219	Solid State Novelty Projects	85pt
BP220	Build Your Own Solid State Hi-Fi and Audio Accessories	85pt
BP222	Solid State Shortwave Receivers for Beginners	95pt
BP223	50 Projects Using IC CA3 130	95pt
BP224	50 CMOS IC Projects	95pt
BP225	A Practical Introduction to Digital ICs	95pt
BP226	How to Build Advanced Short Wave Receivers	£1.20†
RCC	Resistor Colour Code Disc Calculator	10pt

BOOKS BY NEWNES

No. 229	Beginners Guide to Electronics	Price £2.25†
No. 230	Beginners Guide to Television	Price £2.25†
No. 231	Beginners Guide to Transistors	Price £2.25†
No. 233	Beginners Guide to Radio	Price £2.75†
No. 234	Beginners Guide to Colour Television	Price £2.25†
No. 235	Electronic Diagrams	Price £1.80†
No. 236	Electronic Components	Price £1.80†
No. 237	Printed Circuit Assembly	Price £1.80†
No. 238	Transistor Pocket Book	Price £3.90†
No. 225	110 Thyristor Projects Using SCRs & Triacs	Price £2.50†
No. 227	110 COS/MOS Digital IC Projects for the Home Constructor	Price £2.75†
No. 226	110 Operational Amplifier Projects for the Home Constructor	Price £2.50†
No. 242	Electronics Pocket Book	Price £3.90†
No. 239	30 Photoelectric Circuits & Systems	Price £1.80†

NUTS AND BOLTS

BA BOLTS — packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
1in OBA	83	£1.20	1/4in 4BA	846	£0.32
1/2in OBA	840	£0.75	1/4in 4BA	847	£0.25
1in 2BA	842	£0.65	1in 6BA	848	£0.40
1/2in 2BA	843	£0.45	1/2in 6BA	849	£0.21
1/4in 2BA	844	£0.52	1/4in 6BA	850	£0.25
1in 4BA	845	£0.44			

BA NUTS — packs of cadmium plated full nuts in multiples of 50

Type	No.	Price	Type	No.	Price
OBA	855	£0.72	4BA	857	£0.30
2BA	856	£0.48	6BA	858	£0.24

BA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	859	£0.14	4BA	861	£0.12
2BA	860	£0.12	6BA	862	£0.12

SOLDER TAGS — hot tinned supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	851	£0.40	4BA	853	£0.22
2BA	852	£0.28	6BA	854	£0.22

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.11*
DPDT standard slide	1974	£0.14*
Toggle switch SPST		
1 1/2 amp 250V a.c.	1975	£0.33*
Toggle switch DPDT		
1 amp 250V a.c.	1976	£0.42*
Rotary on-off mains switch	1977	£0.50*
Push switch — Push to make	1978	£0.13*
Push switch — Push to break	1979	£0.18*

ROCKER SWITCH
A range of rocker switches SPST — moulded in high insulation. Material available in a choice of colours ideal for small apparatus.

Colour	No.	Price
RED	1980	£0.30*
BLACK	1981	£0.30*
WHITE	1982	£0.30*
BLUE	1983	£0.30*
YELLOW	1984	£0.30*
LUMINOUS	1985	£0.30*

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	£0.50*
Miniature SPDT toggle, 2 amp 250V a.c.	1959	£0.85*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	£0.70*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	£0.85*
Push-button SPST, 2 amp 250V a.c.	1962	£0.78*
Push-button SPDT, 2 amp 250V a.c.	1963	£0.83*
Push-button DPDT, 2 amp 250V a.c.	1964	£0.98*

MIDGET WAFER SWITCHES
Single-bank wafer type — suitable for switching at 250V a.c. 100mA or 150V d.c. in non-reactive loads make-before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing.

Description	Order No.	Price
1 pole 12 way	1965	£0.48*
2 pole 6 way	1966	£0.48*
3 pole 4 way	1967	£0.48*
4 pole 3 way	1968	£0.48*

MICRO SWITCHES

Description	Order No.	Price
Button gives 1 pole change over action	1970	£0.25
Rating 10 amp-250V a.c.		

FUSE HOLDERS AND FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	506	£0.07*
1 1/4in x 1/4in chassis mounting	507	£0.12*
1 1/4in car inline type	508	£0.15*
Panel mounting 20mm	509	£0.20
Panel mounting 1 1/4in	510	£0.30

QUICK BLOW 20mm

Type	No.	Type	No.	Type	No.
150mA	611	1A	615	3A	619
250mA	612	1.5A	616	4A	620
500mA	613	2A	617	5A	621
800mA	614	2.5A	618	6p	

ANTI-SURGE 20mm

Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628
250mA	623	2A	626	3.15A	629
500mA	624	1.6A	627	5A	630

QUICK BLOW 1 1/4in

Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634

QUICK BLOW 1 1/4in

Type	No.	Type	No.	Type	No.
1A	635	2.5A	638	5A	642
2A	637	3A	639		

QUICK BLOW 1 1/4in

Type	No.	Type	No.	Type	No.
1A	635	2.5A	638	5A	642
2A	637	3A	639		

CASES AND BOXES

INSTRUMENT CASES. In two sections, vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.25
156	11in	6in	3in	£2.12
157	6in	4 3/4in	1 3/4in	£1.30
158	9in	5 1/4in	2 1/2in	£1.76

ALUMINIUM BOXES. Made from bright ali., folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/4in	2 1/4in	1 1/2in	62p
160	4in	4in	1 1/2in	62p
161	4in	2 1/4in	1 1/2in	62p
162	5 1/4in	4in	1 1/2in	70p
163	4in	2 1/2in	2in	84p
164	3in	2in	1in	44p
165	7in	5in	2 1/2in	£1.04
166	8in	6in	3in	£1.32
167	6in	4in	2in	86p

METAL FOIL CAPACITOR PAK

Containing 50 metal foil Capacitor-like Mullard C280 series. Mixed values ranging from .01uF-2.2uF. Complete with identification sheet O/N 16204

TRANSFORMERS

MINIATURE MAINS Primary 240V

No.	Secondary	Price
2021	6V-0-6V 100mA	90p*
2022	9V-0-9V 100mA	90p*
2023	12V-0-12V 100mA	95p*

MINIATURE MAINS Primary 240V
with two independent secondary windings

No.	Type	Price
2024	MT280-0-6V 0-6V RMS	£1.50*
2025	MT150-0-12V 0-12V RMS	£1.50*

1 AMP MAINS Primary 240V

No.	Secondary	Price	P & P
2026	6V-0-6V 1 amp	£2.50*	45p
2027	9V-0-9V 1 amp	£2.90*	45p
2028	12V-0-12V 1 amp	£2.60*	55p
2029	15V-0-15V 1 amp	£2.75*	66p
2030	30V-0-30V 1 amp	£3.45*	86p

STANDARD MAINS Primary 240V
Multi-tapped secondary mains transformers available in 1/2 amp, 1 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50V.
Voltages available by use of taps: 4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 25-0-25V.

No.	Rating	Price	P & P
2031	1/2 amp	£5.50*	86p
2032	1 amp	£6.60*	86p
2033	2 amp	£8.40*	£1

AUDIO LEADS

107	FM Indoor Ribbon Aerial	£0.60*
113	3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m	£0.75*
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m	£0.85*
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m	£0.85*
116	Car aerial extension. Screened insulated lead. Fitted plug & socket	£1.10*
117	AC mains connecting lead for cassette recorders & radios, 2 metres	£0.68*
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.05*
119	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£0.90*
120	Car stereo connector. Variable geometry plug to fit most car cassette, 8-track cartridge & combination units. Supplied with inline fused power lead and Instructions	£0.60*
123	6.8m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK	£1.50*
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.75*
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0.75*
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.75*
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.30*
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0.80*
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.05*
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.68*
131	5 pin DIN plug to 3 pin DIN plug, 1 & 4 and 3 & 5. Length 1.5m	£0.83*
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£0.98*
133	5 pin DIN plug to 2 phono plugs. Connected pins 3 & 5. Length 1.5m	£0.75*
134	5 pin DIN plug to 2 phono sockets. Connected pins 3 & 5. Length 23cm	£0.68*
135	5 pin DIN socket to 2 phono plugs. Connected pins 3 & 5. Length 23cm	£0.68*
136	Coiled stereo headphone extension lead. Black. Length 6m	£1.75*
178	AC mains lead for calculators, etc.	£0.45*

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniature electrolytics.

16201	— values from 47mF-10mF	80p*
16202	— values from 10mF-100mF	80p*
16203	— values from 100mF-680mF	60p*

BI-PAK CATALOGUE

NEW EDITION NOW AVAILABLE

Send for your copy of our revised catalogue and price list NOW! It contains 127 pages packed with literally hundreds of semiconductor components and our famous range of BI-KITS audio modules.

ONLY 65p POST FREE

ORDERING Do not forget to state order number and your name and address.

V.A.T. Add 12 1/2% to prices marked*. 8% to those unmarked. Items marked are zero rated.


P.&P. 35p unless otherwise shown.

BI-PAK

DEPT. ET110, P.O. Box 6, Ware, Herts

COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.

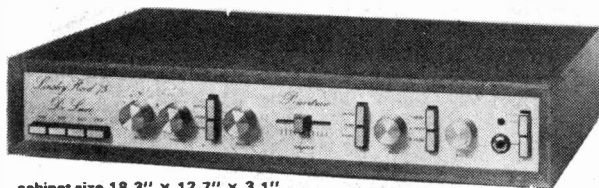AUDIO KITS OF DISTINCTION FROM **POWERTRAN**



cabinet size 18.3" x 12.7" x 3.1".

DE LUXE EASY TO BUILD LINSLEY-HOOD 75W AMPLIFIER £99.30 + VAT


This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring whilst distortion is less than 0.01%.

WIRELESS WORLD FM TUNER £70.20 + VAT

A pre-aligned front-end module makes this Wireless World published design very simple to construct and adjust without special instruments. Features include an excellent a.m. rejection, push-button station selection as well as infinitely variable tuning and a phase locked loop stereo decoder incorporating active filters for "birdy" suppression.



cabinet size 18.3" x 12.7" x 3.1".

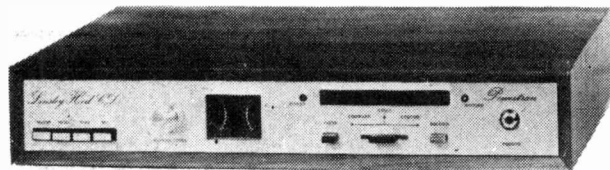


cabinet size 18.3" x 12.7" x 3.1".

LINSLEY-HOOD CASSETTE DECK £79.60 + VAT


This design, published in Wireless World, although straightforward and relatively low cost provides a very high standard of performance. There are separate record and replay amplifiers and switchable equalisation together with a choice of bias levels are also provided. The mechanism is the Goldring-Lenco CRV with electronic speed control.

T20 + 20 AMPLIFIER £33.10 + VAT

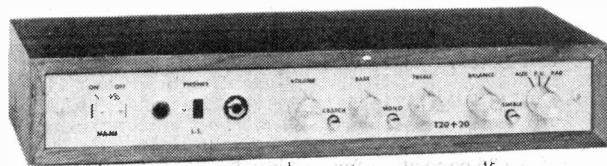This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30 + 30) is also available for £38.40 + VAT.



cabinet size 15.5" x 6.7" x 2.8".

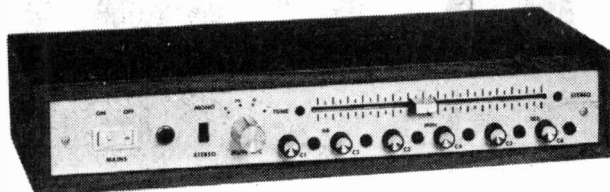


cabinet size 15.5" x 6.7" x 2.8".

WWII TUNER £47.70 + VAT

This cost reduced model of our highly successful Wireless World FM Tuner kit was designed to complement the T20 + 20 and T30 + 30 amplifiers and the cabinet size, front panel format and electrical characteristics make this tuner compatible with either. Facilities included are pre-aligned front-end module, switchable afc, adjustable switchable muting, LED tuning indication and both continuous and push-button channel selection (adjustable by controls on the front panel).

POWERTRAN SFMT TUNER £35.90 + VAT

This is a simple low cost design which can be constructed easily without special alignment equipment but which still gives a first-class output suitable for feeding any of our very popular amplifiers or any other high quality audio equipment. A phase-locked-loop is used for stereo decoding and controls include switchable afc, switchable muting and push-button channel selection (adjustable by controls on the front panel). This unit matches well with the T20 + 20 and T30 + 30 amplifiers.

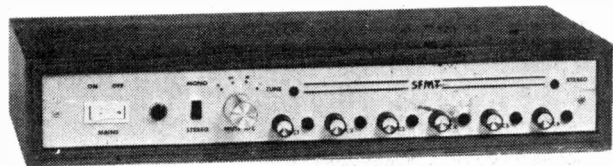

cabinet size 15.5" x 6.7" x 2.8".

COMPLETE KITS: Our complete kits really are complete. All of the projects shown on this page are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cables, nuts, bolts, etc., and full instructions — in fact everything!

All of the kits shown on this page are available as separate packs (except the Powertran SFMT Tuner) for those customers who wish to spread their purchase or perhaps make their own cabinets or metalwork. Prices are given in our FREE CATALOGUE.

PRICE STABILITY: Order with confidence! Irrespective of any price changes. We will honour all prices in this advertisement until January 31st, 1979. If ETI December, 1978 issue is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus 50p handling and documentation.

U.K. ORDERS: Subject to 12½% surcharge for VAT* (i.e. add ½ to the price). No charge is made for carrier, *or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect your kit from the factory. Call at Sales Counter (at rear of factory). Open 9 a.m.-4.30 p.m. Monday-Thursday.

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER HANTS SP10 3NM


ANDOVER
(0264) 64455

news digest

Be boring better!

This is known as a Bimdrill (Don't blame us — it's their name). It costs £19.50 + VAT and comes complete as you see it here. It

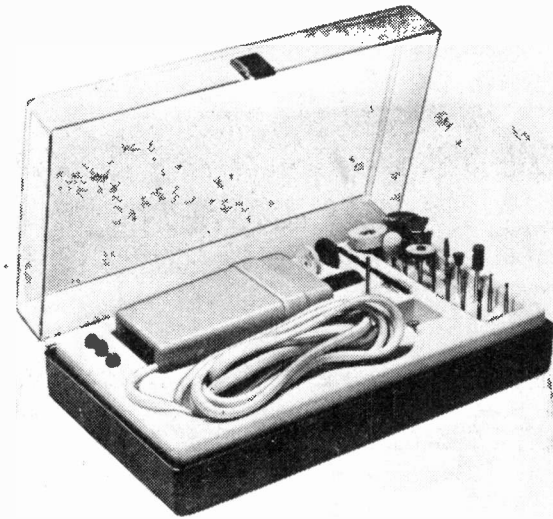is mains powered, runs at 7500 RPM, and looks very useful indeed. Any more questions to: Boss Mouldings Ltd, Higgs Industrial Estate, 2 Herene Hill Road, London SE24 0AU.





Catch these

Two more companies sent us in catalogues this month. The first was ACE who do a 36 page affair for 30p. The range they stock is pretty good as are the prices. A nice touch is the new range of new kits for the beginner. Worth having.

The other was Stevenson. This catalogue is produced superbly and as it's free it's worth a look just to see how these things

should be done. IC's are a strong point here, and a range of books is also included. Some very useful data is given in the back of the booklet which should also be on your bookshelves.

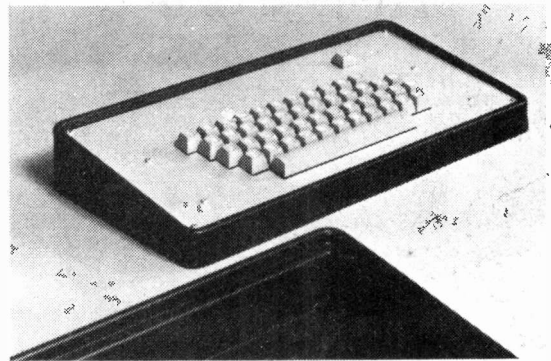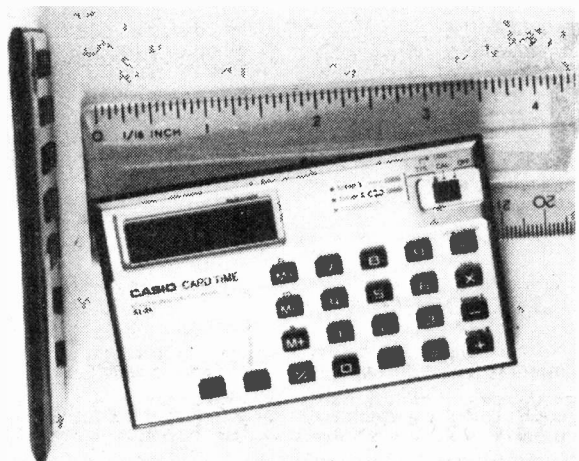
Addresses for these people appear on their ads elsewhere in this issue. Catalogues are things you should collect if you're serious about the hobby, as there is always something you'll want from somewhere at sometime or other!



Key feature

New from Vero of box frame is this new keyboard enclosure. Supplied as a kit it comes complete as a one piece ABS enclosure, anodised aluminium cover plate with self adhesive

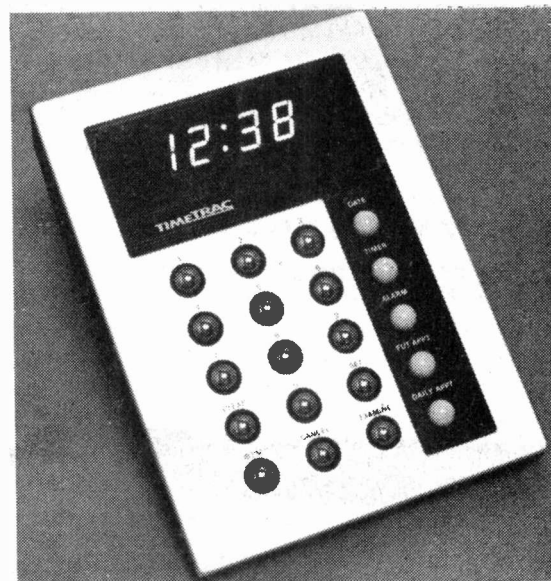feet and all fixings. It will house a standard keyboard or individual keys as required — ideal for small desk-top terminals. Vero Electronics Ltd, Industrial Estate, Chandlers Ford, Eastleigh, Hampshire.



Just the thing for Casanova?

Timetrac is a new little helper for people with busy lives and lousy memories. It contains a calendar preprogrammed, and can sound alarms

when required. Two stopwatch facilities are also included.

Power is normally from AC adaptor, but battery power is provided as standby. Optimisation Ltd, 45 South Street, Bishop's Stortford, Hertfordshire.

Time to calculate?

'Credit card' calculators do have advantages. Here's another one that can tell you how long you took to spend a fortune. Called the ST 24, it is a four-function plus % and stopwatch calculator. Maximum time to be

watched — 23hrs 59mins 59secs. Lap timing, second place timing normal stop/start and 1/10th sec indication are all possible.

The calculator can be used while the timers (with possible repeat option) or stopwatch is being used. The most you'll pay for it is £24.95 anywhere. Available now.




KEY:

- 1: The bit of chocolate you thought you'd leave for later.
- 2: Coffee stains (instant).
- 3: A useful-sized bit of stiff paper to stop the window from rattling.
- 4: Rough calculations for your new combined egg timer/laser cannon project.
- 5: ETI makes a fair soldering iron stand.
- 6: The dog insisted on carrying your copy to you along with your slippers.

WHAT A BIND!

Half our orders for binders are repeats: we think that says a lot for their quality. At £3.00 all inc. you get a great deal of peace of mind too!

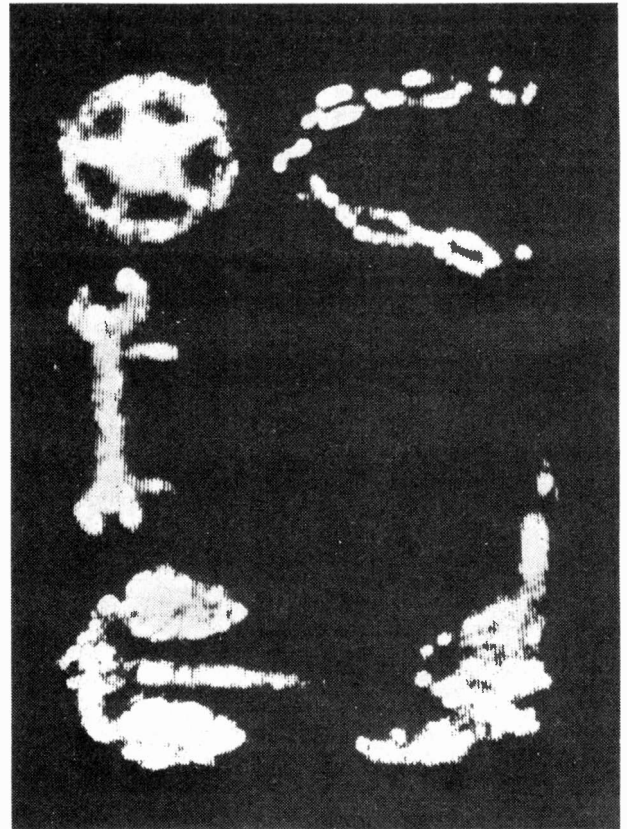ETI Binders
25-27 Oxford Street,
London W1R 1RF.




The image of it

The picture shows images achieved in lousy conditions by EMIs new wonder underwater TV system. The system has just won the IR100 award in America for its solving of the problems associated

with the quartz and frequency troubles earlier systems experienced.

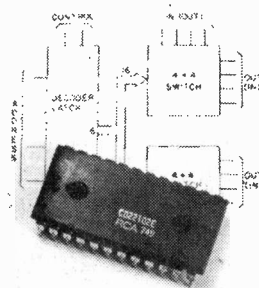The whole thing is comparatively simple, and uses 201 lines per frame, 12½ frames per second. A range of several meters is possible even in atrocious conditions.



Cross point

Now available from Jermy are 2 new Crosspoint Switches complete with control memory which are ideally suited where numerous analogue or

data lines have to be switched.

These CD22101 and CD22102 devices consist of 4x4x2 arrays of crosspoint transmission gates, 4 to 16 line decoders and 16 latch circuits, with any one of the 16 crosspoint pairs being selected by applying the appropriate four-line address and any number of crosspoints being ON simultaneously.

Bandwidth is 10 MHz and low ON resistance is typically 75ohms @ 12 Volts V_{DD} . Other significant features include closely matched switched characteristics, high linearity and standard CMOS noise immunity.

Mogul Electronics Ltd, 272 High Street, Epping, Essex CM16 4DA.

digest



Less than (h)armless?

This mechanical arm is controlled by a microcomputer and has been designed to enable even the most severely paralysed patients to fend for themselves. The electronic super-arm of the future was amongst new developments shown for the first time at a two-day 'Aids to Independence' exhibition organised by North Surrey, Community Health Council at Ashford Hospital, Middlesex.

Although the arm is only in its prototype form, Dr. Jackson Todd of Queen Mary College, London (pictured above), demonstrated that it could be programmed to carry out separate or a series of quite delicate movements. A patient only able to move his head could con-

trol it using a stick held in his mouth to activate control buttons.

The so-called bionic arms that are now becoming available depend on the patient having some muscle movement. But this microprocessor controlled version can be programmed to carry out any type of function independently of the patient. The project has been underway at Queen Mary College for about a year and the control system, believed to be the first of its kind in the world, is complete. The next step is to produce a properly engineered prototype arm and integrate it with the input devices and the microprocessor control unit.

For further information contact:
Tom West, Director of Public Relations, Surrey Area Health Authority.



It's not all old hat


A new magazine is to be launched soon — January

— specifically for enthusiasts of vintage sound equipment. It will be bi-monthly and on subscription only. Among the areas covered will be wireless equipment, gramophones and cylinders, valves, pre-war pioneering exploits and tales of the companies involved.

It will begin life as a 32 page job and sample Nols can be obtained for 65p all inc. Subs rates will be £5.80.

U.K. Sounds Vintage, 28 Chestwood Close, Billericay, Essex.

NON-SUBSCRIBERS START HERE

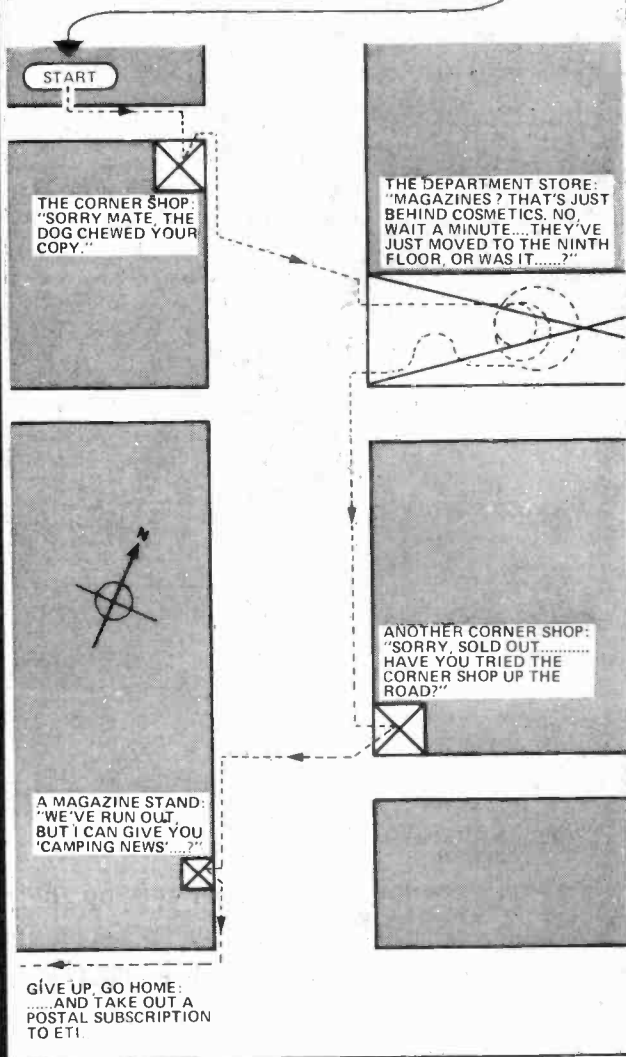

It can be a nuisance can't it, going from newsagent to newsagent? "Sorry squire, don't have it — next one should be out soon."

Although ETI is monthly, it's very rare to find it available after the first week. If it is available, the newsagent's going to be sure to cut his order for the next issue — but we're glad to say it doesn't happen very often.

Do yourself, your newsagent and us a favour. Place a regular order for ETI; your newsagent will almost certainly be delighted. If not, you can take out a postal subscription so there's nothing for you to remember — we'll do it for you.

For a subscription, send us £7.00 (£8.00 overseas) and tell us which issue you want to start with. Please make your payment (in sterling please for overseas readers) to ETI Subscriptions and keep it separate from any other services you want at the same time.

ETI Subscription Service
Electronics Today International
25-27 Oxford Street, London W1R 1RF

WATFORD ELECTRONICS

33 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER CALLERS WELCOME.
Tel. Watford 40588/9

ALL DEVICES BRAND NEW FULL SPEC AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 30p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. SEND 45p FOR OUR CATALOGUE.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12 1/2%.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type (Values are in μ F).
400V: 0.001, 0.0015, 0.0022, 0.0033 7p; 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 0.047, 0.068 14p; 0.1 15p; 0.15, 0.22, 0.22p; 0.33, 0.47 19p; 0.68, 1.0 22p; 1.5 29p; 2.2 32p; 3.3, 4.7 39p; 6.8, 10 47p; 15, 22 55p; 33, 47 63p; 68, 100 79p; 150 95p; 220 111p; 330 127p; 470 143p; 680 159p; 1000 175p; 1500 191p; 2200 207p; 3300 223p; 4700 239p; 6800 255p; 10000 271p; 15000 287p; 22000 303p; 33000 319p; 47000 335p; 68000 351p; 100000 367p; 150000 383p; 220000 399p; 330000 415p; 470000 431p; 680000 447p; 1000000 463p; 1500000 479p; 2200000 495p; 3300000 511p; 4700000 527p; 6800000 543p; 10000000 559p; 15000000 575p; 22000000 591p; 33000000 607p; 47000000 623p; 68000000 639p; 100000000 655p; 150000000 671p; 220000000 687p; 330000000 703p; 470000000 719p; 680000000 735p; 1000000000 751p; 1500000000 767p; 2200000000 783p; 3300000000 799p; 4700000000 815p; 6800000000 831p; 10000000000 847p; 15000000000 863p; 22000000000 879p; 33000000000 895p; 47000000000 911p; 68000000000 927p; 100000000000 943p; 150000000000 959p; 220000000000 975p; 330000000000 991p; 470000000000 1007p; 680000000000 1023p; 1000000000000 1039p; 1500000000000 1055p; 2200000000000 1071p; 3300000000000 1087p; 4700000000000 1103p; 6800000000000 1119p; 10000000000000 1135p; 15000000000000 1151p; 22000000000000 1167p; 33000000000000 1183p; 47000000000000 1199p; 68000000000000 1215p; 100000000000000 1231p; 150000000000000 1247p; 220000000000000 1263p; 330000000000000 1279p; 470000000000000 1295p; 680000000000000 1311p; 1000000000000000 1327p; 1500000000000000 1343p; 2200000000000000 1359p; 3300000000000000 1375p; 4700000000000000 1391p; 6800000000000000 1407p; 10000000000000000 1423p; 15000000000000000 1439p; 22000000000000000 1455p; 33000000000000000 1471p; 47000000000000000 1487p; 68000000000000000 1503p; 100000000000000000 1519p; 150000000000000000 1535p; 220000000000000000 1551p; 330000000000000000 1567p; 470000000000000000 1583p; 680000000000000000 1599p; 1000000000000000000 1615p; 1500000000000000000 1631p; 2200000000000000000 1647p; 3300000000000000000 1663p; 4700000000000000000 1679p; 6800000000000000000 1695p; 10000000000000000000 1711p; 15000000000000000000 1727p; 22000000000000000000 1743p; 33000000000000000000 1759p; 47000000000000000000 1775p; 68000000000000000000 1791p; 100000000000000000000 1807p; 150000000000000000000 1823p; 220000000000000000000 1839p; 330000000000000000000 1855p; 470000000000000000000 1871p; 680000000000000000000 1887p; 1000000000000000000000 1903p; 1500000000000000000000 1919p; 2200000000000000000000 1935p; 3300000000000000000000 1951p; 4700000000000000000000 1967p; 6800000000000000000000 1983p; 10000000000000000000000 1999p; 15000000000000000000000 2015p; 22000000000000000000000 2031p; 33000000000000000000000 2047p; 47000000000000000000000 2063p; 68000000000000000000000 2079p; 100000000000000000000000 2095p; 150000000000000000000000 2111p; 220000000000000000000000 2127p; 330000000000000000000000 2143p; 470000000000000000000000 2159p; 680000000000000000000000 2175p; 1000000000000000000000000 2191p; 1500000000000000000000000 2207p; 2200000000000000000000000 2223p; 3300000000000000000000000 2239p; 4700000000000000000000000 2255p; 6800000000000000000000000 2271p; 10000000000000000000000000 2287p; 15000000000000000000000000 2303p; 22000000000000000000000000 2319p; 33000000000000000000000000 2335p; 47000000000000000000000000 2351p; 68000000000000000000000000 2367p; 100000000000000000000000000 2383p; 150000000000000000000000000 2399p; 220000000000000000000000000 2415p; 330000000000000000000000000 2431p; 470000000000000000000000000 2447p; 680000000000000000000000000 2463p; 1000000000000000000000000000 2479p; 1500000000000000000000000000 2495p; 2200000000000000000000000000 2511p; 3300000000000000000000000000 2527p; 4700000000000000000000000000 2543p; 6800000000000000000000000000 2559p; 10000000000000000000000000000 2575p; 15000000000000000000000000000 2591p; 22000000000000000000000000000 2607p; 33000000000000000000000000000 2623p; 47000000000000000000000000000 2639p; 68000000000000000000000000000 2655p; 100000000000000000000000000000 2671p; 150000000000000000000000000000 2687p; 220000000000000000000000000000 2703p; 330000000000000000000000000000 2719p; 470000000000000000000000000000 2735p; 680000000000000000000000000000 2751p; 1000000000000000000000000000000 2767p; 1500000000000000000000000000000 2783p; 2200000000000000000000000000000 2799p; 3300000000000000000000000000000 2815p; 4700000000000000000000000000000 2831p; 6800000000000000000000000000000 2847p; 10000000000000000000000000000000 2863p; 15000000000000000000000000000000 2879p; 22000000000000000000000000000000 2895p; 33000000000000000000000000000000 2911p; 47000000000000000000000000000000 2927p; 68000000000000000000000000000000 2943p; 100000000000000000000000000000000 2959p; 150000000000000000000000000000000 2975p; 220000000000000000000000000000000 2991p; 330000000000000000000000000000000 3007p; 470000000000000000000000000000000 3023p; 680000000000000000000000000000000 3039p; 1000000000000000000000000000000000 3055p; 1500000000000000000000000000000000 3071p; 2200000000000000000000000000000000 3087p; 3300000000000000000000000000000000 3103p; 4700000000000000000000000000000000 3119p; 6800000000000000000000000000000000 3135p; 10000000000000000000000000000000000 3151p; 15000000000000000000000000000000000 3167p; 22000000000000000000000000000000000 3183p; 33000000000000000000000000000000000 3199p; 47000000000000000000000000000000000 3215p; 68000000000000000000000000000000000 3231p; 100000000000000000000000000000000000 3247p; 150000000000000000000000000000000000 3263p; 220000000000000000000000000000000000 3279p; 330000000000000000000000000000000000 3295p; 470000000000000000000000000000000000 3311p; 680000000000000000000000000000000000 3327p; 1000000000000000000000000000000000000 3343p; 1500000000000000000000000000000000000 3359p; 2200000000000000000000000000000000000 3375p; 3300000000000000000000000000000000000 3391p; 4700000000000000000000000000000000000 3407p; 6800000000000000000000000000000000000 3423p; 10000000000000000000000000000000000000 3439p; 15000000000000000000000000000000000000 3455p; 22000000000000000000000000000000000000 3471p; 33000000000000000000000000000000000000 3487p; 47000000000000000000000000000000000000 3503p; 68000000000000000000000000000000000000 3519p; 100000000000000000000000000000000000000 3535p; 150000000000000000000000000000000000000 3551p; 220000000000000000000000000000000000000 3567p; 330000000000000000000000000000000000000 3583p; 470000000000000000000000000000000000000 3599p; 680000000000000000000000000000000000000 3615p; 1000000000000000000000000000000000000000 3631p; 1500000000000000000000000000000000000000 3647p; 2200000000000000000000000000000000000000 3663p; 3300000000000000000000000000000000000000 3679p; 4700000000000000000000000000000000000000 3695p; 6800000000000000000000000000000000000000 3711p; 100 3727p; 15000000000000000000000000000000000000000 3743p; 22000000000000000000000000000000000000000 3759p; 33000000000000000000000000000000000000000 3775p; 47000000000000000000000000000000000000000 3791p; 68000000000000000000000000000000000000000 3807p; 1000 3823p; 1500 3839p; 2200 3855p; 3300 3871p; 4700 3887p; 6800 3903p; 100 3919p; 15000 3935p; 22000 3951p; 33000 3967p; 47000 3983p; 68000 3999p; 1000 4015p; 1500 4031p; 2200 4047p; 3300 4063p; 4700 4079p; 6800 4095p; 100 4111p; 15000 4127p; 22000 4143p; 33000 4159p; 47000 4175p; 68000 4191p; 1000 4207p; 1500 4223p; 2200 4239p; 3300 4255p; 4700 4271p; 6800 4287p; 100 4303p; 15000 4319p; 22000 4335p; 33000 4351p; 47000 4367p; 68000 4383p; 1000 4399p; 1500 4415p; 2200 4431p; 3300 4447p; 4700 4463p; 6800 4479p; 100 4495p; 15000 4511p; 22000 4527p; 33000 4543p; 47000 4559p; 68000 4575p; 1000 4591p; 1500 4607p; 2200 4623p; 3300 4639p; 4700 4655p; 6800 4671p; 100 4687p; 15000 4703p; 22000 4719p; 33000 4735p; 47000 4751p; 68000 4767p; 1000 4783p; 1500 4799p; 2200 4815p; 3300 4831p; 4700 4847p; 6800 4863p; 100 4879p; 15000 4895p; 22000 4911p; 33000 4927p; 47000 4943p; 68000 4959p; 1000 4975p; 1500 4991p; 2200 5007p; 3300 5023p; 4700 5039p; 6800 5055p; 100 5071p; 15000 5087p; 22000 5103p; 33000 5119p; 47000 5135p; 68

WE'RE OUT TO FINISH

YOU OFF!

Rapitape #
eti PANEL TRANSFERS

MOD MAGS 1977 no 1

GOOD AND PROPER!


... or at least your projects. If there is one thing which is impossible to do at home is lettering front panels to professional standards. At least until now. If you cast your eyes right a while you'll see our new panel transfers sheet, which has been carefully designed to allow you to do exactly that.

The transfers are easily rubbed down, and the two sheet set contains a mass of lettering and —uniquely— control scales for both rotary and slider puts.

Each sheet measures 180mm X 240mm and comes packed flat in a stiff cardboard envelope for protection. There should be enough for dozens of projects here — and the longer you wait the worse they'll look!

Send £1.75 (includes VAT and postage) for the two-sheet set to:

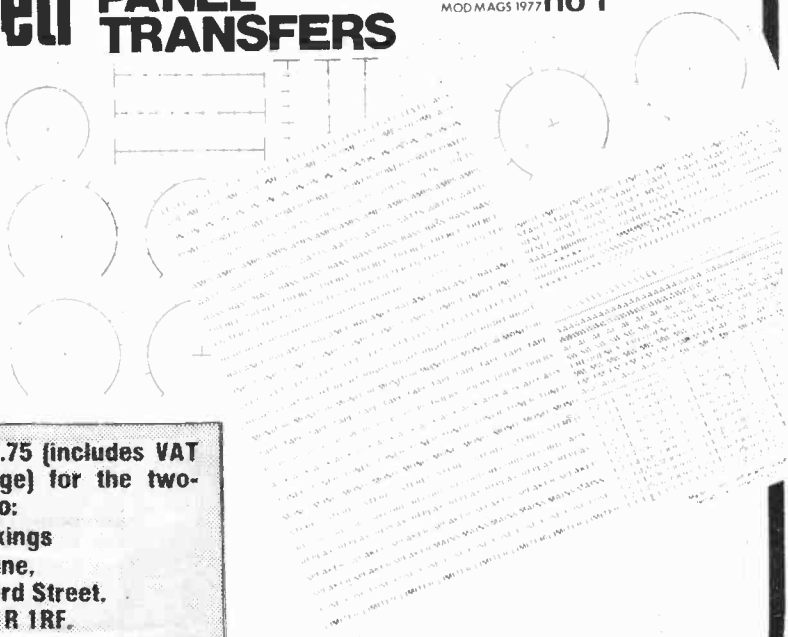Panel Markings
ETI Magazine,
25-27 Oxford Street,
London W1R 1RF.



DISCOVER LOST TREASURE!

Super performance true TR/IB machine. Professional tone on/off method of indication. Utilises the very latest circuitry including a special IC customised to our specification, reducing quiescent current to < 5mA, lowering total component count (less to go wrong) and producing a detector of outstanding stability and detection capability. Loudspeaker operation (padded headphones available £5.50 extra). Shaft and search head angle fully adjustable. Waterproof search head. You could pay pounds more for a detector as good as this.

"Shadow" detector — £38.95 + £1 towards p&p.
"Shadow" kit (pre-wound coils) — £29.95 + £1 p&p.

Building your own detector? Then we can supply the hardware "shell". Including fully adjustable shaft with handle. Special clips to mount your own control housing (any box is suitable) and search head mouldings with adjustable ball joint hinge. Suitable for any type of detector (BFO-TR-IB-PI etc.) including those published in this and other magazines. As used for our own "Shadow" detector. Supplied undrilled as a kit with full instructions.

Detector "Shell" kit £9.50 + £1 p&p

SPECIAL OFFER To every purchaser of our "Shell" kit we are giving away a copy of our publication "Metal detector design notes" which gives much useful information on many different types of metal detectors and detection techniques, including TR, IB, BFO, PI, VLF, Proton Magnetometer, Discriminators, Phase locked loops, Harmonix mixing, hall effect, Off resonance, Coupled field, Faraday shields, Push button tuning, Legal frequencies, other legal requirements, how to obtain Home Office approval, etc., etc. Contains many interesting circuits (including commercial designs) too numerous to list. A wealth of priceless information much of which has not been published before.

QUALITY NOTE All Altek detectors use high grade epoxy/glass roller tinned boards. Some manufacturers still use plain copper which quickly corrodes in damp weather. All Altek detectors are Home Office approved. Phone in your credit card number now (24 hour answering)

A good all round low cost metal detector. 200mm (B) annular search head gives wide scan with easy pinpointing. Simple high efficiency B.F.O. circuitry draws < 5mA, inexpensive battery gives over 100 hours search time. Ferrous/non ferrous discrimination possible. Extra lightweight, 300 gms (10.5 ozs) with battery — eliminates arm fatigue, even for a child. The lowest priced metal detector.

ALT3 — £12.95 + £1 towards p&p

Build it yourself. Very detailed manual — ideal for a beginner as a first project (must be able to solder). Pre-wound search loop and tuning coil, absolutely everything supplied except tools and battery. The least expensive way of buying. The parts bought separately might cost you more, certainly it'd take more time. Makes a great present for a younger brother, etc. (buy it for him — use it yourself!)

ALT3 (kit) — £9.95 + £1 towards p&p.

Stethoscope adaptor for the ALT3. Converts the earpiece (supplied with detector) to two ear listening. More comfortable — cuts down background noise. 85p post paid.

All prices include VAT



Mail Order only please Callers by appointment
Altek Instruments
Dept. ETI 1 Green Lane
Walton-on-Thames Surrey



Write or Phone - Now!!
(093 22)
44110
ANYTIME!

<p>SAME AS ETI OFFER</p> <p>5 FUNCTION LCD</p> <p>Hours, mins, secs, month, date, auto calendar, back-light, quality metal bracelet.</p> <p>£8.65</p> <p>Guaranteed same day despatch</p> <p>Very slim, only 6mm thick.</p> 	<p>SPECIAL TO ETI READERS</p> <p>Genuine SOLAR ALARM WATCH</p> <p>Solar + alarm LCD watch</p> <p>Hours, mins, secs displayed. * Day, date, day of week. * 24 hour penetrating alarm. * Quality metal bracelet. * Powered from solar panel. * With battery back-up. * Back-light + auto calendar.</p> <p>£24.95</p> <p>Guaranteed same day despatch</p> 	<p>* QUARTZ LCD ALARM *</p> <p>Snooze + backlight. Batteries last 1 year approx. Includes batteries and travel pouch. Excellent value</p> <p>£17.65</p> <p>Guaranteed same day despatch</p> 	<p>THOUSANDS SOLD</p> <p>11 FUNCTION SLIM CHRONO</p> <p>6 digit 11 functions</p> <p>Hours, mins, secs. * Day, date, day of week. * 1/100, 1/10, secs, 10 x secs, mins. * Split and lap modes. * Back light, auto calendar. * Only 8 mm thick.</p> <p>This same watch is being sold for £22.00 in newspaper and magazine special offer ads.</p> <p>Metac Price £12.65</p> <p>Guaranteed same day despatch</p> 
<p>SEIKO SUPERIOR WATCHES</p> <p>World famous piercing alarm chronograph</p> <p>Please ring for delivery details</p> <p>ALARM CHRONO List price £130 Metac Price £98</p> 	<p>SEIKO SUPERIOR WATCHES</p> <p>Please ring for delivery details</p> <p>CHRONOGRAPH List price £85 METAC PRICE £68</p> 	<p>SEIKO SUPERIOR WATCHES</p> <p>6 digit, 7 function watch with 4 alarms & volume control.</p> <p>Please ring for delivery details.</p> <p>MULTIPLE ALARM List price £120 METAC PRICE £98</p> 	<p>SEIKO SUPERIOR WATCHES</p> <p>Full spec. calculator + 6 function watch.</p> <p>Please ring for delivery details.</p> <p>CALCULATOR WATCH List price £165 METAC PRICE £125</p> 
<p>HANIMEX Electronic LED Alarm Clock</p> <p>Same as ETI offer Thousands sold</p>  <p>Feature and Specification</p> <ul style="list-style-type: none"> ★ Hour/minute display ★ Large LED display with p.m. and alarm on indicator ★ 24 Hours alarm with on-off control ★ Display flashing for power loss indication ★ Repeatabe 9-minute snooze ★ Display bright/dim modes control <p>Size 5.15 x 3.93 x 2.36 (131mm x 100mm x 60mm) Weight: 1.43 lbs (0.65 kg).</p> <p>Guaranteed same day despatch</p> <p>£8.65</p>	<p>GENUINE SOLAR</p> <p>5 function LCD</p> <ul style="list-style-type: none"> * Solar panel with battery back-up. * Back light + auto calendar. * Hours, mins, secs, day, date. * Quality metal bracelet. <p>£10.95</p> <p>Guaranteed same day despatch</p> 	<p>LADIES LCD</p> <p>Only 25 x 20 mm and 6 mm thick. 5 function: hours, mins, secs, day, date, + back light and auto cal. Elegant metal bracelet in silver or gold. State preference.</p> <p>£10.95</p> <p>Guaranteed same day despatch</p> 	<p>ALARM LCD</p> <p>6 digit 7 functions + penetrating alarm.</p> <p>Hours Mins Secs Day Date Alpha Day Year. Back light + 200 year calendar.</p> <p>ONLY £22.95</p> 
<p>All products carry full 12 months guarantee. Please add 30p p&p with all orders. All prices include VAT.</p> <p>Shops open 9.30 to 6.00 daily.</p> <p>Trade enquiries welcome. Delivery: One week. Except where same day delivery is stated.</p>	<p>COMPONENTS</p> <p>2N3055 transistors 50p 2 inch LED's, red 12p green 15p yellow 15p orange 15p</p> <p>DL 704 displays 80p DL 707 displays 80p Watch batteries 70p (state type) Mercury tilt switches 50p Crystal mic. inserts 50p</p> <p>Also useful for sonic applications and sound transmitters (buzzers etc)</p>	<p>GENUINE SOLAR CHRONOGRAPH</p> <p>£16.95</p> <p>6 digit, 11 function. Hours Min Secs 1/100 1/10 Secs Mins Split & lap modes, Auto cal + back light. Powered from solar panel with battery back-up.</p> 	<p>TV GAMES</p>  <p>Black & white £8.95 Colour £12.95. 4 games, 2 ball speeds, 2 ball angles, 2 bat sizes.</p>
<p>METAC Electronics & Time Centre</p> <p>267 HIGH STREET DAVENTRY, NORTHANTS Tel. (032 72) 76545</p> <p>327 EDGWARE ROAD LONDON W2 Tel. (01) 723 4753</p> <p>Barclay & Access welcome Phone or Send Card Number with order</p>  			


SUPERIOR INDUCTION BALANCE METAL DETECTOR



- * Visual meter with audible indication.
- * Distinguishes between gold, silver, copper, bronze and non-ferrous metals and useless metal objects such as bottle tops, etc.
- * Range up to 10 inches on a single coin. Three feet for large objects.
- * Battery lasts 50 hours.
- * Telescopic 2-3 1/2 foot stem.
- * Volume & tuning controls.

METAC PRICE £39.95

LCD CLOCK RADIO

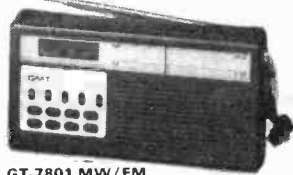

GT-7801 MW/FM LCD CLOCK RADIO. Radio with earphone and DC jack. IC controlled clock gives minimum 15,000 hrs., battery life from UM3x1. Features Wake to music or alarm, sleep timer, snooze, dual time zones, stop watch function, time lock-on/off, back light. 190 x 97 x 43mm.

METAC PRICE £22.95

FLUORESCENT DISPLAY CLOCK RADIO



- * Mains operated
- * Soft glow green display
- * MW/FM radio
- * Alarm with 9 min. snooze feature
- * Programmable play-to-sleep setting

METAC PRICE ONLY £19.95

DIGITAL LED CLOCK



- * Automatic brightness control
- * Weekend alarm cancel
- * 9 minute snooze alarm

OUR PRICE £10.95

MILITARY STYLE RADIO



Medium wave. Long battery life. Good sound reproduction

SPECIAL OFFER

£2.45

CASIO SPORTS WATCH

Model F-100
Black plastic case. (Epoxy based glass filled nylon.) Stop-watch. 11 functions.

METAC DISCOUNT PRICE £23.95

CASIO CHRONOGRAPH 45CS-22B

£49.95

CASIO WORLD TIME WATCH 29cs-11B

£59.95



METAL DETECTOR

BFO Principal Audible indication Telescopic stem Ideal for beginners but also excellent for finding hidden pipes and wires

ONLY £11.95



CBM ALARM WATCH

Superb 6 digit, 8 function alarm watch, with snooze repeater and conference warning bleep. (It bleeps once 4 seconds before alarm sounds giving option to cancel).
Hours - Mins - Secs - Day - Date - Month - Back Light - Auto. Call.



Top quality 'CBM' finish

METAC PRICE £29.95

CBM EXTRA LARGE DIGIT 5 FUNCTION LCD

- * Hours mins secs
- * Month date Auto calendar
- * Back-light
- * Real leather strap
- * Big digits in a slim 9mm thin case
- * Digits 50% larger than all other watches.




METAC SPECIAL OFFER

£9.95

CBM CALCULATORS

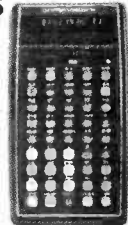METAC Discount price
72 Step programmable model PR100 **£36.85**
Full scientific 3 memory model 4912 **£12.14**
Full scientific 9 memory model 9190 **£29.00**



RADIO CONTROLLED CAR

A fabulous new toy will give hours of fun. Forward and reversing controls. Outdoor range 150 ft. Indoor range 50 ft. A scale model of Bertoni's famous Lancia sports car. List price as sold in well-known mail order catalogues and top stores, £16.

METAC SPECIAL CHRISTMAS PROMOTION OFFER

£10.95



AQ-1000 CALCULATING ALARM CLOCK PLUS 3-WAY STOPWATCH

- * Calculator with %, $\sqrt{\quad}$ & memory.
- * Continuous clock with Hz, mins, secs, day, month, day of week
- * Alarm
- * Stop-watch with 1/10 secs to 10 hours + lap and split-time modes. 1st and 2nd.
- * Batteries last 1 year continuous operation
- * Dimensions 1/2" x 2 3/4" x 4 1/4" in.
- * Complete with leatherette wallet.

LIST PRICE £21.95

METAC SPECIAL EXCLUSIVE PRICE

£19.95

Cannot be found cheaper anywhere else




GOOD QUALITY CALCULATOR MODEL 3000

x + - $\frac{1}{\square}$ memory constant 8 digits with red display

METAC SPECIAL OFFER

£3.95

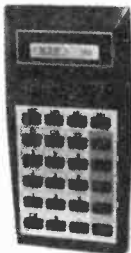

ALARM CHRONOGRAPH WITH DUAL TIME ZONE FACILITY

- Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication.
- Perpetual calendar: day, date, month and year.
- 24 hour alarm with on/off indication
- 1/100 second chronograph measuring net, lap and first and second place times.
- Dual time zone facility. Night light.



TOILET-ROLL HOLDER

Wall mounting reel type. Incorporates good quality medium-wave transistor radio.

SPECIAL OFFER £4.90

- Fully adjustable bracelet.

Please note Metac are probably the only people with this watch in stock. A very good alarm watch.

METAC PRICE ONLY £37.95

PLEASE NOTE

All our products carry full money back 10-day reassurance.

Watches are despatched by **FIRST-CLASS POST**. They are fitted with new batteries, and include guarantee and instructions.

Battery fitting service is available at our shops for no extra charge. We stock most watch batteries and this service is available to all.

Metac have been selling electronic watches probably longer than anyone else in the UK. We take care of your watch not just this year but next year and the years after that.



67 HIGH STREET DAVENTRY, NORTHANTS Tel. (032 72) 76545


METAC Electronics & Time Centre

327 EDGWARE ROAD LONDON W2 Tel. (01) 723 4753

Barclay & Access welcome Phone or Send Card Number with order



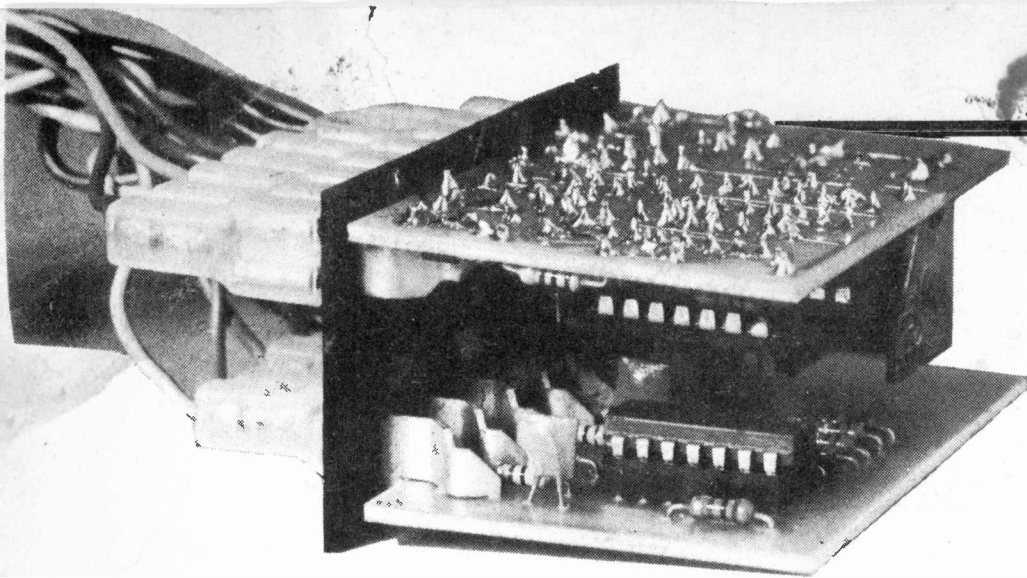1.70
x sent for JAN 76. received & returned.
2nd complaint 7-2-79.
phoned 29-3-79.



A straightforward, low cost design, with a number of sophisticated features, that should protect your car from unwelcome attention.

CAR ALARM

THERE IS ONLY ONE way to ensure that you never have a car stolen and that is not to be stupid enough to buy one in the first place. However accepting the fact that many of us will feel the need to own a car how do we ensure that it remains ours amongst the ever increasing crime levels in this country. Well you could do worse than to fit the alarm system described here. Not *only* does this system protect the car itself, monitoring all doors and disabling the ignition when set, but also offers protection to the car's accessories.

The alarm provides an entry and exit delay before the horn is sounded, this means that there is no need to fit an external lock switch to the car. When leaving, the concealed alarm switch is activated whereupon the owner has 30 seconds before the alarm is set. On entry a 15 second delay is provided.

When triggered the system will sound the horn intermittantly for two minutes before resetting. However, if the initial cause of the alarm is still present, the alarm will retrigger.

The alarm provides for both active high and active low inputs allowing all types of sensor to be employed.

An additional accessory protection module provides an independent monitor of the car's accessories.

Construction is quite straightforward. The use of Incar connectors will allow the unit to be readily fitted and removed from any

BUYLINES

Compu-Tech Systems of 7 Sandhole Lane, Lt Plumstead, Norwich, NR13 5HZ will supply a complete kit of parts for this project.

car. These connectors should be fitted first. The rest of the components can then be fitted as shown in the appropriate overlay. Note that any polarity sensitive device is mounted in the correct position. The main board's jumper should be fitted when construction is complete. If your car's horn has one wire coming from it fit jumper A, if it has two wires with one going to earth also fit jumper A. If the horn has two wires neither going to earth, fit jumper B.

With construction complete the PCBs can be glued into the housing chosen for the alarm.

Installation of the alarm in the car must be left up to the constructor. The overall interconnection diagram is shown and it should be clear how to proceed in general. The detailed installation will however vary widely from car to car.

PARTS LIST

RESISTORS

R1,9	-	1kΩ
R2	-	100R
R3	-	1MΩ
R4,5,7,8,10	-	10MΩ
R6,11	-	4k7
R12	-	47R
R13	-	4M7

CAPACITORS

C1,2	10n ceramic
C3	16u 16 V tantalum
C4,6,7	4u7 16 V tantalum
C5	47n polyester

SEMICONDUCTORS

IC1,2	4001
Q1	BC337
D1-7	1N4148
ZBL	15 V 400mW

SWITCH

SW1 DPDT

RELAY

RLa 12 V 85R with 15A contacts

MISCELLANEOUS

PCB as pattern, connectors, case to suit, cable, etc.

RESISTORS

R14,16,18,20	10k
R15,17,19,21	100k
R22,24	100R
R23	1kΩ

CAPACITORS

C8-13 10n ceramic

SEMICONDUCTORS


IC3	4002
D9	1N4148

SWITCH


SW2 SPST

MISCELLANEOUS


PCB as pattern, connectors, cable, etc.

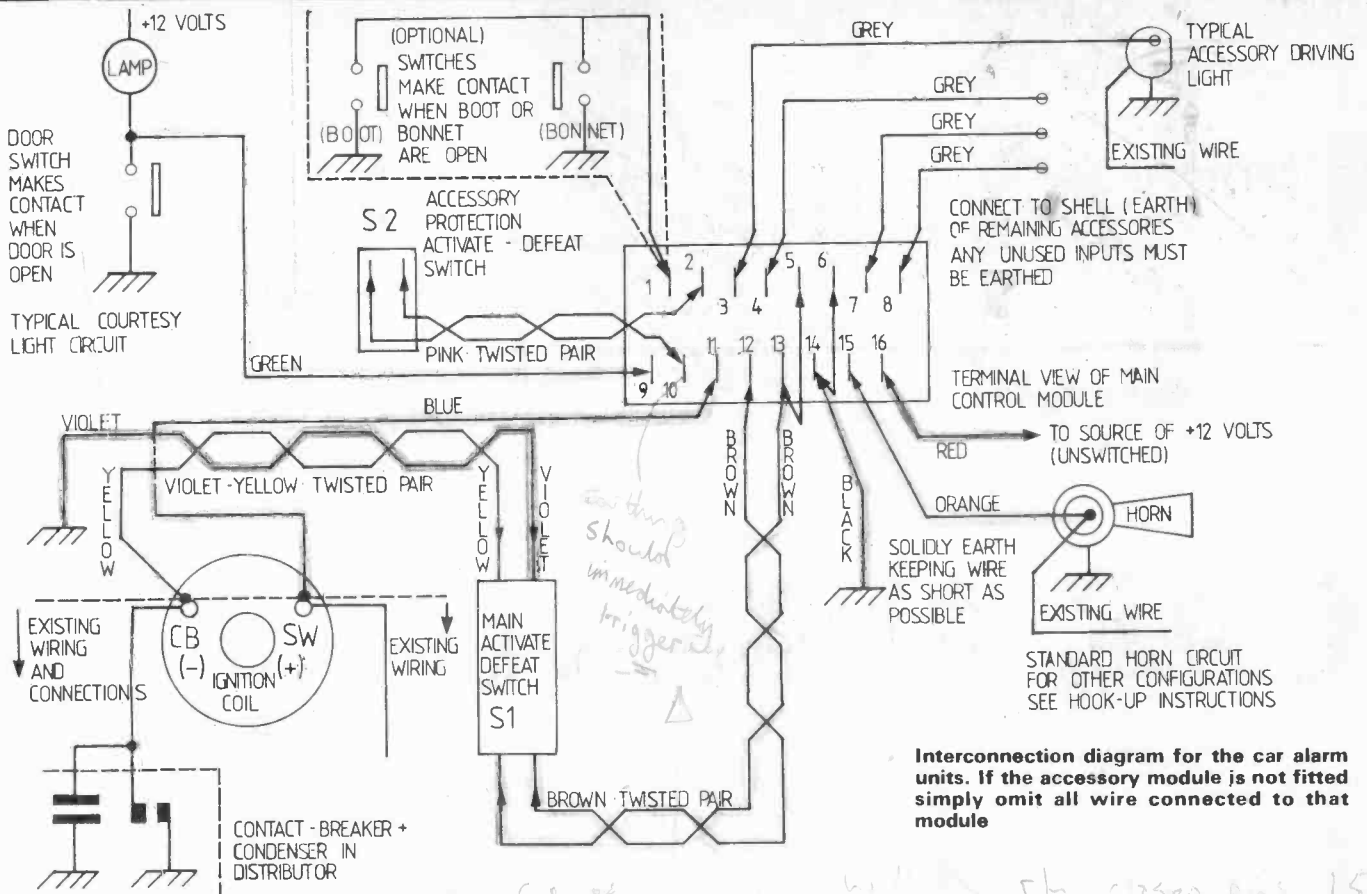


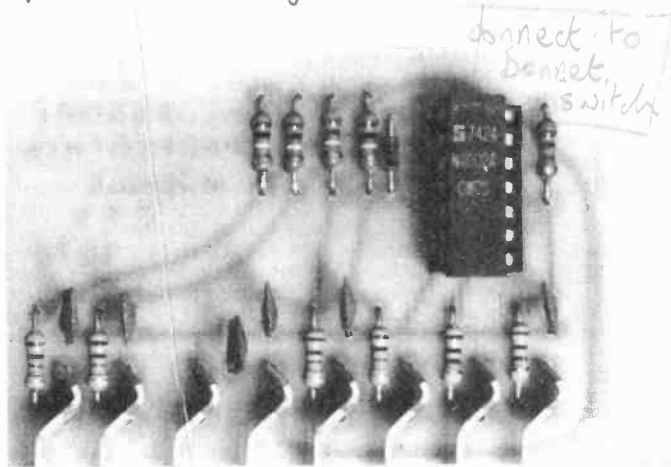
Interconnection diagram for the car alarm units. If the accessory module is not fitted simply omit all wire connected to that module





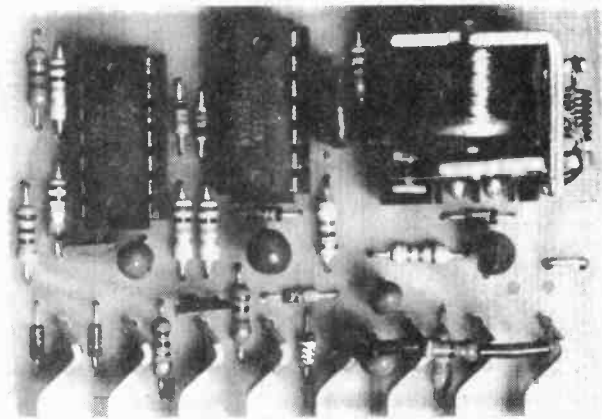Overlay for the accessory protection board.



Overlay for main control board.

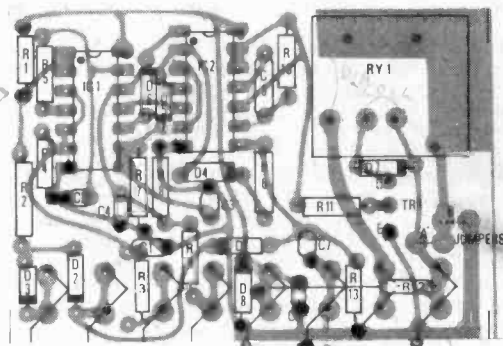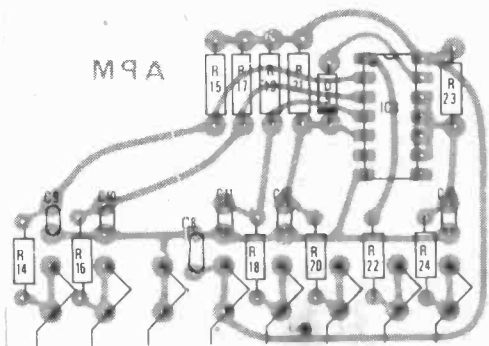

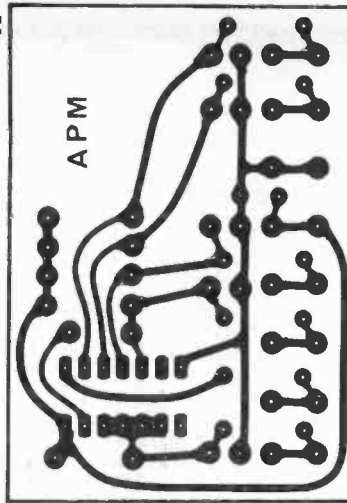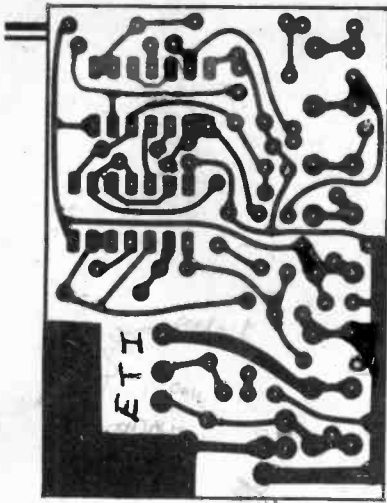

IC1A - either

To the far left is the foil pattern for the main control unit while left is the accessory module's PCB layout.

pulsating "normal" join for

HOW IT WORKS

In the quiescent state with the alarm defeated via S1 the following logic levels are present at the outputs of the gates indicated. IC1a-0, IC1b-1, IC1c-0, IC1d-0, IC2a-1, IC2b-0, IC2c-0, IC2d-1, transistor Q1 is cut-off, and RY1 is de-energized. R12, ZD1 and C6 form an overvoltage and electrical noise suppression circuit that protects the power supply rail of the circuit from spikes and battery overvoltage. The input of IC1a is held at logic 1 by pull-up resistor R1. R2 protects the input of IC1a from noise spikes.

If an earth appears at the inputs taken to D2 and D3 the logic 1 normally present at the input of IC1a changes to logic 0 which is inverted to a logic 1 by IC1a and connected to pin 5 of IC1b. D2 and D3 isolate the two inputs from each other. The input at D2 has a special function which is explained at the end of the text. Pin 6 of IC1b is held at Logic 0 by pull-down resistor R4. R3 and C1 form a noise suppression circuit for this input. If this input goes to +12 volts a logic 1 will be present at pin 6 of IC1b. Thus under normal conditions both inputs of IC1b are at logic 0 and in any alarm condition the input (s) will be at logic 1. Any logic 1 at the input of IC1b will force its output to logic 0. R5 and C2 form another noise suppression circuit to increase the noise immunity and prevent any noise spikes from reaching pin 13 of IC1c.

Whenever S1 is in the DEFEAT position a logic 1 is present at pin 12 of IC1c and pin 1 of IC2b. This logic 1 is buffered by R9 (spike protection). With a logic 1 at pin 12 of IC1c the output of this gate will remain logic 0 and ignore the input at pin 13. The vehicles ignition system works normally with S1 in the DEFEAT position. By placing S1 in the ACTIVATE position an earth is placed across the contact breaker and the vehicles ignition system will be disabled. Also when S1 is in the ACTIVATE position the logic 1 is removed from R9 and C4 will begin to discharge thru R8. D6 prevents C4 from discharging into IC1d.

In approximately 30 seconds C4 will have discharged to the threshold of IC2b pin 1 and IC1c pin 12 and a logic 0 will now be present at these points. The logic 0 present at pin 12 of IC1c will enable it and any alarm condition sensed by the inputs will be reflected by a logic 1 being present at the output of IC1c which is passed to IC2a pin 5. The 30 second delay after S1 changes states to the ACTIVATE position and IC1c being enabled is the EXIT delay.

IC2a and IC2b form a set reset flip-flop with the normal state as a logic 1 at pin 4 of

IC2a. It is set by a logic 1 at pin 5 of IC2a (alarm condition) and is reset by a logic 1 at pin 1 of IC2b (defeated or timed reset/validate condition). Once the flip-flop changes states it can only be changed back again by applying a logic 1 to the opposing input. Thus even a momentary logic 1 at pin 5 of IC2a would latch the flip-flop into the alarm status and initiate the alarm sequence. A momentary logic 1 would be generated by opening one of the vehicles doors and then closing it. When the flip-flop senses a logic 1 at pin 5 of IC2a it will change state and lock with a logic 0 at pin 4 of IC2a.

When the logic 0 appears at pin 4 two things happen: First C7 will begin to discharge through R13. D4 prevents C7 from discharging into IC2a. In approximately 15 seconds C7 will have discharged to the threshold of IC2c and a logic 0 will be present. With a logic 0 at pin 8 of IC2c the 1 Hertz astable multivibrator formed by IC2c, IC2d, R10 and C5 is enabled. Pin 10 of IC2c will alternate between logic and Logic 1 at a 1 Hertz rate driving Q1 in and out of condition via R11. As Q1 goes in and out of conduction RY1 energizes and de-energizes, closing and opening the contacts. These contacts are wired thru jumper "A" or "B" providing a pulsating +12V or pulsating earth which is connected to the horn circuit sounding the horn and raising the alarm. The 15 second delay between the flip-flop changing states (alarm detected) and the horn beginning to sound is the ENTRY delay.

The second thing that happen when the flip-flop changes states is that C3 will begin to discharge thru R7. D5 prevents C3 from discharging into IC2a. In approximately 2 minutes C3 will have discharged to the threshold potential of IC1d and a logic 0 will be present. IC1d inverts this to a logic 1 and presents it via D6 to pin 1 of IC2b resetting the flip-flop and to pin 12 of IC1c inhibiting the alarm condition (if present) from reaching IC2a. When the flip-flop resets a regenerative action takes place and begins to recharge C3 and C7. When C3 has charged past the threshold of IC1d a logic 0 will be present at its output and IC1c will be enable in a few seconds as the small charge placed on C4 prior to the regenerative action will have discharged thru R8. If the alarm is no longer present C3 and C7 will completely charge and the alarm will reset and wait for another intrusion. If the alarm condition is still present the flip-flop will again latch and the small charges that developed on C3 and C7 will discharge thru R7 and R13 respectively

in a few seconds. Thus every two minutes the alarm will reset itself for approximately 3 seconds and then start over again.

This cycle is the RESET/VALIDATE cycle and is provided to prevent the battery from being completely discharged by a momentary intrusion. The input T(OD)2 is a special function input and is for use with the accessory protection module. When this input goes to earth C7 is immediately discharged via D1 and the alarm will begin to sound, R6 prevents IC2a from being destroyed by the pull-down action. This earth is sensed by IC1a and will latch the alarm (providing the exit delay cycle is complete). This input is verified by the RESET/VALIDATE cycle in the manner described above. The main ACTIVATE/DEFEAT switch S1 does not affect this input making it completely independent of the main system.


Accessory Protection Module — Theory of Operation

In the quiescent state IC3a output is logic 1 and the output of IC3b is logic 0. Under normal conditions, i.e. no alarms sensed, all inputs to IC3a will logic 0 (sunk to earth via R14, R16, R18, R20 and the sense wires). The input to IC3b will be open or at +12 volts, R23 being the pull-up resistor for an open circuit, R23-C13 are noise suppression components. C8 by-passes any noise present on the supply rail to earth. If any of the sense wires open R15, R17, R19, or R21 will pull the respective input to logic 1. C9 thru C12 in conjunction with R14, R16, R18, R20 form a noise suppression circuit for these inputs. Any logic 1 present at IC3a inputs will result in a logic 0 at the output which is connected via buffer resistor R22 to the unit's output. This is connected through ACTIVATE/DEFEAT switch S2 to the main control unit. S2 has been provided to make the accessory protection system independent of the main system and will normally be activated continuously.


An earth at the active low I/P will force the output of IC3b to logic 1. This logic 1 is coupled via D9 to IC3a forcing pin 5 to logic 1 regardless of the status of the sense wire this will result in a logic 0 at the output of IC3a as explained above. D9 is provided to that IC3b can only force pin 5 of IC3a to logic 1, it cannot force it to Logic 0.

Any time a logic 0 is present at terminal () and S2 is in the activate position the alarm will sound immediately as explained in the description of the main control unit.

PROJECT: Car Alarm

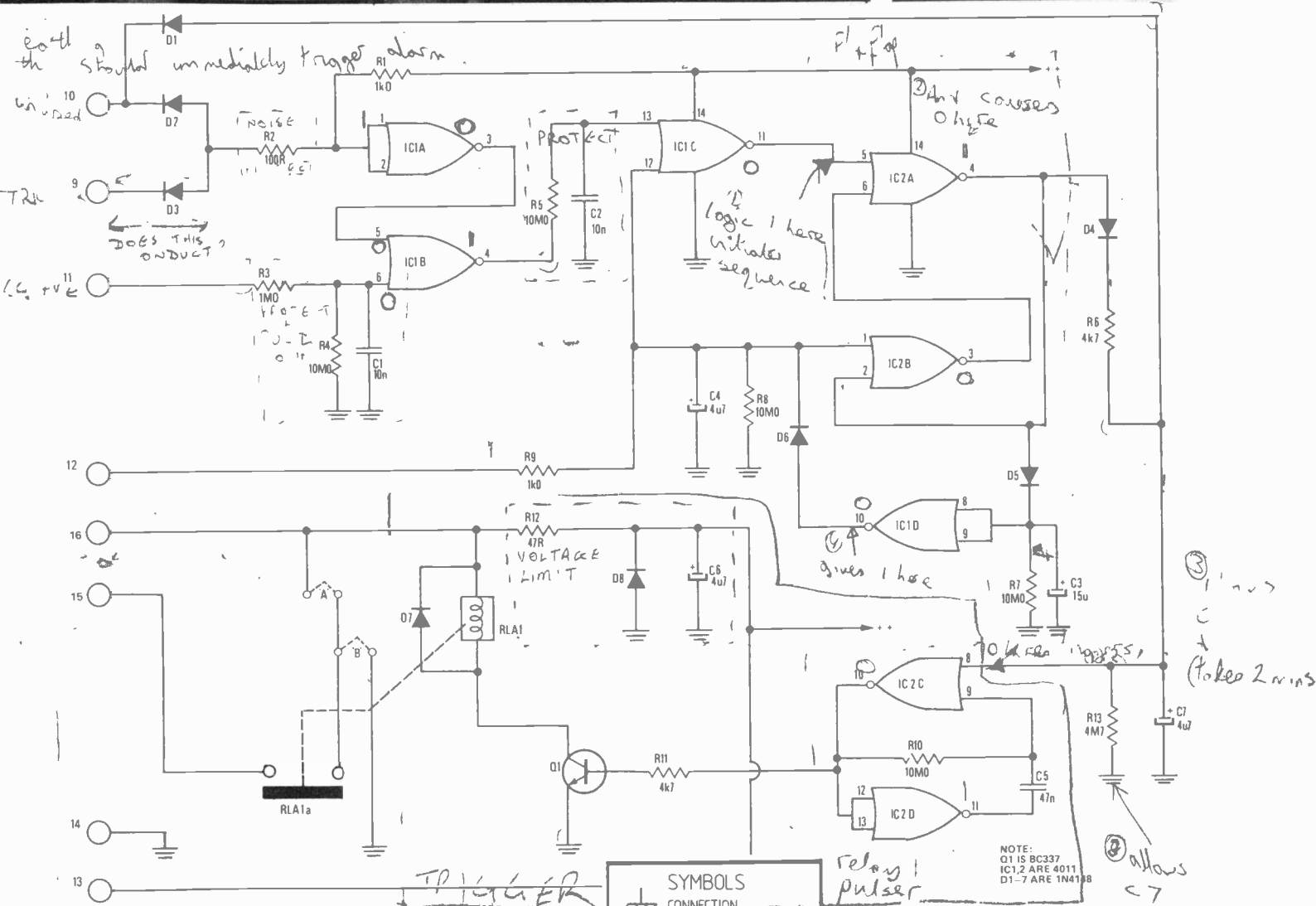

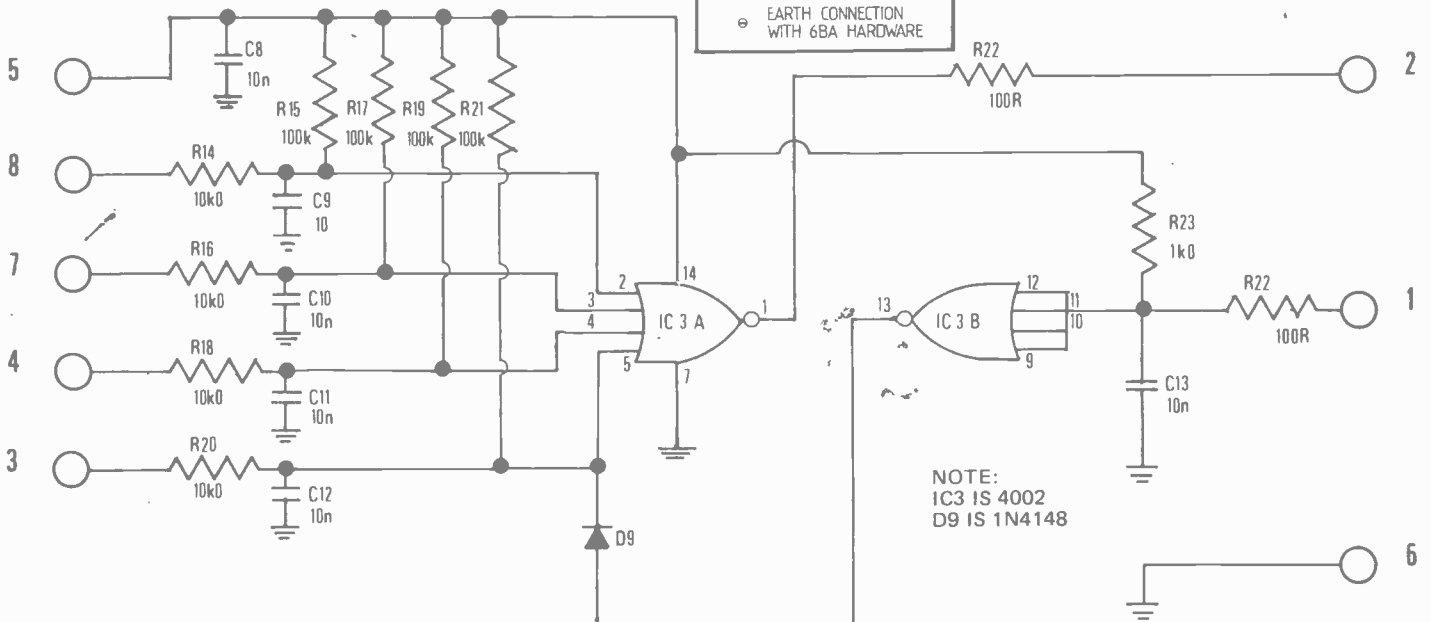Circuit diagram of the main control unit.



OSTS "One Stop Technology Shopping" now from **ambit international** ®

Ambit stoppress...news on items available.....KV1210: triple AM tuning diode with 2-9v bias only £2.75....DT1200 Digital frequency readout module 91T223 ultra low THD/IMD mpX decoder module £9.95.....944378 'Hyperfi' mpX decoder with post decoder muting and pilot cancel £19.95..... V MOS

COUNTER ATTRACTIONS:

New this month from Intersil, the ICM 7216. This is probably the most significant new IC for frequency counter/timer applications ever devised. It drives a full 8 digit display (LED) and operates on inputs up to 10MHz minimum. The single 28 pin DIL also has: *Leading zero blanking *Frequency ratio *Period *Unit counter *Time Interval *overrange. The IC cost is £19.82, and the 10MHz HC18U Xtal £2.50 (for timebase functions). The circuit data is free with the IC, or £1 purchased separately. Input preamp board £7.00.

New from Ambit is the MC3357, 6v, 2mA standby NBFM IF, detector and squelch with 10.7 - 455 kHz balanced mixer, onboard oscillator device, and 5uV sensitivity. It is ideally suited to our CFM and LFY filter series, and costs £3.12 with full data. Xtal £2.50.

Please note that OSTs prices exclude VAT at 8% throughout this side of the page. Most ambit items are at 12% except those marked *. Please keep orders separately totalled, although a single combined payment, and 25p postage charge, will be sufficient.

CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4016	52p	4074	20p	4541	141p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	60p	4078	20p	4554	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	75p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	100p	4561	65p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4580	600p
4033	145p	4162	90p	4581	218p
4034	200p	4163	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4586	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	96p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	55p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

Micromarket PRICES SLASHED

8800 series	8216 1.95	2114 £10
6800P 6.50	8224 3.50	2708 £10.55
6820P £6	8228 4.78	
6850P 2.75	8251 6.25	
6810P £4	8255 5.40	
6852 3.65		
MEMORIES		
8080 series	2102 £1.70	
8080 6.30	2112 £3.40	
8212 2.30	2513 £7.54	
	4027 £5.78	

Voltage Regs

NEW LOW PRICES	
7800 series UC TO220 package 1A all 95p	
7900 series UC TO220 package 1A all £1	
78MUC series TO220 package 1/2A all 90p	
78LCP series TO92 100mA all 35p	
L200 up to 3A/adjustable V&A 195p	
78MGT2C 1/2amp adjustable volts 175p	
79MGT2C 1/2amp adjustable volts 175p	
723C precision controller 65p	
MAINS FILTERS FOR NOISE/RFI etc	
1 amp in 1EC connector £4.83	
5 amp in 'wire in' case £3.87	
NE550A 73p	

LINEARS non-consumer

BLMOS	LM324N 71p
LM339N 66p	
LM348N 186p	
LM3900N 60p	
LM3410T 35p	
CA3140T 72p	
709HC to5 64p	
CA3160E 90p	
709PC diil 36p	
CA3160T 99p	
710HC to5 65p	
710PC diil 59p	
723CN 66p	
741CN to5 66p	
LM301AH 67p	
LM301AN 30p	
LM308N 121p	
747CN 77p	
LM308N 121p	
LM318N 279p	
LM318N 224p	
NE531N 105p	

OPTO 7 seg displays

0.43" High Efficiency HP:	
5082: 7650 red CA } 233p	
5082: 7653 red CC } 233p	
5082: 7660 yellow CA } 233p	
5082: 7663 yellow CC } 233p	
5082: 7670 green CA } 233p	
5082: 7673 green CC } 233p	
0.3" Standard HP	
5082: 7730 red CA } 147p	
5082: 7740 red CC } 147p	
0.5" Fairchild	
FND500 red CC £50p	
FND507 red CA £50p	

TLL: Standard AND LP Schottky

All prices listed in pence *

N	LSN	N	LSN	N	LSN	N	LSN	N	LSN	
7400	13	20	7455	35	24	74126	57	44	74185	134
7401	13	20	7460	17	24	74128	74		74188	275
7402	14	20	7463		24	74132	73	78	74190	115
7403	14	20	7470	28	24	74133		29	74191	
7404	14	24	7472	28	74	74136	22	40	74192	105
7405	18	26	7473	32	74	74138	60	74	74193	180
7406	38	7474	27	38	74139	60	74194	105	87	137
7407	38	7475	38	40	74141	56	74195	95	137	ICL7106CP - LCD
7408	17	24	7476	37	74142	265	74196	99	110	DVIM IC £95.55
7409	17	24	7478		74143	312	74197	85	110	KIT £24.80
7410	15	24	7480	48	74144	312	74198	150		LED DVM with ICL7107 £20.65
7411	20	24	7481	86	74145	65	74199	160		
7412	17	24	7482	69	74147	175	74248		90	Ambit overspill
7413	30	24	7483A		74148	109	74261		90	the remainder of the
7414	51	130	7484	97	74150	99	74253		108	column is not OSTs
7415	30	24	7485	104	99	74151	64	84	74257	
7416	30	24	7486	61	40	74153	64	54	74279	
7417	30	24	7489	205	90	74154	96	110	74283	
7420	16	24	7490	33	90	74155	54	110	74290	
7421	29	24	7491	76	110	74156	80	110	74295	
7422	24	24	7492	38	78	74157	67	55	74298	
7423	27	24	7493	32	99	74159		60	74258	
7424	27	24	7494	20	90	74160		210	74260	
7426	36	27	7495A	65	99	74169	210	130	74365	
7427	27	29	7496	58	120	74161	92	78	74366	
7428	35	32	7497	185	74162	92	130	74367	49	43 matching to a max of 6 diodes
7430	17	24	74100	119	74163	92	78	74368	49	per diode (1%)
7432	25	24	74104	63	74164	104	74375	60	74379	
7433	40	32	74105	62	74165	105	74399	130	150	KV1210 275p
7437	40	24	74107	32	38	74167	20	74447	92	PIN & switching
7438	33	24	74109	63	38	74168	20	74475	92	VAT 12.5%
7440	17	24	74110	54	74168			74477	90	BA479 pin 35p
7441	74	24	74111	68	74169			74490	140	tda1061 pi-network
7442	70	99	74112	88	74170	230	200	74668	110	attenuator
7443	115	74	74113	38	74172	625	200			BA182 bandswitch diode 21p
7444	112	74	74114	38	74173	170				10 for 150p
7445	94	74	74116	198	74174	87	120	NE555	30p	Requests for
7446	94	74	74118	93	74175	87	110	NE558	78p	the next issue of the
7447	82	74	74119	119	74176	75		NE558	180p	catalogue now being
7448	56	99	74120	115	74177	78		LM3909	72p	"booked" for des-
7449	99	74121	25	74180	85			11C900C	1400p	patch immediately
7450	17	24	74122	46	74181	165	350			is ready (about
7451	17	24	74123	48	74182	160				November).
7453	17	24	74124	38	74183					Please send 45p to reserve
7454	27	24	74126	38	74184	135	210			a copy.

From the World's leading radio innovation source:

Apart from the MC3357, mentioned alongside, Ambit has the first easy-to-use low noise, low cost UHF dual gate MOSFET - the BF960 from Siemens. With a gain of 18dB, and a noise figure of only 2.8dB at 800MHz, you will see what we mean. At 200 MHz, the gain is 23dB, and NF only 1.6dB. Combine these figures with the famous ease of use of a dual gate MOSFET, and you have the easiest and most effective front end device yet. £1.60 each

Moving Coil Meters

Ambit offers a very wide range of low cost meters, together with the unique 'Meter Made' scale system for professional grade scale customizing:

Series	Scale Area	illumination	cost*
900	14x31mm	internal 12v	250p
920	30x50mm	from behind	275p
930	36x63mm	internal 12v	375p
940	36x63mm	from behind	350p
950	55x45mm	from behind	300p

Stock movement 200uA/750uL. The 930 series is 5% linear, others are 77uA at 50% FSD. These and many others available in quantity for OEMs. SAE for full scale details please. (Not in cat.)

Coils & Filters by TOKO

After a period of relative price stability, please note that some prices are increased as a direct result of the failure of £ versus stronger trading currencies. (Mainly Yen)

7 & 10mm IFts for AM/FM - 1000s	
455/470kHz	most types of appcos 30p
10.7MHz	80p
Short Wave Coils sets	
Now two ranges of illumination/coupling ea 33p	
TV video and sound IFs/detectors	
Another new range in 10mm	33p
6MHz ceramic IF sound filter	80p
Molded VHF coils full catalogue 15p	
Ultra stable coils for 30 - 200MHz from 20p	
Chokes - biggest range/biggest stocks	
Most £12 values ex stock, any to order	
78A series 1uH to 1mH	16p
88R series 100uH to 33mH	19p
108R series 33mH to 120mH	33p
FM IF FILTERS ceramic and linear phase	
CFSE/SE10.7 stereo ceramic IF 10.7MHz	
filters in 5 groups	50p
CF5B10.7 mono/roofing IF filter	50p
88R3125N 4pole linear phase 10.7MHz	150p
88R3132A 6pole linear phase 10.7MHz	250p
MPX pilot tone filters for 19 & 38kHz	
BLR3107N Stereo 4k7 impedance	215p
BLR2007 Stereo 3k3 impedance	220p
BLR3152 Mono 4k7 impedance	100p
BLR3157 Mono 4k7/3k0 imp	100p
AM/FM/SSB IF FILTERS	
MFL series 2.4kHz ssb 455kHz carrier	1195p
MFH series 4/5.7kHz BW on 455kHz	195p
MFK series 7/9kHz BW on 455kHz	165p
LFY455D 12kHz 4 ele ladder on 455kHz	125p
CFM2455 6kHz micro mechanical	65p
SFD455/470kHz murata 1F filter	85p
CFT455B/C 6/8kHz min 4 21FTs	60p
CFU470C 6kHz on 470kHz	65p
Ratio Detectors for FM/NBFM	
TA6517/7 455kHz ratio det	135p
KA1N508/9 10.7MHz ratio detector	66p
94ACS1106/7 10.7MHz ratio detector	66p
Quadrature detectors for CA3089E etc	
CA3CSK586NH single	33p
CA3CS4342/3 double	66p
Polyarcon tuning capacitors + trimmers	
2A20S71 2x265p AM	95p
CY22121Z 2x35p AM	
2x20p FM	175p
CY23217PX 2x35p FM	
3x20p FM (2 trimmers)	245p

Radio/Audio/Comms ICs:

Only the very best quality - and only types we have used in our laboratory tests	
Radio frequency + mixers + oscillator(s)	
TDA1062	DC to VHF front end system 1.95

HOW IT WORKS~ TELEVISION RECEIVERS

Ever wondered just how your TV actually works — all those cunningly interconnected and interrelated bits of high-voltage circuitry? Gordon King takes a good long look in this, the first of a series of How It Works articles based around consumer electronics products.

THIS FIRST ARTICLE in the 'How It Works' series looks at monochrome television based on a recent mains/ battery chassis from Thorn Consumer Electronics. In addition to providing an insight into modern television technology the article is also styled to give a fair impression of how the picture is developed on the screen of the picture tube. The basic principles are common to all receivers except that for the reception of colour there are circuit additions for the decoding of the colour information (and a tricolour tube for display!)

Sound and vision signals are modulated on to two carrier waves, the former using frequency-modulation (FM) and the latter amplitude-modulation (AM). On the prevailing UK 625-line system the signals are transmitted in Bands IV and V which are located in the UHF spectrum. Each channel occupies a width of 8MHz with the sound carrier being 6MHz above the vision carrier. For example, Channel 21 has sound and vision frequencies of 477.25 and 471.25 MHz respectively,

while the frequencies for Channel 68 are 853.25 and 847.25 MHz.


Vision modulation is negative-going (see Fig. 3) and is transmitted in 5.5MHz upper sideband and 1.25MHz lower sideband. Peak FM deviation is 50kHz (as distinct from 75kHz on FM sound radio) based on 50µs pre-emphasis. Ratio of peak vision to peak sound power is 5:1. Further information on the signal is given later.


Tuner-Front-End

The start of any television receiver is the 'front-end' or tuner (Fig. 1), whose job it is to select the required channel and to convert the sound and vision carriers to lower frequency ones for subsequent intermediate-frequency (IF) amplification and response tailoring. In Fig. 1 the aerial signals are coupled to an aperiodic RF amplifier, VT1, through an 'isolator' for preventing spurious mains voltages in the receiver from reaching

Fig 1. Circuit diagram of UHF varicap tuner, which uses two RF amplifiers and a mixer stage. Resonant lines tuned by capacitor-

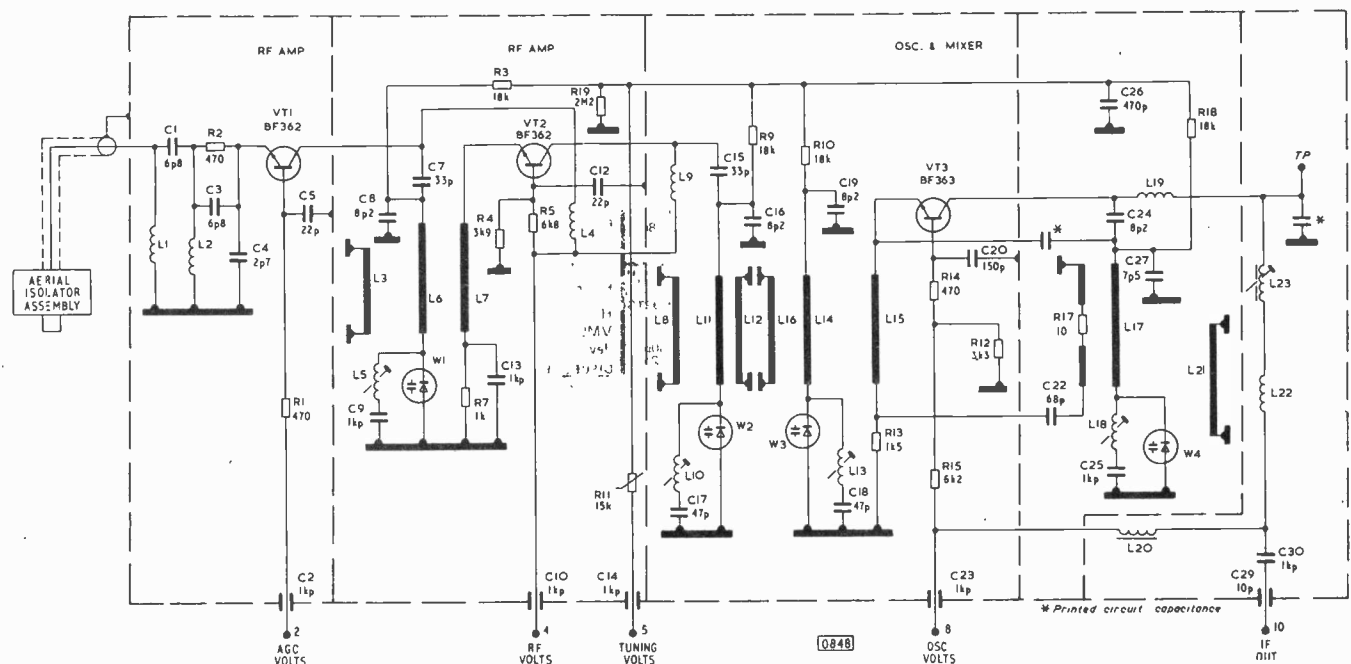diodes select the required channel and provide the necessary front-end selectivity.



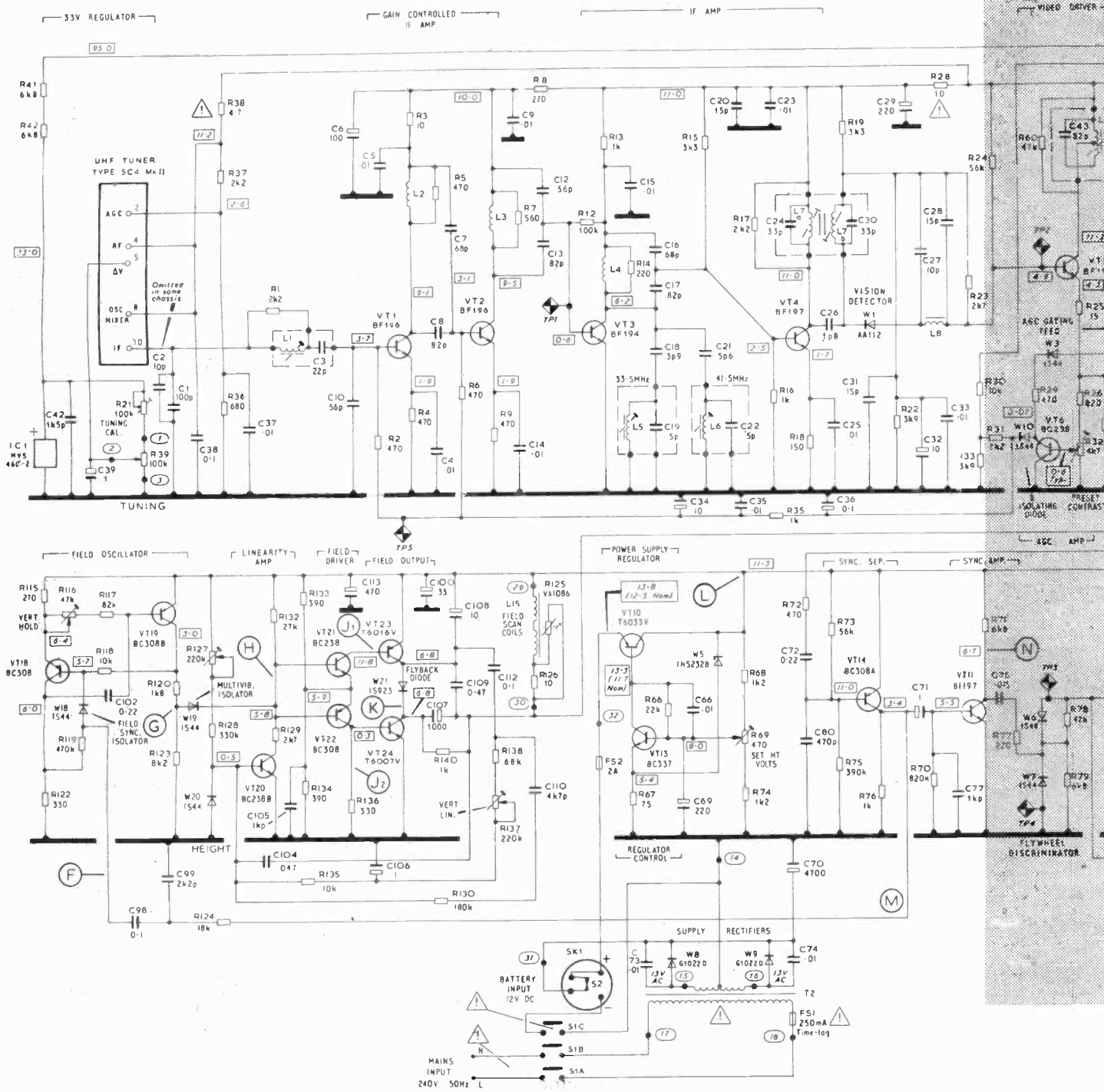

the aerial at lethal power! The transistor is in common-base mode so that the input is applied to the low-impedance emitter. Further input matching is provided by the emitter components and the base is biased either from a constant potential or from an AGC potential (see later).

VT2 is a tuned RF amplifier, also in common-base mode, but the tuning is by resonant lines rather than coils. Any transmission line whose length is adjusted to correspond to a tuned frequency is the equivalent of a tuned LC circuit. An open-circuit line is resonant at $1/2$, $3/2$, $5/2$, etc. wavelength. Excluding velocity factor,

the physical length of a line for, say, Channel 33 would be around 280mm. Happily, it is possible to reduce the physical length while retaining the required electrical length by cutting off the ends of the line and replacing them with capacitance, which reduces the physical length to about 50mm. Moreover, tuning the channels then becomes a question of varying the capacitance at one end.

Looking at line L6 in Fig. 1 shows that the bottom connects to varicap W1 and the top to C8 and VT1 collector capacitance. A varicap is essentially a junction diode. As the reverse bias is increased so the depletion

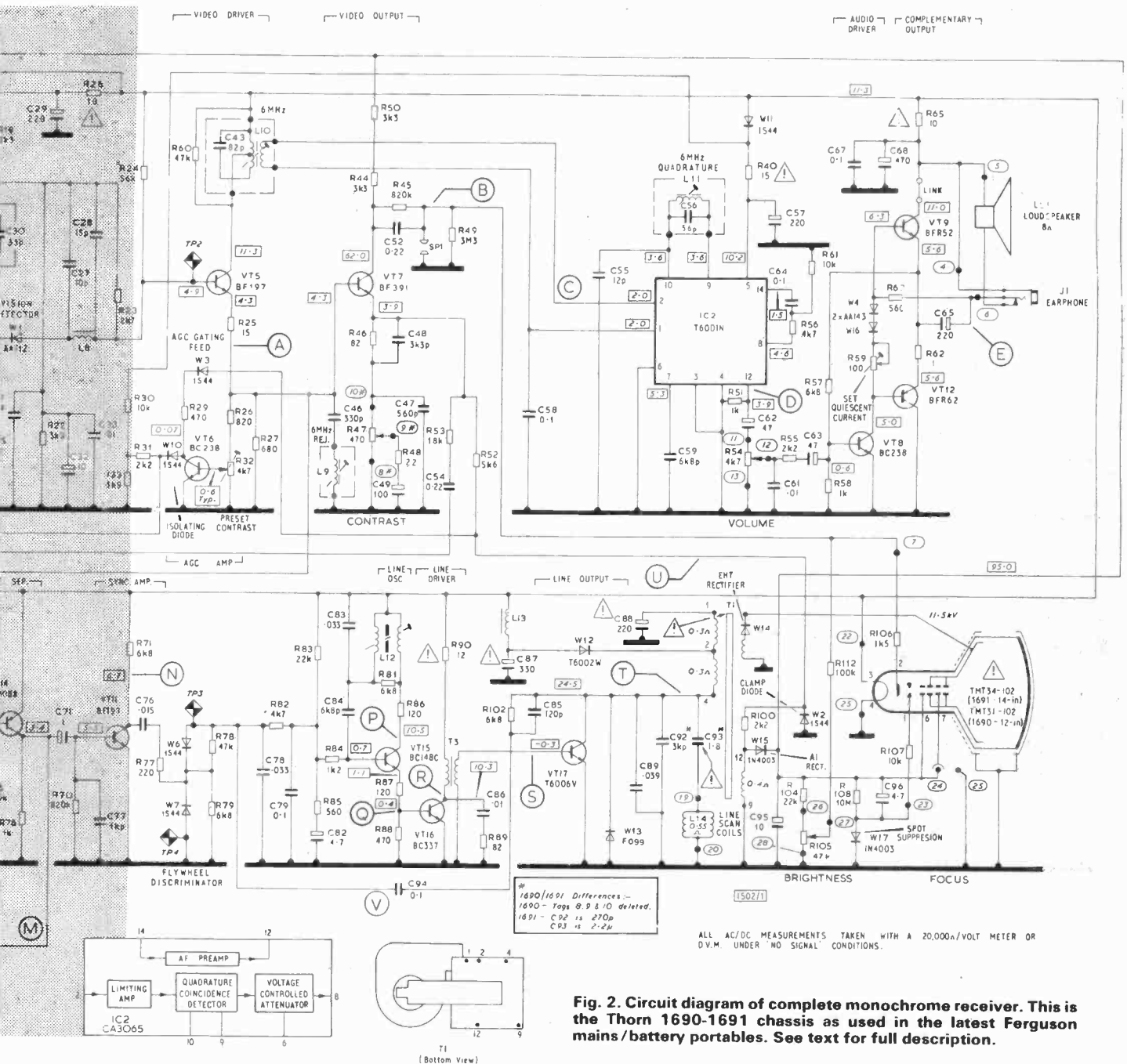


Fig. 2. Circuit diagram of complete monochrome receiver. This is the Thorn 1690-1691 chassis as used in the latest Ferguson mains/battery portables. See text for full description.

region widens, and as this constitutes the dielectric between the n and p regions. The effect is tantamount to the two plates of a capacitor being moved away from each other, with a consequent reduction in capacitance. The four varicaps in Fig. 1 are biased by a positive potential being applied to the 'tuning volts' input. The potential is obtained from a stabilised (by IC1) supply in the main chassis (Fig. 2) via tuning potentiometer R39. Thus as this control is tuned so the resonance frequency of the lines alter in step and tune over the UHF channels.


The second RF amplifier stage VT2 starts to give selectivity. Emitter coupling is via low impedance aperiodic line L7. Further selectivity is provided by the bandpass coupling between VT2 collector and VT3 emitter formed by lines L11, L12, L16 and L14, tuned

by varicaps W2 and W3. Common-base VT3 uses collector/emitter feedback for the local oscillator tuned by line L17 and varicap W4. Line L15 couples the RF signal to the oscillator/mixer stage. The circuits are trimmed by L5, L10, L13 and L18 (so they all tune in step), while the closed lines L3, L8 and L21 also assist with the tuning and matching.

The oscillator is arranged to operate at the IF frequency above the input frequency, and additive mixing yields the IF output, which is resonated by L23 and associated components. The IF signal is coupled to the IF input of Fig. 2 via C30. The high degree of selectivity minimises spurious responses such as image, IF, repeat spot, etc., while also providing a good 3rd-order intermodulation rejection ratio. This is further

Oscillograms

These were taken from a typical receiver at the points indicated by corresponding letters in the circuit diagram. The voltage and time figures refer to the sensitivity per division of the graticule. The receiver was set up for normal reception (test card with tone on sound) and the oscillograms were taken via a +10 probe having an input capacitance of 12pF in parallel with 10MΩ. The mixed mode timebase facility was used for G and M.

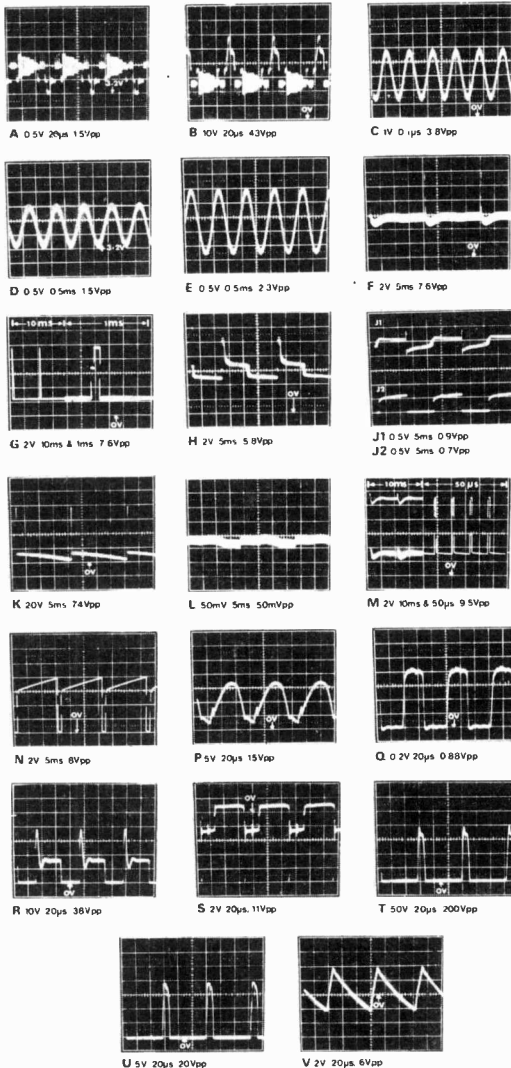

aided by the nature of the transistor and design of the first stage VT1.

The circuit also reveals various signal coupling, decoupling and isolating components, which are essential for the stable performance of this important part of the receiver. The tuner is built into a fully screened box with feed-through capacitors for the inputs and outputs.

IF Channel

Sound and vision signals of the selected channel undergo amplification with bandpass and selectivity tailoring in the IF channel comprising VT1/2/3/4. Tuner signal is applied to VT1 base from the tuned coupling L1/C3, and the amplified and bandpass defined output is yielded by transformer L7a/b. Gain is controlled automatically (AGC) to suit the level of the

input signal by a bias fed to the bases of VT1 and VT2. The four stages are each in common-emitter mode, and impedance matching at the couplings is achieved essentially by capacitor divide-down.

The bandpass characteristic is provided in the main by L1/C1/C3/C10/R1 at the input and by L7a/b at the output. Additional selectivity is provided by collector inductors L2/L3/L4, while sound and adjacent channel sound rejections are introduced at 33.5MHz by L5/C18/C19MHz and at 41.5MHz by L6/C21/C22.

With the 625 line system (system 'I' is used in the UK) the sound carrier is 6MHz above the vision carrier, but because the local oscillator of the tuner is working at the IF above the signal frequencies, the IF appears at 33.5MHz for sound, which is 6MHz below the 39.5MHz vision IF. The sound and vision signals are handled simultaneously by the IF channel, which is possible because frequency modulation (FM) is used for the sound signal. Vision bandwidth of the 'I' system is 5.5MHz upper sideband, accommodated by the IF bandwidth, and overall channel width 8MHz.

Vision Detector

Sound and vision signals from L7b are coupled to vision detector W1, which yields a changing amplitude output corresponding to the picture information (Fig. 3) and also an output at 6MHz resulting from intermodulation of the sound and vision signals by the diode non-linearity, the difference frequency of the two signals being 6MHz. The intercarrier sound signal (as it is called) retains the FM of the sound signal because this is one of the components from which it is derived.

If the ratio of the levels of the sound and vision signals is incorrect a buzz occurs on sound — called intercarrier buzz. Hence the reason for the 33.5MHz trap, which sets the sound signal level below that of the vision carrier while helping to establish one side of the bandpass. The 41.5MHz trap avoids the sound signal from the next channel causing interference while helping to establish the other side of the bandpass. The vision carrier is set 6dB down the response to equalise for the single side band signal.

Video Channel

Picture and intercarrier signals from W1 are directly coupled to the base of the video driver VT5 via low-pass filter L8/C27/C28, which removes residual IF signal. VT5 collector is loaded into transformer L10 which tunes the 6MHz intercarrier signal and couples it to the sound section for FM demodulation and subsequent pre and power amplification for driving the loudspeaker.

VT5 also serves as an emitter-follower for the video signal with network R26/R27/R32 as the load. The signal across this is directly coupled to the base of the video output transistor VT7, which feeds negative-going picture signal to the cathode of the picture tube from its collector. A series rejector L9/C46 tuned to 6MHz is also active at VT7 base to prevent intercarrier signal from getting into the video output stage, where it would cause picture interference. The level of video signal reaching the tube is adjustable by R47, the contrast control, which is a kind of current feed-back control working by the progressive shunting effect across R47 emitter resistor by R48. C49 is a DC isolator. Video-frequency compensation is also provided by capacitors in the feedback loop.

Automatic Gain Control (AGC)

VT5 base is biased from a resistive divider complex (R24/R33/R22/etc.) from the supply rail. It is also partly biased from rectified IF signal at W1 anode, and since direct-coupling is used an increase in IF signal level results in a reduction in positive bias at VT5 base and hence a fall in potential across VT5 emitter load.

The voltage across R32 (the preset contrast control part of the load) is fed to the base of the AGC amplifier VT6 at a level established by the setting of the control. Because VT6 collector is energised via W3 from positive-going 5Vpp pulses derived from a winding on the line output transformer (bottom right-hand corner of Fig. 2, next to the picture tube), the transistor conducts only during the line sync pulses when there is no picture content which the AGC circuit might otherwise falsely read. The degree of conduction and hence the level of the collector potential are determined by the DC level of the line sync pulses at VT6 base. This is called line-gated AGC.

Thus with increase in input signal level (such as when tuning to a stronger channel) VT6 is turned down and the positive potential at its collector rises. This is reflected via forward conducting W10 to the bases of VT1 and VT2 by way of R2/R6 and the filter consisting of C34/C35/C36/R35, which removes line pulses. The small-signal transistors VT1 and VT2 are the type designed for forward AGC; that is, increased gain reduction resulting from positive-going AGC potential.

The preset contrast control R32 sets the operating range of the AGC. With a test card signal of average strength the control is adjusted for 1.5Vpp picture *plus* sync signal at VT5 base.

Some sets include delayed AGC for the tuner RF amplifier which comes into effect after the gain has been reduced initially on a strong signal by the IF AGC; but for the monochrome portable this is barely necessary as maximum front-end gain is generally necessary for most of the time for the best signal-to-noise ratio when a simple set-top aerial is utilised. It will be seen that the tuner 'block' in Fig. 2 has an AGC input which, in this model, is terminated to a supply potential-divider.

Field Timebase

The electron beam needs to be deflected both vertically and horizontally to build up the raster upon which the picture appears. The vertical deflection is handled by the field timebase which deflects the beam from the top to the bottom (scanning stroke) and then very swiftly back to the top again (retrace) at 50 Hz repetition rate.

This is achieved by a 50Hz sawtooth current passing through the field scan coils (L15) on the tube neck. The oscillatory requirements are provided by the field oscillator VT18/19, which is an RC multivibrator. The retrace is initiated by the arrival of a field sync pulse at VT18 base (see later), while the repetition rate is determined by the vertical hold control R116 with R117/118 and C102.

Consider the circuit during the scanning stroke when a rising voltage (ramp) occurs at the base of high-gain amplifier VT20 owing to C104 charging through R127/128. This turns on VT20, VT22 and VT24, and turns off VT21 and VT23. At the conclusion of the stroke VT24 is fully 'bottomed', at which time a positive-going

pulse from VT19 collector 'hits' the bases of VT21 and VT22 via the multivibrator isolating diode W19. The pulse is initiated from the field sync action. The retrace is thus triggered by VT21 and VT23 turning on, and VT22 and VT24 turning off.

During the retrace, VT24 collector voltage rises at a rate established by the L/R ratio of the scan coils, and when the supply line voltage is exceeded W21 goes into reverse conduction and VT23 is isolated. The rate of rise is then defined by C109. After a peak, the retrace voltage falls until W21 goes into forward conduction again. This allows the remainder of the retrace energy to be fed back into the supply line, after which the scanning stroke recommences.

The resulting rise in current through the field scan coils during the scanning stroke produces a magnetic field such that the electron beam is drawn downwards. To avoid vertical non-linearity for the display the *rate of change of current* must be linear. Owing to resistive losses in the scan coils and circuit non-linearities, a slight correction to the current waveform is required, and this is achieved by a parabola waveform produced by R138/R137/C106 being added to the ramp via the linearity amplifier VT20. The degree of correction is adjustable by the vertical linearity control R137.

When the retrace is initiated the rapid reversal of scan coil current deflects the beam swiftly upwards to start a new downward scan, and during the retrace diode W20 goes hard into forward conduction so that the base of VT20 is clamped to earth.

Line Timebase

Horizontal deflection of the beam is achieved by the line timebase driving a sawtooth current wave through the line scan coils (L14) during the scanning stroke. Deflection is from left to right, and at the end of the scanning stroke a swift reversal of current deflects the beam back to its starting point again. During the retrace a considerable amount of energy stored in the inductive elements of the line output stage is released to provide the extra high tension (EHT) for the final anode and the high voltage for the first anode (A1) of the picture tube. Boosted voltage is also used to energise the line output transistor VT17 once the line oscillator has started.

Line repetition rate of the 625 line system is 15625Hz. Thus the horizontal rate is significantly greater than the vertical rate. We have seen that in the UK the vertical rate is 50Hz. This means, then, that a raster of 312½ lines is produced (15 625/50). For a complete picture there are two vertical scans, each producing a raster of 312½ lines, so that the complete picture is made up of 615 lines and produced every twenty-fifth of a second (in actual fact not all the lines are used for the picture as some occur during the field sync period when the electron beam is cut off).

A complete full-line-picture is achieved because the scanning lines of one field *interlace* in the spaces between the lines of the partnering field. To obtain 625 lines without interlacing the line frequency would need to be increased to 31 250Hz. This in turn would call for a greater rate of change in beam intensity and hence spot brightness to trace out the fine detail over each line, and because a greater rate of change of signal amplitude involves a greater bandwidth, more radio space would be needed to accommodate the picture detail of each

channel. With the 5.5MHz vision bandwidth of the 'I' system good definition is obtained at the 15 625Hz line rate.

Interlacing *could* be avoided without using up extra radio space by reducing the field rate to 25Hz, but then the picture would suffer bad flicker (subjectively apparent up to about 45Hz). Interlacing thus solves the problems of bandwidth and flicker without unduly detracting from the displayed information.

Returning to the circuit in Fig. 2, the line frequency is established by a blocking oscillator incorporating VT15. Forward base bias through R83 turns the transistor on so that the current through the collector winding of L12 rises. The reversed phase of the other winding puts a negative-going pulse on the base which cuts the transistor off. The on/off cycles are timed by L12/C83/C84 with the oscillator in the free-running mode, the frequency being set by L12 core. The oscillator is synchronised to the line pulses of the signal (as will be explained later).

VT16 amplifies and shapes the pulses from VT15 emitter and transformer T3 couples them to the base of output transistor VT17. The pulses switch this transistor on during the scan so that current flows through the upper left-hand windings of the line output transformer (LOT) T1 and scan coils L14. Because the coils are essentially inductive the current rises as a fairly linear ramp. However, because the effective length of the beam changes with scanning stroke owing to the wide scanning-angle and flat screen of a contemporary tube, 'S-correction' is required. This is achieved by C93 which reduces the rate of scan at the start and end of a line with respect to the centre. Further linearity correction and width adjustment are provided by a closed-loop sleeve set under the scan coils. The field produced by the current induced into this counteracts the non-linearity of the field produced by the scan coils themselves.

VT17 switches off at the end of a scan and the swiftly collapsing current through the scan coils and LOT windings returns the beam to its starting point and yields a high voltage pulse owing to the sudden release of the inductively-stored energy. The repetitive pulses are increased in voltage by the overwind at the top right-hand side of T1, rectified by W14 and smoothed by a capacitance formed by the inner and outer conductive layers on the tube flare, the inner connected to the final anode. The result is a potential of 11.5kV for the final anode. After rectification by W15, pulses from the lower right-hand winding charge C95 to yield a 95V line for the tube first and third anodes, video output VT7 (to provide about 50V video swing for the tube) and varicap tuning.

Oscillatory energy is rectified by the booster diode W12 conducting during the retrace to charge C87/C88. This not only damps the unwanted energy which would otherwise cause vertical lines at the left of the picture, but the potential developed from it is used to energise VT17 collector, and contribute to the line scan, thereby improving the efficiency of the line output stage. The stage also adopts 3rd harmonic tuning of the pulses. This tends to flatten the tops of the pulses, which leads to improved EHT regulation. The tuning capacitor is C89 in parallel with a low-inductance disc capacitor C92 providing flashover protection.

Sync Stages

Video signal at VT5 emitter is coupled to the base of the sync separator transistor VT14 through R72/C72. On the 625 line system the picture signal is negative-going (modulation level falling with increasing brightness), and at the end of each line a line sync pulse occurs whose tip reaches 100% amplitude, as shown in Fig. 3 a.

Composite video (picture plus sync) from VT5 emitter is fed to the base of VT14 (sync separator) which is biased to conduct only during the sync pulses so that they resolve free from picture signal at the collector. For line sync, coupling is to VT11 (sync amplifier/inverter), whose output drives 'flywheel' discriminator W6/W7 etc. The discriminator is also fed positive-going line pulses from the LOT via C94 which, after RC integration,


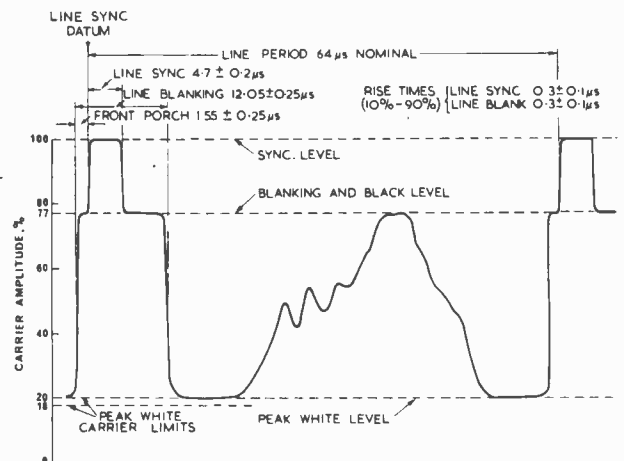


Fig. 3. BBC 625-line television signals. (a) One line of signal showing sync pulses. These keep the line scan in step with that at the transmitter, while the picture signal causes the deflected scanning spot on the face of the picture tube to change in brightness at a rate determined by the detail of the transmitted picture and by an amount governed by the brightness of the transmitted scene at any instant. (b) Pulses transmitted during the synchronising period at the end of one field scan and the start of the next (upper end of odd fields and beginning of even ones, and lower end of even fields and beginning of odd ones). The pulses provide correct interlacing while keeping the line timebase in sync during the field synchronising period (see text).

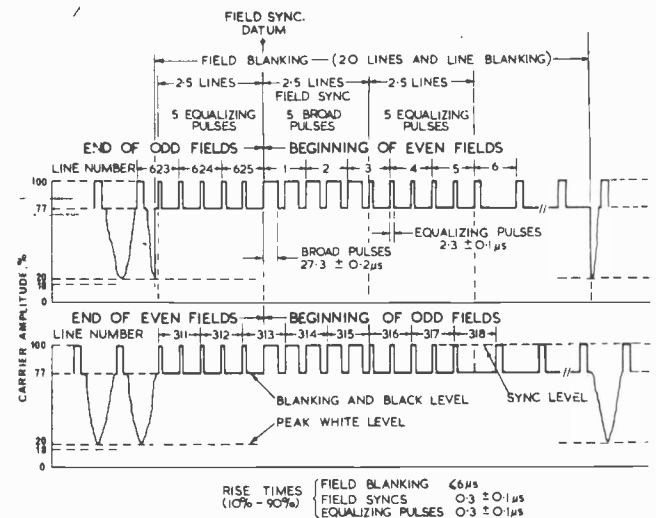

form a ramp whose phase is compared with that of the line sync pulses. Phase error results in a potential at the top of R78 which, after being filtered by C78/C79/R82 to remove pulse residual, is applied to the line oscillator. As this is a VCO, frequency correction and hence line synchronisation are achieved.

From the end of one field scan to the start of the next one, five narrow equalising pulses are followed by five broad field sync pulses and then by another five equalising pulses. The width and spacing of the pulses keep the line synchronised during the field sync period, while the equalising pulses ensure equal blanking on both even and odd fields, and also identify the two fields for accurate interlacing by cutting off the picture half way through a line at the end of odd fields and starting it after a line is half over at the beginning of even fields, as shown in Fig. 3 (b).

It is worth noticing that test signals and certain teletext data are transmitted on blank lines — the latter at a bit rate of 7 megabits per second. The 1.55 and 5.8 μ s front and back porches to the line sync pulses provide time for the line retrace, and it is the 5.8 μ s porch which carries colour burst signal.

The positive-going field sync pulses at VT14 collector are integrated by C99/R124 and applied to VT18 base through W18. The integration builds up a composite pulse for triggering the field retrace and attenuates line pulses.

Tube Biasing and Video Feed

During normal working the tube grid is held at chassis potential by W17. When the set is switched off W17 is reverse-biased and the charge held by C96 drives the grid negative, thereby suppressing the beam, while the supply voltages collapse.

Beaming current cut-off is set by R105 (brightness control) which merely adjusts the tube cathode potential. Video signal from VT7 collector is also applied to the cathode, and as the signal is negative-going the beam current increases with increasing picture brightness. Beam cut-off or black-level is set by the brightness control so that the sync pulses drive the tube below black.

Sound Channel

Intercarrier signal from L10 is fed to IC2 which incorporates a 6MHz limiting amplifier; quadrature coincidence detector tuned by L11; voltage-controlled attenuator operated by the volume control R54 and an audio preamplifier for driving the class B push-pull output transistors VT9/VT12 via driver VT8. The bases of the output transistors are driven together from VT8 collector, which is possible because VT9 is NPN and VT12 PNP (a complementary pair). Quiescent current is set by R59 at 8mA. Negative feedback is from the emitters of the output pair via R57 to VT8 base. Since the mains supply is isolated by transformer T2 it is possible to use a headphone set or earphone connected to jack J1.

For those not familiar with the quadrature FM detector the following brief description may help. After passing through the limiting amplifier chain, the intercarrier signal is changed to squarewave and the signal fed two ways. one way to a synchronous detector and

the other way to a 90-degree phase shift circuit and thence to the synchronous detector. The synchronous or coincidence detector combines the two inputs vectorially so that the output consists of the vector sum which, relative to the fixed 90-degree phase shift, changes with the FM deviation. The result is a variable width squarewave (pulse width modulation) which, after integration, yields the audio signal.

Power Supplies

The receiver can be operated from a 12V car battery or the mains supply. On mains, isolation is provided by transformer T2 and full-wave rectification by W8/W9, with C70 the reservoir. The supply is fed to the emitter of series regulator VT10. VT13 is the error amplifier which compares a ratio of the collector output voltage with a reference potential provided by zener W5. Starting current is provided by R66 and the base potentiometer R69 sets the output voltage for the correct value of EHT voltage. Stabilisation is effective over a mains input of 220-264V. The high V_{be} rating of VT10 provides automatic protection against reversed battery polarity.


Final Points

Finally, one or two minor points: SP1 at VT7 collector is a spark gap which liberates energy in the event of a flashover inside the tube, directing current away from VT7 collector. The tube is a quick-heat type whose heater is energised from the 11.3V line and one which is happy with a relatively low focus electrode voltage.

Acknowledgement

I would like to thank Thorn Consumer Electronics and Mr. R. V. Arnaboldi and Mr. D. A. Pike of this Company for permission to use the circuit of the 1690-1691 chassis in this article.

ETI

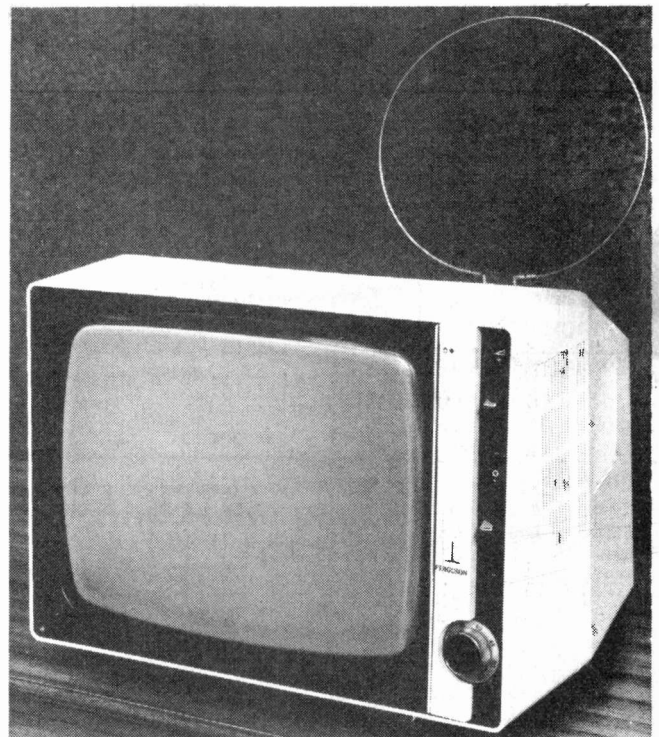

DIODES/ZENERS				SOCKETS/BRIDGES				TRANSISTORS, LEDS, etc.				
1N914	100v	10mA	.05	8-pin	pcb	.20	ww	.35	2N2222	NPN (2N2222 Plastic)	.10	.15
1N4005	600v	1A	.08	14-pin	pcb	.20	ww	.40	2N2907	PNP		.15
1N4007	1000v	1A	.15	16-pin	pcb	.20	ww	.40	2N3906	PNP (Plastic - Unmarked)		.10
1N4148	75v	10mA	.05	18-pin	pcb	.25	ww	.75	2N3904	NPN (Plastic - Unmarked)		.10
1N4733	5.1v	1 W Zener	.25	22-pin	pcb	.35	ww	.95	2N3054	NPN		.35
1N753A	6.2v	500 mW Zener	.25	24-pin	pcb	.35	ww	.95	2N3055	NPN 15A 60v		.50
1N758A	10v	"	.25	28-pin	pcb	.45	ww	1.25	T1P125	PNP Darlington		.35
1N759A	12v	"	.25	40-pin	pcb	.50	ww	1.25	LED Green, Red, Clear, Yellow			.15
1N5243	13v	"	.25	Molex pins .01	To-3 Sockets	.25			D.L.747	7 seg 5/8" High com-anode		1.95
1N5244B	14v	"	.25	2 Amp Bridge	100-prv	.95			MAN72	7 seg com-anode (Red)		1.25
1N5245B	15v	"	.25	25 Amp Bridge	200-prv	1.95			MAN3610	7 seg com-anode (Orange)		1.25
									MAN82A	7 seg com-anode (Yellow)		1.25
									MAN74A	7 seg com-cathode (Red)		1.50
									FND359	7 seg com-cathode (Red)		1.25

C MOS		- T T L -									
4000	.15	7400	.10	7473	.25	74176	.85	74H72	.35	74S133	.40
4001	.15	7401	.15	7474	.30	74180	.55	74H101	.75	74S140	.55
4002	.20	7402	.15	7475	.35	74181	2.25	74H103	.55	74S151	.30
4004	3.95	7403	.15	7476	.40	74182	.75	74H106	.95	74S153	.35
4006	.95	7404	.10	7480	.55	74190	1.25			74S157	.75
4007	.20	7405	.25	7481	.75	74191	.95	74L00	.25	74S158	.30
4008	.75	7406	.25	7483	.75	74192	.75	74L02	.20	74S194	1.05
4009	.35	7407	.55	7485	.55	74193	.85	74L03	.25	74S257 (8123)	1.05
4010	.35	7408	.15	7486	.25	74194	.95	74L04	.30		
4011	.20	7409	.15	7489	1.05	74195	.95	74L10	.20	74LS00	.20
4012	.20	7410	.15	7490	.45	74196	.95	74L20	.35	74LS01	.20
4013	.40	7411	.25	7491	.70	74197	.95	74L30	.45	74LS02	.20
4014	.75	7412	.25	7492	.45	74198	1.45	74L47	1.95	74LS04	.20
4015	.75	7413	.25	7493	.35	74221	1.00	74L51	.45	74LS05	.25
4016	.35	7414	.75	7494	.75	74367	.75	74L55	.65	74LS08	.25
4017	.75	7416	.25	7495	.60			74L72	.45	74LS09	.25
4018	.75	7417	.40	7496	.80	75108A	.35	74L73	.40	74LS10	.25
4019	.35	7420	.15	74100	1.15	75491	.50	74L74	.45	74LS11	.25
4020	.85	7426	.25	74107	.25	75492	.50	74L75	.55	74LS20	.20
4021	.75	7427	.25	74121	.35			74L93	.55	74LS21	.25
4022	.75	7430	.15	74122	.55			74L123	.85	74LS22	.25
4023	.20	7432	.20	74123	.35	74H00	.15			74LS32	.25
4024	.75	7437	.20	74125	.45	74H01	.20	74S00	.35	74LS37	.25
4025	.20	7438	.20	74126	.35	74H04	.20	74S02	.35	74LS38	.35
4026	1.95	7440	.20	74132	.75	74H05	.20	74S03	.25	74LS40	.30
4027	.35	7441	1.15	74141	.90	74H08	.35	74S04	.25	74LS42	.65
4028	.75	7442	.45	74150	.85	74H10	.35	74S05	.35	74LS51	.35
4030	.35	7443	.45	74151	.65	74H11	.25	74S08	.35	74LS74	.35
4033	1.50	7444	.45	74153	.75	74H15	.45	74S10	.35	74LS86	.35
4034	2.45	7445	.65	74154	.95	74H20	.25	74S11	.35	74LS90	.55
4035	.75	7446	.70	74156	.70	74H21	.25	74S20	.25	74LS93	.55
4040	.75	7447	.70	74157	.65	74H22	.40	74S40	.20	74LS107	.40
4041	.69	7448	.50	74161	.55	74H30	.20	74S50	.20	74LS123	1.00
4042	.65	7450	.25	74163	.85	74H40	.25	74S51	.25	74LS151	.75
4043	.50	7451	.25	74164	.60	74H50	.25	74S64	.15	74LS153	.75
4044	.65	7453	.20	74165	1.10	74H51	.25	74S74	.35	74LS157	.75
4046	1.25	7454	.25	74166	1.25	74H52	.15	74S112	.60	74LS164	1.00
4049	.45	7460	.40	74175	.80	74H53J	.25	74S114	.65	74LS193	.95
4050	.45	7470	.45			74H55	.20			74LS367	.75
4066	.55	7472	.40							74LS368	.65

9000 SERIES		MICRO'S, RAMS, CPU'S, E-PROMS		LINEARS, REGULATORS, etc.							
9301	.85	95H03	1.10	MCT2	.95	LM320T5	1.65	LM340K15	1.25	LM723	.40
9309	.35	9601	.20	8038	3.95	LM320T12	1.65	LM340K18	1.25	LM725N	2.50
9322	.65	9602	.45	LM201	.75	LM320T15	1.65	LM340K24	1.25	LM739	1.50
				LM301	.45	LM324N	1.25	78L05	.75	LM741 (8-14)	.25
				LM308 (Mini)	.95	LM339	.75	78L12	.75	LM747	1.10
				LM309H	.65	7805 (340T5)	.95	78L15	.75	LM1307	1.25
				LM309K (340K-5)	.85	LM340T12	.95	78M05	.75	LM1458	.65
				LM310	.85	LM340T15	.95	LM373	2.95	LM3900	.50
				LM311D (Mini)	.75	LM340T18	.95	LM380 (8-14 PIN)	.95	LM75451	.65
				LM318 (Mini)	1.75	LM340T24	.95	LM709 (8,14 PIN)	.25	NE555	.35
				LM320K5(7905)1	1.65	LM340K12	1.25	LM711	.45	NE556	.85
				LM320K12	1.65					NE565	.95
										NE566	1.25
										NE567	.95

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd., San Diego, CA 92111 U.S.A.
No Minimum

All prices in U.S. dollars. Please add postage to cover method of shipping. Orders over \$100 (U.S.) will be shipped air no charge. Payment should be submitted with order in U.S. dollars. All IC's Prime/Guaranteed. All orders shipped same day received.

SPECIAL DISCOUNTS


Total Order	Deduct
\$35 - \$99	10%
\$100 - \$300	15%
\$301 - \$1000	20%

Phone (714) 278-4394 BarclayCard / Access / American Express / BankAmericard / Visa / MasterCard

ETIPRINTS

ETIPRINTS are a fast new aid for producing high quality printed circuit boards. Each ETIPRINTS sheet contains a set of etch resistant rub down transfers of the printed circuit board designs for several of our projects. ETIPRINTS are made from our original artwork ensuring a neat and accurate board. We thought ETIPRINTS were such a good idea that we have patented the system (patent numbers 1445171 and 1445172).

HOW IT WORKS

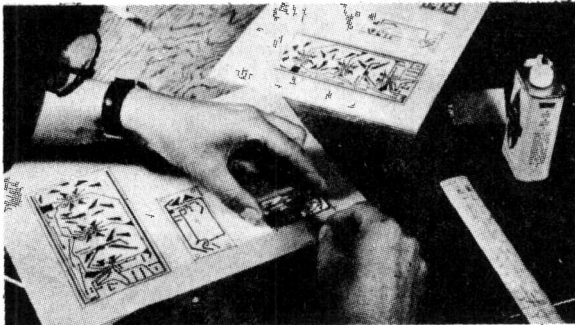

Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

BUYLINES

ORDER TODAY

Send a cheque or P.O. (payable to ETI Magazine) to—

ETI PRINT
ETI MAGAZINE,
25/27 OXFORD STREET, LONDON W1R 1RF.

75p inc p&p

PARTS LIST

001	3 Channel Tone Control	Oct 77
	Spirit Level	Oct 77
	Clock A	Nov 77
	Digital Thermometer	Oct 77
	Skeet Game	Nov 77
	Compander	Nov 77
002	House Alarm	Jan 78
	Rev Monitor	Dec 77
	Clock B	Dec 77
003	Race Track Game	Jan 78
	Hammer Throw	Jan 78
	Freezer Alarm	Dec 77
004	Metal Locator Mk II	Feb 78
	Ultrasonic Tx/Rx	Feb 78
	5 Watt Stereo Amp (modified)	
	Metronome	Jan 77
	Shutter Time	Feb 78
		Feb 78
005	Op-Amp Supply	
	Frequency Shifter	Mar 78
	LCD Panelmeter	
	Light Dimmer (3 times)	
006	CMOS Switched	
	Preamp	
	From Experimenters	"Electronics
	P.S.U.	Tomorrow"
	555 Boards (twice)	
007	Star Trek Radio	May 78
	CD Ignition	May 78
	CCD Phaser	May 78
	White Line Follower	April 78
008	Tank Battle	
	Helping Hand	May 78
009	AM/FM Radio	
	Bridge Oscillator	June 78
	CMOS Stars & Dots	
010	Bench Amplifier	
	Freezer Alarm	
	Marker Generator	Project
	LED Dice	Book
	Watchdog (2 PCBs)	Six
	Stars & Dots PSU	
011	Noise Generator	
	General Preamp	Project
	Flash Trigger	Book
	Compander	Six
	Active Crossover	
	(2 PCBs)	
012	Disco Lightshow	
	Stereo Simulator	Project
	Digital Thermometer	Book
		Six
013	Amplifier Module	
	Amplifier PSU	Project
	Equaliser	Book
	Equaliser PSU	Six
014	Skeet Game	
	Sweep Oscillator	Project
	Burglar Alarm	Book
	GSR Monitor	Six
015	UFO Detector	July 78
	Torch Finder (twice)	July 78
	Etiwet (twice)	Aug 78
016	Stac Timer	
	Xhatch Gen	Sept 78
	Wheel of Fortune	
017	Complex Sound Gen	
	Tele Bell Extender	Oct 78:
	Power Bulge	
018	RF Power Meter	Oct 78
	Proximity Switch	Oct 78
	Audio Oscillator (2)	Nov 78

FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY

FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY FAST AND EASY

Complete the Circuit at Breadboard '78

Lektrokit have made sure that, no matter how often you go round the exhibits at Breadboard '78, you'll keep coming back to Stands D8 and D9. "Completing the circuit" every time.

Because Lektrokit—as only Lektrokit could—have combined their vast array of components with those of AP Products Inc to bring you the most comprehensive

range of breadboarding and testing devices on earth.

Nowhere else at Breadboard '78 will you see everything you're likely to need all in one place, all in one go, and at the right price.

If you can't get to Breadboard '78 contact us for more details and the name of your nearest Lektrokit dealer and take a look at how much you can get for how little.


Lektrokit Breadboards

FROM £3.25, inc p & p and VAT

Hole for hole, top value! Lektrokit Breadboards are modular, so they can be linked together to form any size. With a pitch of 0.1", even the smallest breadboard—217L—can accept 8, 14, 16 or 18 pin DII devices. You just take a component, choose a hole, and push it in.

Model No.	Contacts	Price, each
217L	170	£3.25
234L	340	£5.75
248L	480	£6.65
264R	512	£6.65
264L	640	£8.32

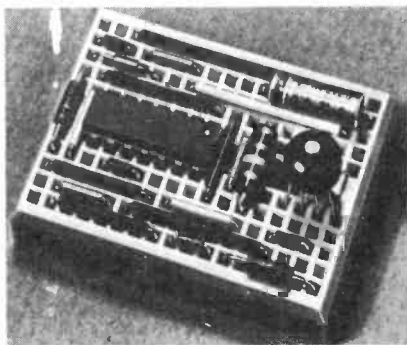(All prices include packing, postage and VAT)



Lektrokit IC Test Clips

FROM £3.08 inc p & p and VAT

Eleven models, from TC-8 to TC-40 to fit all DIP sizes. Prices from £3.08 for the TC-14, £3.25 for the TC-16, etc.



Test clip grips IC's without slipping or shorting between pins—makes testing IC's on boards easier, aids removing and inserting DIP's without damage. Each IC pin can be brought up to a convenient contact post for test leads or probe connections.

Lektrokit Super Strip SS2

ONLY £11.05 inc p & p and VAT

Super Strip accepts ALL DIP's— as many as nine 14-pin at a time— and/or TO-5's and discrete components. With interconnections of any solid wire up to 20 AWG.

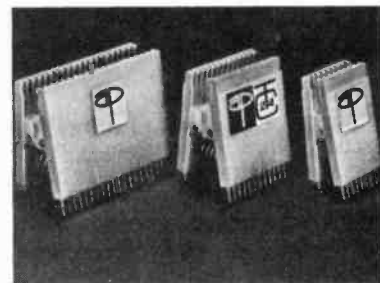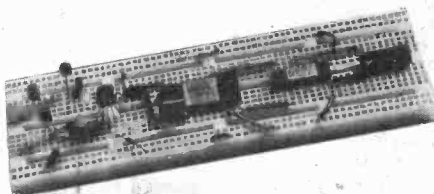Super Strip has 840 contact points, combining a power/signal distribution system with a matrix of 640 contacts in groups of 5. Distribution system has eight bus-bars, each with 25 contact points.



Lektrokit All-Circuit Evaluator FROM £12.53 inc p & p and VAT

"ACE" in the hole for home constructors and project builders who do things faster and easier! No laying out circuit diagrams, printed circuit boards, soldering everything together, trouble-shooting, making mods, then chucking it and starting the whole time-consuming business all over again!


With ACE, you just plug in components and make connections with ordinary 22-gauge solid wire. No soldering. You can build any working project complete, as fast as you could lay out a circuit diagram before.

Seven ACE models altogether—with from 728 to 3,648 contacts. IC capacity (all 14-pin DIP's) from 9 to 36. Buses from 2 to 36. Posts from 2 to 4. Prices from £12.53 including packing and postage and VAT.

Lektrokit's policy is the right product, whatever the project, at the right price. And it's backed by a nationwide network of retailers.

Send for the name of the dealer nearest you—plus a FREE full-colour catalogue.

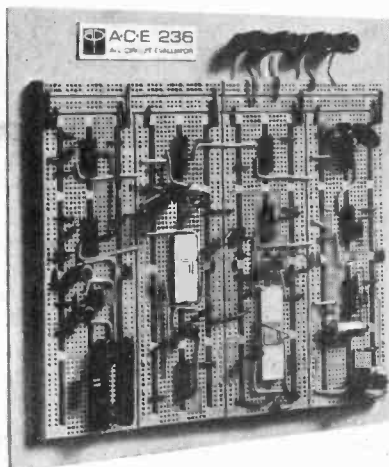And, if you can, see and try out the great Lektrokit range at Breadboard '78—from Nov. 21 to Nov. 25 at Seymour Hall, Seymour Place, London.



To Lektrokit Limited, London Road, Reading, Berks, RG6 1AZ. Tel. Reading (0734) 669116/7.
Please send me the name of my nearest Lektrokit dealer—plus FREE catalogue.
Please supply the following (list items required)

..... I enclose P.O./cheque for £

(Allow 28 days for delivery. All prices above include packing, postage and VAT).

Name

Address

LEKTROKIT

COMPLETES THE CIRCUIT



SEE LEKTROKIT ON STANDS D8 AND D9 AT BREADBOARD '78!

WINE TEMPERATURE METER

Ensure your wine is at the correct temperature with this little idea from our project team

WINE, WOMEN AND SNOG — no not another misprint but ETI's updated version of that phrase that so aptly describes that which a young man's fancy turns to in spring, or any other time of year for that matter. We at ETI can't do much about the provision of the above items but this project will at least ensure that when you get your hands on one of them it will be in perfect condition. Before going any further let's make it clear that its the wine we're talking about in this connection.

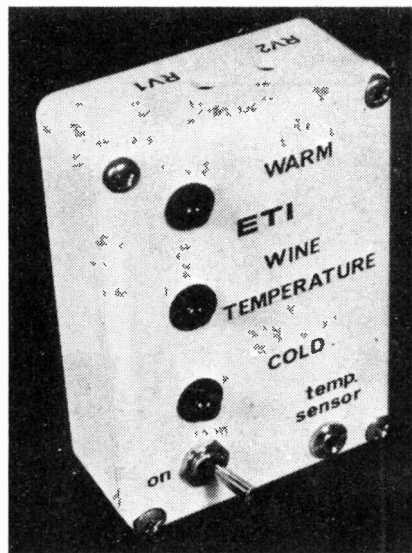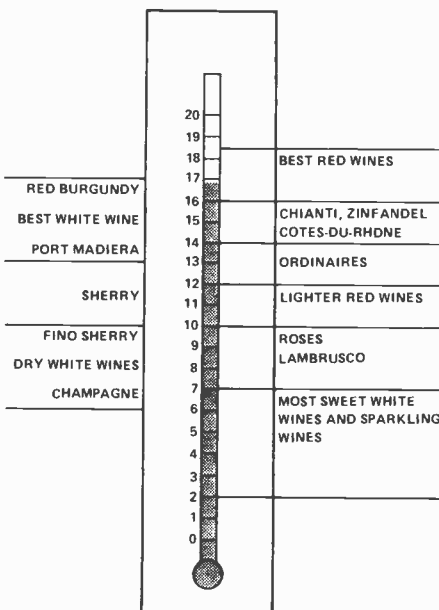In use the wine temperature meter's sensor is clipped to the plunk of your choice and the condition of the booze, with regard to temperature, read off from the three LEDs on the meter's front panel. To set up the instrument consult our table showing the range of temperatures considered acceptable



Above, the complete unit while below the sensor, a bicycle clip painted black with the sensor epoxied to it.


for the various types of wines. Turn RV2 fully anticlockwise and bring the sensor to a temperature that is in the middle of the desired range. Adjust RV1 until the centre LED just lights

Next lower the temperature of the sensor until it is at the lower temperature limit. Adjust RV2 until the lower LED is just extinguished.

Construction of the project is quite straightforward. Assemble all the components according to the overlay shown. Space is at a premium if the case chosen for our prototype is used so keep everything tidy.

Our sensor was made from a bicycle clip. The thermistor was epoxied to the clip — we smeared a small amount of silicon grease on the clip before mounting the sensor — this provides a good thermal contact. We coated the sensor in a layer of black paint when it was complete leaving the area under the sensor as bare metal.

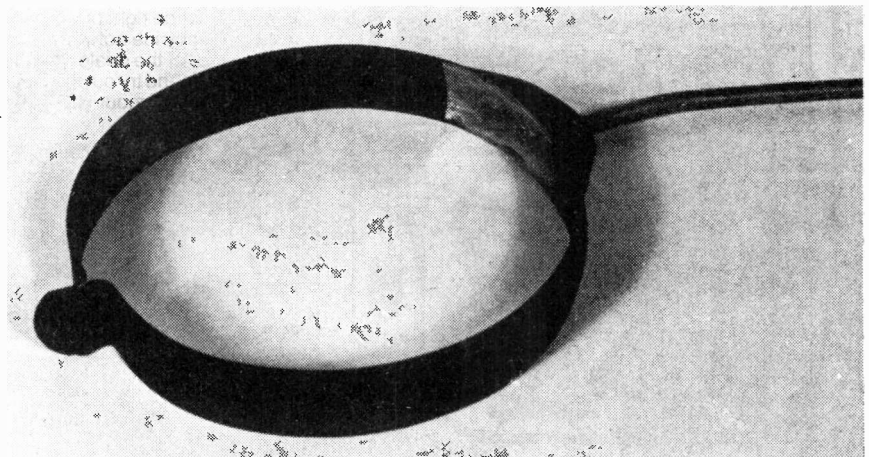Insert the battery and start getting your grapes as they should be enjoyed.



HOW IT WORKS

The project is based on the TCA965 window discriminator IC. This device can be used in a number of different modes, the one selected for this application allows the potentiometers RV1 and RV2 to set up a "window height" and "window width" respectively.


R1 and thermistor TH1 for a potential divider connected across the supply lines. The value of R1 is chosen such that at ambient temperature the voltage at the junction of these two components will be approximately half supply.

As the temperature of the sensor changes so the voltage will change and it is the temperature dependent voltage that is input to IC1.

RV1 will set the point which corresponds to the centre voltage of a window the width of which is set by RV2. The switching points of the IC feature a Schmitt characteristic with low hysteresis.

The outputs of IC1 indicate whether the input voltage is within the window or outside by virtue of being either too high or too low..

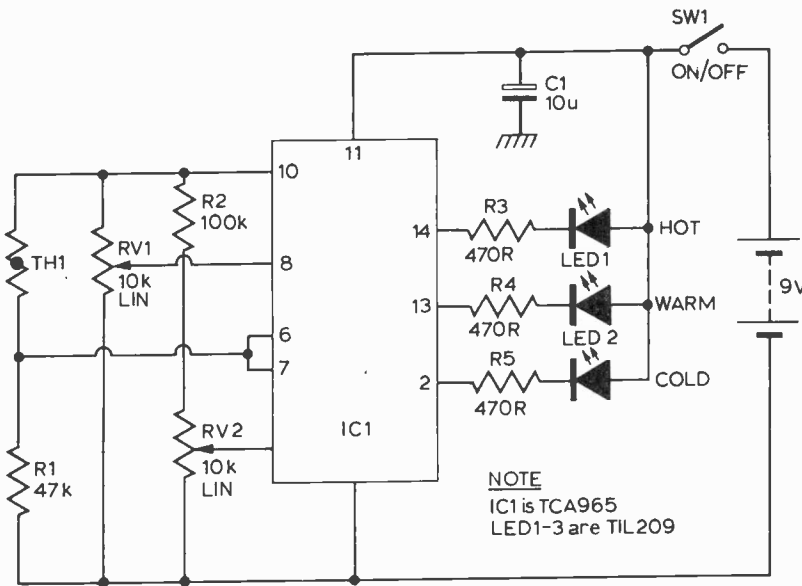The outputs of IC1 are all open collectors capable of providing up to 50mA. In our circuit however they are only required to drive a LED via a current limiting resistor.





NOTE
IC1 is TCA965
LED1-3 are TIL209

Circuit diagram of the wine temperature meter.

BUYLINES

All the components for this project should be available from most local shops — no problems.

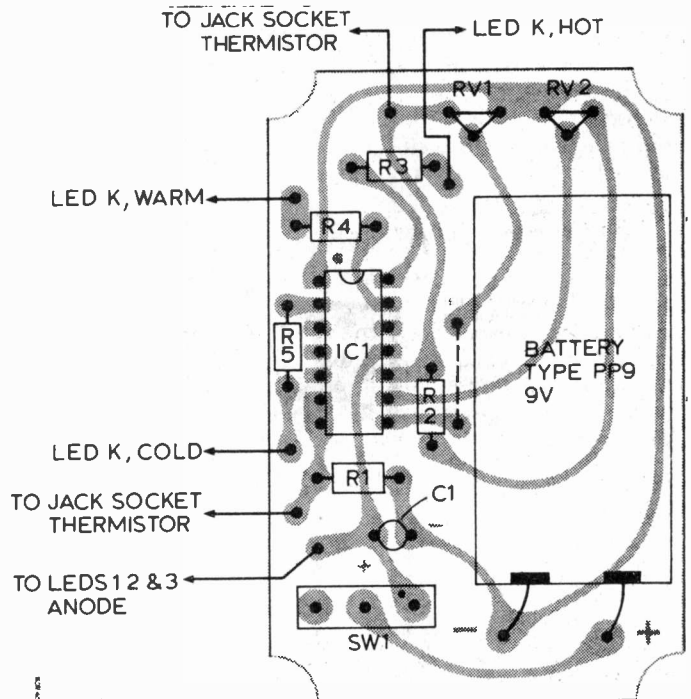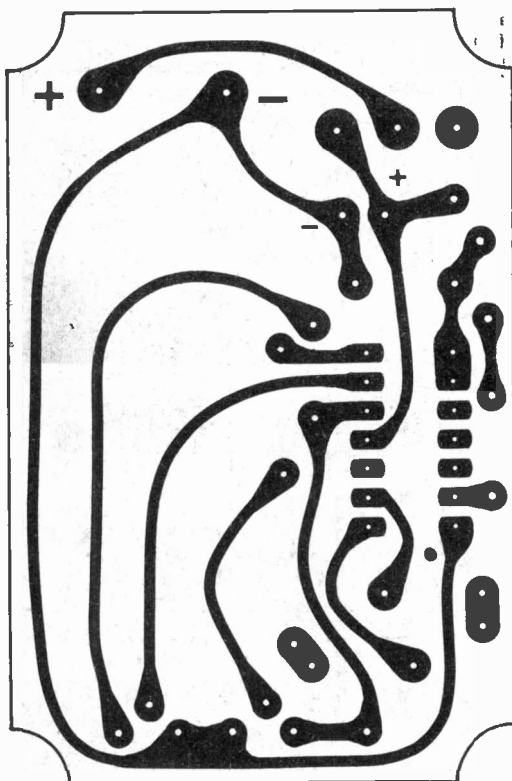Foil pattern of the wine temperature meter.



PARTS LIST

RESISTORS

R1 47k
R2 100k
R3, 4, 5 470R

POTENTIOMETERS

RV1, 2 10k sub. min. preset

CAPACITORS

C1 10u 10V tantalum

SEMICONDUCTORS

IC1 TCA965
LEDs1-3 TIL209

SWITCH

SW1 SPDT

MISCELLANEOUS

PCB as pattern, Vero potting box, 2.5mm jack socket, battery wire, wire etc.

NO DISCO SYSTEM IS COMPLETE WITHOUT...



CITRONIC MM 313 MIXER

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch. mono, inc. LED indicators; connections via phono sockets at rear. Bargain price, including PSU **£80.46** inc. VAT (P.P. £1.50)

PIEZO HORNS

FANTASTIC SPECIAL OFFER TO READERS OF PRACTICAL ELECTRONICS

Tweeters for your disco, PA system or Hi-Fi. Frequency range 5K-20K No X over required. They can be used in any PA system up to 100W. Why pay more? **OUR PRICE ONLY £4.99** each (P&P 35p each)



BULGIN OCTAL PLUGS AND SOCKETS

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET **£0.65** (P&P 35p) P551 PLUG **£1.84** (P&P 35p) Carriage on 10 or more nominal £1.00 Also available 6-way multicore cable (6 Amps per core) ex stock **£0.65** per metre. Please phone for carriage quote.




PROJECTORS

SQUIRE MULTIFECT 150

Including rotator and effects wheel. A truly versatile projector which uses a powerful 150W Tungsten bulb, all effects attachments simply slot in ready for use. **A BARGAIN AT £40.50** (P&P £1.00)

PLUS MANY DISCO ACCESSORIES

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES. For example: Fane and H Hi Disco Speakers 12" and 15" BSR and Garrard decks at discount prices

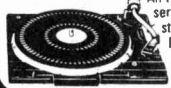

STARLITE 250

An exclusive new line to Roger Squire's Disco Centres. Superb high powered 250 W quartz halogen bulb, fan cooled, accepts wide range of multifect attachments. Unique connection slot for orbit prism revolvers. Only **£65.00** + VAT attachments extra



Plus sockets, Fuses, Plugs, etc etc

Roger Squire's DISCO GEAR

Send Mail Orders to: Roger Squire's Mail Orders, Barnet Trading Estate, Park Road, Barnet, Herts EN5 5SA. 01-441 3527 (Hotline) 01-441 1919 (Switchboard) Open: Mon-Fri, 9.5-3.0 Personal callers: ROGER SQUIRE'S DISCO CENTRES LONDON: 175 Junction Road, Tufnell Park N19 5QQ 01-272 7474 BRISTOL: 125 Church Road, Redfield, Bristol BS5 9JR 0272-550550 MANCHESTER: 251 Deansgate M3 4EN 081-831 7676 GLASGOW: 1 Queen Margaret Road Kelvinside, Glasgow, G20 6DP 041 946 3303

Open from 10-5 Tues-Sat 10-8 Weds Closed Mondays

TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safeloc

Miniature & Sub Miniature

Volts	Milli-amps	Ref. No.	Price £	P&P
3.0-3	200	238	1.95	.55
0.6-0.6	1A 1A	212	2.60	.55
0.9-0.9	100	13	1.85	.40
0.9-0.9	330 330	235	1.95	.40
0.9-0.9	500 500	207	2.35	.55
0.8-9, 0.8-9	1A 1A	208	3.50	.55
0.15-0.15	200 200	236	1.95	.40
0.20-0.20	300 300	214	2.35	.70
20-12-0-12-20	700(DC)	221	3.10	.70
0.15-20, 0.15-20	1A 1A	206	4.20	.85
0.15-27, 0.15-27	500 500	203	3.65	.70
0.15-27, 0.15-27	1A 1A	204	4.75	.85

50 VOLT (Pri: 220-240V) (Sec: 0-19-25-33-40-50V)

Amps	Ref. No.	Price £	P&P
0.5	102	3.20	.70
1.0	103	4.20	.85
2.0	104	6.10	1.00
3.0	105	7.85	1.00
4.0	106	9.80	1.10
6.0	107	14.95	1.50
8.0	108	15.75	1.50
10.0	109	20.50	2.00

60 VOLT (Pri: 220-240V) Sec: 0-24-30-40-48-60V

Amps	Ref. No.	Price £	P&P
0.5	124	3.40	.70
1.0	126	4.65	.85
2.0	127	6.50	1.00
3.0	125	9.15	1.00
4.0	123	11.25	1.30
5.0	40	11.80	1.30
6.0	120	14.75	1.40

12 AND/OR 24 VOLT

12V	24V	Ref.	Price £	P&P
0.5	0.25	111	1.95	.55
1.0	0.5	213	2.30	.70
2	1	71	2.90	.70
4	2	18	3.75	.70
8	4	108	6.25	1.00
10	5	72	6.95	1.00
12	6	116	7.85	1.00
16	8	17	9.25	1.10
20	10	115	12.75	1.30
30	15	187	16.60	1.30
60	30	226	22.90	1.60

30 VOLT (Pri: 220-240V)

Amps	Ref. No.	Price £	P&P
0.5	112	2.45	.70
1.0	79	3.05	.70
2.0	3	4.80	.85
3.0	20	5.80	1.00
4.0	21	6.85	1.00
5.0	51	7.75	1.00
6.0	117	9.50	1.00
8.00	88	11.35	1.30
10.0	89	12.00	1.30

CATALOGUE 30p

Please add VAT at 8%
Barclaycard and Access facilities available
Trade and Education Welcome

AUTO TRANSFORMERS

Input/Output Tapped 0-115-210-240V

VA	Price		
(Watts)	Ref. No.		
20	113	2.25	.70
75	64	3.50	.70
150	4	5.35	.85

Input/Output Tapped

VA	Price		
0-115-210-220-240V	Ref. No.	Price	P&P
300	66	7.15	1.00
500	67	10.75	1.30
1000	84	17.00	1.40

Also 1500/2000/2000/3000VA

MAINS ISOLATING (Centre Tapped & Screened)

VA	Price		
(Watts)	Ref. No.	Price	P&P
60	149	5.75	.85
100	150	6.40	1.00
200	151	10.00	1.10
250	152	11.95	1.30
350	153	14.45	1.40
1000	156	35.00	3.00

BAYDIS


54a Mortimer Street
Herne Bay, Kent
Herne Bay 64586

CHESS CHALLENGER "10"

"It's You Against the Computer"

Are YOU good enough to challenge the CHALLENGER in any of the following 10 levels and WIN??

LEVEL	AVERAGE RESPONSE TIME
1 Beginner	5 Seconds
2 Intermediate	15 Seconds
3 Experienced	35 Seconds
4 Advanced	1.20 Minutes
5 Superior	2.20 Minutes
6 Mate In Two	(2 move Puzzlers) 60 Minutes
7. Excellent	6 Minutes
8. Tournament Practice	3 Minutes

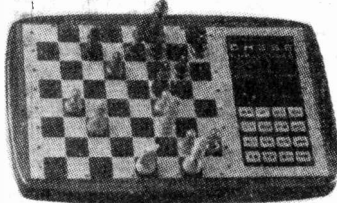

AVAILABLE SINCE OCTOBER


1. Ten Levels of play, from beginner to expert including "Mate in two" and "Chess by mail".
2. Levels changeable during game. Change from level 1 to any level through 10 at any time on any move.
3. Random Computer Responses vary every game.
4. Selection of Legal Offense or Defense. Play from the bottom board or the top of the board. Choose either black or white.
5. Does not permit illegal moves. Never makes an illegal move according to all the rules of chess.
6. Position verification by computer memory recall.
7. Plays opening defenses from chess books, i.e. Sicilian, French, Ruy Lopez, Queen Gambit declined.
8. Analyzes as many as 3,024,000 board positions.
9. Audio Feedback. Single tone each time you press a key. Double tone when computer responds.
10. Problem Mode. Establish your own chess positions and watch the computer react.
11. Override key to make multiple moves. Make two, three, or more moves before the computer responds.
12. Add or subtract pieces during game. Put back the piece you lost by override and take away the computer's Queen for a more even game.
13. Pawn Promotion to selected piece. Promote a pawn to a Queen automatically, or select a knight or another piece instead.
14. En Passant. The computer captures legally or accepts your legal capture.
15. Castling.

Numerous other features, including a solid walnut case, 13 x 8 x 1 1/4 inches high, with a deluxe simulated leather and brushed gold foil playing surface, large 1/2-inch LED display, and hand-carved solid wood, magnetized French Chess Pieces. CHESS CHALLENGER "10" available from **KRAMER & Co., Dept. ET1 9 OCTOBER PLACE, HOLDERS HILL ROAD, LONDON NW4 1EJ** TEL. 01-203 2473. TELEX 8BB941 ATTN. KRAMER K7. SAE for brochure and further details, book your order now and ensure delivery. Export orders welcome, Access and Barclay by arrangement. PRICE **£199**, INCL. VAT, P&P

We will match any lower advertised price on a cash with order basis of competitor has goods in stock.

BULK PURCHASE — EXCLUSIVE TO HENRY'S
ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!

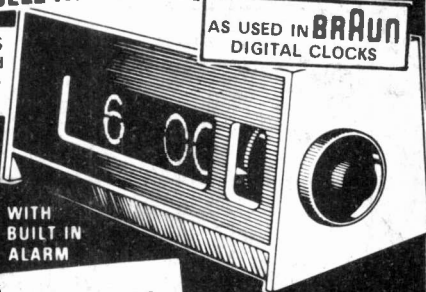
QUALITY ITEMS
Compare performance and specification with units costing 3 times as much!



DIGITAL 24 HOUR CLOCK

WITH BUILT IN ALARM

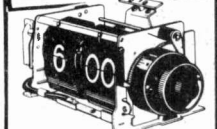- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS ● SIZE 6 1/2 x 2 1/2 x 2 1/4



MECHANISM ONLY



Assemble it in an evening!
MECHANISM & CASE
Inc. assembly instructions



Modern Styling
COMPLETE UNIT

£5.00

£6.99

£7.99

THREE FOR £13.50

THREE FOR £20

THREE FOR £23

Send cheque, P.O./M.O. for the correct amount which includes VAT and P & P or pay by Access/Barclaycard. Send name/card number (if applicable) and address to:

HENRY'S RADIO
404 EDGWARE ROAD,
LONDON W2 1ED

AVAILABLE ONLY FROM

Henry's Radio



DELIVERY FROM STOCK


Video games have only been around for a short period of time. The original units were developed by the Magnavox Corporation in America, with these early units you could play any game — as long as it was Tennis! Besides being reasonably boring, they were built from dozens of separate logic devices and cost a small fortune.

The first major breakthrough, in cost and versatility, came from General Instruments — with their introduction of the AY-8500 game chip. The now famous (and obsolete) AY-8500, allowed you to play up to six games and also produced sound effects.

Since the days of the AY-8500 General Instruments have produced several other dedicated devices, allowing you to race a motorbike, command a tank and even drive a Formula One racing car (to name just a few). By continually introducing new and exciting products General Instruments have become the major T.V. game device manufacturer in the World.


Every time a new game is launched the electronic magazines publish a D.I.Y. version, but you always need a new case and U.H.F. modulator. By the time you have paid for all the bits & pieces, the £10 chip has turned into a £30 project — and probably used up a lot of time.

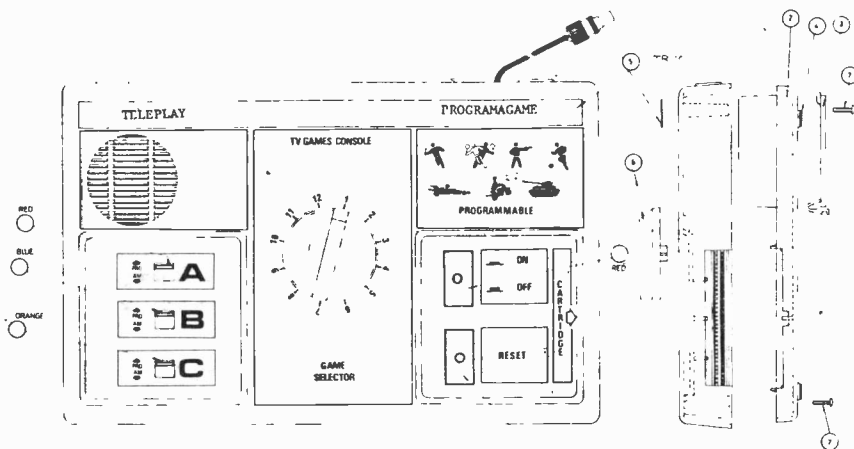Teleplay have developed the Programgame as the answer to the D.I.Y. enthusiasts need — for an inexpensive, easy to construct, up-to-the-moment, professional looking, full colour T.V. game system.



GO FASTER CONTROLS

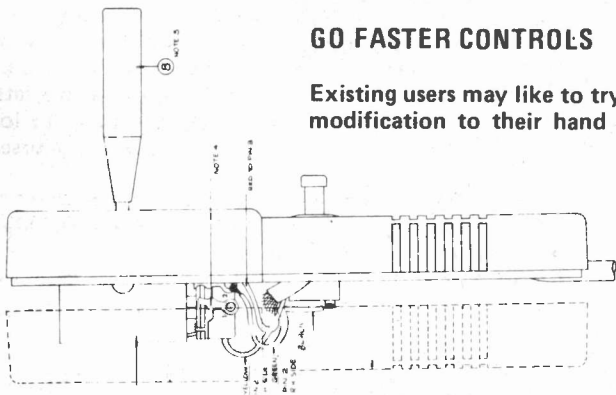Existing users may like to try this simple modification to their hand controllers.




Remove the 220k resistor and 470p capacitor from each controller. Then set both joysticks to the bottom right position. Set the PRO/AM switch to give small bats, then adjust the cartridge preset until both bats are just on the bottom boundary.

This modification gives a much better feel to the controllers. You can also give the plastic sleeves a sharp tap, with a

blunt instrument (the wrong end of your screwdriver), to make them fit closer to the case - this also improves the feel of the controllers.

If you want to use the Road Race after making the modification, you will need to fit the two 470p capacitors inside the cartridge. They go between pins 10 & Earth and 14 & Earth.

REALISTIC
SOUND EFFECTS

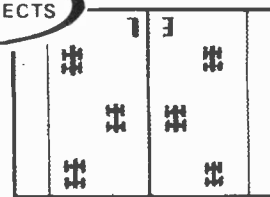


ROAD
RACE

£12.90

Road race has two different games inside it. The first is a two player version, with a switchable handicap on the left-hand track. The second game is you against the machine, see if you can score 15 laps without crashing! Uses the normal Joystick.

NEW

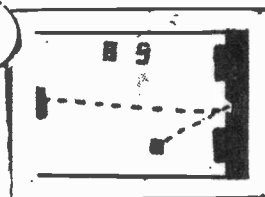


WIPEOUT
SIX GAMES

£13.90

The latest game from General Instruments, brought to you by Teleplay first! Based on the popular arcade game Breakout, the cartridge has 6 games built into it. On each of the games there are 3 variables - bat size, ball size and ball speed. The device type is an AY-3-8606.

The games are single and double Wipeout, single and double Breakout, two player Wipeout with barrier, and solo Wipeout (not the same as single).

EX-STOCK
IMMEDIATE
DELIVERY

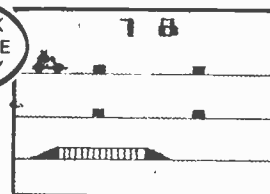

STUNT
CYCLE

£14.90

You too can be a dare-devil Stunt Rider with the AY-3-8765 and special hand controls. With 4 different games, this cartridge is bound to give hours of pleasure over Christmas and the New Year.

Main Console has
3 Facility Handicapping
Switches.




TANK
BATTLE



£13.90*

Complete with special hand controls but without the Tank chip. Due to extreme supply difficulties we are unable to provide any Tank chips at present. If you have one of these AY-3-8710 in your workshop why not take advantage of this £6 off offer.

COLOUR PROGRAMAGAME

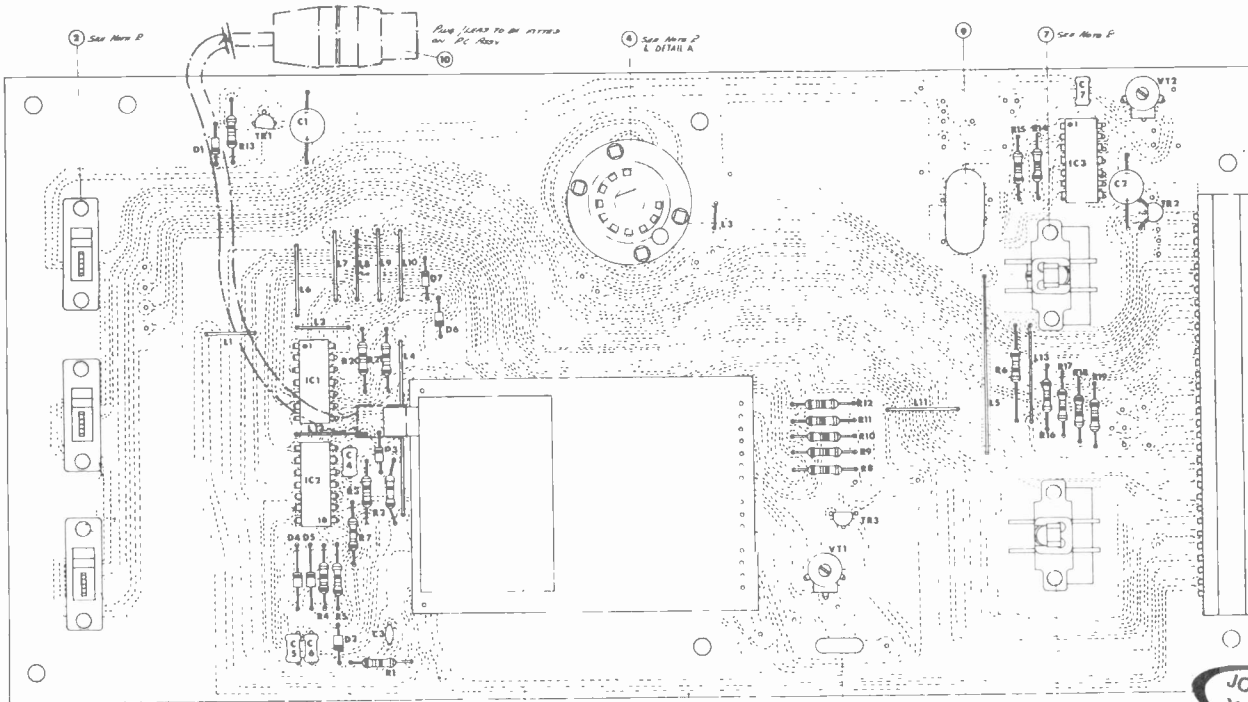

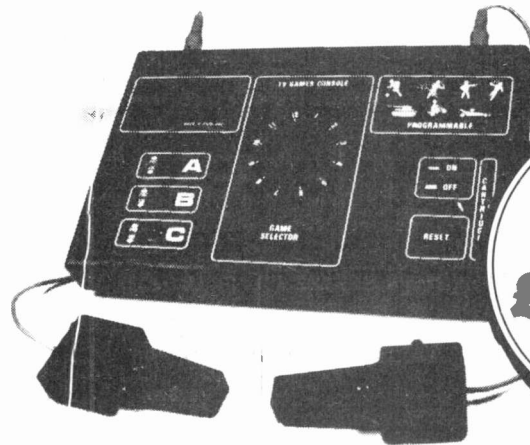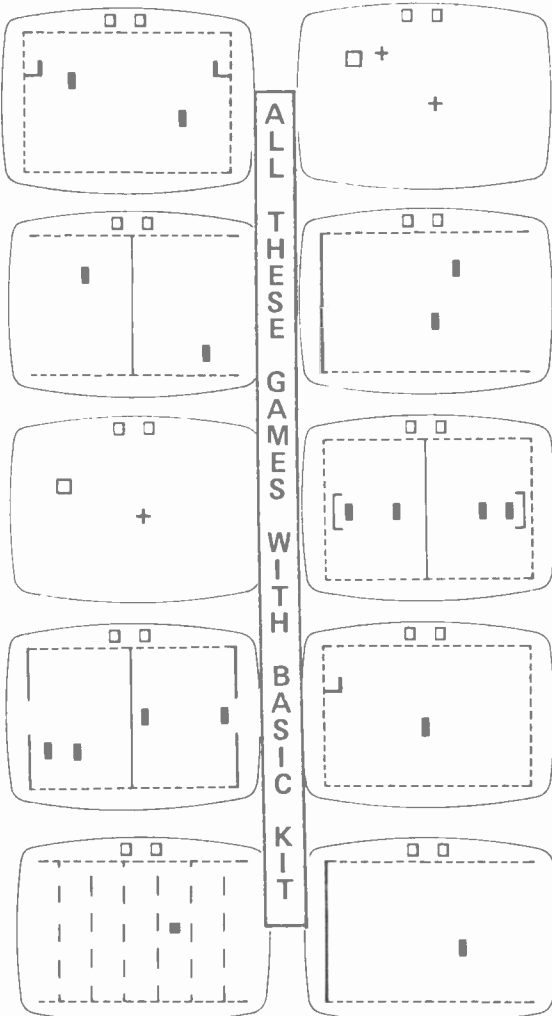On the left is the main circuit for the console. All the colour encoder circuitry is inside the large square in the centre, which is a ready made module. The various game cartridges slot into the 32 way connector on the right hand side. All the switches are mounted on the PCB itself.



JOYSTICKS GIVE X-Y MOVEMENT

We offer all this to you for ONLY ~~£31.30~~ **£28.90** Fully Assembled £35.90

The Programagame uses a main console to house the U.H.F. colour modulator, and the ancillary electronics needed to play any of the available games — just slot in a game cartridge and play a new set of games! Add new cartridges as they become available and your colour game centre will be up to the latest level in T.V. game technology. You will save pounds in the long run, and get the extra pleasure from having built it yourself!

All prices are VAT and postage inclusive, order now and beat the Xmas rush! Kit includes full instructions and even the Mains adaptor has a plug fitted — the only tools needed are a small soldering iron, Phillips screwdriver and wire cutters. Assembly can be completed in an evening, with minimal electrical knowledge.

Cheques or Postal Orders should be made payable to TELEPLAY
Send your order Freepost (no stamp needed) to:
TELEPLAY, FREEPOST, BARNET, EN5 2BR.

Or telephone your order quoting your Visa or Access number.
Personal callers welcome at our shop, units on demonstration.

14 Station Road, New Barnet, Herts EN5 1QW
Telephone : 01-440 7033 or 01-441 2922



SHOP OPEN - 10am to 7pm - Monday to Saturday

CLOSE TO NEW BARNET BR STATION - MOORGATE LINE





impedance for the motor, thirdly a delayed action can be switched in and out so that the controlled inertia of a heavy train can be simulated together with brake levers; and lastly it's short-circuitproof by virtue of heavy duty transistors and an overload trip. The last is indeed essential because short-circuits abound on the model railroad!

Though the circuit I've shown uses two darlington transistors, commercial versions are available, particularly from the USA, using op amps, SCR control or pulse width modulation. Even the renowned Heathkit has introduced a version. The most important feature is probably that superimposed pulse, for if it's too small in amplitude or too high in frequency, it is not effective; but if it goes too far in the opposite direction, the resulting buzz or rattle from the motor becomes objectionable. Anyway, you electronic fans with a dusty train set in your attic, dig it out, build a momentum-pulse-throttle and you just might pick-up an extra hobby!

In terms of current rating, the power pack shown should be capable of about 2A5 at 12V. This is adequate for any HO scale models, which scale 1:87, even with double heading locomotives. As you'd anticipate, the current requirements decrease with scale size—the second most popular scale is 1:160 (n for Nine mm, which is the track width) scale. Going up as size to O scale (1:48) many motors will need the full 2A5. By the way, in case you home computer builders are thinking "why waste money on electronics for toys" some of these "toy" locomotives retail for over £500 apiece and lately have been appreciating in value at well over 20%.

Signals

A natural for digital IC application is signaling. Model signals in two (red and green) or three aspect (red, yellow, green) with operating miniature 12V 60mA lamps are available. Until recently, relays were widely used by modellers to operate these lamps in controlled sequence and often automatically disconnected a section of track ahead of a red signal for automatic train control. The relays used were typically low resistance coils in series with the power supply to the track. When the locomotive entered a particular track section, the relay contacts closed. All model railroads use track sections from 2 to 20 feet long insulated from each other and switchable to alternate power packs. This facilitates the operation of multiple trains.

Complete model railroads still exist using these series relays for automatic control and signalling; but they're a maintenance nightmare for their intermittently proud owners. Up to date techniques use TTL gates driving red, yellow and green LED's for signals.

Relay driver ICs can be added to drive the small 12 V signal lamps if preferred and also to operate good solid 12 V relays for automatic stops and starts.

The interface between train and TTL is a little more tricky; you've noticed, of course, that the track has only two rails which are required to conduct power (in either direction) to the locomotive. The requirement to detect locomotive presence led a few years back to a widely used detector circuit known as a "Twin-T".

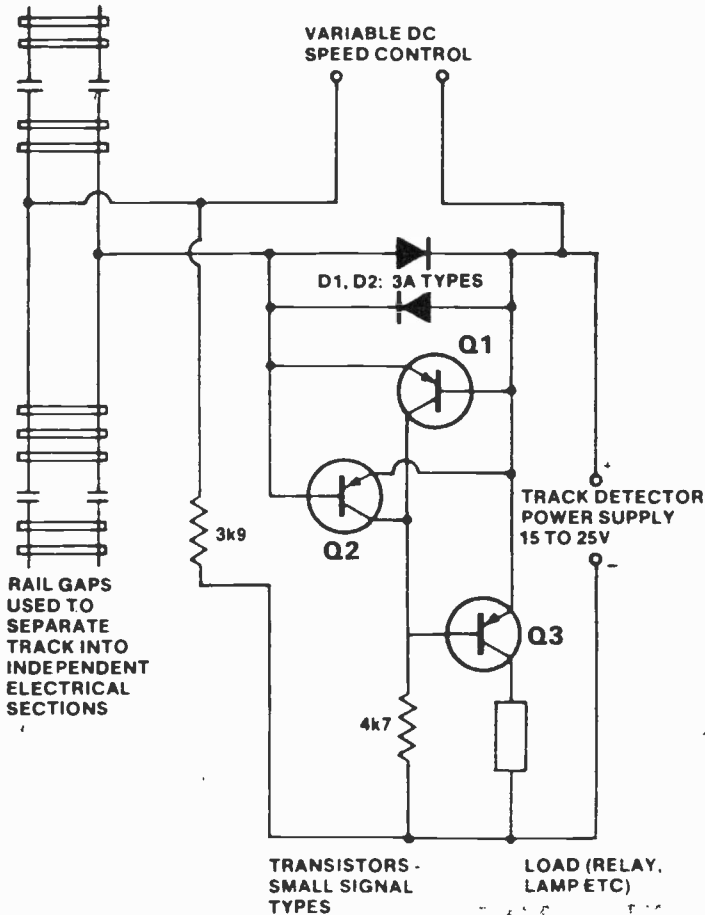
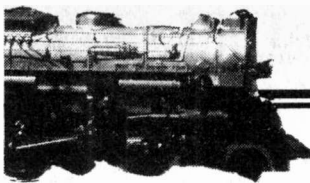


Fig. 2. Widely used "Twin T" track detector circuit. Q3's load de-energises whenever a resistance appears across track in the section being detected, regardless of whether power is connected to that track section. Consequently presence of any train or item of rolling stock can be sensed remotely.

The simple circuit is shown in Fig. 2. The circuit detects resistance between the rails as high as 50k, but is insensitive to the connection of the power supply in the circuit, so it will respond only to the presence of a locomotive motor or any rolling stock with a 10k to 4.7k resistor wired between its wheels. Other less subtle interfaces are magnetic reed switches between the track, triggered by disc magnets under rolling stock—ideal for JK flip-flop operations, or opto-electronics, where ambient light can be interrupted by the movement of rolling stock to trigger or detrigger a light activated SCR, for example.

With a light activated system, the light source and the opto detector must be angled to the track to avoid gaps between moving rolling stock causing light modulation.

All three track detection systems are, of course, suitable input interface for microprocessor control of signals . . . and track voltage, polarity, etc.

Turnout Control

Turnouts, (switches, or points) control train routing. Remote control of these, on the models as on the prototype has nearly always been electric. The usual method is the use of a solenoid motor (Fig. 5). A soft iron armature can be moved into either of two high flux

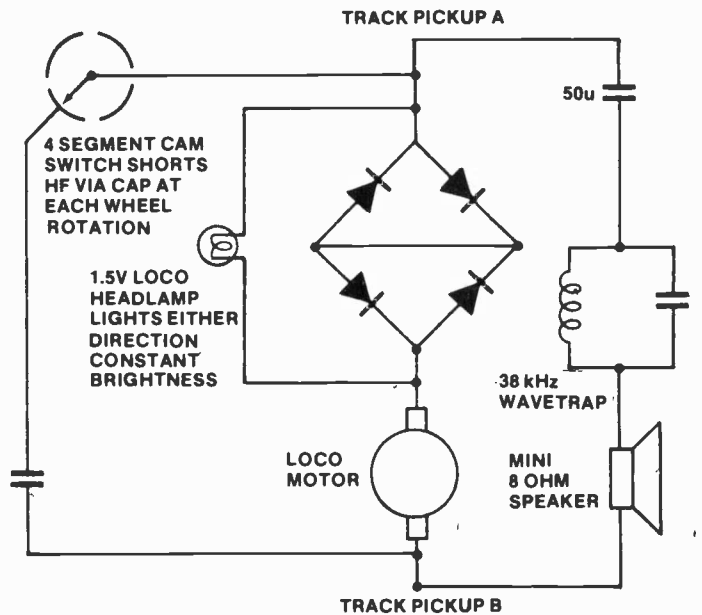


Fig. 3. These components, mounted in locomotive tender reproduces audio signals superimposed on DC motor voltage. Cam switch signals synchronization of "chuff" sound to trackside audio generator.

copper wound coils, depending on which is energised — using 16 Volt AC or DC. The armature is linked mechanically to the movable track section to control the train's alternate paths. These coils of necessity are about 2 to 4 ohms resistance and hence can draw a 4 A: if left connected to the supply for more than a second or so, the 50 W of heat show—rapidly. So recently the electronically minded modeller adopted capacitor discharge.


Typically a 220 u capacitor, charged to 25 V stores enough energy to operate a couple of the low resistance coils and as you can see from the circuit, there's no fire hazard if the power is left on. Also a small transformer can be used. Also shown is a method of discharging the capacitor into the coil via an SCR, which permits the controlling push button to carry only the low SCR gate current, instead of a contact-blowing multi-ampere current.

Again, this basic control circuit is adaptable to TTL control.

Sound

Now you hi-fi fans know it's impossible to reproduce the sound of a gigantic steam locomotive without a 100 W amp and a 4 cubic foot bass reflex enclosure. Except those model railroad nuts don't believe you! Quite expensive, at about US \$350, is a Pacific Fast Mail sound unit that transmits sound and motor power through just those two rails. The sound is synchronized to the piston position, that is for a two cylinder steam engine there are four "chuffs" per driver wheel revolution. Plus bell sound and the required wailing steam chime can also be sent from the trackside to be nicely reproduced in a miniature speaker located in the locomotive tender.

Fig. 4. Model railroad signals. Normally supplied with 12 V lamps, LED's can be fitted.

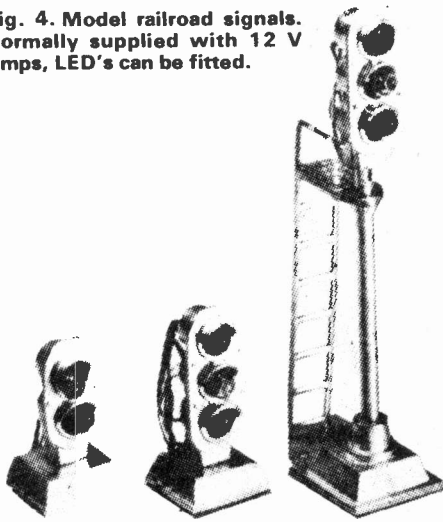

The PFM unit synchronizes the "chuff" sounds by transmitting a 2 V 38 kHz (approx.) signal superimposed on the DC motor voltage going to the track. The DC voltage source (a transistorized circuit, which is a simplified version of the circuit shown in Fig. 1) has a low resistance choke in series with its output: this prevents the 38 kHz and the audio tones from disappearing into the speed circuitry. When the 38 kHz reaches the locomotive, it is intermittently shorted out in a capacitor (see Fig. 3). The capacitor is grounded four times per drive wheel revolution via a phosphor-bronze contact, which rubs on the inside of a drive wheel equipped with insulated quarter sections. As the 38 kHz signal shorts out, a relay operates in the track-side unit, sending out transistorized hiss to the locomotive-borne speaker. Being highly inductive, the locomotive motor bypasses neither the 38 kHz nor hiss—nor bell nor steam chime sounds, all of which are solid-state generated in the PFM box with full operator control. And even though the speaker is less than 2 inches in diameter, the sound is very effective.

Another electronic gimmick in the PFM system is the bridge rectifier of Fig. 3. There's a constant voltage drop of 1V4 across the bridge, since it's in series with the motor—regardless of the motor/voltage polarity. Connect a miniature 1V5 headlamp across the bridge and presto—constant brightness, regardless of motor speed.

A California based firm — Modeltronics, produces sound systems that are completely contained in the model — also synchronized for "chuff". The supply voltage for the noise generator and miniature amplifier is derived from the track voltage much as the PFM "constant lighting section". Of course, the Modeltronics system does not offer bell or chime — yet.

LED Hazard Flashers

Pop a 3mm red or yellow LED into the cabin roof of a model diesel, drive it from an internal LM3909 flasher integrated circuit, oscillating at 0.3 Hz, powered up from 0V5-3V, and you've duplicated real life on the "Atchafalaya Topeka and the Santa Fe".

Grade crossing flashers in model form are available ready made, with miniature 12 V lamps, just like signals. To flash, take on 555 IC timer, put one pair of lamps from IC output to + rail, another pair from output to-rail, apply 12 V, time at 20/minute and grade flashers are in business.

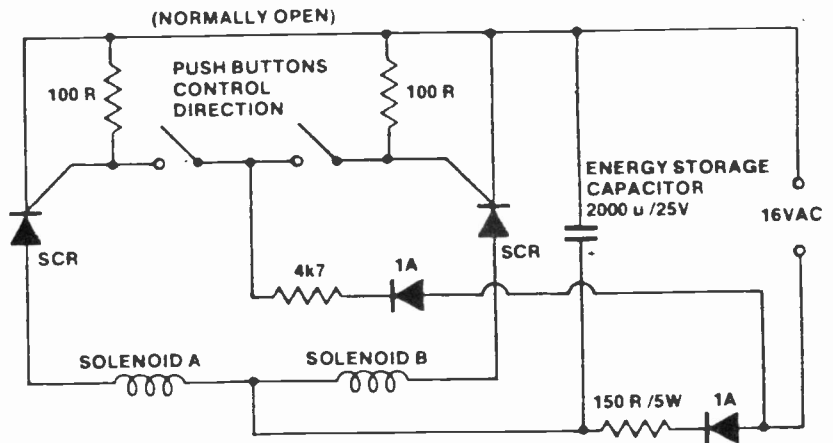


Fig. 5. Capacitor discharge system enables solenoids to be thrown with small average energy. System also prevents solenoid burnup if accidentally left powered-up. SCR switch control enables small current push buttons to switch heavy current. The SCR's automatically switch off when capacitor stored charge zeroes.

Lighting

Whole passenger trains can be lit up using a super-sonic generator at around 25-40 kHz. This can be fairly easily constructed using a 10 W audio power amplifier with the conventional negative feedback rephased to positive. Connected in parallel with the train motor power, with a blocking choke between the two, constant lighting can give a superb visual effect with artificial twilight on a layout. Switch off the generator — and the lights go out. Each train group of lights uses a 220nF capacitor in series to block the otherwise additive lighting power from the DC motor voltage.

Radio Control and Carrier Control

As a purely personal observation, I feel the next and imminent step in electronics with model railroads is radio control. At least one experimental, but practical circuit has already been published. Taken to the ultimate, needed are very low current motors powered by rechargeable NiCd batteries together with the radio receiver, variable speed and direction controls, and sound generator circuit plus amplifier. Of necessity the concept requires extreme miniaturization because for HO scale (the most widely used size), the space available for everything is hardly more than 5 or 6 cubic inches. The entire receiver and motor drive circuit can easily be derived from model aircraft RC designs, particularly if the new Signetics NE544 motor/servo driver chip is employed. On-board sound — for example a diesel horn sound, can use a 556 IC in the self-oscillating mode generating two tones, each around 250 Hz, amplified by an LM380 audio chip.

Individual function control is practical using 555 tone generators in the transmitter with phase lock loop decoders in the receiver. The advantage of this type of control is that the modeller has become free of the power-to-the-rails restriction.

In summary, I hope this overview shows how another hobby can adapt techniques of electronics in order to add to the fun. Maybe I've tempted you to pop round to your nearest Model Railroad emporium.

ETI

TEKTRONIX OSCILLOSCOPES

Main frames 545 with CA £225; 536, 585 with type 82 £395; 581A; 661 with 5T1A & 453 £325; 555; 561A with Plug-in 10 MHz £425; 551; 502 High gain, Special £160. The prices of main frames will vary enormously on condition and plug-ins. Hence prices are guides only. The fact we don't advertise modern oscilloscopes, etc., doesn't mean we don't handle them, only that at our prices they are not normally around long enough to advertise. For example H.P. OSCILLOSCOPE type 183A with 1830A and 1840A 3db 250MHz £950. TEKTRONIX 453 3db 50MHz £650. TEKTRONIX 454 3db 150MHz £1,000. S.E. LABS SM111 3db 20MHz £325. TEKTRONIX SPECTRUM ANALYSER 1L40 Plug-in 1.5GHz to 40GHz £550.

R&S RECEIVER 44.210MHz HUZ BN15012 Poor £60.
BONTOON RX METER type 250A 0.5 to 250MHz. Clean £85.
MARCONI Q METER type 1245 with 1246 £350.
Optional 1247 £100.
TEKTRONIX Sig Gen Type 190A 350KHz to 50MHz and Fixed 50KHz freq. £45 ea.
TEKTRONIX TIME MARK GEN type 180A £60 ea.
SOLARTRON PULSE GEN GO1101 £30 ea.
R&S SWEEP GEN 50KHz-12MHz SWH BN4242/2 £100.
R&S ENOGRAPH-G ZSG BN18531 £120.
R&S AM / FM GEN SMAF BN41404 4MHz-300MHz £300 ea.
R&S AM / FM GEN SDAF BN41023/2 170-940MHz £300.
R&S POWER SIG GEN SMLR BN41001 0.1MHz-30MHz £80.
R&S Z-G DIAGRAPH 30-300/420MHz type ZDU BN35610 £140.
R&S AM GEN 30-300MHz SMLM BN4105 £90 ea.
R&S ATTENUATOR DPU BN18044 / 50 0-3000MHz 0.109db 50 ohm £150.

MARCONI AM / FM GEN TF1066 10-470MHz £275
MARCONI FM GEN TF1077/1 £120.
PHILIPS AM / FM GEN type 201 £160.
BONTOON AM / FM GEN type 202H with Low freq. adaptor £525.
R&S AM GENERATORS 300-1000MHz £120 ea.
AIRMEC AM / FM GENERATOR TYPE 365 £140.
HP SAMPLING Oscilloscope type 185B 1000MHz complete with Plug-in, probes, etc. £195 ea.
SOLARTRON Oscillator C0546 25Hz-500KHz. Sine wave only. Metered. Good attenuator £25 ea.
SOLARTRON PRECISION VOLTMETER VF252. Large clear scale. 1.5mV full scale to 150V full scale £25 ea.
H.P. Oscilloscope type 140A with sampling plug-in 1425A and 1410A DC-1000MHz £550.
H.P. Oscilloscope type 140A with Sampling plug-in 1425A, 1411A and 1432A Sampling head DC-4GHz £750.
SOLARTRON DVM type LM1440 £75 ea. Other Solartron models available. Call and see.
H.P. Digital Recorders 11 digit £35 ea.
AIRMEC AM / FM MODULATION METER type 210 £80.
BIRD TERMINALINE WATTMETER 67C 30-1000MHz 50 ohm £95.
E.H. PULSE GEN model 122 £140.
MARCONI AM / FM MODULATION METER TF2300 with TM8045 £450.
R&S POLYSCOP SWOB1 Scruffy, working £250 ea. Nice condition £350 ea.
R&S POLYSCOP SWOB2 Fair condition, working £425 ea. Very clean £550 ea.
EX-MINISTRY American USM16 AM / FM SWEEP SIG GEN 10MHz-420MHz. Incremental controls. Auto lock. Crystal calibrator and many other features. In transit case with accessories and manual £195 ea.
COSSOR OSCILLOSCOPE type CDU150 DB DC-35MHz £425 ea.
R&S-Z-G DIAGRAPH 300-2400MHz BN3512 Good condition £60 ea.
MARCONI SIG GEN TF801D/8/S. Very good condition £325 ea.

MARCONI RF POWER METER TF1152A / 1 50 ohm £55 ea.
PLUG-INS for Telonic Sweeper SM2000. Various form £50 ea.
TELONIC SWEEPER SD3M 425-930 MHz £80 ea.
MARCONI TF868 Universal Bridge £70 ea.
AIRMEC SIG GEN type 204 1-320MHz £225.
MARCONI SIG GEN TF801B £160 ea.
POLARAD SPECTRUM ANALYSER TSA with STU-1A 10-1000MHz £350.
POLARAD MICROWAVE RECEIVER MODEL TR 1GHZ to 2.04GHz £200 ea.
BRUEL & KJØER Automatic Vibration Exciter type 1016 Sine Wave sweep from 5Hz to 10KHz £75 ea.
GENERAL RADIO Osc. Unit 1209B 250-920 MHz £50.
POLARAD SPECTRUM SIGNATURE MONITOR 140HZ - 12.5MHz Sensitivity 120dbm Price £250.
POLARAD SIGNAL GENERATOR GB2 / G-711 £250.
GENERAL INSTRUMENTS TRANSFER FUNCTION & IMMUTANCE BRIDGE type 1607A in transit case £425.
MARCONI SIGNAL GENERATOR TF1060 £185.
BRADLEY MULTI METER CT471 £45 ea.
H.P. PULSE GEN 212A £55 ea.
H.P. Microwave Freq. Converter type 2590B £175.
MARCONI CT44 Watt Meter 0-6 Watts £25 ea.
AVO TRANSISTOR & DIODE TESTER CT 537 £50 ea.
AUTO TRANSFORMER 240V input. 110V output 1.25KVA £14 ea.
FLUKE AC-DC VOLTMETER Model 8038 £75 ea.

TELETYPE ASR33 with 20MA LOOP. Good condition. Special low price £395 ea. KSR33s from £275.
DON'T FORGET YOUR MANUALS S.A.E. WITH REQUIREMENTS

TELETYPE ASR33 with 20MA LOOP. Good condition. Special low price £395 ea. KSR33s from £275.

STEPPING MOTORS

All motors 200 steps per revolution. 20oz. inch torque. 120V 1000-0-1000 ohm. Can be changed with care to 12/24V. Data supplied. £8 ea.
Supplied for 12/24V operation £13 ea. P&P £1.
Just think about the uses!

JUST IN

A SUPERIOR KEYBOARD Size 3 x 2½ x 2" high with 12 ALMA REED SWITCHES. Blue keys marked in green 0-9 and a star with one blank. ONLY £5 ea. P&P 75p.

Photo Resistor ORP 12-35p ea.
Small TELESCOPIC AERIAL extending to 22½" with swivel base 40p ea. P&P 20p.
Small Black SUCKER FEET — always useful 10 for 50p.
MERCURY SWITCHES. Heavy duty with lever & flyleads 20p ea.
PHOTODIODE DETECTOR & EMMITTER. Independently mounted with 4" flyleads — 50p per pair.
ZENER DIODES 4.7V Sub-min. 5p ea.
TEXAS I.C. type SN15862N 4p ea.
RESISTORS 680 Ohms 5 Watt — 10 for 50p.

VIEWLEX INSTRUCTIONAL SUPER VIEWERS MODEL 136 with Headphones. 9" screen. Takes standard cassette. Front keys. Brand new boxed £55 ea. Slightly used £45 ea. Carriage £3.25 ea.

★ TRANSISTORS/DIODES/RECTIFIERS. ETC★

Guaranteed all full spec. devices. Manufacturers' Markings.
At 5p ea.
BC147; 2N3707; BC172B; BC251B; BC348B; BC171A/B; BC413; D10; BAX15; 1N937; BA102BE; BZX83; TIS61; 2N5040.
At 10p ea.
1N4733A; SN7451N; BYX10-15V 0.36A; BYZ10 15p ea.
TIP34A — 50p ea. BD538 — 40p ea. Heavy Duty Bridge Rectifier — 20p ea. CA3123E — £1 ea. BDY55 — £1 ea.
2N3055 — 40p ea. TIP31B 12p ea. BFY51 — 12p ea.
2N5293 — 16p ea.
TBA560CO £2 ea. 1N4436T-TO3 Flat mount 10A 200Vip £1 ea. 2N5897 with 2N5881 Motorola 150W Comp pair £2.
BU208 £1.20 ea.
BD535, BD538 Comp. pair — 75p.
Linear Amp 709 25p ea.
P&P extra on all items.
FINNED HEAT SINK — single TO3 — size 4¼in x 3in x 1¼in 50p ea. P&P 75p.
Texas Bridge Rectifier 5S805-50V 5A 60p ea. P&P 20p.
MOTOROLA POWER TRANSISTORS type W0993/441 TO3 Min. voltage 500. 20p ea. P&P 15p.

A MILLION MUST GO

HIGH NOISE IMMUNITY LOGIC.
DUAL IN LINE 16-PIN CERAMIC. 12V Rail. Conventional TTL package. Guaranteed spec. devices. Full data. 2p ea.

OSCILLOSCOPE TUBES

Brand New Boxed — Carriage all tubes £3.25.
Teletype S52 £10 ea; D51 £15 ea; S42 £10 ea; D53A £20 ea; D52 £15 ea; S31 £10 ea; Bradley 200 £85 ea; Advance OS3000 £85 ea; GEC types 924F £25 ea; 924E £17.50 ea; 14968 £75 ea; Brimar D13-51HG £65 ea; D10-210GH/32 £40 ea; D13-46GM £35 ea.
NOT BOXED — NEW — WARRANTED. Telefunken D14-131 replacement for Solartron CD1740, Cossor CDU150, S.E. Labs SM112 and GEC/MOV1474 at £55 ea.

BUILD YOUR OWN BUS

Approx. 1½ metre multiway ribbon cable terminated each end with a 50V type female edge connector. Takes 0.1 printed circuit board. £2 ea. P&P 75p.

TELEPHONES. Post Office style 746 Black or two-tone £6.50 ea. Modern style 706 Black or two-tone grey £4.50 ea. P&P £1.

HANDSETS 706 style £1.75 each. Older style £1. P&P 75p.

TELEPHONE EXCHANGES. EG 15-way automatic exchange only from £95.

74S00	12p	74S10	5p	74H51	7p
7401	5p	7417	14p	7453	5p
74S02	12p	74S38	10p	74H74	12p
74S04	12p	7451	5p	74S74	12p
MC4028	60p	MC7441	40p	7402	12p

75325 — Memory Core Drivers. 600ma capability. Fast. Other uses. RIDICULOUSLY at £1 ea.

75453 — Dual Peripheral or Drivers 75p ea.

NOW—INCREASE AREA GIVEN TO PICK-A-PACK AT 50p per lb

Larger volume of new components you can't afford to miss

ALMA Min. PUSHBUTTON REED SWITCHES. High reliability 18 x 27 x 18mm. Ideal for KEYBOARD 50p ea. P&P extra.

MINIATURE FANS 3" square (like muffins) 115V £5 ea. P&P 75p.

HONEYWELL HUMIDITY CONTROLLERS 25p ea. P&P 25p.

SPRAGUE 100mfd + 500mfd 210VDC working. Brand new. 5 for 50p. P&P 50p.

REED SWITCHES. Sub-min. Size 20mm 10p ea.

SMITHS encapsulated transistorised AUDIBLE WARNING DEVICES 4V-12V. Can be driven from TTL. 50p ea. P&P 25p.

AMPHENOL 17-WAY CHASSIS MOUNT EDGE CONNECTOR. 0.1 spacing 20p ea. P&P extra.

BURROUGHS 9 digit PANAPLEX numeric display. 7 segment 0.25 digits with red bezel. With date. £1.95 ea. P&P 30p.

TRANSFORMERS 115V AC input. Secondary 30V and 2.6V 10VA. 50p ea. P&P 50p.

21-WAY SELECTOR SWITCH. Single pole with reset coil 240V AC coils. Additional switch contacts for auto reset. etc. £1.45 ea. P&P 75p.

As ABOVE with additional 240V relay on base and full black plastic cover. £2.45 ea. P&P £1.50.

SNAIL BLOWER 110V AC 500 MA Brand new by Airflow Developments. Quiet and very good looking. £2.50 ea. P&P £1.

POTTER & BRUMFIELD 18-48V DC Relay. 3 pole c/o. Heavy Duty. Plug-in type with base 50p ea. P&P 25p.

MINIATURE KEYBOARD. Push contacts, marked 0-9 and A-F and 3 user definable keys. £1.75 ea. P&P 35p.

MULLARD CORE LA4245 at 15p ea. P&P 10p.

CLARE REED RELAYS 24V DC Coil. Single pole make. Size 1¼ x 7/16 x 7/16 at 25p ea. P&P 10p.

ROTRON CENTAUR FANS. Size 4.5 x 4.5 x 1.5" 115V 5 blade. £4 ea. P&P 75p.

MIN. PLUG-IN type RELAYS. Plastic covers. 2-pole c/o 24V 25p ea. P&P 15p.

CROUZET/MURTEN SCHWEIZ MOTORS. 110V 50HZ 4 rpm. Gearbox can be removed 75p ea. P&P 75p.

FRAMCO MOTORS. 115 50HZ. Input single phase. 1/12th HP. 1,450 rpm; on silent mount. As new. £2.75 ea. P&P £1.75.

PYE DYNAMICS THICK FILM. 1 MHz Clamping Osc 5V supply. Size 19 x 25 x 6mm. Drives one TTL load. 75p ea. P&P 15p.

COMPRESSOR UNIT. Compact. 115V 50HZ single phase 1.5A continuous 1.425 rpm. Outside piston housing approx. £18 ea. P&P £2.

MAGNET DEVICES. Plug-in RELAYS 240V AC. 3-pole c/o. Heavy duty 10 amp. Complete with base. BRAND NEW EQUIPMENT NOT USED. 3 on sub assembly £2.50. P&P £1 or £1.25 ea. P&P 45p.

SMALL MAINS TRANSFORMER 240V Pri. 12V 100MA sec. 60 x 40 x 42mm. 50p ea. P&P 75p.

G.I. BRIDGE RECTIFIER type W01 (ideal for above) 17p ea. FAIRCHILD FND10 7 segment display 0.15. Red. Common cathode 65p ea. P&P 15p. Info supplied.

MULLARD TUNER MODULES — with data.
LP1171 combined AM/FM IF strip. 10.7MHz. £3.50 ea.
LP1179 FM front end with AM tuning and 87.4MHz to 104.5MHz tuning. 10.7MHz IF. £3.50 ea. P&P 50p each unit. The Pair £5.75. P&P 75p.

POWER UNIT MODULE containing 2 small, 3 med. & 1 large ferrite cores; 3-TO3 power transistors, caps, resistors, high powered diodes, 9 transistors, 3 min. fuse holders, etc. £1.50 ea. P&P £1.25.

GENERAL ELECTRIC OPTO-ISOLATORS type H15VX504 65p ea. P&P 15p. 10 for £5. P&P £1.

MINIATURE REED SWITCHES 9p ea. P&P 15p.

ROTARY SWITCHES 250V 10A 10p ea. P&P 15p.

LEDEX ROTARY SOLENOIDS 115V DC. No switch assembly 25p ea. P&P 25p.

POTTER & BRUMFIELD TIMER RELAYS. 24/48V. Heavy duty 2 pole c/o with 5 secs. delay at 48V increasing with voltage reduction. Timing can be altered by changing value of resistor/capacitance 50p ea. P&P 25p.

CABLE NEATERS — neaten up your wire on a chassis with these push-on clips. 10 for 20p. 100 for £1.50. P&P extra.

AUDIO AMPLIFIER BOARD. Size 4½ x 2½. Output pair of TIP31s. Circuit supplied. £1.50 ea. P&P 30p.

DIGITAL 24-HOUR CLOCK with built-in alarm as used in BRAUN Digital Clocks. Silent running. Large illuminated Numerals. AC Mains. Size 6½ x 2½ x 2¼. ONLY £4.25 ea. P&P 50p.

BROOKE CROMPTON & PARKINSON extractor fan assembly 115V operation. £1 ea. P&P £2. OR TWO for £1.50. P&P £3.25.

½" MAG TAPE

Approx. 1,500ft. Now 20p each. P&P £1, or 7 for £1, carr. £3.25.

FOR THE VDU BUILDER, tube M28-13GH 23 x 17cm at £12. Base connections supplied.

Limited quantity of 35R0-20ma loop — can be changed to ASC11 code (3 hours' simple work and £10 parts). OUR PRICE EXCLUDING PARTS REQUIRED £70 ea.

Ex-Ministry Teletype Punches B level 110 char per sec. £50 ea. Polished Wooden Cases to take normal 'QWERTY' KEYBOARDS, or can be carefully cut to take any size. £3 ea. P&P £1.50.

TELETYPE ASR28 with built-in tape reproducer and print on tape facility. £375.

TELETYPE ASR35. Nice condition. £425.

VARIACS — ex-ec. 2 amp £8 ea; 8 amp old style £18 ea. later style £22 ea. 15 amp £35 ea; 20 amp £45 ea. 3 Phase variacs available — please enquire.

A LARGE QUANTITY OF MISCELLANEOUS TEST GEAR — CHASSIS UNITS, ETC., ON VIEW AT LOW COST

Minimum Mail Order £2. Excess postage refunded. Unless stated — please add £3.25 carriage to all units

VALUE ADDED TAX not included in prices — Goods marked with * 12½% VAT, otherwise 8%

Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order.

Open 9 a.m. to 5.30 p.m. Monday to Saturday



CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS (rear Technical College, King's Road). Tel: Reading 582605

AUDIO AND TEST EQUIPMENT CENTRE

MICROCOMPUTERS LEVEL I AND II TRS/30 IN STOCK
ALL PRICES INCLUDE VAT

Only regular stocks listed — other makes and models available.
Telephone your order with Access and Barclaycards



4D10A



DM235



TE20D

LONDON'S TEST GEAR CENTRE
OPEN 6 DAYS A WEEK 9 am-6 pm


SCOPES — IN STOCK

3" 5MHz single beam	92.50
4810, 5MHz single beam (4)	107.00
MS15, 15MHz Batt/ mains, portable	286.00
MS21B, Dual trace version of above	360.00
Super 6/45S Scope x 6MHz single beam	149.00
Super 10/4010A, Scope x 10MHz Dual trace	229.00
4025, Scope x 25MHz Dual trace	338.00

PROBES x 1 x 10 14.50, x 10 9.95 x 1 7.95 For 456/4D10A/4D25

LED AND LCD DIGITAL MULTIMETERS

DM235 Sinclair portable 3 1/2 digit LED	52.90
PDM35 Sinclair Pocket 3 1/2 digit LED	29.95
DM350 New Sinclair 3 1/2 Digit	74.50
DM450 New Sinclair 4 1/2 Digit	96.00
(30kV Probes 18.25, Mains adaptors 3.75, DM235 carrycase 8.95)	
LM3A 3 Digit Miniature with large LED displays	96.00
LM3.5A 3 1/2 Digit Recharge Batts and charger 17 ranges	106.00
LM40A 4 Digit Miniature battery operated 17 ranges	210.00
LM300 3-digit Miniature battery operated 17 ranges	87.00
LM350 3 1/2-digit with LCD displays 1µA/mV resolution	98.00

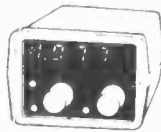

IM3.5A

MULTI-METERS — GENERAL PURPOSE & ELECTRONIC

Multi-Range Instruments featuring AC/DC volts, DC current, Resistance Ranges all with mirror scales except T1/T1.2/T1.2/TM3A (TM3 AC volts only), some with AC current etc.

TM11 incredible 120 Range Electronic Multi-meter	136.00
TM3B AC Micro voltmeter 3MHz >4 Megohm	130.00
TM6B Broadband/voltmeter 300KHz-400MHz	196.00
360TR 100k/volt 23 Range (plus transistor checker) Large scale	35.50
PROE 20k/volt 26 Range, Large scale	32.00
70B1 50k/volt 36 Range Multi-meter	23.50
TM500 30k/volt 22 Range Multi-meter (plus Continuity Buzzer)	21.00
680R 20k/volt 52 Range Pocket Multi-meter	34.50
7200 20k/volt 22 Range Double Multi-meter	17.95
Micro80 20k/volt 26 Range Pocket Multi-meter	17.90
IT1-2 20k/volt 16 Range Popular Multi-meter	11.95
LT22 20k/volt 19 Range Pocket Multi-meter with carry case	14.50
LT2 20k/volt 13 Range Pocket Multi-meter	8.95
LT12 5k/volt 12 Range Pocket Multi-meter	7.50
LT101 1k/volt	
EM2000 FET IC VOM 20 Ranges 10 Meg Input	55.00
K200 FET VOM 38 Ranges	77.00
GT101, 20K/Volt 23 Ranges/Transistor Checker/Continuity Checker	17.95

AVO 8s and a large range of replacement tests leads in stock

GENERAL EQUIPMENT

TE7 Signal Tracer	8.95
SWR50 SWR/Power Meter	19.50
LP30 30MHz Low Pass Filter	4.95
CX33A 150Watt 3-way AE Switch	7.50
DC25kV 100 Meg HV Probe	11.95
9 Value CAP Subs Box	2.95
DRS10 36 Value Resis. Box	3.90
FX2000 Xtal Marker	11.95
TR1000 Transistor checker in/out circuit	11.95
MOD63 Signal Injector	7.50
TT169 In Circuit Trn Checker	49.95
L81 Transistor/Diode Checker	21.50
3101 Clamp Meter 0/1 K ohm 0/150/300/600 AC Volts 0/300 Amp	32.95
C3042 SWR & FS Meter	9.95
MS319 2x100 Watt Audio Watt Meter	17.50
500V Megohmmeter 500 Megohms	48.00
1000V Megohmmeter 1000 Megohms	55.00
2 1/2 Amp Variable Transformer	19.95
5 Amp Variable Transformer	33.00
10 Amp Variable Transformer	46.00
Decade Resis. Boxes:	
1-11, 110 ohm in steps of 1 ohm	33.00
10-111, 110 ohm in steps of 10 ohms	33.00
1-1,111, 110 ohm in steps of 1 ohm	42.50
Cap. Decade Box:	
10pF — 111, 110pF in steps of 10pF	33.00

GENERATORS

TG152 Series RC Oscillators Sine/Square output, 3Hz-300KHz	75.00
TG152D TG152 Dm (with meter)	95.00
TG200 Series RC Oscillators Sine/Square output, 1Hz-1MHz	100.00
TG200D TG200 Dm (with meter)	121.00
TG200 Dmp (Meter & Fine control)	126.00
TG66A Digital Sine Wave Decade control 0.2Hz-1.22MHz	267.00
TE22D (audio) 4 bands Sine 20-200KHz Square 20-150KHz	65.00
TE20D (RF) 6 bands 120KHz-500MHz	57.00

LOGIC PROBES AND MONITORS

LT2000 Economy Probe 10MHz	11.95
LM1 Monitor	31.00
LP1 Probe 10MHz	33.48
LP2 1.5MHz	19.44
16 Pin IC test clip	2.20

PIEZO HORN TWEETERS

Up to 100 watts each, No x-over reqd. Only 4.95 each (P/P 20p) 10% Discount for 10 Plus



MICROPHONES, SPEAKERS AND COMPONENTS LARGE RANGE IN STOCK




TM11



TMK500



FM7 7 Digit 60MHz Resch. Batt. Freq. counter 156.00
SC5 512MHz Prescaler for above 81.00
MAX100 100 MHz 8 digit batt operated counter 83.75

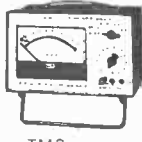

TM3

PRICES CORRECT AT OCT. 3rd. E & OE

AUDIO ELECTRONICS

301 EDGWARE RD., LONDON W2 1BN
01-724-3564. OPEN 9-6, MON-SAT.

ALSO AT 248 TOTTENHAM COURT ROAD, W. 1

FREE CATALOGUE

SEND STAMPED (12" x 3" U.K.)
ADDRESSED ENVELOPE (MIN 9" x 4 1/2")
FOR YOUR COPY NOW



ANOTHER WORLD FIRST!

NEW KEYBOARD KIT

Catronics Ltd are proud to announce the introduction of the world's first modular Keyboard Kit available to the home constructor!

The printed circuit board is designed to take a maximum of 70 keys but may be assembled with a smaller number of keys for a simpler keyboard.

The board is not dedicated to any specific coding, allowing it to be used for any project whether it requires ASC11, Baudot or any other code. This makes it suitable for many projects including:

E.T.I. — System 68 MPU (54 keys)
Auto mouse sender, etc.

The Keyswitches themselves are single pole push-to-make type and require no extra mechanical mounting arrangements.

A legend sheet is provided with each kit enabling the constructor to label the keys to suit individual requirements.

Catronics price: Kit for 70 station Keyboard: £29.00.
Please add 50p for post & packing.

FREQUENCY COUNTER CHIPS

We have the widest range of counter chips in stock as follows:

74C926 £5.30; MK50395 £7.55; ICM 7208 £15.70; ICM 7216C £22.70; ICM 7216D £19.65; ICM 7726 £27.20.

Application information also available. Try us for 7 segment displays, display drivers and prescaler i.c.s.

SPECIAL PRICES FOR CMOS

4001	18p	4018	90p	4047	95p	4082	21p
4002	18p	4020	96p	4049	52p	4508	£2.30
4006	£1.80	4021	92p	4050	52p	4510	93p
4011	18p	4023	22p	4051	74p	4511	£1.30
4012	18p	4025	18p	4053	81p	4518	93p
4013	45p	4030	67p	4060	£1.07	4521	£2.30
4016	62p	4040	90p	4078	21p	4528	£1.12
4017	86p	4042	£1.03	4081	21p		

VERO CABINETS

All Plastic Range

Code No	Size (mm)	Price
65-2514F	100x50x25	£1.70
65-2516G	100x50x40	£1.91
65-2518H	120x65x40	£2.15
65-2520J	150x80x50	£2.45
65-2522K	188x110x60	£3.25

Metal Fronted Range

Code No	Size (mm)	Price
75-1237J	85x40x154	£2.67
75-1238D	85x60x154	£2.91
75-1239K	85x80x154	£3.47
75-1411D	205x140x75	£4.06
75-1412K	205x140x110	£5.27
75-1410J	205x140x40	£3.64

Aluminium top panel — 65-3851A (120x65x40) £3.31
Sloping front panel — 75-1798K (171x121x75/37.5) £4.30
Sloping front panel — 65-2523E (220x174x100/52) £6.70

19" CARD FRAME / CASE SYSTEM

Card Frame / case	71-3841-L	£20.91 + £1.25 p&p
Pair end plates	71-3842-F	84p
8" Module	71-3843-A	£4.04
4" Module	71-3844-G	£3.08
Veroboard	09-3979-K	£1.40
2" Front panel	71-3845-B	£1.03
1" Front panel	71-3846-H	98p
Veroboards (less c'n'ct'r)	09-1034-F	£1.33
Plain board (less c'n'ct'r)	09-1040-J	90p
DIP board (less c'n'ct'r)	10-1041-J	£3.60
Connector, plug, 31 way	17-0267-H	98p
Connector, socket, 31 way	17-0268-C	£1.07
VQ DIP board	01-0044-C	£1.12

All prices include VAT at current rates
Please note our minimum U.K. post and packing charge, except where indicated, is 20p. EXPORT ORDERS welcomed.

COMMUNICATIONS HOUSE

DEPT. 852 20 WALLINGTON SQUARE,
WALLINGTON, SURREY, SM6 8RG

Tel: 01-669 6700 (9 a.m. to 5.30 p.m., 1 p.m. Sat.)

ETI BOOK SERVICE

BEGINNERS

Beginners Guide to Electronics Squires £2.65
Beginners Guide to Transistors Reddihough £2.65
Electronic Measurement Simplified C. Hallmark £2.20
Electronics Self Taught Ashe £4.40
Beginners Guide to Integrated Circuits Sinclair £3.15
Principles of Transistor Circuits S. Amos £4.75
Understanding Electronic Circuits Sinclair £4.10
Understanding Electronic Components Sinclair £4.10
Beginners Guide to Radio King £3.15
Beginners Guide to Audio Sinclair £3.10
Beginners Guide to Audio L. R. Sinclair £3.20

COOKBOOKS

TV Typewriters Cookbook £7.75
CMOS Cookbook £8.20
Active Filters £11.30
IC Timer Cookbook £7.50
IC Op-Amp Cookbook £10.00

APPLICATIONS

Advanced Applications for Pocket Calculators J. Gilbert £4.20
Build Your Own Working Robot D. Heiseman £3.55
Electronics and Photography R. Brown £2.30
Fire and Theft Security Systems B. Wels £2.00
How To Build Proximity Detectors and Metal Locators J. Shields £3.90
How To Build Electronic Kits Capel £2.10
Linear Integrated Circuit Applications G. Clayton £5.40
Function Circuits Design & Applications Burr Brown £15.95
110 Electronic Alarm Projects R. M. Marston £3.45
110 Semiconductor Projects for the Home Constructor R. M. Marston £3.25
110 Integrated Circuit Projects for the Home Constructor R. M. Marston £3.25
110 Thyristor Projects Using SCRs R. M. Marston £2.95
Handbook of IC Circuit Projects Ashe £2.30
Practical Electronic Project Building Ainslie and Colwell £2.45

TV AND HI-FI

Audio Handbook G. King £6.50
Cassette Tape Recorders J. Earl £5.25
Solid State Colour TV Circuits G. R. Wilding £6.35
Hi-Fi Loudspeakers and Enclosures Cohen £8.20
How To Build Speaker Enclosures Badmateff £3.90
Master Hi-Fi Installation King £2.80

LOGIC

Logic Design Projects Using Standard ICs J. Wakerly £5.10
Practical Digital Design Using ICs J. Greenfield £12.50
Designing With TTL Integrated Circuits Texas Instruments £9.00
How To Use IC Circuit Logic Elements J. Streater £3.65
110 COSMOS Digital IC Projects for the Home Constructor R. M. Marston £3.20
Understanding CMOS Integrated Circuits R. Melen £4.00
Digital Electronic Circuits and Systems R. M. Morris £3.50
MOS DIGITAL ICs G. Flynn £4.60

COMPUTING

Microprocessors and Microcomputers B. Sowick £18.00
Microprocessors D. C. McGlynn £8.40
Introduction to Microprocessors Aspinall £5.90
Modern Guide to Digital Logic (Processors, Memories and Interfaces) £4.30

OP-AMPS

Applications of Operational Amplifiers Graeme (Burr Brown) £8.30
Designing With Operational Amplifiers Burr Brown £16.65
Experiments With Operational Amplifiers Clayton £3.40
110 Operational Amplifier Projects for the Home Constructor R. M. Marston £2.95
Operational Amplifiers Design and Applications G. Tobery (Burr Brown) £7.40
Op-Amp Circuit Design & Applications J. Carr £4.00

TEST INSTRUMENTS

The Oscilloscope In Use Sinclair £3.10
Test Instruments for Electronics M. Clifford £2.40
Working With the Oscilloscope A. Saunders £1.95
Servicing With the Oscilloscope G. King £5.60
Radio Television and Audio Test Instruments King £5.90

SERVICING

Electronic Fault Diagnosis Sinclair £3.20
Rapid Servicing of Transistor Equipment G. King £2.95
Tape Recorder Servicing Manual Gardner Vol. 1: 1968-70 £8.50
Vol. 2: 1971-74 £8.50
FM Radio Servicing Handbook King £4.80
Basic Electronic Test Procedures J. M. Gottlieb £2.45

COMMUNICATIONS

Communication Systems Intro To Signals & Noise B. Carlson £7.50
Digital Signal Processing Theory & Applications L. R. Rabiner £23.80
Electronic Communication Systems G. Kennedy £8.50
Frequency Synthesis. Theory & Design Mannassewitsch £20.40
Principles of Communication Systems H. Taub £8.10

THEORY

Introduction to Digital Filtering Bogner £9.40
Transistor Circuit Design Texas Instruments £9.35
Essential Formulae for Electrical and Electronic Engineers N. M. Morris £1.65
Modern Electronic Maths Clifford £6.70
Semiconductor Circuit Elements T. D. Towers £6.40
Foundations of Wireless Electronics M. G. Scroggie £4.45
Colour Television Theory Hudson £6.20

REFERENCE

Transistor Tabelle (Includes physical dimensions) £4.10
Electronic Engineers Reference Book (Ed. 4) L. W. Turner £27.70
Solid State Circuit Guide Book B. Ward £2.25
Electronic Components M. A. Colwell £2.45
Electronic Diagrams M. A. Colwell £2.45
Indexed Guide to Modern Electronic Circuits Goodman £2.30
International Transistor Selector T. D. Towers £6.00
International FET Selector T. D. Towers £4.35
Popular Valve/Transistor Substitution Guide £2.25
Radio Valve and Semiconductor Data A. M. Bell £2.60
Master Transistor/Integrated Circuit Substitution Handbook £5.60
World Radio TV Handbook 1978 (Station Directory) £8.00
Radio, TV and Audio Technical Reference Amos £24.85
TV Technicians Bench Manual (New Ed.) Wilding £5.10

MISCELLANEOUS

Integrated Electronics J. Milman £7.90
Microelectronics Hallmark £3.90
Practical Solid State DC Supplies T. D. Towers £6.20
Practical Triac/SCR Projects for the Experimenter R. Fox £2.25
Printed Circuit Assembly Hughes & Colwell £2.45

Fallen behind recent advances?
Just starting out?
Need a decent reference book?
ETI Book Service provides an easy
way of getting your hands
on the right title.

How to order: Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P&P.

SOUND~TO~LIGHT UNIT

Designed by Richard Bekker of Powertran, especially for ETI, this superb light show can act as strobe, linear five channel sound-to-light or random switching unit and can be digitally controlled!

OVER THE YEARS several lighting control units have appeared, some performing switching and others performing modulation of the light output according to the musical input. The Chromatheque combines both of these functions in a most original way. It is capable of controlling five banks of lamps — of up to 500 watts each in either analogue or digital mode. By being a five channel controller not only is the sound to light modulation made more exciting than three or four channel systems by virtue of the extra colours, but linear and random sequencing between the channels gives a tantalizing effect which could not occur with a smaller number of channels.

Singled Out

Being conceived as a single board design wiring is minimal and construction very simple. All components are cheap, readily available items but a complete kit is being made available by Powertran of Andover, including metalwork.

Modes

In the analogue mode the audio signal first passes through an amplifier stage with automatic gain control. This ensures that sound to light modulation occurs smoothly even when the overall sound level changes. After this the signal is split into active filter bands the outputs of which are used to phase control triacs which determine the current in the lamps.

By doing this channel 1 (red) responds to the lowest frequencies varying the light in time with the bass notes in the music. Channel 5 (blue) responds to the highest frequencies. The other 3 channels handle the intermediate frequency bands. separate light level control is provided for each channel to allow for intensity adjustment to personal taste to suit different types of music.

Fingers and Digits

In the digital mode TTL integrated circuits are used to

selectively switch either all the lamps in strobe fashion or alternatively one lamp at a time either sequentially or randomly. The speed at which the switching is carried out is controlled either manually with a potentiometer on the front panel or automatically. In this case the switching rate increases with the level of the audio signal. This is particularly effective in the sequential or random switch positions — a crescendo sets the lights racing whilst they freeze when the music stops.


On music with a heavy beat the lights will step round one position on each beat.

Because of the light level controls, the lamps can be turned just partially on to suit the mood of the occasion.


Construction

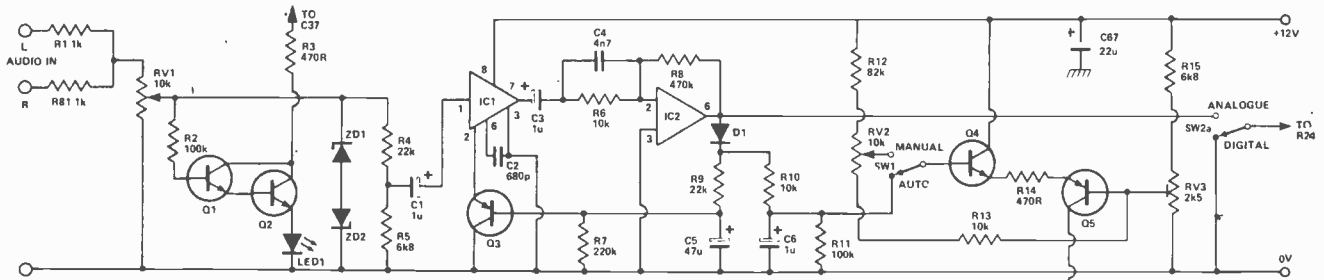Start by assembling the board. This is entirely straightforward — just follow the overlay. All the potentiometers mount directly on the board though the switches are hardwired.





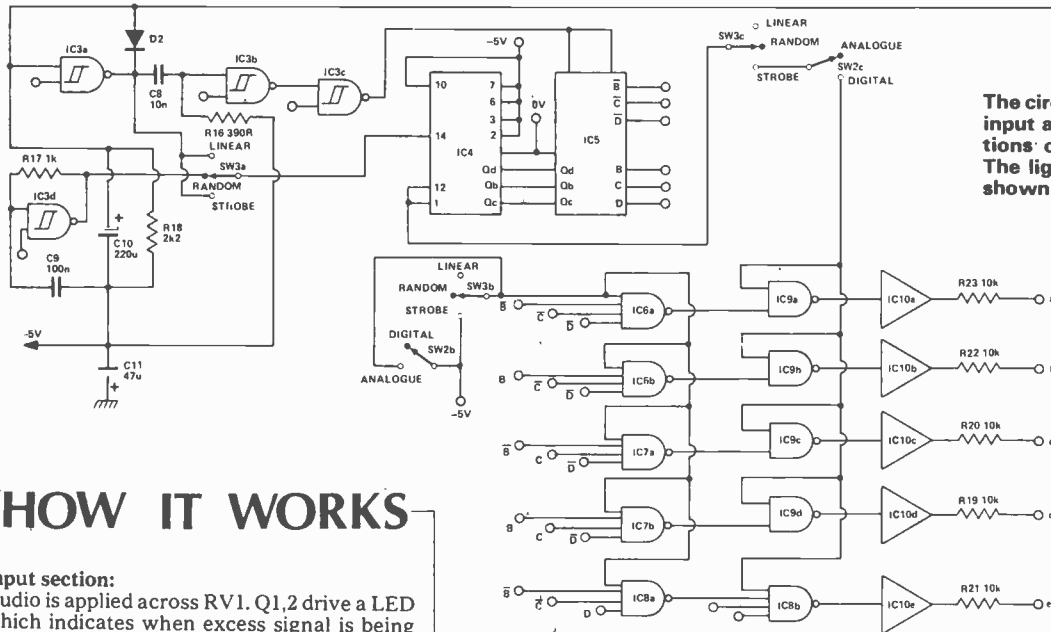The circuit diagram for the audio input and digital switching sections of the lightshow circuit. The light drivers and filters are shown overleaf.




HOW IT WORKS


Input section:


Audio is applied across RV1. Q1,2 drive a LED which indicates when excess signal is being taken off RV1. ZD1,2 clip the signal in cases of gross overload. IC1 is a variable attenuator, the output of which is amplified by IC2. This feeds a 'diode' pump' setting up a voltage on C5 which rises as the output increases. This voltage is used to control Q3 which in turn controls the attenuation of IC1.

Digital section:

IC3 is a block of 4 Schmitt triggers two of which are used to form oscillators. C9,R17 determine the speed of the fast oscillator and fast clock pulses are produced at pin 8. The slow oscillator rate is determined by the rate at which C10 is charged via Q5, the current through which is either varied by RV2 or else the signal on C6, depending on the position of S1. D2 is a germanium type for the benefit of its low turn-on voltage. In the linear sequencing or strobe mode the low speed clock is applied to IC4 which is a +2, +5 counter, the outputs of which are applied to decoding ICs 6,7,8 via 4 bit latch IC5. The outputs of IC6,7,8 are taken via gates in IC9 and half of IC8 to inverters in IC10 to provide negative turn voltages to the triac driver stages. In the linear mode only one of the inverter outputs a,b,c,d,e is negative at any instant whilst in the strobe mode all the outputs are at 0V. In the random mode the fast clock is applied to the counter, the output of which is sampled at a low rate by means of the slow clock being applied to IC5. C8 and two trigger sections of IC3 convert the slow clock into narrow pulses suitable for this sampling. As the two clocks are independent the sampling will be at a totally random point of the count by IC4 thereby making the lamp selection truly random.

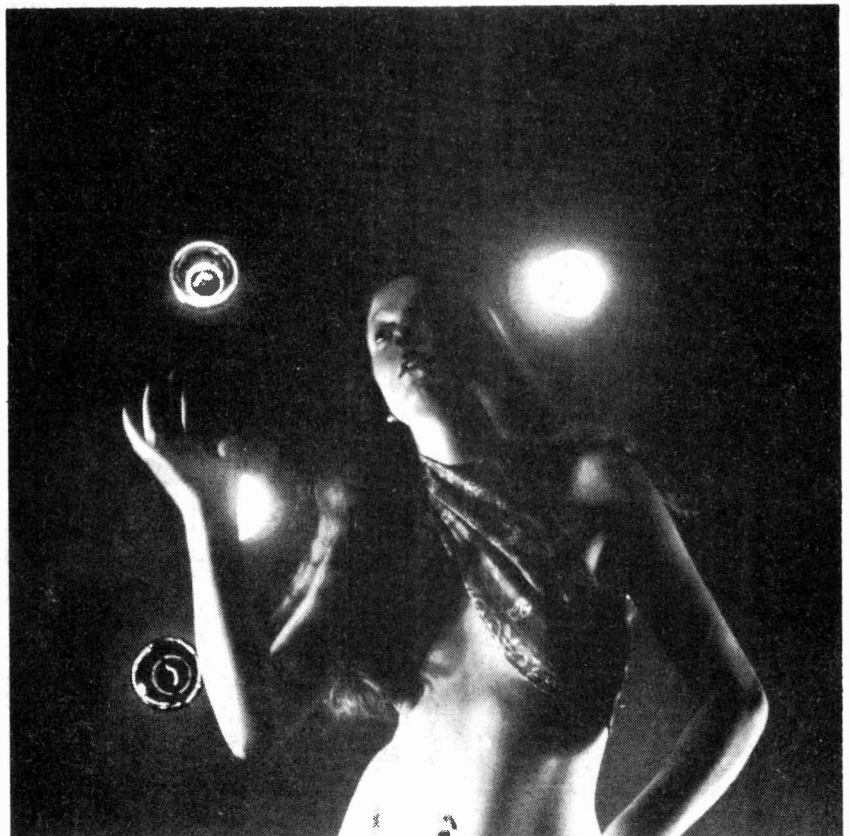

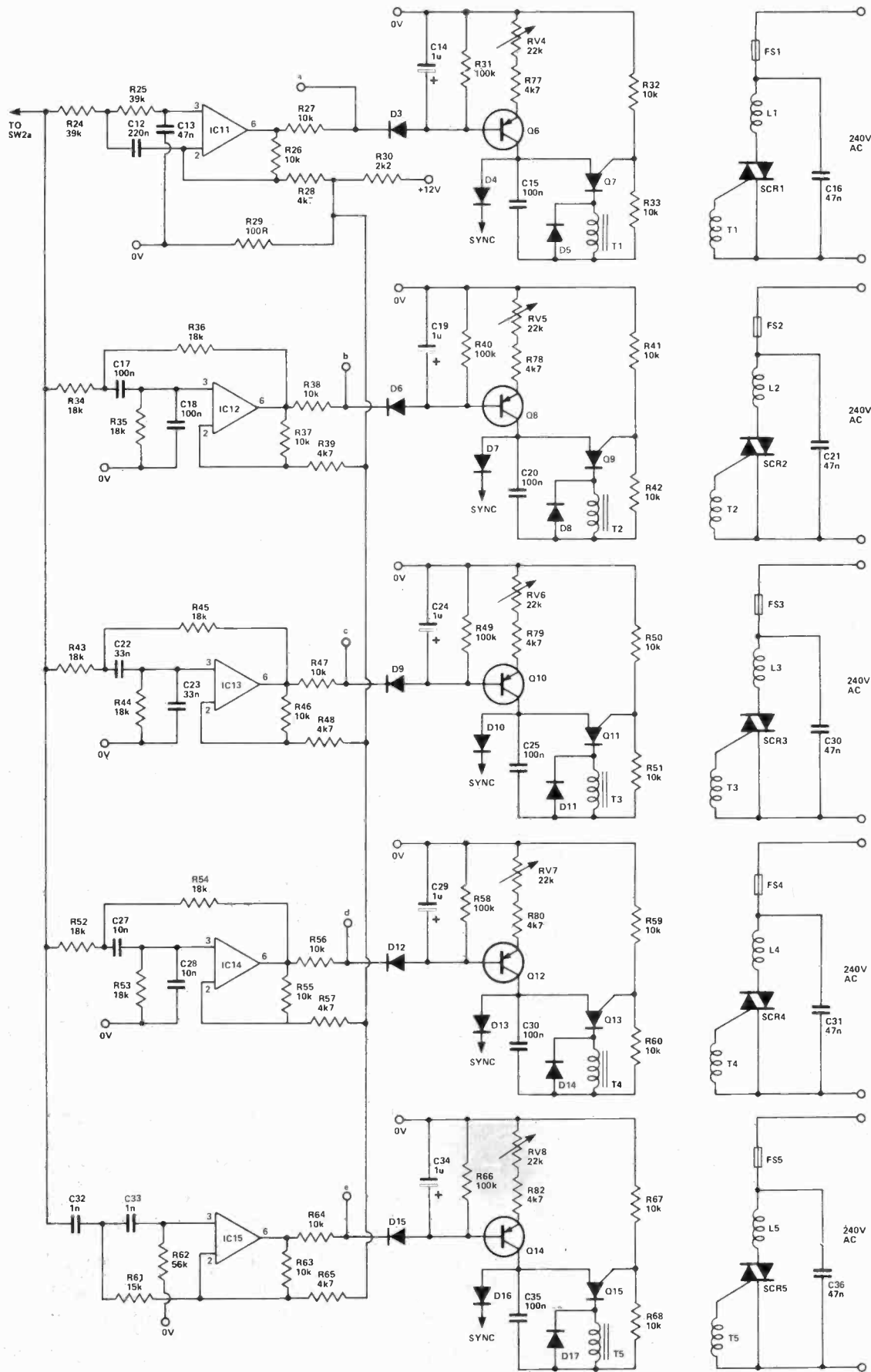

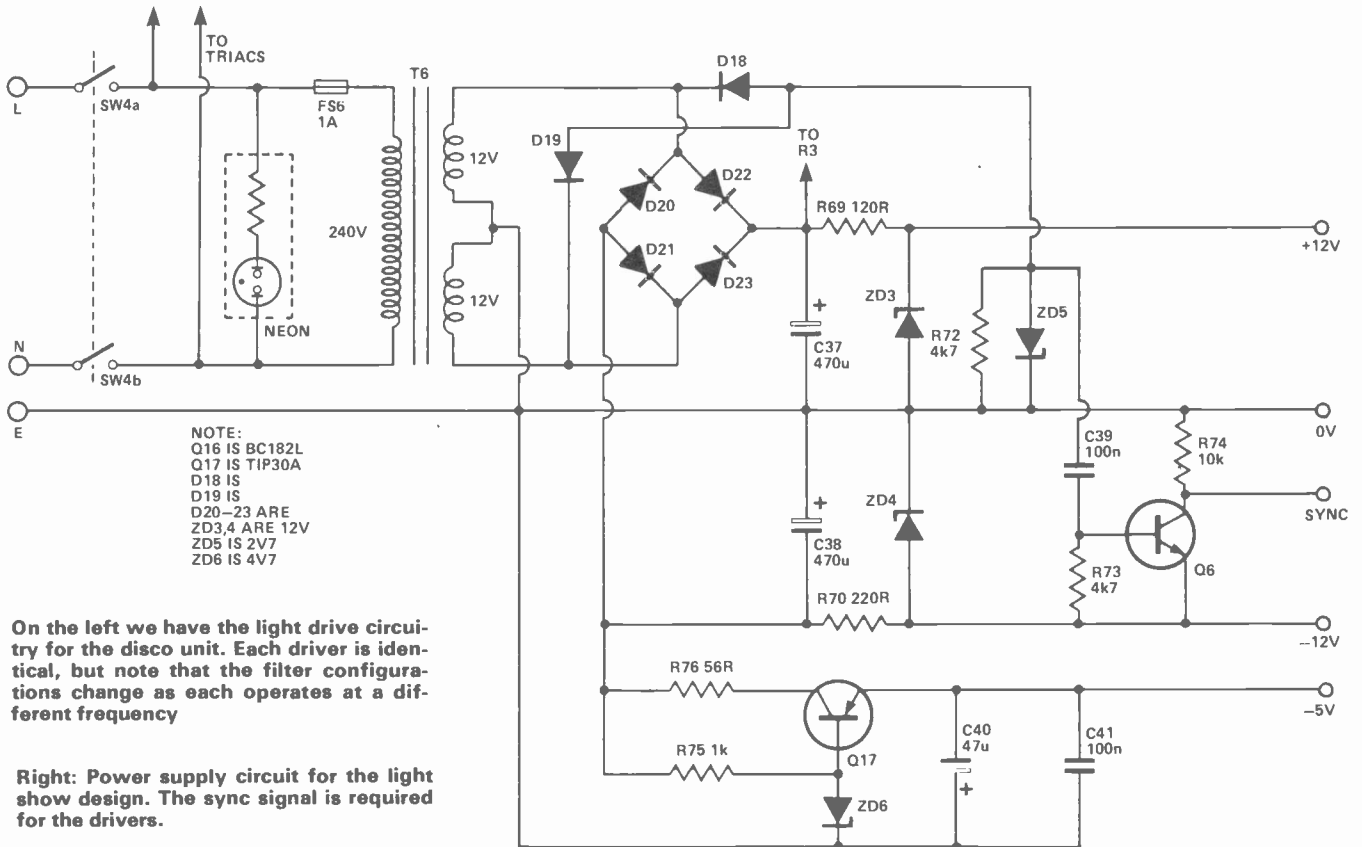

HOW IT WORKS

Filter section:

The output of IC2 is taken to 5 active filters based round IC11-15. IC11 is the low pass filter, IC15 the high pass and IC12-14 band-pass. The cut-off and centre frequencies are 40 Hz, 120 Hz, 400 Hz, 1200 Hz, 4 KHz. R29,30 are used to bias the filters to give a small negative offset voltage at the outputs which are applied to the triac driving stages. This means that the series diodes are biased on and control of the lamp can start even when the signal level is very low thereby improving the smoothness of the modulation.

Triac drivers:

All 5 stages are identical so only the low frequency one will be considered. Signal from IC11 charges C4 via R27,D3. The voltage

across C4 causes Q6 to conduct and charge C15. When this reaches about 6 volts PUT Q7 suddenly conducts discharging C15 through transformer T1 generating a pulse to turn on the triac SCR1. At the zero voltage point of the 50 Hz mains cycle a sync. pulse is generated which discharges C15 via D4. For a given charging, current C15 will always reach 6 V at the same point in the mains cycle. We therefore have phase control which is dependent on the audio signal level and the setting of RV4. Phase control is used in preference to burst control because of its superiority in producing smooth flicker free modulation of the lamps. Filtering of the switching surges is performed, most effec-


tively by C16,L1 and the RF interference generated is substantially less than that from a domestic light dimmer.

Syncing:

To generate the 100 Hz sync pulses the 12 V. AC output of T6 is full wave rectified by D18, 19 and without smoothing is applied to ZD5 across which is produced a spiky waveform. This is then applied via C39 to Q16 which is sufficiently turned on by the spikes to sink the charge on C15,C20 etc.

Power supply:

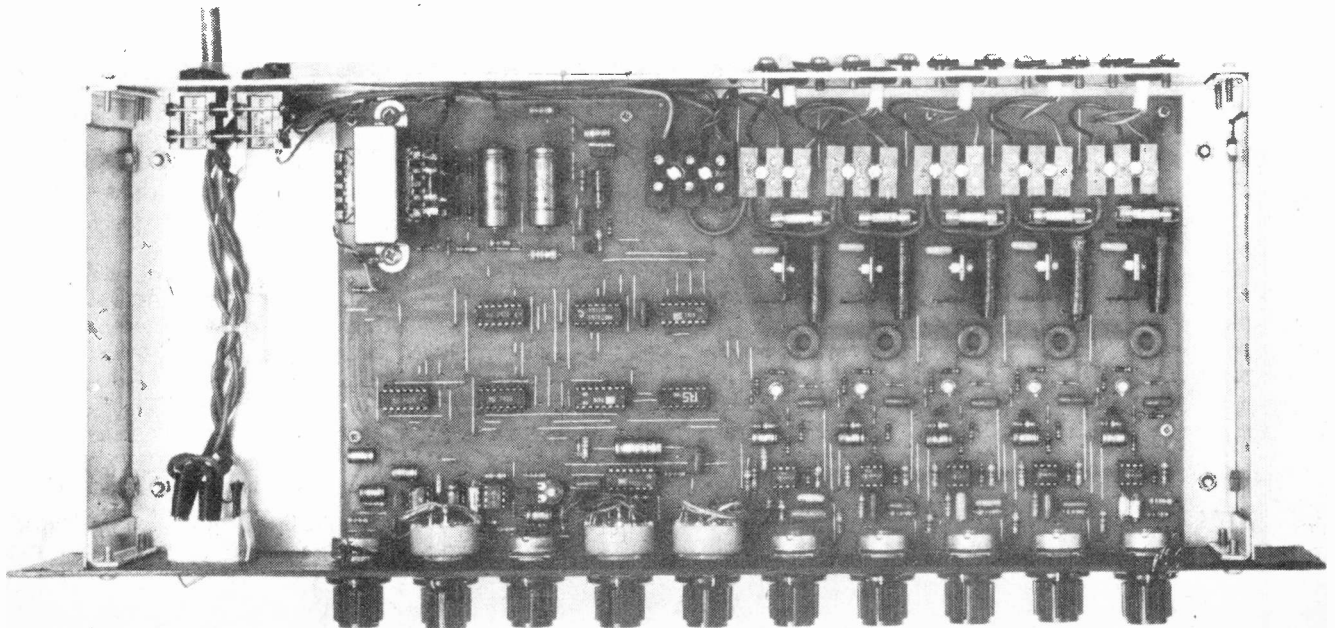Highly stable voltages are unnecessary and the 12 V lines for the op. amps are taken off simple zener regulators whilst the TTL-5 V line is regulated by a single series transistor Q17.



PARTS LIST

RESISTORS 1/4W 5% except where stated

R1, 17, 71, 74, 81	1k
R2, 11, 31, 40, 49, 58, 66	100k
R3, 14	470R
R4, 9	22k
R5, 15	6k8
R6, 10, 13, 19-23, 26, 27, 32, 33, 37, 38, 41, 42, 46, 47, 50, 51, 55, 56, 59, 60, 63, 64, 67, 68, 73	10k
R7	220k
R8	470k
R12	82k
R16	390R
R18, 30	2k2
R24, 25	39k
R28, 39, 48, 57, 65, 72, 76-80	4k7
R29	100R
R34-36, 43-45, 52-54	18k
R61	15k
R62	56k
R69	120R 1/2W
R70	220R 1/2W
R75	56R 1W

POTENTIOMETERS

RV1	10k log " "
RV2	10k lin PCB mounting
RV3	2k5 preset " "
RV4-8	22k lin " "

CAPACITORS

C1, 3, 6, 14, 19, 24, 29, 34	1u 63V electrolytic
C2	680p polystyrene or ceramic
C4	4n7 polystyrene
C5, 11, 40	47u 10V electrolytic
C7	22u 25V electrolytic
C8, 27, 28	10n polycarbonate
C9, 15, 17, 18, 20, 25, 30, 35, 39, 41	100n polycarbonate
C10	220u 4V electrolytic
C12	220n polycarbonate
C13	47n polycarbonate
C16, 21, 26, 31, 36	47n 400V polycarbonate
C22, 23	33n polycarbonate
C32, 33	1n polystyrene
C37, 38	470u 25V electrolytic

SEMICONDUCTORS

Q1, 2, 4 16
Q3, 5, 6, 8, 10, 12, 14
Q7, 9, 11, 13, 15
Q17
SCR1-5
IC1
IC2, 11-15
IC3
IC4
IC5
IC6-8
IC9
IC10
D1, 3-19
D2
D20-23
ZD1, 2, 6
ZD3, 4
ZD5

SWITCHES

SW1-3	4p 3w adjustable stop rotary illuminated mains switch DPDT 10 Amp
SW4	

TRANSFORMERS

T1-5	FX3008 with 10 turns 35g for both windings
T6	240V to 15V-0-15V at 200mA

INDUCTORS

L1-5	FX1089 with 40 turns 25g
------	--------------------------

FUSES

F1-5	2A fast
F6	1A anti surge

MISCELLANEOUS

Two 1/4" mono jack sockets, 5 cooling clips, 13A mains cable, cable clamps, five 3 terminal 5A connector blocks, 3 terminal 10A connector block, fibre glass ready drilled PCB, metalwork to suit ten knobs, grommets, spacers, nuts, bolts etc.

BC182L
BC212L
BRY39
TIP30A
8A Triac
MC3340p
741
74132
7490
7475
7420
7400
7405
IN4148 or IN4151
OA95
IN4002
4V7 zener
12V zener
2V7 zener

Use 3" lengths of coloured wire for these. The switches supplied in Powertrain kits are of the adjustable stop variety. The tag on the stop plate goes in the hole stamped 2 for two way switches and the hole stamped 3 for the 3 way switch.

Mains transformer T6 is bolted onto the board and the 15 V windings connected to the board by means of short wire links from the tags down to the holes directly beneath them.

Pulse transformer T1-5 you wind yourself. Wrap round the ferrite rings 10 turns of 35g wire for both the primary and secondary. It doesn't matter which you call the start or the finish of the windings as the circuit operates with them either way round. The wire supplied in the kits is self fluxing polyurethane covered and can be soldered directly to the board.

Wind coils L1-5 with about 35 turns of 25g wire. A smear of glue on the windings will help them stay in place before

fitting and reduce buzzing when in use. The triacs are kept cool by means of a finned tab bolted to each of them. The outputs to the lamps are taken from the board via connector blocks screwed to the board and linked to it with short lengths of 18g wire.

Testing and Setting Up


Plug in the unit between your amplifier and speakers, wire in the lamps securing the cables with the clamps on the rear panel, turn all controls anticlockwise, switch on and set auto level to where the LED only comes on occasionally. Switch SW2 to A and turn up the level controls and watch the lamps operate smoothly in time with the different frequency bands in the music. Switch SW2 to D, SW3 to S, SW1 to A, adjust the level controls for the lamps to be equally turned on by the strobing and set the one and only pre-set (RV3) for a strobe rate as fast as the lamps will follow.

ETI

BUYLINES

A complete kit of parts including metalwork is to be made available by Powertran Electronics. Address from the inside front cover. The PCB will be available only from them as it is their design. All components are available separately.

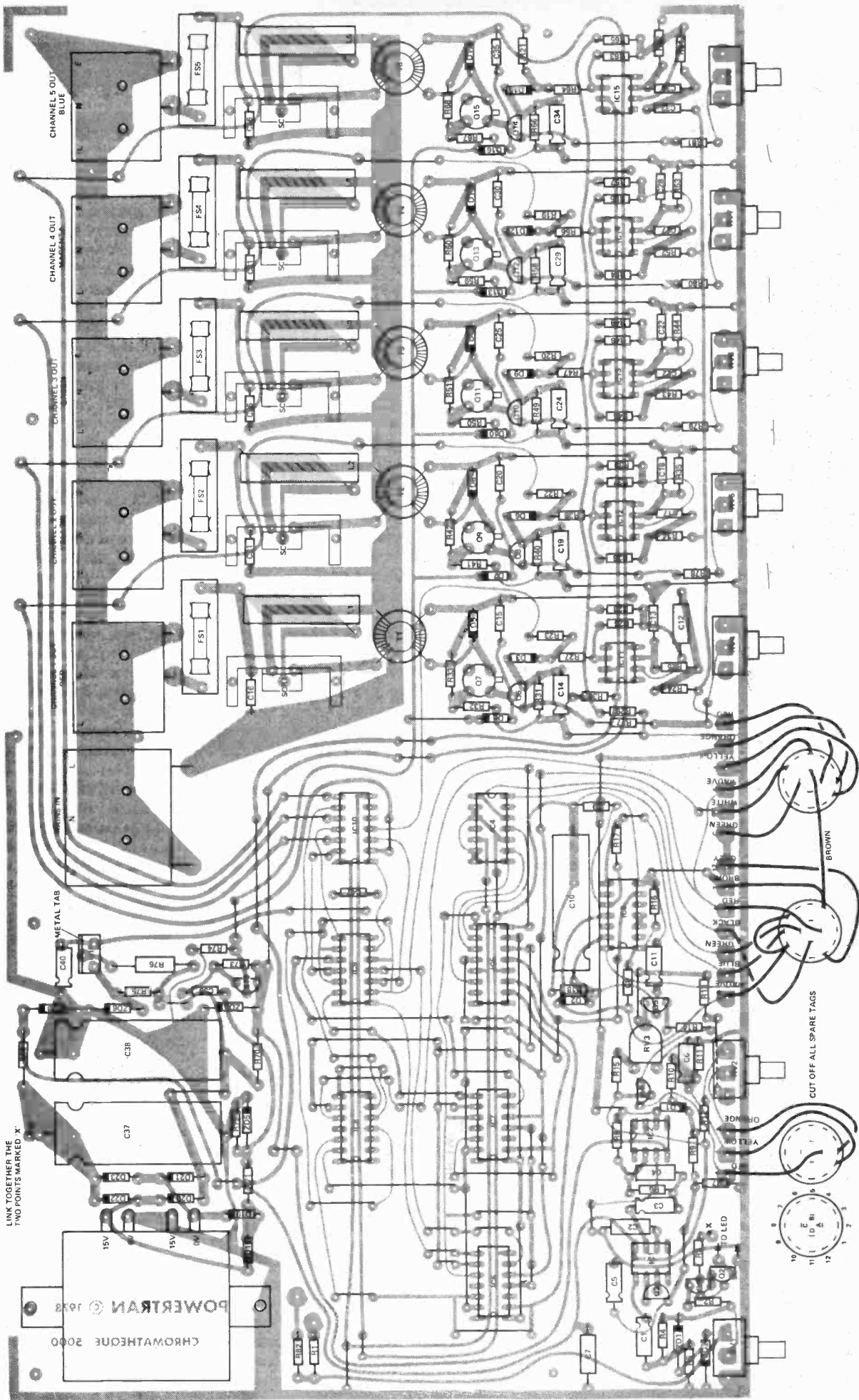Below: Component Overlay for the lightshow



MAINS OPERATED

ELECTRONIC DIGITAL ALARM CLOCK

IMMEDIATE DELIVERY

£8.95


INCL. V.A.T
POST PAID

THREE FOR £26.00
POST FREE

ETI RECOMMEND THIS MODEL

BARCLAY ACCESS

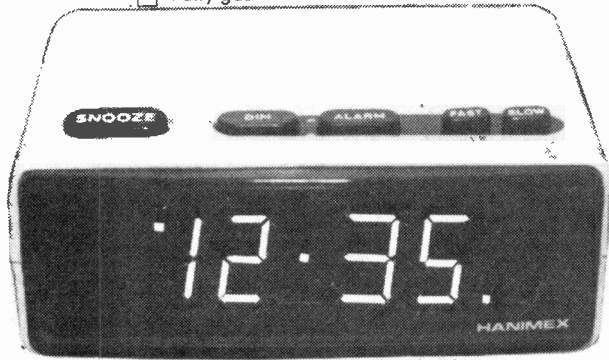- Hanimex HC-1100
- Large Bright LED display
- White case with red display on black background
- Adjustable dim / bright control
- Silent operation, all electronic
- Space age technology L.S.I. circuitry
- Alarm and 9 minute snooze repeater
- P.M. indicator
- Seconds Display
- Size 100mm x 130mm x 60mm high
- Fully guaranteed




HENRY'S
RADIO

HENRY'S RADIO
404 Edgware Rd. London W2
PHONE (01)723 1008

DORAM

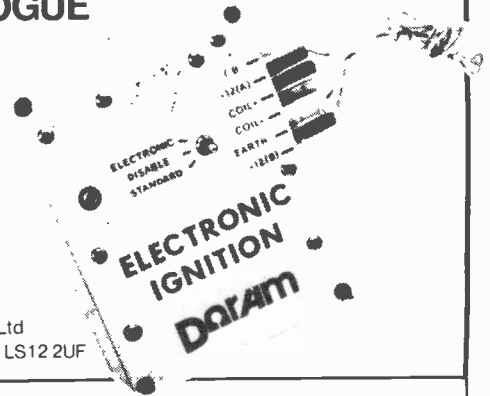SEE THE ELECTRONIC IGNITION MKII IN THE NEW HOBBIES CATALOGUE



Doram Electronics Ltd
PO Box TR8, Leeds LS12 2UF

Please send my FREE Hobbies Catalogue.

I enclose **25p** contribution to p. & p.

Name.....

Address.....


ET18

DORAM

Doram Electronics Ltd
PO Box TR8, Leeds LS12 2UF

Overseas customers (except for N. Ireland) - 60p including despatch by Air (or all-up post).

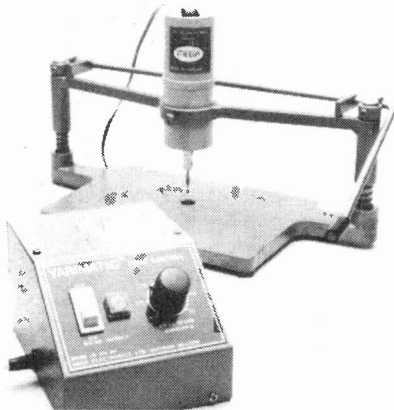All-in-one p.c. drill system - only £44.50.




- Fully controlled drill speed up to 15,000 r.p.m.
- Smooth torque pick-up with varying loads
- Precision collets for exact drill centering
- Accepts 1/8 in. and 3/32 in. turbo drill shanks
- 42W power consumption
- Drill stand takes 10 x 9 in. boards
- Complete with three tungsten carbide drills
- Works hand-in-hand with our photolab kit - still only £49.50. See us at Breadboard '78, Stand A7; or, enquiries, top speed, to



Mega Electronics Ltd.,
9 Radwinter Road,
Saffron Walden,
Essex CB11 3HU.
Tel: (0799) 21918.

vero

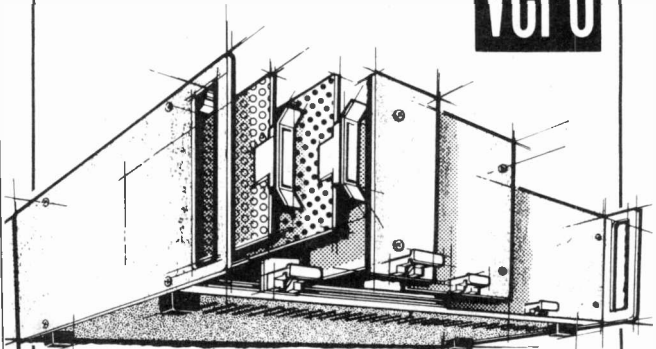


Our new 1978 catalogue lists a card frame system that's ideal for all your module projects - they used it in the ETI System 68 Computer. And we've got circuit boards, accessories, cases and boxes - everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

HELP!

ETI NEEDS YOU!

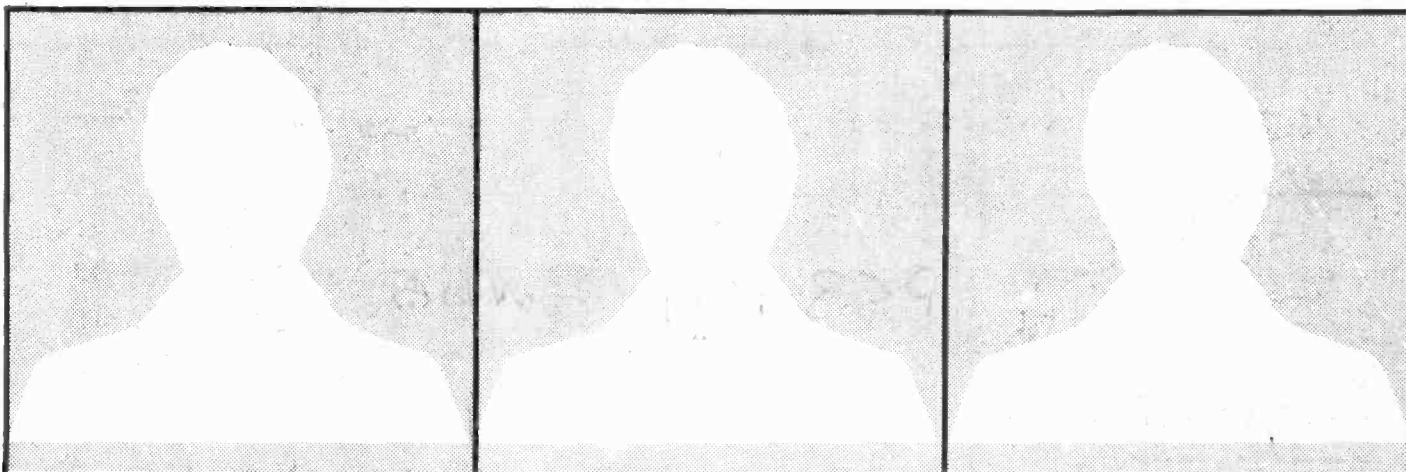Last month we advertised for someone to fill the position of Editorial Assistant, and we are still receiving applications for that. However our expansion plans now mean we need three additional recruits!



IF YOU have a genuine interest in electronics and project building and an above-average ability to express yourself in writing, you could be the person we're looking for. We are being serious.

We are looking for someone to join the editorial team and reckon that an enthusiastic reader is likely to be the type to join us. Not an uncritical reader — we want to continue to improve. The work will entail dealing with articles and news — licking them into shape — and making them better than anyone else's articles and news. The applicant will work on both ETI and our new sister publication Hobby Electronics. Readers employed in journalism at the moment will be considered but we are not primarily looking for someone with magazine experience.

We are flexible about age and experience but imagine that the person who gets the job will be between 21 and 28.

Salary will depend upon age and experience but will be in the range £3,700 to £4,100, possibly more for someone with exceptional qualifications.

Experience has told us that people who read ads like this think a) that it doesn't apply to them b) that their own knowledge is far too limited or c) that ads of this type are only put in because we have to fill half a page. None of these is true.

Editorial Assistant (Home Computing):— in order to complement and add to our existing staff skills we are looking for someone with a real knowledge of this ever-expanding field. Everyone here at ETI is fascinated by the field — PET nearly stopped the magazine dead — but we feel we need a person who has a broad overall knowledge of the systems around today and the principles behind them, in order to assist with the magazine generally and our 'Computing Today' supplement in particular.

Salary in the range £3,700-£4,100.
Age flexible.

Project Engineer:— the person who fills this position will be able to design and build up projects to the standard of finish ETI readers are used to seeing in their magazine. This calls for someone with a good knowledge of circuit design, and with the patience to carry the design through to a finished state. Existing staff are available to assist in all aspects of design work. The easiest part of the job will be writing up the project once it is completed. None of the present ETI staff were journalists previous to joining, and no-one has found the writing a difficult task.

One again we have no preconceived notions of age required, and salary will be negotiable upwards from £4,000.

**Apply in writing to:
Halvor Moorshead,
Editor,
Electronics Today International,
25-27 Oxford Street,
London W1R 1RF.**

Applications should reach us as soon as possible with C.V. Prospective applicants may telephone the Editor for further details but this must be followed by written application.

Marshall's

Come and get a great deal

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat.
Tel. orders on credit cards £10 min.
Trade and export enquiries welcome

A. Marshall (London) Ltd., Dept. ETI. Head Office mail order; Kingsgate House, Kingsgate Place, NW6 4TA, Tel. 01-624 0805. **Retail Sales London:** 40-42 Cricklewood Broadway, NW2 3ET, Tel. 01-452 0161/2. **Telex:** 21492. **London:** 325 Edgware Road, W2, Tel. 01-723 4242. **Glasgow:** 85 West Regent Street, G 2 2QD, Tel. 041-332 4133. **Bristol:** 1 Straits Parade, Fishponds Road, BS16 2LX, Tel. 0272 654201.

TRANSISTORS																													
2N696	0.39	2N2218	0.35	2N3393	0.17	2N4637	0.60	2N5192	0.80	2N6124	0.45	BC108A	0.16	BC1789	0.35	BC307	0.20	BD240A	0.49	BF160	0.33	BF79	0.30	ME4001	0.16	TIP30C	0.70		
2N697	0.31	2N2218A	0.38	2N3394	0.19	2N4638	0.22	2N5193	0.75	2N6125	0.47	BC108B	0.16	BC1790	0.25	BC308	0.23	BD240C	0.59	BF161	0.65	BF80	0.30	ME4002	0.16	TIP31A	0.54		
2N698	0.49	2N2219	0.30	2N3396	0.19	2N4640	0.22	2N5196	0.97	40362	0.55	BC109	0.16	BC1790C	0.25	BC213B	0.17	BC547A	0.13	BD241C	0.65	BF173	0.37	BF81	0.30	ME4003	0.16	TIP31C	0.72
2N699	0.58	2N2219A	0.39	2N3397	0.19	2N4641	0.19	2N5245	0.37	40363	1.45	BC109B	0.17	BC1792	0.26	BC213C	0.17	BC547B	0.13	BD242A	0.55	BF177	0.27	BF83	0.34	ME4102	0.11	TIP32C	0.82
2N706	0.30	2N2220	0.39	2N3438	0.85	2N4662	0.20	2N5246	0.38	40408	0.82	BC109C	0.18	BC182	0.12	BC214	0.17	BC548	0.13	BD242C	0.62	BF178	0.27	BF84	0.30	ME4103	0.11	TIP41A	0.76
2N706A	0.30	2N2221	0.25	2N3440	0.75	2N4664	1.35	2N5247	0.44	40409	0.82	BC140	0.30	BC182A	0.12	BC214A	0.17	BC549	0.14	BD243A	0.65	BF179	0.33	BF85	0.38	ME4104	0.11	TIP41B	0.76
2N708	0.30	2N221A	0.25	2N3441	0.92	2N4674	2.65	2N5248	0.44	40410	0.82	BC141	0.32	BC182B	0.13	BC214C	0.17	BC549A	0.14	BD243C	0.65	BF180	0.37	BF86	0.30	ME4105	0.22	TIP42A	0.86
2N710	0.30	2N2222	0.25	2N3442	1.45	2N4711	0.27	2N5294	0.44	40411	3.10	BC147	0.13	BC182C	0.15	BC214D	0.18	BC551	0.14	BD244C	0.67	BF182	0.37	BF88	0.30	ME4106	0.22	TIP42B	1.08
2N718A	0.54	2N2224	0.25	2N3636	0.17	2N4722	0.27	2N5295	0.44	40594	0.87	BC147B	0.13	BC182D	0.15	BC214E	0.18	BC552	0.14	BD244D	0.65	BF183	0.44	BF90	0.30	ME4107	0.16	TIP42C	0.86
2N720A	0.85	2N2225	0.27	2N3638A	0.17	2N4723	0.19	2N5296	0.44	40595	0.98	BC148	0.13	BC182E	0.15	BC214F	0.18	BC553	0.14	BD244E	0.69	BF183A	0.44	BF91	0.30	ME4108	0.16	TIP42D	0.70
2N722	0.45	2N2269A	0.27	2N3702	0.14	2N4724	0.19	2N5298	0.44	40673	0.80	BC148B	0.13	BC183	0.12	BC237B	0.15	BC559	0.15	BD245C	0.85	BF184	0.41	BF92	0.27	ME4109	0.62	TIP34	1.05
2N727	0.50	2N2646	0.80	2N3703	0.14	2N4725	0.19	2N5447	0.16	40669	1.30	BC148C	0.13	BC183A	0.12	BC238A	0.13	BC770	0.21	BD246A	0.72	BF185	0.37	BF93	0.27	ME4110	0.86	TIP42	0.50
2N914	0.38	2N2647	1.55	2N3704	0.14	2N4726	0.19	2N5448	0.16	40670	0.48	BC149	0.15	BC183B	0.13	BC238B	0.13	BC771	0.26	BD246C	0.44	BF186	0.16	BF94	0.16	ME4111	0.27	TIP42E	0.47
2N916	0.33	2N2903	1.60	2N3705	0.14	2N4728	0.38	2N5449	0.20	40671	0.48	BC149C	0.15	BC183C	0.13	BC238C	0.16	BD115	0.88	BD44	0.44	BF195	0.16	BF91	1.35	ME4120	0.70	TIP90	0.22
2N917	0.38	2N2904	0.31	2N3707	0.14	2N4728	0.22	2N5458	0.35	40672	0.48	BC151A	0.15	BC183D	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N918	0.45	2N2904A	0.31	2N3707	0.14	2N4728	0.22	2N5458	0.35	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N923	0.37	2N2905	0.31	2N3708	0.12	2N4728	0.22	2N5459	0.32	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N929A	0.37	2N2905A	0.31	2N3709	0.12	2N4729	0.22	2N5460	0.35	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N930	0.37	2N2906	0.25	2N3721	2.16	2N4731	2.20	2N5484	0.37	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N930A	0.95	2N2906A	0.25	2N3722	2.20	2N4732	2.65	2N5485	0.40	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N1711	0.30	2N3207	0.25	2N3727	0.36	2N4919	0.70	2N5490	0.64	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N1889	0.30	2N3207A	0.25	2N3819	0.25	2N4919	0.70	2N5490	0.64	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N1890	0.30	2N3223	0.17	2N3820	0.39	2N4920	0.83	2N5492	0.64	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N1893	0.30	2N2924	0.17	2N3820	0.39	2N4920	0.83	2N5492	0.64	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2102	0.50	2N2925	0.19	2N3900	0.28	2N4922	0.60	2N5496	0.67	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2192	0.58	2N2926	0.17	2N3901	0.30	2N4923	0.75	2N5627	0.64	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2193	0.50	2N3251	0.25	2N3902	0.20	2N4924	1.15	2N6107	0.95	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2193A	0.52	2N3254	0.72	2N3904	0.18	2N4926	0.30	2N6108	0.55	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2194	0.42	2N3055	0.75	2N3905	0.18	2N4927	0.30	2N6109	0.55	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2194A	0.45	2N3930	0.50	2N3906	0.18	2N4928	0.30	2N6111	0.49	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2194B	0.40	2N3931	0.40	2N4031	0.55	2N4929	0.30	2N6121	0.41	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2195A	0.40	2N3931A	0.45	2N4032	0.65	2N4930	0.65	2N6122	0.44	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33
2N2217	0.55	2N4032	0.72	2N4033	0.72	2N4931	0.75	2N6123	0.48	40673	0.48	BC151B	0.15	BC183E	0.13	BC239E	0.17	BD131	0.55	BD45	0.46	BF197	0.18	BF93B	0.55	ME4121	0.51	TIP92	0.33

EXPAND AND GROW WITH KIM 2

AMERICA'S FASTEST SELLING MOST POPULAR 6502 BASED SYSTEM - EASILY EXPANDED INTO A PERSONAL HOME COMPUTER

The basic KIM 2 includes Hex keyboard and display, audio cassette interface, VDU interface. Superb documentation, 2K monitor software in ROM. Powerful instruction set. The beauty of this system is the ease of extension and versatility, with all the possible future requirements catered for. Up and running in minutes. Any future benefits from Commodore's PET computer will be software compatible with their KIM system and in fact your KIM system has the design flexibility to suit any requirements.

KIM IS EXPANDABLE - Expand as you learn up to 65K.

KIM 1 - Basic board with above features assembled £160.92

KIM 3 - BK static RAM card plugs into motherboard £193.00

KIM 4 - Motherboard (takes 6 x KIM 3) power supply £96.00

KIM 6 - Prototype board for user designation £42.00

The Commodore PET and KIM are both based on the 6502 micro **VDU INTERFACE** - VDU card - takes control £150.00

Fully assembled TTY Card - ASC II keyboard in - converts TV set to cheap computer terminal via serial socket. Also standard RS232C connector for micro, computer or modem - 16 lines x 64 characters.

SEND SAE NOW FULL DETAILS.

CMOS

4000	0.22	4022B	1.05	4050R	0.85	4077	0.70
4001	0.22	4028A	1.00	4051B	0.85	4078	0.27
4002	0.22	4028B	0.22	4052B	0.86	4078B	0.24
4006	1.25	4028C	0.76	4053B	0.98	4082	0.27
4007	0.22	4028D	0.22	4054	1.48	4085	0.89
4008	0.99	4028E	0.55	4055	1.65	4086	0.89
4009	0.99	4028F	0.92	4056	1.85	4088	2.10
4009	0.99	4028G	1.10	4059	6.00	4093B	1.00
4010	0.58	4031B	2.25	4063	1.15	4094	2.30
4011	0.22	4035B	1.30	4066B	1.75	4096	1.30
4012	0.22	4037	1.20	4067	4.85	4097	4.65
4013	0.52	4040	0.85	4068	0.27	4098	1.00
4014	1.00	4042B	0.96	4069B	0.24	4510R	1.20
4015	1.05	4043	1.05	4070R	0.85	4511	1.75
4016	0.52	4044	1.00	4071B	0.24	4516	2.10
4017B	1.05	4045	1.76	4072	0.27	4518B	1.20
4018	1.05	4046B	1.50	4073B	0.24		
4019	0.52	4047B	0.96	4075B	0.64		
4020B	1.15	4049	0.96	4076B	0.99		

MANY MORE TYPES STOCKED - SEND FOR OUR CATALOGUE

LEDS + OPTO SIEMENS

Diaplays 7 seg	Red	Gr	Yell	
Com anode or cath	Small 3mm	.18	.19	.19
	Large 5mm	.20	.20	.20
	8mm HT	£1.50	Extra bright	.

INDEX 78

INTRODUCTION

IT WAS APRIL last year when we last provided an index of our own efforts. That one went right back to our first issue in April 1972. This month's brings us once more up to date. In future these listings will appear each December issue (there's long-term planning!).

Producing a definitive index is not simply a matter of reading from the contents pages and rearranging to nice neat alphabetical order. There will be some items which can be classified in several ways, and which are usually

entered more than once as a result. All articles here are included just once for simplicity.

All articles, except Tech-Tips and the news features, are included in the index. Projects are simply listed consecutively, whilst the features are divided into categories for ease of reference.

Computing Today is a separate entity from ETI, and articles appearing within it are not eligible for inclusion in our index.

Projects

A			G		
ALARM ALARM	JUL 77	p.29	GAS MONITOR	APR 78	p.32
ASC II KEYBOARD	APR 77	p.25	GRAPHIC EQUALISER	SEP 77	p.27
AUDIO AMPLIFIER (200W)	APR 78	p.43	GSR MONITOR	JUL 77	p.11
AUTOCHORD			H		
Pt 1	NOV 78	p.57	HAMMER THROW GAME	JAN 78	p.29
Pt 2	DEC 78	p.80	HELPING HAND	MAY 78	p.16
B			I		
BASS ENHANCER	JUN 77	p.53	IB METAL LOCATOR	FEB 78	p.32
BELL EXTENDER	OCT 78	p.65	INJECTOR-TRACER	MAY 77	p.37
BENCH SUPPLY	APR 77	p.47	L		
BURGLAR ALARM SYSTEM	APR 77	p.57	LED PENDANT	NOV 77	p.41
BURGLAR ALARM (CMOS)	JAN 78	p.16	LCD MULTIMETER	AUG 78	p.23
C			LCD PANEL METER	MAR 78	p.26
CAR ALARM	DEC 78	p.16	LIGHT DIMMER	MAR 78	p.55
CLOCK (LED)	NOV 77	p.23	LIGHT SHOW	DEC 78	p.44
CLOCK (Fluorescent)	DEC 77	p.19	LOUDHAILER	SEP 77	p.56
COMPUTER (Triton)	NOV 78	p.16	LOUDSPEAKERS (ER II)	MAY 77	p.31
COMPANDER	NOV 77	p.11	M		
CONTINUITY TESTER	SEP 77	p.38	MASTERMIND	JUN 77	p.41
CROSSHATCH GENERATOR	SEP 78	p.33	METRONOME (Accentuated)	FEB 78	p.17
CURVE TRACER	DEC 78	p.73	METRONOME	MAY 77	p.39
D			MICROAMP	JUL 77	p.30
DRUNKEN SAILOR PUZZLE	JAN 78	p.46	MOISTURE INDICATOR (Soil)	AUG 77	p.19
E			O		
EGG TIMER	AUG 77	p.26	OSCILLATOR (Sweep)	AUG 77	p.10
ELECTRONIC BONGOS	AUG 77	p.24	OSCILLATOR (LCD)	NOV 78	p.71
ELECTRONIC IGNITION	MAY 78	p.41	OSCILLATOR (Wide range)	JUN 78	p.90
F			P		
FM/AM RADIO	JUN 78	p.79	PHASER (CCD)	MAY 78	p.57
FM TUNER (Digital)	SEP 78	p.21	PHASER		
FREEZER ALARM	DEC 77	p.41	PLANT WATERER (Auto)	AUG 78	p.61
FREQUENCY METER (Digital)	JUN 77	p.19			
FREQUENCY SHIFTER	MAR 78	p.40			
FUZZ BOX	APR 77	p.48			

PORCH LIGHT	FEB 78	p.28
POWER BULGE	OCT 78	p.41
POWER METER (R.F.)	OCT 78	p.30
POWER SUPPLY	AUG 78	p.75
PROXIMITY SWITCH	OCT 78	p.75

R

RACE TRACK GAME	JAN 78	p.36
RAIN ALARM	APR 78	p.62
REV MONITOR	DEC 77	p.37

S

SHUTTER TIMER	FEB 78	p.57
SKEET GAME	NOV 77	p.34
STAC TIMER	SEP 78	p.71
STAR TREK RADIO	MAY 78	p.62
STARS & DOTS	JUN 78	p.17
STEREO SIMULATOR	SEP 77	p.16
SOUND GENERATOR	OCT 78	p.17
SPECTRUM ANALYSER	JUN 78	p.27
SPIRIT LEVEL	OCT 77	p.28
SYNTHESISER (Transcendent)	JUL 78	p.38
	and AUG 78	p.45

SYSTEM 68

PSU	MAY 77	p.55
VDU	JUN 77	p.33
	and JUL 77	p.54
BUS STRUCTURE	AUG 77	p.45
CPU CARD	SEP 77	p.22
	and OCT 77	p.63
TTY	NOV 77	p.45
INTERFACING	DEC 77	p.59
CUTS CARD	JAN 78	p.61
	and FEB 78	p.45
ETIBUG	MAR 78	p.59

T

TACHOMETER	JUL 77	p.32
TANK BATTLE	MAY 78	p.50
TEMPERATURE METER	JUL 78	p.21
THERMOMETER (Digital)	OCT 77	p.20
tone CONTROL (3-channel)	OCT 77	p.34
TORCH FINDER	JUL 78	p.31
TV CHESS		
PT 1	OCT 78	p.48
PT 2	NOV 78	p.44

U

UFO DETECTOR	JUL 78	p.63
ULTRASONIC SWITCH	FEB 78	p.62

V

VOLTMETER (True RMS)	MAR 78	p.13
----------------------	--------	------

W

WATCHDOG	OCT 77	p.10
WHEEL OF FORTUNE	SEP 78	p.61
WHITE LINE FOLLOWER	APR 78	p.23
WINE TEMP METER	DEC 78	p.31

FEATURES

Audio

AM STEREO	OCT 77	p.25
CLASS G AMPS	DEC 77	p.34
ELECTRETS IN AUDIO	DEC 77	p.24
NOISE REDUCTION	NOV 77	p.16
SWITCH IN LINE	NOV 78	p.51
PICKUP PRINCIPLES	AUG 77	p.56
PIRATE RECORDINGS	OCT 78	p.45
ROCK SOUND	SEP 78	p.15
VALVE SOUND	JUN 77	p.57
VALVE SOUND ON THE REBOUND	JUL 77	p.34
VOCODERS	AUG 77	p.34
(See also AUDIOPHILE)		

Circuit design

ACTIVE FILTER		
Pt 1	JUL 77	p.23
Pt 2	AUG 77	p.36
Pt 3	SEP 77	p.52
AUDIO AMPS	JUN 78	p.21

DIGITAL ELECTRONICS BY EXPERIMENT

Pt 1	OCT 77	p.49
Pt 2	NOV 77	p.58
Pt 3	DEC 77	p.76
Pt 4	JAN 78	p.67
Pt 5	FEB 78	p.78
Pt 6	MAR 78	p.66
Pt 7	APR 78	p.38
Pt 8	MAY 78	p.74
Pt 9	JUN 78	p.98

GAIN CONTROL

Pt 1	OCT 78	p.22
Pt 2	NOV 78	p.65

HOW IT WORKS — TELEVISION RECEIVERS HI-EST FI AMPS

Pt 1	AUG 78	p.15
Pt 2	SEP 78	p.39

OSCILLATORS OP AMPS

Pt 1	FEB 78	p.22
Pt 2	MAR 78	p.49
Pt 3	APR 78	p.29
Pt 4	MAY 78	p.69

OP AMP (741) SUPPLEMENT

	APR 77	p.10
--	-------------------	------

Components

BATTERIES EXPLAINED	DEC 77	p.65
CASINGS SURVEY	APR 78	p.67
CCD-	SEP 77	p.10
COMPONENTS		

Pt 9	APR 77	p.53
Pt 10	MAY 77	p.60
Pt 11	JUL 77	p.59
Pt 12	AUG 77	p.52
Pt 13	SEP 77	p.47

INSIDE VCT	MAR 78	p.19
LCD-DISPLAYS	JUN 77	p.13
MOSFETS	JUN 78	p.41
TRANSFORMERS	SEP 77	p.18
V-FETS FOR EVERYONE		
Pt 1	JUL 78	p.25
Pt 2	AUG 78	p.67

Computing

GAMES	JUN 78	p.73
GLOSSARY	JUN 78	p.76
HIGH LEVEL LANGUAGES	JUN 78	p.57
MEMORIES	JUN 78	p.63
ONE ARMED MPU	OCT 77	p.15
PERIPHERALS	JUN 78	p.69

SOFTWARE GAMES	JAN 78	p.56
SOFTWARE TECHNIQUES	JUL 77	p.18
SYSTEM SURVEY	JUN 78	p.53
SYSTEM 68 UPDATE	JUN 78	p.95
(See also 'MICROFILE')		

General

DANGERS OF LIGHTNING	FEB 78	p.50
----------------------	--------	------

ELECTRONICS—IT'S EASY!		
Pt 38	APR 77	p.65
Pt 39	MAY 77	p.64
Pt 40	JUN 77	p.64
Pt 41	JUL 77	p.64
Pt 42	AUG 77	p.64
Pt 43	SEP 77	p.62

ELECTRONICS IN PHOTOGRAPHY	AUG 77	p.28
ELECTRONICS IN SURVEYING	JAN 78	p.24
ELECTRONICS 2000	MAY 77	p.25
ELECTRONICS ON TAP	FEB 78	p.38
ELECTRONICS IN MODEL		
RAILWAYS	DEC 78	p.36
ELECTRONICS IN MOTORING	AUG 78	p.33
ELECTRONIC NEWS GATHERING	DEC 77	p.14

IONOSPHERE	DEC 78	p.61
PL EXPLAINED	MAY 77	p.18

KENNEDY SPACE CENTRE	JUN 77	p.25
LASER LIGHTSHOWS	SEP 77	p.34
QUARKS	JUN 78	p.34
RACE FOR THE BOMB	JUL 78	p.69
ROCKWELL SPACE SHUTTLE	SEP 78	p.50
ROBOTS	MAY 78	p.22

SOLDERING IRON SURVEY	OCT 77	p.52
ULTRASONICS IN MEDICINE	NOV 78	p.79
VENUS PROBE	NOV 78	p.37

Reviews

AIWA AD 6800	JAN 78	p.72
BATTLE OF THE KEYS	NOV 77	p.28
CAMBRIDGE PROGRAMABLE	JUL 77	p.15
CRIMSON CPR1	NOV 78	p.85
COMMODORE PET	APR 78	p.13

GARRARD MRM 101	OCT 78	p.70
GOLDRING G900SE-2	AUG 78	p.79
HITACHI SR 903	DEC 77	p.34
HITACHI HMA 750	JUN 78	p.41
HP 67 CALCULATOR	JUN 77	p.30
KOSS ESP10	MAR 78	p.63

MK 14 KIT	SEP 78	p.27
SCRUMPI 3 KIT	OCT 78	p.35
SOUND GUARD	JAN 78	p.71
T159 CALCULATOR	JUN 78	p.85
TRS 80 COMPUTER	AUG 78	p.39
VIDEOCRAFT TELETXT	AUG 77	p.18
WIRELESS SHOW	JAN 78	p.50

Data Sheet


HD0165 ENCODER	APR 77	p.40
ICL 8038 VCO	JUL 77	p.50
ICM 7205 STOPWATCH	JUL 77	p.52
L911 COMPARATOR	JUN 78	p.97
LM1812 TRANSCEIVER	MAY 77	p.48
LM 1830 FLUID DETECTOR	AUG 77	p.62
LM 2907/17 CONVERTORS	AUG 77	p.60
LM 3919 TEMP SENSORS	SEP 77	p.59

MC14490 BOUNCE ELIMINATOR	JUN 77	p.49
MC14433 A-D CONVERTOR	SEP 77	p.60
MK50362N CLOCK	APR 77	p.38
MM57160 TIMER	SEP 78	p.65
MM5837 NOISE SOURCE	FEB 78	p.71
NE570/1 COMPANDER	OCT 77	p.59
NSL 4944 LED	NOV 77	p.55

3-TERMINAL REGULATORS	JUN 77	p.50
TDA 1023 DELAY LINE	MAY 77	p.49
TGS 812 GAS SENSOR	APR 78	p.57
TL080 OP AMPS	JAN 78	p.53
2102 RAM	JUL 78	p.51
2112 RAM	JUL 78	p.52
2107 RAM	JUL 78	p.54
5204 EPROM	JUL 78	p.56
7208 COUNTER/DECODER	AUG 78	p.57

Understanding Digital Electronics


New teach-yourself courses

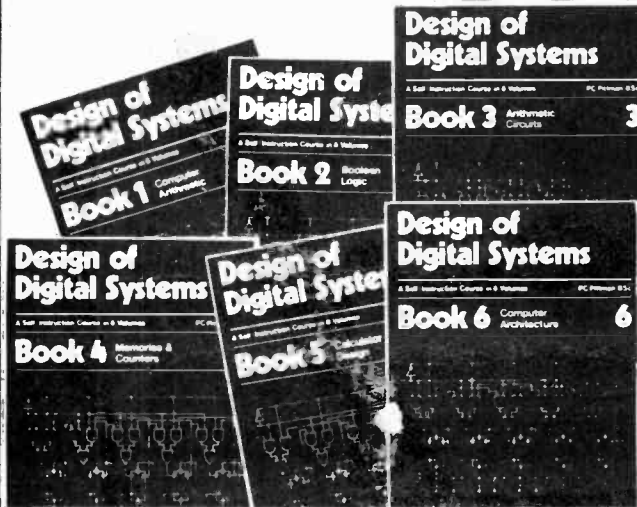

Design of digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes — each A4 size — are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates: NOT, exclusive OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.
- Book 6** Central processing unit (CPU); memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

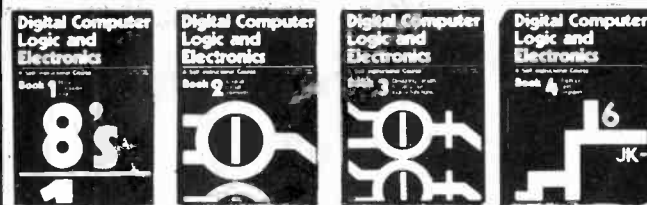

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes — each A4 size — and serves as an introduction to the subject of digital electronics. Everyone can learn from it — designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, UNIT 12, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND
 TELEPHONE: ST. IVES (0480) 67446
 PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES
 REGD. IN ENGLAND No. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and petrol consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of **Design of Digital Systems** cost only: **£8.10** + 90p. post & packing
 And the four volumes of **Digital Computer Logic and Electronics** cost only: **£4.60**
 But if you buy both courses, the total cost is only: **£12.00** - + £1 post & packing

Price includes surface mail anywhere in the world — Airmail extra.

Flow Charts & Algorithms

HELP YOU PRESENT

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

THE ALGORITHM WRITER'S GUIDE explains how to define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size A5, 130 pages. This book is a MUST for those with things to say.

£2.95 + 45p post & packing by surface mail anywhere in the world. Airmail extra.

GUARANTEE

If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, Unit 12, Rivermill Site, Freepost, St. Ives, Huntingdon, Cambs. PE17 4BR England.

Please send me the following books

- sets Digital Computer Logic & Electronics @ £5.50, p & p included
- sets Design of Digital Systems @ £9.00, p. & p. included
- Combined sets @ £13.00, p & p included
- The Algorithm Writer's guide @ £3.40, p & p included

Name

Address

I enclose a cheque/PO payable to Cambridge Learning Enterprises for £

Please charge my Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number


Signature

Telephone orders from credit card holders accepted on 0480-67446 (ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank.

ETI 12

ETI MARKET PLACE

Digital Alarm

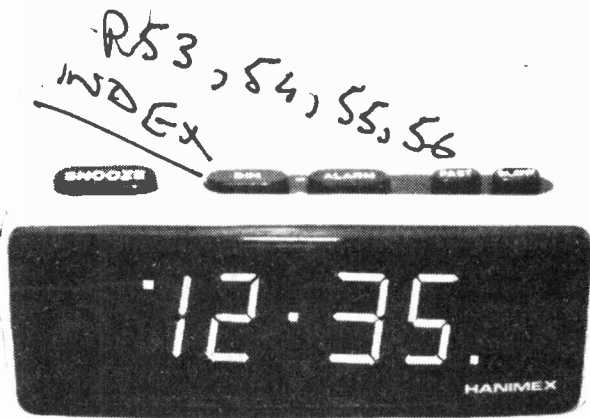

Size: 105mm wide 115mm deep x 55 mm high.

THIS IS THE THIRD digital alarm clock that we are offering (we regret the earlier versions are no longer available). We have sold thousands and thousands of these and our buying power enables us to offer a first rate branded product at a really excellent price.

The Hanimex HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking' switch is provided under the clock. A 9-minute 'snooze' switch is located at the top.

£8.95

(Inclusive of VAT and Postage)

An example of this clock can be seen and examined in our reception at our Oxford Street offices.

LCD Watch



New low price!

The enormous numbers involved in ETI offers has enabled us to arrange a real bargain — a full spec LCD watch with adjustable metal bracelet for under half the going rate.

This watch gives continuous display of hours and minutes press the button once and you'll get the date (American style). After a couple of seconds the display automatically reverts to time but if you press again you'll get a continuous seconds display.

Press another button and you get a back light, enabling you to see the display in the dark. Setting, or resetting is simplicity itself and a 'hold' facility allows you to set the watch spot on. The accuracy is magnificent, as with all the current range of digital watches and battery life is well in excess of a year.

£8.95

(Inclusive of VAT and Postage)

An example of this watch can be seen and examined in our reception at our Oxford Street offices.

DIGITAL ALARM

To:
Hanimex Alarm Offer
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please find enclosed my cheque/PO for £8.95 (payable to ETI Magazine) for a Hanimex Digital Alarm Clock.

Name

Address

.....

.....

Please allow 14 days for delivery

LCD WATCH

To:
LCD Watch Offer
ETI Magazine
25-27 Oxford Street
London W1R 1RF

Please find enclosed my cheque/PO for £8.95 (made payable to ETI Magazine) for my LCD Digital Watch.

Name

Address

.....

.....

Please allow 14 days for delivery

ELECTROVALUE Buying Guide

Section 1

If you have bought before from Electrovalue, you will know just how large and varied our stocks are. Those who have yet to know are finding our series of monthly ads to give up-to-date information and prices on the most important items we carry. BY DETACHING AND SAVING THESE PAGES, YOU WILL BUILD UP A VALUABLE AND COMPREHENSIVE MONEY-SAVING CATALOGUE. All goods brand new and to published specifications.

Transistors/Zeners

IN914	5p
IN9142	7p
IN916	6p
IN4007	8p
IN4148	5p
IN5402	16p
IN5407	20p
IS920	10p
IS940	5p
2N697	38p
2N706	22p
2N930	21p
2N1132	24p
2N1302	48p
2N1303	48p
2N1304	52p
2N1305	52p
2N1306	56p
2N1307	56p
2N1308	60p
2N1309	60p
2N1599—SCR	88p
2N1613	23p
2N1711	22p
2N1893	35p
2N2218	24p
2N2218A	24p
2N2219	24p
2N2219A	24p
2N2270	75p
2N2369A	22p
2N2484	26p
2N2646	69p
2N2904	22p
2N2904A	22p
2N2905	22p
2N2905A	22p
2N2924*	25p
2N2925*	25p
2N2926*	25p
2N3053	26p
2N3054	73p
2N3055	70p
2N3391A*	41p
2N3405*	64p
2N3663*	52p
2N3702*	11p
2N3703*	10p
2N3704*	11p
2N3705*	10p
2N3706*	9p
2N3707*	12p
2N3708*	8p
2N3709*	12p
2N3710*	12p
2N3711*	12p
2N3794*	21p
2N3819*	28p
2N3820*	56p
2N3823E*	24p
2N3904*	24p
2N3906*	28p
2N4036	68p
2N4058*	12p
2N4059*	12p
2N4060*	12p
2N4061*	12p
2N4062*	12p
2N4124*	22p
2N4126*	27p
2N4286*	18p
2N4289*	23p
2N4291*	24p
2N4292*	21p
2N4303*	30p
2N4410*	39p
2N4443	£1.14
2N4444	£1.50
2N4906	£1.00
2N4915	£1.00
2N4991	80p
2N5062*	45p
2N5163*—SCR	24p

2N5192	85p
2N5195	99p
2N5457*	39p
2N5458*	39p
2N5459*	39p
6F40	£1.46
16F40	£1.65
40HF10	£1.64
40HF40	£2.28
40250	95p
40361	38p
40362	35p
40406	40p
40408	40p
40412	56p
40594	£1.18
40595	£1.50
40602	75p
40636	£1.80
40673	86p
A9903	44p
AA113	9p
AA116	9p
AA117	9p
AA118	10p
AA119	9p
AC126	30p
AC127	48p
AC128	28p
AC151R	53p
AC153	40p
AC153K	40p
AC176	58p
AC176K	40p
AC187K	70p
AC188K	70p
ACY17	92p
ACY18	91p
ACY19	99p
ACY20	70p
ACY21	85p
ACY22	50p
ACY39	£1.70
ACY40	45p
ACY41	54p
ADY136	£2.09
AD142*	90p
AD149	80p
AD161	96p
AD162	96p
AF114	27p
AF115	30p
AF116	30p
AF117	34p
AF124	25p
AF125	32p
AF126	25p
AF127	36p
AF139	32p
AF200U	15p
AF239	89p
AF279	30p
AFY12	£2.04
AFY16	£2.69
AFY18D	£5.74
AFY18E	£6.15
AFY42	£2.91
AL102	£1.60
ASY26	£1.39
ASY27	£1.39
ASY28	£1.39
ASY29	£1.39
AU111	£2.25
AUY21	£7.31
AUY22	£10.95
BO126—SCR	30p
BO140	35p
BO226	35p
BO240	40p
BO246	96p
BO680	10p
B1906	38p
B1912	38p

BA102	28p
BA127D	5p
BA133F	9p
BA138	20p
BA145	20p
BA156	14p
BA379	25p
8AX13	5p
8B103B	37p
8B103G	37p
8B104G*	53p
8B105B	28p
8B109G*	37p
BC107A	14p
BC107B	14p
BC108A	14p
BC108B	14p
BC108C	14p
BC109B	14p
BC109C	14p
BC121W	20p
BC122Y	61p
BC125*	20p
BC126*	20p
BC140	43p
BC147A*	21p
BC147B*	21p
BC148A*	21p
BC148B*	21p
BC148C*	21p
BC148C*	21p
BC149C*	21p
BC154*	16p
BC157A*	21p
BC157B*	21p
BC158B*	21p
BC159B*	21p
BC160	49p
BC167A*	8p
BC167B*	12p
BC168A*	8p
BC168B*	12p
BC168C*	8p
BC169C*	8p
BC177A	18p
BC177B	20p
BC178A	16p
BC178B	17p
BC179B	20p
BC182L*	12p
BC182*	12p
BC183L*	12p
BC183*	12p
BC184L*	12p
BC184*	12p
BC202Y	75p
BC212L*	12p
BC212*	12p
BC213L*	12p
BC213*	12p
BC214L*	12p
BC214*	12p
BC238B*	8p
BC238C*	8p
BC239C*	12p
BC257A*	8p
BC257B*	8p
BC258A*	8p
BC258B*	8p
BC259B*	8p
BC267	16p
BC268C	17p
BC269C	18p
BC300	26p
BC301	24p
BC303	30p
BC327*	16p
BC328*	12p
BC337*	14p
BC338*	12p
BC447	29p
BCY31A	96p

BCY58	15p
BCY59	16p
BCY70	18p
BCY71	18p
BCY72	18p
BCY78	25p
BD130	50p
BD131	62p
BD132	77p
BD135*	38p
BD136*	42p
BD139*	41p
BD140*	46p
BDX18N	£1.10
BDY12	90p
BDY20	50p
BF115	38p
BF167	30p
BF173	34p
BF177	24p
BF178	24p
BF194*	18p
BF195*	17p
BF244B	30p
BF254*	30p
BF255*	14p
BF457*	36p
BF458*	37p
BF459*	40p
BFR39*	24p
BFR40*	24p
BFR41*	24p
BFR79*	24p
BRF80*	24p
BRF81*	24p
BFT66	£1.83
BFX29	24p
BFX84	24p
BFX85	24p
BFX87	24p
BFX88	24p
BFY50	24p
BFY51	24p
BFY52	24p
BFY90	£1.05
BRB1WA	80p
BR92QA	£1.36
BRY39	60p
BSX20	22p
BSX46	45p
BSX63	£3.89
BT106	£1.47
BT107	£1.60
BU105	£2.50
BU208	£3.90
BUX28	£4.20
BY164	90p
BY238	8p
BYX38-300	65p
BYX38-300R	65p
C106D1	45p
C0326—SCR	£4.40N
C0340	£5.14N
C407*	17p
C1406	90p
C1412	90p
CS2925	20p
E99A40—Triac	£7.87
E2506	£1.48
E2512	£1.74
MJ481	£1.48
MJ491	£1.63
MJ2955	78p
MJE340	78p
MJE2955	72p
MJE3055	68p
MKY7C38E	70p
MPF102*	44p
MPS6531*	24p
MPS6534*	25p
NAS206 S 5—SCR	81p

NAS0164W3—Triac	58p
NAS0654X5	80p
NAS0654W5	£1.04
NAS1001X5	60p
NAS1004W5	18p
NAS1004X5	£1.60
NKT211	25p
NKT212	25p
NKT213	25p
NKT274	25p
NKT275	25p
NKT405	DIS
OA47	12p
OA90	6p
OA91	6p
OA95	8p
OA202	10p
OC28	£1.02
OC29	£1.07
OC35	£1.07
OC36	£1.02
OC45	£1.15
OC71	70p
OC72	70p
OC75	DIS
OC81	80p
OC83	80p
OC84	80p

PM7A2	£2.68
PN70*	6p
PN72*	6p
PN109*	6p
PN1613*	6p
PN2904*	6p
S2CN1	15p
SIOM1	12p
T2700D	£1.55
T2800D—Triac	£1.04
TAG3-400—SCR	£1.00
TAG302-400—Triac	85p
TAG302-600—Triac	£1.05

TIP31A	45p
TIP32A	45p
TIP41A	60p
TIP41C	64p
TIP42A	60p
TIP42C	64p
TIS43*	35p
W02	30p
ZTX107*	12p
ZTX108*	11p
ZTX109*	12p
ZTX300*	12p
ZTX301*	16p
ZTX302*	14p
ZTX303*	18p
ZTX304*	21p
ZTX330*	19p
ZTX331*	19p
ZTX500*	12p

ZTX500*	15p
ZTX502*	17p
ZTX503*	19p
ZTX504*	22p
ZTX530*	12p
ZTX530*	20p

HEAT SINKS	
Type	Orilled
2P1	53p
2YT03	1xT03 54p
2YT066	1xT066 57p
2.75R	— £2.80
5.5R	— £3.95
5F	T05 clip 10p
5F2	T05 clip 10p
6W1	— £1.75
6W4	2xT03 £1.95
100MA	— 88p
100NC	2xT03 £1.14
17C2	2xAD161 20p
18F	T018 clip 10p
18F2	T018 clip 10p
224F	T01 clip 10p
244F	O01 clip 10p
266F	O03 clip 10p
A1032	T01 clip 6p
A1053	2xT01 clip 8p
A1058	1xT03 22p
T0921	T092 clip 7p
T0922	2xT092 clip 9p
TV2	T066 24p
TV3	T03 25p
TV4	80131 21p
TV5	T0220 21p

ZENER DIODES	
400mW 2.7—3.3V	9p
1.3W 3.3—200V	15p
1.5W 3.3—75V	55p
(1.5W are metal cased)	
20W 7.5V—75V	£1.25 each

MOTOROLA
Micro processor Evaluation Kit (for M. 680 Microcomputer)
£175.87 + VAT (net)

MEET US
AT
BREADBOARD
'78
STAND B8

WE ARE NOW NATIONAL
DISTRIBUTORS FOR
NASCOM I
MICROCOMPUTER KITS

for delivery from
stock, net from

+ V.A.T.

£197.50

Quantity discounts

Trade Enquiries invited

All communications, orders, etc., to Dept ET1.12

● GOODS SENT POST FREE U.K. WITH C.W.O. orders over £5 list value. If under, add 27p handling charge.

● ATTRACTIVE DISCOUNTS on C.W.O. mail orders—5% where list value is over £10; 10% where list value is over £25.

● TOP QUALITY MERCHANDISE—ALL GUARANTEED.

● V.A.T.—Add 8% to value of order. For items marked *, add 12½%.

● For ACCESS or BARCLAYCARD orders, just phone or write your number.

● No discounts allowable on prices marked NET or N.

● TAKE GOOD CARE OF THIS PAGE AND REMEMBER TO LOOK OUT FOR NEXT MONTH'S TO ADD TO IT

● OUR COMPUTER-AIDED SERVICE TAKES GOOD CARE OF YOUR ORDER NO MATTER HOW LARGE OR SMALL.

● Comprehensive price list free on request.

MEET US AT BREADBOARD 78 STAND B.8

ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN,
EGHAM, SURREY TW20 0HB

Telephone Egham 3603 Telex 264475

Northern Branch - 680, BURNAGE LANE,
BURNAGE, MANCHESTER M19 1NA(061)432 4945

electronics today

international

What to look for in the January issue: On sale Dec 1st

CLICK! ELIMINATOR

Fed up with low quality records? Had a hard day and dropped your favourite LP? Kiddies used Bach for target practice?

We can help — do not despair.

Next month we present a design to remove the clicks and scratches from records. The system works in a novel manner, and the system can be built at a fraction of the cost of commercial units.




DIGITAL TACHO

Compact, easy to build, 10 rev resolution, fast response due to PLL technique and a range to 9999 rpm. With all that going for it how can you afford to miss it? Suitable for standard, CDI, and transistor assisted ignition systems.

LOG/EXP CONVERTER

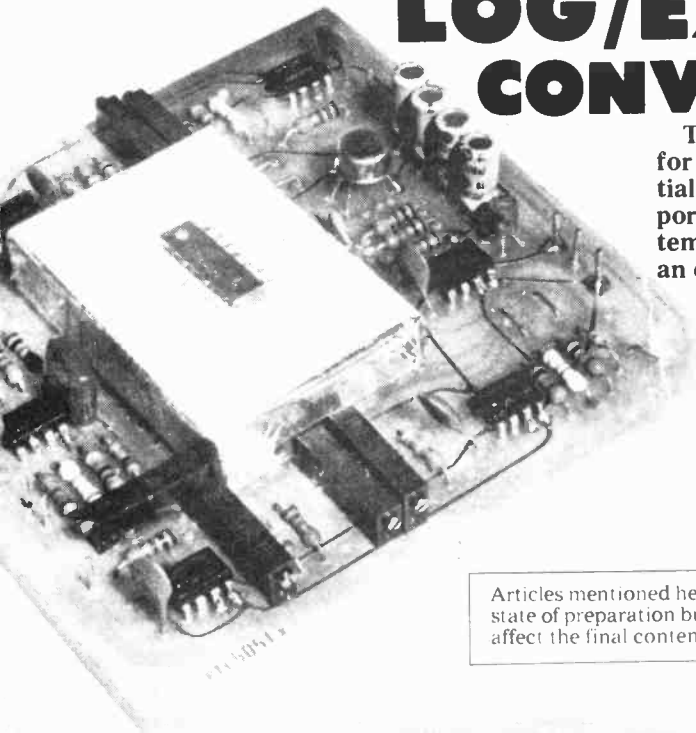This design can be set up for either log or exponential conversion, and incorporates a neat heater for temperature stability. Has an eight octave range.



Articles mentioned here are in an advanced state of preparation but circumstances may affect the final contents.

LOUDSPEAKERS PRINCIPLES



An article to explain what goes on behind the grilles on those large wooden boxes dominating the living room. All the major types will be covered, moving coil electrostatic piezo-electric etc, as well as explanations of 'loading' the units to do their job better.

computing today no 3

NEWBEAR'S BEARGAGS are an economical way of adding extra power to any small system. Next month we take a look at a typical bag — the petitevid VDU II kit.



BASIC II


Tandy's level two BASIC upgrade for TRS-80 machines is now available in this country — what extra power does this conversion provide?

COMPUTERS IN BUSINESS. A look at how one small businessman uses a microcomputer at work.

The Sinclair PDM35.

A personal digital multimeter for only £29.95

(+8% VAT)

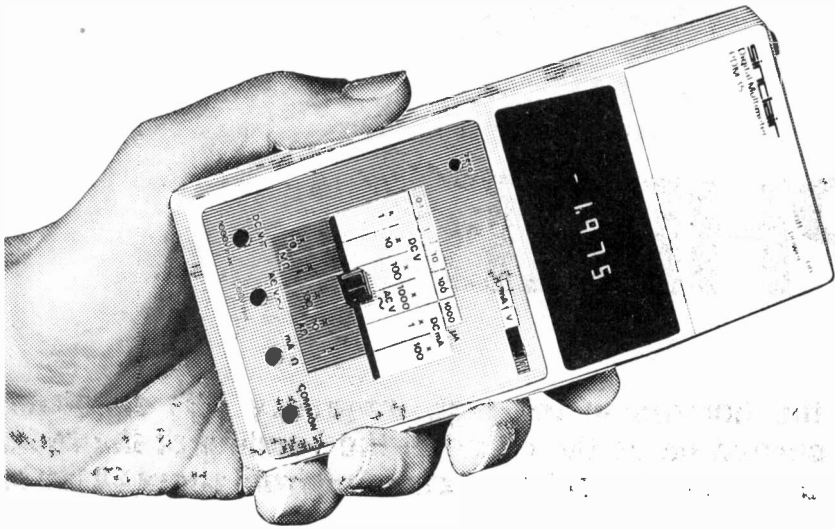

Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light 'pocket-size' case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field; while its angled display and optional AC power facility make it just as useful on the bench.

What you get with a PDM35

3½ digit resolution.

Sharp, bright, easily read LED display, reading to ±1.999.

Automatic polarity selection.

Resolution of 1 mV and 0.1 nA (0.0001 μA).

Direct reading of semiconductor forward voltages at 5 different currents.

Resistance measured up to 20 MΩ.

1% of reading accuracy.

Operation from replaceable battery or AC adaptor.

Industry standard 10 MΩ input impedance.

Compare it with an analogue meter!

The PDM35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 MΩ is 50 times higher than a 20 kΩ/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

Technical specification

DC Volts (4 ranges)

Range: 1 mV to 1000 V.

Accuracy of reading: 1.0% ± 1 count.

Note: 10 MΩ input impedance.

AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading: 1.0% ± 2 counts.

DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading: 1.0% ± 1 count.

Note: Max. resolution 0.1 nA.

Resistance (5 ranges)

Range: 1 Ω to 20 MΩ.

Accuracy of reading: 1.5% ± 1 count.

Also provides 5 junction-test ranges.

Dimensions: 6 in x 3 in x 1½ in.

Weight: 6½ oz.

Power supply: 9 V battery or Sinclair AC adaptor.

Sockets: Standard 4 mm for resilient plugs.

Options: AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts – from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ, England. Regd No: 699483.

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.

Please send me _____ (qty) PDM 35(s)

@ £32.35 (incl. VAT) each.....£..... Name.....

_____ (qty) De-Luxe carrying cases

@ £3.24 (incl. VAT) each.....£..... Address.....

_____ (qty) AC adaptor(s) for 240V

power @ £3.24 (incl. VAT) each.....£.....

Post and packing (please add).....£0.65

I enclose cheque/PO made payable


to Sinclair Radionics Ltd for

(indicate total amount).....£.....

I understand that if I am not completely satisfied with my PDM 35, I may return it within ten days for full cash refund.



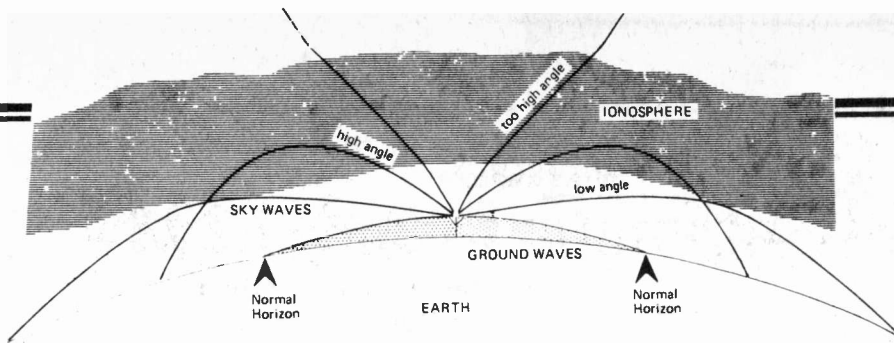sinclair
World leaders in fingertip electronics



IONOSPHERE

Radio communications beyond the horizon in the high frequency (HF) spectrum between 3 MHz and 30 MHz are carried on as the result of the bending of the radio waves in the ionosphere, that region of our atmosphere extending from about 60 km to about 1000 km above the earth.

THE IONOSPHERE CAN bend radio waves so that they return to earth from hundreds of kilometres to many thousands of kilometres distant.

Without the existence of the ionosphere, long distance radio communications, shortwave broadcasting, amateur radio 'DX' etc. would not be possible — and one G. Marconi would probably have died an unknown pauper!

The ionosphere enables shortwave radio stations such as Radio Peking, The Voice of America etc to broadcast programmes across the world. It enables radiotelephone communications to ships at sea and contact with international aircraft.

The Solar Prime Mover

The sun, which dominates almost every phase of our lives, influences all HF radio communications beyond the horizon. The sun generates the ionosphere; solar activity has a considerable influence on this area of our atmosphere and thus affects propagation of HF radio waves.

Ionisation of the upper atmosphere is brought about largely by ultraviolet radiation from the sun, along with solar X-ray radiation. This solar radiation strips electrons from the atoms of the rarified atmospheric gases existing in our upper atmosphere.

The result is not a single, thick region of 'band' ionisation, as you may suppose. The ionosphere separates into several readily defined regions having varying densities, located in layers at different heights.

Each layer has a relatively dense region, called the *peak* of the layer, the ionisation tapering off above and below this region. The peak is not necessarily located in the centre of the layer, nor does the ionisation always disappear completely between layers.

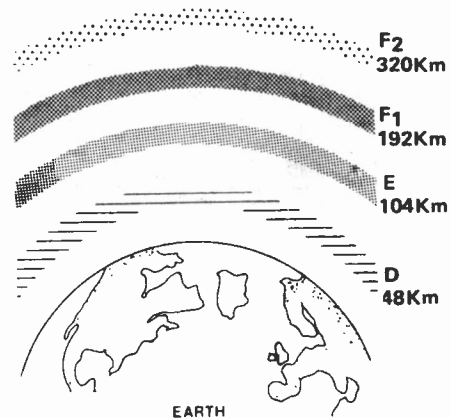


Figure 1. The ionosphere divides into readily defined regions which have been designated as illustrated here. The amount of ionisation in each layer varies diurnally (i.e.: throughout the day), seasonally (through the year) and through the 11-year sunspot cycle. Disturbances on the sun have a variety of effects on the ionosphere and thus on radio communications.

Spotting Good Propagation

The sun's UV radiation output varies over an approximately 11-year cycle, greatly influencing the behaviour of the ionosphere. For many years this cyclic behaviour of the sun has been monitored by means of sunspots - dark areas which appear on the face of the sun, and over the last two decades, by measurement of the *solar flux* (RF noise radiation) at 2800 MHz (10.7 cm wavelength).

Sunspots are enormous areas on the sun's surface which are cooler, and thus do not appear as bright as the surrounding area. Hence they look like 'spots' on the face of the sun. Their size can range from several hundred kilometres across to greater than 100,000 km. By comparison, the earth's diameter is only 13,000 km.

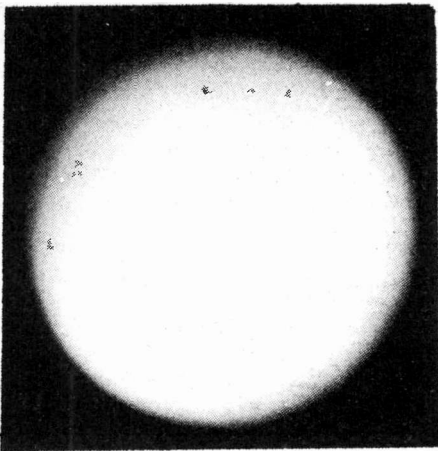


Figure 2. The sun as viewed in the visible light region showing several small spots, a relatively large spot and sunspot groups. (Photo courtesy of the Ionospheric Prediction Service.)

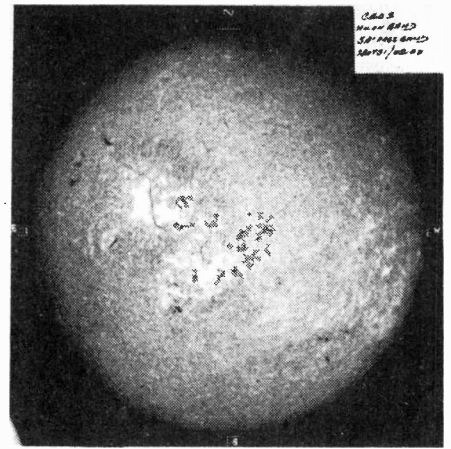


Figure 3. The sun as viewed in the red wavelength region emitted by hydrogen — H-alpha emission. Two large active regions can be seen along with associated 'filaments'. (Photo courtesy of the Ionospheric Prediction Service.)

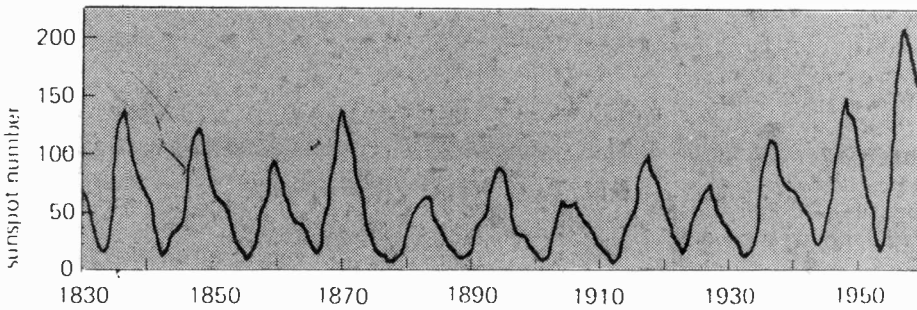
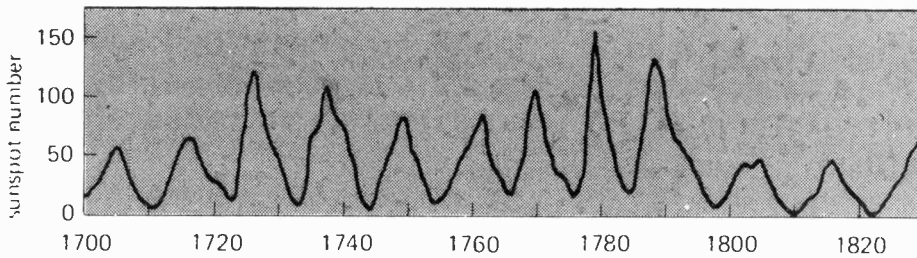


Figure 4. The 11-year solar cycle is clearly evident from this plot of the Sunspot Number from 1700 to 1960.

Rate of production of electrons

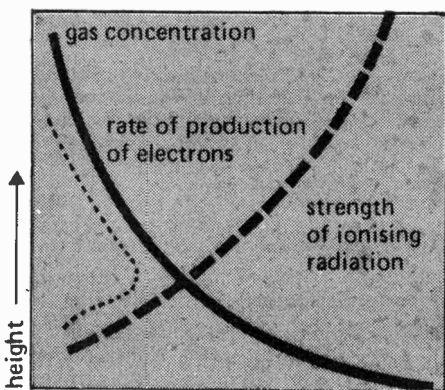


Fig. 5. How a layer of electrons is produced when ionising radiation comes from above the atmosphere. The gas concentration increases with decreasing height while the radiation strength decreases. Peak production of electrons occurs at the height where the curves cross.


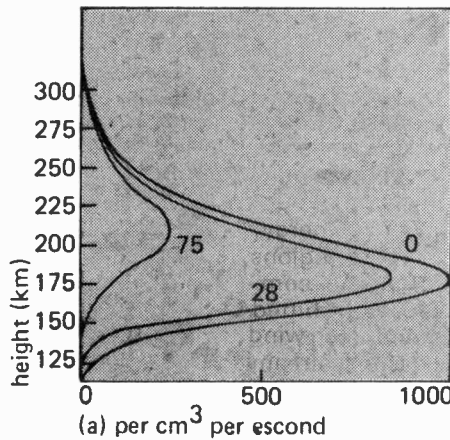


Fig 6. (a) Theoretical 'Chapman' layers showing how electron production is affected by the angle of the sun's rays — best when sun is overhead (0° zenith angle).

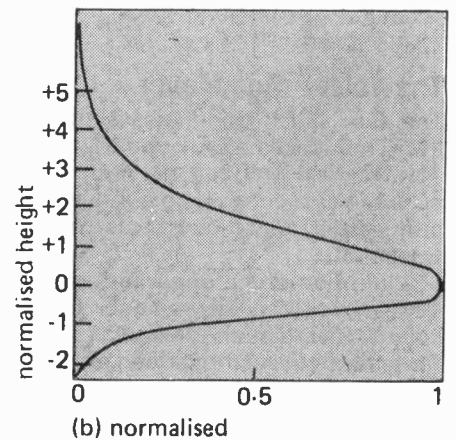

(b) If all curves are 'normalised' about peak height, regardless of the sun's zenith angle, they all have the same shape.

Records of systematic sunspot observations date back some 300 years. However, reasonably reliable data is only available since about 1850.

The sun is monitored continuously from a number of observatories around the world. Sunspot observations are statistically smoothed to provide a continuous record — this is termed the Zurich Sunspot Number, which is a statistical 'fudge factor' on which ionospheric propagation predictions are based. More of this later.

On the Spot

Sunspot Number does not mean 'numbers of sunspots'. It is a statistical term which allows comparison with past figures and provides an index of sunspot activity.

The sunspot number has a cyclical variation with a mean period of 11 years. Periods between sunspot peaks have been as short as nine years and as long as 13 years. The sunspot number between the peaks and minimums of the cycles also vary greatly. The sunspot cycles have been 'numbered', for the convenience of reference, back for 200 years. Cycle 18 peaked in 1947, cycle 19—the biggest on record — peaked in 1957 with a sunspot number in excess of 200. Cycle 20 peaked in 1969 reaching a sunspot number of about 120, which is about average intensity.

If you thought the DX wasn't anything spectacular in 1969-70, you should have been around in 1907 when the sunspot number barely reached 60 during the peak!

Sunspot cycle minimums don't always reach zero levels. Some minimums however have shown little or no activity for many months.

The sunspot cycle, while having an 11-year mean period as observed between peaks, has been identified in recent years as actually being a roughly 22-year period based on the magnetic field variations of the sun. Alternate sunspot cycles show a pole reversal in the solar magnetic field.

Solar Disturbances

On occasions, the surface of the sun is disturbed by sudden 'storms'. These disturbances are not normally visible but are readily detected when the sun is viewed at a particular red light wavelength, known as H-alpha, emitted by hydrogen.

These very intense, localised outbursts increase very rapidly to a peak taking a minute or less, and then the intensity of the H-alpha emission decreases to its normal value in about half an hour or so.

This phenomenon is called a *solar flare*, usually occurring near, or associated with, a sunspot.

Solar flares generate enormous amounts of energy, and increased solar X-ray radiation from these regions cause disturbances to the ionosphere and to communications. Electrons and protons are also emitted from solar flares, and these travel through solar wind towards the earth. The particles are emitted in a stream and are much more numerous and move at greater velocities than those particles contained in the normal solar wind.

Upon reaching the region near the earth these particles have a considerable influence on the earth's ionosphere and magnetic field, producing sudden and dramatic changes as well as precipitating other events — such as aurorae — which will be described in more detail later.

Apart from flares, disturbances not associated with sunspots also cause disturbances to the ionosphere and the earth's magnetic field. *Hot Spots* — which are of longer duration than flares, are emitting regions on the sun's surface that expel streams of particles which affect the ionosphere. These, and other areas on the sun's surface which emit persistent streams of particles, have longer durations than flares but the effects of the particles emitted is less severe.

Formation of the Ionosphere

As mentioned previously, the ionosphere is produced principally by ultraviolet radiation from the sun. The amount of ionisation produced is almost wholly dependent on the strength of the UV radiation and its wavelength. Different wavelengths of the radiation ionise different gases.

The process of ionisation absorbs energy from the UV wave, and as the radiation proceeds down through the atmosphere, it is almost completely absorbed in this way.

This process of creation of ions and free electrons in the ionosphere is offset by recombination which is continually taking place between the two to form neutral atoms once again.

In the lower atmosphere, the molecular density is so great that recombination occurs almost immediately after ionisation, the rate of recombination is very rapid. However, in the upper atmosphere, where the number of molecules is very much smaller, the chances of a free electron meeting up with an ion is very much less. Hence, recombination occurs at a much slower rate.

These two opposing mechanisms result in regions in the upper atmosphere where a large amount of ionisation is present, the amount being determined by the balancing forces between the rate of ion production and the recombination rate.

The gases of the upper atmosphere which the solar UV radiation meets first are very rarified, hence little ionisation results and little of the radiation energy is lost. As the radiation penetrates further, the molecular density of the gases increases and hence the ionisation increases.

Height Maximum

More and more energy is extracted from the ionising radiation as it penetrates further and at some stage the amount of ionisation which the radiation can produce begins to decrease. There is thus a certain height at which ionisation is maximised. The region around this height is known as an ionisation layer.

This is how the ionosphere comes to derive its name. It is the region of the upper atmosphere where appreciable ionisation can take place.

The lower limit of the ionosphere is about 50 km and it extends to beyond 1000 km.

Sydney Chapman, a British scientist, investigated the production of ionisation in the early 1930s and showed that the rate of production of ionisation would vary with height as shown in figure 6. The corresponding layers of electrons have been called Chapman layers.

The height of the 'peak' is determined by the concentration at particular heights of the atmospheric gas and by the ability of the gas to absorb the solar radiation. The less easily absorbed wavelengths of the radiation penetrate lower in the atmosphere before forming a layer of electrons. The *height* of the layer does *not*


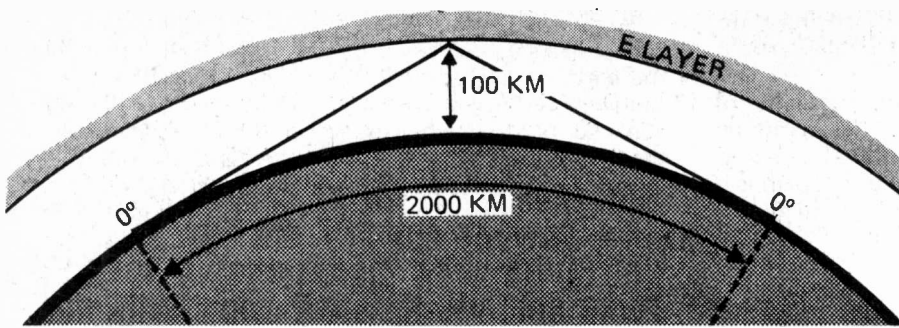


Fig. 7. Geometry of E-layer propagation. As the layer height is about 100 km, low angle radiation from a transmitter will reach distances of about 2000 km maximum.

Fig. 8. The transmitter (TX) radiating RF at several different angles illustrates how signals are propagated by the various layers. A wave radiated at a high angle will be deviated by one or both of the layers, but unless the layer is dense enough, will pass through (A). A ray at a lower angle (B) will skip a relatively short distance and may do so several times (R2-R4 etc). A low angle ray from TX will skip a maximum of 4000 km from the F2 layer (TX to R3) and subsequently further. The ionosonde measures the heights and critical penetration frequencies of the layers vertically.

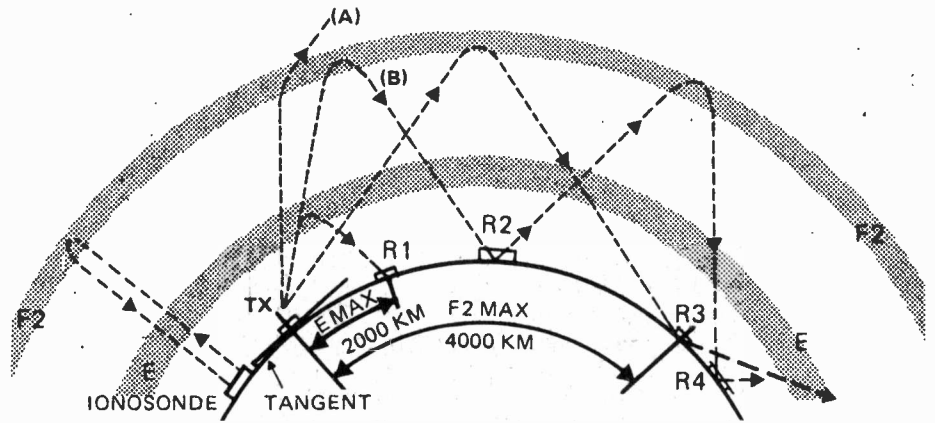

depend on the strength of the ionising radiation.

The production rate of electrons at the peak of the layer depends on the strength of the ionising radiation and on its direction of arrival. When the radiation is vertically incident on the layer, ionisation is maximum, less when it arrives at an angle.

When curves representing the production rate of electrons of all possible shapes are 'normalised' with respect to the layer peak, they all look the same.

The Three Regions

There are three main regions of the ionosphere. They are designated by the symbols 'D', 'E', and 'F.' The F-layer actually divides into two layers, F₁ and F₂, which I will go into shortly.

The structure of the ionosphere varies widely over the earth's surface as the strength of the sun's radiation will obviously vary with geographical latitude.

The D-layer

This is a region of low ionisation density which does not show the well-defined 'peak' of maximum ionisation density associated with the other layers.

The D-layer only appears during daylight hours and extends rather diffusely from about 50 km to about 90 km. The density of electrons in the D region is generally insufficient to cause appreciable bending of radio waves but they do suffer considerable attenuation in passing through this region.

Solar X-ray radiation with wavelengths less than about 20 Angstroms contributes to some of the ionisation in the D-layer. This radiation can ionise all the gases present at these heights in the atmosphere, but this alone does not account for the level of free electrons found in this region.

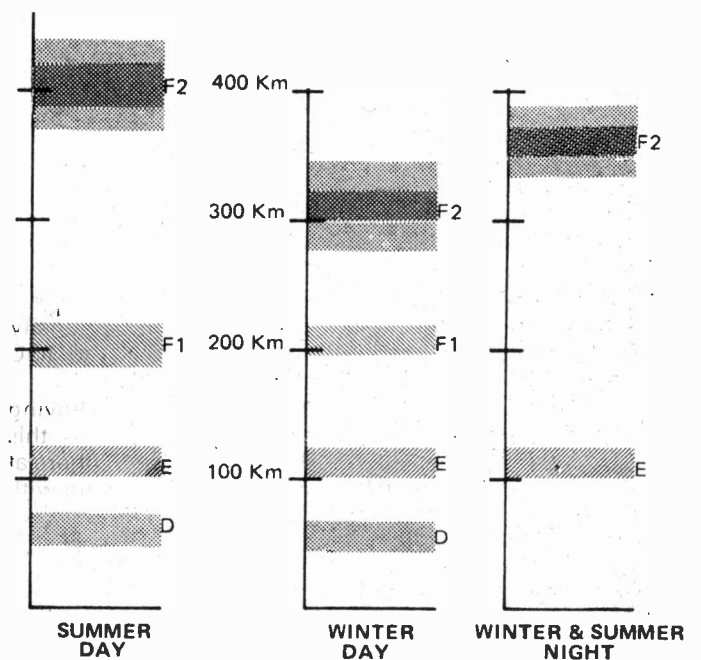


Fig. 9. Illustrating the diurnal and seasonal variations in the various layers.

Nitric oxide (NO) is formed at heights between 60 and 90 km by a photochemical process that diffuses atomic nitrogen down from the E-layer above 100 km. This nitric oxide is ionised by UV radiation from the sun having a wavelength of 1216 Angstroms — the Lyman-Alpha wavelength.

Hydrogen in the sun radiates very strongly at this wavelength which coincides almost exactly with a 'spectral window' in the atmosphere which allows this radiation to penetrate to very low levels in the atmosphere with little attenuation.

Because it penetrates down to where the nitric oxide is produced there is an abundant supply of electrons which contribute to the general ionisation of the D-layer at a height of around 75 km. Solar X-ray and Lyman-Alpha radiation contribute in roughly equal proportions to the ionisation of the D region. However, the strength of the X-rays varies by a large factor both daily and through the solar cycle as well as with solar disturbances. There is no appreciable change in the strength of the Lyman-Alpha radiation.

Up the X-rays

Increased X-ray radiation associated with solar flares can increase the ionisation of the D layer thus causing increased absorption of radio waves travelling through the D region. These solar disturbances can be the cause of a complete 'radio blackout' at times.

As cosmic rays are deviated by the earth's magnetic field ionisation of the lower D region is greater near the magnetic poles than it is near the equator.

Since the D-layer absorbs radio waves it affects the propagation of radio signals. During the day signals below about 5 MHz are almost completely absorbed. Only signals radiated at a very high angle, and above a critical frequency where all signals are absorbed, manage to pass through the layer, being subsequently reflected by the E-layer.

Communication during daylight hours on the lowest frequencies of the HF spectrum from 3 MHz to about 5 MHz or so is thus limited to short distances, not much beyond ground-wave coverage.

Low angle radiation on these frequencies during the day travels a long way through the D-region and is thus absorbed.

The D-layer of course affects higher frequencies but its attenuation affect lessens as the frequency is increased.

The E-layer

This occurs during daylight hours, the maximum density or peak of the layer lying between about 100 and 150 km. It remains weakly ionised at night.

E-layer ionisation is produced jointly by X-rays having wavelengths less than about 100 Angstroms — this ionising oxygen and nitrogen in the upper atmosphere at heights close to 100 km — as well as UV radiation with wavelengths near 100 Angstroms which ionise oxygen.

The atmosphere in the E-region is still dense enough for recombination to take place fairly rapidly. As a consequence, the E-layer can only maintain its signal reflecting ability when it is continuously in sunlight.

Ionisation is generally the best around noon, disappearing rapidly some time after local sunset. (The sun sets on the ionosphere at a height of 100 km about half an hour after local sunset.)

The F-layer

The F-layer is that region of the ionosphere above about 150 km extending up to 800 km and beyond.

During daylight hours, two distinct layers appear in the F-region of the ionosphere — the lower is known as the F₁ layer, the upper as the F₂ layer.

The F₁ layer generally occurs around a height of 200 km and does not vary greatly in height. Its ionisation density is lower in winter than in summer.

As one would expect, the F₂ layer, being the uppermost has the considerable variations in density and height.

There is only one layer during the night in the F-region which is likewise dependant on atmospheric temperature. The height and density of the nighttime F-layer is also very variable owing to a number of factors.

The principal ionising agent of the F-layer is the extreme ultra-violet region (EUV). Solar UV with wavelength between about 200 and 800 Angstroms does most of the work in this respect. Radiation at these wavelengths ionises molecular nitrogen and atomic oxygen at heights between about 150 and 180 km.

The resulting electronic distribution with height does not always show a peak at this level — when there is a peak it is usually that of the F₁ layer.

The shape of the F₂ layer electron distribution, and thus the height of the peak, is largely determined by the variation with height of the loss process and by diffusion of the electronics to other regions. Ions and electronics diffuse above the peak of the layer, the production and loss of electronics (by recombination, etc) below the peak determine both the position of the peak and the shape of the layer. The peak then occurs at a height where the effects of diffusion and loss of electrons reaches an equilibrium.

The F-layer will provide communications out to a range of 4000 km on a single 'hop,' multi-hop propagation being used for distances greater than this.

The F₁ layer will provide communications up to about 9 or 10 MHz during the day. The F₂ layer will support propagation beyond 30 MHz under favourable conditions, even higher in frequency and for longer durations at lower frequencies, during a sunspot maximum.

The maximum usable frequency of the F-layer varies seasonally, being greater during summer than during winter.

Summary So Far

The *daytime* ionosphere consists of an absorbing region — the D-region — with three reflecting ionised layers above that — the E, F₁ and F₂ layers.

The night-time ionosphere consists almost entirely of the F-layer.

It should be noted that the allocation of the letters of these layers above that — the E, F₁₋₅₂ and F₂ layers.

The night-time ionosphere consists almost entirely of the F-layer.

It should be noted that the allocation of the letters of these layers was made by Sir Edward Appleton. It was he who did most of the early investigative work on the ionosphere. The F-layer, which he discovered, is also known as the "Appleton Layer." The E-layer was originally named the "Kennelly-Heaviside Layer" (or just the Heaviside Layer) after the two gentlemen who discovered its existence.

ETI

15 — 240 Watts!

HY5 Pre-amplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (Mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up, 3mV Ceramic Pick-up, 30mV Tuner, 100mV Microphone, 10mV Auxiliary, 3,100mV input impedance 47k Ω at 1kHz
OUTPUTS: Tape 100mV; Main output 500mV R.M.S.


ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz, Bass \pm at 100Hz.

DISTORTION: 0.1% at 1kHz, Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE:** \pm 16.50V

Price £6.27 + 78p VAT. P&P free.

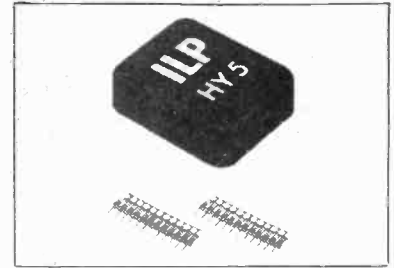HY5 mounting board B1 48p + 6p VAT P&P free



HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P., it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build.
APPLICATIONS: Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator.


SPECIFICATIONS:

OUTPUT POWER: 15W R.M.S. into 8 Ω **DISTORTION:** 0.1% at 15W.

INPUT SENSITIVITY: 500mV **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB

SUPPLY VOLTAGE: \pm 18V

Price £6.27 + 78p VAT. P&P free.

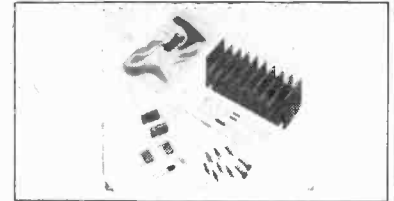

HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS: **INPUT SENSITIVITY:** 500mV

OUTPUT POWER: 25W RMS in 8 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.04% at 25W at 1kHz

SIGNAL/NOISE RATIO: 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB

SUPPLY VOLTAGE: \pm 25V **SIZE:** 105.50, 25mm

Price £8.18 + £1.02 VAT. P&P free.



HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ.

SPECIFICATIONS:


INPUT SENSITIVITY: 500mV

OUTPUT POWER: 60W RMS into 8 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.04% at 60W at 1kHz

SIGNAL/NOISE RATIO: 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** \pm 35V

Size: 114 x 50 x 85mm.

Price £19.01 + £1.52 VAT. P&P free.

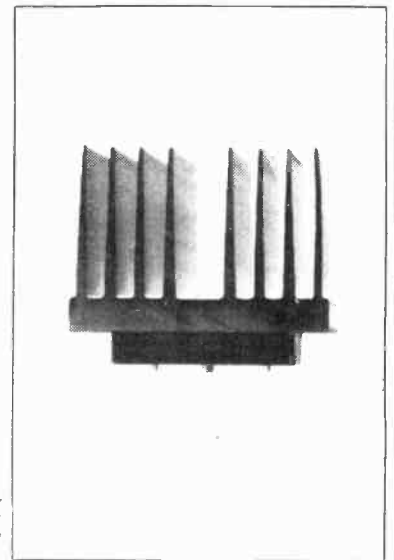

HY200 120 Watts into 8 Ω

The HY200, now improved to give an output of 120 Watts, has been designed to stand the most rigorous conditions, such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral Heatsink — No external components

APPLICATIONS: Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address.

SPECIFICATIONS:

INPUT SENSITIVITY: 500mV

OUTPUT POWER: 120W RMS into 8 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.05% at 100W at 1kHz

SIGNAL/NOISE RATIO: 96dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** \pm 45V

SIZE: 114 x 100 x 85mm.

Price £27.99 + £2.24 VAT. P&P free.

HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — very low distortion — Load line protection — No external components

APPLICATIONS: Public address — Disco — Power slave — Industrial.


SPECIFICATIONS:

OUTPUT POWER: 240W RMS into 4 Ω **LOAD IMPEDANCE:** 4-16 Ω **DISTORTION:** 0.1% at 240W at 1kHz

SIGNAL/NOISE RATIO: 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** \pm 45V

INPUT SENSITIVITY: 500mV **SIZE:** 114 x 100 x 85mm

Price £38.61 + £3.09 VAT. P&P free.

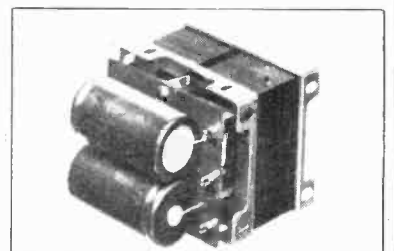

POWER SUPPLIES

PSU36 suitable for two HY30's **£6.44 + 81p VAT**

PSU50 suitable for two HY50's **£8.18 + £1.02 VAT**

PSU70 suitable for two HY120's **£14.58 + £1.17 VAT**

PSU90 suitable for one HY200 **£15.19 + £1.21 VAT**


PSU180 suitable for two HY200's or one HY400 **£25.42 + £2.03 VAT**

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel. (0227) 64723

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name & Address _____
Signature _____

SPECIALS

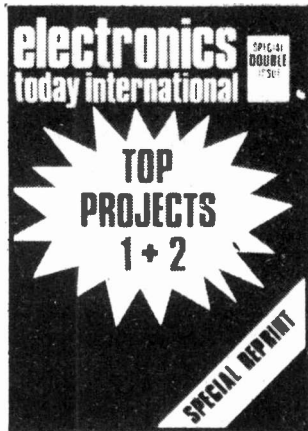

£2.50 + 25p P&P

ETI top projects 1 + 2 include:
Master mixer, 100 W guitar amp., low power laser, printmeter, transistor tester, mixer preamp, logic probe.



£1.00 + 25p P&P

Ni-Cad charger; loudhailer, scope calibrator, electronic ignition, car theft alarm, turnindicator canceller, brake

light warning, LM380 circuits, temperature alarm, aerial matcher, UHF TV preamp, metal locator, four-input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50 W stereo amp. plus many more...
ETI Top Projects 3. This issue was so popular that it is now sold out!

ETI Top Projects 4 includes:
Sweet sixteen stereo amp., waa-waa, audio level meter, expander/compressor, car theft alarm, headlight reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit!...

ETI Top Projects 5. Twenty-two complete projects, including:
5 W stereo amp., stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, gen-purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter...

ETI Top Projects 6, just published, includes:
Graphic equaliser, 50-100 W amp. modules, active crossover, flash trigger, "star and dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show...



75p + 25p P&P

Comprised entirely of new material, the edition covers such diverse subjects as Star Wars and hi-fi! The magazine contains projects for everyone — none of which have appeared in ETI or Hobby Electronics and a look at the future of MPUs, Audio, Calculators and Video. How can you not read it?



£3.00 + 25p P&P

This book is rather an unusual reprint from the pages of ETI. The series appeared a couple of years ago in the magazine, and was so highly thought of by the University of New England that they have re-published the series

splendidly for use as a standard textbook. Written by Peter Sydenham, M.E., Ph.D., M.Inst.M.C., F.I.C.A., this publication covers practically every type of transducer and deals with equipment and techniques not covered in any other book. Enquiries from educational authorities, universities and colleges for bulk supply of this publication are welcomed. These should be addressed to H. W. Moorshead Editor, Hobby Electronics.

HOW TO ORDER

Postage and packing also refers to overseas. Send remittance in sterling only.

Specials
Modmags Ltd
25-27 Oxford Street
London W1R 1RF

Please mark the back of your cheque or PO with your name and address.

Please supply me with the following Specials:

.....
.....
.....
.....
.....
.....

Total cheque/PO enclosed = £ ..

Address:

M

.....
.....
.....



£1.50

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data.
Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each! Each volume costs

£1.50 + 25p P&P



£1.20

ETI's successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics. Each volume costs

£1.20 + 25p P&P

SHUDEHILL SUPPLY COMPANY LTD.

Component Stockist of Electronics — Hi-Fi — Radio and T.V.

53 SHUDEHILL MANCHESTER M4, 4AW

We are now stockists of:

Yaesu—musen—Frgy's (P.L.L.) General S.W. coverage and Sony 8800 9 band receiver.

Also for the car we have:

The Alpha 23 channel—transceiver; 4 channel scanner wide (pocket size) sei wa M.R.2 and MRS 12 channel, selection of Xtals and Standard hand held 2 watt transceivers.

Microwave modules in stock at all times

Anodised instrument cases — Denco coils and radio spares components besides many other makes.

Metal Detectors — TV Games — Hi-fi. You name it, we stock it — SAE for information.

Discount available when producing this advert

LINES FROM OUR VAST STOCKS—IMMEDIATE DELIVERY

All below manufacturers' prices — all new stocks. Quantity discounts — export enquiries invited.

Postage & packing 35p per order
CALCULATOR CHIPS General instrument G1M4 on anti static foam 24 pin D 1 L socket for use with Bowmar display **£1.50** ea Pack of 25 chips **£25**.

BOWMAR 9 DIGIT CALCULATOR DISPLAY with PC connector O 2 digits Common cathode with red bezel **£1.25** ea 10—**£10**.

TEXAS 19 gold plated snap key contacts on gold plated P C board Size 70x80x2mm **75p** ea 10 for **£8**.

ORP12 light dependent resistance (Eq = RPY30) 2 for **£1**, 10—**£4**, 100—**£35**.

FAIRCHILD FN10 D 15 7 segment display C cathode **50p** 10 for **£4.50**.

TBA 120A TV I C amplifier Siemens **75p** 10—**£6**, 100—**£50**, 1000—**£350**.

BECKMAN 500 kcs Triggerable clocking oscillator for use with calculator chips 5v supply with circuit **£1** 10 for **£8**.

BURROUGHS 9 DIGIT Panplex calculator display 7 segment O 25 digits Neon type with red bezel socket and data **£2.50** ea 10 for **£20**.

ALMA PUSHBUTTON high reliability reed switches Push to make 18x27x18mm **40p** ea 10 for **£3.50**.

SMITHS INDUSTRIES Audible warning devices 6-12 volts 2 transistors 30x10mm encapsulated **50p** ea 10 for **£8** 100 for **£30**.

HONEYWELL PROXIMITY DETECTOR integral amplifier Bv D C **£2.50** ea 10 for **£20** 100 for **£175**.

OSMOR CHANGE OVER REED RELAY 12v coil 20mA operating current 59x17x13mm **75p** ea 10 for **£5** 100 for **£45**.

MAINS TRANSFORMERS (miniature) all with 240v primary per per
12 volt 100 m/amp ea 10 100
60x40x42 m/m **95p** **£8** **£60**

12 0 12v 100 m amp 28x25x27mm **£1.20** **£10** **£80**
Valve output 40 1 61x15x42 m/m **75p** **£6** **£50**

EL84 output 80x53x34mm **95p** **£8** **£65**
SOLDER (multicore type) by Servisol
10 metres for **£1**. 50 metres for **£4**.

SPEAKERS (miniature) per per
2 1/2 8 ohms **75p** **£6** **£50**
2 1/2 8 ohms **75p** **£6** **£50**
2 1/2 40 ohms **75p** **£5** **£40**

CLOCKING OSCILLATOR (Pye-Dynamics) thick film 1mHz supply 5v 19x25x6mm **85p** 10 for **£7**.

T.V. TUNERS by GEC UHF 3B mcs size
3 1/2 x 2 1/2 x 1 1/2 **£2.50** ea 10 for **£20**.

T.V. SOUND TUNER KIT. Through your F.M. tuner Kit of parts with instructions **£5.50**. Ready-built, tested, **£7.00**.

JOYSTICK CONTROLS. (ideal for TV Games, model control) sturdy constructed compact giving full 360 movement and control. Each unit fitted 4-off 100K linear. controls. Pair **£4.00**.

T4/RFLONG-MEDIUM & F/M TUNER WITH MC1310 DECODER * 5-BUTTON SELECTOR SWITCHES * INPUT SELECTORS FOR GRAM AND TAPE * SUPPLIED COMPLETE WITH FRONT-END TUNER AND FERRITE AERIAL * SIMPLE INTERCONNECTIONS * Size 19x13x6cm
THIS QUALITY AMPLIFIER £10.95 WITH CIRCUIT

POWER UNIT KIT FOR ABOVE MODELS 25/28 VOLTS £2.95
TAPE HEADS 1/4 track Record Marriot XRPS36 **£5**. XES11 erase **£1.25**. XRPS 18 **£3.50**.

MULLARD TUNER MODULES with data LP1171 combined AM/FM IF strip — **£3.50**. * LP1179 FM front end with AM tuning gang, used with LP1171 — **£3.50**. * LP1171 and 79 pair — **£5.75**. * LP1157 complete AM strip — **£2.05**. * Ferrite Aerial — **95p**.

SEVEN DIGIT MINIATURE COUNTER by Durant 12-24 volts D C 3 Watts Size 40x25HX 55Lmm **£1** each. 10 for **£9**. 100 for **£80**.

INDUSTRIAL RELAYS Price ea 10 100+
By I M U-OMRON
At less than Distributor prices
60-43 24V DC **£1.10** **£9.00** **£85.00**
2-Pole Open **£1.10** **£9.00** **£85.00**
60 13 48V AC
Octal Plug in type enclosed **£1.20** **£10.00** **£90.00**

60 02 12V AC
2-Pole C Over Octal
Enclosed type **85p** **£7.50** **£65.00**
All relays are 250V 6 Amp AC Current Rating

2N3055A TO3 POWER 80 VOLT VERSION 10 for **£2.50** 100 for **£22.00** 1 000 for **£200.00**
Carriage £2 00 on 1 000 Lots

FREE TRANSISTOR CATALOGUE
SEND STAMPED 12" x U.K. 1" ADDRESS ENVELOPE (min 9 1/2" x 6 1/2") FOR YOUR COPY NOW

Buy it with Access **Henry's RADIO** All mail to: Henry's Radio 404 Edgware Rd London W2 Phone (01) 723 1008

FLADAR DUAL VOLTAGE TRANSFORMERS

PRIMARY 220-240 50HZ. ALTERNATIVE SECONDARY VOLTAGE AND CURRENT AVAILABLE BY SERIES OR PARALLEL CONNECTION

Type	Voltage	Current	£	p/p	Type	Voltage	Current	£	p/p
08FE06	6+6	0.5A each	1.50	50p	08FE24	24+24	0.15A each	1.80	50p
08FE06	6+6	0.5A each	1.80	50p	12FE24	24+24	0.2A each	2.00	60p
12FE06	6+6	1A each	2.00	60p	20FE24	24+24	0.4A each	2.60	70p
20FE06	6+6	1.6A each	2.60	70p	50FE24	24+24	0.8A each	3.10	70p
50FE06	6+6	3A each	3.10	70p	80FE24	24+24	1.2A each	3.60	85p
60FE06	6+6	4A each	3.60	85p	80FE24	24+24	1.5A each	4.50	1.00
08FE09	9+9	0.3A each	1.50	50p	50FE28	28+28	0.75A each	3.10	70p
08FE09	9+9	0.5A each	1.80	50p	60FE28	28+28	1.1A each	3.60	85p
12FE09	9+9	0.75A each	2.00	60p	80FE28	28+28	1.4A each	4.50	1.00
20FE09	9+9	1A each	2.60	70p	20FE30	30+30	0.35A each	2.60	70p
50FE09	9+9	2.5A each	3.10	70p	50FE30	30+30	0.75A each	3.10	70p
60FE09	9+9	3A each	3.60	85p	60FE30	30+30	1A each	3.60	85p
08FE12	12+12	0.25A each	1.50	50p	80FE30	30+30	1.2A each	4.50	1.00
08FE12	12+12	0.3A each	1.80	60p	Multi-Tap Range. Voltage Available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 12-0-12 CR 15, 0-15 0-12-15				
12FE12	12+12	0.5A each	2.00	70p					
20FE12	12+12	0.8A each	2.60	70p	30FE30	24+30	1A	3.40	70p
50FE12	12+12	2A each	3.10	70p	60FE30	24+30	2A	3.70	85p
60FE12	12+12	2.5A each	3.60	85p	80FE30	24+30	3A	4.50	1.00
80FE12	12+12	3A each	4.50	1.00	100FE30	24+30	4A	5.60	1.15
08FE15	15+15	0.2A each	1.50	50p	Centre Tap Secondary				
08FE15	15+15	0.25A each	1.80	60p					
12FE15	15+15	0.4A each	2.00	70p	FE06	6-0-6	1A each	2.00	60p
20FE15	15+15	0.6A each	2.60	70p	FE09	9-0-9	1A each	2.60	70p
50FE15	15+15	1.6A each	3.10	70p	FE12	12-0-12	1A each	2.60	70p
60FE15	15+15	2A each	3.60	85p	FE15	15-0-15	1A each	3.10	70p
80FE15	15+15	3A each	4.50	1.00	FE20	20-0-20	1A each	3.10	70p
08FE20	20+20	0.15A each	1.50	50p	60FE28	26-0-26	1A each	3.60	1.00
08FE20	20+20	0.2A each	1.80	60p	60FE28	28-0-29	1A each	3.60	1.00
12FE20	20+20	0.25A each	2.00	70p	60FE30	30-0-30	1A each	3.60	1.00
20FE20	20+20	0.5A each	2.60	70p	100FE26	26-0-26	2A each	5.15	1.15
50FE20	20+20	1.2A each	3.10	70p	100FE30	30-0-30	2A each	5.15	1.15
60FE20	20+20	1.5A each	3.60	85p	100FE36	36-0-36	2A each	5.15	1.15
80FE20	20+20	2A each	4.50	1.00	Air cored Audio Cross Over Coils				
Charger Transformer									
48FE12	0-6-12	4A	3.19	70p	FE01	0.1mH		0.26	20p
66FE12	0-6-12	5A	3.64	85p	FE03	0.3mH		0.26	20p
70FE12	0-6-12	6A	4.86	1.00	FE05	0.5mH		0.30	20p

FLADAR ELECTRIC P.O. BOX 19 WESTCLIFF-ON-SEA ESSEX, 0702-613314

TRADE ENQUIRIES WELCOME
PLEASE ENQUIRE FOR OTHER TYPES NOT SHOWN

PAYMENT TERMS C.W.O., Cheques Postal Orders Please add 8% VAT After post & packing

TARGET ELECTRONICS FORMERLY "THE RADIO SHOP"

16 Cherry Lane Bristol BS1 3NG Telephone: 0272-421196

Official orders welcomed Gvt / Educational Depts etc

Size 60 mm x 45 mm x 40 mm

T21	0-50µA	T30	0-1Amp
T22	0-100µA	T33	0-50v AC
T23	0-500µA	T34	0-300c AC
T24	0-1mA	T35	"S" Meter
T25	0-5mA	T36	Vu Meter
T26	0-10mA	T40	50-0-50µA
T27	0-50mA	T41	100-0-100µA
T28	0-100mA	T42	500-0-500µA
T29	0-50mA	T43	0-30v DC

Price **£4.65**

PANEL METER with ILLUMINATION WIRING
Dials are clearly figured on bright white for easy reading 2 1/2% F.S.D. accuracy Zero adjustment at front. Cushioned pointer stops. Complete with mounting nuts and washers
Prewired and have lamp terminals installed on rear
Snap off front cover and insert Lamp Kit (opp extra) **65p**

Size 110mm x 82mm x 43mm

043	0-30µA	0420	0-200µA
045	0-50µA	0450	0-500µA
0410	0-100µA		

Price **£5.70**
10 or more 10% Discount P&P 50p

TRANSISTOR SPEAKERS

64SS	2 1/2	64ohms	60p
3W80	2 1/2	8ohms	50p
1W2	2 1/2	8ohms	50p
50F12	2	8ohms	60p
4512	1 1/2	8ohms	60p
3812	1 1/2	8ohms	60p

10 or more 10% Discount P&P 25p

BUZZERS
Very loud note. Cream plastic case 50mm dia 30mm high 3 fixing feet with holes spaced at 50mm
9201 / 6V — **55p**
9201 / 12V — **70p** P&P 25p

TR4A 13 Volt 500MA Twin Bobbin **70p**
P&P 45p
All above 10 or more 10% Discount

NASCOM 1 Z80 MICROCOMPUTER KIT
Includes interface for: TV or Monitor — cassette, dump — Teletype — spare, PIO, Expansion RAM-BOARD up to 32K
Potential: High Level Language Mini Floppy Disk. Excellent Z80 evaluation kit **£197.50** + VAT P&P £2 50
Please add 12 1/2% VAT Remainder 8% VAT
Large selection of aluminium boxes & Instrument Cases
Phone in your Access or Barclaycard order. Catalogue 25p post paid

data sheet

LH0063/LH0063C DAMN FAST BUFFER

NATIONAL

TYPICAL APPLICATIONS

The LH0063/LH0063C is a high speed, FET input, voltage follower/buffer designed to provide high current drive at frequencies from DC to over 100MHz. It will source or sink 250 mA into 50 ohm loads (500 mA peak) at slew rates of up to 6000V/ μ s. In addition, it exhibits excellent phase linearity up to 20 MHz.

It is intended to fulfil a wide range of buffer applications such as high speed line drivers, video impedance transformation and high impedance input buffers for high speed A to Ds and comparators.

It can also be used as a diddle yoke driver for high resolution CRT displays*.


FEATURES

- Damn fast **6000V/ μ s**
- Wide power bandwidth
DC to 100 MHz
- High output drive
+ or - 10 V with 50 ohm load
- Low phase non-linearity
2 degrees
- Fast rise times **2 ns**
- High current gain **120dB**
- High input impedance
10 000 M


These devices are constructed using specially selected junction FETs and active laser trimming to achieve guaranteed performance specification. The LH0063 is specified for operation from -55 to $+125$ C, while the LH0063C is specified from -25 to $+85$ C. Both are available in a 5W 8-pin TO-3 package.

*NOTE. In VDUs where the basis of operation is for the beam to be pointed at the start of the character and then 'diddled' by means of a separate set of coils in order to form the shape of the character on the screen, the beam being switched on and off as required.


Gamma Ray Pulse Integrator

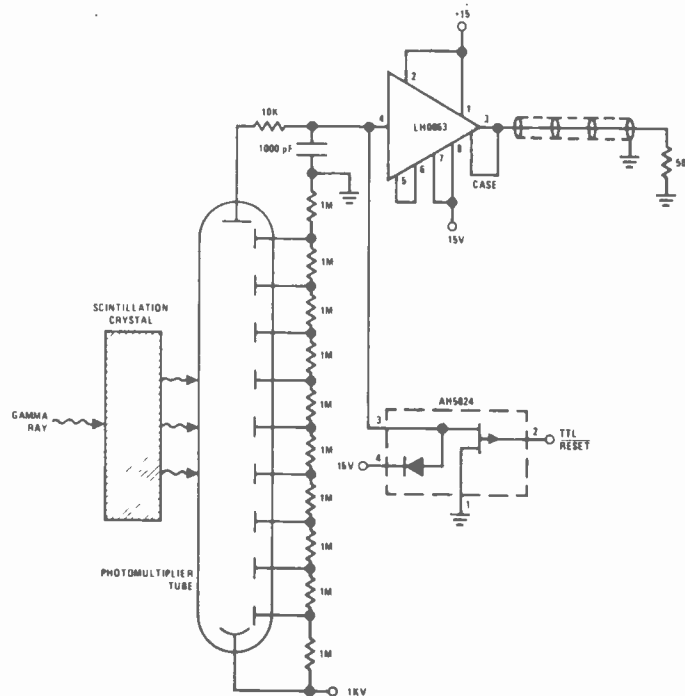


1W CW Final Amplifier

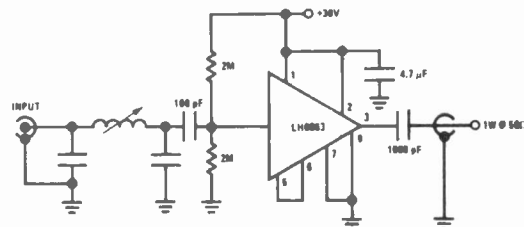

4.5 MHz Notch Filter

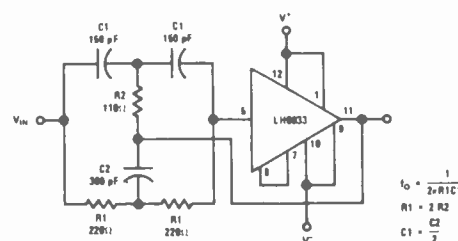

Nuclear Particle Detector

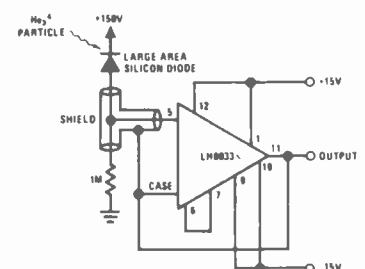


LH0063/LH0063C DAMN FAST BUFFER

NATIONAL


DC ELECTRICAL CHARACTERISTICS

LH0063/LH0063C (Note 1)


PARAMETER	CONDITIONS	LIMITS						UNITS
		LH0063			LH0063C			
		MIN	TYP	MAX	MIN	TYP	MAX	
Output Offset Voltage	$R_S \leq 100 \text{ k}\Omega$, $T_C = 25^\circ\text{C}$ $R_S \leq 100 \text{ k}\Omega$		10	25		10	50	mV
Average Temperature Coefficient of Output Offset Voltage	$R_S \leq 100 \text{ k}\Omega$		300			300		$\mu\text{V}/^\circ\text{C}$
Input Bias Current	$T_C = 25^\circ\text{C}$.1	.2		.1	.2	nA
Voltage Gain	$V_{IN} = \pm 10\text{V}$, $R_S \leq 100 \text{ k}\Omega$, $R_L = 1 \text{ k}\Omega$.96	.98	1	.96	.98	1	V/V
Voltage Gain	$V_{IN} = \pm 10\text{V}$, $R_S \leq 100 \text{ k}\Omega$, $R_L = 50\Omega$, $T_C = 25^\circ\text{C}$.94	.96	.98	.92	.96	.98	V/V
Input Resistance		10^{10}	10^{11}		10^{10}	10^{11}		Ω
Input Capacitance	Case Shorted to Output		8			8		pF
Output Impedance	$V_{OUT} = \pm 10\text{V}$, $R_S = 100 \text{ k}\Omega$		1	4		1	4	Ω
Output Current Swing	$V_{IN} = \pm 10\text{V}$, $R_S \leq 100 \text{ k}\Omega$.2	.25		.2	.25		Amps
Output Voltage Swing	$R_L = 50\Omega$	± 10	± 13		± 10	± 13		V
Output Voltage Swing	$V_S = \pm 5\text{V}$, $R_L = 50\Omega$, $T_C = 25^\circ\text{C}$	5	7		5	7		V_{PP}
Supply Current	$T_C = 25^\circ\text{C}$, $R_L = \infty$, $V_S = \pm 15\text{V}$		60	75		60	80	mA
Supply Current	$V_S = \pm 5\text{V}$		50			50		mA
Power Consumption	$T_C = 25^\circ\text{C}$, $R_L = \infty$, $V_S = \pm 15\text{V}$		1.80	2.25		1.80	2.40	W
Power Consumption	$V_S = \pm 5\text{V}$		500			500		mW

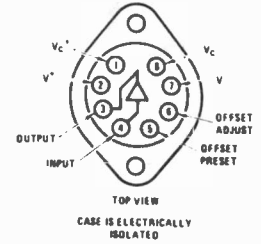

LH0063 Small Signal Rise Time

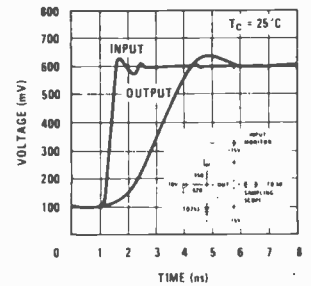

LH0063 Supply Current vs Supply Voltage

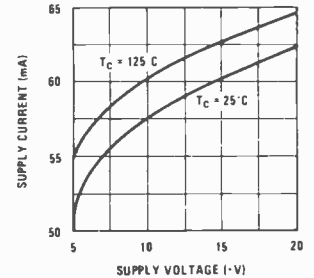

NOTE 1: Unless otherwise specified, these specifications apply for +15V applied to pins 1 and 2, -15V applied to pins 7 and 8, and pin 5 shorted to pin 6. Unless otherwise


noted, specifications apply over a temperature range of -55 C to 125 C for the LH0063 and -25 C to 85 C for the LH0063C. Typical values shown are for 25 C.

AC ELECTRICAL CHARACTERISTICS


LH0063/LH0063C: ($T_C = 25^\circ\text{C}$, $V_S = \pm 15\text{V}$, $R_S = 50\Omega$, $R_L = 50\Omega$)

PARAMETER	CONDITIONS	LIMITS						UNITS
		LH0063			LH0063C			
		MIN	TYP	MAX	MIN	TYP	MAX	
Slew Rate	$R_L = 1 \text{ k}\Omega$, $V_{IN} = \pm 10\text{V}$		6000			6000		V/ μs
Slew Rate	$R_L = 50\Omega$, $V_{IN} = \pm 10\text{V}$, $T_C = 25^\circ\text{C}$	2000	4000		2000	4000		V/ μs
Bandwidth	$V_{IN} = 1 \text{ Vrms}$		200			200		MHz
Phase Non-Linearity	8W = 1 to 20 MHz		2			2		degrees
Rise Time	$\Delta V_{IN} = 5\text{V}$		1.6			1.9		ns
Propagation Delay	$\Delta V_{IN} = .5\text{V}$		1.9			2.1		ns
Harmonic Distortion			<0.1			<0.1		%


LH0063 Large Signal Pulse Response

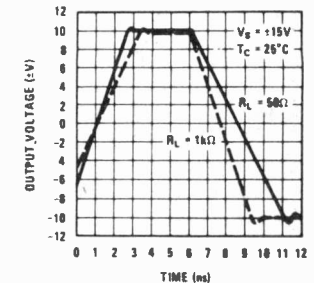


LH0063 Frequency Response

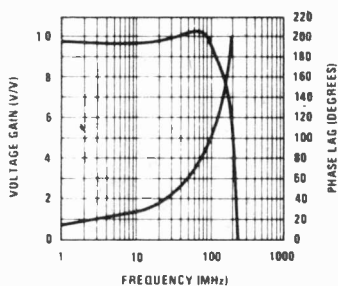


LH0063 Power Dissipation

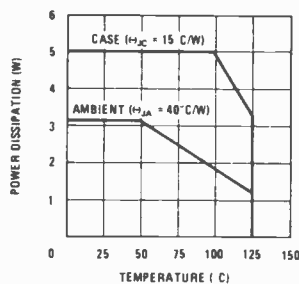

LH0063 DC Safe Operating Area

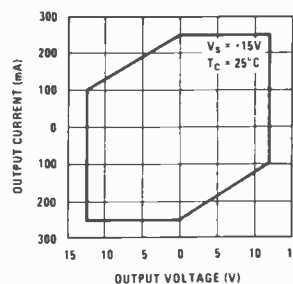

LH0063 Output Voltage vs Supply Voltage

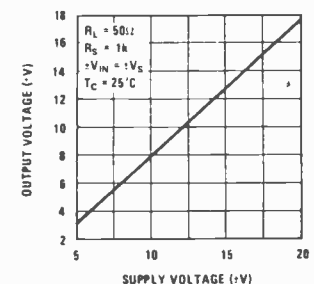

SANTA'S GOODIES

7409N 10p, £8-100, 7460N 10p, £8-100
74109N 15p, £12-100, 74155 35p, Min
Order 10 of one type — 100+ POA p/p 20p

PIHER SLIDER POTS 47K Log Track 70 mm
Overall 85mm, Singles 20p, £15-100, Doubles
50p, £40-100; Min Order 10, 100+ POA, p/p
20p

SUPERB STEREO CASSETTE DECKS —
Brand New Piano Keys, 6v motor, end of tape
stop, digital counter, heads, pulleys, etc., as
used in National Panasonic music centres, very
high quality £8.75 + £2 p/p.

VERO EDGE CONNECTOR 0.1 inch 42 + 42
w/w key at 7, type 1360-2 £1 + p/p 20p.

TRIMPOTS 50Ω T05 20p, 100Ω Cermet 20p,
100Ω Painton PCB 20p, 200Ω ditto 20p, 250Ω
ditto 20p, 500Ω ditto 20p, 1K ditto 20p, 2K
ditto 20p, 2K Helitrim 20p, 5K PCB 20p, 1M
skeleton min. vert. 12p p/p 20p.

CANNON D-TYPES 15 way plugs 50p, 15
way sockets 50p, 25 way plug 60p, 25 way
socket 60p, 37 way plug 80p, 50 way socket
£1.20, 50 way w/wrap sockets £1.30, 25 way
ribbon plugs 90p, covers with retainers 15 way
60p, 25 way 80p, 37 way £1.25 way plastic
(3M) 50p, all above limited stocks. P/P 20p.

TTL 74 SERIES

7400 12p	7401 12p	7402 15p
7404 14p	7407 30p	7409 16p
7410 13p	7412 18p	7414 45p
7416 24p	7417 25p	7420 15p
7427 30p	7428 32p	7430 15p
7432 26p	7438 30p	7442 50p
7451 15p	7472 76p	7460 15p
7474 28p	7475 30p	7485 95p
7486 30p	7490 30p	7491 80p
7495 60p	7496 55p	7497 £1.50
74107 30p	74109 50p	74121 25p
74123 48p	74150 90p	74151 60p
74153 70p	74154 £1.10	74155 80p
74157 60p	74162 90p	74163 90p
74164 £1.00	74165 £1.10	74188 £2.50
74190 £1.00	74192 90p	74195 90p
74198 £1.30	74279 £1.20	74284 £3.60
74368 £1.35	75450 35p	76660 50p

P/P 20p

SUPERSAVER 1 cassette recorder motor 9v
Speed governed, brand new, fantastic value,
95p p/p 20p.

SUPERSAVER 2 Hybrid Systems DAC 371-8
(8-bit) DIL packaged + data, ideal MPU users,
brand new £2 (fraction of original cost) p/p
20p.

SUPERSAVER 3 ICL P.S.U. 12v 1.8A (7.5v-
15v) in maker's carton £10 p/p £2.

MEMORIES 2708 £6-85, 2102 (Signetics)
£1, 1702A £2.95, 2513 (upper case) £5, p/p
20p.

SUBMIN. TOGGLES (C & K, USA) spco
extended toggle (1.25 inch) superb quality 75p.
Standard submin. toggle dpco 80p, p/p 20p.

9-WAY MALE/FEMALE connector (Elco
8129) 0.1 inch pitch, PCB mounting ideal for
bussing two PCBs together 35p/pair p/p 20p.

LEDS (red) TIL 209 8p, 0.2 10p, Vernitron
Ceramic filters FM-4 10.7MHz 45p, BD 236
40p, 2N3055 (TI) 40p, BC183L 10p, BC213L
10p, BF195 10p, 2521V (Dual 128 bit static
shift register 65p), RS 12-0-12 50mA sub-
miniature transformer £1.35, 5LT01 (green
phosphor) £4, suitable clock IC £3.25,
N82S126N (PROM 256x4 bit) £1.30,
TMS3128NC (static shift reg) £1.25,
LM711CH T0-99 (Voltage comparator) 25p,
FPE 100 infra red emitter + data 15p,
MM5314 £2.95, DIL SWTS 4 way 60p,
TBA810S + DATA 65p.

P/P 20p

All enquiries SAE please, Cat. SAE 8x6
or free with goods. P/P same for
quantities except where greater than
£1.

Merry Christmas to all customers and
ETI

L. B. ELECTRONICS
43 WESTACOTT, HAYES,
MIDDLESEX UB4 8AH, ENGLAND

BUILD THE TREASURE TRACER



MK III METAL LOCATOR

AS SEEN
ON BBC-1
& BBC-2
TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit, 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components sited printed on.
- Complete after sales service.
- Weighs only 22oz.; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil

£15.95
Plus £1.20 P&P
Plus £1.37 VAT (8%)

Built, tested and Guaranteed

£20.95
Plus £1.20 P&P
Plus £1.77 VAT (8%)

MINIKITS ELECTRONICS,
6d Cleveland Road, South Woodford,
LONDON E18 2AN
(Mail order only)

CALCULATORS

SCIENTIFIC

SPECIAL OFFER
TEXAS T159 (together with PC100B
(Complete as manufacturer's specifications)
£285.00

TEXAS/HP Accessories available	
*TEXAS T159 (New Card prog 960 prog steps of 100 mem)	£156.50
*TEXAS T158 (New Key prog 480 steps or 60 mem)	£60.00
*TEXAS PC100B (New updated Printing Unit for T158/T159)	£140.00
*TEXAS T157 (Key Prog 8 Mem. 150 Key Strokes / 50 Prog Steps)	£26.20
TEXAS T133 (New — same spec. as T130, but 3 Mem)	£13.95
*TEXAS T145 (New updated version of the Texas T140)	£19.95
*TEXAS 42M4A (10 Dig Fin / Stat Prog 12 Mem 32 key strokes)	£42.95
*TEXAS TI PROGRAMMER (Hexadecimal Oct)	£46.50
*TEXAS T151/iii (New 8 Dig + Exp 10 Mem 32 Prog Steps Stat/Sci)	£26.30
TEXAS T125 (new LCD Sci/Stat)	£18.90

"SLIM-LINE" Chronograph BARGAIN OFFER

You will not believe the luxury of this "Slim-line" 12 function Chronograph until you have worn it... until you have enjoyed the compliments it generates.

The "Slim-line" Chronograph gives continuous easy to read LCD display of hours, minutes, seconds, AM/PM. At the touch of a button you have date — month date — day of week — reverting to normal display time at the release of the button.

Press again for immediate stop watch/lap time facility to 1/100 second. The "Slim-line" even has a powerful back light for easy light use. The casing is chrome finished with matching linked bracelet.

We are so certain you will be delighted and satisfied with this "Slim-line" Chronograph that in addition to the One Year Warranty we are offering a 14-day money back guarantee if you are not entirely satisfied.



ONLY £27.50 + £1.00 p/p ins. Send cheque/P.O. or order via Barclay/Access credit card today under our Special 14-day Trial Offer.

*TEXAS T158 with Applied Statistics **£80.00**
*TEXAS T159 with PC100B and Applied Statistics **£305.00**

AUTUMN SALE

TEXAS T159 Calculator (complete as manufacturer's spec., master module, charger, etc.) PLUS statistics modular and extra set of 40 Blank Prog Cards with wallet, etc.
ONLY £180

*CBM S61 (Stat + Sci 6 Mem M & S Div Ch; Sq Dis Lin Rev. Etc.)	£46.00
*CBM M55 (Adv Math / Sci 6 mem)	£46.00
*CBM 9190R (as 4190R but with 9 memories)	£27.50
*CBM Pro 100 (12 Step Prog)	£29.50
*HP 19C (Cont Mem Key prog Printer)	£163.00
*HP 29C (as 19C but no Printer)	£110.00
*HP33E (8 mem Pro Sci/Stat)	£64.00
*HP25C (Key Prog Con Mem)	£99.00
*HP27 (10 Mem Sci/Fin/Stat)	£73.50
*HP31E (New Sci replaces HP21)	£35.00
*HP67 (Card Prog 224 Steps 26 Mem)	£277.00
*HP97 (Fully prog with Printer)	£466.50
All HP range avail, inc. new 'E' range.	
*CASIO FX201P (Sci. 11 mem. 127 step Key prog) Fortran System	£44.50
*CASIO PRO FX1 (127 Step Card Prog 11 Mem — Fortran System)	£99.00
CASIO FX360 (New 10 Dig + Exp 7 Mem) (St. Div Lin Regr. Etc.)	£45.00
CASIO FX5000 EP (Alphanumeric Sci / Stat Desk Printer 10 Dig + Exp 7 Mem, etc.)	£185.00
CASIO AQ 1000 (LCD Cal 3-way Stop Watch / Alarm)	£20.00
CASIO CQ1 (4 stag alarm / Cal)	£24.50
CASIO FX3100 (New version of FX3000-LCD Sci/Stat/div. Polos Rec. etc.)	£22.50
CASIO FX8000 (as above + Stop Watch / Alarm)	£27.73

LOW PRICED COMPUTING
THE COMMODORE PET COMPUTER
with 8K bytes RAM 2001-8
A complete personal computer that operates anywhere by simply plugging into Mains supply. Allows communications directly from BASIC to IEEE — 488 standard devices —

Cassette, Video Display Unit and Keyboard built into PET
Fully guaranteed Warranty by CBM complete only **£643**

FREE — Mains/Charger included

GOODS FULLY GUARANTEED
PRICES EXCLUDE VAT (ADD 8%)
BUY/INC. P&P CHEQUE WITH ORDER
Company/hospital and Government orders accepted by phone
Barclaycard/Access accepted by phone.


Tel. 01-455 9855

EXPORT ORDERS WELCOMED
Air Freight / Air Post Delivery
Quotations on request. Payments via Letter of Credit/Int. Money Order / American Express, etc.

**MOUNTAINDENE
LTD.**

22 Cowper St., London, EC2

CURVE TRACER

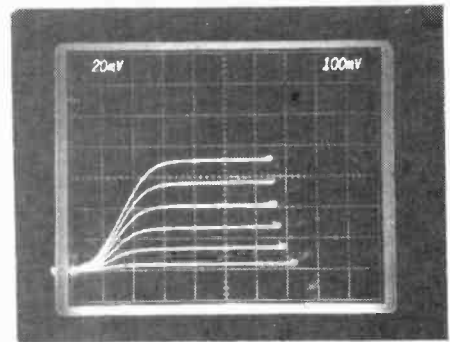


Display the dynamic characteristics of a variety of semi conductor devices with out curve tracer. Design by J. H. Adams.

THE CURVES INVOLVED in this design are not unfortunately those of the Bardots and Welchs of this world but curves that, to some, are just as interesting. The design will allow the dynamic voltage-current characteristics of diodes and transistors to be displayed on the screen of a DC 'scope capable of taking an external X input.

The performance of the unit will not be up to that of a commercial machine but considering such commercial designs are priced in the thousand pound range while our design could be built for around five pounds, we're not doing too badly.



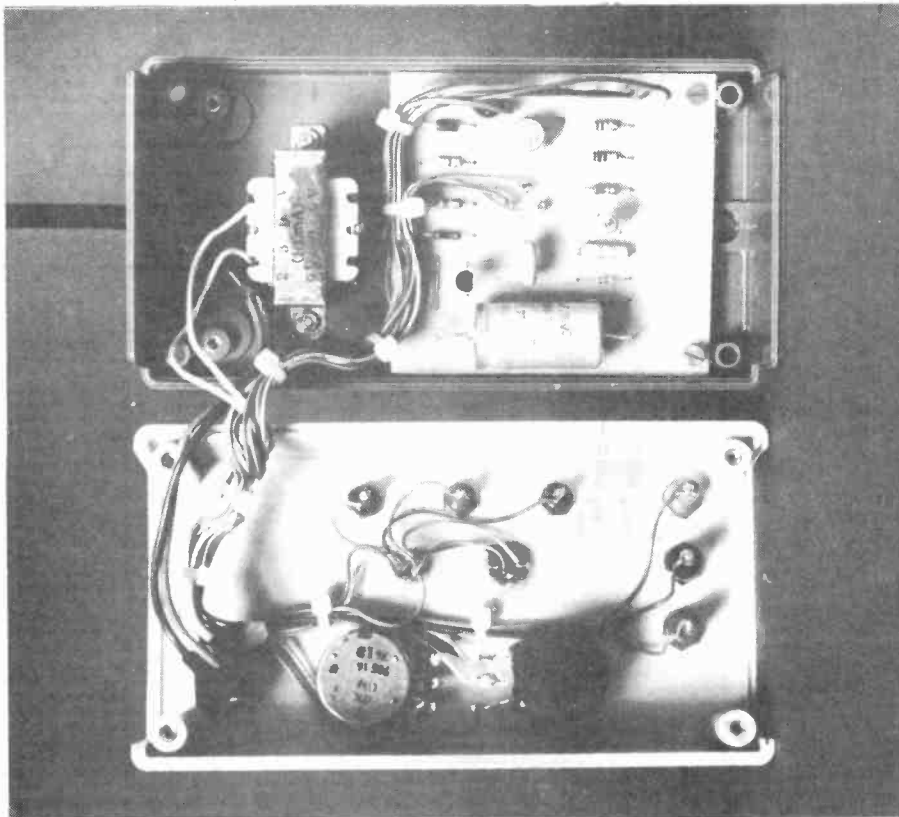View of the internal layout of the prototype version



Construction of the curve tracer is straightforward. Mount all the components on the PCB according to the overlay. The internal layout of our prototype is shown in the photographs. The unit is mains powered and a battery supply is not suitable for this circuit.

Initially try the curve tracer with a high gain nrn transistor, a BC108 will be ideal. Connect it to one of the tracer's sockets and connect the unit to the 'scope. Set the Y gain on the 'scope at maximum and set up the maximum required level of collector voltage by adjusting RV1. RV2 will control the number of steps displayed on the screen. The X sensitivity of the 'scope should be 1V per division.

The performance of the unit is degraded by the slight drop in the DC potential on C1 during the 10mS sweep and the slight effect of the 100R sampling resistor, in that its volt drop is included in the observed collector potential. However as stated above the unit will give a good indication of the dynamic performance of a wide range of semiconductor devices (as the photograph shows) at a price that is a fraction of similar commercial equipment.

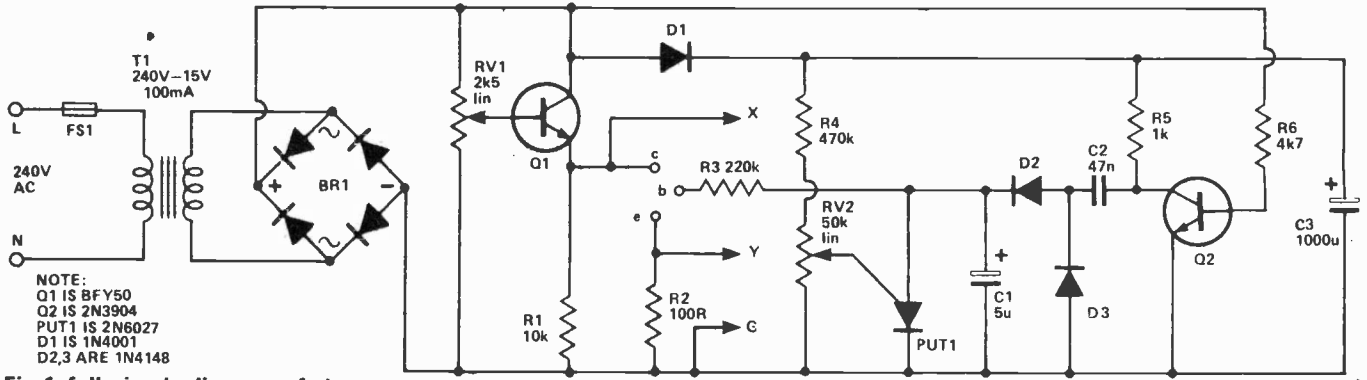


Fig. 1 full circuit diagram of the curve tracer.

HOW IT WORKS

The principles of the full circuit can perhaps be best explained by consideration of a simpler form of the circuit. Figs. 2 and 3 show circuits for investigating the dynamic characteristics of a diode and transistor (at fixed base current) respectively.

The 'diode circuit' will, unless an inverter is available, produce a trace that will appear upside down.

Operation of this circuit is quite straightforward. RV1 allows the peak value of the AC supply to be adjusted. This is then applied to the device under test via a current limiting resistor as well as to the X input of the scope. The current flow in the device at any time is proportional to the voltage developed across a low value sampling resistor in the current path. This voltage is fed to the Y input of the scope.

The simple transistor tester functions in much the same way. RV1 allows the base current to be adjusted within the range 10µA to 100µA.

The characteristics of an N-Channel FET (2N3819) may also be examined with this basic building block. The output characteristics are displayed for a gate voltage selected by RV1. Transfer characteristics (gate voltage vs. Drain Current) may be shown by transferring lead X to the gate terminal and mining the 1000µF capacitor to the 15V supply (observing the change in polarity).

Moving now to the full circuit of Fig 1 that allows a far more informative display providing, as it does, simultaneous displays of the characteristic curves for several equally spaced values of base current.

The circuit operates as follows. Every 10 ms the collector supply swings up and back over a half cycle of the full-wave rectified supply. At the end of each half cycle, there is a short period during which the supply potential is below about 0.6 V, and during this time, Q3 turns off, sending a pulse from its collector into the charge store C1 C2 D3 D2. Each pulse increases the potential in C1 by approximately 0.2 V. This would go on until the potential on C1 was 20 V were it not for Q2, the little known and much mis-described programmable unijunction transistor, PUT. This device is the semiconductor version of a neon lamp, insulating up to a certain p.d. and conducting heavily at potentials above this breakdown value, but with the added advantage in that, through a third terminal, this breakdown potential is programmable over quite a wide range. Varying this control potential through the setting of VR2 sets the

number of steps that will occur before the potential on C1 is great enough to make Q2 fire, reducing the capacitor's potential to approximately 0.6 V and so re-starting the sweep sequence.

The tracer can hardly be expected to match all the performance of a commercial curve tracer, the prices of which range into thousands of pounds. There are errors, due to the slight droop in d.c. potential on C1, and hence in base current, during the 10ms sweep, and due to the slight effect of the 100R sampling resistor, in that its volt drop is included in the observed collector potential, but as can be seen, these are quite insignificant as regards the final display. The only problem which may arise is the appearance of Radio 4 on the current axis (seen as a thickening of the trace). This is easily cured by placing a 10n disc capacitor across the actual Y-inputs of the oscilloscope.

A suitable transistor for the device under test is any reasonably high gain npn transistor, e.g. BC108. VR1 controls the maximum collector voltage, whilst VR2 sets the number of sweeps displayed. With the values given, the difference in base current between one step and the next is approximately given by:

$$\frac{1}{5R} \mu\text{A, where } R \text{ is in megohms.}$$

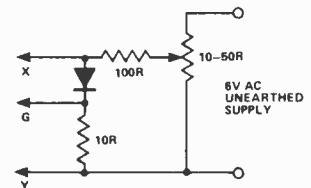


Fig. 2 simple diode tester

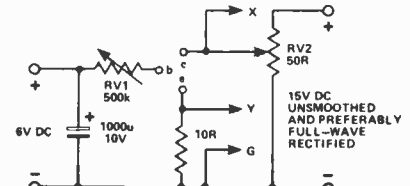


Fig. 3 fixed current transistor tester


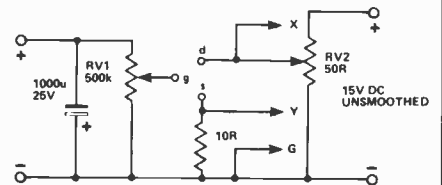


Fig. 4 circuit for investigating FET transfer characteristics.

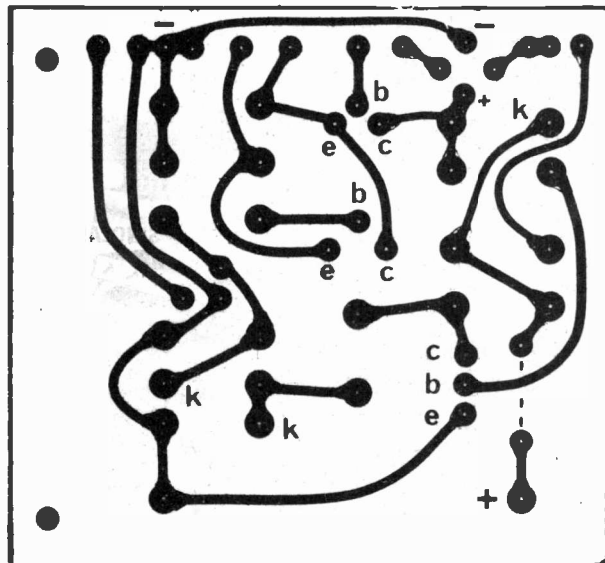

PARTS LIST

RESISTORS

R1	10k
R2	100R
R3	220k
R4	470k
R5	1k0
R6	4k7

CAPACITORS

C1	5u0 25 V electrolytic
C2	47n polyester
C3	1 000 25 V electrolytic

SEMICONDUCTORS

Q1	BFY50
Q2	2N3904
PUT1	2N6027
D1	1N4001
D2,3	1N4148
BR1	0.9A 400V

POTENTIOMETERS


RV1	2k5 1in
RV2	50k 1in

MISCELLANEOUS

PCB as pattern, case to suit, sockets, knobs, cable, etc.

BUYLINES

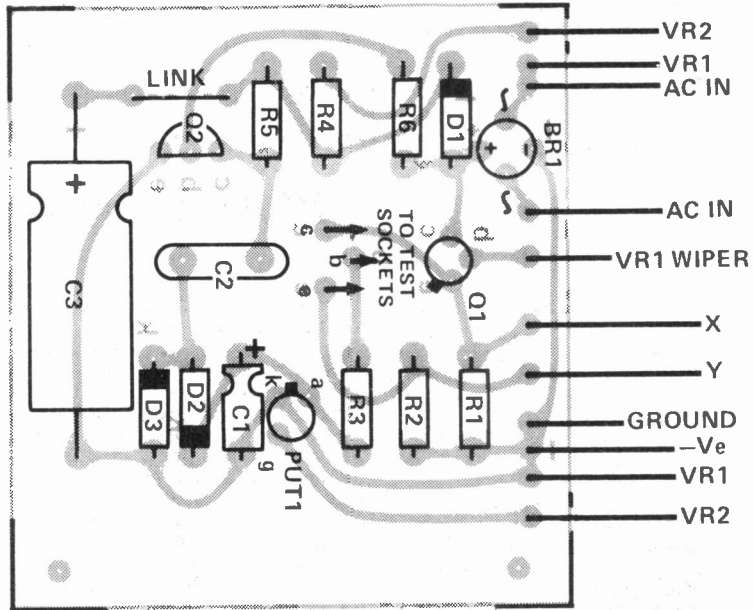The components used in this project should in the main, be generally available — the only component likely to cause problems is the PUT, but this should be available from the larger mail order outlets.



7400 TTL		74151		74522		74500	
7400	.10	74151	.58	74522	.38	74500	.18
7401	.12	74154	1.00	74537	.38	2N3053	.20
7402	.12	74156	.60	74551	.26	2N2054	.57
7403	.12	74157	.54	74564	.20	2N3055	.57
7404	.10	74160	1.04	74574	.38	2N3752	.12
7406	.27	74162	.80	745112	.56	2N3754	.12
7406	.27	74163	1.18	745124	3.25	2N3819	.29
7406	.12	74164	.87				
7409	.13	74165	.93				
7410	.12	74175	.67				
7411	.21	74176	.84				
7412	.21	74180	.86				
7413	.24	74190	1.04				
7417	.64	74192	.98				
7416	.26	74193	.98				
7417	.33	74194	.86				
7420	.12	74196	.86				
7426	.24	74197	.86				
7427	.24	74198	1.41				
7430	.12	74 LS TTL					
7432	.23	74LS00	.18				
7433	.50	74LS01	.18				
7437	.23	74LS02	.18				
7438	.23	74LS04	.19				
7440	.16	74LS06	.21				
7441	.50	74LS08	.21				
7442	.38	74LS09	.21				
7443	.85	74LS10	.21				
7445	.67	74LS11	.21				
7446	.67	74LS14	1.10				
7447	.59	74LS20	.18				
7448	.48	74LS21	.21				
7450	.16	74LS22	.24				
7451	.16	74LS27	.26				
7453	.16	74LS28	.29				
7454	.16	74LS40	.25				
7450	.16	74LS42	.54				
7470	.36	74LS51	.29				
7472	.32	74LS54	.32				
7473	.21	74LS86	.33				
7474	.26	74LS90	.66				
7475	.29	74LS93	.86				
7476	.31	74LS107	.34				
7483	.68	74LS112	1.00				
7485	.84	74LS123	.85				
7486	.25	74LS124	2.20				
7489	1.95	74LS151	.95				
7490	.38	74LS153	.64				
7491	.62	74LS157	.64				
7482	.42	74LS164	1.42				
7493	.29	74LS175	1.05				
7495	.51	74LS193	1.33				
7496	.67	74LS194	2.06				
74104	.48	74S TTL					
74105	.48	74S TTL					
74107	.27	74S04	.26				
74109	.45	74S05	.48				
74111	.29	74S12	.28				
74122	.47	74S08	.38				
74123	.38	74S10	.38				
74141	.71	74S11	.38				

IBEX SYSTEMS
32 Dunville Drive, Coventry CV2 2HS

THE SINCLAIR PDM35 digital Multimeter

Now a digital multimeter at an analogue price and look at the spec!

D.C. VOLTS 1mv-1000v(1% — 1 count) 10mΩ input.

A.C. VOLTS 1v-500v, 40Hz-5kHz (1% + 2 counts).

D.C. CURRENT 1 inA-200mA (1% count).

RESISTANCE 1Ω-20mΩ (1.5% + 1 count).

£29.80 cash with order or £30.95 company purchase order.
Adaptor £3.20. Padded case £3.20 30kV probe £18.64

THE SINCLAIR MICROVISION

The amazing pocket T.V. that will pick up programs throughout the world, complete with rechargeable batteries.

£189.95 inc. VAT
See (for detailed Brochure ex-stock)

SINCLAIR DM235

Portable 3 1/2 digit 6 function Multimeter
DC volts 1mV to 1000V
AC volts 1mV to 750V
AC & DC current 1μA to 1A
Resistance (Ω to 20MΩ)
Diode test 0.1μA to 1mA
10mΩ input. DC acc 1.0% AC acc 1.5% 30Hz-10kHz

Cash with order
£52.80 inc VAT or £53.70 on company purchase order

PORTABLE ALARM CLOCK

Only **£18.20** inc. P&P

- Battery operated
- Quartz crystal accuracy
- Back light
- Simple to set
- Electric Alarm
- Snooze button
- Colour Rinwn

CA-OBAL
Case E8 95 Adaptor E3 75

We accept govt / company purchase orders on all goods

KRAMER & CO

We will match any lower advertised price on a cash with order basis if competitor has goods in stock
9 October Place, Holders Hill Road, London NW14 1EJ
Tel: 888941 Attn. Kramer K7. Tel. 01-203 2473
Mail order only SAE for data sheets Export enquiries welcome

ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in **£2.50** with all symbols for direct application to P.C. board. Individual sheets 25p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Lead and 3 Lead and Pads (6) DILS (7) BENDS 90 and 130 (8) 8-10-12 T.O.5. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13). Quad in Line.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc. Choice of colours, red, blue, black, or white. Size of sheet 12in x 9in. Price **£1**.

GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours red, blue, black or white. Each sheet 12in. x 9in contains capitals, lower case and numerals 1/8in kit or 1/4in kit. **£1** complete. State size.

All orders dispatched promptly.
All post and VAT paid.
Ex U.K. add 50p for air mail
Shop and Trade enquiries welcome
Special Transfers made to order

E. R. NICHOLLS
P.C.B. TRANSFERS
Dept. HE/1
46 LOWFIELD ROAD
STOCKPORT, CHES.061-480 2179

**SECOND GENERATION
INDUCTION
BALANCE
METAL
DETECTOR**

**DESIGNED SPECIALLY
FOR THE HOME
CONSTRUCTOR**

**EASY
TO
BUILD**



**EASY
TO
USE**

- A second generation Induction Balance system with improved Variable-Tone detection.
- Designed by professionals for easy assembly by amateurs but with very good performance.

- The search coils are fully assembled and adjusted for you.
- Coils pre-assembled and tested wedge shaped search field

Uses include:

- ★ Treasure hunting — it's amazing what you can find in the garden or on the beach.
- ★ Finding lost metallic items.
- ★ Locating waterpipes and cables under floorboards or in walls.
- ★ Checking old timber for nails before cutting, etc., etc., etc.

KIT - COMPLETE WITH PRE-ASSEMBLED SEARCH COILS

£16.50

Plus £1-00p&p Plus £1-32 VAT

ASSEMBLED & TESTED

£22.50

Plus £1-00p&p Plus £1-80 VAT

Send see for free components stocklist

Communication Measurement Ltd
15 MALLINSON OVAL, HARROGATE, YORKS

Greenbank
Greenbank Electronics (Dept. T12E),
92 New Chester Road, New Ferry,
Wirral, Merseyside L62 5AG.
Tel: 051-645 3391.

CATALOGUE. Free on request (when available)
CWO. Add VAT to all prices at 8% except where
stated otherwise.

Post etc: UK 25p (+2p=27p) per
order. Export add 75p (Europe),
£2.50 elsewhere, no VAT. Polys,
universities, govt. depts., etc., can
telephone their orders for
immediate despatch.

TERMS

VAT

CMOS

These cut prices for Amateur Users and Export. Note: Industrial users —
quantity prices available.

Mostly Motorola, RCA

4000	15p	4051	72p	40109	£1.02	4512	81p
4001	17p	4052	72p	40181	£3.35p	4514	£2.85
4002	17p	4053	72p	40182	£1.40	4515	£2.95
4006	£1.05	4054	£1.10	40192	£1.40	4516	£1.08
4007	18p	4055	£1.20	40193	£1.40	4517	£3.82
4008	87p	4056	£1.34	40194	£1.18	4518	£1.02
4009	50p	4057	£25.70	40257	£1.48	4519	51p
4010	50p	4058	£4.80	4100	£1.00	4520	£1.08
4011	19p	4059	£1.15	4101	£1.08	4521	£1.08
4012	18p	4061	£15.67	4152	£1.08	4522	£1.08
4013	42p	4062T	£10.00	4153	£1.08	4524	N/S
4014	86p	4063	£1.09	4174	£1.08	4526	£1.08
4015	89p	4064	N/S	4175	99p	4527	£1.52
4016	45p	4065	N/S	4194	£1.08	4529	99p
4017	89p	4066	57p	4408	£8.59	4529	£1.50
4018	89p	4067	£3.80	4409	£6.59	4530	85p
4019	48p	4068	22p	4410	£5.73	4531	£1.45
4020	99p	4069	20p	4411	£9.58	4532	£1.27
4021	91p	4070	23p	4412V	£17.14	4534	£5.13
4022	86p	4071	21p	4412FL	£12.92	4536	£3.69
4023	79p	4072	21p	4413V	£7.50	4537L	£13.23
4024	66p	4073	21p	4415F	N/S	4538	£1.25
4025	19p	4075	23p	4419	£2.68	4539	91p
4026	£1.80	4076	85p	4422	£5.00	4541	£1.14
4027	45p	4077	23p	4431	TBA	4543	£1.59
4028	40p	4078	21p	4433	£11.32	4549	£3.69
4029	99p	4081	20p	4435	£7.93	4552	£3.05
4030	58p	4082	21p	4440L	£11.58	4553	£3.87
4031	£2.05	4085	74p	4450	£2.67	4554	£1.19
4032	£1.00	4088	73p	4451	£2.67	4555	78p
4033	£1.45	4089	£1.50	4452	TBA	4556	78p
4034	£1.96	4093	65p	4461	£2.19	4557	£3.08
4035	£1.11	4094	£1.50	4462	£2.42	4558	£1.14
4036	£2.45	4096	£1.05	4490F	£6.54	4559	£3.69
4037	£1.00	4096	£1.05	4490P	£4.92	4560	£1.84
4038	£1.00	4097	£3.72	4700	£1.75	4561	65p
4039	£2.45	4098	£1.10	4500	£5.56	4562	£5.33
4040	£1.05	4099	£1.45	4501	17p	4566	98p
4041	80p	4066I	N/S	4502	91p	4568	£2.38
4042	75p	40100	£2.50	4503	69p	4569	£2.57
4043	84p	40101	£1.61	4505	£5.71	4572	25p
4044	90p	40102	£2.12	4506	£5.74	4574	£5.00
4045	£1.45	40103	£2.12	4507	59p	4581	£2.62
4046	£1.28	40104	£1.09	4508	£2.48	4582	98p
4047	87p	40105	£1.06	4510	99p	4583	76p
4048	58p	40106	61p	4511	£1.38	4584	43p
4049	48p	40107	88p			4585	£1.01
4050	48p	40108	£5.36			4599	£2.06

74C

74C00	24p	74C90	£4.38	74C193	£1.10	74C918	£1.06
74C02	24p	74C90	85p	74C195	£1.04	74C921	£1.83
74C04	24p	74C93	85p	74C200	£6.78	74C922	£3.66
74C06	24p	74C95	£1.04	74C221	£1.36	74C923	£3.73
74C08	24p	74C107	£1.22	74C233	£1.73	74C924	TBA
74C10	24p	74C150	£4.12	74C301	54p	74C925	£4.84
74C12	24p	74C151	£2.46	74C302	54p	74C926	£4.84
74C14	£1.41	74C154	£3.67	74C303	54p	74C927	£4.84
74C20	24p	74C157	£2.20	74C304	54p	74C928	£4.84
74C30	24p	74C160	£1.10	74C305	£7.26	74C929	£11.83
74C32	24p	74C161	£1.10	74C306	54p	74C948	TBA
74C34	24p	74C162	£1.10	74C307	54p	80C95	54p
74C38	£1.38	74C163	£1.10	74C308	96p	80C96	61p
74C73	54p	74C164	£1.04	74C309	£1.63	80C97	54p
74C74	56p	74C165	£1.04	74C310	£6.78	80C98	61p
74C76	54p	74C173	98p	74C311	TBA	80C19	£1.13
74C83	£1.29	74C174	£1.51	74C312	£7.13	88C29	61p
74C85	£1.29	74C177	98p	74C314	£1.41	88C30	£1.93
74C86	64p	74C192	£1.10	74C315	£1.10		

DATA

Note: In this section all data books are subject to
0% VAT. For postage see 'Terms' at top of page.

c650 page COSMOS Databook (RCA)	£4.95
c200 page CMOS Databook (Motorola)	£3.50
CMOS Databook (National)	£2.30
MC 145000 ICU Handbook (Motorola)	£1.50
Understanding Microprocessors (Motorola)	£2.75
M8000 Microprocessor Applications Manual (Motorola)	£9.95
A Guide to SC/MP Programming (Kamitar)	£3.50
SC/MP Technical Description (National)	£2.78
SC/MP Microprocessor Applications Handbook (National)	£3.45
SC/MP Programming + Assembler Manual (National)	£3.00
NBL Reference Manual (National)	£3.45
16-page data for IMS B154 (ISP-BA/650) (National)	50p
20-page data for SC/MP II (National)	50p
CP 1802 MPU User Manual (RCA)	£4.50
CP 1802 Subroutines (RCA)	£4.50
COSMAC MPU Guide (National)	75p

SPECIAL: 280 DATA PACK £13.95
A set of the following 5 280 data manuals and all the
related data we can find of interest to the 280 user.
c90-page 280 CPU Technical Manual
c10-page 280-CTC Product Specification
c25-page 280-P10 Technical Manual
c20-page 280 Programming Manual
c25-page 280 Micro Reference Manual

Memory Data Book (National)	£2.30
Interface Data Book (National)	£2.30
Special Functions Data Book (National)	£2.00
MOS/LSI Data Book (National)	£2.40
Data Acquisition Handbook (National)	£2.00
Memory Applications Handbook (National)	£2.00

MICROPROCESSORS

6802	£9.95
80C	£9.50
280A (4 MHz)	£13.95
280A (4 MHz)	£17.95

COMPUTER KITS
(Check stock before ordering)
Science of Cambridge MK 14
MASCOW 1 £39.95
MASCOW 1 £197.50

MPU I/O
AY-5 1013 UART £4.41
AY-3 1015 £5.60
INS 8154 RAM I/O £7.50
6820 P10 £4.25
6821 P10 £4.25
6850 A/D £7.17
280 CTC £7.95
280 P10 £7.95
81LS 85/6/7/8 £1.25

ROM SOFTWARE
[FIRMWARE]
MC 6807 (Mk-80) £13.70
5204 (M.S. Kit-80) £14.95

ROM CHARACTER GENERATORS
MCM 6571/6576 £6.71
MCM 6670 £9.75
MK 5829 46p £15.20
RO-3-13 £5.50
DM 8678 CAB/DM 8678 BWF £12.95

MPU CHIPS
COSMAC 1802 £13.95
SC/MP II (4MHz) £7.95
8080 £7.95
14500 TCU £5.56
6800 £5.95

FANCY A NIBL?

Add this superior version of
'TINY BASIC' to SC/MP II
and make your computer
INTELLIGENT! Available in
two versions with 4K or 16K
15P-8F/351 (8 x 5204/
5214 ROMs) £50.25
15P-8F/352 (2 x 2316A
ROMs) £46.90
(Prices include books!)

**NEW! VDU-From-TV
CHIP**

Thompson CSF TV-CAT
controller (16 lines by 64
characters)
SF-F96546 £11.75
(The ideal companion to NBL
firmware, to turn your TV
into a Personal Computer!)

UV Erasable EPROMs
2284 (512x8) £7.50
2708 (1Kx8) £7.95
2716 (2Kx8) £25.00
68708 (1Kx8) £9.25
EPROM (not erasable)
MC2708P £7.78

74LS

74LS00	18p	74LS27	28p	74LS76	40p	74LS125	60p	74LS164	£1.14	74LS241	£2.32	74LS293	£1.28	74LS379	£2.15
74LS01	18p	74LS28	43p	74LS78	40p	74LS126	60p	74LS165	75p	74LS242	£2.32	74LS295	£1.85	74LS384	86p
74LS02	20p	74LS30	22p	74LS83	£1.15	74LS132	95p	74LS166	£2.26	74LS243	£2.32	74LS298	£1.68	74LS386	86p
74LS03	20p	74LS32	27p	74LS85	£1.18	74LS136	95p	74LS170	£2.88	74LS244	£2.70	74LS324	£2.40	74LS390	£2.30
74LS04	20p	74LS33	39p	74LS86	£1.16	74LS138	85p	74LS171	£1.05	74LS247	£1.90	74LS325	£2.90	74LS393	£2.30
74LS05	20p	74LS37	39p	74LS90	60p	74LS139	85p	74LS174	£1.06	74LS248	£1.90	74LS326	£2.94	74LS395	£1.88
74LS06	20p	74LS40	39p	74LS91	£1.04	74LS145	£1.08	74LS175	£1.08	74LS249	£1.90	74LS327	£2.86	74LS396	£2.15
74LS10	23p	74LS42	28p	74LS92	89p	74LS147	£1.70	74LS181	£1.30	74LS251	£1.34	74LS347	£1.48	74LS398	£2.76
74LS16	22p	74LS44	98p	74LS93	89p	74LS148	£1.73	74LS183	£2.98	74LS253	£1.42	74LS348	£1.86	74LS399	£2.90
74LS19	22p	74LS47	98p	74LS96	£1.16	74LS151	96p	74LS190	£1.40	74LS257	£1.10	74LS352	£2.28	74LS445	£1.30
74LS20	20p	74LS48	£1.20	74LS98	£1.16	74LS153	76p	74LS191	£1.40	74LS258	£1.46	74LS355	£2.90	74LS447	£1.44
74LS21	22p	74LS49	£1.20	74LS107	44p	74LS155	96p	74LS192	£1.30	74LS259	£1.60	74LS365	65p	74LS490	£1.81
74LS22	23p	74LS51	24p	74LS109	55p	74LS156	96p	74LS193	£1.30	74LS261	£4.50	74LS367	65p	74LS568	£1.82
74LS23	23p	74LS54	20p	74LS112	55p	74LS157	76p	74LS194	£1.66	74LS266	52p	74LS368	65p	74LS669	£1.48
74LS24	38p	74LS55	30p	74LS113	50p	74LS158	96p	74LS195	£1.36	74LS273	£2.44	74LS376	66p	74LS760	£2.82
74LS25	30p	74LS56	£1.50	74LS114	45p	74LS160	£1.28	74LS196	£1.00	74LS275	£2.50	74LS377	£1.80		
74LS26	20p	74LS57	46p	74LS122	70p	74LS161	96p	74LS197	£1.40	74LS279	46p	74LS379	66p		
74LS27	22p	74LS74	41p	74LS123	70p	74LS162	£1.38	74LS221	96p	74LS283	£1.92	74LS379	66p		
74LS28	48p	74LS75	48p	74LS124	£1.80	74LS163	£1.18	74LS240	£2.3	74LS290	£1.28	74LS378	£1.84		

microfile.....

Gary Evans has been out and about this month, taking in a Personal Computer show and visiting a TV studio amongst other things.

THE NUMBER OF shows/seminars concerning themselves with many aspects of Microprocessors and personal computers has, like the hardware itself, shown a dramatic increase over the past few years. Unfortunately not all these events live up to their initial promise and some are not worth the cost of travelling to the venue, let alone the extortionate prices charged for admission to some of these gatherings. The PCW show towards the end of September was a refreshing change.

When it comes to exhibitions, about the only thing to do is to get as many people with products likely to be of interest to visitors to set up a stall. If you can arrange to have some new products launched, a competition and some interesting activity going on in the sidelines — all well and good. PCW did just this and it worked.

I'd have liked to have gone to all three days of the show in order to attend the various seminars held — as it was, last month's ETI was printed at the same time as the show and I was only able to get to the exhibition on the Saturday morning. I suspect the seminars were up to the general high standard of the rest of the event however.

The fact that the exhibition was crowded when I was there, it took me all my time trying to get from one stall to another amongst the multitude of people who see their role in life as standing in the middle of gangways, is not a criticism, more a testament to the show's success.

I look forward to more shows along these lines in the future.

Anita Harris — Pet?

A couple of months ago I went to the recording of a TV show pilot where one of the stars of the show, along with Anita Harris and Roger Elliott, was a Pet Computer.

I'll say more about the show but may I just digress for a couple of lines to tell one of the few after dinner stories I know — this desire having been brought on by the mention of the word pilot above.

If you do certain jobs, being a pilot or trendy journalist are amongst them, when at parties that information is dragged out of you the same string of inevitable questions pour out — different questions for different jobs — but the same questions for the same jobs — if you know what I mean. Very boring. Well, my story concerns a pilot who, being fed up with the situation, in response to the next such interrogation replied "I travel in aluminium tubing" — that at least proved no questions. That's the story then — not very exciting but it's the way I tell 'em

Back to the PET and the TV show however and to why the PET was there. One of the computer's co-stars may have given some of you a clue. Roger Elliott is the TV Times astrologer and — slight groan — the PET was put to the task of flashing Anita's details (astrological) over it's screen.

They say that an actor should never go on stage with animals or small children, for fear of being upstaged. To this list, although for a different reason, should be added small computers. The reason is they very rarely behave for any length of time as Roger Elliott found out when the PET started promising that it was "Time for a song" when Anita obviously was ready for no such thing.

The program was made by HTV who's main claim to fame, or is it eternal damnation, in my book to date is that they produce Mr and Mrs. While not in that league — the pilot was much better — I did not enjoy the show that much but the production team seemed to think it was OK so maybe you'll see it on your screens at some time in the future.

I can't resist just one more tilt at Mr and Mrs — it appears that four of these dreadful things are reeled off in the same day — not all in front of the same audience, who could stand the strain?, especially when you consider that the people who have parted with their hard earned time to watch this entertainment are in the main, old age pensioners, who should really be taking things easier at their age.

I mustn't be too unkind to Mr and Mrs though, after all there is Nicholas Parsons.

Pet Problems

When Julian Allason of PETSOFTE phoned this month to ask if I had any problems I was just about to mention the fact that my car had just fallen to bits, and that my dog had a limp amongst other things when he explained that he was merely reading from the screen of PET which was running a new program called Eliza. Eliza simulates a consultation with a psychiatrist and my encounter with the machine went something like this.

PET What is your problem?
 ME Emotional insecurity
 PET Do you have any psychiatric problems?
 ME Yes
 PET Are you sure?
 ME Yes
 PET: Do not repeat yourself.
 ME Oh God!
 PET What does that suggest to you?
 ME I'm not sure
 PET: Did you come to be because you're not sure?
 ME Yes
 PET: I see
 ME Where do we go from here?
 PET: Why do you ask?
 ME Because I'm not sure
 PET How long have you been not sure?
 ME Five years
 PET: I see

Well, follow that — Petsoft have probably the widest range of PET software in this country with 70 titles in their current catalogue and aims for 100 in the next. A reciprocal arrangement with Personal Software Inc, whereby Petsoft material will be distributed in the United States and Canada and the best of Personal Software's material sold over here means even more to choose from.—If you have a PET, Petsoft are worth knowing.

PETSOFT,
P.O. BOX 9,
NEWBURY,
BERKSHIRE, RG13 1PB.

Put A Chrysler Sidelight In Your Life

I've been exposing myself this month, but before you get the wrong idea — although I suspect most of you already have, I mean to say that I've been out and about talking to computer clubs.

The meetings ranged in size from the 400 or so at the first meeting of the North London Computer Club,

through a 100 or so at Sussex University to the twenty or so at the Thames Valley group of the ACC's meeting. I enjoyed myself at each event, and picked up some very good ideas from the very high calibre of people that numbered among the audience at each event. Among the handy things I learn't at Sussex was that the exact sequence of operations required to turn the sidelights of a Chrysler Sunbeam on this could not be discovered by your humble reporter, a number of undergraduates and a lecturer in mathematics, but had to be resolved by a call to the car hire firm.

All the clubs would welcome new members — The North London Computing Club is held at the North London Polytechnic, Holloway, LONDON N7 8DB. Tel. Stephanie Bromley — 01-607 8663 (Office), 01-359 2282 (Home), or Mike O'Reilly, — 01-607 2789 ext 2100.

The Thames Valley ACC group meets on the first Thursday of every month at the Griffin (A pub—good move ACC) 10 Church Road, Caversham, Reading, Berkshire.








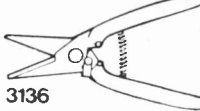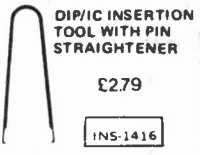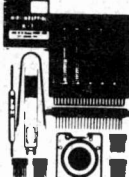
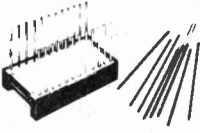

For the Sussex University Group — who will welcome outsiders to their meeting with open arms and hands, for the money you know — Contact. Pete Guile, University of Sussex, Falmer, BRIGHTON, Sussex.

ET

ok

WIRE WRAPPING CENTRE

ok

<p>HOBBY WRAP Model BW 630</p>  <p>Battery Wire-Wrapping Tool Complete with Bit and Sleeve</p> <p>NEW</p> <p>£26.75 B£31.95 C£2.82 D£7.44</p>	<p>WIRE-WRAPPING TOOL For .025" (0.63mm) sq post "MODIFIED" wrap, positive indexing, anti-overwrapping device</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>A Bit for AWG 30</td> <td>BW-630</td> </tr> <tr> <td>B Bit for AWG 26-28</td> <td>BW-2628</td> </tr> <tr> <td>C Bit for AWG 30</td> <td>BT-30</td> </tr> <tr> <td>D Bit for AWG 26-28</td> <td>BT-2628</td> </tr> </table>	A Bit for AWG 30	BW-630	B Bit for AWG 26-28	BW-2628	C Bit for AWG 30	BT-30	D Bit for AWG 26-28	BT-2628	 <p>3 IN 1 WIRE DISPENSER New wire dispenser cuts and strips three different colours of wire. Quick and easy to use pocket size. Wire Size: 30 AWG. 50 ft. Red, Blue, White Kynar insulated.</p> <p>£4.07</p>	<p>OK PLIERS AND CUTTERS UNIVERSAL CUTTER Cuts everything. Leather, wire, plastic, tin-plate, cardboard. Stainless steel blades. Just one of the range of high quality pliers, cutters, tweezers and screwdrivers.</p>  <p>3136 £3.46</p>				
A Bit for AWG 30	BW-630														
B Bit for AWG 26-28	BW-2628														
C Bit for AWG 30	BT-30														
D Bit for AWG 26-28	BT-2628														
<p>DIP/IC EXTRACTOR TOOL £1.19 The EX-1 Extractor is ideally suited for hobby enthusiast or lab engineer. Featuring one piece spring steel construction. It will extract all LSI, MSI and SSI devices of from 8 to 24 pins. Extractor Tool EX-1.</p>  <p>INS-1416 £2.79</p>	<p>DIP/IC INSERTION TOOL WITH PIN STRAIGHTENER INS-1416 £2.79</p> 	<p>WIRE-WRAPPING KIT Contains: Hobby Wrap Tool WSU-30 M, Wire Dispenser WD-30-B, (2) 14 DIP's, (2) 16 DIP's, Hobby Board H-PCB-1, DIP/IC Insertion Tool INS-1416 and DIP/IC Extractor Tool EX-1.</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>Wire-Wrapping Kit</td> <td>WK-4B (Blue)</td> </tr> </table> <p>£19.22</p>	Wire-Wrapping Kit	WK-4B (Blue)	<p>IC TEST CLIPS £2.97 FOR DUAL-IN-LINE PACKAGES</p> <ul style="list-style-type: none"> • Provide full access to integrated circuit DIP leads. • Remove DIP's damage free. • Simplify prototype and production testing, field service work, and quality control. • Available in sizes to accommodate all DIP's; TC-14 fits 14-pin DIP's etc. 										
Wire-Wrapping Kit	WK-4B (Blue)														
<p>FROM 80P TERMINAL AND DISTRIBUTION STRIPS Bread boarding building blocks with universal matrices of solderless plug-in tiepoints.</p> <ul style="list-style-type: none"> • Facilitate quick, solderless circuit build-up and check-out on universal .1" x .1" matrix. • Are offered in ten configurations. • Accept all components with leads up to .032" diameter. • Require no special patch cords. • Includes integral non-shorting instant mounting backing. 		<p>HOBBY WRAP TOOL Wire-wrapping, stripping, unwrapping tool for AWG 30 on .025 (0.63mm) Square Post.</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>Regular Wrap</td> <td>A</td> <td>WSU-30</td> </tr> <tr> <td>Modified Wrap</td> <td>B</td> <td>WSU-30M</td> </tr> </table> <p>A £4.74. B £5.07</p> 	Regular Wrap	A	WSU-30	Modified Wrap	B	WSU-30M	<p>DIP SOCKET Dual-in-line package, 3 level wire-wrapping, phosphor bronze contact, tin-plate finish pins .025 (0.63mm) sq., .100 (2.54mm) centre spacing.</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>14 Pin Dip Socket</td> <td>14 Dip</td> </tr> <tr> <td>16 Pin Dip Socket</td> <td>16 Dip</td> </tr> </table> <p>FROM 29p</p> 	14 Pin Dip Socket	14 Dip	16 Pin Dip Socket	16 Dip		
Regular Wrap	A	WSU-30													
Modified Wrap	B	WSU-30M													
14 Pin Dip Socket	14 Dip														
16 Pin Dip Socket	16 Dip														
<p>RIBBON CABLE ASSEMBLY £2.92</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>With 14 Pin Dip Plug - 2" Long</td> <td>DE 14-2</td> </tr> <tr> <td>With 14 Pin Dip Plug - 4" Long</td> <td>DE 14-4</td> </tr> <tr> <td>With 14 Pin Dip Plug - 8" Long</td> <td>DE 14-8</td> </tr> <tr> <td>With 16 Pin Dip Plug - 2" Long</td> <td>DE 16-2</td> </tr> <tr> <td>With 16 Pin Dip Plug - 4" Long</td> <td>DE 16-4</td> </tr> <tr> <td>With 16 Pin Dip Plug - 8" Long</td> <td>DE 16-8</td> </tr> </table> 		With 14 Pin Dip Plug - 2" Long	DE 14-2	With 14 Pin Dip Plug - 4" Long	DE 14-4	With 14 Pin Dip Plug - 8" Long	DE 14-8	With 16 Pin Dip Plug - 2" Long	DE 16-2	With 16 Pin Dip Plug - 4" Long	DE 16-4	With 16 Pin Dip Plug - 8" Long	DE 16-8	<p>OK Machine & Tool U.K. Limited 48a The Avenue Southampton SO12SY Telephone Southampton (0703) 38966 7 Telex 477222 Cablegram OKMAC</p> <p style="text-align: center; font-size: 1.5em; font-weight: bold;">DISTRIBUTORS WANTED***</p>	
With 14 Pin Dip Plug - 2" Long	DE 14-2														
With 14 Pin Dip Plug - 4" Long	DE 14-4														
With 14 Pin Dip Plug - 8" Long	DE 14-8														
With 16 Pin Dip Plug - 2" Long	DE 16-2														
With 16 Pin Dip Plug - 4" Long	DE 16-4														
With 16 Pin Dip Plug - 8" Long	DE 16-8														

See us at
BREAD BOARD '78
21st-25th November.
Seymour Hall, London
Stand Nos. A5-A6

ETI PROJECT

'TOLINKA' CHESS REPORTER — FULL KIT OF PARTS

The original unit used in conjunction with the World Chess Championship at Manila, August to October, 1978, by both Chess Champion Viktor Korchnoi and BBC TV news.

Records every game step, auto en passant, queening and castling. Entire games may be recorded on most domestic cassette recorders. Based on 8060 Mk II Scamp. Full kit including all components — No extras required — **£109.50***



MICRO-PROCESSOR GAMES

A COMPLETE RANGE OF ROM PROGRAMMABLE GAMES

**AS SEEN
ON TV AND
NATIONAL
PRESS**

ATARI VIDEO COMPUTER

with big range of Cartridges
7 currently available

plus
NEW cartridges.
Available November



INTERTON VC4000


(based on Signetics micro) complete with joystick/keypad controls and mains adaptor. Cartridge extra. Multicolour (on colour TVs) with TV sound.

Cartridges — (1) Car Races (2) Blackjack (3) Paddle Games (4) Tank / Air Battle

**ONLY
£109.95
CARTRIDGES
£13.95**

EACA VIDEO PROGRAMMABLE SYSTEM

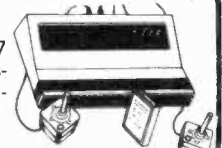Comes complete with 27 Game combat cartridge, joystick controls and mains adaptor.



**ONLY
£99.95**

New cartridges to follow


Full details on request

**FREE
FITTED
SOUND
MODULATOR**

'MERCURY COMMANDER' READY BUILT ECONOMY CARTRIDGE SYSTEM (G.I. DEDICATED CHIPS)

Designed and built in Britain by Teleng, one of Europe's largest TV Games manufacturers.

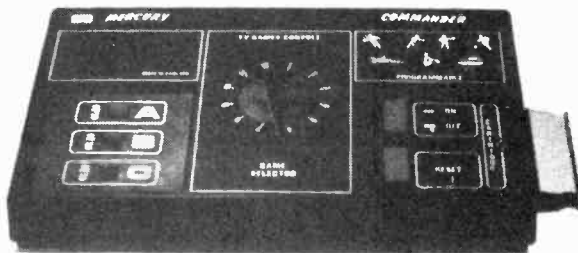Mercury Commander — Complete with 10 Game Cartridge, 2 joysticks. Mains adaptor — in colour with Videotime TV Sound — No Additional Costs **£39.95***



Plus additional cartridges

Stunt Rider with hand control, 4 games **£16.90***

Road Race 2 games **£10.90***

Tank Battles with 2 joystick controls **£21.90***

More to follow . . . Submarine & Spacewar, Wipeout & Breakthrough, Shooting Gallery.

Game / Aerial Switch Box **£3.95***



BARGAIN TV GAMES KITS AND COMPONENTS



Stand Alone Kits

Kits — full instructions, all PCB components. **Mini-kits** — instructions, chip, skt, coil, PCB.

	kits	minikits
B&W Tank Battle (AY-3-8710)	£15.90	£9.75
B&W Stunt Rider (AY-3-8765)	£15.90	£9.95
B&W Road Race (AY-3-8603)	£14.90	£8.50
B&W 10 Game B/B (AY-3-8610)	£13.90	£8.50
B&W Submarine/Spacewar (AY-3-8605)	TBA	TBA
NEW B&W Wipeout/Breakout (AY-3-8606)	£14.90	£8.50

Astec Modulators & Encoders

UM1263 Sound Osc	£1.95
UM1111 E36 UHF Mod	£1.95
UM1233 UHF (high quality)	£4.95
UM1168 Pal Encoder	£2.50
UM1163 Pal Enc + UHF Mod	£4.95

European Equivalents available

NEW Astec Switched Mode Power Supplies

AC9221S 5 volt 5 amp	} details on application
AC5201S 5 volt 10 amp	

Accessories

AB Joystick controls 200k lin	£1.95
Crystal 4.4 Mhz	£1.00
Crystal 3.57 Mhz	£1.25
Oscillator coil 100µH	£0.45
Mains adaptor + 150mA 8v reg i/c	£3.50

* Prices include VAT, packing & delivery charges and money back guarantee. Send cheque or P.O. to


VIDEOTIME PRODUCTS 56 Queens Road, Basingstoke, Hants RG21 1REA
Tel: (0256) 56417. Telex: 858747.

(Trade & Export Enquiries welcome)



AUTOCHORD

PART TWO

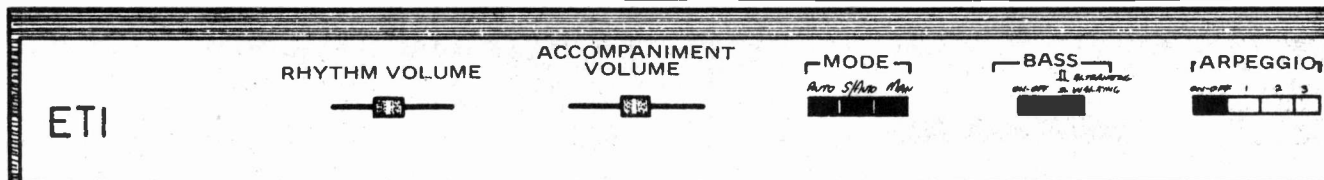

THIS MONTH WE complete the description of the auto chord instrument. Last month's article covered the circuit descriptions of the various blocks that make up the unit and of the operation of the complete design.

This month we complete the project by describing the construction of the instrument.

Construction


The components should be mounted on the PCBs according to the overlays shown. Pay particular attention to the diodes, capacitors and other polarity sensitive devices.

The project involves a great deal of interwiring between the various boards and switches of the design.


The interconnections are shown in the accompanying diagrams and great care should be taken to ensure that no errors are made at this stage — they will prove difficult to trace at this stage.

We give no details of the housing of the project as this will depend entirely upon the instrument in which the auto chord is to be installed.

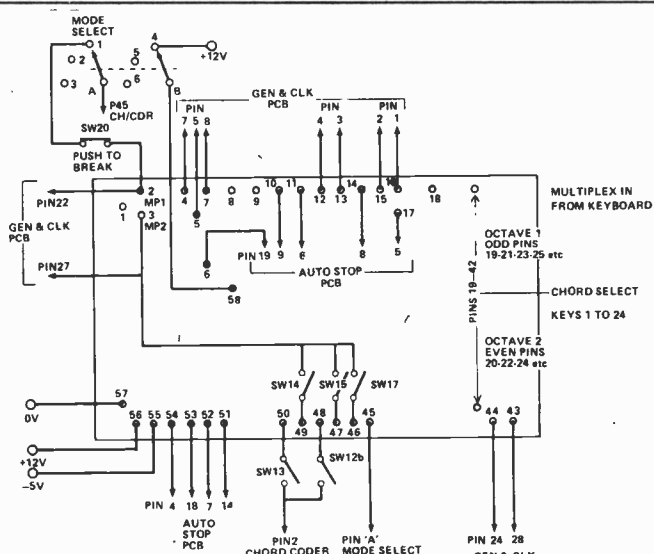The finished unit can be added to most organs, being easiest to fit to a unit that uses DC keying. In use the project should add an extra dimension to even the most limited of musicians efforts.



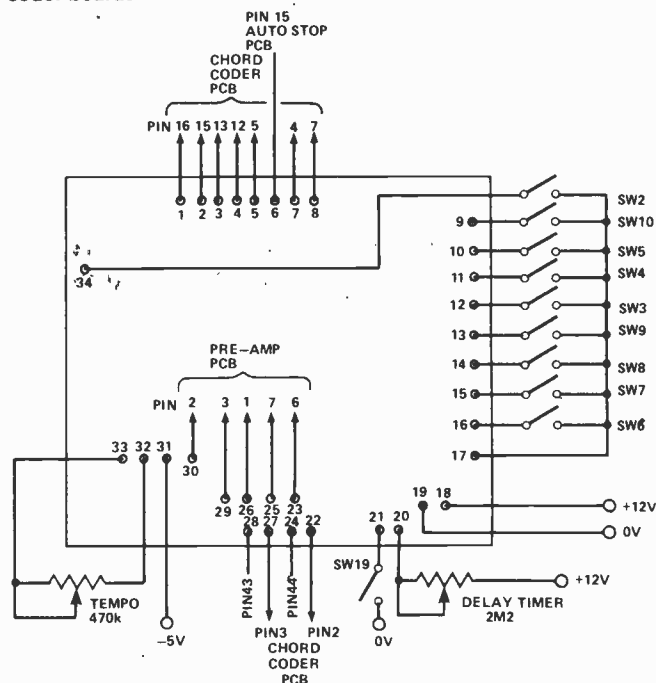Above and below interconnection details for the generator and coder boards



Part two of the autochord project details the construction of the instrument

Maplin
Electronic Components
1000 High Street, London W15 7PN
Tel: 01-899 6909


RHYTHM SELECT
Auto Stop Timer
Auto Stop Timer

AUTO STOP TIMER
Auto Stop Timer


Auto Stop Timer
Auto Stop Timer

Auto Stop Timer
Auto Stop Timer

Auto
Organ


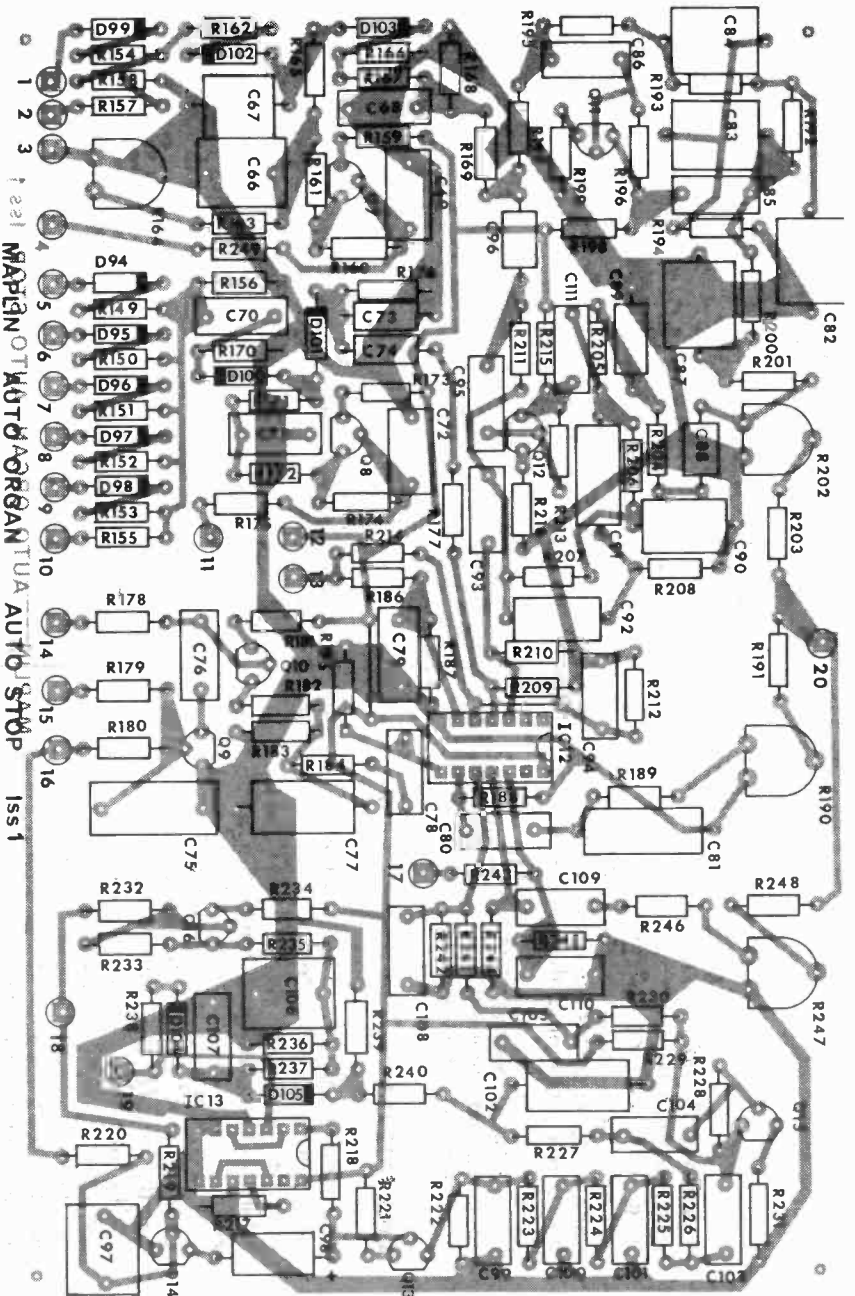


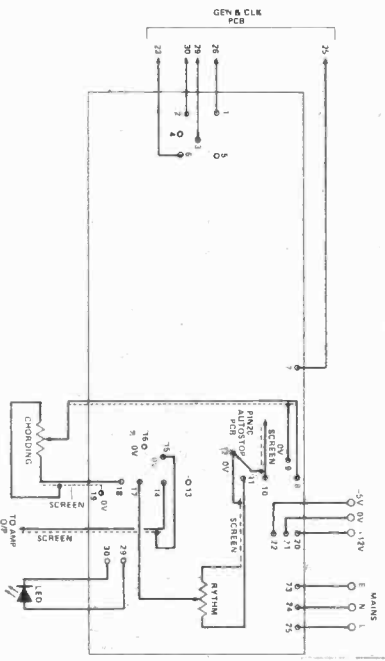Power supply and voice generator connection details





Maplin Electronics will supply a complete kit of parts, including screened boards, for this project. See their advert for address and telephone number.

BYLINES

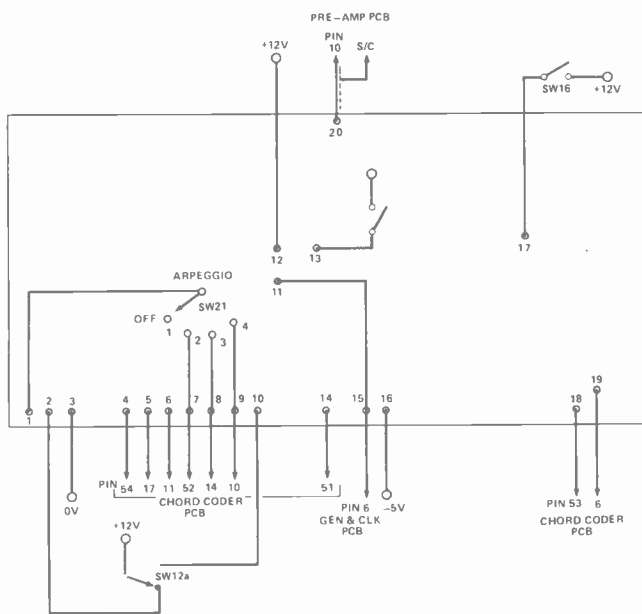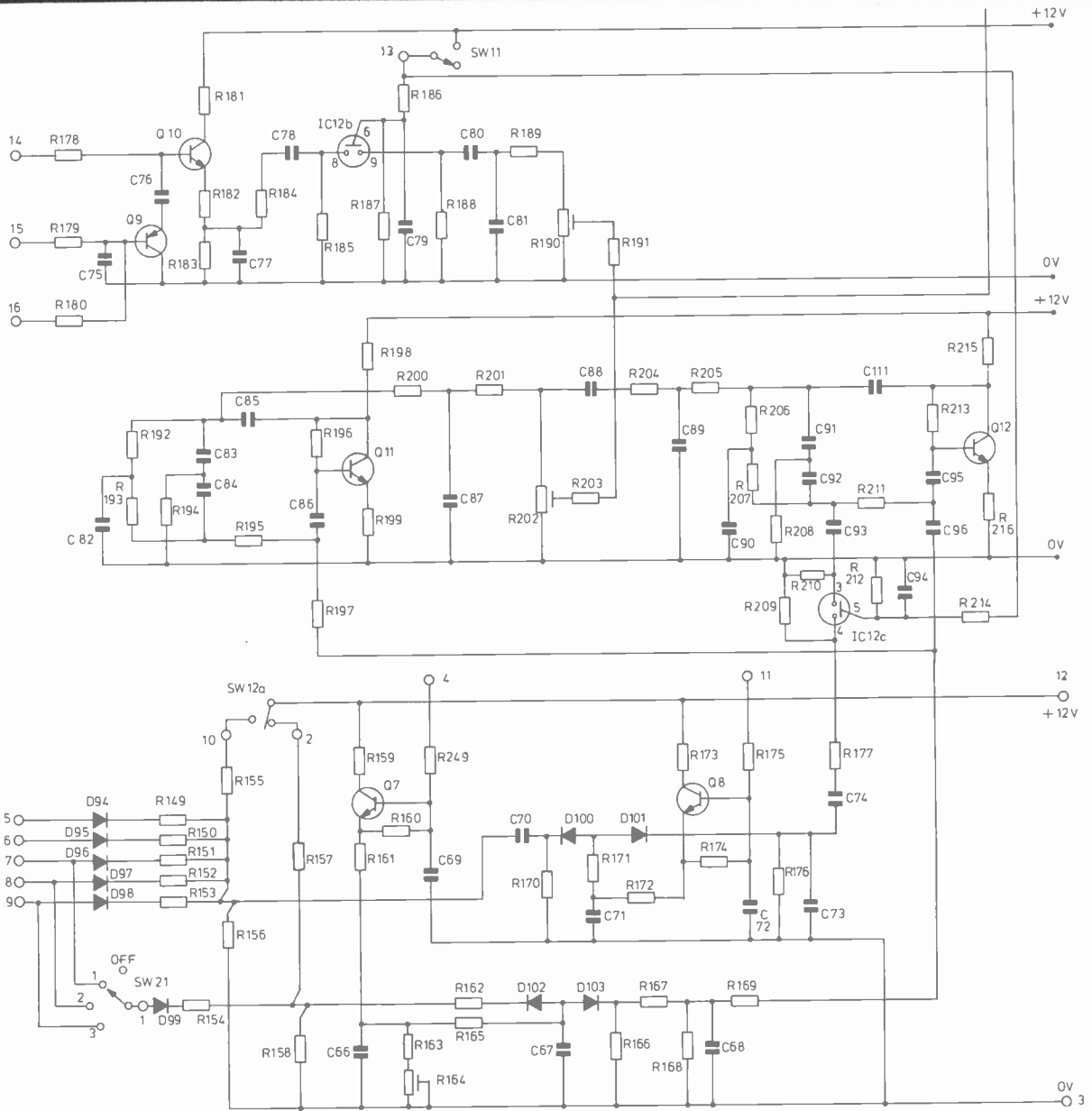


KEYING ARRANGEMENTS


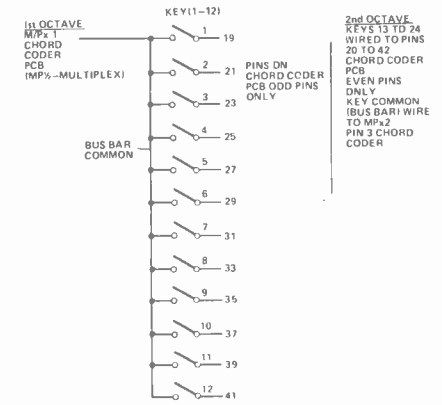


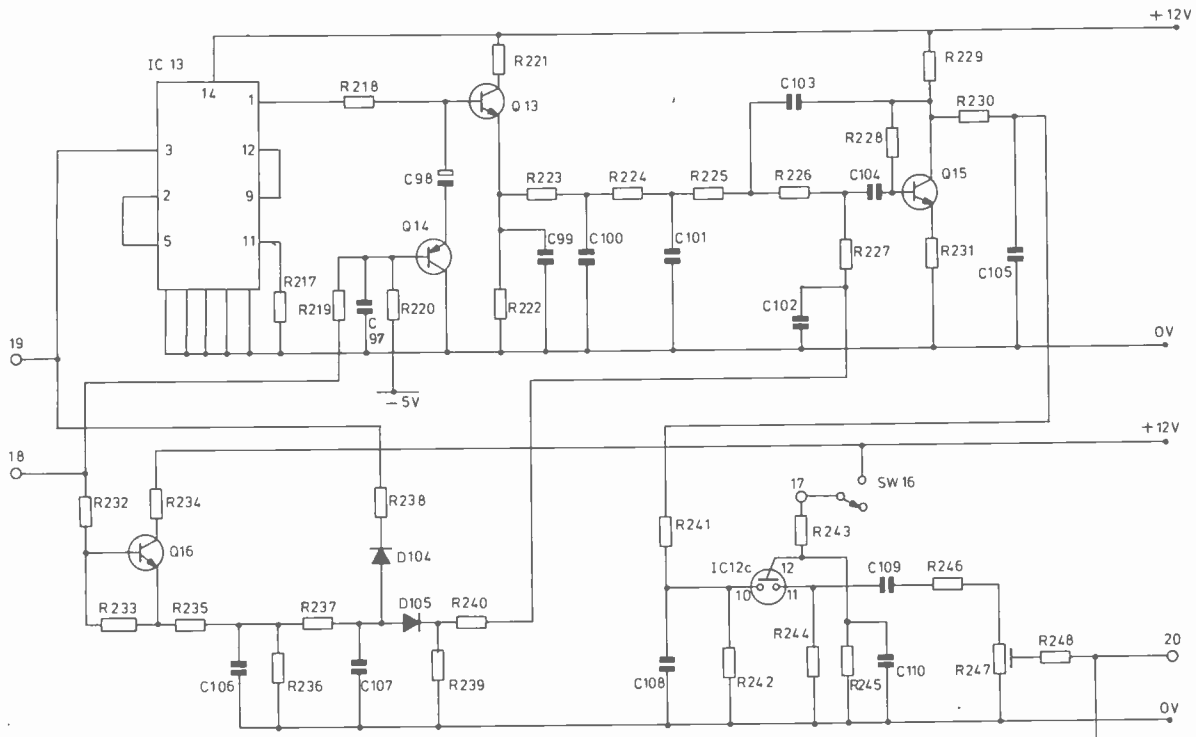

Above, and to the left, circuit diagram of the auto stop module

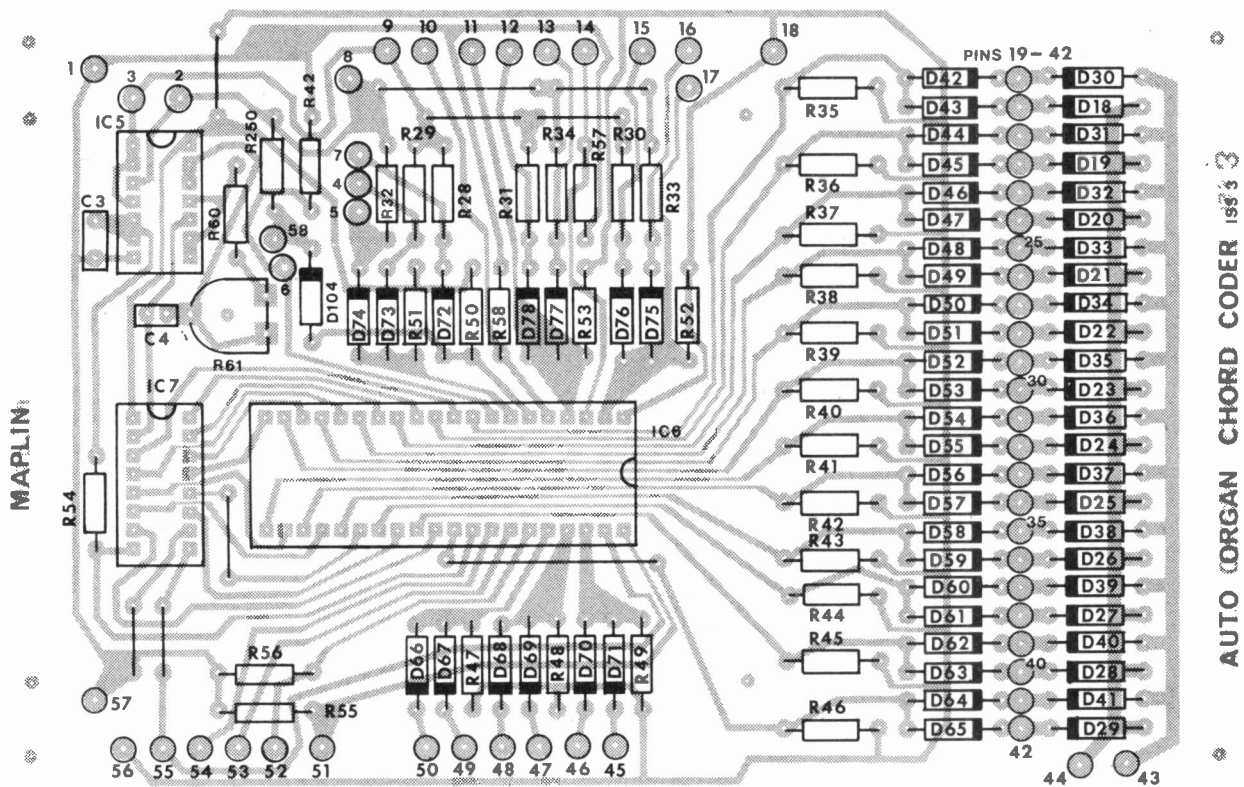The overlay for the chord coder is shown below take care that all the diodes are inserted in the right position.



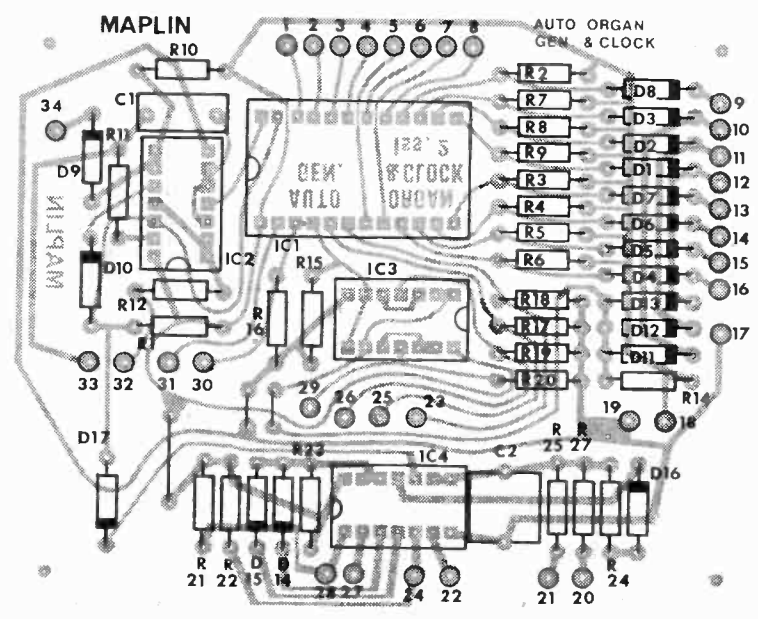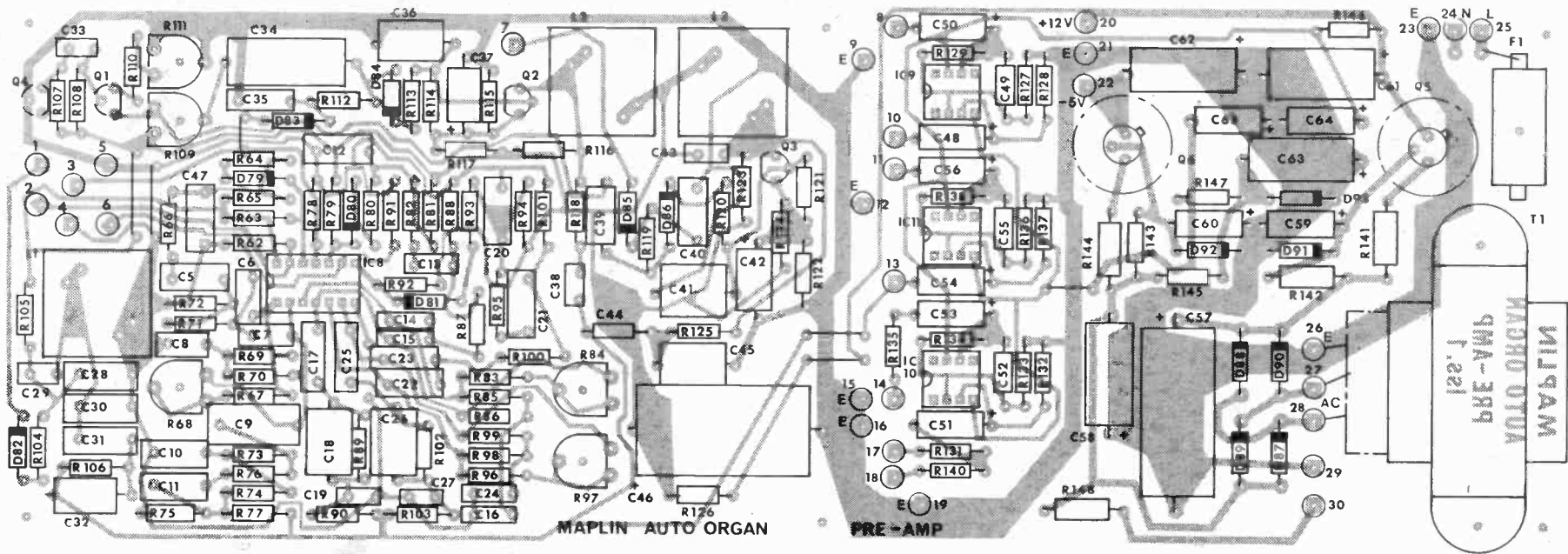

Above the power supply and pre-amp board of the auto organ. The interconnections between this and the rest of the boards are shown in the accompanying drawings.

Left is the overlay for the generator and clock section of the auto organ.

SEIKO 20% OFF!

Analogue and digital from stock or to order.

NEW

FX003 MEMORY BANK



"STAR" of the 1979 Seiko range, available NOW from Tempus. Continuous display of hours, minutes, seconds, day, date, month. Displays past and future calendars from 1930 to 2009.

Flashing reminder for important dates in the coming 12 months.

R.R.P. £130

£104



NEW FB011
R.R.P. £135

£104



FK009
R.R.P. £55

£44



NEW FH003
R.R.P. £165

£125

BORIS Communicating Chess Computer. One of the world's most advanced portable chess games. NO TV required.

£195

CASIO FREE! Spare batteries worth up to £1.95 with calculators below. (On request with order)

NEW

QL-10 CIGARETTE LIGHTER/CALCULATING ALARM CLOCK



Soft piezoelectric system gas lighter. 6-digit LCD clock, ± 15 seconds/month. Permanently prog. calendar (1901-2099). Two alarms plus countdown alarm/timer. Dual time zone. Calculator, with time/date calculations. K, %, $\frac{1}{2}$ x $2\frac{3}{4}$ x 4 inches. 3.6oz. 18 months battery. Pouch.

Prov. price **£39.95**

(RONSON electronic lighters, 10% off)

AQ-1000 CALCULATING ALARM CLOCK PLUS 3-WAY STOPWATCH

Hours, minutes, seconds, am/pm. 24 hour Alarm with sign. Stopwatch: Net times, lap times. 1st & 2nd place times from 1/10 sec. to 10 hrs. with ST & LAP signs. Calculator: 4 key memory. %, $\sqrt{}$ 1 year batteries. ± 20 secs/month. $\frac{1}{4}$ x $2\frac{3}{4}$ x $4\frac{1}{2}$ in. RRP £26.95

Our Price **£21.95**



CQ-81 CALCULATING ALARM CLOCK. Plus 2 Alarm/Timers. 24 hour alarm and alarm/timers. 6 digit LCD clock. One year battery life. $1\frac{1}{2}$ x $2\frac{3}{4}$ x 5 inches. (RRP £22.95)

£17.95

CQ-2. Special Offer. Clock, calendar, 4 alarms, stopwatch, Time/Date calculator. (R.R.P. £39.95) P.O.A.

The INCREDIBLE FX-8000. 41 sc. funct., 1/100 sec. stopwatch, 2 x 5 alarm/timers. (£35.95) **£29.95**

MINI CARD CALCULATORS $\frac{1}{2}$ x $3\frac{1}{2}$ x $2\frac{1}{2}$ in. **£16.95**

FX-48 Math. Card. Full Scientific with S.D. **£19.95**

ST-24 Card Time. 24-hour stopwatch (or clock), 2 Alarm/Timers, Calculator as LC-78. **£19.95**

ALL Casio scientifics. Lowest prices

ST-1. Four way stopwatch **£24.95**

CARTRIDGE T/V GAMES

OPTIM Coronet 600 **£48.50**

Cartridges from £9.95

FAIRCHILD TIMEBAND Grandstand **£119.95**

Cartridges from £12.50

ATARI Video Computer System **£169.95**

The very best available to date!

Cartridges from £14.95

★ SPECIAL INTRODUCTORY OFFER


TWO FREE extra cartridges worth £29.90 with Atari

WATCH BATTERIES 65p each D.I.Y. KIT 35p

THIS MONTH'S



STAR BUY

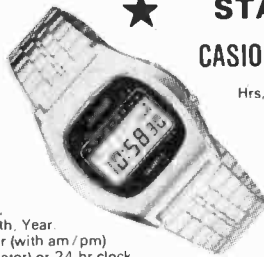

CASIO 54QS-16B


Hrs, mins, secs, day.
OR Hrs, mins,
date, day,
10 secs, secs
by flash

Day,
Date,
Month, Year.
12-hr (with am/pm)
indicator) or 24-hr clock.

Stainless steel. Mineral glass.
Water resistant to 100 feet.

£39.95

NEW

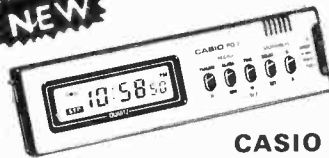

CASIO PQ-7

TRAVEL ALARM CLOCK

Battery-powered quartz alarm clock with repeat feature. Countdown alarm/timer 1/10 second stopwatch. Constant LC Display. Nightlight. 1 year batteries. $4\frac{1}{4}$ x $1\frac{1}{4}$ x $\frac{1}{2}$ inch. 1.6oz. For caravan or boat. (£24.95) **£19.95.**

SOLAR powered watches — so called. We won't sell them. Send us a S.A.E. and we will tell you why not.

CBM Giant 4 digit. 5 functions. Light.



5903 (£15.95)
Chrome
Bracelet

5902 (£14.95)
Gilt
Strap

£9.95
1803 (right)
ALARM

6 digits, 6 functions, plus backlight and alarm setting.
5-minute snooze facility (£28.95)

£22.95

PH-ALARM/CHRONO

Hours, minutes, seconds or date, day, am/pm indicator. Day, date, month, year. Chrono measuring net, lap and 1st and 2nd place times from 1/100 second to 1 hour. All Stainless Steel, Mineral Glass. Not to be confused with cheaper models with chromed case and plastic.

£39.95



LADIES' LCD WATCHES

5 functions, backlight. Gold or Silver finish (please specify).
Dress Watch. Round. Milanese bracelet **L1 £14.95**
Cocktail Watches. Integral bracelet. 3 styles **£18.95**



CASIO LADIES' LCD WATCHES



7 + 2 functions
27CL-15B
Round (Left)
(£35.95)

£29.95

27CL-17B
Stopwatch
(£49.95)

£39.95

Send 25p for our illustrated catalogue. Price include VAT and P&P. Send your cheque. PO or phone your credit card no. to —

TEMPUS

CASIO QUALITY

All CASIO watches have a calendar display, night illumination, mineral glass and stainless steel cases, water resistant to 100 ft (except sports watches — 66).

SPORTS WATCHES

F-100

Left, 9.45 mm
(£29.95)

£24.95

52QS-14B

Right 8 mm
(£44.95)

£34.95



Up to 25 functions. Net, lap and first and second place times to 1/100th sec. F-100. Resin case, strap 52QS-14B S/S encased version and bracelet.

4 DIGIT WATCHES (except World Time). Hours, minutes, ten seconds, seconds by flash, am/pm. Day, date, month. Stopwatch. Dual time (except 31QR-20B)



31QR-20B Left, 4 digit
(£35.95)

£29.95

51QR-19B. 6 digit
(£44.95)

£34.95

6 DIGIT WATCHES (except Sports and Alarm). Hours, minutes, seconds, day OR Hours, minutes, date, day, ten seconds, seconds by flash. Day, date, month, year. Selectable 12 hour (with am/pm) or 24 hour clock.

54QS-16B
Left, 6 digit
(£49.95)

£39.95

54QS-15B
6 digit
(£54.95)

£44.95



CHRONOGRAPH. 6 digits as above, with stopwatch measuring net, lap and 1st & 2nd place times from 1/100 sec to 6 hrs. Dual time facility.



45CS-22B
Chronograph
Left, 6 digit (£69.95)

£54.95

29CS-11B
World Time (£84.95)

£69.95



WORLD TIME WATCH. The time in ten capitals plus one optional time. Instant summertime correction. Hrs, mins, 10 secs, secs by flash. Perpetual calendar, day, date, month. Running digital seconds display.

ALARM WATCHES

25CR-16B
Round (£74.95)

£54.95

25CS-16B
Square (£84.95)

£69.95



Hours, mins, seconds (or hrs, mins, date) day, am/pm. Day, date, month, year. 24 hr. alarm, on/off indicator.

ULTRA SLIM DRESS WATCHES (Not 24 hour)

53CS-18B
Left, 4 digit (£74.95)

£59.95

49CS-25B
6 digit (£84.95)

£69.95



Not illustrated 53CS-19B, 4 digit, barrel shaped, **£64.95.** 49CS-24B, 6 digit (£79.95) **£64.95.** 53CGS-17L. Gold plated, on strap (£84.95) **£69.95.**

Dept. HE, Talk of the Town
19/21 Fitzroy Street
Cambridge CB1 1EH. Tel 0223 312866



TOPS THE PACK!

ACE MAILTRONIX LTD
Dept. Tantal Street
Walsfield, W. Yorkshire WF1 5AR

COMPONENTS - Now over 1,000 types in stock.
KITS - See the new range of low-cost 'ELEKITS'.
MODULES - New ready-built functions.
SERVICE - 1st Class same day despatch.
QUALITY - All guaranteed products.
PRICES - Many reductions!
MAGAZINE PROJECTS - Trouble-free!

LOOK

Our 2nd edition illustrated catalogue is now available. The much increased range shows many welcome price reductions.


INTRODUCING FABULOUS 'ELEKITS'

Easy build introduction to electronics. Many hours of enjoyment. NOW AVAILABLE!

The new range of easy build kits complete with simple to follow instructions. Battery powered (not supplied). With case.

- * BURGLAR ALARM * ROULETTE
- * BICYCLE SOUND FLASHER
- * WATER LEVEL ALARM * SIREN
- * BLINKER * TIME SWITCH

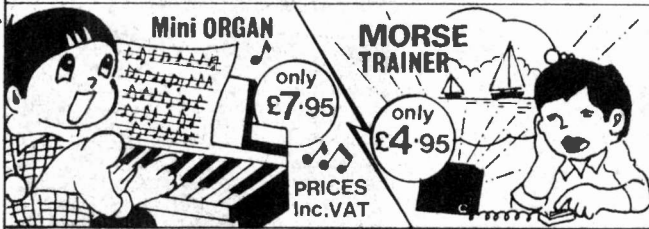Many others in preparation - included in full ACE catalogue - send S.A.E. for free brochure of kit range.



Mini ORGAN

only £7.95

MORSE TRAINER

only £4.95

PRICES Inc.VAT

I enclose 30p*, please send catalogue.

Name _____
Address _____

* Refundable with future orders over £5.00.

CHROMASONIC electronics

56 FORTIS GREEN ROAD, MUSWELL HILL, N10 3HN
TELEPHONE: 01-883 3705

OUR LATEST CATALOGUE

CONTAINS FREE
45 pence WORTH
OF VOUCHERS



CONTAINS MICROPROCESSORS + BOARDS,
MEMORIES, TTL, CMOS, ICs, PASSIVES, ETC., ETC.

SUPERSAVERS

ALL FULL SPEC DEVICES

TEXAS
741

5 for

£1.00

TIMER
555

4 for

£1.00

RED LED
TIL209
(INC CLIP)

10 for

£1.00

VAT INCLUSIVE PRICE + 25p P. & P.

A4 IC BOOKLET

SUPPLIED FREE WITH ORDERS OF ANY ICs WORTH £5.00
OR MORE. CONTAINS CIRCUITS, PIN CONNECTIONS AND
DATA (35p + SAE IF SOLD ALONE).

7400N AND 74LS00N SERIES TTL

7400	7401	7402	7403	7404	7405	7406	7407	7408	7409	7410	7411	7412	7413	7414	7415	7416	7417	7418	7419	7420	7421	7422	7423	7424	7425	7426	7427	7428	7429	7430	7431	7432	7433	7434	7435	7436	7437	7438	7439	7440	7441	7442	7443	7444	7445	7446	7447	7448	7449	7450	7451	7452	7453	7454	7455	7456	7457	7458	7459	7460	7461	7462	7463	7464	7465	7466	7467	7468	7469	7470	7471	7472	7473	7474	7475	7476	7477	7478	7479	7480	7481	7482	7483	7484	7485	7486	7487	7488	7489	7490
10	20	21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50	51	52	53	54	55	56	57	58	59	60	61	62	63	64	65	66	67	68	69	70	71	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86	87	88	89	90	91	92	93	94	95	96	97	98	99	100									

74175	74176	74177	74299	74300
-------	-------	-------	-------	-------

4024	4025	4026	4199	4200
------	------	------	------	------

70	71	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86	87	88	89	90	91	92	93	94	95	96	97	98	99	100	101	102	103	104	105	106	107	108	109	110	111	112	113	114	115	116	117	118	119	120	121	122	123	124	125	126	127	128	129	130	131	132	133	134	135	136	137	138	139	140	141	142	143	144	145	146	147	148	149	150	151	152	153	154	155	156	157	158	159	160	161	162	163	164	165	166	167	168	169	170	171	172	173	174	175	176	177	178	179	180	181	182	183	184	185	186	187	188	189	190	191	192	193	194	195	196	197	198	199	200
----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	-----	-----	-----	-----	-----


20	21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50	51	52	53	54	55	56	57	58	59	60	61	62	63	64	65	66	67	68	69	70	71	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86	87	88	89	90	91	92	93	94	95	96	97	98	99	100
----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	-----

Hobby Electronics

Next
Month


The December issue will be on sale on November 10th

Light Beam Phone

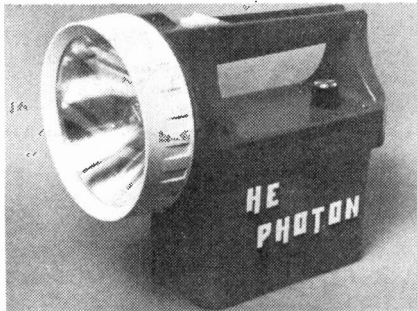

True wire-less communication for which you don't need a licence! Our project next month — which we are calling the 'HE Photon Phone' uses two standard torches which we've converted — all the electronics fit into it beautifully. In our tests we've been able to make our units work over a distance of 50 feet; even if you don't want to build it, you'll be fascinated by the techniques there's even a remote control facility included.

Audio Mixer Project

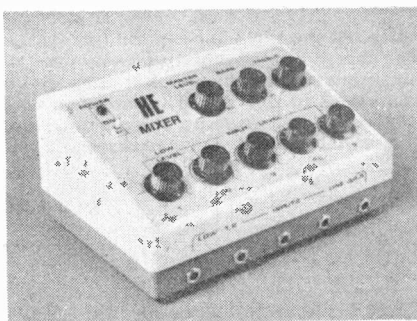


A really neat project designed by a professional audio engineer — that's a quick summary of our mixer, choose your own number of inputs (we've opted for three high level and two low level ones). There's a bass and treble control and of course a master level control. Building it should be simplicity itself as everything, including the level controls is on a single printed circuit board. Power is supplied by two PP3 batteries; inputs and outputs are via standard jack sockets.

Bias


No — not political, tape. Why do you need a high frequency signal added to a tape recording — you never hear it so why is it necessary? Next month we tell you.

DIY PCB's

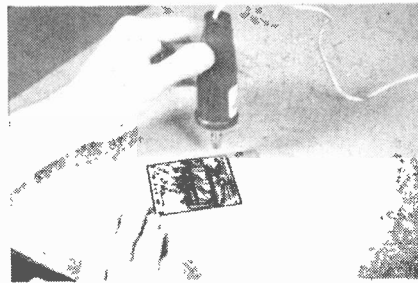


The neatest way to build a project is on a PCB — few would deny that, yet PCB's are frightening to those who haven't tackled them before. Next month we will be launching Hobbiprints — a really easy way to make the PCB's which we show in HE and we'll show you how to use them.

Calculators

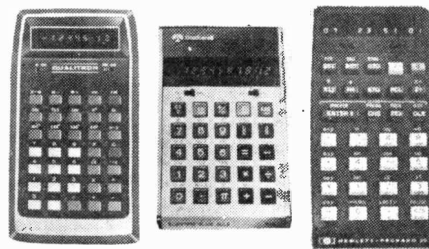


The world of calculators has gone the way of HiFi — the facilities offered often cause confusion. We take a look at the current terminology of the calculator market enabling you to find out if the facilities offered are really the ones you want.

Electronic Dice

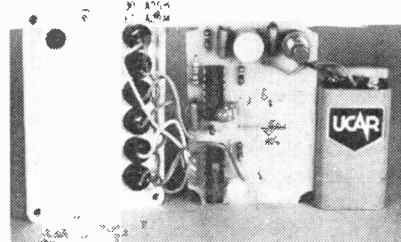


Press the button and one of six LED's comes on at random. From the photograph you can see this is really a straightforward project. The light stays on automatically — there isn't even an on-off switch!

The Tesla Controversy

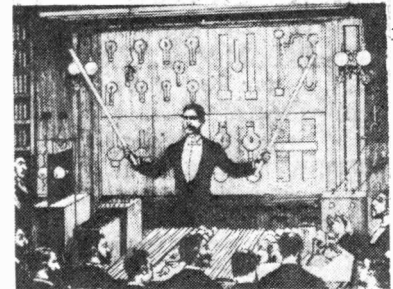

Nikola Tesla was without doubt a genius — he even has a unit of measurement named after him — but even 35 years after his death there are those who believe that much of his work has been suppressed.

Metronome

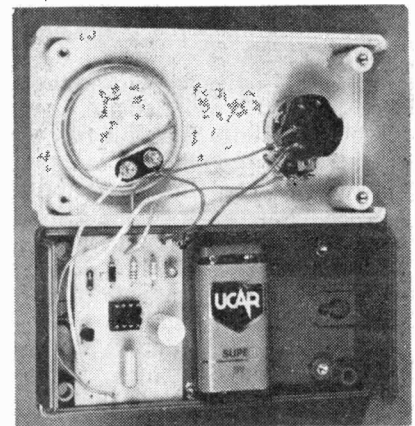

Using just a single 555 IC, this project can be built on either a PCB or Veroboard — we give you details for both. The beat rate can be varied from 30 to 120 beats a minute.

SPECIAL OFFER

Next month you'll be able to get a top quality soldering iron, either 240V or 12V, through our offer in HE. Today's regular price is £4.00 but next month you can get this for:

£2.35 inc.

audiophile.

Ron Harris takes to the high seas this month — well the Thames anyway — to discover a remarkable new drive unit from Strathearn. Back on dry land news of a linear motor tone arm

IT WAS ENOUGH to make Nelson spin in his grave. One of Her Majesty's ships, battle-worn from the fire of enemy guns, put to use as an area to hold a press reception! And for something as totally unmaritime as loudspeakers!

Mind you, HMS Belfast can only be considered appropriate, for it was Strathearn Audio (based in Belfast and government owned) who sent me the music echoing through the wardrooms.

The occasion was the launching — for once no pun intended — of their new speaker system, the 21000. This is a 'four box' affair with the base units cast loose from the rest. Frequencies up to 500Hz are handled by the 8" bass drivers reflex mounted in the enclosures. Above 500Hz everything is produced by the real star of the system, Strathearn's new driver, the SLC2.

Film Star?

The principle on which these speakers operate is very similar to that of the Wharfedale Isodynamic headphones. In the SLC2 an aluminium conductor, about a metre long, is bonded onto a polyester film which is stretched inside a moulded frame about 130mm x 600mm. Rows of magnets flank the diaphragm creating a high uniform field in the vicinity. When the signal current passes through the conductor it is driven by the force generated due to its being in a magnetic field.

Thus the polyester film is the speakers 'cone' if you like. Since this will radiate from both front and back (dipole radiation) the unit has damping pads fitted to absorb the anti-phase rear radiation. Mass of the driver is very low, so very little overhang to worry about. As the area is effectively all driven, it should not 'break up' at all on any input signal.



The only drawback is the very low impedance of the aluminium strip itself — about 0R5 in fact. In order to make this usable Strathearn have transformer coupled — which at least makes the unit adaptable to any required input impedance.

To claim, however, that this produces a purely resistive load is at best extremely optimistic, at worst



Sound Track

I'm going to reserve judgement on the 21000 system as a whole until I've had an opportunity to listen under more favourable conditions than HMS Belfast at 100°F with 49 other people crowding me lugholes! It was clear though that the SLC2 is a remarkable unit, and is perhaps worthy of better. We shall see.

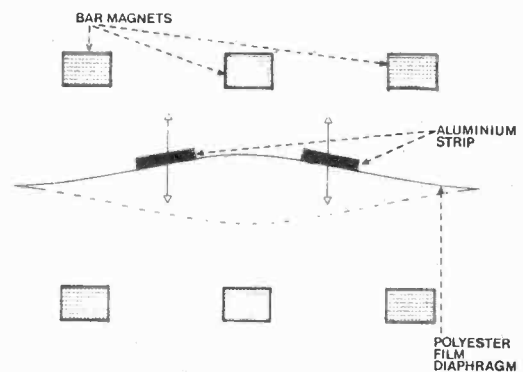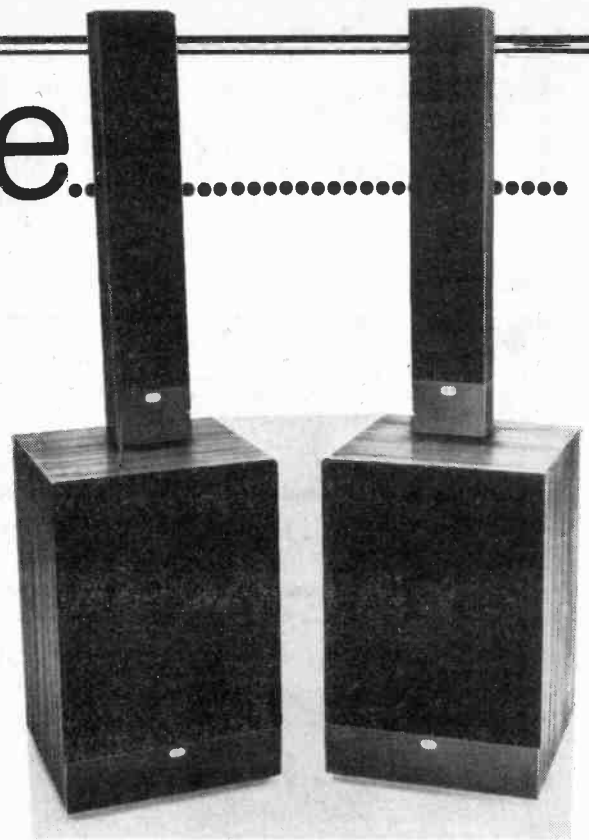The system sells for £375 RRP, and is expected to have appeared in the shops by the time you can get down there.




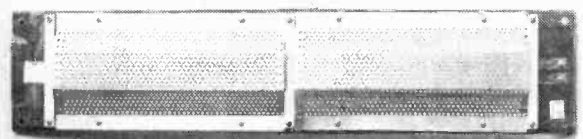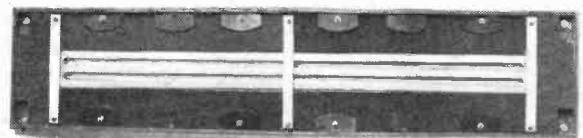The 21000 from all angles. At the top we have the full system. Below that the diagram shows the operating principle of the SLC1. The polyester diaphragm acts as the speaker cone. Below this caption two internal views of the unit. The radiating areas can be seen in the top diagram, and the lower rear view illustrates the damping material to control rear radiation.



Decked Out

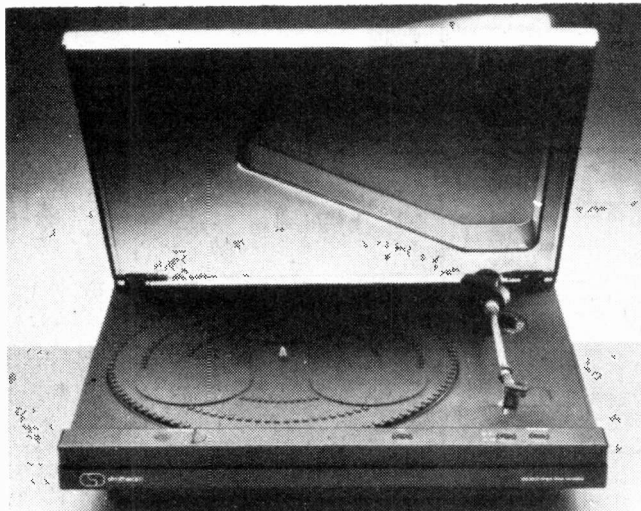At the same demo Strathearn were using their SM2000 turntable as the sound source. It was a good advert. They had a line of Sonus, Supex, ADC, Shure and Ortofon cartridges all neatly installed in spare carry arms, and all of which tracked very well when asked to. Several people — me included — were surprised at the ease with which the SM2000 handled these devices and




how well the sound each is capable of was preserved. Indeed on this evidence the SM2000 is a very capable unit indeed — a comparison with some better established machines (including schhh — you know what) might be very interesting indeed. How about it, Strathearn?

Details of both from Strathearn Audio Ltd, Kennedy Way Industrial Estate, Kennedy Way, Belfast.

Arms Against The British?

There can be only two basic ways of doing a job — simple and complicated. Both can take vast amounts of thoughts to realise (who said simple meant obvious?) and are capable of excellent results. Witness belt and direct drive turntables as represented by the Linn and the Technics SP10.

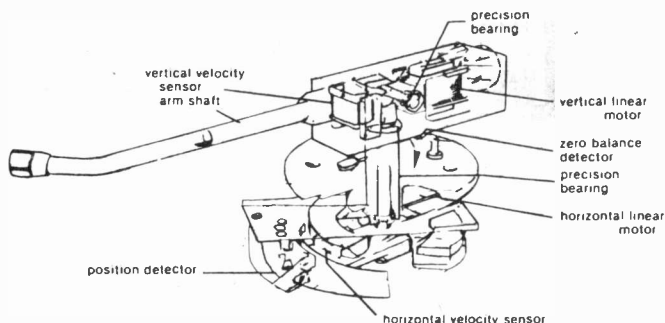
Sony have applied the latter approach to pickup arm design with the result that they end up with two linear motors, two velocity sensors, two position sensors, a deal of electronics and potentiometers to set tracking weight!



Exploded view of the Sony motorised pickup arm. Tracking weight is applied by a potentiometer mounted remotely on the plinth.

In fact the velocity sensors are simply two more linear motors used as generators. Servos drive the motors which take the arm across the record in the proper manner. In the vertical direction too all control of the arm movement is down to a linear motor. Arm resonance is suppressed, by varying the current to the coils — from somewhere around 25dB in an undamped system to about 3dB in the Sony system using their XL55 cartridge.

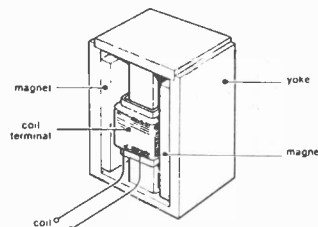Right: A close up of the linear motors used in the arm design. These double as position sensors by using the same device as a generator, i.e. allowing them to be moved by the arm and measuring the current generated in the coils.



Advantage Complications

Gains from this method are claimed to be insensitivity to external vibration, improved tracking and better definition and imaginery. Bias of course can be forgotten, as the motor controls movement across the vinyl canyons, and tracking weight can be changed while the stylus is in action.

All this sounds well-nigh perfect does it not? On paper the design looks marvellous (so did the Titanic — cynic) but we shall have to wait until they market it in this country to find out *how* good it is. Meanwhile eat your heart out SME!

From Service to Taste

A little congratulation and a whoopee cushion to finish on. Firstly many thanks to Celestion for some fast excellent service this month. Some nameless person from the pit (no not me — *another* one!) blew a bass unit in one of our Ditton 66's. One phone-call later I was on my way to pick up a replacement from Ipswich. And that four years after buying the speakers — and it was our fault. Nice to be able to commend a big hi-fi firm for service for a change.

Now Audiophile enquiry service is normally dealing with people with impeccable taste. However it appears there is one exception. So that this person does not have derision heaped upon his unworthy shoulders and be cast from the company of his peers let us refer to him as Mr Smith.

This person wrote in — nothing wrong there you may say — he even dated his letter. Again nothing amiss about that. Trouble was he 'dayed' and timed it too. I quote with shaking head and furrowed brow . . .

"So at 8.05 pm on Thursday evening I am turning off some corny comedy on the television set to write enquiring about . . ."

There we have it. The heronion crime is in the open. Thursday eh? 8.05 eh? Corny comedy eh? The only comedy on TV at that time is the 'Good Life' — which any human male with a micro-gram of taste and appreciation of the opposite gender should be watching avidly for the glorious presence of Felicity Kendal!

Oh Mr Smith may your hi-fi forgive you — I cannot!

ETI

IT'S FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived — often bargains which sell out before our advertisement can appear — it's an interesting list and it's free — just send S.A.E. Below are a few of the bargains still available from previous lists.

Pot Cores. We have now received our delivery of Ferro pot cores. These are ex unused equipment. They contain the bobbins but of course these have to be wound and you would have to unwind. Three pairs available.

FX 2243	4.5 cm	3.0 cm	81
FX 2242	3.5 cm	2.3 cm	70 per pair
FX 2240	2.5 cm	1.6 cm	60 per pair

Quantity discounts apply.

Component Panel Ref. 3055. Taken from unused P.S.U.s, these contain 4x2N 3055 power transistors with mica insulators all on heat sink and 4 variable pots, preset type with spindle locks. Real bargain at £1.08 each.

Component Board 421. Again from unused equipment, major items on these are two power silicon transistors, Motor Rola ref. SJ 5433 mounted on a heat sink with mica insulators, also behind the panel are two power rectifiers ST NS 100B. Price 9.6p.

E.H.T. Mains Transformer. With induction control, normal primary and output voltage approx. 4kV 3mA. Voltage can be varied by applying DC to lower bobbin. Unused, ex P.S.U.s. Price £4.32.

Mus. Centre Dust Cover. Size 12 x 10 x 1 1/2" with attachments for hanging. Price £3.95. Covers only.

Hi-Fi Console. Pleasingly designed shelving arrangement which could tidy up your equipment, sorry it's called only but a real bargain at £7.35.

Telephone Answering Machines. Used but apparently complete and probably in working order. However, we are allowed to supply these only for breaking up, they should be very suitable for conversion to open reel tape recorder, background music machine, echo chamber, etc. All untested but we guarantee to replace any major item in the machine should it be faulty. Machines less outer case £7.50 case slightly broken but substantially whole £10.26. Unbroken cases £12.45 and finally with new looking cases £14.50. Post £2.50 per machine. Many accessories available for these machines. Please enquire.

Wall Mounting Thermostat. The Satchwell room stat. Mains 20 amp suitable over normal air temperatures between 30-80 F. Suitable also for greenhouse control. Nicely finished in white enamel. Price £3.25.

10 r.p.m. Motor with 230v mains coil. Not like the usual of these geared motors this has a good length of 1/4" shaft. Price £2.50+20p.

Rigonda Intermzzo 10+10 hi-fi amplifier with belt driven record deck with speed control and strobe check. The best hi-fi offered by Rigonda. Original selling price was in excess of £125. We have approx. 50 of these unused but with various faults. Untested. Believed complete except for cartridge and speakers. Offered at £33.50, less than the price of the very high quality deck incorporated. If cannot collect add £3 to cover the special packing and carriage charge.

Loudspeaker Grill. Good quality rigid plastic, ideal for use in car or home systems on speakers. Two sizes available 12 x 12 — 85p, 18 x 18 — 60p.

6 Digit Counter — Resettable, coil voltage 48 DC or 115V AC, current 100 mA approx. Price £2.10.

10 Digit Switch Pad. Made, we believe, for GPO pushbutton telephones, each button operates 2 pole switch which returns when depressed, panel size 2 1/2" x 3 1/2" x 1 1/2" pushbuttons with clear plastic protected digits 0-9. Price £2.16.

Mains Blower. Real bargain blower made by Smiths, the motor is let into the turbulator so these can be stacked sideways to give variable air outlet using the minimum of space. Overall size of the blower is 7 dia x 2 1/2" and the air outlet 1 1/2" x 2 1/2". Price only £2.50.

Dial Indicator used for tool making and precision measuring, the famous John Bull shows differences of 0.1 mm. A beautifully made precision instrument, price in most tool shops would be £12-£15. We have a fair quantity, price £10.75.

MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field they would make a wonderful gift to almost any one in easy to assemble modular form and complete with a pair of Plessey speakers this should sell at about £30 — but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.



High Voltage Mains transformer. Normal mains primary secondary by our measuring equipment is 8kV approx. at 5mA. We are offering these at a bargain price of £4.50.

A Special Bulk Purchase enables us to offer this keyboard at a lowest ever price. 49 Coded keys encoded into a direct TTL compatible 7 bit output. Features: such as delayed strobe, 5 volt D.C. single rail operation and rollover protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector, at a secondhand "no time to test" price of only £18.63, post £1.50.

WHAT COULD YOU BE DOING?

In one year's time, if you understood computer and microprocessor technology? Think it over, then join the "Doing it digitally" course which is starting now.

You will learn mainly by doing, not just reading, it's easy to understand that way. Pay as you learn — Just £5 deposit and eleven monthly payments of £3. (or £35 cash now). £23 worth of components sent now, more will follow as course requires them.

REMEMBER THIS IS YOUR CHANCE?

Interested in Tape Control? American made type punches really beautiful units full of sophisticated parts, designed, we believe, to automatically operate typewriters and they can of course be used to operate other punch tape controlled machines. Reference No. is NCR Class 46-2 reference 205 H8 R56, these are B bit tape punches, powered from 115V 50HZ in very good condition with tape £1.6, carriage £3.20.

High voltage Mains transformer. Normal mains primary, secondary by our measuring equipment is 8kV approx. at 5mA. We are offering these at a bargain price of £4.50.

Terms, Prices (Except Transformers) include Post & VAT. But orders under £6.00 please add 50p to offset packing. Bulk enquiries — Please phone for Generous Discounts 01-688 1833.

J. BULL (ELECTRICAL) LTD
103 TAMWORTH RD.
CROYDON CR8 1SG

MAINS TRANSFORMERS (TM)

All these have 230/240V 50Hz
All these have 230/240V 50Hz Primary

Voltage	Our Ref	Price	Post	
1v	2 amp	TM 1	£1.94	45p
2.4v	5 amp	TM 2	£1.62p	50p
4v	7 amp	TM 32	£2.70	60p
6.5v	3 amp	TM 3	85p	40p
6.5v	100 mA	TM 37	85p	40p
6.5v-0.6 5v	200 mA	TM 21	£1.62	40p
6.5v-0.6 5v	100 mA	TM 21	£1.62	40p
6.3v-0.6 3v	100 mA	TM 33	£1.62	40p
6.3v	2 amp	TM 4	£1.89	50p
8.5v	1 amp	TM 12	£1.62	40p
8.5v+8.5v sep. winding	1/2 amp	TM 12	£1.62	40p
9v	1 amp	TM 5	£1.62	45p
9v	3 1/2 amp	TM 11	£2.70	50p
9v	5 amp	TM 38	£3.24	60p
10v	2.5 amp	TM 15	£4.86	£1.25
10v-0-10v	4 amps	TM 50	£3.78	£1.25
10v-0-10v	12 1/2 amp	TM 15	£4.86	£1.25
12v	1/2 amp	TM 9	£1.05	50p
13v	100 mA	TM 21	£1.62	40p
13v	1/2 amp	TM 7	£2.16	50p
12v	1 amp	TM 10	£1.89	50p
12v-0-12v	50 mA	TM 18	£1.62	40p
12v-0-12v	1 amp	TM 41	£3.24	50p
15v tapped 9v	2 amp	TM 11	£2.70	50p
17v	1/2 amp	TM 12	£1.62	50p
18v	3/4 amp	TM 13	£1.90	50p
20v	1/2 amp	TM 14	£1.62	50p
20v (with 5v 1/2 amp)	2 amp	TM 50	£3.78	£1.25
20v	6 amps	TM 46	£4.32	£1.25
20v	12 1/2 amp	TM 15	£4.86	£1.25
20v-0-20v	6 amp	TM 15	£4.86	£1.25
24v	1 1/2 amp	TM 16	£2.12	60p
24v	2 amp	TM 17	£2.70	60p
24v+2v 7 amp	2 amp	TM 39	£2.70	70p
24v	4 amp	TM 40	£3.78	80p
25v	1 1/2 amp	TM 18	£2.43	60p
26v	2 amp	TM 39	£2.98	60p
30v	8 amp	TM 15	£4.86	£1.25
37v	37 amp	TM 34	£31.86	enquire
40v	3 amp	TM 46	£4.32	£1.25
40v	5 amp	TM 48	£5.02	£1.25
40v	6 amp	TM 15	£4.86	£1.25
40v-0-40v	2 1/2 amp	TM 48	£5.02	£1.25
50v & 6.3v	2 amp	TM 22	£4.86	£1.25
50v	2 amp	TM 29	£11.65	£1.75
60v tapped 40v & 20v	2 amp	TM 46	£4.32	£1.25
70v	4 1/2 amp	TM 24	£7.02	£2.50
75v & 63v	3 amp	TM 23	£8.10	£2.00
75v	4 1/2 amp	TM 24	£7.02	£2.50
80v tapped 70v & 75v	4 amp	TM 24	£7.02	£2.50
80v centre tapped	2 1/2 amp	TM 48	£5.02	£1.25
100v	1 amp	TM 25	£7.02	£1.75
100v-0-100v	1/2 amp	TM 25	£7.02	£1.75
200v	1/2 amp	TM 25	£7.02	£1.75
250v-0-250v & 6.3v	50 mA	TM 36	£3.78	£1.00
250v	100 mA	TM 36	£3.78	£1.00
500v	50 mA	TM 36	£3.78	£1.00
260v	100 mA	TM 26	£3.24	£1.00
1000v	60 mA	TM 43	£6.50	£2.00
4 kv	5 mA	TM 49	£4.05	70p
5 kv	5 mA	TM 30	£7.02	£1.00
8 kv	5 mA	TM 45	£4.05	£1.00

B. BAMBER ELECTRONICS CASH WITH ORDER. (MINIMUM ORDER £2.00)
DEPT. ETI, 5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE
Tel. ELY (0353) 860185 (Tues. to Sat.)
PLEASE ADD VAT AS SHOWN
POST PAID (UK ONLY), SAE WITH ENQUIRIES
CALLERS WELCOME BY APPOINTMENT ONLY

ALL BELOW — ADD 8% VAT

IC TEST CLIPS, clip over IC white still soldered to pcb or in socket. Gold-plated pins. Ideal for experimenters or service engineers. 28 pin DIL £1.75, 40 pin DIL £2.00. Or save by buying one of each for £3.50.

MAINS TRANSFORMERS, TYPE 157300 240V input, 15V at 300mA output, £1.50 each

MAINS TRANSFORMERS, TYPE 45/100, 240V 240V 110, 20.0V input, 45V at 100mA output, £1.50 each

SLOW-MOTION MOTORS, 120V 50Hz 1RPM. Size approx 2 dia 1 1/2" deep, with 1/2" spindle, 60p each, or 2 for £1.00

1 1/2 V DC MOTORS (ideal for model makers, quite powerful) 50p each

SUB-MINIATURE ROTARY SWITCHES, 4 x 5-way make contacts. Size approx 3/4 dia 1" deep, 3/16" spindle 50p each

30p BEEHIVE TRIMMERS. Brand new, 4 for 50p

Min. Spf AIR SPACE TRIMMERS, approx. 1/8" square, 3 for 50p

Min. Spf COMPRESSION TRIMMERS, 1/2" x 5/16" 4 for 50p

LARGE ELECTROLYTIC PACKS. Contain range of large electrolytic capacitors. Low and high voltage types, over 40 pieces. £3.00 per pack (+ 12 1/2% VAT)

ALL BELOW — ADD 8% VAT

MIXED COMPONENT PACKS. Containing resistors, capacitors, switches, pots etc. All new, and hundreds of items. £2.00 per pack, while stocks last.

IC AUDIO AMP PCB. Output 2 watts into 3 ohm speaker. 12V DC supply, size approx 5 1/2" x 1 1/2" x 1 1/2" high, with integral heatsink. Complete with circuit. £2.00 each

NICAD CHARGER CONVERTER PCB. (Low power inverter) Size approx. 4" x 1 1/4" x 1 1/2" high. 12V DC supply. 60V DC output, through pot on pcb, for charging Nicads etc. (ideal for charging portable batteries from mobile supply). Only needs one BFY50 51/52 or similar transistor, which can be mounted direct on the pcb pins on board, fitted with a star type heatsink (not supplied). £2.00 each

THE NEW EAGLE INTERNATIONAL CATALOGUE IS AVAILABLE ON REQUEST containing Audio, In-car, and test equipment, etc

DECIMAL KEYBOARDS, pressure sensitive type, when pressed contacts go from 0 to C to approx. 25 ohms. Switches only, no encoders. Size approx 3" x 3" with large square touch plates. 0-9 + Clear, A, B, Dual Watch and spare. Few only. £2.00 while stocks last

TRANSISTORS
BFY51 Transistors 4 for 60p
BCY72 Transistors 4 for 50p
BSX20 (VHF osc. mult.) 3 for 50p
BC107 (metal can) 4 for 50p
BC108 (metal can) 4 for 50p
PBC108 (plastic BC108), 5 for 50p
BF152 (UHF amp/mixed) 3 for 50p
2N3819 Fet. 3 for 60p
BC148 NPN SILICON, 4 for 50p
BC158 PNP SILICON, 4 for 50p
BAY31 Signal Diodes, 10 for 35p
741CG RCA Op Amps 4 for £1.00
SCRS400V at 3A, stud type, 2 for £1.00
TIP2955 Silicon PNP power transistor, 60V at 15A, 90 Watts. Flat pack type, 2 for £1.50
GERMANIUM DIODES, approx 30 for 30p
1N4148 (1N914) diodes 10 for 25p

VALVES
QV003/20A (ex. equipment) £3.00
QV003/10 (ex. equipment) 75p or 2 for £1.20
6BH6 (ex. equipment), 2 for 50p
All the above valves are untested, except for heaters and no guarantee of percentage of emission is given.
Softly on-resistors
MULLARD 85A2 85V STABILISER VALVES (brand new) 70p each or 2 for £1.20

ALL BELOW — ADD 8% VAT

RED LEDs (Min. type), 5 for 70p

VIDICON SCAN COILS (Transistor type, but no data), complete with vidicon base. £6.50 each. Brand new AEI CS108-R MICROWAVE DIODES, up to X-Band, max. nose figure 8.5dB at 9.375GHz. 80p each.

DIE-CAST BOXES
SIZE APPROX.
4.3 x 2.3 x 1.2 (111 x 60 x 30mm) £1.25
4.8 x 2.3 x 1.5 (121 x 60 x 38mm) £1.75
4.8 x 3.8 x 1 (121 x 95 x 25mm) £2.10
4.8 x 3.8 x 2 (121 x 95 x 51mm) £2.45
6.8 x 4.8 x 2 (171 x 121 x 51mm) £3.10
4.8 x 3.8 x 3 (121 x 95 x 76mm) £3.50
6.8 x 4.8 x 4 (171 x 121 x 101mm) £4.47
8.6 x 5.8 x 2 (222 x 146 x 51mm) £4.25
10.6 x 6.8 x 2 (273 x 171 x 51mm) £5.30

SPIRALUX Tools for Electronics enthusiasts SAE for list

4MHz XTAL PACKS (10 assorted xtals between 4MHz and 5MHz) Our selection only £1.00 pack

SOLDER SUCKERS (Punger Type)
Standard Model, £5.50
Skirted Model, £6.00
Spare Nozzles 65p each
WELLER WP60D Mains operated temperature control, soldering iron. £15.00

SPARE TIPS (WP60D): Two types available TYPE CC7 (W60D) Standard TYPE AA7 (W60D) Finer tip. £1.60 each

WELLER TCP2 temperature controlled soldering iron, and PU220 power unit (replaces Weller TCP1) iron + PSU £30.00. Spare tips: CC7 (standard), or K7 (finer tip) £1.50 each

Slider Switches 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins). 4 for 50p

PLASTIC PROJECT BOXES, with screws on lids (fin. black ABS) with brass inserts
Type NB1 approx 3" x 2 1/2" x 1 1/2" 45p each
Type NB2 approx 3 1/2" x 2 1/2" x 1 1/2" 55p
Type NB3 approx 4 1/2" x 3 1/2" x 1 1/2" 65p each
Type NB4 approx 8 1/2" x 5 1/2" x 3 1/2" £1.50 each
Slider Switches 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins). 4 for 50p

OSMOR 110V REED RELAY COILS (1k ohm coil to fit 5V reeds (not supplied) 2 for 50p

HF CHOKES wound on 1/4" x 1" long ferrites, 4 for 50p

VHF CHOKES wound on 6-hole tubular ferrites 5 for 40p

ALL BELOW — ADD 8% VAT

DUAL TO18 HEATSINKS 1 x 1/2" x 1/2" with screw-in clamps, 3 for 50p

GLASS BEAD FEEDTHROUGH INSULATORS, solder-n type, overall dia. 5mm, pack of approx. 50 for 50p

LARGE GLASS BEAD FEEDTHROUGH INSULATORS, as above but 8mm dia. pack of approx. 50 for 70p.

20V RELAYS, PCB mounting type, single pole change-over, 35p each

10 7MHz SSB XTAL FILTERS (2.4kHz Bandwidth) Low imp. type, Carrier and unwanted sideband rejection min. -40dB (need J0.69835 & 10.70165, xtal for US/LSB, NOT SUPPLIED). Size approx 2 x 1 x 1" £10.00 each

LOW PASS FILTERS (low imp. type), 2.9MHz, small metal encapsulation, size approx 1 1/2" x 1/4" x 1/4" 75p each

ALL BELOW — ADD 12 1/2% VAT

CELESTION 8 x 5 ELECTRIC SPEAKERS 20 ohm, 3 watts rated, £1.50 each + 12 1/2% VAT

VARI-CAP TUNERS, Mullard type, ELC1043/05 £5.00

BSR AUTOCHANGE RECORD PLAYER DECKS with cue device, 33-45-78 rpm, for 7 1/2" 12" records. Fitted with SC12M Stereo Ceramic cartridge and stylus. Brand new, £14.00 + 12 1/2% VAT

GARRARD AUTOCHANGE RECORD PLAYER DECKS Model 6300, with cue device, 33-45-78 rpm, for 7 1/2" 12" records. Fitted with KS418 Stereo Ceramic cartridge and stylus. Brand new, £16.00 + 12 1/2% VAT

TV LINEARITY COILS, Special offer 10 for £1.00

DUBILER ELECTRONICS 50V F 450V, 2 for 50p

DUBILER ELECTRONICS 100V F 275V, 2 for 50p

DUBILER ELECTRONICS 400V F 63V, 3 for 50p

TTC ELECTRONICS 6800V F 25V high grade screw terminals, with mounting clips, 50p each

Resistor PKs, approx 300 pieces 1/2" to 2 watt types, mixed values, our selection, £1.00 each

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES
Aluminium Boxes with Lids

AB10	5 1/2 x 4 x 1 1/2	75p
AB13	6 x 4 x 2	£1.00
AB14	7 x 5 x 2 1/2	£1.50
AB15	8 x 6 x 3	£1.75
AB16	10 x 7 x 3	£1.75
AB17	10 x 14 x 3	£1.50
AB25	6 x 4 x 3	£1.25

Vinyl Coated Instrument Cases
Blue Tops with Plastic Lids Sections
Very smart finish

WB1	5 x 2 1/2 x 2 1/4	75p
WB2	6 x 4 1/2 x 1 1/4	£1.35
WB3	8 x 5 x 2	£1.80
WB4	9 x 5 1/2 x 2 1/4	£2.00
WB5	11 x 6 x 3	£2.25
WB6	11 x 7 1/2 x 3 1/2	£2.50
WB7	12 x 6 x 5 1/4	£2.95
WB8/3	8 x 5 1/2 x 3 1/2	£2.25

FULL RANGE OF BERNARDS' BABINI ELECTRONICS BOOK IN STOCK S.A.E. FOR LIST

VALVES
QV003/20A (ex. equipment) £3.00
QV003/10 (ex. equipment) 75p or 2 for £1.20
6BH6 (ex. equipment), 2 for 50p
All the above valves are untested, except for heaters and no guarantee of percentage of emission is given.
Softly on-resistors
MULLARD 85A2 85V STABILISER VALVES (brand new) 70p each or 2 for £1.20

RESISTOR PKs approx 300 pieces 1/2" to 2 watt types, mixed values, our selection, £1.00 each



RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. SAE FOR LIST.

'Cold-start' For CD Units

T. Lyons

Many cars are fitted with cold-start coils, which operate at full current only on starting, then are fed via a ballast resistor. This resistor is normally discarded when CD ignition is fitted, and the coil is run at 'full power' all the time. It's a simple matter to arrange for the cold-start circuit to operate a relay inside the CD unit which switches in a second capacitor C2 across the main one, thus increasing the energy of the spark when the engine is starting. After starting, C2 is no longer in circuit and the main capacitor C1 alone supplied current to the coil, thus alleviating any charging problems with attendant loss of power at high revs.

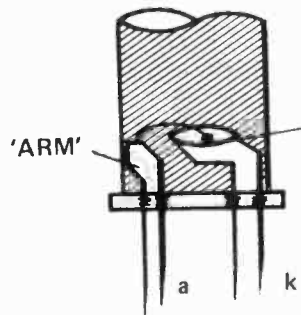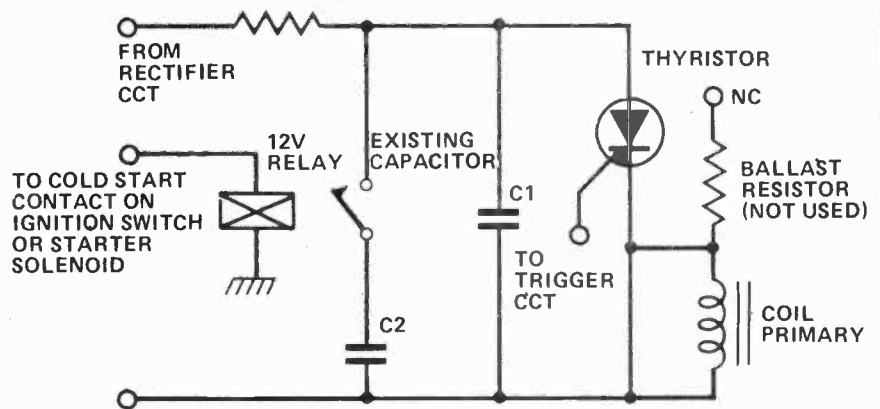RLA is any 12 volt relay, and C2 can have the same value as the existing capacitor C1, usually 470n or 1u0.



LED Spotting

A. Kenny

Since the leadout on LED's varies according to the manufacturers preference, leadout diagrams are not always worthy of the trust placed in them. In some cases a reverse connection will destroy the device being used.

A simple way to avoid this is to use the following technique:


If the LED is held up to the light, the structure can be clearly seen. There is a "cup" and an "arm" carrying a fine wire to the LED itself, which is in the "basin" of the cup (see drawing).

The lead with the cup is the cathode, and the other is the anode (of course).

TV Game Resurrection

S. Rice

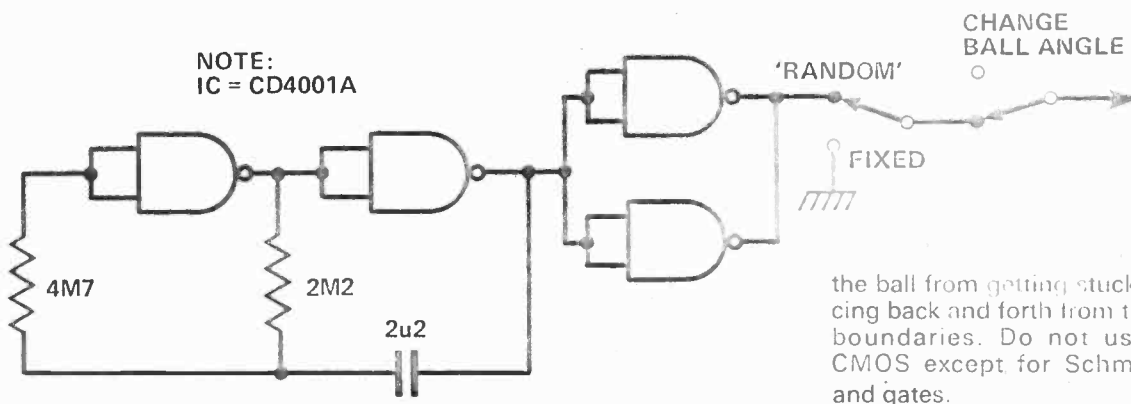Now that the novelty of TV games has worn thin and most of the units are gathering dust in the corner reserved for other five-minute wonders, here's a chance to add new spice to leisure time. The circuit is an oscillator clocking at about one cycle per 4 seconds. This switches the ball angle "randomly" making the game unpredictable and difficult. Also this prevents



the ball from getting stuck and bouncing back and forth from the bats and boundaries. Do not use B suffix CMOS except for Schmidt trigger and gates.

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.


ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.

SINTEL

THE SINTEL SIX DIGIT MAINS CLOCK KIT

with BLEEP ALARM and TOUCH SWITCH SNOOZE

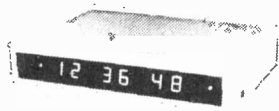- HIGH BRIGHTNESS DISPLAY
- AUTOMATIC INTENSITY CONTROL
- DEEP RED DISPLAY FILTER
- SLIM WHITE CASE 205mm x 40mm x 140mm
- BATTERY BACKUP
- CRYSTAL CONTROL FOR IMPROVED ACCURACY



Order as **ACK + BBK + XTK** £34.50
 The ACK is also available without battery backup and crystal control. Order as **ACK** £28.80
 The kit is supplied complete with the exception of a mains plug, cable and battery

DATABOOKS


BEST OF BYTE Volume 1 380 pages	£11.95
Illustrating Basic	£2.45
Intel Memory Design Handbook	£5.20
Intel 8080 Microcomputer Systems User's Manual	£6.50
Intel 8085 Microcomputer Systems User's Manual	£6.50
Motorola Booklet From the Computer to the Microprocessor	£3.50
Motorola CMOS Databook (Vol 5 Series B)	£12.95
Motorola M6800 Microprocessor Applications Manual	£5.35
Motorola M6800 Programming Manual	£0.75
National SC/MP Introtkit User's Manual	£1.80
National SC/MP Technical Description	£1.80
National Semiconductor TTL Databook	£5.45
RCA CMOS and Linear IC Databook	£2.95
Texas Instruments Pin Configuration Guide. A very useful set of gloss cards showing top and bottom pin-out views of 7400 ICs plus many others (T 1 Memories Op-Amps, etc.)	£7.50
Z80 Assembly Language Programming Manual	£5.80
Zilog Z80 CPU Technical Manual	£0.80
Zilog Z80 CTC Product Specifications	£3.30
Zilog Z80 P10 Technical Manual	
DATASHEETS at 75p each on IM6100, 6800, SC/MP, CDP 1802, 2650, TMS5501, TMS8080, 9131	
Z80 P Intel 8085. Also free data on some components	

Some Popular Memories available from SINTEL

(See ETI DATA SHEET SPECIAL July 1978)

2102 450 nsec 1K STATIC RAM	£1.85
2102 650 nsec STATIC RAM	£1.85
2708 1K x 8 bit UV ERASABLE ROM	£8.80
6508 6D0 nsec 1K STATIC RAM	£8.05

ASSEMBLED LATCHED COUNTER MODULES

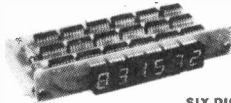

SIX DIGIT TTL COUNTER MODULE

Our range of Industrial Latched Counter Module Kits is now available ready-built. These counters use both CMOS and TTL ICs and will save you considerable design, purchasing, building and de-bugging time. Each module uses a set of red LED displays, and features a single in-line plug and socket. Instructions are provided. For full details please send for Catalogue

	TTL		CMOS			
	Part No	Built	Part No	Kit	Part No	Kit
2 digit	401-484	£13.22	526-412	£10.52	985-568	£13.02
4 digit	715-484	£23.38	657-412	£17.98	512-568	£22.83
6 digit	293-484	£33.76	721-412	£25.66	393-568	£32.31
					191-470	£25.85

NEW PRICES AND SOME NEW CMOS ADDITIONS

If you need your CMOS by return - buy it from SINTEL

CD4000	0.15	CD4027	0.44	CD4051	0.82	CD4086	0.84	CD40182	1.40
CD4001	0.17	CD4028	0.77	CD4052	0.82	CD4089	1.39	CD40192	1.40
CD4002	0.17	CD4029	1.03	CD4053	0.82	CD4093	0.80	CD40193	1.40
CD4006	1.04	CD4030	0.50	CD4054	1.04	CD4094	1.69	CD40194	1.19
CD4007	0.18	CD4031	2.00	CD4055	1.18	CD4095	0.94	CD40257	1.48
CD4008	0.87	CD4032	0.89	CD4056	1.18	CD4096	0.94	CD4502	0.81
CD4009	0.50	CD4033	1.25	CD4059	4.29	CD4097	2.35	CD4510	1.01
CD4010	0.50	CD4034	1.71	CD4060	1.00	CD4098	0.98	CD4511	1.25
CD4011	0.18	CD4035	1.06	CD4063	0.98	CD4099	1.65	CD4514	2.47
CD4012	0.20	CD4036	2.88	CD4066	0.55	CD40100	2.50	CD4515	2.82
CD4013	0.43	CD4037	0.85	CD4067	3.35	CD40101	1.61	CD4516	1.01
CD4014	0.83	CD4038	0.96	CD4068	0.20	CD40102	2.13	CD4518	0.97
CD4015	0.83	CD4039	2.78	CD4069	0.20	CD40103	2.13	CD4520	1.04
CD4016	0.48	CD4040	0.97	CD4070	0.48	CD40104	1.10	CD4527	1.43
CD4017	0.79	CD4041	0.75	CD4071	0.20	CD40105	1.06	CD4532	1.21
CD4018	0.83	CD4042	0.69	CD4072	0.20	CD40106	0.62	CD4556	0.78
CD4019	0.50	CD4043	0.88	CD4073	0.20	CD40107	0.89	CD4558	0.78
CD4020	1.11	CD4044	0.84	CD4075	0.20	CD40108	5.38	MC14528	0.93
CD4021	0.90	CD4045	1.26	CD4076	1.17	CD40109	1.03	MC14553	4.43
CD4022	0.82	CD4046	1.20	CD4077	0.39	CD40160	1.19	IM6508	8.05
CD4023	0.18	CD4047	0.89	CD4078	0.20	CD40161	1.19		
CD4024	0.70	CD4048	0.50	CD4081	0.20	CD40162	1.19		
CD4025	0.20	CD4049	0.50	CD4082	0.20	CD40163	1.19		
CD4026	1.55	CD4050	0.43	CD4085	0.84	CD40181	3.40		

For our full range of components send for Free Catalogue

Our offices are at Chapel Street, Oxford, but please do not use this as a postal address. PRICES VALID UNTIL 31st DECEMBER 1978

OFFICIAL ORDERS ARE WELCOME from Companies, Govt. Depts, Natn. Inds, Univs, Polys. ORDERS: C.W.O. add VAT @ 8% + 35p p&p. TELEPHONE and CREDIT (invoiced) ORDERS add VAT @ 8% + 60p p&p minimum charge (the balance will be charged at cost). Please see FAST SERVICE EXPORT ORDERS welcome no VAT but add 10% (Europe) 15% (Overseas) for Air Mail p&p. For export postage rates on heavy items - contact us first

ORDERS TO: SINTEL, PO BOX 75A, OXFORD
 Tel: 0865 49791

FAST SERVICE: We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon.-Fri.) will be despatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number, with a minimum order value of £5. Official orders, no minimum.

SINTEL

THIS MONTH'S SPECIAL OFFER

"Motorola Audio Amplifier 1watt I.C."

1 watt plus into 8-16 Ω, 9-16V, 10-400 MV sensitivity. Short circuit proof, no heatsink required. **Only 90p** with Data and circuits

Sentinel Smoke and Gas Detector. This beautifully made unit uses quality components on fibreglass board, encased in heavy duty, domed diecast box, 3 1/2 diam. x 1 1/2 high. LED indicator. **TGS105** plug in sensor, 24v, or 12v by altering 3 resistors, will drive relay or lamp. Ideal for caravans, boats, kitchens, etc., etc. £6.45 with circuit and data. Suitable relay for above £1. state voltage

Miniature **Vemtron FM4 10.7MHz** ceramic filters. Data and circuits 20p

Crystal earpieces with lead 50p each, 3 for £1

Magnetic earpieces with lead and plug 40p each, 3 for £1

Ultrasonic transducers transmitter and receiver, 14mm diam 40 kcs 25p each 5 for £1

4 aluminium boxes 128 x 44 x 38mm, ideal for signal injectors, etc. £1.00

100 miniature reed switches, ideal for burglar alarms, model railways, etc. £3.30

6.6-pole 12 volt reed relays on board £2.45

High quality **computer panels** smothered in top-grade components

5lbs £4.75

10lbs £8.95

New **U.H.F. transistor TV tuners**. Rotary type with slow motion drive, aerial socket and leads £2.50

Aluminium TV coax Plus 8 for £1

Miniature edgewise panel mounting level meters 200µ a F.S.D. 90p

300 mixed resistors 1/2 & 1/4 watt £1.50

300 modern mixed caps most types £3.30

100 mixed **electrolytics** £2.20

300 mixed printed circuit components £1.50

300 mixed printed circuit resistors £1.00

100 high-wattage resistors, W.W., etc. £2.20

20 assorted **VDRs** and thermistors £1.20

25 assorted **presets**, skeleton, etc. £1.20

25 assorted **pots** and **presets** £1.50

150 mixed 1- and 2-watt resistors £1.50

100k varicap pots, can be banked side by side, very compact 10 for £1

100 mixed modern miniature ceramic and plate caps £1.20

Don't let your environment dehydrate you. BUY OUR "HONEYWELL HUMIDITY CONTROLLER". Membrane actuated, adjustable by 1/4 shaft. Ideal for greenhouses, offices, centrally heated homes, etc. 3 75A contacts at 250V. Build Humidifiers or dehydration alarms with this novel gadget at a fraction of original cost. £1 each, 3 for £2.50

Semiconductor Bargains

1000 Mixed Diodes, mostly unmarked, similar to 1N4148 etc, 70% okay £1.50

New Improved Transistor Packs: 100 New and marked transistors including BC 149, BC 154, BF 274, BC 212L, BF 200 and lots of others, **only £4.95.**

200 transistors as above and including 2N3055, AC128, BD131, BFY50, **only £9.95.**

ITT 25kV c/v eht triplers for Decca "Bradford" chassis brand new £2.50, 5 for £10

BD131 4 for £1.00

SN76115N (equivalent MC 1310) 50p

TBA 120A 50p

BF 200 6 - £1 BF 274 12 - £1

BC 212L 10 - £1 BC 148 12 - £1

BC 154 12 - £1

Deluxe Fibre Glass Printed Circuit Etching Kits

Includes 150 sq ins copper clad f/g board, 1lb ferric chloride, 1 dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions. **Only £5.30**

150 sq. ins. fibre glass board £2.00

Dalo pen 90p

1lb ferric chloride to mil spec £1.25

5lbs ferric chloride to mil spec. £5.00

Instruction sheet 20p

30p P&P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY DEPT., ETI 149A BROOKMILL ROAD, DEPTFORD, LONDON, SE8

Callers by appointment only

UNBEATABLE LOW PRICES WE STOCK PARTS TO BUILD MUSICAL PROJECTS

As published by leading magazines
 Send large s.a.e. for lists

DALSTON ELECTRONICS
 40A Dalston Lane
 Dalston Junction E8 2AZ
 Tel. 01-249 5624

HOME COMPUTING

NASCOM 1 Build and tested £267.30


Texas I.C. Sockets Low Profile Packs of 10	1/12 Scale R/C Electric Car Kit Just add Porsche or two channel R/C £44.87 Escort Body	TV GAMES Programmable TV Game in colour Main console + mains adaptor £38.90 Cartridge Price No. 1-10 games FREE (with above) No. 2 Stunt rider £20.25 No. 3 Roadrace £18.95 No. 4 Tank battle £23.50
8 pin 1.10 22 pin 1.90	4 Digit Alarm Clock chip and display G1 CK 3000 I.C. + Plasma Display £4.90	No. 2 Stunt rider £20.25
14 pin 1.20 24 pin 2.20	Microminiature Mercury Tilt Switch £1.00	No. 3 Roadrace £18.95
16 pin 1.40 28 pin 2.60	Universal Mains Adaptor 6-7 1/2-9V 250ma £2.90	No. 4 Tank battle £23.50
18 pin 1.70 40 pin 3.30	Sound Modulator £2.90	Hand controls supplied with cartridges
BC172 4p	Vision Modulator £2.90	Minimum order £1
OC28/35/36 80p	Colour Encoder £2.50	LOOK!!!
BD 133 35p	Encoder/Vision Mixer £4.90	8500 based T.V. Games £3.50. All work but have chip faults
BD 135/6/7/8 35p		Chess sets from £7.30
BD 139/40 35p		
BT106 1.00		
BU126 1.10		
DU 204/5 1.10		
TBA 800 Amp I.C. 70p		
P.C.B. Pushbutton Micro movement 35p		

All prices include P&P & VAT

NIC MODELS
 27 Sidney Road, London N22 4LP

Automatic Stereo Tuner

J. P. Macaulay

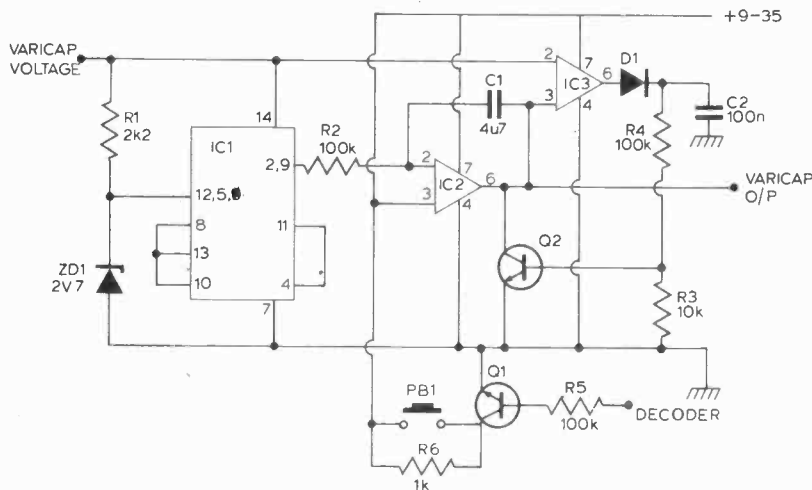

The circuit shown will automatically tune an FM tuner to stereo broadcasts only. On switch on the indicator pin of the stereo decoder is at 0V. In consequence Q1 is biased off and pins 6 and 3 of IC1 are at the positive varicap supply voltage. As this IC, a 4007, is wired as a transmission gate this voltage holds the gate on. The impedance across the gate is in the region of 300 ohms. IC2, a 741, is used as an integrator, the input voltage from across ZD1 is connected through the gate. The output of this IC therefore is a positive going ramp which is fed to the varicap tuning diodes.

On reception of a stereo broadcast the voltage at the decoder indicator pin goes positive driving Q1 into saturation and closing the transmission gate.


Since the closed position of the gate places an impedance of the order of 10^9 ohms in series with the integrator the output is "frozen" keeping the station in tune. This state of affairs continues until PB1 is pressed, whereupon the integrator will once again start to ramp positively in search of another station.

A second 741, IC3, is used as a comparator. The varicap voltage is sampled by the inverting input whilst the tuning voltage feeds the non-inverting input. As soon as the tuning voltage reaches the same level as the varicap voltage the comparator's output swings positive forward biasing Q2 and discharging C1. The circuit will now go through the entire sequence again.

The varicap voltage must not exceed 15V unless the transmission gate is operated from a stabilised supply of less than 15V output. The supply line to the op amps should be several volts greater than this.

Rain Alarm/Door Bell

S. Lamb

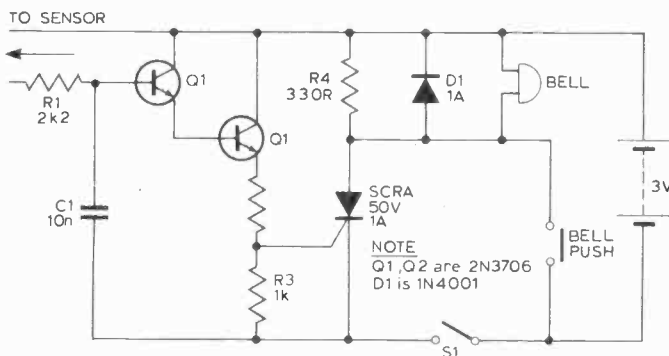


With S1 open the circuit function as a doorbell. With S1 closed, rain falling on the sensor will turn on Q1, Q2 and the thyristor will trigger activating the

bell. R4 provides the holding for the thyristor while D1 prevents any damage to the thyristor from back EMF in the bell coil. The sensor is

made from 3 square inches of copper clad board with a razor cut down the centre. C1 prevents any mains pickup in the sensor leads.

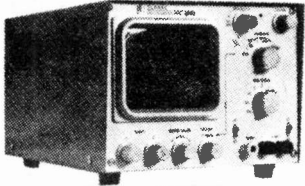BUY DIRECT FROM THE IMPORTERS AND GET MORE SCOPE FOR YOUR MONEY




SPECIFICATIONS

ELECTRICAL DATA
VERTICAL AXIS (Y) Deflection Sensitivity — 100m V/division
 Bandwidth (between 3 dB points) — DC — 5MHz. Input Attenuator — (calibrated) — 9 step 0.1, 0.2, 0.5, 1, 2, 5, 10, 20 50/div.
 Input Impedance — 1 Meg/40 pF in shunt. Input Voltage — Max — 600V P P
HORIZONTAL AXIS (X) Deflection Sensitivity — 0.400mV/division
 Bandwidth (between 3 dB points) — 1Hz-350KHz. Gain Control — Continuous when time bases in EXT position. Input Impedance — 1 Meg. Input Voltage — Max — 600V P P
TIME BASE Sweep Range (calibrated) — 100msec/div to 1µ sec/div in 5 steps FINE Control — Variable between steps — includes time-base calibration position. Blanking — Internal — on all ranges
SYNCHRONISATION Selection — Internal, external Synchronisation Level — Continues from positive to negative
POWER SUPPLY Input voltage — 115/220V AC± 10% at 50/60Hz Power Dissipation — 18W
CRT DATA — 4in — flat face, single beam — Maximum high voltage — 1.5kV — Fitted with 8x10 division blue filter graticule.
PHYSICAL DATA Dimensions — 15cm(h)x20.5cm(w)x28cm(d) Weight — 4.3kg(approx.) Stand — 2 position flat and inclined. Case — Steel, epoxy enamelled. Front panel — Aluminium, enamelled epoxy printing

Test leads available £2.00


Cash with order
£99 (+ £7.92 V.A.T.)

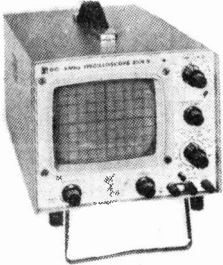

6 MHz OSCILLOSCOPE

Large 5" flat CRT.
 DC to 6MHz bandwidth.
 10mV to 50V/cm in 12 calibrated steps.
 0.5µs to 0.1 Sec/cm sweep range in 6 calibrated steps plus 12 1 Vernier.
 Magnifier x5.
 Fully automatic trigger.
 DC to 1.5MHz horizontal bandwidth.

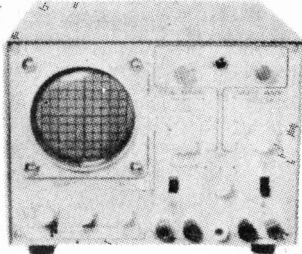£120 (+ V.A.T.) S.a.e. for further details.



3 inch medium-persistence tube response up to 5 MHz (—3dB) — good enough for colour TV work adjustable +ve, —ve or external sync.

External x-input
 y-sensitivity down to 10mV/div
 Timebase 100ms/div to 1 us/div in 5 steps.
 Dimensions 15cmx20cmx28cm.
 Weight 3.8kg (8½ lbs)

£89 (inc. V.A.T. & P & P)

Model 2201. Function Generator. Sine, square, triangle + mixed wave forms. 0.02Hz-2MHz, range, 1mV to 10V pp into 50Ω, variable symmetry to 20:1, VCO range of 1000:1, constant duty cycle pulse operation, DC offset to ± 10V. **£138** (+ V.A.T.)

Model 2205. AM/FM Sweep Function Generator. Has all the basic specification of the 2201 (above) plus internal or external AM/FM, 400-1000Hz. Internal modulation 0-100%, adjustable AM depth, 1000:1, sweep range

£246 (+ V.A.T.)

KRAMER & CO.
 9 October Place, Holders Hill Road
 London NW4 1EJ. Telex: 888941
 attn. Kramer k7. Tel: 01-203 2473
 Mail order only. Callers by appointment

SEMICONDUCTOR OFFERS ALL FULL SPEC.

Common anode 0.3 7 seg displays Toshiba type TLR303 65p. F.E.T.s. similar to 2N3819 18p. Mosfet Sim to 40673 35p. 3N140 Mosfets 50p. M203 Dual Matched Pairs Mosfets Single Gate per F.E.T. 40p. Intel 1024 bit MOS Rams 95p. Mullard 8B113 Triple Varicap Diode 35p. MC1310 Stereo Decoder I.C.s £1.20. CD4051 CMOS 50p. 741 8-pin D I L 23p. 500V 600mA Bridge Recs (ex equip.) 25p. 1N4002 100V 1A Diodes 4p. 1400S 800V 1A Diodes 7p. E.H.T. SIL Rec 15kV 2.5mA. 15mm x 5mm 30p. 7812 12V 1A Plastic V. Regs 95p. Min. Nixies ITT 5870Si 13 x 6mm Fig Size 85. Nixies ITT GN/9A 13 x 8mm 65p. 0.2 or 0.125 Red LEDs 12p each. MAN3A 3mm LED Displays 50p. 741S (wide bandwidth) 35p. LM380 80p. LM381 90p. ZN414 75p. TIL305 Alpha-numerical Displays, with data. £2.75. DRP61, Mullard, new, boxed 30p. Special Offer: SGS TBA800 ICs, 10 for £5.00.

MICROPHONES. EM506 Condenser Mikes, Uni-directional, F.E.T. Amp. Dual imped., 50K/600ohms, 30-18KHz, on/off switch, £11.00. Miniature Tie Pin Condenser mike 1K imp., omni-directional, uses hearing aid battery (supplied) £4.95. Grundig Electret Inserts with built-in F.E.T. Preamp £1.50. Crystal Mike Inserts 37mm 45p. Electret Condenser Mikes 1KΩ Imp with std. Jack Plug £2.85. Cassette Condenser Mikes with 2.5 and 3.5 Jack Plugs £2.85. Standard Cassette Mikes 200 ohm Imped with 2.5 and 3.5 Jack Plugs £1.20.

MORSE KEYS — Hi-speed Type, all metal, £2.25. Plastic Morse Keys, 95p. Belling Lee L4305 Masthead Amplifiers and 240v AC power unit Group "A" UHF Only £7.50.

CRYSTALS. 300KHz HC6U 40p. 0.1 Edge Connectors. 64 way 65p. 32 way 40p.

RELAYS. Min. 220v AC Sealed Relay 2 pole C/O 45p. 240v AC Sealed Relay 3 pole C/O 5 amp Contacts 11-pin base 80p. 12 volt 4 pole N/O Reed Relay 20p. Min. 24v DC Sealed 2-pole C/O relays 3-amp contacts. New 55p. 12v DC 4pc.c. open type, new 50p each.

MOTORS. 1.5 to 6v DC Model 20p. 115v AC min 3 R.P.M. with Gearbox 30p. 240v AC Synchron Motor 1/5th R.P.M. 65p. 240v AC Synchron Motor 1/24th R.P.M. 65p. Crouzet 115v AC 4 R.P.M. Motors, new 95p. 12v DC 5-pole 35p.

BOXES. Black A B S Plastic with brass inserts and lid, 75 x 56 x 35mm 40p. 95 x 71 x 35mm 49p. 115 x 95 x 16mm 57p. 225 x 130 x 84mm £1.95

TOOLS. Radio pliers, 5in, insulated handles £1.40. Diagonal side cutters, 5in, insulated handles £1.40.

MAINS TRANSFORMERS, all 240v AC primary. Postage shown in brackets per transformer.
 6.0-6 100mA, 9.0-9 75mA, 12.0-12 50mA, 75p each (15p)
 0.4-6.9 150mA, no mounting bracket, 65p (20p) 12.0-12 100mA, 95p (15p), 12v 500mA, 95p (22p), 12v 2 Amp, £2.25 (45p), 12v 4 Amp, £2.75 (54p), 15.0-15v 1 Amp, £2.10 (45p) 30.0-30v 1 Amp, £2.75 (54p) 0-12-15-20-24-30v tapped at 2 Amp, £4.50 (54p) 20.0-20v 2 amp, £3.50 (54p) 25v 1.5 Amp, £1.45 (45p) 18v 1.5 Amp rectified, £2.00 (45p) 35v, 2 Amp, 2.5v 2 Amp toroid, £2.95 (54p) 20v 2.5 Amp, £2.20 (54p), 1 1 Xenon/tnac pulse transformer, 30p

SWITCHES — Min Toggle, SPST 8 x 5 x 7mm 45p. DPDT 8 x 7 x 7mm 60p. DPDT Centre Off 12 x 11 x 9mm 75p. DPDT C/O Sliders 20p. R S Single Pole C/O Push Buttons 45p. Roller Micro Switches 15p. Min. Micro Switches 13 x 10 x 4mm 20p. Min Push to make or push to break Switches 16 x 6mm 15p.

SOLDER SUCKER, Plunger type, eye protection, replaceable nozzle, high suction, £4.95. Reed switches 28mm norm. open, 6p each.

TAPE HEADS — Cassette Stereo £3.00, BSR MN 1330 1/2 Track Dual Impedance Rec / Playback 50p. BSR SRP90 1/4 Track Stereo Rec / Playback £1.95. TD10 Assemblies, two heads, 1/4 Track Rec / Playback Staggered Stereo with built-in erase per head £1.20. Tape Head Demag 240v AC £1.95.

BUZZERS — GPO Type 6-12v 20p. Min. Solid State Buzzers 6-9-12 or 24v 15mA 75p. All Metal Buzzer, 30mm diam, 6-12 volts, high tone, 25p.

U.H.F TV Transistorised Push Button Tuners (not Varicap), new and boxed, £2.50

MURATA MA401L, 40kHz Transducers, rec./send, £3.25 pair

METERS — Grundig Batt Level Meter 1mA 40 x 40mm £1.10. Min. Level Meter 200µa 25 x 15mm 75p. Ferranti 600v AC Meter £3.95

EDGE METER — Large scale 0-100, new £2.75

POT CORE UNIT. Has 6-pot cores, including 1 FX2243 (45mm) and 2 FX2242 (35mm), 3 20mm Panel Fuseholders, 3 TO3 SIL Power Transistors on heat sink, panel with various transistors and diodes with a 5-amp plastic S.C.R. New £1.75 + 75p P&P

LA1230 adj. core 15mm dia. 14mH-18mH. HI, O, 10p each

8 TRACK 12 volt motors new, £1.25
CASSETTE MOTORS 6 volt new, £1.25

SOLENOIDS — 240v AC 45p. 12v OC H Duty 75p. 240v 25lb 2 travel £3.95.

12-WAY MOTORISED CAM UNITS. 50v AC low rev. motor driving 12 C/O micro switches, supplied with a capacitor for 240v AC use. Ex equip. £1.95 + 35p P&P.

13 Amp rubber trailer extension sockets, 38p.

8 WAY RIBBON-CABLE, min solid core, 15p metre

POSTAGE 30p UNLESS OTHERWISE SHOWN (EXCESS POSTAGE REFUNDED WITH ORDER) OVERSEAS POST AT COST VAT INCLUDED IN ALL PRICES


S A E FOR LISTS

ORDER ADDRESS

PROGRESSIVE RADIO
 31 CHEAPSIDE, LIVERPOOL 2
 051-236 0982

HI-PERFORMANCE ELECTRONIC (CAPACITOR DISCHARGE) IGNITION UNIT

... Good for your car and your pocket

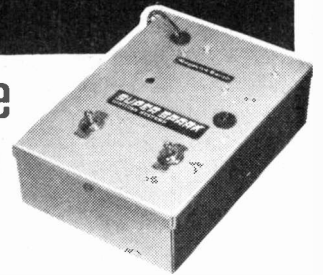

Fit one to-day and SAVE, SAVE, SAVE!

Why pay more when you can enjoy the advantages of true capacitor discharge ignition (CDI) at virtually pre-inflation prices? The benefits to your car and your pocket are enormous — easy starting in the coldest of cold weather, an end to burnt contacts and arcing problems, better engine wear and petrol consumption and, of course, easy and secure fitting to your vehicle. ORDER NOW WHILE WE CAN HOLD TO THESE PRICES — State if pos. or neg. earth.

INC. V.A.T. AND POST FREE IN U.K.

READY BUILT ONLY

£14.95

DIY KIT COMPLETE

£12.75

Why be without?

- MADE IN OUR OWN U.K. FACTORY
- SWITCH FOR INSTANT RETURN TO ORDINARY IGNITION
- NEG. OR POS. EARTH MODELS
- HEAVY GAUGE ENCLOSED METAL CASE
- BUILT FOR YEARS OF DEPENDABLE SERVICE
- FULL 12 MONTHS' GUARANTEE

Pay by Access or Barclaycard if you wish

STIRLING SOUND
 37 VANGUARD WAY, SHOEBOURNESS, ESSEX
 Tel (03708) 5543
 Shop — 222/224 West Road, Westcliff-on-Sea

To Stirling Sound, 37 Vanguard Way, Shoeburyness, Essex

Please send Mark 5 Ready Built @ £14.95

Kit @ £12.75

NAME

ADDRESS

ET 12

AT BREADBOARD '78 Stand D3



Unijunction Pulse Stretcher — Door Bell Extender

D. Wedlake

The circuit presented is a practical monostable timer which was designed to extend the ringing time of a door bell. It can be useful in cases when the bell push button might not be engaged long enough to attract attention, though it could be used in many other applications.

When the push button is closed the thyristor will switch on delivering power to the unijunction transistor timing circuit and energising the relay, the contacts of which are used to control the bell circuit. At the same time, capacitor C2 quickly charges to the load voltage potential via R3. After a time interval given approximately by $0.8 C1 R1$ (about 6 seconds in this case) the unijunction transistor will fire and the corresponding output pulse which is coupled to

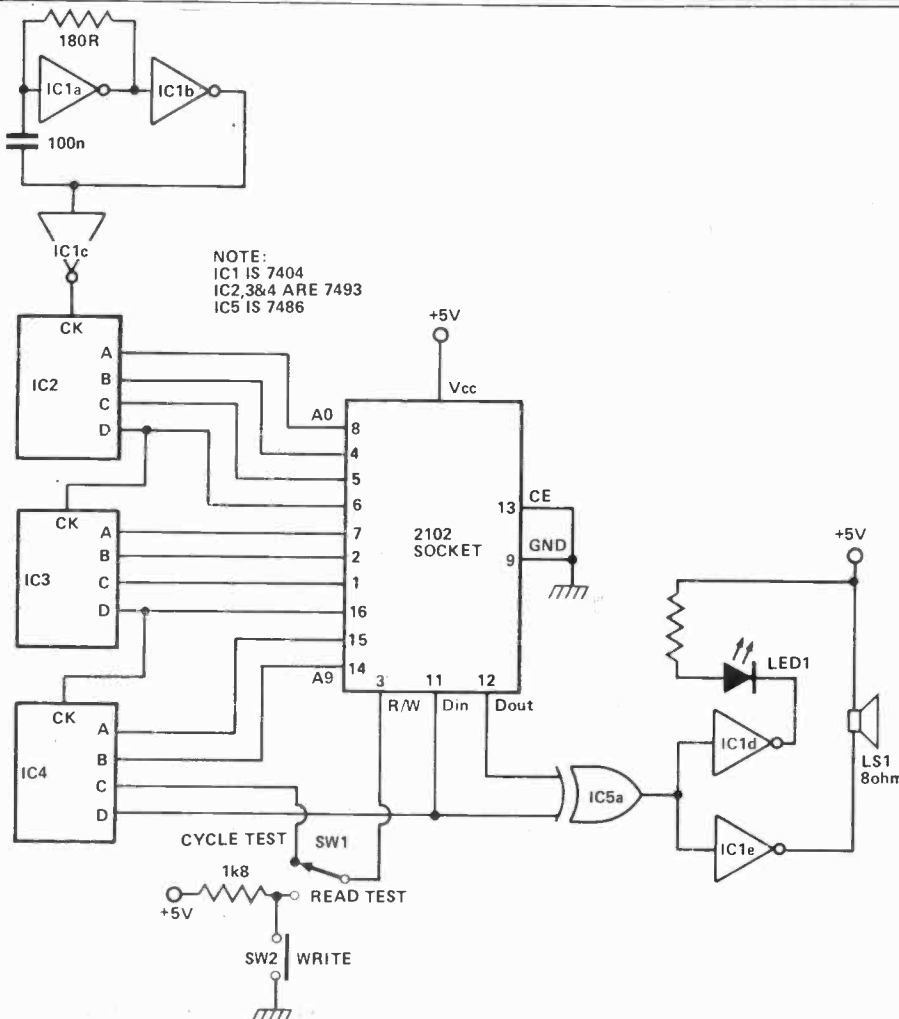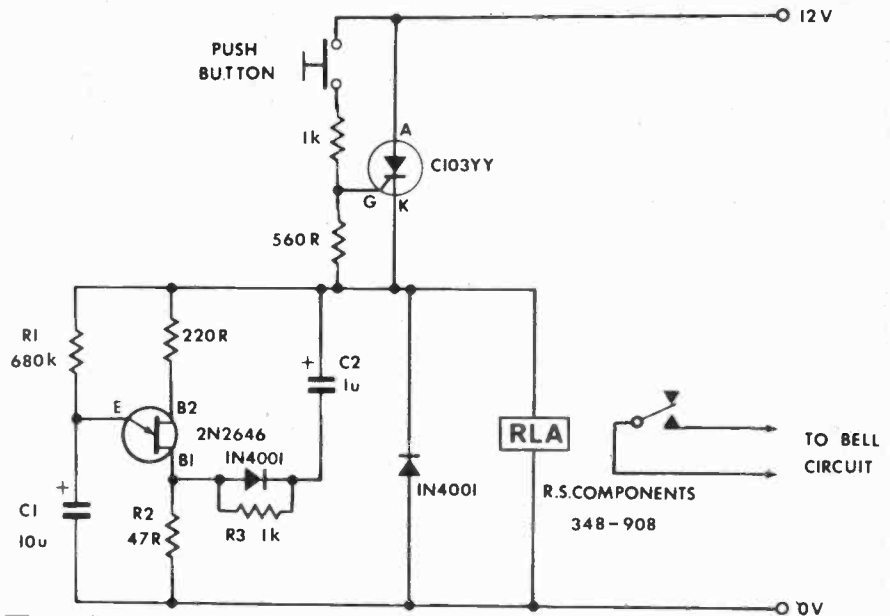the cathode of the thyristor via C2 will put the thyristor in reverse bias switching it off. With these values the relay will become energised for at least 6 seconds.



2102 Memory Tester

S. Sunderland

This circuit provides for the testing of 1024 Bit X1 memories, such as the 2102 series, in two modes. Mode-1 cycles the memory continuously through write and read, alternately writing zeros and ones then reading to ensure the write was successful. Mode-2 allows the write of a signal onto the memory, then continuously reads it to ensure the data is stable.


In both modes, the output from the memory is compared with what should be there, and if there is a difference, an LED flashes, accompanied by a click from the speaker. In mode-2, on power on, a continuous noise will be heard from the speaker, on pressing the 'WRITE' button this should vanish, similarly, a brief pulse of noise will be heard in mode-1 before the write is completed. The oscillator frequency is about 20 kHz with components shown.

In mode-2, when the supply voltage drops below 4.5V memory is not stable for more than a fraction of a second, although this does not show up using mode-1.

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS

STEREO PRE-AMPLIFIERS

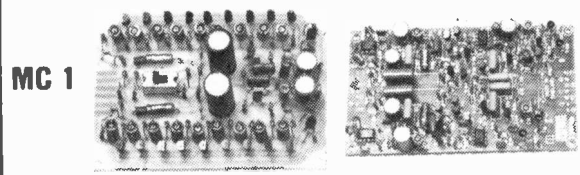

CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3mV, distortion < 0.05% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc., up to power amp signal levels. Signal to noise ratio 86dB, slew-rate 3V/μs; T.H.D. 20Hz - 20kHz < 0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ±15 volts.

MC 1 PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170μV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

REG 1 — POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS



It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc., who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification. T.H.D. typically 0.1% any power 1kHz 8 ohms. F.O. insignificant, slew rate limit 25V/μs, signal to noise ratio 110dB, frequency response 10Hz-35kHz, -3dB, stability unconditional; protection drives any load safely, sensitivity 775mV (250mV or 100mV on request), size 120 x 80 x 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER AMPLIFIER KIT

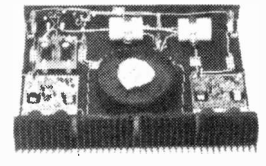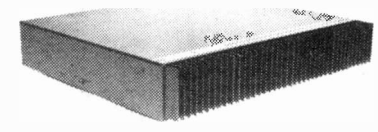The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



POWER AMPLIFIER MODULES

CE 608	60W/8 ohms 35.0-35v	£16.30
CE 1004	100W/4 ohms 35.0-35v	£19.22
CE 1008	100W/8 ohms 45.0-45v	£23.22
CE 1704	170W/4 ohms 45.0-45v	£29.12
CE 1706	170W/8 ohms 60.0-60v	£31.90

TOROIDAL POWER SUPPLIES

CPS1	for 2 x CE 608 or 1 x CE 1004	£14.47
CPS2	for 2 x CE 1004 or 2/4 x CE 608	£16.82
CPS3	for 2 x CE 1008 or 1 x CE 1704	£17.66
CPS4	for 1 x CE 1008	£15.31
CPS5	for 1 x CE 1708	£22.68
CPS6	for 2 x CE 1704 or 2 x CE 1708	£23.98

HEATSINKS

Light duty, 50mm, 2 C/W	£1.30
Medium power, 100mm, 1.4 C/W	£2.20
Disc/group, 150mm, 1.1 C/W	£2.85
Fan, 80mm, state 120 or 240v	£18.60
Fan mounted on two drilled 100mm heatsinks, 2 x 4 C/W, 65 C max with two 170W modules	£29.16

THERMAL CUT-OUT, 70 C £1.90

POWER AMP KIT £32.40

PRE-AMPS: These are available in two versions — one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPR1	£29.49	CPRIS	£39.98
MCI	£18.50	MCIS	£29.49

POWER SUPPLY:

REG1	£6.75	TR6	£1.75
------	-------	-----	-------

BRIDGE DRIVER, 80I
Obtain up to 340W using 2 x 170W amps and this module 80I £5.40

CRIMSON ELEKTRIK
1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COO 90p extra. £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

TRANSISTORS	8C328 15p	8U208 160p	2N4061 12p	7490 32p	74194 92p	4501 19p	DIODES	18p	ZENER DIODES 400mW	10p
AC126 18p	8C338 15p	OC25 76p	2N4062 20p	7491 65p	74195 85p	BY127 59p	BY127 18p	2.7V to 33V		
AC127 17p	8C547 11p	OC28 108p	2N4123 23p	7492 45p	74196 92p	0A47 10p	0A47 10p			
AC128 24p	8C548 10p	OC35 108p		7493 34p	74197 92p	0A81 15p	0A81 15p	VERO BOARDS 0.1" copper		
AC141 24p	8C549 11p	OC71 19p		7494 80p	74198 150p	0A200 6p	0A200 6p	2.5" x 5"	57p	
AC142 24p	8C557 14p	OC72 34p		7495 55p	74199 150p	0A202 9p	0A202 9p	3.75" x 5"	67p	
AC151 42p	8CY30 67p	OC84 46p	TTL	7496 62p		0A204 4p	0A204 4p			
AC152 53p	8CY34 74p	OC84 46p	TIP29 40p	7497 240p	CMOS	0A204 4p	0A204 4p			
AC153 56p	8CY59 24p	TIP30 40p	TIP30 40p	7400 7400	4000 15p	0A204 4p	0A204 4p	CERAMIC CAP 50V	2p	
AC176 18p	8CY70 14p	TIP31 50p	TIP31 50p	7401 7401	4001 15p	0A204 4p	0A204 4p	22pF to 47000pF		
AC187 23p	8CY71 14p	TIP32 55p	TIP32 55p	7402 7402	4002 16p	0A204 4p	0A204 4p			
AC188 23p	8O115 52p	TIP33 75p	TIP33 75p	7403 7403	4006 110p	0A204 4p	0A204 4p	POLYESTER CAP 250V		
AD149 65p	8O121 79p	TIP34 98p	TIP34 98p	7404 7404	4006 110p	0A204 4p	0A204 4p	.01, .015, .022, .033, .047, .068, .1 uF	5p	
AD161 38p	8O123 79p	TIP35A 253p	TIP35A 253p	7405 7405	4007 16p	0A204 4p	0A204 4p	.15, .22, .33	7p	
AD162 38p	8O124 97p	TIP36A 389p	TIP36A 389p	7406 7406	4007 16p	0A204 4p	0A204 4p	.47, .68 uF	13p	
AF114 30p	8O131 35p	TIP41A 59p	TIP41A 59p	7407 7407	4008 15p	0A204 4p	0A204 4p	1 uF	17p	
AF118 30p	8O132 35p	TIP42A 59p	TIP42A 59p	7408 7408	4011 15p	0A204 4p	0A204 4p	2.2 uF	28p	
AF125 27p	8O135 38p	TIP2955 126p	TIP2955 126p	7409 7409	4012 16p	0A204 4p	0A204 4p	6.8 uF	48p	
AF126 27p	8O136 36p	TIP3055 64p	TIP3055 64p	7410 7410	4012 16p	0A204 4p	0A204 4p			
AF127 27p	8O137 38p	ZTX108 14p	ZTX108 14p	7411 7411	4013 35p	0A204 4p	0A204 4p	ELECTROLYTIC CAP 25V		
AF139 36p	8O138 38p	ZTX109 14p	ZTX109 14p	7412 7412	4013 35p	0A204 4p	0A204 4p	1 uF to 47 uF	7p	
AF186 54p	8O139 35p	ZTX300 16p	ZTX300 16p	7413 7413	4014 108p	0A204 4p	0A204 4p	68uF, 100uF	8p	
AF239 40p	8O140 35p	ZTX500 16p	ZTX500 16p	7414 7414	4015 80p	0A204 4p	0A204 4p	150uF	9p	
ASYS3 81p	8F115 25p	2N706 13p	2N706 13p	7415 7415	4016 80p	0A204 4p	0A204 4p	220uF	10p	
ASYS4 81p	8F167 29p	2N1131 23p	2N1131 23p	7416 7416	4017 65p	0A204 4p	0A204 4p	330uF	12p	
ASYS5 69p	8F173 27p	2N1132 23p	2N1132 23p	7417 7417	4018 90p	0A204 4p	0A204 4p	470uF	15p	
8C107 8p	8F178 34p	2N1302 38p	2N1302 38p	7418 7418	4019 65p	0A204 4p	0A204 4p	RESISTORS 0.25W	1p	
8C108 8p	8F179 37p	2N1304 54p	2N1304 54p	7419 7419	4020 95p	0A204 4p	0A204 4p	4.7 ohms to 1 Mohm		
8C109 8p	8F180 37p	2N1305 25p	2N1305 25p	7420 7420	4021 98p	0A204 4p	0A204 4p	POTENTIOMETERS (carbon)	26p	
8C113 17p	8F181 37p	2N1306 39p	2N1306 39p	7421 7421	4022 85p	0A204 4p	0A204 4p	5 Kohm to 1 Mohm log switched	60p	
8C117 20p	8F182 37p	2N1308 40p	2N1308 40p	7422 7422	4023 15p	0A204 4p	0A204 4p	PRESETS 0.1W horizontal	8p	
8C119 29p	8F183 37p	2N1613 22p	2N1613 22p	7423 7423	CMOS	0A204 4p	0A204 4p	100 ohm to 1 Mohm		
8C140 34p	8F184 28p	2N1711 21p	2N1711 21p	7424 7424	68p	0A204 4p	0A204 4p	TRANSFORMERS 240V primary	95p	
8C142 27p	8F185 30p	2N1893 44p	2N1893 44p	7425 7425	15p	0A204 4p	0A204 4p	6-0-6V 100mA	360p	
8C143 27p	8F194 13p	2N2217 27p	2N2217 27p	7426 7426	35p	0A204 4p	0A204 4p	0-6Vx2 1AX2	250p	
8C147 7p	8F196 13p	2N2219 21p	2N2219 21p	7427 7427	70p	0A204 4p	0A204 4p	9-0-9V 1A	290p	
8C149 8p	8F197 16p	2N2369 16p	2N2369 16p	7428 7428	100p	0A204 4p	0A204 4p	9-0-9V 2A	400p	
8C157 9p	8F198 16p	2N2483 26p	2N2483 26p	7429 7429	15p	0A204 4p	0A204 4p	0-12V 2A	370p	
8C158 9p	8F200 36p	2N2484 22p	2N2484 22p	7430 7430	24p	0A204 4p	0A204 4p	0-15Vx2 200mAx2	240p	
8C159 9p	8F224 16p	2N2905 22p	2N2905 22p	7431 7431	24p	0A204 4p	0A204 4p			
8C168 8p	8F257 37p	2N2906 22p	2N2906 22p	7432 7432	24p	0A204 4p	0A204 4p			
8C170 9p	8F258 40p	2N2907 22p	2N2907 22p	7433 7433	24p	0A204 4p	0A204 4p			
8C171 9p	8F259 44p	2N2926 10p	2N2926 10p	7434 7434	24p	0A204 4p	0A204 4p			
8C172 9p	8F299 30p	2N2926 8p	2N2926 8p	7435 7435	24p	0A204 4p	0A204 4p			
8C173 9p	8F299 30p	2N3053 18p	2N3053 18p	7436 7436	24p	0A204 4p	0A204 4p			
8C182 10p	8F299 30p	2N3054 50p	2N3054 50p	7437 7437	24p	0A204 4p	0A204 4p			
8C183 10p	8F299 30p	2N3055 50p	2N3055 50p	7438 7438	24p	0A204 4p	0A204 4p			
8C184 10p	8F299 30p	2N3072 8p	2N3072 8p	7439 7439	24p	0A204 4p	0A204 4p			
8C186 23p	8F330 38p	2N3703 8p	2N3703 8p	7440 7440	24p	0A204 4p	0A204 4p			
8C187 26p	8F385 29p	2N3704 8p	2N3704 8p	7441 7441	24p	0A204 4p	0A204 4p			
8C207 13p	8F386 31p	2N3706 9p	2N3706 9p	7442 7442	24p	0A204 4p	0A204 4p			
8C212 10p	8F387 20p	2N3707 9p	2N3707 9p	7443 7443	24p	0A204 4p	0A204 4p			
8C213 10p	8F550 15p	2N3710 8p	2N3710 8p	7444 7444	24p	0A204 4p	0A204 4p			
8C214 10p	8F551 15p	2N3711 8p	2N3711 8p	7445 7445	24p	0A204 4p	0A204 4p			
8C237 14p	8F553 28p	2N3772 177p	2N3772 177p	7446 7446	24p	0A204 4p	0A204 4p			
8C238 14p	8SX19 25p	2N3773 230p	2N3773 230p	7447 7447	24p	0A204 4p	0A204 4p			
8C301 30p	8SX20 21p	2N3866 61p	2N3866 61p	7448 7448	24p	0A204 4p	0A204 4p			
8C303 36p	8U205 140p	2N3904 8p	2N3904 8p	7449 7449	24p	0A204 4p	0A204 4p			


Add 25p for p&p. All items new and full spec

DELTA TECH & CO.
62 NAYLOR ROAD, LONDON, N20 0HN

wonderboard

patents pending

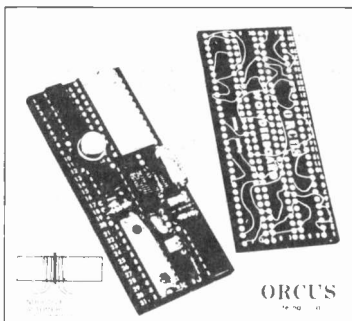Build
Your Circuits
Just Once
In Minutes...



It's crazy to build, unbuild, construct and destruct your circuits on expensive "Breadboards". Now very economically on WONDERBOARD, you plug your components into one side of the board, the wires into the other, and you install the finished circuit in your equipment. They're like PC boards, but no soldering (which is enemy No. 1 of prototypes). Change any wire or component any time without disturbing others. Up to six interconnecting wires and one component lead into one multicontact. WONDERBOARDS accept all IC's from 4 to 60 pins and discrete components too.

Reliable? They conform to applicable sections of USA Military Standard MIL-A 46 146 and are used by the US Navy. You can't ask for better. WONDERBOARDS the universal board for equivalents of single-sided, double-sided, plated-thru hole, and multilayer printed circuits.

"Small Wonder"
12 IC DIL-14 capacity
(Equiv. No. tie points 1302)

£2.80

"Big Wonder"
48 IC DIL-14 capacity
(Equiv. No. tie points 5208)

£11.20

All prices include VAT and P&P. Send cheque or postal order to:-

CHARCROFT ELECTRONICS LIMITED
Charcroft House, Sturmer, Haverhill, Suffolk CB9 7XR
Telephone Haverhill (0440) 5700 Telex 817574

See us at BREADBOARD '78 21st-25th November '78
Seymour Hall, London W1. Stand F10

SOLDERLESS CIRCUIT BOARDS
"One for each circuit"

DORAM

SEE THE
RANGE OF BOOKS IN THE NEW
DORAM HOBBIES
CATALOGUE.



Doram Electronics Ltd
PO Box TR8, Leeds LS12 2UF

Please send my FREE Hobbies Catalogue.

I enclose 25p contribution to p. & p. (AVAILABLE LATE SEPT)

Name.....


Address.....

ET19

DORAM

Doram Electronics Ltd
PO Box TR8, Leeds LS12 2UF

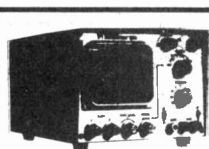Overseas customers (except for N. Ireland)-60p
including despatch by Air (or all-up post).



AS RECOMMENDED BY
ELECTRONICS TODAY
INTERNATIONAL
JULY 1978

4" Oscilloscope

ALTERNATIVE MODEL
3" OSCILLOSCOPE

otherwise specification as 4" model

£83.25

Add VAT £6.66
Carriage £1.50

FROM STOCK
SOLE UK
IMPORTERS

FROM STOCK

£99

Add VAT £7.92
Carriage £2.08

Appointed
London Stockist

SPECIFICATIONS

ELECTRICAL DATA

VERTICAL AXIS (Y)

Deflection Sensitivity

Bandwidth (between 3 dB points)

Input Attenuator - (calibrated)

Input Impedance

Input Voltage - Max

- 100mV/division
- 0C-5MHz
- 3 step 0.1, 0.2, 0.5, 1, 2, 5, 10, 20 50V/div
- 1 Meg/40 pf in shunt
- 600V P.P.

HORIZONTAL AXIS (X)

Deflection Sensitivity

Bandwidth (between 3dB points)

Gain Control

Input Impedance

Input Voltage - Max

- 0-400mV/division
1Hz-350kHz
- Continuous, when time base in EXT position
- 1 Meg
600V P.P.

TIME BASE

Sweep Range (calibrated)

FINE Control

Blanking

- 100msec/div to 1µ sec/div in 5 steps
- Variable between steps - includes timebase calibration position
- Internal - on all ranges

SYNCHRONIZATION

Selection

Synchronization Level

- Internal, external
- Continues from positive to negative Input Voltage
- 18V

POWER SUPPLY

Power Dissipation

- 4in. - flat face, single beam
- Maximum high voltage - 1.5kV
- Fitted with 8x10 division blue filter graticule

CRT DATA

PHYSICAL DATA

Dimensions

Weight

Stand

Case

Front Panel

- 14cm (h) x 20.5cm (w) x 28cm (d)
- 4.3kg (approx)
- 2 position, flat and inclined
- Steel, epoxy enamelled
- Aluminium, enamelled epoxy printing

Also from 248 Tottenham Court Road, London W1
301 Edgware Road, London W2

Henry's
RADIO

All mail to: Henry's Radio 404 Edgware Rd, London W2

LONDON W2: 404 6 Edgware Road. Tel: 01 723 1008

SINCLAIR PRODUCTS'

Microvision TV £172. PDM35 £27.25, mains adaptor £3.24, case £3.25. 30kv probe £18.95. DM235 £47.50. Rechargeable battery units £7.95. Adapter/charger £3.70. Case £8.50. 30kv probe £18.95. Cambridge prog calculator £13.15, prog. library £2.95, mains adaptor £3.20. Enterprise programmable calculator £20.95.

S-DECS AND T-DECS'

S-Dec £3.39, T-Dec £4.44, µ-DeCA £4.52, µ-DeCB £6.73, 16 dil or 10T05 adaptors with sockets £2.14.

CONTINENTAL SPECIALITIES PRODUCTS'

EXP300 £6.21. EXP350 £3.40. EXP600 £6.50. EXP650 £3.89. EXP48 £2.48. PB6 £9.94. PB100 £12.74. LM1 £30.99. LP1 £33.48. LP2 £19.44.

TV GAMES

Send s a e for free data AY-3-8500 - chip £4.95, economy kit £4. Tank battles - AY 3 8710 chip £6.90, economy kit £7.05. Stunt cycle - AY-3-8760 chip £6.90, economy kit £5.60. 10 game paddle 2 chip - AY-3-8600 plus economy kit £12.50. Racing car chip - AY-3-8603 plus economy kit £19.95. Modified shoot kit £4.95. Rifle kit £4.95. Colour generator kit £7.50.

MAINS TRANSFORMERS

6.0-6V 100ma 79p, 1½ £2.35, 6 3V 1½ £1.89, 9-0-9V 75ma 79p, 1a £1.99, 2a £2.60, 12-0-12V 50ma 79p, 100ma 90p, 1a £2.49, 13V ½ 95p, 15-0-15V 1a £2.79, 30-0-30V 1a £3.59.

JC12, JC20 AND JC40 AMPLIFIERS

A range of integrated circuit audio amplifiers supplied with free data and printed circuits. JC12 6 watts £1.60. JC20 10 watts £2.95. JC40 20 watts £3.95. Send s a e for free data on our range of matching power and preamp kits

FERRANTI ZN414

IC radio chip £1.05. Extra parts and pcb for radio £3.85, case £1. Send s a e for free data

PRINTED CIRCUIT MATERIALS

PC etching kits economy £1.70, standard £3.82. 50sq ins pcb 40p, 1 lb FeCl1 £1.05, etch resist pens economy 45p, dialo 73p, small drill bits 1/32 ins or 1mm 20p each etching dish 68p, laminate cutter 75p.

BATTERY ELIMINATORS

3-way models with switched output and 4-way multi-pack 3/4V/6V 100ma £2.71, 6/7½/9V 300ma £2.95, 100ma radio models same size as a PP9 battery with press stud connectors. 9V £3.35, 6V £3.35, 4½V £3.35, 9V+9V £4.50, 6V+6V £4.50, 4½V+4½V £4.50, cassette recorder mains unit 7½V 100mA with 5 pin din plug £3.35, car converters 12V dc input, output 9V 300ma £1.50, output 7½V 300ma £1.60, output 3/4V/1/2V 800ma £2.50.

BATTERY ELIMINATOR KITS

Send s a e for free leaflet on range 100ma radio types with press stud connectors 4½V £1.80, 6V £1.80, 9V £1.80, 4½+4½V £2.50, 6+6V £2.50, 9+9V £2.50, cassette type 7½V 100ma with din plug £1.80, heavy-duty 13 way types 4½/6/7/8½/11/13/14/17/21/25/28/34/42V 1 Amp £4.65, 2 Amp £7.25, transistor stabilized 8-way types for low hum 3/4V/6/7½/9/12/15/18V 100ma £3.20, 1 Amp £6.40. Variable voltage stabilized models 2-18V 100ma £3.60, 2-30V 1A £6.95, 2-30V 2A £10.95. Car converters 12V dc input, output 9/7½/6V 1A stabilized £1.95.

BI-PAK AUDIO MODULES



Send s a e for data S450 tuner £23.51, AL60 £4.86, PA100 £16.71, SPM80 £4.47, BM780 £5.95 MK60 £38.74, Stereo £20.12.

BULK BUY OFFERS

Minimum purchase £3 any mix from this section 1N4148 1.4p, 1N4002 3.6p, BC212 8p, 741 8d 15p, NE555 8d 23p, 723 14d 43p, AC76023N exact equi of SN76023N with improved heat sink 85p. Plastic equips of popular transistors BC107 4.7p, BCY71 4.9p, BCY72 4.7p. Fuses 20mm x 5mm cartridge 25 5. 1. 2. 3 5Amp quickblow type 1p, antsurge type 3.4p. Resistors 5% E12 10 ohm to 10M. ¼W 0.9p, 1W 1.9p. Polyester capacitors 250V 01 022. 033. 047mf 2.7p, 015mf 1.5p, 068mf 1.5p, 0 1mf 1.5p, 0 22mf 3p, 0 33mf 2.5p, 0 47mf 4.5p. Polystyrene capacitors E12 63V 15 to 10,000pf 2½p. Ceramic capacitors 50V E12 22pf to 1000pf 1.7p. 6E 1500pf to 3300pf 1.7p, 47000pf 2p. Electrolytics 50V, 47 1 2mf 5p, 25V 5mf 5p, 10mf 5p, 18V 22mf 5p, 33 47 100mf 6p, 220 330mf 9p, 470mf 11p, 1000mf 10p. Zeners 400mW E24 2V to 33V 6.1p. Preset pots sub-miniature 0 1W horiz or vert 100 to 4M 7.6p. Potentiometers ¼W 4K7 to 2M2 log or lin single 26p, dual 76p.

SWANLEY ELECTRONICS

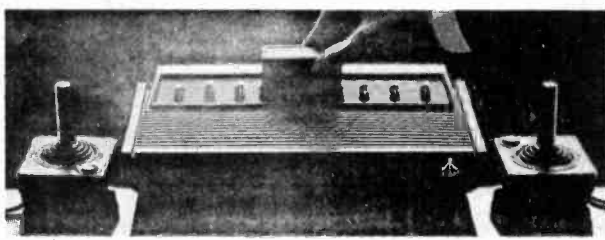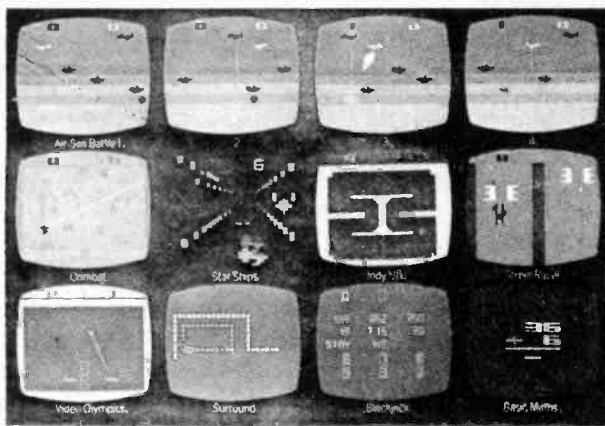DEPT. ET1, 32 Goldsel Road, Swanley, Kent BR8 8EZ
Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked * and 11% on others. Official credit orders welcome



THE WORLD'S MOST ADVANCED
MICROPROCESSOR VIDEO GAME
DIRECT FROM THE USA

THE 'ATARI' VIDEO COMPUTER SYSTEM

— READY BUILT CARTRIDGE SYSTEM
EX-STOCK

**192
GAMES**

Just look at a few of the numerous games available to you in multi-colour (on colour TV's) with realistic sound effects.

★ This Video Computer System (based on Signetics 2550) is available complete with the 27 game Combat Cartridge, multi-function joysticks, mains adaptor and aerial switching unit. Fully guaranteed for 12 months. **£135.90 + VAT**

★ At present there are 9 cartridges available — a total of 192 games — plus many more on the way. Price per cartridge) **£12.95 + VAT**

Full colour brochure available on request.

Securicor delivery available — Add £4.00.



Please make cheques and postal orders payable to **DISCOUNT COMPUTING**, or phone your order quoting **BARCLAYCARD** or **ACCESS** number.



**Discount
COMPUTING**

14 STATION ROAD · NEW BARNET · HERTS. TEL: 01-441 2922/01-449 6596
CLOSE TO NEW BARNET BR STATION — MOORGATE LINE
OPEN — 10 a.m. to 7 p.m. — Monday to Saturday

HB COMPUTERS LTD. and Electronic Components Division

22 Newland Street, Kettering
Telephone: Kettering 0536 83922/520910

BULK OFFERS

TRANSISTORS	PER 10	PER 100
BC107/8/9	£0.85	£7.50
PBC107/8/9	£0.65	£6.50
BC547/8/9	£0.75	£6.50
BC557/8/9	£0.75	£6.50
BC212/3/4	£0.75	£6.50
BC194/5	£0.80	£7.00
BF199	£1.50	£11.00
BF200	£2.50	£22.00
BFY50/1/2	£1.65	£15.00
TIP31A/2A	£3.20	£30.00
TIP41A/2A	£4.80	£43.00
2N3055 (TO3)	£4.20	£38.50
2N3702/3/4	£0.80	£7.00
2N3819	£1.70	£14.50

DIODES		
1N4001/2/3	£0.48	£3.90
1N4004/5	£0.55	£5.00
1N4007	£0.70	£6.00
1N4148	£0.80	£2.20
Zener Diodes 400mW	£0.75	£5.80

LEDs		
0.2 Red	£0.90	£8.00
0.125 Red	0.95	£8.00
0.2 Red Flat Sides CQX10	£1.60	£15.00
0.2 Yellow/Green	£1.30	£11.00
0.125 Yellow/Green	£1.30	£11.00
0.2 Yellow/Green Flat Sides CQX11/12	£2.20	£20.00

BARGAIN PACKS

ICs		
LM324 (14 KIL)	£7.00	£51.00
LM555 (8 DIL)	£2.80	£23.00
LM741 (8 DIL)	£1.80	£15.50

TANT BEADS		
0.1µf. 0.22µf. 0.47µf.		
1µf 35v	£0.75	£6.30
2.2µf 35v	£0.95	£8.00
4.7µf 35v	£1.20	£11.00
10µf 35v	£1.80	£12.00
22µf 16v	£1.50	£12.00

HARDWARE		
8 pin DIL Socket	£1.00	£9.00
14 pin DIL Socket	£1.10	£9.50
16 pin DIL Socket	£1.20	£10.00
24 pin DIL Socket	£2.00	£18.00
Min slide switches	£1.50	£12.00
Min push to make switches	£1.50	£12.00

RESISTORS 1/2 Watt Carbon Film (Min Type)		
Single. Values £1.25 per 100		
Mixed lots of 100	£10.00	per 1000

MICRO PROCESSORS		
Wide range of micro parts stocked. Send for free list or visit our showrooms in Kettering and get hands on experience of the PET2001 and Apple II in stock now. (PET 2001 is distributed by our sister company HB Computers)		

ORDERING DETAILS

VAT: Add high rate to items. Standard rate to others.
POST & PACKING: 30p on all orders under £5.00. Otherwise free. Overseas please add freight costs and state surface or air. No VAT on overseas or BFPO orders. All orders sent first class post in heat sealed padded bags.
DELIVERY: All orders processed on day of receipt. Goods offered subject to availability.

and our conditions of sale. Cash returned for out of stock items.
PAYMENT: Cash, cheque, postal order. Credit card orders accepted by letter or telephone.
GUARANTEE: All devices are brand new and full spec. No manufacturers' fail outs or rejects. Any faulty items returned in good condition will be replaced or refunded.
ENQUIRIES: Please enclose a suitable S.A.E.

DISCOUNT BOXES INSTRUMENT CASES AND COMPONENTS



Aluminium box with lid and screws.	Professional black P.V.C. coated case with satin anodised front panel and trim.	Black P.V.C. top with U-shaped aluminium chassis.
L W H	W D H	L W H
3 x 2 x 1	9 x 6 x 3	6 x 4 1/2 x 2
4 x 3 x 1 1/2	9 x 6 x 4 1/2	6 x 4 x 3 1/2
4 x 3 x 2	9 x 6 x 6	8 x 5 1/2 x 2 1/2
6 x 4 x 2	12 x 8 x 3	10 x 6 1/2 x 3
6 x 4 x 3	12 x 8 x 4 1/2	
8 x 6 x 2	12 x 8 x 6	
8 x 6 x 3		

AD161/2 MP	83p	BC347A	14p	BF274	24p
OC36	60p	BD183	80p	BF394	30p
BC108A	9p	BD263A	42p	BF422	20p
BC148	8p	BF137	24p	LM741C	17p
BC149C	9p	BF194	10p	TBA120A	75p
BC154	9p	BF195	10p	SN76013N	120p
BC171B	9p	BF198	21p	SN76033N	120p
BC172B	9p	BF200	21p	SN76110N	75p
BC183A	10p	BF255	23p	SN76131N	150p
BC30B	15p	BF256 FET	33p	SN76660N	75p

Ceramic Filters SEF 6. OMA 40p. TV Colour Crystals 4.433619 MHz £1.50.

AXIAL ELECTROLYTIC			
10/25v	5p	330/25v	10p
15/16v	6p	330/63v	16p
22/10v	5p	470/16v	15p
22/16v	6p	470/40v	15p
22/25v	7p	1000/25v	18p
33/35v	8p	2000/30v	20p
33/50v	9p		
47/40v	10p		
100/10v	8p		
100/63v	10p		

MIXED PACK OF 100 AXIAL AND P.C. ELECTROLYTICS 300p
DISCOUNT ON ALL ORDERS OVER £5 5% OVER £10 10% OVER £20 15%, OVER £30 20%
All prices include post and packing
All orders under £1. please add 20p for handling charge
HARRISON BROS., P.O. BOX 55, Westcliff-on-Sea, Essex SSO 7LQ. Phone: Southend 32338

SERVICE TRADING CO

WHY PAY MORE?!

MULTI RANGE METERS Ty - MF15A.
A.C./D.C. volts 10, 50, 250, E, 1000, Ma.
0-5, 0-10, 0-100. Sensitivity 2000V, 24 ranges,
dimensions 133 x 93 x 46mm. Price £7.00 plus
50p P&P (£8.10 inc. VAT & P).



TRIAC.

Raytheon tag symmetrical Triac. Type Tag 250/500v. 10 amp 500 p.w.
Glass passivated plastic triac. Swiss precision product for long term
reliability. £1.25 P&P 10p (£1.46 inc. VAT & P) (inclusive of date and
application sheet). Suitable Diac 22p.

0 to 60 MINUTES CLOCKWORK TIMER.

Double pole 15 amp 230AC. Contacts (no dial) £1.50. P&P 30p (£1.94
inc. VAT & P) N.M.S.

MERCURY SWITCH

Size 27m x 5mm, 10 for £5.00. P&P 30p. total
including VAT £5.72. Min. quantity 10. N.M.S.



230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete with
5 blade 6 1/2" aluminium fan. New reduced
price £3.00 P&P 65p (£3.94 inc. VAT & P).
N.M.S.



21-WAY SELECTOR SWITCH with reset coil

The ingenious electro mechanical device can be
switched up to 21 positions and can be reset from
any position by energising the reset coil
230/240V. A.C. operation. Unit is mounted on
strong chassis. Complete with cover. Price £5.50
P&P 75p (£6.75 inc. VAT & P) N.M.S.



VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9
rotor with max. air delivery of 1.5 cubic
metres per min. Max. static pressure
600mm W.G. Suction or blow from 2
side-by-side 37mm I.D. circular apertures
fitted to base of unit. Powerful continuously
rated 115v a.c. motor mounted on alloy base
with fixing facilities. Dimensions Length
222cm x width 25cm x height 25cm.



These units are ex-equipment but have had minimum use. Fully tested
prior to despatch. Price £12 + £1.50 P&P (£13.58 inc. VAT & P).
Suitable transformer for 230/240v a.c. £6 + £1 P&P (£7.56 inc. VAT & P).

CENTRIFUGAL PLOWER

Smith type FF8 1606 02/220/240V. A.C.
Aperture 10x4 1/2cm overall size 16x14cm. Price
£3.75 P&P 75p (inc. VAT £4.86). Other types
available. S.A.E. for details.
N.M.S.



CROWD 230V A.C.

2 R.P.M. synchronous brand new £2.90. P&P 30p (£3.46 inc. VAT).
N.M.S.



MINIATURE UNISELECTOR

12v. 11 way 4 bank (3 non-bridging, 1 homing).
£2.50 P&P 35p (£3.08 inc. VAT & P).




MICRO SWITCHES

Sub min lever m/switch type MML46. 10 for £2.50.
Type 3 115M 906T 10 for £2.50 post paid (£2.70 inc. VAT
& P).
BF lever operated 20a. c/o. mf. Unimax USA 10 for £4.00
plus 50p P&P (min. order 10) (£4.86 inc. VAT & P).
D.P. C/O lever m/switch, mfg. by Cherry Co. USA. Precious metal, low
resistance contacts. 10 for £2.50. P&P 30p. Total inc. VAT £3.02 (min
10). N.M.S.



NEW HEAVY DUTY SOLENOID

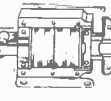Mfg by Magnetic Devices 240v A.C.
Operation approx. 10lb pull at 1.25". Price
£4.00 P&P 60p (£4.96 inc. VAT).
N.M.S.



240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass
body, stainless steel core and spring 1/2 in. b.s.p. inlet,
outlet. Precision made. British mfg.
PRICE £3.50 Post 50p (£4.32 inc. VAT & P).



PARVALUX 230/250V a.c. MOTOR

Diamond H heavy duty AC relay 230/240v a.c. two c/o contacts 25
amps res at 250v a.c. £2.50 P&P 50p (£3.24 inc. VAT & P&P). Special
base 50p.



INSULATION TESTERS (NEW)

Test to I.E.E. spec. Rugged metal construction
suitable for bench or field work constant speed
clutch Size L 8 in. W 4 in. H 6 in., weight 6 lb
500 VOLTS 500 megohms
£49.00 Post 80p (£57.78 inc. VAT & P)
1000 VOLTS 1000 megohms
£55.00 Post 80p (£60.26 inc. VAT & P). SAE for
leaflet.



VARIABLE VOLTAGE TRANSFORMERS



Carriage extra

INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260v. A.C.
BRAND NEW. All types.
200W (1 Amp) fitted A/C
volt meter £14.50
0.5 KVA (Max. 2 1/2 Amp) £17.00
1 KVA (Max. 5 Amp) £22.50
2 KVA (Max. 10 Amp) £37.00
3 KVA (Max. 15 Amp) £45.50
5 KVA (Max. 25 Amp) £74.00
10 KVA (Max. 50 Amp) £168.00
17 KVA (Max. 75 Amp) £260.00

LT TRANSFORMERS

0-10-15v at 3 amp. (ex new equip) £2.50 P&P 50p (£3.24 inc. VAT).
13-0-13v at 1 amp £2.50 P&P 50p (£3.24 inc. VAT).
25-0-25v at 2 1/2 amp. £4.50 P&P 75p (£5.67 inc. VAT & P).
0-4v 6v/24v/32v at 12 amp. £15.00 P&P £1.50 (£17.82 inc. VAT & P).
0-6v 12v at 20 amp £13.50 P&P £1.50 (inc. VAT £16.20).
0-12v at 20 amp or 0-24v at 10 amp £12.00 P&P £1.50 (£14.58 inc. VAT & P).
0-6v 12v at 10 amp £8.25 P&P £1.25 (inc. VAT £10.26).
0-6v 12v/17v/18v/20v at 20 amp £18.50 P&P £1.50 (£19.44 inc. VAT & P).
0-10v/17v 18v at 10 amp. £10.00 P&P £1.40 (inc. VAT £12.31).
Other types in stock, phone for enquiries or send sae for leaflet.

ROTARY VACUUM AIR COMPRESSOR & PUMP

Carbon vane oil free vacuum pump and compressor.
Approx. 20 inch vacuum. 10 PSI at 79 CFM.
Powered by 110V a.c. 1 1/8 amp Parvalux motor.
fitted with additional shaft at rear, suitable light
loads. Inc. capacitor £14.00 P&P £1.50 (£16.74
inc. VAT & P&P).
Suitable transformer for 230/240v a.c. operation
£5.00 P&P £1.00 (£6.48 inc. VAT & P&P).
N.M.S.



STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT Mk. IV

Latest type Xenon white light tube. Solid state timing and triggering
circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s.
Designed for large rooms, halls, etc. Light output greater than many
(so called 4 Joule) strobes. Price £19.00 post £1 (£21.60 inc. VAT
& P). Specially designed case and reflector for Hy-Light £8.80 Post
£1.00 (£10.58 inc. VAT & P).


ULTRA VIOLET BLACK LIGHT

FLUORESCENT TUBES
4ft. 40 watt £8.70 (callers only). 2ft. 20 watt £6.20. Post 75p
(£7.51 inc. VAT & P). (For use in stan. bi-pin fittings.) Mini 12in. 8
watt £2.80. Post 35p (£3.40 inc. VAT & P). 9in. 6 watt £2.25.
Post 35p (£2.81 inc. VAT & P). 6in. 4 watt £2.25. Post 35p
(£2.81 inc. VAT & P).

Complete ballast unit. Either 6, 9 or 12 tube 230v A.C. op.
£3.50. Post 45p (£4.27 inc. VAT & P). Also available for 12v d.c.
op. £3.50 plus P&P 45p (£4.27 inc. VAT & P).
400w UV lamp and ballast complete, £31.50. Post £3 (£37.26
inc. VAT & P). 400w UV lamp only £11.25. Post £1.20 (£13.45
inc. VAT & P).

SQUAD LIGHT

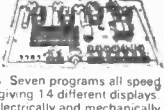A new conception in light control. Four channels each
capable of handling 750 watts. Range
of spotlights or dozens of small mains lamps. Seven programs all speed
controlled plus flash modulation, effectively giving 14 different displays.
Makes sound-to-light obsolete. Completely electrically and mechanically
noise free.
S.A.E. (foolscap) for further details. Price only £60.00



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (foolscap) for details

XENON FLASH GUN TUBES

Range of Xenon tubes available from
stock. S.A.E. for full details.



RELAYS

Wide range of AC and DC relays available
from stock. Phone or write in your en-
quiries.

230/240V A.C. Relays: Arrow, 2 c/o 15 amp £1.50 (£1.84 inc. VAT
& P).
T.E.C. open type 3 c/o 10 amp £1.10 (£1.40 inc. VAT & P). Omron or
Keyswitch 1 c/o 7 amp £1.00 (£1.30 inc. VAT & P).

D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 (£1.30 inc. VAT
& P). Sealed 12V 1 c/o 7 amp octal base £1.00 (£1.30 inc. VAT & P).
Sealed 12V 2 c/o 7 amp octal base £1.25 (£1.56 inc. VAT & P). Sealed
12V 3 c/o 7 amp 4 pin £1.35 (£1.67 inc. VAT & P). 24V Sealed 3
c/o 7 amp 11 pin £1.35 (£1.67 inc. VAT & P) (amps = contact rating).
P&P on any Relay 20p (inc. VAT & P).
Other types available - phone for details.
N.M.S.

Diamond H heavy duty AC relay 230/240v a.c. two c/o contacts 25
amps res at 250v a.c. £2.50 P&P 50p (£3.24 inc. VAT & P&P). Special
base 50p.

VAT AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED

ACCOUNT CUSTOMERS MIN. ORDER £10.00
SERVICE TRADING CO.

ALL MAIL ORDERS, ALSO CALLERS AT

57 BRIDGMAN ROAD, CHISWICK,
LONDON, W4 5BB. Phone: 01-995 1560
Closed Saturdays.

SHOWROOMS NOW OPEN
AMPLE PARKING


PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET,
LONDON, WC2H 7JJ.
Tel.: 01-437 0576

GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

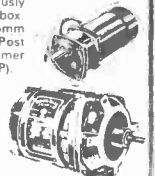115 lb. ins. 110 volt, 50Hz, 2 1/8 amp, single phase,
split capacitor motor. Immense power. Continuously
rated. Totally enclosed fan cooled in-line gearbox.
Length 250mm. Dia. 135mm. Spindle Dia. 15.5mm.
Length 115mm. ex-equipment tested £12.00 Post
£1.50 (£14.58 inc. VAT & P). Suitable transformer
230/240 volt £8.00 Post 75p (£9.45 inc. VAT & P).
R&T.



GEARED MOTORS

28 r.p.m., 20lb. inch 115v a.c. Reversible motor.
71 r.p.m., 10 lb. inch 115v a.c. Reversible motor.
Both types similar to above drawing. Price either type £4.75 + 75p
P&P (£5.94 inc. VAT & P&P).
Supplied with transformer for 240v a.c. operation £7.25 + P&P £1.
(£8.91 inc. VAT & P&P).
N.M.S.

FRACMO MOTOR

56rpm 50lbs inch 240vAC reversible 0.7 amp
sharplength 35mm, dia. 16mm, weight 6 kilos,
600 grams. Price £15.00 P&P £1.50 (£17.82).
N.M.S.



RESET COUNTER

230 volts AC 3 digits mfg. Veeder Root type
LL/144L £1.75 P&P 25p (£2.18 inc. VAT & P).
7 kg. 24v d.c. non set £1.50 P&P 25p (£1.89 inc.
VAT & P).



CITENCO

FHP motor type C 7333/15 220/240V AC 19
rpm reversible motor, torque 14.5 kg. Gear ratio
1:44.1 Brand new incl. capacitor, our price
£14.25 + £1.25 P&P (£16.74 inc. VAT & P).
N.M.S.



REVERSIBLE MOTOR 230V A.C.

General Electric 230v A.C. 1.600 r.p.m. 0.25 amp. Complete with
anti-vibration mounting bracket and capacitor O/A size 110mm x
90mm. Spindle 5/16 dia. 20mm long. Ex-equipment tested £3.00.
Post 50p (£3.78 inc. VAT & P).



RODENE UNISET TYPE 71 TIMER

0-60 sec. 230V a.c. operation. Incorporating a lapsed time indicator and
repeat facilities. A precision motorised timer ideal for process timing,
photography, welding, mixing, etc. Price £6.6 P&P 60p




METERS (New) - 90mm DIAMETER

A.C. Amp. Type 62T 0-1A, 0-5A, 0-20A. A.C. Volt.
0-15V, 0-300V. D.C. Amp. Type 62C 0-2A, 0-10A,
0-20A. 0-100A. D.C. Volt. 0-15V, 0-30V. All types
£3.50 ea + P&P 50p (£4.32 inc. VAT), except 0-100A
D.C. price £5.00 + 50p P&P (£5.94 inc. VAT).



'VENNER TYPE' ERD TIME SWITCH

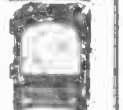200/250V AC 30 amp. 2 on/2 off every 24 hrs. at any
manually pre-set time. 36-hour spring reserve and day
on/setting device. Built to highest Electricity Board
specification. Price £7.75 P&P 75p (£9.18). R & T



SANGAMO WESTON TIME SWITCH

Type S251 200/250 V a.c. 2 on 2 off every 24 hours. 20 amps contacts with
override switch diameter 4 x 3. Price £6.00 P&P 50p (£7.02 inc. VAT & P).
Also available with Solar dial. R & T

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single-
pole switch, which can be preset for any period up
to 12 hrs. ahead to switch on for any length of
time, from 10 mins to 6 hrs. then switch off. An
additional 60 min. audible timer is also incorpo-
rated. Ideal for Tape Recorders. Lights. Electric
Blankets etc. Attractive satin copper finish. Size
135 mm x 130 mm x 60 mm. Price £2.25. Post
40p (Total inc. VAT & Post £2.87). N.M.S.



POWER RHEOSTATS


New ceramic construction, wirebus enamel,
embedded winding, heavy duty brush assembly,
continuously rated.

25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm £2.40 Post
20p (£2.81 inc. VAT & P). 50 WATT 100, 250 ohm £2.90 Post 25p
(£3.40 inc. VAT & P). 100 WATT 1 / 5 / 10 / 25 / 50 / 100 / 250
/ 500 / 1k / 1.5k / 2.5k / 5k ohm. £5.90 Post 35p (£6.75 inc. VAT
& P).

Black Silver Skirted Knob calibrated in Nos. 1-9. 1 1/2 in. dia brass
brush. Ideal for above Rheostats. 24p ea.

600 WATT DIMMER SWITCH

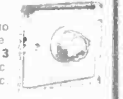Easily fitted. Fully guaranteed by makers. Will control up to
600w of lighting except fluorescent at mains voltage.
Complete with simple instructions. £3.95 Post 25p (£4.53
inc. VAT & P). 1000 watt model £5.60 Post 25p (£6.32 inc.
VAT & P). 2000 watt model £9.75 Post 40p (£10.96 inc. VAT
& P).



YET ANOTHER OUTSTANDING OFFER


New IMF6 500V Dubilier wire ended capacitors. 10 for £1.50 P&P 50p.
(£2.16 inc. VAT & P&P) (Min 10).

N.M.S. - New Manufacturers' Surplus
R & T - Reconditioned and Tested

The latest kit innovation!

from Sparkrite

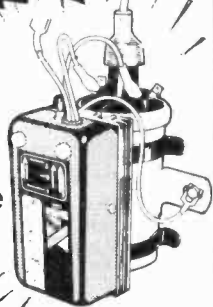*Sparkrite -
was featured by Shaw Taylor
in "DRIVE IN"*



the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistor or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT, post & packing.

Electronics Design Associates, Dept. ET 12
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

Send SAE if brochure only required

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X4 KIT £14.95

TACHS PULSE SLAVE UNIT £3.35

£

Cheque No.

Access or Barclaycard No.

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

- * **SAVE ON TIME** - No delays in waiting for parts to come or shops to open!
- * **SAVE ON MONEY** - Bulk buying means lowest prices - just compare with others!
- * **HAVE THE RIGHT PART** - No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW, MARKED DEVICES - SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%. 10 of each value 22pF to 1000pF. Total 210. **£3.35**

K002 Extended range, 22pF to 0.1µF. 330 values **£4.90**

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for **£4.75**

K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for **£3.75**

K009 Extended mylar pack. Contains all values from 1000pF to 0.47µF. Total 290 capacitors to **£11.25**

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF. E12 Series 5% 160V. Total 370 for **£12.30**

K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25, 15/16, 22/16, 33/10, 47/6, 100/3. Total 170 tants for **£14.20**

K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.50**

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for **£5.90**

K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.00**

K022 Extended range, total 850 resistors from 1R to 10M **£8.30**

K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 36V, E24 series. Total 280 for **£15.30**

K042 As above but 5 of each value **£8.70**

STEREO AMPLIFIER CHASSIS £5.50

Complete and ready built. Controls Bass, treble, volume/on-off, balance. 8 transistor circuit gives 2 watts per channel output. Just needs transformer and speakers for low cost stereo amp. Suitable metal cabinet (W374) **£2.00** - or buy the amp, case and transformer for **£10.00**, and get DIN speaker sockets and knobs free!

AMPLIFIER KIT £1.75

Mono gen. purpose amp with tone and vol./on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add **£2.20** for suitable transformer). Blue vinyl covered aluminium case to suit (W372) **£1.30**.

BC182B OFFER

Special Offer for quantity users. 1k .035 + VAT; 5k .032 + VAT Price negotiable on 10k + approx. 80k available.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **£4.25**.

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price!
18 way 41p; 21 way 47p; 32 way 72p; 40 way 90p.

THE NEW 1978-9 GREENWELD CATALOGUE

FEATURES INCLUDE:

- * 50p Discount Vouchers
 - * Quantity prices for bulk buyers
 - * Bargain List Supplement
 - * Reply Paid Envelope
 - * Priority Order Form
 - * VAT inclusive prices
- Price 30p + 15p Post.

HEAT SINK OFFER

Copper T05 sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1,000 for £25.

74 SERIES PACK

Selection of boards containing many different 74 series ICs. 20 for £1; 50 for £2.20; 100 for £4.

TMS4030 RAM

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock I/P; Fully TTL compatible; Low power dissipation. Supplied with data **£2.75**.

MISCELLANEOUS ICs

Supplied with data if requested. MC3302 quad comp. **120p**; 710 diff comp. (T099) **40p**; ZN1034E precision timer **£2.25**; LM711 Dual diff comp **65p**; LM1303 dual stereo pre-amp **75p**; MC1469R voltage reg **£1.50**; UPC1025H audio **£3.50**; 575C2 audio **£2.88**; TDA2640 audio **£2.92**; TBA810S audio **70p**; SN75110 dual line driver **70p**; MC8500 CRCC gen POA.

EXPERIMENTERS CALCULATOR

Based on the C500 chip, this pack of parts enables the more experienced constructor to make an 8 digit 4 function calculator. The comprehensive data supplied includes full-size layout of PCB required, types of suitable display and keyboard that can be used etc. Components included in the pack are C500 calculator chip, driver IC, all components for inverter/clock circuits, Rs Cs etc. All for only **£3.50**.

RELAYS

W847 Low profile PC mntg 10 x 33 x 20mm 6V coil, SPCO 3A contacts **93p**.
W832 Sub. min type, 10 x 19 x 10mm 12V coil DPCO 2A contacts **£1.15**.
W701 6V SPCO 1A contacts 20 x 30 x 25mm Only **56p**.
W817 11 pin plug in relay, rated 24V AC, but works well on 6V DC. Contacts 3 pole c/o rated 10A. **95p**.
W819 12V 1250R DPCO 1A contacts. Size 29 x 22 x 18mm min. plug-in type **72p**.
W839 50V ac (24V DC) coil. 11 pin plug-in type. 3 pole c/o 10A contacts. Only **85p**.
W846 Open construction mains relay. 3 sets 10A c/o contacts **£1.20**.
Send SAE for our relay list - 84 types listed and illustrated.

LQW COST PLASTIC BOXES

Made in high impact ABS. The lids are retained by 4 screws into brass inserts. Interior of box has PCB guide slots (except V219).

V210	80x62x40mm black	58p
V213	100x75x40mm black	72p
V216	120x100x45mm black	86p
V219	120x100x45mm white	86p

SPECIAL SUMMER OFFERS

AUDIO ICs			
76003N	£1.40	76013N	£1.00
76023N	£1.00	76033N	£1.40
LM380	80p	TBA810S	90p

Linear ICs etc.			
741(BDIL)	18p	BD131	24p
555	25p	BD132	28p
TN4148	2p	2N3819	18p

DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices - signal diodes, high voltage rets and zeners may all be included. These are being offered at the incredibly low price of **£1.25/1,000** - or a bag of 2,500 for **£2.25**. Bag of 10,000 **£8**. Box of 25,000 **£17.50**. Box of 100,000 **£60**.

STEVENS ON

Electronic Components

SWITCHES


Real cell charges.

Subminiature toggle. Rated at 3A 250V.
 SPDT 65p SPDT centre off 70p
 DPDT 75p DPDT centre off 90p

Standard Toggle.
 SPST 34p DPDT 48p

Wavechange switches.
 1P12W, 2P6W, 3P4W or 4P3W
 all 37p each.

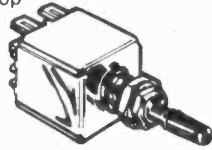Miniature switches (non-locking)
 Push to make 15p Push to break 20p



POTENTIOMETERS

5K-2M2 single 26p ea. 100Ω-2M2 horizontal
 5K-2M2 stereo (dual) 75p ea. or vertical preset 6p ea.
 5K-2M2 DP switched 60p ea.

KNOBS

Ideal for use on mixers, etc. Push on type
 with coloured cap in red, black, green, blue,
 yellow and grey.
 Position line marked 14p each.



MICROPROCESSORS

6800	670p	6820	350p	21L02	110p
8080A	525p	6850	360p	2112	175p
6810	300p	AY5-1013	380p	2114	700p

REGULATORS

78L05	30p	79L05	70p	LM309K	110p
78L12	30p	79L12	70p	LM317	220p
78L15	30p	79L15	70p	LM323K	530p
7805	60p	7905	80p	LM723	35p
7812	60p	7912	80p		
7815	60p	7915	80p		

THYRISTORS AND TRIACS

Plastic cased Thyristors. Texas.

	4A	8A	12A
100V	36p	45p	62p
200V	42p	53p	68p
400V	51p	66p	86p

Plastic cased Triacs. Texas.

All rated at 400V

4A	70p	12A	90p	20A	185p
8A	80p	16A	95p	25A	215p

We now have an express telephone order service. We guarantee that all orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Telephone: 01-464 2951/5770.

**ORDERS
 DESPATCHED
 BY RETURN
 POST**

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 25+ 10%, 100+ 15%. Prices VAT inc. Please add 30p for carriage. All prices valid to 30th April 1979. Official orders welcome.

BARCLAYCARD AND ACCESS WELCOME.



TRANSISTORS

AC127	17p	BCY71	14p	ZTX109	14p
AC128	16p	BCY72	14p	ZTX300	16p
AC176	18p	BD131	35p	2N697	12p
AD161	38p	BD132	35p	3N1302	38p
BC107	8p	BD135	38p	2N2905	22p
BC108	8p	BD139	35p	2N2907	22p
BC109	8p	BD140	35p	2N3053	18p
BC147	7p	BF244B	36p	2N3055	50p
BC148	7p	BFY50	15p	2N3442	135p
BC149	8p	BFY51	15p	2N3702	8p
BC158	9p	BFY52	15p	2N3704	8p
BC177	14p	MJ2955	98p	2N3705	9p
BC178	14p	MPSA06	20p	2N3706	9p
BC179	14p	MPSA56	20p	2N3707	9p
BC182	10p	TIP29C	60p	2N3708	8p
BC182L	10p	TIP30C	70p	2N3819	22p
BC184	10p	TIP31C	65p	2N3904	8p
BC184L	10p	TIP32C	80p	2N3905	8p
BC212	10p	ZTX107	14p	2N3906	8p
BC212L	10p	ZTX108	14p	2N4058	12p
BC214	10p			2N5457	32p
BC214	10p	1N914	4p	2N5458	30p
BC477	19p	1N4001	4p	2N5459	32p
BC478	19p	1N4002	4p	2N5777	50p
BC479	19p	1N4004	5p		
BC548	10p	1N4006	6p		
BCY70	14p				

DIODES

1N4148	3p
1N5401	13p
1N5402	15p
1N5404	16p
1N5406	18p

BZY88 series 2V7 to 33V 8p each.

LINEAR

A SELECTION ONLY!
 DETAILS IN CATALOGUE.

709	25p	LM324	50p	NE556	60p
741	22p	LM339	50p	NE565	120p
747	50p	LM380	75p	NE567	170p
748	30p	LM382	120p	SN76003	200p
CA3046	55p	LM1830	150p	SN76013	140p
CA3080	70p	LM3900	50p	SN76023	140p
CA3130	90p	LM3909	60p	SN76033	200p
CA3140	70p	MC1496	60p	TBA800	70p
LM301AN	28p	MC1458	35p	TDA1022	650p
LM318N	125p	NE555	25p	ZN414	75p

OPTO

LEDs 0.125in. 0.2in.
 Red TIL209 TIL220 9p
 Green TIL211 TIL221 13p
 Yellow TIL213 TIL223 13p
 Clips 3p 3p



DISPLAYS

DL704 0.3 in CC 130p
 DL707 0.3 in CA 130p
 FND500 0.5 in CC 100p

RESISTORS

Carbon film resistors.
 High stability, low noise 5%.
 E12 series, 4.7ohms to 10M. Any mix:
 100, 1k, 2, 3, each
 0.25W 22 1p 0.9p 0.8p
 0.5W 22 1.5p 1.2p 1p
 Special development packs consisting of 10 of each value from 4.7 ohms to 1 Megohm (650 res.)
 0.5W £7.50. 0.25W £5.70

CAPACITORS

HERE ARE JUST A FEW OF THE CAPACITORS STOCKED

TANTALUM BEAD each
 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V 9p
 4.7, 6.8, 10uF @ 25V 13p
 22 @ 16V, 47 @ 6V, 100 @ 3V 16p

MYLAR FILM
 0.001, 0.01, 0.022, 0.033, 0.047 3p
 0.068, 0.1 4p

RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
			22	33	47	7p
	100					13p
		220				20p
25V	10	22	33	47		5p
	100					8p
		220				10p
			470			15p
						23p
10V		220				5p
			470			9p
						13p
			2200			23p

74LS

LS00	16p	LS95	65p
LS01	16p	LS123	56p
LS02	16p	LS125	40p
LS03	16p	LS126	40p
LS04	16p	LS132	60p
LS08	16p	LS136	36p
LS10	16p	LS138	54p
LS13	30p	LS139	50p
LS14	70p	LS151	50p
LS20	16p	LS153	50p
LS30	16p	LS155	80p
LS32	24p	LS156	80p
LS37	26p	LS157	45p
LS40	22p	LS164	90p
LS42	53p	LS174	60p
LS47	70p	LS175	60p
LS48	48p	LS190	80p
LS54	16p	LS192	70p
LS73	29p	LS193	70p
LS74	29p	LS196	80p
LS75	44p	LS251	60p
LS76	35p	LS257	55p
LS78	35p	LS258	55p
LS83	60p	LS266	40p
LS85	70p	LS283	60p
LS86	33p	LS290	55p
LS90	45p	LS365	45p
LS93	45p	LS366	45p
		LS367	45p
		LS368	45p
		LS386	35p
		LS670	180p

TTL

7400	12p	7493	34p
7401	12p	7494	52p
7402	12p	7495	52p
7404	12p	7496	50p
7408	14p	74121	25p
7410	12p	74122	33p
7413	25p	74123	40p
7414	48p	74125	35p
7420	12p	74126	35p
7427	24p	74132	50p
7430	12p	74141	56p
7442	43p	74148	90p
7447	55p	74150	70p
7448	58p	74151	50p
7454	14p	74156	52p
7473	25p	74157	52p
7474	25p	74164	70p
7475	32p	74165	70p
7476	28p	74170	125p
7485	70p	74171	68p
7489	145p	74177	58p
7490	32p	74190	72p
7492	35p	74191	72p
		74192	64p
		74193	64p
		74196	55p
		74197	55p

CMOS FULL DETAILS IN CATALOGUE

4001	15p	4029	60p
4002	15p	4040	68p
4007	15p	4042	54p
4011	15p	4046	100p
4013	35p	4049	28p
4015	60p	4050	28p
4016	35p	4066	40p
4017	55p	4068	20p
4018	65p	4069	16p
4023	15p	4071	16p
4024	45p	4075	16p
4026	95p	4093	48p
4027	35p	4510	70p
4028	52p	4511	70p
		4518	70p
		4520	65p

SKTS

Low profile by Texas

8 pin	10p	24 pin	24p
14 pin	12p	28 pin	28p
16 pin	13p	40 pin	40p

Soldercon pins: 100: 50p
 1000: 370p

AT LAST! OUR NEW 40 PAGE CATALOGUE OF COMPONENTS IS AVAILABLE. SEND S.A.E.




Mail orders to: STEVENSON (Dept ET)

236 High St, Bromley, Kent, BR1 1PQ, England

BAD NEWS FOR KNOB TWIDDLEDERS
A 300W Lightdimmer with NO knob. Dimming and on/off functions are controlled by touch. Features include

- ★ No mains rewiring
- ★ Switches on to preset brightness
- ★ Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy

★ ★ PRICE £8.99 TDE/K
£1.00

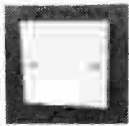

LIGHTING CONTROL KITS (300W)
TSD300K TOUCHSWITCH & DIMMER combined. One touch-plate for on/off. Small knob controls brightness. **£5.50**
TS300K TOUCHSWITCH. Two touchplates. ON/OFF **£4.00**
TSA300K AUTOMATIC. One touchplate. Preset time delay off. **£4.00**
LD300K LIGHTDIMMER. **£2.80**

DIGITAL VOLTMETER THERMOMETER KIT

Based on the 7106 single IC 3½ digit DVM the kit contains a PCB, resistors, capacitors, presets, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single transistor as the sensor.
ONLY £21.99



24 HR. CLOCK/APPLIANCE TIMER KIT

Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains AY-5-1230 Clock/Appliance Timer IC, 0.5 LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. **£13.75**
White box (56x131x71mm)—drilled and undrilled **£2.50**



PLEASE ADD 8% V.A.T. (*12½% TO ABOVE PRICES)
QUANTITY DISCOUNTS ON REQUEST. ADD 25p POSTAGE & PACKING. MAIL ORDER ONLY TO:

T. K. ELECTRONICS, 106 Studley Grange Road, London W7 2LX

TRIAC BARGAINS

400V Plastic Case
3A **58p**
6.5A with trigger **80p**
8A **74p**
12A **84p**
16A **105p**
20A **165p**
25A **190p**
SCR (C106D) 5A/400V **50p**
Diac **21p**

COMPONENTS

0.2" L.E.D.S.
Red 12p **£1/10**
Green 21p. Yellow **25p**
DL727 5' display **£1.50**
LCD 5' 4 digit **£9.00**
LDR 5' dia
NE555 (4 for **£1.00**)
741 (5 for **£1.00**)
LM3911 temperature IC **£1.00**
AY-5-1224 **£3.25**
AY-5-1230 **£4.85**
ZN1034E **£1.80**
ICL7106 DVM IC **£9.25**
1N4001 **6p**
1N4148 **4p**
BC182L **10p**
2N3819 **20p**

MINI MAINS TRANSFORMERS

Standard 240V mains primary
100mA secondary
6-0-6V **85p**
9-0-9V **90p**
12 -0-12V **95p**

For a merry musical Christmas an electronic musical door chime which can play 24 different tunes!



A complete CHROMA-CHIME Kit for only £15.95

includes P&P + V.A.T.

The CHROMA-CHIME is exclusively designed by
CHROMATRONICS
River Way, Harlow, Essex

In CHROMATRONICS River Way Harlow Essex UK

£15.95

Please send Chroma Chime Kits at £15.95 each including VAT and post and packing. PLEASE USE BLOCK CAPITALS

Name _____
Address _____
Enclose cheque PO value £ _____
or debit my ACCESS BARCLAYCARD account No _____
Signature _____

ETI

Please allow 7-21 days for delivery.

*These tunes play longer if the push button is kept pressed

TAMTRONIK LTD. (DEPT. ETI)

217 Toll End Road, Tipton
West Midlands DY4 0HW. Tel. 021-557 9144

Mag. issue	PROJECT	Ref.	PCB	Component Pack	Hardware Pack	Case (Screened)	Total	
TOP	Graphic Equaliser	601	1.60	14.23	4.30	—	20.13	
	Graphic Equaliser PSU	602	.55	1.29	—	—	1.84	
	R.F. Attenuator	603	—	1.29	1.54	1.35	3.15	
	Watchdog	604	.85	4.69	7.68	5.53	18.75	
	Watchdog PSU	605	.65	1.49	3.95	—	6.09	
	PROJECTS	Sweep Oscillator	606	2.60	21.07	8.16	4.28	36.11
		Stereo Simulator	607	.60	2.30	.53	2.24	5.67
		Freezer Alarm	608	.55	.92	3.85	1.65	6.97
		General Purpose Pre-Amp	609	.65	3.13	—	—	3.78
		G.S.R. Monitor	612	.70	4.70	7.10	3.95	16.45
		Burglar Alarm	613	.60	2.15	6.15	—	8.90
		Headlight Reminder	614	—	.55	1.65	—	2.20
		Bench Amplifier	615	.70	3.40	2.95	3.95	10.00
		Audio Visual Metronome	616	—	1.31	1.62	—	2.93
Componder		617	1.60	10.10	8.90	3.15	23.15	
NO	50 watt High Power Amp	618	1.30	6.46	—	—	7.76	
	100 watt High Power Amp	619	1.30	6.46	—	—	10.46	
	High Power Amp PSU	620	1.10	5.66	7.89	—	14.65	
	LED Dice	624	.50	2.92	.66	1.65	5.73	
	Marker Generator	626	.80	3.68	1.49	.90	6.87	
	Skeet	627	1.60	11.12	.97	4.53	18.22	
	Flash Trigger	628	.65	3.48	.84	1.65	6.62	
	Disc Lightshow	629	3.05	12.79	5.85	—	21.69	
	Pink Noise Generator	630	.60	1.00	—	1.65	3.25	
	6	541 Train Controller	T001	.75	5.27	5.84	3.95	15.81
		444 5-watt Stereo	T002	2.00	14.03	6.84	3.45	26.32
		448 Stereo Disco Mixer	T003	1.60	13.74	.87	—	16.21
		Clock B	T004	2.10	11.31	—	—	13.41
		House Alarm A	T005	2.00	10.93	—	—	12.93
House Alarm B		T006	.85	3.04	3.05	9.50	29.37	
Metal Locator Mk II		T007	.92	5.91	8.76	3.38	18.97	
Frequency Shifter PSU		T008	.65	4.14	—	—	4.79	
Frequency Shifter		T009	1.50	16.99	—	2.40	20.89	
LCD Meter		T010	1.00	24.62	—	—	25.62	
Light Dimmer		T011	.55	3.40	3.12	—	7.07	
Gas Monitor		T012	.80	10.11	1.10	1.35	13.36	
Star Trek Radio		T013	.84	6.19	.83	—	7.86	
Stars & Dots		T014	1.83	5.33	11.49	3.46	22.11	
Spectrum Analyser		T015	1.50	35.76	16.02	5.00	65.10	
Wein Oscillator		T016	.89	6.36	4.80	2.40	14.45	
UFO Detector		T017	1.45	10.18	.80	—	12.43	
Torch Finder		T018	.45	1.27	—	—	1.72	
Temperature Meter		T019	1.00	24.41	1.76	—	25.41	
ETIvet		T020	.90	5.93	3.66	1.65	12.64	
Cross Hatch Generator		T021	2.30	14.27	11.04	1.65	29.26	
Stac Timer		T022	1.35	4.34	.43	2.24	8.36	
Wheel of Fortune		T023	2.95	10.15	8.78	—	21.88	
Complex Sound Generator		T024	1.10	2.24	7.12	2.38	12.84	
R.F. Power Meter		T025	.60	.71	.78	7.9	2.88	
Power Bulge		T026	.95	3.48	3.02	2.15	9.60	
Telephone Bell Extension		T027	1.95	7.91	3.25	—	13.11	
Proximity Switch		T028	.60	3.38	4.95	—	8.93	
Ultra Sonic Receiver		T029	.60	3.38	4.95	—	8.93	
Ultra Sonic Transmitter		T030	.45	.82	3.20	—	4.47	

ONE STOP SHOPPING — P.C.B.s

Components, Hardware, Cases, Part Kits, Full Kits. A complete service to the ETI Constructor. All Prices incl. VAT, P&P 30p per order.

Except where copyright restrictions exist PCBs are available for all projects from Sept. 1976, and include

560 A, B, C (set 3)	4.60	Bongos	.65
710 2m Power Amp	.90	Loudhailer	.60
Double Dice	1.35	Continuity Tester	.50
152 A, B TV Patter Gen. (set 2)	2.85	Spirit Level	.85
Heart Rate Monitor	1.00	3 channel Tone Control	.70
Reaction Tester	1.45	Clock A	1.05
Metal Locator 549	.85	Experimenters Power Supply	.90
Door Bell	.65	555 Timer Board	.60
Drill Controller	.60	Hammer Throw (set 3)	4.80
630	.60	Porch Light	.70
Digital Frequency Meter (set 4)	2.90	RMS Meter	.85
Digital Thermometer	1.20	Rain Alarm	1.00

SYSTEM 68

M/F PSU	.90	VDU A'	2.70	VDU B	2.65
CPU	2.35	631	2.50	TTY	2.00
Cuis & Ram	2.25	(PCBs are modified)			

Discounts on any 3 PCBs 5%, any 4 PCBs 10% Full Set £12.00
568, any 5 PCBs 12½%, any 6 PCBs 15%

"SON OF ETI" HOBBY ELECTRONICS

THIS MONTH'S BARGAINS

100 x ½W 1K carbon resistors **30p**

PCBs and Kits available from TAMTRONIK.

PCBs and Kits also available for everyday electronics, send SAE for details.

For a few kits it is not possible to supply ALL components. To avoid disappointment we recommend you send SAE requesting kit details. Please quote project and kit reference number when details of a specific kit is required. SAE automatically brings free catalogue.

OVER 100 KITS NOW AVAILABLE

TRADE AND EDUCATIONAL ENQUIRIES WELCOME

Visit our shop at:
32 MARKET PLACE, GREAT BRIDGE, TIPTON, WEST MIDLANDS

Mail Order or Telephone

Access

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround; 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95 Per stereo pair + £3.40 p&p.

★ As above but complete with all woodwork in kit form, finished in simulated teak veneer, with instructions. **£28.00** Per stereo pair + £5.00 p&p. Size approx 20" x 11" x 9 1/2"



EASY BUILD RECORD PLAYER KIT



for the D-I-Y man who requires a stereo unit at a budget price, comprising ready assembled stereo amp, module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record/replay socket including 2 SPHERICAL HIFI speakers. **£19.95** p&p £4.05

BARGAINS FOR PERSONAL SHOPPERS

PORTABLE STEREO RADIO CASSETTE RECORDER UNREPEATABLE



MW, LW, SW and Stereo VHF. 6 watts output Battery/Mains operation. **£69.95**

160 16 VOLT MAINS TRANSFORMER, 2 1/2 amp. **£2.50**

BSR Record auto deck on plinth with stereo cartridge ready wired. **£11.95**

LED 5 function men's digital watch stainless steel finish. **£5.95**

LCD 5 function men's digital watch stainless steel finish. **£6.95**

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish. **£13.95**

POCKET CALCULATOR. With LED display, memory and percentage key. **£2.95**

AM/FM DIGITAL CLOCK RADIO. Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer. **£11.95**



125 Watt Power Amp Module **£13.95**

Mains power supply for above unit. **£3.50**

MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30 1/2" x 14 1/2" x 7 1/2" approx. **£5.95**

MULLARD Built power supply. **£1.50**

DECCA DC 1000 Stereo Cassette P.C.B complete with switch oscillator coils and tape-heads. **£2.95**

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3 1/2" approx. tweeter inc. crossovers. **£20.00**

"VIDEOMASTER" Super Score TV Game with pistol mains operation. **£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock. **£41.95**

7" TAPE TRANSPORT Mechanism—a selection of models from. **£8.95**

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 3/4" x 1 1/4" x 2" approx. **£7.50** p&p £1.50p



AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE. Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vol On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW and 5 button rotary selection switch. Power Output 5 watts per channel. Sine at 2% THD into 15 Ohm 7 watts speech and music. Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz (1150mV/100K) deviation FM signal Frequency Range (Audio) 50Hz to 17KHz within ±1dB Radio FM sensitivity for 3dB below limiting better than 10 uV AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre Size approx length 16" x height 2 3/4" x depth 4 1/4" **£19.95** p&p £2.25

240 Volts AC Complete with Circuit diagram.

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE PRICE £ **25** PER PACK


SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE p+p £1.00 £4.95**

2 PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **OUR PRICE p+p £1.00 £7.45**

3 PACK 3. 1 x LP1179/2 FM Tuning head with AM gang, 1 x LP1165/1 AM/FM IF module, 2 x LP1173/10w. RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE p+p £1.00 £9.95**

TRADE ENQUIRIES INVITED

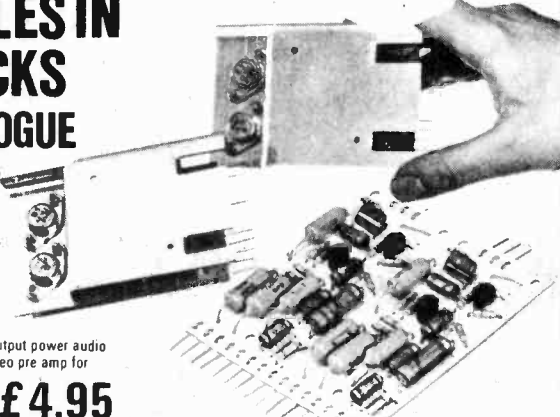

ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. **£1.00 p+p £1.95**

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE. **p+p 50p 95p**

THIS MONTHS OFFER
added to our bargain packs
When you buy Pack 3 at £9.95, together with a mains transformer at £1.95 and a set of controls for 95p you receive FREE a Mullard LP1400 Decoder to match listed at £11.90 **£12.85**



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak finished cabinet. Silver fascia with aluminium rotary controls/pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers. **£29.90** + £2.50 p&p

SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

FREE. 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier.

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet. p&p £2.50 in each case.

£23.00 + £2.50 (NOTE Cabinet not available separately.) **£29.00** + p&p £2.50 complete with cabinet.

SPECIAL OFFER Complete with 30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3/4" approx. tweeters and crossovers. **£49.00** + p&p £4.00

BUILT AND READY TO PLAY 30x30 Viscount. Available fully built and tested. **39.00** + p&p £2.50

BARGAIN

PORTABLE DISCO CONSOLE



with built-in pre-amp

Here's the big-value portable disco console from RT-VCI. It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simple connects into your existing slave or external amplifier.

£64.00 p & p £6.50

50 WATT MONO DISCO AMP

£29.95 P&P £2.50

Size approx. 13 1/2" x 5 1/2" x 6 1/2"

50-watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume. **SPECIAL OFFER.** The above 50 watt amp plus 4 Goodmans Type 8P, 8" speakers. Package price £45.00 + £4.00 P&P.



70 & 100 WATT MONO DISCO AM

Size approx. 14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls.

Five vertical slide controls: master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **100 watt £65**



BOS 95 TYPE Belt drive chassis turntable

less cartridge. **£2.55 p & p £24.95**

BSR MP60 TYPE Single play record player less cartridge. **£15.95** £2.55 p & p

CARTRIDGES to suit above Tenor magnetic stereo. **£4.95**

GARRARD DECK CC10A. Record changer with cue and stereo ceramic cartridge. Size 12" x 8 1/2" approx. **£7.95** £2.00 p & p

BARGAINS FOR PERSONAL SHOPPERS

GARRARD 86SB Deck **£26.95**

GARRARD SP25 MKIV Deck **£24.95**

GARRARD J55B Deck with Shure head **£25.95**

Plinth and cover for BSR decks **£6.00**



323 EDGWARE ROAD, LONDON W2
21 HIGH STREET, ACTON W3 6NG
ALL PRICES INCLUDE VAT AT 12 1/2%
All items subject to availability. Price correct at 1.4.78 and subject to change without notice.

MINI-ADS & CLASSIFIED

MICROPROCESSORS AND MEMORIES

STATIC RAMS

1K x 1 21L02 (250 nS)	£1.23
256 x 4 2112 (450 nS)	£2.07
1k — 4 2114 (450 nS)	£7.00

MPUs

Z80	£15.00
6800	£15.00
8080A	£10.00

WIRE WRAP SOCKETS

16 pin	45p
18 pin	50p
24 pin	60p
40 pin	£1.12

(15p postage & packing)

IMPS

Box 131, Reading RG6 2DR

SPECIAL OFFERS

VDU 80 characters 13 lines. ASCII/Baudot TTL or loop inputs/outputs. video and UHF outputs. Keyboard serialiser. complete cased unit new **£250.**

COMPONENTS

Digital	Others		
2513 UC (5v)	535p	741 (8-pin)	15p
2525	195p	7805 (TO220)	60p
2532	165p	78M12 (TO220)	60p
AY3 1015 (5v)	495p		£58p
		1N4002	04p
		1N5404	11p
TTL (mainly Texas more in list)		Dil reed relay	
7400	11p	5v SPNO	40p
7404	13p	10.0007MHz Hc6U	200p
7410	12p	10.000uf 16v	38p
7420	12p	Mains TX 250v Pri.	
7475	37p	9v 2a plus 17v .25a	
7490	26p		500p

SAE for full list of VDU details. All offers subject to availability. All new surplus. Min orders £2.00. Post 20p

DIGITEX ELECTRONICS
238 Stamford Rd., Briarly Hill
West Midlands DY5 2QE

DIGITAC DIGITAL REV. COUNTER

The Digitac is a voltage impulse digital tachometer, which is suitable for all negative earth ignition systems. It has a 2 digit 7 segment display housed in a black case. Please specify no. of cylinders and if 6 or 12 volt system.

Ready built **£19.78**
Kit form **£14.96**
Prices are fully inclusive
(Quantity discounts)

ELECTRONEQUIP

36 Merton Avenue, Portchester
Hants PO16 9NE. 07018 73455

STRATHAND SECURITY ALARMED?

If not you should be. We specialise in Alarm equipment suitable for home, office or factory. All items brand new top quality fully guaranteed.

101 Magnet and reed switch. Flush fitting. 4 wire. Requires hole 12mm diameter by 34mm deep	90p
102 Magnet and reed switch. Flush fitting screw terminals. Requires hole 15mm diameter by 14mm deep	£1.05
103 Magnet and reed switch. Surface fitting. 4 wire. Size 65mm by 13mm by 11mm	90p
104 Magnet and reed switch. Heavy duty. Size 103mm by 20mm by 18mm. Two hole fixing	£3.00
105 Pressure pad — stair tread 22½" by 6½"	£1.35
106 Pressure pad — large 29½" x 15"	£2.05
107 Window foil — self-adhesive — top quality. 70" roll by ¼" wide	£3.17
108 Foil blocks — self-adhesive. (Joins foil to cable)	19p
110 Keyswitches with mounting plate and cover	£3.70
111 Bell boxes heavy duty plastic coated metal	£8.05
112 Bell 6" heavy duty — very loud 12v D.C.	£10.25
116 4 core cable 100mm — white	£10.75
123 Control panel to British Standard. Mains/battery, silent entry/exit. Anti-lapse alarm circuitry	£46.40

PLUS Radar (microwave) units, automatic 999 dialling units with tape message, and many other items.

STRATHAND SECURITY
44 St. Andrew's Square
Glasgow, G1
Tel: 041-552 6731/2
Callers Welcome



PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components. Full range of ETI printed circuit boards, normally ex-stock, same day despatch at competitive prices. P.C. Boards to individual designs. Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Alfarc range of etch resist transfers, and other drawing materials for p.c. boards.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASON'S ROAD
STRATFORD-ON-AVON
WARWICKS. Tel. 4879

1.2V NICADS

For UK orders add 60p for post and packing
All prices include V.A.T.

BUTTON CELLS

	Dia.	Hgt.	Price / Cell
225mAh	25.0	7.5	0.65
600mAh	34.5	10.0	1.15

VENTED CELLS


(for fast charge)

0.45 Ah	17.5	28.0	0.95
0.5 Ah	HP7 or	Size "AA"	1.10
1.2 Ah	22.5	49.0	1.45
1.8 Ah	HP11 or	Size "C"	1.95
2.5 Ah	32.5	43.0	2.35

Tags available at extra 10p per cell for 0.5Ah, 1.2 Ah and 1.8 Ah nicads only.
Charger — Suitable for any of the above vented nicads — charges up to twelve similar cells in a series at a 50mA or 200mA rate **£9.95**

Sizes approx. in mm
Mail order only

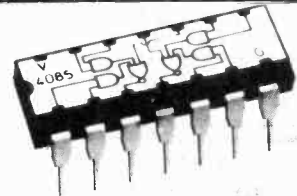V&F SMALLCRAFT (POPLAR) LTD.
38 Stoneleigh Road, Clayhall, Ilford
Essex
01-550 6642



LIVING LOGIC!

STICKIES are printed self-adhesive labels that stick to the top of ICs. They make dull, anonymous plastic blocks into diagrams that come ALIVE! See at-a-glance where to place your test probe or soldering iron — take the hassle out of ICs.

STICKIES are great for building and debugging prototypes, faultfinding, experimenting, teaching — even designing PCB layouts.

STICKIES come in packs for 7400- or 4000-series ICs. Each pack contains a sensible mix of more than 60 different IC types.

120-label pack — **80p**. 480-label pack — **£2.80**, or 2-10 packs at **£2.50** each, 11-plus **£2.20** each.

Prices include VAT and first-class postage. Official orders welcome. Please state whether TTL or CMOS required.

For your STICKIES by return of post
CONCEPT ELECTRONICS, 8 Byham Road
Sevenoaks, Kent TN13 3XA
Phone: 0293 514110

ETI PCB'S



Available for all ETI projects from day one of ETI, phone your order

SPECIAL OFFER — Single sided Pax PCB mat, four off, 4¾" x 6½", 99p all up

CROFTON ELECTRONICS LIMITED

35 GROSVENOR ROAD, TWICKENHAM
MIDDLESEX TW1 4AD · Tel: 01-891 1923

Sound to Light Fantastic!



Videograph II links to the aerial socket of your tv and provides a full colour oscilloscope display! A must for hi-fi, home entertainment, discos, organs etc.

New — signal invert control, integral square wave generator. **Plus** — full details for testing your audio system for transient distortion, cross-talk etc.

Complete £19.95 Luxury cabinet and Kit only **£9.95**

INC. POST, PACKING, VAT. READY BUILT VIDEOGRAPH **£59.95**

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road,
Heronsgate, Brentwood,
Essex CM13 3SD.
Telephone: Brentwood (0277) 810244

THIS SECTION IS A PRE-PAYMENT SERVICE ONLY

MINI-ADS: 31/4" x 21/8", 1-3 £38, 4-11 £36, 12 or more £34 per insertion. CLASSIFIED DISPLAY: 19p per word. Minimum 25 words. Boxed classifieds are £6.33 per col. centimetre. No P.O. Box Numbers can be accepted without full address.

Enquiries to: Advertising Department, 01-437 5982. 25-27 Oxford Street, London W1R 1RF

NEW QUALITY STEREO AMP CHASSIS. 60W (RMS). Protected 3Qmin, 0.03% TAD 12/30V Wkg 20 Trans, din socks controls; select, V/C etc. Boxed data £9.95 (inc.) K. Lawrence, 1 Regent Road, Ilkley, W. Yorks.

L.C.D. WATCHES. 22 function £13.00. Solar 22 function £18.50. LCD portable alarm clock £15.00. All post free 1 yr. guarantee. Powditch, 5, De Vere Gardens, Ilford, Essex. Mail order only. SAE for info.

LINSLEY-HOOD 75 Watt Power Amp modules, built and tested, from £12.50. Complete module kit £10.50 inclusive. Lindsey-Hood 75 watt amplifiers constructed and repaired, comprehensive range of spares in stock. Details and list free. I. G. Bowman (Dept. ETI), 59 Fowey Avenue, Torquay, S. Devon.

MC6800P £8.90. MC6802P improved 6800 MPU with clock and RAM £13.60. 6810 £4.10. 6820 £4.95. Static RAM boards 1Kx8 £21.20 4Kx8 £62.60. VAT. P&P included. Data sheets, 9p+SAE. JK ELECTRONICS, 11-15 Saiters Lane North, Darlington, County Durham.

PRECISION POLYCARBONATE CAPACITORS

All high stability — extremely low leakage

440V AC RANGE (± 10%)	63V DC RANGE (€) each	µF	L (mm)	D	Each	µF (Tol ± 1% ± 2% ± 5%)
0.1	27	12.7	1.34	0.01-0.2	1.80	1.22 0.88
0.22	33	16	1.66	0.22-0.47	1.82	1.24 0.90
0.25	33	16	1.78	1.0	2.26	1.52 1.08
0.47	33	19	2.08	2.2	2.80	1.94 1.42
0.5	33	19	2.24	4.7	4.00	2.72 2.24
0.68	50.8	19	2.48	6.8	4.88	3.36 2.66
1.0	50.8	19	2.64	10.0	6.94	4.68 3.56
2.0	50.8	25.4	3.74	22.0	13.32	9.98 6.80

(Additional values and closer tolerances avail. upon request.)

TRANSISTORS, DIODES, I.C.s. Bridge Rectifiers, Capacitors, Plugs + Sockets, Vero, Fuses, etc. — a complete range is carried, please send for our free detailed price list which will be sent by return of mail.

RESISTORS High stability, low noise, carbon film +5% tol 1/2W @ 40 C 1/3W @ 70 C E12 series only — from 2.2 ohm to 4.7M. All 2p each; 15p/10 of any one value; 95p/100 of any one value; £4.35/500 (may be mixed in 100s); £8/1000 (may be mixed in 100s).

SPECIAL DEVELOPMENT PACK: 10 of each value 2.2 ohm to 2.2M (730 resistors) — £6 50p each.
1W c/f 5% 2.2 ohm to 10M — 5p each; 2W c/f 5% 10 ohm to 10M — 8p each.

PRESETS: 01.W submin. skeleton presets — vertical or horizontal. 100 ohm to 1M. 7p each, £3/50, £5/100, £22.50/500, £40/1,000. Values may be mixed.

ZENER DIODES: 1+ 10+ 50+ 100+ (Values 400mW +5% 3V-33V 10p 9½p 9p 8p may be 1W 3V3-200V 18p 17½p 16½ 15p mixed)

TANTALUM BEAD CAPACITORS: µF/V. 0.1 0.22 0.33 0.47 0.68. 1µF all at 35V @ 10p. 1.5/35, 2.2/25, + 11p. 2.2/35 @ 12p. 4.7/35 @ 15p. 8.8/35 @ 17p. 10/25 @ 17p. 10/35 @ 21p. 15/20, 22/15, 33/10. 47/6.3 @ 21p. 68/3 @ 17p. 100/3 @ 21p (deduct 1p each for qty. of 10+ — values may be mixed).

25p P&P — UK/Export add cost air/sea mail. Add 8% VAT except those marked * add 12½% Wholesale price lists available to bona fide companies. Shop open 9 00 am-5.00 pm, Mon.-Fri.

MARCO TRADING
(Dept. T10)
The Old School, Edstaston, WEM,
Shropshire
Tel. WHIXALL 464 (STD: 094872)
(Props.: Minicost Trading Ltd.)

FIFTEEN CMOS PROJECTS — e.g. 70m.p.h. Alarm; Mini-trombone; Mystery Maze; Micro-power Indicator. Only £1 inc. brings FIFTEEN detailed circuits PLUS 14-pin socket and kits voucher, from DAVID IAN DESIGNS, 47 Hampton Court Parade, East Molesey, Surrey.

GOOD PRICES PAID for electronics / computing books and magazines of recent publication, eg projects, theory, reference etc. Send details to Hart, 41 Luton Pl., Edinburgh.

MEMORY IC's: 2K dynamic RAMs, type MM5262 — 90p each. Data sheets 20p; free with order. Jarvis, 150 Weston Road, Aston Clinton, Aylesbury, Bucks. HP22 5EP.

6800 D2 MICROPROCESSOR. Development system. Fully assembled and tested. Consists of processor board with user I/O interface and keyboard/display board with cassette interface. Full documentation. Offers around £150. Ring 01-398 7146.

SWTPC 6800 MICROCOMPUTER. At a bargain price. Guaranteed in full working order and hardly used. 28K CPU with 3 serial interfaces. Twin mini-floppy disc drives and controller. Cassette interface. Soroc IQ120 VDU. Teletype 43 printer. Full documentation. Offers around £2,800. Individual units available at pro rata prices. Ring 01-398 7146.

LOCMOC LOGIC SWITCHES 2A AT 60V IN 20ns! Using VMOS VN67AF Power FET 99p. FAST LOCMOS: (Brief Data 5p) 4001B/7/11B/69 17p, 4013B 35p, 4016B 40p, 4017B 65p, 4020B 80p. CHEAP LINEAR: 741 19p, CA3140E 40p, LF13741N (JFET 741) 35p, MC3401P (18V LM3900) 45p, 555 24p, 2N3819 14p, 1S923 (200V 200mA) 10/15p. 10% Discount over £5. P&P 20p. Mail Order Only. More bargains in new spec/price list. SAE to J. W. RIMMER, 367 GREEN LANES, LONDON N4 1DY.

CEH manufacture top Home Office approved security gear. Boost your projects with our grade 1 semiconductors, components, modules. — Boards/kits soon. E.g. **Waterproof** vehicle alarm keyswitch/immobiliser. 2 n/o, 2 n/c contacts — £3.68.

Commercial pre-drilled, oil-resistant project cases. 106 x 60 x 50 mm. internal — 75p. Upgrade with list, 18p (9p stamp + S.A.E.) to.

CEH Audio-Visual, 48 Whistler Road, Tonbridge, Kent.

COLOUR MODULATOR

Kit **FOR ALL TV GAMES!**

£6.95

● Red, Green & Blue inputs ● Switchable background colours ● FREE Interface

Complete details for tank battles — lifelike effects

WILLIAM STUART SYSTEMS

137 Billericay Road, Herongate, Brentwood, Essex CM13 3SD
Telephone (0277) 810244

SPECIAL CLEARANCE — BRIDGE RECTIFIERS. WS04 — 1 amp 400V — Pack of 6 — £0.90, includes VAT & PAP — Videotime, 56 Queens Road, Basingstoke, Hants.

ADVERTISEMENT INDEX


ACE	86
ALTEK	13
AMBIT	20
ASTRA-PAK	86
AUDIO	42
BAMBER	90
BAYDIS	33
BI-PAK	4 & 5
B.N.R.S.	71
BULL, J.	90
CAMBRIDGE LEARNING	56
CATRONICS	42
CHARCROFT	97
CHILTMead	41
CHROMASONICS	86
CHROMATRONICS	102
COMMUNICATIONS MEA.	76
COMP, COMP, COMP	107
CRIMSON ELECTRIK	96
DALSTON ELECTRONICS	92
DELTA-TECH	96
DISCOUNT COMPUTING	98
DORAM	50 & 97
E.D.A.	100
ELECTROVALUE	58
FLADAR	68
GREENBANK	70
GREENWELD	100
HARRISON BROS.	98
H.B. COMPUTERS	98
HENRY'S	50, 63, 68 & 97
IBEK	75
I.L.P.	66
INTEGRATED CIRCUITS	28
KRAMER	33, 40, 75 & 94
L.B. ELECTRONICS	72
LEKTROKIT	30
MAPLIN	108
MARSHALLS	52
MEGA	50
METAC	14 & 15
MINIKITS	72
MOUNTAINDENE	72
NICHOLLS	75
N.I.C. MODELS	92
O.K. MACHINE	78
POWERLL	40
POWERTRAN	2 & 6
PROGRESSIVE RADIO	94
R.C.S.	106
ROGER SQUIRES	33
R.T.V.C.	103
SENTINEL	92
SERVICE TRADING	99
SHUDEHILL	68
SINCLAIR	60
SINTEL	92
STEVENSON	101
STERLING SOUND	94
STRUTT	40
SWANLEY	97
TAMTRONIK	102
TARGET	68
TECHNOMATIC	12
TELEPLAY	34 & 35
TEMPUS	85
T.K. ELECTRONICS	102
TRAMPUS	71
TRIDENT EXHIBITIONS	106
VERO	50
VIDEOTIME	79
WATFORD	10 & 11
WILMSLOW	71

RESISTORS (5% 1/4W Carbon Film). 25 of each value. 220Ω, 270Ω, 390Ω, 1kΩ, 2.7kΩ, 3.9kΩ, 4.7kΩ, 10kΩ, 15kΩ, 27kΩ, 33kΩ, 47kΩ, 100kΩ, 220kΩ, 470kΩ, 1MΩ. (400 resistors). Only **£2** Post Paid.

D. Johnston, 12 Balgillo Road, Dundee DD5 3LU

INTERNATIONAL 4600 SYNTHESISER, with switched patching (eliminates fiddly plugboard), all IC's in sockets. Requires additional construction work. Parts originally cost £530, will accept £390 or offers. Telephone Aylesbury (0296) 630364.

DEAD or ALIVE OR JUST MIXED UP?
5-FUNCTION
13 AMP SOCKET TESTER
SAFELY SHOWS YOU!




Safety fast! Shows: **1**, If all wires correct, **2**, Live wire faulty, **3**, Live and Neutral wires reversed, **4**, Earth faulty, **5**, Neutral faulty. Shows exact fault instantly. British made. **£3.95** post free. Save time. Be sure. Be safe.

PERSONAL SAFETY CO.
Dept. ETI, P.O. Box 2
LLANRWST
Gwynedd, North Wales

LOW FREQUENCY GENERATOR

TYPE 203

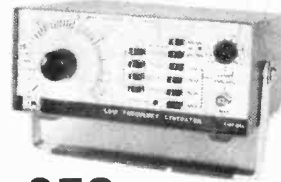4 Ranges
10Hz-100KHz
Square and Sine Wave
2.5 Volts Max.
80db variable Attenuator
Amplitude Stability — 0.1%
Harmonics — Less than 0.03%



£78

Manufacturers of Frequency Counters — Frequency Standards — Off Air Receivers.

RCS

R.C.S. ELECTRONICS

6 Wolsey Road, Ashford, Middx.
Tel: Ashford 53661 (Postal Code TW15 2RB)

MICROCOMPUTER I.C.s. 21L02 low power RAM. 1Kx1 450ns, £1.00 each, 8 for £7.25, 16 for £13.50. 32 for £27.00. Also 2708 EPROM, 1Kx8 450ns. £7.25 each. Inclusive prices. A. C. Gidlow, 7 Cypress Road, Newport, Isle of Wight, PO30 1EY.

**PLEASE MENTION ETI
WHEN REPLYING
TO ADVERTS**

HIGH QUALITY 3 POLE DRIVE MOTOR

with variable pulse width controller and information.

Only £1.75
including VAT
and postage

**ELECTRONIC CENTRE
Stockport Ltd
45 Lower Hillgate
Stockport**

Tel: 480 9791

**BREAD
BOARD**

→ goto
Marble sch. N.
01

1978

The kits & bits show for the home electronics enthusiast

Seymour Hall Seymour Place London W1

21-25 November 1978

Seventy stands packed with the gear that the home electronics constructor needs. From kits for keen youngsters just starting — to components for the dedicated enthusiast intent on building his own computer, it can all be seen and bought on the spot in the Seymour Hall this November. Browse through the range of instrumentation, test gear, components and circuit boards. Kits for making everything from an electric grandfather clock to an electronic organ. Build your own microprocessor, construct your own television games and choose hi-fi audio modules for the ultimate in sound!

Watch the Demonstrations in adjoining halls — electronic projects brought to life by the experts — and a chance for you to try for yourself the latest ideas from manufacturers and journals.

Competitions — Win a microprocessor kit — a frequency counter — a 'starter' kit for the kids — and many other daily prizes throughout the show.

Open 10 a.m. — 7 p.m. daily.
Entrance £1.00 adults, 70p students.

Organised by Trident Conferences and Exhibitions Limited, Abbey Mead House, 23a Plymouth Road, Tavistock, Devon. PL19 8AU.
Tel: 0822 4671 Telex: 45412 TRITAV.

THE SORCERER HAS ARRIVED

Z80
BASED
32k RAM
COMPUTER
FOR LESS
THAN
£1,000

I WANTED
TO SPEND LESS
THAN £1,000
MY SORCERER
COST ME
£950



Introducing the personal computer you've waited for. The Exidy Sorcerer.

I didn't buy my personal computer until I found the one that had all the features I was looking for.

The Exidy Sorcerer does everything I wanted to do and a few things I never dreamed of.

It isn't magic. Exidy started with the best features of other computers, added some tricks of their own, and put it all together with more flexibility than ever before available. Presto! My reasons for waiting just disappeared.

I wanted pre-packed programs.

Software on inexpensive cassette tapes for the Sorcerer is available from Exidy and many other software makers.

I wanted user programmability

The Sorcerer's unique plug-in ROM PAC™ Cartridges contain programming languages such as Standard (Altair 8k*) BASIC, Assembler and Editor (so I can develop system software), operating systems such as DOS (so I can also use FORTRAN and COBOL) and applications packages such as Word Processor.

*Altair is a trademark of Pertec Computer Corp.

I wanted Graphics, and the Sorcerer is super. Its 256 character set — more than any other personal computer — includes 128 graphic symbols that I can define.

I wanted high resolution video.

With 122,880 points in a 512 x 240 format, I get the most detailed illustrations.

I wanted to display more information.

The Sorcerer displays 1920 characters in 30 lines of 64 characters — equal to a double-spaced typed page.

I wanted a full, professional keyboard.

The Sorcerer's 79-key data processing keyboard provides designated graphics, the complete ASCII character set in upper and lower case, and a 16-key numeric pad.

I wanted memory. The 12k of ROM holds a Power-On Monitor and Standard BASIC; 32k of RAM is supplied on board.

I wanted expandability. Serial and parallel I/Os are built in, and the op-

tional 6-slot S-100 expansion unit lets my system grow.

I wanted a computer that's easy enough for children to use. I just connect my Sorcerer to a video display and a cassette tape recorder, and if I have any questions the easy-to-understand Operation and BASIC Programming manuals have the answers.

I wanted to buy from an experienced Manufacturer. In five years Exidy has become the third largest producer of microprocessor-based video arcade games.

I wanted to spend less than £1,000.

(This is where COMP. does a little magic). My Sorcerer cost me £950!.

Now, what are you waiting for?

Call COMP. on 01-441 2922 or write to

COMP COMPUTER COMPONENTS


14 Station Road,
New Barnet, Herts. EN5 1QW.

(Price shown ex. VAT)

DEALER ENQUIRIES INVITED, A LIMITED NUMBER OF DEALERSHIPS STILL AVAILABLE.


MAPLIN

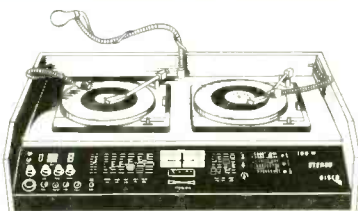everything for the modern D.I.Y. electronics enthusiast and more.




100W RMS STEREO DISCO

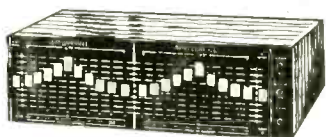A genuine 100W RMS per channel (both channels driven) stereo disco with auto fade on microphone, VU meters, full monitoring and cueing facilities and a very high quality light show. Complete construction booklet MES41 price 25p. Cabinet comes complete with lid and carrying handles.



10 CHANNEL STEREO GRAPHIC EQUALISER

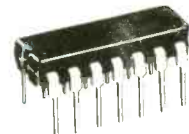A new design with no difficult coils to wind, but a specification that puts it in the top-flight hi-fi class. All this for around £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 25p. (All prices include V.A.T. and p.&p.).




INTEGRATED CIRCUITS

Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applications circuits and projects to build. Post the coupon now!




VERY LOW-DISTORTION AUDIO OSCILLATOR

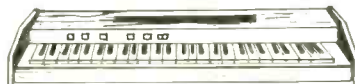The very low distortion sine wave (0.01%) output is suitable for testing very high quality hi-fi audio equipment. Also includes square wave output. Range 20Hz to 26kHz. Output 0V to 1V in three continuously variable steps. Total cost around £21. Full construction details in our catalogue. Send the coupon below now! (All prices include V.A.T. and p.&p.).




TOUCH-SENSITIVE PIANO

The revolutionary new IC AY-1-1320 first seen on 'Tomorrow's World' now available. Complete kit of ICs to build a 60-note piano (18 x ICs) order as HQ53H price £36.86. Preliminary circuit details in our October newsletter. Complete design, pcb's attractive veneered wooden cabinet available soon. It's the most realistic-sounding electronic piano we've ever heard and includes simulated damping, loud and soft pedals. Full details in our newsletters. (All prices include V.A.T. and p.&p.).

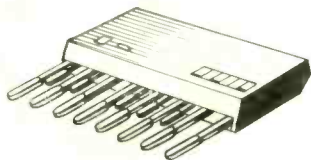


PEDAL UNIT

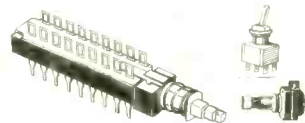A completely self-contained pedal unit, 13-note, 2-octave range, 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue - post the coupon below, now!



SWITCHES

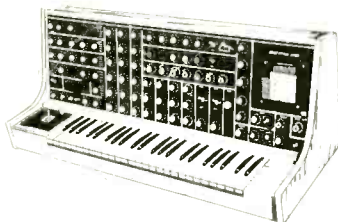We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches - there are dozens to choose from, but it's only a tiny part of our fantastic range.



SYNTHESISER

The International 4600 Synthesiser. A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart leak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request. Full construction details in our construction book £1.50. (All prices include V.A.T. and p.&p.).



'PE' STRING ENSEMBLE

Unbeatable prices and finest quality components only when you buy from Maplin. All parts available to build this fascinating project. Component schedule available shortly (see appreciated). Demonstration model in our shop soon. Phone now and compare our prices.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).



IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 715157

POST THIS COUPON NOW FOR YOUR COPY OF OUR 1979-80 CATALOGUE PRICE 75p

Please rush me a copy of your 280-page catalogue as soon as it is published (8th January 1979)

I enclose 75p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded.

NAME _____

ADDRESS _____