

# electronics today

INTERNATIONAL

JUNE 1984 95p

## SIMPLY THE BEST THAT YOU CAN BUILD

A new pre and power amp combination from John Linsley Hood



**PLUS**

**PROJECTS TO BUILD:**

**Loudspeaker with novel drive unit**

**EPROM board for the Oric/Atmos**

**Centronics interface for the Cortex**

**SPECIAL AUDIO ISSUE**



# High performance, low price kits for today's musicians

## DIGITAL DELAY LINE




Digital delay circuitry is an absolute necessity for high quality studio work, but usually comes with a four-figure price tag.

Powertran can now offer you digital quality for the price of a high analog unit. The unit gives delay times from 1.6mSecs to 1.6 secs with many powerful effects including phasing, flanging, A.D.T., chorus, echo and vibrato. The basic kit is extended in 400mSec steps up to 1.6 seconds simply by adding more parts to the PCB.

Complete kit (400mS delay) ..... **£179**    Parts for extra 400mS delay (up to 3) ..... **£19.50**
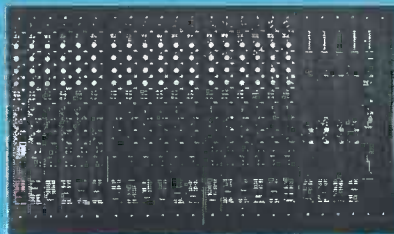
## 'DESTINY' MIXER

This versatile mixer offers a maximum of 24 inputs, 4 outputs, and an auxiliary channel. Input channels have Mic/Line, variable gain, bass/treble, and middle frequency equaliser. Output channels have PPM displays and record/studio outputs. There are send/return jacks, auxiliary, pan and fader controls, and output and group switching. There is also a head-phone jack and built-in talk-back microphone.



Input channel ..... **£23.00**  
 Output channel ..... **£23.00**  
 Aux. channel ..... **£26.00**  
 Blank panel ..... **£3.50**  
 Base unit and front ..... **£33.00**  
 Pair of end cheeks ..... **£25.00**  
 Power supply and cabinet ..... **£22.50**

## TRANSCENDENT 2000

ETI single board synthesizer.




This professional quality 3-octave instrument is transposable 2 octaves up or down, giving an effective 7-octave range.

There is portamento pitch bending, VCO with shape and pitch modulation, VCF with high and low pass outputs and separate dynamic sweep control, noise generator and an ADSR envelope shaper. Other features include special circuitry with precision components to ensure tuning stability.

Complete kit ..... **£150**

## MPA 200

100 watt mixer/amplifier

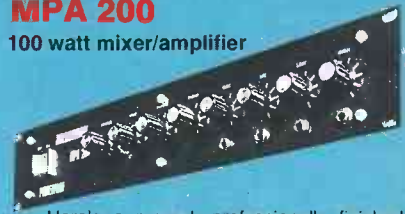

Here's a rugged, professionally finished mixer amp designed for adaptability, stability and easy assembly. Using new super-strength power transistors and a minimum of wiring, it offers a wide range of inputs (extra components are supplied for additional inputs), 3 tone controls, each with 15dB boost and 15dB cut, and a master volume control.

Complete kit ..... **£79.50**

## SP2-200

2-channel, 100-watt amplifier



The SP2-200 uses two of the power amplifier sections of the MPA 200 (above), each with its own power supply. A custom designed toroidal transformer enables both channels to simultaneously deliver over 100W rms into 8 ohms. Each channel has its own volume control, and a sensitivity of 0.775mV (0dBm) makes this amplifier suitable for virtually all pre-amps or mixers.

Complete kit ..... **£99.50**

## CHROMATHEQUE 5000

ETI 5-channel lighting effects system




Many lighting control units are now available. Some perform switching and others modulation of light output according to musical input. The Chromatheque combines both functions. It controls 5 banks of lamps up to 500W each in either analog or digital mode. And the 5 channels give more colours and more exciting linear and random sequencing than is possible with 3 or 4-channel systems. Versatile light level controls enable the lights to be partially on to suit the mood of the occasion. Wiring is minimal and construction straightforward.

Complete kit ..... **£79.50**

All goods subject to availability.

Allow 21 days for delivery

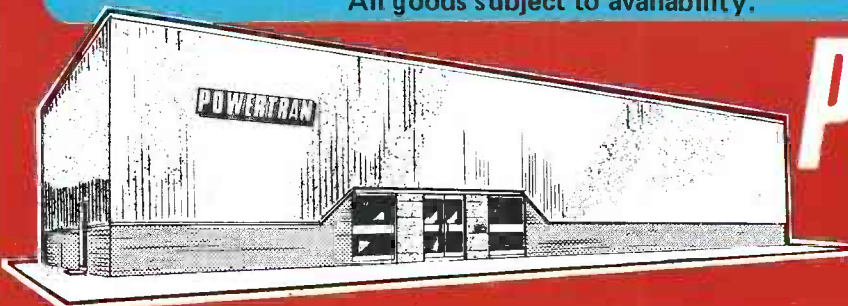

# POWERTRAN cybernetics Ltd.

POWERTRAN CYBERNETICS LTD, PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3ET. TEL: (0264) 64455

ALL PRICES ARE EXCLUSIVE OF VAT AND APPLY TO THE U.K. ONLY - ALLOW 21 DAYS FOR DELIVERY. OVERSEAS CUSTOMERS - PLEASE CONTACT OUR EXPORT DEPARTMENT FOR THE NAME AND ADDRESS OF YOUR LOCAL DEALER.

# electronics today

INTERNATIONAL JUNE 1984 VOL 13 NO 6

EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.  
Telex 8811896.



**Dave Bradshaw:** Editor  
**Phil Walker:** Project Editor  
**Ian Pitt:** Editorial Assistant  
**Jerry Fowler:** Technical Illustrator  
**Paul Stanyer:** Ad. Manager  
**Lynn Collis:** Copy Control  
**Ron Harris B.Sc:** Managing Editor  
**T.J. Connell:** Chief Executive

**PUBLISHED BY:**  
Argus Specialist Publications Ltd.,  
1 Golden Square, London W1R 3AB.

**DISTRIBUTED BY:**  
Argus Press Sales & Distribution Ltd.,  
12-18 Paul Street, London EC2A 4JS  
(British Isles)

**PRINTED BY:**  
The Garden City Press Ltd.  
**COVERS PRINTED BY:**  
Alabaster Passmore.

**OVERSEAS EDITIONS and their EDITORS**  
AUSTRALIA -- Roger Harrison  
CANADA -- Halvor Moorshead  
GERMANY -- Udo Wittig  
HOLLAND -- Anton Kriegsmann



Member of the  
Audit Bureau  
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1984 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription Rates, UK £14.35 including postage. For further details and Airmail rates etc, see the Readers' Services page.

## FEATURES

**DIGEST** ..... 9  
A spoonful of sarcasm helps the press releases go down.

**STOP CRACKLE AND POP**..... 19  
Vivian Capel on how to take the wincies out of Wogan without losing any of the waffle.

**THE WORLD OF MICROTAN 65** ..... 33  
Mike Bedford concludes his guide to plug-in cards for the Microtan.

**QED AMPLIFIER REVIEW** ..... 45  
A little something to cheer up those who really can't be bothered to build John Linsley Hood's Audio Design amplifier and who happen to have £99 to spare.

**KIT LOUDSPEAKER REVIEW**... 52  
Ian Pitt gets stuck into a new Peerless kit from Wilmslow Audio.


**DETAIL FOR DETAIL**..... 63  
Stan Thatcher explains how not to get your signals in a twist.


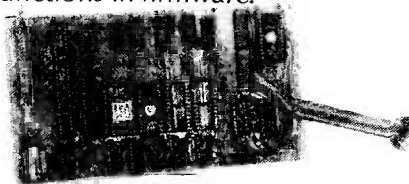
## PROJECTS

**AUDIO DESIGN AMPLIFIER**... 24  
The long-awaited sequel to John Linsley Hood's Audio Design series — the first of three articles describing an audio pre and power amplifier combination of exceptional quality.

**EPROM BOARD FOR THE ORIC/ATMOS**..... 36  
A versatile design which allows users of the Oric and Atmos microcomputers to program EPROMs and also implement a wide range of functions in firmware.



**SPECTRUM JOYSTICK INTERFACE** ..... 49  
Now you can really give those aliens some stick with this design by Mike Wynne-Jones.

**NOVEL LOUDSPEAKER DESIGN**..... 57  
Carl Pinfold's flat-diaphragm loudspeakers have created quite a flap — now ETI readers can build a pair for themselves.

**CORTEX CENTRONICS INTERFACE** ..... 65  
No, we haven't forgotten the Cortex owners among our readership, and to prove it here's an interface for use with the Centronics ports found on many popular printers.

## INFORMATION

**NEXT MONTH'S ETI**..... 6  
**ETI BOOK SERVICE**..... 61  
**PCB FOIL PATTERNS**..... 68

**ETI PCB SERVICE**..... 70  
**ADVERTISERS' INDEX**..... 74



# WATFORD ELECTRONICS

33/34 CARDIFF ROAD, WATFORD, HERTS. ENGLAND

MAIL ORDER. CALLERS WELCOME

Tel. Watford (0923) 40588. Telex. 8956095

ALL DEVICES FULLY GUARANTEED. SEND CHEQUE, P.O.s, CASH, BANK DRAFT WITH ORDERS. TELEPHONE ORDERS BY ACCESS/MASTER CHARGE ACCEPTED. GOVERNMENT & EDUCATIONAL ESTABLISHMENTS OFFICIAL ORDERS WELCOME P&P ADD 75p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car parking space available.

**ELECTROLYTIC CAPACITORS:** (Values in  $\mu$ F) 500V: 10u52, 47 78p, 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 8p 10 10p, 15, 22, 12p, 33 15p, 47 12p, 68 20p, 100 19p, 220 26p, 1000 70p, 2200 99p, 50V: 60 20p, 100 17p, 220 24p, 330 22p, 33 12p, 330, 470 32p, 1000 48p, 2200 90p, 25V: 1.5, 4.7, 10, 22, 47 8p, 100 15p, 150 12p, 220 15p, 330 22p, 470 25p, 680, 1000 34p, 1500 42p, 2200 50p, 3300 76p, 4700 92p, 16V: 47, 68, 100 9p, 125 12p, 330 16p, 470 20p, 680 34p, 1000 27p, 1500 31p, 2200 26p, 4700 72p.

**TAG-END CAPACITORS:** 64V: 2200 139p, 3300 198p, 4700 245p, 50V: 2200 110p, 3300 184p, 40V: 4700 180p, 25V: 2200 90p, 3300 98p, 4000, 4700 98p, 10,000 320p, 15,000 345p, 16V: 22,000 350p.

**POLYESTER CAPACITORS: Axial Lead Type**  
400V: 1nF 1.5nF, 2n2, 3n3, 4n7, 6n8 11p, 10n, 15n, 18n, 22n 12p, 33n, 47n, 68n, 100n, 220n, 330n, 470n, 52p, 330n, 470n, 52p, 330n, 470n, 52p, 680n, 1uF 68p, 2uF 82p. 1000V: 1nF 17p, 10nF 30p, 15n 40p, 22n 36p, 33n 42p, 47n, 100n 42p.

**POLYESTER RADIAL LEAD CAPACITORS: 250V**  
10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 8p; 150n, 220n, 330n, 470n 15p, 680n 19p; 1uF 40p, 2uF 48p.

**TANTALUM BEAD CAPACITORS**  
35V: 0.1uF, 0.22, 0.33 15p, 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p, 10 28p; 16V: 2.2, 3.3 16p; 4.7, 6.8, 10 18p, 15, 36p; 2.2 25p; 3.3, 4.7, 50p; 100 85p; 10V: 1.5, 2.2, 26p; 3.3, 4.7 50p; 100 80p; 6V: 100 55p.

**MYLAR FILM CAPACITORS**  
1000V: 1nF, 2, 4, 4nF, 10 6p; 15nF 22n, 30n, 40n 47p, 75p, 56n, 100n, 200n 9p; 50V: 47nF 12p.

**CERAMIC CAPACITORS 50V:**  
Range 0.5pF to 10nF 4p, 15nF 22nF 33nF, 47pF, 50pF, 100nF/300V 7p, 200nF/6V 8p.

**POLYSTYRENE CAPACITORS:**  
10pF to 1nF 8p; 1.5nF to 12nF 10p.

**SILVER MICA (Values in pF)**  
2.3, 3.3, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 130, 150, 180, 220, 270, 330, 390, 470, 500, 600, 820, 1000, 1200, 1500, 2000, 3000, 4700pF 80p.

**MINIATURE TRIMMERS Capacitors**  
2-60pF 2-10pF 22p; 2-25pF; 5-65pF 30p; 10-88pF 36p.

**RESISTORS** Carbon Film, miniature, Hi-Stab, 5%.  
0.25W 2R2 - 10M E24 3p 1p  
0.5W 2R2 - 4M E12 3p 1p  
1W 2R2 - 10M E12 6p 4p  
1/2 Metal Film 51R - 1M E24 6p 4p  
1/2 Metal Film 51R - 1M E24 8p 6p  
100+ price applies to Resistors of each type not mixed.

**RESISTORS NETWORK S.I.L.**  
7 Commoned (6 pins) 100n, 680n, 1K 2K, 4K7, 10K, 47K, 100K, 25p  
8 Commoned (9 pins) 150n, 180n, 270n, 330n, 1K, 2K, 4K7, 6K8, 10K, 22K, 47K & 100K 26p.

| DIODES |     | BRIDGE RECTIFIERS |     | 75 SERIES |    |
|--------|-----|-------------------|-----|-----------|----|
| AA118  | 15  | 75107/8           | 98  | 5A/40V    | 32 |
| AA129  | 20  | 75110             | 90  | 5A/400V   | 36 |
| AA130  | 15  | 75114/15          | 130 | 5A/600V   | 40 |
| BA100  | 15  | 75121/2           | 150 | 8A/300V   | 90 |
| BAX    | 20  | 75150             | 125 | 8A/300V   | 90 |
| BY100  | 20  | 75154             | 125 | 8A/300V   | 90 |
| BY126  | 12  | 75158             | 150 | 8A/300V   | 90 |
| BY127  | 14  | 75159             | 150 | 8A/300V   | 90 |
| CRO33  | 250 | 75182/4           | 99  | 8A/300V   | 90 |
| OA8    | 40  | 75185/9           | 95  | 8A/300V   | 90 |
| OA7    | 12  | 75322             | 140 | 8A/300V   | 90 |
| OA70   | 12  | 75324             | 360 | 8A/300V   | 90 |
| OA75   | 15  | 75325             | 200 | 8A/300V   | 90 |
| OA81   | 20  | 75361/3           | 150 | 8A/300V   | 90 |
| OA85   | 15  | 75365             | 150 | 8A/300V   | 90 |
| OA90   | 15  | 75450             | 86  | 8A/300V   | 90 |
| OA91   | 8   | 75452             | 52  | 8A/300V   | 90 |
| OA92   | 8   | 75454             | 70  | 8A/300V   | 90 |
| OA93   | 8   | 75491/2           | 65  | 8A/300V   | 90 |
| OA202  | 8   |                   |     | 8A/300V   | 90 |
| OA202  | 8   |                   |     | 8A/300V   | 90 |
| IN914  | 4   |                   |     | 8A/300V   | 90 |
| IN916  | 4   |                   |     | 8A/300V   | 90 |
| IN917  | 4   |                   |     | 8A/300V   | 90 |
| IN918  | 4   |                   |     | 8A/300V   | 90 |
| IN919  | 4   |                   |     | 8A/300V   | 90 |
| IN920  | 4   |                   |     | 8A/300V   | 90 |


| ZENERS   |    | SCR THYRISTORS |    |
|----------|----|----------------|----|
| 1N4001/2 | 5  | 5A/40V         | 32 |
| 1N4003   | 5  | 5A/400V        | 36 |
| 1N4004   | 5  | 5A/600V        | 40 |
| 1N4007   | 7  | 8A/300V        | 90 |
| 1N4148   | 4  | 8A/300V        | 90 |
| 1N5401   | 15 | 8A/300V        | 90 |
| 1N5404   | 16 | 8A/300V        | 90 |
| 1N5406   | 17 | 8A/300V        | 90 |
| 1N5408   | 19 | 8A/300V        | 90 |
| 1S4      | 9  | 8A/300V        | 90 |
| 1S921    | 9  | 8A/300V        | 90 |
| 6A/100V  | 40 | 8A/300V        | 90 |
| 6A/400V  | 50 | 8A/300V        | 90 |
| 6A/600V  | 60 | 8A/300V        | 90 |

| VARICAPS |     | DIAC       |     |
|----------|-----|------------|-----|
| BA102    | 50  | RO-3-2513U | 650 |
| BB105B   | 40  | RO-3-2513U | 650 |
| BB106    | 40  | RO-3-2513U | 650 |
| BB109    | 45  | RO-3-2513U | 650 |
| BB200    | 105 | RO-3-2513U | 650 |

## TRANSISTORS

|           |    |          |     |          |     |          |     |          |    |          |    |         |     |
|-----------|----|----------|-----|----------|-----|----------|-----|----------|----|----------|----|---------|-----|
| AC126/7   | 35 | BC327    | 15  | BF387/8  | 35  | MPSU6    | 60  | ZTX107/8 | 12 | 2N3820   | 60 | 2SC2335 | 200 |
| AC127     | 35 | BC328    | 15  | BF394    | 40  | MPSU5    | 65  | ZTX109   | 12 | 2N3824/3 | 60 | 2SC2547 | 40  |
| AC176     | 35 | BC447/1  | 34  | BF451    | 40  | MPSU5    | 60  | ZTX122   | 28 | 2N3866   | 90 | 2SC2612 | 200 |
| AC181     | 35 | BC447/2  | 34  | BF494/5  | 40  | MPSU6    | 60  | ZTX300   | 13 | 2N3903/4 | 15 | 2SD234  | 74  |
| AC198     | 35 | BC516/7  | 40  | BF594/5  | 30  | OC26     | 170 | ZTX302   | 16 | 2N3905/6 | 15 | 2SK45   | 80  |
| AC199/1   | 75 | BC547/8  | 12  | BF939/40 | 30  | OC28     | 220 | ZTX303   | 25 | 2N3906   | 17 | 2SK288  | 225 |
| AD12/1    | 75 | BC549C   | 15  | BF944/7  | 25  | OC35     | 330 | ZTX304   | 17 | 2N4037   | 60 | 2SK305  | 60  |
| AD149     | 75 | BC559/9  | 15  | BF988    | 105 | OC42     | 75  | ZTX305   | 17 | 2N4061/2 | 15 | 2SK325  | 225 |
| AD161     | 42 | BCY39/40 | 85  | BFX29    | 35  | OC71/72  | 50  | ZTX500   | 14 | 2N4264   | 30 | 3N140   | 115 |
| AD162     | 42 | BCY41/42 | 30  | BFX81    | 45  | OC75/76  | 55  | ZTX501/2 | 15 | 2N4286   | 25 | 40315   | 90  |
| AF115/6   | 80 | BCV45    | 50  | BFX84    | 35  | OC81/82  | 50  | ZTX503   | 15 | 2N4289   | 25 | 40316   | 95  |
| AF118     | 80 | BCV58/59 | 36  | BFY85/6  | 35  | OC83/84  | 35  | ZTX504   | 15 | 2N4295   | 25 | 40317   | 95  |
| AF124/26  | 70 | BCY70/11 | 12  | BFY90    | 60  | OC87/88  | 35  | ZTX505   | 15 | 2N4303   | 15 | 40324   | 100 |
| AF178     | 75 | 1CY72    | 25  | BFY52    | 30  | OC90     | 40  | ZTX510   | 25 | 2N4427   | 80 | 40347   | 90  |
| AF186     | 70 | BD114    | 190 | BFY55/56 | 56  | TIP29A   | 32  | ZTX512   | 25 | 2N4671   | 55 | 40348   | 120 |
| AF239     | 55 | BD121    | 95  | BFY64    | 40  | TIP29C   | 38  | ZTX513   | 25 | 2N4672   | 55 | 40360   | 80  |
| BC107     | 12 | BD124    | 115 | BFY81    | 120 | TIP30A   | 35  | ZTX514   | 25 | 2N4673   | 25 | 40362   | 70  |
| BC107B    | 14 | BD131/32 | 65  | BFY90    | 60  | TIP30C   | 37  | ZTX515   | 25 | 2N4674   | 25 | 40363   | 75  |
| BC108     | 12 | BD133    | 70  | BFY93    | 50  | TIP31A   | 30  | ZTX516   | 25 | 2N4675   | 25 | 40364   | 75  |
| BC108B    | 14 | BD135    | 45  | BSX20    | 30  | TIP31B   | 39  | ZTX517   | 25 | 2N4676   | 25 | 40365   | 75  |
| BC108C    | 14 | BD136/37 | 40  | BSX26/29 | 45  | TIP31C   | 45  | ZTX518   | 25 | 2N4677   | 25 | 40366   | 75  |
| BC109     | 12 | BD138/40 | 40  | BSY26    | 35  | TIP32A   | 43  | ZTX519   | 25 | 2N4678   | 25 | 40367   | 75  |
| BC109B    | 14 | BD144    | 120 | BSY26A   | 35  | TIP32B   | 43  | ZTX520   | 25 | 2N4679   | 25 | 40368   | 75  |
| BC114/5   | 30 | BD158    | 68  | BU105    | 180 | TIP33A   | 70  | ZTX521   | 25 | 2N4680   | 25 | 40369   | 75  |
| BC117/8   | 25 | BD205/6  | 110 | BU206    | 200 | TIP33B   | 75  | ZTX522   | 25 | 2N4681   | 25 | 40370   | 75  |
| BC137/9   | 40 | BD245    | 65  | BU208    | 200 | TIP33C   | 105 | ZTX523   | 25 | 2N4682   | 25 | 40371   | 75  |
| BC140     | 38 | BD378    | 70  | BU210    | 225 | TIP33A   | 120 | ZTX524   | 25 | 2N4683   | 25 | 40372   | 75  |
| BC142/3   | 38 | BD434    | 30  | M80801   | 250 | TIP35A   | 120 | ZTX525   | 25 | 2N4684   | 25 | 40373   | 75  |
| BC147     | 12 | BD517    | 75  | MJ2955   | 90  | TIP36A   | 130 | ZTX526   | 25 | 2N4685   | 25 | 40374   | 75  |
| BC147B    | 15 | BD645    | 80  | MJE170   | 150 | TIP36B   | 140 | ZTX527   | 25 | 2N4686   | 25 | 40375   | 75  |
| BC148     | 12 | BD695A   | 150 | MJE160   | 150 | TIP41A   | 50  | ZTX528   | 25 | 2N4687   | 25 | 40376   | 75  |
| BC148B    | 15 | BD696A   | 150 | MJE340   | 54  | TIP41B   | 52  | ZTX529   | 25 | 2N4688   | 25 | 40377   | 75  |
| BC149     | 15 | BF148/9  | 30  | MJE300   | 100 | TIP42    | 58  | ZTX530   | 25 | 2N4689   | 25 | 40378   | 75  |
| BC149C    | 15 | BF154/8  | 30  | MJE310   | 100 | TIP42B   | 58  | ZTX531   | 25 | 2N4690   | 25 | 40379   | 75  |
| BC152     | 15 | BF167    | 35  | MJE520   | 85  | TIP212   | 70  | ZTX532   | 25 | 2N4691   | 25 | 40380   | 75  |
| BC183L    | 10 | BF173    | 35  | MJE521   | 98  | TIP121/2 | 73  | ZTX533   | 25 | 2N4692   | 25 | 40381   | 75  |
| BC184     | 10 | BF177    | 35  | MJE295   | 96  | TIP412   | 120 | ZTX534   | 25 | 2N4693   | 25 | 40382   | 75  |
| BC185     | 10 | BF181    | 35  | MJE355   | 70  | TIP35A   | 120 | ZTX535   | 25 | 2N4694   | 25 | 40383   | 75  |
| BC186/7   | 25 | BF179    | 40  | MFF102   | 40  | TIP295   | 70  | ZTX536   | 25 | 2N4695   | 25 | 40384   | 75  |
| BC188/6/7 | 25 | BF145/3  | 38  | MFF103   | 30  | TIP305   | 70  | ZTX537   | 25 | 2N4696   | 25 | 40385   | 75  |
| BC192     | 10 | BF194/5  | 12  | MFF104   | 30  | TIS43    | 40  | ZTX538   | 25 | 2N4697   | 25 | 40386   | 75  |
| BC212L    | 12 | BF198/9  | 18  | MFF105   | 30  | TIS44/5  | 45  | ZTX539   | 25 | 2N4698   | 25 | 40387   | 75  |
| BC213     | 10 | BF200    | 18  | MFF106   | 30  | TIS45/6  | 45  | ZTX540   | 25 | 2N4699   | 25 | 40388   | 75  |
| BC214     | 10 | BF202A   | 40  | MFF107   | 30  | TIS90/1  | 30  | ZTX541   | 25 | 2N4700   | 25 | 40389   | 75  |
| BC214L    | 12 | BF245    | 50  | MFF108   | 30  | UC       | 65  | ZTX542   | 25 | 2N4701   | 25 | 40390   | 75  |
| BC237/8   | 15 | BF268A   | 45  | MFF109   | 30  | MPSA12   | 32  | ZTX543   | 25 | 2N4702   | 25 | 40391   | 75  |
| BC256B    | 35 | BF258    | 50  | MFF110   | 30  | MPSA50   | 30  | ZTX544   | 25 | 2N4703   | 25 | 40392   | 75  |
| BC257     | 35 | BF259    | 50  | MFF111   | 30  | MPSA50   | 30  | ZTX545   | 25 | 2N4704   | 25 | 40393   | 75  |
| BC308     | 16 | BF259    | 50  | MFF112   | 30  | MPSA50   | 30  | ZTX546   | 25 | 2N4705   | 25 | 40394   | 75  |
| BC318     | 40 | BF275    | 55  | MFF113   | 30  | MPSA50   | 30  | ZTX547   | 25 | 2N4706   | 25 | 40395   | 75  |

|        |     |         |     |         |     |      |     |        |     |      |      |       |     |
|--------|-----|---------|-----|---------|-----|------|-----|--------|-----|------|------|-------|-----|
| CA3140 | 45  | MC1469  | 300 | TD2A20  | 320 | 7473 | 35  | 7473/3 | 170 | S412 | 380  | LS169 | 90  |
| CA3160 | 95  | MC1494  | 694 | TD2A20  | 320 | 7474 | 35  | 7472/6 | 120 | S470 | 325  | LS170 | 100 |
| CA3161 | 160 | MC1495  | 350 | TDB0791 | 420 | 7475 | 60  | 7472/8 | 120 | S471 | 620  | LS171 | 100 |
| CA3162 | 620 | MC1486  | 70  | TL170   | 50  | 7476 | 40  | 7479   | 45  | S472 | 1150 | LS172 | 100 |
| CA3169 | 275 | MC1487  | 70  | TL171   | 50  | 7477 | 40  | 7479/2 | 45  | S473 | 1150 | LS173 | 100 |
| CA3186 | 275 | MC1488  | 290 | TL507   | 110 | 7481 | 120 | 7478   | 220 | S474 | 800  | LS174 | 100 |
| HA1388 | 255 | MC1709G | 90  | TL509   |     |      |     |        |     |      |      |       |     |

|  |  |  |  |  |   |  |
|--|--|--|--|--|---|--|
| <b>SWITCHES</b><br>TOGGLE: 2A, 250V<br>SPST<br>DPDP<br>48p<br>SUB-MIN TOGGLE<br>SPST on/off 58p<br>SPST c/wover 54p<br>SPDT centre off 85p<br>SPDT biased both ways 105p<br>DPDT 6 tags 80p<br>DPDT centre off 88p<br>DPDT biased both ways 145p<br>DPDT 3 positions on/over 185p<br>4-pole 2 way 220p<br>SLIDE 250V:<br>DPDT 1A 14p<br>DPDT 1A c/w/ 15p<br>DPDT 1/2A 13p<br>PUSHBUTTON 6A with 10mm Button<br>SPDT latching 150p<br>DPDT latching 200p<br>SPDT moment 150p<br>DPDT moment 200p<br>Mini Non Locking Push to Make 15p<br>Push to Break 25p<br>DIGITAl Switch Assorted Colours 75p each<br> ETI PROJECTS We stock most parts  | <b>DIP SWITCHES</b><br>(SPST) 4 way 85p<br>10 way 125p (SPDT) 4 way 180p<br><b>ROTARY SWITCHES</b><br>(Adjustable Stop Types)<br>1 pole/2 to 12 way, 2 pole/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 48p<br><b>ROTARY:</b> Mains DP 250V 4 Amp on/off 68p<br><b>ROTARY:</b> (Mak-a-switch) Make a multiway switch Shuffling assembly has adjustable stop Accommodates up to 6 wafers (max. 6 pole/12 way + DP switch). Mechanism only 90p<br><b>WAFERS:</b> (make before break) to fit the above switch mechanism. 1 pole/2 way, 2 pole/6 way, 3 pole/4 way, 4 pole/3 way, 6p/2 Way 65p<br>Mains DP 4A Switch to fit Spacers 4p. Screen 6p. 45p<br><b>ROCKER SWITCHES</b><br>ROCKER 5A/250V SPST 28p<br>ROCKER 10A/250V SPDT 39p<br>ROCKER 10A/250V DPDT c/w/ 95p<br>ROCKER 10A/250V DPST with neon 85p<br><b>THUMBWHEEL</b> Mini front mounting switches<br>Decade Switch Module 275p<br>B.C.D. Switch Module 298p<br>Mounting Leads (per pair) 75p<br><b>JUMPER LEADS</b> (Ribbon Cable Assembly)<br>Length 14 pin 16 pin 24 pin 40 pin<br>Single ended DIP (Header Plug) Jumper 24 inches 145p 185p 240p 380p<br>Double ended DIP (Header Plug) Jumper 6 inches 185p 205p 300p 485p<br>12 inches 198p 215p 315p 480p<br>24 inches 210p 235p 345p 540p<br>36 inches 290p 370p 480p 525p<br><b>IDC Female Header Socket Jumper Leads</b> 36" C15W 510p<br>C19W 530p<br>CS17W 525p<br>Spare Bits 85p<br>Elements 230p<br>Iron Stand 175p<br>Heat Shunt 30p | <b>VEROBOARD</b><br>9 1/2" x 9 1/2" 95p<br>2 1/4" x 9 1/2" 110p<br>1 3/4" x 9 1/2" 125p<br>1 1/4" x 1 1/2" 420p<br>4 1/4" x 1 1/2" 590p<br>Pkt of 100 pins 55p<br>Spot/hole cutter 150p<br>Pin insertion tool 185p<br><b>VERO WIRING PEN</b> 340p<br>Spare spool 75p<br>Combs 85p<br><b>FERRIC CHLORIDE</b> 1 lb bag Anhydrous 195p + 50p p&p<br><b>COPPER CLAD BOARDS</b><br>Fibre glass Single-sided Double-sided S.R.B.P. S.Speed<br>6" x 6" 100p 125p 9.5" x 8.5" 110p<br>6" x 12" 175p 225p<br><b>DILL SOCKETS</b><br>Low Wire Prol Wire<br>8 pin 8p 25p<br>14 pin 10p 35p<br>16 pin 10p 42p<br>18 pin 15p 52p<br>20 pin 20p 60p<br>22 pin 22p 65p<br>24 pin 25p 70p<br>28 pin 28p 80p<br>40 pin 30p 90p<br><b>EDGE CONNECTORS</b><br>2x8 way - 111p<br>2x12 way - 160p<br>2x15 way - 165p<br>2x18 way - 210p 175p<br>18 pin 22p 175p<br>2x22 way 215p 250p<br>2x23 way 175p<br>2x25 way 285p 275p<br>2x26 way 190p -<br>2x30 way 310p -<br>2x36 way 360p -<br>2x40 way 390p -<br><b>SIL SOCKET 0.1" Pitch 20 way 65p</b><br><b>ANTEX SOLDERING IRONS</b><br>C15W 510p<br>CS17W 525p<br>C19W 530p<br>XS25W 545p<br>Spare Bits 85p<br>Elements 230p<br>Iron Stand 175p<br>Heat Shunt 30p | <b>PROTO DECS</b><br>Veroblock 480p<br>5-Dimm 395p<br>Euroboardboard<br>Bimbro 1 575p<br>Superstrip 5S2 135p<br><b>DALO ETCH RESIST PEN</b> 100p<br>Plus spare tin   | <b>IDC CONNECTORS</b><br>PCB with Plugs Female Female<br>latch Header Card Card<br>Pms Pins Plug Edge<br>Strt Angle Conct<br>10 way 90p 99p 85p 120p<br>16 way 130p 150p 110p -<br>20 way 145p 166p 125p 195p<br>26 way 175p 200p 150p 240p<br>34 way 205p 236p 180p 320p<br>40 way 220p 250p 190p 340p<br>50 way 235p 270p 200p 395p<br>60 way - 230p 495p<br><b>EURO CONNECTORS</b><br>Gold Flashed Contacts<br>Solder IDC Female Socket Male Plug<br>Strt Strt Strt Strt<br>Angle Angle Angle Angle<br>DIN41617 31 way 170p - - 175p<br>DIN41612 2 x 32 A + B 275p 320p 220p 285p<br>DIN41612 2 x 32 A + C 295p 340p 240p 300p<br>DIN41612 3 x 32 A + B + C 360p 385p 280p 395p<br><b>DIL PLUG (Header)</b><br>Solder IDC 9 15 25 37<br>14 pin 40p 80p<br>16 pin 48p 105p<br>24 pin 88p 178p<br>28 pin 290p 295p<br>40 pin 250p 255p<br><b>RIBBON CABLE</b> price per foot<br>Grey Colour<br>10 way 15p 28p<br>15 way 25p 40p<br>20 way 29p 50p<br>24 way 40p 65p<br>28 way 55p 80p<br>34 way 80p 85p<br>40 way 70p 90p<br>50 way 100p 135p<br>64 way 120p 160p<br>24 pin 565p<br>28 pin 715p<br>40 pin 845p<br><b>'D' CONNECTORS</b><br>Male Solder lugs 80p 105p 160p 250p<br>Angle pins 150p 210p 250p 355p<br>PCB pins 120p 130p 195p 295p<br>Female Solder lugs 105p 160p 200p 335p<br>Angle pins 165p 215p 290p 440p<br>PCB pins 150p 180p 240p 420p<br>COVERS 80p 75p 75p 90p<br>IDC 25 way 'D' Plug 385p, Socket 450p<br><b>25 way 'D' CONNECTOR (RS232)</b><br>Jumper Lead Cable Assembly<br>18" long, Single end, Male 475p<br>18" long, Single end, Female 510p<br>36" long, Double Ended, M/M 995p<br>36" long, Double Ended, F/F 910p<br>36" long, Double Ended, M/F 995p<br><b>AMPHENOL PLUGS</b><br>24 way IEEE 475p<br>36 way Centronix 450p<br>24 way Female 525p<br>IDC Solder 475p<br>450p<br>475p<br>490p | <b>PANEL METERS</b><br>FSD 60 x 46 x 35mm<br>0-50mA<br>0-100mA<br>0-500mA<br>0-1mA<br>0-5mA<br>0-10mA<br>0-50mA<br>0-100mA<br>0-500mA<br>0.2A<br>0.25V<br>0.50V AC<br>0.300V AC<br>"S"<br>"VU" 490p each<br><b>CRYSTALS</b><br>32 768KHz 100<br>100KHz 235<br>200KHz 200<br>455KHz 265<br>1MHz 275<br>1.008MHz 390<br>1.28MHz 275<br>1.6MHz 295<br>1.8MHz 295<br>1.8432M 250<br>2.0MHz 225<br>2.4576M 200<br>3.12MHz 240<br>5.2425MHz 200<br>3.5794M 98<br>3.6864M 300<br>4.0MHz 150<br>4.032MHz 290<br>4.19430M 150<br>4.433619M 200<br>4.608MHz 200<br>4.80MHz 200<br>4.80MHz 200<br>5.0MHz 160<br>5.185MHz 300<br>5.2425MHz 390<br>6.0MHz 150<br>6.144MHz 140<br>6.5538MHz 225<br>7.0MHz 150<br>7.358MHz 250<br>7.7328MHz 250<br>7.68MHz 200<br>8.0MHz 150<br>8.089333M 395<br>8.86723M 220<br>9.00MHz 200<br>10.0MHz 175<br>10.0MHz 175<br>10.24MHz 200<br>10.5MHz 250<br>10.7MHz 150<br>10.7MHz 150<br>12.528M 300<br>14.31814M 170<br>15.0MHz 240<br>16.0MHz 220<br>16.0MHz 160<br>16.0MHz 150<br>19.968MHz 150<br>20.0MHz 200<br>24.0MHz 170<br>24.30MHz 325<br>26.68M 150<br>27.548M 170<br>27.145M 180<br>38.6667M 240<br>48.0MHz 240<br>100.0MHz 295<br>116.3MHz 300<br><b>ASTEC UHF MODULATORS</b><br>Standard 6MHz 325p<br>Wideband 8MHz 450p<br><b>BUZZERS</b><br>miniature, solid state 6V, 9V & 12V 70p<br><b>PIEZOELECTRIC TRANSDUCERS</b> P82720 70p<br><b>LOUDSPEAKERS</b><br>Miniature, 0.3W-8 80p<br>2in, 3/4in, 2 1/2in, 3in 80p<br>2 1/2in 40, 64 or 80 | <b>RELAYS</b><br>Miniature, enclosed, PCB mount<br>SINGLE POLE Changeover<br>RL-91 205R Coil, 12V DC, 110V to 19.5V 10A at 30V DC or 250V AC 195p<br>DOUBLE POLE Changeover, 6A, 30V DC or 250V AC<br>RL-100 53R Coil, 6V DC (5V4 to 9V), 190p<br>RL-111 205R Coil, 12V DC (10V to 19.5V) 195p<br>RL-6 114 740R Coil, 24V DC (22V to 37V) 200p<br><b>BUZZERS</b><br>miniature, solid state 6V, 9V & 12V 70p<br><b>PIEZOELECTRIC TRANSDUCERS</b> P82720 70p<br><b>LOUDSPEAKERS</b><br>Miniature, 0.3W-8 80p<br>2in, 3/4in, 2 1/2in, 3in 80p<br>2 1/2in 40, 64 or 80<br><b>MONITORS</b><br>ZENITH - 12" Green, Hi-Resolution Popular £75<br>MICROVITEC 1431, 14" Colour RGB input. Connecting cable incl £189<br>KAGA 12". Med-res. RGB Colour. Has flicker-free characters. Ideal for BBC, Apple, VIC, etc £199 (car £7)<br>KAGA 12". As above but Hi-Resolution £259 (car £7)<br>Connecting Lead for KAGA £5<br>Carriage £7 Securocar<br><b>BROTHER HR15 PRINTER</b><br>High quality Daisy Wheel Printer, 18CPS, Bidirectional, 3K Buffer, Proportional spacing, Underlining, Bold print and Shadow print. Centronics & RS232 interface standard. Carbon & Fabric ribbon. Red & Black print.<br>Only: £349 |
| <b>TRANSFORMERS</b><br>3.0-3V, 6.0-6V, 9.0-9V, 12.0-12V, 15.0-15V @ 100mA 98p<br>pcb mounting Miniature, Split Bobbin<br>3VA: 2x6V-0.25A, 2x9V-0.15A, 2x12V-0.12A, 2x15V-0.1A 200p<br>6VA: 2x6V-0.5A, 2x9V-0.3A, 2x12V-0.25A, 2x15V-0.2A 270p<br>Standard Split Bobbin type:<br>6VA: 2x6V-0.5A, 2x9V-0.4A, 2x12V-0.3A, 2x15V-0.25A 250p<br>12VA: 2x4.5V-1.3A, 2x5V-1A, 2x9V-0.6A, 2x12V-0.5A, 2x15V-0.4A, 2x20V-0.3A 345p (35p p&p)<br>24VA: 2x6V-1.5A, 2x9V-1.2A, 2x12V-1A, 2x15V-0.8A, 2x20V-0.6A 385p (60p p&p)<br>50VA: 2x6V-4A, 2x9V-2.5A, 2x12V-2A, 2x15V-1.5A, 2x20V-1.2A, 2x25V-1A, 2x30V-0.8A, 2x20V-60p (60p p&p)<br>Specially wound for Multirail computer PSUs<br>50VA: Outputs +5V/5A +12V, +25V -5V, -12V at 1A 620p (60p p&p)<br>100VA: 2x12V-4A, 2x15V-3A, 2x20V-2A, 2x25V-2A, 2x30V-1.5A, 2x50V-1A 965p (75p p&p)<br>P&P charge to be added over and above our normal postal charge | <b>VOLTAGE REGULATORS</b><br>1A TO220 Plastic Casing<br>5V 7805 45p<br>12V 7812 50p<br>15V 7815 45p<br>18V 7818 45p<br>24V 7824 45p<br>7824 45p<br>100mA TO92 Plastic package:<br>5V 78L05 30p<br>6V 78L06 30p<br>8V 78L08 30p<br>12V 78L12 30p<br>15V 78L15 30p<br>ICL7680 248p<br>RC1750 150p<br>RC4195 160p<br>LM309X 135p<br>LM317K 250p<br>LM317KP 250p<br>LM323K 450p<br>LM337 175p<br>LM723 Var 30p<br>7805 45p<br>7808 60p<br>7812 45p<br>7815 45p<br>7818 45p<br>7824 45p<br>7912 50p<br>7915 60p<br>TA5550 50p<br>10A112 150p<br>78H05 + 5V/5V 550p<br>78H12 + 12V/5A 640p<br>78HG + 5V to + 25V 585p<br>79HG - 2.25V 585p<br>-24V, 5A 685p  | <b>SOLDERCON PINS</b><br>Ideal for making SIL or DIL Sockets<br>100 pins 75p<br>500 pins 350p<br><b>ALUM BOXES</b><br>3 x 2 x 1 85p<br>4 x 2 1/2 x 2 100p<br>4 x 2 1/2 x 2 103p<br>4 x 4 x 2 105p<br>4 x 4 x 2 1/2 120p<br>5 x 4 x 1 1/2 99p<br>5 x 4 x 2 1/2 120p<br>5 x 2 1/2 x 1 1/2 90p<br>5 x 2 1/2 x 2 1/2 100p<br>6 x 4 x 2 1/2 120p<br>6 x 4 x 3 150p<br>7 x 5 x 3 180p<br>8 x 6 x 3 210p<br>10 x 4 x 3 240p<br>10 x 7 x 3 275p<br>12 x 5 x 3 280p<br>12 x 8 x 3 295p<br><b>ISOLATORS</b><br>ILO74 115<br>LCD 8 Digits 220<br>TIL1 1/2/4 70<br>ILC76 Darlington 135<br>4N33 Photo Darlington 136   | <b>COMPUTER CORNER</b><br>EPSON RX80 PRINTER: 100 CPS, 9 x 9 matrix, dot addressable graphics, condensed & double width printing, Normal, Italics & Elite Char, Tractor Feed, Bidirectional, Logic seeking ..... £235<br>RX80 F/T Epson Printer. As above but has both Tractor and Friction feed facilities. .... £259<br>EPSON FX80 PRINTER 10" Tractor & Friction Feed, 160 CPS, bidirectional Logic seeking, 9 x 11 matrix, hires bit image, Normal, Italic & Elite Char. Super & Subscript. Proportional spacing. .... £345<br>SEIKOSHA GP100A, 10" Tractor Feed, 80 Colmn, 30CPS, Normal and Double width Char. Dot Res Graphics ..... £144<br>SEIKOSHA GP250X, 10", 50 CPS, Normal and Double width and height Char. RS232 and Centronix intrf. standard. .... £199 (£7 car)<br>Printer Cable for our printers and BBC MICRO. .... £12<br>TEX EPROM ERASER Erases up to 32 ICs in 15-30 minutes. .... £33<br>TEX EPROM ERASER with a safety switch. .... £35<br>SPARE UV Lamp bulb. .... £8<br>C12 COMPUTER GRADE CASSETTES in library cases ..... 40p<br>8 1/2" & 9 1/4" Fan Fold paper (1000 sheets) ..... £7 + 150p carr<br>Call in at our shop for demonstration. Be satisfied before you buy or write in for our descriptive Micro Peripherals Leaflet. | <b>FLOPPY DISC DRIVES 5 1/4"</b><br>(BBC Compatible)<br>CS100 - Single Cased with PSU, 40 Track, 5 1/4" S/S 100K ..... £145<br>CD200 - Twin Cased with PSU, 40 Track, 5 1/4" S/S 200K ..... £275<br>CS200 - Single Cased with PSU, 80 Track, 5 1/4" S/S 200K ..... £210<br>CD400 - Twin Cased with PSU, 80 Track, 5 1/4" S/S 400K ..... £365<br>MITSUBISHI 5 1/4" SLIM LINE DISC DRIVES<br>Double Sided, Double Density Track Density 96 TPI, Track to track access time 3msec.<br>MITSUBISHI Single Slimline, 5 1/4" Cased with PSU D5DD, 1 Megabyte (400 K with BBC) ..... £259<br>MITSUBISHI Twin Slimline, 5 1/4" Cased with PSU OSDD 2 Megabyte (800 K with BBC) ..... £425<br>5 1/4" DISKETTES (Lifetime Warranty)<br>10 3M Diskettes Single side Double Density ..... £17<br>10 3M Diskettes Double side Double density ..... £27<br>N.B Carriage on Drives £7 securocar  | <b>SPECTRUM 32K UPGRADE</b><br>Upgrade your 16K Spectrum to full 48K with our RAM Upgrade Kit. Very simple to fit. Fitting instructions supplied. .... £22<br>BBC SPEECH SYNTHESISER Unit ..... £44<br>BBC EPROM PROGRAMMER ..... £89<br>BBC 13 ROM SOCKET Board ..... £33<br>BEEBROM ROM ..... £39<br>BEEBMON ROM ..... £19<br>BBC DISASSEMBLER ROM ..... £16<br>EPSON DUMP ROM ..... £16<br>DISC-DATA Database on Disc ..... £15  | <b>BBC &amp; MICROCOMPUTER &amp; ACCESSORIES</b><br>Model A ..... £299 Model B £399 (incl VAT)<br>We stock the full range of BBC Micro peripherals, Hardware & Software like, Disc Drives (Top quality Cumana & Mitsubishi), Diskettes, Printers, printer, Paper, Interface Cable, Dust Covers, Cassette Recorder & Cassettes, Monitors, Connectors (Ready made Cables, Plugs & Sockets), Plotter (Graphic Tablet) EPROM Programmer, Lightpen Kit, Joysticks, Sideways ROM Board, EPROM Eraser, Machinecode ROM. The highly sophisticated Watford's 16K BEEB DFS, WORDWISE, BEEB-CALC, Software (Educational Application & Games), BOOKS, etc, etc. Please send SAE for our description leaflet.   |

|             |      |      |      |       |
|-------------|------|------|------|-------|
| <b>CMOS</b> | 4072 | 25   | 4538 | 80    |
| 4000        | 20   | 4073 | 26   | 4539  |
| 4001        | 20   | 4075 | 25   | 4541  |
| 4002        | 22   | 4076 | 68   | 4543  |
| 4006        | 65   | 4078 | 25   | 4548  |
| 4007        | 22   | 4081 | 25   | 4549  |
| 4008        | 48   | 4082 | 25   | 4553  |
| 4009        | 33   | 4086 | 60   | 4554  |
| 4010        | 33   | 4086 | 60   | 4554  |
| 4011        | 22   | 4089 | 125  | 4556  |
| 4012        | 25   | 4093 | 37   | 4557  |
| 4013        | 60   | 4094 | 70   | 4558  |
| 4014        | 60   | 4095 | 95   | 4559  |
| 4015        | 60   | 4096 | 100  | 4560  |
| 4016        | 40   | 4097 | 275  | 4561  |
| 4017        | 60   | 4098 | 80   | 4562  |
| 4018        | 60   | 4099 | 110  | 4566  |
| 4019        | 58   | 4160 | 95   | 4568  |
| 4020        | 90   | 4161 | 96   | 4569  |
| 4022        | 43   | 4162 | 96   | 4572  |
| 4021        | 58   | 4163 | 96   | 4580  |
| 4022        | 67   | 4174 | 96   | 4581  |
| 4023        | 30   | 4175 | 105  | 4582  |
| 4024        | 50   | 4194 | 105  | 4583  |
| 4025        | 22   | 4408 | 850  | 4584  |
| 4026        | 90   | 4409 | 850  | 4585  |
| 4027        | 43   | 4410 | 725  | 4587  |
| 4028        | 45   | 4411 | 750  | 4599  |
| 4029        | 60   | 4412 | 800  | 4608  |
| 4030        | 35   | 4415 | 590  | 4609  |
| 4031        | 130  | 4419 | 280  | 4609B |
| 4032        | 70   | 4422 | 770  | 4610  |
| 4033        | 130  | 4435 | 850  | 4610  |
| 4034        | 146  | 4440 | 900  | 4610  |
| 4035        | 70   | 4450 | 320  | 4610  |
| 4036        | 275  | 4451 | 350  | 4610  |
| 4037        | 115  | 4490 | 450  | 4610  |
| 4038        | 75   | 4500 | 395  | 4610  |
| 4039        | 280  | 4501 | 38   | 4610  |
| 4040        | 60   | 4502 | 60   | 4610  |
| 4041        | 57   | 4503 | 40   | 4610  |
| 4042        | 50   | 4504 | 99   | 4610  |
| 4043        | 42   | 4505 | 385  | 4611  |
| 4044        | 50   | 4506 | 100  | 4611  |
| 4045        | 110  | 4507 | 45   | 4613  |
| 4046        | 60   | 4508 | 130  | 4617  |
| 4047        | 60   | 4510 | 55   | 4617  |
| 4048        | 55   | 4511 | 55   | 4618  |
| 4049        | 38   | 4512 | 55   | 4618  |
| 4050        | 35   | 4513 | 160  | 4619  |
| 4051        | 45   | 4514 | 115  | 4619  |
| 4052        | 60   | 4515 | 115  | 4619  |
| 4053        | 80   | 4516 | 55   | 4619  |
| 4054        | 85   | 4517 | 275  | 4624  |
| 4055        | 85   | 4518 | 48   | 4625  |
| 4056        | 85   | 4519 | 32   | 4625  |
| 4057        | 1000 | 4520 | 53   | 4617  |
| 4058        | 435  | 4521 | 115  | 4637  |
| 4059        | 88   | 4522 | 125  | 4618  |
| 4061        | 500  | 4526 | 60   | 4618  |
| 4062        | 988  | 4527 | 65   | 4618  |
| 4063        | 85   | 4528 | 50   | 4618  |
| 4066        | 45   | 4529 | 150  | 4637  |
| 4067        | 245  | 4530 | 90   | 4637  |
| 4068        | 25   | 4531 | 30   | 4637  |
| 4069        | 25   | 4532 | 65   | 4637  |
| 4070        | 25   | 4534 | 400  | 4637  |
| 4071        | 25   | 4536 | 275  | 4637  |

|                         |                 |            |    |
|-------------------------|-----------------|------------|----|
| <b>OPTO ELECTRONICS</b> | LEDs with clips | TIL209     | 10 |
|                         | LEDs with clips | TIL212 GRN | 14 |

**NEXT  
MONTH**

AN ARGUS SPECIALIST PUBLICATION


# **electronics today**

**INTERNATIONAL**
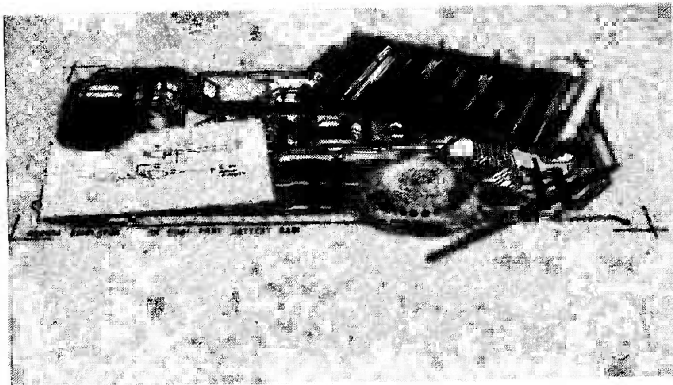
## **Accept an Imitation!**

Next month we shall be asking all our readers to accept an imitation — not for ETI, because we know that would never satisfy you — but for the common-or-garden EPROM. The project concerned is an EPROM emulator, and it is designed to work using a very large variety of host computers.

The idea of an EPROM emulator is that you should plug it into a system (which could be any sort of digital circuit, not just a microcomputer) in the place of an EPROM; to the circuit, the system 'looks like' an EPROM; however, the emulator is linked to a host computer, and this can be used to modify the emulator contents, with the minimum of fuss. Once you've got the data you want in the emulator, all you do next is to program this into your EPROM using the ETI EPROM programmer — couldn't be simpler, could it?



## **Communications Satellites**

The first communications satellite — Telstar — was successfully launched over 20 years ago. There was, at the time, a popular 'hit', record by the Tornadoes, named after Telstar! Nowadays, satellite communications seem more mundane — do many people realise that, sometimes, when they dial a foreign number, their call will be going through space? Next month we'll be taking a look at the technology involved in satellite communications.

## **MOSFET Power Amplifier**

As you will see on page 24, John Linsley Hood has commenced his description of the 'Audio Design' amplifier system with the preamp section. Next month it will be the turn of the power amplifier . . . can the Editor's neighbours possibly wait until then?

## **Security**

The July issue of ETI has been designated a 'Security Special', and this means that there will be features and projects aimed at helping you make your house or flat — and car — more protected from unwelcome attention. We hope to arrange a couple of rather good readers' offers, but details of these are still under negotiation as we go to press.

**ALL IN THE JULY ISSUE OF ETI —  
ON SALE FRIDAY JUNE 1st.  
PLACE YOUR ORDER NOW  
OR RISK MISSING OUT!**





# Rapid Electronics

**MAIL ORDERS:**  
Unit 1, Hill Farm Industrial Estate,  
Boxted, Colchester, Essex CO4 5RD.  
Tel. Orders: Colchester (0206) 36412.  
Telex: 987756.



**ACCESS AND  
BARCLAYCARD  
WELCOME**

### MIN. D CONNECTORS

|                   |        |        |        |
|-------------------|--------|--------|--------|
| 9 way             | 15 way | 25 way | 37 way |
| Plugs solder lugs | 60p    | 85p    | 170p   |
| Right angle       | 120p   | 180p   | 350p   |
| Sockets lugs      | 90p    | 130p   | 195p   |
| Right angle       | 160p   | 210p   | 290p   |
| Covers            | 100p   | 90p    | 110p   |



### SOLDERING IRONS

|                              |     |
|------------------------------|-----|
| Antex GS 17W Soldering iron  | 495 |
| 2.3 and 4.7mm bits to suit   | 85  |
| CS 17Wor XS 25W element      | 210 |
| Antex XS 25W                 | 525 |
| 3.3 and 4.7mm bits to suit   | 85  |
| Solder pump desoldering tool | 480 |
| Spare nozzle for above       | 70  |
| 10 metres 22sw solder        | 100 |

### CONNECTORS

|              |                      |
|--------------|----------------------|
| DIN Plug Skt | Jack Plug Skt        |
| 2 pin 9p     | 2.5mm 10p 10p        |
| 3 pin 12p    | 10p 3.5mm 9p 9p      |
| 5 pin 13p    | 11p Standard 16p 20p |
| Phone 10p    | 12p Stereo 24p 25p   |
| 1mm 12p      | 13p 4mm 18p 17p      |

### SCRs

|          |    |
|----------|----|
| C106D    | 30 |
| 400V 8A  | 70 |
| 400V 12A | 95 |

### VERO

|                           |       |     |
|---------------------------|-------|-----|
| Verobloc                  | 4     | 375 |
| Veroboard Size 0.1 matrix |       |     |
| 2.5 x 1                   | 22    |     |
| 2.5 x 3.75                | 75    |     |
| 2.5 x 5                   | 85    |     |
| 3.75 x 5                  | 95    |     |
| New size 3.75 x 17        | 330   |     |
| New size 4.75 x 17        | 415   |     |
| VQ board                  | 160   |     |
| Veropins per 100:         |       |     |
| Single sided              | 50    |     |
| Double sided              | 60    |     |
| Spot face cutter          | 130   |     |
| Pin insertion tool        | 162   |     |
| Wiring pen                | 330   |     |
| Spare spool 75p           | Combs | 6   |

### VOICE SYNTHESISER

Now your computer can talk. The GI SPO256 speech processor is able through stored program to synthesize speech. Allophone (extended phoneme) system gives unlimited vocabulary. Easily interfaced with any digital system; ten TTL compatible signals are used to select the allo-phones. SPO256 850p. Data: 50p.

### MICRO

|           |      |          |     |          |     |
|-----------|------|----------|-----|----------|-----|
| 6116P3    | 600  | 6852     | 240 | 8228     | 220 |
| 6502CPU   | 325  | 6875     | 495 | 8251     | 250 |
| 6522 VIA  | 295  | 6880     | 100 | 8253     | 390 |
| 6532      | 570  | 81L595   | 85  | 8255     | 225 |
| 6551 ACIA | 650  | 81L596   | 85  | 8259     | 390 |
| 2114L2    | 200  | 6800CPU  | 220 | 81LS97   | 85  |
| 2176      | 295  | 6802CPU  | 250 | 8080A    | 250 |
| 2532      | 290  | 6803CPU  | 620 | 8085AC   | 340 |
| 27128-25  | 2150 | 6810RAM  | 115 | 8156     | 350 |
| 2732      | 350  | 8521 PIA | 110 | 8212     | 110 |
| 2782      | 250  | 6840     | 360 | 280ASCTC | 260 |
| 4116P20   | 85   | 6850     | 110 | 8224     | 120 |

### SWITCHES

Submin toggle: SPST 55p. SPDT 60p. DPDT 65p. Miniature toggle: SPDT 80p. SPDT centre off 90p. DPDT 90p. DPDT centre off 100p. Standard toggle: SPST 35p. DPDT 48p. Miniature DPDT slide 14p. Push to make 14p. Push to break 22p. Rotary type adjustable stop. 1P12W, 2P2W, 3P4W all 55p each. D.I.L. switches: 4SPST 80p. 5SPST 80p. 8SPST 100p.

### SOCKETS

| Low profile | Wire wrap |
|-------------|-----------|
| 8 pin       | 6p        |
| 14 pin      | 8p        |
| 16 pin      | 9p        |
| 18 pin      | 12p       |
| 20 pin      | 13p       |
| 22 pin      | 15p       |
| 24 pin      | 18p       |
| 28 pin      | 23p       |
| 40 pin      | 25p       |

### COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. 5W 5% Resistor kit. Contains 10 of each value from 4.7 ohms to 1M (total of 650 resistors) 530 Ceramic Cap. kit. 5 of each value - 22p to 0.01uF (135 caps) 370 Polyester Cap. kit. 5 of each value from 0.01 to 1uF (65 caps) 575 Preset kit. Contains 5 of each value from 100 ohms to 1M (total 65 presets) 425 Nut and Bolt kit (total 300 items): 180p 25 6BA 1/4" bolts 50 6BA washers 50 6BA nuts 25 4BA 1/4" bolts 50 6BA washers 25 6BA 1/4" bolts

### LINEAR

|               |              |            |              |               |             |
|---------------|--------------|------------|--------------|---------------|-------------|
| 555CMOS 80    | ICL7106 680  | LM339 40   | LM3911 120   | NE566 140     | TL064 96    |
| 556CMOS 150   | ICL7811 95   | LM348 60   | LM3914 225   | NE567 100     | TL071 30    |
| 709 25        | ICL7821 180  | LM358 50   | LM3915 225   | NE570 370     | TL072 45    |
| *741 14       | ICL7822 180  | LM377 170  | LM13600 105  | NE571 370     | TL074 95    |
| 748 35        | ICL8038 295  | LM380 75   | MC1496 68    | PC936 55      | TL081 25    |
| 9400CJ 350    | ICL8111A 200 | LM382 120  | MC3340 135   | RC4558 40     | TL082 45    |
| AY-3-1270 70  | ICM224 785   | LM384 130  | MF10CN 350   | SL480 250     | TL170 50    |
| AY-3-8912 540 | LF351 85     | LM386 90   | ML922 420    | SL76018 150   | UA2240 120  |
| CA3046 60     | LF353 85     | LM387 120  | ML925 210    | SN76477 380   | ULN2003 70  |
| CA3080 65     | LF356 90     | LM393 40   | ML926 140    | SPO256-L2 850 | ULN2004 70  |
| CA3089 190    | LM101 325    | LM709 25   | ML927 140    | TBA1205 70    | XR2206 290  |
| CA3090AQ 375  | LM101A 750   | LM725 80   | ML928 140    | TBA414 70     |             |
| CA3130E 85    | LM311 70     | LM725 80   | ML929 140    | TBA810 96     | ZN423 135   |
| CA3140E 36    | LM318 120    | LM733 75   | MMS5397A 465 | TBA820 70     | ZN424 135   |
| CA3161E 100   | LM324 30     | LM741 14   | NE529 225    | TBA950 220    | ZN425E 350  |
| CA3189 290    | LM334Z 100   | LM747 60   | NE631 140    | TD1008 320    | ZN429E 300  |
| CA3240E 100   | LM335Z 125   | LM1458 40  | NE644 205    | TD1022 690    | ZN4275 600  |
|               |              | LM2917 200 | NE555 16     | TD1024 125    | ZN428E 410  |
|               |              | LM3900 45  | NE555 45     | TL061 40      | ZN459 285   |
|               |              | LM3909 75  | NE565 110    | TL062 60      | ZN1034E 200 |

### TRANSISTORS

|          |         |         |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |          |
|----------|---------|---------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|
| AC126 30 | BC149 9 | BC517 9 | BC549 10 | BC558 10 | BC570 18 | BC571 18 | BC572 18 | BC578 25 | BC101 35 | BC103 35 | BC104 35 | BC105 35 | BC106 35 | BC107 35 | BC108 35 | BC109 35 | BC110 35 | BC111 35 | BC112 35 | BC113 35 | BC114 35 | BC115 35 | BC116 35 | BC117 35 | BC118 35 | BC119 35 | BC120 35 | BC121 35 | BC122 35 | BC123 35 | BC124 35 | BC125 35 | BC126 35 | BC127 35 | BC128 35 | BC129 35 | BC130 35 | BC131 35 | BC132 35 | BC133 35 | BC134 35 | BC135 35 | BC136 35 | BC137 35 | BC138 35 | BC139 35 | BC140 35 | BC141 35 | BC142 35 | BC143 35 | BC144 35 | BC145 35 | BC146 35 | BC147 35 | BC148 35 | BC149 35 | BC150 35 |
|----------|---------|---------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|----------|

### CABLES

|  |         |
|--|---------|
| 20 metre pack single core connecting cable ten different colours | 75p     |
| Speaker cable  | 10p/m   |
| Standard screened  | 16p/m   |
| Twin screened  | 24p/m   |
| 2.5A 3 core mains  | 23p/m   |
| 10 way rainbow ribbon  | 26p/ft  |
| 20 way rainbow ribbon  | 47p/ft  |
| 10 way grey ribbon   | 147p/ft |
| 20 way grey ribbon   | 28p/ft  |

### HARDWARE

|                               |     |
|-------------------------------|-----|
| PP3 battery clips             | 6   |
| Red or black crocodile clips  | 6   |
| Black pointer contact knob    | 150 |
| Pr Ultrasonic transducers     | 390 |
| 6V Electronic buzzer          | 60  |
| 12V Electronic buzzer         | 65  |
| PB270 Piezo transducer        | 75  |
| 64mm 64 ohm speaker           | 70  |
| 64mm 8 ohm speaker            | 70  |
| 20mm panel fuseholder         | 25  |
| Red or black probe clip       | 35  |
| 4mm terminals                 | 33  |
| 12 way 'chocolate' block      | 30  |
| ultra-min. 6 or 12v rel. SPDT | 130 |
| ditto, but DPDT               | 195 |

### CAPACITORS

|  |
|--|
| Polyester, radial leads, 250v. C280 type: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 20, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 2200, 3300, 4700, 6800, 10000, 22000, 33000, 47000, 68000, 100000, 220000, 330000, 470000, 680000, 1000000, 2200000, 3300000, 4700000, 6800000, 10000000, 22000000, 33000000, 47000000, 68000000, 100000000, 220000000, 330000000, 470000000, 680000000, 1000000000, 2200000000, 3300000000, 4700000000, 6800000000, 10000000000, 22000000000, 33000000000, 47000000000, 68000000000, 100000000000, 220000000000, 330000000000, 470000000000, 680000000000, 1000000000000, 2200000000000, 3300000000000, 4700000000000, 6800000000000, 10000000000000, 22000000000000, 33000000000000, 47000000000000, 68000000000000, 100000000000000, 220000000000000, 330000000000000, 470000000000000, 680000000000000, 1000000000000000, 2200000000000000, 3300000000000000, 4700000000000000, 6800000000000000, 10000000000000000, 22000000000000000, 33000000000000000, 47000000000000000, 68000000000000000, 100000000000000000, 220000000000000000, 330000000000000000, 470000000000000000, 680000000000000000, 1000000000000000000, 2200000000000000000, 3300000000000000000, 4700000000000000000, 6800000000000000000, 10000000000000000000, 22000000000000000000, 33000000000000000000, 47000000000000000000, 68000000000000000000, 100000000000000000000, 220000000000000000000, 330000000000000000000, 470000000000000000000, 680000000000000000000, 1000000000000000000000, 2200000000000000000000, 3300000000000000000000, 4700000000000000000000, 6800000000000000000000, 10000000000000000000000, 22000000000000000000000, 33000000000000000000000, 47000000000000000000000, 68000000000000000000000, 100000000000000000000000, 220000000000000000000000, 330000000000000000000000, 470000000000000000000000, 680000000000000000000000, 1000000000000000000000000, 2200000000000000000000000, 3300000000000000000000000, 4700000000000000000000000, 6800000000000000000000000, 10000000000000000000000000, 22000000000000000000000000, 33000000000000000000000000, 47000000000000000000000000, 68000000000000000000000000, 100000000000000000000000000, 220000000000000000000000000, 330000000000000000000000000, 470000000000000000000000000, 680000000000000000000000000, 1000000000000000000000000000, 2200000000000000000000000000, 3300000000000000000000000000, 4700000000000000000000000000, 6800000000000000000000000000, 10000000000000000000000000000, 22000000000000000000000000000, 33000000000000000000000000000, 47000000000000000000000000000, 68000000000000000000000000000, 100000000000000000000000000000, 220000000000000000000000000000, 330000000000000000000000000000, 470000000000000000000000000000, 680000000000000000000000000000, 1000000000000000000000000000000, 2200000000000000000000000000000, 3300000000000000000000000000000, 4700000000000000000000000000000, 6800000000000000000000000000000, 10000000000000000000000000000000, 22000000000000000000000000000000, 33000000000000000000000000000000, 47000000000000000000000000000000, 68000000000000000000000000000000, 100000000000000000000000000000000, 220000000000000000000000000000000, 330000000000000000000000000000000, 470000000000000000000000000000000, 680000000000000000000000000000000, 1000000000000000000000000000000000, 2200000000000000000000000000000000, 3300000000000000000000000000000000, 4700000000000000000000000000000000, 6800000000000000000000000000000000, 10000000000000000000000000000000000, 22000000000000000000000000000000000, 33000000000000000000000000000000000, 47000000000000000000000000000000000, 68000000000000000000000000000000000, 100000000000000000000000000000000000, 220000000000000000000000000000000000, 330000000000000000000000000000000000, 470000000000000000000000000000000000, 680000000000000000000000000000000000, 1000000000000000000000000000000000000, 2200000000000000000000000000000000000, 3300000000000000000000000000000000000, 4700000000000000000000000000000000000, 6800000000000000000000000000000000000, 10000000000000000000000000000000000000, 22000000000000000000000000000000000000, 33000000000000000000000000000000000000, 47000000000000000000000000000000000000, 68000000000000000000000000000000000000, 100000000000000000000000000000000000000, 220000000000000000000000000000000000000, 330000000000000000000000000000000000000, 470000000000000000000000000000000000000, 680000000000000000000000000000000000000, 1000000000000000000000000000000000000000, 2200000000000000000000000000000000000000, 3300000000000000000000000000000000000000, 4700000000000000000000000000000000000000, 6800000000000000000000000000000000000000, 100, 22000000000000000000000000000000000000000, 33000000000000000000000000000000000000000, 47000000000000000000000000000000000000000, 6800000000 |
|--|




# DIGEST

## Speakers Corner

Compact loudspeakers are not, on the whole, noted for their extended bass response, and many owners of such systems must have sought ways to overcome this deficiency without going to the expense and trouble of purchasing larger loudspeakers. One solution is to add a single sub-bass unit, the idea being that, since very little directional information is carried at low frequencies, a single unit can handle the bass from both channels of a stereo system without serious loss of stereo imaging. The drawback with this approach is that a bass driver in a reasonably large cabinet is likely to be far more sensitive than the main loudspeakers, small systems being notoriously inefficient, resulting in a very poor balance across the frequency range. The only sure way to restore the balance is to use an active crossover and a second amplifier, thus greatly increasing the cost and complexity of the system.

With this problem in mind, Volt loudspeakers have introduced two new drive units whose sen-

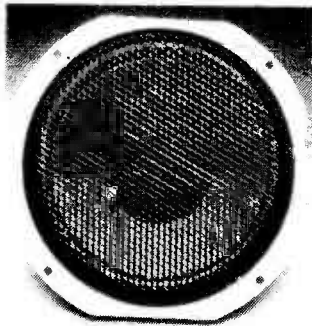sitivity is tailored to match that of such popular small 'speaker systems as the LS3/5a (which sounds like a long-winded way of saying that they are not very sensitive), and which have dual voice coils so that the amplifier outputs can be combined using only simple crossover networks. The 8" DVC220DS is designed to be




mounted directly into a wall or into a conventional loudspeaker enclosure. The 10" DVC250 offers a more extended bass response and is designed to be mounted in a conventional enclosure only, and both types can be supplied with or without fitted grilles. They are available from Wilmslow Audio, who can also supply computer optimised tuning details to suit your chosen cabinet volume.

Also available from Wilmslow are three new additions to the Wharfedale Speakercraft range of designs for the home constructor. They are the L50, L90B and L140 models, two way systems of 11, 17 and 20 litres respectively, all featuring the ferrofluid T/02/2 3/4" tweeter. They are all of 8 ohms




impedance, a change from the 6 ohms which has long been Wharfedale's standard for small 'speakers, and the full Speakercraft manual is available free-of-charge from Wilmslow.

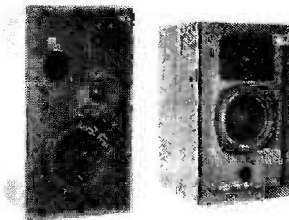Other recent additions to the range of products stocked by Wilmslow Audio are six new Loudspeaker kits and a novel high power, high efficiency PA loudspeaker, both using drive units manufactured by Peerless of Denmark. Wilmslow have been appointed UK distributors for Peerless, and the new kits employ four



polypropylene bass units which have not previously been available to the home constructor, a 5" a 6 1/2", an 8" and a 10". Full details of the new range, two of which are said to have been designed specifically for use in digital audio systems, are contained in the Peerless Manual For Loudspeaker Constructors which is available from Wilmslow, and a review of one of the new models appears elsewhere in this issue.

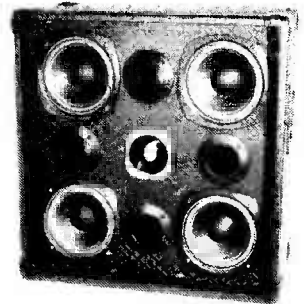The new PA loudspeaker uses four high power 8" drive units and a bullet tweeter in an unusual




reflex configuration, and will handle 250 watts RMS with, it is claimed, high quality and very high efficiency. Suggested applications are folk bands, overhead disco 'speakers and side fill on large PA rigs, and it can be purchased as a kit with or without cabinet. For details of any of the items listed, send a 12" x 9" SAE to Wilmslow Audio Ltd, 35-39 Church Street, Wilmslow, Cheshire, tel 0625 - 529599.


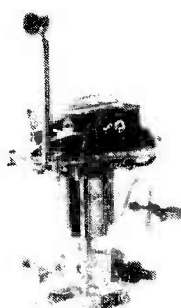
## Movits

Prism Consumer Products has launched a range of kit form electronic robots which they call Movits. There are five models in the range of varying complexity and with progressively more sophisticated guidance and sensory systems. They are all battery powered, making them safe for use by children, and Prism say the assembly instructions are so comprehensive that the whole family can take part in the construction. They cost from £9.99 to £34.99 and further information can be obtained from Prism Technology Holdings Ltd, Prism House, 18-29 Mora Street, City Road, London EC1V 8BT, tel 01-253 2277.



## World's Smallest Lithium Battery

Matsushita have developed what they claim is the smallest pin-type lithium battery in the world. Designated the BR211, the new battery is rated at 3V, 5.4 mAh, measures 2.2 mm diameter by 11 mm high and weighs just 90 mg.

The BR211 has a poly-carbon monofluoride cathode and a lithium anode, and is specified for use over the temperature range -10 C to +60 C. Matsushita say that the advantages of using a lithium battery are that it maintains a constant operating voltage

when loaded, has a long shelf life and offers twice the voltage of silver-oxide and mercury cells, allowing a single battery to be used to light an LED. The new battery will initially be marketed for use in small fishing floats which have LEDs for night-time fishing, but Matsushita expect it to be widely adopted for use in wrist watches, calculators, microphones, hearing aids, etc.

Panasonic UK Limited, 300-318 Bath Road, Slough, Berkshire SL1 6JB, tel 0753-34522.







## See Hear

For reasons best known to themselves, Pioneer have decided that it is not enough for loudspeakers just to occupy space and annoy the neighbours. They want them to do useful things too. Why else would they attach a section of bathmat to front of their Decor'speakers and



advertise them as bulletin boards?

Pioneer claim that the new loudspeakers are practical and attractive home accessories. They are available with either a cork facia for use as bulletin boards or with a glass panel behind which photos, etc, can be mounted. There is a lot in the press release about changing attitudes to home entertainment and narrowing the gap between home accessories

and home entertainment, but precious little about how the new units perform as loudspeakers. All we are told is that they have a 140mm woofer, a 66 mm cone tweeter and can handle 60 watts music power. They cost £159.90 and should be in the shops by the time this issue appears.

Also new from Pioneer is a modular loudspeaker system called Adlib. Each 'speaker consists of three separate units which can be stacked on top of one another, side by side, or dispersed around the room to your taste. One unit contains a 66 mm tweeter and a

100 mm mid-range unit while the other two boxes contain rectangular, flat-diaphragm bass drivers. The crossover is contained in one of the two bass cabinets and further wiring carries the signal from it to the other two units. The cases come in a choice of silver or black finish and have an alternately raised and recessed surface pattern which is both decorative and allows them to interlock when stacked. The S-7MS (silver) and S-7MB (black) cost £289.90 and again, should be in the shops by the time this issue appears.

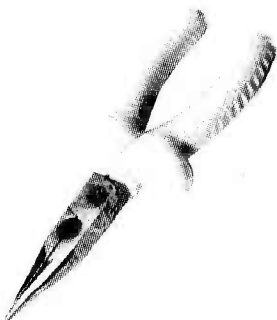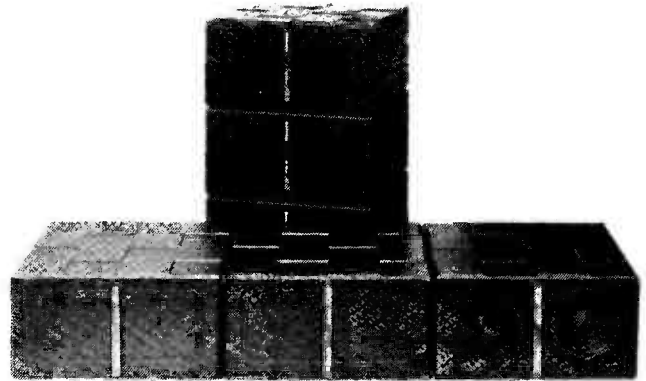

## EHT-Insulated Tools

Toolrange have introduced a small range of handtools with double sheathing which provide electrical insulation up to 10,000 volts. The double sheath is bonded to the tool so that it cannot be removed in normal use, and the insulation and bonding properties remain constant over the temperature range -20 C to +60 C. Toolrange do not specify the tools available with this insulation and they point out that the range is limited, but they also say that virtually any tool can be double sheathed if required, presumably to special order. The 10,000 volt insulated tools are described in the 1983/84 Toolrange catalogue, along with over 3,000 other tools and production aids. Toolrange Ltd, Upton Road, Reading, Berkshire RG3 4JA, tel 0734-22245.

## Gallium Arsenide ICs

Harris Microwave Semiconductor claim to have produced the world's first commercially available digital integrated circuits based on gallium arsenide (GaAs) technology. They will operate at up to five times the processing speed of the fastest silicon-based integrated circuits available today.

The new products are the first of a comprehensive family of GaAs integrated circuits being developed by Harris. They claim that the speed limitations of silicon in high-frequency communications equipment and very-high-speed computer systems are now being reached, and that

the availability of GaAs-based equivalents opens up important new performance horizons.

Harris produces GaAs crystal material in-house to ensure the control of quality and technical performance. The company recently brought on-line the world's largest high-purity gallium arsenide ingot-growing capacity, which is producing single-crystal GaAs ingots up to five inches in diameter and 10 kgm in weight.

The first two devices in Harris' new family of GaAs digital integrated circuits are the HMD-11141-1, a four-bit universal shift register, and the HMD-11016-1, a divide-by 2/4/8 binary counter. A key design principle of this new Harris family is that all circuits are compatible in their signal levels, not only within the family but with the fastest available ECL silicon

devices. This will allow access to slower speed circuitry for the less speed-critical portions of a system's processing task.

The GaAs shift register performs the standard operations of shift left, shift right, parallel outputs and hold, accepting either serial or parallel inputs. It operates with clock inputs of 1.4 GHz typical, and 1.0 GHz minimum. Silicon-based ECL products with similar functions operate at under 500 MHz. The GaAs binary counter provides simultaneous synchronous outputs at 1/2, 1/4 and 1/8 the data rate input, working with clock speeds of 2.2 GHz typical.

For further information contact Ralph Kaplan, Harris-MHS Semiconductor, 153 Farnham Road, Slough, Berkshire SL1 4XD, tel 0753 34666.

- The South Warwickshire College of Further Education is running a series of adult summer school courses from the 23rd to the 27th of April, including one entitled 'Hobby Electronics'. The course assumes no previous knowledge but promises advanced projects for the more adventurous, materials and tools provided, and the cost is £75. Details from Graham Winton, South Warwickshire College of Further Education, The Willows North, Alcester Road, Stratford-upon-Avon CV37 9QR, tel 0789-66245.

- Business Information company Dun and Bradstreet Ltd tell us that 189 electrical companies went into liquidation in the first quarter of this year, four more than in the previous quarter but 4% less than in the same quarter last year. There were 28 bankruptcies among firms, partnerships and individuals in the industry, 1 less than in the previous quarter but 9 more than in the same quarter last year.

- The University of Strathclyde are running a four-day course

entitled "The Principles of Optical Systems" from the 19th to the 22nd June this year. The course is aimed at technical managers, engineers and recent graduates who plan to carry out research in this field, and the cost will be £445 less £50 for those who do not wish to take part in the laboratory work. Details from Katrina Flack, Department of Electronic & Electrical Engineering, University of Strathclyde, Royal College building, 204 George Street, Glasgow G1 1XW, tel 041-552 4400 extension 2543.



# COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

## HARD DISK DRIVES

Fully refurbished DIABLO/DRE series 30 2.5 Mb disk drives.  
**DEC RK05, NOVA, TEXAS** compatible.  
 Front load Free stand or rack mount **£590.00**  
 Exchangeable type (via lid removal) **£295.00**  
 me3029 PSU unit for 2 drives **£125.00**  
**DIABLO/DRE 44-4000A/B 5+5** ex stock from **£995.00**  
 1000's of spares for S30, 4000, 3200, HAWK ex stock.  
 Plus in house repair, refurbishing service.  
 Call for details or quotation.

## HOT LINE DATA BASE

# DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base  
 1000's of stock items and one off bargains.  
**ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit word, no parity.**  
**01-679 1888**

## COMPUTER 'GAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling.  
 Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man.  
**Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high.**  
 Useable area 16" w. 10.5" h. 11.5" d.  
 Also available **LESS PSU**, with FANS etc. Internal dim. 19" w. 16" d. 10.5" h. **£19.95** Carriage & insurance £9.50.

## EX STOCK INTEGRATED CIRCUITS

**D8085AH-2 D8086 D8257-5**  
**D8202 D8271 AM2764-3DC**  
**74LS86 74LS112 74LS373**  
**7407 2102-6 4116-3**  
**CALL SALES OFFICE FOR PRICES**

## MAINS FILTERS

Cure those unnering hang ups and data glitches caused by mains interference.  
 SD5A As recommended by ZX81 news letter matchbox size up to 1000 watt load **£5.95**  
 L2127 compact completely cased unit with 3 pin fitted socket Up to 750 watts **£9.99**

## COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.  
**ETRI 89XUOI** Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. **£9.95**  
**GOULD JB-3AR** Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £6.95**  
**BUHLER 89.11.22.8-16** v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost **£32.00. OUR PRICE ONLY £12.95 complete with data.**  
**MUFFIN-CENTAUR** standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at **£6.25** or 110 v at **£4.95** or BRAND NEW 240 v at **£10.50**. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans **£1.60**

SAVE £250

## SUPER PRINTER SCOOP

### BRAND NEW CENTRONICS 739-2



The "Do Everything Printer" at a price that will NEVER be repeated. Standard CENTRONICS parallel interface for direct connection to BBC, ORIC, DRAGON etc. Superb print quality with full pin addressable graphics and 4 type fonts plus HIGH DEFINITION internal PROPORTIONAL SPACED MODE for WORD PROCESSOR applications. 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available ONLY from DISPLAY ELECTRONICS at the ridiculous price of **ONLY £199.00 + VAT** Complete with full manual etc. Limited quantity - Hurry while stocks last.  
 Options: Interface cable (specify) for BBC, ORIC, DRAGON or CENTRONICS 36 way plg **£12.50**. Spare ribbon **£3.00** each. BBC graphics screen dump utility program **£8.50**. Carriage and Ins. **£10.00 + VAT**

ONLY £199

## VIDEO MONITORS

**5" CASED** Superb little unit made by HITACHI in ergonomically designed free standing case. Very high definition will display small but readable 132 columns wide 12v DC opp. @ 800 ma. so ideal for mobile use. Supplied in AS NEW condition complete with data. Composite 75 ohm vid inp. Black & White CRT **£45.00** or Green CRT **£55.00** Carr & Ins **£5.00**  
**12" CASED**. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as, internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although ungaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**  
**24" CASED**. Again made by the KGM Co with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs shops etc. Supplied in a used but working condition.  
**ONLY £55.00 PLUS £9.50 CARR & INS.**

## EPROM COPIERS

The amazing SOFTY 2. The 'Complete Toolkit' for writing, copying, modifying, and listing EPROMS of the 2516, 2716, 2532, 2732 range. Many other functions include integral keyboard, cassette interface, serial and parallel I/O, UHF modulator.  
**ONLY £189.00 + PP £2.50**  
**NEW 'GANG OF EIGHT'** intelligent Z80 controlled gang bang programmer for all 2716 single V rail EPROMS. Copies up to 8, 27128 in typ. **ONLY 2 MINUTES!** Internal LCD display and checking routines for IDIOT PROOF operation. **ONLY £395.00 + PP £3.00**. Data sheets on request.

## GE TERMIPRINTER

A massive purchase of these desk top printer terminals enables us to offer you these quality 30 cps printers at a SUPER LOW PRICE against their original cost of over £1000. Unit comprises of full QWERTY, electronic keyboard and printer mech with print face similar to correspondence quality typewriter. Variable forms tractor unit enables full width - up to 13.5" 120 column paper, upper - lower case, standard RS232 serial interface, internal vertical and horizontal tab settings, standard ribbon, adjustable baud rates, quiet operation plus many other features. Supplied complete with manual. Guaranteed working **£130.00** or untested **£85.00**, optional floor stand **£12.50** Carr & Ins **£10.00**.

## TELETYPE ASR33 I/O TERMINALS

Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order.  
 Options: Floor stand **£12.50 + VAT**  
 KSR33 with 20ma loop interface **£125.00 + VAT**  
 Sound proof enclosure **£25.00 + VAT**

## PROFESSIONAL KEYBOARD OFFER

An advantageous purchase of brand new surplus allows a great QWERTY, full travel, chassis keyboard offer at fractions of their original costs.  
**ALPHAMERIC 7204/80** full ASCII 60 key, upper, lower + control key, parallel TTL output plus strobe. Dim 12" x 6" x 4.5" - 12 DC. **£39.50**  
**DEC LA34** Unencoded keyboard with 87 quality, GOLD, normally open switches on standard X.Y matrix. Complete with 3 LED indicators & i/o cable - ideal micro conversions etc. pcb DIM 15" x 4.5" **£24.95** Carriage on keyboards **£3.00**

## COLOUR MONITORS

**NOVEX NC-1414-CL** Fully cased brand new 14" colour monitor. Many exciting features such as RGB TTL and PAL composite video inputs, internal speaker and audio amp. "GREEN TEXT" switch for high def text applications and matching BBC colour scheme make this monitor ideal for the most exciting user. Brand new and Fully Guaranteed only **£199.00 + £10.00 carr.**

## DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.  
**MODEM 2B "Hackers Special"** fully fledged up to 300 baud full duplex, ANSWER or CALL modes. AUTO ANSWER. Data i/o via standard RS232 25 way 'D' socket. Just 2 wire connection to comms line. Ideal networks etc. Complete with data, tested, ready to run at a **NEW SUPER LOW PRICE of ONLY £65.00 + VAT + Carr**  
**MODEM 20-1** Compact unit for use with MICRONET, PRESTEL or TELECOM GOLD etc. 2 wire direct connect. 75 baud transmit 1200 baud receive. Data i/o via RS232 'D' socket. Guaranteed working with data. **£99.95**  
**MODEM 20-2** Same as 20-1 but 75 baud receive. 1200 baud transmit. **£130.00**  
**TRANSDATA 307A** 300 baud acoustic coupler RS232 i/o **£95.00**  
**NEW DSL2123 Multi** Standard modem selectable V21 300-300 bps, V23 75-1200, V23 1200-75 full duplex. Or 1200-1200 half duplex modes. Full auto answer via modem or CPU. LED status indicators. CALL or ANSWER modes. Switchable CCITT or BELL 103 & 202. Housed in ABS case size only 10.5" x 8.5" x 9". **£286.00 + VAT**  
 For further data or details on other EX STOCK modems contact sales office  
 Carriage on all modems **£10.00 + VAT**.

## SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter BRAND NEW AT ONLY **£499 + VAT**

Made to the very highest spec the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUEME command compatibility and full control via CPM Wordstar etc. Many other features include bi-directional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information.  
 Optional extras: RS232 data cable **£10.00**. Tech manual **£7.50**. Tractor feed **£140.00**. Spare daisy wheel **£3.00**. Carriage & Ins. (UK Mainland) **£10.00**.

Save over **£400**  
 a fraction of its original cost.

## 66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of IC's, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the 'BARGAIN PARCEL OF A LIFETIME'. Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.  
 2.5kls **£4.25 + pp £1.25**      5kls **£5.90 + £1.80**  
 10kls **£10.25 + pp £2.25**      20 kls **£17.50 + £4.75**

## ALL PRICES PLUS VAT

## SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s, triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed, 50+ **£2.95** 100+ **£5.15**.  
**TTL 74 Series** A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ **£6.90** 200+ **£12.30** 300+ **£19.30**

## DEC CORNER


**MOSTEK CRT 80E** Brand new dual emulocard, Z80 based VT100 PLUS emulator with graphics etc **£499.00**  
**BA11-MB 3.5"** Box, PSU, LTC **£385.00**  
**DLV11-J 4 x EIA** interface **£310.00**  
**RK05-J 2.5 Mb** disk drives **£450.00**  
**PDP1105 Cpu, Ram, i/o, etc.** **£70.00**  
**RT11 ver. 3B** doc kit **£270.00**  
**LA34A** Decwriter EIA or 20 ma **£175.00**  
**MIB6 PDP 8** asynch i/o **£175.00**  
**DILOG DQ100 RK05 LSI 4 x RK05** disk controller **£450.00**  
**MSC480A** (Equip MSV11-L) 256k bytes ram card **£499.00**  
**LAX34-AL LA34** tractor feed 1000's of EX STOCK spares for DEC PDP8 PDP11 PDP15 & peripherals. Call for details. All types of Computer equipment and spares wanted for prompt CASH PAYMENT **£85.00**

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**. Minimum Credit Card order **£10.00**. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies **£20.00**. Where post and packing not indicated please ADD **£1.00**. + VAT Warehouse open Mon-Fri 9.30 - 5.30 Sat 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.
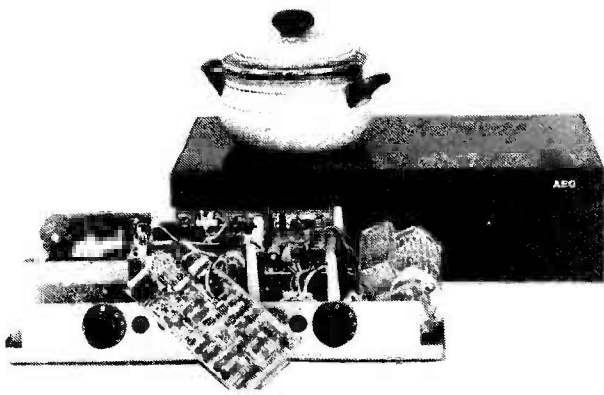
# DISPLAY ELECTRONICS

32 Biggin Way, Upper Norwood, London SE19 3XF  
 Telephone 01-679 4414 Telex 27924





## Induction Cooking

**T**raditional methods of cooking involve either an electrically heated 'hotplate' or a gas ring upon which the vessel containing the food to be heated is placed. A more recent innovation is the microwave cooker, in which there is no heated surface or area and heating takes place only in the food itself as a result of molecular vibrations set up by microwave activity. A third method, induction heating of the cooking pan, is shortly due to join the existing methods and promises to combine many of their individual advantages.

Inductive heating of metallic


surfaces has been used in some industries for over fifty years, but it is only now that the supporting technology exists to allow its use in the home. The principle is quite simple: the cooking pan is placed on an electrically and magnetically non-conductive plate underneath which is an induction coil. The coil generates an electromagnetic field in the base of the pan, thus causing it to heat up. There are a number of distinct advantages in this approach. The 'hotplate' itself remains virtually cold, receiving heat only by conduction from the bottom of the pan, and thus poses no danger of burning. Similarly, liquids spilled from the pan during cooking will not burn on contact with the cooking surface. The cooking time is considerably reduced

compared with traditional hotplates, and since there is no heat accumulation in the hotplate itself and the induction energy can be precisely controlled, the cooking process can be regulated quickly and easily. A pan of milk which is on the verge of boiling can be saved from boiling over by switching off at the right moment.

Several manufacturers already have induction cookers in their catalogues, but the cost is fairly high and this is probably why they are not selling in large quantities. With this in mind, AEG-Telefunken have developed a twin-hotplate table top induction cooker which they hope to have ready for volume production in a couple of years time and which should sell for rather less than currently available models. The AEG-Telefunken design will use an induction coil in a parallel tuned circuit fed at a constant frequency by an inverter, the current being controlled to provide regulation of the energy output. Most of the existing designs use a series tuned circuit and regulate power by adjusting the inverter frequency, an approach which leads to losses when the tuned circuit is not at resonance and which provides a limited range of control since the frequency range is limited by the switching properties of the semiconductors at the top

end and the onset of audibility at the bottom end. AEG say the optimum frequency for use with thin sheet steel pans is 10kHz but they use a frequency above 25kHz which is beyond the audible range for both humans and domestic animals. They extend the range of control available by pulsing the supply to the coil when very low outputs are required and claim infinitely variable control down to about 2% of maximum output. The two hotplates in the cooker have maximum power consumptions of 1500W and 2000W and AEG claim that around 75% of the energy taken from the mains actually reaches the food being cooked, compared with about 60% for a ceramic hotplate and 58% for an iron hotplate.

The induction method is suitable for cooking, frying, heating-up and thawing, and combines some of the advantages of speed and electrical efficiency found in microwave cookers with the versatility and constant access during cooking enjoyed with conventional hotplates. AEG say that there are still a few problems to be overcome and that more development is needed, but now that the major problems such as radio interference have largely been overcome, it should not be too long before the benefits of this method of cooking can be made more widely available.

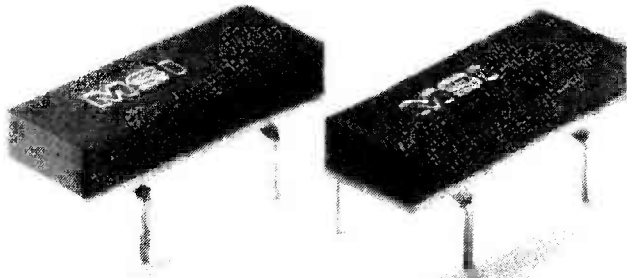

## Miniature Solid-State Relays

**N**orbain Electro-Optics Ltd have launched a completely new range of Switch-DIP miniature solid state relays. Manufactured by MSI, the range consists of three DC and seven AC types covering a number of voltage and current options with opto or transformer isolation and synchronous or zero voltage switching.

Housed in standard 14 and 16 pin sealed ceramic DIL packages, the devices employ thick film hybrid techniques to achieve a high power handling capability. Heading the range is the E24E-2H 16

pin package which has a 1A RMS rating and input-to-output isolation of 400V RMS. The device switches at the zero voltage point of the AC wave form, requires an input signal of 8mA at 5V and has a peak voltage rating on the output switch of 600V. Anti-parallel SCRs in the power switch ensure enhanced DV/DT surge current and thermal characteristics.

Other devices in the range include the E40-1 capable of switching AC and DC currents to  $\pm 80\text{mA}$  at  $\pm 60\text{V}$ , the E41-2H rated at 1A RMS AC with a triac output rated at 600V, the E43-1 designed for DC switching a current of 500mA at 60V and E43-2 designed for 200mA current switching at 250VDC. Norbain Electro-optics Limited, Norbain House, Boulton Road, Reading, Berkshire RG2 0LT, tel: 0734 864411.

## Triac With Integral Firing Circuit

**U**nited Automation have produced an 18mm x 16mm hybrid thick film which contains a 240VAC 6, 10 or 15 amp glass passivated triac together with a complete firing circuit integrated within a 3 terminal isolated package. A family of derivatives include a control potentiometer (open or enclosed) allowing single hole fixing and 2 wire connection, and extension to 35 Amps with 300 Amp surge capacity. Larger units up to 300 Amps with surge ratings to 3,000 Amps are also available to order.

Applications include control of heaters, ovens, furnaces, large lamp loads and many AC motors, giving potential energy savings and wide control ability to almost any function or process that is electrically powered. UA claim the cost of the device is lower than that of an equivalent triac and discrete firing circuit. Contact United Automation Sales/Publicity Dept, 17 King Street, Knutsford, Cheshire WA16 6DW, tel 0565 54863.

- The British Amateur Electronics Club have issued their April Newsletter which contains the usual range of features and articles plus details of the Amateur Electronics Exhibition which takes place in Penarth, South Glamorgan in July. Details from C. Bogod, "Dickens", 26 Forest Road, Penarth, South Glamorgan CF6 2DP.

- Axiom Electronics Ltd have published a quick reference guide and price list covering their range of components, tools and instruments. The guide has almost 200 pages, lists more than 10,000 product lines and is available free from Axiom at Turnpike Road, Cressex Industrial Estate, High Wycombe, Buckinghamshire HP12 3NR, tel 0494 - 442181.



**pantechnic**

## THE ULTIMATE PREAMP HAS TONE CONTROLS

OK, so your system is perfect. Cartridge and loudspeakers are perfectly integrated with the room acoustics. Tone controls are an irrelevancy, and anyway just having them worsens the noise and distortion of the system.

But . . . what if after tiring of your direct cut audiophile discs you choose to listen to one of those less than ideal recordings where the middle positively snarls at you. Or . . . you're having a party and all those extra bodies just soak up the top and the speakers, pushed back against the wall, boom away.

What if there were tone controls that were essentially quiet and imperceptible in operation and could be switched, individually out of circuit when not required. What if they were part of a stereo preamp board that has the lowest noise and distortion figures you could buy, superb overload capability due to its active/passive gain control, tape monitor facilities and on board PSU.

The PAN30 with the new topology tone control circuit could change the facias of hifi.

**PAN30** Stereo preamp board — **£43.25**

### PFA 250 Assembly

Mono power amp and 10,000 uF storage capacitors pre-wired and mounted on a gold chromate heatsink (67 mm x 250mm). 200 Watts into 8 ohms, 300 Watts into 4 ohms, plus headroom. Powerful and very, very clean. — **£58.75**

Full info. on receipt of a large SAE. OEM enquiries, contact Phil Rimmer on 01-361 8716.

## THE POWERFET SPECIALISTS **pantechnic**

Dept ET1/5, 132 High Road, New Southgate  
London N11 1 PG  
Tel: 01-361 8715/6

## SPEECH SYNTHESIZER

KIT **£17.95**  
BUILT **£19.95**

- ★ Suitable for SPECTRUM and ZX81
- ★ Easy to use and program with full documentation supplied
- ★ Allophone system gives unlimited vocabulary
- ★ Volume control for internal speaker

Talking clock program on cassette (Spectrum only) has many spoken alarm calls **£2.50**

## JOYSTICK INTERFACE

KIT **£7.95**  
BUILT **£9.95**

- ★ Used with Kempston compatible software for Spectrum
- ★ Uses any Atari type compatible joystick controller

These kits are suitable for beginners in both electronics and computing. They contain detailed instructions and ALL parts including drilled case. A small soldering iron & wire cutters are all that's required. No extra leads or power supply are needed.

SPO256 Speech Synthesizer IC available separately at **£8.00**

Send Cheque or P.O. to:

**BELVEDERE ELECTRONICS**  
15 Belvedere Mount, Leeds LS11 7ED  
Tel: (0532) 707600

All Prices Include VAT But Please Add £1.00 For P & P.

COMING SOON: 16 channel I/O for controlling Robots,  
FOR SPECTRUM: Motors, Lights etc.  
8 bit DAC/ADC with 8 multiplexed inputs.  
2716/2732 EPROM programmer and ROM board.

## Component

# MINI FILE

**For**  
Electronic and other small parts. A large variety of components can easily be kept well organized. 60 storage pockets per unit.

### Unit size:

L400 W125 H77mm.

**Material:** Injection-moulded in impact resistant polystyrene.

4 and 6 Drawer Steel cabinets available.

The 6 Drawer cabinet, practical for field service, has lock and carrying handle.

Recommended prices (excluding V.A.T.):

|                                       |        |
|---------------------------------------|--------|
| 6 drawer cabinet with lock and handle | £92.00 |
| 4 drawer cabinet with lock and handle | £59.00 |
| Single drawer.                        | £11.00 |


### Typical Minifile applications:

R & D Departments    Prototype Kits  
Production Test & Rework Service Departments  
Field Service Engineers    The Electronic Hobbyist  
Repair kits for computers    CNC- machines.
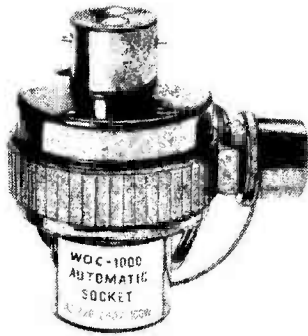
### Stocked by:

Bradley Marshall, 325 Edgware Road, London W2 1BN Tel: 01-723 4242  
Enfield Electronics, 208 Baker Street, Enfield, Middlesex EN1 3JY. Tel: 01-366 1873  
Henry's, 404-406 Edgware Road, London W2. Tel: 01-724 0323  
TK Electronics, 11-13 Boston Road, London W7 3SJ. Tel: 01-579 9794  
Watford Electronics, 33/34 Cardiff Road, Watford, Herts. Tel: (0923) 40588.





## Night Light

As we pointed out in our Automatic Light Switch project last month, a simple way of deterring would-be burglars when the house is empty is to arrange for the lights to come on at dusk, thus giving the impression that someone is at home. Our project allows you to do just that. CSR International have now introduced a similar device, and if it isn't quite as sophisticated as our design it is certainly a lot easier to fit.


The TSAS Auto Socket is a light activated switch built into a small moulded housing which has a bayonet plug on one side and a bayonet socket on the other. The bayonet plug is inserted into a standard lamp socket, a light bulb of up to 60 watts is placed in the socket on the other side of the device, the supply is switched on and the Auto Socket then does the rest. A Cd-S cell senses the ambient light level, switching the bulb on when it gets dark and off again when it gets light. Just how they avoid the problem of reflected light from the bulb getting back to the Cd-S cell is not made clear, but we suspect this may be why they recommend a 60 watt bulb when the unit appears to have a rating of 100 watts (see illustration). The manufacturers say the case is fully weather-protected and that the device can be used with both indoor and outdoor light fittings.

CSR International are promoting the Auto Socket as a burglar deterrent, but an obvious drawback is that it will leave the lights on all night, perhaps attracting more attention than if the house were left in darkness. The design we published last month switched the lights on at dusk but off again four hours later, thus avoiding the problem. The Auto Socket would seem to be better suited for use with porch or path lights or any other light that you actually want to leave on all night. It costs £15.00 inclusive and is available by mail order from CSR International, Suite 26, Fourth Floor, Morley House, 320 Regent Street, London W1R 5AF, tel 01-636 8444.
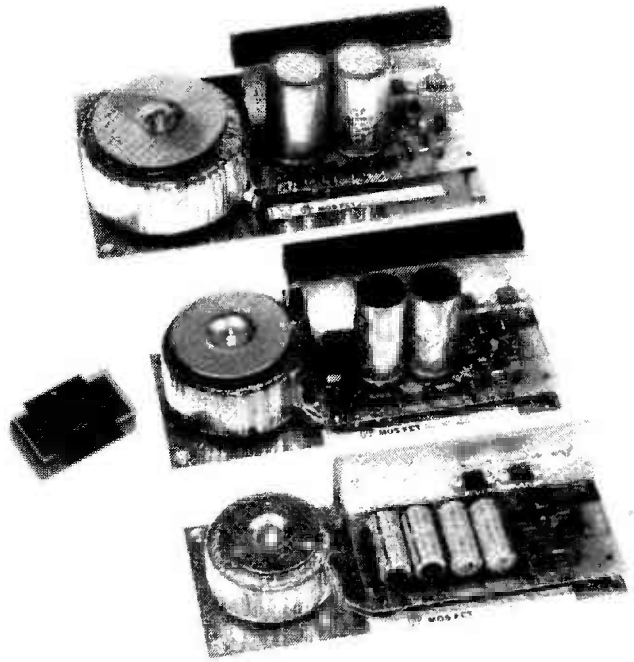
## MOS-FET Amplifier Modules

Following on from their successful 100 watt bipolar power amplifier module, B.K. Electronics have introduced three new MOS-FET models. The OMP/MF100, OMP/MF200 and OMP/MF300 have power ratings of 100, 200 and 300 watts RMS respectively, come complete with power supply and feature an optional eleven segment LED VU meter.


The modules are completely self-contained, having a toroidal transformer, smoothing capacitors and heatsink all built onto the aluminium chassis. Specifications include a typical THD figure of 0.001% rising to 0.002% at full output, a signal-to-noise ratio of 125dB and a slew rate of 45V/us. The output impedance is 4 ohms and the input sensitivity is 500 mV, although models with a 775 mV input sensitivity can be supplied. The bandwidth is 1Hz to 100 kHz but models with a reduced upper frequency limit can be supplied to order. All models run from 240VAC mains, feature a glass fibre printed circuit board and have drive circuits to power the optional eleven segment LED VU meter. The OMP/MF100 measures 60 x 123 x 300 mm, the



OMP/MF200 measures 100 x 150 x 300 mm and the OMP/MF300 measures 102 x 147 x 330 mm.

B.K. Electronics expect the new modules to find applications in the instrumental, PA, disco, hi-fi, DIY and studio and leisure industries. They are currently developing a pre-amplifier to complement the modules and also plan to offer stereopairs in 19" racks with facilities to bridge the outputs. The modules are available direct from B.K. and, for the benefit of those in a real hurry, Barclaycard,

Access and COD orders can be placed over the telephone. The OMP/MF100 costs £34.79 plus VAT and £2.50 postage and packing, the OMP/MF200 costs £54.80 plus VAT and £3.50 postage and packing, and the OMP/MF300 costs £69.59 plus VAT and £4.50 postage and packing. The LED VU meter is available separately and costs £7.39 plus VAT and 50p postage and packing. B.K. Electronics, Unit 5, comet Way, Southend-on-Sea, Essex SS2 6TR, tel 0702-527572.

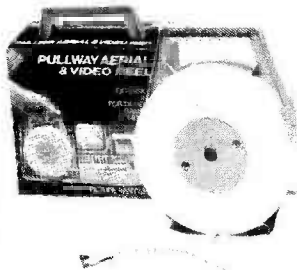

## A Reel-y Good Idea

The Pullaway Reeler is simply a length of TV aerial lead in a handy cable drum. It was designed principally for use with video recorders, to allow a portable TV to be operated in another room without moving the video recorder around, but is also likely to be of interest to home computer users, boating and caravaning enthusiasts and anyone else who wants to operate a TV set at a distance from the aerial or signal source.

The Reeler is available in two

versions, having 30 or 45 feet of standard 75 ohm co-axial cable terminated in a free plug at one end and a socket mounted on the side of the drum at the other. The drum is made of tough ABS plastic and has an integral handle. The Reeler is available from Currys, W.H. Smiths, Sainsburys Homebase and Saracentres and costs around £7.95 including VAT.

Pullway Ltd, Venn House, 11 Clayton Road, Hayes, Middlesex, tel 01-848 7747.

- Bulgin now offer plugs and sockets moulded directly onto lengths of cable. The range includes standard 13A plugs with or without insulated pins and IEC plugs and sockets in both straight and right-angle versions, all moulded to either 2, 2.5 or 3 metres of black cable. Single ended or double ended moulded leads are available, allowing you to choose, for example, a 13A plug to IEC socket lead. Contact Brian Diggle, A.F. Bulgin and Company PLC, Bypass Road, Barking, Essex IG11 0AZ, tel 01-594 5588.

- VSO (Voluntary Service Overseas) is looking for electronics technicians to work in Africa, Asia and the Pacific Islands. The work involves repair of various types of electrical equipment and the period of service is for two years, starting in September. Applicants should hold a craft certificate, have at least five years experience, be aged between 20 and 65 and have a UK, EEC or Commonwealth passport and no dependents. Details from the Enquiries Unit, VSO, 9 Belgrave Square, London SW1, tel 01-235 5191.

- The Anglia Components Group have launched a subsidiary company, Anglia Consumer, which will supply semiconductors to the consumer market. The new company will have full access to the parent company's on-line ICL computer system and claims an order turnaround time of 15 minutes. A semiconductor wall-chart will be sent free to customers, and those interested should contact Anglia Components, Burdett Road, Wisbech, Cambridgeshire PE13 2PS.

ETI

**BBC Micro Computer System**

**OFFICIAL DEALER**

Please phone for availability



Software from ACORNSOFT/  
PROGRAM POWER/GEMINI in  
stock

BBC Model B £348  
B + Econet £389  
B + DFS £429  
B + DFS + Econet £470  
Carriage £7

Model A to Model B  
Upgrade Kit £95  
Installation £15

**LANGUAGE ROMs**  
BCPL ROM + Disc +  
Manual £87

**UTILITY ROMs**  
BBC Ultracalc £65 Toolkit £20  
EXMON £20; DISC DOCTOR  
£30; FX Dump £15; Graphics  
ROM £28; Termi ROM £29

**FLOPPY DISC INTERFACE**

£84 + £15 installation

**BBC COMPATIBLE DISC DRIVES**

All drives are supplied with manual, form disc and cables.

Single Drive: 100k £140; 200k £175\*;  
400K £195

Single Drive with PSU: 100k £165; 200k £210;  
400k £225

Dual Drive with PSU: 2 x 100k £320

2 x 200k £400\*; 2 x 400k £420

\* These drives are switchable between 40/80 tracks. 40/80 Switch Module 1 x 400k and 2 x 400k Drive £32

**DISKETTES:** in packs of 10 W: Wabash M: 3M 40 track SSSD W: £14 M: £16.00; 40 track DSDD M: £22;

80 track SSDD W: £24 M: £26; 80 track DSDD W: £26 M: £30;

**FLOPPICLENE** Drive Head Cleaning Kit £14.50

**Phone or send for our BBC leaflet**

**TORCH Z80 DISC PACK**

Your BBC computer can be converted into a business machine with the additional TORCH Z80 disc pack. The Torch pack with twin disc drive and the Z80 processor card greatly enhances the computer's data storage and processing capabilities. £90 card comes complete with 64K RAM and a CP/M compatible operating system. In addition to BBC owner's user guide and a systems disc the package is supplied with PERFECT software package comprising of DATABASE, WORD PROCESSOR & SPREADSHEET and COMANEX a interactive business management game. Complete Package for £730 + £8 carr.

**CASSETTE RECORDERS**


SANYO DR101 Data Recorder £34 +  
£2.50 carriage  
DATEX SLIM LINE £24 + £1.50 carriage  
BBC Tape Recorder £28.50 + £2.50 carriage  
Cassette Lead £3 + £1 carriage  
HOBBIT Floppy Tape £135 + £2.50 carriage  
HOBBIT Zero Memory Option £25 + £1 carriage  
Computer Grade C12 cassette 50p each.  
£4.50 for 10 + £1 carriage

**MONITORS**

MICROVITEC 1431P 14" RGB/PAL Std Res £249  
MICROVITEC 1451 14" RGB Med Res £299  
MICROVITEC 1441 14" RGB Hi Res £420  
MICROVITEC 2031 20" RGB Std Res £287  
KAGA VISION 12" RGB Std Res £230  
KAGA VISION II 12" RGB Hi Res £260  
KAGA VISION III 12" RGB Super Hi Res £358  
KAGA 12" GREEN Hi Res £106  
SANYO DM812CX 12" Green Hi Res £99  
All leads included. Carriage £7

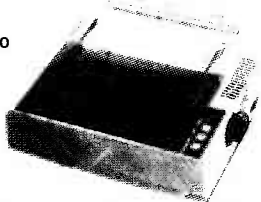**PRINTERS & PLOTTERS**

EPSON FX80 £350  
EPSON RX80 FT £250  
EPSON FX-100 £450  
PRINTER SHARER + cable set £88.00  
SEIKOSHA GP 100A £160  
JUKI 6100 Daisy Wheel £350  
MCP 40 Col Printer/Plotter £120  
Colour Graphics Plotter A3 size £270  
GRAFPAD Graphics Tablet £125  
Carriage £7



**ACCESSORIES**

Parallel Printer Lead £10 + £1 carriage  
Serial Printer Lead £8 + £1 carriage  
Epson Serial Interface 2K £60 + £1 carriage  
Epson Serial Interface £55 + £1 carriage  
NEC Serial Interface £42 + £1.50 carriage  
Epson Paper Roll Holder £17 + £1.50 carriage  
FX Tractor Attachment £37 + £1.50 carriage  
Printer Sharer Parallel 3 Computers - 1 Printer  
£65.00 + £1.50  
Paper Fanfold 2000 sheets £13.50 +  
£2.50 carriage

**'TIME-WARP'**

**BBC REAL-TIME-CLOCK/CALENDAR:**

A low cost unit opens up the total range of Real-Time applications. With its full battery backup, possibilities include an Electronic Diary, automatic document dating, precise timing & control in scientific applications, recreational use in games etc - its uses are endless and are simply limited by one's imagination. Simply plugs into the user port - no specialist installation required - No ROMS. Supplied with extensive applications software. £29.00

**BBC EPROM PROGRAMMER**

A fully self-contained Eprom Programmer with its own power supply, able to program 2516, 2716/32/32A/64/128 single rail Eproms.  
★ Personality selection is simplified by a single rotary switch.  
★ Programming voltage selector switch is provided with a safe position.  
★ Warning indicator to show programming in progress.  
★ Programmer can read, blank check, program and verify at any address/addresses on the EPROM.  
★ Simple menu driven software supplied on cassette (transferable to disc).  
★ Full editor with ASCII disassembler.  
Programmer complete with cables, software and operating instructions. £89.00 - £2 p. & p.

**BOOKS (no VAT; p&p £1)**

Advanced User Guide (£2 p&p) ..... £12.95  
Assembly Lang Prog. for BBC ..... £8.95  
Assembly Lang programming on BBC  
Micro by Ferguson and Shaw ..... £7.95  
Basic Prog. for BBC ..... £5.95  
BBC An Expert Guide ..... £6.95  
Easy Programming on BBC ..... £5.95  
Further Programming on BBC ..... £5.95  
Introducing BBC Micro ..... £5.95  
Programming the BBC ..... £6.50  
30 Hour Basic ..... £5.95  
35 Educational Programs ..... £6.95  
BBC Sound & Graphics ..... £7.95  
Creating Adventure Programs ..... £6.95  
Discovering Machine Code ..... £6.95  
Structured Programming ..... £6.50  
The Friendly Computer Book BBC ..... £4.50  
Beyond Basic BBC ..... £7.25

Many more books in stock.

**EPROM ERASERS**

UV1T Eraser with a built-in timer and mains indicator. Built-in safety interlock to avoid accidental exposure to the harmful UV rays. It can handle up to 5 eproms at a time with an average erasing time of about 20 mins. £59 + £2 p&p.  
UV1 as above but without the timer £47 + £2 p&p.  
UV140 up to 14 Eproms £61  
UV141 as above but with timer £79

★★ ATTENTION ★★

All prices in this double page spread are subject to change without notice.

**PRODUCTION PROGRAM: P8000**

P8000 provides reliable gang programming of up to 8 EPROMS simultaneously with device sizes up to 16k x 8 bytes. Devices supported range from 2704 to 27128 in single and three rail versions. Simple menu driven operation ensure easy eprom selection and reliable programming in minimum programming times. £695 + £6 carriage.

**ACORN IEEE INTERFACE**

This IEEE 488 standard interface is a general purpose system for exchanging digital data between a number of devices in a local area. The interface complies with the IEC 625-1 standard and can be connected to upto 14 other devices.  
Interface board is supplied complete with software in ROM, interconnecting cables IEEE cable for connection to an external device and a comprehensive manual. £282.50 + £2.50 carr.

**SMARTMOUTH.**

Speech Synthesiser for BBC

The 'infinite vocabulary' self-contained speech synthesiser unit. Uses only 5-10 bytes per word - no ROMs required - simply plugs into the user port. (Has Aux. Audio output skt.). Supplied with Demo/Development programs and simple software instructions. £37 + £2 p. & p.

**NEW COMPREHENSIVE CATALOGUE AVAILABLE - PLEASE SEND FOR PRICE LIST**

**CONNECTOR SYSTEMS**

**I.D. CONNECTORS**

(Speedlock Type)

| No of ways | Header Plug | Receptacle | Edge Conn |
|------------|-------------|------------|-----------|
| 10         | 90p         | 85p        | 120p      |
| 20         | 145p        | 125p       | 195p      |
| 26         | 175p        | 150p       | 240p      |
| 34         | 200p        | 160p       | 320p      |
| 40         | 220p        | 190p       | 340p      |
| 50         | 235p        | 200p       | 390p      |

**D CONNECTORS**

No. of ways

|                 | 9    | 15     | 25   | 37   |
|-----------------|------|--------|------|------|
| MALE Solder     | 80p  | 105p   | 160p | 250p |
| Angled          | 150p | 210p   | 250p | 365p |
| FEMALE          |      |        |      |      |
| Solder          | 105p | 160p   | 200p | 335p |
| Angled          | 165p | 215p   | 290p | 440p |
| Hoods           | 90p  | 85p    | 90p  | 100p |
| IDC 25-way plug | 385p | Socket | 450p |      |

**TEXTUOL ZIF**

SOCKETS 24 pin £5.75

28 pin £8.00 40 pin £9.75

**DIL SWITCHES**

4-way 70p 8-way 130p

6-way 100p 10-way 150p

**JUMPER LEADS**

24" Ribbon Cable with Headers

|        | 14 pin | 16 pin | 24 pin | 40 pin |
|--------|--------|--------|--------|--------|
| 1 end  | 145p   | 165p   | 240p   | 350p   |
| 2 ends | 210p   | 230p   | 345p   | 540p   |

24" Ribbon Cable with Sockets

|        | 20 pin | 26 pin | 34 pin | 40 pin |
|--------|--------|--------|--------|--------|
| 1 end  | 160p   | 200p   | 280p   | 300p   |
| 2 ends | 290p   | 370p   | 480p   | 525p   |

Ribbon Cable with D Conn

25 way Male: 500p Female: 550p

**RS 232 JUMPERS**

(25 way D)

|                      |        |
|----------------------|--------|
| 24 Single end Male   | £5.60  |
| 24 Single end Female | £5.25  |
| 24 Female-Female     | £10.00 |
| 24 Male-Male         | £9.50  |
| 24 Male-Female       | £9.50  |

**DIL HEADERS**

Solder Type IDC Type

|       |      |      |
|-------|------|------|
| 14pin | 40p  | 100p |
| 16pin | 50p  | 110p |
| 24pin | 100p | 150p |
| 40pin | 200p | 225p |

**AMPHENOL CONNECTORS**

36-way plug Centronics Parallel

Solder £5.25 IDC £5.25

36-way socket Centronics Parallel

Solder £5.50 IDC £5.50

24-way plug IEEE Solder £5 IDC £4.75

24-way socket IEEE Solder £5 IDC £4.75

PCB Mtg Skt

Any Pin 24 way Solder 600p

36 way ZOC 650p

**RIBBON CABLE**

(Grey/meter)

|        |      |
|--------|------|
| 10 way | 40p  |
| 16 way | 60p  |
| 20 way | 85p  |
| 26 way | 120p |
| 34 way | 160p |
| 40 way | 180p |
| 50 way | 200p |
| 64 way | 280p |

**EURO CONNECTORS**

DIN 41612

2 x 32 way St Pin 230p 275p

2 x 32 way Ang Pin 275p 320p

3 x 32 way St Pin 260p 300p

3 x 32 way Ang Pin 375p 400p

1 DC Skt A+B 275p

A+C 350p

For 2 x 32 way please specify spacing (A+B, A+C)

**EDGE CONNECTORS**

0.1" 0.156"

|                     |      |      |
|---------------------|------|------|
| 2x6-way (commodore) | —    | 300p |
| 2x10-way            | 150  | —    |
| 2x12-way (vic 20)   | —    | 350p |
| 2x18-way            | —    | 140p |
| 2x23-way (ZX81)     | 175p | 220p |
| 2x25-way            | 225p | 220p |
| 2x28-way (Spectrum) | 200p | —    |
| 2x36-way            | 250p | —    |
| 1x43-way            | 260p | —    |
| 2x22-way            | 190p | —    |
| 2x43-way            | 395p | —    |
| 1x77-way            | 400p | 500p |
| 2x50-way (S100conn) | 600p | —    |

**TEST CLIPS**

14-pin 375p 16-pin £4

40-pin £10.30

74 SERIES

Table listing electronic components under the 74 series, including various logic gates, flip-flops, and timing devices with their respective part numbers and prices.

74LS SERIES

Table listing electronic components under the 74LS series, including low-power Schottky logic devices with their respective part numbers and prices.

4000 CMOS

Table listing electronic components under the 4000 CMOS series, including CMOS logic devices with their respective part numbers and prices.

LINEAR ICs

Table listing linear integrated circuits such as operational amplifiers, comparators, and voltage regulators with their respective part numbers and prices.

VOLTAGE REGULATORS

Table listing various voltage regulators, including fixed and adjustable types, with their respective part numbers and prices.

OTHER REGULATORS

Table listing other types of voltage regulators and related components with their respective part numbers and prices.

OPTO ELECTRONICS

Table listing optoelectronic components such as LEDs, phototransistors, and optoisolators with their respective part numbers and prices.

OPTO-ISOLATORS

Table listing optoisolators with their respective part numbers and prices.

DISPLAYS

Table listing various display devices such as LEDs and liquid crystal displays with their respective part numbers and prices.

DRIVERS

Table listing driver components used for controlling displays and other devices with their respective part numbers and prices.

DIL SWITCHES

Table listing dual in-line package (DIP) switches with their respective part numbers and prices.

COMPUTER COMPONENTS

CPUs

Table listing central processing units (CPUs) from various manufacturers with their respective part numbers and prices.

MEMORIES

Table listing memory modules and chips with their respective part numbers and prices.

SUPPORT DEVICES

Table listing support devices such as buffers, decoders, and timing devices with their respective part numbers and prices.

DIODES

Table listing various types of diodes with their respective part numbers and prices.

BRIDGE RECTIFIERS

Table listing bridge rectifier components with their respective part numbers and prices.

COUNTERS

Table listing digital counters with their respective part numbers and prices.

REAL TIME CLOCK

Table listing real-time clock components with their respective part numbers and prices.

TELETEXT DECODER

Table listing teletext decoder components with their respective part numbers and prices.

CAT CONTROLLER

Table listing CAT controller components with their respective part numbers and prices.

INTERFACE ICs

Table listing interface integrated circuits with their respective part numbers and prices.

PROMs

Table listing programmable read-only memory (PROM) devices with their respective part numbers and prices.

DISC CONTROLLER ICs

Table listing disc controller integrated circuits with their respective part numbers and prices.

KEYBOARD ENCODERS

Table listing keyboard encoder components with their respective part numbers and prices.

CHARACTER GENERATORS

Table listing character generator components with their respective part numbers and prices.

TRANSISTORS

Table listing various types of transistors with their respective part numbers and prices.

BAUD RATE GENERATORS

Table listing baud rate generator components with their respective part numbers and prices.

UARTs

Table listing universal asynchronous receiver/transmitter (UART) components with their respective part numbers and prices.

MODULATORS

Table listing modulator components with their respective part numbers and prices.

CRYSTALS

Table listing crystal oscillators with their respective part numbers and prices.

TRIACS

Table listing triac components with their respective part numbers and prices.

PCB MOUNTING RELAYS

Table listing PCB mounting relays with their respective part numbers and prices.

ZENERS

Table listing Zener diodes with their respective part numbers and prices.

TECHNOMATIC LTD. MAIL ORDERS TO: 17 BURNLEY ROAD, LONDON NW10 1ED. SHOPS AT: 17 BURNLEY ROAD, LONDON NW10. (Tel: 01-452 1500, 01-450 6597, Telex: 922800) 305 EDGWARE ROAD, LONDON W2. PLEASE ADD 40p p&p & 15% VAT (Export: no VAT, p&p at Cost). Orders from Government Depts. & Colleges etc. welcome. Detailed Price List on request. Stock items are normally by return of post.



# B. BAMBER ELECTRONICS

|  |       |
|--|-------|
| Marconi Modulation Meter Type TF 2301A                                   | £330  |
| Marconi RMS AC/DC Voltmeter Type TF 2607                                 | £185  |
| Marconi RF Power Meter Type OA 7024/4                                    | £195  |
| Marconi UHF Attenuator Type TF2168                                       | £100  |
| Wavetek LF Generator Type 155  | £380  |
| Solartron DVM Type 14202   | £65   |
| Hewlett Packard Power Supply 0-40v @ 30amp. Type 6268B                   | £450  |
| Schomandl Modulator Type MAF BN B41962                                   | £650  |
| Schomandl Synthesizer Type ND 100 M                                      | £1200 |
| Rohde & Schwarz Decade Signal Generator 0.3 - 500 Mhz Type SMDV BN 41104 | £1200 |
| Rohde & Schwarz Sweep Signal Generator 50Khz - 12Mhz Type BN4242/2       | £75   |
| Rohde & Schwarz Power Signal Generator 0.1 - 30Mhz Type BN41001          | £125  |
| Rohde & Schwarz Frequency Indicator Type BN47051                         | £50   |
| Rohde & Schwarz Group Delay Measuring Equipment Indicator                | £50   |
| Marconi AM Signal Generator 10 - 500Mhz Type TF 801B                     | £125  |
| Marconi AM Signal Generator 10 - 310Mhz Type TF 801A/1                   | £85   |
| Marconi Standard Signal Generator 15Khz - 440Mhz Type TF867              | £85   |
| Marconi RC Oscillator 20Hz - 200Khz Type TF 1101                         | £85   |
| Marconi AM/FM Signal Generator Type TF 995A/5                            | £230  |
| Marconi VHF Signal Generator Type TF 1064B/5M                            | £125  |
| Marconi Tx & Rx Output Test Set Type TF 1065                             | £85   |
| Pye Modulation Meter 68 - 510Mhz Type MM1                                | £80   |
| Airmec Sweep Signal Generator 20Hz - 200Khz Type 352                     | £45   |
| Marconi Universal Bridge Type TF 868B                                    | £110  |
| Marconi Universal Bridge Type TF 1313                                    | £220  |
| Tektronix Oscilloscope Type 647  | £250  |
| Tektronix Oscilloscope Type R647A Less Plug ins                          | £195  |
| EMI Wide Band Amplifier Plug-in Type 7/1                                 | £25   |
| Advance Oscilloscope Type OS15A LP Tube 3Mhz                             | £85   |
| Advance Oscilloscope Type OS25A Twin Beam 3Mhz                           | £125  |

|  |      |
|--|------|
| Tektronix Oscilloscope Type 502                            | £85  |
| Pye Base Station Type F30 AM High Band & Low Band from     | £200 |
| Pye Base Station Type F401 AM High Band                    | £250 |
| Pye Base station Type F17 FM High Band                     | £250 |
| Pye Reporter Type MF6 AM High Band & Low Band              | £90  |
| Pye Europa Type MF5U FM High Band                          | £70  |
| Pye Olympic Type M201 AM High Band                         | £65  |
| Pye Motofone Type MF5 AM High Band & Low Band              | £45  |
| Pye Westminster Type W30 Low Band                          | £25  |
| Pye Pocketphone Type PF UHF Complete with Batteries        | £35  |
| <b>WANTED Second Hand Radiotelephone Equipment.</b>        |      |
| Pye Bantam Battery Chargers                                | £10  |
| Rank Telecoms Battery Chargers                             | £10  |
| Pye Pocketphone PF1 Battery Chargers 12 Way                | £10  |
| ITT Starphone Battery Chargers                             | £10  |
| Tektronix Hard Copy Unit Type 4601                         | £125 |
| Advance Pulse Generator Type PG 5002                       | £85  |
| Siemens Millivoltmeter 50ohm 500mW/0 - 12Ghz               | £95  |
| Gaumont - Kalee Flutter Meter                              | £40  |
| Siemens Transistor Power Unit 0 - 30v 2amp.                | £30  |
| Avo Valve Characteristic Meter Type 3                      | £40  |
| Airmec Wave Analyser Type 853 30Khz - 20Mhz                | £45  |
| Sullivan RC Oscillator 40Khz - 125Khz                      | £35  |
| MESL Sweep Oscillator Type M1000 8 - 12Ghz                 | £125 |
| Electrohome 9" Video Monitor metal case                    | £50  |
| Aztec 20" Video Monitor metal case                         | £40  |
| ITT 20" & 24" Video Monitors wooden case                   | £30  |
| General Radio Microwave Oscillator Type 1360B 1.7 - 4.1Ghz | £125 |
| Wayne Kerr Component Bridge Type B521                      | £95  |
| Marconi Oscillator Type TF 1246 40Khz - 50Mhz              | £95  |
| Wandel & Gottmann Level Meter Type TFFM 43 10Khz - 14Mhz   | £80  |
| Servomex AC Voltage Stabiliser Type AC2 240 vac 9amp       | £45  |
| Servomex AC Voltage Stabiliser Type AC7 240 vac 40amp      | £95  |
| Hewlett Packard Sweep Generator Type 692D 1.8 - 4.2Ghz     | £300 |

|   |                            |
|---|----------------------------|
| Tektronix Plug in Power Unit Type 133 with Type O Plug in     | £83                        |
| Tektronix Storage Display Unit Type 611                       | £120                       |
| Tektronix Oscilloscope Type 515A                              | £85                        |
| Tektronix Plug in Type CA                                     | £25                        |
| Schomandl Frequency Meter Type FD1 30 - 900Mhz                | £50                        |
| Rohde & Schwarz AF Wave Analyzer Type BN48302                 | £50                        |
| Airmec Modulation Meter Type 210 3 - 300Mhz                   | £95                        |
| Marconi Carrier Deviation Meter Type TF 791D 4 - 1024Mhz      | £125                       |
| Marconi FM Signal Generator Type TF 1066B/1 10 - 470Mhz       | £280                       |
| Marconi AM Signal Generator Type TF 144H/4S 10Khz - 72Mhz     | £125                       |
| Marconi Out of Limits Indicator Type TF 2404                  | £80                        |
| UCC Micro - Film Reader Cassette Type                         | £35                        |
| Marconi Transmission Line Test Set Type TF 1267               | £40                        |
| Marconi Variable Attenuator 75ohm Type TF 1073A/2S            | £20                        |
| 60 amp Alternator & Generator Noise Filter                    | £1.00 each                 |
| Instrument Fans 4 1/2" x 4 1/2" 240vac                        | £3 each, 110vac £1.50 each |
| Garrard Car Cassette Player Mechanisms, Stereo Head           | £2.50                      |
| Tektronix Oscilloscope Probes                                 | £10 each                   |
| Pye Pocketphone Rx Ni-Cad Batteries                           | 3 for £1.00                |
| Mullard Var-cap TV Tuners ELC 2003 Ex Band New Sets           | £3.50                      |
| Pye Cambridge/Vanguard 18 Way Control Leads                   | £2.00                      |
| BNC Plugs 75 ohm  | 50p each                   |
| IC Test Clips 28 pin & 40 pin                                 | £2.00 each                 |
| Circulators 500 - 720 Mhz 'N' sockets                         | £25                        |
| Transformers Type 2N3055                                      | 4 for £1.00                |
| Transformers 30 volt @ 1 amp.                                 | £1.00                      |
| Transformers 36 volt @ 1.5 amp.                               | £1.00                      |
| Transformers 600 - 0 - 600 @ 250mA plus 460 - 0 - 460 @ 230mA | £10.00                     |
| 'Variaes' 12 amp, 5 amp, 8 amp, 15 amp, 20 amp, 25 amp        |                            |
| Loudspeakers Richard Allan Type CP12, 12" 15 ohm              | £6.00                      |
| Capacitors 16 mfd 6.5kv £25 each, 0.33 mfd 10kv £4.00 each.   |                            |

## PYE POCKETPHONE PF1 UHF RECEIVER

440-470 MHz, Single Channel, int. speaker and aerial. Supplied complete with rechargeable battery and service manual, £6 each plus £1 p.p. plus V.A.T.

## BREAKING TEK 545A SCOPES FOR SPARES

CRT type T543 P2 £12 each. Mains Transformers T601 £15. High Volume Transformer T801 with valves £25. Also Switches, Knobs, Fans, Capacitors and Metalwork.

## RADIOSONDE RS21 METEOROLOGICAL BALLOON TRANSMITTER


With Water Activated Battery, contains all-weather sensors, fully solid state, £5 each plus £1 p.p. plus V.A.T.

P. & P. or Carriage and V.A.T. at 15% on total must be added to all orders. Callers very welcome, strictly between 9 a.m. and 1 p.m. and 2 and 5 p.m. Monday to Friday inc.

Barclaycard and Access taken Official orders welcome



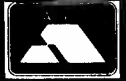
5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE  
PHONE: ELY (0353) 860185


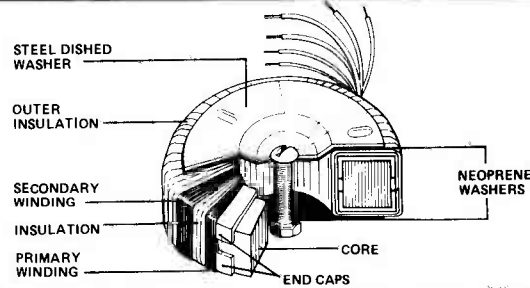
# TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 14 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



| 15 VA<br>62 x 34mm<br>0.35Kg<br>Regulation 19% | 50 VA<br>80 x 35mm<br>0.9Kg<br>Regulation 13% | 120 VA<br>90 x 40mm<br>1.2Kg<br>Regulation 11% | 225 VA<br>110 x 45mm<br>2.2Kg<br>Regulation 7% | 500 VA<br>140 x 60mm<br>4Kg<br>Regulation 4% |
|--|---|--|--|--|
| <b>SERIES SECONDARY</b>                        |   |  |  |  |
| No   | Volts   | RMS Current                                    |  |  |
| 0x010  | 6+6   | 1.25   | 6x012  | 12+12  |
| 0x011  | 9+9   | 0.83   | 6x013  | 15+15  |
| 0x012  | 12+12   | 0.63   | 6x014  | 18+18  |
| 0x013  | 15+15   | 0.50   | 6x015  | 22+22  |
| 0x014  | 18+18   | 0.42   | 6x016  | 25+25  |
| 0x015  | 22+22   | 0.34   | 6x017  | 30+30  |
| 0x016  | 25+25   | 0.30   | 6x018  | 35+35  |
| 0x017  | 30+30   | 0.25   | 6x019  | 40+40  |
|  |   |  | 6x020  | 45+45  |
|  |   |  | 6x021  | 50+50  |
|  |   |  | 6x022  | 55+55  |
|  |   |  | 6x023  | 60+60  |
|  |   |  | 6x024  | 65+65  |
|  |   |  | 6x025  | 70+70  |
|  |   |  | 6x026  | 75+75  |
|  |   |  | 6x027  | 80+80  |
|  |   |  | 6x028  | 85+85  |
|  |   |  | 6x029  | 90+90  |
|  |   |  | 6x030  | 95+95  |
|  |   |  | 6x031  | 100+100                                      |
|  |   |  | 6x032  | 105+105                                      |
|  |   |  | 6x033  | 110+110                                      |
|  |   |  | 6x034  | 115+115                                      |
|  |   |  | 6x035  | 120+120                                      |
|  |   |  | 6x036  | 125+125                                      |
|  |   |  | 6x037  | 130+130                                      |
|  |   |  | 6x038  | 135+135                                      |
|  |   |  | 6x039  | 140+140                                      |
|  |   |  | 6x040  | 145+145                                      |
|  |   |  | 6x041  | 150+150                                      |
|  |   |  | 6x042  | 155+155                                      |
|  |   |  | 6x043  | 160+160                                      |
|  |   |  | 6x044  | 165+165                                      |
|  |   |  | 6x045  | 170+170                                      |
|  |   |  | 6x046  | 175+175                                      |
|  |   |  | 6x047  | 180+180                                      |
|  |   |  | 6x048  | 185+185                                      |
|  |   |  | 6x049  | 190+190                                      |
|  |   |  | 6x050  | 195+195                                      |
|  |   |  | 6x051  | 200+200                                      |
|  |   |  | 6x052  | 205+205                                      |
|  |   |  | 6x053  | 210+210                                      |
|  |   |  | 6x054  | 215+215                                      |
|  |   |  | 6x055  | 220+220                                      |
|  |   |  | 6x056  | 225+225                                      |
|  |   |  | 6x057  | 230+230                                      |
|  |   |  | 6x058  | 235+235                                      |
|  |   |  | 6x059  | 240+240                                      |
|  |   |  | 6x060  | 245+245                                      |
|  |   |  | 6x061  | 250+250                                      |
|  |   |  | 6x062  | 255+255                                      |
|  |   |  | 6x063  | 260+260                                      |
|  |   |  | 6x064  | 265+265                                      |
|  |   |  | 6x065  | 270+270                                      |
|  |   |  | 6x066  | 275+275                                      |
|  |   |  | 6x067  | 280+280                                      |
|  |   |  | 6x068  | 285+285                                      |
|  |   |  | 6x069  | 290+290                                      |
|  |   |  | 6x070  | 295+295                                      |
|  |   |  | 6x071  | 300+300                                      |
|  |   |  | 6x072  | 305+305                                      |
|  |   |  | 6x073  | 310+310                                      |
|  |   |  | 6x074  | 315+315                                      |
|  |   |  | 6x075  | 320+320                                      |
|  |   |  | 6x076  | 325+325                                      |
|  |   |  | 6x077  | 330+330                                      |
|  |   |  | 6x078  | 335+335                                      |
|  |   |  | 6x079  | 340+340                                      |
|  |   |  | 6x080  | 345+345                                      |
|  |   |  | 6x081  | 350+350                                      |
|  |   |  | 6x082  | 355+355                                      |
|  |   |  | 6x083  | 360+360                                      |
|  |   |  | 6x084  | 365+365                                      |
|  |   |  | 6x085  | 370+370                                      |
|  |   |  | 6x086  | 375+375                                      |
|  |   |  | 6x087  | 380+380                                      |
|  |   |  | 6x088  | 385+385                                      |
|  |   |  | 6x089  | 390+390                                      |
|  |   |  | 6x090  | 395+395                                      |
|  |   |  | 6x091  | 400+400                                      |
|  |   |  | 6x092  | 405+405                                      |
|  |   |  | 6x093  | 410+410                                      |
|  |   |  | 6x094  | 415+415                                      |
|  |   |  | 6x095  | 420+420                                      |
|  |   |  | 6x096  | 425+425                                      |
|  |   |  | 6x097  | 430+430                                      |
|  |   |  | 6x098  | 435+435                                      |
|  |   |  | 6x099  | 440+440                                      |
|  |   |  | 6x100  | 445+445                                      |

**Why a Toroid?**

- \* Smaller size & weight to meet modern 'slimline' requirements.
- \* Low electrically induced noise demanded by compact equipment.
- \* High efficiency enabling conservative rating whilst maintaining size advantages.
- \* Lower operating temperature.

**Why ILP?**

- \* Ex-stock delivery for small quantities.
- \* Gold service available. 21 days manufacture for urgent deliveries.
- \* 5 year no quibble guarantee.
- \* Realistic delivery for volume orders.
- \* No price penalty for call off orders.

Prices including P&P and VAT

| VA  | Size | £     | VA  | Size | £     |
|-----|------|-------|-----|------|-------|
| 15  | 0    | 7.43  | 160 | 5    | 12.90 |
| 30  | 1    | 8.08  | 225 | 6    | 16.30 |
| 50  | 2    | 10.10 | 200 | 7    | 18.55 |
| 80  | 3    | 10.81 | 500 | 8    | 25.73 |
| 120 | 4    | 11.73 | 625 | 9    | 31.63 |

For 110V primary insert "0" in place of "X" in type number.  
For 220V primary (Europe) insert "1" in place of "X" in type number.  
For 240V primary (UK) insert "2" in place of "X" in type number.  
**IMPORTANT: Regulation - All voltages quoted are FULL LOAD.**  
Please add regulation figure to secondary voltage to obtain full load voltage.



Post to: ILP Electronics Ltd., Dept. 2  
Graham Bell House, Roper Close,  
Canterbury, Kent. CT2 7EP  
Tel: (0227) 54778 Telex: 965780

**ELECTRONICS LTD.**

# STOP CRACKLE AND POP

No, this is not a plea for quieter breakfast cereals, but rather it is Vivian Capel's guide on how to eliminate interference on the car radio.

This time of year seems to send many of our readers out from their dens and onto the roads, to seek blue skies, the lonely trail and wide open spaces. What they find will be bank-holiday drizzle, traffic jams and, if they ever arrive at their destinations, crowded beaches. Never mind, there's that cheerful Terry Wogan on the radio to keep the spirits up! But what's this? Where is the crystal-clear reception that was heard when the radio was tried out at home? What are all the crackles and bangs?

The answer is not that it is the saviours of humanity, trying to save us from Wogan's dreadful jokes, but that it is the gremlins under the bonnet — we didn't try running the engine when we set up the radio, did we? And now all those interfering little gremlins are showing themselves in force.

Suppressing interference is rather a hit-and-miss procedure, and often garage hands can do a good job based purely on experience of what has worked in the past. Also some cars and some radios are more prone to give trouble. However, a knowledge of the causes and possible cures for interference should help you to solve your own problems, even ones that defeat experienced mechanics — provided, of course you check them out before you set out on your Odyssey.

## A Bit Of Theory

So, what is the cause of interference, and what can be done to avoid it? In the electrical circuits of a car, there is quite a lot of switching of electrical currents going on. These switchings can be regular, as in the case of the ignition system, or irregular, in the case of the instrument voltage stabiliser or battery charging regulator (although modern cars will have solid-state equivalents of the last two).

Nature doesn't like sharp ons and offs, and, as anyone familiar with Fourier analysis will know, treats these electrical signals as assemblages of lots of sine waves added together. In theory, to get an infinitely steep rise in a voltage, then sine waves of up to infinite frequency must be present; in practice, there is no such thing as an infinitely steep voltage rise, but the simple act of opening and closing a contact carrying a DC current into a resistive load can generate momentary RF signals well into the MHz region. These can be picked up by a car radio either as in-band signals, or as such strong out-of-band signals that they break through the tuned circuits.

Looking at the ignition system of the car, not only do we have the switching of current to and from the induction coil, but in the induction coil itself, we obviously have a fair amount of reactance. Added to this, we have

leads on the primary and secondary side of the induction coil which will make excellent aeriels. In fact, the modern car ignition bears such a similarity to Guglielmo Marconi's original spark-gap transmitter that it would be very surprising indeed if it did not radiate RF!

There are three ways that the RF can reach the radio from the interfering circuit, this being the ignition circuit or other source: firstly, it could be directly radiated from the source to the aerial or some other section of the signal input to the radio; it can be picked up and re-radiated to the aerial by some other metallic object, which could be either an adjacent electrical lead or some other object in the car such as a body panel (here the *secondary radiation*, as this is called, could be having a greater effect than the original radiation!); and finally, the RF could be reaching the radio via the supply leads — although, in theory, with competent design of the radio, this should never occur.

## Aerial

A common cause of trouble can be something wrong with the aerial and associated circuit. For a start, is the aerial in the best position? People always seem to install it on one of the wings, which is right next to the sources of most of the interference (at least, on most cars). If you're just about to install your aerial there, you could save yourself a lot of trouble by putting it elsewhere, such as on the roof or at the back. At the very least, it should be on the wing furthest from the distributor. And if all the other solutions detailed below fail, it may be worth moving an existing aerial.

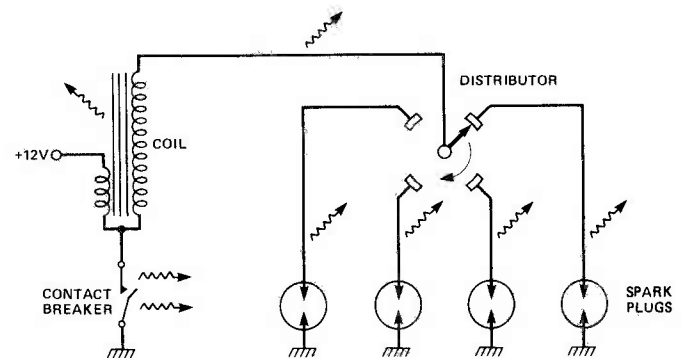


Fig. 1 Although some interference is radiated from the spark at the contact breakers, most is radiated by the supply lead which acts as an aerial.

## SUPPRESSORS

There are a variety of suppressors available, each having a different effect, and each being most suitable for a particular type of circuit.

### Resistive Suppressors

These are connected in series with the interference-producing circuit and impede the oscillatory current. Obviously, they also produce some power loss on the DC current and so can only be used in the HT ignition circuits. The resistance value must be something of a compromise in order to give adequate suppression of interference currents without significant degradation of engine performance. Common values are 5k and 10k.

### Inductive Suppressors

Also connected in series with the offending circuit, they too work by impeding the interfering currents. However, having a low DC resistance, they have little effect on the normal DC currents in the circuit and so introduce virtually no power loss. Inductive reactance rises with frequency, so the impedance to RF is very high and it is strongly inhibited.

For the ignition circuit to work, it is necessary for a current flowing on the primary to build up fairly quickly to a maximum value and then be interrupted, which produces the spark in the secondary. Adding an inductor in series with the primary prevents this, and so inductive suppressors cannot be used for the ignition system.

A factor that affects the efficiency of inductor suppressors is self-capacitance. Each turn in a coil has a capacitance to the adjacent one, so the effect is of a string of capacitors in series. The combined capacitance is therefore a fraction of that of the single turn to its neighbour (the single turn capacitance divided by the number of turns, assuming all are equal). As the single

turn value is not great, the total is much less; however, it can be sufficient to bypass the inductor at very high frequencies. Good suppressors are wound to minimise self-capacitance; however, inferior suppressors would have a poorer suppression factor for VHF, although they may be quite adequate for medium and long AM wavebands.

### Capacitive Suppressors

These are wired across the interference source and thereby shunt RF currents without affecting DC. Connection must be to the actual terminal of the source so that no part of the circuit wiring is carrying RF. Also the lead to the capacitor should be as short as possible otherwise it will radiate, because it is conducting RF to the capacitor. Likewise, the point to which the suppressor is earthed should be to the casing of the source not a nearby earthing point because RF currents would flow from this point to the source-earth and thereby possibly radiate.

Even the inch or so of essential connecting wire may radiate at very high frequencies sufficiently to give some interference. Co-axial or lead-through capacitors are recommended for VHF. With these the lead-out wire passes through the centre of the capacitor which thereby can be positioned right up to the terminal. Circuit leads are connected to the other end of the lead-out. Thus the suppressor may appear to be in series but in fact is not.

Just as inductors possess capacitance so do capacitors possess inductance. This is often due to the rolls of metal foil used in many capacitor types. Such inductance, being in series with the capacitance, offers a high impedance to high frequencies and thereby reduces the shunting effect of the suppressor. Though inductance is low, it becomes significant at VHF. Low induction capacitors can be formed by doubling back the foil to give inductance cancellation, and these are the type that should be used for high-frequency suppression.

### Earthing Straps

Heavy copper braid can be used to earth various parts, particularly the bonnet to the main frame or engine block. This inhibits secondary radiation. A point to watch with these is that the ends should be tinned with solder otherwise the contact between copper and steel in the presence of moisture could set up an electrolytic reaction which could start corrosion. Even if only mild, this would increase the contact resistance and could nullify the effect of the strap.

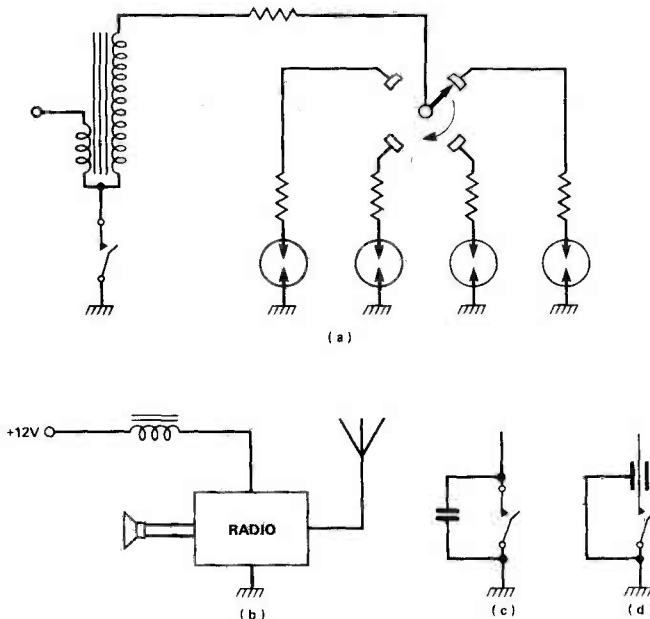


Fig. 2 Different types of suppressor: (a) resistive, impedes both AC and DC current, so can only be used on the high-voltage, low current spark circuit; (b) inductive, usable in most places except ignition coil primary; (c) capacitive, not suitable for EHT circuit (think about it!); (d) lead-through capacitive, minimum radiation for FM.

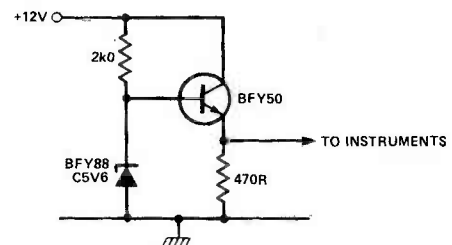


Fig. 3 A circuit for a simple voltage stabiliser to replace the mechanical vibrator type; of course, if you want to design something more complicated...



Water conducts electricity, and this can lead to problems if there is an ingress of moisture into the cable linking the aerial to the radio, or into the join between the aerial and the cable. Check also that there is a very low resistance between the top of the aerial and the aerial terminal — poor contact between sliding sections in a telescopic aerial can mean that only one or two sections are actually providing any signal to the radio!

Check, also, that there is a good connection between the aerial and cable earths, and the body of the car. It may be necessary to scrape off some paint from the concealed section of the bodywork around the aerial. With old aerials, corrosion can occur and impair existing contacts — an ohmmeter can be very handy for checking this, provided it has a good low-ohms scale.

## Ignition

The principal source of interference is undoubtedly the ignition system. This can be readily identified by revving the engine and then switching it off. Ignition interference consists of a stream of rapid crackling noise which varies with engine speed and stops immediately the engine is switched off. However, some other sources produce interference that dies down with the engine.

All new cars must conform to certain EEC regulations which provide for a minimum standard of interference suppression. To fulfill these, resistive HT cables are normally fitted. Older cars will probably not have these and either new leads or, depending on the state of the existing leads, separate in-line resistive suppressors should be fitted. For stubborn cases, especially for FM reception, suppression may be required in all plug leads as well as the HT cable from coil to distributor.

Before doing that, though, fit a  $1\mu\text{F}$  capacitive suppressor from the ignition coil terminal that takes the lead from the ignition switch to earth. For FM, use a non-inductive lead-through type. The coil itself should be encased in metal and the case should be well earthed to the engine block; the paint beneath the fixing clip may need to be removed to get a good contact. If a plastic encased coil is fitted, change it.

If the interference persists, listen with engine running with the bonnet open and with it closed. It should be much less with it closed; if not, there are two possibilities. One is that the bonnet is not well earthed and is acting as a secondary radiator. Earth it temporarily across the hinge with some heavy wire, making sure of good contact at both ends to bare metal. If there is now a difference with the bonnet closed, replace the wire with copper braid. This can be obtained from firms specialising in car radio installation. Screening stripped off some co-ax or other screened cable may not be heavy enough but can be worth trying.

Unabated interference, even with a closed, well-earthed bonnet suggests that it is not being picked up by the aerial at all. This can be checked by removing the aerial plug and fitting a dummy consisting of a plug with a  $68\text{ pF}$  (or near) capacitor wired across it. Continuing interference shows that it is getting in by some other path.

The power lead to the radio is the prime suspect now, and an in-line inductive suppressor should be fitted in series. Loudspeaker wiring is another though less likely possibility. If this is so, wire the speaker circuit with twin screened wire and earth the screen at one point only.

Yet another path could be by secondary radiation from the steering column or gearlever. This has been found with some French-made cars. Try a temporary earth to check it, then fit a braid to the offending item from a near-by earthing point.

## Electronic Ignitions

In theory, electronic ignitions should be a lot less troublesome than electromechanical ones; in practice, some models can be more troublesome. Assuming that yours is the type that doesn't replace the coil, the first step is to check that the leads between the coil and the ignition, and the ignition and earth (or the positive supply, depending on which way the coil current flows) are as short as is practicable.

Some systems you install yourself tell you to remove completely the coil suppressor capacitor. It may be necessary to reinstate the capacitor, and this should, obviously, be done fairly cautiously to avoid damaging the ignition output stage, so start with a fairly low value, say  $100\text{ nF}$ , and work up to whatever value the ignition will stand without mis-firing; the maximum you should need to use is around  $3\mu\text{F}$  and if this does not solve the problem, you will need to look elsewhere.

Interconnecting leads, already dealt with above, can be screened with metallic adhesive tape, such as is used for protecting windows in alarm systems; suitable tape can be obtained from security equipment shops. Wind the tape around the lead, leaving no gaps, in a spiral. Earth the screen by wrapping several turns of tinned copper wire around the tape at a convenient point, twisting together the ends, and connect to a near-by earth point.

## Generator

This may be a dynamo with old models, but for recent ones will be an alternator. Interference from both is similar, a whine that varies with engine speed, but dies down rather than cuts out immediately when the ignition is switched off. Suppression is by means of a  $1\mu\text{F}$  capacitor from the output or D terminal in the case of a dynamo, or a  $3\mu\text{F}$  for an alternator.

## Voltage Regulator

A whine or crackle that appears some moments after starting is the characteristic of interference from this source. It will disappear when a heavy electrical load is switched on such as headlights and fog lights or window demisters, and stops when the engine is just idling.

Suppression can be effected by fitting a  $1\mu\text{F}$  capacitor from the positive or D terminal to earth. Do not connect a capacitive suppressor to the F terminal. Should further suppression may be required, fit an inductive suppressor in series with the F terminal lead.

## Instrument Stabiliser

The usual bi-metallic strip type of stabiliser can produce an intermittent burst of crackling which often can be provoked by tapping the dashboard. A  $1\mu\text{F}$  capacitor across this device or from its feed terminal to earth should cure it. If not, a series inductor in addition should do the trick. Actually, electronic stabilisers are available which can be fitted in place of the mechanical ones, or a simple circuit can be built up. This will generate no interference and as a bonus give more accurate instrument readings.

## Electrical Fuel Pump

Interference from this can sound like a whine, crackling or ticking. It can be identified inasmuch as it starts as soon as the ignition is switched on but before the engine is started.  $1\mu\text{F}$  across the terminals plus a series inductor if required should suppress it.

# FEATURE : Crackle And Pop

## Ancillary Equipment

This is simply identified by the fact that interference is present only when the particular item is switched on. Examples are: windscreen wipers, washer, heater fan, direction indicators, stop lamps and clock. The latter of course is on all the time and produces a characteristic ticking in the case of electro-mechanical types.

In each case the treatment is the same, a 1  $\mu$ F from the feed terminal to earth, and if this does not completely cure it, an inductive suppressor in series with the supply lead.

## Bodywork

Fibre-glass bodies can pose a lot of problems, in that the screening that would be present with a metal body is absent, unless some other allowance has been made. The result will be that all the forms of interference will come through much more strongly than otherwise could be the case. To get rid of this, as much of the engine compartment as possible should be lined with aluminium foil, including the bonnet, and all earthed to the main frame and engine block. Even with this treatment, some problems with FM may be experienced and other measures will have to be taken.

Static discharges between body panels, or exhaust system, suspension and differential units can give spasmodic interference. As vibration often triggers it, it can be identified by coasting down a long incline with the engine off. Pin-pointing the precise member is not as

easy and can only be a matter of trial and error. Start off by bonding with braid everything that can be reasonably easily bonded, and go on from there.

If the noise has a regular repetition rate corresponding to the wheel rotation, it can be that one of the wheels has a poor earth through its bearings. Packing the offending bearing when discovered, with graphite grease can effect a cure.

It is rarely necessary to suppress everything or to suppress to the fullest extent. With many vehicles the built-in suppression is sufficient especially for AM reception. For FM though as stated before, things are more critical.

## And Finally . . .

Do not test in areas of high signal strength as this could give a false picture. Interference that is almost inaudible in such places will rise to annoying levels when the signal is weak, and in many holiday areas the signal is poor.

Interference is possible with tape players too, although they are much less vulnerable. In most cases the interference affects the playback head or associated circuitry from the power supply. Check to see if interference is the same with the player held in different positions; a cure is a series inductor in the power lead and/or an electrolytic capacitor from the power rail to earth inside the unit.

If the interference changes as the player is moved, the trouble is due to a magnetic field, most likely from the wiring harness. Often just moving the harness away will cure the trouble.

ETI

## REQUIREMENT: AMPLIFICATION SOLUTION: CRIMSON!



More than ever, Engineers, Enthusiasts, & Professionals require a reliable source of quality amplification, crimson continue to meet this demand with a comprehensive range to suit virtually every application and support this with friendly advice and back-up. Our prices have remained stable for 18 months and with two regional distributors and our own mail order system, there has never been a better time to choose the best.

### MODULES



Power amplifiers bipolar type. Incorporating full electronic protection, integral heatsink bracket, high slew/low distortion circuitry (<0.01% THD TYPICAL)

| TYPE   | MAX O/P | SUPPLY (DC) | PRICE  |
|--------|---------|-------------|--------|
| CE608  | 60W/8R  | +/-35V      | £21.50 |
| CE1004 | 100W/4R | +/-35V      | £25.00 |
| CE1008 | 120W/8R | +/-45V      | £28.00 |
| CE1704 | 200W/4R | +/-45V      | £35.50 |
| CE1708 | 180W/8R | +/-60V      | £35.50 |
| CE3004 | 320W/4R | +/-60V      | £49.50 |

### NEW LOW POWER

|       |        |        |        |
|-------|--------|--------|--------|
| CE308 | 30W/8R | +/-25V | £15.90 |
|-------|--------|--------|--------|

Power amplifiers Mosfet type. Ideal for heavy duty use — i.e. disco's or driving line transformers, integral heatsink bracket, (<0.02% THD TYPICAL)

|        |         |        |        |
|--------|---------|--------|--------|
| FE908  | 90W/8R  | +/-45V | £30.00 |
| FE1704 | 170W/4R | +/-45V | £39.00 |

Pre-amplifiers stereo modules with R.I.A.A. eq. M.M. & line input, needs vol and bal pots and input switching. Can be used with MC2 module to allow use of low O/P MC cartridges.

|       |        |             |        |
|-------|--------|-------------|--------|
| CPR1X | STEREO | +/-12V/20mA | £33.90 |
| MC2   | STEREO | +/-12V      | £23.00 |

### NEW SUPER CPR

|      |        |           |        |
|------|--------|-----------|--------|
| CPR2 | STEREO | +/-12V/20 | £47.95 |
|------|--------|-----------|--------|

Full details of our complete range including heatsins, toroidal power supplies, active crossovers etc. available on S.A.E.

### HIFI KITS



Still the reference kit amplifier! for less than £250 you can own an esoteric pre-power combination with the added pleasure of building it yourself.

Write for our full brochure and review reprints.

|        |                        |         |
|--------|------------------------|---------|
| CK1010 | Stereo pre-amplifier   | £92.00  |
| CK1040 | Stereo P/A 40+40 WPC   | £121.00 |
| CK1080 | Stereo P/A 80+80 WPC   | £134.00 |
| CK1100 | Stereo P/A 100+100 WPC | £151.00 |
| MC2K   | M/C kit for CK 1010    | £25.00  |
| P.S.K. | Pre-amp power supply   | £20.00  |

### PRO POWER

A new range of 19" rack mounting power amplifiers are undergoing field trials for launch later this year. Please contact us if you have a particular requirement for this type of amplifier as the final design will depend on your needs!

### TO ORDER

Send cash with order or quote Acces/Mastercharge card no. All prices include VAT, P&P.

### DISTRIBUTORS

London: Bradley Marshall Ltd.,  
325 Edgware Road,  
Wilmslow Audio,  
North: 35/39 Church Street Wilmslow.

### EXPORT

No problem, but as postage varies so much please write for a proforma invoice.



# CRIMSON ELEKTRIK STOKE

PHOENIX WORKS, 500 KING STREET, LONGTON, STOKE ON TRENT, STAFFS.

PHONE 0782 330 520

**RVM** Audiotronic

50 Marlborough Road,  
Derby, DE2 8DT

Tel: Derby 0332/382433

**MAIL ORDER ONLY**

RVM RANGE OF POWER MOSFET AMPLIFIER MODULES. These Power Mosfet Modules are very reliable, driving difficult loads is no problem. Application from hi power systems to studio to domestic hi-fi.

All of our modules are built and tested and carry a 2 year guarantee.

We also supply a range of heat sinks, specially recommended for RVM modules.

| Modules                      | Power RMS | Load                  | Volt Max | Size (mm)  | Price |
|------------------------------|-----------|-----------------------|----------|------------|-------|
| RVM150S                      | 70-150W   | 4 $\Omega$ 8 $\Omega$ | $\pm$ 60 | 31x80x100  | 23.50 |
| RVM300S                      | 120-300W  | 4-8 $\Omega$          | $\pm$ 65 | 31x102x136 | 32.87 |
| RVM400S                      | 170-400W  | 4-8 $\Omega$          | $\pm$ 65 | 47x89x136  | 40.92 |
| RVM700S                      | 300-700W  | 2-8 $\Omega$          | $\pm$ 70 | 47x90x197  | 60.96 |
| RVM700S Mounted on Heat Sink |           |                       |          |            | 70.40 |

|       | Size of Heat Sink Range |      |
|-------|-------------------------|------|
| HS110 | 52x91x110mm             | 5.90 |
| HS150 | 52x91x150mm             | 7.20 |
| HS210 | 52x91x210mm             | 9.44 |

All prices include post & packing.  
(Quantity discount available)

To order send cash with order, or cheque/postal order. Delivery on our Modules and Heat Sink or same day dispatch when order is received with cash, allow 7 days with cheque or postal order.

**cortex** SOFTWARE  
HARDWARE

MDEX disc operating system — from £95


MDEX. Language power  
FORTH PASCAL SPL QBASIC META  
Software to make the CORTEX go!

CORTEX 1 Mb Disc Drives  
80 track double-sided double-density  
£235

TMS9909 disc controller I.C. £24.50

CORTEX game tapes  
Space Bugs, Nibblers, Pontoon each £6


Please add VAT to all prices

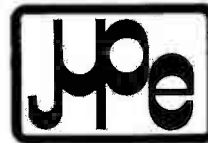

MICRO PROCESSOR ENG LTD  
21 HANLEY ROAD SHIRLEY  
SOUTHAMPTON  
SO1 5AP  
TEL: 0703 780084




# Guess who builds this great

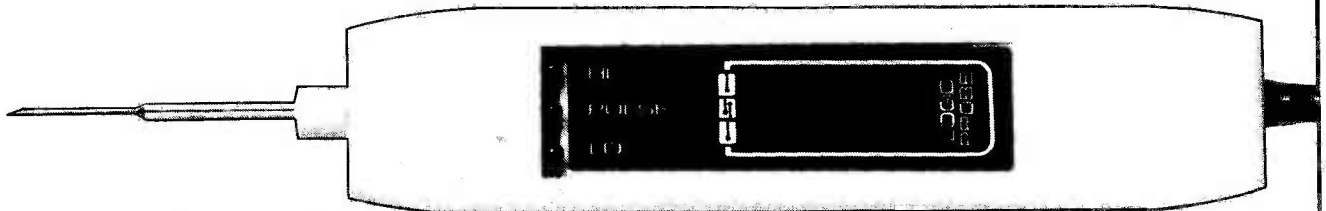
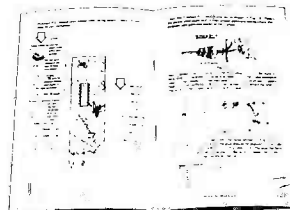
## Logic Probe...YOU! for only £14.50

With this easy-to-build Logic Probe Kit from GSC and just a few hours of easy assembly — thanks to our very descriptive step-by-step manual — you have a full performance logic probe.

With it, the logic level in a digital circuit is indicated by light from the Hi or Lo LED; pulses as narrow as 300 nanoseconds are stretched into blinks of the Pulse LED, triggered from either leading edge. You'll be able to probe deeper into logic with the LPK-1, one of the better tools from GSC.



Complete, easy-to-follow instructions help make this a one-night project.

GLOBAL SPECIALTIES CORPORATION



G. S. C. (U. K.) Limited, Dept. 9Z  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex. CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682  
Telex: 817477.

ETI JUNE 1984

GLOBAL SPECIALTIES CORPORATION. DEPT 9Z  
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
 Inc P&P and 15% VAT  I enclose cheque/  
**LPK-1 £17.83**  PO for £ \_\_\_\_\_  FREE Catalogue  
 Phone your order with Access, Barclaycard tick box   
 or American Express Card No. \_\_\_\_\_ Expiry date \_\_\_\_\_



# AUDIO DESIGN

**This article, and the two parts that are to follow, provide the practical complement to John Linsley Hood's earlier, theoretical series of the same name. Many amplifiers have claimed to be the best ever published for the home constructor; but take it from us — this is.**

**T**he earlier parts of this series on Audio Circuit Design have mainly been aimed at explaining, in as simple a manner as I could, how circuits were designed, and their values specified, to do a specific job — in an engineering sense. Fifteen years or so ago, this would have been all that the user would have asked, and he would probably have been delighted with the performance given by what would be considered a run-of-the-mill design exercise. However, things have now changed.

As I mentioned in the article which dealt with audio amplifiers, I have an ambivalent attitude towards the whole 'hi-fi' scene, in the sense of that conspiracy which appears to exist between the editorial staff of 'hi-fi' journals, and the manufacturers of 'hi-fi' equipment, by which fulsome praise is lavished only upon rare items of audio exotica — which must be very expensive, in addition to being relatively infrequently seen — and staff writers are flown half way round the world to see, hear and inwardly absorb the latest propaganda in the cause of the most recent technological miracle.

Meanwhile, the bulk of the readers of the magazines continue to use, and frequently to enjoy, the equipment which they bought at a modest price from their local dealer or discount warehouse, and which never received any rave reviews from anyone, except a consumer magazine which said it was good value for money!

I am not so calloused, mentally, that I cannot recognise that some of these hi-fi exotica are indeed very good, and well designed and made, to boot. However, this presents a problem to the designer of any kit which is to be described in an electronics constructional magazine. Whatever it is, it must provide an incentive to the would-

be constructor. Not only must it be sensible value for money, but it must also offer some quality advantage over the nicely made and prettily finished units offered at such tempting prices in the local High Street.

One advantage, which it is perhaps a little unkind to stress, is that the things you build yourself are repairable by you — the others may not be. However, if you are known, or mistakenly thought, to have any skills in the repair field, you are likely to have to fend off a kind of fan-club of friends and relatives who have bought some pretty tin-ware a few years ago, and now can't find a dealer who wants to know about it.

The other advantages may be those which are concerned with audio quality, in its various aspects. You may be able to include amenities or facilities which only you may want, but which are absent from the less expensive commercial gear, or it may be that you can gain some advantages in sound quality. This latter task is made a bit easier, certainly in respect of the equipment at the cheaper end of the market, by the fact that the need for a low sale price forces the manufacturer into the use of specialised, custom designed, circuit hardware which does an adequate though not marvellous job.

Many of the circuit designs which have been offered for the DIY constructor have relied for their appeal on the provision of a lot of electronic facilities, and I have been down this road myself, as testified by the JLH domestic preamp, published elsewhere. However, while it was fun to design and build the bits of gadgetry included in this design, the fact remains that most of these facilities are very seldom used. So, since I know that I can dispense with most of these, with very little

real loss, and since I suspect that I could do those things which remain just a little bit better than I have done them so far, my intention here is to offer a fairly simple design in which all the small practical quality improvements are incorporated, in the hope that the final unit, within the power budget decided upon, will equal or exceed in sonic quality anything available anywhere else, at any price.

This may sound both vain, and impracticable; well perhaps it may be. But my problem, in the evolution of this design — and the problem of any other designer — is that unless one has a reasonable chance of matching the quality of the best, it is hardly worth while cluttering up the printed pages with yet one more design.

## Design Philosophy

Like many of my readers, I suspect, I have read a lot about the recent trend in hi-fi thinking, in respect of Class A operation, and valves, and enormous power outputs, and the importance of connecting wires the right way round. Since I know that the people who espouse these causes are neither foolish nor easily led, I have had to try to work out a rational explanation for this collective attitude, in the hope of some design guidance emerging from this. For what it is worth, here it is.

Most of the audio quality judgments on audio amplifiers and ancillary equipment, made by the writers on this subject, are made on the basis of extended listening trials, most of which are at very high sound levels, with music of a type which has relatively few quiet passages. Valve amplifiers have the great advantage, because of their inherent tendency to 'soft' clipping, that when they are driven into overload they sound much

less awful than transistor designs which have a 'brick-wall' clipping characteristic. Also, with valves, their distortion products — of which there are usually quite a lot — are mainly 2nd and 3rd harmonic: these can, curiously, tend to enhance the sound of certain music, to make it sound 'richer'. Also, for practical reasons, not a lot of NFB can be employed, which makes LS load compatibility less demanding of design. Finally, the output transformer, which does so much to impair the electrical quality of the amplifier, does at least ensure that it can push a lot of current into a low impedance LS load.

Since most of the reviewers' auditioning is apparently done at very high sound levels, the preference for high powers is also understandable.

The case for class-A is harder to fault. With junction transistors, particularly, the sluggishness in operation of the higher current types makes crossover distortion an ever present problem, in class-B (no quiescent current) or class-AB (some zero signal level quiescent current) operation. Class-A (standing output stage current the same for zero or maximum power) operation makes for much better power output transistor HF response, and also has the big advantage that the HF characteristics of the power transistors are just as good at low signal levels as they are at high ones.

However, a class-A amplifier is unavoidably inefficient, with efficiencies in the range 25-30% being normal. This means that an 80 watts/channel class-A stereo amplifier must dissipate, perhaps, 640 watts of heat. This either implies enormous heat sinks, to keep the operating temperature down to 80 to 100°C, or fan cooling, which is noisy. Either way, such an amplifier will make quite a contribution to room heating. Now think of what life would be like with a 200 WPC class-A system! Sliding-bias class-A systems have often been tried, but never liked.

## MOSFETs To The Rescue

So far as I am concerned, the availability of power MOSFETs is a nearly complete solution to the power amplifier design problem. The recent design types of this kind are so fast that the difficulties of output stage sluggishness are abolished, and the nature of the device ensures that the HF res-

ponse is the same at all drain current levels, thereby avoiding the normal class-AB junction transistor problem of subtly different sound quality at low and high sound levels.

Power MOSFETs do have design problems, which is why, in spite of their many and conspicuous virtues, in comparison with junction transistors and transformer coupled valves, relatively few commercial designs exploit these qualities.

As for the third hi-fi fetish, connecting wires, this is less to do with the wires themselves than with the connections made to them, in interconnecting the component units of the complete audio system. It makes little sense to go to a lot of trouble in the circuit design, and then put the results in jeopardy by the use of cheap connectors. For the LS circuit, in particular, there is a great deal to be said for solid screw-down terminals.

So — to summarise the design thoughts so far. The amplifier should employ power MOSFETs in a suitable design, and have good quality wiring connectors. The preamp should have only the neces-

sary facilities, but those that are there should be as good as possible.

## The Necessary Facilities

In my own experience, a good quality RIAA input stage, an input selector switch, a volume control, a balance control, a rumble filter and some reproducible means of modifying the relative levels of bass and treble response — where both of the latter circuits must be capable of being switched out — are all that are really essential in the preamp. However, a separate class-A headphone amp is a desirable addition, and if this is included in the preamp, this unit can work on its own. You will infer from this that I prefer the preamp and the power amp to be separate units. This form of construction does make life a lot easier for the constructor. Also, for reasons of practical convenience, I think that it is sensible to house the moving coil head amp, if used, in its own separate enclosure. It can still be powered from the preamp to avoid the inconvenience of battery replacement.

So far as the power amp goes, I

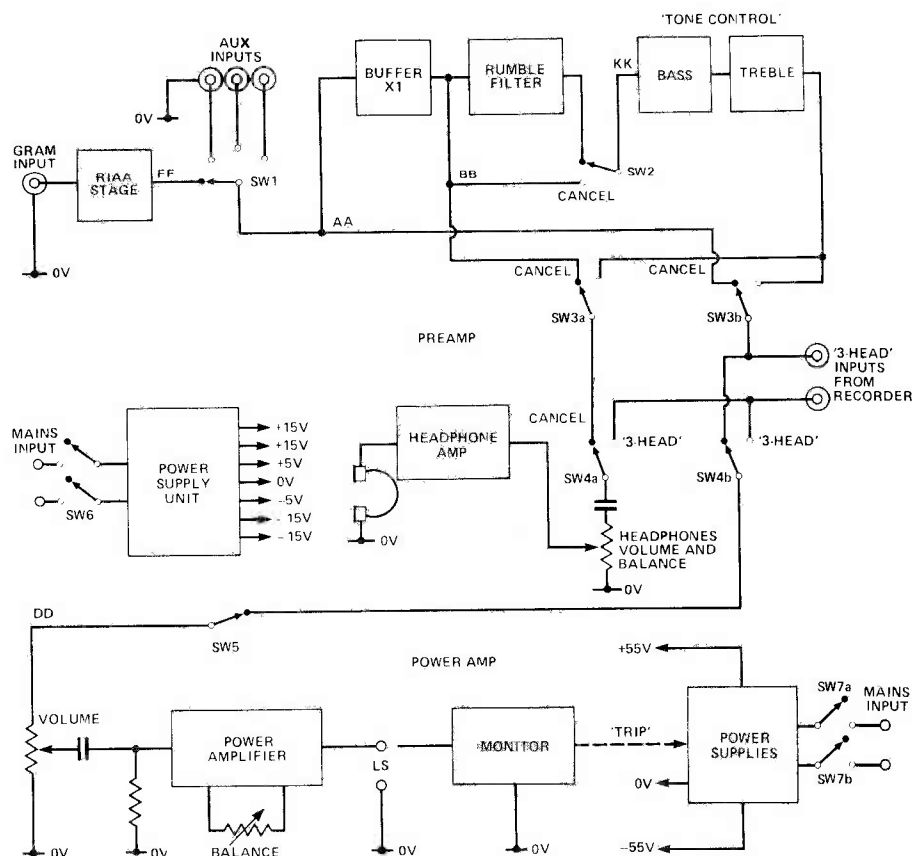


Fig. 1 Layout of the pre-/power amp system.

think that there is a lot to be said for designing this so that it has enough sensitivity (say 150mV for max output) that it can receive signals directly from ancillary units (cassette recorders, tuners and the like) without further amplification — on the grounds that the less one handles signals, the better the final result is likely to be. This implies that the volume control will be at the input to the power amp, and the channel balance control will also require to be included somewhere within the power amp. Fortunately this is easy to organise.

This arrangement also implies that the preamp needs to have provision for a 'straight through' path from the input selector to the power amp input position. The final layout is shown in Fig. 1. A minor point, occasionally exhorted by the hi-fi pundits, is that the overall system is non-inverting in signal phase, and that switching out sections does not affect the overall phase polarity.

Both the power amp and pre-amp are operated from stabilised power supplies. In the preamp case, these are voltage regulator ICs, and in the power amp, where higher voltages and currents are necessary, a discrete component unit is employed. LS protection is provided without the need for relays or fuses in the output line to the LS. (There are good relays with gold plated contacts, and some fuse holders also are soundly made, however, if one can do without them this must be better). This is accomplished by monitoring the DC offset on the LS line, and switching off the PSU electronically if this exceeds some pre-determined value, averaged over a fraction of a second.

This doesn't confer on the circuit the useful facility of disconnecting the LS for a few seconds, following switch-on, to remove the normal switch-on 'plop', for which a relay is so useful, but it is possible, as an option, to connect a clamp circuit across the power amp input, to hold this down to the 0V line for a few seconds after switching on. A junction FET will do this job very well, since it conducts, bi-directionally, until a voltage is applied to its gate to cut it off, when it will become a very good quality open circuit.

This concludes the outline of the design 'architecture'. The only other point which seems worthwhile exploring before we get down to the detailed considera-

tion of the circuitry is what kind of gain blocks we should use. I think that some of the new '741' pin connection op-amps such as the TL071, and the LF351 (or the PMI OP27 if money is less of a consideration) make excellent audio gain blocks. Moreover, for the convenience of the stereo enthusiast, these are available as dual op-amps in their TL072 and LF353 versions. Although I indicated earlier in this series that I thought that it was possible to do this job a little bit better by the use of discrete component 'gain blocks', the advantage is small, and the IC is simpler and more cost effective.

So, what I propose is that these 'discrete component' units should be restricted to the two input gain blocks in the RIAA stage, where their qualities may best be seen. In the case of the tone-control stage, or the rumble filter, my feeling is that if it is necessary to use these signal modifying elements there is an implied admission that the signal is less good than one would wish anyway, so the very slight tonal penalty (and it really is very small) which would be paid by using an op-amp is not likely to be enough to justify more complex and costly alternative circuitry.

Since I have already discussed, and analysed, the design techniques of most of the circuit blocks employed in the preamp (Audio Design, parts 1-7, ETI Sept. 1983 - March 1984), I will not examine them in detail again, except where some additional information would be useful, or where differences in application may modify the circuit choice somewhat.

### RIAA Stage

Although in normal circumstances, I would prefer a two-stage input system, using two consecutive active stages, of the type shown in Fig. 10 of part 3 of this series, there is no tonal difference between the use of a passive and


an active network as the second stage integrator — it is simply that the passive network will have an attenuation of 10 at 20kHz, which will require the first gain block to have an output at least 10 times greater at this frequency.

However, in the circumstances of this preamp where the output signal level required for maximum power amplifier output is only 150mV, this is not a significant problem, especially in view of the 10V RMS output capability of the gain block used (Fig. 8b, part 3). So, since using the passive network to give the second part of the RIAA attenuation curve will save 16 transistors, it seems a sensible move.

The advantages of breaking down the composite 30Hz - 1KHz, 1KHz - 20KHz RIAA equalisation curve into two separate stages were discussed in part 3 of this series, and in earlier articles of mine, and other writers elsewhere. Unfortunately, there still remain designers to be convinced, I am sorry to say, and it is difficult, by remote control, to have them listen to the two choices so that one may say 'There you are. It does sound better, doesn't it?'. So, may I make the argument that very seldom, in human experience, can one make any device do two different jobs at once with as good a performance as two separate more specialised units. Why therefore should one expect a single gain stage to do two separate equalisation functions simultaneously with equal — let alone better — results than when these functions are separated.

The final gramophone PU input stage therefore becomes as shown in Fig. 2 (Fig. 7 of part 2), and its complete layout as shown in Fig. 3, with the gain block instead of the schematic op-amp diagram. Since for optimum results many PU cartridges require a measure of cap-

Fig. 2 Simplified circuit of the PU input stage.

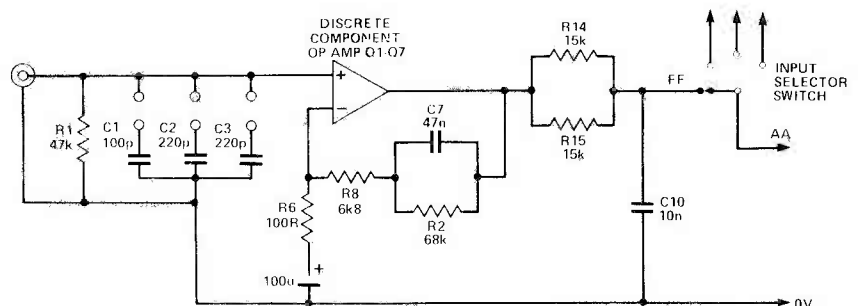





## PARTS LIST — RIAA STAGE

| RESISTORS (all 2% 0.4W metal film) |   |
|------------------------------------|---|
| R1,101                             | 47k   |
| R2,102                             | 10k   |
| R3,5,103,105                       | 15k   |
| R4,104                             | 2k7   |
| R6,11,106,111                      | 100R  |
| R7,107                             | 100k  |
| R8,108                             | 6k8   |
| R9,13,109,113                      | 47R   |
| R10,110                            | 680R  |
| R12,112                            | 68k   |
| R14,15,114,115                     | 15k   |
| CAPACITORS                         |   |
| C1,101                             | 100p polystyrene                            |
| C2,3,102,103                       | 220p polystyrene                            |
| C4,104                             | 470μ 6V3 low ESR electrolytic, tubular      |
| C5,105                             | 470μ 6V3 low ESR electrolytic, PCB mounting |
| C6,106                             | 100p polystyrene                            |
| C7,107                             | 47n polycarbonate, 1%                       |
| C8,9                               | 470μ 16V electrolytic                       |
| C10,110                            | 10n polycarbonate, 1%                       |
| SEMICONDUCTORS                     |   |
| Q1-5,7,101-105, 107                | BC416                                       |
| Q6,8,106,108                       | BC414                                       |
| MISCELLANEOUS                      |   |
| PCB, wire, etc                     |   |

acitative loading in addition to the 47K input resistor, a group of three capacitors are mounted on the board to allow the choice of input capacitance values from 100pF to 540pF by simple bridging of pins on the board.

**Fig. 3 Full circuit of the PU input stage;** note that if you're cutting costs by using 5% resistors, components marked with \*\* must be 2% or better.

**Fig. 4 Overlay diagram of the PU input stage —** note the allowance for different capacitor sizes.

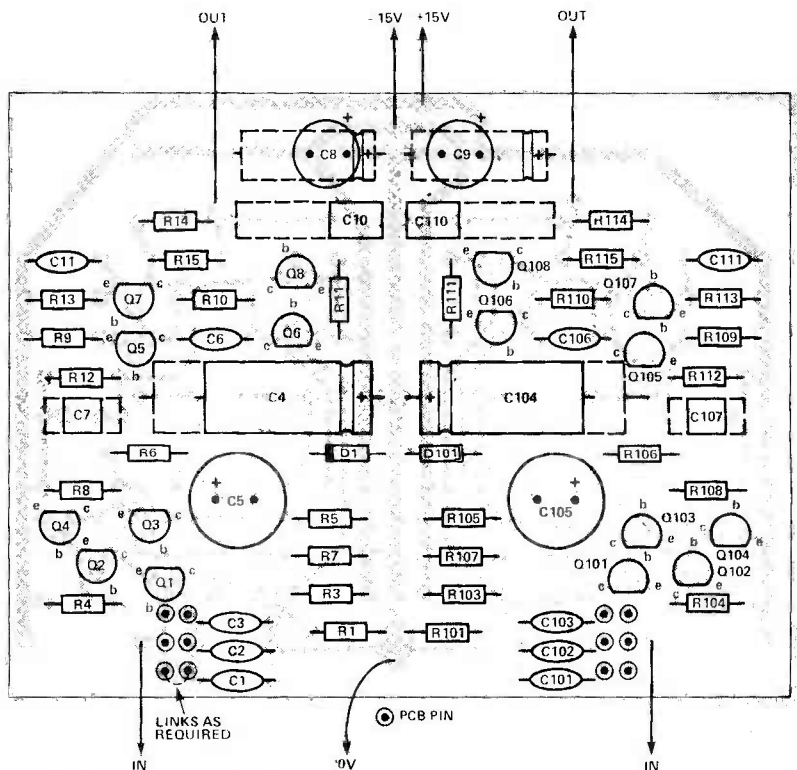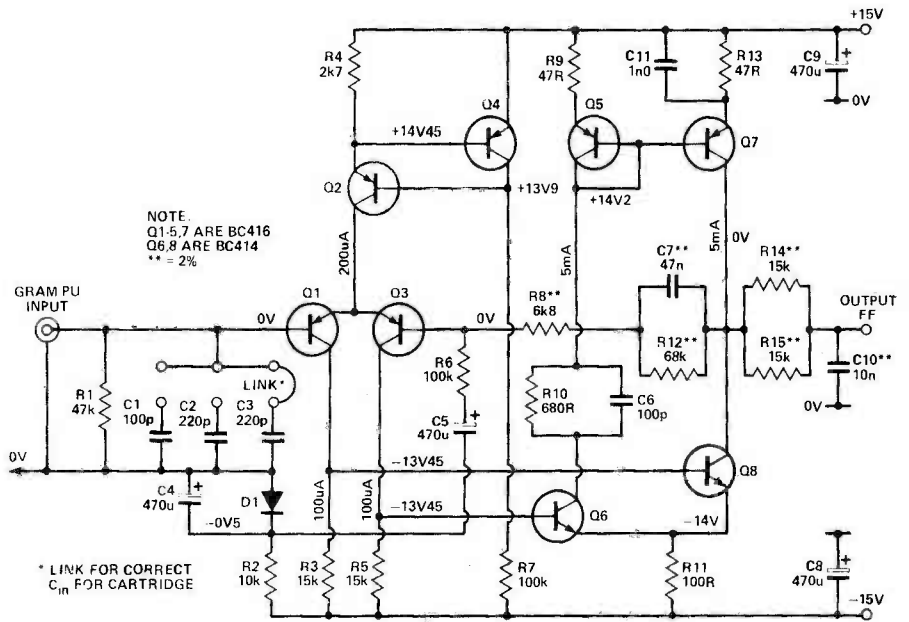

## Tone Control Stage

My experience with my rather more elaborate domestic preamp which has a tone control circuit which is capable of modifying the frequency response, in a series of 3dB plateau steps, up or down, at various frequencies, has encouraged me in the belief that this is the kind of tone control to have. However, I do not use all the possibilities it offers, and most of the time it is switched out of circuit. So, in the light of experience I feel that a simpler, cheaper, and

easier to build unit would have served me just as well.

My second thoughts on this stage are shown in Fig. 5. This is largely shown in Fig. 12 in part 4 of this series, but with a few modifications to the component values used. Because two inverting stages are employed, in cascade, the system is non-inverting in phase, and the cancel switch should make no audible difference to the sound if this stage is switched in or out when in its flat response position. Each switch, S2 - S9, generates a click-free modification to the fre-

quency response, in a controlled and reproducible manner. (Note, each 'lift' switch operation should be accurately cancellable by the equivalent 'cut' button, to restore the status quo, as a test of the correct operation of this stage.)

I have only aimed at a small (3dB) step increment or decrement in frequency response given by this stage, because the intention in this design is to compete in the upper audio bracket. If a very large treble or bass cut or lift is needed, it would seem to imply that there is something badly

amiss elsewhere in the system. It would, I think, be better to try to remedy this where it exists than to try to make the preamp compensate for it. The 3dB value has the merit, in practice, that is just big enough to be noticeable, without being so big that it is intrusive.

Two LF353 dual op-amps are used to operate this circuit, and these are fed from the + and - 15V lines derived from a pair of IC voltage regulators, and used to power the remaining units in the preamp. Push-on, push-off switches actuate the frequency steps and cancel functions. The frequency response of this circuit is shown in Fig. 7.

### PARTS LIST — BUFFER/FILTER

#### RESISTORS (all 2% 0.4W metal film)

R1,101 100k  
R2,102 330R  
R3,4,5,103,104,105 6k8

#### CAPACITORS (all polycarbonate)

C1,101 470n  
C2,102 100n  
C3,103 2μ2  
C4,104 220n

#### SEMICONDUCTORS

IC1,101 LF353.

#### MISCELLANEOUS

SW2 3p (min), 2w  
push-on, push-off

PCB, wire, etc

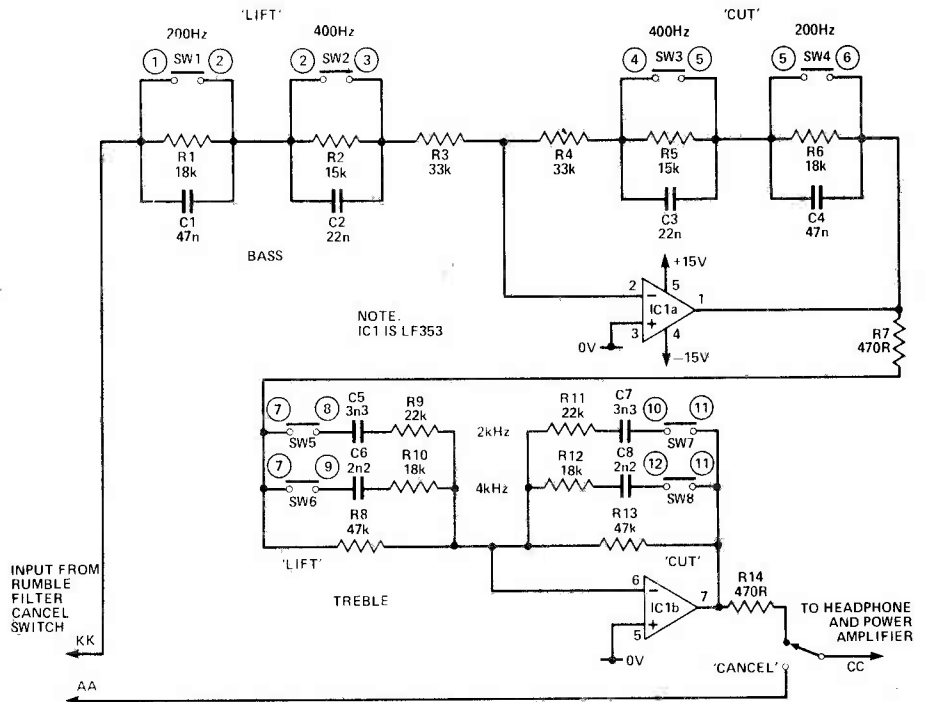


Fig. 5 Circuit diagram of the tone stage.

### PARTS LIST — TONE STAGE

#### RESISTORS (all 2% 0.4W metal film)

R1,6,10,12,101, 106,110,112 18k  
R2,5,102,105 15k  
R3,4,103,104 33k  
R7,14,107,114 470R  
R8,13,108,113 47k  
R9,11,109,111 22k

#### CAPACITORS (all polycarbonate)

C1,4,101,104 47n  
C2,3,102,103 22n  
C5,7,105,107 3n3  
C6,8,106,108 2n2

#### SEMICONDUCTORS

IC1,101 LF353

#### MISCELLANEOUS

SW5-12 DPST panel-mounting switches.

PCB, wire, etc.

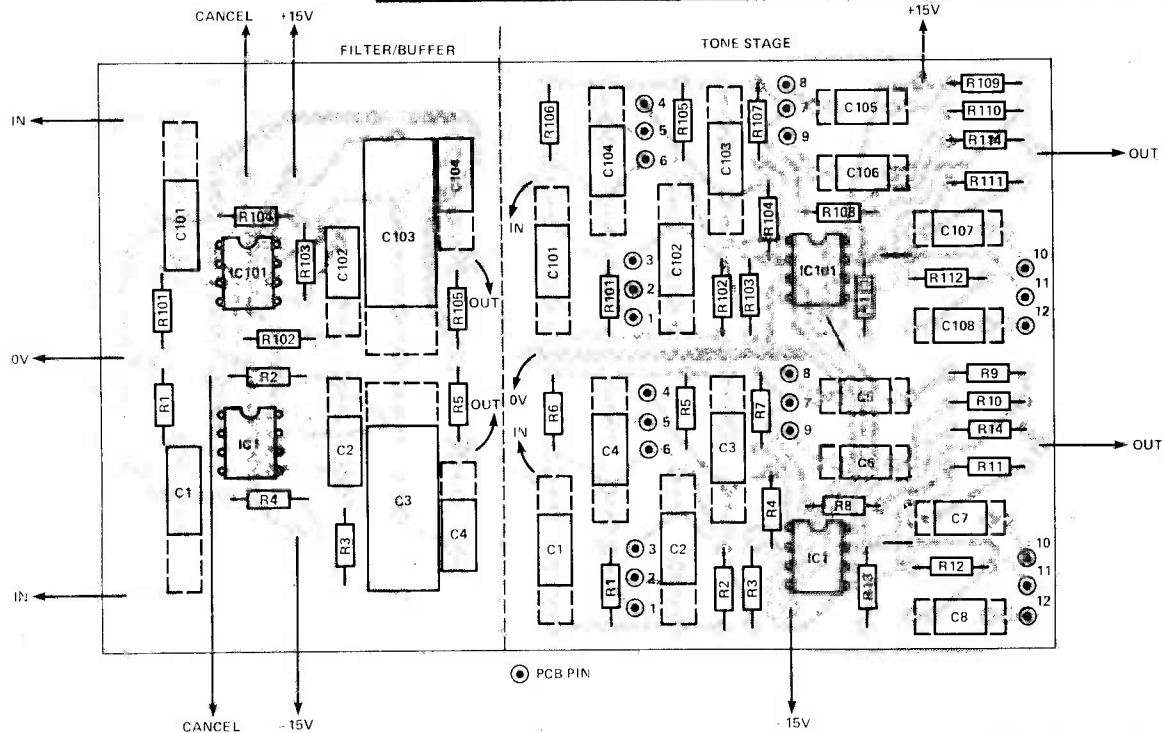


Fig. 6 Overlay diagram of the buffer/filter stage (left) and the tone stage (right). Be very careful not to get component numbering confused!


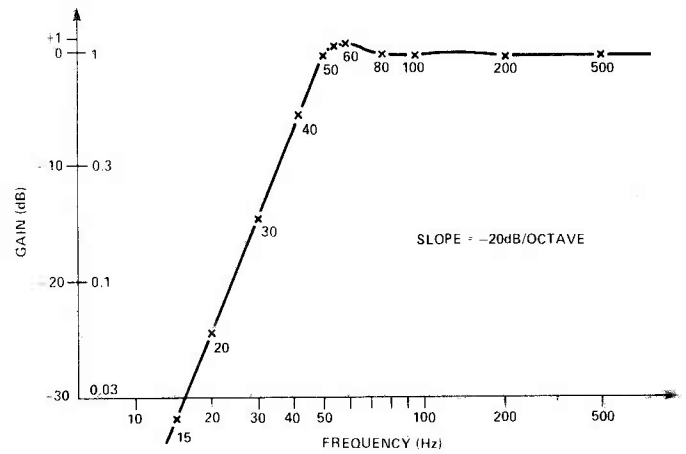
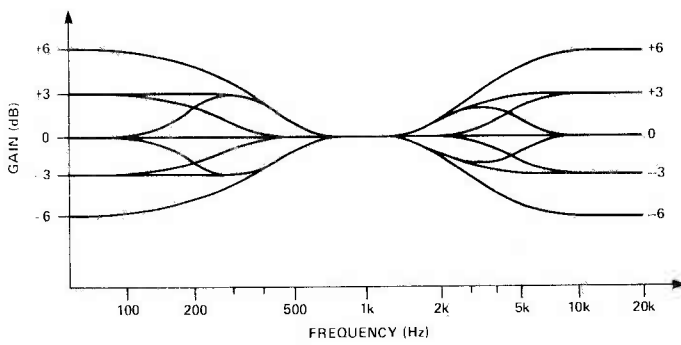


Fig. 7 (above) Response of tone stage.  
 Fig. 8 (below) Circuit of the buffer/filter.  
 Fig. 9 (right) Measured rumble filter response.

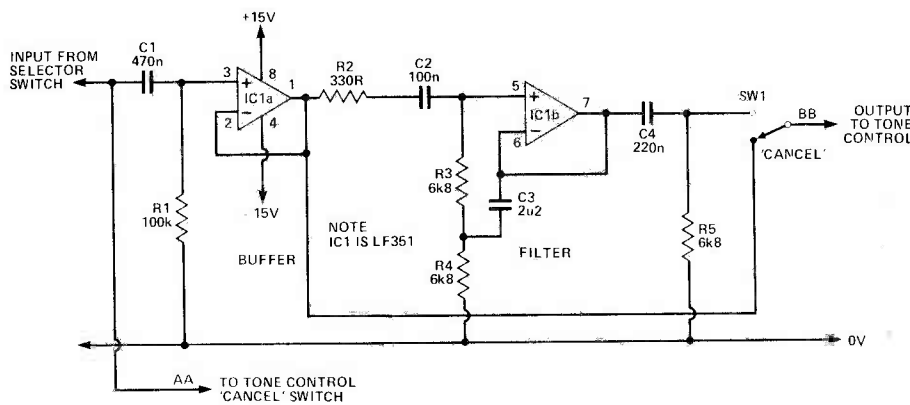

## The Rumble Filter Stage

Some otherwise very good records can suffer from rumble in the recording, and even those played by the BBC are not always free from this fault. If one is lucky enough to have LS units with a good low frequency response, this can be a very irritating problem. My practice, in the past, has been to choose the LF turn-over point at 30-32Hz, on the grounds that, with a  $-20\text{dB}$  per octave filter slope, this should adequately deal with the rumble components in the 5-8Hz region. Well, I suppose it would, if this is where they were. Unfortunately, experience shows that the really irritating LF noises are often in the 20-25Hz region, and a turn-over frequency of around 50Hz is really needed to get rid of them.

So, where one has this nuisance, it is, in reality, much better to be without it than to try to hold on to such signals as may occur in the half octave between 32 and 50Hz.

The filter block employed is the bootstrap filter circuit shown in Fig. 19 of part 4 of this series, and the frequency response given by the circuit of Fig. 8 is shown in Fig. 9. Again, an LF353 dual op-

amp is used to implement this stage, and, as before, a push-button cancel switch is wired to bypass it when better quality programme material is available.

## The Headphone Amp

If the preamp is a separate unit from the power amp, it is a very useful thing to have a small headphone amp capable of driving a couple of pairs of phones, within the preamp box. However, if this amplifier is to be an accurate monitor of the signal delivered to the power amp and if, in the sort of architecture proposed for this unit, in many cases the signal from the auxiliary units will be routed directly to the power amplifier, the standard of accuracy and quality of the headphone amp must, if anything, be higher than that for the power amp itself.

Fortunately, the headphone amp has a much easier job to do, in that neither the output power requirements nor the load characteristics are so severe, since headphones typically have a load impedance of 100-2000 ohms, and only require 1-2V max RMS, for normal output. There are of course electrostatics, which may demand 5-10 watts, at loads down to a few

ohms, but these are best driven from the power amp anyway, and the '8 ohm' headphones, will require a very low drive voltage anyway.

Since only a low power output is required, a class-A stage is perfectly feasible. Because only smallish output transistors are needed, 10MHz  $F_t$  devices are easily found, and, in any case, class-A operation makes the HF response good. The only other thoughts which commend themselves are that the design should be completely symmetrical, and direct coupled to the output, and that where NFB bypass capacitors of electrolytic type are used these should have a polarising voltage across them. It will also help sound quality if the amplifier has few stages, using discrete components, and no slew-rate limiting internal HF roll-off components are needed.

A design which meets these requirements, and gives an excellent sound quality, is shown in Fig. 10, with a suitable PCB layout in Fig. 11.

Since I haven't analysed this type of circuit earlier in the 'Audio Design' series, I will explain how it works, and how the circuit component values are worked out.

The basic amplifier system is as shown in the very simplified layout of Fig. 12. In this, a pair of push-pull input transistors, Q1 and Q2, drive a push-pull pair of output transistors, Q5 and Q6. Negative feedback is taken from the output point to the emitters of Q1 and Q2, and the load is connected between the joined collectors of Q5 and Q6 and the 0V line. For adequate class A operation the output transistors should pass, say, 100mA each. With a  $\pm 15\text{V}$  supply, this would mean 1.5 watts dissipation, so a smallish heatsink, perhaps 1.5" square, will be needed

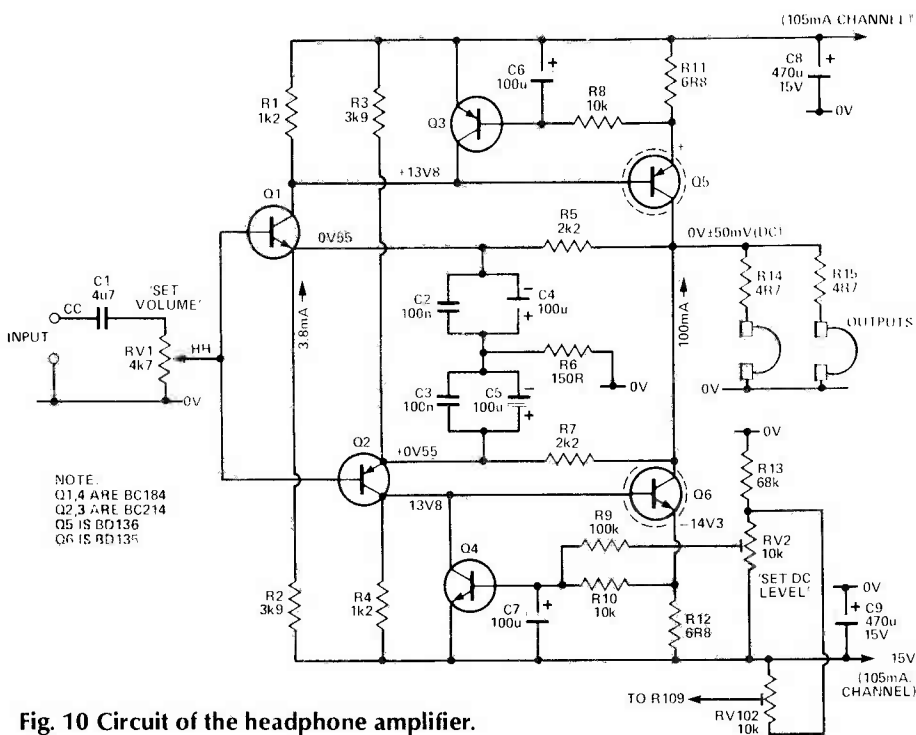


Fig. 10 Circuit of the headphone amplifier.

for each.

If the output transistors have a minimum current gain of 50, then each may require a maximum current input to their bases of 2mA. In order to provide this, with a bit to spare, the input transistors, Q1 and Q2 should normally pass about 4mA. If these have a current gain of 150, their base currents will be  $.004/150 = 26.7\mu\text{A}$ , which gives an input impedance of about 19k. The input gain control (and since this has to provide a 'balance' feature too, this should be the twin concentric spindle type) must therefore be a good bit less than this: a value of 4k7 will be fine. Unfortunately, some of the aux

input signal sources will have too high an output impedance to be able to drive this. It is therefore necessary that the input switching (Fig. 1) shall be organised so that the input buffer (incorporated to generate a low source impedance for the rumble filter and the tone control stages) is used also as the headphone amp input buffer, where otherwise a 'straight through' signal path would have been used. (A 3-head recorder system will normally have a 'line' output impedance (600 ohms) so this can drive the headphone amp without problems.)

Returning to the headphone amp circuit, we must now provide

a source of emitter current for Q1 and Q2, and a means of controlling the current through Q5 and Q6. Looking now at the full circuit diagram of Fig. 10, the emitter current for Q1/Q2 is derived from the  $\pm 15$  volt lines through R2 and R3. For a 14.5V drop and 4mA flow, this would require a resistor value of 3625 ohms. The nearest preferred value is 3k9, which will pass a current of 3.7mA, though some 250uA will also flow through R6 and R8.

Looking now at Q5, (the circuit operation for Q6 is the same), a small resistor (6R8 ohms) in its emitter circuit senses the current flow. If this is too high, a forward bias is applied to the DC amplifier transistor Q3, through R11, (C5 removes all audio signals from this point), which will cause Q3 to conduct and steal drive current from Q5 base, holding the collector currents of Q5 (and Q6 for which the operation is identical) to the chosen average value.

Negative feedback is applied from the outputs of Q5 and Q6 to the emitters of Q1 and Q2. This gives a measure of DC output voltage control, but this can be fine-trimmed by R9, R10 and R12, which operate to adjust the collector current of Q6 relative to Q5. A

## PARTS LIST — HEADPHONE AMP

|   |   |
|---|---|
| <b>RESISTORS</b> (all 2% 0.4W metal film)       |   |
| R1,4,101,104                                    | 1k2   |
| R2,3,102,103                                    | 3k9   |
| R5,7,105,107                                    | 2k2   |
| R6,106  | 150R  |
| R8,10,108,110                                   | 10k   |
| R9,109  | 100k  |
| R11,12,111,112                                  | 6R8   |
| R13   | 68k   |
| R14,15,114,115                                  | 4R7   |
| RV1   | 2k2 twin concentric stereo log pot          |
| RV2,102   | 10k lin preset, horizontal                  |
| <b>CAPACITORS</b>                               |   |
| C1,101  | 4u7 non-polarised                           |
| C2,3,102,103                                    | 100n polycarbonate                          |
| C4,5,6,7,104,105,106,107                        | 100u 6V3 low ESR electrolytic, PCB mounting |
| C8,9  | 470u 16V electrolytic                       |
| <b>SEMICONDUCTORS</b>                           |   |
| Q1,4,101,104                                    | BC184                                       |
| Q2,3,102,103                                    | BC214                                       |
| Q5,105  | BD136 or BD538*                             |
| Q6,106  | BD135 or BD537*                             |
| <b>MISCELLANEOUS</b>                            |   |
| PCB, wire, etc                                  |   |
| * BD538 and BD537 should only be used together. |   |

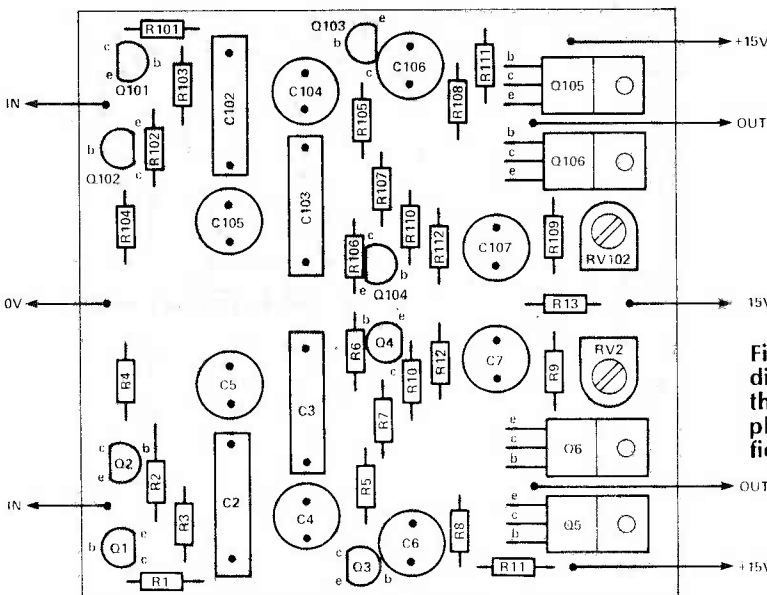


Fig. 11 Overlay diagram for the headphone amplifier.



# PROJECT: Audio Design

DC output level of  $0V \pm 50mV$  is adequate. Because the bases of Q1/Q2 are joined together, their emitters will sit at  $-0.55V$  and  $+0.55V$  respectively, which provides a standing  $0.55V$  potential across C1/C2 and C3/C4. C3/C4 should be low ESR aluminium electrolytics bypassed by C1/C2 polypropylene or polycarbonate

100nF types.

On typical headphone load impedances, the output THD is substantially that of the input signal, as is the transient response.

## Power supplies

These are quite straightforward, and use a 15-0-15V toroidal transformer, in the interests of low hum

field, a bridge rectifier, and two pairs of 15V IC voltage stabilisers. Low equivalent series resistance electrolytic capacitors are used to bypass the output DC lines to the 0V rail, and similar capacitors are used as bypass elements at the supply line connections to the pre-amp circuit modules. A  $\pm 5V$  take-off point, from another pair of stabilisers is employed, optionally, to power a MC head amp module.

In the next part of this series, I will describe the power amp, its power supplies, and the protection circuits.

## PARTS LIST — PSU

| CAPACITORS                               |  |
|--|--|
| C1,2                                     | 2000 $\mu$ 25V tubular electrolytic                    |
| C3,5,7,9                                 | 220n   |
| C4,6,8,10                                | 470 $\mu$ 16V electrolytic, PCB mounting               |
| C11,13*                                  | 100n   |
| C12,14*                                  | 100 $\mu$ 10V electrolytic, PCB mounting               |
| SEMICONDUCTORS                           |  |
| IC1,2                                    | 7815   |
| IC3,4                                    | 7915   |
| IC5*                                     | 7805   |
| IC6*                                     | 7905   |
| MISCELLANEOUS                            |  |
| T1                                       | 15-0-15V 10VA mains transformer, toroidal PCB mounting |
| FS1                                      | 100mA fuse + panel-mounting holder                     |
| SW13                                     | double-pole mains switch to suit                       |
| PCB, wire, etc.                          |  |
| * = not needed if M/C head amp not used. |  |


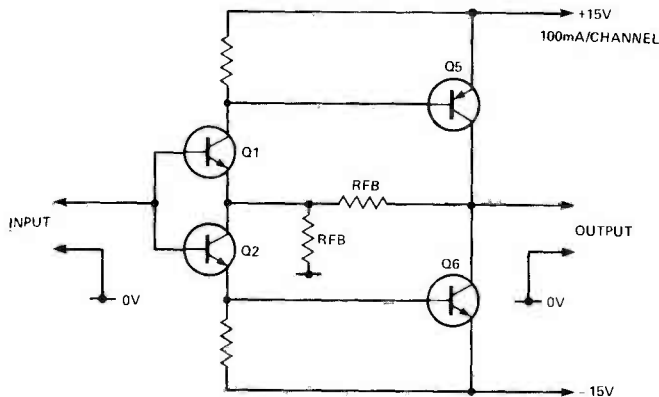



Fig. 12 (left) Simplified headphone amp.


Fig. 13 (below) PSU circuit.

Fig. 14 (bottom) PSU overlay.

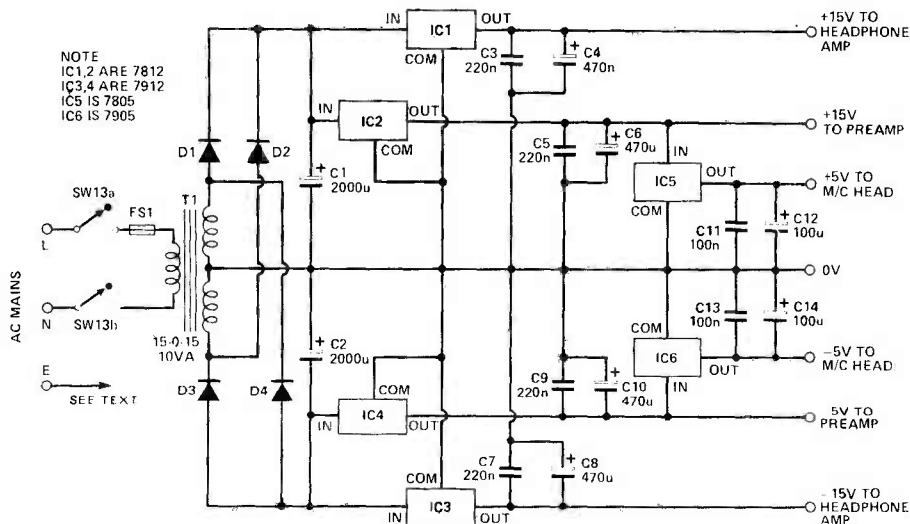

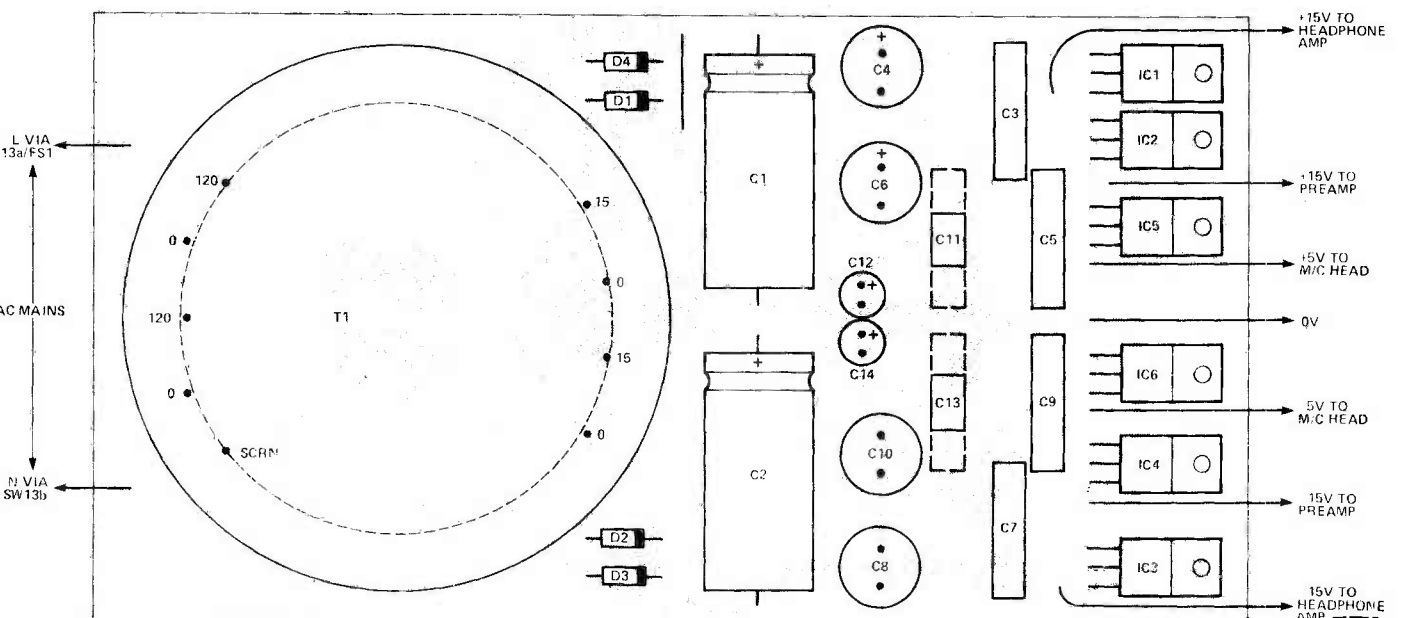NOTE  
IC1,2 ARE 7812  
IC3,4 ARE 7912  
IC5 IS 7805  
IC6 IS 7905



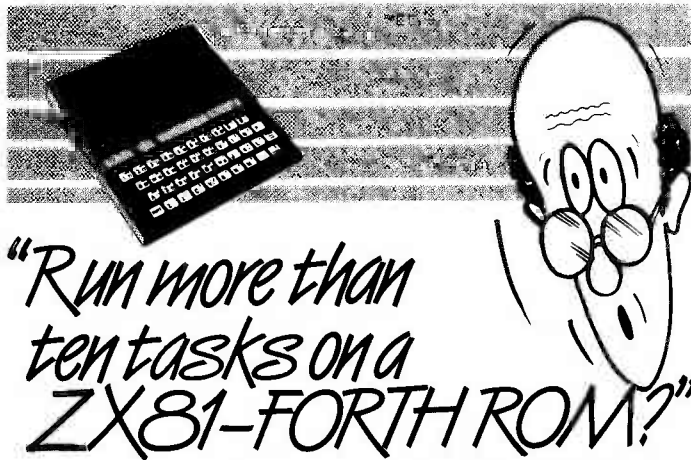

**"Run more than ten tasks on a ZX81-FORTH ROM?"**

Sure! More than 10 tasks simultaneously and, in some cases, up to 300 times faster! That's what replacing the basic ROM with the new FORTH does for the ZX81 — and more!

The brains behind the breakthrough belong to David Husband, and he's building Skywave Software on the strength of it. Already orders are flooding in and it's easy to see why.

The ZX81-FORTH ROM gives you a totally new system. In addition to multi-tasking and split screen window capability, you can also edit a program while three or four others are executing, schedule tasks to run from 50 times a second to once a year, and with a further modification switch between FORTH and BASIC whenever you like.

The ZX81-FORTH ROM gives you a normal keyboard with a 64 character buffer and repeat, it supports the 16k, 32k, 64k RAM packs, it is fig-FORTH compatible and it supports the ZX printer.

The price, too, is almost unbelievable. As a "fit it yourself Eprom", complete with manual, it's just £25 + VAT. Add £2 p&p UK (£5 Europe, £10 outside Europe) and send your order to the address below.



David Husband  
73 Curzon Road, Bournemouth,  
BH1 4PW, ENGLAND  
Tel: (0202) 302385.  
International +44 202 302385.

ETI/6

**TRANSEL DOT MATRIX PRINTER Compact**  
Serial interface 230V. With info. £65 ea  
TELETYPE ASR33 — DATA DYNAMIC (Printer,  
Keyboard, Punch & Reader) RS232 £75  
RACAL MODEM type 220/24 £100  
TRT SEMATRON'S 1022 Modem £20  
CREED TELEPRINTER75. Very Good Condition. £25  
9" MONITOR Cased Non-Standard With info. £20 ea  
12" MONITOR Cased Non-Standard With info. £15 ea  
AZTEC 20" Black & White MONITOR Videopin. £50 ea  
TV Style 20" MONITOR Black & White. Video in. £30 ea  
GENERAL ELECTRIC TERMINET Printer with  
Keyboard Upper/Lower case. £125 ea  
ICL Version of above. No keyboard. £95 ea  
QWERTY KEYBOARD Push to make. Uncased. £15 ea  
P&P £4  
CARRIAGE ALL UNITS £7.

**STEPPING MOTORS**

Type 1. 200 Steps 4 Phase (5 wire) 12/24V 25 oz inch.  
2 1/2" dia. £15  
Type 2. 6. 12 Steps 3 Phase 12/24V. 1 1/2" dia. £2 ea  
5 1/2"  
Type 3. 24 Steps 4 wire 5V 3.3A 0-250rpm 0-200PPs  
2 1/4" dia. £10 ea  
Type 4. 200 Steps 120V (3 wire) 25 oz inch.  
2 1/2" dia. £4 ea

**MOTORS**

SYNCHRONOUS 2 Phase 9V AC. 375rpm Cap start  
With DC steps — 8 steps per rev. £1 ea  
GEARED 117/234V 50HZ 4" dia. £5 ea P&P £4  
GEARED 115/230V 1 RPM 2 1/2" dia. £4 ea P&P £2  
MOTOR 12V DC 3" dia. £3.50 ea P&P £3

**TRANSFORMERS**

TOROIDAL 135-0-13.5V 8VA £1.50 ea 10 off £12  
TOROIDAL 0-12V. 0-12V. 10VA per winding. £4 ea  
10 off £35 P&P £2  
AUTO 240V Input 115V 1A. £1.25 ea  
Sub-Min 120-12V 4VA. 75p ea. 10 off £5 P&P £2  
Printed Circuit Mounting 120/240V. Input Sec.  
15V 0.4A twice. £1.50 ea  
Chassis Mounting 120/240V.  
9V0.33A twice — £1.50 ea; 20V0.15A twice — £1.50 ea;  
6V0.5A twice — £1.50 ea; 12V0.96A twice — £1.50 ea;  
7.5V 3.34A twice — £3 ea.  
Sub-Min PULSE TRANSFORMER Centre tapped.  
Suitable Thyristor triggering — 20p ea. 10 off £1.80.  
Many other transformers available — please enquire.

**CAPACITORS**

Electrolytic 15,000mfd 25mfd 25V 20pea 10 off £1.80  
Sprague Compulytic 18,000 mfd 10V Screw  
terminal. £1 ea  
Electrolytic 900mfd 100V Screw  
terminal. 50p ea. 10 off £4

**OSCILLOSCOPES**

TELEQUIPMENT D75. Dual Trace 50MHZ  
Delay Sweep. £400  
SE LABS SIM111 Dual Trace 20MHZ. £200  
TEKTRONIX 585A with 82 Plug-in. Dual Trace  
85MHZ Dual TB Delay Sweep. £200  
TEKTRONIX 545B with CA Plug-in. 24MHZ Dual Trace  
Dual TB. £160  
Ex-Ministry CT436 Dual Beam 6MHZ. £60  
SE LABS STROBE S88. £125  
METROHM BATTERY MEGGER 500V. £40  
ADVANCE Dual Slab DC Power Supply PP3. 0-30V.  
0-1A. Iwice. Metered. £50  
AVO TRANSISTOR TESTER TT169 With leads. £20  
P&P £2.  
CARRIAGE ALL UNITS £7  
RANGE OF NEW SCOPES AVAILABLE —  
Please enquire

Tantalum Bead 0.1mfd 35V. 10 off £1. 100 off £7.50  
De-Coupling — 0.4725V. 0.005 100V; 0.47 12V.  
0.001 200V/133pF. 10 off 30p. 100 off £2

**SWITCHES**



ILLUMINATED ROCKER 2 pole 250V 8A.  
Orange. 50p ea. 10 off £1  
ROCKER 2 pole c/o — 12p each. 10 off £1.80  
TOGGLE Centre off DPDT. 20p each 10 off £1.80  
SLOTTED OPTO SWITCH with data 50p each 10 off £4  
MINI MICRO SWITCH V3-Button. 30pea 10 off £2.50  
I.C. SOCKETS  
10 pin-10p; 22 pin-15p; 14 pin-8p 100 off £6  
36 pin-15p; 40 pin-25p; 16 pin-8p 100 off £6  
RIBBON CABLE  
10 way-50p per metre. 10 metres £4  
14 way-75p per metre. 10 metres £6  
PCB KEYBOARD PAD 19 Push Contacts. 0-9-A-F plus 3  
optional — £1.50 ea. 10 off £12  
KEYBOARD PAD 12 Alma Reed Switches Push to make  
0-9-A Blank. £4 ea. 5 off £15 P&P £3  
TOKIN NOISE FILTER VG215FU. 250VAC 15A  
50/60 HZ With fixing bracket. £2 each  
BLACK RIBBONS for Teletypes/  
Teletprinters. 75p ea 6 off £4  
I.T. LOUDSPEAKER 2 1/2" 50ohm  
0.2W. 75p ea 10 off £6.50  
FERRANTI PHOTOCELL type MS15. 50p ea 10 off £4  
VUMETER Scaled 0-5 Size 1 1/2" x 1/2". 50p ea 10 off £4  
I.E.C. MAINS LEAD 2 metre Heavy duty 50p ea 10 off £5  
MICROPHONE/EARPIECE INSERTS 75p ea 10 off £6  
CINCH CONNECTOR STRIP 12way. Screw  
connections. 35p ea 10 off £3.  
CABLE TIES White 9cm; Black 12cm. 50 for 50p

**EXECUTIVE TELEPHONES — PUSH BUTTON**

Many functions including 10 number memory; repeat  
dialing etc. Will connect to GPO system. Brand New.  
£25 each P&P £4.

**SAMPLE OF STOCK — SAE or TELEPHONE for LISTS** Please check availability before ordering. Min order  
of Goods £4. Min P&P £1.50. VAT at 15% MUST be added to TOTAL of Goods & Packaging.

**STEWART OF READING**  
110 WYKEHAM ROAD, READING, BERKS RG5 1PL.  
Tel: 0734 68041  
Callers welcome 9am-5.30pm Monday to Saturday inclusive





**MICROTANIC COMPUTER SYSTEMS**

**MICROTAN 65**  
*NO OTHER COMPUTER IS AS PERSONAL!*

For less than £60 you can start building your own Computer that truly suits your needs and, of course, eventually far more superior to any Computer available off-the-shelf

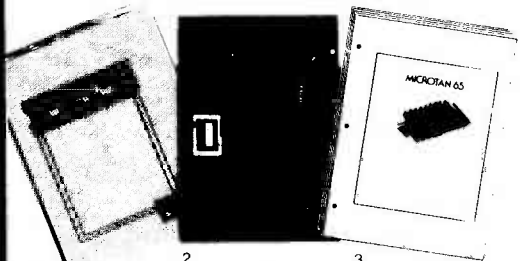MICROTAN 65 comes in kit form, complete with manual, full instructions, board with components, (kit form or fully built) our full back-up service, and your own Microtan World Magazine available on subscription.



**BUILD AS FAST OR SLOW AS YOU LIKE!**

**FLEXIBLE & EXPANDABLE SYSTEM — 1K to 256K!**

Just look at the options:

- |                      |                               |
|----------------------|-------------------------------|
| 1 DISK CONTROLLER    | 8 INDUSTRIAL CONTROLLER BOARD |
| 2 REAL TIME CLOCK    | 9 MASS EPROM STORAGE BOARD    |
| 3 EPROM PROG CARD    | 10 HIGH RES. GRAPHICS 256x256 |
| 4 SOUND BOARD        | 11 PRINTER FACE BOARD         |
| 5 SERIAL I/O BOARD   | 12 40K RAM BOARD              |
| 6 PARALLEL I/O BOARD |                               |
| 7 ASCII KEYBOARD     |                               |

Microtan World Magazine



Full range of hardware and software products available

**ACE TRACE**

**NEW PRODUCT**



**FOR DRAGON 6809**

**Machine Language Monitor-Disassembler**  
**Line Editor & Trace Facilities**

This unique piece of software combines all the tools required to write and debug machine code programmes. It is written in position independent code and hence can reside anywhere in the Dragon's memory map from \$0600 to \$7FFF. It enables you to TRACE through both RAM and ROM, simulating the 6809 in slow motion displaying the CPU's every move as it happens. Also included is a powerful Monitor Disassembler Line Editor and standard 6809 Assembler supporting all Motorola mnemonics.

**CASSETTE BASED £14.95 Plus 60p P&P**

**Microtan Computer Systems Ltd**  
Showroom: 16 Upland Road, Dulwich, London SE22

Tel: 01-693 1137 & 01-299 1419

**DEALER ENQUIRIES WELCOME**

# THE WORLD OF MICROTAN-65

**Mike Bedford concludes his survey of what's available for this computer-freak's machine.**

## TANGERINE USERS' GROUP

To all intents and purposes, Tangerine Users' Group is no more; outstanding creditors can contact the owner, Bob Green, at 1 Marlborough Drive, Worle, Avon. We strongly advise that no one should send TUG any further money. A former director of the company, Colin Nowell, would very much like to hear from those TUG software writers he has not already managed to contact, and from anyone who ordered, but did not receive, a TUG speech synthesiser board. Colin is prepared to help out anyone having any software or hardware problems; his number is 0934 510089, but please be considerate, this is a private number.

All is not lost, though, as regards TUG boards for the Microtan, because Microtanic Computer Systems Ltd, whom we talked of last month, intend to take over most of them. Details of the boards which are set to reappear are given below; however, at the time of writing, these are not yet back on the market, and it would be particularly worthwhile contacting MCS for further details. We have given the old TUG price, but this is **for guidance only**: MCS are having to re-negotiate all the agreements with suppliers and designers, and the prices may well turn out to be very different.

Finally, although MCS are a separate company from TUG, and therefore have no financial responsibility at all to TUG's members and creditors, they have said that they will attempt to deal sympathetically and helpfully with them.

## Video 80/82

Although this product is essentially a high resolution graphics board, it is quite different in concept to the high resolution graphics card offered by Microtanic. The first difference is the resolution, this being DIL switch selectable to either the 256 x 256 offered by the MCS product or alternatively 256 x 512. This is not the most fundamental difference however — what makes this board totally different is that it is intelligent, having an on-board 6502A processor running at 2MHz. Used in conjunction with VBUG, the on-board firmware package residing in a 2732 EPROM, this processor removes much of the graphics software overhead from the main Microtan-65 processor.

The following functions are provided by VBUG: clear screen, set point, reset point, invert point, test point, draw vector, undraw vector, invert vector, cursor control, scrolling region control and alphanumeric characters in five widths with underlining, reverse video, superscript and subscript. It will be noted that these commands include the handling of text and since if the 256 x 512 option is selected the format would be 25 lines of 80 characters, this board makes an attractive alternative to the standard Microtan-65 display even without considering graphics.

One inevitable outcome of writing characters on a bit-mapped screen, however, is that scrolling of text is slower than on a dedicated text VDU. To simplify text handling, TUG also sells a TANBUG replacement called TUGBUG, one of the facilities of which is text output routine to the Video 80/82 board.

The board has 16K of 6116 RAM of which only 8K need be fitted for the 256 x 256 resolution. Since the board has its own processor with a memory map where this RAM resides, it does not take a large bite out of the Microtan memory map — in actual fact it only occupies two bytes in the I/O area through which all communication takes place.

There is no modulator on board so if this card is to be used with a monitor, the video signal will require patching through to the modulator on Microtan-65. As was suggested with the MCS high resolution card, three cards could be used in conjunction with a colour monitor to give a colour display.

**Prices:** board + VBUG V1.1 + manual — £59.25 + VAT; assembled excluding RAM — £137.50 + VAT; assembled including 8K RAM — £157.50 + VAT; assembled including 16K RAM — £172.50 + VAT.

## Programmable Graphics Module

This card provides yet another option to obtain high resolution graphics in a Microtan system. This is undoubtedly the least expensive method and although this means it is also the least versatile, it can give effective results in many applications. The approach here is not to replace totally the display circuitry on Microtan-65 but to supplement it by an extra 64 characters which may be

defined under program control to any shape within the 8 x 16 character cell. This gives an effective resolution 256 x 256.

Although a little thought would reveal that this approach does not allow any possible high-resolution pattern to be drawn within the 256 x 256 framework, many applications do lend themselves to this method and animated graphics are in fact easier to implement on this board than on a Video 80/82 or Microtan high resolution graphics card. In addition to the normal system connection via TANBUS, the PGM also requires a few connections to Microtan-65.

**Price:** 19.50 + VAT

## Combo And EPROM Storage Card

The amount of EPROM space possible within the memory-map of the Microtan system can be a severe limitation to those users with a non-disc based system. Such users could well require access to languages other than BASIC, such as assemblers, word processors, etc, more quickly than loading from cassette would allow. Storing this software in EPROM is the obvious answer but all that is left in the way of EPROM space after installing XBUG and BASIC is 2K.

The purpose of the EPROM storage card (ESC) is to overcome this limitation by providing space for sixteen 2716s or 2732s — a maximum of 64K EPROM space. This space does not reside within the main memory map of Microtan, but instead each ESC has its own memory map, communicating with the system via PIAs and hence only occupying a few bytes within Microtan's I/O area.

To use software stored on the ESC, it is first loaded into RAM memory on TANEX or one of the expansion RAM cards in a similar way to loading from cassette or disc but much quicker. Routines to facilitate this downloading are provided in TUGBUG. The COMBO board is an extension to the ESC concept in which battery backed up 6116 RAMs may be used in place of the 2716s or 2732s hence giving read/write access to 32K with data retention on power down. Recently the 64K ESC has been discontinued in favour of the COMBO which of course may be used as such. In addition a 128K ESC is on the cards (sorry!) but as yet only in prototype form.

**Price:** COMBO — £20.75 + VAT; assembled — £69.25 + VAT.

## 64K Dynamic RAM Card

To some extent, one expansion RAM card is very much the same as another and this board's title describes exactly what it does; however a few comments are still appropriate. Unlike TANRAM, which fills in those portions of Microtan's memory map which are not already filled with RAM and EPROM on Microtan-65 and TANEX, this memory card overlays the complete memory map of the system. To avoid the possibility that would therefore exist of having two devices being accessed at the same address, this board has DIL switches which allow the memory to be enabled in 2K segments, hence allowing those blocks already used in the system to be disabled. This allows a large degree of flexibility in that a user may decide, for example, to remove all EPROMs (except TANBUG/TUGBUG) from TANEX, overlaying this area with RAM on the 64K Dynamic RAM Card and calling software into this memory from an ESC or COMBO board as required. The devices used are 4146 64K x 1 dynamic RAMs.

**Price:** £33.00 + VAT.

## CP/M Card

This card has not yet been released and is mentioned here as a future product. The card however has been running for some time in a prototype form so it shouldn't be too long in making an appearance. Not much preliminary information is available as yet except for the fact that this card works on the lines of similar products for some other 6502 computers, utilising a Z80 processor to give a dual processor system which can run the industry standard disc operating system CP/M.

## RALPH ALLEN ENGINEERING CO.

This company first became involved in Microtan a number of years ago when they marketed an interface between this machine and the IBM I/O typewriter. Recently, however the company has released an EPROM to RAM conversion card and other TANBUS compatible cards are under development. The address is Forncett End, Norwich, NR16 1HT.

## EPROM To RAM Conversion Card

The purpose of this board is to allow the EPROM address space on the TANEX board to be replaced by RAM hence giving the system a full 64K of RAM (less with I/O space and boot EPROM) when used in conjunction with TANRAM. This will be particularly useful to those wishing to use a disc operating system or those who have a library of software on EPROM storage cards which requires to be loaded into RAM. The method of using the card is to remove some or all of the TANEX EPROMs, configure the conversion card to overlay those address areas which are thereby released and plug the card into the system rack. The 14K of available RAM on board may be enabled in blocks of 2K. This card will be of particular interest to those already having a TANRAM card, for those not in this situation it may be a more economic solution to go straight for the 64K dynamic RAM card.

**Price:** bare PCB — £22.00; built (less 6116 RAMs and buffers) — £46.28.



ETI

ETI JUNE 1984



# JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail-Order Prices.

## EC50 Mains Electronic Iron. £26.19




Features spike-free, solid state

proportional electronic temperature control inside the handle. Adjustable 280° to 400°C. Burn-proof 3-wire mains lead. Fitted 3.2mm Long Life bit. 1.6, 2.4 and 4.7mm available. 240v a.c.
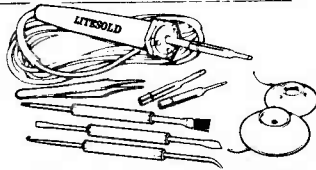
## SK18 Soldering Kit. £15.24

Build or repair any electronic project. LC18 240v 18w iron with 3.2, 2.4, and 1.6mm bits. Pack of 18 swg flux-cored 60/40 solder. Tweezers. 3 soldering aids. Reel of De-Solder braid. In PVC presentation wallet.




## ADAMIN Miniature Iron. £5.97

Possibly smallest mains iron in the world. Ideal for fine work. Slim

nylon handle with finger grip. Interchangeable bits available 1.2, 1.6, 2.4, 3.4 and 4.7mm. Fitted with 2.4mm. 240v 12w (12v available). Presentation wallet.

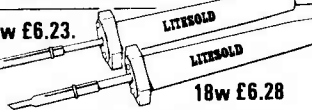
## 'L' Series Lightweight Irons. 12w £6.23.

High efficiency irons for all electronic hobby work. Non-roll handles with finger guards. Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12



model, 12w, 2.4mm bit. LC 18 Model, 18w, 3.2mm bit. 240v Std - 12v available. Presentation wallet.

## Soldering Iron Stands. £5.11

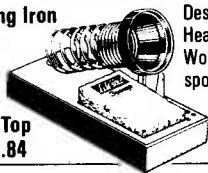

Designed specially for LITESOLD irons. Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits.

No 5 stand for EC50 iron No 4 stand for ADAMIN miniature Iron No 3 stand for LA12 and LC18 Irons All same price

## Spring/Top only. £1.84

## Replacement Bits

For all above irons. Non-stick designs, machined from special copper alloy, with Inconel retaining rings. Two types - Chromium plated with copper face (for economy and ease of use) and Iron plated with

Pre-tinned face (Long Life). State tip size, iron and type.

|                    | Copper | L/L   |
|--------------------|--------|-------|
| EC50               | -      | £1.58 |
| Adamin 12 and LA12 | 92p    | £1.56 |
| LC18               | £1.01  | £1.70 |

## BRADEWICK De-Solder Braid.



£1.05 per Reel

For simple, safe and effective de-soldering of all types of joint, using a standard soldering iron. Handy colour-coded packs of 1.5 metres in 3 widths: Yellow - 1.5mm, Green - 2mm, Blue - 3mm.


## De-Solder Pumps. £6.19

High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy



thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.

## Miniature Tool Sets

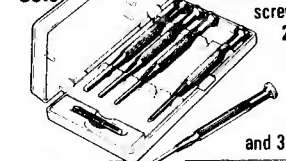

Top quality Japanese metric hardened and tempered tools. Swivel-top chrome plated brass handles. Fitted plastic cases. 113 set - 6 miniature screwdrivers 0.9 to 3.5mm £2.70

227 set 5 socket spanners 3 to 5mm £2.80

305 set 2 crosspoint and 3 hex wrenches 1.5 to 2.5mm £2.70

228 set 20 piece combination: 5 open, 5 sct spanners, 2 crosspoint, 3 hex and 3 plain drivers, scriber, handle/holder £4.83

**Microcutters. £3.21** Light weight hardened and precision ground. Flush cutting. Screw joint, return spring, cushion-grip handles. Safety wire-retaining clip.



## Soldering Aids.



Set of 3 £3.63  
Scraper/Knife, Hook/Probe, Brush/Fork. 3 useful double-ended aids to soldering/desoldering/assembly. In plastic wallet.

## Solder. £0.90

Top grade resin flux cored 60/40 wire, 18 swg, in handy plastic dispenser. Approximately 3 metres (26gm).



## ADAMIN Electric Stylus. £15.04

Writes like a ballpoint in Gold, Silver, Copper or 6 colours, on card, plastics, leather etc. Personalise wallets, bags, albums, books, models... Operates at 4.5v from its own plug/transformer - totally safe. Supplied with coloured foils.

Prices include p&p and VAT. Send order with Cheque/PO. Ring for Access/Visa sales, or ask for order forms

**LIGHT SOLDERING DEVELOPMENTS LTD. DEPT. ET**  
97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 01 689 0574

# SECURITY

Install your own system and save using built and tested modules


## A COMPLETE INTRUDER ALARM

EASILY ASSEMBLED ULTRASONIC UNIT CK 5063

Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft.
- Built-in entrance & exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865, Key Switch 3901, 3" Speaker 3515

only £37.00 + V.A.T.

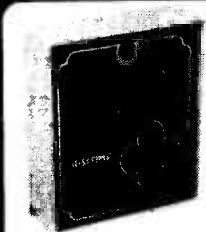

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90dbs of sound, or even 110dbs with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm Order as CK 5063

## DIGITAL ULTRASONIC DETECTOR US 5063



only £13.95 + V.A.T. **NEW**

- 3 levels of discrimination against false alarms
  - Crystal control for greater stability
  - Adjustable range up to 25ft.
  - Built-in delays
  - 12V operation
- This advanced new module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions. The module has a built-in exit delay and timed alarm period, together with a selectable entrance delay, plus many more outstanding features.

## ALARM CONTROL UNIT CA 1250



Price £19.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

## ULTRASONIC MODULE US 4012



£10.95 + V.A.T.

- Adjustable range from 5-25ft.
- This popular low cost ultrasonic detector is already used in a wider range of applications from intruder detectors to automatic light switches and door opening equipment, featuring 2 LED indicators for ease of setting up.

## INFRA-RED SYSTEM IR 1470

only £25.61 + V.A.T.



Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft, operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 80 by 50 by 35mm.

## POWER SUPPLY & RELAY UNIT PS 4012

Provides stabilised 12V output at 85mA and contains a relay with 3 amp contacts. The unit is designed to operate with up to 2 ultrasonic units or 1 infra-red unit IR 1470. Price £4.25 + V.A.T.

## SIREN MODULE SL 157

Produces a loud penetrating sliding tone which, when coupled to a suitable horn speaker, produces S.P.L.'s of 110dbs at 2 metres. Operating from 9-15V. Price £2.95 + V.A.T.

## 5 1/2" HORN SPEAKER HS 588

This weather-proof horn speaker provides extremely high sound pressure levels (110dbs at 2 metres) when used with the CA 1250, PS 1865 or SL 157. Price £4.95 + V.A.T.

## 3-POS. KEY SWITCH 3901

Single pole, 3-pos. key switch intended for use with the CA 1250. Price £3.43 + V.A.T.

Add 15% VAT to all prices  
Add 50p post & packing to all orders.  
Units on demonstration  
Shop hours 9.00 to 5.30 p.m.  
Closed Wednesdays  
Saturday 9.00 to 1.00 p.m.  
SAE with all enquiries  
Order by telephone or post using your credit card

## SIREN & POWER SUPPLY MODULE PSL 1865



only £9.95 + V.A.T. **NEW**

A complete siren and power supply module which is capable of providing sound levels of 110dbs at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

## HARDWARE KIT HW 1250



only £9.50 + V.A.T. **NEW**

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 by 180 by 70mm

## ULTRASONIC MODULE ENCLOSURE




only £2.95 + V.A.T. **NEW**

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063; for US 4012 order SC 4012.

# RISCOMP LIMITED

Dept. ETI 12  
21 Duke Street,  
Princes Risborough,  
Bucks HP17 0AT  
Princes Risborough (084 44) 6326

# EPROM CARD FOR THE ORIC/ATMOS

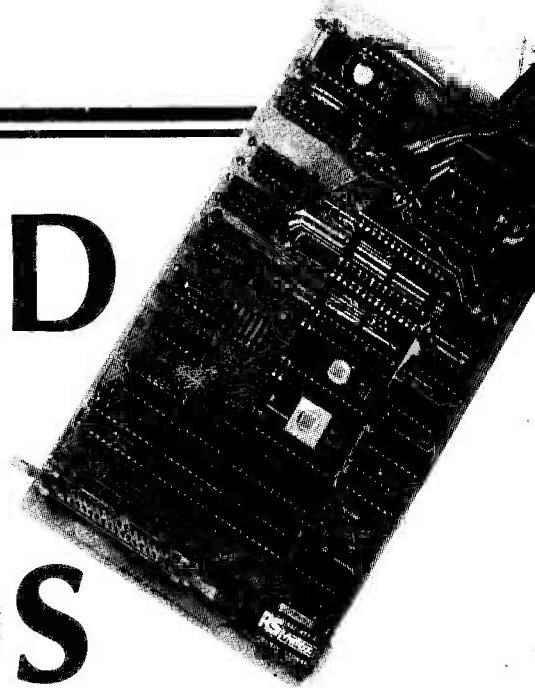

**Phil Walker describes a card that can be used as a way of storing machine code routines, or simply as a computer-controlled EPROM programmer/verifier/duplicator.**

An interesting feature of the Oric-1 and the new Atmos home computers is that they have two extra ways of adding machine code routines to BASIC programs. Most machines offer a `USR` statement which can pass parameters and control to machine code routines and some also have a `CALL` statement or equivalent. The Oric-1 and Atmos machines also sport `!` and `&` which are recognised by the interpreter as extensions to its usual capabilities. On encountering one of these symbols in a program the interpreter transfers control to routines starting at locations in memory previously specified by the program. In addition parameters following the extension symbol are available to the routine. This makes them much more useful than the simple `USR` or `CALL` statements and more like a proper BASIC keyword.

This project is designed to enable the owner of one of these machines to develop machine code routines for graphics, games or other special purposes in non-volatile RAM and at some later date program it into EPROM. Routines already in EPROM may be transferred to the RAM, modified and incorporated into other programs before being put into EPROM. Another feature of this project is that the effective addresses of the EPROM sockets on the board can be modified under program control in 2K blocks. The

effective RAM and programming sockets can also be similarly modified and the functions available in any block can be set up at any time by the use of a memory write operation to one of four locations.

The whole board appears to the computer as a block of memory occupying 8K from 8000h to 9FFFh and four locations BFFCh to BFFFh, the latter being the control locations for the configuration and EPROM programming functions. The main memory block was chosen both from the ease of decoding point of view and to be reasonably out of the way of normal use of the machine. However if hi-res graphics are used on a 48K machine there may be some conflict with the character sets between 9800h and 9FFFh.

## Facilities

This project has been designed with machine code programming in mind but could be used equally well to provide access to blocks of data which are permanently stored in EPROM. It provides all the facilities needed to develop and store routines in association with one of the assembler programs available. A notable feature of the project is that up to four EPROMs can be accommodated on the board each up to 8K x 8. These can be selected in 2K blocks and used directly or copied into the on-board RAM for modification. This can be very useful if, for example, you have a large

machine code program in a 8K x 8 EPROM; you can copy 2K of it into RAM, modify it and run it before programming the whole lot into another EPROM.

Another way to use this project is to build up a library of routines in EPROM, possibly up to 64K in total, and to select any of them at will with the minimum of fuss.

The project is not designed as a straight EPROM copier but it can perform that function too by way of the on-board RAM or the main memory and some simple software. The programming section operates on a one byte at a time basis and from one to 8192 bytes can be programmed into the target device with standard handshake operation. Timing in programming mode is derived from the mains input frequency (beware 60Hz areas!).

The main feature of this project is that the function performed by each 2K block of addresses in the 8K total can be programmed individually to be one of four functions. These can be:—

- a) Read only from any one EPROM socket;
- b) Read from an EPROM socket, write into the RAM;
- c) Read and write to the RAM;
- d) Read EPROM programming socket, program a byte into EPROM in socket.

Thus the RAM can be set to occupy any or all of the 2K slots, any EPROM socket can be enabled in any 2K slot, the RAM

and an EPROM socket can be selected for writing and reading respectively at the same address slot and the EPROM can be programmed at any or all address slots.

All these functions are selected by writing data into control addresses separate from the main address range. There are four of these control addresses, one for each 2K address slot. Each control address responds to four data bits: D7 and D6 control the function to be performed and D1 and D0 select which EPROM socket is to be used (if any). These codes are written into a fast bipolar memory and stored as four words of four bits each. When written, their location in the memory is determined by address bits A1 and A0 but when read for use by the control logic the required word is selected by address bits A12 and A11. It should be noticed that the data input and output terminals of this device are totally separate and are separately and independently controlled.

The use of such a device effectively allows the address-decoding of the board to be reconfigured at will with no hardware changes and a minimum of software intervention. In this circuit, the two data bits used to set the function are decoded with the addition of the R/W,  $\phi 2$  and SEL signals to give eight possible combinations.

These are then combined to give the three main control signals for the EPROM sockets, RAM and programming logic.

The signal to the EPROM sockets is further decoded with the remaining two data outputs from the configuration RAM to select a particular socket. The RAM control signal goes to the RAM via the power fail circuitry. Lastly the programming signal passes to the programming logic where it and the state of the R/W line determine the next course of action.

Whenever the programming function is accessed, the state of the R/W line is sampled at the end of the cycle. If it is high throughout, then the relevant buffers are enabled to allow data to be read from the device in the programming socket. No other action is taken by the logic in this case. If, however, the R/W line is low during an access, then the current address on A0 to A12 and the contents of the data bus are captured in latches and, at the end of the cycle, the low state of the R/W initiates a programming sequence. This then puts the data in the latch into the EPROM at the address stored in the address latch. The logic is arranged such that no computer intervention is required or possible during a programming sequence. The only thing possible is for the computer to read any of the control addresses and set data

bit 7 which will be high during programming and low when it has finished.

The programming section has been designed with the 25XX series of EPROMs in mind but 27XX series devices should be possible with a little modification to the wiring of the socket. Note that only single supply devices are permitted.

When using EPROMs in the non-programming sockets it is necessary to connect the associated links to reflect the type used.

## Construction

The PCB for this project has been made with plated-through holes. Although this costs a little more than the same design without through plating, we feel that this is more than offset by the easier construction and lower possibility of missed links especially underneath IC sockets. From experience with the prototype, we know it takes a very long time to solder all the through-links on both sides of the board and it is easy to miss one or forget to solder a component on both sides where necessary. If you decide to make your own board you will find out what we mean!

The order of construction we recommend for this project would be to start with (through links on your own board then) IC sockets


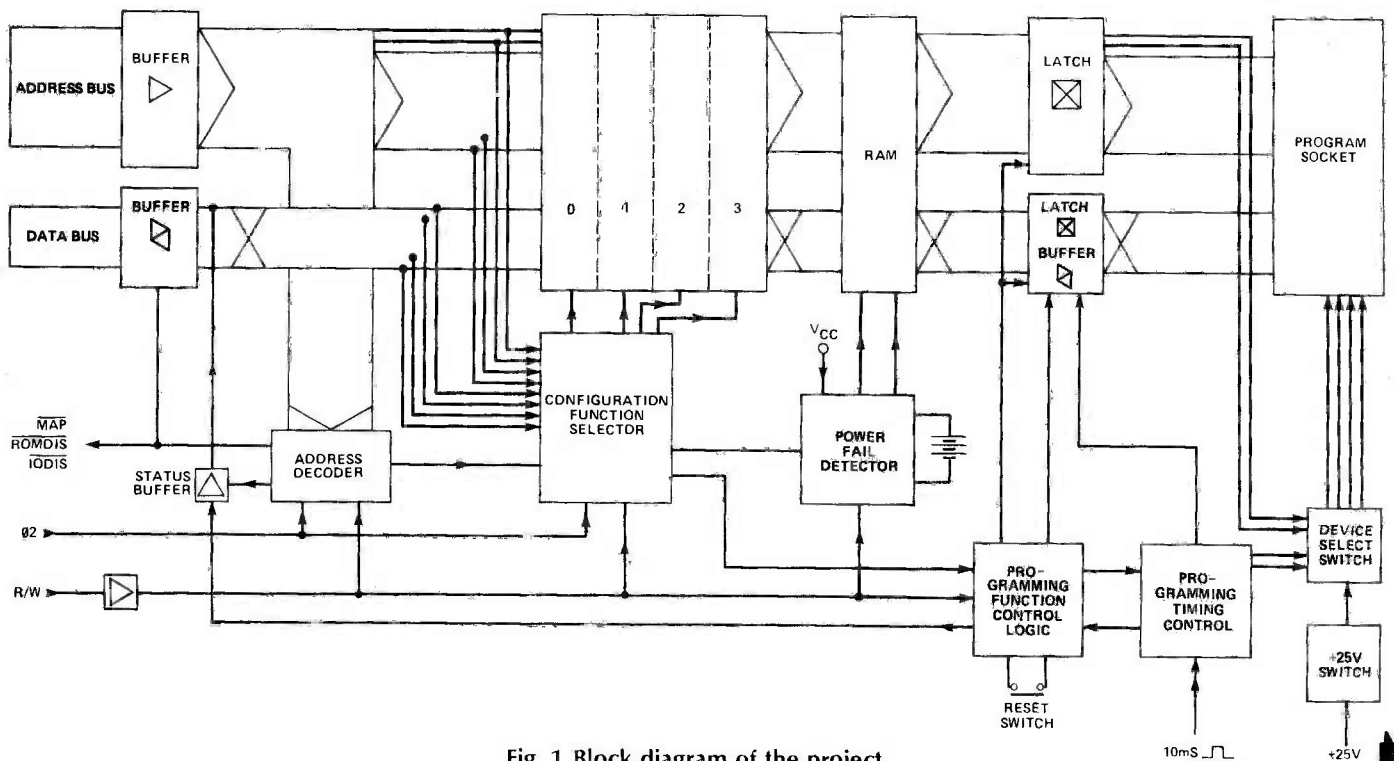


Fig. 1 Block diagram of the project.

# HOW IT WORKS

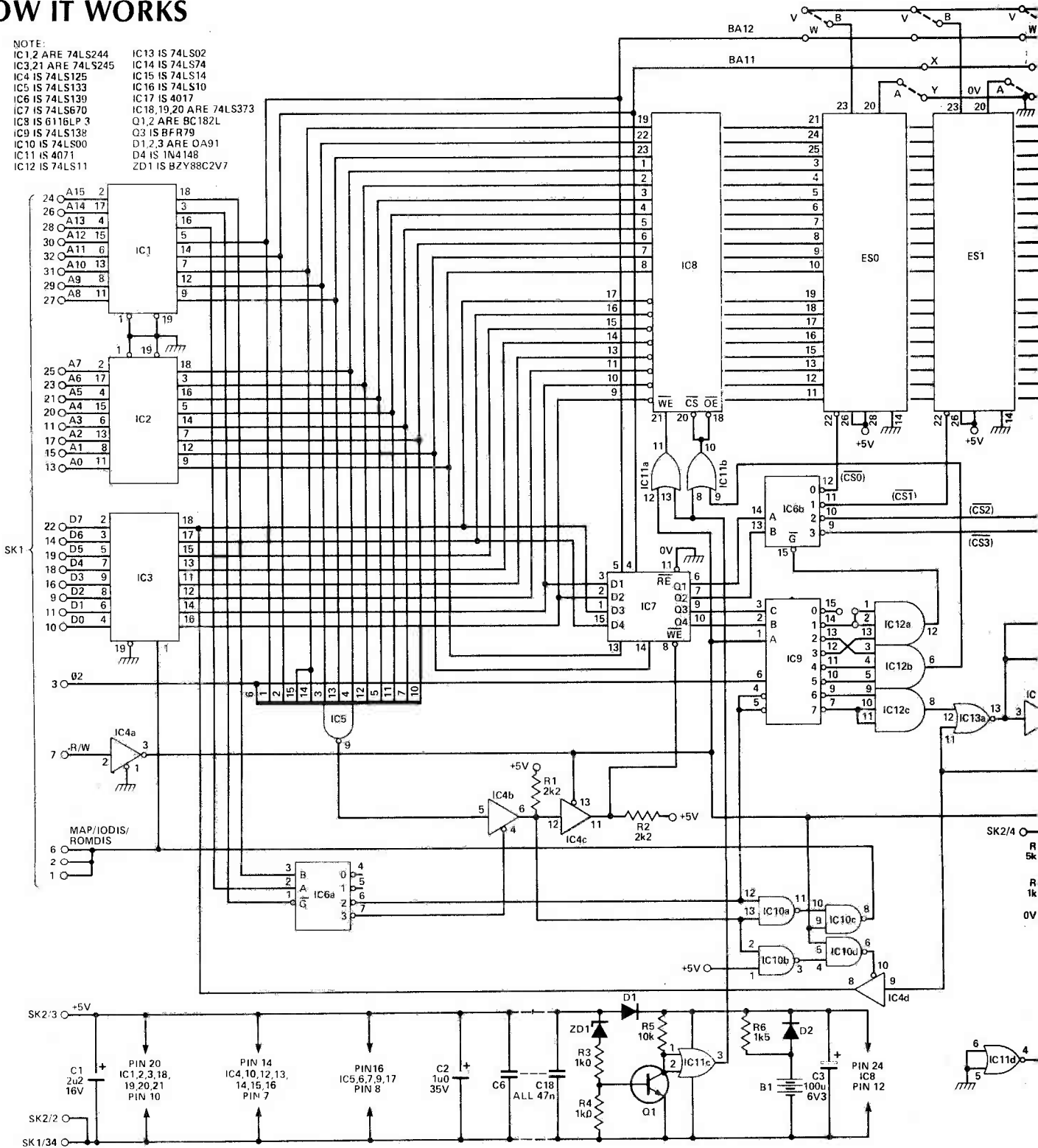**NOTE:**

- IC12 ARE 74LS244
- IC13 IS 74LS02
- IC3,21 ARE 74LS245
- IC14 IS 74LS74
- IC4 IS 74LS125
- IC15 IS 74LS14
- IC5 IS 74LS133
- IC16 IS 74LS10
- IC6 IS 74LS139
- IC17 IS 4017
- IC7 IS 74LS670
- IC18,19,20 ARE 74LS373
- IC9 IS 6116LP 3
- Q1,2 ARE BC182L
- IC9 IS 74LS138
- Q3 IS BFR79
- IC10 IS 74LS00
- D1,2,3 ARE OA91
- IC11 IS 4071
- D4 IS 1N4148
- IC12 IS 74LS11
- ZD1 IS BZY88C2V7



This project divides into two major parts. The first is the memory and its associated control logic while the second is the programming socket and timing control.

All the address and data lines from the ORIC or ATMOS are buffered by IC1,2 and 3. IC3 is a bi-directional buffer which is normally set to drive the board DATA bus rather than back into the computer. Only when a read operation is performed which accesses the on board memory or control function does IC3 drive towards the computer.

The R/W line is buffered by IC4a since there are six TTL inputs driven from this line and it would probably be overloaded. The  $\phi 2$  line is not buffered as it only drives two TTL inputs

and this is usually allowable. The same signal which controls the direction of IC3 also serves to disable the memory and I/O functions in the computer so that no disagreements occur with two devices trying to drive the data bus at the same time.

IC6a decodes the three top address bits to give outputs which are active in the ranges 8000h — 9FFFh and A000h — BFFFh. The first of these is used to activate the memory function while the second is used to enable IC4b. The other input to IC4b comes from IC5 which is a 13-input NAND gate. The inputs to this gate are  $\phi 2$  and A2 to A12 inclusive. The output of IC5 will be low when  $\phi 2$  is high and the address bus contents are:— XXX1 1111 1111


11XX (X=don't care). Only when the output of IC5 is low and the enable input to IC4b is low can the output of IC4b go low. The enable input will be low when the address bus pattern is:— 101X XXXX XXXX XXXX and therefore IC4b output is only low for addresses:— 1011 1111 1111 11XX which fall in the range BFFCh to BFFFh and the  $\phi 2$  signal is also high. These four addresses are used to write into the control logic and read from the programming logic.

When a WRITE operation is performed to one of the four addresses, the output of IC4c will go low and allow data to be written into IC7. This device is a four-word, four bits per word memory. When writing data into it, the



# PROJECT : EPROM Card

Fig. 2 Circuit diagram of the project.

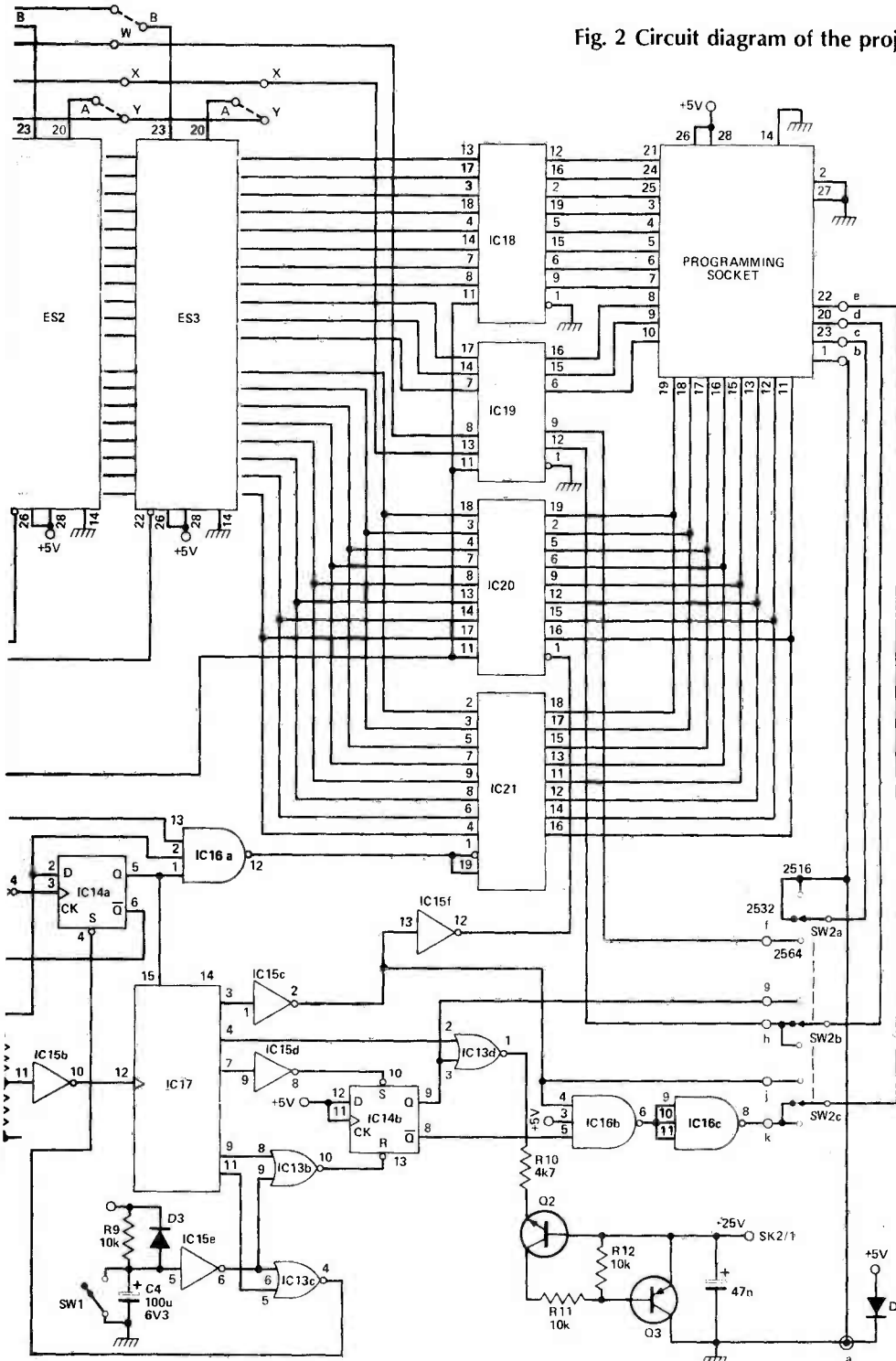

See scan of centre circuit for more information

word to be written is selected by address bits A0 and A1 and the data is taken from data bits D0, D1, D6, D7. (Note that there is no way to read the stored data back into the computer!)

If a read operation is performed to any of the four control addresses it will cause IC4d to be enabled via IC10b and IC10d. This will put the state of the programming status logic on to bit 7 of the data bus.

When an address in the range 8000h to 9FFFh is written to or read from, the relevant output from IC6a activates IC9 and IC10a. The output from IC10a and the state of the R/W line will activate IC10c if a READ operation is in progress. This will set its output low

causing IC3 to drive towards the computer and set the MAP, IODIS and ROMDIS pins on the computer connector low to turn off its internal memory and I/O functions.

Also, A11 and A12 connected to IC7 will select one of the four words stored in it and present it to IC6b and IC9. The bits presented to IC9 correspond to the original D6 and D7 and are used to select the function to be used. The two bits from IC9 and the R/W line cause one output from IC9 to go low when  $\phi_2$  is high and the address decode function from IC6a is low. These outputs are combined in IC12a, b and c to give outputs to enable the EPROM sockets, the RAM or the programmer. The two remaining bits from IC7 are passed to IC6b

and select the EPROM socket to be accessed when enabled by the output from IC12a. These bits correspond to D0 and D1 of the original data and now represent 2K blocks of memory space.

The output from IC12a activates the EPROM sockets, from IC12b the RAM and from IC12c the programmer logic. The circuitry around IC11 and Q1 and D1, D2 and B1 ensures that the power supply to IC8 never drops too low and that the WE, OE and CS inputs are held high and inactive when the main power supply is absent or low.

## PROGRAMMER SOCKET FUNCTIONS

When IC7 has been programmed such that IC12c is activated by a read operation and no programming is in progress, the output of IC13a will go high and cause IC18, 19 and 20 to capture the current state of the address and data busses. Also as the R/W line will be high and IC14a Q output will be high, IC16a will be low and will enable the buffer IC21 to transfer data from an EPROM in the program socket to the data bus. At the end of the memory cycle as the output of IC13a goes low the state of the R/W line will be latched into IC4a. If this was a read operation then IC14a will stay in its set state (Q output high).

When the same conditions are set up but a write operation is in progress, the only difference is that IC16a output remains high and thus IC21 is not enabled. However at the end of the cycle, when the current state of the R/W line is clocked into IC14a, it will send the Q output low and the  $\bar{Q}$  output high. The high level on the Q output holds the output of IC13a low and effectively prevents further read and write operations to the programming socket for the time being. This output also forms the status output from this part of the logic and a high level shows that the programmer is 'busy'.

When the Q output of IC14a goes low, this removes the reset signal from IC17. Now this device can respond to the 10ms pulses on pin 12 derived from the rectified mains by IC15b. The first pulse sets pin 3 low which in turn drives IC15c output high and IC15f output low. This last output enables the output from IC20 which has previously stored the data on the data bus to be programmed into the EPROM. The output from IC15c is also used to drive one pin of a 2516 EPROM or indirectly via IC16b and IC16c for 2532 and 2564 devices.

After the next 10ms pulse, IC17 pin 4 goes high and forces IC13d output high. This turns Q2 and Q3 on thus switching the +25V supply through to the EPROM.

The next pulse sends IC17 pin 7 high and hence IC15d output low. This sets IC14b Q output high and keeps the +V supply on via IC13d. The Q output forces IC16b output high and hence IC16c output low. The Q output is also used as input to 2516 devices.

The next four pulses cause no changes in the logic states, but the next pulse after these causes IC17 pin 9 to go high which then puts IC13b output low. This resets IC14b Q output low and Q output high and turns off the programming voltage.

The last pulse puts IC17 pin 11 high which forces IC13c output low which sets IC14a Q output high. This then resets IC17 to have pin 3 high and signals the end of a programming cycle by the Q output of IC14a going low.

IC15e, C1 and R9 form a power-on-reset function which forces IC13b and IC13c outputs low for a short time to ensure that IC14a, IC14b and IC17 are in the correct initial states.

SW2 is used to select the correct logic signals to program 2516, 2532 and 2564 EPROM devices. For 27XX devices some rearrangement of wiring may be required.

then terminal pins, resistors, diodes, capacitors (take care that there is enough space for ICs), transistors and connectors. Do not fit the battery yet. Check at this stage that the +5V supply line is not shorted to 0V and that it is connected to all the IC sockets except IC11 (there is a germanium diode in there). Check also that the 0V rail is connected to all IC sockets. Check carefully that the tantalum bead capacitors are the right way round and also check the diodes and transistors.

Once this has been done and any faults corrected you are ready to start inserting ICs and testing the board. It would be advisable to have a fine pointed soldering iron with a 15W element or temperature controlled if possible. A solder sucker is almost essential if you make a serious mistake on this type of PCB. Be very careful to avoid creating solder bridges between adjacent tracks or lifting tracks by excessive heat.

### Setting Up And Testing

For the present you will need a supply to give 5 volts at up to 500 mA. Whenever you insert or remove ICs this power supply should be disconnected from the board.

The first stage in getting the project working (if you are not so reckless as to put all the ICs in, turn on and tune for minimum smoke) is to put IC1,2,4,5,6 and 10 into their sockets. Notice that all

**Control Address**  
BFFCh (49148)  
8FFDh (49149)  
BFEFh (49150)  
BFFh (49151)

**Controlled Address block**  
8000h — 87FFh (32768 — 34815)  
8800h — 8FFFh (34816 — 36863)  
9000h — 97FFh (36864 — 38911)  
9800h — 9FFFh (38912 — 40959)

**Table 1 Relationship between control address and controlled address blocks.**

the ICs on the board are the same way round — make sure yours are too!

With a few miniature test probes connect SK1 pin 26 and 28 to 0V. With +5V applied to the board check that IC6 pin 6 and SK1 pin 1,2 and 6 are low. Connect SK1 pin 7 to 0V and check that SK1 pin 1,2 and 6 is now high. Remove the 0V connection from SK1 pin 28; no change should occur at SK1 pin 1,2 and 6 (still high) but IC6 pin 7, IC4 pin 6 should now be low and IC10 pin 6 high. Now remove the 0V connection from SK1 pin 7 and SK1 pin 1,2 and 6 should go low along with IC10 pin 6 and IC4 pin 11. If all went well remove the +5V supply and insert IC3,7,8,9,11 and 12.

Now you can connect the board to your computer using a length of ribbon cable and two IDC plugs. It is most important that the ribbon cable linking the board to the Oric should be only two or three inches long. Total failure to read EPROMs correctly was caused by a 12 inch cable, possibly, to capacitance loading as there does not seem to be any internal buffering on the address lines. Glitches on the address lines when the long cable was used caused the chip select for the EPROMs to be less than 200 ns wide — not enough to ensure that valid data was ready in time for the processor to read it.

Connect the +5V and power-up your computer and all should be well. Your ORIC or ATMOS should now display its normal

**Control Function**

**Control Word**  
**Bits**  
D7 D6  
0 0  
0 1  
1 0  
1 1

Read only from selected EPROM socket\*  
Read only EPROM socket\*, write only RAM  
Read and write RAM  
Read Programming socket or Program EPROM in it

**Table 2 Function select bits of control word in control addresses.**

With the power supply disconnected and the board unplugged from the computer, plug in the rest of the ICs but temporarily remove IC12. Connect the +5V supply but not the computer for the time being and monitor IC14 pin 5. Initially this should be at a logic high level, as should IC14 pin 8. Monitor IC16 pin 12 and momentarily connect IC13 pin 12 to 0V: this should cause IC16 in 12 to go low momentarily but IC14 pin 5 will stay at a high level. Repeating this with SK1 pin 7 held low, IC16 pin 12 should stay high but now IC14 pin 5 should go low. Also IC13 pin 13 should be permanently low, whereas with SK1 pin 7 high it should be the inverse of the input at pin 12. To get back to that situation, SW1 may be closed momentarily to reset the logic.

If possible, connect a low frequency oscillator to the junction of R7 and R8. Frequency should be about 1 Hz and amplitude +5V unipolar. Monitor IC15 pin 2, apply a logic low level to SK1 pin 7 and momentarily bring IC13 pin 12 low. IC15 pin 2 should start off low, go high for about 8 secs and then go low again. During this time, IC13 pin 1 will go low for 6 secs and IC14 pin 8 for 5 secs.

Control Word EPROM socket selected  
**Bits**  
D1 D0 E50  
0 0 E51  
0 1 E52  
1 0 E53  
1 1

**Table 3 Socket select for**

**BUYLINES**  
Despite the complexity of this project, there are few problems here. The battery is the only one we can think of: we used an RS type (stock number 591-477); you may have to use your initiative! The PCB is, as ever, available through our PCB service.

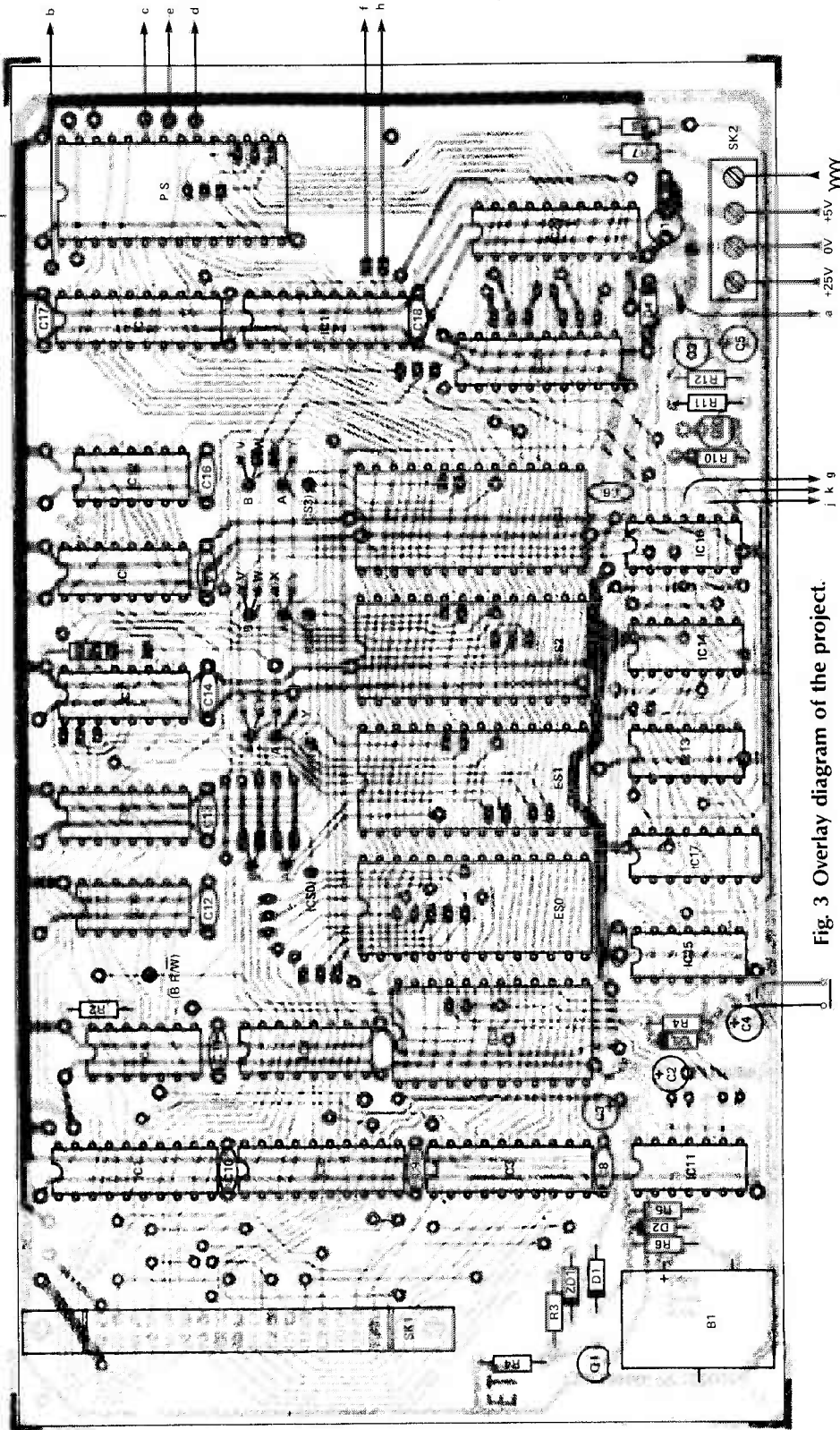


Fig. 3 Overlay diagram of the project.

## PARTS LIST

### RESISTORS (all 5% carbon film 1/4 watt)

R1,2 2k2  
 R3,4,8 1k0  
 R5,9,11,12 10k  
 R6 1k5  
 R7 5k6  
 R10 4k7

### CAPACITORS

C1 2u2 16V Tant. bead  
 C2 1u0 35V Tant. bead  
 C3,4 100u 6V3 Tant. bead  
 C5-18 47n Min. ceramic disc (14 off)

### SEMICONDUCTORS

IC1,2 74LS244  
 IC3,21 74LS245  
 IC4 74LS125  
 IC5 74LS133  
 IC6 74LS139  
 IC7 74LS670  
 IC8 6116LP-3  
 IC9 74LS138  
 IC10 74LS00  
 IC11 4071  
 IC12 74LS11  
 IC13 74LS02  
 IC14 74LS74  
 IC15 74LS14

IC16 74LS10  
 IC17 4017  
 IC18,19,20 74LS373  
 Q1,2 BC182L  
 Q3 BFR79  
 D1,2,3 OA91  
 D4 TN4148  
 ZD1 BZY88C2V7

### MISCELLANEOUS

B1 PCB mounting Ni-Cd 3V6 100mA-h if required

SW1 Single pole push button switch, normally open  
 SW2 3 pole 3 way switch (slide type or rotary wafer)  
 SK1 34-way IDC socket PCB mounting (also 2 off plugs plus ribbon cable)  
 SK2 4 way PCB mounting screw connector

DIL sockets: 8 off 14 pin, 5 off 16 pin, 7 off 20 pin, 1 off 24 pin, 5 off 28 pin (one may be ZIF type); Veropins, wire etc; PCB.

Using the same procedure it should be possible to check that the correct signals appear on the programming socket via SW2.

If all is well so far, remove the oscillator and connect the programming supply to SK2 pins 1 and 4 as shown on the diagram. Repeating the above procedure should not put pulses of +25V on the selected pin(s) of the programming socket and suitable logic levels on the others. The actual sequence is best checked with an oscilloscope if one is available.

Having reached this stage, IC12 can be replaced and you should have a fully operational board which can be reattached to your computer. If you wish to make the RAM on board non-volatile, the NiCad battery should be soldered onto the PCB. This battery should be charged, before serious use is made of the board, at 10mA for 14 hours. After this, periodic use should keep it topped up but occasional charges at 1 mA in addition are advisable.

If you find that the start up routine of the computer is corrupting the RAM contents then fit a switch across R4 and close it to protect the RAM. (You cannot read it with this switch closed.) Note, also, that the programming supply switches between +5v and +25v.

## Programming 27XX Series Devices

Although the project was not designed for it, there should not be too many differences to take account of when programming 27XX series devices so long as single rail only types are used. In fact, 2716 devices should work in place of 2516 without modification. The details for other types should be as follows:

### 2732 types:

remove D3, connect 4k7 resistor from collector Q3 to 0V;

| EPROM Type | Links            |
|------------|------------------|
| 2516       | A-Y, B-V         |
| 2532       | A-X, B-V         |
| 2564       | A-X, B-W         |
| 2716       | A-Y, B-V (1)     |
| 2732       | A-Y, B-X (1) (2) |
| 2764       | A-Y, B-X (1) (3) |

**Notes:**  
 (1) To restore low current operation of 27XX series EPROMs connect A to the track feeding pin 22 of the socket instead of to Y;  
 (2) High current operation;  
 (3) High current; also need to connect pin 2 to W and cut track under board to isolate pins 2 and 27 from 0V and connect pin 27 to +5V.

Table 4 EPROM type selection links.

connect collector Q3 to pin 22 on socket;  
 connect IC19 pin 12 to pin 23 on socket;  
 connect IC16 pin 8 to pin 20 on socket;

### 2764 types:

cut tracks to pins 2 and 27 under PCB;  
 connect IC19 pin 9 to pin 2 of socket;  
 connect IC19 pin 12 to pin 23 of socket;  
 connect Q3 collector to pin 1 of socket;  
 connect pins 20 and 22 on socket to 0V;  
 connect IC14 pin 8 to pin 27 on socket;  
 The 2732 and 2764 connections are instead of the switch.

## "ROM" Packs

If you have one of the non-volatile "ROM" packs which usually consist of CMOS memories together with a small battery, it is possible to 'program' one of these in one of the normal EPROM sockets by breaking the connection between IC12a pins 1 and 2 and linking IC12 pin 1 to IC9 pin 15 (C on the circuit diagram). This will select the EPROM sockets for read and write operations instead of read only. Note, however, that it is not advisable to have EPROMs in the sockets when this is done as this will mean that their outputs will conflict with the bus buffers during a write cycle.

The ETI PseudoROM (June '83) is a device of this type and could be used with minor modifications to take account of the difference in pin function. Do not try to program such a device in the programming socket!!!

## Power Supplies

The power requirement for this project is fairly simple and can be derived from a transformer with two 12 volt secondaries and rated at about 15 VA. We used a toroidal type because it was convenient. The secondaries are connected in series and full wave rectified by a bridge rectifier. This gives in the region of 34 to 36 volts across the reservoir capacitor. This voltage is regulated down to the required 25V by a 7812 IC regulator and its associated resistor chain. The +25V supply to the main PCB goes via a relay switch which makes sure that this supply is not applied until a manual push button has been pressed. Another push button serves to turn the +25V off when not required.

The raw supply for the +5V rail is taken from the centre tap of the transformer windings via a diode and dropping resistors to a substantial reservoir capacitor. From here another IC regulator provides the +5V supply to the main board. The isolating diode is present so that an unsmoothed 100Hz waveform can be tapped off the transformer for use as a timing signal on the main PCB. The resistors are used to reduce power dissipation in the +5V regulator as it is operating with a high input voltage.

If alternative arrangements are to be used for these supplies, they should be able to deliver +5V at 0.5A, +25V at 0.1A and 12V RMS unsmoothed rectified (100Hz) at 10mA. Alternatively a 100Hz pulse generator could be used.

Also provided on our power supply design are facilities to charge the Ni-Cd battery at 1mA or 10mA if needed.

ETI

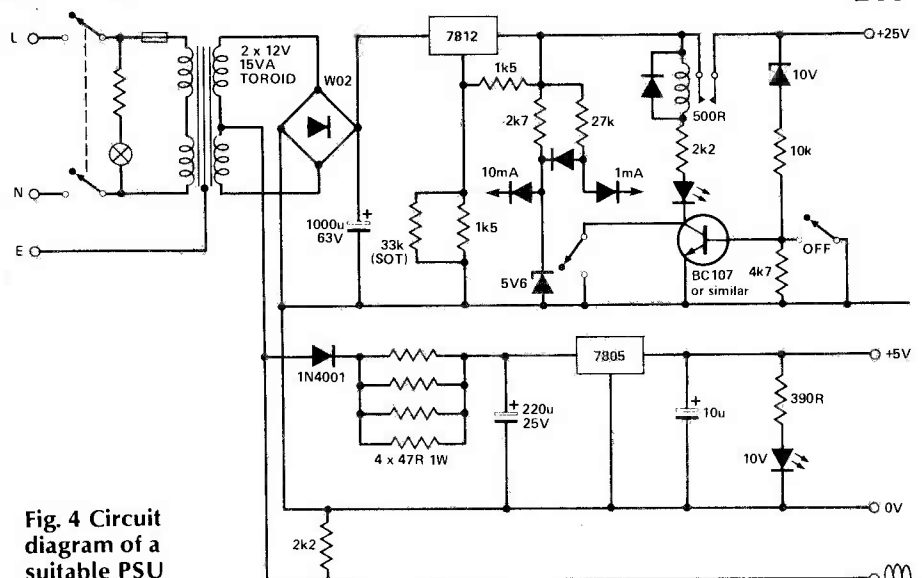


Fig. 4 Circuit diagram of a suitable PSU



# hobbyboard

## COMPUTING AND ELECTRONICS

### Project development materials



### Computer Cables & Connectors

We now offer an extensive range of computer cables & connectors including a spectrum user port extender cable. The following are just a few of our extensive range, send for new cable & connector price list.



#### Spectrum User Port Extender

This 56 way IDC connector & ribbon cable assembly specially produced to fit the Sinclair Spectrum overcomes the interconnection problems associated with user port add-ons. Available as a double ended assembly with a user-port PCB male converter or single ended for wiring onto your own equipment.

**HB/2069 6" double ended extender & PCB £8.85\***

**HB/2068 9" single ended assembly £4.76\***

**HB/2093 56 way IDC connector only £3.34\***

**HB/3005 1 slot flexible backplane £12.70\***

#### BBC Printer Lead

26 way BBC/Centronics parallel printer lead **HB/3001 £7.00\***

BBC Tape Recorder lead **HB/3002 £1.53\***

Printer leads (centronics) available for many other machines.


#### VIC/CBM64 Cassette Interface

Works with most data recorders & will load commercial programs!  
**HB/3000 £12.50\*** Kit **HB/3003 £8.60\***
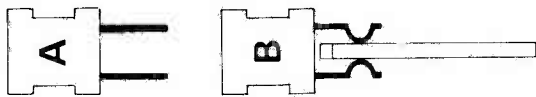
#### Edge Connectors

Double sided edge connectors 0.1" pin to pin and 0.2" row to row. All sizes are available in straight wire wrap Style 'A' or with the leads cranked to clip on the edge of a 1.6 mm circuit board Style 'B'. The range is chosen for compatibility with commonly found home computers, as well as for general use.

28 + 28 way, tinned contacts, keyed pin 5 suitable for use with Sinclair SPECTRUM



28 + 28/5 Connector Style 'A' **HB/440 £1.70\***

28 + 28/5 Connector Style 'B' **HB/441 £1.75\***

23 + 23 way, tinned contacts, keyed pin 3 suitable for use with Sinclair ZX81

23 + 23/3 Connector Style 'A' **HB/438 £1.40\***

23 + 23/3 Connector Style 'B' **HB/439 £1.65\***

Universal user port extension PCB as supplied in Micro Interface Kit. **HB/2012 £0.87\***

Interface Prototype board can be used with style 'A' connectors & user port extension to give flexible add-on system **HB/2091 £4.25\***

#### Micro Interface Kit

Professionalise your add on projects. Kit comes complete with attractive black ram pack style case, pre-etched & drilled double sided PCB, 28 way 0.1 pitch connector, 9 way D output plug & extender card. Suits Spectrum, ZX81, etc.

**Order ref. HB/2090 £9.50\***

### ZX/Spectrum Intelligent Joystick I/F

\*Treble your game scores overnight!\*

Suitable for Atari type joysticks. The kit provides an interface to enable ALL games programs to be played with joystick control. Tell it once & the keys for that game are remembered forever.

**Spectrum Kit & Joystick HB/2061 £27.31 less joystick £20.80**

**ZX81 Kit & Joystick HB/2060 £27.31 less joystick £20.80**

### Easy Add-ons for ZX Spectrum & ACE

17 exciting electronic projects to build and run your own micro.

- LIGHT PEN
- PICTURE DIGITISER
- KEY PAD
- MODEL CONTROLLER
- WEATHER STATION
- + OTHER EXCITING & INTERESTING PROJECTS

#### REALISE THE REAL WORLD POTENTIAL OF YOUR MICRO

A newly released book written by well known author Owen Bishop and published by Bernard Babani gives full descriptive details on how to build all 17 projects - all are fairly simple and inexpensive to construct - The most complex component (the DECODER) is supplied in kit form ready to assemble with all components and plated through PCB. Components for the projects are readily available locally or found in your workshop drawers.

Simple programmes are included to get you started but of course the more experienced programmer can have hours of fun writing complex programmes. Please state computer when ordering.

|   |               |
|---|---------------|
| Order ref HB/2000 "EASY ADD-ONS" BOOK + DECODER KIT | <b>£24.00</b> |
| Order ref HB/2001 "EASY ADD-ONS" BOOK ONLY          | <b>£3.00</b>  |
| Order ref HB/2002 DECODER KIT ONLY                  | <b>£22.00</b> |
| Order ref HB/2003 DECODER PCB ONLY                  | <b>£8.00</b>  |

## AVAILABLE SOON

Easy Add-on Projects for  
BBC, Electron, Commodore 64, VIC 20

### ZX81 Hi Resolution Graphics Kit

Improves screen resolution to 256x176 pixels enabling superior graphics to be easily programmed. Plugs directly into ZX81 ROM socket & is complete with extensive software tape.

**Order ref. HB/2070 £22.00**

## PLUS


- ★ U.V. Sensitised Printed Circuit Laminate, Chemicals & Equipment.
- ★ Daylight Photography & Label System.
- ★ Printed Circuit Artwork Aids.
- ★ Connectors, Cases & Hardware.

### HOBBYBOARD CATALOGUE

The Complete Printed Circuit Workshop.

Newly Published Full Catalogue price £1.50 (refundable with 1st order over £10)

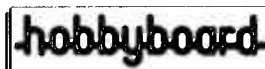\*Prices inclusive of VAT, carriage 60p in U.K. Overseas orders please add extra carriage to published prices.




complete P.C.B. workshop

a division of  
**KELAN ENGINEERING Ltd**  
Hookstone Park  
Harrogate, N. Yorks



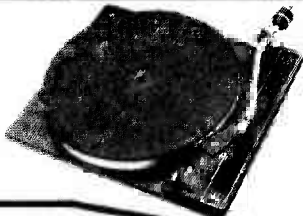
### BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm  
● Belt driven ● Aluminium platter ● Precision  
calibrated counter balance ● Anti-skate (bias  
device) ● Damped cueing lever ● 240 volt AC  
operation (Hz) ● Cut-out template supplied ●  
Completely manual arm. This deck has a com-  
pletely manual arm and is designed primarily  
for disco and studio use where all the advan-  
tages of a manual arm are required  
Price £32.35 each. £2.50 P&P


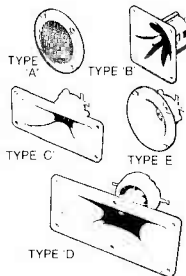
### PIEZO ELECTRIC TWEETERS — MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER**




**TYPE 'A'** (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each + 30p P&P.  
**TYPE 'B'** (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each + 30p P&P.  
**TYPE 'C'** (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each + 30p P&P.  
**TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each + 30p P&P.  
**TYPE 'E'** (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each + 30p P&P.

**LARGE S.A.E.**  
For details of  
disco mixers,  
speakers, kits,  
amp - modules,  
buglar alarms,  
turntables, etc.

### OMP POWER AMPLIFIER MODULE

READY BUILT

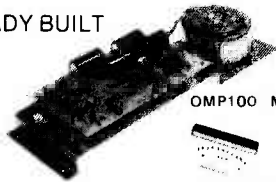

OMP100 Mk.II

New model.  
Improved specification

**NEW OMP100 Mk.II POWER AMPLIFIER MODULE** Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

**SPECIFICATION**  
Output Power:— 110 watts R.M.S.  
Loads:— Open and short circuit proof 4/16 ohms.  
Frequency Response:— 15Hz - 30KHz - 3dB  
T.H.D.:— 0.01%  
S.N.R. (Unweighted):— 118dB ± 3 5dB  
Sensitivity for Max Output:— 500mV at 10K.  
Size:— 360 x 115 x 72mm Price:— £31.99 + £2.50 P&P. Vu Meter Price:— £8.50 + 50p P&P.

### MOS-FET HIGH SPEC. MODULES

MOS-FET VERSIONS AVAILABLE UP TO 300 W. R.M.S.  
100 Watt 300mm x 123mm x 60mm Price: £39.99 + £2.50 P&P  
200 Watt 300mm x 150mm x 100mm Price: £62.99 + £3.50 P&P  
300 Watt 330mm x 147mm x 102mm Price: £79.99 + £4.50 P&P

### PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

**FM MICROTRANSMITTER (BUG)** 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £7.99 + 75p P&P.  
**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled, professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £12.49p + 75p P&P.  
**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £16.49. Transmitter 80 x 50 x 15mm (9/12 volt). Price: £10.29 P&P + 75p each. S.A.E. for complete list.




3 watt FM Transmitter
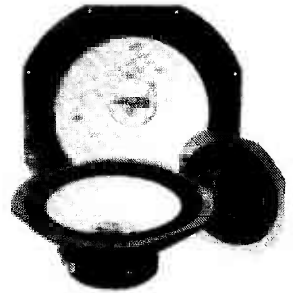
### LOUDSPEAKERS POWER RANGE

**THREE QUALITY POWER LOUDSPEAKERS** (15", 12" and 8" See 'Photo'). Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. Specifications and Prices.

15" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P.  
12" 100 watt R.M.S. Impedance 8 ohms. 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P.  
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz. magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. Black Cone. Price: £9.50 each. Also available with black protective grille. Price: £10.50 each. P&P £1.50.



12" 85 watts R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB. Price £24.99 + £3 carriage.  
12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone. 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz. Price £24.99 + £3 carriage.  
15" 150 watt R.M.S. McKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price £49 + £4 carriage. Cabinets fixings in stock S.A.E.

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★



**B. K. ELECTRONICS**

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
ESSEX SS2 6TR TEL 0702 527572



## AURAK

### HIFI CONSULTANTS AND RETAILERS

*Have you ever built an audio project and been disappointed with the results?*

It has become apparent to us that he who builds audio equipment with the cheapest components he can find is asking for compromise and disappointment.

It is now a well documented fact that component quality can have considerable effects on sound quality.

We have conducted extensive listening tests on a large variety of components and can offer advice on component selection.

We can also supply top quality components including:—

'WONDERCAPS' from America, the finest capacitors for audio use.


'FILMCAP' prosec 85 ultra low ESR capacitors  
Metalised film resistors

High speed, ultra low output impedance regulators  
We also stock high quality decks, arms, cartridges, amplifiers and loudspeakers — see HiFi Answers and HiFi News for agency lists.

2nd Floor Suite  
46 Wood Street  
St Annes on Sea  
Lancashire FY8 1QC  
0253 729 111



## Musician 2B Loudspeaker

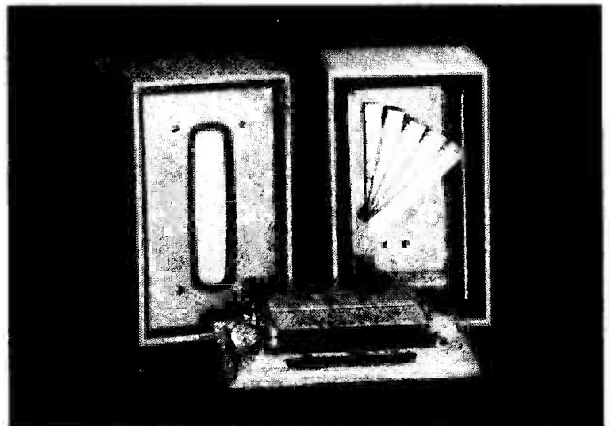

At last the ideal of all the sound coming from one piston-like diaphragm, unspoiled by crossover units and resonant enclosures.

These radically novel loudspeakers set new standards both in sonic realism and spatial presentation — "The best stereo you are likely to hear... Quad class nuff said" ... Paul Messenger Hi-Fi News Nov '83.

Drive units for building into enclosures as described in this magazine are £140 per pair plus VAT and postage. Complete loudspeakers in Luxury & Basic enclosures are available. Details and prices from:

Merseyside Acoustic Developments  
131 Mount Pleasant  
Liverpool L3 5TF  
Tel: 051-709 0427

# QED A230 STEREO AMPLIFIER

**The A230 stereo amplifier heralds the arrival of a complete, British designed and built hi-fi system from QED. The ETI team have been putting it through its paces.**

**T**he A230 stereo amplifier is the forerunner of a complete new range of hi-fi components from QED Audio Products Limited. Over the next year or so they plan to introduce a turntable, a cassette deck and a loudspeaker system to complement the amplifier and the T231 tuner which has been launched alongside it. All the items will be designed and built in this country and there are plans to offer the turntable as a kit.


QED are perhaps best known at present for their 79 strand loudspeaker cable, but they actually manufacture a wide range of audio accessories including tape and loudspeaker switching units, headphone adaptors, mains suppression and distribution units, loudspeaker stands and a moving coil input amplifier. In extending this range to cover complete systems they have fixed their sights very firmly on the Japanese competition. The components are stackable, allowing them to compete with the rack and tower systems which are so popular at the less expensive end of the market, but they are also available in no less than seven different wood veneer finishes in addition to the basic metal-

cased version, thus broadening their appeal considerably. The front panels have an attractive graphite-grey finish with light green legending, and this too is intended to set them apart from the standard silver finish found on most Japanese systems. The amplifier is also going to be sold at a price which will allow it to compete directly with the Japanese imports—£99 including VAT.

The same philosophy, that of beating the Japanese at their own game as QED put it, is extended to the actual design of the amplifier. The uncluttered front panel reflects an attempt to avoid all circuitry which is not absolutely essential, both to improve the overall sound quality and to make the amplifier as simple to operate as possible. There are no tone controls, no electrolytic capacitors in the signal path, no output fuses, and no output limiting circuit. There are two sets of loudspeaker output terminals, one of which is switched out when a jack is inserted into the headphone socket while the other remains in circuit permanently. It is thus possible to connect a pair of loudspeakers to the out-



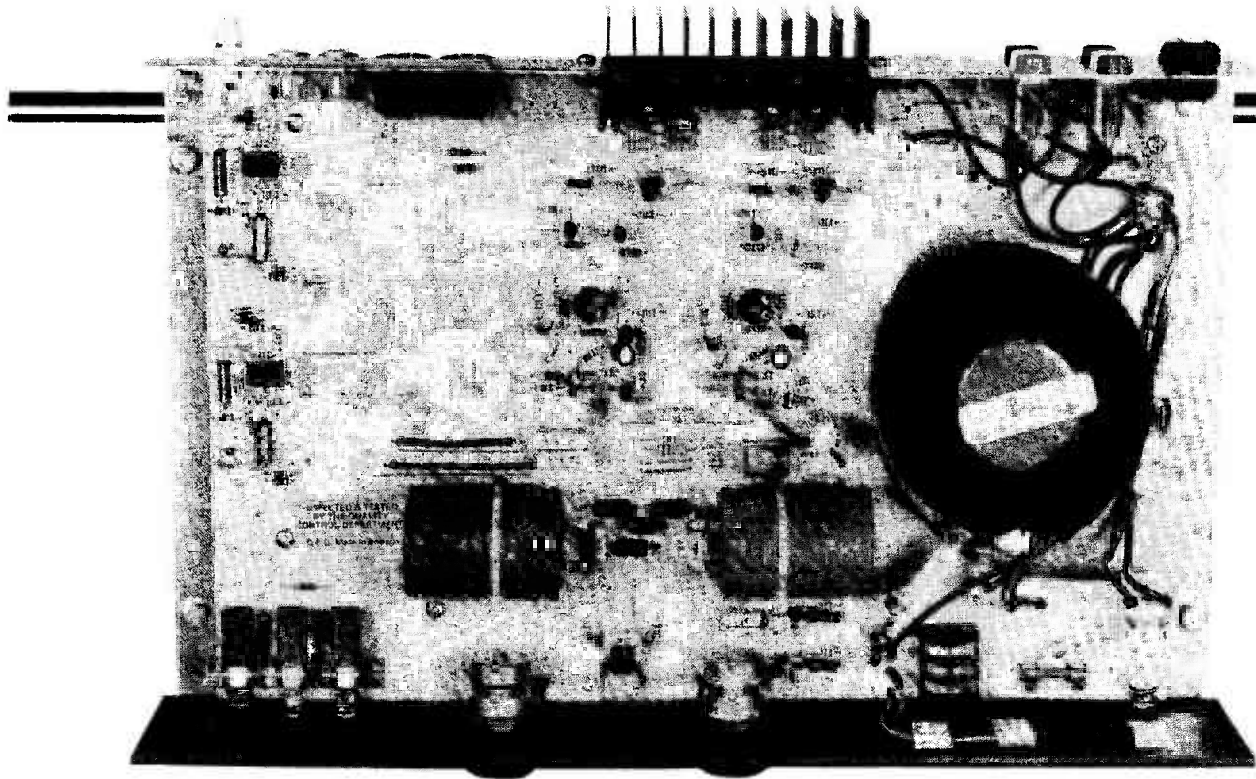The A230 with the matching T231 tuner, which, unfortunately, we didn't get our hands on . . .



**Internal shot of the A230 showing the transformer and heatsink, whose sizes gave initial cause for concern.**

put of the amplifier without any intervening switch contacts, fuses, limiting circuits or other potential source of signal degradation.

The A230 is built almost entirely on one large PCB which extends into every part of the case. A semi-circular cutout in it provides clearance for the toroidal transformer which is the only major component mounted directly to the case. The potentiometers, switches, reservoir capacitors and most of the sockets are all soldered directly to the PCB and the heatsink mounts through the back of the case to link up with the output transistors which are also on the PCB. 1% metal film resistors are used throughout and the PCB itself is made of a material called FRG 50 which QED claim is very tough.

The manufacturers' specifications for the A230 are given in the accompanying table. A peak output power in excess of sixty watts per channel is claimed and QED say that high peak powers are maintained even into difficult loads. Inputs for disc, tuner and tape are provided and the tape selector also provides a tape monitor

function for use during recording. The disc input is equipped with phono sockets while DIN sockets are used for tuner and tape. 4mm sockets are used for the loudspeaker outputs. A jack socket on the front panel is provided for use with high impedance headphones only and this can be arranged to switch out the loudspeakers as explained earlier. The only remaining controls are the volume and balance potentiometers, the mains switch and a green LED to indicate power on.

### On Test

One of the first things we did when the amplifier arrived was to take the cover off and have a look inside. The use of a single large PCB makes for a very clean layout with an absolute minimum of interwiring and just about everything is immediately visible and readily accessible. Good quality components do indeed seem to have been used throughout and the quality of the general construction is also high. The only things which caused us any concern were the toroidal transformer and the heatsink, both of which seemed very small in view of the output levels claimed by the manufacturers.

Rather than subject the amplifier to a group listening test in a single location, we decided to let each of the ETI staff try it out individually in their homes. This allowed us to compare it with four very different stereo systems (two largely home-grown and two made up of commercially available components) and to try it in differing domestic surroundings. It also enabled us to listen to the amplifier over an extended period and to find out what it is like to live with.

Bearing in mind our reservations about the size of the transformer and heatsink, we were pleasantly surprised at the QED's ability to supply high power levels without apparent effort. Dave Bradshaw found that very high volume levels could be coaxed from his relatively inefficient transmission line loudspeakers, and the volume had to be wound up very high indeed before the QED showed any signs of stress. Others were unable to try the amplifier to its limits in this direction (mainly for social reasons!) but all reported adequate power delivery up to the maximum required under normal domestic listening conditions.

Bass response drew a more varied set of reports, leading us to suspect that the amplifier behaved very

|  |  |
|--|--|
| RMS Power Outputs (both channels driven) | 30 Watts per channel into 8 Ohms<br>48 Watts per channel into 4 Ohms |
| Single channel driven                    | 36 Watts RMS into 8 Ohms<br>56 Watts RMS into 4 Ohms                 |
| Total Harmonic distortion                | Less than 0.1% 20Hz to 20kHz.  |
| Power Bandwidth                          | -3db @ 10Hz and 30kHz.   |
| Signal to noise                          | Disc = -65db. Tape and tuner = -80db                                 |
| Disc input overload                      | Better than 32db   |
| RIAA Accuracy                            | +0db -1/2db (30Hz to 20kHz)  |
| Disc input sensitivity                   | 3mV into 47K and 150pf   |
| Tape and Tuner sensitivity               | 300mV (inputs and outputs)   |
| Headphone socket                         | Only suitable for use with high impedance headphones (600 Ohms etc)  |
| Mains fuse                               | 0.5 Amp (anti-surge)   |
| Dimensions (mm)                          | 355 x 237 x 64   |
| Finish                                   | Graphite grey  |
| Weight (inc carton)                      | 4.75 Kg.   |

**Table 1. Manufacturers' specifications**



# REVIEW : QED A230 Stereo Amplifier

differently into the load presented by each set of loudspeakers. Phil Walker described the bass response as being a little light but clean, Ian Pitt found the level of bass similar to that achieved with his usual set-up and described it as dynamic and well-controlled, while Dave Bradshaw found the bass to be very extended and prominent, at times almost unnatural, as though a loudness control was in circuit. The difference may be explained in part by the material each chose to audition the amplifier on, but it does seem that the bass performance varies considerably from loudspeaker to loudspeaker.

There was more agreement about the frequency response across the rest of the audio spectrum. Everyone found it very clean and largely neutral, the treble was generally praised as being free from ringing and sibilance effects, and the mid-range was felt to be well-balanced, although Dave Bradshaw reported it seeming slightly recessed in relation to the prominent bass response.

All of the controls worked well and there were no problems in using the facilities. The only exception was the headphone output; QED say that only headphones of 600 ohms impedance or higher should be used, but in practice the solution is not as simple as that. Dave Bradshaw found that his 150 ohm Yamaha headphones worked perfectly well, but Ian Pitt found that the volume control had to be set to very low levels and the circuit noise became apparent when using his AKG K160/4 600 ohm headphones. Phil Walker reported similar problems and difficulty in balancing the channels when using lower impedance headphones. It was

felt that some sort of attenuator circuit would be helpful here, either built into the amplifier or as an extra for use with those headphones that don't match it well.

The only other point which received any comment was the possible need for a mains filter. Phil Walker found that loud clicks were produced whenever mains driven equipment was switched on or off elsewhere in the house, but the problem was not felt to be a serious shortcoming and others found the performance no worse in this respect than their own equipment.

To sum up, the QED A230 was judged to be a very fine amplifier indeed and certainly well worth auditioning if you are looking for an amplifier in this price bracket. The sound is the equal of that provided by many more expensive amplifiers, and if you are more interested in this than in tone controls and other frills then the QED should be a very attractive proposition. It does seem to be affected quite critically in the bass region by the loudspeakers it is coupled to, so it would be a good idea to audition it carefully in this respect, and if you are buying a system from scratch, to listen to it with as many different loudspeaker systems as possible.

The QED A230 amplifier costs £99.00 including VAT in its basic (metal) case. Wood veneer cabinets in the following finishes are available for £20.00 extra: mahogany, pine, beech, light oak, teak and walnut. Rosewood is also available to order, price on application. The accompanying T231 tuner (not reviewed here) costs £119 in its basic (metal) case and can be ordered with the same range of wood finishes for the same extra charge.

ETI

## Newrad

NEWRAD INSTRUMENT CASES LTD

Unit 19, Wick Industrial Estate, Gore Road  
New Milton, Hants BH25 6SJ  
Tel: New Milton 615774/621195

John Linsley Hood is famous for his high quality amplifier designs. We have collaborated with him to produce two kits based on the current ETI pre-amp and power amp projects. We have a reputation for designing high quality enclosures and complete electronic systems. These kits employ the best engineering techniques we know. The enclosures were specially designed with a pleasing blend of Satin Anodising and hard wood finish.

Cost of Pre-amp Kit (complete)  
**£98 inc p/p** please add 15% VAT

Part kits are also available plus PCB's.

To be announced:- Price details of Power Amplifier Kit, Conversion hardware for fitting both units into a HI-FI tower system and also 19" Rack mounting options.

**"Changing from bell wire or mains lead to QED 79 STRAND SPEAKER CABLE is the cheapest upgrade you will ever make"**

*HI FI Answers November, 1982.*

That is a typical statement endorsed by Dealers, magazines and most important of all satisfied customers using QED 79 strand cable.

Many people however, still make the mistake of using thin "bell wire" to connect their speakers, not realising that the dynamic losses involved are enormous.

QED 79 Strand Speaker Cable avoids such losses, and offers an AUDIBLE improvement over all other stranded cables, with an increase in clarity across the full frequency range.

Please contact your local QED Dealer or write to us directly at the address shown below

**QED AUDIO PRODUCTS LIMITED**

Unit 12, Ashford Industrial Estate, Shield Road, Ashford, Middx. Tel: Ashford 46236

Beware of cheap imitations, genuine QED 79 strand cable is embossed

"QED AUDIO PRODUCTS"

Price: 77p/metre.  
available in black or white.

**CABLE TERMINATION ACCESSORIES.**

**TO FIT QED 79 STRAND CABLE.**

|                               |       |
|-------------------------------|-------|
| Pack of four 4mm plugs        | £2.50 |
| D.I.N. Adaptors (pack of 2)   | £2.20 |
| Cable Terminators (pack of 2) | £1.40 |
| Pack of 4 spade terminals     | £2.50 |



# SPECTRUM JOYSTICK INTERFACE



Feeling like using your Spectrum to zap the aliens, but put off by having to remember which keys to use? Discover the joy of a stick, using this interface by Mike Wynne-Jones

This interface can be used to connect any Atari or Commodore Vic compatible joystick to the Sinclair Spectrum. It is read by the function IN 31, like several other interfaces on the market (notably those made by Kempston and Quickshot) and can be used with any commercial software compatible with these and several other joystick systems.

The different movements cause a 1 to appear in different bits of the number read in, as follows:

| POSITION | BIT |
|----------|-----|
| right    | 0   |
| left     | 1   |
| down     | 2   |
| up       | 3   |
| fire     | 4   |

Bits 5,6,7 are always 0.

So, for example, if the stick is in the top right corner, and the 'fire' button is pressed, the number read will be 25.

## HOW IT WORKS

The circuit diagram is shown in Fig. 1. In an I/O operation with the Spectrum, address bus bits A0-4 must be high, to indicate that there is not a keyboard read taking place. To use IN 31, A5,6,7 must all be low, and for an I/O read, IORQ and RD must both be low.


Note that the joystick can also be read at addresses 31 plus any multiple of 256. This is extremely unlikely to cause a problem, as any software/hardware system which requires further address decoding would also, probably, need far more sophisticated analogue joysticks.

IC1a output goes high when A5, A6 are low, and IC1c goes high when IORQ and RD are both low. This means that when, and only when, the address busses hold all the correct signals, all inputs to IC2 are high. Under these circumstances, the output of IC2, an eight-input NAND gate, goes low.

IC3 is a 20-pin device consisting of eight tri-state buffers. Four have a common OE (output enable) pin, and the other four a common OE pin, enabling the chip to be used as a quad transceiver if required. Here, however, all buffers are required to switch on at the same time, so the OE is driven directly from the output of IC2 (low when all signals are correct) and OE is driven from the output of IC1d.

Whenever IC3 is activated, the inputs are buffered on to the outputs, ie on to the computer's data bus. Inputs 5,6 and 7 are permanently low, causing the signals on D5,6 and 7 to be low when the interface is activated, and inputs 0 to 4 are pulled low by R1 to R5, or high if the corresponding joystick switch is closed, putting a 1 or a 0 on the data bus.

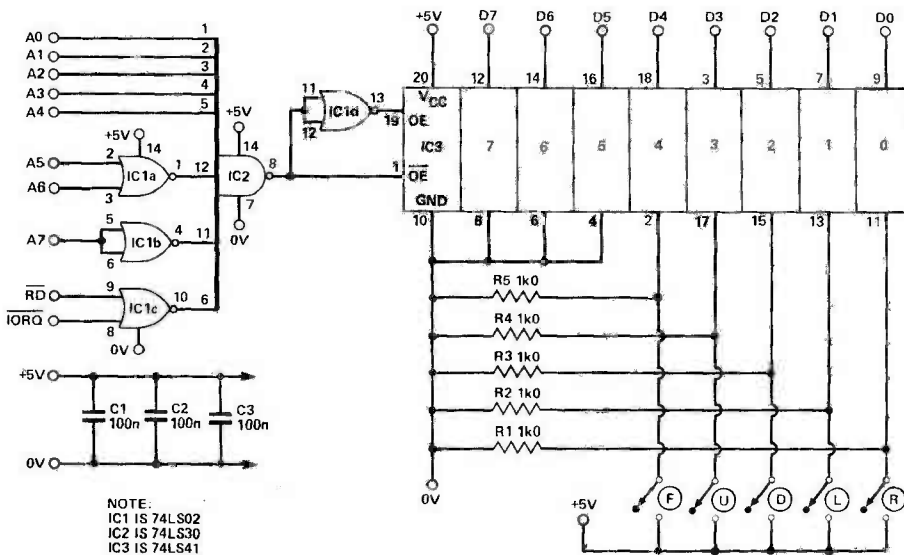When it is not activated, the outputs of IC3 will all be at their high-impedance state.



NOTE:  
IC1 IS 74LS02  
IC2 IS 74LS30  
IC3 IS 74LS41

Fig. 1 Circuit diagram of the interface.

# PROJECT : Joystick Interface

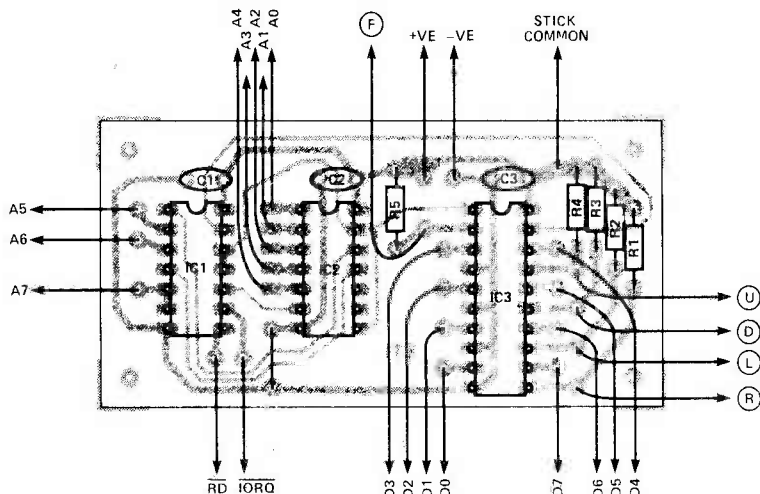


Fig. 2 Overlay diagram of the interface.

## PARTS LIST

|   |                   |
|---|-------------------|
| <b>RESISTORS (all 1/4 W 5%)</b>   |                   |
| R1-5  | 1k0               |
| <b>CAPACITORS</b>   |                   |
| C1-3  | 100n ceramic disc |
| <b>SEMICONDUCTORS</b>   |                   |
| IC1   | 74LS02            |
| IC2   | 74LS30            |
| IC3   | 74LS241           |
| <b>MISCELLANEOUS</b>  |                   |
| 9-way D-type plug, panel-mounting; Sinclair edge connector (for Spectrum); PCB; case; wire, etc |                   |

## Construction

A small PCB was used for the project, and the component overlay is as shown in Fig. 2. Whilst it would have been possible to design a PCB so that the edge connector could fit directly onto it, this would have required a much larger double-sided PCB, which would have made the unit rather costly to make. So we're afraid that neatness has been sacrificed for price!

The project was housed in a plastic case, with a slot cut for the edge connector and a hole for the D-type plug. The height of the plug in the case is fairly important, as otherwise it will be difficult to plug in the interface to the back of the computer. No edge connector has been provided at the back of the case as it was judged that joysticks are most likely to be used for game-playing when it is unlikely that other peripherals will be required. If this is found to be inconvenient, there is no reason why an expander plug could not be improvised. The edge connector itself should be glued in position using an epoxy adhesive.

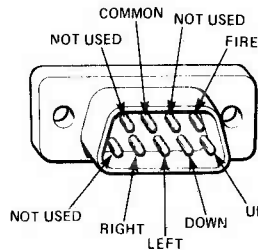


Fig. 4 Wiring details of the joystick socket.

Connections between the PCB and the socket can be made using either ribbon cable (although a bit of 'hacking' will be necessary) or with thin flexible wire. The D-type plug can be connected up in the same way, and for two-player use, another plug can be connected in parallel (although only one of you must use a joystick at any one time unless you are working co-operatively!).


Figure 3 shows which pins are which on the pin side of the D-type connector, and details of the Sinclair edge connector are given in Fig 4.

## Testing


Before inserting any ICs, make a thorough visual check of the board and the interconnections. Next plug in the computer and switch on; the copyright message should appear on the screen as usual. If this doesn't happen, there must be a fault on the board, so switch off quickly and start looking! If all is well, switch off the computer, insert IC1 and switch on again. If all is well, repeat for the remaining three ICs, checking each time.

When this is complete, run the following short program:  
 10 PRINT IN 31  
 20 POKE 23692, 100 : REM AUTO SCROLLING  
 30 PAUSE 10  
 40 GOTO 10  
 Check that moving the stick in different directions changes the numbers printed in the expected way. If the interface works satisfactorily, it's time to start zapping the aliens (or is it the fruit?).

ETI

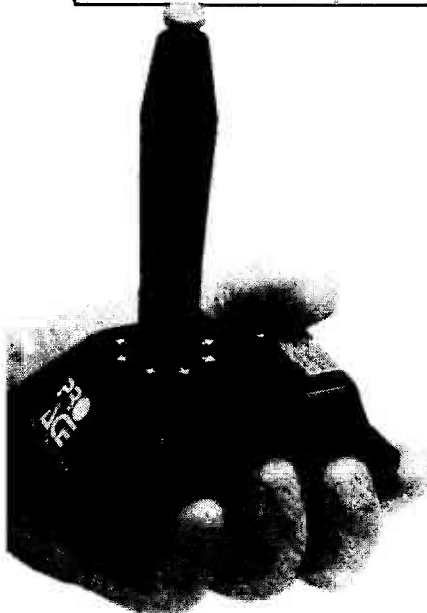

COMPONENT SIDE

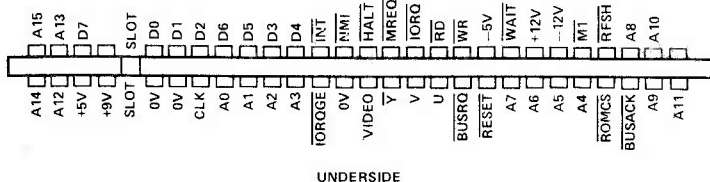

UNDERSIDE

Fig. 3 Edge connector details for the ZX Spectrum.

## BUYLINES

Well, here's a real initiative test — can you possibly find anything that it's hard to buy? Edge connector from Watford, Rapid, and others, PCB from our PCB service . . . you'll really have to work at this one!



**NEW INTERFACE E** - ONLY £55.00  
Simply plug in and it's ready to use. All operating commands are held in an EPROM so L.LIST, L.PRINT and COPY can be used at any time without using up valuable user RAM. COPY will allow the reproduction of high resolution graphics with Epson (or derivatives) and Seikosha 80, 100 and 250 Series printers. Print width selection from 32 characters to full width depending on printer used

**INTERFACE S** - ONLY £39.99  
Visually identical to Interface E but without the EPROM, Interface S also recognises the L.LIST & L.PRINT commands and will allow print width selection from 32 characters to full width.

However, software routines will need to be loaded before use. Full screen dump to reproduce high resolution graphics is also possible and supporting software is supplied to operate this facility with Epson and Seikosha printers. The software routines that are necessary to initialise the interface are held in the printer buffer so valuable user RAM will not be used up. There is a growing range of Business/Utility software that includes these routines. Details available on request.

Either interface simply plugs into the ZX Spectrum expansion port or interface and is supplied fully cased with a one metre ribbon cable which connects to the printer of your choice. Full instructions are included and driving software is supplied with Interface S.


We recommend Epsoms, NEC, TEC, Seikosha, OKI Microline Tandy GP115, Star DP 510, Shinwa, Brother HR15, etc.

At last you can have real print performance from your ZX Spectrum with the Kempston Centronics Interfaces

# THE INDUSTRY STANDARD INTERFACE

For ZX Spectrum

From **£39.99** Inclusive

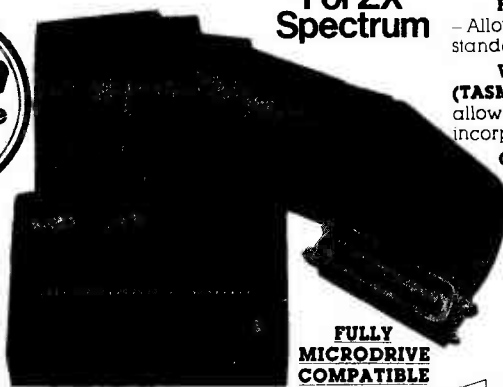

FULLY MICRODRIVE COMPATIBLE

Interface S available from W H Smith and Spectrum Computer Centres. All prices direct from

**KEMPSTON** MICRO-ELECTRONICS LTD

Unit 30 Singer Way, Woburn Road Industrial Estate, Kempston, Bedford MK42 7AF. Tel: (0234) 856633 Telex: 826078 KEMPMI G

All prices include VAT and P & P Overseas orders please add £4 00 P & P Please allow 21 days for delivery of interfaces and software. Printers available within 48 hours

TRADE ENQUIRIES WELCOME

SEE US ON STAND 135 THE COMPUTER FAIR LONDON

**KEMPSTON CENTRONICS INTERFACE COMPATIBLE SOFTWARE UTILITIES.**  
FOR THE 48K SPECTRUM.

**FINANCE MANAGER (OCP)** - Menu driven program for all domestic and business accounting applications. **£19.95**

**ADDRESS MANAGER (OCP)** - Simple index filing system ideal for names, addresses, etc. Various search facilities. **£19.95**

**FULL SCREEN EDITOR/ASSEMBLER (OCP)** - Allows you to write Z80 assembly code using standard mnemonics on full screen. **£19.95**

**WORD PROCESSOR (TASWORD TWO)** - (TASMAN) A professional word processor allowing 64 characters per line and incorporating all usual editing facilities. **£13.90**

**OMNICALC (MICROSPHERE)** - The only spreadsheet written entirely in machine code. The easy and fast way of solving any numerical problem. Ideal for cash flow forecasting, concrete stress analysis. **£9.95**

**MASTERFILE (CAMPBELL SYSTEMS)** - Filing and retrieval system for domestic or business use. Files can be loaded and saved independently. Microdrive compatible. **£9.95**

**NOW WE CAN ALSO SUPPLY YOUR PRINTER.**

We've looked at the printers currently available and have selected what we feel is best value for money in dot matrix and daisy wheel printers:

**EPSON RX-80 F/T** - A dot matrix printer allowing full graphics dumping and a choice of printing styles. Speed: 100 C.P.S. Price **£325 Inc. VAT and Delivery**

**BROTHER HR15** - A daisywheel printer ideal for letters, mail shots, documents, etc. Many typefaces available by changing daisywheel. Duplication facility but no graphics. Speed: Up to 18 C.P.S. Price **£425 Inc. VAT and Del.**

**LEN'S ELECTRONICS**  
1 BOOKHAM HOUSE  
WIMBLEDON PARKSIDE  
LONDON SW19 6AA  
Tel: 01-789 7656

**PCB SERVICE S.A.E.**

ETI MIXERS 8 channels **£500.00**  
ETI 413/100watt Amplifier Kits or 200watts **£30.00 & £60.00**  
ETI 419/Pre Amplifiers Kits **£15.00** Fet ETI 401 **£15.00** Kits  
LEN'S Power Supply, Please State Voltage & Current. S.A.E.  
Capacitors, Resistors, Diodes, Zeners, Transistors S.A.E.

|                      |        |                        |        |
|----------------------|--------|------------------------|--------|
| INS 8255N            | £5.00  | Computer CHIPS         |        |
| C 8008-1             | £1.50  | SN 7400                | 47p    |
| INS 8080 N           | £4.00  | SN 7404                | 52p    |
| D 8085 AC            | £4.50  | SN 5405                | 56p    |
| INS 8251 N           | £4.50  | SN 7413                | 81p    |
| INS 8212 N           | £1.50  | SN 7420                | 60p    |
| D 8259C-5            | £4.50  | SN 7428                | 80p    |
| D 8257C-5            | £4.50  | SN 7437                | 80p    |
| D 8279C-5 (8086)     | £20.00 | SN 7476                | £1.70  |
| AY-5-2376            | £9.50  | RCA                    |        |
| AY-5-3507            |        | CDP 1833               | £6.00  |
| MM 5233 CPA/N        |        | CDP 1834               | £6.00  |
| MEMORIES             |        | CDP 1802               | £10.00 |
| 2101 AL              | £3.50  | CD4059                 | £5.50  |
| 2102 B               | £3.50  | CD 4007                | 57p    |
| D2716                | £6.00  | CD 4011                | 56p    |
| D 2708               | £5.00  | CD 4511                | £1.63  |
|                      |        | CD 4029                | £2.00  |
|                      |        | LM 309K                | £1.50  |
|                      |        | LM323                  | £4.50  |
|                      |        | LM 3900                | £1.00  |
|                      |        | SN 741                 | 30p    |
|                      |        | LM 741                 | 30p    |
|                      |        | ML 307S                | 45p    |
|                      |        | LM 380N                | 90p    |
|                      |        | LM 381N                | £1.50  |
|                      |        | LM 324                 | 30p    |
|                      |        | LM 339                 | 45p    |
| Display & Drivers    |        | Seven Segment Displays |        |
| ICL 7106 CPL         | £9.50  | TIL 312                | £1.80  |
| ICL 7109 CPL         | £9.50  | TIL 311                | £8.50  |
| ICL 7103 ACP1        | £6.00  | SL 403 3watt Amp       | £2.00  |
| 3 1/2 Digit Displays | £12.00 |                        |        |
| FETs & J. FETs       |        | J112                   | £50p   |
| 2N 5457              | 50p    | BF 224                 | 30p    |
| 2N 5458              | 40p    | 2N 5248                | 40p    |
| 2N 5459              | 45p    | 2N 5484                | 40p    |
| BF 244B              | 30p    | 2N 4871                | 60p    |
| BF 245B              | 40p    | 2N 3823                | £1.30  |
| BF 245C              | 40p    | MPF 102                | 50p    |
| BF 256L              | 50p    | MPF 103                | 50p    |
| LF 356N              | £1.00  | MPF 105                | 50p    |
| 40673                | £1.00  | MRF 502                | £1.00  |
| BFW 10               | £1.50  | BFW 11                 | £1.50  |
|                      |        | RF Transistors         |        |
|                      |        | BF 494                 | 45p    |
|                      |        | 2N 3866                | £1.35  |
|                      |        | BFY90                  | £1.12  |
|                      |        | 2N 3553                | £1.35  |
|                      |        | BFR 90                 | £2.50  |
|                      |        | BFR 79                 | 25p    |
|                      |        | BSX 20                 | 38p    |
|                      |        | BF 180                 | 35p    |

**FREE CAREER BOOKLET**  
**Train for success, for a better job, better pay**

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today—at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

|                                |                          |                                  |                          |
|--------------------------------|--------------------------|----------------------------------|--------------------------|
| <b>ELECTRONICS ENGINEERING</b> | <input type="checkbox"/> | <b>TV &amp; AUDIO SERVICING</b>  | <input type="checkbox"/> |
| <b>ELECTRICAL ENGINEERING</b>  | <input type="checkbox"/> | <b>RUNNING YOUR OWN BUSINESS</b> | <input type="checkbox"/> |

Name .....


Address .....

**ICS** Dept EB164  
ICS School of Electronics  
160 Stewarts Road  
London SW8 4UJ

01 622 9911 (all hours)

---

# WILMSLOW LOUDSPEAKER KIT



**Loudspeaker kits appear to offer a genuine saving on your hi-fi system costs, but do they really match up to factory built units? Ian Pitt gets to grips with a new Peerless design from Wilmslow Audio.**

**M**y first stereo system consisted of the audio stages from two elderly, valve radios, the remains of two damaged BSR record decks out of which I conjured one, almost functional deck, and two loudspeakers which differed not only in size, shape, impedance and power handling but also in that one required a separate energising supply. The whole assembly was no better to look at than it was to listen to and I lost no time in planning its replacement. The only obstacle was my chronic lack of cash.

Being an essentially practical soul I approached the problem in the following way. Good quality turntables, I reasoned, could be purchased from discount houses quite cheaply, and if finances were really tight one could always purchase the chassis only, support it on a pile of breeze blocks and explain the resulting mess away as a product of the *avant garde*. Amplifiers could be built from scratch, and even though the fledgling ETI had not then produced its first hi-fi amplifier design there were still a number of published designs to choose from. That only left the loudspeakers. Here I adopted a more radical approach and decided to spend the majority of my remaining money on a pair of good quality headphones which could be used for 'serious' listening while putting the rest towards the purchase of some cheap drive units which could be built into home-made cabinets and used for 'background' music.

The surprising thing is that, conceit aside, those cheap, home-made loudspeakers actually sounded rather good, and this despite the fact that the cabinet design and dimensions were determined more by the materials that were to hand than by any degree of informed planning. I mention this mainly for the benefit of those who still believe that the only way to get acceptable sound quality is to spend around half of their hi-fi budget on a pair of ready-built loudspeakers. Great advances have indeed been made by the more innovative loudspeaker designers, but the gap between the exotic (and expensive) and what you can build yourself is still not as large as some would have you believe. And now that there are loudspeaker kits available to save you doing the basic carpentry...

## **The Peerless CD825/2R**

Having decided to review a pair of loudspeaker kits in this issue, we left the actual choice of system to Wilms-

low Audio. They sent us a kit based upon one of the seven new designs in the Peerless Manual for Loudspeaker Constructors and using Peerless drive units. The particular model we were sent, the CD825/2R, occupies a position roughly in the middle of the new range and is one of two models said to be designed specifically for compact disc systems. Wilmslow explained that this is because the bass drivers in these two models have paper cones whereas the others have polypropylene cones; paper is regarded as having the better transient response, making it ideal for the fast attack and wide dynamic range of CD systems, while polypropylene is regarded as having the more neutral tonal balance. The bass driver unit in the CD825/2R is 8" in diameter and has a 38 mm voice coil, while frequencies above 1800 Hz are handled by a 1" dome tweeter. The enclosure is a bass reflex design of 25 litres volume, and the completed 'speakers have a nominal impedance of 8 ohms and are recommended for use with amplifiers rated at between 20 and 140 watts per channel (presumably peak although this is not stated).

The kit we received from Wilmslow included pre-cut and machined woodwork, the drive units, BAF wadding (which also serves as a packing material during transit), bituminous felt tiles for lining the interior of the enclosure, a roll of grille-cloth, the reflex tube, the crossover components, 4mm terminals complete with plugs to suit, and all the necessary screws, clips, and other fixings. There was some delay in sending out the 'speakers (Wilmslow had apparently intended to send us an even newer model, but this was not ready in time) and to help us get the review done as quickly as possible they assembled the crossovers for us.

The kit also included the Peerless Manual for Loudspeaker Constructors which contains individual information and constructional drawings on each of the models in the range, and a set of general instructions drawn up by Wilmslow. It is worth emphasising that the kits are only Wilmslow's realisations of the original Peerless designs. There is nothing to stop you obtaining the Peerless manual, doing your own carpentry and just purchasing the drive units from Wilmslow. Indeed, the Wilmslow kits differ slightly from the designs in the manual in that Peerless specify a chipboard enclosure assembled onto a batten frame while Wilmslow supply smooth-surfaced Medium Density Fibre (MDF) board which is grooved so as to make a frame unnecessary. In


spite of this difference, the information in the Peerless manual remains helpful and relevant.

## Construction

Having struggled manfully on rush-hour tubes to get the kit home, I opened it up and set about reading the instructions. As explained previously, there are both specific instructions from Peerless and more general instructions from Wilmslow in the kit. The Peerless manual is well presented on glossy paper but I was slightly disappointed by the Wilmslow instructions which simply consist of several photocopied sheets stapled together and which in places are almost unreadable. I was encouraged, however, to see that the Wilmslow sheets include a kit parts list on which each item has been ticked off by hand by the packer. I would recommend reading both the manual and the instructions through thoroughly first so as to get an idea of what information is presented in each.

Wilmslow recommend that you inspect all the panels for transit damage upon opening the kit, and then remove all dust, etc, with a vacuum cleaner. The next stage is to assemble the cabinets without gluing so as to check the fit, and then to swap around matching panels where this will achieve a better fit. This confirmed my original impression that the quality of the machining was generally very high, for the panels assembled readily with almost no visible gaps and the grooving was sufficiently positive to hold the whole assembly together with no external support. Wilmslow recommend that, if the baffle board is to be painted, the painting is done at this stage rather than when the cabinet is finally assembled and glued.

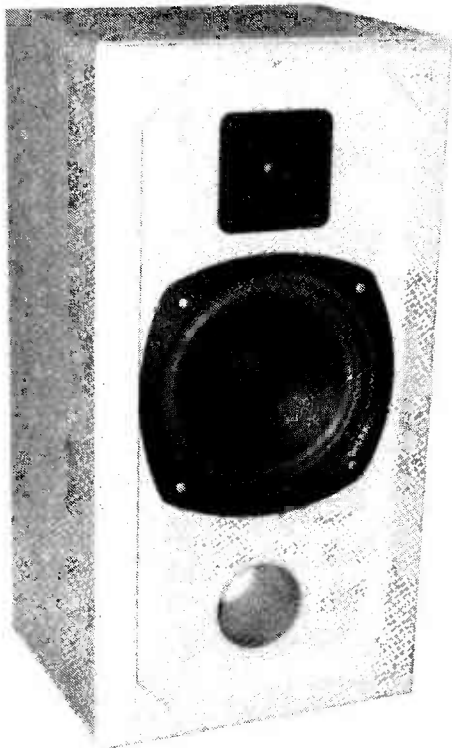Evo Resin W wood glue is recommended for the cabinet construction, and you are advised to use plenty so as to ensure an airtight seal. In fact, the quality of the cabinet joints is such that only a comparatively small amount of glue is needed to seal them, and my first



attempt left me with large quantities of wood glue issuing from every seam. This is not a problem as the glue can easily be removed with a damp cloth whilst still wet, but the stuff does have a tendency to get everywhere before you notice it.

One side of the cabinet has to be assembled at this stage but not glued, so that it can be removed later to allow you to install the bituminous felt tiles and the crossover. This is not quite as simple as it sounds because, as I have explained, the glue tends to seep along the joints as soon as you apply pressure. When the time came to remove this panel from the first of the two enclosures, I found that it required a considerable amount of force before it came free and that small chunks of panel remained attached to the glued cabinet. This can be overcome by inserting small pieces of paper between the side panel and the main cabinet opposite to the glued joints. Provided the paper is fairly thin it will not upset the tightness of the joint, and when the glue is dry and the side panel has been removed it can be pared away quite readily with a sharp knife.

While the glue is setting, the cabinets must be held together in some way. Wilmslow recommend the use of either clamps or masking tape, and I opted for the latter. Two bands of tape wound horizontally around the cabinet and two vertically, both pulled fairly tight, were sufficient to pull the panels tightly together during setting. The only slight drawback with this approach is that glue tends to seep under the tape, but again, this is fairly easy to pare away with a sharp knife later.

When the glue is dry and the side panel has been removed, the bituminous felt panels are cut to size and glued to the inside walls of the enclosure. Wilmslow suggest that they be held in place with panel pins while the glue dries. Mounting holes can then be drilled for the drive units and the grille-frame clips. As mentioned previously, Wilmslow suggest that if the baffle is to be painted it should be done before the cabinet is assembled, but I would be inclined to add that if you are going to use a fairly transparent grille-cloth and a light-coloured baffle it might be a good idea to drill the drive unit mounting holes also before assembling the cabinet. You can just rest the drive units in place and mark and drill the holes, but you stand a much better chance of getting the square tweeter bezel straight and the bass unit mounting holes neatly aligned if you take careful measurements across the baffle, and that might mean marking the painted surface.

Wilmslow provide you with two options for mounting the bass driver, a decorative fixing ring or four metal brackets. Both seem to secure the drive unit quite adequately, but I would recommend using the fixing ring when marking out your drilling positions since the resulting hole pattern will just as readily accommodate the metal brackets, while the positions obtained by using the brackets may not suit the fixing ring should you subsequently wish to use it.

The crossovers have next to be assembled into the cabinet. Although our crossovers were supplied ready-built, the accompanying instructions are excellent and I cannot imagine anyone who can handle a soldering iron having any trouble here. Each component position is identified in white lettering on the PCB itself and a series of black and white photographs show how the finished crossover for each model should look.

The crossover for the CD825/2 R comes with a choice of two tweeter series resistors, and an accompanying note explains that the lower value is intended to satisfy the requirements of continental listeners who reputedly favour a slightly brighter treble than their British counter-

# REVIEW: Wilmslow Loudspeaker Kit

parts. Our pre-assembled crossovers came with the higher value (giving a less-bright treble) already in place, and I decided to leave well alone until I came to the listening tests.

The other jobs which need to be done at this stage are the fitting of the reflex tube and the marking and drilling of the grille frame fixing holes and the input connector holes. The reflex tube and grille frame presented no problems when tackled in accordance with the instructions but I did have some difficulties with the input connectors. Peerless point out in the manual that the 4 mm input connectors do not have sufficient depth to pass right through the 18 mm thick panel, and that you will probably have to rebate the hole on one side in order to expose sufficient thread to attach the nut. It is easy enough to rebate the hole on the outside with the cabinet assembled but it is then difficult to stop the connector rotating while the nut is tightened, and this is not, in any case, a very satisfactory solution if the appearance of the finished job is important to you. Rebating the hole on the inside is a better idea but this is not easy when the cabinet is assembled, especially if you are relying upon only the most basic of tools. When I came to assemble the second enclosure I drilled and rebated these holes before assembling the cabinet, and this made life a lot easier. I also found it helpful to secure the nuts in the rebated holes with Araldite so that the connectors could simply be screwed into place from the back.

All that now remains is to fit the crossover in place, lead out the connections through the input connector and drive unit holes, fill the remaining space in the cabinet with the acoustic wadding and then glue the final side panel in place. No means of fixing the crossover is provided, but it seemed to be quite secure when simply wrapped in the wadding. When the glue on the side panel is dry, the drive units can be soldered to the trailing leads and then screwed into place.

The MDF panels have a smooth, plain surface and can be finished in a number of ways. Wilmslow suggest either painting the enclosure or covering it with iron-on veneer, plastic laminate or self-adhesive plastic film, although I suspect that painting would not be the most attractive approach since the exposed panel ends are, inevitably, not as smooth as the other panel surfaces and are probably more porous. I have not yet decided how to finish mine, but the raw end result is not unattractive and it saves me the trouble of steering the conversation round to my loudspeaker-building exploits when friends call.

## Sounding Them Out

For the listening tests I was able to borrow the QED A230 amplifier and the Musician loudspeakers which are the subject of other articles in this issue. I was thus able to compare CD825/2Rs with these as well as with my own system, a home-grown 30 watt per channel class B amplifier and a pair of dual-cone drive units in sealed, 20 litre enclosures. These components were tried out in various combinations over a period of several days, using inputs from both disc and tuner, and listening mainly to choral/orchestral music and jazz with some folk, male and female solo vocal, and a little light rock.

The CD825/2Rs are the only system in this line-up with separate tweeters, so it should come as no surprise to find that they offer more sheer treble energy and handle high frequency transients better than either of the other systems. I am tempted to characterise their sound as being slightly bright, but I think the difference is not so much one of colouration as of attack. By comparison, the other two loudspeaker systems sounded slightly

recessed, almost timid. I found the CD825/2Rs less easy to ignore, more forward and aggressive and very exciting on material with a wide dynamic range. I am not completely convinced of their tonal neutrality, but the sound is well balanced and never became tiring to listen to. The bass is well extended and tightly controlled and there is no suggestion of resonance or other unwelcome cabinet noise. Midrange is smooth and clear, while the treble is open and clean and has only the slightest tendency to 'tizziness' on cymbal clashes and the like.

More complex differences between the three systems emerged when I came to compare stereo imagery. Bearing out Carl Pinfold's views expressed elsewhere in this issue, I found the Musician loudspeakers easily the best in this respect with my own loudspeakers a little way behind and the CD825/2Rs offering the poorest performance. However, while the imagery offered by the Musician units was undoubtedly almost razor-sharp, the sound stage seemed remarkably compressed, wholly enclosed in the space between the loudspeakers and apparently lacking any vertical dimension. My own loudspeakers and the CD825/2Rs both offered a wider, if less well focussed sound stage, and with both there was a greater sense of physical depth. It's a pity that I was not able to compare the CD825/2Rs with an established, multi-drive-unit loudspeaker system, but I feel sure the imagery would compare well.

I was unable to listen to the three systems at very high volume levels for fear of being evicted, but a few brave moments of Pictures At An Exhibition at window-rattling volume convinced me that the CD825/2Rs can comfortably handle the highest volumes I am ever likely to be allowed to feed them with. They are also quite sensitive, something which makes high volume levels all too easy to achieve. The highest levels I dared use required no more than a quarter full-scale setting of my volume control, a fact which suggests mind-boggling implications should the remaining three-quarters of its travel ever be used.

In summary, perhaps the best thing I can say about the CD825/2Rs is that, since having them, I have started using my stereo system more. The sound is altogether more lively and arresting than that of my own loudspeakers, and if this has been bought at the expense of a slight increase in colouration the difference is marginal and the benefits easily outweigh it. I greatly regret not having been able to try them with a compact disc system, but I can readily imagine how well they would then sound. As far as I am aware, Peerless do not produce a ready-built loudspeaker which is the direct equivalent of this design so I cannot urge you to go along to a dealer and listen to it, but if you've been put off building your own loudspeakers by the thought of construction difficulties and eventual inferior sound, let me reassure you — kit loudspeakers are great!

*The Peerless CD825/2Rs are available from Wilmslow Audio in three forms: the Basic Kit comprises the drive units and the crossovers for a pair of loudspeakers and costs £88.95 plus £5.00 carriage; the Plus Kit includes everything needed for a pair of loudspeakers except the woodwork and costs £104.50 plus £6.00 carriage; the Total Kit, as reviewed in this article, includes all woodwork and other parts and costs £128.50 plus £10.00 carriage. All prices include VAT. The Peerless Manual for Loudspeaker constructors will be sent free-of-charge on receipt of a 12" x 9" SAE. Wilmslow Audio Ltd, 35-39 Church Street, Wilmslow, Cheshire SK9 1AS, tel 0625 - 529599.*



NEW from



This exciting new range of designs covers all domestic HiFi applications. There are 20, 30 and 40 litre designs using the famous Peerless Polypropylene bass units (newly released to the DIY market), a 7 litre mini speaker and two designs

specifically intended for use with digital systems. The Wilmslow Audio Total kits include all cabinet components, accurately machined from MDF board, drive units, crossover kits, wadding, grille fabric, terminals, nuts, bolts, etc. Full details are in the Peerless Manual for Loudspeaker Constructors which is available F.O.C. (send 12" x 9" SAE)

**Total kit Prices per pair inc. VAT**

|  |                        |        |
|--|------------------------|--------|
| Design 50/2R (7 litre, reflex)                 | £92.50 plus carr./ins  | £8.00  |
| Design 65/2R (20 litre, reflex, Polyr.)        | £111.00 plus carr./ins | £6.50  |
| Design 825/2R (30 litre, reflex, Polyr.)       | £115.00 plus carr./ins | £10.00 |
| Design 100/3 (40 litre, H8, Polyr.)            | £172.00 plus carr./ins | £10.00 |
| Design CD825/2R (25 litre, reflex) for digital | £128.50 plus carr./ins | £10.00 |
| Design CD825/3R (30 litre, reflex) for digital | £185.00 plus carr./ins | £10.00 |

**Basic kits (drive units and crossovers only) per pair**

|                 |                        |       |
|-----------------|------------------------|-------|
| Design 50/2R    | £87.50 plus carr./ins  | £4.50 |
| Design 65/2R    | £77.00 plus carr./ins  | £4.50 |
| Design 825/2R   | £77.00 plus carr./ins  | £4.50 |
| Design 100/3    | £128.00 plus carr./ins | £5.50 |
| Design CD825/2R | £88.95 plus carr./ins  | £5.00 |
| Design CD825/3R | £144.00 plus carr./ins | £5.50 |

Active versions of the three 825 designs are available

**VERY COMPETITIVE PRICES**

on speaker drive units:  
**AUDAX • CELESTION  
 DECCA • ELAC • FANE  
 G.I.USS • GOODMAN'S  
 KEF • MCKENZIE  
 PEERLESS • SCANSPEAK  
 SEAS • TANNAY • VOLT  
 WIMSFEDALE etc.**  
**COMPREHENSIVE CATALOGUE!**  
 Pages & pages of drive units, kits, crossovers, cabinet components, designs for PA cabinets, crossover calculations etc.  
**£1.50 Post Free (Export £3.50 or 4.00)**

**WHARFEDALE SPEAKERCRAFT NEW Range**

Basic kits (drive units and crossovers) per pair inc VAT

|      |         |                  |
|------|---------|------------------|
| L50  | £49.95  | carr./ins. £4.50 |
| L90B | £57.95  | carr./ins. £5.00 |
| L140 | £66.50  | carr./ins. £5.00 |
| E50  | £140.00 | carr./ins. £5.50 |
| E70  | £172.00 | carr./ins. £6.00 |
| E90  | £285.00 | carr./ins. £8.00 |


Total and PRO kits available for E series



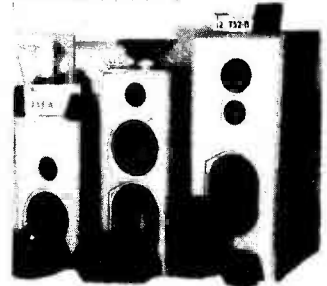**Constructor Series Speakers**

IT'S SO EASY

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit. No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of. Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc. The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl. Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.



Prices per pair

|                          |                                    |        |
|--------------------------|------------------------------------|--------|
| CS1 (As 101)             | £111 pr. inc. VAT, plus carr./ins. | £6.00  |
| CS1A (simplified LS3/5A) | £108 pr. inc. VAT, plus carr./ins. | £6.00  |
| CS3 (as 103.2)           | £131 pr. inc. VAT, plus carr./ins. | £10.00 |
| CS5 (as Carlton II)      | £195 pr. inc. VAT, plus carr./ins. | £15.00 |
| CS7 (as Caniata)         | £263 pr. inc. VAT, plus carr./ins. | £18.00 |

Kef Constructor Series basic kits (drive units and crossovers only)

|      |                    |       |
|------|--------------------|-------|
| CS1  | £88.50 carr./ins.  | £5.00 |
| CS1A | £84.00 carr./ins.  | £5.00 |
| CS3  | £100.50 carr./ins. | £5.00 |
| CS5  | £139.95 carr./ins. | £5.50 |
| CS7  | £193.05 carr./ins. | £5.50 |

|  |                 |
|--|-----------------|
| Wilmslow Audio Catalogue                     | post free £1.50 |
| Celestion Cabinet Handbook                   | post free £1.00 |
| Fane loudspeaker enclosure design            | post free £2.95 |
| Peerless Manual for Loudspeaker Constructors | FOC             |

ALL the above £5 post free

**CRIMSON ELECTRONIC amplifier kits, modules, active crossovers, YAMAHA Professional and Producer series products, 3rd Generation mixers, amplifiers, McGregor PA amplifiers, combos etc.**  
 All at very competitive prices!  
 Lightning service on telephoned credit card orders.  
**EFFICIENT EXPORT SERVICE**


**FREQUENCY COUNTERS**

- The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.
- ★ Measuring typically 2Hz - 1.2GHz
  - ★ Sensitivity < 50mV at 1GHz
  - ★ Setability 0.5ppm
  - ★ High Accuracy
  - ★ 3 Gate Times
  - ★ Low Pass Filter
  - ★ Battery or Mains
  - ★ Factory Calibrated
  - ★ 1-Year Guarantee
  - ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

|                     |         |
|---------------------|---------|
| METEOR 100 (100MHz) | £104.36 |
| METEOR 600 (600MHz) | £134.26 |
| METEOR 1000 (1GHz)  | £184.86 |

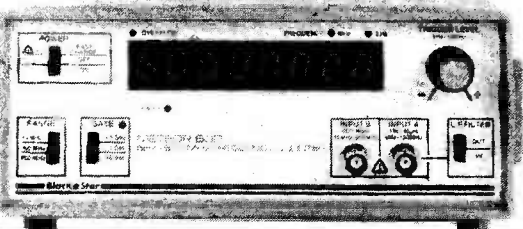Illustrated colour brochure with technical specification and prices available on request.




Designed and manufactured in Britain.




**BLACK STAR LTD (Dept. ET1), 9A Crown Street, St. Ives, Huntingdon, Cambs, PE17 4EB, England.**  
 Tel: (0480) 62440 Telex: 32339

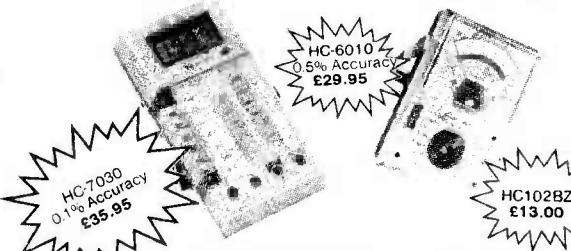**Affordable Accuracy - Low Cost Multimeters from Armon**

- SPECIFICATION MODELS HC-6010 & HC-7030 DIGITAL**
- ★ 10 amp AC/DC
  - ★ Battery: Single 9V drycell. Life: 200 hrs.
  - ★ Dimensions: 170 x 89 x 38mm
  - ★ Weight: 400g inc. battery
  - ★ Mode Select: Push Button
  - ★ AC DC Current: 200µA to 10A
  - ★ AC Voltage: 200mV to 750V
  - ★ DC Voltage: 200mV to 1000V
  - ★ Resistance: 200Ω to 20MΩ
  - ★ Input impedance: 10MΩ
  - ★ Display: 3 1/2 Digit 13mm LCD
  - ★ O/Load Protection: All ranges



- SPECIFICATION HM 102R ANALOGUE**
- ★ DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts
  - ★ AC Voltage: 0-10, 25, 100, 250, 1000 volts
  - ★ Decibels: -20 to +22dB
  - ★ DC Current: 0-50, 500µA, 0-5, 50, 500mA
  - ★ Ohmmeter: 0-6 Megaohms in 4 ranges, 30 ohms Centre Scale.
  - ★ Power Supply: One 1.5 V Size 'A' battery (incl.)
  - ★ Size & Weight: 135 x 91 x 39mm, 280gr.
- HC 102 BZ WITH BUZZER BATTERY SCALE, 10A DC RANGE**

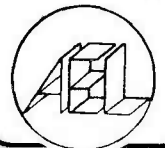

**ARMON ELECTRONICS LTD.**  
 Dept. E, Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH  
 Telephone 01-902 4321 (3 lines). Telex 923985

Please add 15% to your order for VAT. P&P free of charge. Payment by cheque with order. Offer applicable to mainland UK only.

Please allow 15 days for delivery.

# ELECTROVALUE

Your **SPECIALIST SUPPLIERS** for  
**SOLDER TOOLS**



From a simple 15 watt model to a precision temperature controlled iron, we stock solder irons to suit all manual requirements together with supporting stocks of bits, de-solder tools, materials etc.

## ANTEX

C240 - 15W/240V;  
CS - 17W/240V  
XS - 25W/240V

Replacement bits from 3/32" to 1/4"

De-solder heads, stands, elements and handles.

## ERSA

'Sprint' high speed iron: 80/150W, 240V. Heats in 10 seconds!

## ORYX

Temperature controlled solder iron TC.82 45W/240 with scale.

Oryx 50 - 50 watt temp. controlled.

### Standard types

Oryx 30 - 30W/240V

Viking - 27W/240V

Oryx M3 - 17 watts, 12 volts.

A wide range of replacement tips available for all models, also tips from 0.8 to 6.4mm dia. and flat tips.

Oryx safety stand.

Oryx de-solder tool.

### MINIATURE SOLDER STATION

SOLDER and DE-SOLDER BRAID

Solder in various grades.

Please mention this journal when sending for latest free A-Z list.

**BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 36 PAGE A-Z LIST**  
ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

**ELECTROVALUE LTD**

28 St. Judes Rd.,  
Englefield Green,  
Egham, Surrey  
TW20 0HB.

(0784) 33603; Telex 264475.


North - 680 Burnage Lane, Manchester. 061-432 4945.

EV Computing Shop

700 Burnage Lane, Manchester. 061-431 4866.

**ACCESS AND  
BARCLAYCARD  
Phoned Orders  
Welcome**

5

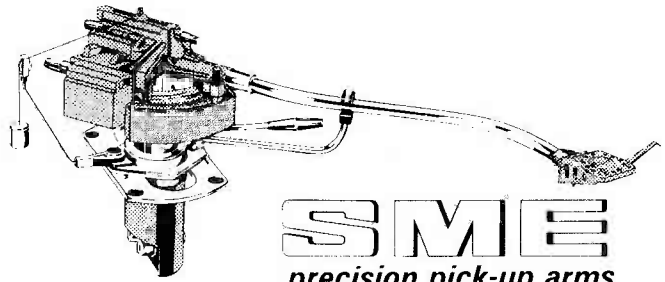

Please call or write:

SME Limited, Steyning, Sussex, BN4 3GY

Telephone: 0903 814321 Telex: 877808 G

## PARNDON ELECTRONICS LTD.

Dept 23, 44 Paddock Mead, Harlow, Essex. CM18 7RR Tel: 0279 32700

### RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance

Bandoliered and colour coded. Full Range 1R0-10M.

£1.00 per hundred mixed (Min 10 per value) £8.50 per thousand mixed (Min 50 per value)

Special stock pack 60 values 10 of each £5.50

### RECTIFIERS

|       |       |       |
|-------|-------|-------|
|       | 1 Amp | 3 Amp |
| 50V   | 3p    | 14p   |
| 100V  | 4p    | 14p   |
| 200V  | 5p    | 14p   |
| 400V  | 6p    | 19p   |
| 600V  | 8p    | 20p   |
| 1000V | 9p    | 25p   |

### VOLTAGE REGULATORS - 1 amp/T0220

Positive voltage 5.8, 12, 15, 24V 40p

Negative voltage 5, 12, 15V 43p

### CAPACITORS - Mixed special

£2.00 pack. Tant bead: 5 off OR

AL. ELEC: 30 off. Our choice of

Values/Voltages.

### DIL SOCKETS

8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p  
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

DIODES: IN4148 £1.60 per hundred

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS  
MIN ORDER - UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE

X-Stock Items Same Day Despatch

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY  
**THIS IS THE AGE OF ELECTRONICS!**  
the world's fastest growth industry...

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer. All the training can be carried out in the comfort of your own home and at your own pace.


A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.



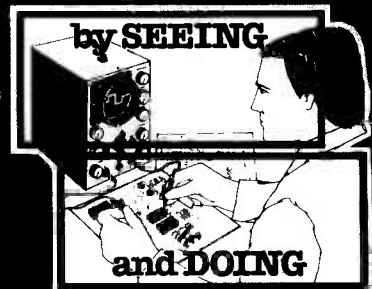**British National Radio & Electronics School Reading, Berks. RG1 1BR**

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



**FREE!**  
COLOUR  
BROCHURE

Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

ETI/6/842

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

Post now to:

**British National Radio & Electronics School Reading, Berks. RG1 1BR**



OR TELEPHONE US  
0734 51515 OR  
TELEX 22758  
(24 HR SERVICE)

# NOVEL LOUDSPEAKER DESIGN



**Carl Pinfold has created quite a stir in the hi-fi world with his full-range, flat diaphragm loudspeakers. This article covers the design philosophy of both the drive units and their enclosure, and goes on to describe the construction of similar enclosures for use with these or any other small-cone-area drive units.**


**T**he majority of loudspeaker designs currently available use a number of separate drive units fed through a crossover so that each handles only a discrete portion of the audible frequency spectrum. There are a number of advantages with such an arrangement but there are also a number of drawbacks. Where only two drive units are used, the crossover frequency will be between 2.5 and 3.5 kHz, the frequency band in which the ear is at its most sensitive and discriminating. The cone diameter of the drivers can be matched to the wavelength of the frequency bands over which they are operating, but this leaves a tweeter of no more than 5 cm<sup>2</sup> diaphragm area to handle the band of frequencies which often contain the greatest power levels in music, further compounding the problems of crossover design. The use of drive units with conventional cone-shaped diaphragms generates further problems in itself. The frontal volume forms a resonant cavity which introduces megaphone-like colourations, while the limited speed of the sound through the cone material results in a phase lag between the inner and outer areas, causing the cone to 'break-up' and producing an irregular response.

ETI JUNE 1984

In designing the Musician Loudspeaker drive unit, Carl Pinfold has attempted to overcome the limitations inherent in multiple drive unit systems using conventional cone loudspeakers by employing a single, full-range drive unit using a flat diaphragm. He argues that the use of a single drive unit rather than a multiple system with crossover makes a lot of sense with the present, almost universal, use of direct-coupled amplifiers since it preserves a high electrical damping factor. He goes on to suggest that a valid alternative to present design philosophies is to start with a good mid-range unit and then concentrate on extending its performance in the upper and lower octaves. This will lead to a sharper stereo image since the most crucial musical and spatial information is carried in the middle frequency range, and he believes the effect will be best achieved by making the sound source substantially narrower than the distance between human ears.

The result of his endeavours is a drive unit with a flat, 'lozenge shaped' diaphragm driven by a similarly elongated coil. The long thin shape fulfils the requirement that, when positioned vertically, the diaphragm is considerably narrower than the distance be-

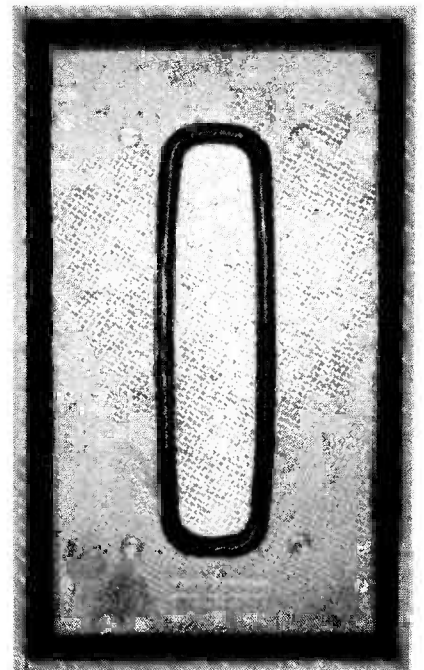tween human ears, and in addition it ensures that the diaphragm is fairly evenly driven since no part of its surface is more than 10 mm from the coil. The flat diaphragm does not have the stiffness of a



A Musician drive unit in an enclosure made of the cement-based inorganic plastic, NIMS 127.

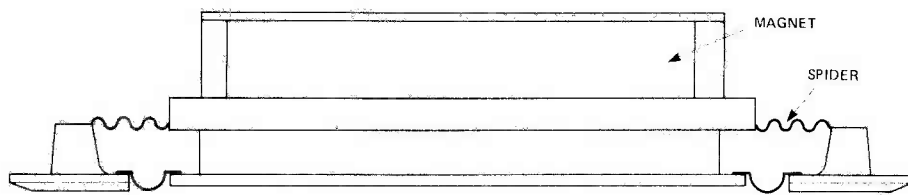


Fig. 1 Vertical cross-section through the Musician drive unit.

cone, but the more evenly-distributed drive overcomes this disadvantage to some extent, and the use of a stiff, lightweight, laminated plastic with a degree of self damping helps ensure that the inevitable flexing is not catastrophic.

The use of a large coil and relatively small diaphragm area does introduce certain limitations. Unless it is to make impossibly large excursions, a small diaphragm cannot produce high acoustic power levels. This prevents the unit delivering the power levels demanded by some heavy rock enthusiasts, but for most other tastes the sound level in a domestic room of average size should be satisfactory. The other limitation is the sensitivity. A low sensitivity is quite normal for small loudspeakers, and even with the substantial magnets used in the prototypes the sensitivity did not exceed 86 dB for 1 watt at 1 metre on axis. This simply means that the loudspeakers could be driven by an amplifier offering in excess of 40 watts per channel, not an uncommon output level for a modern, high quality amplifier.

The Musician Loudspeaker, at the expense of introducing these minor limitations, has been designed to offer a sound which is largely free of colouration. There is little point, therefore, in mounting such a drive unit in a conventional resonant enclosure. There are two major sources of resonance in a loudspeaker enclosure, cavity resonance generated within the space and resonances set up within the panels of which the enclosure is constructed. Both of these sources have been considered and dealt with in arriving at a design which complements the low colouration of the drive units.

Considering first the question of cavity resonance, standing waves always occur in an enclosure which has flat, parallel

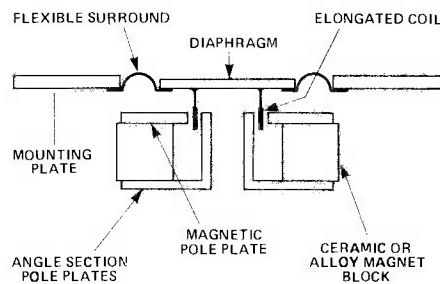


Fig. 2 Horizontal cross-section through the Musician drive unit.

interfacing surfaces. The wavelengths of the resulting resonances will be comparable to the distance between the faces.

Thus in a rectangular box 300 x 250 x 200 mm there will be resonances at approximately 1125, 1350 and 1700 Hz. Absorbent filling in the cavity will reduce these resonances but will not kill them altogether. The designers of musical instruments avoid the formation of standing waves by making their sound boxes in irregular shapes eg, the violin, the 'cello, the lute and the guitar. Reflections inside these sound-boxes are so diffuse that standing waves cannot occur. An instrument with a rectangular sound box would produce some notes much more loudly than others.

It is inconvenient and impractical to house loudspeaker drive units in irregularly shaped enclosures but the same effect can be obtained by inserting an irregularly shaped object inside the cavity which similarly diffuses reflections between the inner surfaces. The 'sound splasher' used for this purpose is shown in Fig. 6 and simply consists of a number of lengths of square section timber glued together to form a spiral. BAF wadding is used in the normal way to fill the remainder of the cavity.

In a conventional box with mitred or butt jointed corners, each panel is rigidly held at all its edges and is readily excited into resonances, the frequencies of

which will depend upon its mass, its stiffness and its dimensions. Again taking a lesson from the designers of musical instruments and noting that a piano string is damped by a resilient pad at one of its ends, the panels of the boxes are separated by a 1 mm gap and fixed together with cork fillets, giving them a degree of acoustic independence and providing a small but useful amount of damping.

The enclosure material must also be carefully chosen if excessive resonance is to be avoided. The best materials are heavy and stiff, and concrete and sand filled panels are among those which have been tried. Glass, ceramics and heavy metal plate are all better than timber or common chipboard, and very good results have been obtained using large (300 x 200 x 8 mm) Italian ceramic floor tiles. The constructional techniques outlined above can be used with all these materials.

The material most favoured by Carl Pinfold is a cement-based inorganic plastic called NIMS 127 which has been developed by Professor Birchall working for ICI. Cement mortar normally has no tensile or compressive strength and is prone to crumbling, the result of having large spaces between its molecules. By mixing a polymer additive with simple cement, Professor Birchall has produced a material which has the strength of aluminium plate, can be readily machined, cast and extruded, and which can be produced in any colour simply by adding pigments into the mix. It is fireproof, waterproof and requires a minimum of energy in its manufacture, but its most attractive features from the loudspeaker designer's point of view are that it is both dense and stiff and hence acoustically very non-resonant. Unfortunately, this material is not yet available to the general public, so the enclosure design presented here is that of Carl Pinfold's 'Basic' enclosure which is constructed from Medium Density Fibre board. Ordinary particle board could also be used, but will not give quite such good results and will need to be at least 18mm thick.

The enclosure to be described is of the fully-sealed or 'infinite baffle' variety. It has been designed principally for use with the Musician drive units which have a free-air resonance at 42 Hz rising to a modest peak at 70 Hz when so enclosed. The peak is not pro-



# electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 1, Golden Square, London W1R 3AB. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

## BEGINNERS GUIDE

|                          |  |       |
|--------------------------|--|-------|
| <input type="checkbox"/> | Beginner's Guide to Basic Programming Stephenson | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Digital Electronics          | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Electronics                  | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Integrated Circuits          | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Computers                    | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Microprocessors              | £5.35 |

## COOKBOOKS

|                          |                                     |        |
|--------------------------|-------------------------------------|--------|
| <input type="checkbox"/> | Master IC Cookbook Hallmark         | £10.15 |
| <input type="checkbox"/> | Microprocessor Cookbook M. Hordeski | £7.70  |
| <input type="checkbox"/> | IC Op Amp Cookbook Jung             | £14.25 |
| <input type="checkbox"/> | PLL Synthesiser Cookbook H. Kinley  | £7.70  |
| <input type="checkbox"/> | Active Filter Cookbook Lancaster    | £13.40 |
| <input type="checkbox"/> | TV Typewriter Cookbook Lancaster    | £11.15 |
| <input type="checkbox"/> | CMDS Cookbook Lancaster             | £11.85 |
| <input type="checkbox"/> | TTL Cookbook Lancaster              | £10.95 |
| <input type="checkbox"/> | Micro Cookbook Vol. 1 Lancaster     | £15.30 |
| <input type="checkbox"/> | BASIC Cookbook K. Tracton           | £6.00  |
| <input type="checkbox"/> | MC6809 Cookbook C. Warren           | £7.25  |

## ELECTRONICS

|                          |  |        |
|--------------------------|--|--------|
| <input type="checkbox"/> | Principles of Transistor Circuits Amos                           | £8.50  |
| <input type="checkbox"/> | Design of Active Filters with experiments Berlin                 | £11.30 |
| <input type="checkbox"/> | 49 Easy to Build Electronic Projects Brown                       | £6.00  |
| <input type="checkbox"/> | Electronic Devices & Circuit Theory Boylestad                    | £13.20 |
| <input type="checkbox"/> | How to build Electronic Kits Capel                               | £3.55  |
| <input type="checkbox"/> | How to Design and build electronic instrumentation Carr          | £9.35  |
| <input type="checkbox"/> | Introduction to Microcomputers Daglecs                           | £7.20  |
| <input type="checkbox"/> | Electronic Components and Systems Dennis                         | £15.00 |
| <input type="checkbox"/> | Principles of Electronic Instrumentation De Sa                   | £11.40 |
| <input type="checkbox"/> | Giant Handbook of Computer Software                              | £12.95 |
| <input type="checkbox"/> | Giant Handbook of Electronic Circuits                            | £17.35 |
| <input type="checkbox"/> | Giant Handbook of Electronic Projects                            | £11.75 |
| <input type="checkbox"/> | Electronic Logic Circuits Gibson                                 | £5.55  |
| <input type="checkbox"/> | Analysis and Design of Analogue Integrated Circuits Gray         | £30.25 |
| <input type="checkbox"/> | Basic Electronics Grob   | £11.30 |
| <input type="checkbox"/> | Lasers - The Light Fantastic Hallmark                            | £7.70  |
| <input type="checkbox"/> | Introduction to Digital Electronics & Logic Joynson              | £5.25  |
| <input type="checkbox"/> | Electronic Testing and Fault Diagnosis Loveday                   | £7.85  |
| <input type="checkbox"/> | Electronic Fault Diagnosis Loveday                               | £6.25  |
| <input type="checkbox"/> | Essential Electronics A-Z Guide Loveday                          | £7.50  |
| <input type="checkbox"/> | Microelectronics Digital & Analogue circuits and systems Millman | £12.70 |
| <input type="checkbox"/> | 103 Projects for Electronics Experimenters Minis                 | £8.30  |
| <input type="checkbox"/> | VLSI System Design Muroga  | £34.10 |
| <input type="checkbox"/> | Power FETs and their application Oxner                           | £9.40  |
| <input type="checkbox"/> | Practical Solid State Circuit Design Olesky                      | £25.00 |
| <input type="checkbox"/> | Master Handbook of IC Circuits Powers                            | £12.85 |
| <input type="checkbox"/> | Electronic Drafting and Design Raskhodoff                        | £22.15 |
| <input type="checkbox"/> | VDM - VTM Handbook Risse   | £8.50  |
| <input type="checkbox"/> | Video and Digital Electronic Displays Sherr                      | £28.85 |
| <input type="checkbox"/> | Understanding Electronic Components Sinclair                     | £7.50  |
| <input type="checkbox"/> | Electronic Fault Diagnosis Sinclair                              | £4.50  |
| <input type="checkbox"/> | Physics of Semiconductor Devices Sze                             | £17.35 |
| <input type="checkbox"/> | Digital Circuits and Microprocessors Taub                        | £32.00 |
| <input type="checkbox"/> | Active Filter Handbook   | £7.60  |
| <input type="checkbox"/> | Designing with TTL Integrated Circuits Texas                     | £15.20 |
| <input type="checkbox"/> | Transistor Circuit Design Texas                                  | £15.20 |
| <input type="checkbox"/> | Digital Systems: Principles and Applications Tocci               | £12.95 |
| <input type="checkbox"/> | Master Handbook of Telephones Traister                           | £10.00 |
| <input type="checkbox"/> | How to build Metal/Treasure Locators Traister                    | £6.00  |
| <input type="checkbox"/> | 99 Fun to Make Electronic Projects Tymony                        | £8.50  |
| <input type="checkbox"/> | 33 Electronic Music Projects you can build Winston               | £6.95  |

## COMPUTERS & MICROCOMPUTERS

|                          |  |        |
|--------------------------|--|--------|
| <input type="checkbox"/> | BASIC Computer Games Ahl                                   | £5.35  |
| <input type="checkbox"/> | From BASIC to PASCAL Anderson                              | £9.95  |
| <input type="checkbox"/> | Mastering Machine Code on your ZX81 T. Baker               | £7.25  |
| <input type="checkbox"/> | UNIX - The Book Banaham                                    | £8.75  |
| <input type="checkbox"/> | Z80 Microcomputer Handbook Barden                          | £10.95 |
| <input type="checkbox"/> | Microcomputer Maths Barden                                 | £11.90 |
| <input type="checkbox"/> | Digital Computer Fundamentals Barter                       | £9.90  |
| <input type="checkbox"/> | Visicalc Book. APPLE Edition Bell                          | £15.55 |
| <input type="checkbox"/> | Visicalc Book. ATARI Edition Bell                          | £15.55 |
| <input type="checkbox"/> | Introduction to Microprocessors Brunner                    | £23.00 |
| <input type="checkbox"/> | Programming your APPLE II Computer Bryan                   | £9.25  |
| <input type="checkbox"/> | Microprocessor Interfacing Carr                            | £7.70  |
| <input type="checkbox"/> | Microcomputer Interfacing Handbook A/D & D/A Carr          | £9.50  |
| <input type="checkbox"/> | Musical Applications of Microprocessors Chamberlain        | £28.85 |
| <input type="checkbox"/> | 30 Computer Programs for the Home Owner in BASIC D. Chance | £9.25  |
| <input type="checkbox"/> | Microcomputers Dirkson                                     | £9.30  |
| <input type="checkbox"/> | APPLE Personal Computer for Beginners Dunn                 | £9.50  |
| <input type="checkbox"/> | Microcomputers/Microcomputers - An Intro Gioone            | £11.80 |

|                          |  |        |
|--------------------------|--|--------|
| <input type="checkbox"/> | Troubleshooting Microprocessors and Digital Logic Goodman                  | £9.25  |
| <input type="checkbox"/> | Getting Acquainted with your VIC 20 Hartnell                               | £8.50  |
| <input type="checkbox"/> | Getting Acquainted with your ZX81 Hartnell                                 | £5.95  |
| <input type="checkbox"/> | Let your BBC Micro Teach you to program Hartnell                           | £7.90  |
| <input type="checkbox"/> | Programming your ZX Spectrum Hartnell                                      | £8.50  |
| <input type="checkbox"/> | The ZX Spectrum Explored Hartnell  | £6.95  |
| <input type="checkbox"/> | How to Design, Build and Program your own working Computer System Haviland | £9.30  |
| <input type="checkbox"/> | BASIC Principles and Practice of Microprocessors Heffer                    | £7.15  |
| <input type="checkbox"/> | Hints and Tips for the ZX81 Hewson   | £5.25  |
| <input type="checkbox"/> | What to do when you get your hand on a Microcomputer Holtzman              | £9.95  |
| <input type="checkbox"/> | 34 More Tested Ready to Run Game Programs in BASIC Horn                    | £7.70  |
| <input type="checkbox"/> | Microcomputer Builders' Bible Johnson                                      | £12.40 |
| <input type="checkbox"/> | Digital Circuits and Microcomputers Johnson                                | £14.55 |
| <input type="checkbox"/> | PASCAL for Students Kemp   | £7.20  |
| <input type="checkbox"/> | The C - Programming Language Kernighan                                     | £18.20 |
| <input type="checkbox"/> | COBOL Jackson  | £9.25  |
| <input type="checkbox"/> | The ZX81 Companion Maunder   | £9.50  |
| <input type="checkbox"/> | Guide to Good Programming Practice Meek                                    | £6.40  |
| <input type="checkbox"/> | Principles of Interactive Computer Graphics Newman                         | £13.95 |
| <input type="checkbox"/> | Theory and Practice of Microprocessors Nicholas                            | £11.35 |
| <input type="checkbox"/> | Exploring the World of the Personal Computer Nilles                        | £12.95 |
| <input type="checkbox"/> | Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll     | £9.80  |

|                          |   |        |
|--------------------------|---|--------|
| <input type="checkbox"/> | Beginner's Guide to Microprocessors Parr  | £5.35  |
| <input type="checkbox"/> | Microcomputer Based Design Peatman  | £11.30 |
| <input type="checkbox"/> | Digital Hardware Design Peatman   | £9.80  |
| <input type="checkbox"/> | BBC Micro Revealed Ruston   | £9.45  |
| <input type="checkbox"/> | Handbook of Advanced Robotics Safford   | £14.45 |
| <input type="checkbox"/> | 1001 Things to do with your own personal computer Sawusch                           | £8.50  |
| <input type="checkbox"/> | Easy Programming for the ZX Spectrum Stewart  | £7.15  |
| <input type="checkbox"/> | Microprocessor Applications Handbook Stout  | £34.40 |
| <input type="checkbox"/> | Handbook of Microprocessor Design and Applications Stout                            | £37.50 |
| <input type="checkbox"/> | Programming the PET/IBM West  | £17.80 |
| <input type="checkbox"/> | An Introduction to Microcomputer Technology Williamson                              | £8.20  |
| <input type="checkbox"/> | Computer Peripherals that you can build Wolfe                                       | £12.40 |
| <input type="checkbox"/> | Microprocessors and Microcomputers for Engineering Students and Technicians Wooland | £7.10  |

## REFERENCE BOOKS

|                          |   |        |
|--------------------------|---|--------|
| <input type="checkbox"/> | Electronic Engineers' Handbook Fink                         | £56.45 |
| <input type="checkbox"/> | Electronic Designers' Handbook Giacoletto                   | £59.55 |
| <input type="checkbox"/> | Illustrated Dictionary of Microcomputer Technology Hordeski | £8.45  |
| <input type="checkbox"/> | Handbook for Electronic Engineering Technicians Kauffman    | £27.50 |
| <input type="checkbox"/> | Handbook of Electronic Calculators Kauffman                 | £35.00 |
| <input type="checkbox"/> | Modern Electronic Circuit Reference Manual Marcus           | £44.00 |
| <input type="checkbox"/> | International Transistor Selector Towers                    | £10.70 |
| <input type="checkbox"/> | International Microprocessor Selector Towers                | £16.00 |
| <input type="checkbox"/> | International Digital IC Selector Towers                    | £10.95 |
| <input type="checkbox"/> | International Op Amp Linear IC Selector Towers              | £8.50  |
| <input type="checkbox"/> | Illustrated Dictionary of Electronics Turner                | £12.95 |

## VIDEO

|                          |   |        |
|--------------------------|---|--------|
| <input type="checkbox"/> | Servicing Home Video Cassette Recorders Hobbs           | £12.95 |
| <input type="checkbox"/> | Complete Handbook of Videocassette Recorders Kybett     | £9.25  |
| <input type="checkbox"/> | Theory and Servicing of Videocassette Recorders McGinty | £12.95 |
| <input type="checkbox"/> | Beginner's Guide to Video Matthewson                    | £5.35  |
| <input type="checkbox"/> | Video Recording: Theory and Practice Robinson           | £14.40 |
| <input type="checkbox"/> | Video Handbook Van Wezel                                | £21.90 |
| <input type="checkbox"/> | Video Techniques White                                  | £12.95 |

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing I wish to pay by Access/Barclaycard. Please debit my account.

5 2 2 4

4 9 2 9

Signed.....

Name.....

Address.....

# PROJECT : Novel Loudspeaker


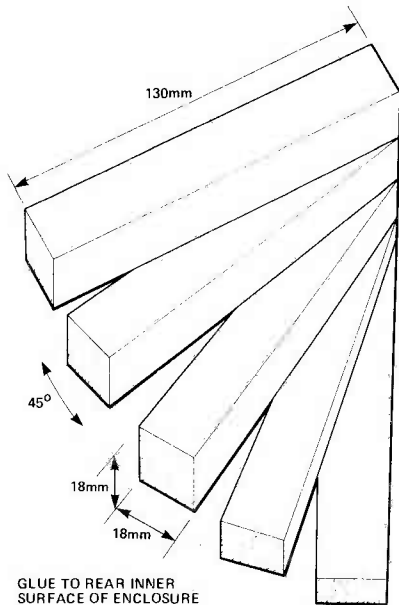


Fig. 6 The 'splasher'.

While the glue on the enclosure is drying, you can get on and produce the 'splasher'. As explained, this simply consists of five pieces of wood laid one-on-top-of-the-other at one end and staggered so as to form a spiral. You will need a clamp or a bench vice or some other means of holding the pieces in the correct position while the glue dries, although it should not be too difficult to devise another means of support if neither of these is available. As with the enclosure itself, the 'splasher' should be left to dry for a reasonably long time and preferably overnight.

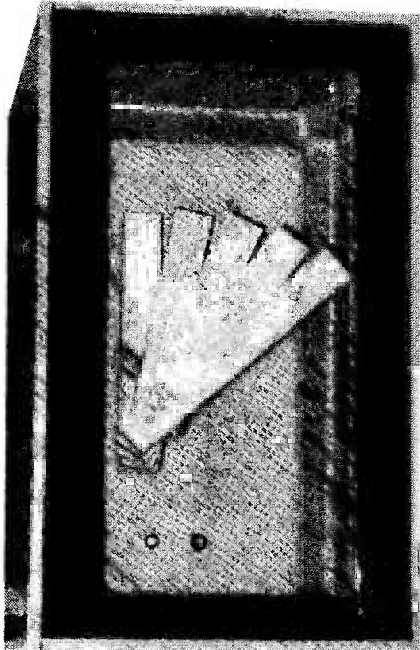

Internal view of an enclosure made of NIMS 127 showing the cork fillets and the 'splasher'. The same construction is used for the MDF board version.

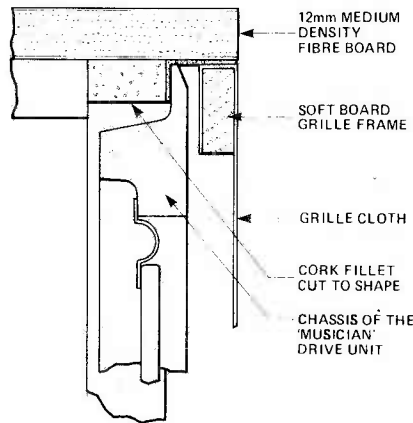


Fig. 7 Vertical cross-section through the enclosure with the Musician drive unit in position.

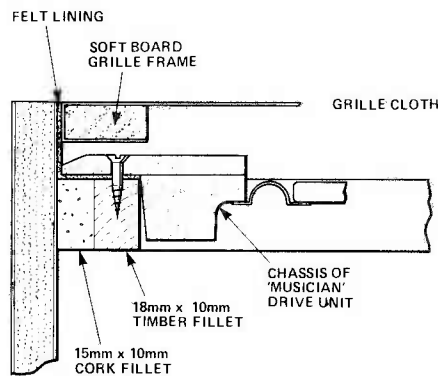


Fig. 8 Horizontal cross-section through the enclosure with the Musician drive unit in position.

When the glue on the enclosure is dry, remove the binding and then seal all of the inside joints with a flexible mastic sealant so as to make the final unit airtight. Depending upon the type of drive unit you are planning to use, identify the spot on the inside back panel directly opposite the driver coil and stick the 'splasher' down. The enclosure can be left on its back whilst the glue dries, but you will still need to tape the 'splasher' in place to stop it tipping over.

If you are using a drive unit other than the Musician loudspeaker, you can now glue the front panel into place. Remember to leave 1 mm gaps around the edges just as you have done with all the other panels. If you are using the Musician drive units, glue the two vertical timber pieces to the cork fillets at the front of the enclosure and support them in place until the glue is dry.

When the final glueing stage is over and the glue is dry, you can finish the exterior surfaces of the enclosure to your taste, either by staining the wood or painting it or

by covering it with veneer or fabric. If you do cover the enclosure with something like veneer remember to expose the gaps between the panels and don't just cover over them. Stick a layer of felt to the inside faces of the front of the enclosure, and make up a simple wooden frame to hold the grille cloth. Provided you make the frame the right size, the cloth will bind against the felt and hold it in place and no other means of support will be necessary. The cloth itself should be as acoustically transparent as possible, and open-weave hessian or something similar is recommended.

The only tasks remaining are to install the drive unit and the input connectors and wire them up. Two 4 mm sockets are ideal as input connectors and only require two small (usually 5/16") holes. If you are using the Musician driver unit, position it within the front of the enclosure and line it up so that it is in the centre of the space. Six holes can then be drilled into the two vertical battens and wood screws used to hold the driver in place. If you are using any other drive unit you will have to devise your own mounting system but for obvious reasons you should avoid using a drive unit which can only be mounted from the rear of the panel. Finally, wire up the drive units to the terminals, loosely fill the cabinets with BAF wadding, secure the drive units in place and then sit back and enjoy them.

## BUYLINES

Medium Density Fibre (MDF) board is widely available from DIY and timber shops, and if you don't have an old cork bathmat to hand you should have no trouble finding someone to sell you a new one. The BAF wadding and the hessian should both be available locally but if you encounter problems you could try Wilmslow Audio who certainly have the wadding and probably have a suitable grille cloth. The Musician drive units are available from Merseyside Acoustic Developments, Merseyside Innovation Centre, 131 Mount Pleasant, Liverpool L3 5TF, tel 051-709 0427, and cost £140.00 per pair inclusive of VAT, carriage and packing. If you don't feel like doing all the hard work but would still like a pair of Musician loudspeakers, they can be obtained from the same address and cost £240.00 inclusive in the 'Basic', MDF board enclosure and £320.00 inclusive in the NIMS 127 enclosures.

ETI

ETI JUNE 1984

# electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 1, Golden Square, London W1R 3AB. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

## BEGINNERS GUIDE

|                          |  |       |
|--------------------------|--|-------|
| <input type="checkbox"/> | Beginner's Guide to Basic Programming Stephenson | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Digital Electronics          | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Electronics                  | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Integrated Circuits          | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Computers                    | £5.35 |
| <input type="checkbox"/> | Beginner's Guide to Microprocessors              | £5.35 |

## COOKBOOKS

|                          |                                     |        |
|--------------------------|-------------------------------------|--------|
| <input type="checkbox"/> | Master IC Cookbook Hallmark         | £10.15 |
| <input type="checkbox"/> | Microprocessor Cookbook M. Hordeski | £7.70  |
| <input type="checkbox"/> | IC Op Amp Cookbook Jung             | £14.25 |
| <input type="checkbox"/> | PLL Synthesiser Cookbook H. Kinley  | £7.70  |
| <input type="checkbox"/> | Active Filter Cookbook Lancaster    | £13.40 |
| <input type="checkbox"/> | TV Typewriter Cookbook Lancaster    | £11.15 |
| <input type="checkbox"/> | CMOS Cookbook Lancaster             | £11.85 |
| <input type="checkbox"/> | TTL Cookbook Lancaster              | £10.95 |
| <input type="checkbox"/> | Micro Cookbook Vol. 1 Lancaster     | £15.30 |
| <input type="checkbox"/> | BASIC Cookbook K. Tracton           | £6.00  |
| <input type="checkbox"/> | MC6809 Cookbook C. Warren           | £7.25  |

## ELECTRONICS

|                          |  |        |
|--------------------------|--|--------|
| <input type="checkbox"/> | Principles of Transistor Circuits Amos                           | £8.50  |
| <input type="checkbox"/> | Design of Active Filters with experiments Berlin                 | £11.30 |
| <input type="checkbox"/> | 49 Easy to Build Electronic Projects Brown                       | £6.00  |
| <input type="checkbox"/> | Electronic Devices & Circuit Theory Boylestad                    | £13.20 |
| <input type="checkbox"/> | How to build Electronic Kits Capel                               | £3.55  |
| <input type="checkbox"/> | How to Design and build electronic instrumentation Carr          | £9.35  |
| <input type="checkbox"/> | Introduction to Microcomputers Daglecs                           | £7.20  |
| <input type="checkbox"/> | Electronic Components and Systems Dennis                         | £15.00 |
| <input type="checkbox"/> | Principles of Electronic Instrumentation De Sa                   | £11.40 |
| <input type="checkbox"/> | Giant Handbook of Computer Software                              | £12.95 |
| <input type="checkbox"/> | Giant Handbook of Electronic Circuits                            | £17.35 |
| <input type="checkbox"/> | Giant Handbook of Electronic Projects                            | £11.75 |
| <input type="checkbox"/> | Electronic Logic Circuits Gibson                                 | £5.55  |
| <input type="checkbox"/> | Analysis and Design of Analogue Integrated Circuits Gray         | £30.25 |
| <input type="checkbox"/> | Basic Electronics Grob   | £11.30 |
| <input type="checkbox"/> | Lasers - The Light Fantastic Hallmark                            | £7.70  |
| <input type="checkbox"/> | Introduction to Digital Electronics & Logic Joynson              | £5.25  |
| <input type="checkbox"/> | Electronic Testing and Fault Diagnosis Loveday                   | £7.85  |
| <input type="checkbox"/> | Electronic Fault Diagnosis Loveday                               | £6.25  |
| <input type="checkbox"/> | Essential Electronics A-Z Guide Loveday                          | £7.50  |
| <input type="checkbox"/> | Microelectronics Digital & Analogue circuits and systems Millman | £12.70 |
| <input type="checkbox"/> | 103 Projects for Electronics Experimenters Minis                 | £8.30  |
| <input type="checkbox"/> | VLSI System Design Muroga  | £34.10 |
| <input type="checkbox"/> | Power FETs and their application Oxner                           | £9.40  |
| <input type="checkbox"/> | Practical Solid State Circuit Design Olesky                      | £25.00 |
| <input type="checkbox"/> | Master Handbook of IC Circuits Powers                            | £12.85 |
| <input type="checkbox"/> | Electronic Drafting and Design Raskhodoff                        | £22.15 |
| <input type="checkbox"/> | VOM - VTVM Handbook Risse  | £8.50  |
| <input type="checkbox"/> | Video and Digital Electronic Displays Sherr                      | £28.85 |
| <input type="checkbox"/> | Understanding Electronic Components Sinclair                     | £7.50  |
| <input type="checkbox"/> | Electronic Fault Diagnosis Sinclair                              | £4.50  |
| <input type="checkbox"/> | Physics of Semiconductor Devices Sze                             | £17.35 |
| <input type="checkbox"/> | Digital Circuits and Microprocessors Taub                        | £32.00 |
| <input type="checkbox"/> | Active Filter Handbook   | £7.60  |
| <input type="checkbox"/> | Designing with TTL Integrated Circuits Texas                     | £15.20 |
| <input type="checkbox"/> | Transistor Circuit Design Texas                                  | £15.20 |
| <input type="checkbox"/> | Digital Systems: Principles and Applications Toccl               | £12.95 |
| <input type="checkbox"/> | Master Handbook of Telephones Traister                           | £10.00 |
| <input type="checkbox"/> | How to build Metal/Treasure Locators Traister                    | £6.00  |
| <input type="checkbox"/> | 99 Fun to Make Electronic Projects Tymony                        | £8.50  |
| <input type="checkbox"/> | 33 Electronic Music Projects you can build Winston               | £6.95  |

## COMPUTERS & MICROCOMPUTERS

|                          |  |        |
|--------------------------|--|--------|
| <input type="checkbox"/> | BASIC Computer Games Ahi                                   | £6.35  |
| <input type="checkbox"/> | From BASIC to PASCAL Anderson                              | £9.95  |
| <input type="checkbox"/> | Mastering Machine Code on your ZX81 T. Baker               | £7.25  |
| <input type="checkbox"/> | UNIX - The Book Banaham                                    | £8.75  |
| <input type="checkbox"/> | Z80 Microcomputer Handbook Barden                          | £10.95 |
| <input type="checkbox"/> | Microcomputer Maths Barden                                 | £11.90 |
| <input type="checkbox"/> | Digital Computer Fundamentals Barter                       | £9.90  |
| <input type="checkbox"/> | Visicalc Book. APPLE Edition Bell                          | £15.55 |
| <input type="checkbox"/> | Visicalc Book. ATARI Edition Bell                          | £15.55 |
| <input type="checkbox"/> | Introduction to Microprocessors Brunner                    | £23.00 |
| <input type="checkbox"/> | Programming your APPLE II Computer Bryan                   | £9.25  |
| <input type="checkbox"/> | Microprocessor Interfacing Carr                            | £7.70  |
| <input type="checkbox"/> | Microcomputer Interfacing Handbook A/D & D/A Carr          | £9.50  |
| <input type="checkbox"/> | Musical Applications of Microprocessors Chamberlain        | £28.85 |
| <input type="checkbox"/> | 30 Computer Programs for the Home Owner in BASIC D. Chance | £9.25  |
| <input type="checkbox"/> | Microcomputers Dirkson                                     | £9.30  |
| <input type="checkbox"/> | APPLE Personal Computer for Beginners Dunn                 | £9.50  |
| <input type="checkbox"/> | Microcomputers/Microcomputers - An Intro Gioone            | £11.80 |

|                          |  |        |
|--------------------------|--|--------|
| <input type="checkbox"/> | Troubleshooting Microprocessors and Digital Logic Goodman                  | £9.25  |
| <input type="checkbox"/> | Getting Acquainted with your VIC 20 Hartnell                               | £8.50  |
| <input type="checkbox"/> | Getting Acquainted with your ZX81 Hartnell                                 | £5.95  |
| <input type="checkbox"/> | Let your BBC Micro Teach you to program Hartnell                           | £7.90  |
| <input type="checkbox"/> | Programming your ZX Spectrum Hartnell                                      | £8.50  |
| <input type="checkbox"/> | The ZX Spectrum Explored Hartnell  | £6.95  |
| <input type="checkbox"/> | How to Design, Build and Program your own working Computer System Haviland | £9.30  |
| <input type="checkbox"/> | BASIC Principles and Practice of Microprocessors Heffer                    | £7.15  |
| <input type="checkbox"/> | Hints and Tips for the ZX81 Hewson   | £5.25  |
| <input type="checkbox"/> | What to do when you get your hand on a Microcomputer Holtzman              | £9.95  |
| <input type="checkbox"/> | 34 More Tested Ready to Run Game Programs in BASIC Horn                    | £7.70  |
| <input type="checkbox"/> | Microcomputer Builders' Bible Johnson                                      | £12.40 |
| <input type="checkbox"/> | Digital Circuits and Microcomputers Johnson                                | £14.55 |
| <input type="checkbox"/> | PASCAL for Students Kemp   | £7.20  |
| <input type="checkbox"/> | The C - Programming Language Kernighan                                     | £18.20 |
| <input type="checkbox"/> | COBOL Jackson  | £9.25  |
| <input type="checkbox"/> | The ZX81 Companion Maunder   | £9.50  |
| <input type="checkbox"/> | Guide to Good Programming Practice Meek                                    | £6.40  |
| <input type="checkbox"/> | Principles of Interactive Computer Graphics Newman                         | £13.95 |
| <input type="checkbox"/> | Theory and Practice of Microprocessors Nicholas                            | £11.35 |
| <input type="checkbox"/> | Exploring the World of the Personal Computer Nilles                        | £12.95 |
| <input type="checkbox"/> | Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll     | £9.80  |

|                          |   |        |
|--------------------------|---|--------|
| <input type="checkbox"/> | Beginner's Guide to Microprocessors Parr  | £5.35  |
| <input type="checkbox"/> | Microcomputer Based Design Peatman  | £11.30 |
| <input type="checkbox"/> | Digital Hardware Design Peatman   | £9.80  |
| <input type="checkbox"/> | BBC Micro Revealed Ruston   | £9.45  |
| <input type="checkbox"/> | Handbook of Advanced Robotics Safford   | £14.45 |
| <input type="checkbox"/> | 1001 Things to do with your own personal computer Sawusch                           | £8.50  |
| <input type="checkbox"/> | Easy Programming for the ZX Spectrum Stewart  | £7.15  |
| <input type="checkbox"/> | Microprocessor Applications Handbook Stout  | £34.40 |
| <input type="checkbox"/> | Handbook of Microprocessor Design and Applications Stout                            | £37.60 |
| <input type="checkbox"/> | Programming the PET/CBM West  | £17.80 |
| <input type="checkbox"/> | An Introduction to Microcomputer Technology Williamson                              | £8.20  |
| <input type="checkbox"/> | Computer Peripherals that you can build Wolfe                                       | £12.40 |
| <input type="checkbox"/> | Microprocessors and Microcomputers for Engineering Students and Technicians Wooland | £7.10  |

## REFERENCE BOOKS

|                          |   |        |
|--------------------------|---|--------|
| <input type="checkbox"/> | Electronic Engineers' Handbook Fink                         | £56.45 |
| <input type="checkbox"/> | Electronic Designers' Handbook Giacometto                   | £59.55 |
| <input type="checkbox"/> | Illustrated Dictionary of Microcomputer Technology Hordeski | £8.45  |
| <input type="checkbox"/> | Handbook for Electronic Engineering Technicians Kauffman    | £27.50 |
| <input type="checkbox"/> | Handbook of Electronic Calculators Kauffman                 | £35.00 |
| <input type="checkbox"/> | Modern Electronic Circuit Reference Manual Marcus           | £44.00 |
| <input type="checkbox"/> | International Transistor Selector Towers                    | £10.70 |
| <input type="checkbox"/> | International Microprocessor Selector Towers                | £16.00 |
| <input type="checkbox"/> | International Digital IC Selector Towers                    | £10.95 |
| <input type="checkbox"/> | International Op Amp Linear IC Selector Towers              | £8.50  |
| <input type="checkbox"/> | Illustrated Dictionary of Electronics Turner                | £12.95 |

## VIDEO

|                          |   |        |
|--------------------------|---|--------|
| <input type="checkbox"/> | Servicing Home Video Cassette Recorders Hobbs           | £12.95 |
| <input type="checkbox"/> | Complete Handbook of Videocassette Recorders Kybett     | £9.25  |
| <input type="checkbox"/> | Theory and Servicing of Videocassette Recorders McGinty | £12.95 |
| <input type="checkbox"/> | Beginner's Guide to Video Matthewson                    | £5.35  |
| <input type="checkbox"/> | Video Recording: Theory and Practice Robinson           | £14.40 |
| <input type="checkbox"/> | Video Handbook Van Wezel                                | £21.90 |
| <input type="checkbox"/> | Video Techniques White                                  | £12.95 |

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing. I wish to pay by Access/Barclaycard. Please debit my account.

5 2 2 4

4 9 2 9

Signed.....

Name.....

Address.....

# CLEF ELECTRONIC MUSIC

## MICROSYNTH

2<sup>1</sup>/<sub>2</sub> Octave Music Synthesizer with two Oscillators, two Sub-Occts, Switched Routing and Thumbwheel. A comprehensive instrument offering the full range of Synth Music & effects.

FULL KIT £137 Also available in 3 parts

## PERCUSSION MICROSYNTH

Two Channel Touch Sensitive unit plus variable angle L.F.O. phaser, internal and external triggering

COMPONENT KIT £89



## BAND-BOX PROGRAMMABLE BACKING TRIO

THREE PIECE BACKING BAND  
Generates the sounds of three instrumentalists to back Soloists

DRUMS + BASS + KEYBOARDS  
Over 3,000 chord changes (60 scores) on 132 different chords - extendable to 200 scores. Master Rhythm also required.  
FULL KIT £235 EXTENSION £82

## 88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation of Piano Key Inertia



### COMPONENT KITS

including Keyboard  
88 NOTE £286  
72 NOTE £234  
The above may also be purchased in four parts.

### DOMESTIC KITS


inc. Cabinet, P.A. & Spkr.  
88 NOTE £442  
72 NOTE £398

### STAGE MODEL

inc. Cabinet & Stand  
72 NOTE £383

ALL PRICES INC. VAT, CARR. & TELEPHONE ADVICE  
S.A.E. for full Specs & MANF. PRICES. VISA-ACCESS  
American Express.

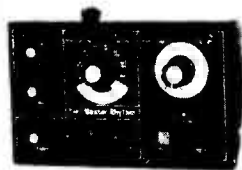11A BRAMHALL LANE, SOUTH BRAMHALL,  
STOCKPORT, CHESHIRE SK11 6AA  
TEL 061334 3297



## MASTER RHYTHM PROGRAMMABLE DRUMS

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.  
COMPLETE KIT £79

STRING ENSEMBLE £198.50  
ROTOR-CHORUS £98.00

SQUARE FRONT KEYBOARDS  
88 NOTE £60 49 NOTE £29  
73 NOTE £50 30 NOTE £19  
KEYSWITCH ITEMS ALSO AVAILABLE

# DISCO's & BANDS



You may know MJL as suppliers of band and theatre systems, but we are now pleased to announce the introduction of a number of products for the disco market. The first two, the digi modulator, a high performance sound to light with programmable automatic chase, and digi chaser, a computer pre-programmed chaser-sequencer with 640 light changes locked away in its EPROM memory. It's impossible to explain in this small space the advantages of such high technology, and we know you don't want to pay any more for the product just so we can take more advertisement space, so how's this: Write or give us a phone call, and we will mail you our colour brochures on all of our lighting packages, including the famous ROCK 12 DESK.

Sales Manager, MJL SYSTEMS LTD,  
45 Wortley Road, W. Croydon, Surrey CR0 3EB  
Tel: 01-689 4138 (Mon-Fri 9-5)

**MJL - power from the future**

# Happy Memories

| Part type             | 1 off | 25-99 | 100 up |
|-----------------------|-------|-------|--------|
| 4116 200ns            | 1.25  | 1.15  | 1.10   |
| 4164 200ns            | 4.95  | 4.40  | 4.20   |
| 2016 150ns            | 4.20  | 3.75  | 3.60   |
| 6116 150ns Low power  | Call  | Call  | Call   |
| 6264 150ns            | Call  | Call  | Call   |
| 2716 450ns 5 volt     | 3.85  | 3.45  | 3.30   |
| 2732 450ns Intel type | 4.20  | 3.75  | 3.60   |
| 2532 450ns Texas type | 3.85  | 3.45  | 3.30   |
| 2764 250ns            | Call  | Call  | Call   |
| 27128 300ns           | Call  | Call  | Call   |

|          |       |          |       |          |       |
|----------|-------|----------|-------|----------|-------|
| Z80A-CPU | £2.99 | Z80A-PIO | £2.99 | Z80A-CTC | £2.99 |
| 6522 PIA | £3.70 | 7805 reg | £0.50 | 7812 reg | £0.50 |

### Low profile IC sockets:

|       |    |    |    |    |    |    |    |    |    |
|-------|----|----|----|----|----|----|----|----|----|
| Pins  | 8  | 14 | 16 | 18 | 20 | 22 | 24 | 28 | 40 |
| Pence | 12 | 13 | 14 | 16 | 18 | 22 | 24 | 27 | 38 |

Soft-sectored floppy discs per 10 in plastic library case:  
5 inch SSSD £17.00. 5 inch SSDD £19.25. 5 inch DSDD £21.00.  
5 inch SSQD £23.95. 5 inch DSQD £26.35.

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.

Please add 50p post & packing to orders under £15 and VAT to total.  
Access & Visa welcome. 24hr 'phone service on (054 422) 618  
Government & Educational orders welcome, £15 minimum.  
Trade accounts operated, 'phone or write for details.


## Happy Memories (ETI)

Gladestry, Kington, Herefordshire HR5 3NY  
Tel: (054 422) 618 or 628

## Interak 1
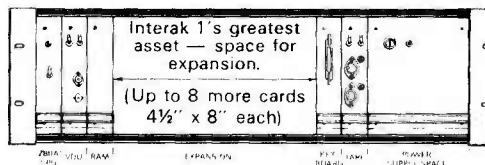
### A METAL Z80A COMPUTER

Colleges, Universities, Individuals: Build your own modular Z80A-based metal 19" rack and card Interak computer. Uses commonly available chips - not a single ULA in sight (and proud of it). If you can get your own parts (but we can supply if you can't) all you need from us are the bare p.c.b.s and the manuals.



(P.c.b.s range in price from £10.95 to £17.75 + VAT; manuals £1 - £5.)

The Interaktion User Group has 14K BASIC, Assembler, Fig Forth, Disassembler, Debug, Chess and a Book Library, Newsletters etc. No fears about this one going obsolete - now in its fifth successful year! Send us your name and address with a 21p stamp and we'll send you 40 pages of details (forget the stamp if you can't afford it!) You've already got a plastic computer for playing games, now build a metal one to do some real work. Interak, Interak, Interak!

## Greenbank

Greenbank Electronics (Dept T6E), 92 New Chester Road,  
New Ferry, Wirral, Merseyside L62 5AG  
Telephone: 051-645 3391

# DETAIL FOR DETAIL

**There's a lot of talk about the 'detail' that any piece of hi-fi gives in its sound. However, there's another sort of detail in hi-fi — the sort that you've got to get right. Stan Thatcher takes a look.**

**A**fter a house and a car, a quality hi-fi system is often the most expensive purchase many of us make. Whether your system is home constructed, bought, or a combination of the two, the amount of money you have spent or propose to spend makes it imperative to realise the full potential of every pound. In pursuit of this objective, there are several minor details to look for when buying and setting up your hi-fi which, for little or no extra expenditure, will greatly augment the detail and sound quality of your system.

As a starting point, try to buy your equipment from a specialist dealer, whose business is installing good sound into peoples homes, and not also selling washing machines, videos and Pac Man games. He will let you listen to all the components of the system in a single speaker demonstration lounge — "A what?", I hear you ask. It is a lounge with just one pair of speakers in it. This is crucial if you are auditioning speakers, because if the pair you are listening to are stacked in a pile with a load of others, the drive units of the speakers you are not auditioning will move in sympathy with the ones you are listening to, seriously upsetting the stereo imagery. One final note on dealers. If the system sounds fine in the shop, but disappointing when you get it home, a serious, committed dealer will let you take the speakers back after a day and let you try another pair until you are completely satisfied.


Once your system is purchased or built, care and attention to details when setting it up in your room will prove well worthwhile. There are many obvious points. Ensure that the pick up arm is tracking at the right weight for the cartridge being used, and of course, don't use a worn stylus! You can get special alignment aids to set up the arm, and this may be well worth considering. Ideally your turntable should be shelf mounted, to isolate it as far as possible from sound vibrations. If you have a really good turntable, you might like to investigate the "coffee tables" which have been designed specifically for the purpose. I personally haven't tried one yet, though I am assured they offer sonic advantages over other, more conventional methods of mounting a turntable.

Given that you have set your turntable up correctly and are getting as much information out of the groove as possible, make sure the connections between the turntable and the amplifier are as tight as possible. For a few pounds you can buy high quality connecting leads which will see that more information gets through (and that you

have fewer problems with bad contacts — Ed.). Any good dealer can supply these.

The information has now passed through the amplifier and is heading for your speakers, and it is this link in the chain, the speaker cable, where the most dramatic improvement can be made. To many this must sound an incredible claim, but, think about it, wires do differ in sonic quality as well as electrical qualities. Cable has varying amounts of capacitance, inductance and resistance, and, yes, you've guessed it, these all add to or, rather, subtract from the sound quality. An obvious example comes to mind if you consider the effect of resistance, ie wasted power. A thicker cable will carry the signal with greater ease, and less of the amplifiers efforts end up as wasted heat. Elementary electronics really! With inductance and capacitance putting their oar in, designing sonically superior cable has almost become as scientific as designing an amplifier! So what sort of cable should you use, and what is the effect on sound going to be?

Once the effect of cable was truly acknowledged, many manufacturers set out in pursuit of the perfect cable, with varying degrees of success, and at various costs to the consumer. There must be some twenty varieties on the market by now, with costs ranging from 25p per metre to, wait for it, £90! I do not recommend spending £90 on a metre of cable. I have auditioned a few cables of various costs and find the difference between them marginal compared to the difference between any of them and standard cable or bell wire, the most widely used type. My personal recommendation is QED 79-strand cable, which doesn't cost an arm and a

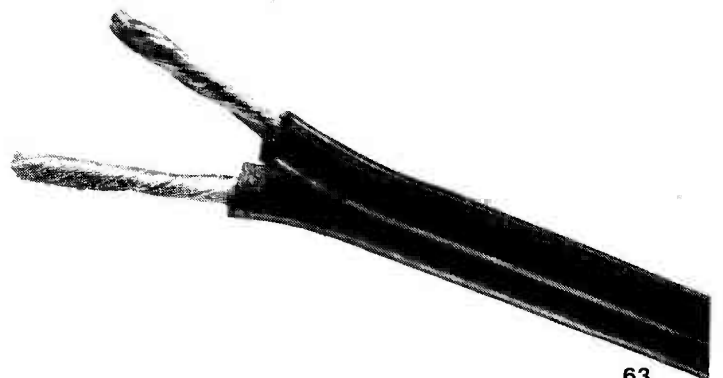



# FEATURE : Detail

leg, and is I believe the best selling cable currently on the market. Retailing at a modest 77p per metre, the manufacturers claim: "QED 79-strand cable directly improves the amplifier's ability to control damping of the loudspeaker's drive units, thus avoiding the blurring effects". A tighter sound is therefore what they are claiming.

My own experience, having auditioned the cable (alongside a couple of others) is that the use of superior cable goes much further. Apart from tightening up the bass, the resultant sound is a greater feeling of naturalness and openness, with detail coming through that simply wasn't there with ordinary cable. It is as if previously there had been curtains in front of the speakers. Stereo imagery also seems significantly improved. If there is any doubt in your mind, then just listen for yourself. For a few pounds (I am not convinced of the superiority of more expensive cables) you will dramatically improve the sound of your system.

Finally, positioning the speakers themselves. Bookshelf speakers are intended to be mounted on a shelf; more than this, they are designed to go on a shelf, and in many cases, this means unless they are mounted with a wall close behind them, they will give a very poor bass performance if mounted on a stand. Not surprisingly, stand-mounted speakers give rather too much bass if mounted on a shelf or on the floor. It's not unknown for people to mount speakers sideways on the floor behind a settee, and then to complain about there being too little treble! It really can make a lot of difference to speaker performance if you follow the manufacturer's suggestions...

Finally, having tightened up all the details, it's time to put on your favourite record, sit back and enjoy the music, because that's what it's all about.



ETI

# HENRY'S AUDIO ELECTRONICS

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS

VISIT OR PHONE • OPEN 6 DAYS A WEEK • ALL PRICES INC VAT

## STEREO TUNER/AMPLIFIER

4 wave-band stereo tuner amplifier by GEC MW/LW/SW/stereo FM radio. 10 • 10 watt stereo amplifier. Inputs for PU tape in/out. Supplied as two assembled units. **£21.95** as illustrated (UK C/P £1.50)

## CASSETTE MECHANISMS

Fitted counter, motor, record and erase heads, solenoid, etc. Brand new available 6V DC or 12V DC (state which) **£5.95** (UK C/P 65p)

## TOROIDAL TRANSFORMER

100 watts isolation 230/240 V AC plus 8-0 8V 4A 15 0-15V 0 645A 30V 0.16A Size approx 4" dia x 1 1/2" **£7.95** (UK C/P 75p)

## ASTEC UHF MODULATORS

UM1233 cased for computers, etc. **£3.50** C/P 40p

## MULLARD MODULES

LP1171 IF and LP1179 AM/FM Tuner pr **£5.75**  
LP1186 Varicap Tuner **£5.00**  
LP1157 AM Tuner **£2.50**

## PRESTEL ADAPTOR

3 card set with data etc (P/S +/- 12V and +5V) **£69.95** inc. VAT

## MODERN CARD

BT approved ready assembled unit with data and accessories **£29.95** inc. VAT

## QWERTY KEYBOARDS

+5V and -12V suitable P/S **£8.95** c/p 60p

## 69SD5

Exclusive Special Purchase compact hall effect 64 keys plus 5 function keys -ve/+ve strobe ASCII but all definable, steel frame all facilities UK c/p **£1.00** **£35.00**

69 key ASCII, General purpose, steel plate Redefinable output, +5 and -12V supply, neg. strobe pulse, 4 user definable keys, shift & control key, etc. **£42.95** (UK C/P 65p)

## I.T.T. 2020 CABINET

Professional Computer Case 18" x 15 1/2" x 4 1/2" (front slopes). As previously advertised. **£27.50** inc. VAT (UK C/P £2.50)

## THERMAL MATRIX & LINE PRINTER

**NEW LOW PRICE**

COMPLETE WITH FULL HANDBOOK 3 ROLLS PAPER (UK post etc £1.05) (List approx £187) **£49.95** inc. VAT  
SUITABLE FOR TANDY • BBC • ORIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc. (interface unit with leads £13 - state model) (Your enquiries invited)

STOCKISTS FOR Frequency counters - Signal generators Power supplies - Plus huge range of components, tools accessories and parts for callers. Send large SAE for leaflets (state items)

## DIGITAL MULTIMETERS

Hand Held Models All feature AC/DC volts. DC Amps (Many with AC Amps) Ohms etc (UK C/P 65p) **models with carry case**  
Controls S - Slide R - Rotary PB - Push Button

KD25C ■ 12 range 0.2A DC 2 Meg ohm (S) **£26.95**  
KD30S ■ 14 range 10A DC 2 Meg ohm (S) **£27.95**  
KD30C ■ 26 range 1A AC/DC 20 Meg ohm (R) **£33.50**  
METEX 3000 ■ 30 range 10A AC/DC 20 Meg ohm (R) **£37.95**  
6010 ■ 28 range 10A AC/DC 20 Meg ohm (P8) **£37.95**  
KD55C ■ 28 range 10A AC/DC 20 Meg ohm (R) **£39.95**  
KD615 ■ 18 range 10A DC 2 Meg ohm Plus HFE tester (R) **£39.95**  
7030 ■ As 6010 but 0.1% basic (PB) **£47.50**  
DM3350 ■ Autorange plus Cont. Tester 18 ranges 10A AC/DC 2 Meg ohm (R) **£49.95**  
Bench Models (UK C/P £1.00)  
TM355 3% Digit 29 range LED 10A AC/DC 20 Meg ohm **£97.75**  
TM356 3% Digit 27 range LCD 10A AC/DC 20 Meg ohm **£109.25**

## GENERATORS

(UK C/P £1.00)  
LSG17 RF 100KHZ to 150MHZ (Up to 450MHZ Harmonics) **£109.25**  
SG402 RF 100KHZ to 30MHZ **£82.80**  
AG202A Audio Sine/Square 20HZ to 200KHZ **£102.35**  
LAG27 Audio sine/Square 10HZ to 1MHZ **£106.95**

## MULTIMETERS

(UK C/P 65p)  
HC6015 15 range pocket 10K/Volt **£8.50**  
M200 30 range 20K/Volt. Many features 20KHz (list £21.85) **£9.95**  
HM102BZ 22 range 20K/Volt 10A DC Plus cont Buzzer 10 Meg ohm **£13.50**  
TMK500 23 range bench 30K/Volt De luxe. 12A DC, plus cont. Buzzer, 20 Meg ohm **£23.95**  
NH56R 22 range 10K/Volt 6 Meg ohm **£11.95**  
830A 26 range 30K/Volt 10 AC/DC 10 Meg ohm **£23.95**  
YN360TR 19 range 20K/Volt plus HFE tester 1 Meg ohm **£13.95**  
ST303TR 22 range 20K/Volt plus HFE tester 12A DC 1 Meg ohm **£17.95**  
KRT5001 Range doubler 35 ranges 50K/volt 10A DC 20 Meg ohm **£19.95**

## HIGH VOLTAGE METER

Direct reading 0/40 KV 20K/Volt **£25.30** (UK C/P 65p)

## DIGITAL CAPACITANCE METER

(UK C/P 65p)  
0.1pF to 2000 mfd LCD 8 ranges **DM6013 £59.95**

## TRANSISTOR TESTER

Meter reading NPN/PNP Hfe and leakage also diode test **£26.95** (UK C/P 65p)

## OSCILLOSCOPES

Specifications any model, send SAE. Single Trace (UK C/P £3.50)

3030 15MHZ 5mV plus components tester (Crotech) **£177.10**  
HM103 10MHZ 2mV plus components tester (Hameg) **£181.70**  
SC110A • 10MHZ battery portable (Thandar) **£189.75**  
\* Carry case £6.84 AC Adaptor £7.99  
Dual Trace (UK C/P £4.50)  
CS1562A 10MHZ with 2 probes (Trio) **£299.95**  
HM203 20MHZ plus components tester (Hameg) **£303.60**  
3132 20MHZ plus component comparator (Crotech) **£325.45**  
CS1566A 20MHZ with 2 probes (Trio) **£374.90**  
HM204 20MHZ sweep delay plus component tester (Hameg) **£419.75**  
V212 20MHZ with 2 probes (Hitachi) **£339.25**  
V203F 20MHZ sweep delay with 2 probes (Hitachi) **£431.25**

## OPTIONAL PROBE KITS

X1 - £7.95, X10 - £9.45, X1/X10 - £11.50.

## ORDER BY POST OR PHONE.

Order by Post with CHEQUES ACCESS: Visa or you can telephone your orders. All orders despatched within 5 days unless advised

**HENRY'S** Shop at 404-406 Edgware Road, London, W2 Computers 01-402 6822 Equipment 01-724 0323 Components 01-723 1008

**AUDIO ELECTRONICS** Shop at 301 Edgware Road, London, W2 Test Equipment, Audio Communications 01-724 3564

Details any model send S.A.E.

All mail to Cubegate Ltd 1st floor, 406 Edgware Road, London, W2 1ED

# CORTEX CENTRONICS INTERFACE

Any follow-up on the Cortex is long overdue, for which we apologise. We're now about to start setting this to rights.

The Cortex 16-bit computer was designed in late 1982 and was featured by ETI in the November 1982, December 1982 and January 1983 editions. It is based on the TMS9995 16-bit microprocessor with a full 64K byte main memory and a separate 16K byte memory for the colour graphics display. The machine can be expanded by simply adding chips to provide features such as floppy disc support and an expansion bus for extra memory, input and output. This article details how to use the EBUS bus expansion to plug an external board into your Cortex to provide a parallel data interface for a Centronics printer.

The E-BUS was developed to provide a compact, high-performance and flexible interface for both memory and input/output expansion. The E-BUS system multiplexes both addresses and data information onto its lines at different times, so as to keep the number of lines needed as low as possible. It can be shared by multiple microprocessors for access to common memory or I/O.

With regard to I/O expansion, some explanation of the computer's operation is necessary. When doing input and output operations, the CPU does not communicate in eight or 16-bit words, in contrast to most common processors which support dedicated I/O commands. Instead, the 9995 sends and receives just one bit at a time. This means that multi-bit input and output functions, like those needed for a Centronics printer for instance, have to be built up or broken down one bit at a time.

However, this operation is made simpler by the fact that each bit can be sent to or received from a unique address. So, to output eight bits to a peripheral, it is necessary to transfer the bits to a latch or similar device with eight successive single bit operations. Only then can the peripheral be told that the data is ready to be acted upon.

An input cycle occurs when the MEMEN (memory enable) control signal goes high (inactive); the bit address is output on the address/data bus and the single bit of data is sampled on the CRUIN signal. An output cycle is similar, except that the data bit is output on the CRUOUT signal and the CRUCLK control signal pulses active low. For multi-bit transfers, the cycle repeats with the address incrementing each time. A timing diagram for this is shown in Fig. 1.

During an I/O operation, the multiplexed address/data lines are forced to output the address

throughout the I/O cycle so no address latches are required, consequently the ALATCH (address latch) control signal remains high. The data bit to be sent appears as the signal CRUOUT on the least significant address line (A15 by the TI convention) when an output operation is performed. The remaining 15 address lines define 32768 addresses to which it can be sent, although the Cortex and the 9995 CPU use some of these addresses internally (see Fig. 2, the Cortex I/O map).

A data bit to be read in is taken via the CRUIN line. Up to 16 bits can be input or output by a single instruction, the specified number of bits being processed serially to or from the target addresses.

## The E-BUS

The kernel of the E-BUS interface on the Cortex is the 74LS-2001 gate array. This device is used to control access to the bus

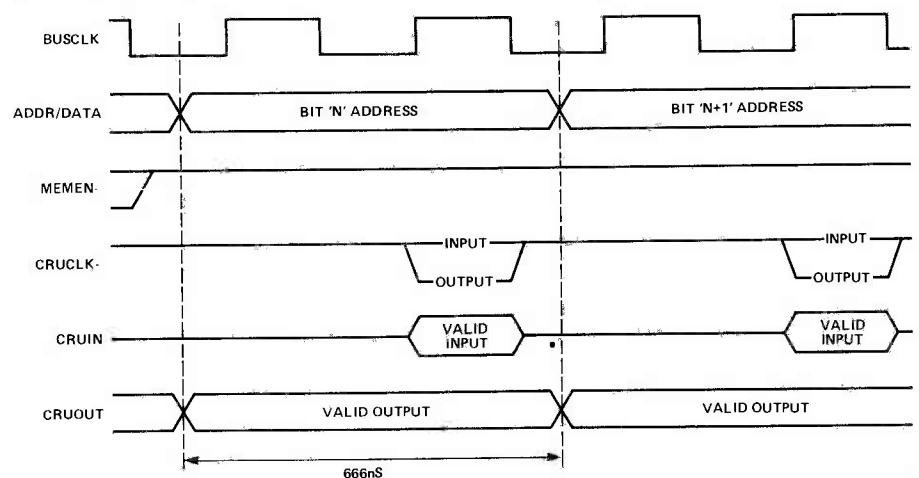


Fig. 1 Timing diagram for multi-bit transfers.

| Address      | Input Function              | Output Function            |
|--------------|-----------------------------|----------------------------|
| 0000         | NOT USED*                   | "BASIC" LED                |
| 0002         | NOT USED                    | KEYBOARD ACKNOWLEDGE       |
| 0004         | DISK SIZE JUMPER            | EBUS INTERRUPT ACK         |
| 0006         | DISK DENSITY JUMPER         | EBUS TIMEOUT ENABLE        |
| 0008         | FLOPPY INTERRUPT FLAG       | DISK SIZE                  |
| 000A         | KEYBOARD INTERRUPT FLAG     | EPROM ON/OFF               |
| 000C         | KEYBOARD INTERRUPT FLAG     | "BELL" ENABLE              |
| 000E         | EBUS TIMEOUT INTERRUPT FLAG | NOT USED                   |
| 0010 to 001E | KEYBOARD DATA               | DUPLICATE OF ABOVE         |
| 0020 to 003E | DUPLICATE OF ABOVE          | DUPLICATE OF ABOVE         |
| 0040 to 007E | NOT USED                    | NOT USED                   |
| 0080 to 00BE | TMS 9902                    | TMS 9902                   |
|              | RS232 PORT                  | RS232 PORT                 |
| 00C0 to 017E | NOT USED                    | NOT USED                   |
| 0180 to 01BE | TMS 9902                    | TMS 9902                   |
|              | CASSETTE PORT               | CASSETTE PORT              |
| 01C0 to 01FE | TMS 9911                    | TMS 9911                   |
|              | DMA CONTROLLER              | DMA CONTROLLER             |
| 0200 to 07FE | external via EBUS           | external via EBUS          |
| 0800 to 080E | external via EBUS           | Centronics data via EBUS   |
| 0810         | external via EBUS           | Centronics strobe via EBUS |
| 0812         | Centronics status via EBUS  | external via EBUS          |
| 0814 to 1EDE | external via EBUS           | external via EBUS          |
| 1EE0         | CPU internal                | CPU internal timer control |
| 1EE2         | " "                         | " " timer interrupt        |
| 1EE4         | " "                         | " " enable                 |
| 1EE6         | " " level 1 interrupt flag  | " " " 3 " "                |
| 1EE8         | " " " 4 " "                 | " " " 4 " "                |
| 1EEA         | " " **                      | " " **                     |
| 1EEC         | " " ***                     | " " ***                    |
| 1F00 to 1FD8 | " " not used                | " " not used               |
| 1FDA         | CPU internal MID flag       | CPU internal               |
| 1FDC to FFFE | external via EBUS           | external via EBUS          |

\* Some systems may have this used for floppy disk interface  
\*\* Cortex Basic uses this bit to enable the display on the TV screen of all control characters.  
\*\*\* Cortex Basic uses this bit to disable the scrolling of a text display on the TV screen.

Fig. 2 (above) Cortex I/O map.

for multiple microprocessors and to synchronise all data transfers, as well as to provide time-out controls to avoid a permanent lock-up of the bus. However, for simple expansion of the Cortex facilities, it is possible to avoid using this device. Four changes to the main PCB have to be made, as follows:

1. Cut the connection to IC99 pin 18 and connect this pin to IC94 pin 11;
2. Connect IC94 pin 9 to IC11 pin 13;
3. Connect IC94 pin 19 to IC27 pin 2;
4. Connect IC89 pin 18 to IC89 pin 19.

For this modification to work, the

### HOW IT WORKS


IC1a, IC1b and IC2 decode address bits A4 to A11 inclusive. Two outputs from IC2 are used each of which will go low when one of their particular group of eight addresses is accessed. Note that the address decoding is not complete and may well respond at other locations (2K interval). The Y1 output from IC2 (address 0088h to 008Fh) enables the output of IC4 (74LS251) the 1 of 8 selector. This device selects the signal on the input specified by the least significant address lines and passes it to the CRUIN line. This would normally be the printer status line in this case and its state will signal whether the printer is ready to receive data.

The data to be output to the printer appears on the CRUOUT line in serial form. This has to be converted to parallel form before being presented to the printer. This is done by IC3 which is an eight bit addressable latch (74LS259). Address lines A12, 13 and 14 determine which bit is to be written into IC3 and the output Y0 of IC2 gated with CRUCLK in IC1d actually causes it to happen. To write a complete eight bits of new data requires eight output cycles. Once this has been done the data is ready to be acted upon by the printer. IC5 is another 74LS259 like IC3 and one bit of its output is used as a strobe signal to tell the printer that the data is ready. Output Q0 is used in this case; it is normally low and is pulsed high under software control. This happens when a 1 and then a 0 is output to 0088h.

For the transfer of one character the sequence is as follows: eight bits of data are written into the eight locations in IC3. The data then appears in parallel form at its output and is available to the printer. The DATA STROBE is taken high and then low to signal to the printer that valid data is ready. The printer signals that it is BUSY by taking the BUSY STATUS line high. This is read by the computer and no further action is taken until it goes low again. Now new data can be sent to IC3 and the process repeated.

Note that some printers give a low on the status line to indicate the BUSY condition, this can be accommodated by connecting the EBUS CRUIN line to IC4 pin 6 instead of pin 5. More difficult is when the STROBE has to be inverted, this requires an additional inverter.

Fig. 3 Interface circuit.

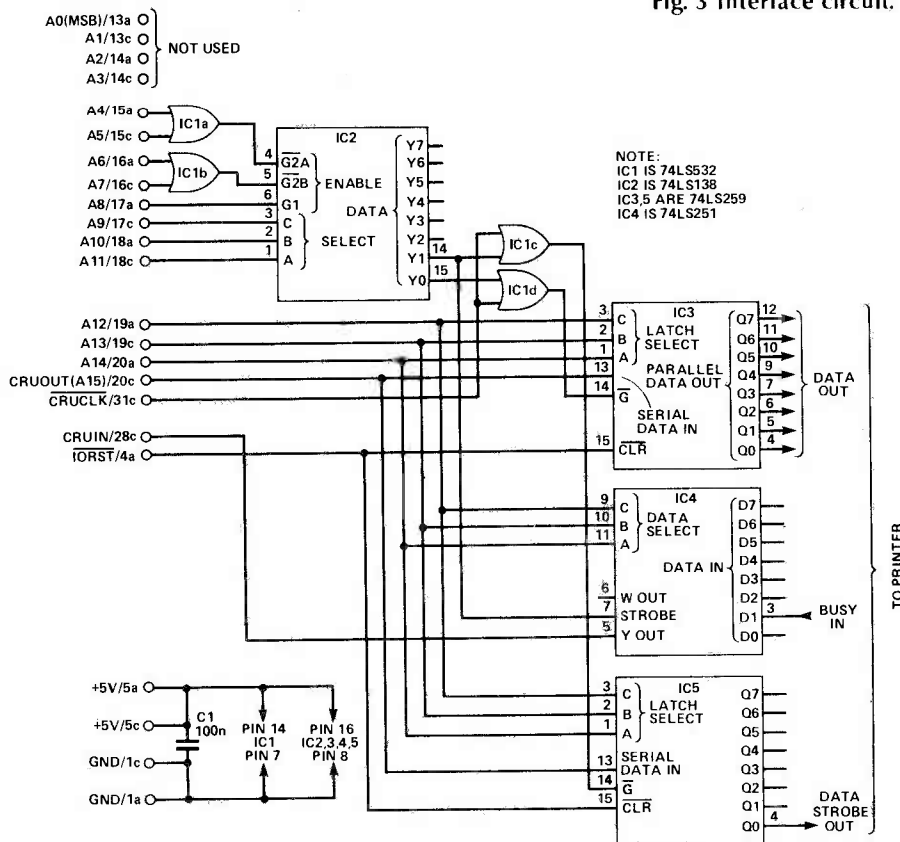

# PROJECT : Cortex Centronics

following devices must be present on the PCB (if your Cortex does not have all the options available, then some of these may be missing, so you will need to check): IC90 (74LS08), IC91 (74LS32), IC92 (74LS74A), IC93 (74LS00), IC94,95,96 and 99 (all 74LS244).

If you wish to use memory expansion, then you must break the links next to IC26 and drill out the shorting links next to IC94, and ensure that you have IC97 (74LS245) and IC26 (74LS612). Note that all the component numbers used here are those given in the original Cortex article.

## It's Already There

Although the Cortex has an RS232 interface for a printer or terminal, it also has the software necessary to drive a parallel data printer port. The hardware necessary to implement this was left off the main PCB to save space. Building the interface described here will therefore free the RS232 for other tasks, and make it possible to use the more common Centronics printers.

The circuit diagram for the

| I/O | ROW A               | PIN | ROW C                     | I/O |
|-----|---------------------|-----|---------------------------|-----|
|     | GND 0V              | 1   | GND 0V                    |     |
| I/O | PRES- (RESET-)      | 2   | BUSCLK (3MHz)             | O   |
|     | +12V                | 3   | -12V                      |     |
| O   | IORST- (I/O RESET-) | 4   | NMI-(NON-MASKABLE INT)    | I   |
|     | +5V                 | 5   | +5V                       |     |
|     | —                   | 6   | —                         |     |
|     | —                   | 7   | —                         |     |
|     | —                   | 8   | —                         |     |
|     | —                   | 9   | —                         |     |
| I   | INTEN- (LEVEL 1)    | 10  | ALATCH (ADDRESS LATCH)    | O   |
| O   | XA0 (MSB ADDRESS)   | 11  | XA1                       | O   |
| O   | XA2                 | 12  | XA3                       | O   |
| O   | A0                  | 13  | A1                        | O   |
| O   | A2                  | 14  | A3                        | O   |
| O   | A4                  | 15  | A5                        | O   |
| O   | A6                  | 16  | A7                        | O   |
| I/O | A8/D8 (DATA MSB)    | 17  | A9/D9                     | I/O |
| I/O | A10/D10             | 18  | A11/D11                   | I/O |
| I/O | A12/D12             | 19  | A13/D13                   | I/O |
| I/O | A14/D14             | 20  | A15/D15/CRUOUT (LSB)      | I/O |
|     | —                   | 21  | MEMEN- (MEMORY ENABLE)    | O   |
| O   | DEN- (MEMORY READ)  | 22  | READY- (MEMORY READY)     | I   |
| I   | GRANTIN             | 23  | GRANTOUT                  | O   |
|     | —                   | 24  | BUSY- (BUS BUSY)          | I/O |
|     | GND                 | 25  | GND                       |     |
|     | —                   | 26  | —                         |     |
|     | —                   | 27  | —                         |     |
|     | —                   | 28  | CRUIN (I/O INPUT)         | I   |
| O   | WE- (MEMORY WRITE)  | 29  | —                         |     |
|     | +5V                 | 30  | +5V                       |     |
|     | —                   | 31  | CRUCLK (I/O WRITE STROBE) | O   |
|     | GND                 | 32  | GND                       |     |

Fig. 4 EBUS signals and their uses.

interface is shown in Fig. 3 and the circuit itself is discussed in the 'How It Works' section.

Next month we will publish the PCB, overlay, parts list and buy-lines.

ETI


## FOR HI-FI & ELECTRONICS ENTHUSIASTS CONCEPT ELECTRONICS LTD

51 Tollington Road, London N7 6PB

Mail order only

We are the specialist of electronic kits and rack mounting cabinets. A catalogue with complete range of products including pre-amp modules, power amp modules, pre and power amplifier modules, complete kits of amplifiers, equalizers, reverberation amplifiers (with cases), alarm clocks, appliance timers, CB amplifiers, test equipment, control modules, music generator, battery fluorescent light and high quality rack mounting cabinets etc. with illustrative pictures now available at the cost of 35p + 25p p&p.

### Professional rack mounting cabinet

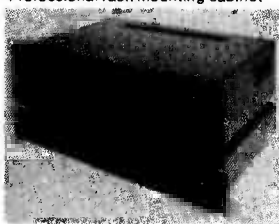

| Panel Size<br>WH (inch) | Rear Box        |             | Price           |             |
|-------------------------|-----------------|-------------|-----------------|-------------|
|                         | WH D            | AL STEEL    | WH D            | AL STEEL    |
| 19 x 5                  | 17 x 4.5 x 10   | 27.54 23.54 | 17 x 4.5 x 10   | 27.54 23.54 |
| 19 x 4                  | 17 x 3.5 x 10   | 25.24 21.24 | 17 x 3.5 x 10   | 25.24 21.24 |
| 19 x 3.5                | 17 x 3 x 10     | 24.09 20.09 | 17 x 3 x 10     | 24.09 20.09 |
| 19 x 3                  | 17 x 2.5 x 10   | 24.09       | 17 x 2.5 x 10   | 24.09       |
| 19 x 2.5                | 17 x 2 x 10     | 22.94 18.94 | 17 x 2 x 10     | 22.94 18.94 |
| 19 x 6                  | 17 x 5.5 x 12   | 28.69 24.69 | 17 x 5.5 x 12   | 28.69 24.69 |
| 19 x 5                  | 17 x 4.5 x 12   | 27.54 23.54 | 17 x 4.5 x 12   | 27.54 23.54 |
| 19 x 4                  | 17 x 3.5 x 12   | 25.24 21.24 | 17 x 3.5 x 12   | 25.24 21.24 |
| 19 x 3.5                | 17 x 3 x 12     | 24.09 20.09 | 17 x 3 x 12     | 24.09 20.09 |
| 17 x 3.5                | 15.5 x 3 x 9    | 21.79 17.79 | 15.5 x 3 x 9    | 21.79 17.79 |
| 17 x 2.5                | 15.5 x 2 x 9    | 20.64 16.64 | 15.5 x 2 x 9    | 20.64 16.64 |
| 17 x 4                  | 15.5 x 3.5 x 12 | 25.24 21.24 | 15.5 x 3.5 x 12 | 25.24 21.24 |
| 17 x 3                  | 15.5 x 2.5 x 12 | 24.09 20.09 | 15.5 x 2.5 x 12 | 24.09 20.09 |

Please add £2.50 p/p per item

★ Wholly made of black anodised aluminium sheets ★ Suitable for high quality amplifiers and many other purposes ★ Top, side and rear cover removable for access ★ Separate front mounting plate ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet.

The low cost steel version is also available. The size and features as well as the front panel is the same as the aluminium cabinets except the rear box is manufactured from steel painted in black.

### CONTROL MODULES



- TY-7 Electronic touch switch £2.90 Kit £4.50 Ass.
- TY-11 Light activated switch £2.20 Kit £3.50 Ass.
- TY-18 Sound activated switch (Clap switch) £4.50 Kit £5.95 Ass.
- TY-38 Sound activated switch (voice-switch) £5.50 Kit £7.50 Ass.
- TY-41 Infra-red remote control (Receiver and transmitter) £17.20 Kit £21.95 Ass.

### HI-FI AMPLIFIER MODULES



- TA-323A 30W + 30W stereo amplifier £18.95 Kit £23.95 Ass.
- TA-820 60W + 60W stereo amplifier £27.50 Kit £33.50 Ass.
- TA-920 70W + 70W stereo amplifier £35.50 Kit £42.50 Ass.

# KITS FROM £7 ...TO £60


## Sparkrite

Buy Sparkrite Brand Leading Auto Electronics in self-assembly kit form – And save pounds!!

- Electronic Ignition systems – contact triggered and contactless
- Electronic Car Security Systems – including a new ultrasonic unit
- Car Drive Computer – with 12 functions

SEND FOR FREE LITERATURE PACK – TODAY!

8 SOPHISTICATED  
KITS TO CHOOSE  
FROM.

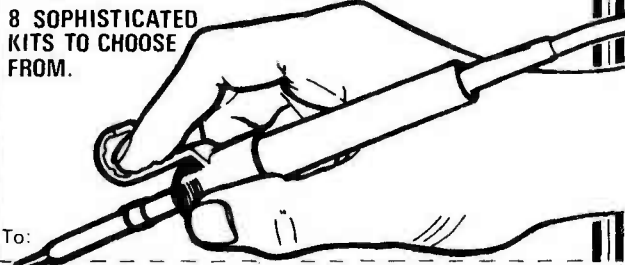

To:

SPARKRITE (A Division of Stadium Ltd.), Queensway, Enfield, EN3 4SD.  
Telephone: 01-804 4343

NAME .....


ADDRESS .....

ETI


---

---

# PCB FOIL PATTERNS

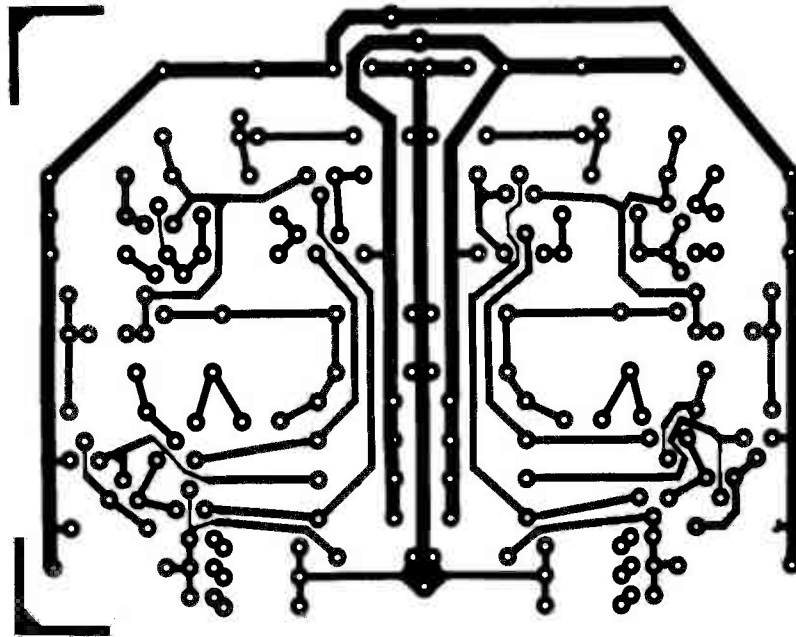


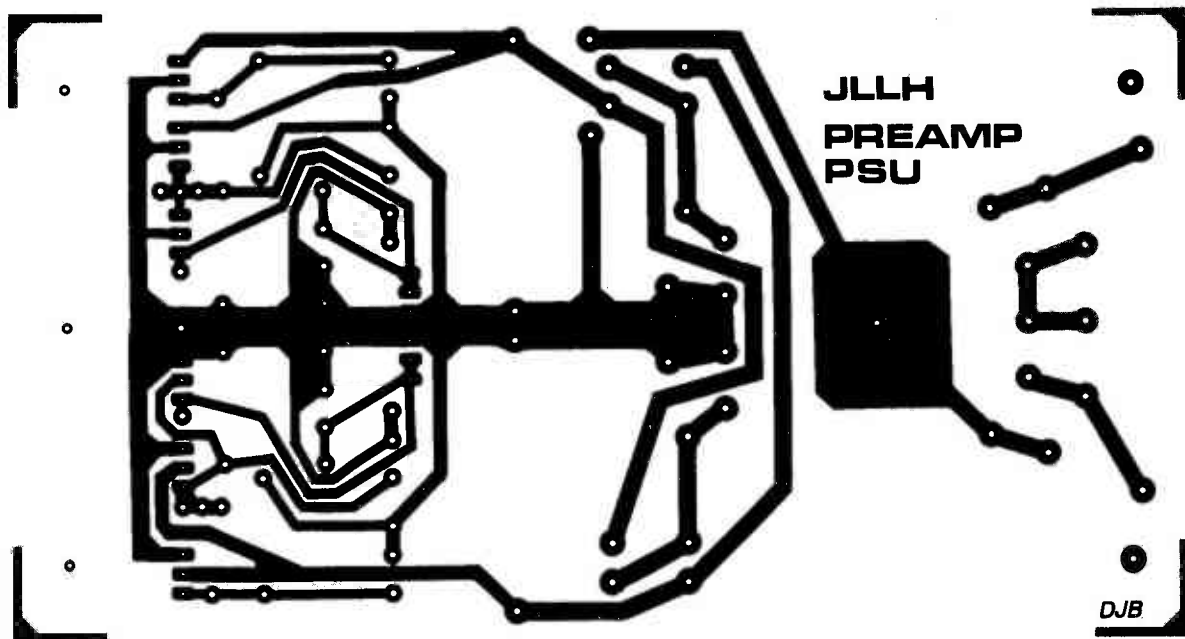The RIAA input board of the JLLH amplifier.




The PSU board of the JLLH amplifier.




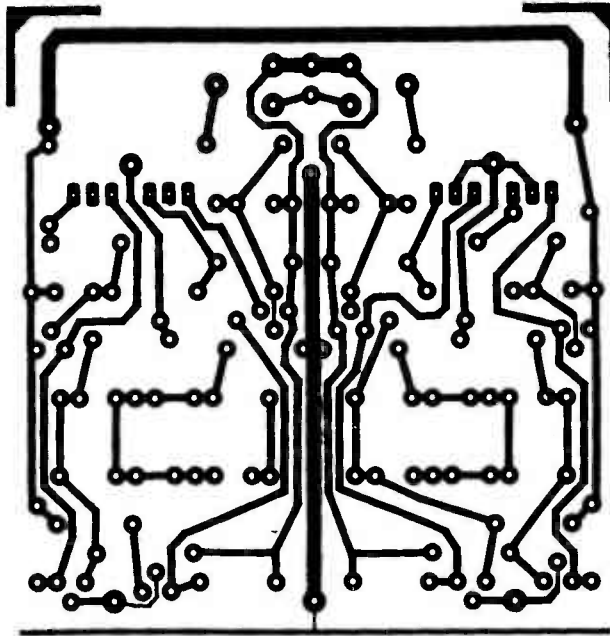

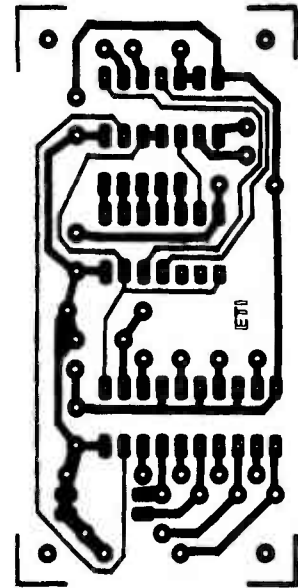The headphone amplifier board of the JLLH amplifier.



The Spectrum Joystick Interface board.

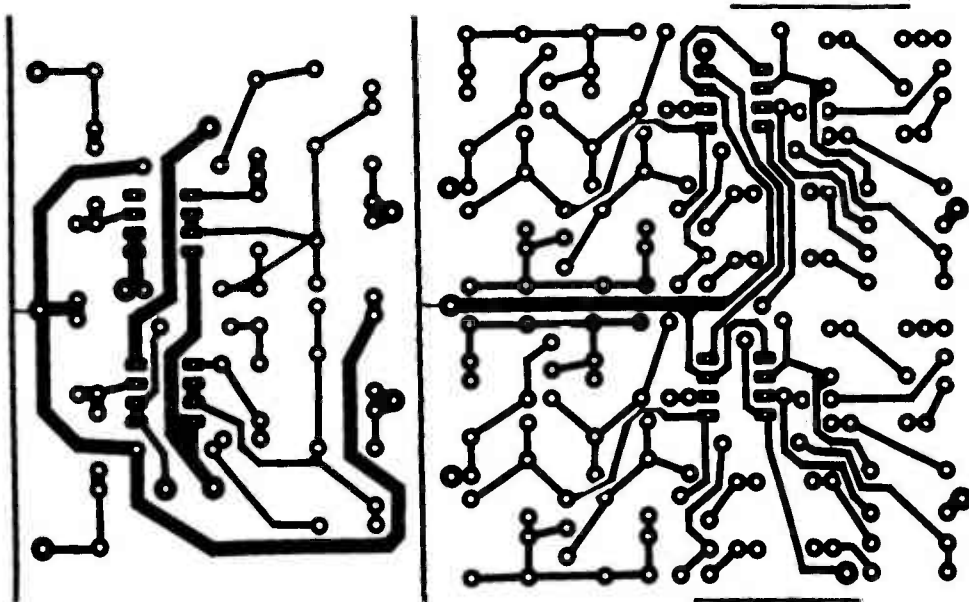

The buffer/filter and tone control board of the JLLH amplifier.

# ETI PCB SERVICE

In order to ensure that you get the correct board, you must quote the reference code when ordering. The code can also be used to identify the year and month in which a particular project appeared: the first two numbers are the year, the third is the month and the number after the hyphen indicates the particular project.

Note that these are all the boards that are available — if it isn't listed, we don't have it.

Our terms are strictly cash with order — we do not accept official orders. However, we can provide a pro-forma invoice for you to raise a cheque against, but we must stress that the goods will not be dispatched until we receive payment.

- |  |   |  |
|--|---|--|
| <p>1979</p> <ul style="list-style-type: none"> <li><input type="checkbox"/> E/794-1 Guitar Effects Unit ..... 3.04</li> <li><input type="checkbox"/> E/794-2 Click Eliminator..... 7.64</li> </ul> <p>1980</p> <ul style="list-style-type: none"> <li><input type="checkbox"/> E/808-3 Ultrasound Burglar Alarm 3.30</li> <li><input type="checkbox"/> E/8010-1 Cassette Interface ..... 3.37</li> <li><input type="checkbox"/> E/8010-2 Fuzz/Sustain Box ..... 3.76</li> <li><input type="checkbox"/> E/8012-3 Four Input Mixer..... 3.04</li> </ul> <p>1981</p> <ul style="list-style-type: none"> <li><input type="checkbox"/> E/811-1 LED Tacho ..... 4.75</li> <li><input type="checkbox"/> E/811-2 Multi-Option Siren..... 3.68</li> <li><input type="checkbox"/> E/812-2 IR Alarm (4 boards) ..... 7.64</li> <li><input type="checkbox"/> E/812-5 Pulse Generator ..... 4.11</li> <li><input type="checkbox"/> E/814-2 Drum Machine (2 boards) 6.44</li> <li><input type="checkbox"/> E/814-4 Guitar Note Expander ..... 3.68</li> <li><input type="checkbox"/> E/816-8 Waa-Phase..... 1.76</li> <li><input type="checkbox"/> E/816-9 Alien Attack..... 4.00</li> <li><input type="checkbox"/> E/817-1 System A-Input<br/>(MM or MC)..... 3.05</li> <li><input type="checkbox"/> E/817-2 System A — Preamp. .... 5.95</li> <li><input type="checkbox"/> E/817-3 Smart Battery Charger..... 2.27</li> <li><input type="checkbox"/> E/818-3 Hand Clap Synth..... 4.57</li> <li><input type="checkbox"/> E/818-5 Watchdog Home<br/>Security (2 boards) ..... 6.11</li> <li><input type="checkbox"/> E/819-1 Mains Audio Link<br/>(3 boards) ..... 8.45</li> <li><input type="checkbox"/> E/819-4 Laboratory PSU..... 5.21</li> <li><input type="checkbox"/> E/8110-1 Enlarger Timer..... 3.91</li> <li><input type="checkbox"/> E/8110-2 Sound Bender..... 3.05</li> <li><input type="checkbox"/> E/8111-1 Voice Over Unit..... 4.57</li> <li><input type="checkbox"/> E/8111-2 Car Alarm..... 3.23</li> <li><input type="checkbox"/> E/8111-3 Phone Bell Shifter..... 3.40</li> <li><input type="checkbox"/> E/8112-4 Component Tester..... 1.71</li> </ul> <p>1982</p> <ul style="list-style-type: none"> <li><input type="checkbox"/> E/821-3 Guitar Tuner (2 boards) ... 6.38</li> <li><input type="checkbox"/> E/822-1 Ripple Monitor ..... 2.21</li> <li><input type="checkbox"/> E/822-2 Allez Cat Pest Repeller .... 1.93</li> <li><input type="checkbox"/> E/822-5 Moving Magnet Stage ..... 4.01</li> <li><input type="checkbox"/> E/822-6 Moving Coil Stage ..... 4.01</li> <li><input type="checkbox"/> E/823-4 Capacitance Meter<br/>(2 boards) ..... 11.66</li> <li><input type="checkbox"/> E/825-1 DV Meg..... 3.13</li> <li><input type="checkbox"/> E/826-1 Ion Generator<br/>(3 boards) ..... 9.20</li> <li><input type="checkbox"/> E/826-4 MOSFET Amp Module..... 7.80</li> <li><input type="checkbox"/> E/826-5 Logic Lock ..... 3.52</li> </ul> | <ul style="list-style-type: none"> <li><input type="checkbox"/> E/826-6 Digital PWM ..... 3.84</li> <li><input type="checkbox"/> E/826-7 Optical Sensor ..... 2.00</li> <li><input type="checkbox"/> E/826-9 Oscilloscope<br/>(4 boards) ..... 13.34</li> <li><input type="checkbox"/> E/827-7 TV Bargraph Main..... 5.24</li> <li><input type="checkbox"/> E/827-3 TV Bargraph Channel..... 2.62</li> <li><input type="checkbox"/> E/827-4 Hotwire..... 3.02</li> <li><input type="checkbox"/> E/827-5 Bridging Adapter ..... 2.74</li> <li><input type="checkbox"/> E/828-1 Playmate (3 boards)..... 8.28</li> <li><input type="checkbox"/> E/828-4 Kitchen Scales..... 2.12</li> <li><input type="checkbox"/> E/829-1 Auto Volume Control..... 2.12</li> <li><input type="checkbox"/> E/829-2 Dual Logic Probe ..... 2.22</li> <li><input type="checkbox"/> E/8211-4 Pulse Generator ..... 6.08</li> <li><input type="checkbox"/> E/8212-1 ELCB ..... 2.77</li> <li><input type="checkbox"/> E/8212-2 Servo Interface<br/>(2 boards) ..... 6.75</li> <li><input type="checkbox"/> E/8212-4 Spectracolumn ..... 5.54</li> </ul> <p>1983</p> <ul style="list-style-type: none"> <li><input type="checkbox"/> E/831-1 Fuel Gauge..... 3.45</li> <li><input type="checkbox"/> E/831-2 ZX ADC..... 2.59</li> <li><input type="checkbox"/> E/831-3 Programmable PSU..... 3.45</li> <li><input type="checkbox"/> E/833-1 SoundBoard..... 12.83</li> <li><input type="checkbox"/> E/833-2 Alarm Module ..... 3.62</li> <li><input type="checkbox"/> E/833-3 ZX81 User Graphics ..... 1.07</li> <li><input type="checkbox"/> E/833-4 Logic Probe ..... 2.50</li> <li><input type="checkbox"/> E/834-1 Real Time Clock ..... 8.74</li> <li><input type="checkbox"/> E/834-2 Thermometer<br/>(2 boards) ..... 9.74</li> <li><input type="checkbox"/> E/834-4 Stage Lighting — Main ... 13.73</li> <li><input type="checkbox"/> E/834-5 Stage Lighting — Display 3.45</li> <li><input type="checkbox"/> E/835-1 Compressor/Limiter ..... 6.19</li> <li><input type="checkbox"/> E/835-2 Single PSU..... 3.16</li> <li><input type="checkbox"/> E/835-3 Dual PSU ..... 4.01</li> <li><input type="checkbox"/> E/835-4.2 NDFL Amp ..... 7.88</li> <li><input type="checkbox"/> E/835-5 Balance Input Preamp..... 3.23</li> <li><input type="checkbox"/> E/835-6 Stage Lighting<br/>Autofade..... 6.19</li> <li><input type="checkbox"/> E/835-7 Stage Lighting —<br/>Triac Board..... 4.74</li> <li><input type="checkbox"/> E/836-1 to 3 PseudoROM<br/>(3 boards) ..... 3.62</li> <li><input type="checkbox"/> E/836/4 Immersible Heater ..... 2.30</li> <li><input type="checkbox"/> E/836-5 Atom Keypad..... 5.18</li> <li><input type="checkbox"/> E/837-1 Flash Sequencer ..... 2.67</li> <li><input type="checkbox"/> E/837-2 Trigger Unit Main Board... 2.67</li> <li><input type="checkbox"/> E/837-3 Trigger Unit Transmitter... 1.66</li> <li><input type="checkbox"/> E/837-4 Switched Mode PSU ..... 16.10</li> <li><input type="checkbox"/> E/838-1 Graphic Equaliser ..... 9.10</li> </ul> | <ul style="list-style-type: none"> <li><input type="checkbox"/> E/838-2 Servo Fail-Safe<br/>(four-off)..... 2.93</li> <li><input type="checkbox"/> E/838-3 Universal EPROM prog.... 9.64</li> <li><input type="checkbox"/> E/839-1 NiCad Charger/Regen..... 3.77</li> <li><input type="checkbox"/> E/839-2 Digger..... 3.40</li> <li><input type="checkbox"/> E/839-3 64K DRAM..... 14.08</li> <li><input type="checkbox"/> E/8310-1 Supply Protector ..... 2.19</li> <li><input type="checkbox"/> E/8310-2 Car Alarm..... 3.98</li> <li><input type="checkbox"/> E/8310-3 Typewriter Interface ..... 4.17</li> <li><input type="checkbox"/> E/8311-1 Mini Drum Synth ..... 3.07</li> <li><input type="checkbox"/> E/8311-2 Alarm Extender..... 3.21</li> <li><input type="checkbox"/> E/8311-3 Multiswitch ..... 3.59</li> <li><input type="checkbox"/> E/8311-4 Multiple Port ..... 4.34</li> <li><input type="checkbox"/> E/8311-5 DAC/ADC Filter ..... 3.22</li> <li><input type="checkbox"/> E/8311-6 Light Pen ..... 4.60</li> <li><input type="checkbox"/> E/8311-7 Logic Clip..... 2.51</li> <li><input type="checkbox"/> E/8311-8 MC Head (JLLH)..... 3.17</li> <li><input type="checkbox"/> E/8312-1 Lightsaver..... 1.85</li> <li><input type="checkbox"/> E/8312-2 A-to-D Board..... 12.83</li> <li><input type="checkbox"/> E/8312-3 Light Chaser (2 bds) ..... 7.54</li> <li><input type="checkbox"/> E/8312-4 ZX Alarm ..... 6.04</li> </ul> <p>1984</p> <ul style="list-style-type: none"> <li><input type="checkbox"/> E/841-1 Vector Graphics ..... 8.27</li> <li><input type="checkbox"/> E/842-1 Speech Board<br/>(Mini-Mynah) ..... 10.97</li> </ul> <p>MODULAR PREAMP:</p> <ul style="list-style-type: none"> <li><input type="checkbox"/> E/842-2 Disc input (mono) ..... 3.73</li> <li><input type="checkbox"/> E/842-3 Output stage (stereo) ..... 3.73</li> <li><input type="checkbox"/> E/842-4 Relay/PSU ..... 3.73</li> <li><input type="checkbox"/> E/842-5 Tone, main (mono)..... 3.73</li> <li><input type="checkbox"/> E/842-6 Tone, filter (stereo) ..... 3.73</li> <li><input type="checkbox"/> E/842-7 Balanced output (st) ..... 3.73</li> <li><input type="checkbox"/> E/842-8 Headphone amp (st) ..... 3.73</li> <li><input type="checkbox"/> E/842-9 Mother board ..... 9.01</li> <li><input type="checkbox"/> E/843-1 Power Meter ..... 5.81</li> <li><input type="checkbox"/> E/843-2 Z80 DRAM..... 9.79</li> <li><input type="checkbox"/> E/843-3 Obedient Die..... 3.76</li> <li><input type="checkbox"/> E/844-1 School Timer ..... 4.07</li> <li><input type="checkbox"/> E/845-1 Auto Light Switch ..... 4.01</li> <li><input type="checkbox"/> E/845-2 ZX81 EPROM Prog. .... 10.53</li> <li><input type="checkbox"/> E/845-3 Mains Borne RC ..... 5.07</li> <li><input type="checkbox"/> E/845-4 Centronics Interface ..... 4.09</li> <li><input type="checkbox"/> E/845-5 Vario ..... 6.62</li> <li><input type="checkbox"/> E/845-6 Midi Drum Synth ..... 3.59</li> <li><input type="checkbox"/> E/846-1 Oric EPROM Bd ..... £19.58</li> <li><input type="checkbox"/> E/846-2 Spectrum Joystick ..... £3.30</li> </ul> |
|--|---|--|

**How to order:** indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Signed .....

Name .....

Address .....

Total for boards £.....  
 Add 45p p&p 0.45  
 Total enclosed £.....

**PLEASE ALLOW  
28 DAYS FOR  
DELIVERY**

# ELECTRONICS TODAY INTERNATIONAL CLASSIFIED

## Lineage:

40p per word (minimum 15 words)


**Semi Display: (minimum 2 cms)**

£11.00 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

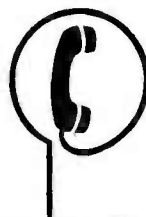Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699

Send your requirements to:  
Debbie Miller  
ASP Ltd.,  
1 Golden Square,  
London W1.

## EQUIPMENT

### CONSTRUCTING AN AUDIO MIXER?

*To achieve a high quality finish you need commercially produced printed panels — sub-frames — main frames etc designed and manufactured specifically for this purpose.*

### PARTRIDGE ELECTRONICS

THE MIXER PEOPLE

56 Fleet Road, Benfleet, Essex, SS7 5JN, England.  
(Large S.A.E. please)

## FOR SALE

**QUALITY HI-FI** Stereoamp Decks £30 inc... Professionally finished + wood-effect case... Mag.PU/Tape/Headphones... 60+60W/Auto Protection/240V... (M.R.P. £69.63) KIA-8, LS29 9DZ.

**ASSORTED S.R.B.P.**, s/speed average 7x5"... 120" £1.. 240" £2 etc. Inclusive — Mr Heal, Taberhill, Marchington, Woodlands, Uttoxeter, Staffs.

**RESISTOR BARGAIN PACKS**, 600 resistors, 1Ω to 10meg Ω 60 values, 10 each value. Cheque or P.O. for £4.85 to W.C.R., 1-3 Blyth St., Seaton Deval, Whitley Bay, Tyne & Wear.

**SHEET METAL FOLDERS** 18" x 18G bench or vice held £38. Leaflet 01-890 7838 (anytime). 90 Granville Av, Feltham, Middx TW13 4JN.

## WANT RESULTS? THEN USE ETI CLASSIFIED

### ADD-ONS

**TANGERINE OWNERS.** We have available an independant switch selectable RAM card to free the Eprom space on Tanex P.C.B. on built. S.A.E. for details. Ralph Allen Eng, Forncett-End, Norwich. Tel (095389) 420.

### SERVICES

**P.C.B. DESIGN & LAYOUT**, manually taped artwork professionally produced at competitive prices. J. Gledhill. Tel: 01-674 8511.

**PRINTED CIRCUIT BOARDS** made to your drawings. Artwork carried out. One offs and small quantities acceptable. Ask for quote. Fennel Industrial Electronics (0203) 382296. 35 Fife Street, Nuneaton, Warwickshire.

**FREE PROTOTYPE** of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited. Tel: halstead (0787) 477408.

### VIDEO TERMINAL BOARD

★ 80 characters x 24 lines ★

Requires ASCII encoded keyboard and monitor to make fully configurable intelligent terminal. Uses 6802 micro and 6845 controller. Program and character generator (7 x 9 matrix with descenders) in two 2716 EPROMS. Full scrolling at 9600 baud with 8 switch selectable rates. RS 232 interface.

Bare board with 2 EPROMS and program listing — £48 plus VAT.

Send for details or CWO to:

**A M ELECTRONICS (T)**  
Wood Farm, Leiston, Suffolk IP164HT  
Tel: 0728 831131

**BRITISH TELECOM** plug sockets & leads etc. Tel C.W.A.S. (0274) 731532. Or visit our showroom opposite Odsal Stadium, Bradford.

### WEST HYDE

THE UK'S LEADING STOCKIST OF CASES, PANELWARE AND ACCESSORIES

Large Stocks — Fast Deliveries

SEND £2 FOR COMPREHENSIVE, ILLUSTRATED CATALOGUE — Includes £2 Worth of Vouchers

UNIT 9, PARK ST. IND. ESTATE  
AYLESBURY BUCKS HP20 1ET  
Telephone: (0296) 20441

**OSCILLOSCOPE** — Tektronix portable D32, Mains/rechargeable, dual trace, case, service manual, working £85. 01-441 1050 daytime.

**Car stereo cassette player**, 4W.p.c. into 4 ohm, slider vol. controls, f.f. eject button, auto-stop, 13.2V DC. —ve. ground. Colour: black size: h41X-w137Xd145mm. (Japanese) £12.50. **Rear window, surface mounting car speakers**, 5W 4 ohm £3.99 pair. 8W 4 ohm. 2-way £21.55.

**25+25W r.m.s.** (4 ohm) 5-band equaliser booster for car stereo (X-80) £22.

**Universal battery charger** for AA(HP7), C(HP11), D(HP2), and PP3 £7.50.

Prices include postage.

Cash with order to:

**L.E.G.S. LTD**  
334 Dickenson Road, Longsight  
Manchester M13 0NG  
(Mail Order Only)

## REPAIRS

**MICRO-COMPUTER** repairs. ZX Spectrum, VIC 20, C64 Pets, Commodore computers, printers and floppy disk. Phone Slough (0753) 48785. Monday to Saturday.

## ILLUSTRATION SERVICE

**SUPERB ILLUSTRATION.**  
01-836 3653.

## SITUATIONS VACANT

### Assistant Maintenance Engineer

At a leading London Recording Studio.

Must have practical electronic experience and driving licence. Apply with C.V. to:

**Peter Suthers**  
11 a Sharples Hall Street  
London NW1

### JBA ELECTRONICS

Manufactures to design or specifications. One offs, small batch prototypes. Analogue digital electronic equipment. Complete electronic service — no job too small.

1st Floor, 4a Lion Yard  
Brecon, Powys, South Wales  
Tel: (0874) 611177

## ALARMS

# ALARMS

**FREE BOOKLET**  
on  
**BURGLAR ALARMS**  
with  
**LOWEST U.K. DIY PUBLISHED PRICES**  
PHONE OR WRITE FOR YOUR COPY  
**051-523 8440**  
**AD ELECTRONICS**  
217 WARBRECK MOOR  
AINTREE, LIVERPOOL L9 0HU

## A1 INTRUDER ALARMS

**Wholesale Alarm Suppliers**  
Latest D.I.Y. & Wholesale Published Catalogue.  
Write off for your copy  
**86 Derby Lane, Old Swan, Liverpool 13**  
Tel: 051 228 3483 or 051-220 0590

**TIMED ENTRY EXIT CONTROL ALARM - PANEL**  
CONTROL PANEL  
MAINS - BATT.  
MODEL 9000E  
- ONLY -  
£29.50 INC.

2 ZONE - £33-89

**FULL 2 YEAR GUARANTEE**

- Adjustable entry-exit with buzzer.
- Regulated power supply (1-2 amp).
- Latching 24 hour circuit.
- Visual & audible walk test.

PLEASE SEND FOR **FREE CATALOG** OF **ALARM EQUIPMENT** FROM  
**SIMPSONS ELECTRONIC ALARMS**  
70 PRIORITY ROAD, LIVERPOOL L4 2RZ  
TRADE SUPPLIES  
051-260-0300

## SECURITY Alarm Systems

**FREE COMPREHENSIVE CATALOGUE!**

- **LOWEST DISCOUNT PRICES**
- **HIGHEST QUALITY EQUIPMENT**
- **FREE DIY DESIGN GUIDE**
- **FULLY ILLUSTRATED**
- **MICROCHIP CIRCUITRY**
- **QUICK DESPATCH SERVICE**
- **FULL INSTRUCTIONS**

SENO SAE OR PHONE

C. TEC SECURITY, Dept E 1,  
60 Market St, Wigan WN1 1HX  
Telephone (0942) 42444

Trade Enquiries Welcome

**LARGE STOCK OF BURGLAR ALARM EQUIPMENT.** As used in the trade. JN Security Centre, 176 Sydenham Rd., London SE26 5J2. 01-778 1111. Showrooms open 6 days.

**BURGLAR Alarm Equipment.** Please visit our 2,000 sq. ft. showrooms or write or phone for your free catalogue. C.W.A.S. Ltd., 100 Rooley Avenue, Bradford BD6 1DB. Telephone 0274 731532.

## COMPUTERS FOR SALE

**CORTEX COMPUTER** built and working, with RS232. £295. Telephone: 0206 251658. Evening/week-ends.

## WIRES 'N CABLES

**THE SCIENTIFIC WIRE COMPANY**  
811 Forest Road, London E17  
01-531.1588

**ENAMELLED COPPER WIRE**

|       |       |      |      |      |
|-------|-------|------|------|------|
| SWG   | 1lb   | 8oz  | 4oz  | 2oz  |
| 8-34  | 3.63  | 2.09 | 1.10 | 88p  |
| 35-39 | 3.82  | 2.30 | 1.26 | 93p  |
| 42-43 | 5.20  | 2.91 | 2.25 | 1.60 |
| 44-47 | 8.56  | 5.80 | 3.49 | 2.75 |
| 48    | 15.96 | 9.58 | 6.38 | 3.69 |

**SILVER-PLATED COPPER WIRE**

|       |      |      |      |      |
|-------|------|------|------|------|
| 14-30 | 9.09 | 5.20 | 2.93 | 1.97 |
|-------|------|------|------|------|

**TINNED COPPER WIRE**

|       |      |      |      |      |
|-------|------|------|------|------|
| 14-30 | 3.97 | 2.41 | 1.39 | 0.94 |
|-------|------|------|------|------|

Prices include P&P and VAT. Orders under £2 add 20p. Dealer inquiries welcome.

**COMPONENTS, COMPUTERS etc**  
*We will help you sell them*

## COMPONENTS

**Selling any components?**  
**Wish to reach the Hobby market?**  
**Then try Hobby Electronics Classified**  
**01-437 0699**

**RESISTORS**

|                |              |
|----------------|--------------|
| C.F. 5%        | M.F. 4w      |
| HI-STAB        | HI-STAB      |
| 1/4w E24 1p ea | 1% 4p ea E24 |
| 1/2w E24 2p ea | 2% 3p ea E24 |

**CAPACITORS**

**TANTALUM BEAD**

|  |
|--|
| 35v 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 14p ea |
| 25v 6.8 20p ea                               |
| 16v 4.7, 10mf 16p ea                         |
| 16v 2.2 12p ea                               |
| 16v 4.7 14p ea                               |
| 16v 10mf 20p ea                              |

Terms C.W.O. £5.00 Min Order  
P.Paid + VAT @ 15%

**E.C.P.S.**  
7, Harehill Cres., Wingerworth  
Chesterfield, Derbyshire  
Tel: 0246 74003

**USE ETI CLASSIFIED SECTION TO SELL YOUR PRODUCT/SERVICE**  
*Either fill in the coupon or phone Debbie on:*  
**01-437 0699**

**AERIAL AMPLIFIERS** improve weak television reception. Price £6.70. S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire, BL0 9AGH.

**IRISH READERS**  
**MAIL ORDER COMPONENTS**

Top quality components  
Great prices  
Return-of-post service

Write or phone for free price list  
**WAVEFORM ELECTRONICS**  
12 Efra Road, Rathmines, Dublin 6.  
Phone (01) 0001 if England 987507  
Mail order only please

**CRYSTALS.** Very large stocks. 100KHz-50MHz. Priced from 55p-£7.50. S.A.E. for full lists. TELERADIO, 325 Fore Street, London N9 0PE.

## BOOKS & PUBLICATIONS

**Be your own boss with our new published business manuals.** Both with full fault guides and business know how  
Domestic appliance reconditioning and repair for profit.  
2 volumes only **£12.50** post free.  
A guide to professional sewing machine repairs for profit.  
2 volumes only **£8.50** post free.  
Leaflets available.  
Mr. Marchant Dept (ETI)  
30 Chester Road East, Shotton, Clwyd, N. Wales

**PARAPHYSICS JOURNAL** (Russian translation); psychotronics, kirlianography, heli-phonics, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

## SURVEILLANCE EQUIPMENT

### MICRO-MINI TRANSMITTERS

— all supplied ex-stock, return post delivery, no special equipment required, built, tested, with instructions.  
**CT10H**, 4 mile range, broadcast quality speech pick-up **£13.98**.  
**CT10M**, prof grade, extra high power, tunable freq 70-120MHz variable microphone sensitivity, **£19.48**.  
**CT10MB**, as above + unique dual microphones to eliminate echoes, noise etc **£21.40**.  
All specialised requirements catered for.  
**EVEN RADIO STATIONS** — + telephone line recording device.  
Please enquire: **061-905 1040**.  
**S.A.T. ELECTRONICS**  
164 Washway Rd, Sale, Cheshire M33 1RH

## PLANS 'N DESIGN

**AMAZING ELECTRONIC** plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue. S.A.E. Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

## WANTED

**TURN YOUR SURPLUS** transistors, IC's etc into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.

**WANTED** Electronic test equipment, large computers, large quantities of Printed Circuit Boards, anything considered, good prices paid: 29 Lawford Crescent, Yateley, Camberley, Surrey Tel 0252 871048.

**WANTED:-** Powertran "Destiny Mixer". Ready built or kit for any combination. Good condition.

**KITS**

**VHF TRANSMITTER MODULE**

Kit, size 2 inches by 1/2 inch. Hyper-sensitive pickup. Hi-fi quality reception on domestic VHF/FM Radio. Sub-min components for exceptional transmission stability. 70-150MHz, range dependent on voltage (6-18V). Includes ultra-sensitive microphone, illustrated plans etc. NB new price reduced to £6.95, post paid, send cash/cheque/PO to Modulex, P.O. Box 102, Dartford, Kent DA1 2PW.

Build your own high performance  
**AUDIO SIGNAL GENERATOR**  
£25.00 incl. case (p.p.£1)


Spec.  
Very low distortion (only .02%)  
Output 1v into 600 Ohms  
(Attenuated)  
10Hz — 100Khz. Sine-Square  
(A Linsley-Hood design)  
**TELERADIO ELECTRONICS**  
325 Fore Street, Edmonton  
London N9 0PE  
Ready made £30.00

**PRINTED CIRCUITS** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**TO BOOK  
THIS  
SPACE  
PHONE  
01-437  
0699**

# ELECTROMART

**MERSEYSIDE**

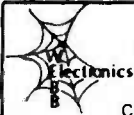

WYMCA Building, College St.,  
St. Helens Tel. 50707  
Open: Mon-Fri 9.30-5.30  
(closed Thurs) Sat 9.30-5  
Components, aerials & burglar alarm  
specialists

**S. WALES**

**STEVE'S ELECTRONIC  
SUPPLY CO. LTD.**  
45 Castle Arcade, Cardiff  
TEL: 0222 41905  
Open: Mon-Sat 9-5.30  
For components to computers

**LANCASHIRE**

**ETESON ELECTRONICS**  
15B Lower Green,  
Poulton-le-Fylde, Blackpool  
Tel: (0253) 885107  
Open: 9.30am-12.30 1.30-5.30 Closed Wed & Sun  
Electronic Component Specialists.

## CLASSIFIED ADVERTISEMENT — ORDER FORM

Advertise nationally in these columns to over 100,000 readers for only 40p per word (minimum charge 15 words).

Simply print your message in the coupon and send with your cheque or postal order made payable to

Argus Specialist Publications Ltd to:

**CLASSIFIED DEPT., ELECTRONICS TODAY INTERNATIONAL**

1 Golden Square, London W1R 3AB. Telephone: 01-437 0699

Please indicate classification required.

|  |  |  |
|--|--|--|
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |
|  |  |  |

Name .....

Address .....

Tel. No. (Day) .....

**WE TAKE ACCESS AND BARCLAYCARD**

Please place my advert in E.T.I for  months. Please indicate number of insertions required.



## ADVERTISERS INDEX

|                                   |           |
|-----------------------------------|-----------|
| Armon Electronics                 | 55        |
| Audio Electronics                 | 64        |
| Aurak Hi-Fi                       | 44        |
| B.Bamber                          | 18        |
| Belvedere Electronics             | 14        |
| B.K.Electronics                   | 44        |
| Black Star                        | 55        |
| B.N.R&E.S.                        | 56        |
| Clef products                     | 62        |
| Concept Electronics               | 67        |
| Cricklewood Electronics           | 10        |
| Crimson Elektrik                  | 22        |
| Display Electronics               | 12        |
| Electrovalue                      | 56        |
| Greenbank Electronics             | 62        |
| G.S.C.                            | 23        |
| Happy Memories                    | 62        |
| ICS                               | 51        |
| ILP                               | 18        |
| Kelan Engineering                 | 43        |
| Kempston                          | 51        |
| L.B.Electronics                   | 74        |
| Len's Electronics                 | 51        |
| Litesold                          | 35        |
| Maplin                            | OBC       |
| Marco Trading                     | 48        |
| Merseyside Accoustic Developments | 44        |
| Micro Processor Engineering       | 23        |
| Microtanic                        | 32        |
| MJL Systems                       | 62        |
| Newrad Instrument Cases           | 47        |
| Pantehnic                         | 14        |
| Parndon Electronics               | 56        |
| Powertran                         | IFC,7,IBC |
| Q.E.D. Audio                      | 47        |
| Rapid Electronics                 | 8         |
| Riscomp                           | 35        |
| R.V.M. Audiotronics               | 23        |
| Ship Co Ltd.                      | 14        |
| Skywave Software                  | 32        |
| S.M.E. Ltd.                       | 56        |
| Sparkrite                         | 67        |
| Stewarts of Reading               | 32        |
| Technomatic                       | 16,17     |
| Watford Electronics               | 4,5       |
| Wilmslow Audio                    | 55        |

## LB ELECTRONICS

**SPEACH SYNTHESISER** kit as in March/April Electronics & Computing. Kit **£24.95** p/p £1.50. Ready Built **£34.95** p/p £1.50. Details S.A.E.

**LOGITEC** FT50001 dot matrices printer 100cps, friction/tractor **£289** + VAT. Carriage £10. S.A.E. leaflet plus print-out.

**PRESTEL** monitors 6" green phosphor screen 12 digit keyboard printer port, cassette port, keyboard port (for full qwerty keyboard) Brand new and boxed **£175** + VAT. Leaflet S.A.E.

### DISC DRIVE BONANZA

**TEAC FD-55F 1/2 Height DSD 80 track/40 track, selectable at our new low price £199** + VAT. £8 carriage. Shinon 1/2 height 5 1/4" drive, 40 track, brand new, single sided, double density **£140** + VAT. Carriage £8. **COMPETITION.** We thank all our customers for purchasing our Teac drive and as a bonus we are now offering every 50th disc drive to be sold will be sent totally **FREE**. The name and address of the winner will be published in this magazine. This offer is excluded from trade or bulk buyers).

**EDGE CONNECTORS** 1" 56x56 wire wrap keyway at 30 **£1.80** p/p 25p. 30x30 156 Gold **80p** p/p 25p 1" 80x80 **£2.85** p/p 25p.

**Twin 5" Cabinets** with power supply £40.00 + VAT (providing a disc drive is purchased from us, if drives purchased elsewhere £50.00 + VAT).

**LS IC's in Stock.** Phone for prices.

**Dual 8" Drive Cabinets** brand new back panel cut out for fan etc... **£25** **Modem PCB** containing uart LS XR2211CP, XR2206CP no data. **£3.95** p/p 75p.

**26way IDC Socket** on short length of Ribbon Cable **£1** p/p 20p.

**KEY BOARD BONANZA.** Brand new ASCII coded single 5 volt rail. Some with numeric key pad, some without **£29.95p** p/p £1.50p.

**Leaflets S.A.E.**

**Mini Mother Board** 18 slot 44 way 1" (X equipment **£9** p/p £1.50p.

**PCB 9 1/2" x 10 1/2"** approximately 97X4116-25 **£25** p/p £1.50p.

**Jermyn Thermaflow Compound** 140 Grams **£1.50p** p/p 40p.

### CABLES

**Dual 5 1/4" disc drive cable** £12.95 p/p 65p. **Single 5 1/4" 9 95** p/p 50p.

**20 Way IDC Socket** plus 1 meter ribbon (BBC user port) £2.75 p/p 30p.

**Centronics Printer 36"** (BBC) £11.95.

**Special Offer Cambion 40 Way IC sockets** wire wrap £1 each, 12

for 10. **5 1/4" Drive Power plug** £1 each. **BBC PSU plug** £1 each.

**8" Drive DC plug** £1.35. **AC plug** £1.35 p/p 25p. **New double density**

interface for BBC machine. S.A.E. Full details £99.95 + VAT p/p £1.50.



## LB ELECTRONICS

11 HERCIES ROAD, HILLINGDON,  
MIDDLESEX UB10 9 LS, ENGLAND  
TEL: UXBRIDGE 55399



## MAIL ORDER PROTECTION SCHEME

If you order goods from Mail Order Advertisers in this magazine and pay by post in advance of delivery, this publication will consider you for compensation if the advertiser should become insolvent or bankrupt, provided:

1. You have not received the goods or had your money returned; and
2. You write to the publisher of this publication explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent to a limit of £1,800 per annum for any one advertiser, so affected, and up to £5,400 p.a. in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedures have not been complied with, at the discretion of this publication, but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of reader's difficulties.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc. received as a result of answering such advertisements):

**CLASSIFIED ADVERTISEMENTS ARE EXCLUDED.**

# Low-price robots from POWERTRAN

— hydraulically powered  
— microprocessor controlled

The UK-designed and manufactured range of Genesis general purpose robots provides a first-rate introduction to robotics for both education and industry. With prices from as low as £470, even the home enthusiast can aspire to his or her own robot.

Each robot in the Genesis range has a self-contained hydraulic power source operated from single phase 240 or 120v AC or from a 12v DC supply. Up to six independent axes are capable of simultaneous operation and all except the grip axis have sensing devices fitted to provide positional control by a closed loop system based on a dedicated microprocessor. Movement sequences can be programmed by means of a hand-held controller or the systems can be interfaced with an external computer via a standard RS232C link.



**GENESIS S101**



**GENESIS P101**

The top-of-the-range P102 has dual speed control, enhanced memory and double acting cylinders for increased torque on the wrist and arm joints. There is position interrogation via the RS232C interface, increasing the versatility of computer control and inputs are provided for machine tool interfacing.

All Genesis robots are available either ready-built or in kit form. The latter provides not only extra economy but also valuable additional training as an assembly project.



**GENESIS P102**

Cortex 16 bit microcomputer



**HEBOT II Turtle-type robot**

For a little over £100, Herbot II takes programming off the VDU and into the real world. Each wheel is independently controlled by a computer, enabling the robot to perform an almost infinite number of moves. It has blinking eyes, a two-tone bleep and a solenoid-operated pen to chart its moves. Touch sensors, coupled to its shell return data about its environment to the computer enabling evasive or exploratory action to be calculated.

The robot connects directly to an I/O port or, via the interface board, to the expansion bus of a ZX81 or other microcomputer.

## HEBOT II

Weight 1.8kg  
complete kit with assembly instructions **£95**  
Interface board kit **£11**

## MICROGRASP



A real, programmable robot for a little over £200! Micrograsp has an articulated arm jointed at shoulder, elbow and wrist positions. The entire arm rotates about its base and there is a motor driven gripper. All five axes are motor driven and four of these are servo controlled giving positive positioning. The robot can be controlled by any microcomputer with an expansion bus – the Sinclair ZX81 being particularly suitable.

## MICROGRASP

Weight 8.7kg, max. lifting capacity 100g  
Robot kit with power supply **£160.00**

Universal computer interface board kit **£54.00**  
23 way edge connector **£3.00**  
ZX81 peripheral/RAM pack splitter board **£3.50**

## GENESIS P101

Weight 34kg, max lifting capacity 1.8kg  
6-axis model (kit form) **£750**  
6-axis complete system (kit form) **£1050**


## GENESIS P102

Weight 36kg, max lifting capacity 2kg  
6-axis system (kit form) **£1350**

Powertran Cortex microcomputer self-assembly kit **£295.00**




All goods subject to availability

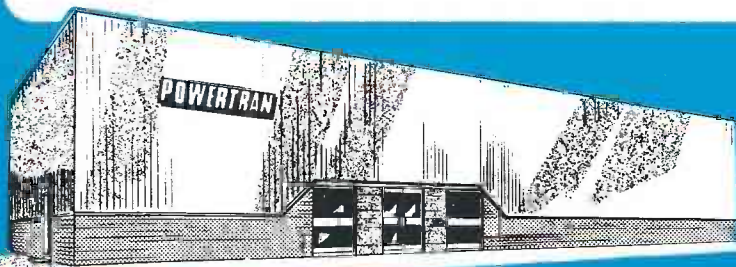
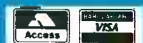
# POWERTRAN cybernetics Ltd.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3ET. TEL (0264) 64455

ALL PRICES ARE EXCLUSIVE OF VAT AND APPLY TO THE U.K. ONLY – ALLOW 21 DAYS FOR DELIVERY. OVERSEAS CUSTOMERS – PLEASE CONTACT OUR EXPORT DEPARTMENT FOR THE NAME AND ADDRESS OF YOUR LOCAL DEALER.





# MAPLIN Massive range of components for your hobby....insist on Maplin quality!

## MAPLIN'S TOP TWENTY KITS

| THIS LAST MONTH   | DESCRIPTION OF KIT           | ORDER CODE | KIT PRICE | DETAILS IN PROJECT BOOK |
|---|------------------------------|------------|-----------|-------------------------|
| 1. (1)  | 75W Mosfet Amp Module        | LW51F      | £12.95    | Best of E&MM            |
| 2. (3)  | Modem                        | LW99H      | £44.95    | 5 XA05F                 |
| <i>Case also available: YK62S Price £9.95.</i>                              |                              |            |           |                         |
| 3. (5)  | ZX81 I/O Port                | LW76H      | £9.25     | 4 XA04E                 |
| 4. (4)  | Car Burglar Alarm            | LW78K      | £6.95     | 4 XA04E                 |
| 5. (8)  | Partylite                    | LW93B      | £9.45     | Best of E&MM            |
| 6. (2)  | Keyboard for ZX81            | LW72P      | £23.95    | 3 XA03D                 |
| <i>Case also available: XG17T £4.95. Complete ready-built: XG22Y £32.50</i> |                              |            |           |                         |
| 7. (10)   | 8W Amp Module                | LW36P      | £4.45     | Catalogue               |
| 8. (14)   | VIC20/64 RS232 Interface     | LK11M      | £9.45     | 7 XA07H                 |
| 9. (7)  | Syntom Drum Synthesiser      | LW86T      | £11.95    | Best of E&MM            |
| 10. (12)  | Harmony Generator            | LW91Y      | £17.95    | Best of E&MM            |
| 11. (17)  | Spectrum RS232 Interface     | LK21X      | £17.95    | 8 XA08J                 |
| 12. (6)   | VIC20 Speech Synthesiser     | LK00A      | £22.95    | 6 XA06G                 |
| 13. (13)  | ZX81 Sounds Generator        | LW96E      | £10.95    | 5 XA05F                 |
| 14. (11)  | Ultrasonic Intruder Detector | LW83E      | £10.95    | 4 XA04E                 |
| 15. (15)  | Logic Probe                  | LK13P      | £9.95     | 8 XA08J                 |
| 16. (26)  | Car Battery Monitor          | LK42V      | £6.25     | Best of E&MM            |
| 17. (18)  | Hexadrum                     | LW85G      | £19.95    | Best of E&MM            |
| 18. (21)  | Synwave Sounds Synth         | LW87U      | £10.95    | Best of E&MM            |
| 19. (25)  | Spectrum Keyboard            | LK29G      | £28.50    | 9 XA09K                 |

Also required: LK30H £6.50; Case: XG35Q £4.95 — Total £39.95.

Also available complete ready-built: XG36P £44.95.

20. (9) ZX81 Speech Synthesiser LK01B £16.95 6 XA06G

Over 80 other kits also available. All kits supplied with instructions.

The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.



## MAPLIN'S FASCINATING PROJECTS BOOKS

Full details in our Project Books Price 70p each.


In Book 1 (XA01B) 120W rms Mosfet Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • 6 Vero Projects.

In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W Mosfet Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to 600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.

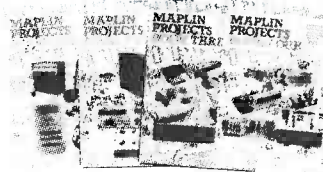In Book 5 (XA05F) 300 Baud Duplex Modem to European Standard • 100W 240VAC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Alarm.



In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 • Module to Bridge two of our Mosfet Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20/Commodore 64 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.

In Book 8 (XA08J) Modem (RS232) Interface for Dragon 32 & Spectrum • Synchime • I/O Ports for Dragon 32 • Electronic Lock • MiniLab Power Supply • Logic Probe • Doorbell for the Deaf.

In Book 9 (XA09K) Keyboard with Electronics for ZX Spectrum • Infra-

Red Intruder Detector • Multimeter to Frequency Meter Converter • FM Radio needs no alignment • Hi-Res Graphics for ZX81 • Speech Synthesiser for Oric 1 • VIC20 Extendi-board • ZX81 ExtendiRAM • Dynamic Noise Limiter for Personal Cassette Players • TTL Levels to RS232 Converter • Logic Pulsar • Pseudo-Stereo AM Radio • Ni-Cad Charger Timer

Adder-Subtractor • Syntom's Interface • Microphone Pre-Amp Limiter. In Book 10 (XA10L) Cassette Easyload for ZX Spectrum • 80m Amateur Receiver • Auto Waa-Waa Effects Unit • Oric 1 Modem Interface • 2.8kW Mains Power Controller • Extendiport for Dragon 32 • 12V Fluorescent Tube Driver • 32-Line Extension for Digi-Tel.

### 1984 CATALOGUE

A massive 480 big pages of description, pictures and data and now with prices on the page. The new Maplin catalogue is the one book no constructor should be without. Now includes new Heathkit section. On sale in all branches of W.H. Smith. Price £1.35 — It's incredible value for money. Or send £1.65 (including p & p) to our mail-order address.

### GREAT PROJECTS FROM E&MM


Our book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first Year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects. Order As XH61R. Price £1.

Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packaging. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65

Name .....

Address .....

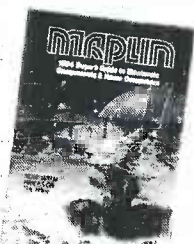

# MAPLIN

ELECTRONIC SUPPLIES LTD


Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 • Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926. • 8 Oxford Road, Manchester. Tel: 061-236-0281. • Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292. • 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000. • 46-48 Bevois Valley Road, Southampton. Tel: 0703 25831.

All shops closed all day Monday.

All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

ETI 6 84

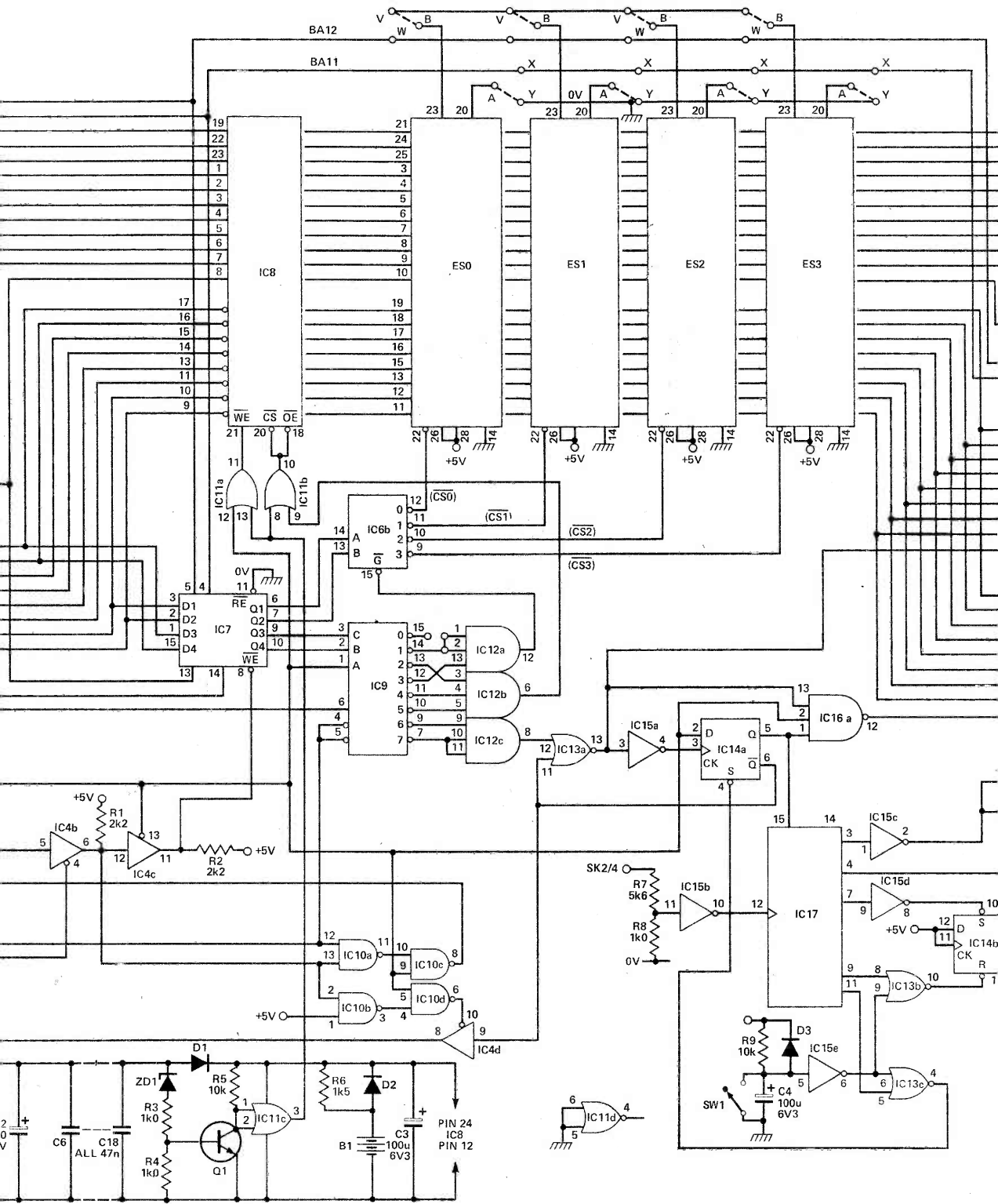Despatch by return of post where goods available.



allowable. The same signal in the direction of IC3 also serves as the enable for memory and I/O functions in that no disagreements occur when trying to drive the data bus.

The three top address bits which are active in the ranges 1011 1111 1111 11XX and A000h — BFFFh. The first three bits activate the memory function and is used to enable IC4b. The output from IC4b comes from IC5 which is a NAND gate. The inputs to this gate are A12 to A10 inclusive. The output goes low when  $\phi_2$  is high and the address pattern is:— XXX1 1111 1111

11XX (X=don't care). Only when the output of IC5 is low and the enable input to IC4b is low can the output of IC4b go low. The enable input will be low when the address bus pattern is:— 101X XXXX XXXX XXXX and therefore IC4b output is only low for addresses:— 1011 1111 1111 11XX which fall in the range BFFCh to BFFFh and the  $\phi_2$  signal is also high. These four addresses are used to write into the control logic and read from the programming logic.

When a WRITE operation is performed to one of the four addresses, the output of IC4c will go low and allow data to be written into IC7. This device is a four-word, four bits per word memory. When writing data into it, the

word to be written is selected by a NAND gate. The address is taken from A0 and A1 and the data is taken from D0, D1, D6, D7. (Note that there is no read data back into the computer!)

If a read operation is performed, the four control addresses it will be enabled via IC10b and IC10d. The state of the programming status bit 7 of the data bus.

When an address in the range 9FFFh is written to or read from, the output from IC6a activates IC9. The output from IC10a and the status of the R/W line will activate IC10c if a read operation is in progress. This will set its