

# electronics today

INTERNATIONAL

FEBRUARY 1985 99p

## CURE THE LOG JAM

Capture one-off events with  
the ETI Data Logger

**PLUS**

**PARAGRAPH EQUALISER** -  
all the advantages of parametric and  
graphic equalisers in one unit


**EXPANSION CARD** -  
for the Digital Delay Line

**DESIGNING MEMORY** -  
the designer of the 64K DRAM  
board reveals all


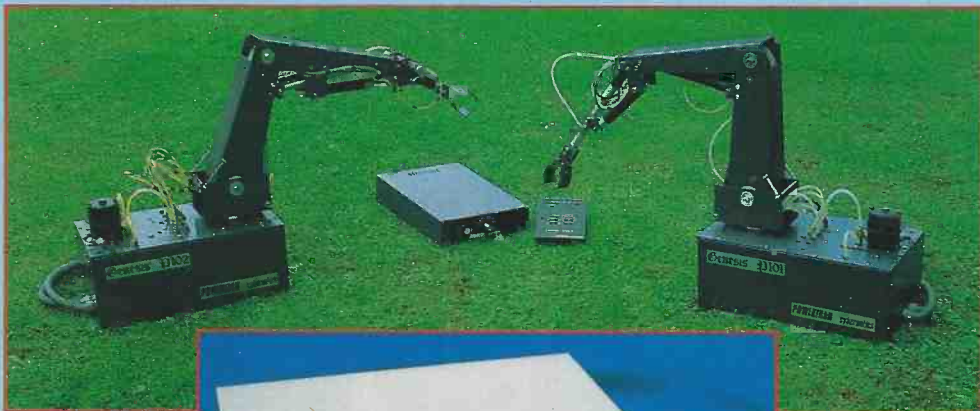
# YOU'LL ENJOY THE EXPERIENCE

**GENESIS P102 MK 2** from Hydraulic Robot System from £1625



**GENESIS P101 MK2** Hydraulic Robot arm from £825

**CORTEX II** 16 bit microcomputer Ready-Built from £399



**CORTEX II** 16 bit microcomputer from £299 in kit form

**HEBOT II** Robot Turtle From £95.00



**MICROGRASP** Electric Robot from £215

Powertran's educational robots and the remarkable Cortex microcomputer have been tried and tested in universities, colleges, schools and homes throughout the world.

Our own experience in the field of electronics kits has been supplemented by the Feedback Group's 25 years of supplying technical equipment to the Educational sector. Our first year as a member of the Group has seen numerous improvements to our already popular products.

All the products illustrated can be supplied either factory-built or in kit form for added economy. Contact our Sales Office for details.

(Prices quoted are exclusive of VAT and apply to the UK only.)

# **POWERTRAN** cybernetics Ltd.




PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3ET Tel: 0264 64455



# electronics today

INTERNATIONAL FEBRUARY 1985 VOL 14 NO 2

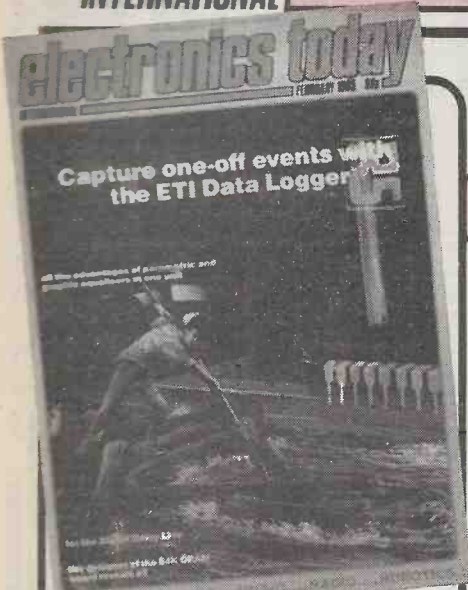

Capture one-off events with the ETI Data Logger

Dave Bradshaw: Editor  
 Phil Walker: Project Editor  
 Ian Pitt: Assistant Editor  
 Jerry Fowler: Technical Illustrator  
 Paul Stanyer: Ad. Manager  
 Kerry Fowler: Copy Control  
 Jim Connell: Chairman

**PUBLISHED BY:**  
 Argus Specialist Publications Ltd.,  
 1 Golden Square, London W1R 3AB.  
**DISTRIBUTED BY:**  
 Argus Press Sales & Distribution Ltd.,  
 12-18 Paul Street, London EC2A 4JS  
 (British Isles)  
**PRINTED BY:**  
 The Garden City Press Ltd.  
**COVERS DESIGNED BY:**  
 MM Design & Print.  
**COVERS PRINTED BY:**  
 Alabaster Passmore.

**OVERSEAS EDITIONS and their EDITORS**  
 AUSTRALIA — Roger Harrison  
 CANADA — Halvor Moorshead  
 GERMANY — Udo Wittig  
 HOLLAND — Anton Kriegsmann

**ABC** Member of the Audit Bureau of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1984 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.




Subscription Rates. UK £15.00 including postage. For further details and Airmail rates etc, see the Readers' Services page.

## EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.  
 Telex 8811896.
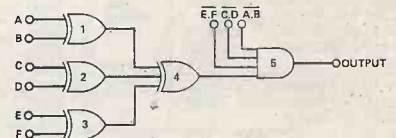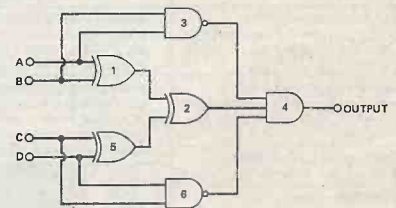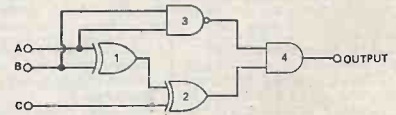
## FEATURES


- DIGEST** .....9  
Newsworthy nosh.
- DESIGNING MEMORY** .....18  
Phil Walker recalls designing the 64K DRAM Card.
- TECH TIPS** .....28  
Another selection of crafty circuits, helpful hints and design dodges from our readers.
- READ/WRITE** .....42  
Contrary to popular belief, not all of the letters we receive go straight in the waste bin.
- DESIGN INTEGRATED CIRCUITS ON YOUR MICRO** .....52  
Go IC on your PC.


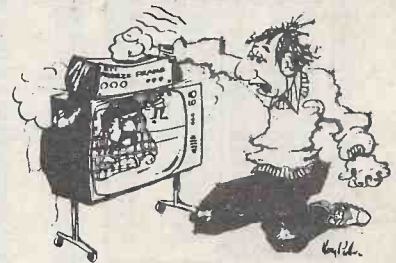
## PROJECTS

- DIGITAL DELAY LINE EXPANSION** .....24  
Keeps you waiting that little bit longer.
- PARAGRAPH EQUALISER** .....31  
There aren't many paragraphs to equal Barry Porter's when it comes to appalling humour.
- DISTORTION METER** .....37  
John Linsley Hood brings you the ungarbled truth about distortion measuring.
- DATA LOGGER** .....45  
Chop your analogue signals up into little bits and then squirrel them away.

- FRAMESTORE** .....55  
The third part of ETI's answer to Channel Four — a device that will keep showing the same old TV pictures.



My God! It's not the picture that's seized up — its Des Lynam! (With apologies to sporting media megastar)

## INFORMATION

- ETI BOOK SERVICE** .....6
- READER'S SERVICES** .....7
- ETI PCB SERVICE** .....59
- PCB FOIL PATTERNS** .....60
- NEXT MONTH'S ETI** .....63
- ADVERTISERS' INDEX** .....66

# WATFORD ELECTRONICS

33/34 CARDIFF ROAD, WATFORD, HERTS, ENGLAND.

MAIL ORDER, CALLERS WELCOME

Tel. Watford (0923) 37774/40588 Telex. 8956095

ALL DEVICES FULLY GUARANTEED. SEND CHEQUE, P.O.s, CASH, BANK DRAFT WITH ORDERS. TELEPHONE ORDERS BY ACCESS/MASTER CHARGE ACCEPTED. GOVERNMENT & EDUCATIONAL ESTABLISHMENTS OFFICIAL ORDERS WELCOME P&P ADD 75p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

## VAT

Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including P&P.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday: 9.00am to 6.00pm. Ample Free Car parking space available.

**ELECTROLYTIC CAPACITORS:** (Values in uF) 500v: 10u52; 47 78p; 63V 0.47, 1.0, 1.5, 2.2, 3.3, 4.7 10 10p; 15, 22, 12p; 33 15p; 47 12p; 68 20p; 100 19p; 220 26p; 1000 70p; 2200 99p; 50V: 68 20p; 100 17p; 220 24p; 400V: 22 9p; 33 12p; 330 4.7 30p; 1000 4.0 30p; 1500 4.0 30p; 25V: 1.5, 4.7, 10, 22, 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680 1.00 34p; 1000 34p; 1500 42p; 2200 50p; 3300 78p; 4700 92p; 16V: 4.7, 6.8, 100 9p; 125 12p; 330 16p; 100 20p; 680 34p; 1000 27p; 1500 31p; 2200 26p; 4700 72p.

**TAG-END CAPACITORS:** 64V: 2200 139p; 3300 198p; 4700 245p; 50V: 2200 110p; 3300 184p; 40V: 4700 160p; 25V: 2200 90p; 3300 98p; 4000 470 98p; 10000 320p; 15000 345p; 16V: 2200 350p.

**POLYESTER CAPACITORS: Axial Lead Type**  
400V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8 11p; 10n, 15n, 22n 12p; 33n, 47n, 68n 16p; 150n 20p; 220n 30p; 330n 42; 470n 52; 680n 1uF 68p; 2u 42p.  
1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n, 100n 42p.

**POLYESTER RADIAL LEAD CAPACITORS: 250V**  
10p; 330n, 470n 15p; 680n 19p; 1u5 40p; 2u2 48p.

**TANTALUM BEAD CAPACITORS**  
35V: 0.1uF, 0.22, 0.33 15p 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p 10 28p; 16V: 2.2, 3.3 16p; 4.7, 6.8 10 18p; 15, 36p; 22 45p; 33, 47 50p; 100 95p; 10V: 15, 22, 36p; 33, 47 50p; 100 80p; 10V: 1.0 55p.

**MYLAR FILM CAPACITORS**  
100V: 1nF, 2, 4, 4nF, 10 6p; 15nF, 22n, 30n, 40n, 47n 7p; 56n, 100n, 200n 9p; 50V: 470nF 12p.

**CERAMIC CAPACITORS 50V:**  
Range: 0.5pF to 10nF 4p, 15nF, 22nF 33nF; 47nF 5p, 100nF/300V 7p, 200nF/6V 8p.

**POLYSTYRENE CAPACITORS:**  
10pF to 1nF 8p; 1.5nF to 12nF 10p.

**SILVER MICA (Values in pF)**  
2, 3, 3.4, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 95, 100, 120, 150, 180pF 15p each  
200, 220, 250, 270, 300, 330, 360, 390, 470, 800, 800, 800 21p each  
100, 1200, 1800, 2200 30p each  
3300, 4700pF 80p

**MINIATURE TRIMMERS Capacitors**  
2-6pF 2-10pF 22p; 2-25pF; 5-65pF 30p; 10-89pF 36p.

**RESISTORS Carbon Film, miniature, Hi-Stab, 5%.**  
RANGE Val 1-99 100+  
0.25W 2n2 - 10M E12 3p 1p  
0.5W 2n2 - 4M7 E12 3p 1p  
1W 2n2 - 10M E12 6p 4p  
2 1/2 Metal Film 51n - 1M E24 6p 4p  
1 1/2 Metal Film 51n - 1M E24 5p 4p  
100+ price applies to Resistors of each type not mixed.

**RESISTORS NETWORK S.I.L.**  
7 Commoned: (8 pins) 100n, 680n, 1K 2k2, 4k7, 10K, 47K, 100K 25p  
8 Commoned: (9 pins) 150n, 10k, 180k, 270k, 330k, 1K, 2K2, 4K7, 6K8, 10K, 22K, 47K & 100K 26p.

**DIODES BRIDGE RECTIFIERS 75 SERIES**

AA119	20	1A/50V	18	751078	98
AA120	20	1A/100V	20	751110	98
AA130	15	1A/100V	20	751145	150
BA100	15	1A/400V	25	751212	130
BAX	20	1A/600V	34	751600	125
BY100	24	2A/50V	30	75154	125
BY126	12	2A/200V	40	75158	150
BY127	14	2A/400V	48	75159	195
CRC03	250	2A/600V	88	75160	420
CA9	40	6A/100V	83	75162	650
CA47	12	6A/400V	96	75162A	99
CA70	12	10A/200V	215	75189	100
CA79	15	10A/800V	295	75322	140
CA81	20	25A/200V	240	75324	380
CA85	15	25A/600V	396	75325	00
CA90	8	BY164	56	75361/3	150
CA91	8	VM18 DIL	50	75365	00
CA95	8			75450	8
CA920	8			75451/2	52
CA924	8			75454	70
CA928	4			75491/2	65
CA931	2				
CA932	2				
CA933	2				
CA1000	2				

**SCR THYRISTORS**  
Range: 2V7 to 39V 400mW  
3p each  
Range: 3V3 to 39V 1.3W  
15p each

**TRIACS**  
3A200V 54 BT108 150 6875 500  
3A300V 54 BT116 150 6875 500  
8A100V 60 C106D 38 8035 525  
8A400V 69 TIC44 24 8080A 425  
8A800V 115 TIC45 29 8085 515  
12A100V 78 TIC47 36 8085A 515  
12A200V 82 TIC48 36 8088 515  
12A800V 136 TIC49 36 8035 525  
16A100V 103 TIC44A 32 8131 475  
16A400V 106 TIC47 36 8154 750  
16A800V 220 TIC48 36 8155 750  
25V500V 220 TIC49 36 8156 750  
25A800V 296 TIC49 36 8157 750  
T2800 125 ST2 25

**ZENERS**  
Range: 2V7 to 39V 400mW  
3p each  
Range: 3V3 to 39V 1.3W  
15p each

**DIAC**  
ST2 25

## TRANSISTORS

AC126/7	35	BC327	15	BF336/7	35	MPSU60	60	ZTX107/8	12	2N3820	60	2SC2335	200
AC141/2	35	BC337/8	15	BF394	40	MPSU62	65	ZTX109/3	23	2N3934	40	2SC2344	40
AC176	35	BC41/61	34	BF451	40	MPSU55	60	ZTX120	12	2N3935	60	2SC2322	200
AC188	35	BC477	40	BF494/5	40	MPSU56	60	ZTX300	13	2N3903/4	18	2SD234	74
AC192	35	BC517/7	40	BF594/5	30	OC28	170	ZTX302	16	2N3905/6	15	2SK45	80
AC222/41	75	BC547/8	12	BF694/4	30	OC22	220	ZTX303	25	2N3906	25	2SK288	225
AD12	120	BC556/7	15	BF808/1	25	OC25	250	ZTX304	28	2N4037	60	2SK383	225
AD149	79	BC558/9	15	BF898	105	OC26/41	75	ZTX326	30	2N4038	60	2SK385	225
AD181	42	BCY39/40	85	BF898	105	OC27/75	75	ZTX451	23	2N4061/2	15	3N128	115
AD182	42	BCY41/42	30	BF898	105	OC27/75	75	ZTX500	14	2N4264	30	3N140	115
AF176/6	45	BCY41/42	30	BF898	105	OC27/75	75	ZTX501/2	15	2N4268	25	40315	90
AF188	80	BCY58/59	38	BF898/5	35	OC33/84	70	ZTX503	18	2N4269	25	40316	95
AF174/26	70	BCY70/71	18	BFY50/51	30	OC37/70	75	ZTX531	125	2N4400	25	40324	70
AF139	40	1BCY72	25	BFY52	30	OC70	40	ZTX550	20	2N4427	80	40347	90
AF178	75	BCY78	30	BFY53	35	OC200	75	2N697	23	2N4471	55	40348	120
AF186	70	BD114	190	BFY55/56	56	PI23A	32	2N699	40	2N5135	25	40381/2	70
AF239	55	BD121	95	BFY64	40	TI23C	38	2N699	40	2N5136	25	40382	70
BC107	14	BD124	115	BFY121	100	TI23D	38	2N706A	25	2N5172	35	40407/8	75
BC107B	14	BD131/32	65	BFY90	80	TI23E	37	2N708	25	2N5179	45	40411	285
BC108	12	BD133	70	BFY93	50	TI23F	38	2N819	40	2N5180	45	40412	90
BC109	12	BD135	45	BSX20	30	TI23G	38	2N131/1/2	40	2N5190/1	70	40467/8	130
BC109C	14	BD136/37	40	BSX26/29	45	TI23H	38	2N1302	40	2N5191	60	40468	85
BC109D	12	BD138/39	40	BSY26	35	TI23I	45	2N1307	70	2N5205/6	15	40534	125
BC109E	14	BD140	40	BSY95	35	TI23J	45	2N1671/1B	100	2N5457/8	30	40603	110
BC109F	14	BD144/45	198	BU105	180	TI23K	45	2N1671/2B	100	2N5459	30	40673	75
BC114/5	30	BD158	68	BU205	180	TI23L	45	2N219A	28	2N5485	35	40871/2	90
BC117/8	25	BD226/6	110	BU206	180	TI23M	45	2N2200A	28	2N5477	46		
BC137/9	40	BD245	65	BU208	180	TI23N	45	2N2200B	28	2N5478	46		
BC140	38	BD378	70	BU69C	225	TI23O	45	2N2200C	28	2N5479	46		
BC142/3	38	BD434	70	MD8001	250	TI23P	45	2N2222A	25	2N6027	32		
BC147	12	BD517	75	MD955	90	TI23Q	45	2N2222B	25	2S6A71	250		
BC148	12	BD518	75	MD955	90	TI23R	45	2N2222C	25	2S6A72	250		
BC149	12	BD519	75	MD955	90	TI23S	45	2N2222D	25	2S6A73	250		
BC149B	15	BD569A	150	MJE340	54	TI23T	45	2N2222E	25	2S6A74	250		
BC149C	15	BD569B	150	MJE340	54	TI23U	45	2N2222F	25	2S6A75	250		
BC149D	15	BD569C	150	MJE340	54	TI23V	45	2N2222G	25	2S6A76	250		
BC149E	15	BD569D	150	MJE340	54	TI23W	45	2N2222H	25	2S6A77	250		
BC149F	15	BD569E	150	MJE340	54	TI23X	45	2N2222I	25	2S6A78	250		
BC149G													



<b>SWITCHES</b> TOGGLE: 2A, 250V SPST 3P DPDT 48p	<b>DIP SWITCHES</b> (SPST) 4 way 85p; 6 way 80p; 8 way 85p; 10 way 125p (SPDT) 4 way 180p	<b>VEROBORD</b> 0.1in 2 1/2 x 3 1/4 95p 2 1/2 x 5 110p 3 1/4 x 3 110p 3 1/4 x 5 125p 3 1/4 x 7 420p 4 1/4 x 17 590p Pkt of 100 pins 55p Spot face cutter 150p Pin insertion tool 185p	<b>VQ Board</b> 195p <b>DIP Board</b> 395p <b>Veri Strip</b> 95p	<b>IDC CONNECTORS</b> PCB Plugs Female Female Pins laich Header Card Strt Angle Plug Edge Concl Concl 10 way 90p 99p 85p 120p 20 way 145p 160p 125p 185p 26 way 175p 200p 150p 240p 34 way 205p 238p 180p 320p 40 way 220p 250p 180p 340p 50 way 235p 270p 200p 395p 60 way — — 230p 495p	<b>PANEL METERS</b> FSD 60 x 46 x 35mm 0-50mA 0-100mA 0-500mA 0-1000mA 0-5mA 0-10mA 0-50mA 0-100mA 0-500mA 0.2A 0.25V 0.50V AC 0.300V AC "VU" 490p each	<b>RELAYS</b> Miniature, enclosed, PCB mount: SINGLE POLE Changeover RL-91 205R Coil, 12V DC, (10V to 19.5V), 10A at 30V DC or 250V AC 195p DOUBLE POLE Changeover, 6A 30V DC or 250V AC RL-100 53R Coil, 6V DC (5V to 9.9V), 190p RL-111 205R Coil, 12V DC (10V to 19.5V), 195p RL-6 114 740R Coil, 24V DC (22V to 37V), 200p
<b>SUB-MIN TOGGLE</b> SPST on/off 55p SPDT centre off 64p SPDT cover off 85p SPDT biased both ways 105p DPDT 6 tags 80p DPDT centre off 150p DPDT biased both ways 145p DPDT 3 positions on/on/off 185p 4-pole 2 way 220p	<b>ROTARY SWITCHES</b> (Adjustable S-Type) 1 pole/2 to 12 way, 2 pole/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 48p <b>ROTARY:</b> Mains DP 250V 4 Amp on/off 66p <b>ROTARY:</b> (Mak-a-switch) Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max. 6 pole/12 way + DP switch). Mechanism only 90p	<b>VERO WIRING PEN</b> + spool 380p Spare spool 75p Combs 6p	<b>DALO ETCH RESIST PEN</b> Plus spare pen 100p	<b>EURO CONNECTORS</b> Gold Flashed Contacts Female Strt Pins Female Srt Pins Male Strt Pins Plug Angle DIN41617 31 way 170p — — 175p DIN41612 2 x 32 A + B 275p — 220p 285p DIN41612 2 x 32 A + C 295p — 240p 300p DIN41612 3 x 32 A + B + C 360p 385p 280p 395p	<b>CRYSTALS</b> 32.768KHz 100 100KHz 345 200KHz 570 455KHz 370 1M 275 1.008M 275 1.28MHz 450 1.6MHz 395 1.8MHz 545 1.8432M 250 2.0MHz 225 2.4576M 200 3.12MHz 240 455KHz 370 1M 275 1.008M 275 1.28MHz 450 1.6MHz 395 1.8MHz 545 1.8432M 250 2.0MHz 225 2.4576M 200 3.12MHz 240 455KHz 370 1M 275 1.008M 275 1.28MHz 450 1.6MHz 395 1.8MHz 545 1.8432M 250 2.0MHz 225 2.4576M 200 3.12MHz 240	<b>ASTEC UHF MODULATORS</b> Standard 6MHz 375p Wideband 8MHz 550p
<b>SLIDE 250V:</b> DPDT 1A 14p DPDT 1A c/off 15p DPDT 1/2A 13p	<b>WAFERS:</b> (make before break) to fit the above switch mechanism 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6p/2 way 65p Mains DP 4A Switch to fit Spacers 4p. Screen 6p.	<b>FERRIC CHLORIDE</b> 1 lb bag Anhydrous 195p + 50p p&sp	<b>ULTRASONIC TRANSDUCER</b> 40KHz 475 pr	<b>RIBBON CABLE</b> price per foot 10 way 15p 28p 16 way 25p 40p 20 way 25p 30p 24 way 40p 65p 28 way 55p 80p 34 way 80p 85p 40 way 70p 90p 50 way 100p 135p 64 way 120p 160p	<b>BUZZERS</b> miniature, solid-state 6V, 9V & 12V 70p <b>PIEZO TRANSDUCERS</b> PB2720 70p	
<b>PUSHBUTTON 6A</b> with 10mm Button SPDT latching 200p SPDT moment 150p DPDT moment 200p	<b>ROCKER SWITCHES</b> ROCKER: 5A/250V SPST 28p ROCKER: 10A/250V DPDT c/off 38p ROCKER: 10A/250V DPST with neon 85p	<b>COPPER CLAD BOARDS</b> Fibre glass sided 6" x 6" 100p 6" x 12" 125p	<b>DIL SOCKETS</b> Low Wire Prof Wrap 8 pin 8p 25p 14 pin 10p 35p 16 pin 10p 42p 18 pin 10p 45p 20 pin 20p 60p 22 pin 22p 65p 24 pin 25p 70p 28 pin 28p 80p 40 pin 30p 90p	<b>DIL PLUG (Header)</b> Solder IDC 14 pin 40p 90p 16 pin 48p 105p 24 pin 88p 178p 28 pin 290p 295p 40 pin 250p 255p	<b>LOUDESPEAKERS</b> Miniature, 0.3W-8Ω 2" 2W, 2 1/2" 3" 2W 4" 4Ω 8Ω or 80Ω 6" x 4" 8Ω 7" x 5" 8Ω 8" x 5" 8Ω 80p 80p 200p 225p 250p	
<b>PUSHBUTTON 6A</b> with 10mm Button SPDT latching 200p SPDT moment 150p DPDT moment 200p	<b>THUMBWHEEL</b> Mini front mounting switches Decade Switch Module 275p B.C.D. Switch Module 298p Mounting Choke (per pair) 75p	<b>EDGE CONNECTORS</b> 2x6 way — 111p 2x12 way — 180p 2x15 way — 185p 2x18 way 210p 175p 2x22 way 215p 250p 2x23 way 175p — 2x25 way 285p 275p 2x28 way 100p — 2x30 way 310p — 2x36 way 360p — 2x40 way 380p —	<b>ZIF TEXT TOOL DIL SOCKETS</b> 24 pin 575p 28 pin 685p 40 pin 845p	<b>AMPHENOL CONNECTORS</b> 24 way IEEE 475p 36 way Centronix 470p 24 way Female 490p 450p	<b>MONITORS</b> ● ZENITH — 12" Green, Hi-Resolution Popular £68 ● MICROVITEC 1431, 14" Colour RGB input. Connecting cable incl. £185 ● MICROVITEC 1451, 14" Medium resolution £285 ● KAGA 12", Med-res. RGB Colour. Has flicker-free characters. Ideal for BBC, Apple, VIC, etc. £195 (car £7) ● KAGA 12", As above but Hi-Resolution £259 (car £7) ● Connecting Lead for KAGA £5 Carriage £7 Securicor	
<b>DIGITAST Switch</b> Assorted Colours 75p each	<b>TURNED PIN Low Profile DIL SOCKET</b> Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header Plug) Jumper 24 inches 145p 185p 240p 380p Double ended DIP (Header Plug) Jumper 6 inches 185p 205p 300p 485p 12 inches 185p 215p 315p 480p 24 inches 210p 235p 345p 540p 36 inches 290p 370p 480p 525p	<b>SIL SOCKET 0.1" Pitch</b> 20 way 85p	<b>ANTOX SOLDERING IRONS</b> C15W 525p; CS17W 545p C18W 580p; XS25W 570p Spare Bits 85p; Elements 230p Iron Stand 175p; Heat Shunt 30p	<b>'D' CONNECTORS</b> Male Solder lugs 80p 105p 180p 250p Angle pins 150p 210p 250p 355p PCB pins 120p 130p 195p 295p Female Solder lugs 105p 180p 200p 335p Angle pins 165p 215p 290p 440p PCB pins 150p 180p 240p 420p COVERS 80p 75p 75p 90p IDC 25 way 'D' Plug 385p; Socket 450p	<b>SOUDERCON PINS</b> Ideal for making SIL or DIL Sockets 100 pins 45p 500 pins 195p	
<b>GAS/SMOKE DETECTORS</b> TGS812 or TGS813 £6 each	<b>JUMPER LEADS</b> (Ribbon Cable Assembly) IDC Female Header Socket Jumper Leads 36' 20 pin 26 pin 34 pin 40 pin Single ended 180p 200p 280p 300p Double ended 290p 370p 480p 525p	<b>ALUM BOXES</b> 3 x 2 x 1" 85p 4 x 2 1/2 x 2" 100p 4 x 2 x 2 1/2" 103p 4 x 4 x 2" 105p 4 x 4 x 2 1/2" 120p 5 x 4 x 1 1/2" 99p 5 x 4 x 2 1/2" 120p 5 x 2 1/2 x 1 1/2" 90p 5 x 2 x 2 1/2" 130p 6 x 4 x 2" 120p 6 x 4 x 3" 150p 7 x 5 x 3" 180p 8 x 6 x 3" 210p 10 x 4 x 3" 275p 10 x 7 x 3" 280p 12 x 5 x 3" 280p 12 x 8 x 3" 295p	<b>VOLTAGE REGULATORS</b> 1A TO220 Plastic Casing +ve 5V 7805 50p 7905 50p 12V 7812 50p 7906 60p 15V 7815 45p 7912 50p 18V 7818 45p 7915 50p 24V 7824 50p 7918 50p 30V 7830 50p 7924 50p 100mA TO92 Plastic package 5V 78L05 30p 79L05 50p 6V 78L06 30p — 8V 78L08 30p — 9V 78L12 30p 79L12 50p 15V 78L15 50p 79L15 60p ICL7660 248p TAA550 50p RC4194 375p IDA1412 150p RC4195 180p 78H05 +5V/5V 585p LM309X 135p 78H12 +12V/5A 640p LM317K 250p 78H5 +5V to +25V 585p LM317KP 450p 5A 78H5 +5V to +25V 585p LM323K 450p 79HG — 2.5V to -24V, 5A 685p LM337 175p 78S40 225p LM723 Var 30p 78S40 225p	<b>TRANSFORMERS</b> 3-0-3V, 6-0-6V, 9-0-9V, 12-0-12V, 15-0-15V @ 100mA 99p pcb mounting, Miniature, Split Bobbin 3VA: 2x6V-0.25A, 2x9V-0.15A, 2x12V-0.12A, 2x15V-0.1A 235p 6VA: 2x6V-0.5A, 2x9V-0.3A, 2x12V-0.25A, 2x15V-0.2A 280p Standard Split Bobbin type: 6VA: 2x6V-0.5A, 2x9V-0.4A, 2x12V-0.3A, 2x15V-0.25A 250p 12VA: 2x4.5V-1.3A, 2x5V-1A, 2x9V-0.6A, 2x12V-0.5A, 2x15V-0.4A, 2x20V-0.3A 345p (35p p&sp) 24VA: 2x6V-1.5A, 2x9V-1.2A, 2x12V-0.8A, 2x15V-0.6A 385p (60p p&sp) 50VA: 2x6V-4A, 2x9V-2.5A, 2x12V-2A, 2x15V-1.5A, 2x20V-1.2A, 2x25V-1A, 2x30V-0.8A 520p (60p p&sp) Specially wound for Multirail computer PSUs 50VA: Outputs +5V/5A, +12V, +25V, -12V at 1A 100VA: 2x12V-4A, 2x15V-3A, 2x20V-2.5A, 2x25V-2A, 2x30V-1.5A, 2x50V-1A 985p (75p p&sp) P&P charge to be added over and above our normal postal charge	<b>TRANSFORMERS</b> 5V 7805 50p 7905 50p 12V 7812 50p 7906 60p 15V 7815 45p 7912 50p 18V 7818 45p 7915 50p 24V 7824 50p 7918 50p 30V 7830 50p 7924 50p 100mA TO92 Plastic package 5V 78L05 30p 79L05 50p 6V 78L06 30p — 8V 78L08 30p — 9V 78L12 30p 79L12 50p 15V 78L15 50p 79L15 60p ICL7660 248p TAA550 50p RC4194 375p IDA1412 150p RC4195 180p 78H05 +5V/5V 585p LM309X 135p 78H12 +12V/5A 640p LM317K 250p 78H5 +5V to +25V 585p LM317KP 450p 5A 78H5 +5V to +25V 585p LM323K 450p 79HG — 2.5V to -24V, 5A 685p LM337 175p 78S40 225p LM723 Var 30p 78S40 225p	

<b>CMOS</b> 4072 25 4536 4000 20 4073 28 4538 80 4001 20 4076 28 4541 95 4002 25 4077 25 4543 70 4006 75 4078 25 4544 150 4007 25 4081 25 4548 40 4008 80 4082 25 4549 400 4009 45 4085 80 4551 245 4010 60 4086 60 4554 180 4011 25 4089 125 4555 35 4012 25 4093 37 4556 55 4013 60 4094 70 4557 250 4014 60 4095 95 4558 120 4015 60 4096 100 4559 395 4016 40 4097 275 4560 180 4017 60 4098 80 4561 104 4018 60 4099 110 4562 325 4019 50 4160 95 4566 185 4020 90 4161 98 4569 250 4022 43 4162 98 4569 175 4021 50 4163 98 4570 45 4022 87 4174 98 4572 30 4023 87 4175 105 4581 99 4024 50 4194 105 4582 99 4025 22 4408 850 4583 100 4026 90 4409 850 4584 60 4027 43 4410 725 4585 70 4028 45 4411 725 4586 225 4029 45 4412 805 4589 185 4030 35 4415 590 4600 95 4031 130 4419 280 40097 45 4032 70 4422 770 40098 42 4033 130 4425 880 40100 215 4034 148 4440 900 40101 130 4035 70 4450 360 40102 140 4036 275 4451 350 40103 412 4037 115 4490 450 40104 120 4038 75 4500 390 40105 220 4039 280 4501 38 40106 80 4040 80 4502 80 40107 55 4041 57 4503 40 40108 325 4042 50 4504 99 40109 100 4043 42 4505 385 40110 235 4044 50 4506 100 40114 240 4045 110 4507 45 40161 194 4046 60 4508 130 40163 75 4047 60 4510 58 40174 75 4048 55 4511 55 40175 25 4049 38 4512 55 40181 220 4050 38 4513 150 40182 80 4051 70 4514 115 40192 75 4052 60 4515 115 40193 95 4053 60 4516 115 40194 140 4054 85 4517 275 40195 75 4055 85 4518 48 40244 198 4056 85 4519 32 40245 198 4057 1000 4520 53 40257 198 4059 435 4521 115 40373 220 4060 88 4522 125 40374 220 4061 500 4526 80 45106 586 4062 988 4527 65 4063 85 4528 68 4066 45 4529 150 4067 245 4530 90 4068 25 4531 130 4069 25 4532 65 4070 25 4534 400 4071 25	<b>OPTO ELECTRONICS</b> LEDs with clips TIL209 10 TIL211 GRN 14 TIL212 Yel. 14 TIL220 2" Red 12 2" Green, Yellow or Amber 14 0.2" Bi colour Red/Green 100p Green/Yellow 115p 0.2" Tri colour Red/Green/Yellow 85p Hi-Brightness Red 58p High-Bi Green or Red 58p Flashing red 55p 0.2" red 55p Square LEDs, Red, Green, Yellow 30p Red/Green Stackable LEDs Red, Green or Yellow 18p Triangular LEDs Red or yellow 18p Green or yellow 22p LD271 Infra Red 46p SF205 Detector 118p ILC32 Infra Red 52p TIL78 Detector 58p TIL36 75p TIL100 75p BARGRAPH, Red 10 segments 275p	<b>ISOLATORS</b> IL74 145 ILD74 145 ILQ74 275 TIL11/2/4 70 ILC76 Darlington 135 TIL117 125 AN33 Photo Darlington 138	<b>7 Segment Displays</b> TIL312 3" CC 120 TIL313 3" CC 120 TIL321 5" CA 140 TIL322 5" CC 140 TIL729/730 140 DL704 3" CC 125 DL707 3" CA 125 FND357 Red 120 FND500 130 3" Green CA 150 5" Green CA 150 3" x 7 Red CA 150 3" x 7 Green CA 150 LCD 3 1/2 Digits 496 LCD 4 Digits 530 LCD 6 Digits 625 Reflective Switch 225 SLOTTED Optical Switch similar to Ref. Comp's 295
---	---	---	---

<b>COMPUTER CORNER</b> ● QL RGB MONITOR, Medium resolution £239 ● EPSON RX80 Printer £229 ● EPSON RX80 F/T Printer £245 ● EPSON FX80 Printer £316 ● EPSON FX100 Printer £435 ● KAGATA/TAXAN KP810 Printer £235 ● KAGATA/TAXAN KP10 Printer £339 ● SEIKOSHA GP100A Printer £170 ● BROTHER HR15 Daisywheel £339 Cable for above printers to interface with BBC Micro £7 ● TEX EPSON ERASER — Erases up to 25 Eproms. Has a built-in safety switch. £30 ● SPARE 'UV' Lamp Bulb £8 ● C12 Computer CASSETTES in library cases 38p ● 8 1/2" & 9 1/2" Fan Fold paper (1000 sheets) £7 (Carr. 150p) (Securicor Carriage charge on printers is £7) CALL IN AT OUR SHOP FOR A DEMONSTRATION ON ANY OF THE ABOVE ITEMS. BE SATISFIED BEFORE YOU BUY OR WRITE IN FOR OUR DESCRIPTIVE MICRO PERIPHERALS LEAFLET.
---

<b>DISC DRIVES</b> (CUMANA) DRIVES CASED WITH PSU & CABLES ● CS100 — Single Cased with PSU, 40 Track, 5 1/4" S/S 100K £129 ● CD200 — Twin Cased with PSU, 40 Track, 5 1/4" S/S 200K £265 ● CS200 — Single Cased with PSU, 80 Track, 5 1/4" S/S 200K £175 ● CD400 — Twin Cased with PSU, 80 Track, 5 1/4" S/S 400K £349 <b>MITSUBISHI 5 1/4" SLIM LINE DISC DRIVES</b> Double Sided, Double Density, Track Density 96 TPI, Track to track access time 3msec. ● MITSUBISHI Single Slimline, 5 1/4" Cased with PSU, DSSD 1 Megabyte (400K with BBC) £199 ● MITSUBISHI Twin Slimline, 5 1/4" Cased with PSU, DSSD 2 Megabyte, (800K with BBC) £425 5 1/4" DISKETTES (Lifetime Warranty) ● 10 3M Diskettes Single side Double density £13 ● 10 3M Diskettes Double side Double density £23 N.B Carriage on Drives £7 securicor
---

**SPECTRUM 32K UPGRADE**  
 Upgrade your 16K Spectrum to full 48K with our RAM Upgrade Kit. Very simple to fit. Fitting instructions supplied. £22

**SPECTRUM CENTRONICS/RS232 PRINTER INTERFACE**  
 ★ It was the first! It is still the best!  
 ★ Centronics and Bi-DIRECTIONAL RS-232 with full hand-shaking.  
 ★ Obvies SPECTRUM LLIST and LPRINT.  
 ★ Split-Speed Operation for RS-232.  
 (Use it to communicate with the BBC MICRO or OTHER PERIPHERALS).  
 ★ Interface 1, Interface \* & Microdrive compatible.  
 ★ Configuration program creates customised M/C driver to suit your printer.  
 ★ Hi-RES screen dumps in 2 sizes on EPSON, SEIKOSHA, STAR, SHINWA, MANNESMAN TALLY, NEC, RITEKAM, KAGA, etc. This is a STANDARD FEATURE! Not an extra.  
 ★ Compatible with TASWORD TWO and most professional programs.  
 Complete Unit incl. Software tape + manual £29.95  
 Special Interface Cable £8

**BBC & MICROCOMPUTER & ACCESSORIES**  
 BBC Model B Only £3@5  
 We stock the full range of BBC Micro peripherals, Hardware & Software like, Disc Drives (Top quality Cumana & Mitsubishi), Diskettes, Printers, printer, Paper, Interface Cable, Dust Covers, Cassette Recorder & Cassettes, Monitors, Connectors (Ready made Cables, Plugs & Sockets), Plotter (Graphic Tablet) EPROM Programmer, Lightpen Kit, Joysticks, Sideways ROM Board, EPROM Eraser, Machinecode ROM. The highly sophisticated Waitford's 16K BEEB DFS, WORDWISE, BEEB-CALC, Software (Educational Applications & Games), BOOKS, etc, etc. Please send SAE for our description leaflet.

# electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 1, Golden Square, London W1R 3AB. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

## BEGINNERS GUIDE

<input type="checkbox"/>	Beginner's Guide to Basic Programming Stephenson	£5.35
<input type="checkbox"/>	Beginner's Guide to Digital Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Electronics	£5.35
<input type="checkbox"/>	Beginner's Guide to Integrated Circuits	£5.35
<input type="checkbox"/>	Beginner's Guide to Computers	£5.35
<input type="checkbox"/>	Beginner's Guide to Microprocessors	£5.35

## COOKBOOKS

<input type="checkbox"/>	Master IC Cookbook Hallmark	£10.15
<input type="checkbox"/>	Microprocessor Cookbook M. Hordeski	£9.50
<input type="checkbox"/>	IC Op Amp Cookbook Jung	£15.10
<input type="checkbox"/>	PLL Synthesiser Cookbook H. Kinley	£7.70
<input type="checkbox"/>	Active Filter Cookbook Lancaster	£14.30
<input type="checkbox"/>	TV Typewriter Cookbook Lancaster	£12.50
<input type="checkbox"/>	CMOS Cookbook Lancaster	£13.50
<input type="checkbox"/>	TTL Cookbook Lancaster	£13.50
<input type="checkbox"/>	Micro Cookbook Vol. 1 Lancaster	£15.30
<input type="checkbox"/>	BASIC Cookbook K. Tracton	£6.00
<input type="checkbox"/>	MC6809 Cookbook C. Warren	£7.25

## ELECTRONICS

<input type="checkbox"/>	Principles of Transistor Circuits Amos	£9.00
<input type="checkbox"/>	Design of Active Filters with experiments Berlin	£11.30
<input type="checkbox"/>	Electronic Devices & Circuit Theory Boylestad	£14.45
<input type="checkbox"/>	49 Easy to Build Electronic Projects Brown	£6.00
<input type="checkbox"/>	How to build Electronic Kits Capel	£3.55
<input type="checkbox"/>	How to Design and build electronic instrumentation Carr	£9.35
<input type="checkbox"/>	Introduction to Microcomputers Daglecs	£7.20
<input type="checkbox"/>	Electronic Components and Systems Dennis	£15.00
<input type="checkbox"/>	Principles of Electronic Instrumentation De Sa	£11.45
<input type="checkbox"/>	Giant Handbook of Computer Software	£12.95
<input type="checkbox"/>	Giant Handbook of Electronic Circuits	£21.00
<input type="checkbox"/>	Giant Handbook of Electronic Projects	£13.60
<input type="checkbox"/>	Electronic Logic Circuits Gibson	£6.45
<input type="checkbox"/>	Analysis and Design of Analogue Integrated Circuits Gray	£42.50
<input type="checkbox"/>	Basic Electronics Grob	£11.30
<input type="checkbox"/>	Lasers - The Light Fantastic Hallmark	£7.70
<input type="checkbox"/>	Introduction to Digital Electronics & Logic Joynson	£6.25
<input type="checkbox"/>	Electronic Testing and Fault Diagnosis Loveday	£7.85
<input type="checkbox"/>	Electronic Fault Diagnosis Loveday	£6.25
<input type="checkbox"/>	Essential Electronics A-Z Guide Loveday	£7.50
<input type="checkbox"/>	Microelectronics Digital & Analogue circuits and systems Millman	£12.25
<input type="checkbox"/>	103 Projects for Electronics Experimenters Minis	£8.30
<input type="checkbox"/>	VLSI System Design Muroga	£34.10
<input type="checkbox"/>	Practical Solid State Circuit Design Olesky	£28.50
<input type="checkbox"/>	Power FETs and their application Oxner	£10.80
<input type="checkbox"/>	Master Handbook of IC Circuits Powers	£12.85
<input type="checkbox"/>	Electronic Drafting and Design Rashkutoff	£26.65
<input type="checkbox"/>	VOM - VTVM Handbook Risse	£8.50
<input type="checkbox"/>	Video and Digital Electronic Displays Sharr	£28.85
<input type="checkbox"/>	Understanding Electronic Components Sinclair	£7.50
<input type="checkbox"/>	Electronic Fault Diagnosis Sinclair	£4.50
<input type="checkbox"/>	Physics of Semiconductor Devices Sze	£16.90
<input type="checkbox"/>	Digital Circuits and Microprocessors Taub	£11.25
<input type="checkbox"/>	Active Filter Handbook	£8.50
<input type="checkbox"/>	Designing with TTL Integrated Circuits Texas	£15.20
<input type="checkbox"/>	Transistor Circuit Design Texas	£15.20
<input type="checkbox"/>	Digital Systems: Principles and Applications Tocco	£14.95
<input type="checkbox"/>	Master Handbook of Telephones Traister	£12.50
<input type="checkbox"/>	How to build Metal/Treasure Locators Traister	£6.00
<input type="checkbox"/>	99 Fun to Make Electronic Projects Tymony	£8.50
<input type="checkbox"/>	33 Electronic Music Projects you can build Winston	£6.95

## COMPUTERS & MICROCOMPUTERS

<input type="checkbox"/>	BASIC Computer Games Ahl	£6.35
<input type="checkbox"/>	From BASIC to PASCAL Anderson	£11.30
<input type="checkbox"/>	UNIX - The Book Bananam	£9.00
<input type="checkbox"/>	Z80 Microcomputer Handbook Barden	£15.05
<input type="checkbox"/>	Microcomputer Maths Barden	£11.90
<input type="checkbox"/>	Digital Computer Fundamentals Barter	£11.75
<input type="checkbox"/>	Visicalc Book. APPLE Edition Bell	£15.55
<input type="checkbox"/>	Visicalc Book. ATARI Edition Bell	£15.55
<input type="checkbox"/>	Introduction to Microprocessors Brunner	£23.00
<input type="checkbox"/>	Programming your APPLE II Computer Bryan	£9.25
<input type="checkbox"/>	Microprocessor Interfacing Carr	£8.50
<input type="checkbox"/>	Microcomputer Interfacing Handbook A/D & D/A Carr	£10.50
<input type="checkbox"/>	Musical Applications of Microprocessors Chamberlain	£28.85
<input type="checkbox"/>	30 Computer Programs for the Home Owner in BASIC D. Chance	£9.25
<input type="checkbox"/>	Microcomputers Dirkson	£9.30
<input type="checkbox"/>	APPLE Personal Computer for Beginners Dunn	£9.50
<input type="checkbox"/>	Microcomputers/Microcomputers - An Intro Gioone	£36.50

<input type="checkbox"/>	Troubleshooting Microprocessors and Digital Logic Goodman	£11.25
<input type="checkbox"/>	Getting Acquainted with your VIC 20 Hartnell	£8.50
<input type="checkbox"/>	Getting Acquainted with your ZX81 Hartnell	£5.95
<input type="checkbox"/>	Let your BBC Micro Teach you to program Hartnell	£7.50
<input type="checkbox"/>	Programming your ZX Spectrum Hartnell	£8.95
<input type="checkbox"/>	The ZX Spectrum Explored Hartnell	£6.95
<input type="checkbox"/>	How to Design, Build and Program your own working Computer System Havilano	£10.50
<input type="checkbox"/>	BASIC Principles and Practice of Microprocessors Heffer	£8.00
<input type="checkbox"/>	Hints and Tips for the ZX81 Hewson	£5.25
<input type="checkbox"/>	What to do when you get your hand on a Microcomputer Holtzman	£9.95
<input type="checkbox"/>	34 More Tested Ready to Run Game Programs in BASIC Horn	£7.70
<input type="checkbox"/>	COBOL Jackson	£9.25
<input type="checkbox"/>	Microcomputer Builders' Bible Johnson	£14.75
<input type="checkbox"/>	Digital Circuits and Microcomputers Johnson	£16.95
<input type="checkbox"/>	PASCAL for Students Kemp	£6.95
<input type="checkbox"/>	The C - Programming Language Kernighan	£19.25
<input type="checkbox"/>	The ZX81 Companion Maunder	£9.50
<input type="checkbox"/>	Guide to Good Programming Practice Meek	£9.50
<input type="checkbox"/>	Principles of Interactive Computer Graphics Newman	£13.75
<input type="checkbox"/>	Theory and Practice of Microprocessors Nicholas	£11.45
<input type="checkbox"/>	Exploring the World of the Personal Computer Nilles	£12.95
<input type="checkbox"/>	Microprocessor Circuits Vol. 1. Fundamentals and Microcontrollers Noll	£9.80
<input type="checkbox"/>	Beginner's Guide to Microprocessors Parr	£5.35
<input type="checkbox"/>	Microcomputer Based Design Peatman	£11.45
<input type="checkbox"/>	Digital Hardware Design Peatman	£10.75
<input type="checkbox"/>	BBC Micro Revealed Ruston	£9.45
<input type="checkbox"/>	Handbook of Advanced Robotics Safford	£14.45
<input type="checkbox"/>	1001 Things to do with your own personal computer Sawusch	£8.50
<input type="checkbox"/>	Easy Programming for the ZX Spectrum Stewart	£7.45
<input type="checkbox"/>	Microprocessor Applications Handbook Stout	£46.45
<input type="checkbox"/>	Handbook of Microprocessor Design and Applications Stout	£46.45
<input type="checkbox"/>	Programming the PET/CBM West	£16.40
<input type="checkbox"/>	An Introduction to Microcomputer Technology Williamson	£8.20
<input type="checkbox"/>	Computer Peripherals that you can build Wolfe	£14.75
<input type="checkbox"/>	Microprocessors and Microcomputers for Engineering Students and Technicians Wooland	£7.10

## REFERENCE BOOKS

<input type="checkbox"/>	Electronic Engineers' Handbook Fink	£66.60
<input type="checkbox"/>	Electronic Designers' Handbook Giacometto	£77.75
<input type="checkbox"/>	Illustrated Dictionary of Microcomputer Technology Hordeski	£8.45
<input type="checkbox"/>	Handbook for Electronic Engineering Technicians Kauffman	£40.50
<input type="checkbox"/>	Handbook of Electronic Calculators Kauffman	£35.00
<input type="checkbox"/>	Modern Electronic Circuit Reference Manual Marcus	£51.95
<input type="checkbox"/>	International Transistor Selector Towers	£14.50
<input type="checkbox"/>	International Microprocessor Selector Towers	£16.00
<input type="checkbox"/>	International MOS Power and other FET Selector	£10.95
<input type="checkbox"/>	International Digital IC Selector Towers	£10.95
<input type="checkbox"/>	International Op Amp Linear IC Selector Towers	£9.50
<input type="checkbox"/>	Illustrated Dictionary of Electronics Turner	£19.75

## VIDEO

<input type="checkbox"/>	Servicing Home Video Cassette Recorders Hobbs	£14.50
<input type="checkbox"/>	Complete Handbook of Videocassette Recorders Kybett	£10.50
<input type="checkbox"/>	Theory and Servicing of Videocassette Recorders McGinty	£13.50
<input type="checkbox"/>	Beginner's Guide to Video Matthewson	£5.35
<input type="checkbox"/>	Video Recording: Theory and Practice Robinson	£16.00
<input type="checkbox"/>	Video Handbook Van Wezel	£24.00
<input type="checkbox"/>	Video Techniques White	£14.45

Please send me the books indicated. I enclose cheque/postal order for £..... Prices include postage and packing. I wish to pay by Access/Barclaycard. Please debit my account.

5 2 2 4

4 9 2 9

Signed.....

Name.....

Address.....

.....

.....

# SERVICE SHEET

## Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;
- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);
- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;
- We receive a large number of letters asking if we have published projects for particular items of equipment. Whilst some of these can be answered simply and quickly, others would seem to demand the compiling of a long and detailed list of past projects. To help both you and us, we have made a full index of past ETI projects and features available (see under Backnumbers, below) and we trust that, wherever possible, readers will refer to this before getting in touch with us.
- We will not reply to queries that are not accompanied by an SAE (or international reply coupon). We are not able to answer enquiries over the telephone. We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.
- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

## Subscriptions

The prices of ETI subscriptions are as follows:

UK:	£15.00
Overseas:	£17.00 Surface Mail
	\$22.00 Surface Mail (USA)
	£42.00 Air Mail

Send your order and money to: ETI Subscriptions Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire, HP1 1BB (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

## Backnumbers

Backnumbers of ETI are held for one year only from the date of issue. The cost of each is the current cover price of ETI plus 50p, and orders should be sent to: ETI Backnumbers Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire, HP1 1BB. Cheques, postal orders, etc should be made payable to ASP Ltd. We suggest that you telephone first to make sure there are still stocks of the issue you require: the number is (0442) 48432.

We would normally expect to have ample stocks of each of the last twelve issues, but obviously, we cannot guarantee this. Where a backnumber proves to be unavailable, or where the issue you require appeared more than a year ago, photocopies of

individual articles can be ordered instead. These cost £1.50 (UK or overseas surface mail), irrespective of article length, but note that where an article appeared in several parts each part will be charged as one article. Your request should state clearly the title of the article you require and the month and year in which it appeared. Where an article appeared in several parts you should list these individually. An index listing projects only from 1972 to September 1984 was published in the October 1984 issue and can be ordered in the same way as any other photocopy. If you are interested in features as well as projects you will have to order an index covering the period you require only. A full index for the period from 1972 to March 1977 was published in the April 1977 issue, an index for April 1977 through to the end of 1978 was published in the December 1978 issue, the index for 1979 was published in January 1980, the 1980/81 index in January 1982, the 1982 index in December 1982, the 1983 index in January 1984 and the 1984 index in January 1985. Photocopies should be ordered from: ETI Photocopies, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Cheques, postal orders, etc should be made payable to ASP Ltd.

## Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you all the boring details. (Don't forget to give us your telephone number).

## Trouble With Advertisers

So far as we know, all our advertisers work hard to provide a good service to our readers. However, problems can occur, and in this event you should:

1. Write to the supplier, stating your complaint and asking for a reply. Quote any reference number you may have (in the case of unsatisfactory or incomplete fulfilment of an order) and give full details of the order you sent and when you sent it.
2. Keep a copy of all correspondence.
3. Check your bank statement to see if the cheque you sent has been cashed.
4. If you don't receive a satisfactory reply from the supplier within, say, two weeks, write again, sending your letter recorded delivery, or telephone, and ask what they are doing about your complaint.

If you exhaust the above procedure and still do not obtain a satisfactory response from the supplier, then please drop us a line. We are not able to help directly, because basically the dispute is between you and the supplier, but a letter from us can sometimes help to get the matter sorted out. But please, don't write to us until you have taken all reasonable steps yourself to sort out the problem.

We are a member of the mail order protection scheme, and this means that, subject to certain conditions, if a supplier goes bankrupt or into liquidation between cashing your cheque and supplying the goods for which you have paid, then it may be possible for you to obtain compensation. From time to time, we publish details of the scheme near our classified ads, and you should look there for further details.

## OOPS!

Corrections to projects are listed below and normally appear for several months. Large corrections are published just once, after which a note will be inserted to say that a correction exists and that copies can be obtained by sending in an SAE.

## ZX81 EPROM Programmer (May 1984)

On the overlay diagram on page 27, the resistance shown between IC9 and IC5 should be R2 not R1, the resistance shown between IC6 and IC7 should be R8 not R5. In the parts list, C1 should be listed as 220 uF not 22 uF; the circuit diagram gives the value correctly. R3 is marked "see text" but no reference is then made to it: it should be chosen to suit the LED used. LED1 is shown reversed on the circuit diagram on page 28 but the connections shown on the overlay diagram are correct. The first statement in program 1 on page 30 should read "SET PERSONALITY SWITCHES THEN PRESS CONT".

## Spectrum Joystick Interface (June 1984)

The PCB and the circuit diagram do not agree; the circuit diagram is correct, and all PCBs sent out by the PCB service should have been amended. IC3 is 74LS241, as correctly stated in the parts list but incorrectly given in the footnote to the circuit diagram.

## CMOS Tester (August 1984)

C3 and C2 are reversed on the overlay: C3 is the electrolytic and C2 the polyester. R33 is 100K, not 1M as given in the parts list, and RV1 is a 1M horizontal skeleton preset. R1-16 are two, eight-resistor SIL packages, the component labelled C14 on the overlay is SK1, and the connections to D2 shown in Fig. 3 are reversed. On the circuit diagram, the eight lines connecting SW9-16 to the inverters are shown in reverse sequence. Some of the inverters have been given the wrong designations; the correct sequence, reading down from the top, is: IC1f, IC2a, IC2b, IC1e, IC1d, IC1c, IC1b, IC1a, IC2c, IC2d, IC2e, IC3d, IC3a, IC3b, IC3c, IC2f. Finally, the pin numbers are missing from ICs 3e and f; the input of IC3e is pin 11 and its output pin 12, and the input of IC3f is pin 14 and its output is pin 15. The PCB is correct in all respects.

## Sharp Joystick Interface (August 1984)

Some of the inverter pins are incorrectly labelled on the circuit diagram. Pins 11 and 10 are shown reversed on IC1b, pins 9 and 8 are shown reversed on IC1c, and the output of IC4d is pin 10, not pin 20. Note that a number of the inverters have been incorrectly shown as non-inverting buffers.

## AM/FM Radio (November 1984)

In Fig. 2, the oscillator and IF sections should be shown connected to ground; the PCB is correct. In Fig. 4, C31 should be 10n to give the 75us deemphasis shown in Fig. 3, but 4n7 has been found to give a brighter midrange. R38 in Fig. 5 should, of course, be 820k rather than 280k and it and the bottom end of C38, C44 etc should be shown connected to ground. In the construction section on page 25, four pieces of 8mm plywood are mentioned but in fact only three are needed — the fourth side is the front panel. See also the note in December News Digest regarding availability of the inductors.

## Digital Control Port (November 1984)

The second sentence in the "Testing" section on page 30 should include the words 'without any ICs in place'. In the second paragraph of that section, the check for +5V should be made on pin 3 of IC101, not IC1. At the bottom of the first column on page 31, the last sentence should finish with B3 = 0.

## Video Vandal (November 1984)

In Fig. 8 on page 54, R16 and R17 should be shown connected to the base of Q4, and C12 and SW2 should be in the D output line rather than the OV line. It may also be beneficial to add a diode across R3 with its anode connected to the slider of RV1. In Fig. 10, R52 and LED2 are shown connected across the +12V supply but it is better to place them across the -12V supply so as to even-up the dissipation in the ICs.

# Rapid Electronics

**MAIL ORDERS:**  
Unit 3, Hill Farm Industrial Estate,  
Boxted, Colchester, Essex CO4 5RD.  
Tel. Orders: Colchester (0206) 36412.  
Telex: 987756.

**ACCESS AND BARCLAYCARD WELCOME**

### MIN. D CONNECTORS

9 way	15 way	25 way	37 way
Plugs solder lugs 55p	65p	90p	150p
Right angle 90p	135p	200p	350p
Sockets solder lugs 50p	100p	135p	260p
Right angle 120p	180p	290p	420p
Covers 100p	90p	100p	110p

### CONNECTORS

DIN	Plug	Skt	Jack	Plug	Skt
2 pin	9p	9p	2.5mm	10p	10p
3 pin	12p	10p	3.5mm	9p	9p
5 pin	13p	11p	Standard	16p	20p
Phono	10p	12p	Stereo	24p	25p
1mm	12p	13p	4mm	18p	17p

### SOLDERING IRONS

Antex CS 17W Soldering iron	430
2.3 and 4.7mm bits to suit	85
Antex XS 25W soldering iron	530
3.3 and 4.7mm bits to suit	85
Solder pump desoldering tool	480
Spare nozzle for above	70
10 metres 22 swg solder	100
0.5kg 22 swg solder	750

### CONNECTORS

DIN	Plug	Skt	Jack	Plug	Skt
2 pin	9p	9p	2.5mm	10p	10p
3 pin	12p	10p	3.5mm	9p	9p
5 pin	13p	11p	Standard	16p	20p
Phono	10p	12p	Stereo	24p	25p
1mm	12p	13p	4mm	18p	17p

### TRANSFORMERS

3VA PCB Mounting	2x6V@0.25A; 2x9V@0.15A	40p
2x12V@0.12A; 2x15V@0.1A	180p	
6VA PCB Mounting	2x6V@0.5A; 2x9V@0.4A	40p
2x12V@0.3A; 2x15V@0.25A	270p	
Standard Chassis Mounting	6VA: 2x6V@0.5A; 2x9V@0.4A	40p
2x12V@0.3A; 2x15V@0.25A	240p	
12VA: 2x6V@0.1A; 2x9V@0.6A	40p	
2x15V@0.4A; 2x20V@0.3A	350p	

### VERO

Veroboard .395	395
Veroboard Size 0.1 in matrix	
2.5 x 1	26
2.5 x 3.75	95
3.75 x 5	120
4.75 x 17	350
4.75 x 17	455
VO board	190
Veroboard per 100	
Single sided	55
Double sided	65
Spot face cutter	145
Pin insertion tool	185
Writing pen	375
Spare spool 75p	6

### SWITCHES

Submit toggle:	SPST 55p, SPDT 60p, DPDT 65p.
Miniature toggle:	SPDT 80p, SPDT centre off 90p, DPDT 90p, DPDT centre off 100p.
Standard toggle:	SPST 35p, DPDT 48p.
Miniature DPDT slide 14p.	
Push to make 15p.	
Push to break 22p.	
Rotary type adjustable stop:	1P12W, 2P25W, 3P4W all 55p each.
DIL switches:	276A 250 495, 276A 300 495, 276A BCC 495.
4SPST 80p, 6SPST 80p, 8SPST 100p.	
Min. DPDT slide 14p, Push-make 15p.	

### MICRO

2712B-250	1225	6800	200	6522	330
6116P3	480	6802	280	6532	520
6264P15	2980	6809	600	6551	540
4116P4	70	6810	140	8085A	320
4164-15	480	6821	140	8156	380
41256-15	2850	6840	360	8251	350
Z80A CPU	290	6850	165	8253	370
Z80A P1	320	6852	240	8255	320
Z80A CTC	320	6875	500	8259	400
Z80A S1	880	6880	100	MC1488	70
Z80A DMA	880	6502	370	MC1489	70

### DIODES

BY127	12	1N4002	3
0A47	10	1N4006	7
0A90	8	1N4007	7
0A100	7	1N5400	12
0A200	8	1N5404	16
0A202	8	1N5406	17
1N914	4	400mW Zen	6
1N1418	3	1.3W zeners	13

### SOCKETS

8 pin	25p	Wire wrap	25p
14 pin	45p	8 pin	45p
16 pin	10p	16 pin	55p
18 pin	12p	18 pin	60p
20 pin	13p	20 pin	65p
22 pin	15p	22 pin	75p
24 pin	17p	24 pin	82p
28 pin	15p	28 pin	95p
40 pin	25p	40 pin	135p
Professional ZIF sockets			
24 pin 430p		28 pin 480p	
40 pin 595p			

### COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. \*W 5% Resistor kit. Contains 10 of each value from 4.7 ohms to 1M (total of 650 resistors). 530

Ceramic Cap. kit. 5 of each value - 22p to 0.01u (135 caps) 370

Polyester Cap. kit. 5 of each value from 0.01 to 1uF (65 caps) 575

Resistor kit. Contains 5 of each value from 100 ohms to 1M (total 65 resistors). 425

Nut and Bolt kit (total 300 items): 180p

25 6BA 1/4" bolts	50 6BA washers	50 6BA nuts
25 6BA 1/2" bolts	25 4BA 1/4" bolts	50 6BA washers
50 6BA nuts	50 6BA washers	50 6BA nuts

### OPTO

3mm red	8	5mm red	8
3mm green	11	5mm green	11
3mm yellow	11	5mm yellow	11
Clips to suit - 3p each			
Rectangular:			
TL32	40	TL11	60
TL17	40	TL18	40
TL19	40	TL20	40
TL21	40	TL22	40
TL23	40	TL24	40
TL25	40	TL26	40
TL27	40	TL28	40
TL29	40	TL30	40
TL31	40	TL32	40
TL33	40	TL34	40
TL35	40	TL36	40
TL37	40	TL38	40
TL39	40	TL40	40
TL41	40	TL42	40
TL43	40	TL44	40
TL45	40	TL46	40
TL47	40	TL48	40
TL49	40	TL50	40
TL51	40	TL52	40
TL53	40	TL54	40
TL55	40	TL56	40
TL57	40	TL58	40
TL59	40	TL60	40
TL61	40	TL62	40
TL63	40	TL64	40
TL65	40	TL66	40
TL67	40	TL68	40
TL69	40	TL70	40
TL71	40	TL72	40
TL73	40	TL74	40
TL75	40	TL76	40
TL77	40	TL78	40
TL79	40	TL80	40
TL81	40	TL82	40
TL83	40	TL84	40
TL85	40	TL86	40
TL87	40	TL88	40
TL89	40	TL90	40
TL91	40	TL92	40
TL93	40	TL94	40
TL95	40	TL96	40
TL97	40	TL98	40
TL99	40	TL100	40

### LINEAR

IC7611	98	LM358	50	LM3915	265	NE567	130	TD1024	115
ICL7621	190	LM377	210	LM13600	100	NE570	370	NE571	370
ICL7622	200	LM380	80	MC13110	250	NE571	370	TL062	65
ICL8038	295	LM381	150	MC1496	70	NE5532	160	TL064	105
ICL8211A	220	LM382	130	MC3302	75	NE5534	105	TL071	60
ICL8224	785	LM383	140	MC3340	130	RC4136	65	TL072	60
ICM755	80	LM386	90	MF10CN	330	RC4568	40	TL073	110
ICM7556	150	LM387	120	ML922	390	SL486	195	TL081	30
ICM7566	150	LM389	60	ML924	290	SL490	220	TL082	50
ICM7567	150	LM390	40	ML925	290	SN76018	150	TL084	105
ICM7568	150	LM391	40	ML926	290	SN76477	380	TL170	50
ICM7569	150	LM392	40	ML927	290	SP9225	250	TL2240	140
ICM7570	150	LM393	40	ML928	210	SP0256A1	245	ULN2003	80
ICM7571	150	LM394	40	ML929	210	Speech data 50	ULN2004	80	
ICM7572	150	LM395	40	ML930	210	TBA800	70	XR2206	365
ICM7573	150	LM396	40	ML931	210	TBA810	90	XN414	80
ICM7574	150	LM397	40	ML932	210	TBA820	90	XN422	85
ICM7575	150	LM398	40	ML933	210	TBA950	220	XN424P	130
ICM7576	150	LM399	40	ML934	210	TCA940	165	XN425E	350
ICM7577	150	LM399	85	ML935	115	TDA1008	320	XN426S	300
ICM7578	150	LM399	85	ML936	140	TDA1022	490	XN427E	600
ICM7579	150	LM399	85	ML937	140	XN428	450	XN429	450
ICM7580	150	LM399	85	ML938	140	XN430	450	XN431	450
ICM7581	150	LM399	85	ML939	140	XN432	450	XN433	450
ICM7582	150	LM399	85	ML940	140	XN434	450	XN435	450
ICM7583	150	LM399	85	ML941	140	XN436	450	XN437	450
ICM7584	150	LM399	85	ML942	140	XN438	450	XN439	450
ICM7585	150	LM399	85	ML943	140	XN440	450	XN441	450
ICM7586	150	LM399	85	ML944	140	XN442	450	XN443	450
ICM7587	150	LM399	85	ML945	140	XN444	450	XN445	450
ICM7588	150	LM399	85	ML946	140	XN446	450	XN447	450
ICM7589	150	LM399	85	ML947	140	XN448	450	XN449	450
ICM7590	150	LM399	85	ML948	140	XN450	450	XN451	450
ICM7591	150	LM399	85	ML949	140	XN452	450	XN453	450
ICM7592	150	LM399	85	ML950	140	XN454	450	XN455	450
ICM7593	150	LM399	85	ML951	140	XN456	450	XN457	450
ICM7594	150	LM399	85	ML952	140	XN458	450	XN459	450
ICM7595	150	LM399	85	ML953	140	XN460	450	XN461	450
ICM7596	150	LM399	85	ML954	140	XN462	450	XN463	450
ICM7597	150	LM399	85	ML955	140	XN464	450	XN465	450
ICM7598	150	LM399	85	ML956	140	XN466	450	XN467	450
ICM7599	150	LM399	85	ML957	140	XN468	450	XN469	450
ICM7600	150	LM399	85	ML958	140	XN470	450	XN471	450

### TRANSISTORS

AC125	35	BC158	11	BC177	7	BC183L	10	BC184L	10
AC126	30	BC159	10	BC178	7	BC184	10	BC185	10
AC127	30	BC160	10	BC179	7	BC185	10	BC186	10
AC128	30	BC161	10	BC180	10	BC186	10	BC187	10
AC129	30	BC162	10	BC181	10	BC187	10	BC188	10
AC130	30	BC163	10	BC182	10	BC188	10	BC189	10
AC131	30	BC164	10	BC183	10	BC189	10	BC190	10
AC132	30	BC165	10	BC184	10	BC190</			



# DIGEST

## Alliance For Science

Three trade unions concerned with science and technology have got together to form the Alliance for Science, a campaign aimed at promoting expansion in the UK's research and development programmes. The Alliance was launched at a press conference in London on December the 3rd and brings together the

Association of Scientific, Technical and Managerial Staffs (ASTMS), the Association of University Teachers (AUT) and the Institution of Professional Civil Servants (IPCS).

The Alliance has published a pamphlet in which they set out their aims. They want to highlight the decline in research and development spending in this country compared with that of our competitors. They claim that R & D spending in this country has been growing at a rate of 2.8% a

year compared with 3.3% in France, 4.7% in Germany and 6.4% in Japan. They also want to bring to public attention the damage they believe is being done by spending cuts in the research councils, government research departments and higher education, the crucial role they believe R & D plays in the regeneration of the economy, and the disastrous effects the economic climate has on investment in innovation. They plan to campaign to reverse the cuts of recent years in public sector R & D, to ensure that long-term high risk capital is available for private sector R & D and to improve the links between public sector research bodies and industry and the spin-off of defence R & D into civil research. Other aims of the

alliance include the securing of better national R & D statistics and fuller disclosure of company data, increased trade union involvement in R & D decision making and the development of a co-ordinated national science strategy.

The Alliance For Science will be campaigning over the coming months to achieve these aims and plans to make available campaign literature on a number of topics. Those interested should contact either Hilary Tivey at ASTMS, 79 Camden Road, London NW1 9EF, tel 01-267 4422; Paul Cottrell at AUT, United House, 1 Pembridge Road, London W11 3HJ, tel 01-221 4370; or Joe Duckworth at IPCS, 75-79 York Road, London SE1 7AQ, tel 01-928 9951.

● American publishers Blacksburg are planning to produce a book of useful scientific and engineering routines written as programmes for small computers. They are sure that many engineers will have developed such programs for their own use and are particularly interested in BASIC routines for popular micros. Copyright for programs used will remain with the authors, and those interested should contact The Blacksburg Press Group, P.O. Box 242, Blacksburg, Virginia 24060, USA. Their telephone number is 703-951 9030, but do remember that they are in the Eastern time zone!

● Dynamic Logic were a little unhappy about our article on London's new auto-loos (Digest, October '84, p.15). They assure us that it is almost impossible for anyone to be stuck inside a faulty auto-loo for more than a few minutes as there are two handles which can be used to open the

door and it will open automatically after fifteen minutes anyway. I'm sure we're all relieved to hear that.


● Velleman have introduced a tape/slide synchroniser which allows the pulses required for automatic operation of a slide projector to be recorded onto a cassette machine. The kit costs £7.95 plus VAT plus £1.00 post and packing and is available from Electronic & Computer Workshop Ltd, 171 Broomfield Road, Chelmsford, Essex CM1 1RY, tel 0245-262149.

● Maplin have brought out the latest issue of their annual catalogue, as bulky as ever and once again with prices on the page. It costs £1.35 and is available at branches of W.H. Smiths or can be obtained direct from Maplin Electronic Supplies Ltd, P.O. Box 3, Rayleigh, Essex SS6 8LR, tel 0702-554155.
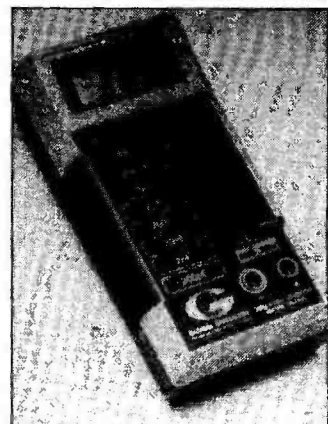
## Hand-Held Capacitance Meter

GSC have introduced a digital capacitance meter designed for hand-held battery operation. Its features include a 3½ digit resolution, accuracy to 0.2% of reading, capacitance measurements of 1pF to 2000 µF and switch selection of capacitance range.

The Model 3000 has a 0.5 inch high numeric liquid-crystal display with annunciators to indicate low battery and excessive compensation of stray capacitance. Designed to operate with a 9V battery, it also has a front-panel zero adjust control to permit nulling of stray and incidental capacitance and a tilt stand for easy positioning. Suggested applications include quality control, inspection, production,



design, calibration, field service, and systems installation.

The Model 3000 comes complete with a pair of test leads, fuses, battery, and an instruction manual and costs £89.50 plus £2.50 post and packing plus VAT.

Global Specialties Corporation, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ, tel 0799-21682.

## It's Quicker By Snail



Quicker, that is, if you're trying to learn a fast-action computer game. For the snail is the symbol of Slomo, a peripheral which actually slows a micro down, even bringing it to a complete halt if desired, to provide infinitely variable skill levels for games, 'freeze-frame' for displays and slow running for development.

Slomo is available in versions to suit the Spectrum, BBC, Electron and Commodore 64 microcomputers and simply plugs into the user port. For all except the BBC a user port extender is provided; Slomo attaches to the tube output on the BBC and an adaptor is used for second processor connections. A push button selects instant freeze-frame which remains for as long as the button is held down. A second button

selects timer mode and operates in conjunction with the speed control to provide continuous adjustment from normal operation to complete stand-still. An LED indicates when the timer mode has been selected.

Slomo works by setting a Bus Request signal on the system bus. The processor acknowledges this and then does nothing further until the signal is removed. The manufacturers claim that it is compatible with any add-on that does not require the Bus Request signal and that it is totally harmless to the host micro. British and World patent applications are pending in respect of the device.

Slomo is expected to find a wide range of applications. In addition to allowing people to cheat at games it can be used as a

software development aid, enabling graphics to be viewed pixel by pixel and sound to be heard note by note. Educational programmes could be controlled using Slomo to suit particular age groups and displays could be frozen for discussion or special emphasis without program modification. Other advantages include the ability to halt a program during interruptions and the possibility of photographing screen displays using the freeze frame.

Slomo is available by mail order and costs £14.95 inclusive of VAT and postage. Customers should remember to state which microcomputer they intend to use it with. Cambridge Computing Research Ltd, 61 Ditton Walk, Cambridge CB5 8QD, tel (trade enquiries only) 0223-214451.

# OMP POWER AMPLIFIER MODULES

\* PRICES INCLUDE V.A.T. \* PROMPT DELIVERIES \* FRIENDLY SERVICE \* LARGE S.A.E. 28p STAMP FOR CURRENT LIST

**OMP POWER AMPLIFIER MODULES** Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi. etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

**Supplied ready built and tested.**



**OMP 100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 360 x 115 x 72mm, PRICE £32.99 + £2.50 P&P.**



**OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm, PRICE £39.99 + £2.50 P&P.**



**OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm, PRICE £62.99 + £3.50 P&P.**



**OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm, PRICE £79.99 + £4.50 P&P.**



**Vu METER** Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order - Standard or P.A.



**19" RACK CASED MOS-FET STEREO AMPLIFIERS** with twin power supplies and L.E.D. Vu meters plus X.L.R. connectors.

Three models (Ratings RMS into 4 ohms)  
**MF200 (100 + 100w) £169.00** Securicor  
**MF400 (200 + 200w) £228.85** Delivery  
**MF600 (300 + 300w) £274.85** £10.00

**LOUDSPEAKERS**  
**5 to 15 INCH Up to 300 WATTS**  
**R.M.S. All speakers 8 ohm**  
**Impedance.**



Cabinet fixing in stock. S.A.E. for details.

**POWER RANGE**

**8" 50 WATT R.M.S. Hi-Fi/Disco.**  
 20 oz. magnet, 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £9.90 Available with black grille £10.90. P&P £1.50 ea.  
**12" 100 WATT R.M.S. Hi-Fi/Disco**  
 50 oz. magnet, 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £26.00 + £3.00 P&P ea.  
**15" 100 WATT R.M.S. Hi-Fi/Disco**  
 50 oz. magnet, 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 20Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. PRICE £34.00 + £3.00 P&P ea.

**McKENZIE**

**12" 85 WATT R.M.S. C1285GP** Lead guitar / keyboard / Disco.  
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £24.99 + £3.00 P&P ea.  
**12" 85 WATT R.M.S. C1285TC** P.A./Disco 2" ally voice coil. Twin cone.  
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £24.99 + £3.00 P&P ea.  
**15" 150 WATT R.M.S. C15** Bass Guitar/Disco.  
 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £49.99 + £4.00 P&P ea.

**WEM**

**5" 70 WATT R.M.S. Multiple Array** Disco etc.  
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £20.00 + £1.50 P&P ea.  
**8" 150 WATT R.M.S. Multiple Array** Disco etc.  
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £27.00 + £1.50 P&P ea.  
**10" 300 WATT R.M.S. Disco/Sound re-enforcement** etc.  
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £30.00 + £2.00 P&P ea.  
**12" 300 WATT R.M.S. Disco/Sound re-enforcement** etc.  
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £38.00 + £3.00 P&P ea.

**SOUNDLAB (Full Range Twin Cone)**

**5" 60 WATT R.M.S. Hi-Fi/Multiple Array** Disco etc.  
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £8.99 + £1.00 P&P ea.  
**6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array** Disco etc.  
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £9.99 + £1.50 P&P ea.  
**8" 60 WATT R.M.S. Hi-Fi/Multiple Array** Disco etc.  
 1 1/4" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £11.99 + £1.50 P&P ea.

**PANTEC HOBBY KITS.** Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

**FM MICROTRANSMITTER (BUG)** 90/106MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 3/4 volt) Price: £8.62 + 75p P&P.

**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £13.74 + 75p P&P.

**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82. Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.27 P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

## BURGLAR ALARM

Better to be 'Alarmed' then terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

**Control Unit** - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

**Indoor alarm** - Electronic swept freq siren. 104dB output.

**Outdoor Alarm** - Electronic swept freq siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

**SAVE £148.00** Usual Price £228.85

**BKE's PRICE £79.99 + £4.00 P&P**

? Why buy a collection of self-assembly boards!

**IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.**



## OMP LINNET LOUDSPEAKERS


The very best in quality and value. Made specially to suit todays need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full Range 45Hz - 20KHz.

**OMP 12/100 watts 20" x 15" x 12" £125.00** per pair

**OMP 10/200 watts 18" x 15" x 11" £145.00** per pair

**OMP 12/300 watts 20" x 15" x 11" £169.00** per pair

Delivery: Securicor £8.00 per pair

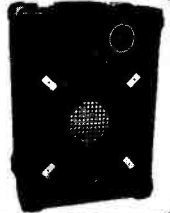

## STEREO CASSETTE DECK

**STEREO CASSETTE DECK**  
 Ideal for installing into Disco and Hi-Fi cabinet/Consoles. Surface mounting (Horizontal). Supplied as one unit with all electronics including mains power supply.

\* Metal top panel Black finish

\* Piano type keys including pause

\* Normal/Chrome tape switch

\* Twin Vu Meters

\* 3 Digit counter

\* Slider Record Level control

Size 171 x 317 mm Depth 110 mm

**PRICE £35.99 + £3.00 P&P**



## 1 K-WATT SLIDE DIMMER

- \* Control loads up to 1Kw
- \* Compact Size 4 1/2" x 1" x 2 1/2"
- \* Easy snap in fixing through panel/cabinet cut out
- \* Insulated plastic case
- \* Full wave control using 8 amp triac
- \* Conforms to BS800

\* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc. PRICE £12.99 + 75p P&P (Any quantity).



## BSR P256 TURNTABLE

- P256 turntable chassis
- S shaped tone arm
- Belt driven
- Aluminium platter
- Precision calibrated counter balance
- Anti-skate (bias) device
- Damped cueing lever
- 240 volt AC operation (Hz)
- Cut-out template supplied
- Completely manual arm.


This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.  
**Price £33.60 each.** + £3.00 P&P ea  
 ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p.


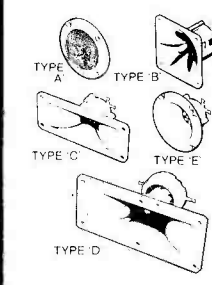
## PIEZO ELECTRIC TWEETERS MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.


- TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.90 each + 40p P&P.
  - TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.49 each + 40p P&P.
  - TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £6.49 each + 40p P&P.
  - TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £8.99 each + 40p P&P.
  - TYPE 'E' (KSN1038A)** 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £5.49 each + 40p P&P.
- LEVEL CONTROL** Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P.



## STEREO DISCO MIXER

**STEREO DISCO MIXER** with 7 band graphic equaliser and 10 segment L.E.D. Vu Meters. Many outstanding features.  
 5 Inputs with individual fader controls:—  
 2 Mag. turntable, 2 Aux. plus Mic. with talk-over switch. Headphone monitor. Master output control with Hi-Low outputs. Compatible with our OMP Power Amplifiers.  
 Size: 360 x 200 x 120 mm. Supply 240V/50Hz AC.

**PRICE £118.00 + £3.00 P&P**

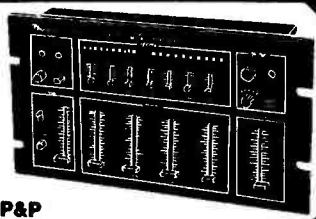

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUDE V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.

# B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572




## Otter Resurfaces

In our April '84 issue News Digest we featured two oscilloscope accessories manufactured by a British company called Otter Electronics. Since then, the company have got into a bit of hot water because another company had registered the same name, so they have now become Waugh Instruments and appear to be on dry land at last.

The re-born company have introduced two new products and have re-launched the two original products in their new livery. One of the new products is another oscilloscope accessory, a calibrator. Waugh claim that it provides all the facilities

necessary for checking and recalibrating oscilloscopes with bandwidths of up to 150MHz. It has a calibrated amplitude square wave generator for checking input attenuators, a wide range of crystal-controlled timing signals with periods from 10ns to 5s, and a 50Hz and 1kHz sine wave generator for checking trigger circuits and for locking sweep circuits whilst checking amplifiers and supply rails for hum. A square wave rise time of less than 1ns allows vertical amplifier rise times to be checked and a fully interlaced composite video generator with both positive and negative going outputs allows the checking of sync separators used for television measurements. The calibrator costs £484.00 plus VAT

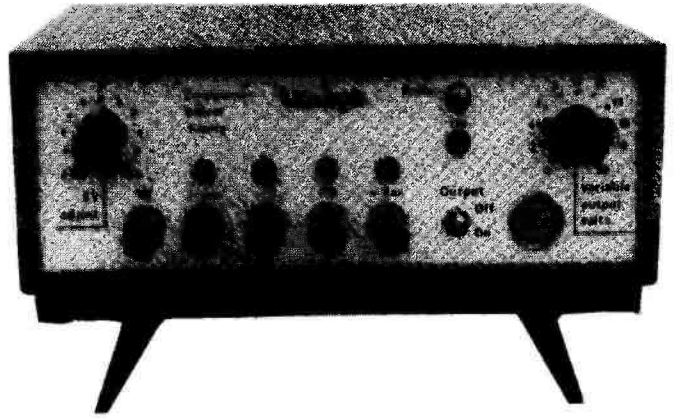


which includes the cost of carriage within the UK.

The other new product is a designer's power supply which offers  $\pm 5V$  rails variable from  $\pm 4.5V$  to  $\pm 5.5V$  and a second pair of supply rails which can be adjusted from 0 to  $\pm 20V$ . The  $\pm 5V$  rails offer up to 500mA with both rails loaded and 700mA with one rail only loaded and the  $\pm 20V$  rails offer up to 200mA with both rails loaded and 250mA with only one rail loaded. Each pair of rails has a single voltage control which affects both rails equally. All of the outputs are protected against overload and shorting to other rails and a LED above each terminal indicates the overload condition. An output switch is provided which connects all of the rails to 0V through suitable bleed resistors when it is put in

the off position. A 5-pin DIN output socket is provided to enable quick connection to test circuits and other frequently used items and the manufacturers claim that the complete unit is small enough to fit under the tilt-stand of most oscilloscopes, thus saving valuable bench space. The designer's power supply costs £144.00 plus VAT which again includes delivery within the UK.

The  $\mu$  amplifier which we described in our April issue now costs £144.00 plus VAT and the isolation amplifier which we also featured costs £157.00 plus VAT. Both prices include delivery within the UK.

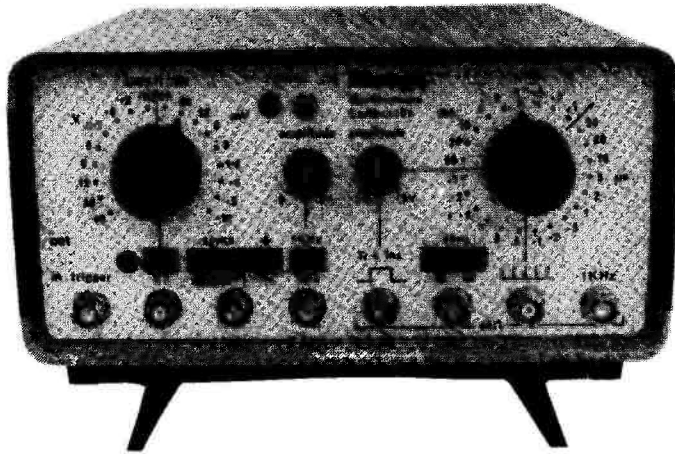Waugh Instruments Ltd, Otter House, Weston Underwood, Olney, Buckinghamshire MK46 5JS, tel 0234-712445.



## The Light That No-One's Seen

Arlen Electronics believe that one of their products is not receiving the attention it deserves. The device is a semiconductor starter for fluorescent lights which is claimed to offer double the tube life obtained with conventional starters, but in spite of this advantage the company have only had moderate success with it so far.

The Pulsestarter has been developed over a period of four years by Arlen and the UK subsidiary of Texas Instruments. Unlike conventional starter switches which apply high voltage pulses and literally kick the tube into fluorescence, the Pulsestarter preheats the tube cathodes and then applies a controlled pulse when the tube is ready. This is much closer to the way in which fluorescent tubes are intended to be used and is similar to the system employed in industrial starterless units. The result is greatly reduced cathode wear since the conventional

system strips emissive material from the cathodes every time the tube is started up. The Pulsestarter is also said to automatically compensate for adverse conditions and will allow a longer period of preheating in cold weather. When the tube reaches the end of its life, the device disconnects the circuits until the tube has been replaced, preventing the repeated attempts at starting which are such an annoying feature of conventional starters and removing the associated risk of control equipment damage and even fire.

In spite of all these advantages,

the Pulsestarter has not taken the lighting industry by storm and Arlen believe that vested interests are doing their best to prevent it being more widely used. Tube manufacturers are obviously not going to be keen on a device which makes their products last longer and thus reduces sales of replacements, and companies with maintenance contracts are also likely to be a little put out at the prospect of fewer repairs.


For details contact Arlen's distributors, C.J. Skilton Ltd, Great Gibcracks Chase, Butts Green, Sandon, Chelmsford CM2 7TR, tel 0245-400535.

## List Watch

Casio have come up with a handy little unit which allows users to keep the names and telephone numbers they need to refer to literally at arms length. The Data Bank 500 behaves like any other digital watch but can store up to fifty sets of six letters and twelve numbers and display any of them on demand. Information is fed in and later recalled

using a couple of buttons, and Casio suggest that in addition to telephone numbers the watch can be used to store bank account codes, birthdays and anniversaries, postal codes, travel schedules and a whole range of other information. It should be available through Casio's normal retail distributors and the recommended selling price is £41.95.

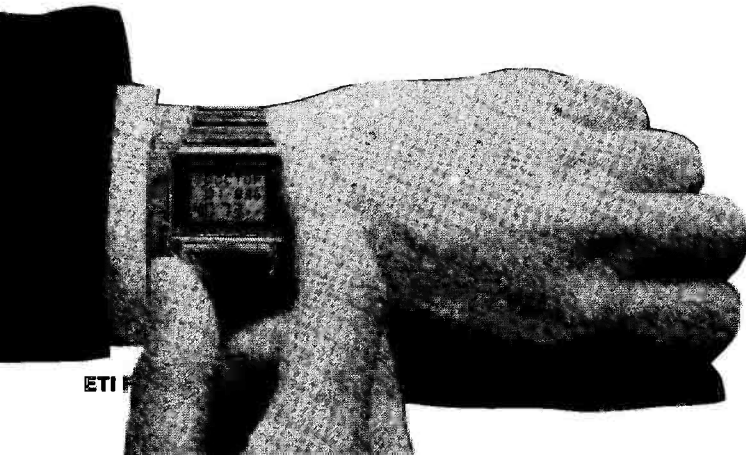Casio Electronics Company Ltd, Unit 6, 1000 North Circular Road, London NW2, tel 01-450 9131.



# COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

## HARD DISK DRIVES

Fully refurbished **DIABLO/DRE** series 30 2.5 Mb disk drives. **DEC RK05, NOVA, TEXAS** compatible.  
Front load. Free stand or rack mount £398.00  
Exchangeable type (via lid removal) £293.00  
me 3022 PSU unit for 2 drives £173.00  
**DIABLO/DRE 44-4000A/B 5+5 ex stock from £995.00**  
1000's of spares for S30, 4000, 3200, HAWK ex stock.  
Plus in house repair, refurbishing service.  
Call for details or quotation.

## EX STOCK INTEGRATED CIRCUITS OVER 100,000 ITEMS INCLUDING:

Intel D8085AH-2 £25.00 D8271 £65.00  
D8202 D8257-5 8255 D3002  
2732 EPROM SPECIAL fully guaranteed  
450ns £3.75, 350ns £4.00, 300ns £4.50

## HOT LINE DATA BASE

# DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base.  
1000's of stock items and one off bargains.  
ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit word, no parity.  
**01-679 1888**

## COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU. Mains filtering, and twin fan cooling. Originally made for the famous **DEC PDP8** computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on All front panel, rear cable entries, etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 18" deep 10.5" high. Useable area 19" x 10.5" x 11.5". With FANS etc. Internal dim. 19" w. 18" d. 10.5" h. £19.95. Carriage & insurance £9.50.

## COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.  
**ETRI 80XU01** Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. £9.95  
**GOULD JB-SAR** Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. NEW £6.95  
**BUHLER 69.11.22.** 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. OUR PRICE ONLY £12.95 complete with data.  
**MUFFIN-CENTRAU** standard 4" x 4" x 1.25" fan supplied tested & EQUIPMENT 240v at £6.25 or 110v at £4.95 or BRAND NEW 240v at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans £1.60

SAVE £250  
**SUPER PRINTER SCOOP**  
BRAND NEW CENTRONICS 739-2



The "Do Everything Printer" at a price that will NEVER be repeated. Standard CENTRONICS parallel interface for direct connection to BBC, ORIC, DRAGON etc. Superb print quality with full pin addressable graphics and 4 type fonts plus HIGH DEFINITION internal PROPORTIONAL SPACED MODE for WORD PROCESSOR applications. 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available ONLY from DISPLAY ELECTRONICS at the ridiculous price of **ONLY £199.00 + VAT** Complete with full manual etc. Limited quantity - Hurry while stocks last.  
Options: Interface cable (specify) for BBC, ORIC, DRAGON or CENTRONICS 38 way pig £12.50. Spare ribbon £3.50 each BBC graphics screen dump utility program £8.60. Carriage and Ins £10.00 + VAT

ONLY £199

## BUDGET RANGE VIDEO MONITORS

At a price YOU can afford, our range of EX EQUIPMENT video monitors defy competition!! All are for 240v working with standard composite video input. Units are pre tested and set for up to 80 col use on BBC micro. Even where MINOR screen burns MAY exist - normal data displays are unaffected.  
**1000's SOLD TO DATE**  
9" HITACHI very compact fully cased, dim. 21cm H x 21cm W x 22cm D. Black and white screen £44.95  
12" KGM 320-321, high bandwidth input, will display up to 132 columns x 25 lines. Housed in attractive fully enclosed brushed alloy case. B/W only £32.95 GREEN screen £39.95  
24" KGM large screen black & white case monitor fully enclosed in light alloy case. Ideal schools, shops, clubs etc. **ONLY £55.00**  
14" BRAND NEW Novex COLOUR type NC1414-CL. Many exacting features such as RGB TTL and composite video input, GREEN TEXT key, internal speaker and audio amp. Even finished in BBC micro matching colours. Fully guaranteed. **ONLY £199.00**  
Carriage and Ins on ALL videos £10.00

## DUAL 5" DISK DRIVES

Current, quality, professional product of a major computer company, comprising 2 x 40 track MPI or Shugart FULLY BBC COMPATIBLE single sided drives in a compact, attractively styled, grey ABS structured case with internal switched mode PSU. The PSU was intended to drive both drives and an intelligent Z80 controller with over 70 ic's. The controller has been removed leaving ample space and current on the +, -, +12 and -12 supply for all your future expansion requirements. Supplied tested with 90 day guarantee in BRAND NEW condition with cable for BBC micro. Ex Stock at only £259.00 + £10.00 carr. Limited Quantity Only

## SPECIAL 300 BAUD MODEM OFFER

Another GIGANTIC purchase of these EX BRITISH TELECOM, BRAND NEW or little used 2B data modems allows US to make the FINAL REDUCTION, and for YOU to join the exciting world of data communications at an UNHEARD OF PRICE OF ONLY £29.95. Made to the highest POST OFFICE APPROVED spec at a cost of hundreds of pounds each, the 2B has all the standard requirements for data base, business or hobby communications. All this and more!!  
● 300 baud full duplex  
● Full remote control  
● CCITT tone standards  
● Supplied with full data  
● Modular construction  
● Direct isolated connection  
● CALL, ANSWER and AUTO modes  
● Standard RS232 serial interface  
● Built in test switching  
● 240v Mains operation  
● 1 year full guarantee  
● Just 2 wires to comms. line

Order now - while stocks last. Carriage and Ins. £10.00

## GE TERMIPRINTER

A massive purchase of these desk top printer-terminals enables us to offer you these quality 30 cps printers at a SUPER LOW PRICE against their original cost of over £1000. Unit comprises of full QWERTY, electronic keyboard and printer mechanism with print face similar to correspondence quality typewriter. Variable forms tractor unit enables full width - up to 13.5" 120 column paper, upper - lower case, standard RS232 serial interface, internal vertical and horizontal tab settings, standard ribbon adjustable baud rates, quiet operation plus many other features. Supplied complete with manual. Guaranteed working £139.00 or untested £85.00, optional floor stand £12.50 Carr & Ins £10.00.

## 8" 19MB WINCHESTER DISK DRIVE

Made in the UK by a subsidiary of the World's largest disk drive manufacturer. This BRAND NEW "end of line" unit offers an outstanding opportunity to add a MASSIVE 19 mb of storage to your computer system. Superbly constructed on a heavy die cast chassis the DRE 3100 utilises 3 x 8" platters in a dust free cavity. All drive functions are controlled by microprocessor electronics using an INTEL 8035 cpu and TTL support logic. Data to the outside world is via two comprehensive 8 bit TTL level bi directional data buses with full status reporting for ease of interfacing. Many features such as Av. seek time 35 ms, 512 bytes per sector, +24, -24 and +5 v DC supply, plug in card system, and compact size of approx. 19cm H x 21cm W and 42cm D etc, etc, make this item a real snip.  
Units are BRAND NEW and BOXED and sold at a FRACTION of original cost - hence unguaranteed. Complete with 150 page manual, circuits and applications guide.

## DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.  
**MODEM 20-1** Compact unit for use with MICRONET, PRESTEL or TELECOM GOLD etc. 2 wire direct connect 75 baud transmit 1200 baud receive. Data i/o via RS232 'D' socket. Guaranteed working with data £99.95  
**MODEM 20-2** same as 20-1 but 75 baud receive 1200 baud transmit £130.00  
**TRANSDATA 307A** 300 baud acoustic coupler RS232 i/o £95.00 brand new. £4.50  
**NEW DBL2123** Multi Standard modem selectable V21 300-300 bps, V23 75-1200, V23 1200-75 full duplex. Or 1200-1200 half duplex modes. Full auto answer via modem or CPU. LED status indicators. CALL or ANSWER modes Switchable CCITT or BELL 103 & 202. Housed in ABS case size only 2.5" x 8.5" x 9". £286.00 + VAT  
For further data or details on other EX STOCK modems contact sales office.  
Carriage on all modems £10.00 + VAT.

ONLY £225.00 Carriage £10.00  
Suitable power supply unit - sold ONLY with drive £39.95.

## PROFESSIONAL KEYBOARD OFFER

An advantageous purchase of brand new surplus allows a great QWERTY, full travel, chassis keyboard offer at fractions of their original costs.  
**ALPHAMERIC 7204/60** full ASCII 60 key, upper, lower + control key, parallel TTL output plus strobe. Dim 12" x 6" x 5.5" - 12 DC £39.50  
**DEC LA34** Unencoded keyboard with 67 quality, GOLD, normally open switches on standard X, Y matrix. Complete with 3 LED indicators & i/o cable - ideal micro conversions etc. pcb DIM 15" x 4.5" £24.95 Carriage on keyboards £3.00

# 66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.s, Transistors, Relays, Caps, P.C.B.s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.  
2.5kls £4.25 + pp £1.25      5kls £5.90 + £1.80  
10kls £10.25 + pp £2.25      20kls £17.50 + £4.75

## SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s, triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed.  
50+ £2.95 100+ £3.15  
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. 100+ £6.90 200+ £12.30 300+ £19.50

## EX STOCK DEC CORNER

**BA11-MB** 3.5" Box, PSU, LTC £385.00  
**DH11-AD** 16 x RS232 DMA interface £2100.00  
**DLV11-J** 4 x EIA interface £310.00  
**DUP11** Sych. Serial data i/o £650.00  
**DZ11-B** 8 line RS232 mux board £650.00  
**LA36** Decoder EIA or 20 ma loop £270.00  
**LAXX-NW** LA180 RS232 serial interface and buffer option £130.00  
**LAX34-AL** LA34 tractor feed £85.00  
**MS11-JP** Unibus 32 kb Ram £80.00  
**MS11-LB** Unibus 128 kb Ram £450.00  
**MS11-LD** Unibus 256 kb Ram £850.00  
**MSC480A** Qbus (Equip MSV11-L) 256 kb £499.00  
**PDP11/05** Cpu, Ram, i/o, etc. £450.00  
**PDP11/40** Cpu, 124k MMU £1850.00  
**RT11** ver. 3B documentation kit £70.00  
**RK05-J** 2.5 Mb disk drives £650.00  
**KLBJA** PDP 8 asynch i/o £175.00  
**M18E** PDP 8 Bootstrap option £75.00  
**VT50** VDU and Keyboard - current loop £175.00


1000's of EX STOCK spares for DEC PDP8, PDP8A, PDP11 systems & peripherals. Call for details. All types of Computer equipment and spares wanted for PROMPT CASH PAYMENT.
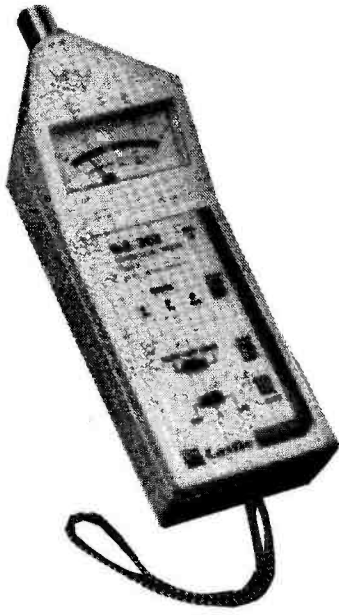
## ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00. + VAT Warehouse open Mon-Fri 9.30 - 5.30 Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

32 Biggin Way, Upper Norwood, London SE19 3XF  
Telephone 01-679 4414 Telex 27924





## Noise Exposure Meter

The GA202 Noise Exposure Meter from Castle Associates is designed to simplify sound exposure measurements in industrial and other environments and includes a scale reading directly in dBA/time. It conforms to the requirements of BS5969, has a measuring range of 40-140 dB and its features include push-button range selection with LED indication and a hold facility for determining maximum RMS or peak values.

In most countries there are legal limits to the noise level industrial employees may be subjected to. The maximum

allowable exposure is expressed as 100% dose, and for each 3dBA increase in the sound level the working time must be halved. The GA202's dBA/time scale allows both the sound level and the maximum permitted exposure time at that level to be read directly, thus simplifying measurements.

The meter has three ranges with shift register selection and LEDs to indicate which range is in use. Switchable slow, fast and peak response times are provided and a maximum hold button allows peak or maximum RMS values to be captured and read. The meter is linearly scaled and both 'A' and linear weightings are provided.

The instrument is housed in a diecast case which is said to be ergonomically designed and very tough, and the battery compartment is made of moulded plastic to reduce the risk of damage from leakage. The battery compart-

ment cover forms the back of the case and is also made of plastic so that the unit can be used on desktops, etc, without scratching the surface. A wrist-strap and tripod mounting thread are supplied as standard and a complete kit of accessories is available which comprises a companion GA602 calibrator, a windshield and a leather shoulder case which holds the meter and the accessories along with an A5 clipboard.

The GA202 and its accessories are the first products in a complete new range promised by Castle Associates. The meter costs £195.00 plus VAT and the kit of accessories costs £162.00 plus VAT and comes with a free noise survey pad.

Castle Associates, Salter Road, Cayton Low Road Industrial Estate, Scarborough, North Yorkshire YO11 3UZ, tel 0723-584250.

## Exhibitions, Conferences, Etc

As this is the first issue of the new year, it seems appropriate to include a round-up of forthcoming exhibitions, conferences, and other electronics get-togethers.

The 1985 Which Computer? Show will take place at the National Exhibition Centre, Birmingham from the 15th to the 18th of January. The organisers believe it will be the largest ever display of computer hardware, software and peripherals and the 350-plus organisations taking part will be exhibiting many thousands of products including over one hundred new items. The show is aimed at everyone from those buying a first computer through to companies seeking to computerise their operations, and the free visitors information pack includes what is claimed to be a 'jargon-free' check list prepared by the National Computing Centre to help purchasers identify their needs. The show also includes beginners workshops and seminars, and further details and a copy of the free information pack can be obtained from Hugh Keeble, Show Manager, Which Computer? Show, Chatsworth House, 59-61 London Road, Twickenham TW1 3SZ, tel 01-891 5051.

A little more specialist in appeal is Lightshow '85 which will be staged at London's Olympia Exhibition Centre from the 20th

to the 24th of January. The show is organised by the Decorative Lighting Association and is trade only. For details contact the DLA at Bryn House, Bishop's Castle, Shropshire SY9 5LE, tel 0588-4658.

Even more specialist, perhaps, is the Fourth Battery Seminar And Exhibition which will be held at the Royal Crest Hotel, London, on the 29th January. The seminar is organised by ERA Technology and will concentrate on maintenance-free batteries for standby power applications. For details contact Miss T.L. Ecclestone, Seminar Organiser, ERA Technology Ltd, Cleeve Road, Leatherhead, Surrey KT22 7SA, tel 0372-374151.

Something completely different will be going on at the Carleton Community Centre, Pontefract, on the 10th of March from 11.00am to 4.30pm. The Pontefract & District Amateur Radio Society are holding a components fair, and although the event is tied closely to the Mobile Radio Rally it will concentrate on home construction and do-it-yourself. A number of traders are expected to attend and only components, surplus equipment and instruments, etc, will be on sale; there will be no new equipment. For details contact N. Whittingham, G4ISU, 7 Ridgedale Mount, Pontefract WF8 1SB, tel 0977-792784.

The Electronic Production Efficiency Exposition '85 will be held at the National Exhibition Centre, Birmingham, from the 30th of April to the 2nd of May. The event is a combined exhibition and conference which is concerned with the factory of the future. Beyond that, we know nothing about it, so if you want to

know more you'll have to contact the organisers, Network Events Ltd, Printers Mews, Market Hill, Buckingham MK18 1JX, tel 0280-815226.

Power '85 is a new exhibition organised by the Power Supply Manufacturers Association and will take place at the Metropole Hotel, Brighton, from the 21st to the 23rd of May. There will be about 140 stands at the exhibition and the products on display will cover both power supplies and alternative sources such as batteries and solar cells. The PMSA are currently evaluating papers for presentation and welcome further submissions from engineers who feel they have constructive comments to make about power supply technology and the application of power supplies in commercial and industrial equipment. Contact M.A. Poflawka, The Power Supply Manufacturers Association, 7-8 Saville Row, London W1X 1AF, tel 01-437 4127.

Gone are the days when telephones all looked the same and were only available from the GPO. Responding to this change, Network Events are organising Phone '85, an exhibition devoted solely to the users of telephone equipment and covering the range from single telephones to large, multi-user systems for international corporations. The event will take place at the Kensington Exhibition Centre, London, and will open to the trade only on June 4th and to the general public on June 5th and 6th. For details, contact Network Events at the address given above for the Electronic Production Efficiency Exposition.

The same people are also organising another event in the

same place and at the same time. Competa '85 is described as a conference and exhibition for all users of computers and peripherals and that's all we know, so for further details get in touch with Network Events.


The Leeds Electronics Show will be held at The University of Leeds from the 3rd to the 5th of July. The show is in its 22nd year and hopes to have 223 stands on display. Details are available from Evan Steadman Services Ltd, The Hub, Emson Close, Saffron Walden, Essex CB10 1HL, tel 0799-266699.

Interconnection Europe '85 is a conference and exhibition concerned with interconnection technology, products and applications and will take place from the 10th to the 12th of September at the Cumberland Hotel, Marble Arch, London. It is claimed to be the only European event dedicated to interconnection technology and the new venue has been chosen to allow for an anticipated expansion of 80% compared with last year's show. Over 100 stands will be on display and a number of papers will be delivered by manufacturers, distributors and end-users. For details contact Ms Teresa Arrowsmith, Conference Secretary, Benn Electronics Publications Ltd, P.O. Box 28, Luton, Bedfordshire LU2 0ED, tel 0582-417438.

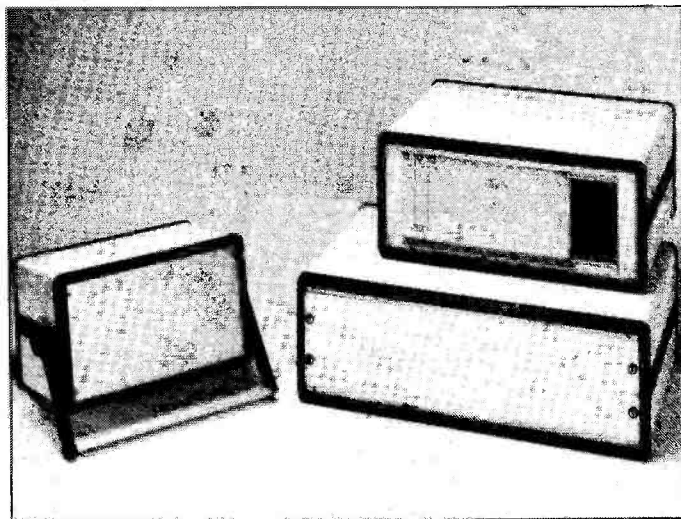Finally, the International Test And Measurement Exhibition and conference (ITAME) will be held at Olympia 2, London from the 27th to the 29th of November. The event covers all areas of electronic test and measurement and is organised by Network Events, whose address appears above.







## Versatile Cases

New from West Hyde Developments is a range of instrument cases which are said to have been designed for maximum versatility. Made from ABS and aluminium, the cases can be used with plug-in cards, in 19" racks or with a plain front panel and the accessories available include prop-up handles and chassis plates.

The Botron cases come in ten sizes which range from 264 to 414mm wide, 249 to 508mm deep and are either 178 or 202mm high. The front and back

bezels are moulded from brown ABS and are connected together by aluminium rails in each corner. The top and bottom panels are moulded in cream polystyrene and have a textured finish. Standard 19" front panels may be fitted using a special adaptor kit and a purpose-designed card frame based on the Critchley Europak system is also available. The prop-up handles and chassis plates are part of a range of accessories for the cases and all items are available ex-stock.

The Botron cases range in price from £34.21 to £48.08 plus VAT. West Hyde Developments Ltd, 9-10 Park Street Industrial Estate, Aylesbury, Buckinghamshire HP20 1ET, tel 0296-20441.

## Miniature Vacuum Cleaner

The minivac is a portable, battery operated vacuum cleaner which is designed for cleaning the interiors of sensitive electronic, photographic and other equipment. Unlike the compressed air blowers which are often used for this purpose and which simply blow minute particles into the air or into other parts of the equipment, the Minivac collects the particles in a small cloth bag for later disposal.

The Minivac operates from a 9V

battery or from the mains using an adaptor. It has two lens-quality fine brush vacuum heads and is claimed to be very powerful in spite of its small weight and size. The cloth collection bag has a velcro flap to allow quick and easy disposal of accumulated debris and a separate attachment is available to turn the device into a blower.

The Minivac is expected to be used in industry and the home for cleaning photographic equipment, typewriters, computers, audio and video cassette recorders, precision models and much more. It costs £19.60 plus VAT and is available from O & S Photographic, South Block, The Maltings, Sawbridgeworth, Hertfordshire, tel 0279-722208.




## Accurate NTC Thermistor

Siemens have introduced a negative temperature coefficient thermistor which operates over the temperature range of  $-40^{\circ}$  to  $+100^{\circ}\text{C}$  and has an accuracy of better than  $0.1^{\circ}\text{C}$  over the body temperature range of  $30^{\circ}$  to  $50^{\circ}\text{C}$ .

The M841 thermistor has silver plated 20mm long leads and is available in 3k or 5k versions. Other versions with resistances of up to 100k will shortly be available. The accuracy of the device corresponds to a resistance tolerance of  $\pm 0.4\%$ , and suggested applications include high resolution electronic thermometers, heating/air conditioning controllers for use in cars and warning sensors to alert drivers to critical outside temperatures.

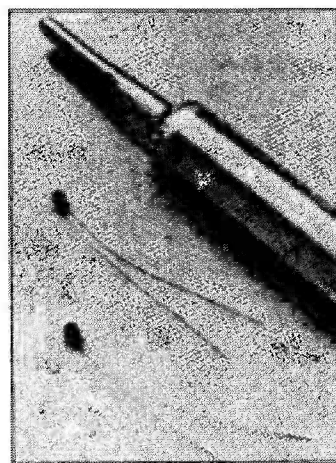Siemens have also announced an extended temperature range version, the M861. This offers an accuracy of  $\pm 0.1^{\circ}\text{C}$  over the entire temperature range from



$-40^{\circ}$  to  $+120^{\circ}\text{C}$ . It is epoxy coated and has 25mm long, 0.25mm thick nickel leads with Teflon insulation. The rated resistance is 30k but both lower and higher values will be available later.

Siemens Ltd, Siemens House, Windmill Road, Sunbury-on-Thames, Middlesex TW16 7HS, tel 09327-85691.

● The new Cricklewood catalogue covers eight sides of A4 and lists semi-conductors, resistors, capacitors, switches, connectors, hardware, tools and even valves. They will accept credit card orders over the telephone as well as supplying goods to mail order and their North London shop is open all week. Copies of the catalogue are available from Cricklewood Electronics Ltd, 40 Cricklewood Broadway, London NW2 3ET, tel 01-450 0995.

● The British Amateur Electronics Club have just sent us a copy of their October Newsletter — and it's now early December. Still, they do apologise for this lateness and it does contain articles on logic gates, display driver circuitry and phase control. If you want to know more contact Mr. C. Bogod, "Dickens", 26 Forest Road, Penarth, South Glamorgan, tel 0222-707813.

● Cambridge Systems Technology have produced an IEEE488 interface for the Sinclair QL

microcomputer. The Q-488 fits the expansion slot on the QL and allows it to communicate at up to 70k bytes/second with up to sixteen IEEE488-compatible test instruments, printers, plotters, disc drives, etc. Contact Cambridge Systems Technology, 30 Regent Street, Cambridge CB2 1OB, tel 0223-323302.

● Chartwell-Bratt are publishing a series of computer textbooks which each deal with a particular topic and will sell for around £4.00. The books have been written by and in conjunction with university lecturers in computer studies from around the country, and are intended to improve the situation for students who frequently have to buy expensive books which only contain a few passages of interest to them. The first seven titles should already be available and further titles will be issued at a rate of about three a month. Chartwell-Bratt Ltd, Old Orchard, Bickley Road, Bickley, Bromley, Kent BR1 2NE, tel 01-467 1956.

### BBC Micro Computer System

#### ACORN COMPUTER SYSTEMS

BBC Model B Special offer.....£320 (a) BBC  
Model B+Econet.....£388 (a)  
BBC Model B+DFS.....£409 (a)  
BBC Model B+DFS +Econet.....£480 (a)

#### UPGRADE KITS

A to B Upgrade Kit.....£75 (c)  
DFS Kit.....£95 (c)  
Econet Kit.....£45 (c)  
Speech Kit.....£47 (c)

#### ACORN ADD-ON PRODUCTS

Z80 2nd Processor.....£352 (a)  
6502 2nd Processor.....£175 (b)  
Telex Adaptor.....£190 (b)  
IEEE Interface £282.....£282 (b)  
Prestel Adaptor.....£99 (b)

RH Light pen.....£39.50 (c)

#### BBC FIRMWARE

1.2 Operating System.....£7.50 (d)  
Basic II ROM.....£22.50 (d)  
View Word Processor ROM.....£48.00 (c)  
Wordwise Word Processor ROM.....£34.00 (d)

BCPL ROM/Disc.....£86.00 (b)  
Disc Doctor/Gremlin Debug ROM £28 (d)  
EXMON/TOOL KIT ROM.....£28 ea (d)  
Printmaster (FX80)/Graphics ROM.....£28 ea (d)  
ULTRACALC spreadsheet ROM £89 ea (c)

#### COMMUNICATION ROM

Termi Emulator.....£28 (d)  
Communicator.....£59 (d)  
Commstar.....£229 (d)

TORCH UNICON products including the IBM Compatible GRADUATE in stock  
For detailed specification on any of the BBC Firmware/Peripherals listed here  
or information on our complete range please write to us.

### PRINTERS

**EPSON**  
RX80FT £225 (a) FX80 £315 (a) FX 100 £435 (a)  
**KAGA TAXAN**  
KP 810 (80col) £255 (a) KP910 £369 (a)  
**JUKI 6100 £340 (a) BROTHER HR15 £340 (a)**

### ACCESSORIES

#### EPSON

Serial Interface: 8143 £28 (c); 8148 with 2K £57 (c)  
Paper Roll Holder £17 (d); FX80 Tractor Attachment £37 (c)  
Ribbons: FX/RX/MX80 £5 (d) FX/RX/MX100 £10 (d)  
RX/FX80 Dust Cover £4.50 (d)

#### KAGA TAXAN

RS232 with 2K Buffer £85 (c) KP810/910 Ribbon £6.00 (d)

#### JUKI 6100

RS232 with 2K Buffer £65 (c) Ribbon £2.50 (d)  
Tractor Attachment £99 (a) Sheet Feeder £199 (a)  
BBC Parallel Lead £7 (d) Serial Lead £7 (d)  
2000 Sheets Fanfold Paper with extra fine perforation.  
9.5" x 11" £13 (b) 14.5" x 11" £18 (b)  
Self Adhesive Labels 2 3/4" x 17/16"  
Single Row £5.25/1000 (d) Triple Row £5/1000 (d)

### MODEMS

— All modems listed below are BT approved

#### MIRACLE WS2000:

The ultimate world standard modem covers all common BELL and CCITT standards up to 1200 Baud. Allows communication with virtually any computer system in the world. The optional AUTO DIAL and AUTO ANSWER boards enhance the considerable facilities already provided on the modem. Mains powered £129(b). Auto Dial Board/Auto Answer Board £30(c) each. Software lead £4.80.

#### TELEMOD 2:

Complies with CCITT V233 1200/75 Duplex and 1200/1200 Half Duplex standards that allow communication with VIEWDATA services like PRESTEL, MICRONET etc. as well as user to user communications. Mains powered £84(b).

#### BUZZ BOX:

This pocket sized modem complies with V21 300/300 Baud and provides an ideal solution for communications between users, with main frame computers and bulletin boards at a very economic cost. Battery or mains operated, £52(c). Mains adaptor £8(d).

BBC to Modem data lead £7.

### DISC DRIVES

These are fully cases and wired drives with slim line mechanisms of high quality. Shuggart A400 standard interface. Drives supplied with cables manuals and formatting disc suitable for the BBC computer. TEAC 80 track drives are supplied with 40/80 track switching as standard. All drives can operate in single or dual density format.

1 x 100K 40T SS:TS55A.....£100(b)	2 x 400K 40/80T DS: TD55F TEAC with psu.....£380(a)
1 x 200K 40/80TSS:TS55E.....£140(b)	2 x 400K 40/80TDS:TD55M Mitsubishi with psu.....£360(a)
1 x 400K 40/80TSS:TS55F.....£155(a)	CS55A with psu.....£125(b)
2 x 100K 40T SS:TD55A with psu.....£250(a)	CS55E with psu.....£150(b)
2 x 200K 40/80T SS:TD55E TEAC with psu.....£325(a)	CS55F with psu.....£168(b)

### 3M 5 1/4" FLOPPY DISCS

High quality discs that offer a reliable error free performance for life. Each disc is individually tested and guaranteed for life. Ten discs are supplied in a sturdy cardboard box.

40T SS DD £15 (c) 40T DS DD £18 (c)  
80T SS DD £22 (c) 80T DS DD £24 (c)

### DRIVE ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives.....£14.50 (c)  
Single Disc Cable.....£6 (d) 10 Disc Library Dual Disc Cable.....£8.50 (d)  
Case.....£1.80(c) 30 Disc Case.....£8 (c)  
30/40 Disc Lockable Box.....£14 (c) 70/80 Disc Lockable Box.....£18 (c)

### MONITORS

#### MICROVITEC 14" RGB:

1431 Standard Resolution.....£165 (a)  
1451 Medium Resolution.....£249 (a)  
1441 Hi Resolution.....£399 (a)  
1431 AP Std Res PAL/AUDIO.....£210 (a)  
1451 AP Std Res PAL/AUDIO.....£310 (a)  
1451 DQ3 Med Res for QL.....£239 (a)

Above monitors are now available in plastic or metal cases, please specify your requirement.

**KAGA Super Hi Res Vision III RGB.....£345 (a)**  
**Hi Res Vision II.....£245 (a)**

#### MONOCHROME MONITORS 12":

Kaga Green KX1201 G Hi Res.....£99 (a)  
Kaga Amber KX1201 A Hi Res.....£105 (a)  
Sanyo Green DM812CX Hi Res.....£90 (a)  
Swivel Stand for Kaga Monochrome.....£21 (c)  
All monitors are supplied with leads suitable for the BBC Computer. Spare leads available.

### ATTENTION

All prices in this double page advertisement are subject to change without notice.

ALL PRICES EXCLUDE VAT  
Please add carriage 50p unless indicated as follows:

(a) £8 (b) £2.50 (c) £1.50 (d) £1.00

### SPECIAL OFFER

2764-25.....£4.90  
27128-25.....£18  
27128-30.....£18  
6264-15.....£28  
6262LP-15.....£31  
6264-12.....£35

### GANG OF EIGHT INTELLIGENT FAST EPROM COPIER

Copies up to eight eproms at a time and accepts all single rail eproms up to 27256. Can reduce programming time by 80% by using manufacturer's suggested algorithms. Fixed Vpp of 21 & 25 volts and variable Vpp factory set at 12.5 volts. LCD display with alpha moving message. £395(b).

### SOFTY II

This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface. Softy II.....£195(b)  
Adaptor for 2764/2564. £25.00(c)

### UV ERASERS

All erasers with built in safety switch and mains indicator.  
UV1B erases up to 6 eproms at a time.....£47(c)  
UV1T as above but with a timer.....£59(d)  
UV140 erases up to 14 eproms at a time.£81(b)  
UV141 as above but with a timer.....£79(b)

### I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header	Receptacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

### D CONNECTORS

No of Ways				
	9	15	25	37
<b>MALE:</b>				
Ang.Pins	120	180	230	350
Solder IDC	60	85	125	170
	175	275	325	-
<b>FEMALE:</b>				
St Pin	100	140	210	380
Ang.pins	160	210	275	440
Solder IDC	90	130	195	290
	195	325	375	-
St Hood	90	95	100	120
Screw Lock	130	150	175	-

TEXT TOOL ZIF	
SOCKETS	24-pin £5.75
	28-pin £8.00
	40-pin £9.75

### EDGE CONNECTORS

	0.1"	0.156"
2 x 6-way (commodore)	—	300p
2 x 10-way	150p	—
2 x 12-way (vic 20)	—	350p
2 x 18-way	—	140p
2 x 23-way (ZX81)	175p	220p
2 x 25-way	225p	220p
2 x 28-way (Spectrum)	200p	—
2 x 36-way	250p	—
1 x 43-way	280p	—
2 x 42-way	190p	—
2 x 43-way	395p	—
1 x 77-way	400p	500p
2 x 50-way (S100conn)	600p	—

### EURO CONNECTORS

DIN 41612			
2 x 32 way St Pin	230p	275p	
2 x 32 way Ang Pin	275p	320p	
3 x 32 way St Pin	260p	300p	
3 x 32 way Ang Pin	375p	400p	
IDC Skt A + B	275p		
IDC Skt A + C	350p		

For 2 x 32 way please specify spacing (A + B, A + C).

### AMPHENOL CONNECTORS

36 way plug Centronics (solder) 500p (IDC) 475p  
36 way skt Centronics (solder) 550p (IDC) 500p  
24 way plug IEEE (solder) 475p (IDC) 475p  
24 way skt IEEE (solder) 500p (IDC) 500p  
PCB Mtg Skt Ang Pin  
24 way 700p 36 way 750p

### GENDER CHANGERS 25 way D type

Male to Male.....£10  
Male to Female.....£10  
Female to Female.....£10

### RS 232 JUMPERS

(25 way D)	
24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female Female	£10.00
24" Male Male	£9.50
24" Male Female	£9.50

DIL SWITCHES	
4-way	90p
6-way	105p
8-way	120p
10-way	150p

### TELEPHONE CONNECTORS

4 way plug	110p
6 way plug	180p
6 way rtang.skt	160p
Flexible cable	
4 way	50p/m
6 way	72p/m

### RIBBON CABLE

(grey/metre)			
10-way	40p	34-way	160p
16-way	60p	40-way	180p
20-way	85p	50-way	200p
26-way	120p	64-way	280p

### DIL HEADERS

Solder IDC	
14 pin	40p
16 pin	50p
18 pin	80p
20 pin	75p
24 pin	100p
28 pin	200p
40 pin	200p
	225p

### MISC CONNS

21 pin Scart Connector	200p
8 pin Video Connector	200p



74 SERIES      4000 SERIES      LINEAR ICs      COMPUTER COMPONENTS

7400	30p	74279	90p	74LS283	80p	4000	20p
7401	30p	74280	105p	74LS290	80p	4001	24p
7402	30p	74281	90p	74LS292	90p	4002	25p
7403	30p	74282	90p	74LS293	140p	4003	25p
7404	30p	74283	180p	74LS297	90p	4004	25p
7405	30p	74284	200p	74LS302	90p	4005	25p
7406	40p	74285	200p	74LS303	90p	4006	25p
7407	40p	74286	80p	74LS309	220p	4007	35p
7408	30p	74287	80p	74LS321	370p	4008	45p
7409	30p	74288	100p	74LS323	500p	4009	45p
7410	30p	74289	100p	74LS324/624	370p	4010	60p
7411	30p	74290	112p	74LS348	200p	4011	24p
7412	30p	74291	112p	74LS349	200p	4012	25p
7413	30p	74292	112p	74LS352	120p	4013	35p
7414	50p	74293	100p	74LS353	210p	4014	35p
7415	30p	74294	140p	74LS356	180p	4015	70p
7416	36p	74295	100p	74LS357	210p	4016	35p
7417	40p	74296	100p	74LS361	100p	4017	55p
7418	40p	74297	100p	74LS362	180p	4018	60p
7419	40p	74298	100p	74LS365	50p	4019	80p
7420	80p	74299	100p	74LS366	50p	4020	80p
7421	80p	74300	100p	74LS367	50p	4021	80p
7422	36p	74301	100p	74LS368A	50p	4022	70p
7423	36p	74302	100p	74LS370	90p	4023	30p
7424	36p	74303	100p	74LS373	90p	4024	45p
7425	40p	74304	100p	74LS375	75p	4025	24p
7426	40p	74305	100p	74LS377	40p	4026	24p
7427	40p	74306	100p	74LS378	40p	4027	40p
7428	43p	74307	100p	74LS379	140p	4028	60p
7429	43p	74308	100p	74LS381	450p	4029	75p
7430	30p	74309	100p	74LS390	80p	4030	35p
7431	30p	74310	100p	74LS393	110p	4031	1125p
7432	30p	74311	100p	74LS394	100p	4032	1125p
7433	30p	74312	100p	74LS399	140p	4033	1125p
7434	30p	74313	100p	74LS400	100p	4034	250p
7435	30p	74314	100p	74LS401	100p	4035	270p
7436	30p	74315	100p	74LS402	100p	4036	270p
7437	30p	74316	100p	74LS403	100p	4037	110p
7438	30p	74317	100p	74LS404	100p	4038	110p
7439	30p	74318	100p	74LS405	100p	4039	250p
7440	40p	74319	100p	74LS406	100p	4040	60p
7441	90p	74320	100p	74LS407	100p	4041	55p
7442	90p	74321	100p	74LS408	100p	4042	55p
7443	90p	74322	100p	74LS409	100p	4043	55p
7444	110p	74323	100p	74LS410	100p	4044	80p
7445	100p	74324	100p	74LS411	100p	4045	100p
7446	100p	74325	100p	74LS412	100p	4046	100p
7447	100p	74326	100p	74LS413	100p	4047	100p
7448	120p	74327	100p	74LS414	100p	4048	55p
7449	120p	74328	100p	74LS415	100p	4049	36p
7450	120p	74329	100p	74LS416	100p	4050	36p
7451	35p	74330	100p	74LS417	100p	4051	85p
7452	35p	74331	100p	74LS418	100p	4052	60p
7453	35p	74332	100p	74LS419	100p	4053	60p
7454	36p	74333	100p	74LS420	100p	4054	80p
7455	47p	74334	100p	74LS421	100p	4055	80p
7456	50p	74335	100p	74LS422	100p	4056	85p
7457	50p	74336	100p	74LS423	100p	4057	85p
7458	50p	74337	100p	74LS424	100p	4058	85p
7459	50p	74338	100p	74LS425	100p	4059	85p
7460	50p	74339	100p	74LS426	100p	4060	85p
7461	50p	74340	100p	74LS427	100p	4061	85p
7462	50p	74341	100p	74LS428	100p	4062	85p
7463	50p	74342	100p	74LS429	100p	4063	85p
7464	50p	74343	100p	74LS430	100p	4064	85p
7465	50p	74344	100p	74LS431	100p	4065	85p
7466	50p	74345	100p	74LS432	100p	4066	85p
7467	50p	74346	100p	74LS433	100p	4067	85p
7468	50p	74347	100p	74LS434	100p	4068	85p
7469	50p	74348	100p	74LS435	100p	4069	85p
7470	50p	74349	100p	74LS436	100p	4070	24p
7471	50p	74350	100p	74LS437	100p	4071	24p
7472	50p	74351	100p	74LS438	100p	4072	24p
7473	50p	74352	100p	74LS439	100p	4073	24p
7474	50p	74353	100p	74LS440	100p	4074	24p
7475	50p	74354	100p	74LS441	100p	4075	24p
7476	50p	74355	100p	74LS442	100p	4076	24p
7477	50p	74356	100p	74LS443	100p	4077	24p
7478	50p	74357	100p	74LS444	100p	4078	24p
7479	50p	74358	100p	74LS445	100p	4079	24p
7480	50p	74359	100p	74LS446	100p	4080	24p
7481	50p	74360	100p	74LS447	100p	4081	24p
7482	50p	74361	100p	74LS448	100p	4082	24p
7483	50p	74362	100p	74LS449	100p	4083	24p
7484	50p	74363	100p	74LS450	100p	4084	24p
7485	112p	74364	100p	74LS451	100p	4085	24p
7486	112p	74365	100p	74LS452	100p	4086	24p
7487	112p	74366	100p	74LS453	100p	4087	24p
7488	112p	74367	100p	74LS454	100p	4088	24p
7489	112p	74368	100p	74LS455	100p	4089	24p
7490	112p	74369	100p	74LS456	100p	4090	24p
7491	112p	74370	100p	74LS457	100p	4091	24p
7492	112p	74371	100p	74LS458	100p	4092	24p
7493	112p	74372	100p	74LS459	100p	4093	24p
7494	112p	74373	100p	74LS460	100p	4094	24p
7495	112p	74374	100p	74LS461	100p	4095	24p
7496	112p	74375	100p	74LS462	100p	4096	24p
7497	210p	74376	100p	74LS463	100p	4097	270p
7498	210p	74377	100p	74LS464	100p	4098	270p
7499	210p	74378	100p	74LS465	100p	4099	270p
7500	210p	74379	100p	74LS466	100p	4100	270p

AD7511	115p	LM711	100p	78A01	90p
AD7512	115p	LM712	100p	78A02	90p
AD7513	115p	LM713	100p	78A03	90p
AD7514	115p	LM714	100p	78A04	90p
AD7515	115p	LM715	100p	78A05	90p
AD7516	115p	LM716	100p	78A06	90p
AD7517	115p	LM717	100p	78A07	90p
AD7518	115p	LM718	100p	78A08	90p
AD7519	115p	LM719	100p	78A09	90p
AD7520	115p	LM720	100p	78A10	90p
AD7521	115p	LM721	100p	78A11	90p
AD7522	115p	LM722	100p	78A12	90p
AD7523	115p	LM723	100p	78A13	90p
AD7524	115p	LM724	100p	78A14	90p
AD7525	115p	LM725	100p	78A15	90p
AD7526	115p	LM726	100p	78A16	90p
AD7527	115p	LM727	100p	78A17	90p
AD7528	115p	LM728	100p	78A18	90p
AD7529	115p	LM729	100p	78A19	90p
AD7530	115p	LM730	100p	78A20	90p
AD7531	115p	LM731	100p	78A21	90p
AD7532	115p	LM732	100p	78A22	90p
AD7533	115p	LM733	100p	78A23	90p
AD7534	115p	LM734	100p	78A24	90p
AD7535	115p	LM735	100p	78A25	90p
AD7536	115p	LM736	100p	78A26	90p
AD7537	115p	LM737	100p	78A27	90p
AD7538	115p	LM738	100p	78A28	90p
AD7539	115p	LM739	100p	78A29	90p
AD7540	115p	LM740	100p	78A30	90p
AD7541	115p	LM741	100p	78A31	90p
AD7542	115p	LM742	100p	78A32	90p
AD7543	115p	LM743	100p	78A33	90p
AD7544	115p	LM744	100p	78A34	90p
AD7545	115p	LM745	100p	78A35	90p
AD7546	115p	LM746	100p	78A36	90p
AD7547	115p	LM747	100p	78A37	90p
AD7548	115p	LM748	100p	78A38	90p
AD7549	115p	LM749	100p	78A39	90p
AD7550	115p	LM750	100p	78A40	90p
AD7551	115p	LM751	100p	78A41	90p
AD7552	115p	LM752	100p	78A42	90p
AD7553	115p	LM753	100p	78A43	90p
AD7554	115p	LM754	100p	78A44	90p
AD7555	115p	LM755	100p	78A45	90p
AD7556	115p	LM756	100p	78A46	90p
AD7557	115p	LM757	100p	78A47	90p
AD7558	115p	LM758	100p	78A48	90p
AD7559	115p	LM759	100p	78A49	90p
AD7560	115p	LM760	100p	78A50	90p
AD7561	115p	LM761	100p	78A51	90p
AD7562	115p	LM762	100p	78A52	90p
AD7563	115p	LM763	100p	78A53	90p
AD7564	115p	LM764	100p	78A54	90p
AD7565	115p	LM765	100p	78A55	90p
AD7566	115p	LM766	100p	78A56	90p
AD7567	115p	LM767	100p	78A57	90p
AD7568	115p	LM768	100p	78A58	90p
AD7569	115p	LM769	100p	78A59	90p
AD7570	115p	LM770	100p	78A60	90p
AD7571	115p	LM771	100p	78A61	90p
AD7572	115p	LM772	100p	78A62	90p
AD7573	115p	LM773	100p	78A63	90p
AD7574	115p	LM774	100p	78A64	90p
AD7575					

# DESIGNING MEMORY

Just what is involved in obtaining a working design? Phil Walker uses the example of the 64K DRAM card and the DRAM fix (ETI Dec '84 and Jan '85 respectively) as an example to show how it's done.

The design of electronic projects can, like most human undertakings, be long or short term, easy or difficult, with all shades of grey in between. In both the hobby world and professional life, it is unusual to go straight from original concept to final hardware with no deviations or modifications along the way. So in the long winter evenings as you sit by the fire working out the details of your next piece of electronic wizardry, don't be in too much of a hurry to commit pen to cheque-book or solder to iron.

The first step is to design what you want: write it down in as much detail as possible. Now try to come up with as many different ways of getting there as possible. Choose two or three of these to consider in detail, and examine their good and bad points.

At this stage you will need information on the various devices and components you may want to use. The catalogues of the larger distributors can be very helpful, but obviously, they do not have the detail that you will find in manufacturers' data books. (One point though, those readers who have access to RS Components will probably already have found that they do produce some very useful data sheets for the semiconductors they distribute.)

When you have all the information, choose a design approach that satisfies your requirements easily, in other words, an approach which does not require you to operate close to the limits of the devices. In particular, be careful that power dissipation, gain and bandwidth at the lower end of the specified (on the device data) range will not lead to trouble in analogue circuits; on digital circuits, look out for propagation delays and over-critical timing, at either the fast or slow limits (or a combination of both).


After this, you should be in a position to draw circuit diagrams and even outline physical dimensions to your project if they are important. Make sure that, at least on paper, your design will do what you want every time and has no hidden modes of operation, especially at power-on and power-off. Examine what you have and check that it is what you want. Look back to your original requirements and see if it fulfils them (it probably won't).

Now is the time to build something. If it is a large project, then it is wise to build the essential part or parts of the circuitry and test them on some sort of breadboard system. Make sure that these bits do what your theory predicts. If not, **find out why!** If you don't do this you will have really wasted your time. You will learn more from understanding why things don't work (first time) than from a series of first-time successes. Naturally it is very frustrating to have your brain-child fail miserably at the first hurdle, but with perseverance your success rate will

improve or the complexity of project will increase. With any luck both will occur.

Having chased all the gremlins out of the wirework so far it is time to take the plunge and make the whole thing. Two things are likely to trip you up now, apart from the sillies such as wrong wiring or PCB error. The first is that your original idea had a flaw which has been overlooked or was not apparent until the whole thing came together. The second is that some external equipment or system does not interact with it as planned. In either case some careful thought will be needed to find the appropriate action. This part is often the most frustrating and expensive and leads to red faces, lost tempers and much burning of midnight oil in industry.

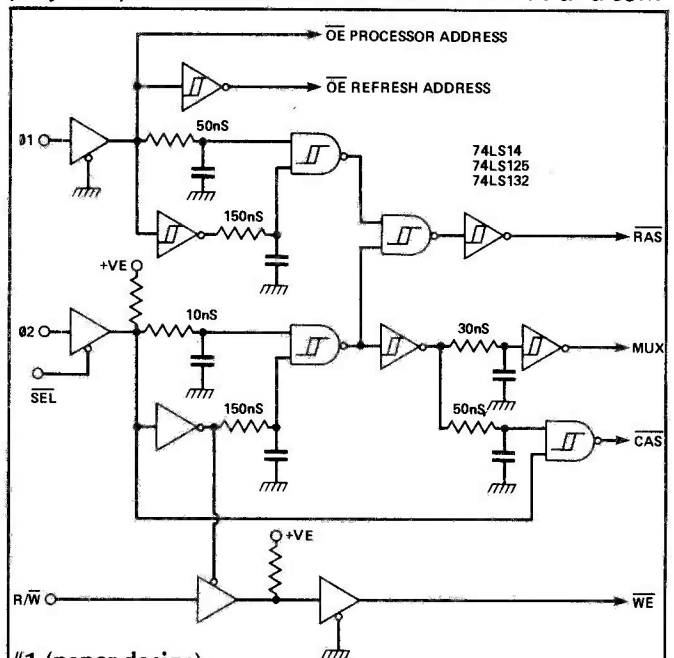A good designer is one who by experience, imagination or both can avoid most of the likely problems in a project by the most suitable choice of method and com-



#1 (paper design)

For: Timing derived from processor clocks.  
All timing periods controllable.  
Only three active packages.

Against: Timing affected by temperature.  
Timing for RAS determined by differences between networks.  
Too many passive components.  
Long time delay  $\phi_1$  and  $\phi_2$  to RAS.  
Address buffer controls too near RAS timing.  
Uses  $\phi_1$  and  $\phi_2$  signals.



ponents. Often he or she will use well-tried circuit elements and configurations as building blocks for the new design. New concepts or components will be tested both in theory and practice before being relied upon. In this way it is made likely that problems arising at the prototype stage will be trivial for the most part (wiring error, etc.) or relatively easy to isolate. The unfortunate thing is that most designers operate under a "wanted yesterday" regime and cannot take all the time needed for such deliberation. This is true possibly to an extreme degree amongst hobbyists.

The alternative to designing projects yourself is, of course, to let someone else do it. In this case you must either pay someone to design what you want (or think you want) or get it from a book or magazine (ETI of course!). In this latter case you are restricted to what is published but must still make the effort to understand fully the circuitry you are making. If you do not understand what you have made, you are going to be in big trouble if anything goes wrong. You may get a little help by writing in but publishers usually have neither the time nor money to employ clairvoyant faultfinders.

To illustrate the design process I have included a section on the recent GNOS-EX memory expansion card. Not that this is necessarily a shining example of perfection but it serves to illustrate some of the foregoing comments.

## GNOS-EX Development

This started in earnest about six months ago. For some time we had been aware that all was not well with our original 64K DRAM card for the Microtan system, especially in the control logic area. Since this was mostly invested in the 74LS608 memory control device there was not a great deal we could do about it.

In the meanwhile, we had published a DRAM card for Z80-based systems using the TM4500 memory controller. It would have been relatively simple to adapt this to 6502 use, but we did not think this the most useful or illuminating approach. Alternatively, we decided to design the project using the simplest standard TTL devices possible for the control section, along with the lesser known 4416 DRAMs. The 4416 is a 16K x 4 variant on the 64K x 1 devices used in the earlier designs. Although it's slightly more expensive than the latter, it offers the considerable advantage that the user need not populate the memory fully to obtain a workable system, as memory devices need be used in just pairs so 16, 32 or 48 Kbyte options are available, besides the full 64K.


The requirements for this project can be summarised as:

1. To provide up to 64K of dynamic memory;
2. To operate from the signals from a 6502 microprocessor;
3. To use standard TTL devices, preferably SSI and MSI types.

Other factors were considered but were deemed subsidiary to these for this purpose.
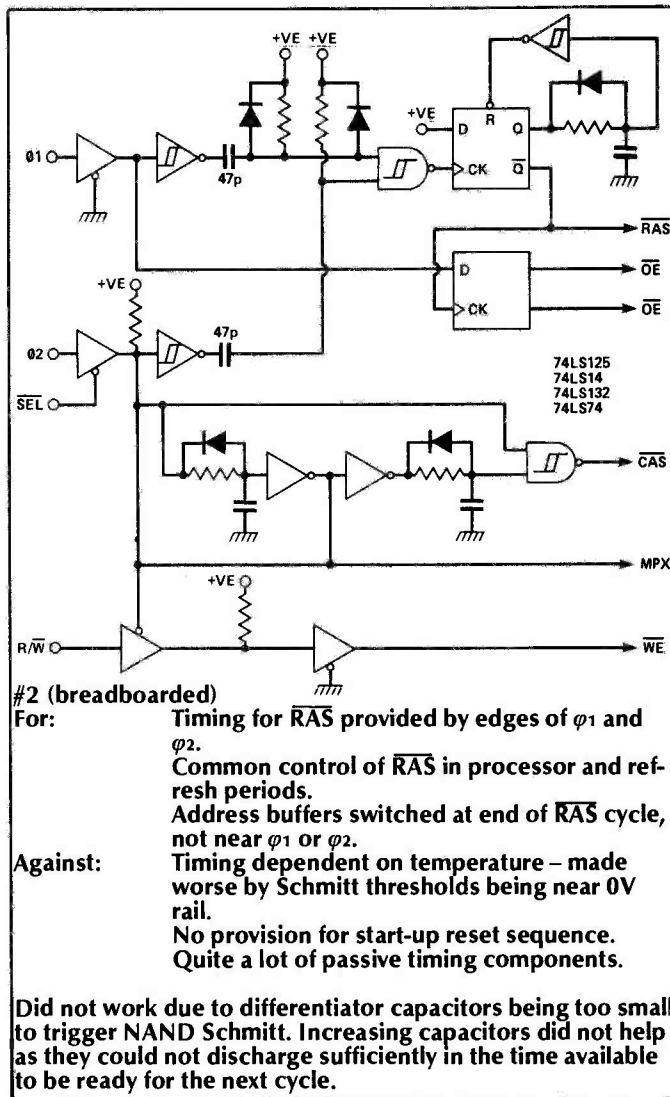
## Design Approaches

**#1** The first ideas on the possible control logic design tended to follow the original circuitry. Both  $\phi_1$  and  $\phi_2$  were used to obtain the requisite timing signals. In the 6502 data sheet these two signals are supposed to be non-overlapping, ie one falls to zero before the other rises. Looking at these on an oscilloscope showed that if this was the case, and it certainly did not appear so, it was of little practical use as a little stray capacitance or variation in gate propagation delay would nullify any benefits it gave.



The first paper design used the  $\phi_1$  and  $\phi_2$  signals to generate the  $\overline{\text{RAS}}$ ,  $\overline{\text{CAS}}$  and MUX signals with the aid of R-C delay networks and Schmitt input gates and inverters. This in fact used only three IC packages – one less than the final design. However it was felt that the number of passive components was excessive and that the timing they would give would be rather critical and temperature dependent.

**#2** The next serious attempt used a D-type latch connected as a monostable to generate the  $\overline{\text{RAS}}$  pulse triggered by two differentiator networks from the  $\phi_1$  and  $\phi_2$  inputs. The other half of the latch package was used to control the processor and refresh address buffer outputs. This was clocked on the rising edge of the  $\overline{\text{RAS}}$  signal and sampled the state of the  $\phi_1$  input to determine whether the next operation would be a refresh or processor operation. This was felt to have great merit as it ensured that the address presented to the memories was stable well before and after the active  $\overline{\text{RAS}}$  falling edge. The idea persisted into the final design.

The MUX and  $\overline{\text{CAS}}$  signals were still generated by R-C delays. In spite of this the circuit was felt to have some merit and was breadboarded. Unfortunately the differentiator networks did not function as planned and the monostable was not triggered reliably. The fault was found to be that the capacitors were too small to overcome the capacitance at the inputs to the gate, and increasing them did not help since then they were too large to recharge before the next cycle.

#3 A deliberate attempt was made in this design to eliminate as many of the R-C delays as possible. This led to the use of the 74LS122 monostable, as it is claimed to operate quite reliably at these time periods. Also with the multiplicity of trigger inputs, it was found possible to make the '122 trigger on both the rising and falling edges of the same input signal. This made it possible to dispense with the  $\phi_1$  signal and refer all timing to the  $\phi_2$  input. This also suited the designer quite nicely, as the  $\phi_1$  signal is not available on the system expansion bus connector.

With the critical timing taken care of by the monostable, the only other timing delays needed were between RAS and CAS and non-critical delay to make the monostable trigger on both edges. The former was very simply accomplished by an R-C network and, although vital, this was found to be stable enough for this project.

The data sheet on the 4416 states that the column addresses must be stable by the time the CAS signal goes low. In this design there is one extra device propagation delay in the CAS signal path more than in the address multiplexer path. In practice, this was found to give about 20ns separation in the right direction. In going from the D-type latch monostable circuit to the 74LS122 and retaining the buffer control part there was a spare D-type latch available. This was quickly put to use to sample the select signal at an appropriate time and provide a CAS signal which could remain low until the end of

a processor access cycle. This configuration not only removed a lot of constraints on the select decoding logic but also keeps data available at the memory devices until the 6502 has captured it. It also makes sure that there are no short or erroneous CAS outputs which would lead to mis-operation of the memory chips.

The essential control logic as designed together with the various address multiplexers, refresh counter and 16K of memory were constructed on a small PCB. This was connected via a simple interface to the designer's Ohio Superboard. This is a rather old 6502 system, which has been much modified, and now runs at a clock speed of 1.25MHz. After sorting out all the usual bugs and making the necessary adjustments, the project seemed to work well... for 10 minutes. No reason for the latch-up was apparent, so freezer spray was applied to various parts to see if there was a thermal problem. Lo and behold, it was the 6502 processor! However, since this had been working satisfactorily for some years, and still did so when not connected to the new memory, it was felt that the fault must be a little more obscure.


The next thing was to dig out all the data on the 6502 and the 4416. A combined timing diagram was drawn to illustrate the interaction between the two devices and the effect of the control logic. It had been noticed that although the data read from a location was not the same as that written to it each read operation was consistent with the last. This pointed to the possibility that there was a problem in the write operation. In fact the specification of the 6502 states that data in a write cycle is only guaranteed stable 200ns after the  $\phi_2$  rising edge. The 4416, however, requires that the data be stable whenever the later of CAS or WE goes low. In the design at this time it was the CAS which was critical. It was easy to adjust the delay to get round this problem, but this immediately raised another in the read cycle.

Here, the 6502 requires that data from the memories be stable 100ns before the  $\phi_2$  falling edge. The 4416 is guaranteed to supply this data 120ns after the CAS signal goes low. Being really pessimistic this would require a minimum  $\phi_2$  high time of 420ns, which looks a little adrift from the observed 360ns. To get around this, at least partly, the WE signal was gated with the CAS and  $\phi_2$  signals such that it occurred after the CAS signal. This meant that there was a little more leeway in the timing and the CAS signal could occur earlier. This was even better in the final design where there was an extra delay through the 'LS139 decoder.
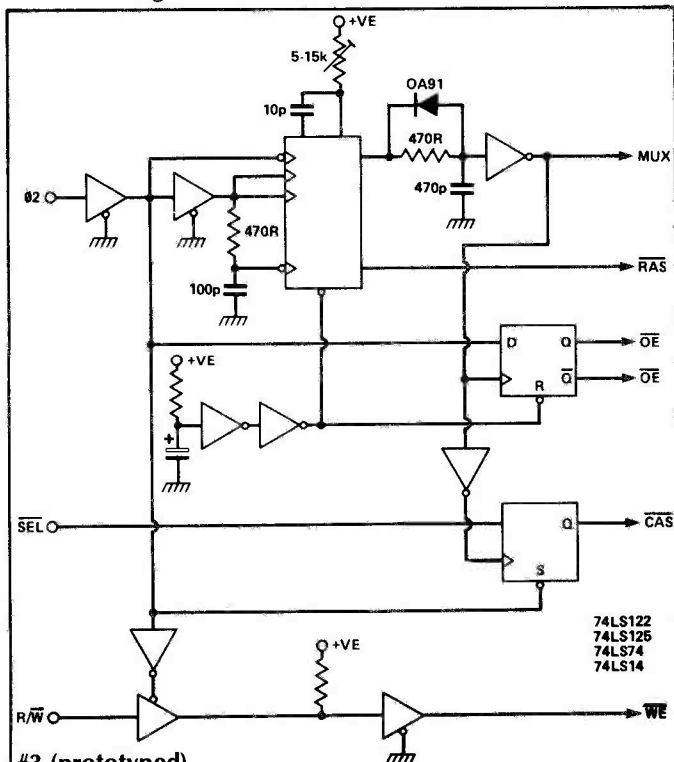
#4 Having got the prototype working satisfactorily, the time arrived to lay out a PCB for the final design. This took about four days for the double-sided artwork and a further three days to have it photographically reduced and a board etched, drilled and populated. A new interface to the Superboard was constructed and the design tested. This brought to light one or two things like the RAS and WE being swapped on the memories and the desirability of more test points on essential signal paths. These items were corrected on the PCB artwork to yield the final PCB pattern.

Once the RAS and WE problem had been solved the project worked as required although it was not possible to check operation with the slower 4416-20 devices as only 4416-15 were available from the suppliers.

One extra feature had been added to the design between the #3 and #4 versions and that was the G signal derived by an inverter from the R/W line. This is necessary because during an active processor access cycle, all the memory devices will perform a read operation except for a pair selected to have data written if the processor wants a write cycle. The G signal is routed by




#3 (prototyped)

- For:
- RAS timing set by one control and not temperature dependent.
  - RAS-CAS delay set by one network.
  - Only two main timing networks.
  - Address buffers switched half-way through cycle.
  - Once CAS triggered stays low to end of cycle - makes data remain on outputs.
- Against:
- Stopped working when processor warmed up

Refer to data sheets for 6502 and 4416 to get probable reason that 6502 guarantees data out valid for 200ns after  $\phi_2$  goes high. 4416 requires data valid whenever the later of WE or CAS goes low for a write cycle.



# FEATURE : Designing

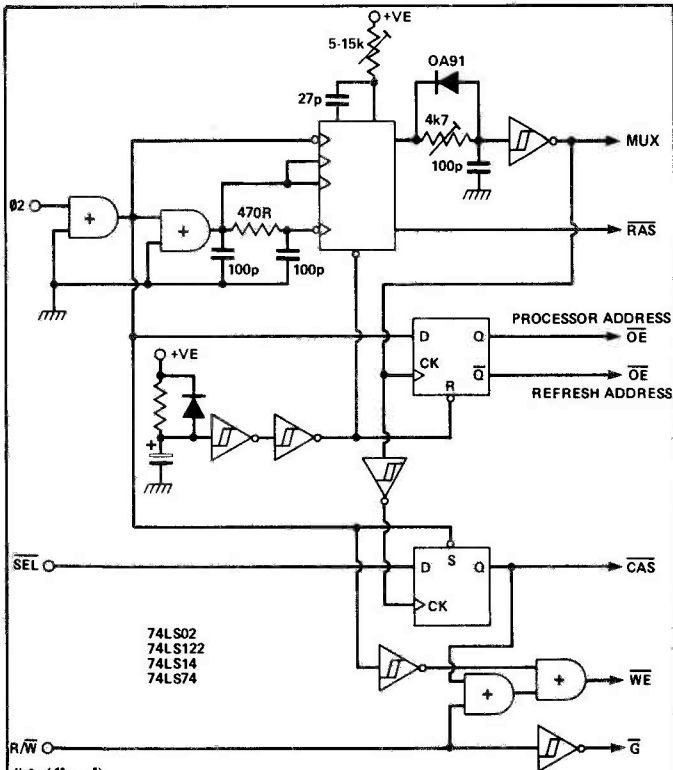

#4 (final)  
For:

All advantages of previous design.  
Uses quad NOR package instead of buffers – one less resistor.  
WE signal slightly after CAS instead of before it.  
G signal available to disable memory data output in WRITE mode.  
Works on a 1.25 MHz 6502 system.  
All edge triggered from  $\phi_2$  – samples SEL signal, CAS cannot be aborted once started.  
Requires adjustment to be made for best operation.  
Relies on short time delays around inputs of monostables.  
Memories must not be accessed for eight cycles after power-up.  
As it stands, is not usable for 4164 devices with data in and data out pins commoded.

Against:

the 'LS139 to the pair of memories to be accessed only during a read operation. At all other times the G pins of the memories will be high thus preventing their data bus drivers fighting for control of the bus. This does not affect the internal operation of the memories.

As a bonus and a service to readers who had built the 1983 DRAM design the control logic was re-configured to fit a small PCB such that it could be used to replace the control logic of the earlier design. Some small changes were necessary because of the select logic polarity difference and the use of 4164 memory devices. This was built onto the original project and tested under the same conditions and worked perfectly, as far as could be ascertained.

This concludes the description of how this project was designed. Although it cannot cover all the thought processes, prejudices, scribbles on odd bits of paper and strange flights of fancy which make up the design process, it serves as an illustration of how one starts with one set of ideas and progresses to the final solution discarding most or all of the original concepts on the way. This is probably quite common in designing electronic or other hardware (and software?) and is probably more useful than doggedly trying to get the first idea to work.

ETI

## LOOK!

**UNBEATABLE VALUE**  
TANDON 5 1/4" LINE FLOPPY DISC DRIVES  
SINGLE SIDED DOUBLE DENSITY £90  
DOUBLE SIDED DOUBLE DENSITY £130  
BRAND NEW

**DON'T DELAY  
ORDER TODAY**

<b>OBCILLOSCOPES</b>	
2 TEK 454 Dual Trace 150 MHz Delay Sweep	£700
6 TELEQUIPMENT D83 Dual Trace 50MHz Delay Sweep	£400
7 TEK 453 Dual Trace 50MHz Delay Sweep	£375
9 COSSOR 4100 Dual Trace 75MHz Delay Sweep	£375
10 SOLARTRON CD1740 Dual Trace 50MHz Dual TB	£250
14 TEK 585A Dual Trace 85MHz Dual TB Delay Sweep	£300
15 COSSOR CDU 150 Dual Trace 35MHz Delay Sweep	£200
17 SELABS SMT11 Dual Trace 20MHz	£175
23 SOLARTRON CD1400 Dual Beam 15MHz	£100
<b>STORAGE OBCILLOSCOPES</b>	
35 TELEQUIPMENT DM64 Dual Trace 10MHz	£350
<b>36 TEK 664 Dual Trace 100MHz Delay Sweep</b>	<b>£275</b>
37 TEK Spectrum Analyser 50Hz-36MHz 547 Mainframe IL5 and IL10 plug in units. P.O.A.	£350
42 H.P. SHF SIG GEN 6206 7-11GHz	£200
46 H.P. UHF SIG GEN 612A 450-1230MHz	£110
62 MARCONI AM/FM Sig Gen TF-10668/6 10-470 MHz	£325
59 MARCONI AM/FM Sig Gen TF995A/ 21.5-220MHz	£250
62 MARCONI VHF Sig Gen TF10648/5M 68-108; 18-185; 450-470MHz	£110
83 MARCONI OUTPUT TEST SET TF 1065 for use with TF1064 & TF995 range Sig Gens	£75
86 ADVANCE AM Sig Gen E2 100KHz-100MHz	£40
72 TEK Constant Amplitude Sig Gen 1908 350KHz/50MHz	£100
74 MARCONI WIDE RANGE OSC 10Hz to TF1370A 10MHz sine and square	£95
80 WAYNE KERR AF Sig Gen S121 10Hz-120KHz	£40
87 H.P. Pulse Gen 214A 10Hz-1MHz	£250
89 EH PULSE GEN 139L 1KHz-20MHz Single/Double Pulse	£200
99 TEK TIME MARK GEN 180	£40
102 BONTON Q METER 260A 50KHz-50MHz	£200
106 MARCONI UNIVERSAL BRIDGE TF1313 0.25%	£250
108 MARCONI INSTITU UNIVERSAL BRIDGE TF2701. Battery Operated	£300

## STEPPING MOTORS

Type 1. 200 steps 4 Phase (5 wire) 12/24V 25 oz inch 2 1/4" dia. £2 ea. 5 for £7.50  
Type 2. 6/12 Steps 3 Phase 12/24V 1 1/4" dia. £2 ea. 5 for £7.50  
Type 3. 24 Steps 4 wire 5V 3.3A 0-250rpm 0-200Pa 2 1/4" dia. £10 ea  
Type 4. 200 Steps 120V (3 wire) 25oz inch 2.375" dia. £4 ea  
P&P and VAT EXTRA

109 Wayne Kerr Autobalance Component Bridge 8421	£250
114 Wayne Kerr Component Bridge B521 (CT375) L 100uH.500KHz: C1pF-5F: R1 milliohm-1000Mohm	£250
117 Wayne Kerr VHF Admittance Bridge B801 with Source S161 & Detector R818	£400
119 MARCONI AM/FM Mod-Meter TF2300S	£375
123 AIRMEC MOD METER AM/FM type 210 2-100MHz	£96
124 MARCONI RF MILLIVOLT METER TF2603 50KHz-1500kHz 1mV-3VSD	£375
125 MARCONI ELECTRONIC VOLT METER TF2604/2Hz-1500MHz AC/DC/Ohms AC300mV-300V FSD: DC 200mV-1KV FSD	£175
144 AVO MULTIMETER MODEL 7 P&P E7	£20
145 AVO MULTIMETER Model 6 P&P E7	£45
152 MULTIMETER UA324 33 switched ranges 20K Ohm per volt. Complete with leads & battery. Brand New. One year guarantee P&P £4.	£18
161 FARNELL STAB PSU TSV30/2 0-30V 2A Current limiting metered	£50
163 ROBAND VARECO PSU type 33-2 0-33V 2A Current limiting metered (In current production)	£100
189 KINGSHILL STAB PSU Model 500 0-60V 0.5A. Current limiting Metered P&P £7	£40
180 BRANDBURGH PHOTOMULTIPLIER PSU 47R 10-2100V 5mA Metered	£200
190 VOLT EX PSU Model 82-635 +/-5V; +12V; -24V High current un-used	£16
191 AC/DC ELECTRONICS PSU MODULE 251 5V 2A +/-12V 0.4A Un-used P&P £3	£18
206 B&K LEVEL RECORDER 2305	£400
209 B&K MEASURING AMPLIFIER 2606 2Hz-200KHz	£300
281 H.P. LOGISTIC ANALYSER 1602A	£480
286 AVO VALUE CHARACTERISTIC METER VCM 183 etc.	£275
293 MARCONI AF POWER METER TF82A	£75
297 MARCONI DIFFERENTIAL DC VOLT METER TF2506 0-1100V	£225
300 RAS POLYSKOP SWDB1 BN 4244/2/50	£350

Also in stock NEW OBCILLOPSES, MULTIMETERS etc.  
THIS IS A VERY SMALL SAMPLE OF STOCK, SAE or Telephone for LIST  
Please check availability before ordering.  
Carriage all units  
£10 VAT to be added to Total of Goods & Carriage

## STEWARTS OF READING

110 WYKENHAM ROAD, READING, BERKS RG6 1PL

Telephone: 0734 68041

Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

**GRIPMATE®**  
NEW! ELECTRONIC ENGINEERS NEED  
'EXTRA HANDS' FOR  
SOLDERING GLUEING  
AND ASSEMBLING


This essential compact tool comes complete with 4 croc-clip flexi-arms to hold components positively and rapidly with infinite positioning....

ONLY **£4.85** USEFUL ACCESSORIES...  
48mm 2.5x MAGNIFIER FLEXI-ARM £2.50  
MAGNET FLEXI-ARM £1.50  
ALL PRICES INCLUDE VAT- POST- PKG

SEND NOW! CHQ/PO OR SAE DETAILS DIRECT FROM THE MAKERS:

**KEMPLANT LTD** (DEPT.1)

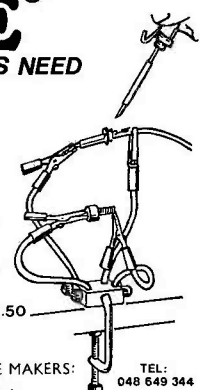DURFOLD WOOD, PLAISTOW, BILLINGSHURST, WEST SUSSEX RH14 0PN



Please  
mention  
**E.T.I.**  
when replying  
to all  
adverts





# components

GILRAY ROAD, DISS, NORFOLK. TEL: 0379 4131

INSULATION DISPLACEMENT CONNECTOR SYSTEM			
HEADERS	SHROUDED		OPEN — STRAIGHT
	90°	90°	PINS
10 way	0.86	0.65	0.47
14 way	1.22	0.83	0.59
16 way	1.34	0.92	0.65
20 way	1.36	1.13	0.77
26 way	1.70	1.40	0.95
34 way	2.04	1.78	1.19
40 way	2.28	2.07	1.37
50 way	2.70	2.54	1.67
60 way	3.20	3.02	1.96

CABLE ASSEMBLIES	
IDC JUMPERS SINGLE ENDED	
36" cable	IDC socket
10 way	1.72
14 way	2.07
16 way	2.22
20 way	3.14
26 way	3.75
34 way	3.98
40 way	4.23
50 way	5.36
60 way	6.36

DIP JUMPERS		
Single Ended — 24" cable		
14 pin	1.73	
16 pin	1.90	
24 pin	2.73	
40 pin	3.96	

SOCKETS		DIP PLUGS		D-TYPE PLUGS	
10 way	0.88	14 way	0.92	9 way	1.38
14 way	1.06	16 way	1.06	15 way	1.85
16 way	1.16	24 way	1.60	25 way	2.52
20 way	1.38	40 way	2.40	37 way	3.34
26 way	1.66				
34 way	1.94				
40 way	2.08				
50 way	2.78				
60 way	3.34				

DISC DRIVE CONNECTING CABLES		
34 way card edge to 34 way card edge 1M		11.30
34 way card edge to 2 x 34 way card edge 1.5M		18.00
34 way card edge to 34 way IDC SKT (BBC) 1M		8.50
34 way card edge to 2 x 34 way IDC SKT (BBC) 1.5M		14.50
BBC Power Cable — Single Drive		3.50
BBC Power Cable — Dual Drive		4.75

RIBBON CABLE (PRICED PER FOOT)		
	GREY	RAINBOW
10 way	0.86	0.90
16 way	1.17	1.20
20 way	1.37	1.40
26 way	1.67	1.70
34 way	1.87	1.90
40 way	2.23	2.26
50 way	2.90	2.93
60 way	3.97	4.00

CARD EDGE		D-TYPE SOCKETS	
10 way	1.84	9 way	1.47
20 way	3.14	15 way	2.02
26 way	3.80	25 way	2.90
34 way	4.90	37 way	3.97
40 way	5.52		
50 way	6.68		
60 way	8.06		

BBC MICRO CONNECTORS	
DIN PLUG 7 PIN	0.40
DIN PLUG 6 PIN	0.40
DIN PLUG 5 PIN 180°	0.40
DIN PLUG 5 PIN DOMINOE	0.40
POWER PLUG (36" CABLE)	3.00
ANALOGUE INPUT PLUG	2.25
5 WAY DIN SKT 180°	0.90
5 WAY DIN SKT DOMINOE	0.90
6 WAY DIN SKT	0.90
7 WAY DIN SKT	0.90
15 WAY DIN SKT	2.15

CONNECTING CABLES FOR PERSONAL COMPUTERS	
Phono plug to phono plug (2M)	1.20
Phono plug to BNC plug (2M)	2.95
BNC plug to BNC plug (2M)	3.95
6 pin DIN to open end (1M)	1.05
6 pin DIN to 6 pin DIN (1M)	1.50
Phono plug to coax plug	1.35
DIN plug to 2 phono plugs	1.20

Part number	Description	Computer	Price
CON100	Phono plug to phono plug (2M)		1.20
CON101	Phono plug to BNC plug (2M)		2.95
CON102	BNC plug to BNC plug (2M)		3.95
CON107	6 pin DIN to open end (1M)		1.05
CON108	6 pin DIN to 6 pin DIN (1M)	BBC	1.50
CON119	Phono plug to coax plug		1.35
CON160	DIN plug to 2 phono plugs	Dragon	1.20

Cassette recorder cables			
CON109	7 pin DIN to open end	BBC	1.25
CON110	7 pin DIN to 2 x 3.5mm + 1 x 2.5mm 1/2 plug	BBC	2.50
CON111	7 pin DIN to 5 pin DIN + 2.5mm 1/2 plug	BBC	2.50
CON118	5 pin DIN to 2 x 3.5mm 1/2 plugs	Spectrum/ZX	2.50
CON117	5 pin DIN to 2 x 3.5mm + 1 x 2.5mm 1/2 plug	Dragon	2.50

Parallel printer cables			
CON130	36 way plug to 36 way plug (2M)	Sirus/Apricot	18.00
CON131	36 way plug to 36 way plug (5M)	Sirus/Apricot	26.50
CON132	36 way plug to 36 way socket (2M)		18.00
CON133	36 way plug to 36 way socket (5M)		26.50
CON144	36 way plug to 25 way male D type (2M)	IBM/TPC	19.00
CON145	36 way plug to 25 way male D type (5M)	IBM/TPC	27.50
CON134	36 way plug to 25 way male D type (2M)	RML/Apple	19.00
CON135	36 way plug to 25 way Male D type (5M)	RML/Apple	27.50
CON142	36 way plug to 20 way IDC socket (2M)	Dragon	13.95
CON139	36 way plug to 26 way IDC socket (2M)	BBC	9.95
CON140	36 way plug to 26 way IDC socket (5M)	BBC	22.95
CON141	36 way plug to 34 way card edge (2M)	TRS80 Lev 1	18.50
CON143	36 way plug to 34 way IDC socket (2M)	TRS80 Lev 2/ Memotech	10.95

RS232 Cables			
CON106	25 way male D type to 5 pin DIN	BBC	5.85
CON128	Universal RS232 cable (pins 1-8, 20 connected and 20 jumpered as required) 2M		15.95
CON164	Universal RS232 cable as above but 5M		20.95
CON120	25 way male to male 1-25 connected (2M)		16.95
CON121	25 way male to male 1-25 connected (5M)		22.50
CON122	25 way male to male 1-25 connected (10M)		32.50
CON123	25 way male to male 1-25 connected (30M)		68.00
CON124	25 way male to female 1-25 connected (2M)		15.45
CON125	25 way male to female 1-25 connected (5M)		21.00
CON126	25 way male to female 1-25 connected (10M)		31.00
CON127	25 way male to female 1-25 connected (30M)		66.50
CON129	25 way male to 9 way male	Spectrum	15.95
CON162	25 way male to 9 way male	Mackintosh	15.95
CON163	25 way male to 5 pin DIN	RML 480Z	14.95

PART NO.	DESCRIPTION	MAIL ORDER PRICE
<b>BBC MICROS AND ACCESSORIES</b>		
ANB01	BBC Model B Micro	£325.00
ANB02	BBC Model B Micro with Econet I/F	£385.00
ANB03	BBC Model B Micro with Disc I/F	£406.00
ANB04	BBC Model B Micro with Disc & Econet	£445.00
ANB21	DNFS ROM	£17.91
ANB23	Disc Interface Kit (Excl DNFS ROM)	£84.00
ANB14	Speech Interface	£40.00
ANK01	iEEE488 Interface Adaptor	£283.00
ANB22	Econet I/F Kits	£35.00
BBC 45	2 BBC Joysticks	£8.00
STAND	Monitor Stand	£7.50
SRE1	Sideways ROM Expansion Board for BBC Micro	£25.95

BBC DISC DRIVES		
HC1	Single 100k 40 track single sided	£75.00
HC15	Single 100k (expandable to dual) 40 track	£90.00
HC1D	Dual (2 x 100k) 40 track single sided	£160.00
BBC44	Single 400k 80 track double sided	£156.50
BBC44S	Single 400k (expandable to dual) 40/80 track switchable double sided	£180.00
BBC44SW	Single 400k 40/80 track switchable double sided	£159.00
BBC44D	Dual (2 x 400k) 40/80 track switchable double sided	£310.00

MECHANISMS		
	100k single sided Alps	£70.00
	400k double sided Epson	£140.00

FLOPPY DISCS		
MD-1C/B	Nashua single sided, single density 40 track (10 discs)	£12.00
MD-1DC/B	Nashua single sided, double density 40 track (10 discs)	£13.00
MD-2DC/B	Nashua double sided, double density 40 track (10 discs)	£15.50
MD-2FC/B	Nashua double sided, quad density 80 track (10 discs)	£17.85

SPECIAL OFFER		
BBC40TD	BASF double sided, double density 40 track (10 discs)	£14.00

DISC STORAGE BOXES		
MDT25/3	3 1/2" Flip 'N' file Micro disc box (cap. 25)	£7.75
DT25/5	5 1/4" Flip 'N' file lockable disc box (cap. 25)	£18.77
DT60/5	5 1/4" Standard lockable disc box (cap. 60)	£10.65

MONITORS		
9MON	9 inch green screen high resolution NEC high quality monitor	£125.00
12MON	12 inch green screen high resolution NEC high quality monitor	£135.00
1431	Microvitec 14" RGB colour monitor	£175.00
1441	Microvitec 14" RGB colour monitor high resolution	£410.00
1451	Microvitec 14" RGB colour monitor medium resolution	£295.00
1431/AP/MS	Microvitec 1431 PAL & RGB inputs and sound facility	£225.00

EPSON COMPUTERS AND ACCESSORIES		
PX-8	Epson portable computer (incl. CP/M and s/w) 64k	£798.00
PX-8/120	120k RAM	£998.00
CX-21	Acoustic coupler	£160.00
PF/10	Disc drive for PX-8	£360.00
P40	Thermal printer for PX-8 and HX-20	£86.91
HX-20	Epson portable computer	£411.00

MATRIX PRINTERS		
RX80	Epson RX80 100cps matrix printer	£204.00
RX80F/T	Epson RX80F/T 100 cps matrix printer friction or tractor feed	£231.00
FX80	Epson FX80 150cps matrix printer	£328.50
MT80SP	Mannesmann Tally MT80 matrix printer friction or tractor feed with film ribbon and tear off facility	£217.00

LETTER QUALITY PRINTERS		
HR5	Brother HR5 Thermal printer A/C mains or battery	£130.00
HR15	Brother HR15 Daisy wheel printer (13cps)	£326.00
HR25	Brother HR25 Daisy wheel printer (23cps)	£550.00
UCHIDA	Uchida DWX305 Daisy wheel printer (20cps)	£227.00

PRINTER SUPPLIES		
11241P160	11 x 9; 1 part plain listing paper (2,000)	£12.56
11241P2C1	11 x 9; 2 part (otc) plain listing paper (1,000)	£15.93
11241P3C1	11 x 9; 3 part (otc) plain listing paper (700)	£17.86
11370R160	11 x 14; 1 part ruled listing paper (2,000)	£16.20
11370R2NC	11 x 14; 2 part (ncr) ruled listing paper (1,000)	£22.50
11370R2C1	11 x 14; 2 part (otc) ruled listing paper (1,000)	£15.00
12235P160S	12 x 9; 1 part plain listing paper with side perms (2,000)	£12.00
HR1R	Brother HR1 ribbon	£2.20
RIB119	Diablo Hytype II Multistrike film ribbon	£1.75
GP205	Diablo Hytype II fabric ribbon	£2.50
MX80	Epson MX80, RX80, FX80, fabric ribbon	£3.00
MT80	Mannesmann Tally MT80 film ribbon	£6.50
RIB117	Uchida DWX305 multistrike film ribbon	£2.75
HR5R	Brother HR5 ribbon	£2.20
HR15R	Brother HR15 multistrike ribbon	£4.00
HR25R	Brother HR25 multistrike ribbon	£4.00
	Brother daisy wheels	£14.00
	Uchida/Qume daisywheels	£4.00
LAB089361C	3:1 7/16 Labels — 1 wide (8,000)	£20.00
LAB089361S	3:1 7/16 Labels — 1 wide (2,000)	£13.00
LAB07363F	2:1 7/16 Labels — 3 wide (1/10") (2,000)	£8.00

# DIGITAL DELAY LINE

Greedy for more, eh? Well here's the expansion card, together with some notes and hints on how to use the unit. Design and development by Ray Lowe.

The memory expansion circuit is shown in Fig. 1. Comparing this with the 'motherboard' memory section (Fig. 3, p19, ETI Dec. '84) shows that the two are identical lumps of circuitry. So, to understand how it works — as if you didn't know — you'll have to find a back issue. Selection between the two memory sections is made by inhibiting them alternately via the inverter preceding the 'EXP' control line.

Installation of the extra

memory is straightforward, but requires careful soldering to the logic PCB (motherboard). The best — and easiest — way to accomplish this is shown in Fig. 2. Remember to follow construction tips given in the earlier articles.

The expansion PCB layout diagram shows connections labelled with the pin no. to which they should be connected. These numbers refer to the pins of ICs in the usual fashion, ie looking downwards on the component

side of the PCB and starting with no. 1 at top left hand corner, adjacent to the notch, and numbering anticlockwise.

### Possible Adaptions

**Drum machine:** if you know a little about digital electronics, you can try adding a simple circuit which will page between memory or expansion card(s), via the INHibit pins, to give a drum machine-like programmability.

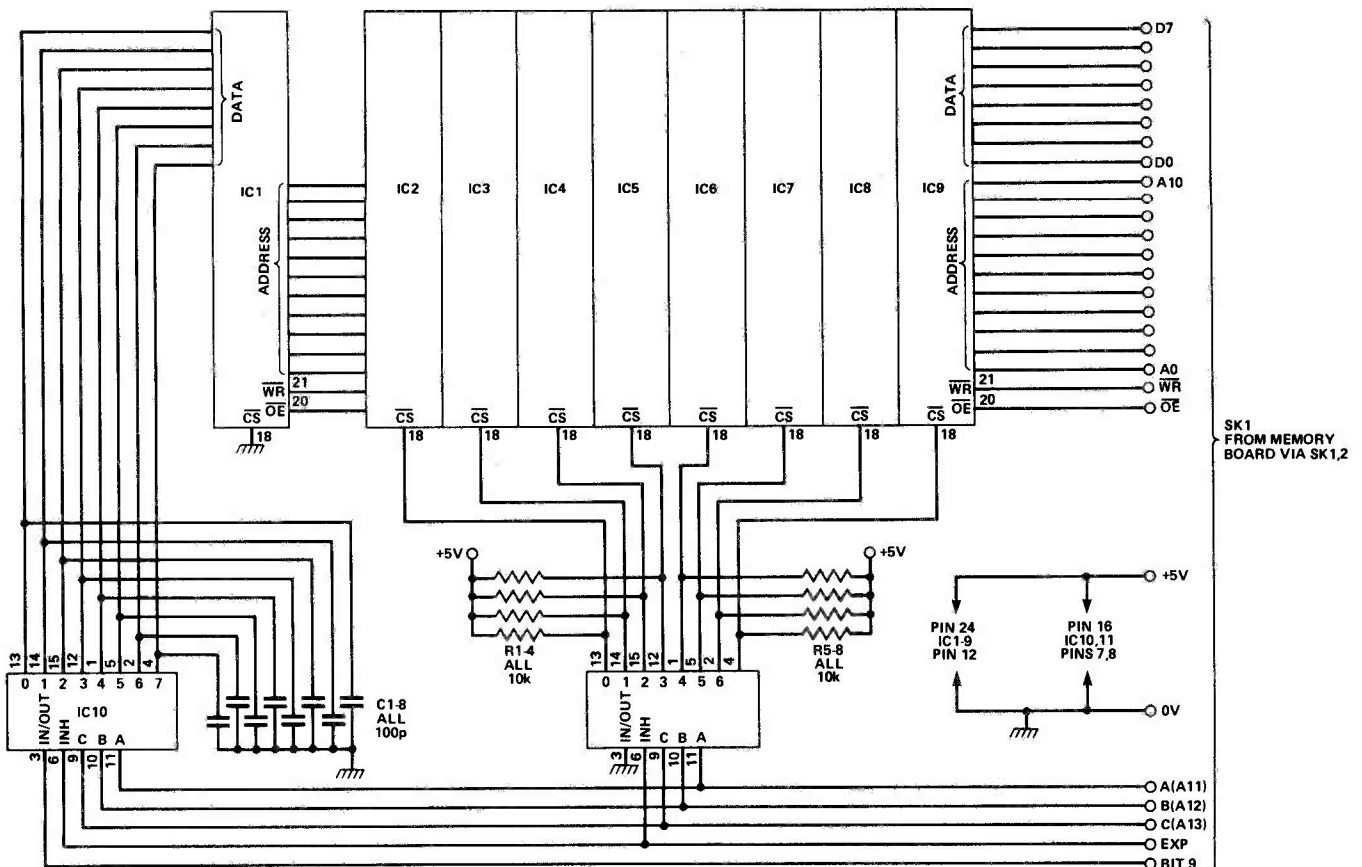


Fig. 1 Circuit diagram of the expansion card. On IC1-9, the data is on pins 9 to 1 and 13 to 17, and the address on pins 1 to 8 and 19, 22, 23; it does not matter one jot in which order these pins are used in this circuit, and, as you'll see on the PCB, the order is changed between some ICs merely to help the track lay-out.

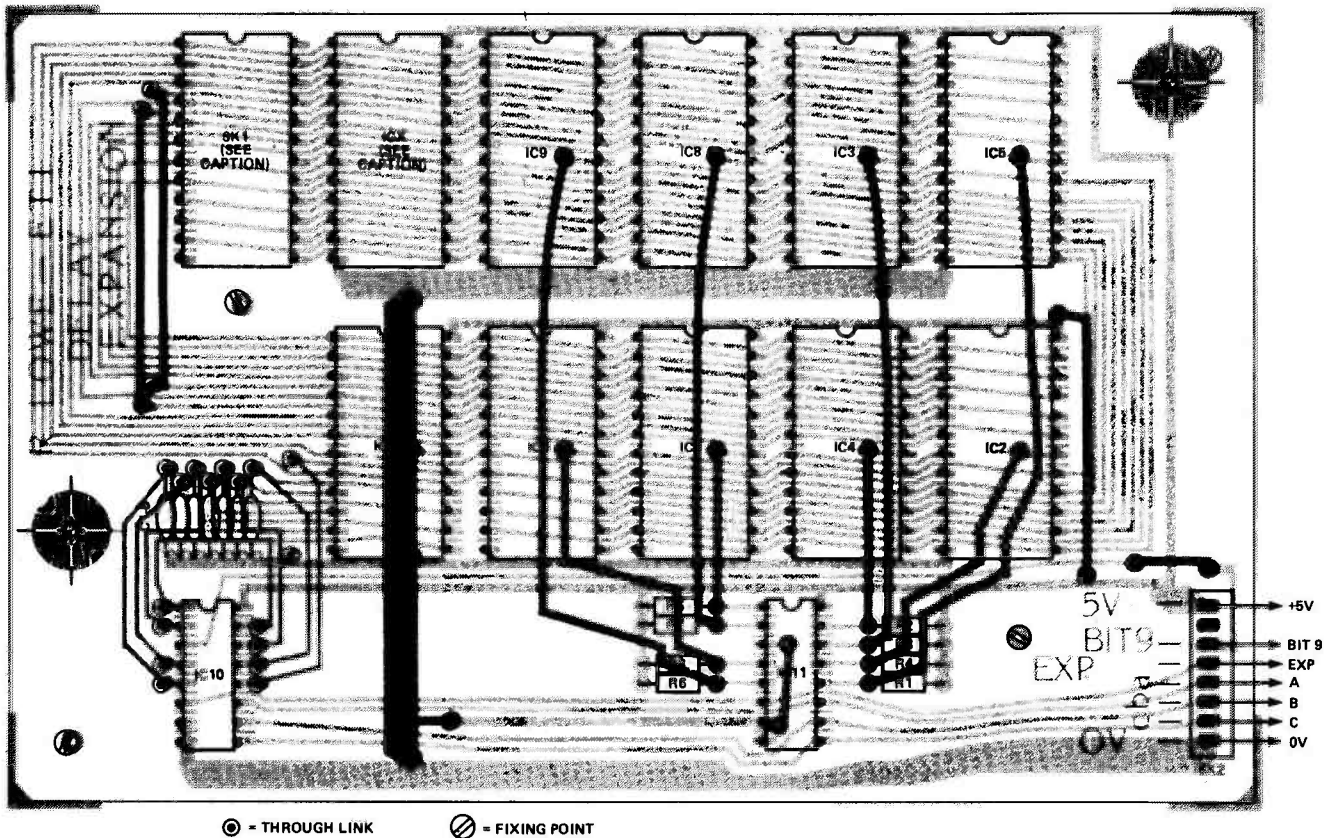


Fig. 2 Overlay diagram of the expansion card, which is connected to the main memory card using a short length of ribbon cable with header sockets at both ends. On the main memory card, one of the memory ICs will have to be removed to allow the header plug to be inserted, and this IC should be transferred to the position marked ICX on the expansion card. Be sure to get the orientation of the header sockets right! Note also that some additional links to the expansion card come in via SK2, and these are all labelled on the expansion card and on the main memory card overlay.

This can be used in the percussion mode, with a trigger input from a sequencer or drum contacts, for example. The amount of memory required to store percussive sounds would be quite small so that only two or three chips need be present per expansion card.

**External delay modulation:** you can apply, via a 100k resistor, an externally-generated control voltage to the inverting input of IC14a — from a foot pedal, for example, to allow external delay (pitch) modulation when playing live.

**Audio storage scope facility:** not very musical, I admit, but the unit will do this job with no modification (although you do need to have a 'scope already to connect to it!). Probably only 4K of memory would be needed for this use.

Finally, pseudo-stereo could be achieved simply, by taking the 'straight' and delayed channels to separate inputs on the stereo amplifier.

## Using The Unit

There now follow some notes on using the unit, with or without the expansion card. One general point which should be noted is that the setting of the input gain control should be done carefully to obtain best results. The gains of other units before and after the unit should be adjusted to compensate. The objective is to use the maximum signal level you can, to avoid quantisation noise, etc, whilst maintaining just enough headroom to prevent transients, etc, grossly overloading the A-to-D.

If the unit is used in conjunction with other effects, then the best position for it will have to be determined by experiment. Obviously you'll obtain different effects from different orders of the effects units. However, if a compression type of effect, such as sustain, is used, then placing the delay line after this effect will take advantage of the reduced dynamic range.

Similarly, a noise gate will probably give better results if used before the delay line.

A footswitch can be connected, via the front panel socket, to switch the delay channel in or out, by shorting the 'EXT' pin to analogue ground. Similarly, externally generated trigger pulses in the range 5 to 20 volts can be

## PARTS LIST

### RESISTORS (all ¼W 5%)

R1-8 10k

### CAPACITORS

C1-8 100p ceramic

### SEMICONDUCTORS

IC1-9 6116, any speed  
IC10,11 4051

### MISCELLANEOUS

IC Sockets: 11 off 24-way (one of these is SK1), 2 off 16 way; 1 off 8-way connector and socket (SK2), 0.1" pitch; 2 off 24-pin header sockets; ribbon cable; PCB: wire, solder, etc.



# PROJECT : Delay Expander

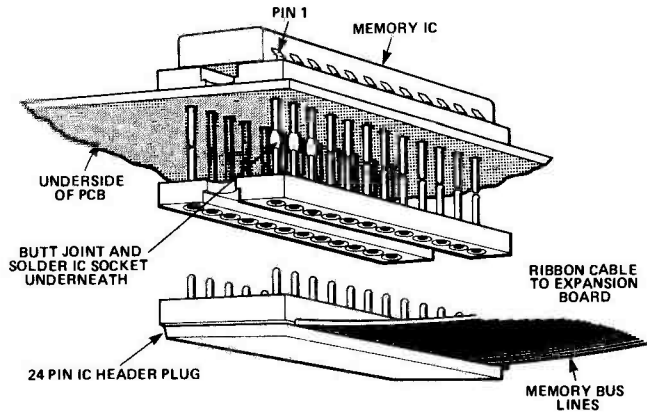


Fig. 3 An alternative method of connecting the expansion card to the main memory, and which avoids having to move one of the memory ICs. However, you must be careful to get the orientation of the header socket right.

applied to the logic board via the trigger input. The delay channel is reset by the leading edge of the pulse and remains reset until the trailing edge. So far, these inputs have proved to be idiot-proof, but don't try to prove us wrong...

## Using 'Freeze' And 'Percussion'

To store a sound, press freeze in at any time, or have the freeze switch out and the percussion switch in. Set the input signal level, then, by either momentarily

releasing the percussion switch or by applying a trigger pulse, start the record cycle and the signal is now recorded. Note that a trigger source can sometimes be derived from a signal source, eg drum contact. With percussion already in, push in freeze to write protect the sound. Applying trigger pulses, etc, will regenerate the sound upon request (percussive mode) or the sound can be continually cycled with the percussion switch out.

The stored sound can be manipulated by means of the

## BUYLINES

Nothing here should cause any problems. The PCB is, as ever, available through our PCB service.

delay time buttons, the bandwidth control, and the low frequency oscillator. The repeat control affects the decay rate once freeze has been released.

## Effects

Chorus and flanging type effects are obtained by using short delays and mixing the original and delayed channels equally. The time delay constitutes a phase difference and results in comb filtering. By modulating the delay time, the filter frequency is modulated and a sweeping type effect is generated. Multi-repeats also enhance some effects. Pitch change is accomplished by using longer delays and varying the delay time. Vibrato and double tracking can be achieved in this way. Varying the delay time can make the sound appear to come from a Coca-Cola tin to a huge cavern, depending upon setting.

These are just a few effects that can be produced — the only limitation is that of imagination!



" I'M SHUNTING THE SLOW SAWTOOTH INTO THE SIDING WHILE THE EXPRESS SINEBURST IS CLOCKED THROUGH ON THE MAIN LINE "

## ELECTRONIC SIREN KIT

Produces an extremely loud piercing swept frequency tone from a 9-15V supply. Enable input for easy connection to alarm circuits. Includes 5in. Horn Speaker. £7.90




### Mini Siren

As above, but with a small speaker (instead of horn speaker) for internal use. Complete with box £4.30
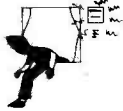
## SECURITY PRODUCTS

Protect your home and property and save by building your own burglar alarm system.



- Stair Mat 23 x 7 in (950 120) £1.70
- Floor Mat 29 x 16 in (950 125) £2.60
- Tamper-proof connecting block (950 110) £0.30
- Door/Window Contacts. Flush mounting, 4 wire, Magnet/switch Per Pair. (950 140) £1.05
- Window Tape 0.5" wide, 50m. (950 145) £2.50
- Window Tape Terminations Per pair. (950 150) £0.36
- Key-operated Switch, 1 5A/250V SPST Heavy chrome metal. (350 128) £4.50
- Passive Infra-Red Detector Detects intruder's body heat. Range 10 metres. 12V DC, n/o & n/c contact (950 135) £40.00
- Alarm Control Unit. 4 input circuits, 2-instant and 2-delayed. Adjustable entry, exit and alarm times. Built and tested. Full instructions supplied. Size: 180 x 130 x 30mm. Supply: 12V DC. (950 160) £26.00
- Ultrasonic Burglar Alarm. Self-contained mains or battery powered unit complete with horn and AC adaptor. Inputs for pressure mats and other sensors together with exit/entry delays enable this unit to be used as a complete system. £45.00 + p&p £2.20
- 8W Horn Speaker, 5.5 ins. 8 ohm. Ideal for sirens, etc. 2.5m lead and 3.5mm jack plug (403 148) £6.15

## TOP QUALITY... TOP SERVICE BOTTOM PRICES!

For FREE CATALOGUE send 9" x 6" SAE - contains full list of stock range all at very competitive prices. Cash with order (except account customers). Access or Barclaycard telephone orders welcome. Add 75p p&p + 15% VAT to all UK orders. Overseas customers add £2.75 p&p Europe, £6.50 elsewhere. Giro No. 529314002. Goods by return subject to availability. Shop open 9am - 5pm (Mon-Fri). 10am - 4pm Sat). ALL PRICES EXCLUDE VAT

## INFRA-RED REMOTE CONTROL KITS




These kits are designed to enable infra-red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The application will determine the interface circuitry between the receiver and the controlled device. General instructions and applications are supplied. The kits are coded and provide a high degree of security and noise immunity.

- MK 18 Transmitter Kit** - for use with MK 11/MK 12 receivers. Requires PP3 battery. Size: 8 x 2 x 13cms. Range approx. 60 ft. £6.80
- Keyboards for MK 18**
- MK 9 4-way for use with MK 12 £1.90
- MK 10 16-way for use with MK 12 £5.40
- MK 13 11-way for use with MK 11 £4.35
- MK 11 Receiver Kit** - mains powered. Provides 10 latched plus 3 analogue outputs ideal for controlling audio amplifiers, TV or lighting where control of light brightness is required. £13.50
- MK 14 AC Power Controller Kit** for (phase) controlling AC loads from MK 11 analogue outputs, eg lamp dimming. £5.20

**MK 19 Stereo Amplifier Controller Kit** - for remote control of bass, treble and volume (or balance) by MK 11. Includes a one of 10 decoder remote channel or input selection. May be connected between the pre-amp and power amp of almost any audio system. £10.70


**MK 12 Receiver Kit** - mains powered with 16 latched or momentary outputs. Latched version is for applications requiring one output on at a time, eg TV channel selection. Momentary type gives an output only during transmission. Lines may be latched as required. £13.50

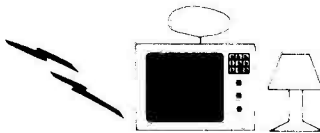**MK 15 Dual Latched Solid State Relay** for switching mains loads such as lamps, TVs, etc. from the outputs of the MK 12 (momentary). 15 items may be switched independently using 8 MK 15s. Triacs (not supplied) switch at mains zero to reduce interference. £4.50



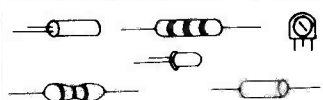
## COMPONENT PACKS

- PACK 1** 650 Resistors 4R 10M 10 per value £4.00
- PACK 2** 40 x 16V Electrolytics 10 1000uF 5per value £3.25
- PACK 3** 60 x Polyester Capacitors 0.01 1uF 250V 5 values £5.55
- PACK 4** 45 Presets 100R 1M £3.00
- PACK 5** 30 x Low Profile IC Sockets 8, 14 & 16 pin £2.40
- PACK 6** 25 Red LEDs (5mm) £1.75



## BT STYLE PHONE CONNECTORS

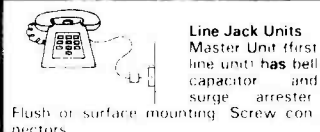

- Line Jack Units Master Unit (first line unit) has bell capacitor and surge arrester. Flush or surface mounting. Screw connectors.
- Master (flush) (960 110) £3.00
  - Master (surface) (960 112) £3.00
  - Master (mini surface) (960 113) £3.50
  - Secondary (flush) (960 114) £2.65
  - Secondary (surface) (960 116) £2.65
  - Secondary (mini surface) (960 117) £3.00
  - Dual outlet adaptor (960 118) £4.20
  - 4 way line cord with plug to spade terminals (960 120) £2.00
  - 4 way line cord (960 130) £0.20 per m

## LCD DIGITAL MULTIMETERS

**LOW COST!** 10M ohm, 3 1/2 digit 0.4 in display. Auto zero and polarity, low batt. indication, overload protection. Includes test leads, battery, spare fuse, manual, carrying case.

AC Volts: 0-200-500.  
DC Volts: 0.2-20-200-1000.  
DC Current: 0-20m-200mA.  
Resistance: 0.2k-20k-200k-2M.  
Size: 138 x 86 x 36mm. (405 202) £25.95

**Professional** - 10M, 0.5 in, 3 1/2 digit. Overrange and low battery indication. Overload protection. Includes leads, spare fuse, battery, manual and case. Transistor Checker. Size: 175 x 93 x 42mm.

AC Volts: 0-200-750.  
DC Volts: 0-200m-2-20-200-1000.  
DC Current: 0-20u-2m-20m-200mA.  
0-10A.  
Ohms: 0-200-2k-20k-200k-2M-0-20M. (405 204) £33.50



**Auto Ranging.** 3 1/2 digit 10mm display. Continuity buzzer, low battery, overload and range indication, 10A internal shunt for AC/DC current measurement. Carrying case supplied.

AC Volts: 0-2-20-200-600.  
DC Volts: 0-0.2-2-20-200-1000.  
DC Current: 0-200mA, 0-10A.  
AC Current: 0-200mA/0-10A.  
Resistance: 0-200-2k-20k-200k-0-2M.  
Size: 160 x 85 x 29mm. (405 206) £44.85

**High Sensitivity Temperature Probe.** For use with a multimeter to measure temperatures from -50°C to +250°C. Accuracy: 1.5°C@25°C, 2°C@100°C. Response time (in water), 5 seconds. Includes case, calibrated scale and instructions. (405 220) £8.50

## MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at preset times over a 7-day cycle. LED display of time and day, easily programmed via 20-way keyboard. Ideal for central heating control (including different switching times for weekends). Battery back-up circuit. Includes box. 18 time settings.



- CT6000K £39.00
- XK 114, Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts £3.90
- 701 115 Additional Relays £1.65

## ELECTRONIC LOCK KIT

With hundreds of uses indoors, garages, car anti-theft devices, electronic equipment, etc. Only the correct easily changed four-digit code will open it! Requires a 5-15V DC supply. Output 750mA. Fits into standard electrical wall box. Complete kit (except front panel) £11.50

**XK 101** Electric Lock Mechanism for use with existing door locks and the above kit. (Requires relay.) 12V AC/DC coil. (701 150) £14.95

## HOME LIGHTING KITS

These kits are designed to replace a standard wall switch to control up to 300w of lighting



- TDR300K Remote Controlled Light Dimmer £14.95
- MK6 Transmitter for above £4.50
- TD300K Touch Dimmer £7.75
- TS300K Touch Switch £7.75
- TDE/K 2 way extension for above kits £2.50
- LD300K Rotary controlled Light Dimmer £3.95

## DISCO LIGHTING KITS

**DL1000K** This value-for money 4 way chaser features bi-directional sequence and dimming. 1kW per channel. £15.95

**DLZ1000K** A lower cost uni-directional version of the above. Zero switching to reduce interference. £8.95

**Optional opto input** allowing audio 'beat' light response (DLA:1) 70p

**DL3000K** 3-channel sound to light kit features zero voltage switching, automatic level control and built in microphone. 1kW per channel. £12.95

## DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (50°C to +150°C) reading 0.1°C. The kit has a sensitivity of 200mV for a full-scale leading automatic polarity and overload indication. Typical battery life of 2 years (PP3). £15.50

## PANTEC KITS


- PN2 FM Micro Transmitter £7.50
- PN3 Stabilised Power Supply £13.70
- PN5 2 x 10w Stereo Amplifier £14.50
- PN6 2 x 40w Stereo Amplifier £24.95
- PN7 Pushbutton Stereo Preamp £12.80
- PN8 Tone & Volume Control £13.60
- PN11 3w FM Transmitter £11.95
- PN13 Single Channel FM Transmitter £9.80
- PN14 Receiver for above £15.50

# ELECTRONICS

11-13 Boston Road  
London W7 3SJ

ORDERS 01-567 8910 ENQUIRIES 01-579 9794

01-579 2842 TECHNICAL AFTER 3pm

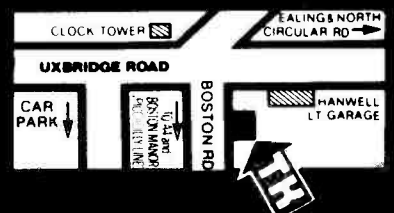


# TECH TIPS

## Auto-Repeat for the Cortex

V.F. Gray  
Purley


For less than 30 pence, a useful auto-repeat function can be added to the Cortex computer keyboard. There are so few components in the circuit that they can easily be soldered directly onto the back of the keyboard PCB.

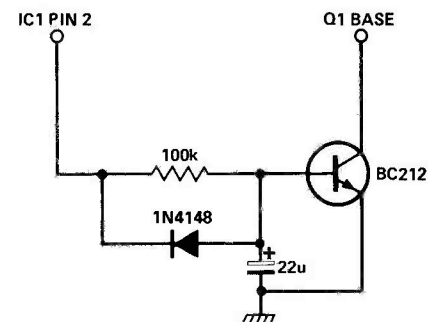When the keyboard encoder strobe signal goes high (key pressed) the 22u capacitor starts to charge via the 100k resistor. Eventually, if the key is still pressed, the BC182 will conduct sufficiently to simulate pressing the



Repeat key. When the key is released, the strobe goes low and the capacitor discharges via the 1N4148 diode and the BC182 stops conducting.

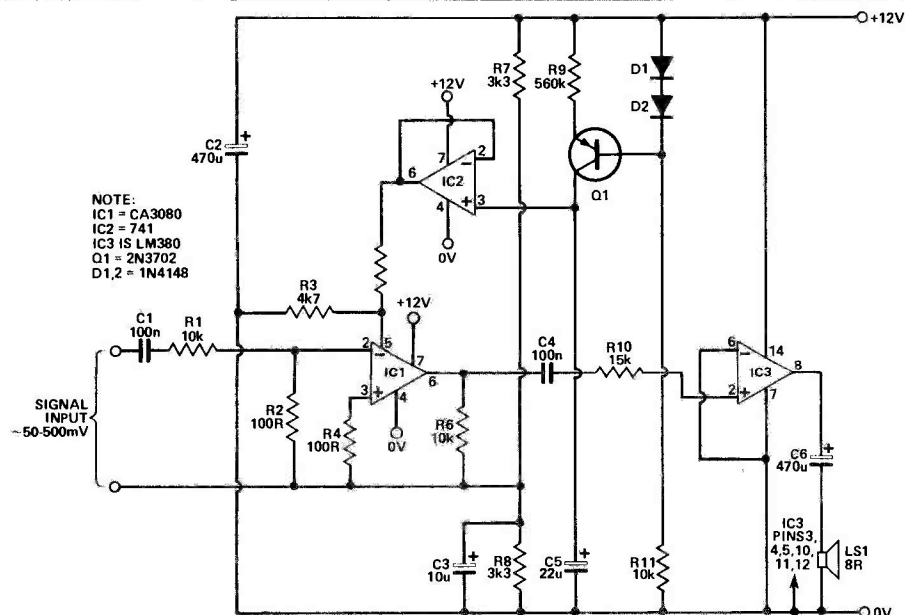With the component values shown, any character key which is held down for more than about half a second will start to automatically repeat.



## Crescendo Alarm

A.N. Collinson  
Doncaster

This circuit is designed for the benefit of those who find the start of the day a little too alarming. It can be coupled to an alarm clock or almost any other timing mechanism and produces an output which builds up from nothing to full volume. The sleeper is thus aroused by the very minimum volume necessary.

The input can be an oscillator or almost any other audio source (eg,


music from a radio-alarm). R1 and R2 provide attenuation and the signal is then fed to IC1, a transconductance amplifier whose gain is controlled by the current entering pin 5. Q1, D1, D2 and R11 provide a constant current of around 1uA which is used to charge capacitor C5. The constant current ensures that the voltage across C5 rises linearly, full charge being reached after about 3 or 4 minutes. This voltage is passed to IC1 via IC2 and R5, R3 being included to compensate for IC2's offset. The output of IC1 is coupled via R10 and C4 to the audio amplifier IC3 and then to the loudspeaker.

## Expanding Ex-OR Gates


L. Robertson  
Aberdeen

Exclusive-OR gates are only obtainable in 2-input packages, and simply cascading two gates does not give the correct truth table. Any application, therefore, which requires an Ex-OR gate with three or more inputs is going to involve some tricky logic combinations.


In the first circuit, inputs A and B are fed into gate 1 and the output of the gate is combined with input C at gate 2. This arrangement satisfies every part of the truth table except  $A = B = C = 1$ , where the output from gate 2 will be 1 instead of 0. To overcome this problem, inputs A and B are also fed to gate 3 so that, when both are high, the consequent high output from that gate will disable gate 4 and so produce a final output of 0.

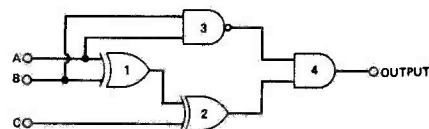

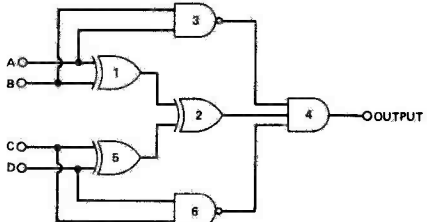If a four-input arrangement is required, the expansion can be achieved by treating inputs C and D in the same way as inputs A and B in the first circuit. Thus, in the second circuit, gate 5 performs a similar function to gate 1 and gate 6 behaves in the same way as gate 3.



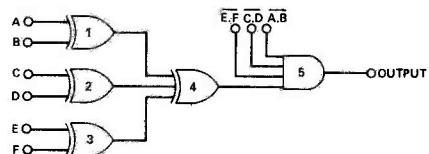The final permutation is a six-input gate, shown in simplified form in the third circuit diagram. The three-input Ex-OR gate shown as gate 4 is made up as shown in the first diagram above and the pairs of inputs AB, CD, EF are combined in three NAND gates and fed to three of the inputs of the final AND gate.






# Automatic Car Aerial

T. Williams  
Shoreham-by-Sea

This circuit, which is for use with negative earth cars, will automatically extend a motorised aerial when the radio is switched on and retract it when the radio is switched off.

The circuit requires two +12V connections, one from the car's electrical system via a suitable fuse and the other from the radio on/off switch. The ground connection can be made to the car body and the only other connections are those to the aerial motor.

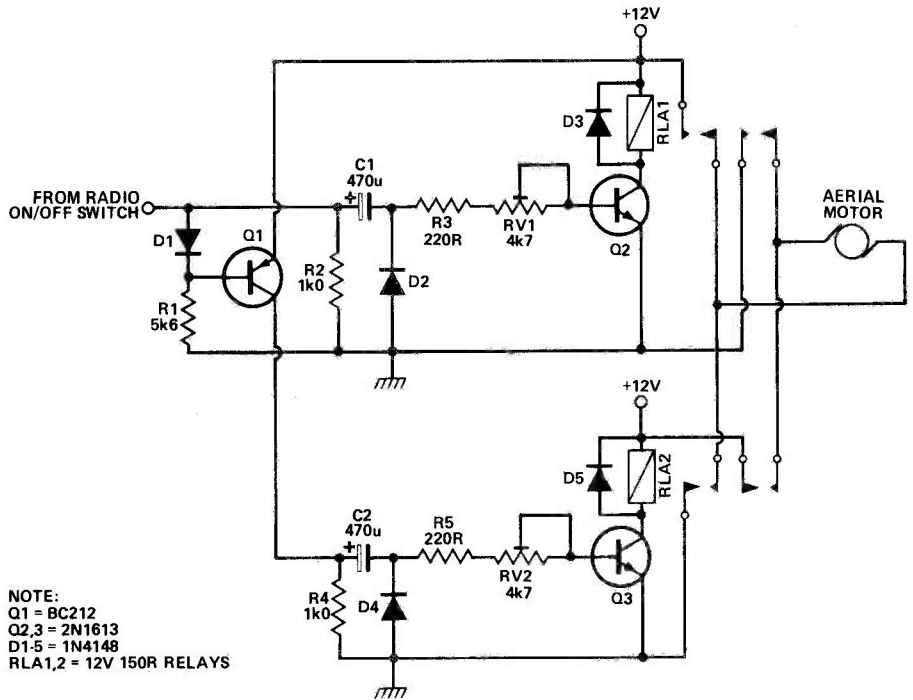Q1 is normally turned on. When the input from the radio on/off switch is applied, Q1 is turned off and current flows through C1, R3, RV1 and into the base of Q2. Q2 then turns on, energising relay RLA1 and thus extending the aerial. The period of time for which power is applied to the aerial motor can be



adjusted by RV1.

When the radio is switched off, Q1 is turned on again and current flows through C2, R5, RV2 and into

the base of Q3. Q3 then turns on, energising RLA2 and retracting the aerial. RV2 adjusts the period for which power is applied. **ETI**



DAMMIT REF, DONT ANY OF YOU KNOW ANYTHING?  
RED IS TWO, BLACK IS NOUGHT, YELLOW IS FOUR--!

# SKYBRIDGE LIMITED

**Mail Order & Shop:**  
**441 Princes Road**  
**Dartford**  
**Kent**  
**DA1 1RB**  
**Tel: (0322) 91454**

<b>CABLE</b>	470pF	15p	1000/83	75p
<b>PER METRE</b>	1000pF	11p	2200/10	39p
<b>Wire Wrapped 6p</b>	2200pF	11p	2200/16	46p
<b>Red/White/Black</b>	.01uF	5p	2200/25	55p
<b>Solid 1/8</b>	.022uF	5p	2200/35	74p
<b>11 Colours</b>	.047uF	8p	3300/25	74p
<b>Hook-up 7/2</b>	.1uF	8p	3300/35	92p
<b>11 Colours</b>	.47uF	15p	4700/10	59p
<b>Heavy Duty 32/2</b>	1uF	15p	4700/16	74p
<b>4 Colours</b>	22pF	13p	4700/25	103p
<b>TINNED COPPER</b>	47pF	8p	<b>NON-POLARISED</b>	
<b>per 4oz reel</b>	68pF	8p	1uF	25p
<b>SWG 16</b>	100pF	8p	2.2uF	25p
<b>SWG 18</b>	150pF	8p	3.3uF	25p
<b>SWG 20</b>	220pF	8p	4.7uF	25p
<b>SWG 22</b>	330pF	8p	6.8uF	50p
<b>SWG 24</b>	470pF	8p	10uF	25p
<b>EN COPPER</b>	560pF	8p	22uF	35p
<b>per 2oz Reel</b>	680pF	8p	33uF	40p
<b>SWG 14</b>	1000pF	8p	47uF	40p
<b>SWG 16</b>	1500pF	8p	100uF	70p
<b>SWG 18</b>	2200pF	8p	<b>THOUSANDS OF</b>	
<b>SWG 20</b>	3300pF	8p	<b>OTHER CAPACITORS</b>	
<b>SWG 22</b>	4700pF	8p	<b>IN STOCK LE</b>	
<b>SWG 24</b>	5600pF	10p	<b>SILVERED MICA</b>	
<b>SWG 26</b>	6800pF	10p	<b>1% POLYSTYRENE</b>	
<b>SWG 28</b>	.01uF	14p	<b>POLYCARBONATE</b>	
<b>SWG 30</b>	.022uF	19p	<b>MYLAR TANTALUM</b>	
<b>SWG 32</b>	.047uF	25p	<b>TRIMMER VARIABLE</b>	
<b>SWG 34</b>	.1uF	49p	<b>etc etc</b>	
<b>SWG 36</b>	<b>POLYESTER</b>		<b>CRYSTALS</b>	
<b>SWG 38</b>	.01uF	8p	100k	460p
<b>SWG 40</b>	.015uF	8p	1M	600p
<b>FIGURE 8</b>	.022uF	8p	2M	220p
<b>Per metre</b>	.033uF	9p	3.2768M	POA
<b>7/25</b>	.047uF	9p	4M	180p
<b>Coloured Ribbon</b>	.068uF	9p	4.19304M	320p
<b>Per Foot</b>	.1uF	9p	4.433819M	320p
<b>10 Way</b>	.15uF	15p	6.144M	130p
<b>20 Way</b>	.22uF	11p	10M	200p
<b>34 Way</b>	.33uF	16p	18.432M	270p
<b>MAINS</b>	.47uF	16p	26.54M	200p
<b>Per Metre</b>	.68uF	26p	26.59M	200p
<b>2 Core</b>	1uF	26p	26.64M	200p
<b>Oval 3A</b>	2.2uF	49p	26.69M	200p
<b>Round 6A</b>	<b>ELECTROLYTIC</b>		26.74M	200p
<b>3 Core</b>	uF/V		26.8M	200p
<b>Round 3A</b>	1/63	8p	26.995M	200p
<b>Round 6A</b>	2/250	9p	27.045M	200p
<b>Round 13A</b>	4.7/63	9p	27.095M	200p
<b>POWER</b>	10/16	8p	27.145M	200p
<b>1mm T&amp;E</b>	10/25	8p	27.195M	200p
<b>1.5mm T&amp;E</b>	10/35	10p	27.245M	200p
<b>2.5mm T&amp;E</b>	10/63	13p	27.255M	200p
<b>6mm T&amp;E</b>	22/10	8p	<b>CONNECTORS</b>	
<b>TV Coax</b>	22/16	10p	Cros Clips	10p
<b>SCREENED</b>	22/25	10p	Terminal Post	40p
<b>Single Round</b>	22/35	11p	1mm Plug	20p
<b>Twin Round</b>	22/63	15p	1mm Socket	15p
<b>Figure 8 Min</b>	47/10	10p	2mm Plug	20p
<b>Figure 8 Std</b>	47/16	13p	2mm Socket	15p
<b>4 Core</b>	47/25	15p	3mm Plug	20p
<b>SPIRAL WRAP</b>	47/35	24p	3mm Socket	15p
<b>1/8"</b>	47/63	25p	4mm Plug	15p
<b>1/4"</b>	100/10	11p	4mm Socket	15p
<b>1/2"</b>	100/16	13p	Phono Plug	11p
<b>WIDE RANGE OF</b>	100/25	15p	Phono Link Skt	20p
<b>CABLE MARKERS</b>	100/35	19p	Jack Plug 2.5mm	15p
<b>SLEEVING TIES</b>	100/63	25p	Jack Plug 3.5mm	15p
<b>FIXINGS IN</b>	220/16	15p	Jack Skt 2.5mm	15p
<b>STOCK - PHONE</b>	220/25	20p	Jack Skt 3.5mm	15p
<b>FOR DETAILS</b>	220/35	23p	Jack Skt Line 2.5mm	25p
	220/63	33p	Jack Skt Line 3.5mm	25p
	470/16	23p	Jack Plug 1/4" Mono	20p
	470/25	27p	Jack Plug 1/4" Stereo	30p
	470/35	31p	Jack Skt 1/4" Mono	25p
	470/63	48p	Jack Skt 1/4" Stereo	35p
	1000/10	24p	Jack Skt Line Mono	25p
	1000/16	29p	Jack Skt Line Stereo	30p
	1000/25	41p	Coax Plug	15p
	1000/35	45p		

Coax Skt Surf	30p	LED WP Std	3p
Coax Skt Flush	25p	Min	3p
Coax Line Skt	45p	<b>LARGE RANGE OF</b>	
Coax Coupler	45p	<b>PANEL LAMPHOLDERS</b>	
Car Aerial Plug	15p	<b>DE LUXE LED's</b>	
FM Aerial Plug	20p	<b>etc etc</b>	
NC Plug	100p	<b>FUSEWARE</b>	
BNC Round Skt	100p	20mm Panel Holder	45p
BNC Square Skt	100p	1 1/4" Panel Holder	59p
BNC Free Skt	110p	20mm Chassis Holder	14p
BNC Str. Adapt	140p	1 1/2" Chassis Holder	17p
BNC T Adapt	300p	Lin Holder	14p
VHF Plug PL259	50p	Fuse Clips	3p
VHF Plug PL259	50p	20mm FUSES	
Small Reducer	20p	100mA 150mA 250mA	
Large Reducer	20p	500mA 1A 1.5A 2A	
PL259 Rt Ang	90p	3A 5A	9p
VHF Round Skt	50p	20mm Antisurge Fuses	
VHF Square Skt	50p	500mA 1A 2A	12p
Elbow Adapt	POA	1 1/2" FUSES	
Straight Adapt	60p	100mA 150mA 250mA	
UHF T Adapt	160p	500mA 1A 2A 3A	
Female T Adapt	180p	5A 10A 13A 15A	9p
XLR Line Plug	180p	1" Fuses 2.3, 5, 13A 15p	
XLR Chassis Skt	330p	<b>RESISTORS</b>	
XLR Line Skt	230p	1/2W 5% E24	2p
XLR Chassis Plug	160p	.4W 1% E24	7p
DIN Plugs 2 pin	10p	1W 5% E12	10p
3 pin	15p	3W 5% E12	10p
4 pin	35p	3W WW R22-1R	30p
5 pin A	15p	3W WW 2R2+	20p
5 pin B	20p	7W WW	30p
6 pin	20p	10W WW	35p
7 pin	20p	25W WW	170p
8 pin	60p	WW Pots 3W	
DIN Sks 2 pin	10p	High Quality	275p
3 pin	20p	10R 25R 50R 100R	
4 pin	15p	250R 500R 1K 5K	
5 pin A	15p	10K 50K	
5 pin B	20p	<b>SEMICONDUCTORS</b>	
6 pin	20p	<b>SO EXTENSIVE</b>	
7 pin	20p	<b>IS THE RANGE</b>	
DIN Line Skt 2 pin	15p	<b>OF LISTED</b>	
5 pin	30p	<b>SEMICONDUCTORS</b>	
D-Type Plug 9W	80p	<b>PLEASE SEND</b>	
15W	150p	<b>LARGE S.A.E</b>	
25W	150p	<b>FOR DETAILS</b>	
DType RtAng Skt 9W	POA	<b>TRANSISTOR MOUNTS</b>	
15W	POA	TO3	10p
25W	POA	TO66	10p
Plug 9W	POA	<b>DIL SOCKETS</b>	
15W	POA	8 pin	9p
25W	POA	14 pin	11p
Covers 9	120p	16 pin	12p
15	120p	18 pin	16p
25	130p	20 pin	17p
Latches 9	30p	22 pin	20p
15	50p	24 pin	21p
25	60p	28 pin	24p
Power Plug 2.1mm 15p		40 pin	35p
2.5mm	15p	<b>RANGE OF HEAT</b>	
IEC Line Skt	95p	<b>SINKS AVAILABLE</b>	
IEC Chassis Plug	90p	<b>PHONE FOR QUOTATION</b>	
IEC Chassis Skt	90p	<b>SPEAKERS</b>	
IEC Line Plug	70p	Miniature Buzzer	
Bulgin P429	50p	6V or 12V	90p
P646	185p	Ultrasonic	600p
P430	125p	Transducers	Pair
P649	135p	Elliptical 5" x 3"	199p
P650	110p	6" x 4"	262p
P635	100p	7" x 5"	314p
P636	100p	7" x 5"	338p
P551	300p	8" x 5" 5W	386p
P552	100p	8" x 5" 8W	521p
SA2403	180p	9" x 6"	431p
SA2404	95p	Miniature 1"	90p
SA2190	50p	1 1/4"	90p
SA1862	50p	1 1/2"	90p
SA2111	200p	2"	90p
SA2019A	150p	2 1/2" 8R	90p
SA2020	140p	2 1/2" 64R	100p
SA2367	180p	Round 5" 4W	174p
SA2368	95p	5" 25W	409p
		5" 60W	1587p
		5 1/2" 10W	476p
		5 1/2" 15W	771p
		6" 5W	297p
		6" 5W	297p
		6" 60W	1632p
		6 1/2" 7W	423p
		8" 6W	359p
		8" 10W	423p
		8" 20W	963p
		8" 60W	1346p
		10" 10W	700p
		10" 20W	1113p
		10" 30W	POA

12" 60W	2862p
12" 100W	4073p
12" 150W	4336p
15" 150W	7185p
15" 200W	8735p
18" 200W	8108p
<b>MOTOROLA PIEZO</b>	
<b>TWEETERS</b>	
2"	231p
3 1/2"	897p
2" x 6" Horn	938p
2" x 5"	795p
2 1/2"	457p
3 3/4"	824p
4" x 10"	1435p
<b>CROSSOVERS</b>	
2 Way 15W	188p
2 Way 100W	690p
3 Way 25W	193p
3 Way 40W	338p
3 Way 60W	502p
4 Way 80W	628p
<b>SWITCHES</b>	
Toggle Std SPST	47p
DPDT	62p
Min SPST	68p
SPDT	70p
SPDT c/off	83p
DPDT	85p
DPDT c/off	117p
4PDT	209p
4PDT c/off	244p
Push to make	20p
Push to break	20p
Key 5W SPST	259p
Rotary IPI2W	62p
2P6W	62p
3P4W	62p
4P3W	62p
Slide Min DPDT	22p
Std DPDT	22p
DIP 4W	105p
6W	128p
8W	1156p
10W	184p
Microswitch	83p
<b>TRANSFORMERS</b>	
6-0-6 @ 100mA	187p
6-0-6 @ 250mA	185p
9-0-9 @ 100mA	167p
9-0-9 @ 250mA	185p
12-0-12 @ 50mA	155p
12-0-12 @ 100mA	171p
12-0-12 @ 250mA	188p
0-12/0-12 @ 500mA	369p
9-0-9 @ 1A	283p
12-0-12 @ 1A	538p
0-12-15-20-24-30 @ 1A	
	666p
6-0-6 @ 2A	440p
9-0-9 @ 2A	478p
12-0-12 @ 2A	538p
0-12/0-12 @ 2A	538p
0-12-15-20-24-30 @ 2A	
	900p
90-0-20 @ 2A	745p
30-0-30 @ 2A	933p
12-0-12 @ 3A	721p
0-15 @ 3A	847p
6-0-6 @ 4A	538p
9-0-9 @ 4A	687p
12-0-12 @ 4A	845p
0-15 @ 6A	949p
6-0-6 @ 8A	980p
12-0-12 @ 8A	1615p
<b>TOROIDS:</b>	
30VA 6V	950p
9V	950p
12V	950p
15V	950p
18V	950p
50VA 6V	1150p
9V	1150p
12V	1150p
15V	1150p
80VA 18V	1200p
22V	1200p
30V	1200p
120VA 30V	1300p
160VA 35V	1500p
300VA 35V	2000p
500VA 35V	2650p

ALL TOROIDS HAVE  
 TWO ISOLATED  
 SECONDARIES AT  
 VOLTAGES SHOWN.

## ORDERING INFORMATION:

P/P 50p on orders less than £

# PARAGRAPH EQUALISER

Barry Porter describes a project guaranteed to raise the blood pressure of members of the anti tone-control brigade — a ten band equaliser with parametric control of frequency and Q.

Graphic equalisers are to be found in almost every audio environment, particularly in the sound reinforcement and public address arenas. Recording studios use them in a vain attempt to make their monitors sound like loudspeakers, and they may be seen lurking amongst the megawatt amplification systems that many pop groups use as an alternative to talent, where they enable the last drop of output level to be extracted before acoustic feedback gets the upper hand and sends twenty tons of hardware and half a dozen superstars into lunar orbit.

Most graphic equalisers consist of a number of small, slider potentiometers arranged so that the positions of their control knobs give an indication of the frequency response setting of the unit. Another type of equaliser, often found as part of the input channels of large studio mixing consoles, is the Parametric. This is an equaliser in which the three main parameters, amplitude, frequency and Q, are continuously variable.

The Paragraph is a combination of both equaliser types. Although it resembles a graphic equaliser, each slider is accompanied by two rotary

controls that allow the frequency and Q of the particular band to be adjusted. As a consequence, an almost infinite number of frequency response variations can be obtained, making the unit far more versatile than other types of equaliser. The circuitry of the ParaGraph is quite elaborate, yet its performance is well up to professional studio standards which means that it is vastly superior to a fair percentage of the esoteric megabuck hi-fi equipment that gets drooled over in certain circles.

A block diagram of the ParaGraph is shown in Fig. 1, and it will be seen that the input and output stages are electronically balanced to simplify connection to professional equipment. As the unit may be used in the tape loop of a hi-fi pre-amplifier, provision is made for a tape output and return, the output capable of being selected to pre or post the equalisation stage so that either a flat or an equalised signal can be recorded. The input level control is arranged so that in its central position the unit is operating at unity gain, with 10dB of gain or attenuation available at the limits of the control.

## Principle Of Operation

The usual method of obtaining band pass and stop characteristics is shown in Fig. 2, where an LC filter is used to shunt the input or feedback signal of a differential amplifier. This arrangement works extremely well but does not allow the centre frequency or Q to be easily adjusted, an essential requirement if you want total freedom over the response variations that can be achieved.

In the ParaGraph, active circuitry is used as the response shaping element in the form of State Variable filters. One of these is shown in Fig. 3, and consists of two matched integrators and a summing stage. The output of IC2 has a bandpass characteristic with unity gain at the resonant frequency ( $f_0$ ), which is decided by the input resistors and integration capacitors of IC2 and IC3 by

$$f_0 = \frac{1}{2 R_1 C}$$

The bandpass Q may be independently adjusted by the input and feedback resistors RQ1 and RQ2, the value being

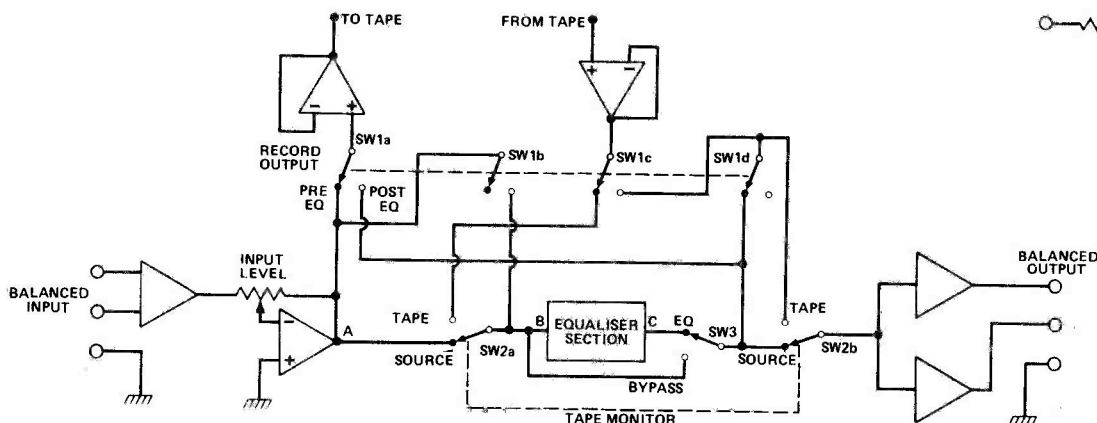


Fig. 1 Block Diagram of the complete ParaGraph equaliser.

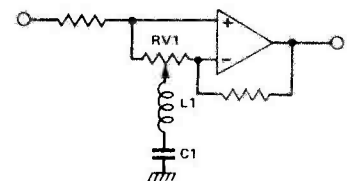


Fig. 2 An example of the type of filter element used in many graphic equalisers.



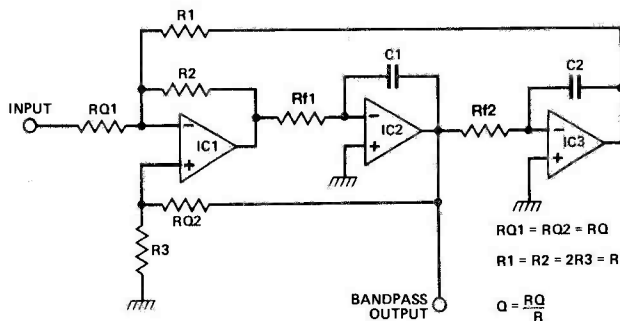


Fig. 3 A state variable filter of the type used in the ParaGraph.

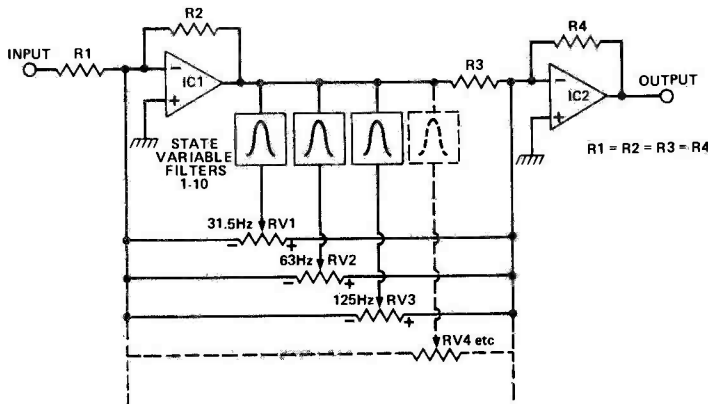


Fig. 4 The amplitude control system used in the ParaGraph.

$$Q = \frac{RQ}{R}$$

The range of each Q control is from 0.5 to 5.5, which in practice has been found to be ideal.

The method of obtaining lift and cut is shown in Fig. 4. The main signal path is through the two inverting stages, IC1 and IC2. The output of IC1 drives the state variable filters, and it can be seen that in the cut position of any of the control potentiometers, the associated filter is placed in the negative feedback loop of IC1. In the lift position R3, the input resistor of IC2, is bypassed by the output of the bandpass filter. This control system is extremely symmetrical so that the lift and cut response curves are virtually identical, and as the outputs of the filters are added to the main signal path at summing points there is no interaction between individual controls when several filter stages are used.

The ParaGraph contains ten stages with octave spacing between them, the nominal operating frequencies being 31.5Hz, 63Hz, 125Hz, 250Hz, 500Hz, 1kHz, 2kHz, 4kHz, 8kHz and 16kHz. The frequency adjustment range of each

band was rather difficult to decide. It would have been nice to have given each band a range of two octaves, making for example, the 1kHz control sweep from 500Hz to 2kHz. Although this is possible, it results in a situation where the 1kHz position of the control is not central, which could cause operational problems. The potentiometer law necessary to give a completely linear frequency sweep is so obscure (a kind of reverse semi-logarithmic) that a compromise was arrived at. This uses

linear controls, and the circuit values are arranged so that the central position gives the required frequency and the range is from approximately three-quarters of an octave below that frequency to one octave above.

## The Circuit

The ParaGraph input stage circuitry is shown in Fig. 5. The RF rejection filter formed by R1, R2, and C1 and C2 has its -3dB point at 88.4kHz, and the network around IC1a gives a balanced input with unity gain. Under normal circumstances, the input may be DC coupled as it will usually be driven by a balancing transformer or an AC coupled output stage, but if there is any danger of DC voltages reaching the input a 10uF capacitor should be placed in series with both R1 and R2. If the unit is to be used exclusively with unbalanced equipment, the input stage may be modified by omitting R1, R3 and C1 and changing R4 to 1kΩ, R5 to 100kΩ and R6 to 10R.

Following the balanced input is a gain adjustment stage, IC1b, which allows the overall gain of the system to be changed from unity by plus or minus 10dB. This should be sufficient to cope with most requirements, but the swing can be increased to 20dB by reducing the value of R7 and R8 to 1kΩ. It will be noted that the track and wiper of RV1 are not isolated from the DC conditions of IC1, and noise may be generated every time the control is adjusted. In practice this is unlikely to cause problems because, once the system gain has been set, it will normally remain untouched while the ParaGraph is in use.

The output of IC1b is AC coupled by C3 and C4 so that clicks are not

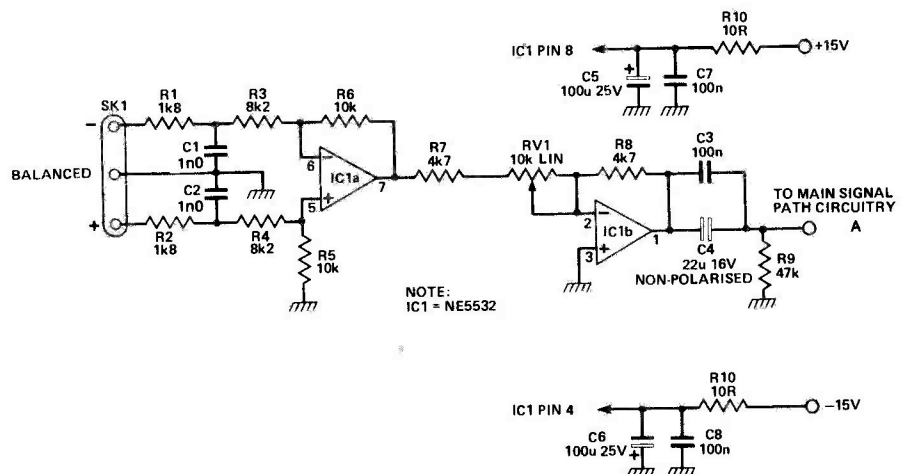


Fig. 5 Circuit diagram of the ParaGraph input stage.

generated by the switches that follow. If you are wondering why the two capacitors are connected in parallel, you are obviously out of touch with current thinking and manufacturing practice. It has been shown that the use of normal electrolytic capacitors in the signal path of high quality audio equipment can cause significant degradation of the signal, sufficient to be quite audible in most cases. The use of special non-polarized electrolytics cures most of the problems but they can cause the high frequency end of the audio spectrum to sound slightly rough. This effect is cured by the addition of a small value bypass capacitor which employs polycarbonate or polypropylene in its construction.

As there may be the odd soul who is brave enough to insert the ParaGraph into his or her hi-fi system (sing three choruses of "The emotion went up the chimney when my response got equalised" to the tune of Beethovens' 9th) provision has been made for the connection of a tape recorder and the monitoring of its output.

With SW1 in the Pre EQ position as shown in Fig. 1, the tape output will be unequalised whereas the main signal and the tape return (when selected by SW2) will pass through the equalisation stage. When SW1 is switched to Post EQ, the tape output originates after the equaliser (except when the Bypass switch, SW3, is operated) so that any response corrections may be applied to the recorded signal. In this situation, the main signal will also be equalised but the tape return will not, so a valid comparison between the recorder input and output can be made by operating SW2.

Both tape input and output signals are buffered from the main signal path so that the operation and performance of the ParaGraph cannot be affected by external equipment. These buffer stages are shown in Figure 6.

The main signal path summing stages are shown in Fig. 7 and hardly need an explanation, other than to note that as the overall signal phase is non-inverting, the section may be bypassed by a simple, single pole switch as shown in Fig. 1.

The ten state variable filters are identical except for the values of the integration capacitors. The filter circuit is shown in Fig. 8, and Table 1 lists the capacitor values and frequency control calibration points.

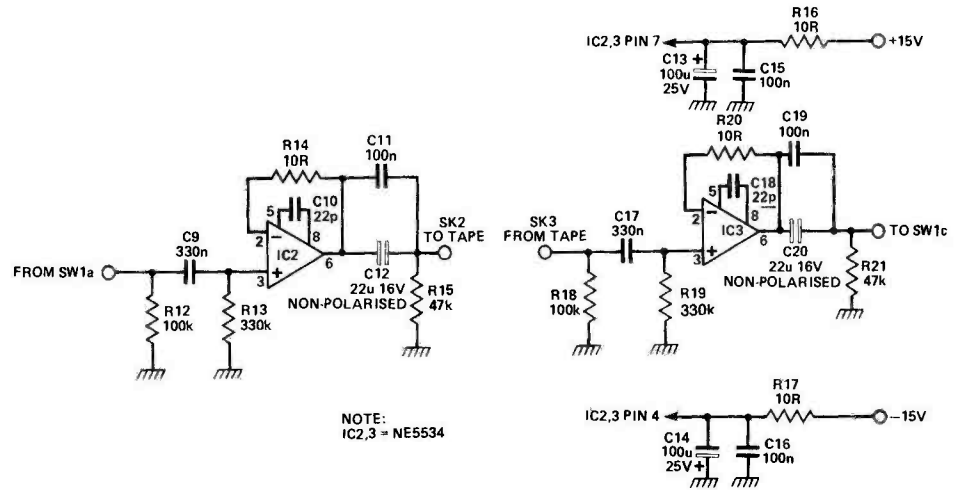


Fig. 6 Circuit diagram of the tape buffers.

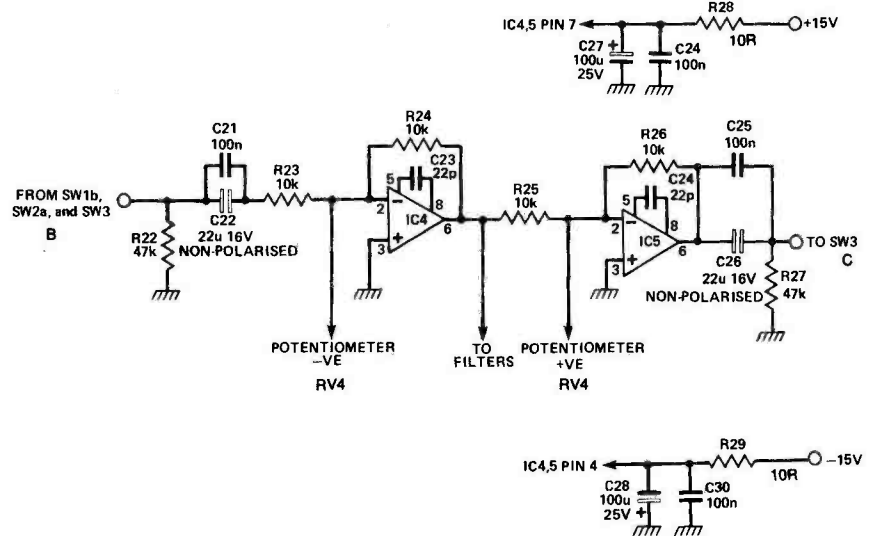


Fig. 7 Circuit diagram of the main signal path.

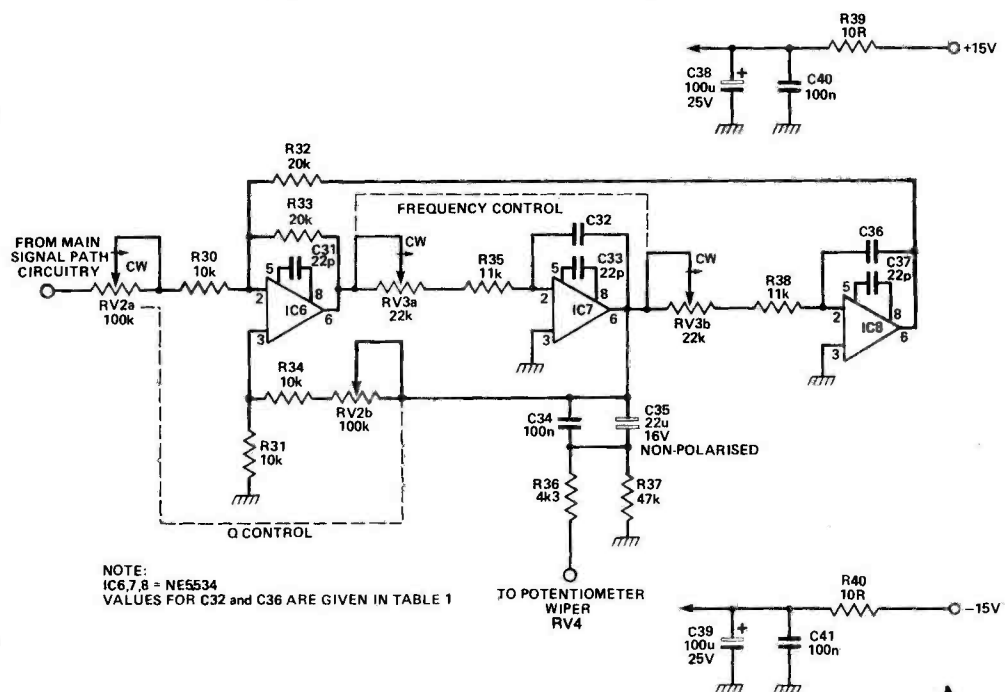


Fig. 8 Circuit diagram of the state variable filters.

# PROJECT : Equaliser

## CAPACITOR VALUES

220n//10n//390p  
 100n//15n//220p  
 47n//10n//330p//220p  
 22n//6n8  
 10n//2n2//2n2  
 3n6//3n6  
 3n6  
 1n8  
 680p//220p  
 220p//220p//10p

## RESULTANT FREQUENCY (Hz) AT:

A	B	C	D	E
20	25	31.5	42	63
42	50	63	84	125
84	100	125	170	250
170	200	250	335	500
335	400	500	670	1k
670	800	1k	1k3	2k
1k3	1k6	2k	2k7	4k
2k7	3k2	4k	5k4	8k
5k4	6k4	8k	10k7	16k
10k7	12k8	16k	21k4	32k

Table 1. Values for C32 and C36, the frequency-determining capacitors on the filter board. Close-tolerance polystyrene or polycarbonate types should be used throughout.

Both the frequency and Q adjustments may be re-calculated to give different ranges to those suggested. It is not recommended that Q values above 10 are used, but the number of bands may be increased or decreased to suit individual requirements. However, the suggested configuration would seem to offer the best compromise between over simplification and operational and constructional over-complexity.


The amount of available lift and cut is controlled by R36 (Fig. 8), the value shown giving a maximum of 10.4dB. A different value may be substituted, the resulting amplitude extremes being given by

$$A(\text{dB}) = 20 \log \left[ \frac{1}{R7} (10 + R7) \right]$$

The ParaGraph uses the balanced output stage shown in Figure 9. Rather than repeat the operating principles of this circuit and of balanced connections in general, interested readers who are still awake are referred to the brief description that was given on Page 57 of the January '84 issue of ETI.

ETI

To be completed.

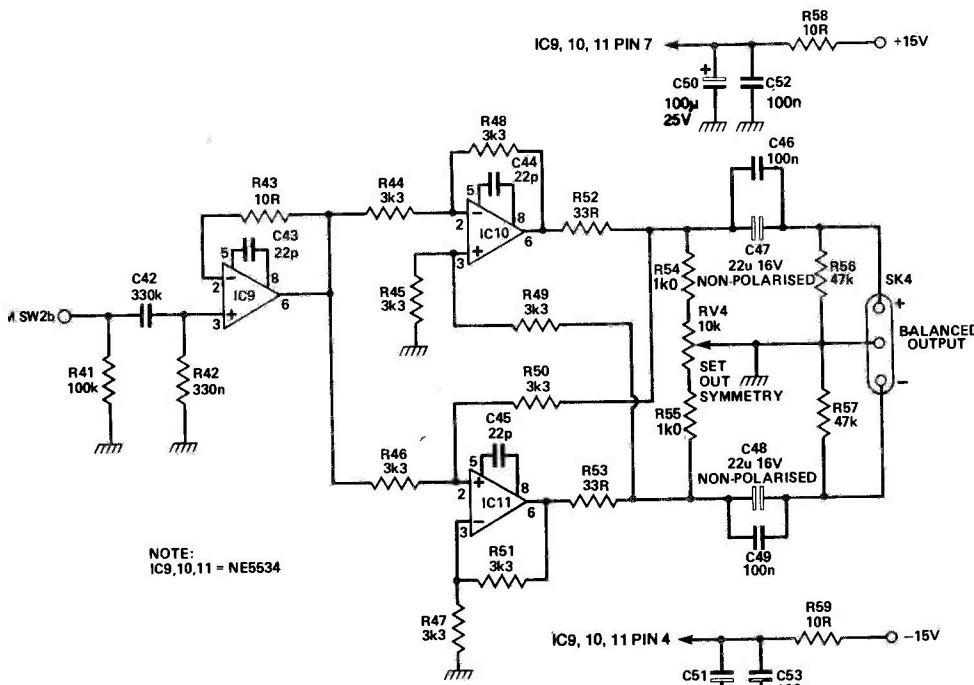

NOTE:  
 IC9,10,11 - NE5534

Fig. 9 Circuit diagram of the balanced output stage.



## BUYLINES

Radial non-polarised electrolytics are not readily available to the amateur but axial 50v types are sold by Maplin, Circuit and Electrovalue and should fit into the space if stood on end. The polystyrene or polycarbonate capacitors used for C32 and C36 should ideally be 1% tolerance types, but if you use 5% types instead you should omit some of the smallest capacitors from the parallel combinations listed in Table 1: there is little point in using either the 330p or the 220p in parallel with 5% tolerance 47n and 10n capacitors, for example, because the tolerance on the larger capacitors considerably exceeds the value of the smaller ones. Maplin stock a range of 1% tolerance polystyrene capacitors which covers some of the values needed, and it is perfectly permissible to use 5% small value capacitors in parallel with 1% tolerance large values. Watford, Rapid, Cricklewood and Technomatic are among those who stock both the NE5532 and the NE5534 and 4-pole double-throw switches suitable for use in the SW1 position are available from most of the above companies and a large number of other advertisers. 1% tolerance metal film resistors are also widely available and Newrad or West Hyde Developments ought to be able to help you with 19" rack-mounting cases. The PC mounting potentiometers are sold by Cirkit and the PCBs are available from our PCB service.



# T.V. SOUND TUNER


**SERIES II BUILT AND TESTED** Complete with case. £26.50 + £2.00 p&p.

TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10 1/2" x 7 1/2" x 2 1/2". E.T.I. kit version of above without chassis, case and hardware £16.20 plus £1.50 p&p.




Also available with built-in headphone amp. ONLY £32.50 + £2.00 p&p. It can also be used in conjunction with your video recorder. Dimensions: 10 1/2" x 7 1/2" x 2 1/2". E.T.I. kit version of above without chassis, case and hardware £16.20 plus £1.50 p&p.

## HI-FI SPEAKER BARGAINS

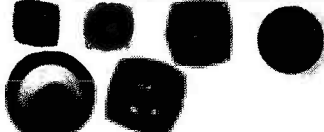

**TOKUDEN** - 8" 8 ohm full range 7 1/2W twin cone speaker. £3.50 + £1.10 p&p  
**GOODMANS** - 7" 60W Bass/Mid. speaker. 8 ohm impedance, Freq. res. 40 - 6,000 Hz. 4 1/2" x 1/2" magnet. £14.95 + £1.75 p&p.  
 With rolled surround. £4.95 + £1.50 p&p  
**Tweeters** - 8 ohm soft dome radiator type. (3 1/2" sq.) For use in systems up to 40 watts. £3.95 each + £1 p&p or £8.95 pr. + £1.50 p&p  
**EAGLE** - Full range 8" 20W, 8ohm, Twin cone with rolled surround. £5.95 + £2.20 p&p. Full range 6 1/2" 15W, Bohm. Twin cone with rolled surround. £5.95 + £2.20 p&p. Full range 4" 8W, 8 ohm With rolled surround. £4.95 + £1.50 p&p.

## PE STEREO CASSETTE RECORDER KIT

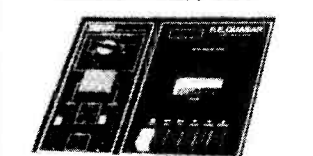

Noise Reduction System  
 Auto Stop Tape Counter Switchable E.O.  
 Independent Level Controls Twin V.U. Meter Wow & Flutter 0.1% Record/Playback I.C. with Electronic Switching Fully Variable Recording Bias for Accurate Matching of all Tapes. - Metal, Chrome Dioxide, etc.  
 Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts i.e. semiconductors, resistors capacitors, hardware top cover, printed scale and mains transformer. You only supply solder and hook-up wire.  
 Featured in April issue P.E. Reprint 50p Free with kit. Special offer prices NOW ONLY £29.95

## 125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PCB board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

Accessories: Stereo mains power supply kit with trans. £10.50 + £2 p&p. Mono: £7.50 + £2 p&p.



**SPECIFICATIONS:**  
 Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

KIT £12.00 + £1.15 p&p. BUILT £17.50 + £1.15 p&p.

## STOCK CLEARANCE (Trade enquiries welcome)

IC regulated P.S.U. utilising (Motorola MC 7818 CT)  
 All components inc. mains transformer are mounted on a 4" x 2 1/2" P.C.B. Input 220/240 AC, output 18V DC @ 350mA. Very low ripple & short-circuit protected. Ready built £2.75p + .50p P&p.  
 Miniature main transformers. sec: 6 - 0 - 6 V @ 4 VA PR1: 220/240V 4 for £2.50p + .50p P&p.  
 6V mains adaptor  
 13 amp plug-in type Flying lead output with 2.1 mm female plug. Max. output 150mA D.C.  
 £2.00p + .50p P&p.  
 Stabilised 9V mains adaptor Fully encapsulated with flying mains & output leads. Max. output: 200mA D.C. Size 2 1/2" x 2 1/2" x 2 1/2" approx. £2.40p + .50p P&p.  
 P.C.B. copper laminate: Single sided 16" x 14" - 1/16" thick. £1.30p + .50p P&p.  
 Ready built Audio modules by MULLARD LP 1183 Stereo preamp module suitable for ceramic p.u., radio/aux. inputs. Direct tag-out connections to bass, treble & level controls. Supply 18-24V D.C. P.C.B. size 3 1/2" x 3 1/2". £1.00p + .50p P&p.  
 LP 1184 as above, but with magnetic p.u. input. Size 4 1/2" x 4 1/2" approx. £1.50p + .50p P&p.  
 LP 1173 10W into 4 ohm Discrete power amp module. Supply 24V D.C. Size 4 1/2" x 2 1/2" x 1" £2.95p + .50p P&p.  
 2N3055 FERRANTI Power Transistors 4 for £1.25p + .50p P&p.  
 TBA 800 SGS/ATES 7 watt audio IC 2 for £1.00p + .20p P&p.  
 SONOTONE KS40e/3509 Stereo Ceramic Cartridge. £2.95p + .50p P&p.

**PAIR 10W SPEAKERS**  
 Incorporates 4 1/2" 10 watt speaker. Finished in teak veneer simulate. Built, ready to use. Ideal extension spkrs. 12 1/2" x 7 1/2" x 4 1/4" ins. £14.95 + £1.75 p&p.

## STEREO TUNER KIT

**SPECIAL OFFER!**  
 £13.95 + £2.50 p&p.

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with PE (July 81) For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. Front scale size 10 1/2" x 2 1/2" approx. With diagram and instructions.

## MONO MIXER AMP

Ideal for halls and clubs.  
 £45.00 + £2 p&p.  
 50 Watt, six individually mixed inputs for 2 pickups (Cer. or mag), 2 moving coil microphones and 2 auxiliary for tape tuner, organs etc. Eight slider controls - 6 for level and 2 for master bass and treble, 4 extra treble controls for mic. and aux. inputs. Size: 13 1/2" x 6 1/2" x 3 1/2" approx. Power output 50 W RMS (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

CALLERS TO: 323 EDGWARE ROAD, LONDON W2. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include VAT.



All mail to: 21E HIGH ST, ACTON W3 6NG  
 Callers: Mon - Sat 9.30 - 5.30. Half day Wed.  
 ACCESS phone orders on 01-892 8430.  
 Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 31/9/84 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

# ANNOUNCING

THE DIGISOUND VOICE CARD



## SOON TO BE FEATURED IN ELECTRONICS AND MUSIC MAKER

The Digisound Voice Card is based on the popular range of custom-designed integrated circuits from Curtis Electromusic Specialities which are currently used as the basis of many of today's most popular synthesisers.

On-board design includes two VCOs, a four pole low pass VCF, two ADSR envelope generators and five VCAs which together compromise an elaborate synthesiser voice.

The Voice Card can be used very effectively as a stand-alone unit and with the addition of a keyboard and related circuitry a "complete" monophonic synthesiser is available. The use of several Voice Cards together could form the basis of an exceptional polyphonic system with the possibility of each voice under independent control if desired. The Voice Card is also fully compatible with the extensive range of modules which make up the Digisound 80 Modular Synthesiser.

The Voice Card is available in kit form or ready built.

The fully inclusive kit prices are:-

- A) PCB and all board components **£74.40**
- B) Set of 18 control pots and 16 control switches **£21.05**
- C) 9 x 9 inch front panel and PCB mounting kit **£17.20**

The PCB is double-sided and very compact. For people who would prefer not to build their own, the Voice Card may be purchased ready built and fully tested. The fully inclusive price is:-

- D) Ready-built Voice Card (Kits A, B & C plus 18 K8 knobs and 20 3.5mm jack sockets) **£178.25**

To order or for further details and our latest price list, contact us at -  
**14/16 QUEEN ST, BLACKPOOL, LANCS, FY1 1PQ.**  
**Tel: (0253) 28900**

# Looking for Components?

DEALERS ENQUIRIES WELCOME

A small selection of our stock:

74LS Series		74LS373 100p		74 Series	
74LS00	28p	74LS374	40p	7400	30p
74LS01	23p	74LS376	31p	7406	40p
74LS02	28p	74LS392	60p	7407	125p
74LS03	22p	74LS109	43p	7412	30p
74LS04	28p	74LS112	45p	7432	36p
74LS05	27p	74LS113	45p	7486	42p
74LS08	29p	74LS123	90p	74121	55p
74LS10	28p	74LS126	50p	<b>CMOS</b>	
74LS11	28p	74LS132	65p	4001	24p
74LS13	34p	74LS138	60p	4013	36p
74LS14	28p	74LS151	70p	4016	24p
74LS15	28p	74LS157	58p	4017	55p
74LS16	28p	74LS163	75p	4019	54p
74LS17	28p	74LS164	75p	4020	80p
74LS18	28p	74LS165	110p	4022	20p
74LS19	28p	74LS166	110p	4027	75p
74LS20	28p	74LS181	128p	4042	50p
74LS21	28p	74LS192	90p	4047	40p
74LS22	28p	74LS193	90p	4049	36p
74LS27	28p	74LS240	90p	4060	68p
74LS30	28p	74LS241	90p	4069	24p
74LS32	28p	74LS244	90p	4070	24p
74LS38	28p	74LS257	70p	4078	25p
74LS42	55p	74LS273	125p	4093	35p
74LS48	90p	74LS367	52p	4099	90p

(exc. VAT)

We stock a full range of 74LS series, and memory and microprocessors. Ring for our FREE catalogue and special quotation.

## Cambridge Microcomputer Centre

153-4 East Road, Cambridge CB1 1DD  
 Telephone (0223) 355404 Telex 817445



Prices correct at time of going to press

# Component

# MINI FILE

**For**  
Electronic and  
other small parts.  
A large variety of  
components can easily  
be kept well organized.  
60 storage pockets per  
unit.

**Unit size:**  
L400 W125 H77mm.

**Material:** Injection-moulded in  
impact resistant polystyrene.  
4 and 6 Drawer Steel cabinets  
available.

The 6 Drawer cabinet, practical for  
field service, has lock and carrying handle.

Recommended prices (excluding V.A.T.):

6 drawer cabinet with lock and handle	£92.00
4 drawer cabinet with lock and handle	£59.00
Single drawer	£11.00

**Typical Minifile applications:**

R & D Departments      Prototype Kits  
Production Test & Rework Service Departments  
Field Service Engineers      The Electronic Hobbyist  
Repair kits for computers      CNC machines.

**Stocked by:**

Bradley Marshall, 325 Edgware Road, London W2 1BN. Tel: 01-723 4242  
Enfield Electronics, 208 Baker Street, Enfield, Middlesex EN1 3JY. Tel: 01-366 1873  
Henry's, 404-406 Edgware Road, London W2. Tel: 01-724 0323  
TK Electronics, 11-13 Boston Road, London W7 3SJ. Tel: 01-579 9794  
Watford Electronics, 33/34 Cardiff Road, Watford, Herts. Tel: (0923) 40588.



## hobbyboard

### Printed Circuit Hardware & Component Catalogue

- ★ COPPER CLAD LAMINATES
- ★ PHOTO-RESIST LAMINATE & CHEMICALS
- ★ PRINTED CIRCUIT DRAUGHTING AIDS
- ★ VERO BOARD & PROTOTYPING SYSTEMS
- ★ CONNECTORS / CASES / GENERAL HARDWARE
- ★ SELECTION OF COMPONENTS
- ★ EDUCATIONAL COMPUTING
- ★ ELECTRONICS KITS

Send for your free catalogue to:



**KELAN ENGINEERING LTD.**  
Circuit Products & Components Division.  
27-29 Leadhall Lane, Harrogate.  
North Yorkshire. HG2 9NJ.  
Tel: (0423) 870938.

A FARNELL ELECTRONICS COMPANY

NAME .....

ADDRESS .....


## Newrad

### NEWRAD INSTRUMENT CASES LTD

Manufacturers for the Electronics Industry

UNIT 19 · WICK INDUSTRIAL ESTATE · GORE ROAD  
NEW MILTON · HANTS · BH25 6SJ

Telephone: NEW MILTON 615774/621195

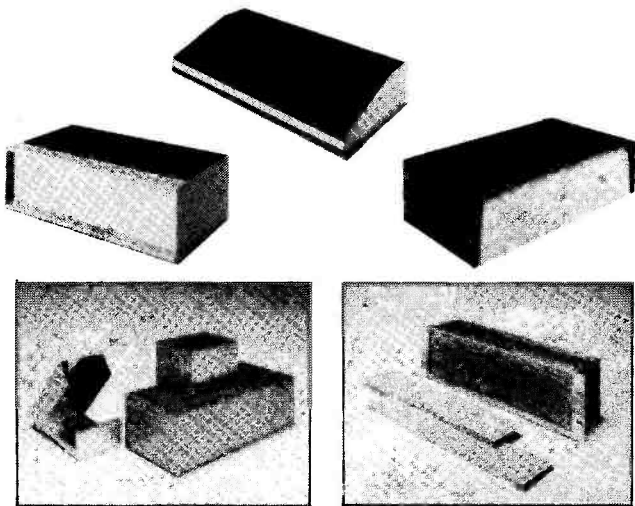

WE MANUFACTURE BEAUTIFUL ENCLOSURES

At prices you will find difficult to beat.

Alloy boxes from 80p to rack mounted units from £15 and a host of ranges and sizes in between. Well made - well finished - and all British.

Send large SAE for catalogue which includes £5 in vouchers.

# DISTORTION METER

Having discussed the basic principles and the design criteria in last month's article, John Linsley Hood goes on to describe the circuitry of this versatile test instrument.

The basic layout of the THD meter is shown in Fig. 6 and the final circuit is shown in Fig. 7. RV1 acts as a gain control in the input circuit of IC1a, a buffer stage which ensures that the Wien network is always driven from a low AC impedance. From the output of this the signal is divided into three paths, the upper RC parallel network, the inverter stage, and a feed to the mode switch, SW2, which allows the network to be effectively bypassed so that the full scale meter setting can be determined.

In the other positions of SW2, the two halves of the network are connected to produce the notch characteristic required. It will be understood that for a perfect balance to be obtained, the input from the inverter to the lower limb needs to be exactly twice as large as the input to the upper limb. To arrange this, a 2k2 10-turn pot, RV4, is connected in series with the op-amp feedback resistor so that its gain can be adjusted. This is the Trim control on the instrument front panel.

Ideally, the tuning of this instrument would be done by two twin gang pots (shown as Ra and Rb in Fig. 6). However, I want to keep the circuit noise level as low as possible, and this depends in part on the circuit resistance values, as does the proneness of the circuit to pick up hum. I don't want to make Ra (RV2 in Fig. 7) much higher than 10k, and sadly, in this country, dual gang pots with a resistance lower than 4k7 ohms are very difficult to come by. The one source of 1k dual

gangs I know of has a rather stiff and rubbery feel, which makes them unsuitable for the fine tuning position.

I have, therefore, with regret — since this makes the instrument a little more awkward to use — opted for a single fine-tune pot, the 100 ohm RV3. This reluctant compromise means that the final notching out of the signal input requires interacting adjustments of both RV3 and RV4. If a decent quality low resistance dual-gang pot can be obtained by the constructor, the other half should be inserted in series with R6, whose value can then be reduced to 470R.

As mentioned before, it is necessary to sharpen up the notch of the system a bit to prevent unwanted attenuation of the lower harmonics. This is done by negative feedback to IC1 from IC2 through R9, R2 and R8.

There are two signal filtration stages. IC3a is a high-pass hum filter with a turn-over frequency of 250Hz and an attenuation of 20dB/octave to give thorough 50/

100Hz removal; A low-pass filter built around IC3b has a similar slope and a turn-over frequency of 4700Hz. These two options are selected by SW3 and SW4. The low-pass HF-noise filter allows an instrumental identification of the type of harmonics associated with crossover distortion, which would be at 7, 9, 11, and 13kHz on a 1kHz signal.

So, if the minimum signal is noted on a test at 1kHz and the low-pass filter is then switched in and the new minimum noted, the amount of high-order harmonics present can be determined by an RMS subtraction of these two values. To distinguish between high-order harmonics and general noise, the extent to which the difference between the filtered and unfiltered signal levels changes when the signal input is removed can be noted.

The final stage of the distortion meter part of the circuit is the buffer amplifier, which precedes the meter attenuator, and from which an oscilloscope monitor signal can be obtained if needed.

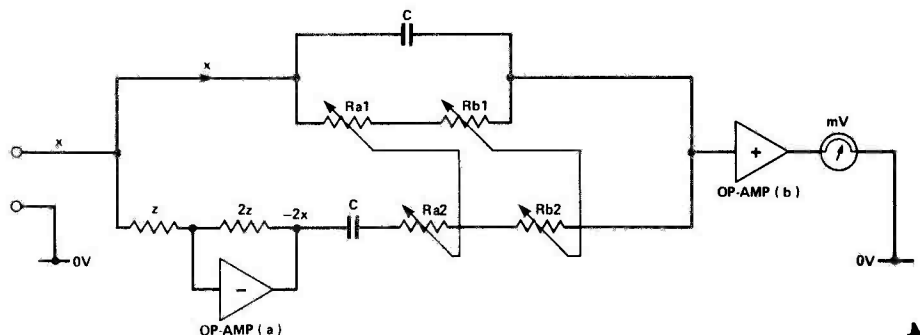


Fig. 6 The basic arrangement used in the THD meter circuit.



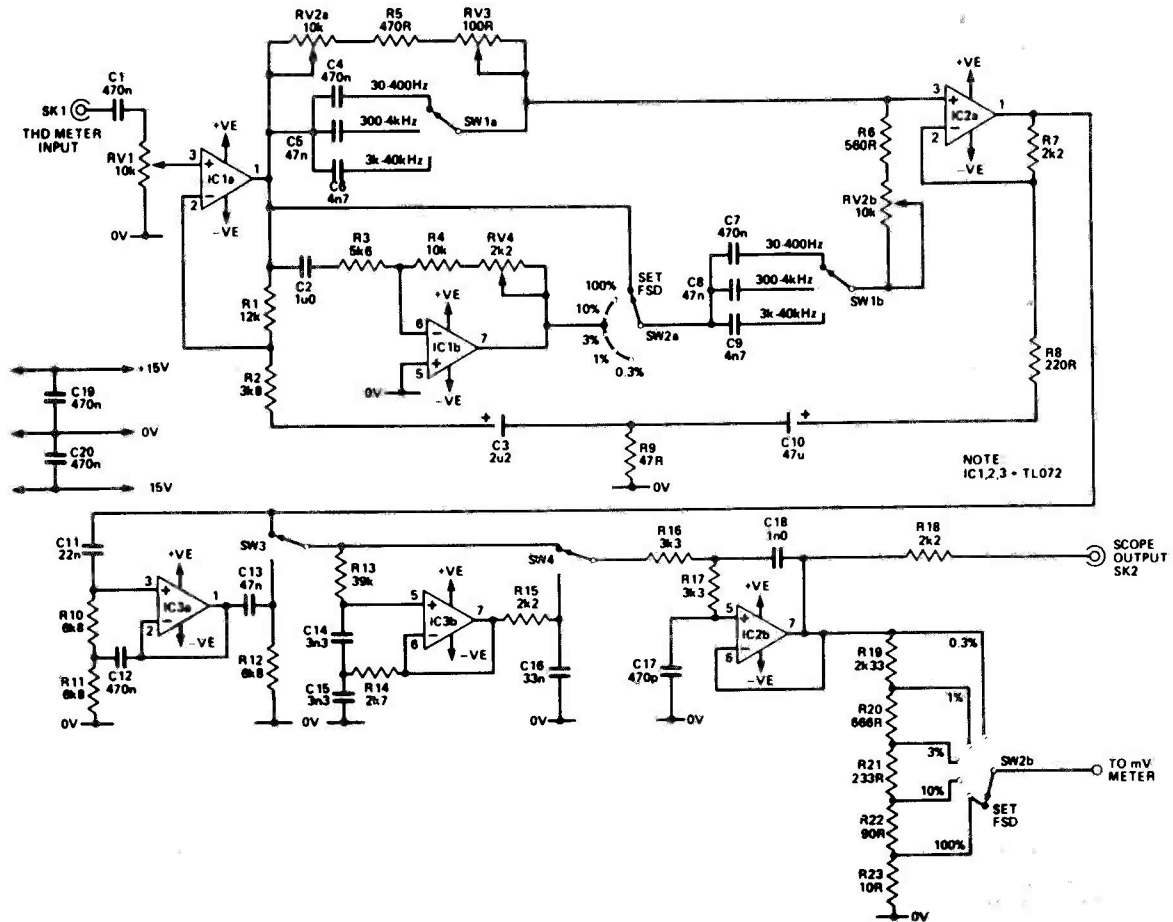


Fig. 7 The final circuit diagram of the THD meter.

An option which is also available is to build a further HF filter into the input circuit of the unity-gain buffer amplifier, IC2b. This should have a -12dB/octave slope and a turn-over frequency of 50kHz, which serves as a useful bandwidth limit. If this is not required, SW4 output can be taken to the non-inverting input of IC2b and C17, C18, R16 and R17 deleted.

### The Millivoltmeter Circuit

Since any distortion meter requires an AC millivoltmeter to display the result, and a millivoltmeter on its own makes quite a useful bench instrument, I have decided to make the input to the measuring circuit available separately by way of an independent switched attenuator (see Fig. 8).

The circuit itself is straightforward enough, with a 100µA meter in a diode bridge in the feedback network of an op-amp. Since the millivoltmeter is intended to be usable as a general purpose instrument, I have used a

two stage circuit built around a dual FET-input op-amp (TL072 or LF353), in which the first half acts just as a gain stage. This permits both a high input impedance, and

a 20Hz-100kHz (-3dB) bandwidth.

Although the input attenuator suggested has a total chain resistance of 100k, this choice was

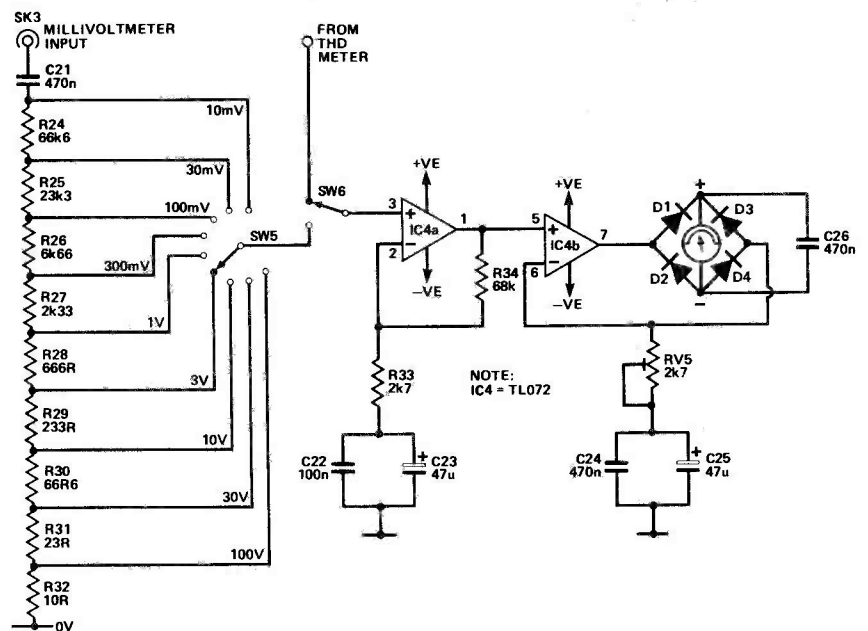


Fig. 8 The circuit diagram of the millivoltmeter.

# PROJECT : Distortion Meter

mainly in the interests of preventing the input from being too sensitive to inadvertent signal pick-up from other parts of the circuit within the same box. If the constructor is happy to screen this part of the circuit well, there is no reason why the quoted attenuator chain resistors should not be scaled up to give an input impedance of 1M ohm or even higher, although this might affect the frequency response flatness.

Calculating the actual resistor values in the chain is a bit awkward if one does not know the method. For simple minded people like me, a lot of confusion is removed if one thinks about the current flow down the chain. So, if we choose a 100k total, 100V RMS will give a current flow of 1mA (RMS). This will develop 10mV across 10 ohms, hence the value of R32. The next full-scale reading required is 30V. This will cause a current flow of  $30/100k = 300\mu A$ . 10mV drop will then require  $10mV/300\mu A = 33.333$  ohms, which gives the value of R31 + R32, from which R31 = 23.3R, and so on.

These can be made up, depending on the accuracy required (which, in turn, will depend on the quality and tolerances of the resistors available, and upon the quality of the meter movement) by placing standard value resistors in parallel. A 6k66 ohm resistor can be approximated by putting a 330k and a 6k8 in parallel (=6.662k), a 23.33k resistor by putting a 33k, a 100k and a 390k in parallel (=23.33k) or by a 22k and a 1k in series (23.0k), and so on.

The proper operation of this type of measurement circuit requires that the return path from the inverting input of the op-amp to the 0V line has a low AC impedance at the highest operating frequencies likely to be used, so it is prudent to bypass the tantalum bead capacitors in the feedback path with small, non-polarised types. The + and - supply lines for the instrument are also bypassed to the 0V lines on the main PCB by 0.47µF non-polarised capacitors.

When the meter is used just as a millivoltmeter the input attenuator presents a more or less constant input impedance regardless of the Range switch position, although, as mentioned earlier, it can be increased if desired.

## The Spot-Frequency Oscillator

It is a great convenience to have a good quality sine-wave signal source actually on the instrument, and from my experience of making measurements of this kind I find that one does not carry out these tests over a continuous spread of frequencies but rather at certain spot points.

The reason for this is not just laziness but because, if one knows how a system behaves at, say, 1kHz and at 3kHz, it is extremely unlikely that its behaviour at 1500Hz or 2300Hz will be anything other than intermediate between the known points.

There are, it is true, certain audio amplifiers which can display very odd behaviour over certain parts of their frequency range due to the feedback loop(s) getting into a state known as conditional stability. However, such amplifiers will almost certainly have a very bad square-wave response and their general behaviour and sound will be so horrid that one shouldn't need a distortion meter to discover that they are sick!

However, to return to the oscillator. The basic circuit I have used is a two op-amp variation of the Wien bridge system shown in Fig. 9. In this, an inverting (virtual earth input) amplifier is fed with two feedback signals through the limbs of the Wien network. A positive feedback signal is obtained from the two inverting amplifiers connected in series through the RC series element, and a negative feedback signal is fed to the same point from the output of the first inverting amplifier.

The gain of the second amplifier is controlled by a thermistor in its feedback path. When the thermistor is cold, its resistance is high and ICb has a high gain. This makes the positive feedback part of the signal fed to

the input of ICa larger than the NFB part, and the system oscillates. This feeds an AC signal to the thermistor which heats it up, and causes its resistance to decrease.

When the gain of ICb has dropped to a level at which the signal output is just enough to keep the thermistor warm, the output stabilises. This then automatically provides just enough positive feedback input to ICa to keep the system oscillating, and no more.

Because op-amps have a lower intrinsic distortion when used in the inverting mode (a fact which is surprising though true) and because there is no 'common mode' signal (ie, a signal fed equally to both inputs, which the op-amp must then cancel), the distortion produced by this circuit is extremely low. In fact, now that this arrangement is known, I cannot see any good reason why anyone wanting a Wien bridge oscillator should use the old conventional system, which has a considerably inferior performance, especially when one bears in mind the relatively low cost of even a high quality dual op-amp such as the TL072 or the LF353.

I have shown the measured performance of the oscillator in Table 1. Above 300Hz the THD is of the order of 0.003% or lower. The worse distortion, at 100Hz and to a slight extent at 300Hz, is third harmonic and is due to the thermistor bead actually heating up during the sine-wave cycle, reducing the gain of the system as the peak of the waveform is approached. This is the type of problem which will always occur with any amplitude-sensitive output stabilisation system. It can only be diminished by increasing the measurement time constant, which in turn makes the oscillator take a bit longer to settle down following a change in its operating frequency.

The output from ICb is about 600-700mV with an RA53, and

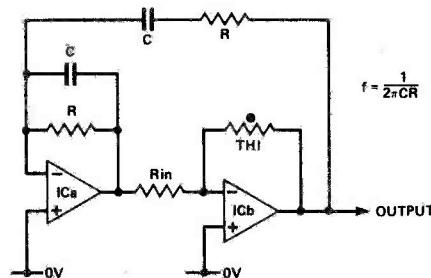


Fig. 9 The basic arrangement used in the spot frequency oscillator.

FREQUENCY (Hz)	THD (%)
100	0.02
300	0.005
1k	less than 0.003
3k	less than 0.003
10k	less than 0.003
20k	less than 0.003

Table 1 Measured performance of the spot frequency oscillator.

# PROJECT : Distortion Meter

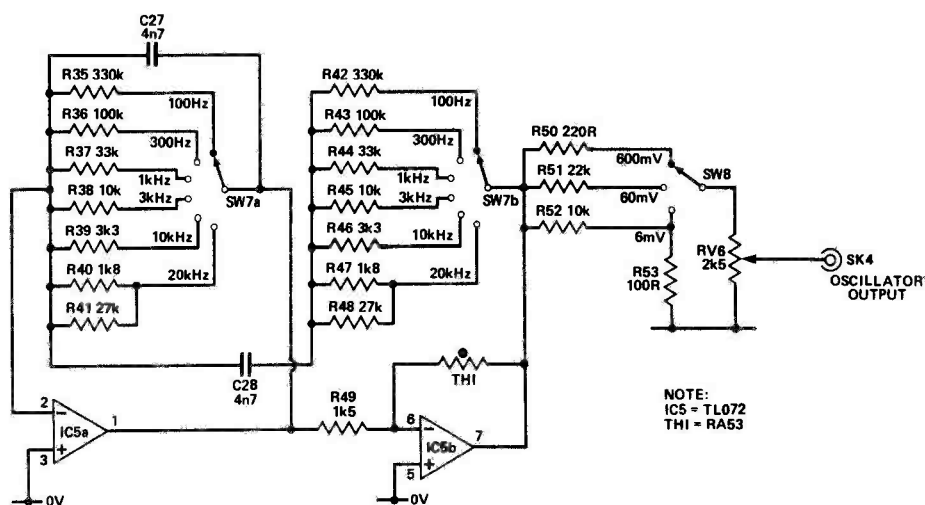


Fig. 10 The final circuit diagram of the spot frequency oscillator.

the signal level at the output of ICa, which is a feasible alternative oscillator output point, is almost exactly half this. I mention this because ICa is an active integrator with a response which decreases with frequency. Because of this, the third harmonic distortion introduced by the thermistor is reduced to about one third at ICa output which gives a very low THD oscillator indeed. However,

potentiometer, giving signal level ranges of 0-6mV, 0-60mV and 0-600mV. If the user wishes to increase the output somewhat, say to 1V, it can be done by putting a resistor of between 500R and 1k5 in series with the RA53. This will lessen the thermistor introduced distortion but will lengthen the setting time. On the prototype this is about 2000 cycles, which is 20 seconds

at 100Hz and 0.1 second at 20kHz, but could vary a bit from one thermistor to another.

## Power supply

The total current consumption of the instrument is 18mA at  $\pm 15V$ , which is obtained from a small stabilised power supply unit shown in Fig. 11.

As mentioned earlier, it is possible to make the instrument operate from batteries. Two options exist here. The first is to use a pair of 6V or 9V transistor radio batteries such as the PP1 or PP9 and to switch both + and - lines. The second method is to operate the unit from a single 9V battery using the adapter circuit of Fig. 12a to give a  $\pm 4.5V$  line pair.

In both cases it is worthwhile substituting TL062s for IC1, IC2, IC3 and IC5, and a TL061 for IC4. This will reduce the battery current demand to some 1.5-2mA, with little performance penalty.

However, if the supply voltage option chosen is the  $\pm 4.5V$  one, a problem would arise because the notch amplifier circuit would overload at the 3V RMS output required from ICs 2 and 3 for FSD on the measuring instrument. It is therefore necessary to down-grade this a bit by cutting out R19 (2k33) so that SW2b becomes as shown in Fig. 12b, giving a minimum FSD sensitivity of 1%. This will only require a 1V RMS swing from the notch amplifier (Fig. 7) which will be comfortably within its capability.

*In spite of last month's promise we still couldn't find room for the rest of the article in this issue. We hope (!) to conclude it next month.*

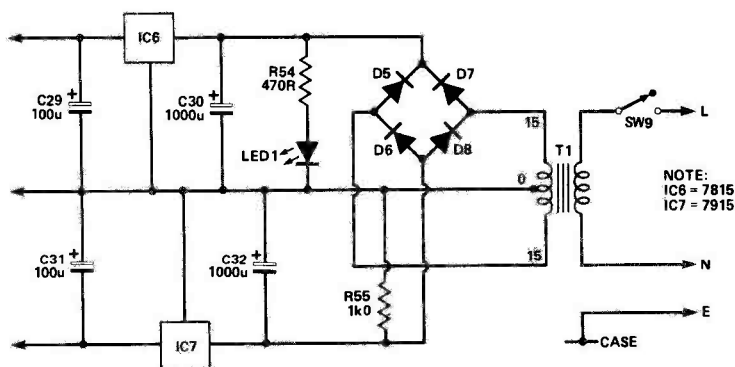


Fig. 11 The circuit diagram of the stabilised mains power supply.

for a THD meter whose minimum scale reading (the prototype, uses a 4 inch scale meter) is 0.005%, the circuit arrangement shown in Fig. 9 seemed adequate.

I have shown the final circuit of the oscillator in Fig. 10. I have opted to keep the value of C constant, and vary R to change the oscillator frequency. This was partly because resistors can be obtained to a higher value of accuracy than big capacitors, and partly because, with the circuit values chosen, it would allow close tolerance, low loss polystyrene capacitors to be used.

A three stage output switched attenuator is used in combination with the 2k5 output


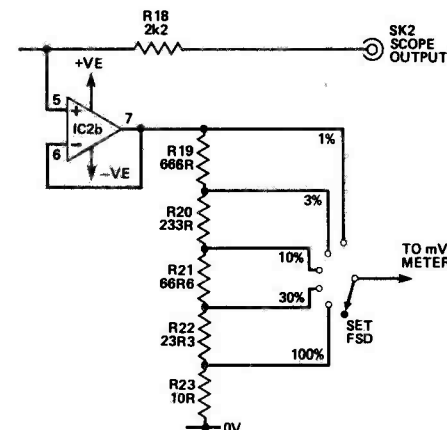


Fig. 12 a) The arrangement used to obtain a dual-rail supply from a single battery and b) the changes which must be made in the circuitry around SW2b to accommodate this arrangement.

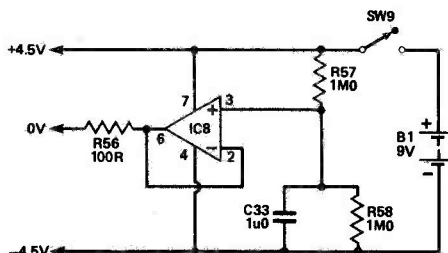

VISIT OR PHONE

OPEN 6 DAYS  
A WEEK  
ALL STOCKS  
ON DISPLAY

# HENRY'S

## AUDIO ELECTRONICS




EQUIPMENT • COMMUNICATIONS • COMPUTERS • COMPONENTS

ALL PRICES  
INCLUDE  
VAT
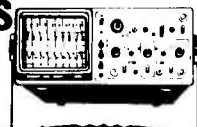
### SCOPES

1UK C/P £6.00  
or H18.00 (Securitor)

**HITACHI**  
2 year warranty  
ALL MODELS WITH  
2 PROBES (Not V212)  
V212 Dual 20 MHz 6" CRT  
Probes see below.  
V222 As 212 plus DC offset, etc.  
All other models available.




£343.85  
£454.25
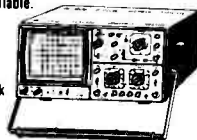
### HAMEG

2 years warranty

HM103 Single track  
10MHz 6 x 7cm  
display component  
tester £192.05  
HM203/5 Dual 20MHz 8 x 10cm  
display component tester, etc.  
HM204-2 Dual 20MHz sweep  
delay, 1mV component tester, etc.  
Also HM605 Dual 60MHz



£303.60  
£419.75  
£592.25

### OPTIONAL SCOPE PROBES

X1-X10 switched.  
£11.50 for all scopes.



### CROTECH

3030 Single trace  
15MHz component  
tester 9"cm display  
3035 Single trace 15MHz 13cm  
(5") display component tester  
3132 Dual 20MHz trig to 40MHz, 2mV/div 130mm (5")  
display, algebraical add/sub Reg DC D/P, 5V and ±  
12V. Built-in component comparator



£205.85  
£227.70  
£341.50

### SCOPEX

1A015 Dual 15 MHz 5" tube  
TV SYNCH Z MOD £373.75



F8 As above plus fitted  
0.2Hz to 200 KHz Function Generator £488.75

### THANDAR

2 year warranty  
SC110A 10MHz battery  
portable 32 x 26mm display  
with batteries  
£189.75  
(UK post, etc. £1.50)



OPTIONS Carry case £6.84  
AC adaptor/charger £7.99 Nicad pack £12.65


### TRANSISTOR TESTER

Direct PNP/NPN and diodes  
Hfe, leakage, etc. General purpose TC1  
(UK C/P 65p) £27.95



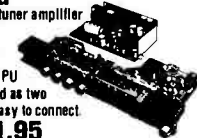
### STEREO TUNER/AMPLIFIER

1000's sold  
4 wave-band stereo tuner amplifier  
by GEC MW/LW/  
SW stereo FM radio  
10 - 10 watt stereo  
amplifier. Inputs for PU  
tape in/out. Supplied as two  
assembled units - easy to connect  
as illustrated £21.95  
(UK C/P £1.50)


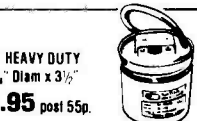
### NICADS

EVEREADY 8.4 Volt HEAVY DUTY  
NICAD approx. 3 3/4" Diam x 3 1/2"  
with magnetic  
switch £5.95 post 55p.



### DIGITAL MULTIMETERS

Controls

s=Slide R=Rotary  
PB=Push button  
All feature AC/DC volts,  
DC amps (many with AC  
amps) others, etc.  
(UK C/P 65p) \* WITH CARRY CASE



\* KD25C 12 range 0.2A DC 2 Meg ohm(s) £27.95  
\* KD30S 14 range 10A DC 2 Meg ohm(S) £29.80  
\* KD30C 26 range 1A AC/DC 20 Meg ohm (R) £35.80  
\* METEX 3500 30 range 10A AC/DC 20 Meg  
ohm (R) £42.26  
\* METEX 3510, 30 range 10A AC/DC 20 meg ohm  
plus Hfe tester plus cont. tester (R) £46.52  
\* 6010 28 range 10A AC/DC 20 Meg ohm (PB) £43.50  
\* KD55C 26 range 10A AC/DC 20 Meg ohm  
(R) £44.50  
\* KO615 18 range 10A DC 2 Meg ohm plus Hfe  
tester (R) £39.95  
\* 7030 As 6010 but 0.1% basic (PB) £53.95  
\* HC 5010 31 range 10A AC/DC Cont. buzzer 20M  
ohm (R) £49.95  
\* DM3350 Autorange plus cont. tester 18 range 10A  
AC/DC 2 Meg ohm (R) £49.95  
\* DM2350 Mini autorange plus cont. tester 19 range  
10A AC/DC (20A Max) 2 Meg ohm (PB) £69.95  
\* 3100 Pen type auto ranging AC/DC V 20 Meg ohm  
- Buzzer  
\* SOAR MES40 Manual/Autoranging plus cont buzzer  
19 range 10A AC/DC 20 Meg ohm (R) £47.77

### ANALOGUE MULTIMETERS

(\*mirror scale) (UK C/P 65p)  
HC1015 15 range pocket 10K/Volt  
1 Meg ohm £8.95  
HM102BZ\* 22 range 20K/Volt 10A DC  
plus cont. buzzer 10 Meg ohm £14.50  
ETU3000 20 range 30K/V 12A DC.  
12 meg ohm £21.00  
NH56R\* 22 range 10K/Volt 6 Meg ohm £12.95  
830A\* 26 range 30K/Volt 10AC/DC 10 Meg  
ohm £24.95  
380TR\* 23 range bench, 100K/Volt large scale  
10A AC/DC plus Hfe tester 10 Meg ohm £45.00  
AT2100\* 31 range de luxe 100K/Volt 10A AC/DC  
100 Meg ohm £34.95  
AT1020\* 18 range de luxe 20K/Volt plus Hfe  
tester 5 Meg ohm £22.50  
YN 380TR\* 19 range 20K/Volt plus Hfe tester  
1 Meg ohm £15.95  
KRT5001\* Range doubler 35 range total 50K/  
Volt 10A DC 20 Meg ohm £21.95  
ST303TR\* 22 range 20K/Volt plus Hfe tester 12A  
DC 1 Meg ohm £21.00



### LCD COUNTERS

(UK C/P & INS 65p)

THANDAR battery portable 8 digit LCD counters.  
Size 255 x 150 x 50mm. Complete with batteries.  
Optional: Carry case £6.84 AC adaptor £7.99  
TF400 10Hz to 40MHz, 1Hz Res. 49mV sensitivity. £138.00  
TF200 10Hz to 200MHz, 1ppm res. 10mV sensitivity.  
many features. A&B inputs, etc. £189.75  
TP600 600MHz prescaler (Powered by computer) £51.75  
TP1000 1000MHz (1GHz) Prescaler with power supply £74.75  
PFM200A Pocket 20Hz to 200MHz LED counter 0.1Hz res.  
10mV sensitivity £79.73  
NEW TF600 LED 600 MHz counter. £152.38



### GENERATORS


Function and Pulse (UK C/P 65p)  
THANDAR bench mains portable. Size 255 x 150 x 50mm  
Options: Carry case £6.84  
TG101 0.02Hz to 200KHz function, sine, square, triangle,  
Variable DC offset. TTL O/P Ext. sweep mode. Variable 600  
ohm 10V PP £120.75  
TG102 0.2Hz to 2MHz function, Sine, square, triangle,  
Variable DC offset. TTL O/P. Ext. sweep mode variable 600  
ohm O/P. 10V PP £178.25  
TG105 5Hz to 5MHz pulse, TTL and Sync O/P. Variable  
50 ohm D/P. Free run, gated or trig. modes. £120.75


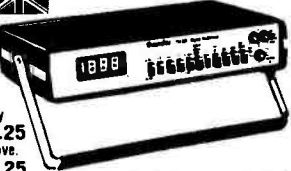
### LCD & LED MULTIMETERS

(UK C/P 65p)

THANDAR BENCH PORTABLES Size 255 x 150 x  
50mm Option: Carry case £6.84  
TM355 3 1/2 digit LED, 29 ranges, 0.25% basic.  
100mV res. 10A AC/DC, 20M ohm £97.75  
(AC adaptor option £8.95)  
TM356 3 1/2 digit LCD 29 ranges as TM355, 3000 hour battery  
life (supplied) £109.25  
TM351 3 1/2 digit LCD, 29 ranges, 0.1% basic. Ranges as above.  
2000 hour battery life. £132.25




### LED COUNTERS

(UK C/P 65p)  
METEOR mains or battery portable 8 digit LED counters.  
Size 219 x 240 x 98mm, 5mV sensitivity 0.1Hz resolution  
100 5Hz to 100MHz £109.25  
600 5Hz to 600MHz A&B inputs £139.15  
1000 5Hz to 1000MHz (1GHz) A&B inputs £189.75  
Options:  
6 NICADS £12.19 RF pickup Aerial £8.91 (AC adaptor included)


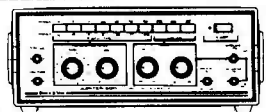
### FUNCTION GENERATOR

(UK C/P 65p)  
JUPITER 500 Function generator 0.1Hz to 500KHz or better.  
Sine, square, triangle O/P to ±30 volts. TTL O/P DC offset =  
15V variable. Ext AM and sweep facilities 220/240V AC  
operated. £126.50




### CASSETTE MECHANISMS

Fitted counter, Motor, Stereo  
record and erase heads.  
Autostop, solenoid.  
Brand new available 6V DC or 12V DC  
(state which) £5.95 (UK C/P 65p)  
ALSO miniature stereo cassette replay mechanism  
12v, 105 x 100 x 40mm. £5.50 (UK C/P 65p)


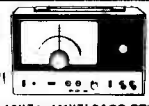
### GENERATORS

220/240V AC  
(UK C/P, etc £1.20)  
AUDIO LEADER LAG271  
5 band/sine/square  
0/P 0.5V RMS Dist 0.05% 10Hz to 1MHz £106.95  
TE220 4 range sine/square 0/P 5V RMS 0.5%  
Dist 20Hz to 200KHz £82.95  
TRIO A 6202A 4 band 20Hz to 200KHz, 10V RMS  
O/P 0.5% dist CR OSC £102.35



### ITT 2020 CABINET

Professional computer case  
with keyboard cutout, 18" x  
15 1/2" x 4 1/2" (front slopes). Ideal  
for single board computers like the  
Multiboard (3 cards, etc). Vary heavy gauge (25")  
plastic with metal base. Attractive silver grey finish.  
£22.95 (UK post £2.05)



LEAFLETS AVAILABLE FOR MOST ITEMS SEND  
LARGE SAE (UK 25p) for latest catalogue.

ALWAYS BARGAINS  
FOR CALLERS

### CB/HAM RADIO

Large range in stock -  
ask for leaflets



### VARIABLE POWER SUPPLIES

(UK C/P £1.00)  
220/240V AC input  
PP241 single meter A/V  
0/30V 1 amp £37.95  
PP243 3 amp version £58.95  
2302 Dual 0/30v, 0/2A Twin meter plus 5V 1A and  
pulse generator. £264.50



SUPPLIERS OF ELECTRONICS FOR EVERY PURPOSE

Official orders welcome.  
(Subject to confirmation)

ALL PRICES  
INCLUDE VAT

ORDER BY POST OR PHONE



Up to £1000 instant credit!  
Available through Lombard Tricity Finance

301 Edgware Road, London, W2  
Test Equipment, Audio, Communications 01-724 3564

404 Edgware Road, London, W2  
Computers 01-402 6822 • Equipment 01-724 0323 • Components 01-723 1008

CALL IN AND SEE FOR YOURSELF All mail to Cubegate Ltd, 1st Floor, 406 Edgware Road, London W2 1ED



# READ/WRITE

Please send your comments to the Editor, ETI, 1 Golden Square, London W1R 3AB.

## Bug In the Middle

Dear Sir,

I appreciated your listing of the three main approaches to fault finding in the article *De-bugging and Fault Finding* (ETI August 1984), but may I suggest an even quicker approach than working from one end or other of a piece of equipment?

It is to start in the middle, immediately eliminating one half of the circuitry, and then to go to a point roughly half-way into the half which contains the fault and so on until the problem is isolated. Taking a simple AM radio as an example, the audio detector is an obvious starting point, followed by the mixer output or the mid-point voltage of a Class B output stage, and so on. But first, and from bitter experience, always check the input and output of the power supply.

To change the subject slightly, I have decided to build John Linsley Hood's amplifier, all I have to do now is to find £250 for the kit as component supply here is not all it might be. So, to stop confusing me, can we have a moratorium on amplifier designs for the next six months?

Yours sincerely,  
Chris Cosgrove  
West Lothian

We take your point about the fault-finding procedure. As for the other matter, whilst we cannot say that there will be another amplifier design in ETI in the next six months, we are certainly not going to promise that there won't be one! After all, why buy ETI if you don't want a magazine that's fast-moving, innovative, up-to-the-minute, (continued on p.109).

## Ripples On The Supply Line

Dear Sir,

As a regular reader of your excellent magazine I feel I must point out my experience of one of your advertisers. I wanted to purchase three MPSU56 transistors and checked with some of your advertisers lists. I found that Watford sold them for 60p but that they would not accept a telephoned order using a Visa card. I tried Rapid who listed

the transistors at 55p each but on telephoning them I discovered that there was a minimum order charge of £5.00 and my three transistors plus some fuses did not come anywhere near that total. So, gritting my teeth, I decided to use Cricklewood Electronics, even though their price was a staggering £1.22 each plus the usual incidentals such as postage, etc.

True to their word the components arrived next day, but the price of the transistors had risen overnight to £1.95 each. I immediately queried this and was told there had been a price increase and that there was nothing they could do. Had I been informed before passing on my Barclaycard number that the price had risen so much I would not have placed the order. I feel I have been conned and wonder how many others have experienced this problem as small customers trying to obtain components and paying the penalty.

Yours faithfully,  
R. Isbourne  
Bracklesham Bay

We are sure that Mr. Isbourne is not the first person to run into this sort of problem. The situation arises partly because advertisers have to prepare their price lists well in advance in order to allow for typesetting, printing and distribution of the magazine. By the time the reader sees an ETI advertisement nearly a month will have elapsed since the advertiser submitted the original copy with its prices, and in a world where such important economic factors as exchange rates change with frightening rapidity, that is a long time. It is for this reason that most advertisers (including Cricklewood) publish a note saying that prices are subject to change.

Cricklewood tell us that anyone placing a telephone order would normally be informed of the current price of the goods but they admit that it is possible that this was forgotten in Mr. Isbourne's case. The moral, perhaps, is that readers should always make a point of asking what price will be charged when placing telephone orders. The problem should not arise with written orders since the normal

practice here is for the supplier to write back to the customer and ask for more money when a price rise occurs, leaving the customer the option of paying the extra or cancelling the order as he or she wishes.

## Some Lines on Delay

Dear Sir,

May I suggest an alternative method of achieving the delay required for the Active-8 loudspeaker (ETI September to December 1984). Please excuse my long-winded arithmetic.

$$c = 343 \text{ m/sec} \quad f_c = 4 \times 10^3 \text{ Hz}$$
$$\lambda = \frac{c}{f_c} = \frac{343 \times 10^3}{4 \times 10^3} = 85.75 \text{ mm}$$

$$\frac{360^\circ}{85.75} = 4.2^\circ/\text{mm} \times 38\text{mm} = 159.6^\circ$$

(38mm = separation in  $D_2$ )

If the voice coil leads on one loudspeaker are reversed, the phase difference becomes

$$180^\circ - 159.6^\circ = 20.4^\circ$$

$$t = \frac{1}{f} = \frac{10^6}{4 \times 10^3} = 250 \text{ } \mu\text{s}$$

$$\frac{250}{360} = 0.694 \mu\text{s}/^\circ \times 20.4^\circ = 14.2 \mu\text{s}$$

Therefore a delay of 14.2  $\mu\text{s}$  could be applied to the LF loudspeaker, saving several stages of delay. Alternatively, since

$$\frac{\lambda}{z} \text{ at } f_c = \frac{85.75}{2} = 42.875 \text{ mm}$$

and  $42.875 - (D) = 4.875 \text{ mm}$

if the mechanical construction will allow, the HF loudspeaker could be brought forward by 5mm or the LF loudspeaker moved back and no delay circuit would be required at all.

Or, let

$$\lambda = 38 (D_2) \times 2 = 76 \text{ mm}$$

$$\text{and, as } f = \frac{c}{\lambda} = \frac{343 \times 10^3}{76} = 4.5 \text{ kHz}$$


By raising the crossover frequency to 4.5 kHz we can again dispense with the delay stages.

Yours sincerely,  
L. R. Burns  
Wokingham

Barry Porter, author of the Active-8 series writes:-

The main error in Mr. Burns' reasoning is his assumption that by reversing the connections to a drive unit a time delay is introduced. Imagine that the HF unit is fed a short, positive-going pulse; with reversed connections the output from the unit will be a negative-going pulse when what is required is a delayed positive-going pulse.

The effects of various filters are shown in Fig. 4 of the first part of the series (reproduced here), and this illustrates that the connection of the HF unit is decided by the filter slope. Upon reflection, the illustration may be difficult to understand and it might have been clearer had the waveforms been drawn as sinewaves (but a certain 2½ year-old ex-mafia hit-man called Timothy prevented this by

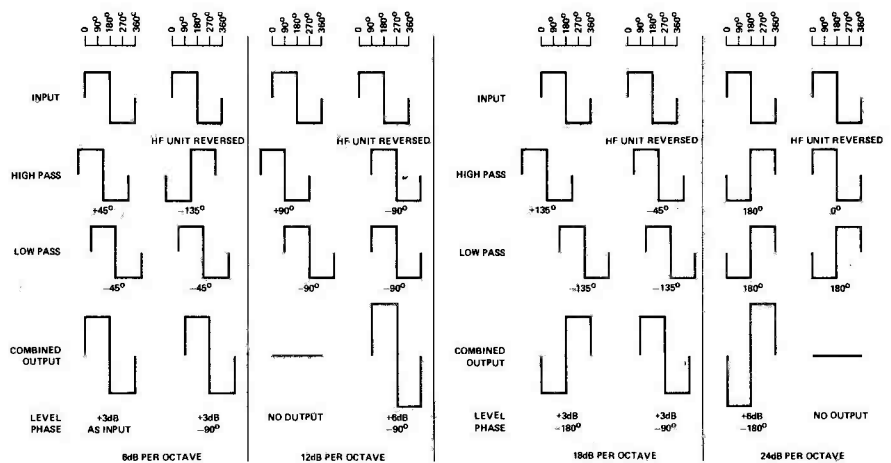


The original figure, intended to show the effect of 6, 12, 18 and 24 dB per octave filters on signal levels and phase.

hiding my sinewave stencil in the washing machine!).

If Mr. Burns does not like the idea of using the delay stages, he may prefer to mount the HF unit on top of the cabinet using a small bracket assembly. However, as the


unit has to be placed about 38mm back, the top edge of the cabinet must be chamfered or rounded and preferably covered with 3mm felt material. The position of the LF unit must then be changed to bring it as near to the HF unit as possible.

ETI

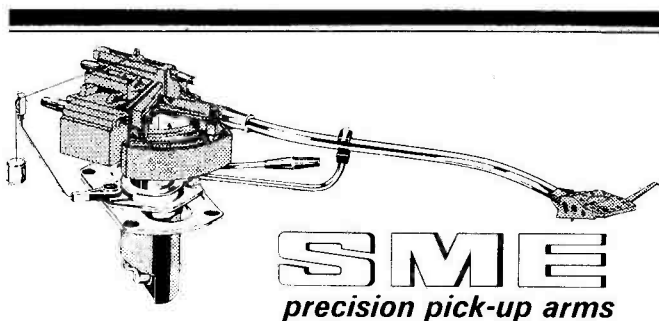

**SME**  
precision pick-up arms

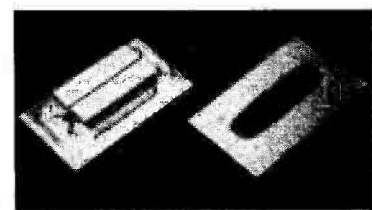Please call or write:  
SME Limited, Steyning, Sussex, BN4 3GY  
Telephone: 0903 814321 Telex: 877808 G



**MUSICIAN  
FULL  
RANGE  
SPEAKER  
DRIVE  
UNITS**


£70 a pair + postage. For details and enclosure construction write or phone:

**MERSEYSIDE ACOUSTIC DEVELOPMENTS**  
131 Mount Pleasant, Liverpool L3 5TF.  
051 709 0427.

## MAGENTA ETI KITS

Full kits include pcbs, hardware, cases (unless stated otherwise), IC sockets, wire, nuts & bolts. Article reprints extra 70p each.

<b>SPECTRUM CENTRONICS INTERFACE</b> Dec 84 less case and printer plug	£8.71	<b>MAINS BORNE REMOTE CONTROL (RECEIVER)</b> Apr 84	£26.84
<b>LOUD SPEAKER SPEAKER</b> Nov 84	£4.13	<b>STEREO POWER METER</b> Mar 84	£57.48
<b>DIGITAL CONTROL PORT (SPECTRUM) I/O BOARD</b> Nov 84 less case	£34.44	Kit less case & panel meters	£33.96
<b>DIRECT READING CAPACITANCE METER</b> Nov 84	£27.32	<b>MINI MYNAM (ZX81 &amp; Spectrum)</b> Feb 84 less case	£48.98
Kit less case & panel meter	£16.98	<b>MINI DRUM SYNTH</b> Nov 83	£11.87
<b>TEMPERATURE CONTROLLER</b> Nov 84 less case	£5.99	<b>FAST LIGHT PEN</b> Nov 83 less cases	£24.92
<b>MAINS FAILURE ALARM</b> Nov 84	£8.20	<b>RADIO CONTROL SERVO FAIL-SAFE</b> less case Aug 83	£3.14
<b>KNIFE LIGHT</b> Nov 84	£12.83	<b>BALANCED INPUT PRE-AMP</b> no case May 83	£11.99
<b>SIMPLE ECHO UNIT (EZEKO)</b> Oct 84	£26.98	<b>COMPRESSOR/LIMITER</b> no case May 83	£21.37
<b>DIGITAL CONTROL PORT (SPECTRUM) CONTROL/PSU BOARD</b> Oct 84 less case	£25.57	<b>HIGH QUALITY PHONO AMPLIFIERS</b> Feb 82	£26.63
<b>SIREN UNIT</b> Sept 84 less key switch	£14.82	<b>MOVING COIL STAGE</b> less case	£20.48
<b>DRY CELL CHARGER</b> Sept 84	£13.79	<b>WATCHDOG SECURITY ALARM</b> less battery Aug 81	£48.48
<b>INFRA RED ALARM</b> July/Aug 84	£31.98	<b>MOVING MAGNET STAGE</b> less case	£20.48
<b>SIMPLE CMOS TESTER</b> Aug 84	£22.85	<b>WATCHDOG SECURITY ALARM</b> less battery Aug 81	£48.48
<b>WARLOCK BURGLAR ALARM</b> July 84	£34.98	<b>LED JEWELLERY</b> June 81	CROSS £3.25 STAR £10.91 SPIRAL £8.00
<b>SPECTRUM JOYSTICK INTERFACE</b> June 84	£12.88	<b>GUITAR NOTE EXPANDER</b> Apr 81	£19.82
<b>AUTOMATIC SECURITY LIGHT SWITCH</b> May 84	£21.57	<b>INFRA RED ALARM</b> Feb 81	£24.98
<b>ZX81 EPROM PROGRAMMER</b> May 84	£32.23	<b>4 INPUT MIXER</b> Dec 80	£23.98
<b>MIDI DRUM SYNTH</b> May 84	£20.98	<b>MUSICAL DOORBELL</b> Dec 80	£13.98
<b>MAINS BORNE REMOTE CONTROL (TRANSMITTER)</b> May 84	£32.71	<b>ULTRASONIC BURGLAR ALARM</b> Aug 80	£24.90
		<b>CAPACITANCE METER</b> Aug 80	£27.78
		<b>CLICK ELIMINATOR</b> Apr 79 Kit less case	£28.98

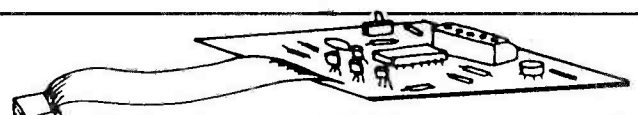

**CATALOGUE**  
1985 CATALOGUE. Brief details of each kit, our books, & illustrations of our range of tools & components etc.  
**CATALOGUE & PRICE LIST** — send £1 in stamps etc or add £1 to your order. Price list — 9 x 4 see.

Catalogue FREE TO SCHOOLS/COLLEGES REQUESTED ON OFFICIAL LETTERHEAD.

**BBC TO ID35 STEPPER MOTOR INTERFACE**  
PCB, driver IC, components, connectors & leads included. Demonstration software listings, circuit diagram, pcb layout & construction details given. Requires unregulated 12V d.c. power supply.  
**INTERFACE KIT (ref ETI)** £13.98  
**OPTIONAL POWER SUPPLY PARTS** £4.87  
**1635 STEPPER MOTOR** £13.98  
**BBC TRACKBALL CONTROLLER**, 2" ball, 2 fire buttons. Analogue input port connector. Includes simple software £17.98

**MAGENTA ELECTRONICS LTD.**  
ET2, 135 Hunter St. Burton-on-Trent  
Staffs. DE14 2ST. Mail Order Only  
(0263) 65435. S.A.E. enquires.  
Add 60p p&p to all orders. Prices include VAT. Access & Visa phone/post.

24 hr answerphone for credit card orders.  
OVERSEAS: Payment must be sterling.  
IRISH REPUBLIC + BFPO - UK PRICES  
EUROPE: UK PRICES + 10%  
ELSEWHERE: WRITE FOR QUOTE.



# Cortex

**HARDWARE  
SOFTWARE**

**MDEX disc O/S + BASIC** £95  
**MDEX Professional Dev. Sys.** £275  
**CORTEX POWER-BASIC disc extensions** £43  
**MDEX Extensions**  
 Editor £35  
 Relocating Assembler/linker £35  
 FORTH — screen editor, assembler £55  
 — graphics — better than BASIC £35  
**PASCAL — by Pre Brinch Hansen** £35  
**QBASIC — fast BASIC compiler** £150  
 UCSD Pascal, SPL, META, WINDOW, SPELL

**CORTEX tape software**  
 Pengo — fast machine code action £6  
 Golf — excellent animation £6  
 Micropede — rampant caterpillar £6  
 Space Bugs, Pontoon, Breakout each £6  
 Cassette/CDOS word processor £13  
 Add £2 for software on CDOS disc

**Disc Drives**  
 80 track double-sided double-density £190  
 40 track single-sided double density £120  
**E-BUS Floppy/Winchester Controller** £135  
**E-BUS 64/128 Kbytes DRAM card** £145/£245  
**E-BUS 9995 Processor card** £145  
**80\*24 Character video card** £48

State disc format and add VAT to all prices  
 !!Brainstem Issue 2 out soon!!



**MICRO PROCESSOR ENG LTD**  
 21 HANLEY ROAD SHIRLEY  
 SOUTHAMPTON  
 SO1 5AP  
 TEL: 0703 780084



# ELECTROVALUE

**Your SPECIALIST SUPPLIERS for  
SOLDER TOOLS**



From a simple 15 watt model to a precision temperature controlled iron, we stock solder irons to suit all manual requirements together with supporting stocks of bits, de-solder tools, materials etc.

**ANTEX**  
 C.240 - 15W/240V:  
 CS - 17W/240V  
 XS - 25W/240V

Replacement bits from 3/32" to 1/4"  
 De-solder heads, stands, elements and handles.

**ERSA**  
 'Sprint' high speed iron: 80/150W, 240V. Heats in 10 seconds!

**ORYX**  
 Temperature controlled solder iron TC.82 45W/240 with scale.  
 Oryx 50 - 50 watt temp. controlled.  
 Standard types  
 Oryx 30 - 30W/240V  
 Viking - 27W/240V  
 Oryx M.3 - 17 watts, 12 volts.  
 A wide range of replacement tips available for all models, also tips from 0.8 to 6.4mm dia. and flat tips.  
 Oryx safety stand.  
 Oryx de-solder tool.  
**MINIATURE SOLDER STATION**  
 SOLDER and DE-SOLDER BRAID  
 Solder in various grades.  
 Please mention this journal when sending for latest free illustrated A-Z list now 44 pages

**BRITAIN'S LEADING QUALITY COMPONENT  
SUPPLIERS - SEND FOR FREE 44 PAGE A-Z LIST**  
 ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

**ELECTROVALUE LTD**

28 St. Judes Rd.,  
 Englefield Green,  
 Egham, Surrey  
 TW20 0HB.


(0784) 33603; Telex 264475.  
 North - 880 Eurnage Lane, Manchester. 061-432 4945.  
 EV Computing Shop -  
 700 Burnage Lane, Manchester. 061-431 4866.

**ACCESS AND  
BARCLAYCARD  
Phoned Orders  
Welcome**
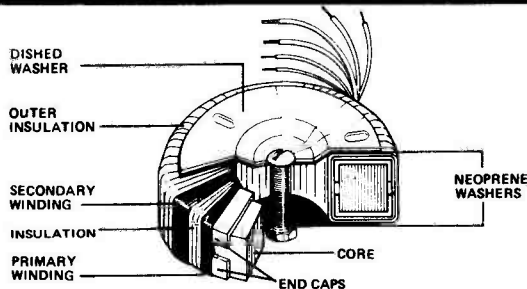
# TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 14 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm 0.35Kg Regulation 19%		
SERIES	SECONDARY No Volts	RMS Current
0x010	6+6	1.25
0x011	9+9	0.83
0x012	12+12	0.63
0x013	15+15	0.50
0x014	18+18	0.42
0x015	22+22	0.34
0x016	25+25	0.30
0x017	30+30	0.25

30 VA 70 x 30mm 0.45Kg Regulation 18%		
SERIES	SECONDARY No Volts	RMS Current
1x010	6+6	2.50
1x011	9+9	1.66
1x012	12+12	1.25
1x013	15+15	1.00
1x014	18+18	0.83
1x015	22+22	0.60
1x016	25+25	0.60
1x017	30+30	0.50

50 VA 80 x 35mm 0.9Kg Regulation 13%		
SERIES	SECONDARY No Volts	RMS Current
2x010	6+6	4.16
2x011	9+9	2.77
2x012	12+12	2.08
2x013	15+15	1.66
2x014	18+18	1.38
2x015	22+22	1.13
2x016	25+25	1.00
2x017	30+30	0.83
2x028	110	0.45
2x029	220	0.22
2x030	240	0.20

80 VA 90 x 30mm 1Kg Regulation 12%		
SERIES	SECONDARY No Volts	RMS Current
3x010	6+6	6.64
3x011	9+9	4.44
3x012	12+12	3.33
3x013	15+15	2.66
3x014	18+18	2.22
3x015	22+22	1.81
3x016	25+25	1.60
3x017	30+30	1.33
3x028	110	0.72
3x029	220	0.36
3x030	240	0.33

120 VA 90 x 40mm 1.2Kg Regulation 11%		
SERIES	SECONDARY No Volts	RMS Current
4x010	6+6	10.00
4x011	9+9	6.66
4x012	12+12	5.00
4x013	15+15	4.00
4x014	18+18	3.33
4x015	22+22	2.72
4x016	25+25	2.40
4x017	30+30	2.00
4x018	35+35	1.71
4x028	110	1.09
4x029	220	0.54
4x030	240	0.50

160 VA 110 x 40mm 1.8Kg Regulation 8%		
SERIES	SECONDARY No Volts	RMS Current
5x011	9+9	8.89
5x012	12+12	6.66
5x013	15+15	5.33
5x014	18+18	4.44
5x015	22+22	3.63
5x016	25+25	3.20
5x017	30+30	2.66
5x018	35+35	2.28
5x026	40+40	2.00
5x028	110	1.45
5x029	220	0.72
5x030	240	0.66

225 VA 110 x 45mm 2.2Kg Regulation 7%		
SERIES	SECONDARY No Volts	RMS Current
6x012	12+12	9.38
6x013	15+15	7.50
6x014	18+18	6.25
6x015	22+22	5.11
6x016	25+25	4.50
6x017	30+30	3.75
6x018	35+35	3.21
6x026	40+40	2.81
6x025	45+45	2.50
6x033	50+50	2.25
6x028	110	2.04
6x029	220	1.02
6x030	240	0.93

300 VA 110 x 50mm 2.6Kg Regulation 6%		
SERIES	SECONDARY No Volts	RMS Current
7x013	15+15	10.00
7x014	18+18	8.33
7x015	22+22	6.82
7x016	25+25	6.00
7x017	30+30	5.00
7x018	35+35	4.28
7x026	40+40	3.75
7x025	45+45	3.33
7x033	50+50	3.00
7x029	110	2.72
7x029	220	1.36
7x030	240	1.25

500 VA 140 x 60mm 4Kg Regulation 4%		
SERIES	SECONDARY No Volts	RMS Current
8x016	25+25	10.00
8x017	30+30	8.33
8x018	35+35	7.14
8x026	40+40	6.25
8x025	45+45	5.55
8x033	50+50	5.00
8x042	55+55	4.54
8x028	110	4.54
8x029	220	2.27
8x030	240	2.08

625 VA 140 x 75mm 5Kg Regulation 4%		
SERIES	SECONDARY No Volts	RMS Current
9x017	30+30	10.41
9x018	35+35	8.92
9x026	40+40	7.81
9x025	45+45	6.94
9x033	50+50	6.25
9x042	55+55	5.68
9x028	110	5.68
9x029	220	2.84
9x030	240	2.60

**Why a Toroid?**  
 \* Smaller size & weight to meet modern 'slimline' requirements.  
 \* Low electrically induced noise demanded by compact equipment.  
 \* High efficiency enabling conservative rating whilst maintaining size advantages.  
 \* Lower operating temperature.

**Why ILP?**  
 \* Ex stock delivery for standard 240v range.  
 \* Fast prototype service available.  
 \* 3 weeks despatch for special orders.  
 \* 2 year no quibble guarantee.  
 \* No price penalty for call-off orders.

Prices including P&P and VAT

VA	Size	£	VA	Size	£
15	0	7.06	160	5	12.17
30	1	7.67	225	6	13.75
50	2	8.90	300	7	14.97
80	3	10.06	500	8	19.60
120	4	10.65	625	9	22.30

For 110V primary insert "0" in place of "X" in type number.  
 For 220V primary (Europe) insert "1" in place of "X" in type number.  
 For 240V primary (UK) insert "2" in place of "X" in type number.  
**IMPORTANT: Regulation - All voltages quoted are FULL LOAD.**  
 Please add regulation figure to secondary voltage to obtain off load voltage.

**Mail Order** - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.  
**Trade** - We will open your credit account immediately upon receipt of your first order.

**Post to:** ILP Electronics Ltd., Dept. 2  
 Graham Bell House, Roper Close,  
 Canterbury, Kent. CT2 7EP  
 Tel: (0227) 454778 Telex: 965780



# THE ETI LOGGIT DATA LOGGER

Don't get caught lying down on the job — let the ETI LOGGIT take the data while you're off having fun. Design, development and words by Phil Walker.

The ETI LOGGIT is a single PCB unit which can automatically measure and store analogue data over a period of minutes, days or weeks. A single LOGGIT card can store over 2000 separate

readings to an accuracy of better than 1% (when suitably calibrated).

The device can be operated in four main modes. These are:—  
measure and store until memory

full; measure and store until trigger signal is detected; measure and store until 1024 measurements after trigger signal; start measuring at the trigger signal and stop when full. All these modes have their uses and others may occur to the user. The most useful as far as the author is concerned is the third:—  
measure and store until 1024 measurements after the trigger signal. In this mode you gather and keep data for an equal time before and after the trigger event, allowing both possible causes and consequences to be observed.


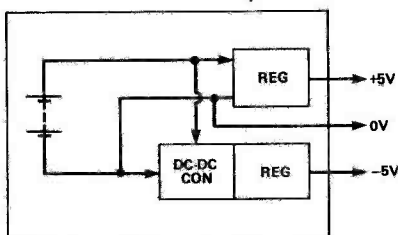


Fig. 1 Block diagram of the ETI LOGGIT.
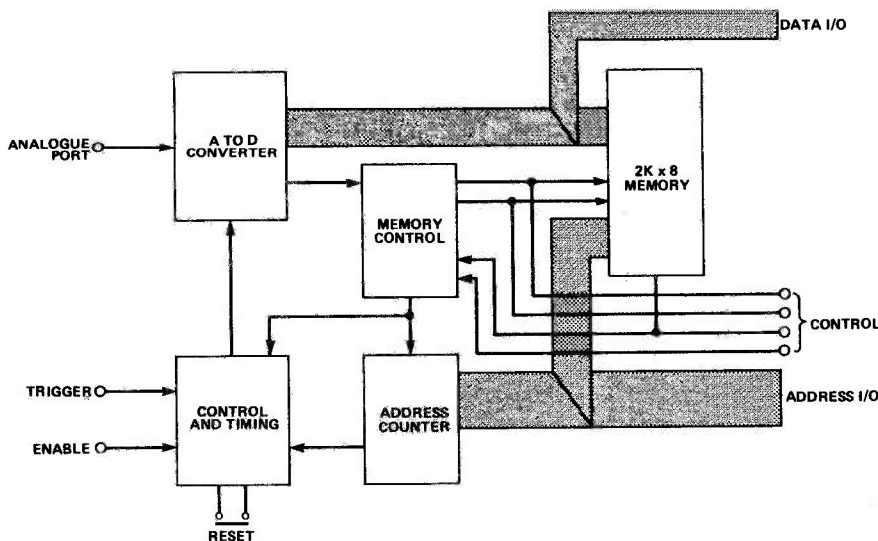
## The circuit

Two devices form the basis of this project. The first is the 8703 A to D converter made by Teledyne. This converts the incoming analogue signal to an 8 bit digital code. This is then stored in the second main device, the 6116 CMOS 2K × 8 memory. The rest of the devices are present to control the operation of the unit and provide the addresses to the RAM and the necessary power supplies for all the devices.

The control logic section of the unit starts with a programmable timer device which produces trigger pulses at a rate of from 10 every second to 1 every 25.5 seconds with the component values specified. These pulses start the ADC conversion cycle which, when it finishes, triggers another pulse which writes the data into the memory. Once this is





The first thing to consider is probably the most important device in the project. This is the 8730 analogue to digital converter. This works by integrating the input current and subtracting pulses of a reference current from it to maintain the integrated charge at or near zero. The number of reference current pulses necessary during a conversion period is counted and latched onto the output data bus at the end of conversion. The input to this device is effectively maintained at virtual earth potential and acts as a summing point for current.

Almost all the necessary control logic is contained within the device for A to D conversion, the only external signals needed being a start command input and busy and data valid outputs. For the convenience of computer bus connection the device is provided with an output enable pin which allows the data output to be forced into a high impedance state.

The rest of the circuit can be considered as four main blocks. The first of these is the memory. This consists of a 2k x 8 CMOS RAM type 6116 or, with a little modification, 5516. This device is used to store all the data gathered by the unit. These CMOS devices are specified because they consume very little power when not actually active. In the data logging mode of operation the memory will be active for only about 1µs at each sample time. Its quiescent current is about 100nA while its operating current is up to 50mA. Since the memory is only active for 1µs in 10ms at the fastest operation rate its average consumption will be only about 5µA worst case.

The next section we shall consider is the power supply. This is a simple split rail ±5 volt supply using low-power IC regulators. The only complication here is that the raw negative supply is generated by a DC-DC converter chip so that the whole unit can run from a single battery. The use of this device does, however, limit the input voltage to 10.5V absolute maximum.

The last two sections make up the control logic of the unit. The first and least complicated of these is the address counter. This consists of a 12-bit CMOS counter which, by means of Q1, is incremented after each data byte has been written into the memory. The outputs from this counter are coupled to the memory and output socket via 4k7 resistors. This is done so that external devices can access the memory without damaging the counter

outputs simply by overdriving the existing logic state. Only 11 addresses are needed to control the memory so the twelfth output is used to indicate that the memory is full in modes 1 and 4.

The final section consists of all the bits and pieces which did not fit into the other categories. IC5 is a CMOS programmable timer which determines the sample rate of the unit. The basic timing period is set by the combination of C6/R26 but by means of SW2 to 9 any multiple from 2 to 256 of the basic period are selectable. Note that at least one switch must be closed to get any pulses at all and that the multiple obtained is one greater than the binary pattern set. SW2 is on the least significant bit.

The pulses generated by IC5 then pass to IC1d. This acts as a gate to allow them through only when required. From here they go to IC6b which generates a narrow pulse each time its input goes high. Note that the enable input from SK1 pin 8 must be high for this to happen. The pulse from IC6b then starts a conversion cycle in IC2. When IC2 has finished its A to D conversion it puts the result on the data bus and sets its DATA VALID output high. The transition from low to high triggers IC6a to produce another narrow pulse — about 1µs wide — which puts the select and write enable inputs of the memory low and writes the data into the location currently set up on the address lines.

The signal on the CS input to the memory is inverted by Q1 and R37 to drive the clock inputs to the address counter and IC4. This inversion is necessary because the counters increment on the negative-going edge of the clock signal and (as was found the hard way on the prototype) it takes a long time for their outputs to stabilise, which causes data to be written into the wrong addresses in some cases. An FET was used in this position so that there would be minimal loading on the CS line, but it still can be overdriven by external sources.

The mode of operation of the unit is determined by connections to IC1a and b and IC4. IC1a and b form a simple set-reset latch whose state is determined by the signals selected on link points A, B, C, D and E. Points D and E are the inputs to the latch; C is the trigger input from an external event — positive true; A is the reset signal from the on-board switch; and B is the memory full signal from IC3. Link points X, Y and Z are used to select the required output signal.

The operation of this section must now be considered in the light of the modes of operation selected on the links.

Mode 1 — link A-D, B-E, X-Z (sample until memory full): this mode starts when the reset button is pressed and released. IC1b output is forced low by the reset line via D3; IC3 and 4 are made to start at zero and pulses are allowed through IC1d. Data sampling will occur until Q12 of IC3 goes high. At this time IC1a output is forced low by the signal from IC3 Q12 via D4. This will cause IC1b output to go high and stop further pulses passing IC1d.

Mode 2 — link A-D, C-E, X-Z (sample continuously, stop when trigger high): in this mode the reset button is pressed only to set the IC1a and b latch into the correct state. Data sampling then proceeds continuously until a high condition via D2 from SK1 pin 9 sets IC1a output low, and thus IC1b output high. This stops pulses passing IC1d as before. The memory now contains 2048 samples up to the trigger point, providing, of course, that more than 2048 samples have been processed since the reset button was pressed. Note that in this mode IC3 can stop with any count but IC4 will be input to it has been held high by IC1a and b latch until the trigger point. This condition can be used when reading data out to provide a trigger or sync signal to indicate where the original trigger signal occurred relative to the stored data.

Mode 3 — link A-D, C-E, X-Y (sample continuously, stop 1024 samples after trigger input high): this is possibly the most useful mode. The reset button is used to set the IC1a and d latch as before, but this time the output from IC1a holds IC4 in a reset condition. The Q11 output from this device is therefore low and enables pulses to pass IC1d as before. As in the previous mode, a high level on the trigger input will cause the IC1a and d latch to change state but this time all it does is to remove the reset condition from IC4. Sampling will continue but IC4 will be clocked as well as IC3. When 1024 more samples have been taken, the Q11 output of IC4 will go high and prevent pulses passing through IC1d. Using this mode means that data can be viewed both before and after the trigger event. The sync output will indicate the original trigger point as before.

Mode 4 — link A-B-E, C-D, X-Z (start on trigger, stop when full): in this

mode, the reset button is used to set the IC1a and d latch with IC1a output low and IC1d high. It also resets IC4 via D5 and IC3 directly. Pulses are prevented from passing IC1d for the time being. When a trigger pulse occurs, IC1b output is set low and thus IC1a high. This then allows pulses to pass IC1d and data sampling will occur. After 2048 samples, IC3 Q12 will go high setting the latch back to its original state and preventing further operation. While sampling is taking place, IC4 would be held in its all zeroes state by IC1a output and thus will indicate the trigger point as usual.

Unfortunately, in this mode if further trigger conditions are supplied extra samples will be taken at the trigger times and may corrupt the data, so multiple triggers should be avoided.

So far we have considered only how to get data into the unit. Now we must look at how to get it out again. There are two main ways that this can be achieved. The first is to use a computer with 24 I/O lines to override the address and control lines and read out the data. In doing this it must set the DStable input to a low level. This prevents IC6a from producing clock pulses and pulsing the memory control lines. It also turns off the data output buffers in the ADC to allow the memory free access to the data path.

A second and much simpler method of examining the data is to attach a D to A converter on the data lines and use the internal counter IC3 to scan through the memory. In this configuration, the DIS pin on SK2 is held low inhibiting IC6a and the ADC data outputs and, via D6, holding the IC1a and d latch such that IC4 is released from the reset condition. WE is left open or connected to +5V. OE is held low or, in the case of the 5516 memory being used, connected to the PCB to CS line. A high frequency clock signal should be applied to the CS pin of SK2. While the signal is low, data is read out of the current location pointed to by the outputs of IC3 and should be stored in the DAC on the rising edge. The rising edge of this clock signal is inverted by Q1 and used to clock IC3 and IC4, in order to be ready for the next low part of the clock input. By this means, if the output of the DAC is displayed on an oscilloscope, a continuous waveform corresponding to the sampled data can be observed. The output from the SYNC pin on SK2 indicates the original trigger point by a high-to-low transition.

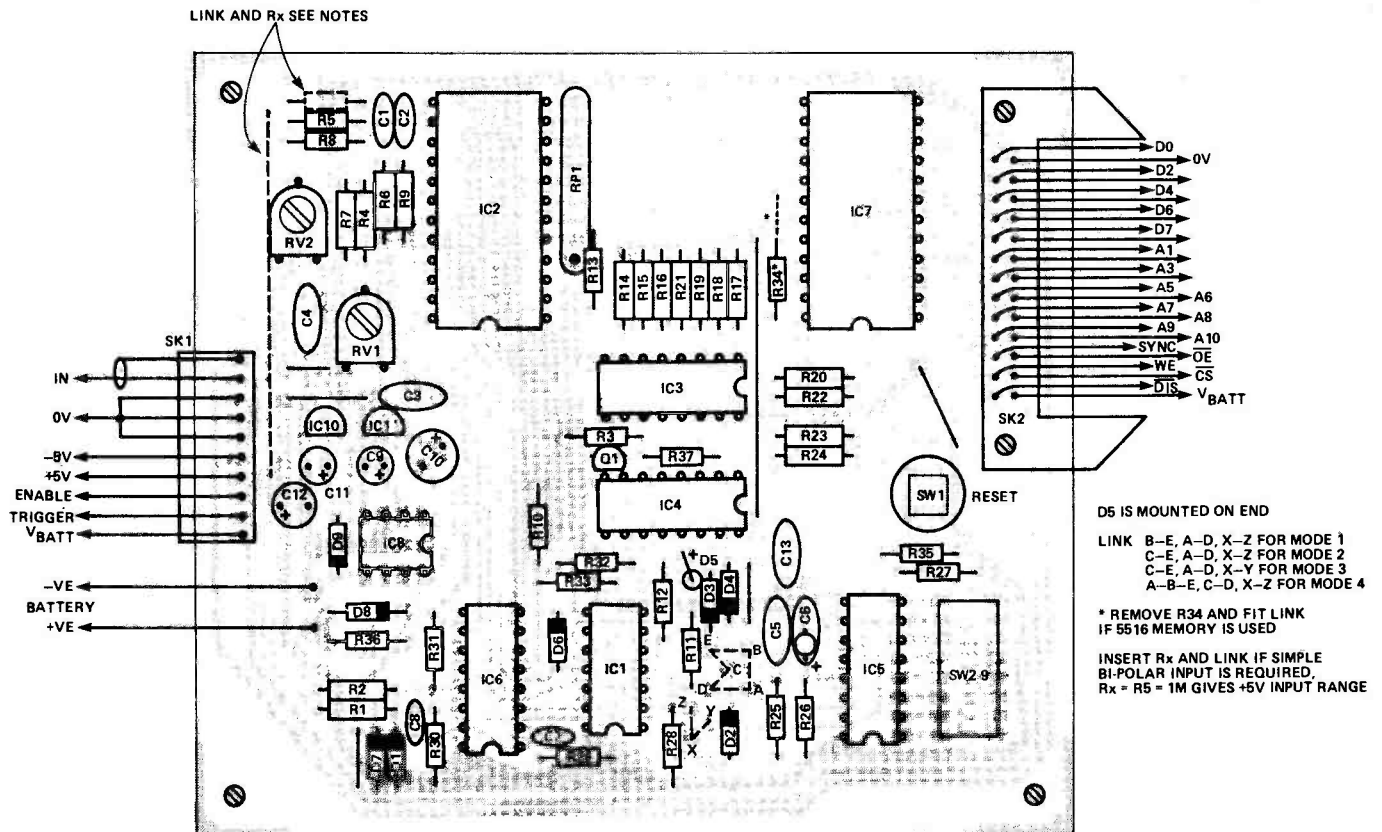


Fig. 3 The PCB overlay for the project.

complete the address counter is incremented ready for the next cycle.

In the control logic there is also a group of devices whose function is to stop and start the whole process according to the particular operational mode required. These act by preventing the trigger pulses reaching the ADC once the memory is full or the trigger condition has occurred. By means of links, four separate modes of operation can be realised. These will be described in greater detail later in this article.

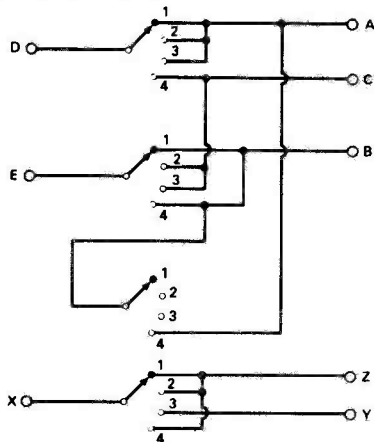


Fig. 4 If the links are a nuisance, you can use a 4P 4W switch instead (yes, we know it's not standard...).

The last part of the unit is the power supply, which is fairly conventional except that a voltage converter is used to get the negative supply for the ADC. This allows us to use a single 9 volt battery; in fact, the battery may be necessary only while transporting the unit, as power can normally be supplied via one of the connectors and anything from about 8 to 10 volts is suitable.

Read-out of data from the unit can be achieved in several ways, the simplest of which is to connect the data bus to the D to A converter and, with OE low and WE high, apply a series of narrow positive-going pulses to the CS input. This will result in output from the D to A converter reproducing the original sampled input. This can then be displayed on an oscilloscope for visual examination. A synchronisation signal is available separately to indicate the trigger point on the original data.

Alternatively, a microcomputer with the capability of at least 24 I/O lines could be used to read all the data and even erase old data if required. Other methods could be used if less than 24 I/O lines are available but with reduced flexibility.

### Construction

You should find that this project is reasonably easy to put together. All the components with the exception of the battery mount on the PCB.

The order of construction is not particularly critical, but we would recommend that you start with the resistors and the six wire links. The wire links should be made with insulated single strand wire to prevent accidental shorts. Next would come the diodes, making sure they are the right way round, followed by IC sockets, IC9 and 10, Q1, capacitors, variable resistors, switches and connector sockets.

When this stage is reached, check the power supply for continuity to the IC sockets and freedom from shorts to other places. Plug in IC8 and apply 8 to 9 volts to the battery terminals. You should be able to detect +5V across C13 and -5V across C4. If you do not, disconnect the battery and check D8, 9, IC8, 9, 10 for correct placement, etc.

Once the power supply section is operational, plug in IC5 and check, if you have access to a scope or logic probe, that pulses appear on pin 10. To do this, close SW2 and open SW3 to 9. This

## PARTS LIST

### RESISTORS (5% carbon film 1/4 watt unless stated)

R1,2,9,36	1k0
R3,24,27,31-35,37	10k
R4,7,10-12,28-30	100k
R5,26,Rx	1M0
R6	100R
R8	220k
R13-23	4k7
R25	5k6
RP1	8 × 100k SIL resistor pack
RV1	22k min. horiz. preset
RV2	100k min. horiz. preset

### CAPACITORS (min ceramic unless stated)

C1	270p
C2	68p
C3,4,5	100n
C5	330p
C6	100n — or as required
C7,8	100p
C9,11,12	10μ 16V electrolytic radial lead
C10	100μ 16V electrolytic radial lead

### SEMICONDUCTORS

IC1	4001
IC2	8703 ADC (Teledyne)
IC3,4	4040
IC5	ICM7240
IC6	4528
IC7	6116 or 5516 see notes
IC8	ICL7660
IC9	78L05
IC10	79L05
Q1	VN10KM
D1-7,9	1N4148
D8	1N4001

### MISCELLANEOUS

SK1	10 way 0.1in pitch PCB connector
SK2	26 way P.O. style IDC connector, rt. angle
SW1	min. PCB mounting keyboard switch
SW2-9	8 way single pole DIL switch

IC sockets: 8,14,4 × 16,2 × 24 way; 10 off 1 mm terminal pins; PP3 size 8.4 volt 110 mA-h Ni-Cd if req'd; PCB (see Buylines).

gives the fastest clock time — note that at least one switch must be closed for proper operation. Next insert IC1, 3, 4 and 6. Link A to D and Z to X. Temporarily connect SK1 pin 8 to pin 7 and with a thin piece of wire bridge pins 21 and 23 on IC2's socket. Power up the unit with the battery, etc., and press the reset button for a moment. It should now be possible to detect a count sequence on the address

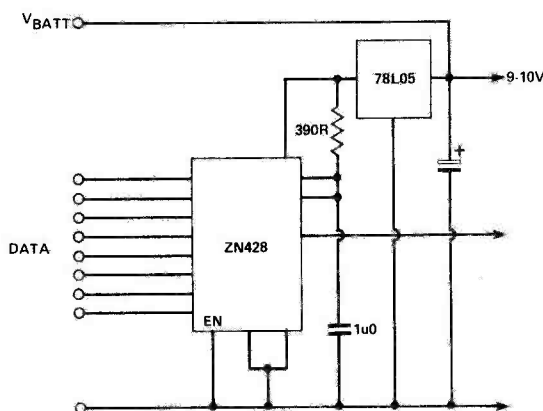


Fig. 5 Setting up circuit.

pins of SK2. Pulling SK2 pin 25 low should stop it, as should removing the link between SK1 pins 7 and 8.

With SK2 pin 25 low and the link removed from SK1, feed in a clock signal to SK2 pin 24: about 1kHz 3 to 5 volt TTL compatible will do. A count sequence should again be observed on the address pins of SK2.

Once this stage is reached successfully, remove the power source and plug in IC2 and 7. Be careful with these as they are sensitive to static damage and are also expensive. Note that if you use the 5516 CMOS RAM instead of the 6116 then R34 should be omitted and a link inserted between IC7 pins 18 and 20. By the way, you should also remove the thin wire between IC2 socket pins 21 and 23 before inserting IC2. You can now repeat the tests and you should get the same results. Check also that the power supply current is not more than 20mA (our prototype weighed in at 13mA). Your LOGGIT should now be ready for action.

### Setting Up And Use

The easiest way to set the unit up for use is with the circuit shown in Fig. 4. The DAC is connected to take the output from the ADC on the PCB without latching it. This works because the ADC holds the data from the last conversion until 5μs or so before presenting the new data. With this arrangement it is possible to monitor the ADC operation while making adjustments.

To make things easy while setting up, link A-D and X-Z only and press the reset button briefly. Make sure that Rx is present if you want to monitor a bipolar input.

With R5 and Rx each at 1M0 and the other components as shown it should be possible to monitor a ±5V input, while omitting Rx will set the range at 0 to +10V. Increasing R5 (and Rx) will increase the full scale input voltage and vice-versa.

It is probably easier to set the circuit up initially if Rx is omitted. Short the analogue input to ground and adjust RV1 to the point just below where the output digital data changes from 0000 0000 to 0000 0001. Next apply the full scale input voltage and adjust RV2 to the point where the digital output has just changed from 1111 1110 to 1111 1111. Go back and check the first adjustment, and repeat both adjustments until they are correct. Next, ramp the input voltage slowly through its range and check that the DAC follows it with no sudden jumps, apart from those caused by the slow sample rate.

When you have got this far, you can insert Rx if you wish and adjust RV1 to the point where the digital output just changes from 0111 1111 to 1000 0000 when the analogue input is grounded.

To use the unit for data collection, set up the mode on the links as described and the sample rate on the switches (and C6/R26 if necessary). The PCB can then be plugged into a suitable connector on which pins 7 and 8 are connected. A supply of 8 to 10 volts should be made available on pin 10, or the unit's battery used. The analogue signal should be applied to pin 2 and the trigger signal, if used, to pin 9. Press the reset button and the unit should start working.

Once the data has been collected, the unit must not be

# PROJECT : Data Logger

disconnected from its power source or the data will be lost. The simplest way to ensure this is to keep a PP3 sized Ni-Cd battery connected to the terminals on the PCB permanently. If this is the case, the unit can be disconnected from the monitoring point and taken away to the readout unit. So long as the PP3 Ni-Cd is reasonably charged, the unit should be able to retain data for a few hours. Note that power can also be supplied via SK2 while reading the data out.

In order to get sensible output pictures on an oscilloscope it is desirable to ensure that several samples are taken in the period of the fastest fluctuation of the monitored voltage.

## BUYLINES

Nothing we have used here should cause any problems for our UK readers. All the components are readily available from advertisers in this magazine, such as Watford, Technomatic, Rapid, and others. The PCB is, as ever, available through the ETI PCB service.

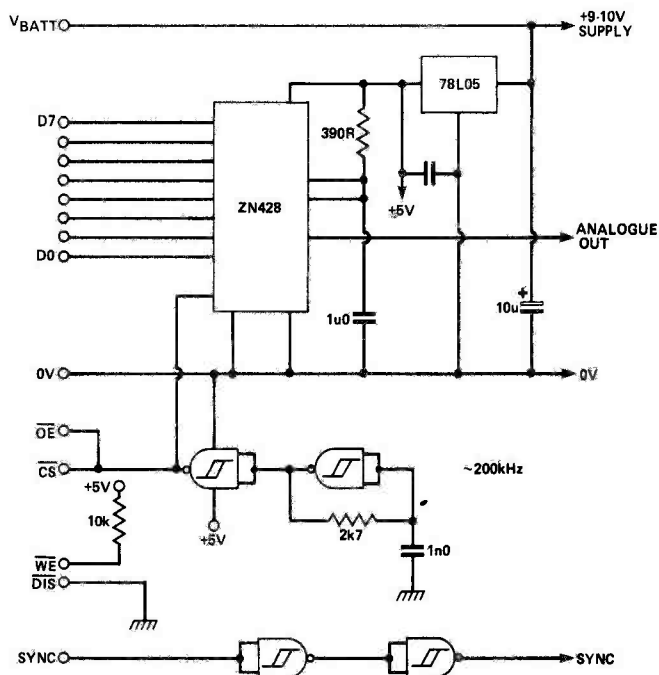


Fig. 6 Using a DAC to produce an oscilloscope display. Another alternative would be to use switches (fully de-bounced) to make the LOGGIT step through data points one at a time, and use this to drive an analogue or digital meter (via a DAC) or suitably buffered LEDs (but you've got to really love hex for that . . .).

ETI



"OK YOU LOT - WE'VE COME TO GET THIS DIGITAL LOGGER PROJECT STOPPED!"



# BI-PAK BARGAINS


### SEMICONDUCTORS FROM AROUND THE WORLD

**100** A collection of Transistors, Diodes, Rectifiers & Bridges SCR's Triacs IC's & Opto's all of which are current every-day useable devices

Guaranteed Value Over £10 Normal Retail Price

Data etc in every pack. Order No. VP56

Our Price **£4.00**

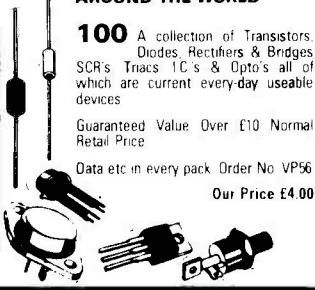

### VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/4-1/2 Watt Pre-Formed	£1.00
VP3	200	1/2 Watt Min Carbon Resistors Mixed	£1.00
VP4	150	1/2 Watt Resistors 100 ohm-1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramics Disc. 1pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc. 68pf - 015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	50	Electrolytics - All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 5.6pf - 150pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	25	01uF 250v Min. layer metallised Polyester Capacitors	£1.00

### VALUE PACKS

Pak No.	Qty	Description	Price
VP16	50	Wirewound Res. 9W (avg) Ass. 1 ohm - 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Rocker Switches 2 Amp 240v	£1.00
VP21	15	2" High Bright RED LEDs in plastic encapsulation - Large area light source	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00

### VALUE PACKS

Pak No.	Qty	Description	Price
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots. 40 mm 22K 5 x Log. 5 x Lin	£1.00
VP25	10	Slider Pots. 40 mm 47K 5 x Log. 5 x Lin	£1.00
VP26	15	Small 125° Red LED'S	£1.00
VP27	15	Large 2" Red LED'S	£1.00

### TRANSISTOR CLEARANCE

All Sorts Transistors. A mixed bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes Instructions for making Simple Transistor Tester. Super Value

Order No. VP60 **£1.00**

### BI-PAK'S OPTO SPECIAL

A selection of large and small sized LED's in various shapes, sizes & colours, together with 7 Segment Displays both anode & cathode plus photo transistors emitters and detectors. Cadmium Cell ORP12 and Germ. photo transistor OCP71 included. In all a total of 25 Opto pieces valued over £12 Normal Price

Order No. VP57

Our Super Value Price Just **£5.00**



50-way x 2.1 pitch Edge Connector (Gold) (O/No. AMP163279-2) **£1.20 each £50 per 50 off**

### VALUE PACKS

Pak No.	Qty	Description	Price
VP28	10	Rectangular 2" RED LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vlt's. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vlt's. Coded	£1.00
VP31	10	5 Amp SCR's TO-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR's TO-66 Up To 400v Uncoded	£1.00
VP33	200	Sil. Diodes Switching Like IN4148 DO-35	£1.00
VP34	200	Sil. Diodes Gen. Purpose Like OA200/BAX13/16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1/4" Std	£1.00
VP42	10	Black Heatsinks To Fit TO-3, TO-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x TO-3 2 x TO-66 Size	£1.00
VP45	50	BC107/8 Type NPN Transistors Good Gen. Purpose Uncoded	£1.00
VP46	50	BC177/8 Type PNP Transistors Good Gen. Purpose Uncoded	£1.00
VP47	10	Silicon Power Trans. Similar 2N3055 Uncoded	£1.00

### ELECT & PIEZO BUZZERS

**PIEZO**  
Miniature round piezo-electronic buzzer. White plastic. Low consumption. Frequency: 4kHz approx. Output: 70dB (A) @ 1 typ. Power: 12Vd.c. 4mA. Dims: 22 (dia.) x 11.5mm. Fixing Centres: 26.5mm.

O/No. VP 107 **£1.05**

**PIEZO**  
Piezo buzzer White plastic. 90mm leads. For use on a.c. mains. Frequency: 3.5kHz approx. Output: 85dB (A) @ 1m typ. Power: 240V.a.c. 5mA. Dims: 32 (dia.) x 14mm. Fixing centres: 38mm.

O/No. VP 108 **£1.25**

**ELECTRONIC**  
Miniature electronic buzzers. Solid state Ivory plastic. 150 leads. Frequency: 500 Hz approx.

Dims: 22 x 16 x 15mm  
Output: 82dB (A) @ 1m typ  
Fixing centres: 26mm  
3V 25mA: D/No. VP 82  
9V 25mA: D/No. VP 84

**95p each**



### HIGH QUALITY MODULES FOR STEREO, MONO & OTHER AUDIO EQUIPMENT

#### Audio Amplifiers

O/No.	POWER	O/P	MAX SUP. VOLTAGE	PRICE
AL 30A	10 Watts		30V	<b>£4.95</b>
AL 60	25 Watts		30-50V	<b>£5.92</b>
AL 80	35 Watts		40-60V	<b>£8.75</b>
AL 120	50 Watts		50-70V	<b>£15.22</b>
AL 250	125 Watts		50-80V	<b>£20.60</b>

#### Stabilised Power Supplies -

O/No.	Output current	2.5 Amps	Price
SPM 120/45	40-48V		<b>£8.05</b>
SPM 120/55	50-55V		<b>£8.05</b>
SPM 120/65	60-65V		<b>£8.05</b>

#### Mono Pre-Amplifiers - Operating Vtg. 40-65V

O/No.	Description	Price
MM 100	Suitable for Disco Mixer	<b>£14.75</b>
MM 100G	Suitable for Guitar Pre-Amp Mixer	<b>£14.75</b>

#### Magnetic Cartridge Pre-Amplifier

O/No. MPA30. Sup Vtg. 20-30V. Price **£4.29**

#### Monographic Equaliser

GE 100 MKII 10 Channel  
OUR PRICE ONLY **£20.00**

Full Specifications and Data available on request. Please send self-addressed envelope.

#### RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size, 2 cross point size 4 & 6. 1 Ratchet handle, 5-in-1 Kit. **£1.45 each.** O/No 329B

### HYBRID LED COLOUR DISPLAYS

Red, Green, Yellow - 3/5/6 inch Mixed types and colours NUMERIC & OVER-FLOW Common Anode/Cathode. GaAsP/GaP. Brand New, Full Data incl.

10 pieces (our mix) **£4.00**  
Normal Retail Value Over £10.00  
Order No. VP58



### IC BARGAINS

40 Assorted TTL CMOS INTEGRATED CIRCUITS 74 Series & CD4000 Series - All new Gates, Flip-Flops - MSI etc. GREAT VALUE Data Book & Sheet included

40 Pieces (Our Mix) **£4.00** O/No VP40

## TECASBOTY THE ELECTRONIC COMPONENTS AND SEMICONDUCTOR BARGAIN OF THE YEAR!

This collection of Components and Semiconductors for the hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc., PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for ONLY at BI-PAK Remember, stocks are limited so hurry! You can call us on 0920 3182/3442 and order with your Barclaycard or Access Card - 24hr Answerphone Service NOW. Order No. VP 85. **just £7.00**



### OPTO 7-Segment Displays

Brand new 1st Quality LITRONIX DL 707R 14-pin

Red 0.3" Common Anode Display 0-9 with right hand decimal point TTL compatible 5v DC Supply. Data supplied

IN	5 pieces	<b>£3</b>	(60p each)
PACKS	10 pieces	<b>£5</b>	(50p each)
OF	50 pieces	<b>£20</b>	(40p each)
	100 pieces	<b>£35</b>	(35p each)
	1,000 pieces	<b>£300</b>	(30p each)

THE MORE YOU BUY - THE LESS YOU PAY

VP38	100 Silicon NPN Transistors - All Perfect. Coded. Mixed Types With Data And Eqvt. Sheet No Rejects. Fantastic Value	<b>£3.00</b>
VP39	100 Silicon PNP Transistors - All Perfect. Coded. Mixed Types With Data and Eqvt. Sheet No Rejects. Real Value	<b>£3.00</b>
2N3055	The best known Power Transmitter in the world - 2N3055 NPN 115W. Our Bi-Pak Special Offer Price.	
10 off	50 off	100 off
<b>£3.50</b>	<b>£16.00</b>	<b>£30.00</b>
BD312	COMPLIMENTARY PNP POWER TRANSISTORS TO 2N3055 Equivalent MJ2955 - BD312 - TO3 Special price <b>£0.70</b> each. 10 off	<b>£5.50</b>

### BI-PAK SOLDER - DESOLDER KIT

Kit comprises: O/No. VP 80  
1 High Quality 25 Watt General Purpose Lightweight Soldering Iron 240v mains incl. 3/16" (4.7mm) bit.  
1 Quality Desoldering Pump High Suction with automatic ejection Knurled anti-corrosive casing and Teflon nozzle 1.5 metres of De-Soldering braid on plastic dispenser.  
2 vds (1.83m) Resin Cored Solder on Card  
1 Heat Shunt tool tweezer Type  
Total Retail Value over **£12.00**  
OUR SPECIAL KIT PRICE **£9.95**



### BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises  
1 Expo Mini Drill 10,000RPM  
12v DC incl. 3 collets & 3 x Twist Bits  
1 Sheet PCB Transfers 210mm x 150mm  
1 Etch Resist Pen  
1 1/2lb pack FERRIC CHLORIDE crystals  
3 sheets copper clad board  
2 sheets Fibreglass copper clad board  
Full instructions for making your own PCB boards  
Retail Value over **£15.00**  
OUR BI-PAK SPECIAL KIT PRICE **£9.95**  
ORDER NO. VP 81



### DIGITAL VOLT METER MODULE

3 - 7 segment displays Basic Circuit 0-2v - instructions provided to extend voltage & current ranges Operating voltage 9/12v. Typ Power Consumption 50mA

O/No. VP99 Once only price **£9.95**

#### SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq. Ins	Price
FB1	4	9 x 2 1/2"	100	<b>£1.50</b>
FB2	3	11 x 3"	100	<b>£1.50</b>
FB3	4	13 x 3"	156	<b>£2.00</b>

#### DOUBLE SIDED FIBREGLASS BOARD


FB4	2	14 x 4"	110	<b>£2.00</b>
-----	---	---------	-----	--------------

### SILICON BRIDGE RECTIFIERS

Comprising 4 x 1 1/2 Amp rectifiers mounted on PCB. VRM - 150 vts IFM - 1.5 Amps

Size: 1 inch square  
10 off **£1.00**  
50 off **£4.50**  
100 off **£7.50**

ORDER NO. 4R1 B Rect.

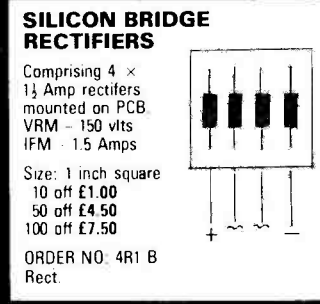

# BI-PAK

Send your orders to Dept EM/2 BI-PAK PO BOX 6 WARE, HERTS SHOP AT 3 BALDOCK ST. WARE, HERTS  
TERMS CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182, GIRO 388 7006  
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING

Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add £1.00 per Total order.



# DESIGN ICs ON YOUR MICRO!

**It will come — but don't hold your breath waiting for a package to run on your trusty ZX81! TI has recently announced a design-it-yourself facility for professional computers.**

**B**y TI's reckoning, the semi-custom IC market will expand from the \$100 million share it has now to around \$990 million in 1990 (a growth from 10% to 30% of a total market that is itself growing). That, in anyone's terms, is big money, but there is a very low penetration of semi-custom ICs to the smaller companies in Europe that, whilst making up 80% of the total in number of all European electronics companies, hold only 40% of the manufactured equipment market.

These companies have a turn-over of \$1m per year, or less, so cannot afford their own in-house semi-custom design team, nor can they afford to have a semiconductor manufacturer design special purpose devices for them. In fact, with such a small turn-over, a large company like TI is kept too busy by its big customers to be particularly worried.

None the less, 40% of the electronic equipment market is not to be sneezed at, especially when this could translate into an extra \$660m of semi-custom ICs! Something had to be done, but it would not have to cost the small companies too much, and it also would have to be relatively cheap on TI's design time.

The solution has been to adapt an existing software package, TI's Transportable Design Utility (TDU) which has been used with success on a number of different main-frame computers. After adaptation, this suite of programs can now run on a fairly heavy-weight micro, such as an IBM XT/PC or TI's own Professional Computer, with 512K of RAM, and 10M Winchester disk (this isn't a complete list of requirements — contact TI for more details if you're seriously interested).

The package allows you to describe the hardware you want to integrate using TI's hardware description language (HDL) and the test patterns you want it to fulfil using test description language (TDL). With some software packages available from other suppliers, but which do not come with the basic package from TI, you can get the facility to actually draw circuit diagrams on the screen. However, TI say that once you are used to it, it is as easy to use HDL to describe a circuit lay-out as it is to draw a circuit diagram.

The software will then check that you have followed the appropriate electrical rules — in particular, it will check fan-in, fan-out and output contention in the design. It also checks to see if the circuit you have designed is easily testable. Finally, it simulates the action

of the circuit, and checks to see that the results you get are the same as your expectations.

The major stage that the software does not do for you is to lay out the IC. To do this, you will have to send a disk containing the circuitry description to TI, who will then use their main-frame to finish the job. However, what you have got at this stage is a finished circuit that, when integrated on silicon, will work.

There are several different ranges of semi-custom logic sold by TI, and the software will support the full range, from SN54/74 HCMOS standard cell family, which is second-sourced by Signetics, to the recently introduced TAHXX HCMOS gate arrays. Further, TI say that any future semi-custom products will be supported.

This all sounds very expensive, you may think. But it isn't — the basic software will cost \$500 for the software itself and all current product information. 'Active' customers, ie those who are actively engaged in designing with semi-custom logic, will receive support and latest releases free of charge.

The basic idea of the system is to transfer the most costly and time-consuming part of the design process — getting a circuit that will work using the standard cells of a semi-custom logic family — to the customer's own personal computer. The final stage, the laying out of the mask, has to be done on a main-frame at the moment, so can only be done by TI themselves. However, there should still be a very significant saving for the small customer for whom semi-custom logic may be presently far too expensive.

The software package described here, the PC TDU, will be available from TI as of the 1st December 1984. TI are at Manton Lane, Bedford, MK41 7PA.

## Making A New IC

The design of new ICs is done with a great deal of help from computer-aided design packages. In fact, the PC TDU package from TI is a cut-down version of the software TI themselves use to design their own devices. Obviously, their in-house packages must be able to deal with non-standard logic cells, whereas PC TDU deals only with standard cells.

All the circuit design and checking is done with the help of the computer, up to and including the die lay

out. However, it has been found that no computer algorithm can substitute for a design engineer's experience in this last stage, particularly when trying to avoid parasitic devices — only certain levels of checking can be performed by computer, so there is a substantial human involvement in the exact details of the final layout, in contrast to semi-custom layout, which can be almost entirely automated.


The end of the design effort is the programme tape, which is used to produce the masks for the different diffusion and metalisation stages of the IC's production. After photo-reduction, these are used to make a batch

of prototype wafers.

Before the wafers are sliced up, the individual dies are 'probed' to see if they can perform certain tests. If this is satisfactory, the wafer is then sliced and the individual ICs packaged.

The next phase is to determine whether the prototype ICs do what they should. They are checked against the provisional data sheet, to see if either or both require ammendment — only in 1% of cases does the actual IC have to be changed.

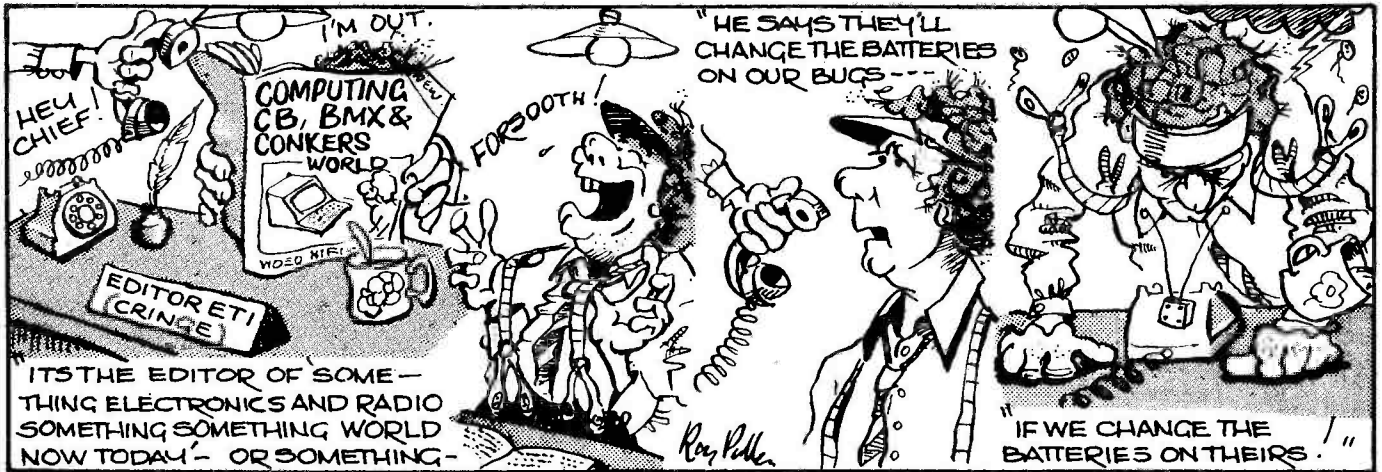
Production now begins, and there's a new IC on the market!



ETI
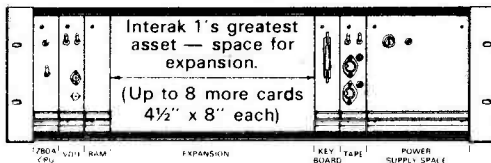
## Interak 1 A METAL Z80A COMPUTER

Colleges, Universities, Individuals: Build your own modular Z80A-based metal 19" rack and card Interak computer. Uses commonly available chips — not a single ULA in sight (and proud of it). If you can get your own parts (but we can supply if you can't) all you need from us are the bare p.c.b.s and the manuals.



(P.c.b.s range in price from **£10.95** to **£17.75** + VAT; manuals **£1 - £5**.)

The Interaktion User Group has 14K BASIC, Assembler, Fig Forth, Disassembler, Debug, Chess and a Book Library, Newsletters etc. No fears about this one going obsolete — now in its fifth successful year! Send us your name and address with a 21p stamp and we'll send you 40 pages of details (forget the stamp if you can't afford it!) You've already got a plastic computer for playing games, now build a metal one to do some real work: Interak, Interak, Interak!

### Greenbank

Greenbank Electronics (Dept T2E), 92 Chester Road,  
New Ferry, Wirral, Merseyside L62 5AG  
Telephone: 051-645 3391

## RVM Audiotronic

Abbots Hill Chambers  
1st Floor, Gower Street,  
Derby DE1 1SD

Tel: Derby 0332/382433

Modules	Power RMS	Load	Volt Max	Size (mm)	Price
RVM150S	70-150W	4-8	+60	31x80x100	1+ <b>27.00</b>
					10+ <b>22.97</b>
					20+ <b>22.77</b>
RVM300S	120-300W	4-8	+65	31x102x136	1+ <b>37.80</b>
					10+ <b>32.13</b>
					20+ <b>30.24</b>
RVM400S	170-400W	4-8	+65	47x89x136	<b>47.05</b>
RVM700S	300-700W	2-8	±70	47x90x197	<b>70.10</b>
RVM700S Mounted on Heat Sink					<b>70.40</b>

### MAIL ORDER ONLY

RVM RANGE OF POWER MOSFET AMPLIFIER MODULES. These Power Mosfet Modules are very reliable, driving difficult loads is no problem. Application from hi power systems to studio to domestic hi-fi.

All of our modules are built and tested and carry a 2 year guarantee.


We also supply a range of heat sinks, specially recommended for RVM modules.

*All prices include post & packing.  
(Quantity discount available)*

To order send cash with order, or cheque/postal order. Delivery on our Modules and Heat Sink or same day dispatch when order is received with cash, allow 7 days with cheque or postal order.

# neptune
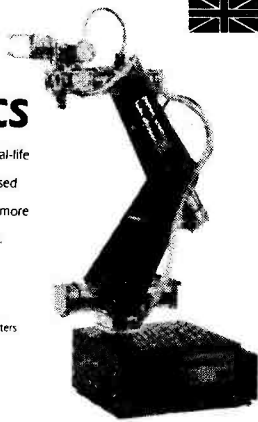
## for low-cost training in real-life robotics



The advanced design of the Neptune 2 makes it the lowest cost real-life industrial robot. It is electro-hydraulically powered, using a revolutionary water based system (no messy hydraulic oil). It performs 7 servo-controlled axis movements (6 on Neptune 1) — more than any other robot under £10,000. Its program length is limited only by the memory of your computer. Think what that can do for your BASIC programming skills!

And it's British designed, British made.

### Other features include:

- Leakproof, freecrossing rolling diaphragm seals.
- Buffered and latched versatile interface for BBC VIC 20 and Spectrum computers (2 bit control system (8 on Neptune 1)).
- Special circuitry for initial compensation.
- Rack and pinion cylinder couplings for wide angular movements.
- Automatic triple speed control on Neptune 2 for accurate 'homeing in'.
- Easy access for servicing and viewing of working parts.
- Powerful — lifts 2.5 kg with ease.
- Hand-lead simulator for processing (requires ADC option).

Neptune robots are sold in kit form as follows:

Neptune 1 robot kit (inc. power supply)	£1250.00	ADC option (components fit to main control board)	£95.00
Neptune 1 control electronics (ready built)	£295.00	Hydraulic power pack (ready assembled)	£435.00
Neptune 1 simulator	£45.00	Gripper sensor	£37.50
		Optional extra three-fingered gripper	£75.00
		BBC connector lead	£12.50
Neptune 2 robot kit (inc. power supply)	£1725.00	Commodore VIC 20 connector lead and plug-in board	£14.50
Neptune 2 control electronics (ready built)	£475.00	Sinclair ZX Spectrum connector lead	£15.00
Neptune 2 simulator	£52.00		

All prices exclusive of VAT and valid until the end of March 1985.

## mentor

### desk-top robot

This compact, electrically powered training robot has 6 axes of movement, simultaneously servo-controlled. It gives smooth operation and its rugged construction makes it ideal for use in educational establishments. Other features include long life bronze and nylon bearings, integral control electronics and power supply, special circuitry for mental compensation, optional on-board ADC, and hand-lead simulator as the teaching pendant. Like Neptune, Mentor's program length is limited only by your computer's memory. Programming is in BASIC.

Mentor is all-British in design and manufacture and comes in kit form at an astonishingly low price.

Mentor robot kit (inc. power supply)	£345.00
Mentor Control electronics (ready built)	£135.00
Mentor Simulator (requires ADC option)	£42.00
ADC option (Components fit to control electronics board)	£19.50
BBC connector lead	£12.50
Commodore VIC 20 connector lead and plug-in board	£14.50
Sinclair ZX Spectrum connector lead	£15.00

All prices exclusive of VAT and valid until the end of March 1985.



## CYBERNETIC APPLICATIONS LIMITED

PORTWAY TRADING ESTATE, ANDOVER, HANTS SP10 3ET  
TEL (0264) 50093 Telex: 477019

## NEW THIS MONTH

**Z917 PSU Panel** 320x190mm with MJ802 (30A 100V 200W) on large heatsink, 7 smaller heatinks contain: 2x7805; 7812; 7905; 2x MJ2955; 2SA473. Also 555, 3x 4A bridge rects, large smoothing caps, multiway plugs and sockets etc. Ex-equip working order. Only £8.50.

### DIP BOARD

Fibreglass DIP board 158x165mm double sided with 58w 0.1" edge connector gold plated. Ver0. £3.50.

### 20 WAY RIBBON CABLE

Twisted and flat computer grade for lower crosstalk. Reformatted into flat sections every 21" for IDC connectors. Only 70p/21" or £25 per 100ft reel.

### 3 1/2 DIGIT LCD DPM

Type 900S self powered, Input range 4-20mA. Contained in std DIN enclosure 96x48x100mm £15.

## 1984/85 CATALOGUE

84 page A4 size — Bigger, Brighter, Better, — more components than ever before! With each copy there's discount vouchers. Bargain List, Wholesale Discount List, Bulk Buyers List Order Form and Reply Paid Envelope. All for just £1.00! (FREE to Schools etc). Winter Supplement due out November — Send large SAE for your free copy.




### 'TREKKER'

Computer-controlled Robot built around the gearbox described below. Complete kit of parts inc PCB, program listings for BBC (other micros soon). £44.85 20W ribbon cable (min 3m recommended — 5m better) — £1.30/m SAE for illustrated leaflet.
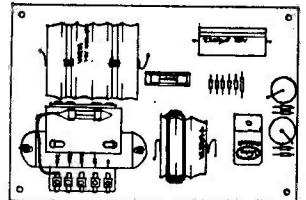
### MOTORIZED GEARBOX

These units are as used in a computerized tank, and offer the experimenter in robotics the opportunity to buy the electro-mechanical parts required in building remote controlled vehicles. The unit has 2 x 3V motors, linked to a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data supplied with the unit showing various options on driving the motors etc. Two new types of wheels can be supplied (the aluminium discs and smaller plastic wheels are now sold out). Type A has 7 spokes with a round black tyre and is 100mm dia. Type B is a solid heavy duty wheel 107mm dia with a flat rigid tyre 17mm wide. Photo shows gearbox with one of each type of wheel on it. PRICES: Gearbox with data sheets: £5.95 ea; Wheel type A: £0.70 ea; Wheel type B: £0.80 ea.



### NEW PACKS:

**K524 OPTO PACK** — a variety of single point and seven segment LEDs (incl. dual types) of various colours and sizes, opto isolators, numerators, multi digit gas discharge displays, photo transistors, infra red emitters and receivers. 25 assorted £3.95; 100 £14.95; 250 £35.

**K525 PRESET PACK** — Big, Big variety of types and sizes — submin, min and std, MP, slider, multiurn and cermets are all included. Wide range of values from 20R to 5M. 100 assorted £8.75; 250 £12.95; 1000 £48.

**K528 ELECTROLYTIC PACK** — All ready dropped for PCB mounting, this pack offers excellent value for money. Good range of values and voltages from 0.47uF to 1000uF, 6V to 100V. 100 £3.95; 250 £8.95; 1000 £32.

**K531 PRECISION RESISTORPACK** — High quality, close tolerance R's with an extremely varied selection of values mostly 1/4 and 1/2w tolerances from 0.1% to 2% — ideal for meters, test gear etc. 250 £3 1000 £10.

**K532 RELAYS** — wide selection of styles voltages and contacts. 4V - 240V, AC/DC, SP to 4PCO. 20 for £6; 100 £25.

### ESTABLISHED FAVOURITES

**K517 TRANSISTOR PACK** — 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114 117 172 182 183 198 239 251 214 255 320 BF198 255 394 2N3904 etc etc. Retail cost £7+ Special low price £2.75p.

**K523 RESISTORPACK** — 1000 — yes 1000 1/4 and 1/2 watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several Meg ohms. Only 250p, 5000 £10 20,000 £36.

**K520 SWITCH PACK** — 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p.

**K522 COPPER CLAD BOARD** — All pieces too small for our etching kits. Mostly double-sided fibreglass, 250g (approx. 110 sq. in.) for 100p.

**K530 100 ASSORTED POLYESTER CAPS** — All new modern components, radial and axial leads. All values from 0.01 to 1uf at voltages from 63 to 1000!! Super value at £3.95.

**K518 200 DISC CERAMIC CAPS** — big variety to values and voltages from few pF to 2.2uF; 3V to 3kV £1.00.

**K203 100 WIREWOUND RESISTORS** — From 1 w to 12w, with a good range of values £2.00.

**K505 20 ASSORTED POTENTIOMETERS** — all types including single, ganged, rotary and slider £1.70.

**W4700 PUSH BUTTON BANKS** — An assortment of latching and independent switches on banks from 2 to 7 way, DPCC to 6PCO. A total of at least 40 switches for £2.95; 100 £6.50; 250 £14.00.

### NI-CAD CHARGER PANEL

177 x 114mm PCB with one massive Varta Deac 57 x 50mm 0 rated 7.2V 1000mAh and another smaller Deac 32 x 35mm 0 rated 3.6V 600mAh. The price of these Ni-cad stacks new is over £20. Also on the panel is a mains input charger transformer with two separate secondaries wired via bridge rectifiers, smoothing capacitors and a relay to the output tags. The panel weighs 1kgm. All this for just £8.00.

### VEROBOARD & RIBBON CABLE

Discontinued lines, some at less than 1/2 price! e.g. Dipboard 158x165mm £3.50; 26W Grey ribbon 24/3m; Red wirewrap wire 24AWG £2.50/100m. Full details in supplement.

### FIBRE OPTICS

Scoop purchase of single and twin cable. For use with visible light or infra-red. Core 1mm dia, overall 2.25mm dia. Single 50p/m; 210m coil £8.30. Twin 90p/m; 20m coil £11.00.

### PCB MOUNTING NI-CADS

Much sought after 4.8V 150mA batts with PCB mntg tags on 25mm pitch. Batt size 25x16. Ideal for paralleling 90p ea; 10+ 85p; 25+70p; 100+80p.

### STEPPING RELAY

Schrack 2 pole 10 way 24V DC (works down to 15V) only 39x20x24mm. Connections by 0.1" pitch edge plug. Special low price £1.95.

### MINIATURE RELAYS

PCB mounting. DPCC size 20x15x15mm. Available in 3, 9 or 12V. £1 each.

### 1W AMPLIFIER

Z914 Audio amp panel 95x65mm with TBA820 chip. Gives 1W output with 9V supply. Switch and vol control. Just connect batt. and speaker. Full details supplied. Only £1.50 10 for £12; 25 for £25; 100 for £75.

Z915 Stereo version of above 115x65mm featuring 2 x TBA820M and dual vol control. £3.50; 10 for £30; 25 for £85; 100 £200.

### AM TUNER PANEL

Z916 For use with mono amp above. Neat panel 60x45mm. Only £1.50; 10 for £12.00.

### NI-CAD CHARGER SCOOP

Ever-Ready model CH4, this charger will take up to 4 AA, c or D cells plus 2 PP3 if required. Smart two tone grey case 212x97x60mm. Only £7.95

# GREENWELD

Min Access order value £5 No min CWO value. Official orders from schools etc. welcome — min invoice charge £10.



Our shop has enormous stocks of components and is open from 9-5.30 Mon-Sat. Come & see us!

443A Millbrook Road  
Southampton SO1 0HX  
Tel (0703) 772501/783740  
ALL PRICES INCLUDE VAT  
JUST ADD 60p P&P

# FREE CAREER BOOKLET

**Train for success, for a better job, better pay**  
Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.  
Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!  
Look at the wide range of opportunities awaiting you.  
Whatever your interest or skill, there's an ICS Diploma Course there for you to use.  
Send for your FREE CAREER BOOKLET today — at no cost or obligation at all.

**GCE** Over 40 'O' and 'A' Level subjects from which to choose. Your vital passport to career success.

COMPUTER PROGRAMMING	<input type="checkbox"/>	RADIO AMATEUR'S LICENCE	<input type="checkbox"/>
ELECTRONICS	<input type="checkbox"/>	INTERIOR DESIGN	<input type="checkbox"/>
COMMERCIAL ART	<input type="checkbox"/>	WRITING FOR PROFIT	<input type="checkbox"/>
TV, RADIO & AUDIO SERVICING	<input type="checkbox"/>	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	<input type="checkbox"/>		

Please send FREE DETAILS for the course ticked above.

Name \_\_\_\_\_  
Address \_\_\_\_\_

P.Code \_\_\_\_\_

**ICS** ICS Dept. EBS25  
8 Elliot Place  
Clydeaway Centre  
Glasgow G3 8EF  
041 221 2926  
or 01 622 9911  
(all hours)





# DIGITAL FRAMESTORE

Have you been framed? If not, you'd better get building! Leading off with construction details, Daniel Ogilvie then proceeds to give details of how the framestore can be used.

**B**oards with plated through holes are available for the framestore or you may construct your own by means of the layouts provided.

The normal care should be taken to ensure the correct orientation of all ICs and transistors — especially for the more expensive ones. Note that the dynamic RAMs have their positive and negative supply pins swapped compared with convention.

For the power supplies, the -5V and +6V should have linear, not switching, regulators to ensure that

switching noise does not adversely affect the high bandwidth video stages. The higher-current 5V can be provided by a switching supply, to ensure a low heat dissipation: the framestore can draw up to 4A.

Construction should begin with the control board. There is no need to socket any of the ICs, and indeed it is preferable not to, as the high capacitance of poor sockets can affect the timing of fast pulses. The ZNA134 is resilient but may be socketed if your nerves are not up to soldering it.

LI is one turn of 18swg wire

wound on a HB pencil (you should obtain similar performance from a B pencil but this has not been tried).

You should ensure that the links in the board are set to the 640 position (there are five of these) and then the board may be powered up; you may cross all your fingers and toes if you wish while doing this.

If you have access to a scope check that the output waveforms appear correct. Of particular importance are the relative timings of 0, RAS, CAS, W, TP and S/L (see

## PARTS LIST — ADC/DAC BOARD

RESISTORS (all 1/4W 5%)	
R1,22	75R
R2	220R
R3,7	22R
R4,13,20	1k0
R5,19	100R
R6,11,15	3k3
R8,18	330R
R9,17	10R
R10,16	1k5
R12	56k
R14	68k
R21	680R

CAPACITORS	
C1,2,5,12	10u 16V axial electrolytic
C3	4n7 ceramic
C4,6,7,8,11	100n ceramic
C9,10	1n0 polystyrene
C13	1u0 polyester film

SEMICONDUCTORS	
IC1	TDC1014
IC2,4	OP-07
IC3	74LS221
IC5	TDC1016j

IC6	74LS04
Q1,3	2N2369A
Q2	2N4393
Q4	2N3906
ZD1,2	ZN423
D1	1N914
D2	1N4001

MISCELLANEOUS  
PCB; IC sockets for ADC and DAC only;  
wire, solder, etc.

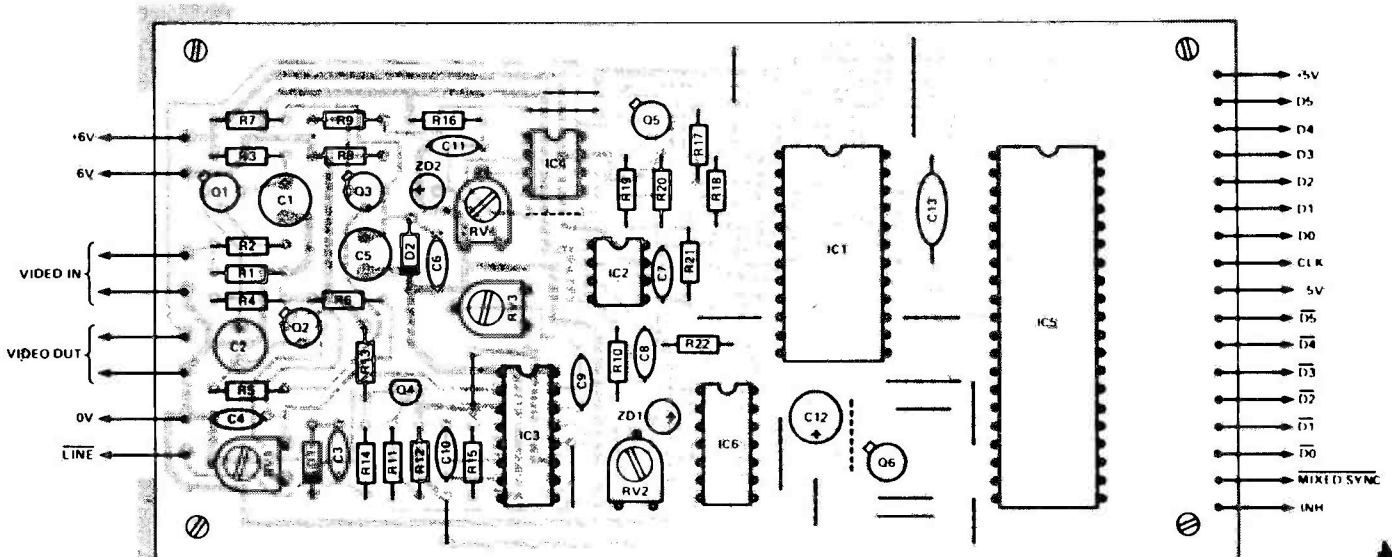


Fig. 9 The component overlay of the ADC/DAC board.

timing diagram, p63, ETI Dec '84). Remember the write output will appear only when the load switch is operated or one of the auxiliary load inputs is held low.

Construction should continue with memory boards. Each board will store one bit and six are required for the complete framestore.

The RAM's specified are Motorola MCM6664L20. These are cheap and contain an auto-refresh function which can be useful for the processor interface but is not necessary under normal use as a framestore. There should be no problem in using any other 200ns 64K X 1 DRAMs, but this is suggested only if you have some DRAMs to hand. If buying specially, the Motorola parts should be ordered unless a significant price difference is apparent, and we would suggest that eight of the alternatives should be tried first. They may be installed one bit at a time to help space the cost. All of the address and control inputs are paralleled up via the IDC connector. ICs 13 and 15 need not be inserted if the processor interface is not to be constructed.

The dynamic RAMs should be soldered in and not socketed: the capacitance of the sockets can cause excessive overshoot on the driving waveforms resulting in false writes to the RAMs. If the processor interface is to be installed, the link of the MPU line to 0V should be put in to enable the address multiplexers. This line would normally be driven by the interface board.

When one of the memory boards has been constructed and checked, connect it to the control card via the IDC connector and power both of them up. If possible, connect a scope to the serial output of the board. On switch on, this will be random, but the A0 address line may be connected to the serial input to the DRAM board and the load switch operated. The DRAM should now provide a regularly spaced waveform across one line. Other boards may now be paralleled up and checked similarly.

Finally the ADC/DAC card can be constructed. The ADC and DAC may be socketed if you wish. Before inserting the DAC set RV4 to achieve -1V at its reference input (pin 4). After turning off the power, the DAC may be inserted and powered up. Load the A0 address line again and connect the serial output of the memory board to the MSB of the DAC.

The video output can now be

connected to a video monitor. Other test inputs can be applied if you wish — remember they must be synchronized to the framestore to prevent tearing or rolling.

Finally the ADC can be inserted and the test input can be applied to the video input or a camera connected. The camera must be synchronized to the framestore to ensure a stable picture using the 75 ohm line and field drive outputs. The gain of the video input may be varied by means of RV1 which alters the reference to the ADC. An offset may be applied to the input by means of RV2. The framestore should now be up and running.

Due to the complexity of the project it is difficult to give any guidelines on fault finding should the worst occur. However to encourage construction the author is willing to offer a trouble-shooting service and will undertake the repair of any one board for £20 plus any parts necessary. This will not apply to any construction that does not use the PTH boards.

### And Now, A Few Tricks

Normally the data from the framestores memory is passed to the DAC and on to the video monitor. Suppose instead we insert a fast RAM between the memory and the DAC, and use the data from the memory to address a location in the high speed RAM, the resultant data read being passed to the DAC. We

have six bytes coming from the framestore's memory which can address one of 64 locations and we require a six-bit byte to come out. This 64 X 6 memory must also be fast — ideally faster than one of our clock cycles (78ns). We also need access to the RAM from outside so we can modify its contents; this can be provided by two, two-input multiplexors on the address inputs. This circuit is, in fact, a humble look-up table, and the circuit of the complete look-up table is shown in Fig. 10.

The RAM chosen is configured in a 256 X 9 bit format and has an access time of 45ns. Adding the delay through the multiplexors (about 5ns) means that the data coming to the DAC will be latched in one clock cycle later. This is not important, although we must delay the inhibit signal to the DAC (NDIS) similarly or we will lose the right hand column of the screen and will display rubbish in the left hand column. The required delay is created by IC2. Access to the RAM by our processor is quite conventional. The CS input from the MPU is the decoded 64-bit address location for the lookup table. When CS is low, the multiplexors switch the address lines to the lookup table over to the MPU address lines. The CS signal is rated with our R/W line to provide a write input to the lookup table, and it also disables the output drivers of the lookup

Fig. 10 The not-so-humble lookup table.

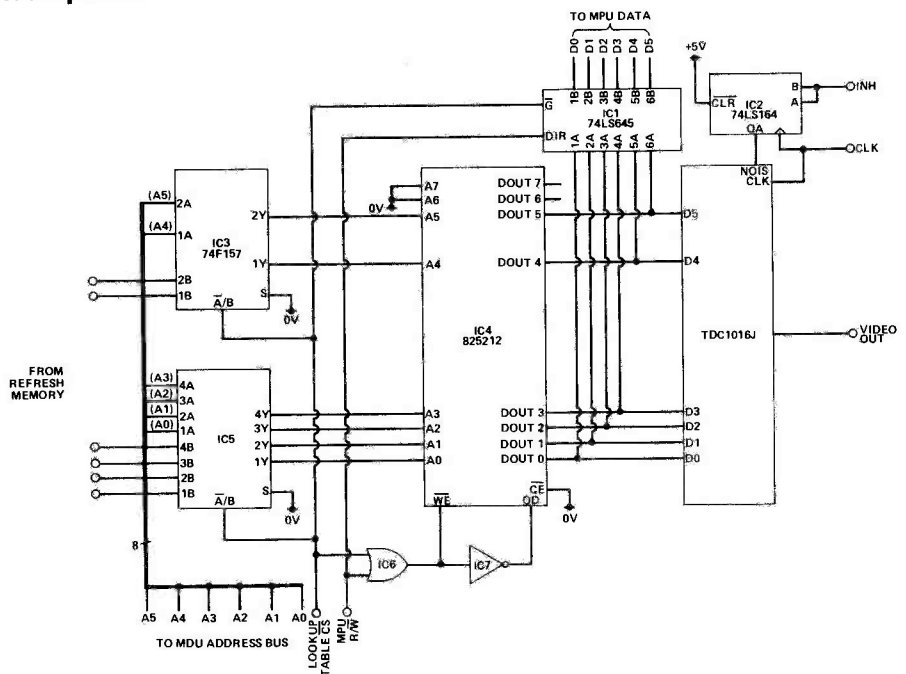


table which enables us to load data in via the tri-state buffer, IC1.

The writing to the lookup table should usually be performed during the blanking (inhibited) period of the display to prevent interference on it.

Normally the lookup table is loaded up such that a normal picture is obtained. All address locations are loaded up with a byte

corresponding to the address bus value, i.e. address 0 is loaded with 0, address 1 is loaded with 1, etc, and address 63 is loaded with 63. The incoming data from the framestore memory just addresses a similar valued byte which is converted by the DAC. This gives us complete control of the grey-level structure of the image. If we want to highlight a pixel value or a range

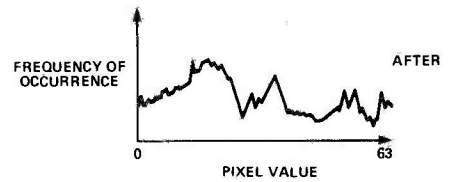


Fig. 13 Enhanced histogram.



Fig. 11 Picture before enhancement.



Fig. 14 Enhanced picture.

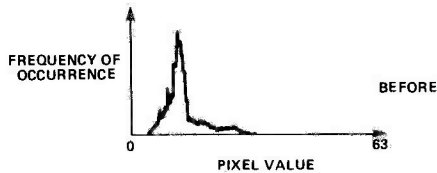


Fig. 12 Histogram of grey levels.

of pixels we can load the corresponding address value with peak white; for example to highlight grey level 24 we load up the lookup table address 24 with the byte 63 to turn it white.

Have a look at Fig. 11. Fig. 12, shown underneath, is a histogram of that picture which has been obtained by counting the numbers of pixels in that image for any particular grey level. As you can see, relatively few different levels are used. In the image there is little in

the dark grey or black tones and little approaching peak white. Because the picture contains few grey levels, it appears flat and little detailed information can be obtained from it. We could improve this by stretching the histogram over our full 63 grey level range. The increments between the pixels are greater, of course, but more detail is apparent. The resultant histogram is shown in Fig. 13 and by loading the lookup table with the new values we obtain the

Fig. 15 Pseudo-colour look-up table.

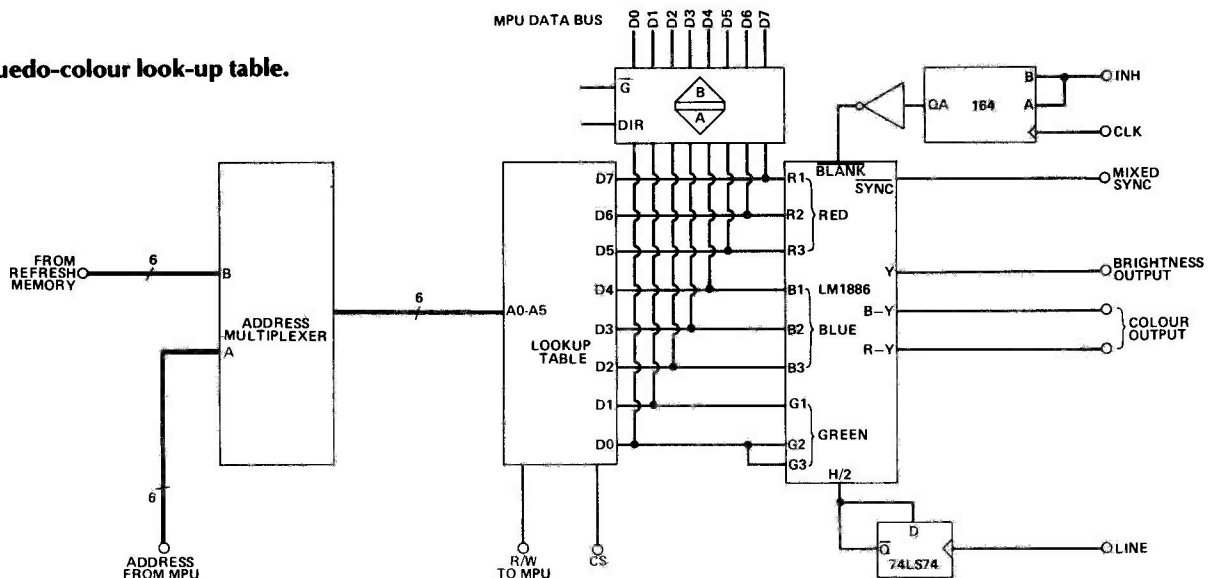


photo shown in Fig. 14. The lookup-table has only manipulated the output of the framestore and is therefore non destructive — we can restore the lookup table to its original values at any time to obtain our original image. On top of that we have only to write to 64 locations which can be done during the field blanking period and allows us to perform virtually real time image processing. One further use of the lookup table is to provide a pseudo-colour output. For example

our highlighted pixel (value 24) could have been turned a different colour which might have highlighted features or differences more efficiently. The six bit output of the framestore can be used to address a video DAC with colour capability. An example of this is shown in Fig. 15, using the National Semiconductor LMI889. This IC will accept a nine-byte binary input and provide a r-y and b-y output to drive a modulator or monitor directly. Readers are referred to the

National Semiconductor linear book for detailed information on the device.

A more effective (and expensive) colour display can be obtained by the use of three look-up tables and three DACs, and this is illustrated in Fig. 16. Each look-up table is dedicated to driving either the red, green or blue output. If we load each look-up table with our initial values (1 to 1, 2 to 2 etc) we will obtain our grey scale output. However we can turn the image into a green, red or blue display by writing zeros into the corresponding lookup tables (e.g. to obtain a blue image we should write zeros to the red and green lookup tables and leave the blue as it is).

In fact it can be shown that we can turn any grey level into any one of  $(2^2)^3 = 262,000$  colours. We can only display any 64 of them at one time, of course.

*Due to circumstances beyond our control, we cannot give the other two overlays this month, so we'll give them next month, when we'll also describe methods of interfacing the frame store to a computer.*


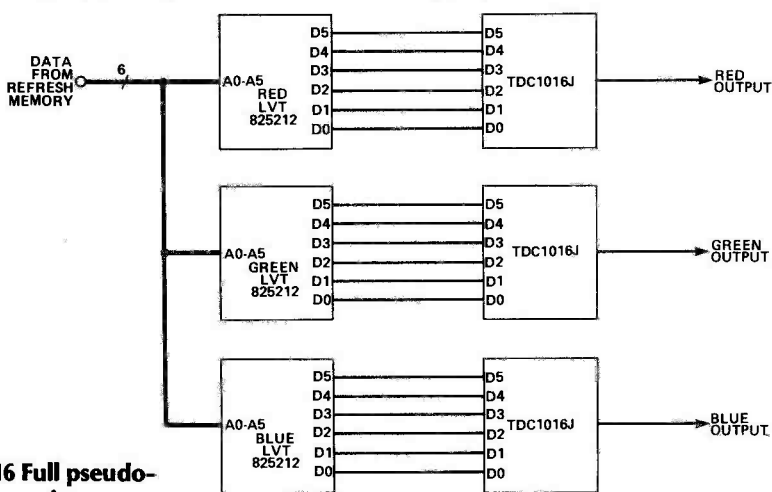


Fig. 16 Full pseudo-colour unit.

ETI
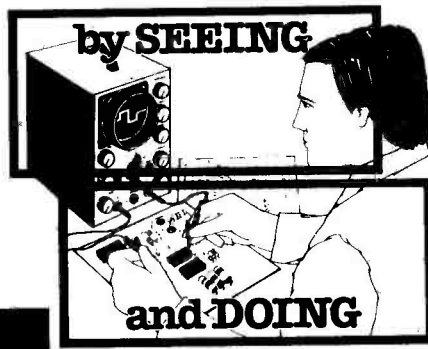
## MASTER Electronics - Microprocessors - Now! The PRACTICAL Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic & computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagrams.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.



**New Job? New Career? New Hobby?**

SEND THIS COUPON NOW.

Please send your brochure without any obligation to:-

I am interested in:

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

- ELECTRONICS  
 MICROPROCESSORS  
 RADIO AMATEUR LICENCE  
 CITY & GUILDS EXAMS

Other Subjects \_\_\_\_\_

BLOCK CAPS PLEASE



**British National Radio & Electronics School** Reading, Berks. RG1 1BR



OR TELEPHONE US  
0734 51515 OR  
TELEX 22758  
(24 HR SERVICE)



# ETI PCB SERVICE

In order to ensure that you get the correct board, you must quote the reference code when ordering. The code can also be used to identify the year and month in which a particular project appeared: the first two numbers are the year, the third and fourth are the month and the number after the hyphen indicates the particular project.

Note that these are all the boards that are available — if it isn't listed, we don't have it.

Our terms are strictly cash with order — we do not accept official orders. However, we can provide a pro-forma invoice for you to raise a cheque against, but we must stress that the goods will not be dispatched until after we receive payment.

- |      |   |  |  |
|------|---|--|--|
| 1981 | <input type="checkbox"/> E/8106-8 Waa-Phase..... 1.76                             | <input type="checkbox"/> E/8305-1 Compressor/Limiter ..... 6.19            | <input type="checkbox"/> E/8402-9 Mother board ..... 9.01          |
|      | <input type="checkbox"/> E/8106-9 Alien Attack..... 4.00                          | <input type="checkbox"/> E/8305-2 Single PSU..... 3.16                     | <input type="checkbox"/> E/8403-1 Power Meter ..... 5.81           |
|      | <input type="checkbox"/> E/8107-1 System A-Input<br>(MM or MC)..... 3.05          | <input type="checkbox"/> E/8305-3 Dual PSU ..... 4.01                      | <input type="checkbox"/> E/8403-2 Z80 DRAM..... 9.79               |
|      | <input type="checkbox"/> E/8107-2 System A — Preamp ..... 5.95                    | <input type="checkbox"/> E/8305-4.2 NDFL Amp ..... 7.88                    | <input type="checkbox"/> E/8403-3 Obedient Die ..... 3.76          |
|      | <input type="checkbox"/> E/8107-3 Smart Battery Charger ... 2.27                  | <input type="checkbox"/> E/8305-5 Balance Input Preamp. ... 3.23           | <input type="checkbox"/> E/8404-1 School Timer..... 4.07           |
|      | <input type="checkbox"/> E/8108-3 Hand Clap Synth. .... 4.57                      | <input type="checkbox"/> E/8305-6 Stage Lighting<br>Autofade..... 6.19     | <input type="checkbox"/> E/8405-1 Auto Light Switch..... 4.01      |
|      | <input type="checkbox"/> E/8108-5 Watchdog Home<br>Security (2 boards) ..... 6.11 | <input type="checkbox"/> E/8305-7 Stage Lighting—<br>Triac Board..... 4.74 | <input type="checkbox"/> E/8405-2 ZX81 EPROM Prog. .... 10.53      |
|      | <input type="checkbox"/> E/8109-1 Mains Audio Link<br>(3 boards) ..... 8.45       | <input type="checkbox"/> E/8306-1 to 3 PseudoROM<br>(3 boards) ..... 3.62  | <input type="checkbox"/> E/8405-3 Mains Borne RC..... 5.07         |
|      | <input type="checkbox"/> E/8109-4 Laboratory PSU ..... 5.21                       | <input type="checkbox"/> E/8306-5 Atom Keypad..... 5.18                    | <input type="checkbox"/> E/8405-4 Centronics Interface..... 4.09   |
|      | <input type="checkbox"/> E/8110-1 Enlarger Timer..... 3.91                        | <input type="checkbox"/> E/8307-1 Flash Sequencer..... 2.67                | <input type="checkbox"/> E/8405-5 Vario ..... 6.62                 |
|      | <input type="checkbox"/> E/8110-2 Sound Bender..... 3.05                          | <input type="checkbox"/> E/8307-2 Trigger Unit Main Board... 2.67          | <input type="checkbox"/> E/8405-6 Midi Drum Synth..... 3.59        |
|      | <input type="checkbox"/> E/8111-1 Voice Over Unit..... 4.57                       | <input type="checkbox"/> E/8307-3 Trigger Unit Transmitter 1.66            | <input type="checkbox"/> E/8406-1 Oric EPROM Bd. .... 19.58        |
|      | <input type="checkbox"/> E/8111-2 Car Alarm..... 3.23                             | <input type="checkbox"/> E/8307-4 Switched Mode PSU.... 16.10              | <input type="checkbox"/> E/8406-2 Spectrum Joystick ..... 3.30     |
|      | <input type="checkbox"/> E/8111-3 Phone Bell Shifter..... 3.40                    | <input type="checkbox"/> E/8308-1 Graphic Equaliser..... 9.10              | <input type="checkbox"/> E/8407-1 Warlock Alarm ..... 8.19         |
|      | <input type="checkbox"/> E/8112-4 Component Tester..... 1.71                      | <input type="checkbox"/> E/8308-2 Servo Fail-Safe<br>(four-off)..... 2.93  | <input type="checkbox"/> E/8408-1 Joystick Interface..... 3.07     |
| 1982 | <input type="checkbox"/> E/8201-3 Guitar Tuner (2 boards) 6.38                    | <input type="checkbox"/> E/8308-3 Universal EPROM prog ... 9.64            | <input type="checkbox"/> E/8408-2 EPROM Emulator..... 9.11         |
|      | <input type="checkbox"/> E/8202-2 Allez Cat Pest Repeller ... 1.93                | <input type="checkbox"/> E/8309-1 NiCad Charger/Regen ... 3.77             | <input type="checkbox"/> E/8408-3 Infrared Transmitter ..... 3.70  |
|      | <input type="checkbox"/> E/8202-5 Moving Magnet Stage.... 4.01                    | <input type="checkbox"/> E/8309-2 Digger..... 3.40                         | <input type="checkbox"/> E/8408-4 Infrared Receiver..... 3.98      |
|      | <input type="checkbox"/> E/8202-6 Moving Coil Stage ..... 4.01                    | <input type="checkbox"/> E/8309-3 64K DRAM ..... 14.08                     | <input type="checkbox"/> E/8408-5 CMOS Tester..... 4.60            |
|      | <input type="checkbox"/> E/8203-4 Capacitance Meter<br>(2 boards) ..... 11.66     | <input type="checkbox"/> E/8310-1 Supply Protector ..... 2.19              | <input type="checkbox"/> E/8409-1 Oric EPROM Bd. .... 3.82         |
|      | <input type="checkbox"/> E/8205-1 DV Meg ..... 3.13                               | <input type="checkbox"/> E/8310-2 Car Alarm..... 3.98                      | <input type="checkbox"/> E/8409-2 Banshee Siren..... 3.19          |
|      | <input type="checkbox"/> E/8206-1 Ion Generator<br>(3 boards) ..... 9.20          | <input type="checkbox"/> E/8310-3 Typewriter Interface..... 4.17           | <input type="checkbox"/> E/8409-3 Dry Cell Charger..... 2.80       |
|      | <input type="checkbox"/> E/8206-4 MOSFET Amp Module ... 7.80                      | <input type="checkbox"/> E/8311-1 Mini Drum Synth ..... 3.07               | <input type="checkbox"/> E/8410-1 Echo Unit ..... 3.92             |
|      | <input type="checkbox"/> E/8206-5 Logic Lock..... 3.52                            | <input type="checkbox"/> E/8311-2 Alarm Extender..... 3.21                 | <input type="checkbox"/> E/8410-2 Digital Cassette ..... 9.80      |
|      | <input type="checkbox"/> E/8206-6 Digital PWM ..... 3.84                          | <input type="checkbox"/> E/8311-3 Multiswitch ..... 3.59                   | <input type="checkbox"/> E/8410-3 Disco/Party Strobe ..... 4.80    |
|      | <input type="checkbox"/> E/8206-7 Optical Sensor ..... 2.00                       | <input type="checkbox"/> E/8311-4 Multiple Port..... 4.34                  | <input type="checkbox"/> E/8411-1 AM/FM Radio (4 bds) ... 13.02    |
|      | <input type="checkbox"/> E/8206-9 Oscilloscope<br>(4 boards) ..... 13.34          | <input type="checkbox"/> E/8311-5 DAC/ADC Filter ..... 3.22                | <input type="checkbox"/> E/8411-2 Control Port-control bd 12.15    |
|      | <input type="checkbox"/> E/8212-2 Servo Interface<br>(2 boards) ..... 6.75        | <input type="checkbox"/> E/8311-6 Light Pen ..... 4.60                     | <input type="checkbox"/> E/8411-3 Control Port-I/O bd ... 6.33     |
|      | <input type="checkbox"/> E/8212-4 Spectracolumn..... 5.54                         | <input type="checkbox"/> E/8311-7 Logic Clip..... 2.51                     | <input type="checkbox"/> E/8411-4 Capacitance Meter..... 3.55      |
| 1983 | <input type="checkbox"/> E/8301-1 Fuel Gauge..... 3.45                            | <input type="checkbox"/> E/8311-8 MC Head (JLLH)..... 3.17                 | <input type="checkbox"/> E/8411-5 Video Vandal (3 bds) ... 12.10   |
|      | <input type="checkbox"/> E/8301-2 ZX ADC..... 2.59                                | <input type="checkbox"/> E/8312-1 Lightsaver..... 1.85                     | <input type="checkbox"/> E/8411-6 Temperature Controller... 2.88   |
|      | <input type="checkbox"/> E/8301-3 Programmable PSU..... 3.45                      | <input type="checkbox"/> E/8312-2 A-to-D Board..... 12.83                  | <input type="checkbox"/> E/8411-7 Mains Failure Alarm..... 2.54    |
|      | <input type="checkbox"/> E/8303-1 SoundBoard ..... 12.83                          | <input type="checkbox"/> E/8312-3 Light Chaser (2 bds) ... 7.54            | <input type="checkbox"/> E/8411-8 Knife Light ..... 3.25           |
|      | <input type="checkbox"/> E/8303-2 Alarm Module..... 3.62                          | <input type="checkbox"/> E/8312-4 ZX Alarm ..... 6.04                      | <input type="checkbox"/> E/8411-9 Stage Lighting Interface... 3.73 |
|      | <input type="checkbox"/> E/8303-3 ZX81 User Graphics ..... 1.07                   | 1984   | <input type="checkbox"/> E/8411-10 Perpetual Pendulum ... 3.14     |
|      | <input type="checkbox"/> E/8303-4 Logic Probe ..... 2.50                          | <input type="checkbox"/> E/8401-1 Vector Graphics..... 8.27                | <input type="checkbox"/> E/8412-1 Spectrum Centronics ... 3.51     |
|      | <input type="checkbox"/> E/8304-1 Real Time Clock..... 8.74                       | <input type="checkbox"/> E/8402-1 Speech Board<br>(Mini-Mynah) ..... 10.97 | <input type="checkbox"/> E/8412-2 Experimenter's DRAM... 14.08     |
|      | <input type="checkbox"/> E/8304-4 Stage Lighting— Main ... 13.73                  | MODULAR PREAMP:  | <input type="checkbox"/> E/8412-3 Active-8: Motherboard ... 9.37   |
|      | <input type="checkbox"/> E/8304-5 Stage Lighting — Display 3.45                   | <input type="checkbox"/> E/8402-2 Disc input (mono) ..... 3.73             | <input type="checkbox"/> E/8412-4 Active-8: Protection Unit 3.67   |
|      |   | <input type="checkbox"/> E/8402-3 Output stage (stereo) ... 3.73           | <input type="checkbox"/> E/8412-5 Active-8: Crossover ..... 3.67   |
|      |   | <input type="checkbox"/> E/8402-4 Relay/PSU..... 3.73                      | <input type="checkbox"/> E/8412-6 Active-8: LF EQ..... 3.67        |
|      |   | <input type="checkbox"/> E/8402-5 Tone, main (mono) ..... 3.73             | <input type="checkbox"/> E/8412-7 Active-8: Equaliser..... 3.67    |
|      |   | <input type="checkbox"/> E/8402-6 Tone, filter (stereo) ... 3.73           | <input type="checkbox"/> E/8412-8 Active-8: Delay Unit..... 3.67   |
|      |   | <input type="checkbox"/> E/8402-7 Balanced output (st) ... 3.73            | 1985   |
|      |   | <input type="checkbox"/> E/8402-8 Headphone amp (st) ..... 3.73            | <input type="checkbox"/> E/8501-1 Active Bass Speaker..... 2.79    |

**How to order:** indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices subject to change without notice.

Total for boards £.....  
Add 45p p&p 0.45  
Total enclosed £.....


**PLEASE ALLOW  
28 DAYS FOR  
DELIVERY**


Signed .....

Name .....



Address .....

# PCB FOIL PATTERNS

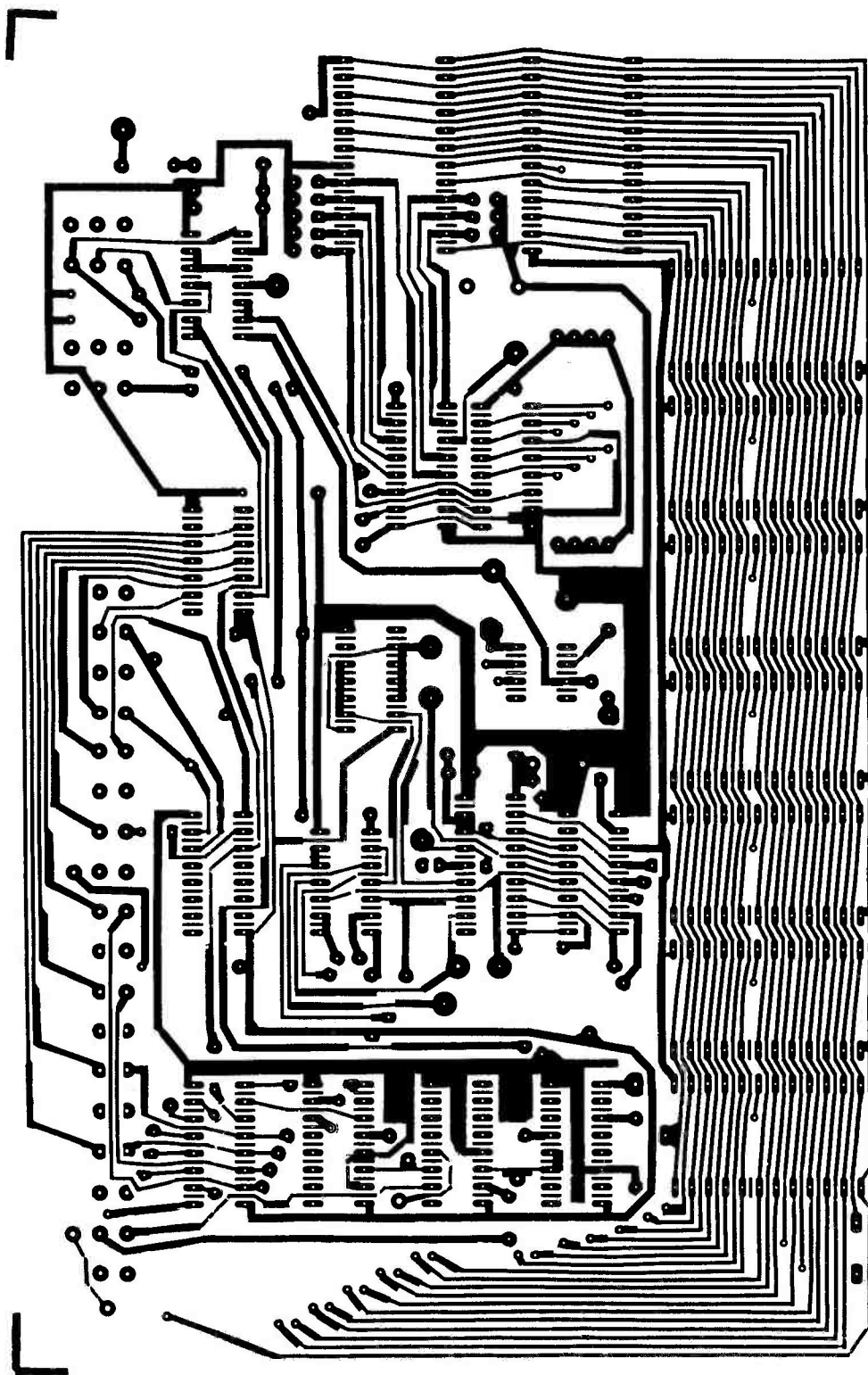

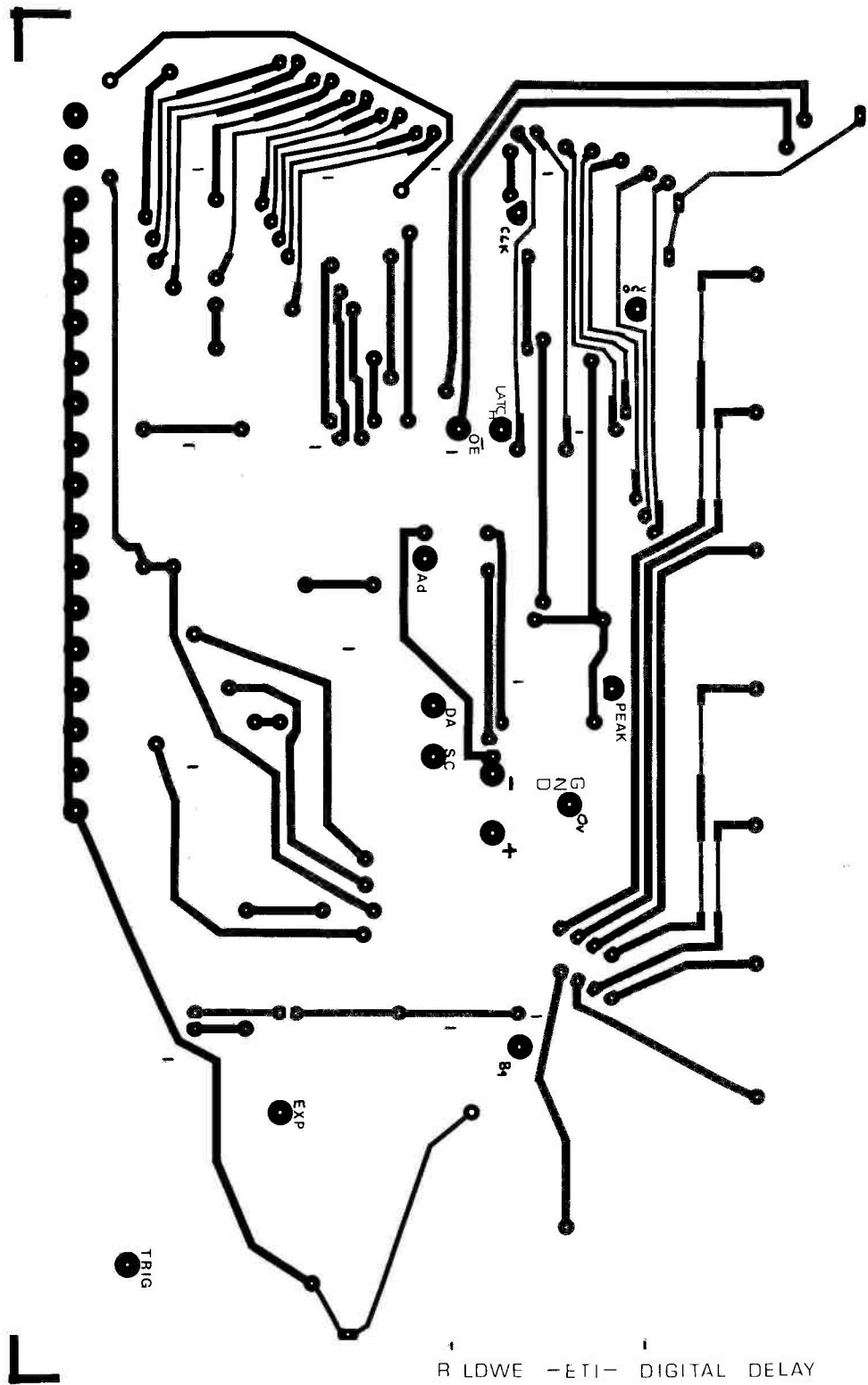

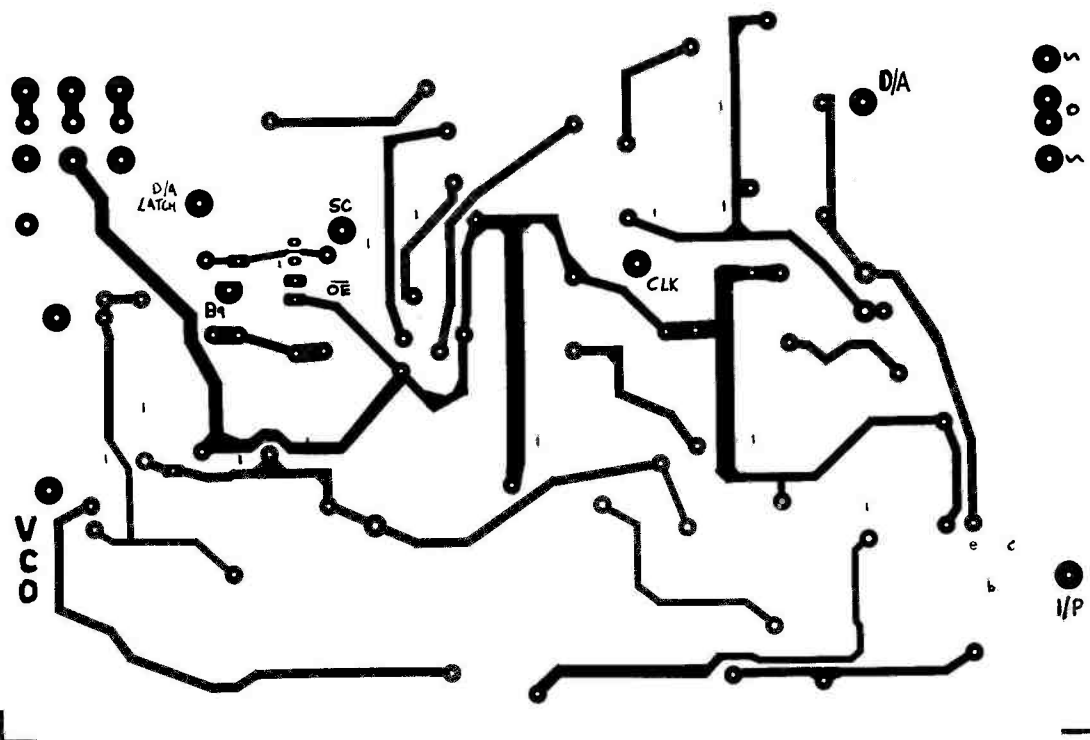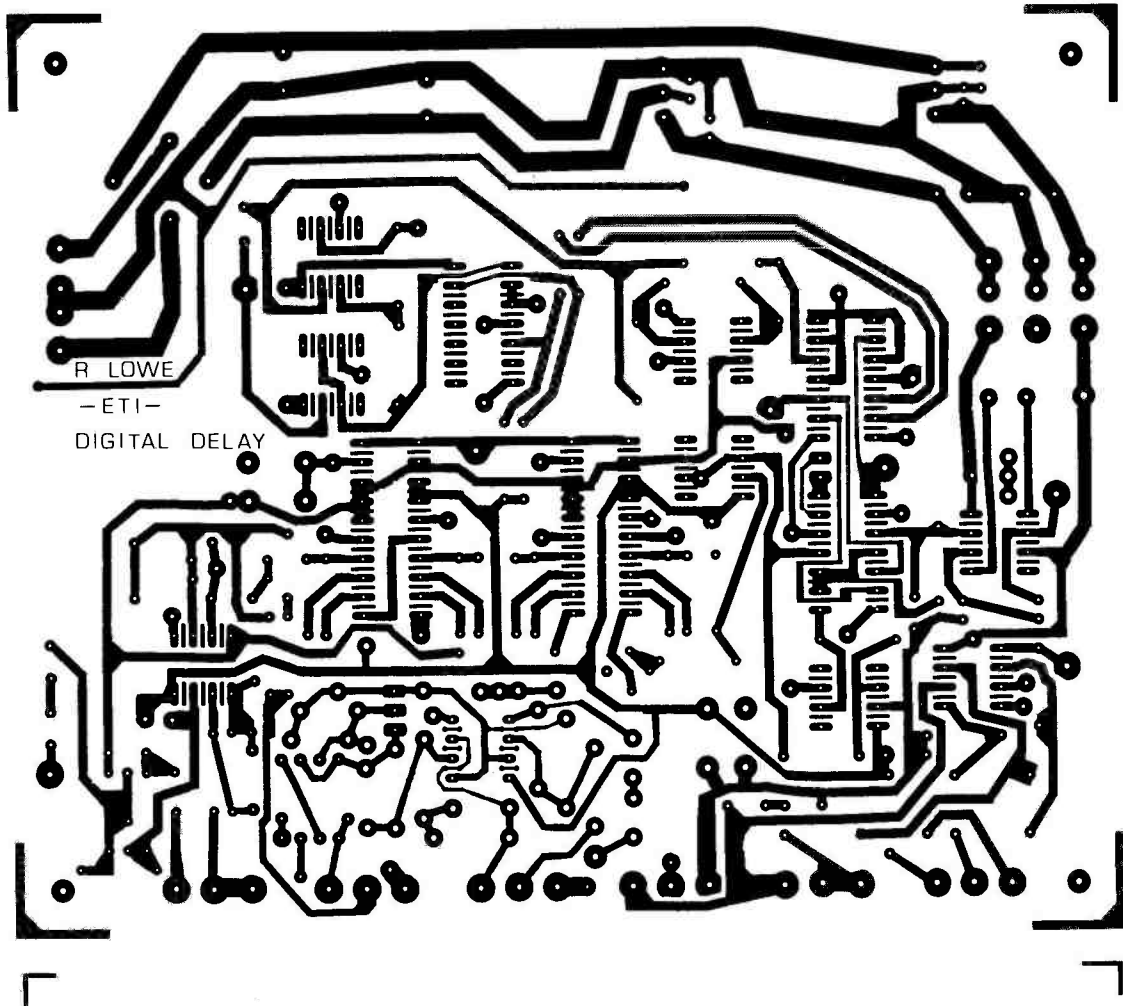Unfortunately, we don't have space to publish both this month's foil patterns and the ones held over from last month. The patterns shown here and overleaf are for the Digital Delay Line from last month, and we will try and publish this month's patterns next month.







## Lineage:

40p per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£11.00 per single column centimetre.

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699

Send your requirements to:  
Jason Inskip  
ASP Ltd.,  
1 Golden Square,  
London W1.

## ALARMS

# ALARMS

A  
D  
E

FREE BOOKLET  
on  
BURGLAR ALARMS  
with  
LOWEST U.K. DIY PUBLISHED PRICES

PHONE OR WRITE FOR YOUR COPY  
**051-523 8440**  
**AD ELECTRONICS**  
217 WARBRECK MOOR  
AINTREE, LIVERPOOL L9 0HU

### SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C. TEC SECURITY, Dept E 1,  
60 Market St, Wigan WN1 1HX  
Telephone (0942) 42444

Trade Enquiries Welcome

### HOME GUARD SYSTEMS

If you want professional alarm/C.C.TV/Door entry/security lighting equipment or DIY kits at genuine trade prices don't delay phone today for our free illustrated catalogue.

**Tel: 01-651 2449**  
Freepost, South Croydon  
Surrey CR2 9PU  
(no stamp required)

## KITS

**MICROBUG** (VHF Transmitter) 140mm x 370mm. Extremely sensitive, powerful. Operates from 1.5V battery ready built tested only £16.50, (in kit form £11.50). Also available Automatic Telephone recorder built tested £18.50, (in kit form £13.50). All fully guaranteed. Send cash, cheque, or P.O. to: Shah Electronics, 11 Livingstone Rd., Southall, Middlesex, UB1 1TH.

**AMTRON ELECTRONIC** kits and instrument cabinets. Over 70 kits in our range plus special offer on obsolete kits. Send S.A.E. for catalogue. Amtron U.K. Ltd., 7 Hughenden Road, Hastings, East Sussex TN34 3TG.

**ELECTRONIC ORGAN KEY-BOARDS** and other parts being cleared out as special offer. Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8. 01-986 8455.

## BOOKS

**PARAPHYSICS JOURNAL** (Russian translation); psychotronics, kirlianography, heliophonic music, telekinetics. Computer software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

## PLANS 'N DESIGN

**AMAZING ELECTRONIC** plans, lasers, gas, ruby, light shows, high voltage teslas, van de graph surveillance devices, ultrasonics, pyrotechnics, new solar generator, 150 more projects, catalogue. S.A.E. Plancentre, Bromyard Road Industrial Estate, Ledbury HR8.

## BOOKS EXCHANGE SERVICE

**BOOKS WANTED FOR CASH** Have you got technical books you no longer need? OR Do you need to read up on a new topic? Then EXCHANGE BOOK CLUB can help YOU! We buy and sell previously read books on electronics and computing. For list of currently available titles and details of our guaranteed buy back plan SAE please to:  
**JAMES ELECTRONICS, P.O. Box 2**  
Rothwell, Leeds LS26 0UY

## SERVICES

**PRINTED CIRCUIT BOARDS** manufactured to your specification. Quality, Quick service. Competitive Prices. **COPPER-CLAD** fibreglass boards cut to size. 1mm thick £1.80 sq. ft. 1.6mm £2.20 sq. ft. Postage 75p. Mondo Circuits Ltd, 35 Grosvenor Road, Twickenham, Middx. Tel: 01-891 5412.

### JBA ELECTRONICS

Manufactures to design or specifications. One offs, small batch prototypes. Analogue digital electronic equipment. Complete electronic service — no job too small.

1st Floor, 4a Lion Yard  
Brecon, Powys, South Wales  
Tel: (0874) 611177

**FREE PROTOTYPE** of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited. Tel: halstead (0787) 477408.

**HEATHKIT.** U.K. spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel (0684) 73127.

## FOR SALE

**100W AMPLIFIER**  
— £9.95 built

Or use the same board for 50W, 150W, 200W into 4 or 8 ohms etc., by using alternative output transistors and P.S.U. SAE for full details to:

**ESS AMPLIFICATION**  
Innovation House  
Guildhall Road, Hull

**TEKTRONIX OSCILLOSCOPES.** 546 dual-trace 50 MHz delay sweep £195, 545A dual-trace 24 MHz delay sweep £125, 564 storage, dual-trace 10MHz £275. Plug-ins. 7B50A £300. Manuals. Texas printer £35. H.P. DVM £20. Advance J1A Audio Oscillator £25. Tel: (01) 868 4221.

**POWERTRAN CORTEX + RS232C** + simple E-Bus + All other IC sockets. Switch selectable BASIC and FORTH. £500+ value. £300. Lincoln (0522) 754643.

**EPROMS** — All types available, sample price: 27128, £12.50; 8" Floppy disc drives available. £12.50. Ring for details: Camberley (0276) 28208.

**KIA RETURN AN AD NO. 17** . . . . Music-centre stereoamps + magnetic pickup preamps + controls, data & 240V power supply. . . . Post ad + £9.50 — 8 Cunliffe Rd., Ilkley, LS29 9DZ . . . A Happy New Year from K.I.A.

## KITS

**PRINTED CIRCUITS** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.50. Developer 35p. Ferric Chloride 60p. Clear acetate sheet for master 15p. Copper-clad fibreglass board, approx. 1mm thick £2.00 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

**MINIATURE FM TRANSMITTERS.** Frequency 60-145 MHz, range ½ mile S.G.F. — P.C.B. All components. Full instructions 9-12v operation, broadcast reception. Super sensitive microphone. Pick-up on FM radio. £6.95 inc; or ready built £8.95: Same day despatch — Zenith Electronics, 21 Station Rd., Industrial Estate Hallsham, E. Sussex BN27 2E

**ECOLIGHT** (ETI July 84) detect burglars from even attempting a break in. Full kit of parts as per article £21.05. p.c. Only £4.50. Reprint of article 75p. G.P. Electronics, 87 Willowtree Ave., Durham DH1 1DZ.

### LINSLEY HOOD DESIGNS LOW DISTORTION AUDIO SIGNAL GENERATORS

AO113 Kit (.02% distortion) £28 P.P.  
AO149 Kit (.0015% distortion) £39 £2.00

Super Hi-Fi Amplifier (ETI)  
P.C. Boards from £4

Send S.A.E. for further details:

**TELERADIO ELECTRONICS**  
325 Fore Street, London N9 0PE  
Tel: 01-807 3719

## SERVICES

### FREELANCE ELECTRONICS ENGINEER

**\* QUALIFICATIONS**  
 \* H.N.C.; M.O.D. training  
**ANYTHING CONSIDERED**  
 \* **SPECIALITY** \* Drafting and P.C.B. artwork, board productions and assembly.

### FAULT FINDING AND TESTING UNDERTAKEN

### HIGHEST QUALITY WORK \* FULL COOPERATION.

Greg Heath, 'Pickwick',  
 No 6 Hillbarn, Sanderstead,  
 Surrey, CR2 0RU

## WANTED

**TURN YOUR SURPLUS** transistors, IC's etc into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. Tel: 0945 584188. Immediate settlement.

## EDUCATIONAL

### IMPROVE YOUR PROSPECTS

with skills that employers want - learn the easy way with modern home study courses from Ideal Schools.

**MODERN ELECTRONICS**  
 Train for success in the fastest ever growing industrial sector.

**COMPUTER PROGRAMMING**  
 The demand for Programmers is increasing constantly - don't miss out!  
 For free booklet write today to



IDEAL SCHOOLS  
 (Ref. ETD2)  
 60 St. Enoch Sq  
 Glasgow G1 UK.  
 Tel: 041-248 5200

### MICROCOMPUTER REPAIRS

**ZX SPECTRUM.** Vic20, C64, BBC, QL 15 40/41, Commodore computers, printers and floppy discs. Send faulty machine to: Trident Enterprises Ltd., 37 Linden House, Common Road, Langley, Slough, Berks. Tel: (0753) 48785.

## MISCELLANEOUS

### AGENTS

Wanted to Sell Computer Software for most computers. We now have the Dialog Electronics Part I in stock, Pools Winner & Course Winner. We can supply business software, games and computer ad ons. Phone (0288) 4179 upto 9pm most nights for your free list and details about our agents.

**TIMESAVING.** Television, audio, circuit diagrams. S.A.E., Model Number; then 75p if available. H.M. Earle, 173 Northbrooks, Harlow.

### ADD-ONS

**TANGERINE OWNERS** at last 2 \*\*6809\*\* C.P.U. board with expandable monitor in colour. FLEX compatible. Also 14K RAM card to free EPROM space on TANEX S.A.E. For details ... Ralph Allen Engineering; Forncett-End, Norwich. Tel: (095 389) 420.

## TEST EQUIPMENT

**TOP PRICES PAID** for surplus electronic test equipment.  
**ALWAYS** a good selection of **SIG-GENS, METERS,** and **SCOPES** for sale.  
 Phone 0920-8714301

## COMPONENTS

**FREE!** Parcel of components worth £10. Send only 80p post-tage. D. Horsley, 113 Clare Rd., Braintree, Essex.

### Betatran Electronics Supplies

**Toroidal transformers primary 250V secondaries 0-40, 0-40V, 0-50, 0-50V, 0.55, 0-55V, 0-70, 0-70V at 300VA £17.55, 500VA £24.70, 625VA £30.50. Can Electrolytics 63V, 6800uF SA 2£4.35, 10,000uF 7A £5.45, 100V 6800uF 8A £6.23, 4700uF 8A £5.50, 3300uF 7A £4.20, 2200uF 7A £3.00. Computer Grade 10,000uF 15A £14.00. MOS-FETs 2SJ 50/2SK 135 £8.50, 2SJ83/2SK 227 £8.20 price per pair. 35A 200V bridge rectifiers £3.25, VAT inclusive £1.00 p&p under £7.00. Full spec. many more. Resistors, capacitors, transistors, heat sinks, amplifiers, speakers, transformers, etc. Send 4 x 9 self addressed envelope for large list.**

Laver St., Cavendish, Suffolk CO10 8AP.  
 Tel: 0787 280639.

### IRISH READERS

#### MAIL ORDER COMPONENTS

Top quality components  
 Great prices  
 Return-of-post service

Write or phone for free price list

**WAVEFORM ELECTRONICS**  
 12 Efra Road, Rathmines, Dublin 6.  
 Phone (01) 0001 if England 987507

Mail order only please

### CHEAP CASES

Absolute bargains, rack mounting & free standing. NEW, but manufacturers seconds. No damage.

Send s.a.e. for list.  
 C. Phillips, 'The Laurels' Tiptoe Road  
 Wootton, New Milton, Hants BH25 5BJ  
 MAIL ORDER ONLY

**VAT inclusive price list. LSTTL,** from 28p, CMOS from 23p, Transistors, Resistors, Capacitors and more. Phone or write (0283) 703071. Hunt Electronics, P.O. Box 57, Derby, DE6 6SN.

### WEBB ELECTRONICS

41 Winwick Street, Warrington WA5 2AS  
 Tel: 54179  
 Diodes: IN4001/2/3 2½p, IN4004/5/6 3p, IN5400 7p, IN5404 9p, IN5408 12p, IN4148 1½p, BZY127 7p, BZY88C Zeners 4½p, BZX88C 7½p.  
 Resistors: ¼ watt 5% metal film ½p.  
 All above items min 100 off.  
 LM380 (IN STOCK!) £1.00; SN7613 £1.47  
 BT Plugs 30p. BT Master Sockets £2.75.  
 BT Slave Sockets £2.07p  
 Add 15% V.A.T. & 50p p&p

## COMPUTERS

**CORTEX SOFTWARE:** Capman and Spacebugs - Arcade action games and shapes 'n' sprites - Graphics toolkit. Tapes £5 each Available soon joystick and sound generator module £25 - SAE for details. Markrosoft, 53 Broughton Road, Croft, Leicester, LE9 6EB.

## AERIAL MAST SPACE

### Aerial Mast Space to Let by Tender

1. Kensington (Kensington Heights)  
72m asl (ref. 38/1/2)
2. Shooters Hill (Shooters Hill Water Tower)  
150m asl (ref. 687/B/3)
3. Croydon (Shirley Hills Water Tower)  
163m asl (ref. 1/L)

Copies of tender document may be obtained from:

**Area Surveyor, Thames Water Authority, 20 Blyth Road, Bromley, Kent. BR1 3UB (Ref. MAS)**

## THAMES WATER

## EQUIPMENT

### BROADCAST QUALITY FOR YOUR NEXT MIXER PROJECT

- Over 100 Audio Sub-Units
- Kit or Ready Built

Our new Mic & Mag Disc Pre-amps incorporate the super low noise Mullard/Signetic NE5534 IC.

All items listed are identical to those used in professional consoles.

### PARTRIDGE ELECTRONICS

56 Fleet Road, Benfleet, Essex SS9 5JN, England  
 (LARGE S.A.E. PLEASE)  
**THE MIXER PEOPLE**

## FOR SALE

**100 WATT FET POWERAMPS** £10. Automatic relay protection - mlrr or input & delayed switch-on... glass/pcb built... KIA-8 Cunliffe Road, Ilkley... Free slider/V.C.

EPROM COPIER - STAND ALONE  
 2716-27128 ..... £175.00  
 TELEPHONE CONVERSATION  
 RECORDER ..... £75.00  
 2 LINES INTO 1 ANSWERING  
 MACHINE  
 Switching Unit ..... £30.00

From L.K.F. Systems Ltd  
 St. Albans. Tel: 55084

## ESSEX

### R JONES ELECTRONICS

287 Rectory Rd., Grays, Essex  
 Tel: (0375) 33158 + 24hr answer phone  
 Components, IC's, Full After Sales Services  
 Electronic repairs - Industrial & Domestic  
 Open 9-5.30pm 6 days a week

## LANCASHIRE

### ETESON ELECTRONICS

15B Lower Green,  
 Poulton-le-Fylde, Blackpool  
 Tel: (0263) 885107  
 Open. 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.  
 Electronic Component Specialists.

## MERSEYSIDE

### PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982  
 47 Whitechapel, Tel 051 236 5489  
 Liverpool 2  
**THE ELECTRONICS SPECIALISTS'**  
 Open: Tues-Sat 9.30-5.30

E  
L  
E  
C  
T  
R  
O  
M  
A  
R  
T


E  
L  
E  
C  
T  
R  
O  
M  
A  
R  
T

# ETI ADVERTISERS INDEX

## FEBRUARY 1985

Armon.....	66	Maplin.....	68
Audio Electronics.....	41	Merseyside Acoustics.....	43
Bi-Pak.....	51	Microprocessor.....	44
B.K. Electronics.....	10	Midwich.....	22/23
B.N.R.E.S. ....	58	Newrad.....	36
Cambridge Microcomputers.....	35	Powertran.....	IFC/IEC
Cricklewood.....	14	Rapid Electronics.....	8
Cybernetic Applications.....	54	RTVC.....	35
Digisound.....	35	RVM.....	53
Display Electronics.....	12	Ship Co. ....	36
Electrovalue.....	44	Skybridge.....	30
Greenbank.....	53	S.M.E. ....	43
Greenweld.....	54	Stewarts of Reading.....	21
I.C.S. ....	54	Systems Electronique.....	66
ILP.....	44	Technomatic.....	16/17
Kelan.....	36	TK Electronics.....	27
Kemplant.....	21	Watford Electronics.....	4/5
Magenta.....	43		
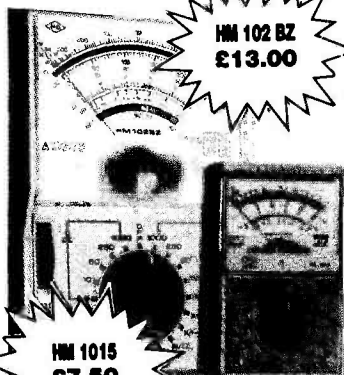
### AFFORDABLE ACCURACY QUALITY MULTIMETERS FROM ARMON



**HM 102 BZ**  
**£13.00**

#### ANALOGUE

**HM-102BZ**  
10ADC Range, 20kΩ/VDC, Buzzer, Battery Test Scale.....**£13.00**  
19 measuring ranges

**HM-102R**  
Low end voltage & current ranges, Jack for Audio o/p Voltages.....**£11.00**  
20 measuring ranges

**HM-1015**  
Rugged, Pocket sized meter, for general purpose use.....**£7.50**  
16 measuring ranges  
Battery, Test Leads and Manual included with each model.

#### DIGITAL

HC-6010 0.5% Accuracy, Standard Model.....**£33.50**  
HC-5010T 0.25% Accuracy, TR Test Facility.....**£36.50**

All models have full functions and ranges and feature:

- 3 1/2 digit 0.5" LED display
- Low battery indication
- Auto zero & Auto polarity
- ABS Plastic Casing & Tilt Stand
- DC AC 10amp Range
- Overload Protection on all ranges.
- Battery, Spare Fuse, Test Leads and Manual

**HC 5010**  
**0.25% accuracy**  
**£36.50**

**HC 7030**  
**0.1% accuracy**  
**£39.50**  
**push button**

### FULL DETAILS ON APPLICATION FROM:- ARMON ELECTRONICS LTD

DEPT K HERON HOUSE, 106 WIMBLEY HILL ROAD, WIMBLEY, MIDDLESEX HA9 8AQ  
TELEPHONE 01-902 4321 TELEX 922985

PLEASE ADD 15% to your order for VAT. P&P Free of charge. Payment by cheque with order  
Other applicable to mainland UK only

Trade enquiries invited

Please allow 28 days for delivery

## LOOK - IT'S HIS NEW YEAR SPECIAL!

TREAT YOURSELF  
THIS NEW YEAR



### BEARPARTS

**CONTENTS OF PACK:**  
BC 612 Transistor, Red LED, 1N4004 Diode, T1 646 Diode, 560pf 200v Capacitor, 10k, 150k Resistors, 2k Multiturn Potentiometer, 48A Crimp Eyelet, Rubber Grommet, Instrument Wire, Sleeving.

We are the main stockists for 'BEARPARTS', the new name in electrical, electronic and audio components.

Interested? Send S.A.E. and receive your

**FREE**

'BEARPARTS' sample pack.

### COMPLETE SOLDERING KIT

(For the Hobbyist/Electronics Engineer)

**FOR LESS THAN £10!!**

Comprises of:-

- Antex Miniature 15W 240v AC Soldering Iron
- Antex Iron Stand c/w Sponge
- Desolder Pump
- 2 mtr Solder
- Desolder Braita
- 13A Plug

**ONLY £9.85**  
Please add 80p P & P + 15% VAT

LIMITED OFFER  
WHILE STOCKS  
LAST!



Iron Stand c/w Sponge



Soldering Iron

Desolder Pump



24 hr answerphone for credit card orders  
Tel: 0244 536699



## SYSTEMS ELECTRONIQUE

(U.K.) LTD.

26 Engineer Park, Sandycroft,  
Deeside, Clwyd CH5 2QD.  
Tel: (0244) 536700.

Call in and see our new counter now open.  
9.00 - 5.00 Mon-Fri & 9.00 - 12.00 Sat  
Too far to call? Don't worry, export/mail order is our speciality. Why not write and find out more.



Featured in Electronics  
& Music Maker

# TAKE COMPLETE CONTROL OF YOUR MUSIC with the

# MCS-1

## professional quality MIDI-controlled sampling unit

Once again, Powertran and E&MM combine to bring you versatility and top quality from a product out of the realms of fantasy and within the reach of the active musician.

The MCS-1 will take *any* sound, store it and play it back from a keyboard (either MIDI or lv/octave). Pitch bend or vibrato can be added and infinite sustain is possible thanks to a sophisticated, looping system.

All the usual delay line features (Vibrato, Phasing, Flanging, ADT, Echo) are available with delays of up to 32 secs. A special interface enables sampled sounds to be stored digitally on a floppy disc via a BBC microcomputer.

The MCS-1 gives you many of the effects created by top professional units such as the Fairlight or Emulator. But the MCS-1 doesn't come with a 5-figure price tag. And, if you're prepared to invest your time, it's almost cheap!

### Specification

Memory Size: Variable from 8 bytes to 64K bytes.

Storage time at 32 KHz sampling rate: 2 seconds.

Storage time at 8 KHz sampling rate: 8 seconds.

Longest replay time (for special effects): 32 seconds.

Converters, ADC & DAC: 8 bit companding. Dynamic range: 72 dB.

Audio Bandwidth: Variable from 12 KHz to 300 Hz.

Internal 4 pole tracking filters for anti-aliasing and recovery.

Programmable wide range sinewave sweep generator.

MIDI control range: 5 octaves.

+1 V/octave control range: 2 octaves with optional transpose of a further 5 octaves.

### Digital Delay Line



Introduced in 1982, Powertran's DDL has brought digital quality effects to thousands of musicians. Still available in kit form at only £179.00 + VAT.

**KIT**  
**£499**  
**+ VAT**

**BUILT**  
**£699**  
**+ VAT**



Write or phone now to place an order  
Powertran Cybernetics Limited,  
Portway Industrial Estate,  
Andover, Hants SP10 3ET.  
Telephone: 0264 64455




# POWERTRAN

# cybernetics Ltd





# All new in the 1985 Catalogue

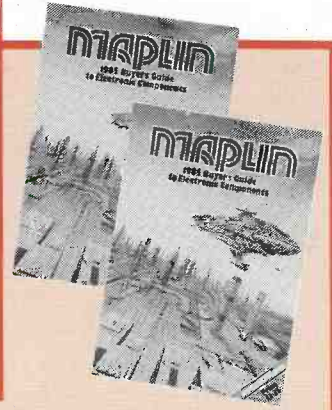

From a gentle purr to a mighty roar, the tightly controlled power of the beast is yours to command!

## PROFESSIONAL QUALITY HIGH POWER LOUDSPEAKERS

A new range of superb quality loudspeakers.

- ★ Virtually indestructible high temperature voice-coil reinforced with glass-fibre
- ★ 100% heat overload tolerance
- ★ Advanced technology magnet system
- ★ Rigid cast alloy chassis
- ★ Linen or Plastiflex elastomer surrounds
- ★ 5-year guarantee (in addition to statutory rights)



Available in 5, 8, 10, 12, 15 and 18 inch models with 8Ω and some 16Ω impedances and with input powers ranging from 50W to 300W e.g.

- 5in. 50W 95dB 8Ω: XG39N / 16Ω: XG40T £17.95§
- 8in. 100W 98dB 8Ω: XG43W £29.95§
- 10in. 100W 100dB 8Ω: XG46A £29.95§
- 12in. 100W 101dB 8Ω: XG49D £29.95§
- 12in. Twin Cone 100W 100dB 8Ω: XG50E / 16Ω: XG51F £31.95§

Note - the output power doubles for each 3dB increase (ref 1W @ 1m).

## PRECISION GOLD MULTIMETERS



A new range of very high quality multimeters offering truly amazing quality at the price.

- Pocket Multimeter, 16 ranges, 2000Ω/V DC/AC £6.95§ (YJ06G)
- M-102BZ with Continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95§ (YJ07H)
- M-2020S with Transistor, Diode & LED tester and 10A DC range, 27 ranges 20,000Ω/V DC £19.95§ (YJ08J)
- M-5050E Electronic Multimeter with very high impedance, FET input, 53 ranges including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95§ (YJ09K)
- M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated PCB for long-term reliability and consistent high accuracy (0.25% +1 digit DCV) £42.50§ (YJ10L)

N.B. All our prices include VAT and Carriage. A 50p handling charge must be added if your total order is less than £5 on mail order (except catalogue).

### MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
- LONDON 159-161 King Street, Hammersmith, W6. Tel: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 25831.
- SOUTHEND 282-284 London Rd. Westcliff-on-Sea, Essex. Tel: 0702-554000  
Shops closed all day Monday.

Our huge range of top quality electronic components at very competitive prices are all detailed in our catalogue, and with well over 600 new lines in our 1985 edition and many design improvements, it's well worth getting a copy. Here are just a few examples from the catalogue. (The items below are NOT kits).

- ★ Most phono and jack plugs now with integral strain relief sleeve - gold-plated types also available from 14p (gold from 70p)
- ★ Stereo Disco Mixer with cross-fade, talk-over, cue monitoring, aux input, slide controls. Only £58.95 (AF99H)



- ★ 10-Channel Stereo Graphic Equalisers - 3 models - basic; with peak level meter; and with spectrum analyser - from £77.95



- ★ Digital Delay Line permits Slap-back, Doubling, Flanging, Chorus and Echo. 11 controls. Only £195.00 (AF98G)
- ★ Video Enhancer improves picture quality when recording from one VTR to another, and with TV's with monitor input. Only 28.95 (XG59P)
- ★ Detailed descriptions of the exciting new 74HC range of IC's which combine the advantages of CMOS and TTL. From 46p
- ★ Keyboards: sloping keys, two-tone grey, mounted in steel frame, very smart cases (extra) available. 61 keys, only £33.95 (YJ12N)  
79 keys, only £37.95 (YJ13P)
- ★ 1% Resistors now 50ppm/°C, 0.4W, only 2p each!
- ★ Auto transformers 120/240V 50VA, £10.75§ (YJ56L). 100VA £14.95§ (YJ57M). 150VA £16.95§ (YJ58N). 250VA £21.95§ (YJ59P).
- ★ Digital Clinical Thermometer. Only £13.95 (FK51F)



Check our 1985 Catalogue for all our other fascinating new lines.



## 1985 CATALOGUE

Pick up a copy now at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).



☎ Phone before 2pm for same day despatch.

Post this coupon now for your copy of the 1985 catalogue. Price £1.35 + 40p post and packing. If you live outside the U.K. send £2.40 or 11 International Reply Coupons. I enclose £1.75.

Name .....

Address .....

.....

.....

ET12 85

§ Indicates that a lower price is available in our shops.

All offers subject to availability.

Prices firm until Feb 9th 1985.