

AN ARGUS SPECIALIST PUBLICATION

# electronics today

INTERNATIONAL

MARCH 1987 £1.30

## FM STEREO TUNER

FROM JOHN LINSLEY HOOD



**PLUS**

THE ETI CAPACITOMETER  
CREDIT CARD CASINO  
COMPUTER INTERFACE  
STANDARDS  
CIRCUIT DESIGN ON  
THE BBC MICRO  
SNUBBER NETWORKS  
INSIDE TRANSPUTERS

**..AUDIO....COMPUTING....MUSIC....RADIO....ROBOTICS..**

# OMP POWER AMPLIFIER MODULES


PRICES INCLUDE V.A.T. \* PROMPT DELIVERIES \* FRIENDLY SERVICE \* LARGE S.A.E. 28p STAMP FOR CURRENT LIST

## OMP POWER AMPLIFIER MODULES

Now enjoy a world wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B. and Drive circuits to power compatible Vu meter. Open and short circuit proof. **Supplied ready built and tested.**



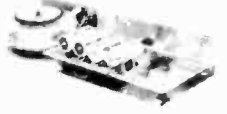**OMP100 Mk II Bi-Polar** Output power 110 watts R.M.S. into 4 ohms. Frequency Response 15Hz - 30KHz -3dB T.H.D. 0.01%. S.N.R. -118dB. Sens for Max output 500mV at 10K. Size 355 x 115 x 65mm. **PRICE £33.99 - £3.00 P&P**



**OMP MF100 Mos-Fet** Output power 110 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB Damping Factor 80. Slew Rate 45V uS. T.H.D. Typical 0.002%. Input Sensitivity 500mV S.N.R. -125dB. Size 300 x 123 x 60mm. **PRICE £39.99 - £3.00 P&P**



**OMP MF200 Mos-Fet** Output power 200 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB Damping Factor 250. Slew Rate 50V uS. T.H.D. Typical 0.001%. Input Sensitivity 500mV S.N.R. -130dB. Size 300 x 150 x 100mm. **PRICE £62.99 - £3.50 P&P**



**OMP MF300 Mos-Fet** Output power 300 watts R.M.S. into 4 ohms. Frequency Response 1Hz - 100KHz -3dB Damping Factor 350. Slew Rate 60V uS. T.H.D. Typical 0.0008%. Input Sensitivity 500mV S.N.R. -130dB. Size 330 x 147 x 102mm. **PRICE £79.99 - £4.50 P&P**

**NOTE** Mos Fets are supplied as standard 100KHz bandwidth & Input Sensitivity 500mV (Required P.A. version 150KHz bandwidth & Input Sensitivity 775mV). Order Standard or P.A.



**Vu METER** Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D diodes (7 green 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 - 50p P&P**

**LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S.** Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E (28p) for free details.



**POWER RANGE**  
 8" 50 WATT R.M.S. Hi-Fi Disco  
 20 or magnet 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.95 available with black grille £11.99 P&P £1.50 ea.  
 12" 100 WATT R.M.S. Hi-Fi Disco  
 50 or magnet 2" ally voice coil. Ground ally fixing escutcheon. Die cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 - £3.00 P&P ea.

**McKENZIE**  
 12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco  
 2" ally voice coil Ally centre dome Res Freq 45Hz Freq. Resp. to 6.5KHz Sens. 98dB PRICE £29.99 - £3.00 P&P ea.  
 12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.  
 Res. Freq. 45Hz Freq. Resp. to 14KHz PRICE £31.49 - £3.00 P&P ea.  
 15" 150 WATT R.M.S. C15 Bass Guitar/Disco.  
 3" ally voice coil Die-cast chassis Res. Freq. 40Hz Freq. Resp. to 4KHz PRICE £57.87 - £4.00 P&P ea.  
 10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.  
 2" voice coil. Res. Freq. 75Hz Freq. Resp. to 7.5KHz Sens. 99dB PRICE £19.99 - £2.00 P&P  
 10" 200 WATT R.M.S. C10200GP Guitar, Keyboard, Disco.  
 2" voice coil Res. Freq. 45Hz Freq. Resp. to 7KHz Sens. 101dB PRICE £44.76 - £3.00 P&P  
 15" 200 WATT R.M.S. C15200 High Power Bass.  
 Res. Freq. 40Hz Freq. Resp. to 5KHz Sens. 101dB PRICE £62.41 - £4.00 P&P  
 15" 400 WATT R.M.S. C15400 High Power Bass.  
 Res. Freq. 40Hz Freq. Resp. to 4KHz Sens. 102dB PRICE £89.52 - £4.00 P&P

**WEM**  
 5" 70 WATT R.M.S. Multiple Array Disco etc.  
 1" voice coil Res. Freq. 52Hz Freq. Resp. to 5KHz Sens. 89dB PRICE £22.00 - £1.50 P&P ea.  
 8" 150 WATT R.M.S. Multiple Array Disco etc.  
 1" voice coil. Res. Freq. 48Hz Freq. Resp. to 5KHz Sens. 92dB PRICE £32.00 - £1.50 P&P ea.  
 10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.  
 1" voice coil Res. Freq. 35Hz Freq. Resp. to 4KHz Sens. 92dB PRICE £36.00 - £2.00 P&P ea.  
 12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.  
 1 1/2" voice coil Res. Freq. 35Hz Freq. Resp. to 4KHz Sens. 94dB PRICE £47.00 - £3.00 P&P ea.

**SOUNDLAB (Full Range Twin Cone)**  
 5" 60 WATT R.M.S. Hi-Fi Multiple Array Disco etc.  
 1" voice coil Res. Freq. 63Hz Freq. Resp. to 20KHz Sens. 86dB PRICE £9.99 - £1.00 P&P ea.  
 6" 60 WATT R.M.S. Hi-Fi Multiple Array Disco etc.  
 1" voice coil Res. Freq. 56Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £10.99 - £1.50 P&P ea.  
 8" 60 WATT R.M.S. Hi-Fi Multiple Array Disco etc.  
 1 1/2" voice coil Res. Freq. 38Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £12.99 - £1.50 P&P ea.  
 10" 60 WATT R.M.S. Hi-Fi/Disco etc.  
 1 1/2" voice coil Res. Freq. 35Hz Freq. Resp. to 15KHz Sens. 89dB PRICE £16.49 - £2.00 P&P

**PANTEC HOBBY KITS.** Proven designs including glass fibre printed circuit board and high quality components complete with instructions.


**FM MICROTRANSMITTER (BUG)** 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P  
**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P  
**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.


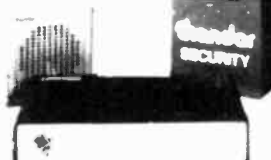
## BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units complete with interconnection cable. FULLY GUARANTEED.

IDEAL for Work Shops, Factories, Offices, Home, etc. Supplied ready built



**Control Unit** - Houses microwave radar unit range up to 15 metres adjustable by sensitivity control. Three position key operated fascia switch - off - test - armed. 30 second exit and entry delay.

**Indoor Alarm** - Electronic swept freq. siren 104dB output.

**Outdoor Alarm** - Electronic swept freq. siren 98dB output. Housed in a tamper proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200-260 Volt AC 50-60Hz. E+pendant with door sensors, panic buttons etc. Complete with instructions.

**SAVE £138.00** Usual Price £228.85

**BKE's PRICE £89.99 - £4.00 P&P**

## OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20 x 15 x 12. Watts R.M.S. per cabinet. Sensitivity 1W 1mtr dB.



**OMP 12-100 Watts 100dB. Price £149.99**

**per pair.**

**OMP 12-200 Watts 102dB. Price £199.99**

**per pair.** Delivery Securicor £8.00 per pair

## OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. Three models (Ratings R.M.S. into 4ohms) Equal Sensitivity 775mV.

**MF200 (100 - 100)W £169.00 Securicor**

**MF400 (200 - 200)W £228.85 Delivery**

**MF600 (300 - 300)W £299.99 £10.00**

## 1 K-WATT SLIDE DIMMER

- Control loads up to 1Kw
- Compact Size 4" x 1" x 2"
- Easy snap in fitting through panel cabinet cut out
- Insulated plastic case
- Full wave control using 8 amp triac
- Conforms to BS800

Suitable for both resistive and inductive loads in numerous applications in industry, the home and disco theatres etc.

**PRICE £13.99 - 75p P&P**

## BSR P295 ELECTRONIC TURNTABLE

- Electronic speed control 45 & 33" rpm
- Plus Minus variable pitch control
- Belt driven
- Aluminium platter with strobed tone
- Cue lever
- Anti-skate (this level)
- Adjustable counter balance
- Manual arm
- Standard cartridge fittings
- Supplied complete with cut out template
- D.C. Operation 9.14v D.C. 65mA



ADC Q4 mag cartridge fit above. Price £4.99 ea. P&P 50p


## PIEZO ELECTRIC TWEETERS MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a result is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER**

**TYPE 'A' (KSN2036A)** 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each - 40p P&P  
**TYPE 'B' (KSN1005A)** 3" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each - 40p P&P  
**TYPE 'C' (KSN6016A)** 2" - 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each - 40p P&P  
**TYPE 'D' (KSN1025A)** 2" - 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each 40p P&P  
**TYPE 'E' (KSN1038A)** 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each - 40p P&P  
**LEVEL CONTROL** Combines on a recessed mounting plate level control and cabinet input jack socket 85 x 85 mm. Price £3.99 - 40p P&P
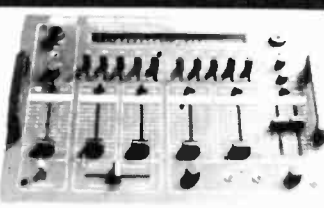
## STEREO DISCO MIXER

**STEREO DISCO MIXER** with 2 - 5 band L & R graphic equalisers and twin 10 segment L & R Vu Meters. Many outstanding features. 5 Inputs with individual faders providing a useful combination of the following:  
 3 Turntables (Mag) 3 Mics 4 Line plus Mic with talk over switch Headphone Monitor Pan Pot L & R Master Output controls Output 775mV. Size 360 x 280 x 90mm. Price £134.99 - £3.00 P&P



**B. K. ELECTRONICS** DEPT ET1  
 UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR TEL: 0702-527572

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED

# electronics today

INTERNATIONAL MARCH 1987 VOL 16 NO 3



**Geoff Bains:** Editor  
**Ian Pitt:** Deputy Editor  
**Paul Chappell:** Project Editor  
**Jerry Fowler:** Technical Illustrator  
**Alisdair Chisholm:** Ad. Manager  
**Nicola Baty:**  
 Classified Sales Executive  
**Andrew Selwood:** Copy Control  
**Dave Bradshaw:** Group Editor  
 — Electronics

**PUBLISHED BY:**  
 Argus Specialist Publications Ltd.,  
 1 Golden Square, London W1R 3AB.  
**DISTRIBUTED BY:**  
 Argus Press Sales & Distribution Ltd.,  
 12-18 Paul Street, London EC2A 4JS  
 (British Isles)

**TYPESET AND ORIGATION BY:**  
 Design International.

**PRINTED BY:**  
 Adlard & Son Ltd, The Garden City Press.

**COVERS DESIGNED BY:**  
 Argus Design.

**COVERS PRINTED BY:**  
 Loxley Brothers Ltd.

ISSN  
 0142-7229



Member of the  
 Audit Bureau  
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1987 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

■ Subscription Rates. UK: £18.10. Overseas: £22.50. USA: \$29.50. Airmail: £49.50.

## EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.  
 Telex 8811896.

## FEATURES

**FOREIGN PORTS ..... 13**  
 The field of computer interface standards is a most confusing one. Mike Bedford makes everything crystal clear with an explanation of RS232, Centronics, 20mA and other standards.

**HARDWARE DESIGN CONCEPTS ..... 20**  
 Mike Barwise continues to build his Pulse Generator. This month he looks at the speed limitations of the circuit designed last month.

**THE TRANSPUTER ..... 23**  
 One new chip from Inmos has come in for a lot of misinformed hype recently. Mike Barwise takes an exploratory trip inside the Transputer.

**SNUBBER NETWORKS ..... 26**  
 Designing triac circuits is not quite as easy as it first appears. Paul Chappell takes a look at the snubber networks that ensure triacs behave themselves.

## PROJECTS

**CIRCUITS ON THE SMALL SCREEN ..... 28**  
 Gareth Connor puts four software packages for the BBC micro through their paces and finds most areas of circuit design can be given a boost with a micro.

**M&A SERIES FOUR MIXER KIT ..... 32**  
 Ian Pitt has been slaving over a hot soldering iron for the past few weeks to build himself a modular mixer from this budget studio-standard kit.

**PLL FM TUNER ..... 34**  
 John Linsley Hood has come up with a novel design for an FM Tuner to

grace the hi-fi shelves of the most discerning listener.

**GEIGER COUNTER ..... 39**  
 Colin Seymour adds a pulse counter to the Geiger ratemeter he produced last month.

**THE ETI CAPACITOMETER ..... 45**  
 Measuring the exact value of any capacitor is made easy with this handy instrument from Ray Bold.

**CREDIT CARD CASINO ..... 50**  
 Paul Chappell has crammed more illicit gambling into a tinier space than most people would have thought possible.

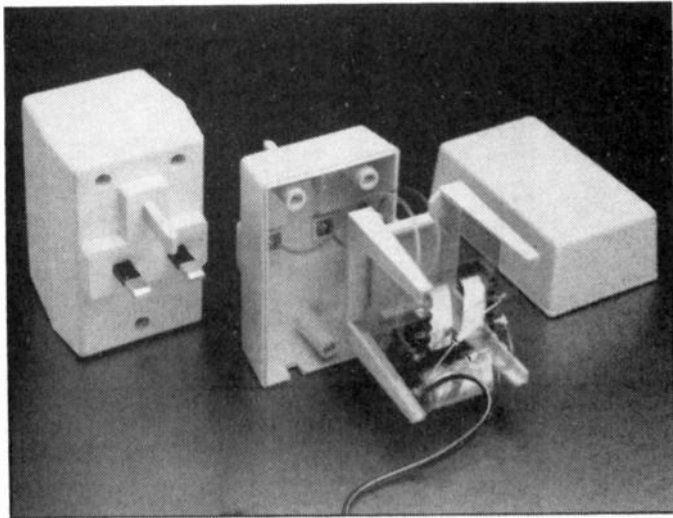
## REGULARS

**NEWS DIGEST ..... 6**  
**NEXT MONTH'S ETI ..... 8**  
**DIARY ..... 9**  
**READ/WRITE ..... 11**  
**SPECIAL OFFER ..... 25**  
**TECH TIPS ..... 54**  
 Auto Battery Charger.  
 Versatile DRAM interface for the 6502.

**OPEN CHANNEL ..... 56**  
**ALF'S PUZZLE ..... 56**  
**PLAYBACK ..... 57**  
**BIRD'S EYE VIEW ..... 57**  
**PCB FOILS ..... 59**  
**READERS' FREE ADS ..... 61**  
**PCB SERVICE ..... 62**  
**OOPS! ..... 63**  
**CLASSIFIED ADS ..... 64**







## Making A Case For Safety

West Hyde Developments has introduced a new power supply case which meets the latest British Standard specification.

The plastic, plug-type enclosure has live and neutral pins which are sleeved for part of their length in accordance with the requirements of BS1363. The sleeving is intended to prevent accidental contact with a live conductor when the plug is being inserted or removed from a socket or at other times when it is not pushed fully home. West Hyde claims to be the first company to market a power supply enclosure which incorporates this feature.

The case is available in either

black or white and has an internal moulded cradle which supports a standard size mains transformer. The cradle also covers the live pins when in position, reducing the risk of contact between mains wiring and the low voltage circuitry. The standard version has a non-conductive earth pin but an optional brass earth pin will be available shortly.

The mains power supply case costs £1.77 including VAT and is featured in the latest catalogue from West Hyde Developments Ltd, 9-10 Park Street Industrial Estate, Aylesbury, Buckinghamshire HP20 1ET, Tel (0296) 20441.

## IEE and IERE To Merge

Members of the Institution of Electrical Engineers (IEE) and the Institution of Electronic and Radio Engineers (IERE) have voted overwhelmingly to join forces.

In a ballot held on 11th December last year, 97% of the members of the two Institutions voted in favour of the merger. The new body will be known as the Institution of Electrical Engineers and will be the largest Chartered Engineering Institution in the UK.

The decision to merge was prompted by a growing recognition that the two Institutions were converging in their fields

of interest. Negotiations began almost three years ago and great care has been taken to seek the views of members at each stage in the process.

The new Institution has members among just about every grade of engineer from students to chief executives and aims to represent the electrical and electronics engineering profession in all matters of public concern. It will cover all aspects of electrical, electronic and software engineering in such fields as power, control, instrumentation, broadcasting, radio, telecommunications, computers and information systems.

A joint statement issued by the two bodies promises an enhanced range of Learned Society activities as a result of the merger and looks forward to the adoption of common standards for professional qualifications. It also suggests that agreement on technical standards will be reached more easily in future.


Work is already going ahead to implement the merger proposals and the new body will come fully into being on the 1st October 1988.

The Institution of Electrical Engineers, Savoy Place, London WC2R 0BL, Tel 01-240 1871. The Institution of Electronic and Radio Engineers, 99 Gower Street, London WC1E 6AZ, Tel 01-388 3071.

● Job prospects in the electronics manufacturing industry look better this year than they did during the first quarter of 1986, says temporary staff specialist Manpower PLC. Slightly fewer employers said they would take on more staff this year (down from 29% to 27%) but only 11% plan to cut the size of their workforce compared with 20% last year. The survey notes that this improvement is not apparent in other sectors of manufacturing industry. Growth in the services sector is tailing off, public sector employment is improving and the gap between north and south is becoming wider. Manpower PLC, Manpower House, 270-272 High Street, Slough, Berkshire SL1 1LJ, Tel (0753) 73111.

● The 1987 Instrument Rentals catalogue has more than 100 pages of test equipment, computers and other instruments available for hire. Over 180 new lines have been added since the last catalogue was issued, among them a range of low-cost spectrum analysers and the latest logic analysers from Philips. There is also a section describing second-hand equipment for sale. Instrument Rentals, Dorcan House, Meadfield Road, Langley, Slough SL3 8AL, Tel 01-897 2434.

● Texas Instruments have joined forces with Stag Electronic Designs and Personal Cad Systems to produce a PAL starter kit. It includes four Impact PAL devices from Texas, supporting software on five floppy discs (in IBM PC format) and comprehensive documentation. Stag are also offering a free-of-charge programming service for kit purchasers. The kit costs £75.00 inclusive and can be obtained from Stag Electronic Designs, Stag House, Tewin Court, Welwyn Garden City, Hertfordshire, Tel (0707) 325 136.

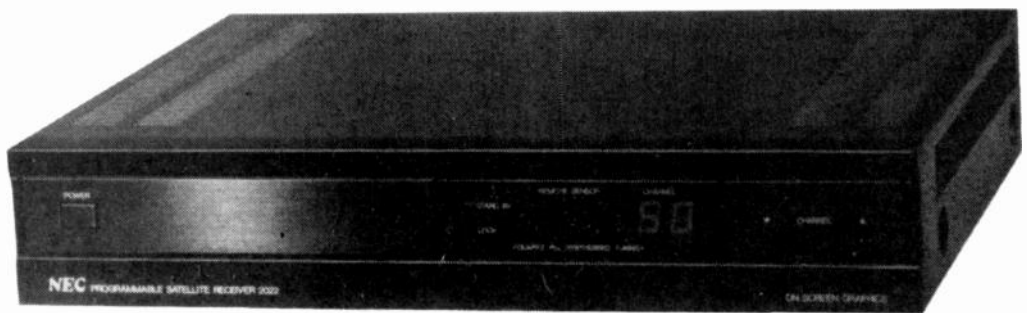

## Satellite Television Receiver Is DBS-Ready

A new satellite television receiver from NEC is claimed to be the first on the market with a DBS facility.

As well as being able to receive existing satellite transmissions, the 2022 includes a MAC format output which conforms to the standard recently selected by EEC countries for future direct broadcasting by satellite (DBS) transmissions. The receiver will drive a B-MAC/D2-MAC adaptor for use with standard television sets and will connect directly to MAC-standard sets when these become available.

The complete system comprises a parabolic dish antenna with a motor drive unit, a low noise block (LNB) downconverter and a set-top demodulator (pictured above) which comes with infra-red remote control.

Up to 89 channels can be preset for instant selection, the 2022 automatically rotating the antenna and selecting X or Y polarisation as required. Selected channels can be locked by the user to prevent children watching them.

The 2022 can be supplied with a 1.5m one-piece antenna or a 1.8m dish made up of separate 'petals'.

The demodulator has 47 of the 89 channels already preset to receive existing satellite transmissions plus French and German DBS broadcasts due to begin within the next two years. The downconverter is completely weather-proof and offers a maximum noise level of 2.3dB.

The 2022 system will be available from selected NEC dealers at prices from £1245.00 inclusive. NEC Business Systems (Europe) Ltd, Camdem Office, 35 Oval Road, London NW1 7EA, Tel 01-267 7000.

## Buy Bi-Hi-Fi

Anyone who has read a hi-fi magazine recently will know that so-called bi-wiring of loudspeakers is the current fashion.

The idea is to separate out the treble and bass sections and feed each of them independently from a single power amplifier. According to the theory, this prevents the high current bass signal interfering with the treble signal and so improves sound quality.

Proponents of the system claim it offers significant improvements at very low cost, the only additional items required being a further set of loudspeaker cables and connectors.

Bi-wiring (and tri-wiring on three-way loudspeakers) has been in use for some time in the USA and is fast becoming popular on top-price audio systems from

other countries. It has had little impact on systems at the lower end of the price range.

Now Marantz is setting out to change that with up-dated versions of its successful Mini-Monitor design. Each loudspeaker is fitted with three terminals, a common signal (+) connection and separate ground (-) connections for the tweeter and the woofer.

A link supplied with the loudspeakers can be used to join the two ground terminals, allowing two-core cable to be used in the usual way. For higher fidelity the link can be removed and three-core cable used, the two ground leads being joined together at the amplifier output terminal.

The Marantz literature notes that four leads are normally used for bi-wiring, with separate ground and signal connections for each drive unit. However, the three-wire system is said to offer

dramatic improvements over simple two-core wiring and has the advantage that three-core cable is cheap and easy to obtain.

The two new loudspeakers are the LD20DMS and the larger LD50DMS which offers higher power handling and an extended bass response. Both use a bass-reflex cabinet design. The LD20DMS measures 230 x 365 x 260mm (9 1/8 x 14 1/8 x 10 1/8 ins) and has a 160mm (6 1/2 in) bass driver while the LD50DMS measures 272 x 414 x 280mm (11 1/8 x 16 1/8 x 11 1/8 ins) and uses a 200mm (8 in) bass driver.

The LD20DMS and LD50DMS are both available now from Marantz dealers and cost £125.00 and £179.00 per pair.

Marantz Audio UK Ltd, 15-16 Saxon Way Industrial Estate, Moor Lane, Harmondsworth, Middlesex UB7 0LW, Tel 01-897 6633.



## The Winners!

Readers with excessively long memories will remember that back in the halcyon days of July last year (was it really that long ago?) we ran the 1986 Readers' Survey along with a free draw for ten free subscriptions to ETI.

Well, we've finally found the key to the office strongbox where the survey entries are stored so here are the ten lucky winners.

Ian McCallum, Kilmarnock. W.S. Potter, Chesterfield. S.W.

Marland, Wigan. Chris Knowles, Stafford. Martin Robertson, Glasgow. Matthew Wood, Swansea. David Hicklin, Derby. D.B. Smith, Sunderland. Alan Todd, Glasgow. K.B. Dales, Middlesbrough.

All the winners were selected by GEOFF (geostationary electronic office form finder) and will receive 12 months free subscription to ETI or have their current subscription extended. Thanks to everyone else who look the trouble to complete the form. Better luck next time!

## World's Fastest Silicon ICs

A new range of frequency dividers from Plessey is believed to offer the highest speeds yet achieved with silicon.

The SP8800 series of prescalars can operate at frequencies from 500MHz to 3.5GHz and are available in divide-by-two, divide-by-four and divide-by-eight versions. They operate from 5V supplies and have a dissipation of around 400mW.

The dividers are fabricated in

bipolar silicon technology and feature complementary output stages with on-chip current sources. Plessey claims the performance exceeds that of comparable gallium arsenide devices in terms of current consumption, phase noise, sensitivity, frequency range and price.

Plessey Microsystems Ltd, Water Lane, Towcester, Northamptonshire NN2 7JN, Tel (0372) 50312.


## New PCB Production Process

A new screen-printing ink from Bayer is the key to a radically different PCB production process.

Unlike conventional screen-printing inks, Bayprint is designed to accept a coating of metallisation when dry. PCB track patterns can be printed onto suitable materials and then covered with copper in an electroplating bath. Because the plating only forms on the printed tracks, no etching is required and both raw materials and energy are saved.

Bayer says the printing can be applied both to rigid board materials and to flexible substrates such as polyester and polyimide film. Large areas and narrow tracks are plated with equal efficiency and a uniform plating thickness is obtained. Soldering properties are said to be excellent and the specific resistance is substantially lower than that obtained with conventional conductive inks.

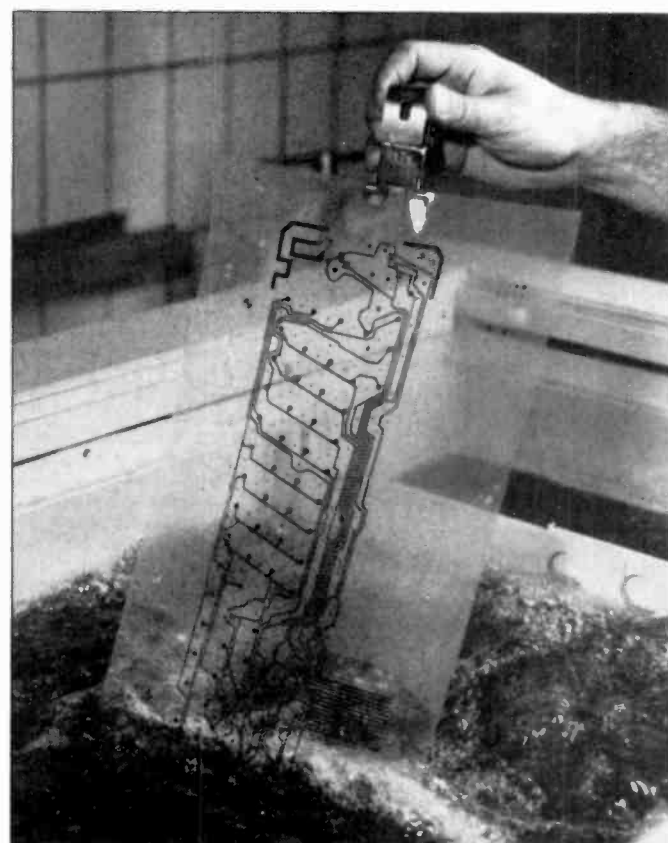Bayer UK Ltd, Bayer House, Strawberry Hill, Newbury, Berkshire RG13 1JA.



● The Image range of 19" racking cases and cardframes is described in an 8-page full-colour catalogue from Imhof-Bedco. Full technical specifications are included along with dimensions, options, accessories, etc. Copies are free from Imhof-Bedco, Ashley Works, Ashley Road, Uxbridge, Middlesex UB8 2SQ, Tel (0895) 37123.

● Monolithic Memories has issued a new LSI data book (7th edition) which is available on request. It covers a wide range of products including PAL and other logic arrays. Contact Monolithic Memories Ltd, Monolithic House, 1 Queens Road, Farnborough, Hampshire GU14 6DJ, Tel (0252) 317 431.

● The snow lies deep and crisp and none-too-even around ETI Towers, so it seems a good time to tell you about an Icy-Road Warning kit from ECW. It's designed for quick-and-easy fitting to the front of a car and has an electronics unit with warning LED which fits below the dashboard. The cost is £12.88 inclusive from Electronics and Computer Workshop, 171 Broomfield Road, Chelmsford, Essex CM1 1RY, Tel (245) 262 149.

NEXT  
MONTH

AN ARGUS SPECIALIST PUBLICATION

# electronics today

INTERNATIONAL

## GRAPHICS PROCESSOR

What are graphics processors and why should you be wanting one? All is revealed next month.

## ROBOTICS TECH TIPS

A bumper collection of short circuits for robot fiends. There are circuits to drive them forwards and circuits to tell them where they're going.

## THE TRUTH ABOUT HI-FI

What colour is the wire in your amp? Does it matter? We separate the fact from the fiction on this and many other supposed design criteria for audio equipment.

## MIDI CONTROL WITH THE BBC MICRO

Continuing our torrid affair with the Musical Instrument Digital Interface, this compact but powerful add-on for BBC micro owners to build offers two MIDI channels to keep the music playing.

## 15 YEARS OLD NEXT MONTH

ETI can leave school when it gets to sixteen. Meanwhile we've got lots of goodies to celebrate this anniversary. Plus there's all the regulars — Tech Tips, letters, news, views, free readers ads, and many other features and projects which go to make ETI the number one electronics mag for April.

## THE APRIL ISSUE OF ETI — ON SALE 6th MARCH ONLY AN APRIL FOOL WOULD MISS IT!

All the articles listed above are in an advanced state of preparation but circumstances beyond our control may prevent publication.



**CRICKLEWOOD**  
ELECTRONICS LTD

**FREE!**  
catalogue

**It's no secret...**

that there is a *real* difference at *Cricklewood Electronics*. That's why you should never be without the **FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE**, for sheer variety, *competitive prices* and *service* from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your **FREE** copy now (no SAE required). You have nothing to lose.

**CRICKLEWOOD ELECTRONICS LIMITED**  
40 Cricklewood Broadway, London NW2 3ET  
Tel: 01-450 0995/01-452 0161  
Telex: 91 4977

VISA Access

ETI

Design your own

**PCB**  
with the

## BBC COMPUTER

Lay out double sided PCB on the screen, separating the layers by colour. Store design on disc, recall for editing or plot it on an Epson HI-80, A-4 plotter ready for 2:1 photo reduction. 40 or 80 Trac disc based software £20.

VINDEREN ASSOCIATES, PO BOX 130,  
BELFAST BT9 6NB. TEL: 0232 667885

## ELECTRONICS & COMPUTING

**INDIVIDUALS** You don't have to continue working on things you don't believe in, with people who'd want you locked up if they knew what you really thought ...

Promoting Equality of Opportunity. For businesses and people who want a say in how their technology is used.  
EIP Ltd, 28 Milsom St, BATH BA1 1DP (0225) 69671

## EXCHANGE RESOURCES

**RECRUITMENT AGENCY  
& BUSINESS CONSULTANCY**

**BUSINESSES** How would you like to try an agency that rewards you for ethical decisions? And deal with businesses which respect your views?

**BATH 0225 69671**



## Low Cost Breadboards

The recently-launched Camboard breadboards are now available at reduced prices thanks to an improved IC socket design.


The breadboards offer most of the facilities common to other solderless breadboard systems but have the added advantage that ICs can be placed in any position rather than being confined to the centre. Potentiometers, switches and other large components can also be mounted directly onto the board using sleeved brass studs. Camboard claims this

flexibility makes it possible to arrange components exactly as they are in the circuit diagram, so simplifying layout and making development easier.

The new IC socket incorporates a plastic spring which pushes IC pins against a tin-plated contact. This arrangement is said to offer a good connection while keeping costs down.

The Camboard breadboard measures 180 x 129mm (7 $\frac{1}{8}$  x 5 $\frac{1}{4}$ ins) and is supplied with a quantity of sleeved studs and up to six IC sockets. Prices start at £2.99 plus VAT.

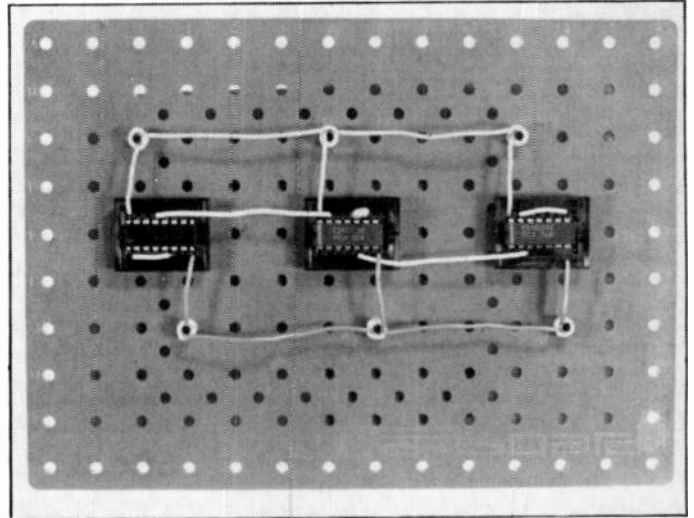Camboard, Unit 16, Barnwell Business Park, Barnwell Road, Cambridge CB5 8UZ, Tel (0223) 240 926.



● The latest Greenweld catalogue lists kits for everyone including amplifiers, light dimmers, timers, transmitters and computer interfaces. There are also a number of breadboard kits which allow components to be re-used many times. For a free copy contact Greenweld Electronics Ltd, 443 Millbrook Road, Southampton SO1 0HX, Tel (0703) 772 501.

● Not a month goes by, it seems, without a new radiation monitor appearing on the market. The latest is the K2654 kit which detects gamma and beta radiation and uses a loudspeaker to indicate the results. It is battery

operated and lightweight and costs £73.75 inclusive from Electronics and Computer Workshop Ltd, 171 Broomfield Road, Chelmsford, Essex CM1 1RY, Tel (0245) 262 149.

● Three new books from Sony provide an insight into fault-finding techniques in audio, television and home computers. The books cost £4.95 each and can be ordered from the Spare Parts Department of Sony (UK) at Thatcham, Newbury, Berkshire. Quote reference S-796-202-01 for the video book, S-796-000-01 for the TV and home computers book, and S-795-100-01 for the audio book.

## Liquid Crystal Adds Colour

A new colour display unit from Ferranti offers high resolution at low cost by combining monochrome CRT technology with a liquid crystal shutter.

The display uses red and green filters which are selected alternately by the shutter. When the red filter is switched on the monochrome tube paints one scan, then the filter changes to green and a second scan is traced on the screen. Any level of brightness can be produced and the two basic colours can be mixed in any proportion to produce various

intermediate colours such as orange and yellow.

The display cannot produce as wide a range of colours as conventional three-gun CRTs but this is not thought to be a problem in many applications. Ferranti expects it to be used in sonars and other military data displays as an alternative to expensive, ruggedised colour CRTs.

Ferranti Computer Systems Ltd, Cheadle Heath Division, Bird Hall Lane, Cheadle Heath, Stockport, Cheshire SK3 0XQ, Tel 061-428 0771.

## DIARY:DIARY:DIARY:DIARY:DIARY:DIARY:DIARY:DIARY:DIARY:

**The Opportunity of a Lifetime — February 3/4/5th**

The Barbican centre, London. The 58th IEE Faraday Lecture presented by ICL at 2.00pm and 6.00pm on Tuesday and 10.30am, 2.00pm and 6.00pm on Wednesday and Thursday. Tickets free (in advance) from the Faraday Officer on (0462) 53331 ext. 292.

**EMC-Susceptibility Of Electronic Equipment — February 4th**

Heathrow Penta Hotel, Hounslow, Middlesex. Seminar and exhibition organised by ERA Technology with the support of the IERE. Contact Laura Christie on (0372) 374 151.

**Batteries: The Cinderella Of The Electronics World — February 10th**

BSI Conference Centre, London. Forum organised by the British Standards Institution. Contact Jackie Mountain on 01-629 9000.

**SMARTEX '87 — February 10-12th**

The Barbican Centre, London. The 2nd Surface Mount and Related Technologies Exhibition. Contact Peter Evans on (01) 855-7777.

**The Electronic Motor Car — February 11th**

The IEE, London. Lecture by M.H. Westbrook of the Ford Motor Company. Contact the IEE at the address below.

**The Which Computer? Show — February 17-20th**

NEC, Birmingham. See February '87 ETI or contact Cahners Exhibitions on 01-891 5051.

**Computer Technology And Architecture For The Next Decade — February 24th**

The IEE, London. Lecture by Dr. Gene Amdahl. Tickets free (in advance) from the Overseas Officer on (0462) 53331 ext. 292

**Power UK/Enclosures '87 — February 24-26th**

Kensington Rainbow Exhibition Centre, London. See February '87 ETI or contact TCM Expositions on (0428) 724 660.

**CADCAM '87 — March 14-16th**

Metropole Hotel and NEC, Birmingham. Conference and exhibition covering the application of computer aided design and manufacturing to many engineering disciplines. Contact Christine Smith on 01-6C8 1161.

**The Code-Breaking Computers Of 1944 — March 26th**

The IEE, London, 2.15pm. Discussion meeting, followed by a lecture on Colossus and German high-grade cyphers in World War II. Contact the IEE at the address below.

**Digitally Implemented Radios — April 1st**  
The IEE, London. Colloquium. Contact The IEE at the address below.

**Fibre Optics In Communications — April 2nd**

University of Cambridge, 7.00pm. Lecture organised by the IEEIE. For details 'phone 01-863 3357.

**The Role of Alternatives In The World Energy Scene — April 7-9th**

University of Reading. International conference jointly organised by a number of bodies including the IEE. Contact them at the address below.

**British Electronics Week 1987 — April 28-30th**

Olympia Exhibition Centre, London. See February '87 ETI or contact the Evan Steadman Communications Group on (0799) 26699.

**Digital Audio Tape Recording — April 30th**


The IEE, London. Lecture by Dr. J. Emmett of Thames Television PLC. Contact the IEE at the address below.

Institution of Electrical Engineers, Savoy Place, London WC2 0BL, tel (01) 240-1871.

# HART

**HART ELECTRONICS** are specialist producers of kits for designs by **JOHN LINSLEY-HOOD**. All kits are **APPROVED** by the designer.

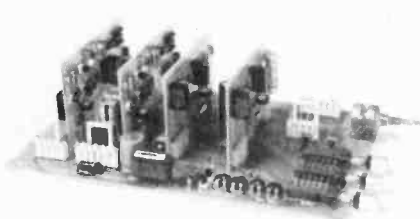**LINSLEY-HOOD CASSETTE RECORDER CIRCUITS**



Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit ..... £33.70  
 VU Meters to suit ..... £2.30 each  
 Reprints of original Articles ..... 75p no VAT  
 860X Stereo Mic Amplifier ..... £8.70

**LINSLEY HOOD 300 SERIES AMPLIFIER KITS**

Superb integrated amplifier kits derived from John Linsley-Hoods articles in 'Hi-Fi News'. Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35 35 Watt. Discount price for Complete Kit ..... £98.79  
 K300-45 45 Watt. Discount price for Complete Kit ..... £102.36  
 RLH485. Reprints of Original Articles from 'Hi-Fi News' ..... £1.05 no VAT

**LINSLEY-HOOD SYNCHRODYNE AM RECEIVER**

Very high quality kit for this recent design featured in 'Wireless World'. This unit represents the first attempt to make a much needed **HIGH QUALITY AM Tuner** since pre-FM days. This will give you Radio 4, or even 1 in better quality than your Eastern 'Tranny'. Advanced construction system, approved by the Author, uses 3 double sided PCBs in a stacked layout for total stability, ease of construction and minimal wiring. This module will form the AM section of an ultra high quality AM/FM switched bandwidth tuner to match our 300 series amplifiers. Power supply and tuning gang will be included with the FM section.  
 K450 JLH Synchrodyne Kit Special Price ..... £59.95

**HIGH QUALITY REPLACEMENT CASSETTE HEADS**



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

**HC20 Permalloy Stereo Head.** This is the standard head fitted as original equipment on most decks ..... £7.66  
**HS16 Sendust Alloy Super Head.** The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response ..... £14.86  
**HQ551 4-Track Head** for auto-reverse or quadraphonic use. Full specification record and playback head ..... £14.80  
 Please consult our list for technical data on these and other Special Purpose Heads. **MA481 Latest version Double Mono (2/2) Record/Play head.** ..... £13.35  
**Replaces R484.** ..... £13.35  
**SM166 Standard Mounting 2/2 Erase head.** Compatible with above or HQ551 4-Track Head ..... £8.85  
**H524 Standard Erase Head.** Semi double gap, high efficiency ..... £2.25  
**H561 Metal Tape Erase Head.** Full double gap ..... £2.35

**HART TRIPLE-PURPOSE TEST CASSETTE TC1**

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.  
**Tape Head De-magnetiser.** Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback ..... £4.54  
**Curved Pole Type for inaccessible heads** ..... £4.85

Send for your free copy of our **LISTS**. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and insurance as follows:

**INLAND** Orders up to £10 - 50p  
 Orders £10 to £49 - £1  
 Orders over £50 - £1.50  
**OVERSEAS** Please send sufficient to cover Surface or Air Post as required.

**HART**  
 HART ELECTRONIC KITS LTD  
 4 PENYLAN MILL  
 OSWESTRY, SHROPSHIRE  
 SY10 8AF

**LED DISPLAY DIGITAL ELECTRONIC CLOCK MODULE**  
 Electronic clock module with MOS LSI circuit, 4-digit 0.5" LED display, power supply and other components on a single PCB. Only needs a transformer and switches to construct a complete pretested digital clock/timer for many applications. Suitable for 50 or 60 Hz mains supplies. Direct (non-multiplexed) LED drive eliminates RF interference. Supplied complete with 240v mains transformer and wiring diagram/data. Order as SOL 144 Alarm Clock Module £6.85


**LIQUID CRYSTAL DISPLAY WATCH MODULE**  
 With LCD display, 2 pieces of Polarising material, backlight diffuser, micro lamp, precision crystal, trimmer, battery contacts and open microcircuit. Untested ..... 5 for £1

**PLESSEY MAINS INTERFERENCE SUPPRESSORS**  
 Filter unit for mains borne interference. Max current 1.5A. Our Price, brand new ..... only £2.27  
 Same item, store soiled ..... only £1.61  
 Similar Unit but 10A. Brand new ..... £3.49

**10W POWER AMPLIFIER MODULE**  
 Mullard LP1173 Amplifier module. Needs 24v DC Supply to give 10 watts into 4 ohm speaker. Size 112x70x29mm. Complete with heat sink ..... Only £2.40 complete with Data

**ALPS FF317U FM FRONT END**  
 Beautiful precision made High Quality variable capacitor tuned FM Front End with Dual-gate MosFet. Covers full FM range of 87 to 109MHz. 12v supply ..... ONLY £8.90  
 Circuit if required 35p

**CAR RADIO IF AND STEREO DECODER**

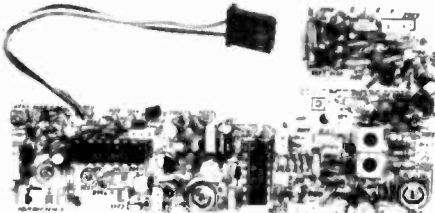

Miniature PCB with 10.7MHz ceramic filters, 2-transformer ratio detector, AX010 noise suppression IC and TCA4500A advanced stereo decoder IC. Only needs front end to make FM tuner or car radio. Complete with circuit. Incredible value at ..... Only £1.99

Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE  
 (0691) 652894

ALL PRICES EXCLUDE VAT UNLESS STATED

**AFFORDABLE ACCURACY**  
 Quality Multimeters from

**Cirkit**

A comprehensive range of Analogue and (Pushbutton or Rotary Switched) Digital Models



**ANALOGUE**

**HM-102BZ** — 10ADC Range, 20kΩ/VDC, Buzzer, Battery Test Scale ..... \$12.50  
 19 measuring ranges  
**HM-102R** — Low end voltage & current ranges, Jack for Audio o/p voltages ..... \$11.00  
 20 measuring ranges  
**HM-101S** — Rugged, Pocket sized meter, for general purpose use ..... \$7.50  
 16 measuring ranges

Battery, Test Leads and Manual included with each model.

Please add 15% for VAT and 70p for p&ap

**DIGITAL**

**HC-7030** 0.1% Accuracy, Standard Model ..... \$39.50  
**HC-6010** 0.25% Accuracy, Standard Model ..... \$33.50  
**HC-5010T** 0.25% Accuracy, TR Test Facility ..... \$39.50  
**DM-105** 0.5% Accuracy, Pocketable ..... \$21.50

All models have full functions and ranges and feature: 3 1/2 digit 0.5" LCD display — low battery indication — auto zero & auto polarity — ABS plastic casing — DC AC 10amp range (not DM-105) — Overload protection on all ranges — battery, spare fuse, test leads and manual

Full details and specification from:

**Cirkit Distribution Ltd**

Park Lane, Broxbourne, Herts, EN10 7NQ  
 Telephone (0992) 444111 Telex 22478

TRADE ENQUIRIES WELCOME




**Interak 1**

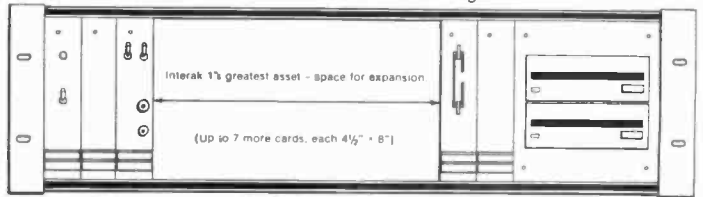**AN EXPANDABLE DISK-BASED Z80A DEVELOPMENT SYSTEM YOU CAN BUILD YOURSELF!**

Universities, Colleges, Industry, Enthusiasts:

Unlike home computers, development systems have entirely "open" architectures, use standard TTL etc. chips (ie no ULA's!), and are built in a proper engineering fashion. Usually these superior products carry a correspondingly superior price tag, but you can build Interak yourself board by board and thus afford a system which would normally be out of your reach and/or understanding.



Interak 1's greatest asset - space for expansion (Up to 7 more cards, each 4 1/2" x 8")

The initial development system has 64K of RAM, a 4 MHz Z80A CPU, parallel ASCII keyboard interface, VDU interface (TV set or monitor), and a floppy disk drive interface for up to 4 drives. Any size (Including 8" double density) can be used, but our 1 Megabyte 3.5" drives are proving very popular because they can fit into the system rack. (and they only cost £89.00 each + VAT). CP/M Plus is available, giving access to thousands of "public domain" programs.

The system can be described as "future proof" because it uses plug in 4.5" x 8" cards in an industrial quality 19" 3U rack. We have been established since 1970, and this system was first made in 1977 so (unlike almost all other computers) it has stood the test of time.

Send two second class stamps, or telephone for a detailed descriptive leaflet, specification, prices, etc.

**Greenbank**

Greenbank Electronics (Dept T1E), 460 New Chester Road, Rock Ferry, Birkenhead, Merseyside L42 2AE. Tel: 051-645 3391

# READ/WRITE

## From QLS To Cars

Having read the January 1987 issue of ETI I must comment on a couple of the articles.

Firstly, the RGB-Composite converter. 'It is useful for QL users' it said. Well, the QL already has a composite video output as well as RGB, mainly because it has an MC1377P chip inside! I wouldn't think another one on the outside would serve any useful purpose!


Secondly, the In-car Circuits featured a 'Thief Staller'. Believe it or not, all the components except the relay can be cut out from this design.

The diagram shows the idea. The relay coil is connected to the auxiliary output of the alternator. This connection gives no output when the engine is stationary and an increasing voltage up to 12V as the engine speed increases. A relay that will open contacts (connected in the ignition coil supply) when 12V is supplied across its coil will prevent the engine from running above idling speed. The Lucas 6RA relay is suitable.

A (hefty) switch in parallel with the relay contacts will act as a bypass.

This is a much simpler circuit and one which has been working well for many years.

H.R. Briggs,  
Adamston, Shropshire.

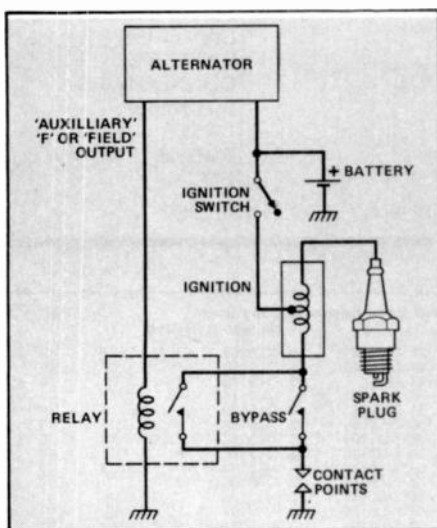

Okay, so we boomed. The QL has got a composite video output but it's cunningly disguised as one pin of the RGB output socket. The circuit itself is none the worse for that.

As to the thief staller, it just goes to show what you can do with a little ingenuity instead of a lot of electronics!

## Aerial Without Smoke

I am writing to you in connection with the 'Aerial without holes' rear window heater aerial In-car Tech Tip in the January issue of ETI.

This company has designed and developed a similar system and it has been manufactured under licence for inclusion in such cars as the Ford Granada and Rover Sterling.

I think your readers should be made aware that building this design according to the instructions given could lead to an inherently dangerous device which could become exceedingly hot and catch fire. If the unit is placed in the car boot (as usually it would) close to the petrol tank, there is the risk of an explosion.

The problem arises from the diameter of wire (0.5mm) specified by the author for the bifilar coils. We have seen Italian devices using 0.8mm wire which have started to smoke in less than five minutes when used. We use 1.2mm wire with only ten turns which we find to be just sufficient for heaters drawing less than 10A. This, we estimate, would cover less than 20% of cars on UK roads today.

D. Waller  
BSH Electronics, Manchester.

Andrew Armstrong, the author of the In-Car Tech Tips, assures us that all the cars he has fitted with this design have continued to run without problems. However, he does admit that these have been modest and older vehicles (of the type prevalent amongst impoverished ETI contributors), which do not draw large currents for the rear screen heater.

It would be advisable for any reader building a heater aerial adaptor to Andrew's design to increase the diameter of the coil wire and to test the device thoroughly before consigning it to the car boot.

## Upgradeable Spec

I have been following the upgradeable amp project over the months, June to November 1986. I have found this to be one of the best projects you have ever published. The explanations and descriptions by Graham Nalty were well informed and easy to follow.

I have built many ETI projects in the past but I've held back from audio designs, being a bit sceptical over sound quality.

Why, then, did the series of articles nowhere mention any measurements? To build the fully upgraded version you are looking at £375 plus. I cannot believe most people will pay out that kind of money without a basic spec. sheet.

Perhaps the figures are too bad to print ...

Rick Hughes,  
Clydach, Swansea.

Graham Nalty replies: When an audio amplifier sounds as good as the Virtuoso preamp, no relevant measurements can be had!

In my experience the only measurement which directly relates to sound quality is power supply ripple rejection. This is tricky to compare between amplifiers.

I could easily have published the input and output specs but I have more productive things to do such as developing the follow-up Virtuoso power amplifier I am currently working on.

I can only invite Mr. Hughes to join the many readers who have completed the project and have been delighted with the sound quality.

## RIAA Again

Although Steve Newing's comments (READ/WRITE, January 1987) on the RIAA equalisation of the Macaulay Experimental Pre-amplifier may be correct, he has fallen into the component tolerance 'trap' like so many others.

When using 5% or even 1% tolerance components it is ridiculous to quote calculated values to six significant figures as he does. If the overall response was  $\pm 1\%$  then a three significant figure result is the best that can be realistically quoted.

A. Moore,  
Handsworth, Birmingham.

ETI welcomes letters from readers on any topic. If you disagree with our learned contributors or just think the world is going to pieces, don't just sit there. Tell us all your troubles. We can't promise to solve anything, but we can print your letter.

Write to: Electronics Today International, 1, Golden Square, London W1R 3AB.

# INSTRUMENTS FROM STOCK

UK's  
**LARGEST**  
**IN-STOCK**  
**RANGE**

**WITH FREE CASE\***

## DIGITAL MULTIMETERS

- \* 105 14 Range 2A DC, 2 Mohm £24.75
- \* 528 14 Range 0.2A DC, 2 Mohm Hfe test £29.95
- \* 615 19 Range 10A DC, 20 Mohm Hfe test £34.95
- \* 6010 28 Range 10A AC/DC 20 Mohm (2MA AC/DC) £38.53
- \* 578 20 Range 10A AC/DC 2M. Buzzer Display Hold £39.68
- \* 5010 28 Range 10A AC/DC 20 Mohm (20µA AC/DC) £41.98
- \* 5010E 34 Range 10A AC/DC 20 Mohm Hfe test Capacitance test, Conductance £59.95
- \* ME540 Auto/manual 10A AC/DC 20M £48.30
- \* 6013 Digital Capacitance meter 8 ranges 200pF-2000 MFD £63.25



**WITH FREE CASE\***

## ANALOGUE MULTIMETERS

- \* 1015 15 Range Pocket 10K/V £8.63
- \* 1035 19 Range Pocket 20K/V 10A DC 10 Mohm £11.95
- \* 102BZ 19 Range 20K/V 10A DC Hfe Buzz 10 Mohm £14.50
- \* 201 19 Range 20K/V 12A AC/DC 10 Mohm £17.95
- \* 2010 20 Range 30K/V 10A DC 20 Mohm £21.95
- \* 3010BZ 24 Range 30K/V 10A DC Buzz 10 Mohm £23.95
- \* 830A 26 Range 30K/V 10A AC/DC 10 Mohm £28.95
- \* 5050E 41 Range 20MEG FET 12A AC/DC 1000 MEG £32.95



## POWER SUPPLIES

- 001c 13.8v 3A DC £14.95 154 5/15v
- 243 0/24v D/3A DC £49.75 0/4A DC £38.25

## LOGIC PROBE

- 07 20MHz Logic Probe £10.95
- TTL CMOS etc.



## OSCILLOSCOPES

- UK TNT DELIVERY £9.00
- HAMEG Dual trace with component testers 8 x 10cm screen: £342.70
- 203/6 Dual 20MHz £462.30
- 204 with a sweep delay
- CROTECH with component tester single trace: £224.25
- 3031 5 1/2 x 6 7/8 cm Display £239.20
- 3036 8 x 10cm Display
- HUNG CHANG
- 620 Dual 20MHz + component test £339.25
- 635 Dual 30MHz Sweep delay £458.85
- 615 Dual 15MHz bat/Mains £458.85

**WITH FREE PROBES**

## STOCKISTS FOR

- Frequency Counters • Generators • Power Supplies • Tools • Computer Equipment • TV/Video Accessories • Nicads • Communications and Security Equipment • Public Address & Audio • [See catalogue]

ALL PRICES INCLUDE VAT

ORDER BY POST OR PHONE. OPEN 6 DAYS A WEEK FOR CALLERS



# HENRY'S AUDIO ELECTRONICS

301 Edgware Road, London W2 1BN. 01-724 3564  
404 Edgware Road, London W2 1ED. 01-724 0323

EDUCATION/TRAINING & EXPORT SUPPLIED


**FREE CATALOGUE**

Send s.a.e. (min 12" x 9") with £1 stamp UK Callers/export £1.00
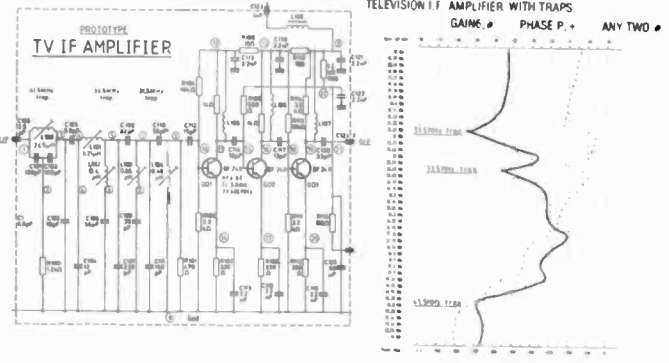
# ELECTRONICS CAD

IBM PC (and compatibles) R.M. NIMBUS, BBC MODEL B, B+ and MASTER AMSTRAD CPC and SPECTRUM 48K.

Number One Systems Limited  
Linear Circuit Analysis Program ANALYSER II  
Circuit Name: IFAMP3 30th September 1986



ANALYSER I and II compute the A.C. FREQUENCY RESPONSE of linear (analogue) circuits. GAIN and PHASE, INPUT IMPEDANCE, OUTPUT IMPEDANCE and GROUP DELAY (except Spectrum version) are calculated over any frequency range required. The programs are in use regularly for frequencies between 0.1Hz to 1.2GHz. The effects on performance of MODIFICATIONS to both circuit and component values can be speedily evaluated.

Circuits containing any combination of RESISTORS, CAPACITORS, INDUCTORS, TRANSFORMERS, BIPOLAR AND FIELD EFFECT TRANSISTORS and OPERATIONAL AMPLIFIERS can be simulated - up to 60 nodes and 180 components (IBM version).

Ideal for the analysis of ACTIVE and PASSIVE FILTER CIRCUITS, AUDIO AMPLIFIERS, LOUDSPEAKER CROSS-OVER NETWORKS, WIDE BAND AMPLIFIERS, TUNED R.F. AMPLIFIERS, AERIAL MATCHING NETWORKS, T.V.I.F. and CHROMA FILTER CIRCUITS, LINEAR INTEGRATED CIRCUITS etc.

STABILITY CRITERIA AND OSCILLATOR CIRCUITS can be evaluated by "breaking the loop". Tabular output on Analyser I. Full graphical output, increased circuit size and active component library facilities on Analyser II.

Check out your new designs in minutes rather than days. ANALYSER can greatly reduce or even eliminate the need to breadboard new designs.

FULL AFTER SALES SERVICE with TELEPHONE QUERY HOTLINE and FREE update service. Used by INDUSTRIAL GOVERNMENT and UNIVERSITY R & D DEPARTMENTS worldwide. IDEAL FOR TRAINING COURSES. VERY EASY TO USE. Prices from £20-£195.

For further details and example computation or for details on our draughting program, please write or phone:

NUMBER ONE SYSTEMS LTD,  
Ref. ETI, Crown Street, St Ives, Huntingdon, Cambs. PE17 4EB.  
Tel: (0480) 61778



# Amplifier Modules

The most sophisticated and highly protected modules available today.

MODULE	POWER/LOAD	PRICE
CE608	60W 8Ω	£21.00 Bi-Polar
CE1004	100W 4Ω	£24.50 Bi-Polar
CE1008	100W 8Ω	£27.50 Bi-Polar
CE1704	170W 4Ω	£35.00 Bi-Polar
CE1708	170W 8Ω	£35.00 Bi-Polar
CE3004	300W 4Ω	£49.00 Bi-Polar
FE908	120W 8Ω	£31.00 MOSFET
FE1704	220W 4Ω	£52.00 MOSFET
FET 3	450W 4Ω	£74.50 MOSFET
CPR 2	Stereo Preamp	£47.95
REG 2	+/-12v Supply	£16.00

Prices include P+P,VAT. All modules are guaranteed for 2 years. For more information on these modules and our other products please write (s.a.e.) or phone.

CRIMSON ELEKTRIK STOKE

PHOENIX WORKS  
500 KING ST.  
LONGTON  
STOKE-ON-TRENT  
STAFFS

TEL.(0782) 330520

Agents:-  
BRADLEY-MARSHALL  
382-386 EDGEWARE RD.  
LONDON.

WILMSLOW AUDIO  
35-39 CHURCH ST.  
WILMSLOW  
CHESHIRE.

# BORELAND

## ELECTRONIC ENGINEERS LTD

26, North Road, Edmonton, London N9 7QY.  
Tel: 01-805 5494

### ELECTRONIC COMPONENT SPECIALISTS

- RESISTORS
- CAPACITORS
- DIODES
- INTERTRATED CIRCUITS
- LEDS
- TRANSFORMERS
- RELAYS
- CRYSTALS
- POTENTIOMETERS
- SWITCHES
- BATTERIES
- CONNECTORS
- SOCKETS
- CASES
- BOOKS
- ETC.

SEND LARGE S.A.E. FOR PRICE LIST

\* FREEPOST your order or enquiry to us \*  
No stamp needed

74LS00	21 74LS38	21 74LS124	90 74LS169	70 74LS257	43
74LS01	21 74LS40	21 74LS125	36 74LS170	90 74LS260	45
74LS02	21 74LS42	47 74LS126	36 74LS173	80 74LS266	30
74LS03	21 74LS48	90 74LS132	50 74LS174	40 74LS273	60
74LS04	21 74LS54	21 74LS133	45 74LS175	40 74LS279	48
74LS05	21 74LS73	30 74LS136	35 74LS190	70 74LS280	150
74LS08	21 74LS74	24 74LS138	35 74LS191	60 74LS283	70
74LS09	21 74LS75	34 74LS139	36 74LS192	60 74LS290	40
74LS10	21 74LS76	34 74LS145	86 74LS193	60 74LS293	39
74LS11	21 74LS78	34 74LS151	65 74LS195	60 74LS295	130
74LS12	24 74LS83	50 74LS153	40 74LS196	70 74LS298	100
74LS13	34 74LS85	52 74LS154	90 74LS197	65 74LS299	210
74LS14	35 74LS86	30 74LS155	45 74LS221	57 74LS348	200
74LS15	24 74LS90	45 74LS156	55 74LS240	65 74LS353	120
74LS20	21 74LS92	40 74LS157	30 74LS241	65 74LS363	180
74LS21	21 74LS93	40 74LS158	39 74LS242	65 74LS366	48
74LS22	21 74LS95	50 74LS160	55 74LS243	70 74LS367	40
74LS27	21 74LS96	67 74LS161	50 74LS244	60 74LS373	60
74LS28	21 74LS107	37 74LS163	50 74LS245	60 74LS374	60
74LS30	21 74LS109	34 74LS164	50 74LS247	60 74LS375	68
74LS32	21 74LS112	36 74LS165	74 74LS249	90 74LS378	94
74LS33	21 74LS114	35 74LS166	74 74LS251	35 74LS393	60
74LS37	21 74LS123	51 74LS168	95 74LS253	52 74LS395	100

Add 70p P & P + 15% VAT  
Turbo International FREEPOST  
LONDON SW16 2BR  
Also: CMOS, LINEAR, MICRO, MEMORY, CRYSTALS. Send for details! Phone 01 769 1639

# FOREIGN PORTS

Mike Bedford sorts out his bits and gets down to some serious handshaking in this comprehensive description of the ways and means of computer interface standards.

Interfacing 'black box' computers to their standard peripherals using the prescribed leads rarely presents problems. For computer enthusiasts with more aspirations in the realm of hardware, impressive systems can be built up at a comparatively low cost by shopping around for printers, VDUs, plotters etc, but only at the expense of complicated interfacing. When home built equipment is to be connected to commercial equipment the challenge of interfacing is even greater. Here we will investigate the various communications standards to which computer peripherals adhere and give advice on how to ensure compatibility between two pieces of equipment.

## Transmission Codes

Before describing the electronic features of common interfaces and how data is transmitted, it will be useful to take a brief look at how data is encoded as this is common to all types of interface. In this context, data is something which can be expressed in the form of letters, figures, punctuation marks and so forth. Encoding schemes allow this character information to be represented in a binary form for transmission by electronic means.

Early codes preceded computers. They were intended for teleprinter applications. One was Baudot code, also known as Murray code. This is a 5-bit code familiar to many radio amateurs where it is used for radio teleprinter (RTTY) communications. A five bit code only allows 32 to the power of 5 (or 32) different characters to be transmitted. This is clearly less than the total number of figures and letters, even if we stick with upper case letters only. This limitation was overcome by providing a special code to switch the receiving set into either numeric or alphabet shift, allowing a single code to be used for both a letter and a figure. However, transmission is slowed as a result of sending frequent shift characters.

The most common codes encountered in computing are ASCII (American Standard Code for Information Interchange) and EBCDIC (Extended Binary Coded Decimal Interchange Code). ASCII may be either 7 or 8 bits. EBCDIC is always an 8 bit code. These sizes allow 128 or 256 character combinations respectively and so obviate the need for an alpha/numeric shift. EBCDIC is generally used on large IBM mainframe computers leaving ASCII as the code usually found on mini and microcomputers, including, of course, home computers. Figure 1 shows the 7-bit ASCII code, illustrated as a code table. 8-bit ASCII is an extension to this allowing 256 characters. The extended form is used to provide semi-graphics characters on a printer or the display of European languages which require extra accented letters. It will be noticed the first two columns of the ASCII code table plus characters 20 (hex) and 7F (hex) are control characters. This means they don't have a printable representation as do most characters. Instead, they

perform some control function at the receiving device. Common examples of control characters are carriage return (CR) and line feed (LF). Control characters can also be used to extend ASCII to give more than 128 (or 256) combinations by using a technique similar to the Baudot shift.

Differences in transmission code is one possible area of incompatibility between communicating devices. Although all the electronics enthusiast is likely to own will use ASCII, it is conceivable an EBCDIC peripheral may be encountered. If the user writes the I/O routines it is an easy task to carry out the code conversion in software. If this is not possible, it may be practical to build a hardware ASCII to EBCDIC convertor. For a serial interface this would not be a trivial task but parallel data may be converted quite easily using an EPROM. (Use of PROMS to carry out data conversion was covered in articles by the author in the February and March 1986 issues of ETI).

## Handshaking

Another concept common to all communications interfaces is handshaking, also known as flagging or flow control. When data is transmitted to a computer or peripheral, the equipment will carry out some operation on it. Depending on the type of device and the particular data received, this operation could take some considerable time. Clearly it will often be possible to send data to a device more rapidly than the data can be handled and so lose some data.

One way to get around this problem is to send the data sufficiently slowly that the receiving device can always accept it. However, if different data patterns take

D3	D2	D1	D0	D7	D6	D5	D4										
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1
0	0	1	0	2	STX	DC2	"	2	B	R	b	r					
0	0	1	1	3	ETX	DC3	#	3	C	S	c	s					
0	1	0	0	4	EOQ	DC4	\$	4	D	T	d	t					
0	1	0	1	5	ENQ	NAK	%	5	E	U	e	u					
0	1	1	0	6	ACK	SYN	&	6	F	V	f	v					
0	1	1	1	7	BEL	ETB	'	7	G	W	g	w					
1	0	0	0	8	BS	CAN	(	8	H	X	h	x					
1	0	0	1	9	HT	EM	)	9	I	Y	i	y					
1	0	1	0	10	LF	SUB	*	:	J	Z	j	z					
1	0	1	1	11	VT	ESC	+	;	K	[	k	[					
1	1	0	0	12	FF	FS	,	<	L	/	l	/					
1	1	0	1	13	CR	GS	-	=	M	]	m	]					
1	1	1	0	14	SO	RS	.	>	N	^	n	^					
1	1	1	1	15	SI	US	/	?	O	_	o	_	DEL				

Fig. 1 ASCII code table.

different lengths of time to execute, selecting a transmission speed which gives the receiving device time to cope with the longest operations means some data is sent slower than necessary. Handshaking is a way to inform the transmitting device that the receiver is ready to receive the next data. This effectively allows for a variable transmission speed.

A slight variation on this theme is concerned with peripherals, such as printers, which can be turned off-line manually. With a printer in this state, the computer connected would need to wait indefinitely before it could send data to be printed. Once again handshaking methods allow this printer-computer co-operation to take place.

Certain methods of handshaking are interface specific. They make use of hardware features of a particular type of interface. However, there are two common systems which can be applied to any interface. These work by sending special control characters down the same lines used to send ordinary data, rather than making use of control lines as is the case for the interface-specific systems. Since this requires data to be sent in both directions, their use is limited to bi-directional interfaces and this tends to limit their application to serial interfaces. Peripherals such as VDUs will always be connected to the host computer by a bi-directional interface, a printer on the other hand may well be interfaced via a uni-directional port.

The terms 'transmitting' and 'receiving' devices, when referring to bi-directional ports means the device's function at a particular time. The roles will swap with a VDU, as the user types data at the keyboard or observes results on the screen.

### XON/XOFF

The first type of handshaking system is called XON/XOFF handshaking. XON and XOFF are mnemonics for two control characters which inform the transmitting device to suspend and to resume transmission respectively. In ASCII terms, XON and XOFF are usually taken to be the control characters DC1 (11 hex) and DC4 (14 hex) respectively. Normally, receiving devices have an internal buffer — an area of memory set aside as a queue into which characters are placed before processing. A point in that queue such as half or three quarters full is the usual time to send XOFF, XON being sent when the buffer becomes almost empty. The receiver does not wait until the queue is full so the transmitting device has time to respond to XOFF.

The second common interface-independent method is ENQ/ACK handshaking. This differs from XON/XOFF in that it is the responsibility of the transmitting devices to specifically check the receiver is ready to accept data, rather than assuming that the receiving device is ready unless instructed otherwise.

When the transmitting device is ready to transmit a block of data it sends the ENQ control character (ASCII 05) to the receiving device. If the receiver has enough room in its input buffer to accept a full block of data it responds with the control character ACK (ASCII 06). Then the data is sent. This system can be operated with a wide variation in the size of a block of data. A pair of devices using ENQ/ACK handshaking are only compatible if they are set up to use the same block size.

Incompatibility of handshaking methods is something which is only likely to be encountered with serial interfaces (such as RS232). The common parallel interfaces all have a single hardware-specific system of flow control. Connecting devices with different handshaking protocols will probably result in data loss by the receiving device. This can be avoided by selecting a very slow transmission speed but this is not an acceptable solution. Differences in handshaking methods can often be over-



*The BBC micro is a home micro with more interfaces as standard than many business and scientific micros.*

come by software if the user has access to the I/O driver routines. Alternatively, it is possible to buy or build special adaptors although these will probably have their own internal processors and are expensive devices.

### Serial And Parallel

Communications interfaces are divided into two broad categories. It is important to recognise this classification, so we will examine the pros and cons of each. As always, when two diverse methods are available for carrying out a particular task each one has its own particular merits. If this were not the case one method would have become obsolete.

The two major types of data interface are serial and parallel. A parallel interface has one conductor for each binary digit (bit) of the character code and so allows a complete character to be transmitted in a single time interval.

A serial interface, on the other hand, uses a single conductor for the data and requires one time interval for each bit of the data which are transmitted consecutively. Assuming a constant bandwidth for a single conductor, data can be transmitted at a higher rate if bits are sent in parallel. For 8-Bit ASCII there will be at least a factor of 8 difference between serial and parallel. (In fact the difference will be in the region of 10 to 12 as a result of start, stop and parity bits which we will come to later).

The price to be paid the greater speed of a parallel interface is a bulkier and more expensive cable. The difference in cost between serial and parallel also increases with the length of the communications path. This means the ideal application for a parallel interface is a short link requiring a large data handling capacity whereas serial interfaces are ideal for longer distance communications where the amount of data to be transmitted is lower.

Whichever is chosen, a long high speed link is going to be expensive!

We will look at a number of different serial and parallel interfaces but at this stage it is worthwhile saying a little about interfacing serial devices to parallel ones. The first point is that the hardware of the interfaces is totally different so it is usually out of the question to carry out a software conversion. Instead a conversion box will be required. This usually consists of a simple microprocessor system with one serial and one parallel interface. The resident firmware will simply read from one interface and write to the other, handling all the handshaking meanwhile.

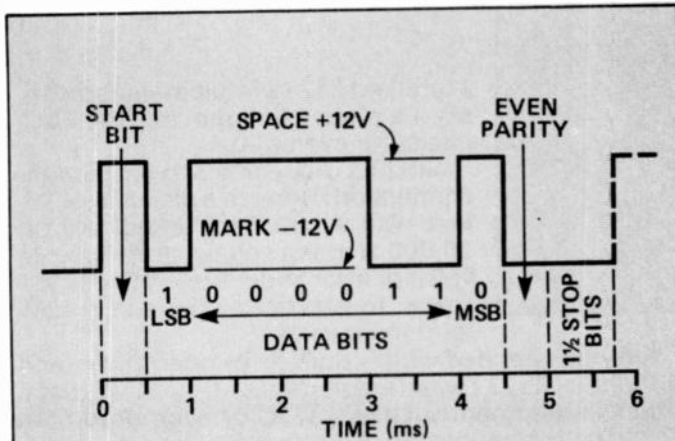


Fig. 2 Example of asynchronous data transmission at RS232 voltage levels. ASCII character 'a' (01100001 binary) with 8 data bits, even parity and 1½ stop bits at 2,000 baud.

## Serial Data Transmission

Serial data can take one of two forms called synchronous and asynchronous transmission. In synchronous transmission the transmitter and receiver are synchronised so the receiving device knows exactly when to expect the next bit of data.

Synchronous transmission may be further divided into 'character synchronous' (such as IBM BISYNC — BSC) and 'bit synchronous' protocols (such as HDLC, SDLC). This needn't concern most readers, but the general technique involves combining a synchronising clock with the data in the transmitter to ensure that the received data stream contains enough transitions to enable the receiver to re-constitute this clock. Furthermore, data is packed into blocks which are bracketed by framing information.

The advantage of synchronous interfaces is that start and stop bits are eliminated with a potential increase in the rate of data exchange. The disadvantage is the equipment is more expensive and transmission needs to be constant to ensure that the two devices remain in synchronisation. Furthermore, the overhead of the framing characters is significant for small blocks of intermittent data such as that from a keyboard.

The type of serial interface most likely to be encountered by the reader is asynchronous. In an asynchronous interface the transmission of characters may start at any time, so long as the previous character has finished. Figure 2 shows the makeup of a 'word' of asynchronous serial data. The diagram shows the composition of a word representing the ASCII character 'a' which has a hex value of 61 (hex) or 01100001 in binary. The serial interface can take one of two states referred to as 'mark' and 'space'. These two states are represented by two different voltage levels, the magnitude of which depend on the electrical specification of the particular interface used. Figure 2 assumes the RS232 interface and accordingly the voltage levels for mark and space are normally -12V and +12V respectively.

Before a character starts, the signal will be at the mark level which represents an idle state. The start of a character is indicated by the signal going to space for a single time interval. This portion of the word is called the start bit.

Next, the binary code for the character is sent using mark to indicate a binary one and space for zero. The least significant bit is transmitted first. The duration of each bit is the same single time interval used for the start bit. Of course, the number of bits depends on the code used. For ASCII this will be seven or eight. The example

of Fig. 2 assumes 8-bit ASCII.

The next time interval is occupied by the parity bit, although this bit may be omitted. If used, the parity bit provides a means of checking the data has been correctly received. This is particularly useful when transmitting high speed data over a long path where interference may be significant. Occasionally the parity bit may be forced to one of the two levels irrespective of the preceding data. This is called mark or space parity but serves no purpose in error checking. More normally, however, even or odd parity is used. In these cases the transmitter sets the parity bit to whatever level is required to ensure that the total number of data and parity bits in the logic 1 (or mark) state is even or odd, respectively. The receiving device carries out the same calculation and checks whether the parity bit is in the expected state. If this is not the case there is a 'parity error' signifying something is wrong with the received data.

To complete the serial word the signal must remain in the mark state for a minimum period of time before the start of the next character. These bits at the end of a word are called stop bits. 1, 1½ or 2 stop bits are commonly encountered. If a space is detected before the prescribed number of stop bits are complete, the receiver recognises this as a 'framing error'.

Even if the data is simple ASCII there are a number of different formats in which the data could be transmitted. There may be seven or eight data bits (although if 8-bit ASCII was in use this would have to be eight), parity may be even, odd, ignored (ie mark or space) or not present and there may be 1, 1½ or 2 stop bits. This gives a total of 30 combinations and shows the difficulty of ensuring compatibility of two pieces of equipment.

## Baud Rates

To complicate matters further, there is the issue of baud rates. This is a measure of the speed of data transmission. High baud rates are clearly preferable. However, high baud rates are more susceptible to noise, this often being a function of the length of the line. In practice this means the longer the transmission path the lower the usable baud rate. As we shall see later some serial interface types allow longer paths and/or higher speeds so the equation includes baud rate, speed, interface type and cable type. A baud is a bit per second and includes the start/stop bits and parity. Commonly encountered baud rates are 50, 75, 110, 134, 150, 300, 600, 1200, 1800, 2000, 2400, 3600, 4800, 7200, 9600, 19600 and 38400. Fortunately some of the lower baud rates are not used much on modern equipment although it may be possible to select them as an option. Nevertheless, the total number of combinations of word composition and baud rates must reach a high number.

It is not usually a hardware task to change these aspects of a serial interface. Serial interfaces are usually driven by a chip called a UART (Universal Asynchronous Receiver/Transmitter) or a ACIA (Asynchronous Communications Interface Adaptor). Common types are the 6850 and 6551. To take these two as typical examples, both allow the word composition to be set up by programming the values of internal registers and the 6551 allows baud rates to be changed in a similar way. Older devices such as the 6850 usually have DIL switches connected to them for altering the baud rate. This means the serial interface characteristics of a computer can be changed by making modifications to the I/O initialisation routines or occasionally by setting DIL switches. On the other hand, peripherals such as printers are usually controlled only by DIL switches, even if this means the firmware reading the DIL switch values and programming the UART accordingly.

ACIAs and UARTS produce data at TTL levels. However, generally data is not transmitted at these levels and


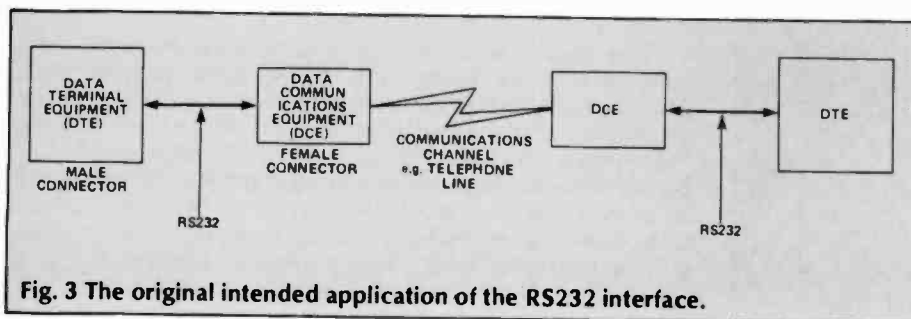


Fig. 3 The original intended application of the RS232 interface.

requires converting to some other voltage before being put onto the transmission line. Conversely, the inputs to these devices are also TTL which will not match the voltage levels found on the received data line. The conversion of transmitted and received data is carried out by line drivers and line receivers.
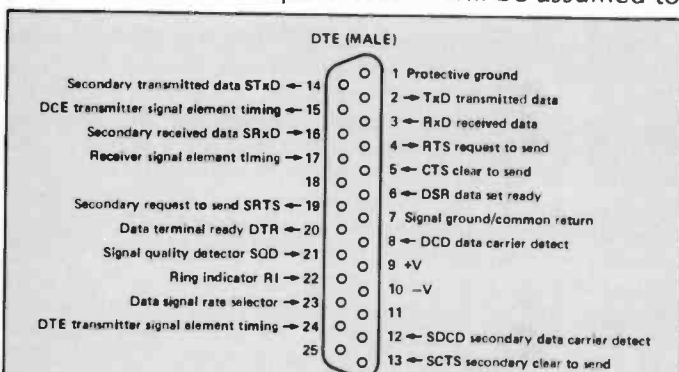
### RS232 Interface

The RS232 interface standard as specified by the Electronics Industries Association (EIA) describes both the functional aspects (the signals available) and electrical aspects (voltage levels, etc) of a serial interface. RS232 runs in parallel with two Comité Consultatif International de Télégraphie Téléphonie (CCITT) standards, namely V24 and V28, which respectively describe the functional and electrical aspects. So RS232 is frequently also referred to as V24. RS232 is usually taken to imply the use of a 25-pin D-type connector. Although this is not actually specified by the EIA, it is covered in ISO (International Standards Organisation) 2110. For the purpose of this description RS232 will be assumed to



**Transmitted Data.** This is the line which carries data from the DTE to the DCE. This will always be present except in the case of a uni-directional link.

**Received Data.** This is the line which carries data from the DCE to the DTE. Once again this will always be present except in the case of a uni-directional link. Clearly either Transmitted Data or Received Data will certainly be present.

**Request To Send.** Direction : from the DTE to the DCE. Requests the transmission of data.

**Clear To Send.** Direction : from the DCE to the DTE. This signal is a handshaking response to RTS and indicates the DCE's readiness to transmit to the DTE, something which can only happen when the DCE is asserting DSR.

**Data Set Ready.** Direction : from DCE to DTE. This indicates the DCE is effectively on line and ready.

**Data Terminal Ready.** Direction : from DTE to DCE. This signal is used to control switching of the DCE to the communications channel.

**Received Line Signal Detector.** (Often called Data Carrier Detect). Direction : From DCE to DTE. This signals the DCE is receiving a valid signal from the DTE.

Fig. 4 The RS232 interface.

a reduced RS232 implementation on say a 5 pin DIN connector (the BBC micro, for example).

RS232 is specified to work with connections of up to a distance of 50 feet with a maximum baud rate of 20,000. It uses a voltage of -15 to -5 volts for mark and +5 to +15 volts for space. In practice -12V and +12V tend to be used.

Although applied widely outside its originally intended sphere, RS232 was designed to connect a DTE (data terminal equipment such as a VDU or computer) to a DCE (data communications equipment like a modem) as shown in Fig. 3.

The assignment of RS232 signals to a 25-way D-type connector is shown in Fig. 4. This also shows the direction of each connection and describes the function of the more commonly encountered ones. The signal descriptions are abbreviated forms of those found in the RS232 specification and it will be noticed they are very much tailored to the modem/telephone line application for which RS232 was intended. Most implementations of RS232 use only a subset of the signals available.

The absolute minimum configuration is Signal Ground plus Transmitted Data and Received Data for a bi-directional interface or Signal Ground plus one of these for a uni-directional link with no handshaking.

The other signals described perform various handshaking functions between the DCE and DTE. DTR is the usual handshaking signal for flow control, a high level (space) indicating to the DCE that the DTE is in a condition to accept data. Conversely, a low level indicates the DTE is not ready. Use of this signal therefore provides an alternative to the XON/XOFF or ENQ/ACK handshaking.

The signals not fully described in Fig. 4 are much less likely to be encountered. They include more obscure handshaking signals, the provision of a secondary data channel complete with its own handshaking and timing signals to enable transmitting and receiving devices to synchronise to the same baud rate.

RS232 interfacing is made difficult because of a number of factors which stem from the fact it is commonly pressed into service outside its specified application. It is often used for connecting a terminal to a computer, or a printer to a VDU without a modem in sight! So there is frequently confusion whether a particular piece of equipment should be considered a DCE or a DTE. Often it is required to connect two DTEs together. It will soon be appreciated that connecting two DTEs together on a pin-to-pin basis does not work. The result would be pairs of transmitters feeding into each other and pairs of receivers connected together, rather than each transmitter feeding a receiver. Another problem encountered is when two devices use different sub-sets of the RS232 signals. One device may require a particular signal which the other device cannot provide. A further situation which, although electrically trivial, can be quite inconvenient is when the two pieces of equipment both use male or both female connectors. Three different cable types are required to cover all eventualities even assuming electrical compatibility.

All this assumes the equipment approximately adheres to the RS232 specification. Experience shows even this can't be taken for granted. RS232 has become one of the most un-standard standards. Some practical suggestions for interfacing RS232 devices will be given in the following up constructional article which describes hardware to simplify the process.



## RS449/RS423/RS422 Interfaces

By the mid 1970s, the limitations of RS232 were becoming obvious. As higher speed hardware became available, the performance of RS232 at high rates of data transmission over long distances became important. To overcome these limitations the EIA introduced a new serial standard, RS449, compatible with existing RS232 equipment. This standard is intended to work in conjunction with one of two electrical specifications, RS423 and RS422, each suited to different applications. The resulting interfaces are therefore referred to as RS449/RS423 or RS449/RS422.

RS449 specifies a 37-way and a 9-way D-type connector. The 9-way connector is only used for the secondary data channel and so is omitted on the majority of equipment. Figure 5 shows the RS449 pin designations.

The major cause of the poor high speed/long distance performance of RS232 is the fact it does not use differential inputs on the line receivers. Failure to use differential inputs increases the likelihood of electrical interference being induced in the communication line. This interference may originate externally or may be induced from other lines within the interface (crosstalk). A further problem occurs when the ground potentials at the two ends of the interface are different. This can cause the receiver to see a quite different signal voltage level to that actually transmitted.

Both RS423 and RS422 use differential inputs. The difference between the two is that RS422 is a balanced interface whereas RS423 and RS232 are unbalanced. In RS423, the differential input is referenced to one of two signal returns, one for each signal direction (an improvement over RS232 where there is only a single signal return). In the RS422 balanced interface each signal also has its own return and the signals are complementary pairs generated by the line drivers. This provides a significant reduction of interference. Any interference induced in a signal line is cancelled by an equal interfering signal in its return. As a result of the much improved electrical specification both RS422 and RS423 specify voltage levels lower than RS232. These are  $-6V$  to  $-4V$  for mark and  $+4V$  to  $+6V$  for space.

The resulting performance of an RS423 interface is 40 feet at  $10^5$  baud or 4000 feet at 900 baud and for RS422, 40 feet at  $10^7$  baud or 4000 feet at  $10^5$  baud. Both are a considerable improvement over RS232. Clearly, if the extra performance of RS422 is not required in a particular application RS423 will be of advantage due to the reduced cabling requirements, balanced interfaces requiring twisted pairs for each circuit. Surprisingly, RS232 still continues to be used in new applications. However, the RS449 standards are certainly starting to make ground.

### 20mA Current Loop

This commonly encountered interface for the transmission of serial data has its origins in teleprinter technology. It does not conform to formal standards in the same way as RS232 or RS449. As the name suggests it is possible to configure a loop with a transmitter and a number of receiving devices although the normal computing application will have a transmitter coupled with a single receiver. A logic 1 is represented by the transmitter causing a current of 20mA to flow through the receiver. A logic 0 is represented by no current. This contrasts with the situation in other serial interfaces where logic levels are represented by voltages.

In a 20mA system, the voltage level required to cause 20mA to flow depends on the internal resistance of the receiving device according to Ohm's Law. Unfortunately, the lack of standardisation of 20mA current

loops means this internal resistance, and hence the voltage required, can vary considerably. Furthermore, the number of receivers in the loop and the length of the cabling will also affect the required voltage level. Use of too low a voltage will simply prohibit a logic level one from being recognised and using too high a voltage will probably destroy the receiver. Fortunately, most modern equipment largely overcomes this problem by use of constant current circuitry.

The voltage source need not even be within the transmitter circuitry. If the transmitter does contain the voltage source it is called an active transmitter but it is also possible to have an active receiver. Obviously an active transmitter must usually be paired with a passive receiver and an active receiver should be connected to a passive transmitter (effectively a current switch). It is

#### Primary Connector (37 way D-type)

Pin	Mnemonic	Description	RS232 Equivalent
1		Shield	Protective Ground
2	SI	Signalling Rate Indicator	Data Signal Rate Selector (DCE Source)
4-22	SD	Send Data	Transmitted Data
5-23	ST	Send Timing	Transmitter Signal Timing Element (DCE Source)
6-24	RD	Receive Data	Received Data
7-25	RS	Request To Send	Request To Send
8-26	RT	Receive Timing	Receiver Signal Timing Element
9-27	CS	Clear To Send	Clear To Send
10	LL	Local Loop Back	
11-29	DM	Data Mode	Data Set Ready
12-30	TR	Terminal Ready	Data Terminal Ready
13-31	RR	Receiver Ready	Received Line Signal Detector
14	RL	Remote Loop Back	
15	IC	Incoming Call	Ring Indicator
16	SF	Select Frequency	
16	SR	Signalling Rate Selector	Data Signal Rate Selector (DTE Source)
17-35	TT	Terminal Timing	Transmitter Signal Timing Element (DTE Source)
18	TM	Test Mode	
19	SG	Signal Ground	Signal Ground
20	RC	Receive Common	
28	IS	Terminal In Service	
32	SS	Select Standby	
33	SQ	Signal Quality	Signal Quality Detector
34	NS	New Signal	
36	SB	Standby Indicator	
37	SC	Send Common	

#### Secondary Connector (9 way D-type)

Pin	Mnemonic	Description	RS232 Equivalent
1		Shield	Protective Ground
2	SRR	Secondary Receiver Ready	Secondary RX Line Signal Detector
3	SSD	Secondary Send Data	Secondary Transmitted Data
4	SRD	Secondary Receive Data	Secondary Received Data
5	SG	Signal Ground	Signal Ground
6	RC	Receive Common	
7	SRS	Secondary Request To Send	Secondary Request To Send
8	SCS	Secondary Clear To Send	Secondary Clear To Send
9	SC	Send Common	

Fig. 5 RS449 pin designations.

nevertheless possible to interface an active receiver and an active transmitter or a pair of passive devices with some additional hardware. Two passive devices require an external power supply to act as the voltage source and two active devices may be interfaced by use of an optical coupler.

As far as wiring is concerned a 20mA current loop interface will have two conductors for each circuit. So a typical bi-directional computer interface without handshaking lines will have four conductors. Usually a simple four way connector will be used but occasionally a device having both RS232 and current loop will use the pins unused by RS232 on the 25 way D-type to implement the current loop signals. It is also worthwhile pointing out that 60mA and even 5mA (in MIDI equipment) current loop interfaces may also be encountered. These both work on the same principle as their 20mA counterpart but are not nearly as common.

Having covered a number of different serial interfaces, it will be useful to say something about converting from one to another. Fortunately this is not usually a complicated task requiring simple conversion of voltage

levels or perhaps a conversion of voltage to or from current. This type of interfacing is quite trivial, the circuitry generally requiring just a number of different line drivers and receivers connected together.

## Centronics Interface

Turning to parallel interfaces we find the type in most common use (certainly on personal computers) does not adhere to a formal standard. Instead the specification is named after the printer manufacturer who first devised the interface. Nevertheless, Centronics interfaces have become accepted as an industry standard.

The voltage levels on the Centronics interface are TTL which means it is not designed for long distance communications. Instead, a typical application is the interfacing of local printers to microcomputers over a distance of a couple of feet. A Centronics interface is only uni-directional so two interfaces would be required for bi-directional operation. However, use of a Centronics interface for a bi-directional channel would be very unusual. Another result of the uni-directional nature of the interface is that XON/XOFF or ENQ/ACK handshaking cannot be used. Instead, specific control lines are used to control the flow of data.

The connector used for this interface is a 36 way type generally referred to simply as a 'Centronics connector'. Both peripherals and computers tend to use the female connector, an interconnecting lead having a male connector on both ends.

Figure 6 describes the pin designations on a Centronics connector. Generally, it will be found there will be none of the problems of interfacing serial devices when connecting together two devices with Centronics interfaces. Certainly, the computer may not support all the status signals such as PE, SLCT and PRIME but this shouldn't prove to be a problem as its I/O routines will be designed to just look at the BUSY signal to get some idea of the printer status.

## IEEE-488 Interface


Otherwise known as the General Purpose Instrumentation Bus (GPIB), the IEEE-488 standard is a parallel interface for the connection of laboratory equipment to computers. GPIB differs from most other interfaces mentioned here in that it is bus structured. That is, it is an interface onto which numerous peripherals may be attached, each accessed individually using a unique address. Since IEEE-488 is not primarily intended for interfacing standard peripherals such as printers or VDUs as are the other interfaces we have covered, we will not deal with it further. Nevertheless, it is a subject worthy of further investigation for the the electronics and computer enthusiast and indeed the construction of IEEE-488 compatible instruments make interesting and useful projects. With automated test equipment made up of a computer and GPIB devices, multiple voltage readings and numerous other measurements can be made in a short period of time and graphs generated by the computer, obviating numerous tedious manual measurements and graph plotting.

## And Finally

Data communications is an enormous field. The subjects covered here should give the reader enough information to attempt connecting together most pieces of equipment which may be encountered whether this involves merely matching interfaces or modifying hardware or software.

Next month Mike Bedford builds the ETIFaker. This useful item of hardware is an RS232 patch box to make easier the connection of any two devices using this most troublesome of standards.

ETI

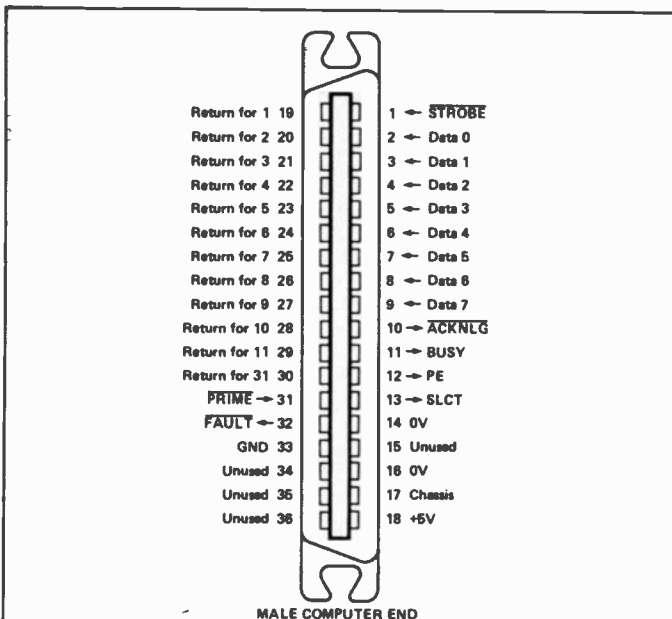

- STROBE** This is a negative going pulse to indicate to the printer that valid data is present on the data lines.
- Data 0-Data 7** These lines carry the actual data to the printer, the least significant bit on DATA 0. A high level represents logic 1 and a low level logic 0.
- ACKNLG** This negative going pulse generated by the printer indicates that it is ready to accept further data.
- BUSY** The level of this signal indicates printer status. The printer outputs a low level if it is ready to accept data or a high level if it is busy, off line or in error condition.
- PE** The printer uses this signal to indicate the out of paper condition. A low level is the normal state.
- SLCT** The printer uses this signal to indicate that it is on line. A high level indicates this selected state.
- PRIME** This is a negative going pulse sent to the printer to cause it to reset to its initial state.
- FAULT** A low level on this printer generated signal indicates a fault condition, including out of paper.

Fig. 6 The Centronics interface.

ElectroMech Industries Limited

Unit 2, Wessex Industrial Estate, Station Lane, Witney, Oxfordshire. Telephone (0933) 75827 or 76605

More Transistors, Thyristors, Triacs, Diodes, 74s, Switch Mode PSU's etc. All at competitive prices. Details on request.

ACCESS or VISA welcome. Just phone your order through, we do the rest. 24hr answerphone. Telex: 83147 Atm. ELMEC Fax: 0665-726753 (GRP 2-3)

BBC Price (Ex VAT) P and P. Master 128K with DFS £395.00 £7.00. Master 128K with DFS & Econet £440.00 £7.00. Master ET-Econet Terminal £319.00 £7.00.

AMSTRAD. New AMSTRAD 1512 Series. Ask for Details. Amstrad PCW850 £389.00 £7.00. Amstrad PCW851 £489.00 £7.00.

MEMOTECH. MTX 512 80K £60.00 5.00. MTX '512 Series II 256K £87.00 5.00. MCL System I combined 1 megabyte drive and controller + system disc £139.00.

EMI DISC DRIVE RANGE. BBC DISC DRIVES. All supplied with Leads, Manual & Utilities Disc. Price (Ex VAT)

5.25" DRIVES, WITHOUT POWER SUPPLY. Single 100K drive, 40 Track £60.00. Single 200K drive, 40 Track D/S £87.00.

5.25" DRIVES, WITH POWER SUPPLY. Single 100K drive, 40 Track £199.00. Single 200K drive, 40 Track D/S £106.00.

5.25" DRIVES, WITHOUT POWER SUPPLY. Single 400K drive, supplied in dual case, with blanking plate, to allow easy upgrade to dual drive £90.00.

3.50" DRIVES, WITH POWER SUPPLY. Single 400K drive, as above £105.00. Dual 400K drive, as above £175.00.

NB: Please add £3.00 P and P per Single Drive, and £5.00 P and P per Dual Drive. Please add £7.00 delivery on Monitors, £3.00 on Modems

CASED/UNCASED FLOPPY DISC DRIVES

5.25" FLOPPY DISC DRIVES. Price (Ex VAT) P and P. 500K 96 TPI D/S 40T £90.00 £2.00.

3.50" FLOPPY DISC DRIVES. 250K SS/DD 40T £35.00 £1.50. 1MB 135 TPI D/S Slimline £75.00 £1.50.

DISC DRIVE ACCESSORIES

DISKETTES. 5 25" Double Sided/Double Density £0.90. 3 50" Double Sided/Double Density £2.50.

MONO/COLOUR MONITORS PHILIPS. High Res Green screen monitor. Model No BM7502 £72.50.

MITSUBISHI - Colour. High Res IBM Compatible Model 1404 £232.00. Med Res IBM Compatible Model 1404E £391.00.

HANTAREX. Bower 12" High-Res Green screen monitor £75.00. CT 9000 14" colour RGB, RGBI - £179.95.

MOEEMS. Nightingale plus Comstar software £120.00. Answer call mini-modem MD101, V21 £73.00.

Miracle Technology WS2000 V21, V23 £95.00. Miracle Technology WS3000 V21, V23 AA AD £275.00.

Miracle Technology WS3000 V22, V21, V22 AA AD £471.00. Miracle Technology WS3000 V22BIS, V22, V23 AA AD £595.00.

Miracle Technology WS3000 V22BIS, V22, V23 AA AD £595.00.

LINEAR ICs

UPCI156H 2.50 1N5401 0.09 79L05 0.33. UPCI182H3 3.25 1N5402 0.09 79L06 0.40.

COMPUTER ICs

HC00 0.28 4000 0.18. HC01 0.28 4001 0.18. HC02 0.28 4002 0.18.

74HC & 74HCT

HC00 0.28 4000 0.18. HC01 0.28 4001 0.18. HC02 0.28 4002 0.18.

CMOS

74VHC00 0.28 4000 0.18. 74VHC01 0.28 4001 0.18. 74VHC02 0.28 4002 0.18.

MONO/COLOUR MONITORS PHILIPS

High Res Green screen monitor. Model No BM7502 £72.50. High Res Amber screen monitor. Model No BM7522 £77.50.

MITSUBISHI - Colour

High Res IBM Compatible Model 1404 £232.00. Med Res IBM Compatible Model 1404E £391.00.

HANTAREX

Bower 12" High-Res Green screen monitor £75.00. CT 9000 14" colour RGB, RGBI - £179.95.

MOEEMS

Nightingale plus Comstar software £120.00. Answer call mini-modem MD101, V21 £73.00.

Miracle Technology WS2000 V21, V23

Miracle Technology WS2000 V21, V23 £95.00. Miracle Technology WS3000 V21, V23 AA AD £275.00.

Miracle Technology WS3000 V22, V21, V22 AA AD

Miracle Technology WS3000 V22, V21, V22 AA AD £471.00. Miracle Technology WS3000 V22BIS, V22, V23 AA AD £595.00.

SPECIAL OFFER

MEMOTECH TWIN 500K DISC CP/M COMPUTER

Includes NewWord Word Processor, Supercalc, BASIC, and Utilities. £399.00 inc VAT & P+P

0 type CONNECTORS. PLUGS. way 9 15 25 37. SOLDER 0.42 0.57 0.81 1.15.

RIBBON CABLE. per metre Grey Colour. 10 way 0.40 0.70. 15 way 0.65 1.10. 20 way 0.80 1.30.

IOC CONNECTORS. PCB Plug. R/A Edge. UMI1286 2.00. UMI1233 3.00.

MODULATORS. UMI1286 2.00. UMI1233 3.00.

HEADER PLUGS. 14 PIN 0.72 28 PIN 1.43. 16 PIN 0.78 40 PIN 1.63.

DIOL DR. 24 PIN 1.04.

TTL74. AC128 0.25 BF200 0.35 MPSA55 0.20. AC142 0.33 BF244 0.30 MPUS05 0.80.

TRANSISTORS. BC107 0.20 BC108 0.20 BC109 0.20. BC127 0.25 BC128 0.25 BC132 0.35.

BC133 0.40 BC134 0.40 BC135 0.40. BC147 0.15 BC148 0.15 BC149 0.15.

BC163 0.25 BC164 0.25 BC177 0.15 BC178 0.15. BC183 0.15 BC184 0.15 BC185 0.15.

BC186 0.15 BC187 0.15 BC188 0.15. BC190 0.15 BC191 0.15 BC192 0.15.

BC245B 0.55 BC245C 0.55 BC245D 0.55. BD131 0.80 BD132 0.80 BD133 0.80.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

CRYSTALS

1 MHz 2.85 40518 0.45. 8432 MHz 1.75 40519 0.40.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

MEMORIES

32768 KHz 0.85 40508 0.25. 100 KHz 2.40 40512 0.40.

VOLTAGE REGS

7805 0.35 45118 0.40. 7808 0.35 45119 0.40. 7812 0.35 45120 0.40.

DIODES

1N4001 0.05 45121 0.40. 1N4002 0.05 45122 0.40. 1N4003 0.05 45123 0.40.

DIODES

1N4001 0.05 45121 0.40. 1N4002 0.05 45122 0.40. 1N4003 0.05 45123 0.40.

DIODES

1N4001 0.05 45121 0.40. 1N4002 0.05 45122 0.40. 1N4003 0.05 45123 0.40.

DIODES

1N4001 0.05 45121 0.40. 1N4002 0.05 45122 0.40. 1N4003 0.05 45123 0.40.

WE MANUFACTURE ANY CABLE ASSEMBLY IN ANY QUANTITY. FULL PRODUCTION FACILITIES. QUOTATIONS ON REQUEST. All items are Brand New and fully guaranteed • Export Orders - carriage at cost. Please add £1.00 P&P to all orders unless otherwise stated. Government and Educational orders welcome • Stock items dispatched by return. All prices are EXCLUSIVE OF VAT - please add VAT to total inc P&P

# HARDWARE DESIGN CONCEPTS

Mike Barwise continues to build his pulse generator. This month he looks at getting the circuit up to speed.

Period, delay and width are the three parameters which combine to produce a controlled pulse train, as opposed to just a square wave output. The pulse period begins with a trigger signal. This is a narrow pulse used for synchronisation of external equipment. Following a specified delay after the trigger a pulse of specified width is generated. The only absolute relation between these three parameters is that the total of delay and width must be less than the pulse period.

## Putting It Together



The correct sequence of events can be accomplished by cascading the programmable counters designed last month (Fig. 1) subject to a few subtle modifications. The delay and width counters are converted to one-shot operation instead of free running by interposition of set/reset (SR) flip-flops between them.

The full theoretical circuit is shown in Fig. 2. The  $\bar{T}$  input of the first stage of each counter acts as a synchronous enable for the whole (three chip) counter. The period counter enable serves as a general run/stop control for the whole pulse generator.

The output pulse (composite RCO) of this counter sets an SR flip-flop, the output of which controls the  $\bar{T}$  input of the next counter (delay). To avoid the counter free running, its own output pulse is fed back to the reset input of the SR flip-flop. The counter thus stops itself when it rolls over. An identical circuit controls the final (width) stage.

The mechanism operates as follows. When enabled, the first (period) stage free runs. It outputs a pulse each time it rolls over. This pulse is output to a trigger out socket, and also enables the second (delay) stage. This outputs a pulse as it rolls over, which stops it and starts the final (width) stage. This last stage outputs a pulse similarly as it rolls over, which stops it. The delay and width stages then wait disabled until the next period pulse arrives.

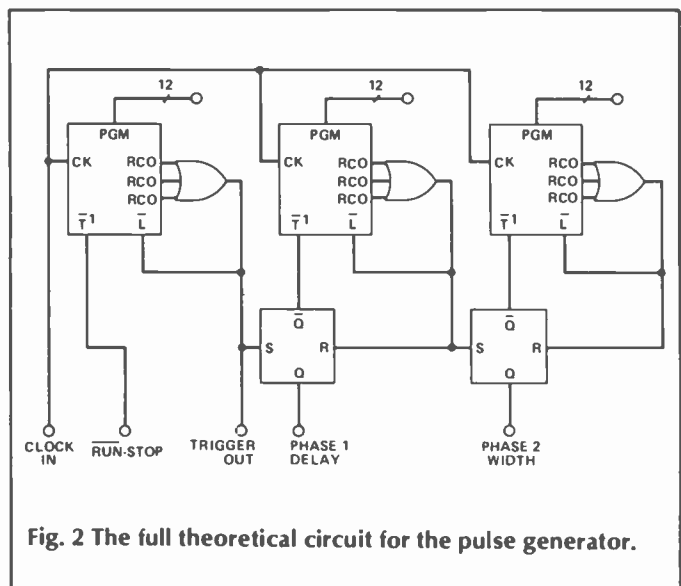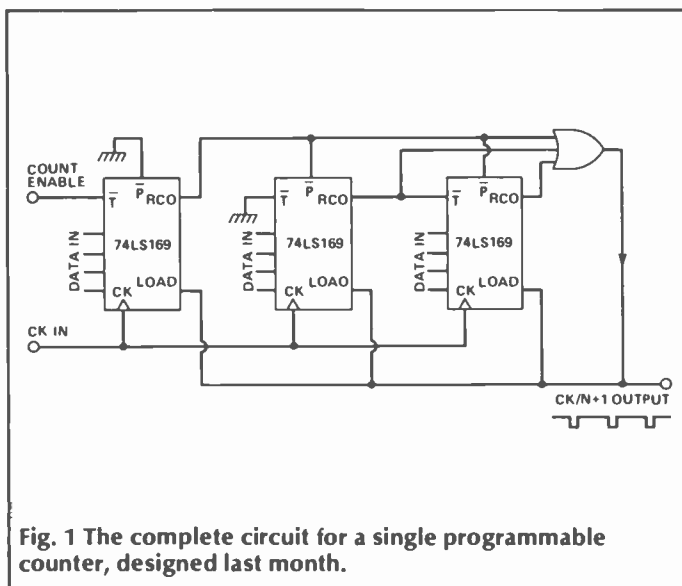Signals can be taken from various points to provide alternative outputs. The most convenient points are the true (non-inverting) outputs of the run/stop flip-flops on the delay and width stages. The output of the final stage (width) flip-flop provides the conventional delayed positive going pulse of specified width, and the output of



the second stage (delay) flip-flop provides a positive going pulse equivalent to the delay duration. Both these signals are useful.

## Practicalities

It would be very easy to just sling the theoretical circuit together without much thought, and it would probably work.

However, I have specified that this is going to be a precision pulse generator. Let's investigate where hazards exist and refinements could be made.

Step one is to look at our three chip counter (three by 74LS169 or 74F169). It is immediately apparent that there is no method of external reset or preset in Fig. 1. The counter will power up at an arbitrary point in its sequence, and we have no over-ride.

This is not a good idea at all. It leads to very messy start-up as each of our three counters (for period, delay and width) will probably power up in a different condition.

However, there is an excellent and simple solution to this problem. Our three RCO signals pass via a three input NOR gate and an inverter to the LOAD feedback. Replacing the inverter with a two input NOR gate (Fig. 3) allows external preconditioning of the counter by taking the spare input to the NOR high, thus enforcing a LOAD state at all stages of the counter. This input must be held LOW to run the counter.

## How Fast Can We Go?

This problem solved, we now have to look at timings. Let's take the 74LS169 to start with. The Texas Instruments data sheet shows the delay between CLOCK and RCO going low as typically 17ns and as a worst case 25ns. The propagation time of the three input NOR (74LS27) or a two input NOR (74LS02) is the same for both transitions — typically 10ns, worst case 15ns.

The total delay for the feedback loop between a clock and the application of a valid LOAD at the 74LS169 LOAD pins is therefore typically 17+10+10ns (37ns) and worst case 25+25+15ns (55ns). The worst case figure is always the important one as you can't assume any individual device will perform better than worst case, although most do.

Looking again at the 74LS169 data sheet, we find that the recommended operating conditions require a setup time for LOAD of minimum 6ns. For safety, we have to call this 10ns. This is the length of time a stable signal must be present at the LOAD pin before the clock which performs the LOAD. This 10ns must therefore be added to the previous propagation delays, yielding a worst case (ie safe) total of 65ns. From this it is simple to calculate the maximum acceptable clock frequency the counter will respond to, in this case 15.38MHz.

## 10 MHz

To make programming more meaningful (65ns increments are silly!) we call it 10MHz for the 74LS components, giving a resolution of 200ns to the counter (remember from last month that the minimum output period is twice the clock period). Note, though, how these results compare with the published maximum frequency for the 74LS169 — typically 35MHz, worst case 20MHz.

These values are for open loop (non-feedback) circuits. Whenever you use feedback with counters, you must expect to roughly halve the maximum operating frequency. Some people will call this excessively

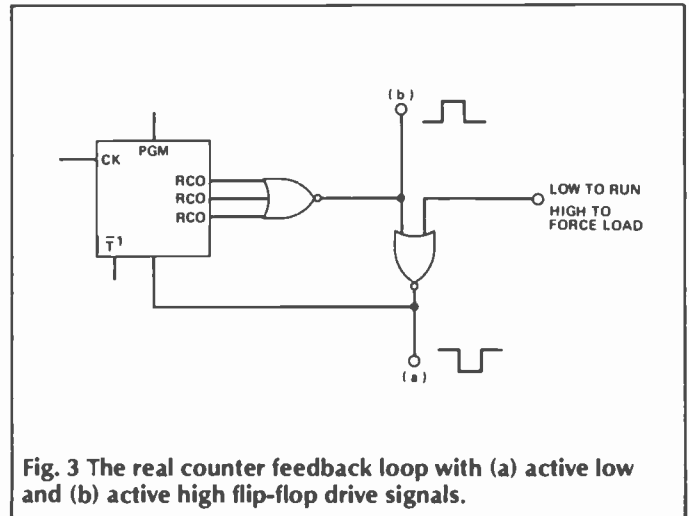


Fig. 3 The real counter feedback loop with (a) active low and (b) active high flip-flop drive signals.

cautious, but at least the result is absolutely guaranteed to run.

Now come the SR flip-flops which control the counters. Unless we are careful, the transition between one counter and the next will be sloppy, and performance will be spoilt.

For example, if the period counter load signal (Fig. 3 (a)) is fed forward to the set input of the SR flip-flop, the propagation delay of that flip-flop plus the set up time for the T input of the next (delay) counter must be added to the previously calculated delay to determine the safety margin available before the clock pulse that will start the delay counter.

## Flip-Flops

A typical SR flip-flop such as the 74LS74 might seem a suitable choice for this application. However, before we jump for this choice we should look more closely at?

The propagation delays for rising and falling outputs are substantially different — 13-25ns (rising) and 25-40ns (falling). This does not bode well but for the moment let's just look at the rising output required to start the following counter.

We already have a cumulative propagation and setup delay of 65ns. Add to this the worst case rising edge propagation delay of the 74LS74 (25ns) and you get 90ns. The flip-flop output is applied to the T of the following counter to enable it and the T input requires a *minimum* 14ns setup time.

The grand total is therefore at least 109ns and probably something like 115ns for real safety, bearing in mind that all these worst case figures are quoted in the data sheets at the almost unachievable 5V and 25°C.

This already reduces the maximum frequency of operation below the 10MHz we just chose and there's worse to come. As each counter stops itself by resetting the flip-flop with the same signal that starts the next counter, the total feedback time is still further increased on reset by the 74LS74 negative going delay of 40ns instead of 25ns.

The grand total is therefore 130ns, yielding a maximum frequency of 7.69MHz, which rationalises to 5MHz for convenience or to 6.66MHz for a moderately useful 300ns resolution. We have thus lost 30% of our single counter performance in cascading two counters and rendering the second a one-shot.

## Improving Performance

Obviously, we need a much faster flip-flop and also one with less discrepancy between rising and falling pro-

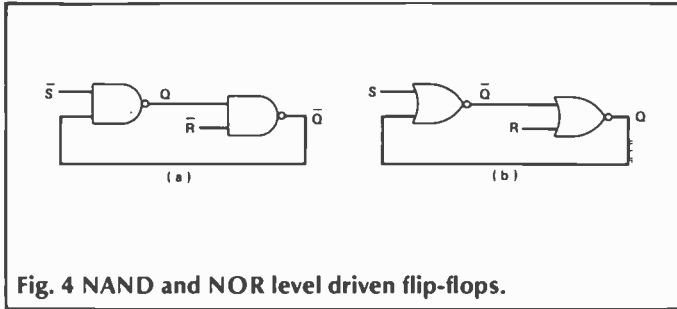


Fig. 4 NAND and NOR level driven flip-flops.

propagation delays. One answer is to build a simple flip-flop out of cross-coupled inverting gates. Either NAND (74LS00) or NOR (74LS02) gates may be used (Fig. 4) and the choice depends on the polarity of the driving signals available. Let's reason it out.

NAND flip-flops require low level inputs to cause change of state and NOR flip-flops require high levels. It is important to appreciate that, although a change of state follows rapidly on the application of the relevant input, these are NOT edge triggered, but level controlled circuits. This means that both inputs must never be activated simultaneously, or an undefined output will result. We don't have a problem here, as our cascaded counters cannot possibly cause this to happen, due to the sequential activation of each by the previous one.

The obvious driving signal is the active low LOAD feedback as in Fig. 3(a), so we will choose a NAND flip-flop to start with.

The propagation delay of the flip-flop is effectively twice the propagation delay of the gates used, so we look this up and find that for a 74LS00 the delay is 9ns (rising) and 10ns (falling) typical, and 15ns (either direction) worst case. Again taking worst case figures this makes our flip-flop propagation time 30ns, or roughly midway between the two extremes of the 74LS74 so the main benefit is equal delays in both transition directions. The total propagation plus setup delay using the NAND flip-flop is thus 25+15+15+10+30+15ns, or 110ns, so we still can't quite achieve 10MHz.

## Fine Tuning

However, we can improve on this a little bit, and achieve a real 10MHz clock rate. As all the timings we've looked at above are guaranteed worst case, we can squeeze every extra nanosecond out of the system as long as we don't cross the specified limits. This is why I insist on worst case timings, so you have a small tuning latitude.

Where can we save a little time? Looking back at Fig.3, we can see the flip-flops are driven simultaneously with the counter LOAD, by a signal which is an inverted replica of the combined RCO. The inverting gate adds a 15ns delay and also introduces a hazard in Fig. 3(a). Did you notice it?

The hazard results from the external reset we built in, combined with the take-off point for flip-flop control. When we enforce the reset (counter LOAD), we also drive the following flip-flop SET. As the next counter is also driven to LOAD condition, it feeds back to drive the RESET of the same flip-flop simultaneously. This is not allowed. In this configuration, the first input to go away would decide the final state of the flip-flop and this would be the result of internal speed differentials in the order of a couple of nanoseconds. Each flip-flop would effectively take up an arbitrary state and we would have no control over the system.

Taking the flip-flop drive from the 74LS27 three input NOR (Fig. 3(b)) before the two input NOR (74LS02) covers this hazard. The SET input of the flip-flop remains undriven, and the succeeding counter reaches round

and resets it ensuring a defined state. However, the big gain is the precious 15ns. We have already established that an individual counter built from three 74LS169 chips can run at 15.38MHz or comfortably at, say, 15MHz, but the cascaded one-shot system would not quite attain 10MHz (110ns cycle).

By covering the reset hazard as above, we save the propagation time of the 74LS02, or 15ns. This yields 95ns total which is well within the 10MHz operating range. The proviso is that we now need flip-flops which respond to *high* level inputs instead of low levels, so we substitute NOR gates in the flip-flops. The propagation time of the NOR gates (74LS02) is the same as the NAND (74LS00) so we are all square, and able to run at 10MHz using 74LS series devices.

## Implementation

At 10MHz, using 74LS series TTL, as long as the circuit is adequately decoupled, you have more or less total freedom of layout and use of redundant gates. The inventory can thus be reduced to nine 74LS169 counters, one 74LS27 triple three input NOR, and two 74LS02 quad two input NOR packages.

In order to attain twice the system speed, the whole circuit must be implemented in 74AS (Texas) or preferably 74F (Fairchild) series TTL. The same calculations apply, but as 74F works at up to about 90MHz (open loop), a 20MHz clock yielding 100ns resolution is quite practicable. However, there are problems.

When using 74F or 74AS very stringent physical layout rules must be adhered to. Device decoupling is essential and should be accomplished by a low inductance ceramic capacitor close to the Vcc pin of every chip. The whole top surface of the PCB should be a common ground plane, with the ground pin of each device directly coupled to it.

It is most important to avoid significant differential clocking rates within a chip, and preferable to ensure that there is a progressive, rather than a sudden rise in speed between adjacent devices.

This means using more chips and leaving redundant gates unused where there could be conflicts. Thus each counter stage of our pulse generator will consist of three 74F169 counters, one 74F27 and one 74F02, leaving two three input NOR gates and one two input NOR gate spare in each stage. These should all have their inputs terminated as in CMOS practice to avoid them switching due to noise, and each counter stage should ideally be well spaced from the others. Even so, the whole circuit should fit on an extended single eurocard of 100x200mm.

In either version, the CLOCK should be buffered with a fast high current driver, as nine chips have to be clocked, which is too much load for a conventional crystal oscillator. One of the neatest solutions is to use a device like a 74LS (or F) 244 buffer, which will deliver enough drive for 10 inputs guaranteed. Once again, when using the 74F device, all unused inputs should be terminated.

## And Now

The complete pulse generator so far has a range of frequencies of 1000:1 controlled by the data inputs to the individual counters. This is not nearly good enough for our proposed top notch instrument. Next month I shall look at the design of a programmable clock divider to accompany the pulse generator to increase that range to 1000000:1.

We shall also begin construction of the pulse generator. As the PCB design and layout for the 74F series TTL used is quite crucial, next month I shall begin with the construction of the range board — a comparatively simple circuit.

ETI

ETI MARCH 1987

# THE TRANSPUTER

Semiconductor saviour or silicon hype? Mike Barwise delves into the workings of the wonder chip from Inmos.

The Inmos Transputer range of microprocessors first became available around November 1985, but has been easily obtainable on a small order basis only within the last few months. It is too new to have been extensively described, but it is worthy of attention as a remarkably innovative design.

The Transputers are the outcome of more than three years development, and represent a radical departure from traditional Von Neumann architecture microprocessors. They were developed simultaneously with the Inmos high level language, Occam, and the machine level architecture and instruction set have been optimised for the support of high level languages, with the emphasis on concurrent processing (multi-tasking).

Concurrency is supported by the hardware implementation, rather than by the software real-time executive (RTE) used in most micro systems. This approach substantially reduces the control overhead in single processor time-multiplexed pseudo-concurrency, and additionally automatically chooses the optimum points for task switching, according to such factors as the size of the restoration parameter block needed, or whether a routine is idling pending input from a data channel.


The Transputers do even better than this. Each processor is equipped with a number of high speed asynchronous serial links. These appear to the processor identical to the mechanisms it sets up for inter-process communication in single processor pseudo-concurrency. It is thus possible to take a set of concurrent procedures running on a single Transputer and install each routine on a separate processor connected to the others by the serial links, allowing true concurrency. This means software can be developed on a (relatively) low cost single processor development system to run on a multi-processor array.

Transputer processor arrays have enormous advantages over conventional multi-processor systems. In multi-tasking systems, the bandwidth available to any task is roughly proportional to the reciprocal of the product of: the memory access cycle time, the number of processors sharing the memory, the scheduling overhead time, and the number of re-arbitrations per second.

From this it is clear there is little gain in throughput by using several conventional processors over task-switching on a single processor. Unless some processors can perform independent tasks without reference to shared memory, the only real gain is any reduction in the scheduling overhead due to local variables being stored in the maps of different processors and thus not requiring saving and reloading to and from parameter blocks.

Multi-tasking on a single Transputer is similarly constrained, although the hardware control of timeslicing reduces the scheduling overhead dras-

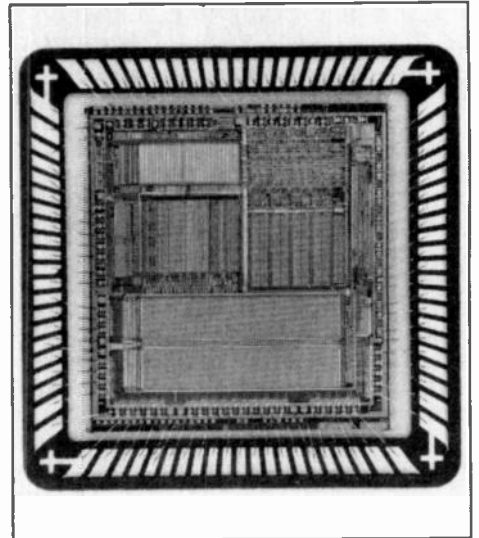The IC mask of the T414 32 bit Transputer chip.



tically. However, the Transputer multi-processor array has bandwidth which rises effectively in proportion to the number of Transputers operating in the system, due to the total absence of shared memory (allowing true concurrency) and the ability of tasks to be scheduled according to data demand and availability.

This means that to upgrade the system performance, you simply add more Transputers. There is obviously a limit, but I have seen a system with 64 Transputers operating concurrently in parallel in a nineteen inch rack about two feet high, and yielding 640 million instructions per second (MIPS)!

The simplicity of the user-visible Transputer hardware implementation is very appealing, as is the rare virtue of compatibility across the range of Transputers:

**T414** 32 bit, 4 Gbyte map, 20 MIPS

**T212** 16 bit, 64 Kbyte map, 10 MIPS

**M212** 16 bit, 64 Kbyte map dedicated disk processor.

**T800** The latest announcement. Floating point maths processor. 32 bit integer, 64 bit floating point processors, 1.5 MFLOPS, 4 Gbyte map.

For practical purposes, a program written for any Transputer can be executed on any other, regardless of processor word length.

## General Architecture

For those of us who can afford Occam (about £10,000) the processor architecture is really irrelevant, but it is worthy of description.

Obviously there are differences in the memory maps of Transputers with different word lengths, but they all obey the same principles. All Transputer address maps are coded in twos-complement. So the lowest address is 80n (hex), and the highest address is 7Fn (hex). In any Transputer, the communication links are positioned at the lowest addresses of the map and

are each one word wide. Above these, a small block of memory is dedicated to processor use and the rest of the map is free to the user.

Each Transputer has fast read/write memory built-in. This is addressed in the lowest 2K or 1K of the map. So it is possible to use the processor for limited tasks without any external memory.

Peripheral devices may be memory-mapped to the external addresses and any device can take command of the external bus for DMA transfers. This is fairly standard on 16 and 32 bit micros, but a feature unique to the Transputers is that during DMA to the external map, a procedure in internal memory can continue executing without interruption.

One minor difference between the 32 bit and 16 bit devices is the external memory interface.

The 32 bit device is designed to drive dynamic RAM, and provides all the required control signals without any external support. The interface can be configured for almost any timing specification likely to be encountered. This causes a small block of memory at the top of the map (where ROM normally resides) to be set aside for RAM interface parameters.

The 16 bit Transputer expects fast static RAM as external memory. It supports the standard interface timing expected by byte-wide devices of 2K, 8K and 32K. A hardware (externally driven) wait state can extend access time for slower memories. Additionally, a real-time command pin can cause dual byte-wide memory access to eight-bit interfaces.

Largely concealed from the user are the communication components — the link interfaces (supporting full duplex 10 or 20 Mbaud asynchronous communication) and two timers used for concurrent task scheduling.

Perhaps the most amazing thing is that all this fits on a single silicon die not quite 12mm square!

### Processor Registers

All Transputers have a common set of word-wide processor registers.

**I register.** The Instruction pointer. This is a standard program pointer which increments as the program runs. All instructions are one byte long, to avoid conflict with differing word lengths across the Transputer range.

**W Register.** The Workspace pointer. This is a pointer to the base address of the current workspace area. There is a minimum of one workspace area per processor in memory, and each is a conventional base plus offset array.

**O Register.** The Operand register. This register holds the operand of the instruction about to be executed. The O Register is cleared after each execution.

**A, B and C Registers.** These three word-wide registers form a three level 'last in, first out' evaluation stack. The stack can be manipulated to a certain extent (inversion of the top two elements) and has a lot in common with the software driven stack in Forth.

All these registers are used by conventional sequential processes. When switching between processes, the contents of the relevant registers are exchanged with RAM parameter blocks. There is also an error flag register for use by arithmetic operations. The error flag can be directly controlled by the user, both in terms of its state, and the action taken when it is active.

A separate set of registers is provided to control concurrent processing. These can be initialised by the user, but are mainly manipulated in the execution of specific instructions associated with concurrent pro-

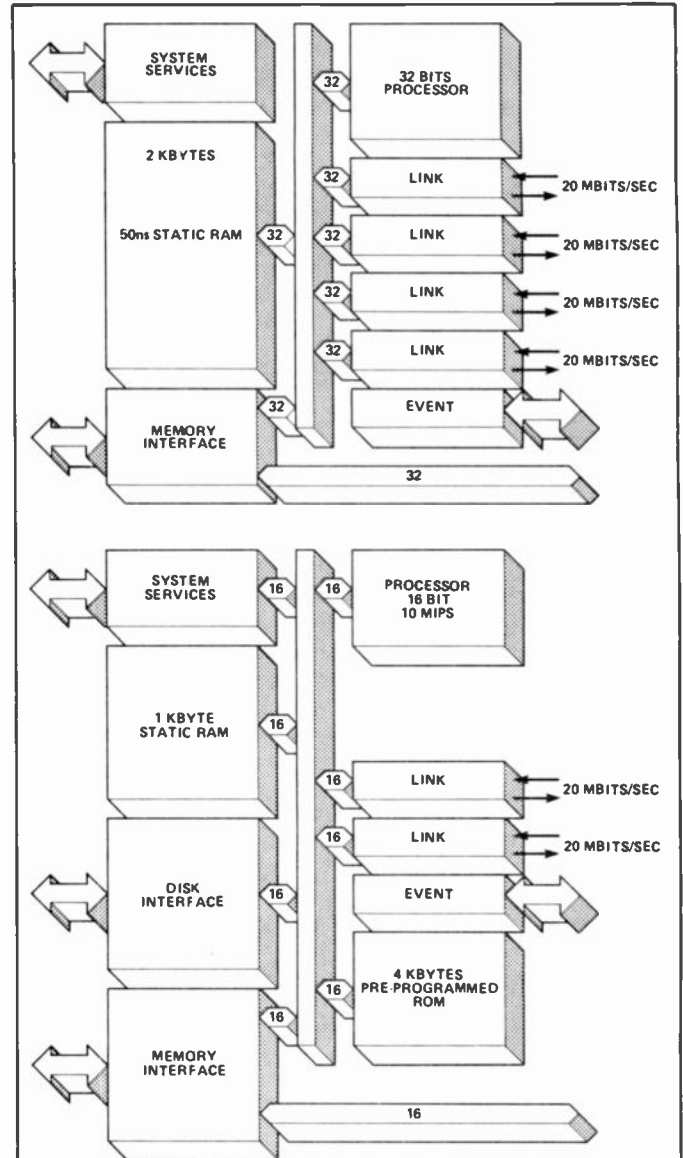


Fig. 1 Architecture of the T414 and M212 Transputers.

cessing. One subset contains pointers to the front and back of two alternative priority queues for concurrent processes, and the remaining subset contains timer and clock control parameters for timeslicing.

### Special Features

The Transputer is equipped with some extremely imaginative solutions to standard 'heavy' problems associated with debugging and initialisation.

According to the logic state of a select pin, RESET either jumps to the highest map address (ROM space) or expects boot data from a hardware link. When starting in ROM, the first instruction will be a backward jump to the real program start as in a conventional system.

If the second option is selected, the first link to go active becomes the boot source and data is then accepted until a specified number of bytes has been received. These are entered sequentially in memory from the lowest free address and when all have been accepted, execution is passed to this address. This facility allows both fast debug and ROMless system operation.

While the Transputer is waiting for a boot from link, a PEEK or POKE instruction may be sent down the link and this will be performed before the wait for boot data is resumed.



On general reset register information is lost. However, the activation of an ANALYSE pin at reset time causes retention of certain critical parameters for debug purposes.

## Interconnections

A support chip, the CO11 link adapter, allows the serial links to be connected to parallel interfaces. This device has two modes of operation. It can act as a memory-mapped bidirectional peripheral look-alike, for coupling to other microprocessors, or as a dual handshaked port, each half of which is reminiscent of a (fast) Centronics interface.

Transputers can be directly interconnected to each other without link adapters if they are no more than about 30cm apart, and in this configuration data transfers are effected at 20MBaud. Over long distances, each Transputer drives a local link adapter, and the long interconnection is via a parallel link between the two back-to-back adapters. The standard data rate in this configuration is 10 MBaud, but as handshake is automatic, two transputer links working at different rates can be coupled without problems. The faster link will be handshaked to intermittent byte transfer, and the overall throughput will be that of the slowest link.

The link adapters also interface to the outside world and other processor families, allowing an enormous variety of intelligent peripheral handling options.

## Appraisal

The Transputers are effectively reduced instruction set processors, and as such have a phenomenal throughput for their clock rate. This, combined with

the almost zero requirement for external support devices, makes them a very attractive solution for compact high performance systems.


The main current objection is one of cost. Although the chips themselves are comparatively cheap (at the time of writing they start from about £160), Occam is horrendously expensive at £10,000. This is obviously not an economic proposition unless you are programming Transputers commercially all day long. On the other hand, most conventional development systems pan out at this sort of figure, even for devices like 8086, so the transputers are by no means unrealistically priced.

Overall, I like the Transputers. All the innovative features are intensely *practical*. They form an entirely new departure in microprocessor concepts. They are essentially high level processors. That is, their hardware conforms to the constructs of high level language practice, rather than being an arbitrary configuration which requires a high level software model.

Among others, a significant outcome of this is the absence of the need for real-time executive, releasing masses of memory to the Transputers for extended user applications. The hardware timeslicing still further reduces the need for RTE, yielding maximal performance at execution time.

The Transputer code's virtual independence of hardware implementation renders extant working targets upgradeable without extensive reconfiguration. The 'it won't run on an XYX model 2' should never arise.

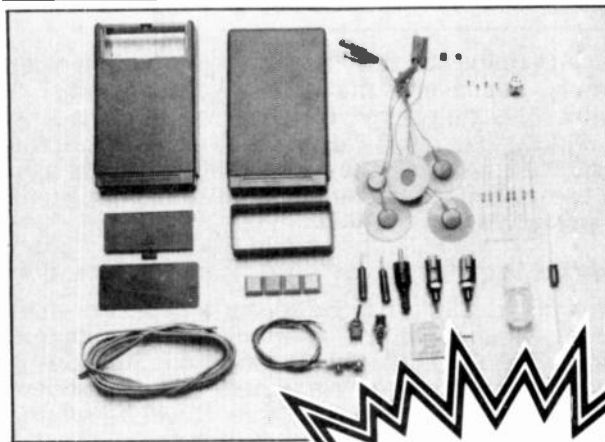To sum up, it's well worth keeping in touch with Transputer developments. Although few of us will be owning or running Transputer systems for a while yet (though there is an Inmos evaluation board for the IBM PC), this is definitely the way of the future. **ETI**



Note. Parts supplied may not correspond exactly to the photograph. Offer while stocks last — order early!

**COMPLETE SET  
ONLY £13.95**  
+ 60p p&p

A complete set of parts, including case, professional electrode pads, special conductive gel and full instructions, to make a highly responsive GSR Bio-feedback monitor, as featured in ETI December 1986. By special arrangement, we can offer the complete parts set for ONLY £13.95 + 60p postage (UK only) inclusive of VAT.

\* The expansion parts set contains all parts except for the PCB and components given away free with the November and December 1986 issues of ETI.

## SPECIAL OFFER!!

### BIO-FEEDBACK PARTS SET

To order by post, please send the order form (or copy) with your remittance to: ASP Readers Services (RO ET4/7), 9 Hall Road, Maylands Wood Estate, Hemel Hempstead, Herts. Please make cheques payable to ASP Ltd.

Phone ACCESS or VISA only: 0442 211882

Order Code RO ET7. Please supply .....  
Bio-feedback complete sets at £14.55

Order Code RO ET4. Please supply .....  
Bio-feedback expansion sets \* at £13.55

Name .....

Address .....

Or, I authorise you to debit my

ACCESS/BARCLAYCARD No. ....

of the sum of £ ..... Signed .....

Please allow up to 28 days for delivery.

# SNUBBER NETWORKS

Paul Chappell makes sure his triacs go on and off on time.

Many circuits in recent issues of ETI have made use of triacs to control mains powered loads. Almost without exception these have included an innocent looking capacitor and resistor across the triac — a snubber network. The action of these components is not quite as simple as it looks. It would be worthwhile to take a close look at snubbers, beginning with some basic triac theory.

A triac can be turned on in several different ways. Applying a suitable current to the gate will do the trick, of course. Exceeding the blocking voltage will also turn it on. In fact, it is quite difficult to destroy a triac by excessive voltage since it will just begin normal conduction and not enter some destructive breakdown mode as other semiconductors often do.

A third method is to cause a sudden change of voltage across the triac. If the rate of change of voltage exceeds a critical value, the triac will turn on regardless of the fact that the voltage may be well below its rated blocking voltage ( $V_{DRM}$ ).

The last two ways of triggering a triac are, generally speaking, a nuisance, and the purpose of the snubber is to prevent the triac being inadvertently turned on by them. To see why it might be so take a look at Fig. 1(a). The triac is driving an inductive load, represented by the inductor and resistor in the box. The control circuit provides current to the triac's gate to turn it on, and as usual the turn off relies on the current through the triac falling to zero. (Strictly speaking, the current must fall below the triac's holding current, which may be 50mA or so for a small device). Figure 1(b) shows the voltage across the triac and load — the mains voltage. Figure 1(c) is the current through the triac which lags behind the mains voltage because of the inductive component of the load.

At point A, suppose that the control circuit removes the gate current from the triac in the hope that it will turn off the next time the current falls to

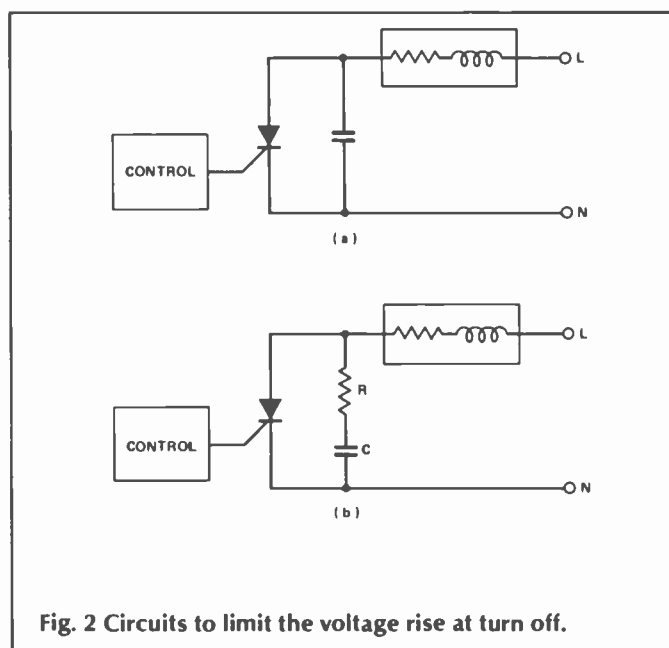


Fig. 2 Circuits to limit the voltage rise at turn off.

zero. At point B this is exactly what happens. However, because of the voltage present across the circuit at this time, the voltage across the triac rises very rapidly, (Fig. 1(c)) causing it to turn straight back on again! At point C, the same thing happens again, with the polarity reversed, and so it continues. The triac will never turn off.

## Snubbing

Our first instinct may be to put a capacitor across the triac to prevent the sudden rise in voltage, as shown in Fig. 2(a). This won't do at all. Suppose the triac happens to turn on when the capacitor is charged to the peak mains voltage. It will be storing a considerable amount of energy which the triac will be expected to get rid of. This is an obvious point, but a fact worth noting is that at turn-on the surge current a triac can handle is very much less than the value shown in the data sheets. This has been the cause of many puzzling failures in circuits apparently designed 'by the book'.

With a resistor in series with the capacitor to limit the surge current (it also has another purpose which we'll come to later) we have the standard snubber shown in Fig. 2(b).

Surely we can relax now. After all, everybody uses that circuit and encapsulated snubbers are readily available. Well, that's OK up to a point. Unfortunately the standard values (100n in series with 100R) do not always work. If we are to be sure of finding the correct values for every eventuality, we must look a little more closely at the effect of the snubber.

At the time the triac turns off, the snubber

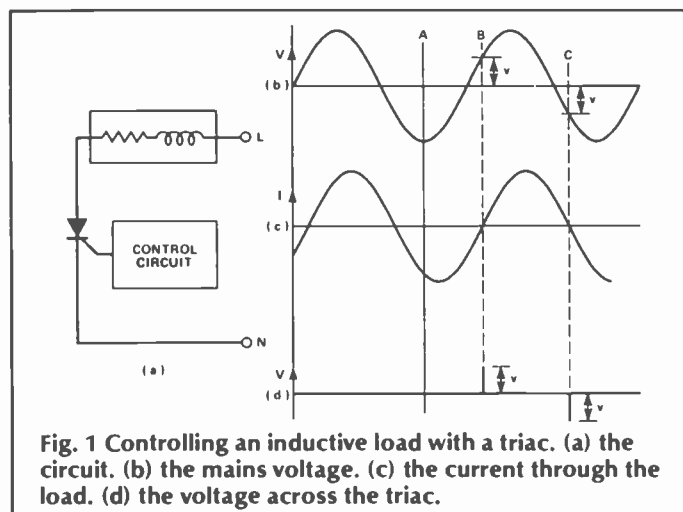


Fig. 1 Controlling an inductive load with a triac. (a) the circuit. (b) the mains voltage. (c) the current through the load. (d) the voltage across the triac.

capacitor will be completely discharged (ignoring the small on-state voltage of the triac), the inductor current will be zero (ignoring the small holding current of the triac) and the snubber and load will have a voltage  $v$  across it (Fig. 1). In this condition the combination of the load and snubber will act like an RLC circuit with a sudden voltage step applied to it.

The exact behaviour will depend on the component values but the basic tendency of the circuit is to oscillate, as shown in Fig. 3(a). If the load inductance is large and the series resistance small, the voltage  $v$  across the triac at turn off will be close to the mains peak voltage. The first cycle of oscillation will approach  $2v$  at its peak — almost twice the peak mains voltage! Clearly a triac with a  $V_{DRM}$  of 400V will turn on again long before the voltage reaches its peak. It seems that as fast as we cure one problem, another one crops up.

Fortunately, it is possible to prevent the circuit from oscillating and thereby avoid the need for a very high voltage triac (although it's interesting to note that most industry standard triacs for mains use are rated at 600V!) Increasing the value of  $C$  reduces the initial rate of rise of voltage across the triac (which is what we set out to do in the first place) and also damps the oscillations, as shown in Fig. 3(b). Increasing the snubber resistor value damps the oscillations too, but unfortunately it increases the rate of change of voltage across the triac.

Somehow, the two values must be balanced so that the initial overshoot is kept to a value below the triac's  $V_{DRM}$  and the rate of change of voltage is also kept low. It seems a safe way to do this is to increase the value of  $C$ , which has all the desirable effects and none of the undesirable ones. But there are problems.

As you might expect, the problems with the usual snubber components arise when the load has a particularly high inductance and low resistance — a powerful solenoid or heavy duty contactor, for example. Inductances of 1H are not uncommon, and a friend recently ran into difficulties when trying to switch loads of 10H!

With inductances such as these, it is possible to find the load and snubber perilously close to resonance at 50Hz. With a 10H load a capacitor of only  $1\mu\text{F}$  would do the trick. Capacitors anywhere near this value would cause all manner of problems. Even with a small enough capacitor to avoid energising the load and to prevent the voltages across the triac from reaching the point where it would turn on, there may still be enough current flowing through the snubber and load to burn out the snubber resistor.

Let's gather the pieces together and see what we can make of them. Having painted rather a black picture of the difficulties, I should say straight away that most loads will not cause any problems, and can be used with the standard component values. Problem loads are essentially those with a low resistance, and since the current will then be limited by the inductance, they will either have a high inductance or will run at a very high current. These need special attention if they are to behave themselves properly.

The general principle is that loads with low resistance and an inductance well below 1H will probably benefit from a capacitor greater than 100n to reduce the rate of voltage rise to an acceptable level.

High inductance loads require a reduced value of  $C$ . The appropriate value of  $R$  to give sufficient damping can then be calculated from the formula given below. Unfortunately, there is no formula into which numbers can be plugged to churn out suitable  $R$  and  $C$  values for any load, but with an understanding of

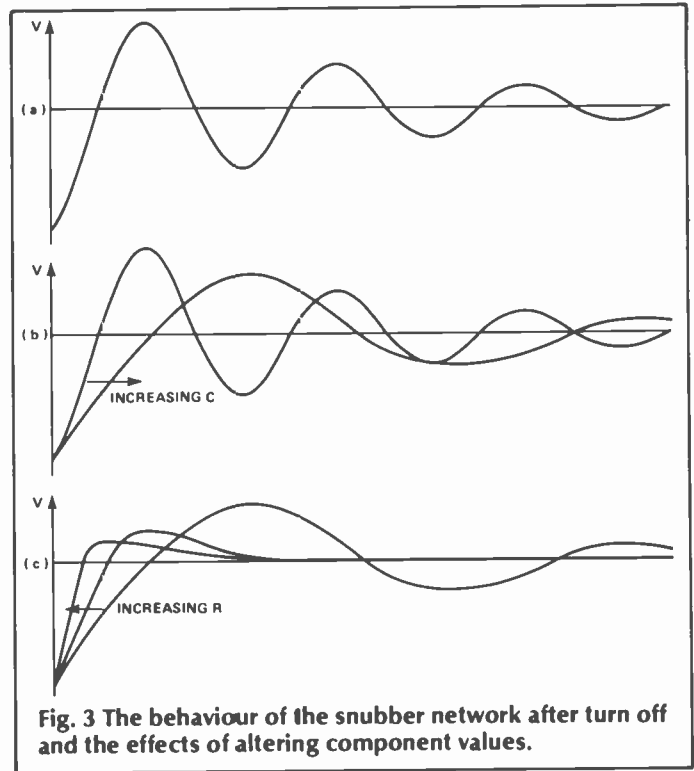


Fig. 3 The behaviour of the snubber network after turn off and the effects of altering component values.

the effects of component changes and a few 'rule of thumb' calculations you can find suitable values without difficulty.

The upper limit for the value of  $C$  is set by the need to avoid excessive current flowing through the snubber and load at mains frequency. A reasonable rule of thumb is to calculate the value of  $C$  needed for resonance at 50Hz then divide by 20 to give the highest value that should be used. For a 10H load,  $C$  should be 50n or below, for 1H it should be below 500n, and so on. The lowest value is determined by the rate of change of voltage the triac will stand. On the data sheet you will usually find this described as 'critical  $\frac{dv}{dt}$ ' and expressed in volts per microsecond. A typical value for a small triac is  $100\text{V}/\mu\text{s}$ . To find the smallest useable value of  $C$ , calculate:

$$C \text{ (in pF)} = \frac{v^2}{\left(\frac{dv}{dt}\right)^2 \times L}$$

where  $\frac{dv}{dt}$  is the critical value in volts per microsecond from the data sheet,  $L$  is the inductance of the load and  $v$  is the voltage across the circuit at the time the triac turns off. If you can't measure  $L$ , estimate it on the low side to be safe. For  $v$  you can use the peak voltage of the mains. This is the absolute worst case and would be the voltage at turn off if the load was a pure inductance.

Having calculated the maximum and minimum values for  $C$ , choose a suitable value somewhere in the middle. Now you can calculate the value of  $R$  needed for critical damping:

$$R = 2 \sqrt{\frac{L}{C} - R_L}$$

where  $R_L$  is the resistance of the load.

If the value you get is less than 30 ohms, use a 33R resistor to avoid turn-on current problems. If greater, add 50% to the answer you get, and use this value for  $R$  so that the circuit is over-damped.

These calculations should cope with just about any problem case, and your triacs should never fail to turn off again!

# CIRCUITS ON THE SMALL SCREEN

Gareth Connor puts his BBC micro to work with four software packages for circuit and PCB design.

For some years computer aided PCB design has been available to industry, but due to the high cost it has remained well out of the reach of hobbyists and small companies. A 1983 PCB design station would not give much change out of £50,000. Its 1986 equivalent running on an IBM PC (or compatible) costs about £10,000.

However, the state of the art is such that even home computer set-ups with £1,000 worth of BBC micro, disk drive and printer can produce professional results.

Each of these software packages has been designed for a particular application. Although they are generally aimed at electronics, useage is limited only by the ingenuity of the user.

**Diagram.** £25 +VAT  
Pineapple Software,  
39 Brownlea Gardens, Ilford,  
IG3 9NL.  
Tel: 01-599 1476

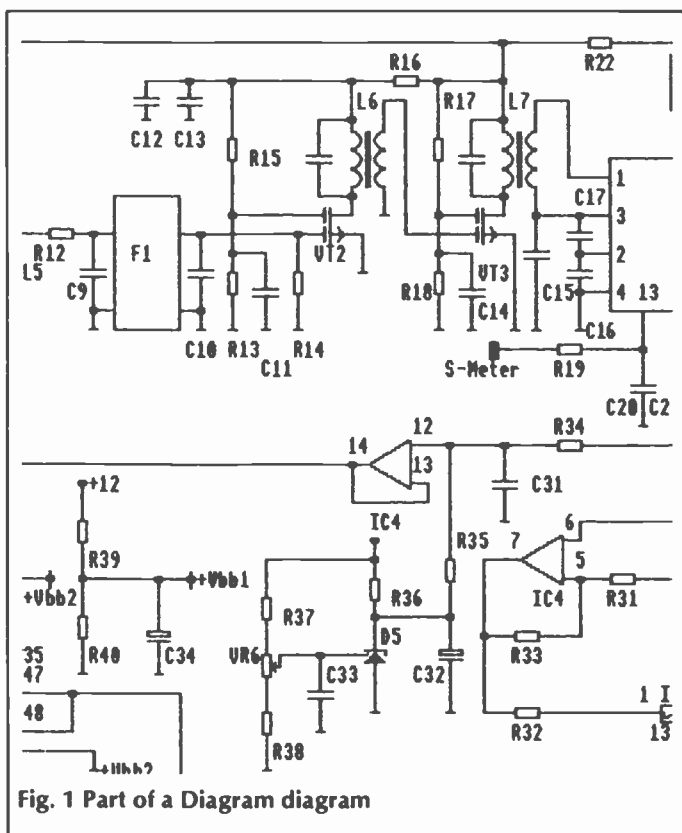


Fig. 1 Part of a Diagram diagram

This program is written for the BBC micro equipped with a disk drive. It is for the creation, storage and printing of any kind of diagram containing large amounts of information in symbolic and textual form. Although only a circuit diagram and a PCB are discussed here, the program could even be used to write sheet music!

Pineapple offers an upgrade service for all registered users to take account of changes to the software. Custom modification is also offered... at a price.

With a blank 80 track disk, the maximum size of a diagram is 39 screens all in mode 0 (the BBCmicro's high resolution mode). If a disk with other files is used, space is reduced to 34 screens (for 40 track disks it's 19 screens and 14 screens respectively). The user can reduce the drawing size (the number of screens used) to accomodate more than one diagram on a disk.

A drawing is created or edited a screenful at a time. A set of user-defined symbols appears at the bottom of the screen. A symbol is selected with two function keys, moved into position with the cursor keys and then 'fixed' with RETURN.

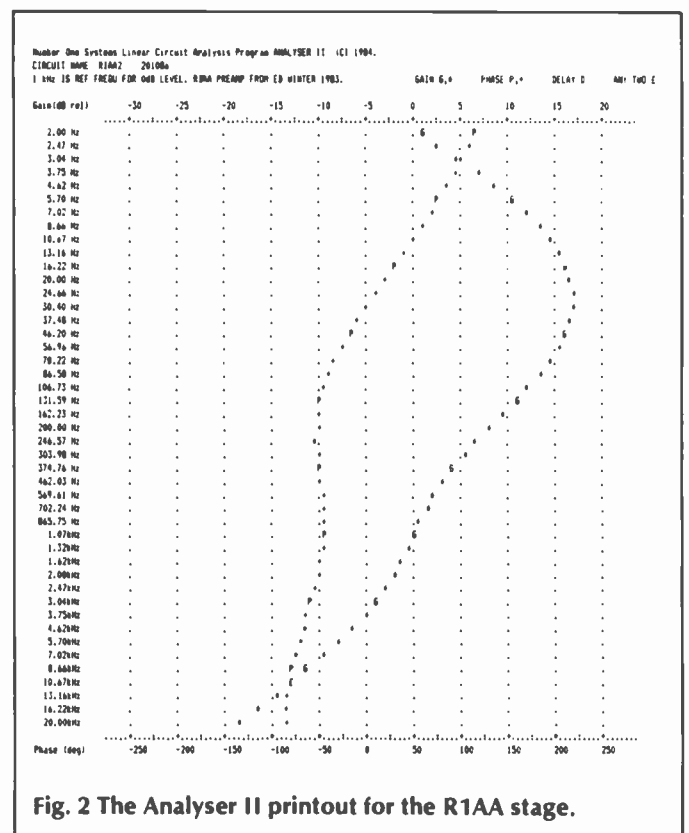


Fig. 2 The Analyser II printout for the R1AA stage.

What distinguishes Diagram from other drawing packages is that symbols can only be placed in discrete grid positions.

There are 16 symbols per set and three sets are provided by Pineapple. Even lines are made up of discrete symbols.

Each symbol consists of up to four by three BBCmicro user-definable characters. The symbols are defined in another section of the program which blows up a symbol to about eight times normal size for editing pixel by pixel. This allows neat, accurate and detailed symbols to be designed. Up to 128 characters can be held in the micro's memory, distributed among the symbols as required by the user.

Whole areas of the screen can be moved, copied or deleted. The copy function will be particularly useful for repetitive circuits. Each screenful of a diagram can then be saved to disk.

Real-time scrolling across the drawing frame is one method used to move around the diagram. If a particular item is required to be located, its reference name can be typed in (say, IC5) and the diagram will then be drawn with IC5 at the centre of the screen.

To familiarise oneself with the system there are two sample drawings, a circuit and a PCB layout. I started by loading the circuit and my initial impression was 'Wow! Just like my professional circuit capture software at work.'

Printing is on a standard dot matrix printer with single or double strike. The results are very impressive — quite suitable for most amateur, and even some professional applications.

For circuit diagrams it's hard to fault this software. If, like me, you tend to misplace or mess up drawings this is the ideal solution. It is a shame it cannot drive a plotter, but reasonably priced at just under £29, anyone wanting plotter drive capability is asking to have his cake and eat it — twice!

**Analyser II. £130 +VAT**  
 Number One Systems,  
 9a Crown Street, St. Ives,  
 Cambs., PE17 4EB.  
 Tel: (0480) 61778

Analyser II is a program for analogue circuit analysis and runs on the BBC B, B+ and Master. There is even a version for IBM PC compatibles.

Analyser II caters for circuits with up to 27 nodes (30 under certain circumstances), and 100 components. Analysis of Input impedance, output impedance, gain (frequency response), group delay and phase are possible. Results are presented in tabular and graphic form and can be printed out. In auto run mode, the computer and printer can be left to do the job while you do other things — a useful time saver. Resistors, capacitors, inductors, transformers, op-amps, bipolar and field effect transistors can all be analysed.

Each of the three semiconductor types has a library of six devices whose parameters can be user defined and the definitions stored on disk.

After parameter editing the main program starts with a menu of nine options. 'Start a new circuit' prompts for a circuit name which becomes the file name on disk. Component values can now be entered. A 4,700 ohm resistor can be entered as 4k7, 4K7, 4700, 4.7E3, 0.0047M or M0047. After entry, the values are returned for checking in exponential form, so it is important you know and fully realise the meaning of E!

Analysis can now begin and the system asks for the number of steps (less than 46) at log or linear intervals,

start frequency and end frequency. The start default is 1Hz, the end default is 1MHz. Higher and lower frequencies can be specified. A second five part gain menu is offered: dB absolute, dB relative, linear absolute, linear relative, real and imaginary. When analysing impedance, gain is replaced by  $Z_{in}$  or  $Z_{out}$ .

The results may be printed and a comment (for identification and reference) can be added to appear on the graph. Typing RETURN to any prompt will re-use the previous entry.

An automatic run allows the results to be calculated and a graph to be printed without the system being attended to. The graph plotter utility is sophisticated and scaling calculations are done automatically to create sensible results.

Several examples are given which can be modified to show different results. These are useful for gaining familiarity and confidence with the program. The circuit I tested was a phono pre-amplifier from the February 1982 issue of ETI. After sorting out my E's I was able to get results that show the chosen component values conform very closely to the RIAA curve and prove Analysers II knows its job.

For anyone involved in analogue circuit design from AF to RF this is a very useful tool for proving circuits before going on to hardware prototyping. It is also a sight cheaper than a spectrum analyser and a storage 'scope! The number of nodes and components should prove more than adequate for most applications.

### PCB Plotting. £20

Vinderen Associates, PO Box 130,  
 Belfast, BT9 6NB.

From the start my experience with this package has been one of frustration. I agree with the opening to the introduction: 'This program is aimed at the experimenter who needs a simple aid to develop small PCB layouts.' The instruction leaflet says enough to enable a

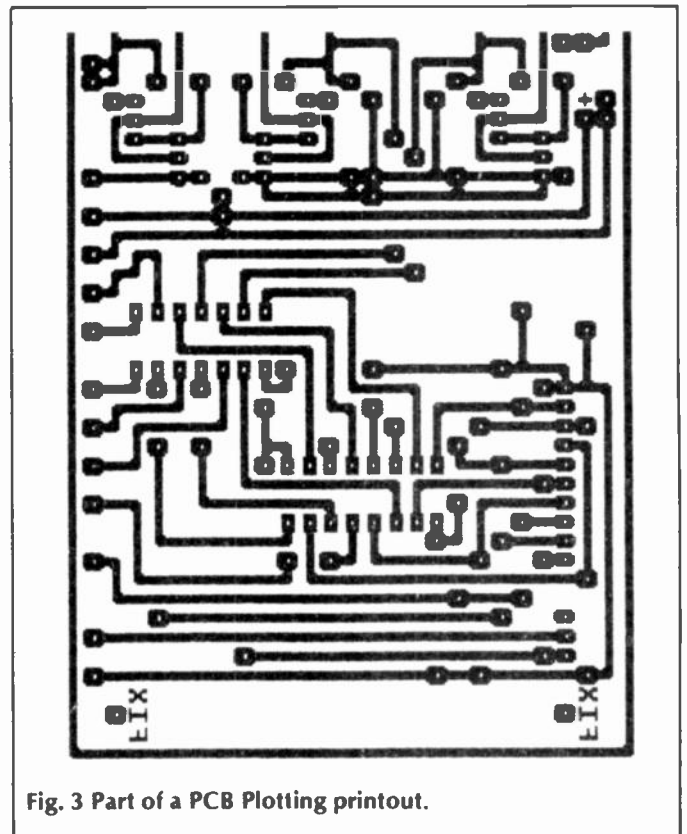


Fig. 3 Part of a PCB Plotting printout.

PCB to be laid out and a component overlay to be created, but is lacking in detailed information on obtaining a printout on a dot matrix printer.

However, there are two very important points in this program's favour. It has plotter drive capability and the tracks can be swapped from side to side of a double-sided board.

The photocopy of the '6809 Mini' board supplied with the package shows the program is capable of a very good finish when used with a plotter. Vinderen advise the Watford Electronics 'Dumpout' ROM to be used for dot matrix printouts. I duly obtained one of these. It is an excellent piece of software but I was faced with a detailed manual and no idea of where to start. It would be to Vinderen's advantage to include a guide to the use of Dumpout for this particular application.

The component overlay cannot be superimposed on the track layout, which makes following a circuit while tracking difficult. The limit of 40 'free' pads that can be placed anywhere is also rather restrictive.

From the educational side, say introducing students to CAD and its application in PCB layout, this program makes a useful guide. Experimenters with time on their hands and who are not very neat with drafting pens or PCB transfers will also find this a good package.

However, for serious layouts or quick turn-around I must give it the thumbs-down. Vinderen has the basis of a good, reasonably priced program, but it is lacking in detailed guidance.

**PCB. £85 +VAT**  
**Pineapple Software,**  
**39 Brownlea Gardens,**  
**Ilford, IG3 9NL**  
**Tel: 01-599 1476**

Like the other programs in this review, PCB requires a BBC micro with a disk drive. However, the software is on ROM. This frees large amounts of memory for the storage of working data. An example PCB is supplied on the disk and both 40 and 80 track formats are catered for.

As with Diagram, Pineapple offers an update service to all registered PCB users. Further improvements are being worked on all the time so this is worthwhile.

The largest size of PCB accommodated is 8.0in x 5.6in (full size). The whole PCB fits onto the screen. If larger boards are required, they can be designed in sections and joined after printing. Unfortunately no scrolling arrangement, as used in Diagram, is provided. A board can contain up to 500 components and 500 ASCII strings.

Printout is on a dot matrix printer and operates in a quad density, three-pass mode. Resolution is about six times that of the screen display. Printouts can be scaled at 1:1 or 2:1. At both scales diagonals are smooth and where tracks pass between IC pads suitable clearance is automatically ensured. The component layout can be printed at 1:1 or 2:1, so can be used for the making of screen printed component labels for commercial applications. However, when this is done a little touching-up is required for a perfect finish.

A sample PCB is provided on a write-protected disk for experimentation. My one complaint about the presentation is that no instructions were given to copy the disk so as not to over-write anything useful. This solved, I proceeded to explore what is a really good and useful program.

The set of components provided is basic, but very flexible. The basic 14 pin IC can be varied in size, both in pin count and pitch between rows, so any size of IC can be created. The same applies to the resistor, which is rep-

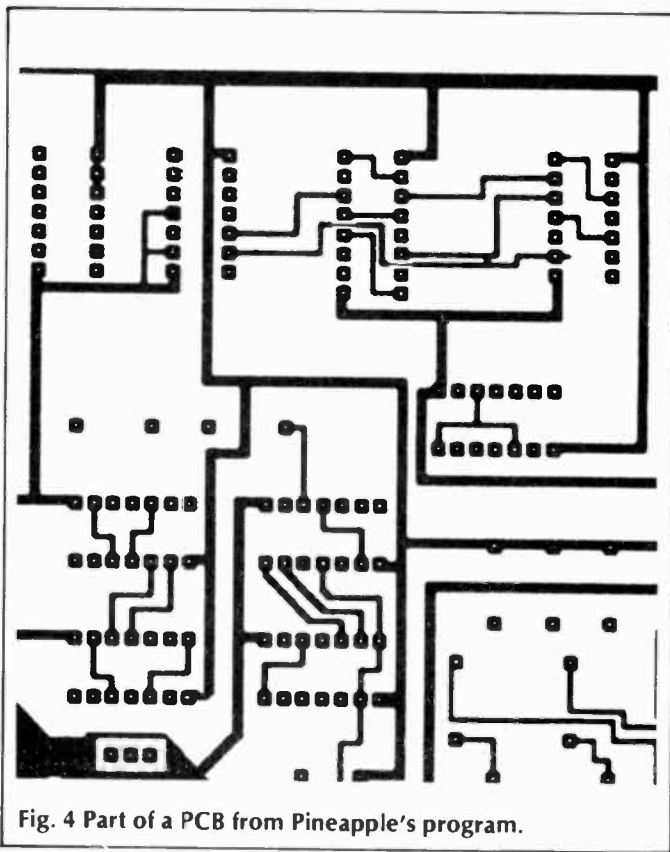


Fig. 4 Part of a PCB from Pineapple's program.

resented by a box with two legs. It can, of course, be used to represent any two leg component and its ASCII label changed to define it as a capacitor, resistor, link or whatever.

Transistors and other circular components must be constructed by the user with the circle drawing routine. Perhaps a sign of the times that the chip is king! Components such as connectors consisting of rows of pads can also be produced very easily by changing the 'size' of a single pad.

The component and solder sides of a double-sided board can be displayed separately or together. Superimposition of the component layout on the track layout is great for getting the whole picture but naturally a bit crowded.

To delete incorrect tracks a flood fill in the background colour is used. For this the cursor must be accurately positioned on the track — not an easy task. Ground planes and other areas of copper are produced in the same way, using a foreground colour.

An area can be defined for printing, deleting or copying. Screen memory is used and this makes copying virtually instantaneous.

To really appreciate this software it must be tried. I had never seriously considered using a BBC micro for quality PCB design until now. As Pineapple admit there is room for improvement, but the present results are good and accurate. I printed at 1:1 and 2:1 and inspected the results on a grid. Across the printer carriage accuracy was almost perfect. Lengthways, both scales showed some slight creep, but not enough to cause worry for most users.

Pineapple's PCB is highly recommended and good value for money at around £100. It compares well with software that costs ten times as much. The results are professionally acceptable and this package will be at home in a small company as well as with hobbyists. Pineapple is working on auto-routing of tracks at the moment. When that's complete the BBC micro will be hard to beat for the electronics hobbyist.

**ETI**

ETI MARCH 1987

# PINEAPPLE SOFTWARE

Programs for the BBC models 'B' with disc drive with FREE updating service on all software

## DIAGRAM

Still the only drawing program available for the BBC micro which gives you the ability to draw really large diagrams and scroll them smoothly around the screen stopping to edit them at any time if required.

Pineapple's unique method of storing the diagram information on disc means that the size of diagrams is limited only by the free space on disc, and not the amount of computer memory you have available. (A blank 80 track disc will allow up to 39 mode 0 screens of diagram).

The superb print routines supplied with the program enable large areas of the diagram to be printed in a single print run in a number of different sizes and rotated through 90 deg. if required. Full use can also be made of printers which have a wider than normal carriage available.

The program is fully compatible with the Marconi Tracker ball described below.

PLEASE STATE 40 or 80 TRACK DISC & WHETHER STANDARD BBC or MASTER VERSION IS REQUIRED

PRICE £25.00 + VAT

## DIAGRAM UTILITIES

A suite of six utility programs which add additional features to the 'Diagram' drawing program. The utilities include the saving and loading of areas of diagram to and from disc. The ability to display the whole of your large diagram on the screen at one time (in either 4\*4 or 8\*8 screen format). The addition of borders and screen indents to diagrams, and the ability to shift a whole diagram in any direction.

PRICE £10.00 + VAT

## MARCONI TRACKER BALL

This high quality device comes with it's own Icon Artmaster drawing program and utilities to enable it to be used in place of keyboard keys, joysticks, or with your own programs.

PRICE £60.00 + VAT p&p £1.75

PRICE INCLUDING 'DIAGRAM' SOFTWARE £79.00 + VAT p&p £1.75

## TRACKER BALL for MASTER series

The Pointer ROM is supplied instead of the Icon Artmaster disc and enables the Tracker ball to work directly with the MASTER series computers. (e.g. to use with TIMPAINT etc.). Prices are the same as for the standard tracker ball.

## POINTER

The Pointer Rom is available separately for people already owning tracker balls, and comes with instructions for use with the MASTER computer.

PRICE £12.50 + VAT

## PCB

This new release from Pineapple is a printed circuit board draughting aid which is aimed at producing complex double sided PCB's very rapidly using a standard BBC micro and any FX compatible dot-matrix printer.

The program is supplied on EPROM and will run with any 32k BBC micro (including Master series). Also supplied is a disc containing a sample PCB layout to demonstrate the programs features.

By using an EPROM for the program code the maximum amount of RAM is available for storing component location and ASCII identification files etc. (Up to 500 components and 500 ASCII component descriptions may be stored for a given layout). There is no limit to the number of tracks for a given PCB, although the maximum size of board is restricted to 8" x 56".

Using a mode 1 screen, tracks on the top side of the board are shown in red, while those on the underside are blue. Each side of the board may be shown individually or superimposed. A component placement screen allows component outlines to be drawn for silk screen purposes and component numbers entered on this screen may be displayed during track routing to aid identification of roundels.

The print routines allow separate printouts of each side of the PCB in a very accurate expanded definition 1:1 or 2:1 scale, enabling direct contact printing to be used on resist covered copper clad board.

This program has too many superb features to describe adequately here, so please write or phone for more information and sample printouts.

PRICE £85.00 + VAT

## CONVERTER LEADS

Converter leads to enable the Trackerball to run mouse software and the mouse to run trackerball software (inc. DIAGRAM). Please state which way round when ordering.

PRICE £8.00 + VAT

## MICROSPICE

A new addition to our range of engineering software. Microspice is a very powerful DC and AC analogue circuit simulator package for any model BBC computer.

As well as all the usual facilities available with this type of program, non-linear effects, small signal, noise measurements and sweeps may be performed. Component values may be swept, allowing component tolerances to be investigated as well as thermal performance etc. Comprehensive transistor modelling is incorporated using a 20 parameter Ebers Moll description. The program is supplied on disc with a very comprehensive 49 page manual.

Please write or phone for more information

PRICE £99.00 + VAT P&P FREE

ALL ORDERS SENT BY RETURN OF POST

39 Brownlea Gardens, Seven Kings, Ilford, Essex IG3 9NL. ☎ Tel: 01-599 1476

## PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT £19.95

- ★ Noise Reduction System
- ★ Auto Stop
- ★ Tape Counter
- ★ Switchable Eq
- ★ Independent Level Controls
- ★ Twin VU Meter
- ★ Wow & Flutter 0.1%
- ★ Record/Playback I.C. with Electronic Switching
- ★ Fully variable recording bias for accurate matching of all tapes, Metal, Chrome, etc.

Kit includes transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply the solder and hook-up wire. Complete with case. As featured in P.E. reprint 50p. Free with kit.



## 125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications — disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. Supplied with all parts, circuit diagram & instructions.

AMP MODULE KIT £12.00 + £1.15 p+p.

AMP MODULE BUILT £17.50 + £1.15 p+p.

ACCESSORIES: Stereo mains power supply w/transformer — £12.50 + £2.00 p&p. SPECIFICATIONS: Max output power (RMS): 125W. Loads: 4 — 16 ohms. Frequency response measured @ 100 watts: 25Hz — 20kHz. Sensitivity for 100 watts: 400mV @ 47K. Dimensions: 205 x 90 and 190 x 36mm.

Built and ready-to-use version with all accessories including power supply and case £42.50 + £2.00 p&p.

## VHF STEREO TUNER KIT — £8.95

Easy to build 3-band stereo AM/FM tuner kit designed in conjunction with PE. For ease of construction and alignment it incorporates 3 Mullard modules and an I.C. IF. System. FEATURES: VHF, MW, LW Bands, Interstation muting and AFC on VHF. Tuning Meter. Two back printed PCBs. Ready made chassis and scale. Aerial: AM — ferrite rod, FM — 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to strict P.E. specification. Front scale size: 10 1/2 x 2 1/2" approx. Complete with diagram and instructions.



Mail to: 21 HIGH ST, ACTON W3 6NG. Callers to Acton or 323 EDGWARE RD, LONDON W2. (Open 6 days a week). Please allow 14 days delivery. Payments to RTVC Ltd.



ETI MARCH 1987

## Zenith Electronics

### Kits — Modules — Hardware

YOU KNOW US FOR OUR TRANSMITTER KITS — NOW TAKE A LOOK AT OUR GROWING RANGE OF QUALITY KITS AND READY-BUILT PROJECTS: MODULES AND ELECTRONIC HARDWARE

The following are examples of our proven product designs in kit form:

- ★ Miniature FM Transmitter, 60—145MHz. Kit £6.95; R/Built £8.95.
- ★ 3 Watt FM Transmitter, 80—108MHz. Kit £13.99; R/Built £18.99.
- ★ 10 Channel Variable Speed Running Light; Drives LEDs or mains lamps. Kit £14.97
- ★ 3 Note Electronic Door Chime unit; 9 volt operation, 3 melodious tones; variable frequency. Kit £9.83
- ★ 300 Watt Light Dimmer unit for 240 volt mains lights. Kit £5.95.
- ★ 5 Code Digital Code unit plus Key Pad—select own code; 9 volt. Kit £14.21.
- ★ 5—100 Watt Electronic Loudspeaker Overload Protector, adjustable. Kit £11.11.
- ★ VU Meter 10 LED indicator; —5 to +12dB range. Kit £12.59.
- ★ Automatic light controller; automatically turns on and off lights at pre-set times and triggered by darkness. Kit £25.08.
- ★ Mains Wiring and Metal Detector; complete with case. £11.00
- ★ Digital Clock module; 12—24 hour timing; LED type—£17.49, or LCD type—£22.80.
- ★ Amplifier Power Meter; 10 LED indicator from 0.25—100 Watt Input—9 volt operation. Kit £9.52.
- ★ Light sensitive relay unit; variable sensitivity trigger control; senses light or dark—selectable. Kit £8.45.

ALL KITS CONTAIN FULL INSTRUCTIONS, P.C.B.s AND COMPONENTS.

ALL PRICES INCLUDE VAT AND POSTAGE & PACKING.

OVERSEAS ORDERS—ADD 10% TO ABOVE PRICES.

PLEASE SEND CHEQUE OR POSTAL ORDERS WITH ORDER.



Zenith Electronics, 14 Cortlandt Business Centre, Hailsham, E. Sussex, U.K. BN27 1AE. Tel: 0323 847973/04353 2647

# M&A SERIES FOUR MIXER KIT

Ian Pitt takes a look at an old friend in an (almost) new guise.

It must come as a bit of a surprise to see ETI reviewing a product which has already been on sale for five years. The Series 4, a budget-priced modular mixer with studio-style facilities, is so well established that M&A is starting to make noises about a Series 5 (of which more later). So why review it now?

The answer is contained in that word kit. Until recently, the Series 4 was officially available only in its ready-built form. It was a modular system, allowing purchasers to start with a minimum of channels and add more as finances allowed, but the modules were sold (and charged for) as factory built units.

Now, with the increasing popularity of home studios and the consequent demand for good-quality equipment at rock bottom prices, M&A has moved firmly into the kits market and is aiming to provide a comprehensive service to small studio owners. In addition to supplying kits, individual parts or even just the plans for the Series 4 mixer, the company provides guidance to users who wish to develop their own add-ons or modifications and will advertise such designs in its advertising literature. Parts and service back-up is still available on mixers built from the kits and M&A also supply a range of cheaply-produced but well illustrated guides which introduce the new mixer owner to recording studio techniques, MIDI, and much else.


The mixer itself is assembled from three basic module types and can be built in any configuration up to 50-16-2. It features electronically balanced inputs which are switchable for microphone or line level, LED VU indicators and comprehensive routing and signal path facilities. The individual channel faders are 100mm types and the input and output sockets can either be fitted to the back of the case or provided in the form of a patch bay at one side. M&A supplies ready-built cases or can provide plans so that users can build their own.

The input module features variable input gain, LED indication of peak signal level, a five-band equaliser, four auxiliary signal sends and a stereo pan pot. A channel-cut switch allows the channel to be isolated from the mixing busses and there is also a pre-fade monitor, both of these being equipped with LEDs to remind the user that they have been selected.

The second type of module is the sub-group which takes its feed from one of the mixing busses and provides a line output (to feed a multi-track tape machine) and separate monitor and auxiliary outputs. An LED bargraph display monitors the mixing bus or line input level and can be set to give either peak or VU indication.

The final main module is the recording master unit, one of which is required in every Series 4 mixer. It provides the output buffers for the four auxiliary channels plus the left and right master stereo outputs, a pair of bargraph LED displays and a pair of monitor outputs.

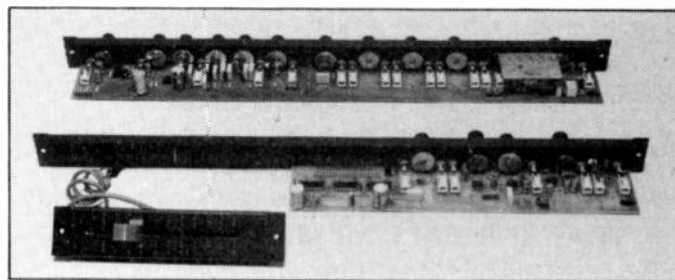In addition to the main modules there are also a number of special types available such as a dual



equaliser and a communications unit, plus blank panels and various other accessories. M&A can also supply a suitable PSU with overload and short-circuit protection which is capable of driving a full complement of Series 4 modules.

## Cue The Review

A sub-group module was chosen for the kit review. As supplied, it included a screen-printed front panel, a separate fader panel already wired, a PCB, a set of instructions with circuit diagram, overlay, etc, and several polythene bags containing the components. The small amount of connecting wire needed was also supplied, leaving the constructor to provide only the solder and the tools.

The components in the kit were of good but not excessively high quality and 741 op-amps were supplied for all the audio stages (the only exception is the microphone stage on the input module where a 4558 dual op-amp is used). Those who want to use higher quality op-amps and are prepared to pay the extra can purchase a kit without the 741s.

The instruction sheets reflect the budget nature of the kit in that they are photocopied and the typeset directions are supplemented by handwritten notes. The 'small is beautiful' approach is also reflected in a rather folksy style of presentation which includes cartoons of Peter Kunzler (owner of M&A) and assorted 'studio types' demonstrating various aspects of the mixer's operation. Thankfully, none of this detracts from the legibility of either the text or the illustrations.

In spite of this overtly 'user friendly' approach, the kit is obviously not aimed at beginners. The instructions recommend a sequence for the insertion of the components and describe the various assembly and connection routines, but the individual components are not identified in any way and there is no mention of the soldering process. In short, the kit is fine for anyone with experience of electronics construction but perhaps not for musicians unless they are very technically-inclined.

My only real complaint about the literature is that the component overlay is not shown against the PCB track pattern. In practice, most component locations were perfectly clear, but once or twice I installed components only to find later that I had used a hole belong-



ing to another component. I spoke to M&A about this and was told that future versions of the kit will probably include a PCB which is screen printed with the component numbers.

These hiccups aside, the kit went together without problems and worked perfectly when tested with a bench power supply and a signal generator. It wasn't practical to make any detailed tests or measurements in this way, and in any case the results obtained from a single module would give little indication of the performance to be expected from a complete mixer.

## Trying Wolf

For the second part of the review I went to the Wolf Studio in Brixton to see a Series 4 mixer in action. The studio was set up about three years ago by Dominique Brethes and featured a 16:16:2 version of the Series 4. Since then a 24-track tape recorder has been installed, an Aces MT24HS, and the mixer has been expanded to suit.

Most of the recordings made at Wolf Studio are of electronic music and the mixer is usually fed via its line inputs from a collection of synthesisers and electronic keyboards. A few channels are set aside for microphone use and patched through to a separate room where they can be used for vocals or to record an acoustic piano. The microphones include a Neumann U87 and several elderly AKG C28s with valve pre-amplifiers. Mindful of all those 741s in the mixer, I asked if noise was a problem. Dominique told me that it had to be taken into account when using the C28s but was not significant with the U87, suggesting that the mixer itself was not particularly noisy.

Another point of possible concern was the quality of the slider faders. The giants of the recording industry often find it necessary to equip their mixers with conductive plastic faders costing £30-40 or more each, whereas the Series 4 uses Japanese-made Alps potentiometers which cost barely a tenth of that sum.

In reality, the difference is not as great as might be expected. Alps potentiometers offer a surprisingly high level of performance for their price, as certain ETI writers have pointed out in the past, and while they lack some of the silky feel of top-grade sliders they remain pleasant to use and are very robust. Dominique could not recall a single fader problem during the studio's period of operation, even though the mixer is usually operated solidly for some 7-8 hours a day.

The only parts of the mixer Wolf Studio has had any problems with are the PCB connectors which link each module to the mixing buss. Several of these have become noisy at some time and needed attention. A permanent solution, Dominique suggests, would be to do away with the connectors and solder the ribbon cable directly to each module. In practice, the problem has not been

sufficiently annoying to warrant such a modification.

In this and countless other matters, Dominique is quick to praise the level of support he has received from M&A. Advice on modifications and matching to other equipment has been freely given and there have been no difficulties with spares or servicing, an important consideration where a piece of equipment forms the heart of a commercial operation.

There was no initial recording work underway on the day I visited Wolf Studio so I had to be content with listening to a multitrack recording made some time earlier. The piece, a song with backing tracks compiled entirely on electronic instruments, was destined for commercial release in France and had come to the studio for mix-down. Watching Dominique at work, I asked how much longer he expected to be using the Series 4. It was still a budget mixer however good it might be. Did he hope to move on to something better soon?


He replied by directing my attention back to the music pouring from the studio's monitor system. This was work of good commercial quality, he felt, and the mixer in no way limited his ability to handle such recordings. There might come a time when the studio's requirements outgrew the Series 4, but that point was a long way off. For the foreseeable future he expected to continue using it, with upgrades if necessary to suit changing requirements.

Which brings us to the future of the Series 4 design itself. M&A is now talking about its successor, the Series 5. That too will be a modular design available in kit form, and for obvious reasons the basic format will remain unchanged. New owners will enjoy such benefits as MIDI control facilities and optional automation while existing owners will find the life of their equipment extended and the scope for improvement significantly increased. If M&A have their way, it seems, the Series 4 and its successors are going to be with us for some time.

*Prices: input module with fader assembly, £55.00 in kit form, £75.00 ready built; sub-group module with fader assembly, prices as for input module; master module with fader assembly (specify recording or PA module as required), £98.00 ready built (no kit available); Ultra-low ripple power supply, 15-0-15V 7A, £109.67 ready built (no kit available). Cases with mahogany end panels and padded arm-rest, approximately £7.00 per channel. Full set of Series 4 circuit diagrams, £9.50. All prices include VAT. Other prices on application. K-Tek PO Box 172A, Surbiton, Surrey KT6 6HN, Tel 01-399 3990.*


*Our thanks to Dominique Brethes of Wolf Studio, 8 Homer House, Rushcroft Road, London SW2 1JT, Tel 01-733 8088.*

**ETI**

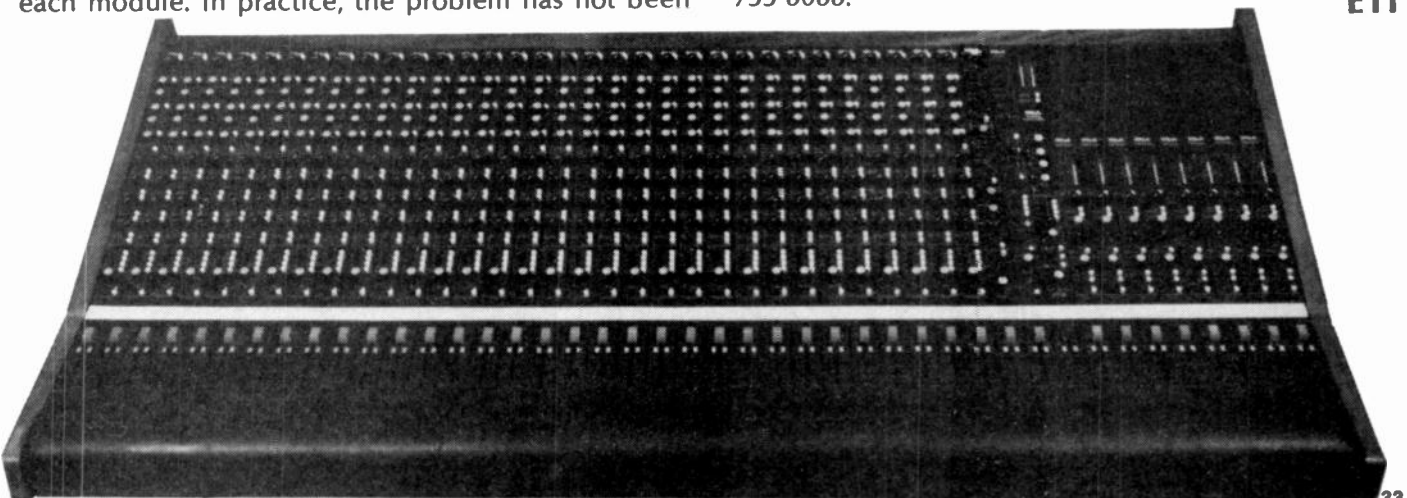
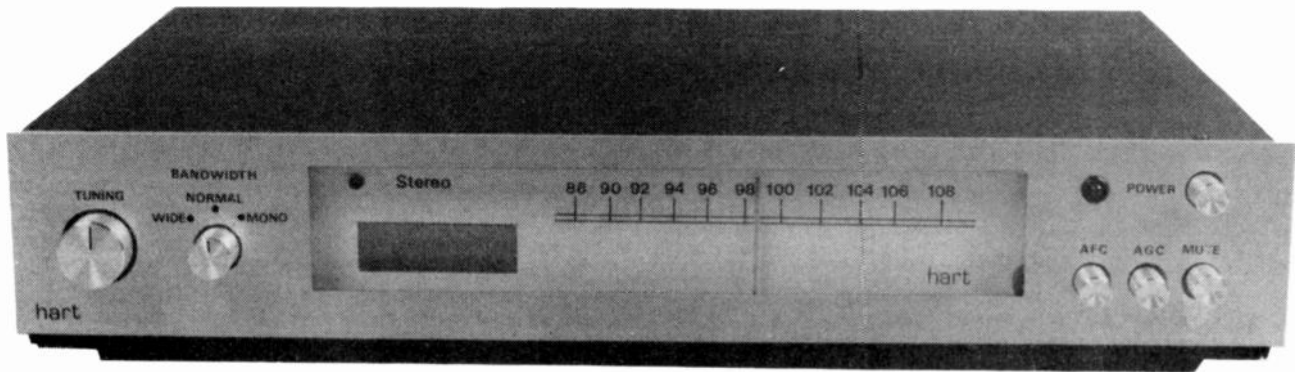
# PLL FM TUNER

John Linsley Hood describes an FM tuner using a phase-locked loop demodulator arrangement, to accompany last month's stereo decoder circuit.



I have long felt that the phase locked loop (PLL) is by far the best way of demodulating an FM signal and I have been both surprised and saddened at the way designers of commercial units have neglected this technique. It is especially curious when one sees the lengths to which they go in order to get a little bit lower distortion, or a slightly higher capture ratio — all benefits which are easily obtained with a PLL.

Most contemporary FM tuners use a demodulator circuit of the type shown in Fig. 1. In this the 10.7MHz IF signal is fed from a wide bandwidth amplitude limited amplifier (A1) to a phase detector, (PD1), for which a second input (reference or quadrature) is derived from an ancillary quadrature coil assembly (L2C3).

This quadrature coil circuit is usually driven from a second output point on the limiting amplifier through a small coupling capacitor, C1, or perhaps through

an inductor having a similar RF impedance, and is tuned to the mid-point of the 10.7MHz tuning range. The idea is that the phase of the reference input at point A will alter relative to the main signal input as the frequency moves up and down, and will cause the phase detector to give a varying voltage output.

The use of a second, inductively-coupled tuned circuit (L1, C2) added to the quadrature coil helps make the phase/frequency relationship of this circuit more linear, and this improved layout is widely used in the better FM receivers.

There are several snags with this quadrature coil arrangement. The principal one is that the phase of the incoming signal is shifted, as a function of frequency, by non-ideal characteristics in the RF or IF tuned circuits or ceramic filters in the preceding amplifier stages. These phase shifts will cause distortions of the audio output signal because

the phase detector cannot distinguish them from actual frequency shifts.

Minimizing these unwanted RF/IF phase shifts is a costly business, which is why tuners with a very low THD figure tend to be very costly.

## The PLL Demodulator

This system (shown in Fig. 2) operates by forcing a voltage controlled oscillator to operate in phase and frequency synchronism with the incoming signal — a condition in which the loop is said to be 'in lock'.

If the output frequency of the VCO has a linear relationship with the input control voltage (and with good design this relationship can be very linear indeed) the VCO control voltage will vary with the incoming frequency. The result is an accurate replica of the variations in the incoming frequency — and inadvertent phase errors in the incoming IF signal will largely be ignored.

To make such a system work, the VCO must be tuned so that its natural oscillation frequency (the frequency at which the filtered DC control signal from the phase detector is at its mean potential) is close in frequency to that of the incoming signal. There must also be sufficient gain in the control loop to make it keep in step as the incoming frequency alters.

There will also be a low-pass filter included in the loop to prevent the VCO from chasing its own tail, and it is essential that this


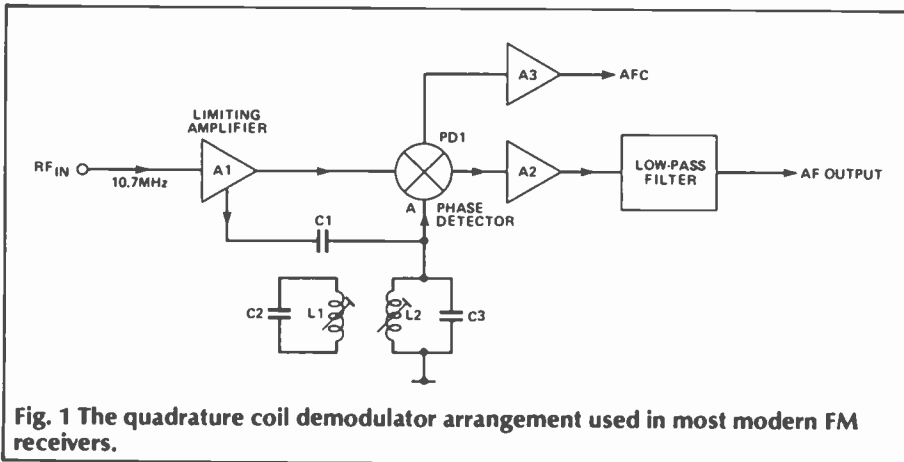
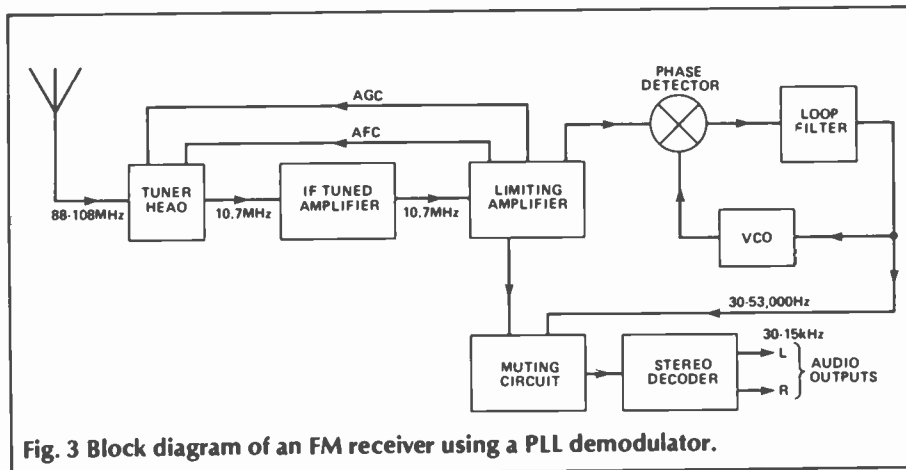


Fig. 1 The quadrature coil demodulator arrangement used in most modern FM receivers.

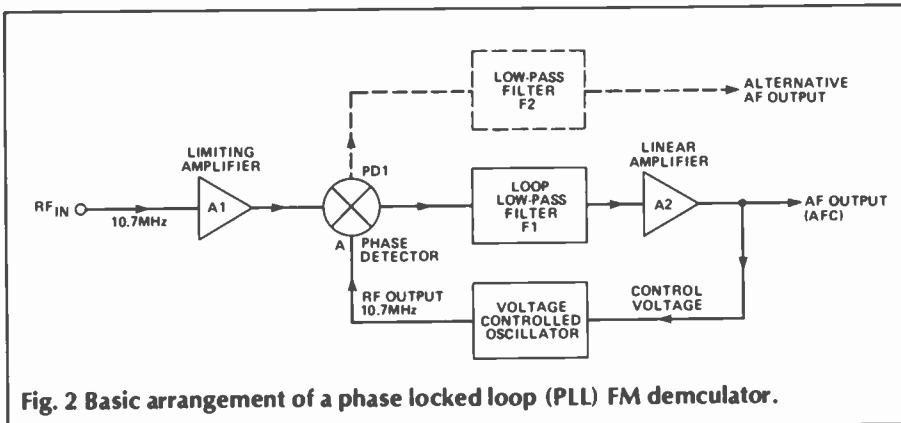

has the correct characteristics to stabilise the loop without restricting its ability to follow fast modulation shifts in the incoming signal frequency. Provided this is done, the control signal fed to the VCO will be an accurate replica of the original signal modulation.

As an alternative, it is possible to take a separate output from the phase detector and give it similar filtration to that of the control loop, thus retaining the quality of the AF signal output but reducing the risk of interfering with the loop operation. This is the layout which I prefer.

Other advantages which the PLL system offers are a very high 'capture ratio' (the ability to reject a slightly weaker interfering signal on the same frequency) and a remarkable ability to extract weak signals from the general background noise. A further useful quality is that the PLL has its own 'selectivity', adjustable by means of the loop gain and quite independent of that of the IF stage. This makes the performance of the receiver (for example, the stereo channel separation) less dependent on the IF stage characteristics, which is useful.

There are, of course, snags — otherwise everybody would use PLLs instead of the technically inferior alternatives. Happily, these

snags can be removed by attention to the design and I will refer to this later.

## The PLL FM Receiver


Apart from the demodulator stage, the circuit layout of a PLL receiver will be very similar to that of more conventional designs, with a form generally as shown in Fig. 3.

If one of the highly-developed modern FM ICs, such as the RCA CA3189, is used for the limiting IF amplifier and phase detector stages, this can also provide automatic gain control (AGC) and frequency control (AFC) signals to the head amplifier. In addition, since the 3089/3189 ICs are by far the most popular among the commercial circuit designers it is possible that the head amplifier unit will have been designed to suit them which saves a lot of work. The major tasks which then remain are to arrange an adequately linear VCO and to marry this to the 3189.

Two general alternatives exist for a VCO circuit which will operate at the required frequency: an LC tuned circuit system, whose frequency can be adjusted by, say, a varicap diode, or some form of multivibrator. The first of these alternatives gives a pure sinewave output and low noise but it is

difficult to get a high degree of linearity since, left to itself, the varicap diode has a highly non-linear capacitance/voltage relationship. This is shown in Fig. 4a.

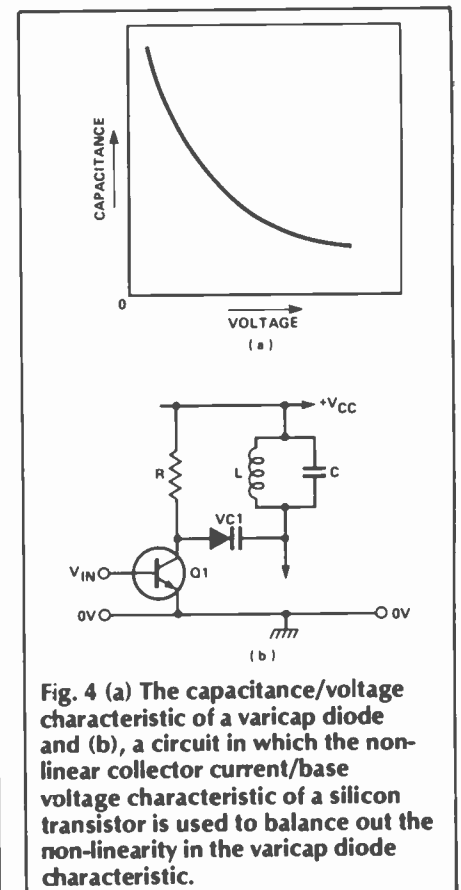On the other hand, although it is possible to design multivibrator systems whose operating frequency can be varied by an input control voltage and which have a high degree of linearity in the relationship between output frequency and input control voltage, such circuits usually have the snag that their frequency will



drift with changes in temperature. This will spoil the distortion performance of the receiver at the moment of switch-on, before things have settled down. Unfortunately, the problem becomes worse at higher frequencies, and at 10.7MHz it can be a major embarrassment.

Happily, a technique exists for linearising the voltage/frequency characteristics of a varicap tuned circuit (Fig. 4b). The curvature in the way in which the collector current of a silicon transistor varies as the base voltage is increased is balanced against the varicap diode voltage/frequency non-linearities, and if the correct value of R is used for the transistor and varicap diode chosen the overall linearity can be very good.

A practical VCO circuit layout is shown in Fig. 5 and the excellent linearity of the voltage/frequency relationship is shown in Fig. 6.

In this circuit Q17 is an input emitter follower which provides the necessary low impedance drive to Q18, and a PNP/NPN pair layout is used for Q17/Q18 to cancel the offset of the base-emitter voltages which would otherwise be affected by ambient temperatures.

Q19 is a conventional grounded-base Colpitts oscillator and the HF output signal is taken from the emitter which is a low impedance point. RV4 is used to set the HF output level.

### The Need For Signal Muting

If the voltage/frequency relationship of the VCO is a linear one, the control voltage will alter linearly with input frequency as I have shown in Fig. 7. However, beyond certain frequency limits above or below the frequency to which the VCO is tuned, the loop will lose lock. The width of this frequency band is known as the lock or capture range.

This illustrates the basic problem of the PLL when used as an FM demodulator. If a frequency modulated signal, as at A, B or C in Fig. 7, is presented to the PLL while it is at the centre of the lock range (position B) all will be well and the incoming signal will be accurately demodulated. However, if the signal is at positions A or C then, as the signal swings up and down in frequency, the loop will jump into and out of lock with quite large swings in the output signal voltage.

This would be heard as loud and unpleasant rasping noises as the receiver was tuned into and away from a station. I suppose this is the principal difficulty which has militated against the use of the PLL in the collective view of the tuner designers.

The solution is to ensure that the loop capture range is wider than the IF bandwidth so that the signal is pretty small by the time the loop is about to lose lock. A good quality 'muting' system can then be used to disconnect the AF output circuit when the signal strength at the loop input falls below some predetermined value.

With this improvement, the behaviour of the PLL receiver from the listener's point of view is quite impeccable with silence in the gaps between clean, low distortion received signals.

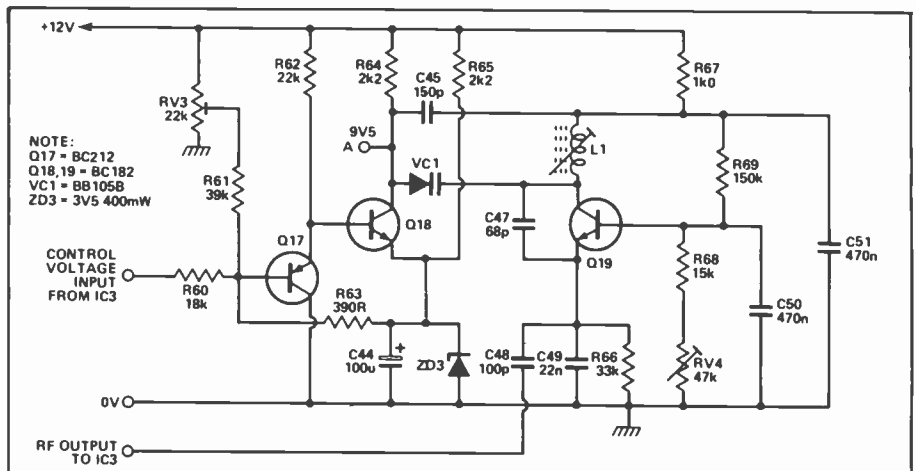


Fig. 5 A practical voltage controlled oscillator circuit using the arrangement of Fig. 4 b to achieve linearity with a varicap diode. Note that the component numbering used here and in Figs. 8, 9, 11 and 12 follows on from the numbering used in last month's stereo decoder circuit.

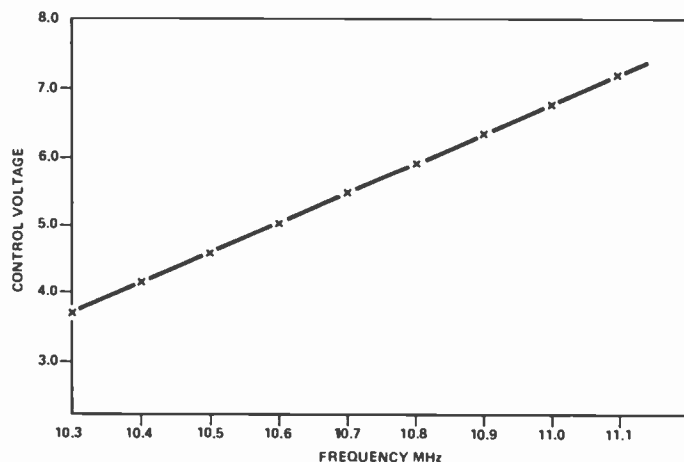


Fig. 6 The control voltage/frequency characteristic of the circuit shown in Fig. 5.

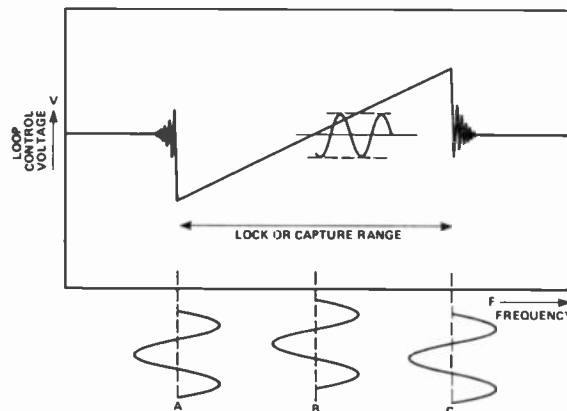


Fig. 7 The control voltage/frequency characteristic is linear only over a certain range and above and below these limits the loop will fail to lock. Signals with a frequency at the limits of the range (A and C) will cause the circuit to swing in and out of lock.

Considering the separate circuit building blocks shown in Fig. 3, I have opted to use a commercially available tuner head unit. There are quite a number of these available, differing in price and specification

but all offering a 10.7MHz IF output.

There is no particular reason why this PLL tuner design should not be built using any head unit available to the constructor.

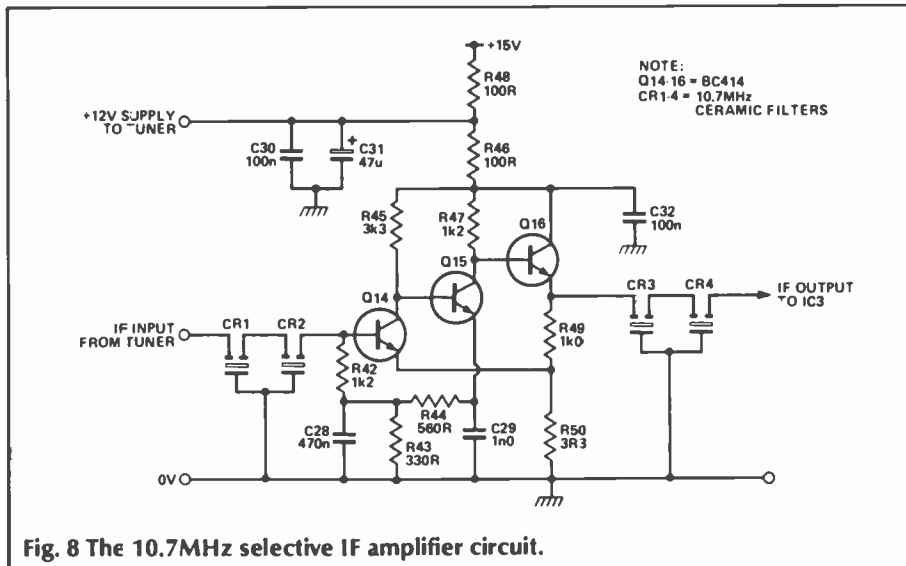


Fig. 8 The 10.7MHz selective IF amplifier circuit.

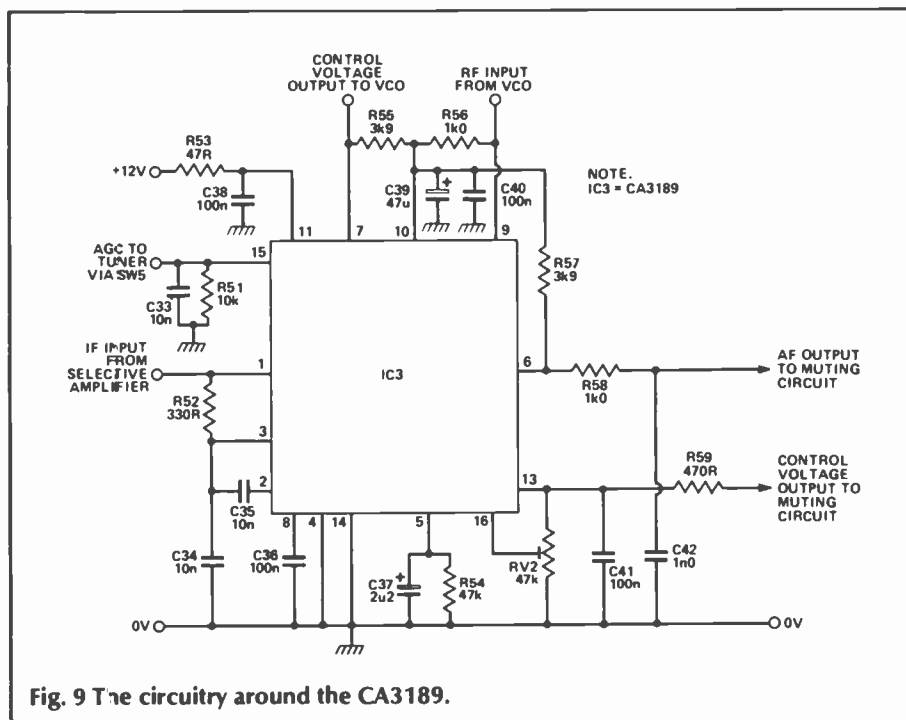


Fig. 9 The circuitry around the CA3189.

However, for the prototype I chose the ALPS FF317U which is a well-designed and sensitive unit, readily available at a reasonable price. This is a variable capacitor tuned unit, avoiding the need to apply thermal compensation to the tuning voltages which would be needed in a varicap tuned unit.

It also has the practical advantage that it is designed to work in harness with the 3189 demodulator IC, so both the AGC and AFC voltages from the IC are suitable for this tuner head. Additionally, as is becoming a fairly common feature with such tuner heads, the IF output impedance is 300 ohms which means it can be directly connected to the input ceramic filter of the tuned IF amplifier.

In order to exploit the high

sensitivity of the PLL, which is helped by the characteristics of the 3189, I have used a high gain, three transistor IF amplifier using two pairs of cascaded 10.7MHz ceramic filters. The complete IF amplifier circuit is shown in Fig. 8 and is based on a wide bandwidth, gain stabilised layout derived from the old valve-type 'ring of three' circuit which has excellent characteristics. Moreover, the performance is not particularly affected by the transistor types used so although I have specified BC414s as a good, modern, low noise type, BC184s would work just as well.

The ceramic 'ladder filters' are a convenient and compact way of obtaining selectivity but they have the disadvantage that they introduce a substantial degree of

attenuation from input to output when compared with a tuned circuit. Typically, a single filter element will lead to a signal loss of 3x. Two, in series, will increase this insertion loss to 5x. If, therefore, two pairs are used, the total signal loss through the filters will be 25x.

The design value for the overall stage gain of the 10.7MHz amplifier of Fig. 8 is 14x, so the stage gain from Q14 to Q16 needs to be 350x. This is set by the feedback resistors R49 and R50. All of the resistors should be reasonably non-inductive, which rules out a wire-wound component for R50.

The tuner head IF output impedance is 300 ohms and since this is the required input/output impedance for the ceramic filters the IF output from the tuner head can be taken directly to CR1.

The circuit connections to the CA 3189 (Fig. 9) are much as recommended by the makers, except where circuit modifications are needed to make it operate within a PLL. There is not space here to discuss in detail the internal circuitry of the 3189, which is an ingenious and carefully designed component. However, in simple terms the input to the limiting amplifier is at pin 1 and the DC bias for this is taken from pin 3. An AGC signal is available from pin 15, which sits at about +6V until the input signal exceeds a value determined by the setting of RV2.

Two audio output points are provided. One is taken from pin 6 and can be controlled by an internal deviation muting circuit, while the other is taken from pin 7 and cannot. I have chosen to use the pin 6 output for the audio signal and that from pin 7 (normally used to operate a centre zero tuning meter and AGC circuitry) as the control voltage output to the PLL.

Since I am using a high quality external muting circuit, I have disabled the muting level control for which pin 5 is provided.

## The Muting Circuit

As I mentioned earlier, the ability to use a phase locked loop system to demodulate an incoming FM signal (as distinct from the ubiquitous PLL circuit used in the stereo decoder) depends entirely on the designer's ability to suppress the nasty noises which would otherwise occur on tuning the receiver into and away from a station.

The method I have used for this


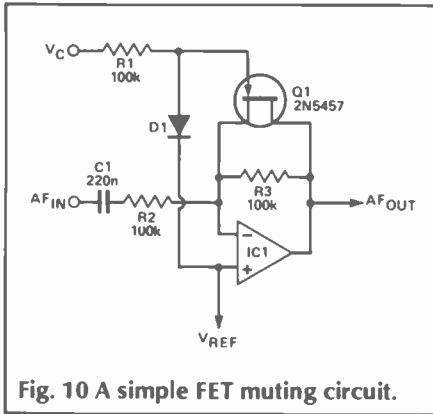


Fig. 10 A simple FET muting circuit.

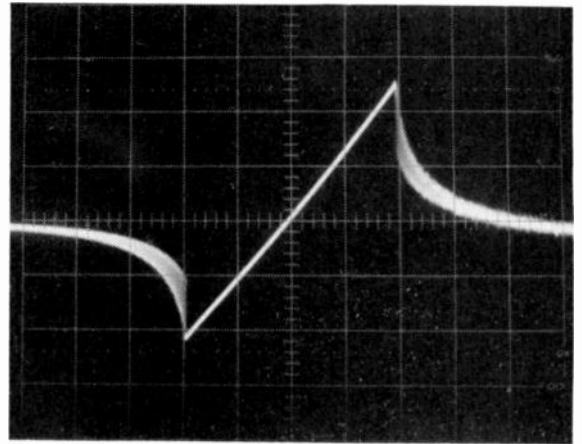Oscillogram showing a linear change of voltage at the audio output of the receiver as an RF input signal is swept in frequency from 95.2 - 95.6MHz. The horizontal scale represents 10kHz/division and the vertical scale is set at 300mV/division.



is shown in simplified form in Fig. 10. A good quality, low distortion op-amp (such as an LF351/3 or a TL071/2) is connected as a unity gain inverting amplifier. I am satisfied that even the most critical audiophile will not fault such an op-amp in unity gain mode. A junction FET (Q1) is then connected across the feedback resistor. When this is conducting the gain of the stage is very nearly zero and any distortion due to the non-linearity of the FET is irrelevant.

If the FET is biased off it becomes an extremely high impedance indeed and, again, there is no significant effect due to its connection across R3. The diode

D1 is included to prevent the FET gate from being biased into conduction, which would disturb the DC output level from the op-amp.

This circuit is incorporated, in practical form, in the muting stage shown in Fig. 11. In this, the output voltage for the signal strength meter from pin 13 of the 3189 (which varies from about 0.8V to between 3 and 4V) is taken to one half of a dual op-amp which converts it to a +14 to +1V swing from noise threshold to signal levels.

Since the TL071/72 does not

include 0V as a permissible input level when run from a single supply line, Q20, D1 and R72 are used as a DC level shifting network. The preset (RV5) is used to set the level at which IC4a output swings from +14 to +1V, to convert the FET (Q21) from its short circuit to its open circuit condition.

The muting circuit can be disabled by SW3, which biases the FET (Q21) into an open circuit state under all signal conditions. The audio output from the tuner is taken from the output of IC4b to the stereo decoder circuit described last month.

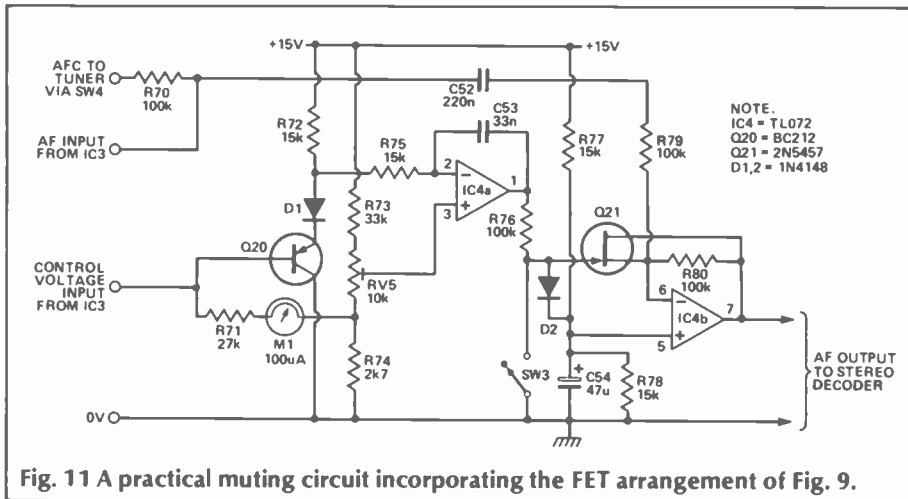


Fig. 11 A practical muting circuit incorporating the FET arrangement of Fig. 9.

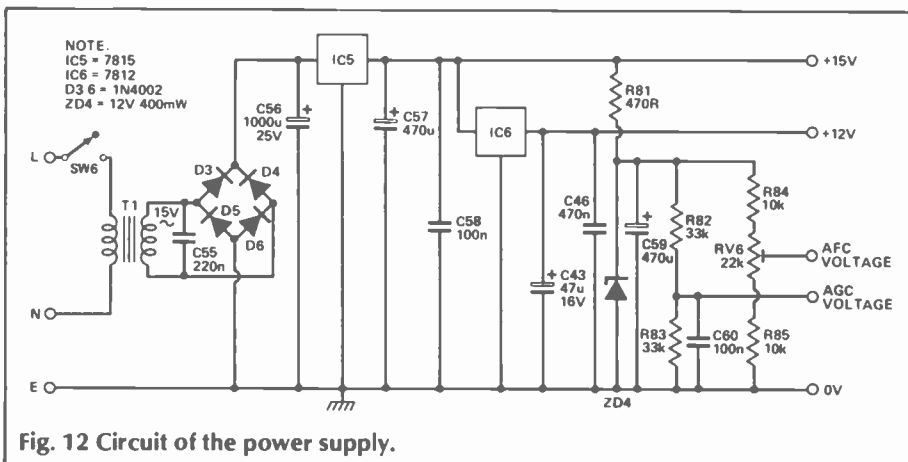


Fig. 12 Circuit of the power supply.

## AFC And AGC Connections

The output voltage at pin 6 of the 3189 normally sits at about 5-6V under no signal conditions and will swing up and down by about  $\pm 1V$  on tuning through a signal. This can be used as an AFC signal to the head but there should be no shift of tuned position when the AFC is switched in. This is achieved by using RV6 (Fig. 12). To preset the same voltage level as that from the 3189.


The AGC control voltage level, taken from pin 15 of the 3189, will normally sit at about 6-8V on no signal. An equivalent potential is set by R43 and R44 for the AGC off setting. The whole tuner circuit is powered by a single +15V supply, but because the VCO is voltage operated, it is essential that the positive line supply voltage to this is held constant. This is done by inserting a standard 12V IC voltage regulator, IC6, between the input +15V supply and the 12V line which feeds the CA3189 and the VCO.

This project will be concluded with a description of the construction and setting up of the complete FM tuner.

ETI

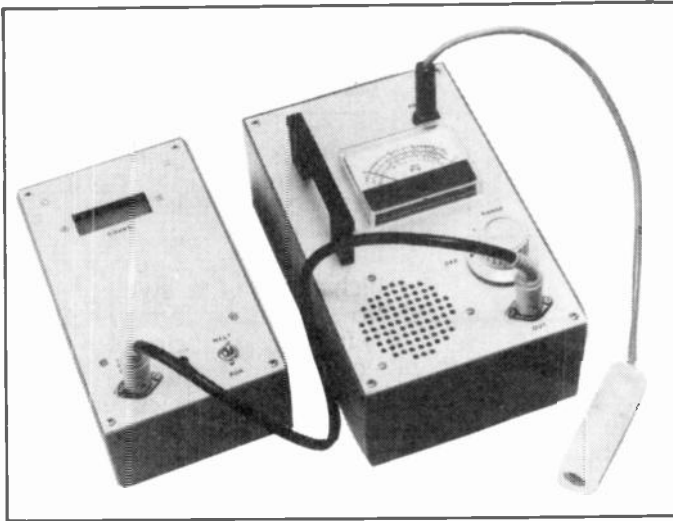
# GEIGER COUNTER

Colin Seymour describes a pulse counter to accompany last month's Geiger Ratemeter project.



The Geiger Counter complete with the ratemeter described last month.

Geiger ratemeters of the type described last month are of little use where the radiation levels being measured are close to the natural background. The count rate will be very low (with the tube specified, around 25 pulses will be detected per minute) and the random nature of the radiation will cause the meter needle to give a series of brief kicks rather than a steady deflection. These problems can be overcome by taking measurements over a reasonably long period of time to average out the fluctuations, and comparing the result with a previously-established background count

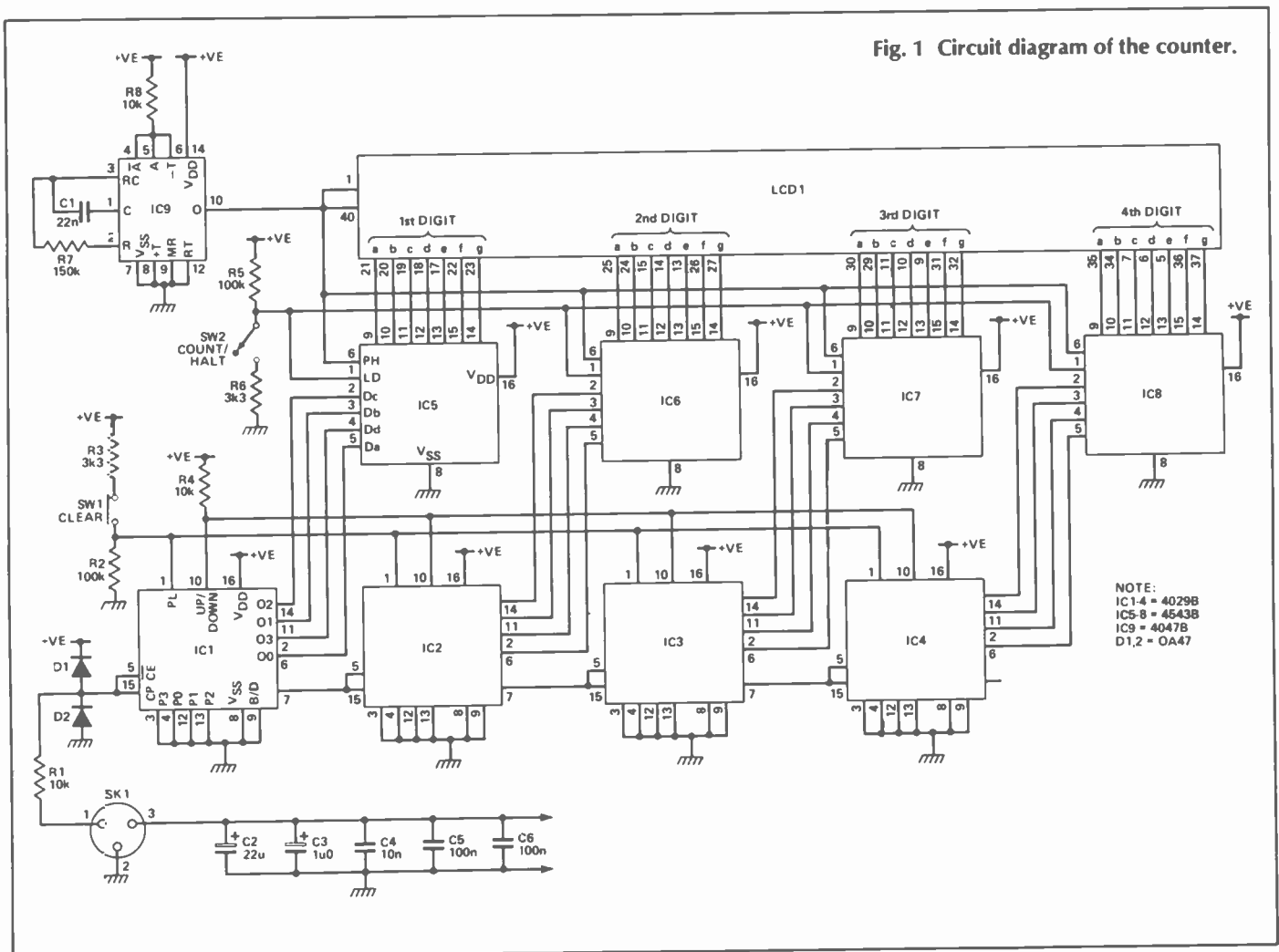

measured over the same period.

The counter described here is a portable unit which connects directly to the Geiger ratemeter. It

takes its power from the ratemeter's 6V battery and counts the pulses detected up to a total of 9999. No timing circuitry is

included in the counter — it is simply left on for the required period of time and the final count noted down. A useful refinement is a halt switch which allows the display to be 'frozen' while the count itself continues. This enables the user to record the count at intermediate time intervals without upsetting the final count.

The counter uses CMOS ICs and a liquid crystal display to keep power consumption to a minimum. The total current drain of the complete circuit is around 0.1mA at  $6V \pm 1V$ . An LSI counter module could have been used to save space and might have cost slightly less, but the MSI approach used here is more resistant to radiation damage.

## HOW IT WORKS

The input from the ratemeter arrives via SK1 pin 1 and is passed to the input of IC1 by R1 and the protection diodes D1, D2. IC1 is a four-stage counter which provides a binary-coded output to the display driver, IC5. It also clocks the next counter, IC2, which in turn clocks IC3, and IC3 in its turn clocks IC4. The binary outputs of ICs 2, 3, and 4 are fed to the display drivers IC6, IC7 and IC8 respectively. The PL inputs to the counters are normally held low but can be taken high by means of SW1 to reset them.

IC9 is an astable multivibrator providing a 70Hz square wave. This signal

feeds the display drivers, IC5, 6, 7 and 8, and the backplane/common connection of the LCD. The latch inputs (LD) of the driver ICs are normally held high by R5, allowing counting to continue in the normal fashion. Pulling these inputs low by means of SW2 causes the current state to be latched and fed continuously to the display. ICs 1, 2, 3 and 4 are unaffected by this and continue to count the incoming pulses. Returning the LD inputs of ICs 5-8 to the logic high state will remove the latched data and cause the current total count value to be displayed.

## THE NATURE

All matter is built up from a number of naturally-occurring atoms which combine with one another in various ways to form molecules of different substances. Atoms consist of clouds of negatively-charged electrons circling a positive nucleus. The nucleus is tiny in relation to the size of the atom as a whole and contains positively-charged particles called protons. In a stable, non-charged atom, the number of protons is equal to the number of electrons and the positive and negative charges cancel each other out. The number of protons in an atom (and hence the number of electrons) is known as the atomic number and is different for each element. For example, hydrogen has one proton and one electron and its atomic number is one, helium has two protons and two electrons and its atomic number is two, and so on.

The electrons are normally some distance from each other in their orbits around the nucleus, but the protons are packed closely together. Since the protons all have a positive charge, we might expect them to repel one another and move apart. This doesn't happen because the nucleus also contains a third type of particle, the neutron. These have no electrical charge and (to put it simply) act as a sort of glue, holding the nucleus together. There are usually about the same number of neutrons as there are protons in the nucleus of an atom, slightly less in atoms with high atomic numbers. However, the number of neutrons is not tied to the number of protons and it is possible to find atoms with the same atomic number which have different numbers of neutrons. These are known as isotopes. The number of neutrons in an atom is indicated by the atomic weight, a figure which is obtained by adding together the number of protons and the number of neutrons. It is therefore convenient to refer to an isotope by naming the element (which implies a certain atomic number) and then stating the atomic weight, for example cobalt <sup>60</sup>, strontium <sup>90</sup>, etc.

It should be clear from all this that there are a very large number of possible atomic constructions. However, most of these will be unstable and will break up or decay by emitting nuclear particles and turning into

other atoms. This process may be repeated until a stable element is created. In this way, most of the unstable atoms which may have existed have vanished and only very long-lasting ones remain such as potassium<sup>40</sup> and the isotopes of lead and heavier elements up to uranium. There also exist shorter-lived isotopes which result from the decay of uranium and thorium.

The radiation emitted from unstable atoms usually takes one of several forms. An alpha particle is the equivalent of a helium nucleus, two protons and two neutrons, travelling at great velocity. It penetrates matter very little and a sheet of paper will stop it. Beta is equivalent to an electron travelling at great speed with high energy. Its mass is 1/1837 that of the proton and it can be stopped by a few millimetres of aluminium. Gamma is a form of electromagnetic radiation, of wavelength one million to 100 million times smaller than light. The energy of such radiation is very high, and it is usually emitted along with an alpha or beta particle as a secondary effect of the nucleus being left in an excited (high energy) state. It is very penetrating, and at least 5 cm of lead would be needed to reduce radiation to one tenth of the unshielded level.

### Units Of Radiation

Measurement of radiation is essential if protection is to be provided, and the process involves many complexities which cannot be covered here.

Radiation is commonly measured either in terms of the absorbed dose or the dose equivalent. The *absorbed dose* is the ratio of the absorbed energy in a volume of matter to the total mass of that matter. The present SI unit for absorbed dose is the Gray (Gy) which is equivalent to one joule of energy absorbed per kilogram. Prior to the introduction of the Gy, the unit of absorbed dose was the Rad. This was equivalent to 0.01 joules of energy absorbed per kilogram, and instruments calibrated in Rads will continue to be seen for some time.

Different types of radiation have different effects on living tissue depending on the range of absorption. Alpha particles do not penetrate the outer layers of



## Construction

With the exception of the socket and the two switches, everything mounts onto one, double-sided PCB. As with the boards used for last month's ratemeter, the upper side of the board carries a ground plane which is formed simply from unetched copper cladding. This removes the need for a second foil pattern and helps to keep the board cost down.

Because the ground plane is formed in this way, the first stage of the construction is to remove some of the copper around component lead holes using a counterbore drill. Refer to the overlay diagram (Fig. 2) and note which holes carry component

leads or links and which are used for earthing. The ones used for earthing are indicated by a small circle. All holes not so indicated should be carefully counterbored until there is sufficient clearance to ensure that component leads cannot come into contact with the ground plane.

When this has been done, insert short wire links through all the earthing holes and solder them on both sides of the board. Refer to Fig. 2 again and install the resistors, the capacitors, the IC sockets (if you intend using them) and the diodes. Note that some of the resistors and all of the capacitors aside from C1 must be soldered to the ground at one end. Diode D2 should have its anode soldered to the ground plane.

Install the two rows of solder pins for LCD1 and then use insulated wire to form the links indicated on the overlay diagram. There are quite a number of these and some of them are close together. You may find it helpful to work through them one row at a time and to use different coloured wires for each row.

With the rest of the construction complete, connect the various flying leads to the points indicated in the overlay and then install the ICs. Solder the two switches and the DIN socket to the ends of the flying leads and the counter is ready for testing.

A short connecting lead is required to link the counter and the ratemeter. Use three-core cable with three-pin DIN plugs at either

## OF RADIATION

### Units of nuclear activity

1 Ci (Curie) =  $3.7 \times 10^{10}$  nuclear disintegrations per second.  
1 Bq (Becquerel) = 1 nuclear disintegration per second.

### Units of absorbed dose

1 R (Rad) = 0.01 joules per kilogram of absorbing material.  
1 Gy (Gray) = 1 joule per kilogram of absorbing material.  
(the absorbing material must be specified).

### Units of dose equivalent

Dose equivalent in Rem = absorbed dose (Rad x Q (relative biological effectiveness))

Dose equivalent in Sv (Sievert) = absorbed dose (Gy) x Q x N  
where Q = 1 for X and Gamma rays and beta particles.  
Q = 20 for alpha particles (formerly 10).

(N is another scale factor accounting for other absorption processes such as dose rate, and is set to 1 until further notice)

### Conversion

1 Ci =  $3.7 \times 10^{10}$  Bq  
1 Gy = 100 Rad  
1 Sv = 100 Rem

the skin, but if an alpha-emitting substance is inside the body the energy will be dissipated in a small area, causing great damage to cells. Beta and gamma radiation are absorbed over a long distance and are less damaging to individual cells. To take account of this we have a number of units which measure dose equivalent. These make use of a factor Q which indicates the Relative Biological Effectiveness (RBE) of the radiation. This factor is one for beta and gamma radiation and 20 for alpha radiation. The present SI unit for dose equivalent is the Sievert (Sv) which is obtained by multiplying the absorbed dose figure in Grays by the Q factor. The previous unit of dose equivalent was the Rem which was obtained in the same way but used Rads as the absorbed dose unit. The majority of instruments are still scaled in Rems (and milliRems) rather than Sieverts, hence the decision to calibrate the instrument described here in this way

## Radiation In The Environment

There is a background of natural radiation always present, which is caused mostly by natural radioactive isotopes in the environment and cosmic radiation. This is around 100mRem/year in Great Britain but can be thousands of mRem/year in some parts of the world.

Table 2 lists radiation levels recorded from various sources using the Geiger counter. The radioactive constituents are indicated where possible.

Location	Level	Level
Typical Background	100 mR/year	0.01 mR/hr
Adjacent to radium paint on WW2 marching compass (Inc. beta)	700 R/year	80 mR/hr
<b>Location</b>	<b>Counts/min</b>	<b>Counts/sec</b>
Background in 1930 s flat	25	0.4
Background in 1980 s office building	16	0.3
Near modern smoke detector (0.6 uCi Americium 241)	43	0.7
Near old smoke detector (60 uCi Americium 241)	817	14
Pack of camping gas mantles (due to thorium oxide)	396	7
Thorium oxide in glass tube (240 mm <sub>3</sub> )	1000	17
Adjacent to radium paint on WW2 marching compass (Inc beta) (Radium-226 including decay products)	90000	1500
Adjacent to case of WW2 marching compass	4668	78
330 mm from compass	52	0.9

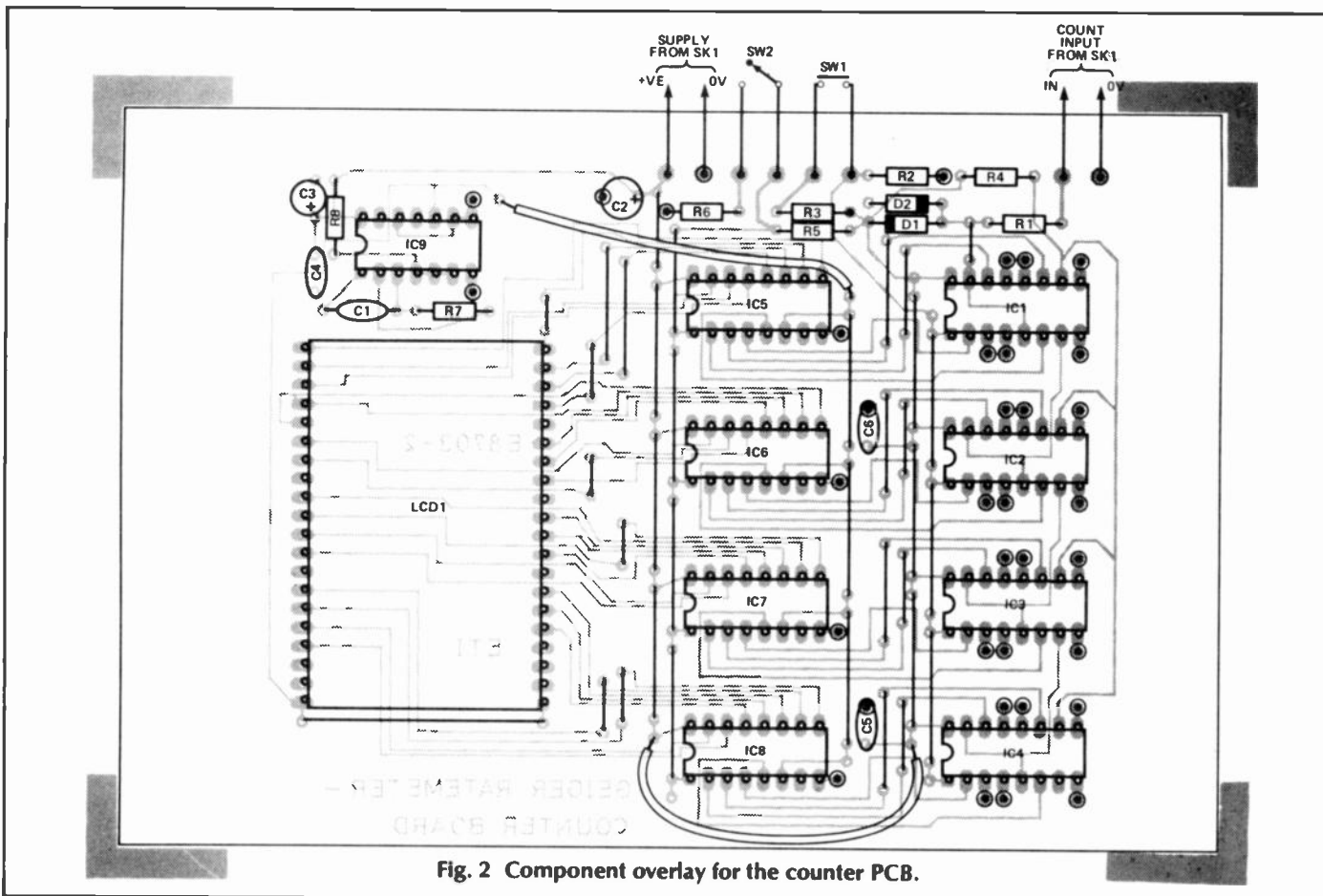


Fig. 2 Component overlay for the counter PCB.

end, and choose a length which allows the two boxes to be held a comfortable distance apart without having loops of cable dangling in the way. About 12-18in (300-450mm) should be sufficient. The cable need not be screened — ordinary light-duty mains flex would be more than adequate — and should be wired with pin 1 connected to pin 1, pin 2 connected to pin 2 and pin 3 connected to pin 3.

Connect the counter board to the ratemeter and switch on. Alternatively, connect the counter directly to a 6V supply. The LCD should indicate 0000. If nothing happens, switch off and check for wiring errors. If the display shows something other than 0000, the counter has probably been powered-up in the HALT condition. Move SW2 into the COUNT position and press SW1 to reset the count. If the display still gives the wrong indication, switch off and check the board.

If all seems well, place the detector assembly of the ratemeter near a source of radiation and check that the display increments with each 'click' from the loudspeaker. If you are testing the counter without using the ratemeter, connect its input to a signal generator with a CMOS-

compatible output. It should count reliably at frequencies up to a few hundred kilohertz. Check that the count can be reset by pressing SW1 and then try halting the display with SW2. The display should 'freeze' at the last figure indicated when the halt button is pressed. If the input signal is left connected while the display is halted, the counter figure should jump forward by a suitable amount when SW2 is set to COUNT again. This indicates that the counting circuitry has carried

on working while the display was held.

The assembled and tested board can now be sprayed with a protective lacquer and then installed in its case. The prototype was housed in a plastic box with an aluminium front panel, similar in style to the box which held the prototype ratemeter but slightly smaller all round. Any box which is large enough to hold the counter PCB should do. It is a nice touch to use something which matches the ratemeter box so that there is a

## PARTS LIST

### RESISTORS (all 1/4W, 5%)

R1, 4, 8	10k
R2, 5	100k
R3, 6	3k3
R7	150k

### CAPACITORS

C1	22n polycarbonate, polyester, mylar or polystyrene
C2	22 $\mu$ 10V tantalum
C3	1 $\mu$ 0 10V tantalum
C4	10n ceramic
C5, 6	100n ceramic

### SEMICONDUCTORS

IC1-4	4029B
IC5-8	4543B
IC9	4047B
D1, 2	OA47

### MISCELLANEOUS

LCD1	4-digit liquid crystal display with 12.7mm high characters (Epson LD-H7916AE or similar)
SK1	3-pin DIN chassis socket
SW1	push-button switch, momentary action, push to make
SW2	SPDT miniature toggle switch

PCB; case (see text); IC sockets if required, 8 off 16-way and 1 off 14-way; IC socket strip, 40-way (2 x 20 way) for mounting LCD1; PCB-mounting pillars, 4 off; perspex or celluloid filter for display if required; nuts, bolts, etc. for mounting pillars, DIN socket and display filter.

# PROJECT: Geiger Counter

strong visual link between the two halves of the project.

In the prototype, the board was attached to the front panel using 15mm (5/8") spacers. The cut-out for the display was covered with a piece of perspex underneath the panel, and the screws holding this and the PCB were countersunk into the aluminium to preserve the appearance of the finished unit. The box chosen was a little longer than the PCB which allowed the socket and the switches to be mounted at the bottom of the front panel. This removed the need to have flying leads attached to various parts of the case and made it possible to remove the complete counter assembly simply by detaching the front panel.

## In Use

A stopwatch will be required in order to use the counter. Zero the counter and start the timer at the same time. After sufficient counts have been taken, stop the timer and simultaneously set the counter to HALT. The count rate is the relative measure of the intensity of radiation intercepting the detection volume of the GM tube. The accumulated dose to a living organism is proportional to the intensity of radiation, the time spent exposed to that intensity, and the relative biological effectiveness (or Q factor) defined for the type of radiation. Hence a higher than background level may not be significant if it occurs only over a few minutes, whereas the constant background radiation is giving an accumulating dose continuously. However, low level radionuclides taken into the body can be concentrated in particular organs and in that case any

presence of abnormal radionuclides may be harmful (for example, the radium-226 in radium paint which concentrates in bones).

Because of the random disintegration of radioactive atoms, the count rate over a fixed time may vary randomly above and below an average. Over a long time period with many counts, the fluctuations are averaged out. The statistics of radioactive decay can be used to estimate how much error is likely in the reading. If there are enough counts (more than 100) then the 'normal distribution' can be assumed. If the standard deviation of the measurement (measure of its variation), is known, the probability of the result falling within a certain number of standard deviations either side of the mean can be found.

For radioactive decay, the standard deviation of a single count can be expressed as the square root of the count. It happens that about 95% (95.44%) of the readings will lie within plus or minus two standard deviations of the mean, that is, twice the square root of the number of counts.

Because of the random fluctuation in count readings, comparison of readings against background counts must bear the error limits in mind. To reduce the error in the background count, the count number must be as high as possible, which means waiting sufficient time for them to accumulate. To get 400 counts with a statistical error of  $\pm 40$  counts might require 20 minutes of counting. You should also bear in mind that the background count varies from place to place and also varies over the course of a day by as much as

## Suggested Reading

- J. Sharpe, "Nuclear Radiation Detectors", Methuen & Co Ltd, 1965.
- K. Kandiah, "Nuclear Instruments Over The Last Fifty Years", Journal of Scientific Instruments (Journal of Physics E) Vol 1 pp. 369-372, 1968.
- F. S. Goulding, "Transistorized Radiation Monitors", IRE Transactions on Nuclear Science, No. 2, August 1958, Vol. NS-5, pp. 38-43.
- "Nuclear Electronics III", Conference Proceedings, Belgrade, 15th-20th May 1961, International Atomic Energy Agency Vienna 1962: p. 429, C. J. Borkowski & R. H. Dilworth, "Personal Radiation Monitor," Oak Ridge National Laboratory; p. 487, J. Keller, "A Single Transistor GM Monitor with A Stabilised GM Supply" Instytut Badan Jadrowych, Warsaw.
- J.N. Andrews & D. J. Hornsey, "Basic Experiments with Radioisotopes", Pitman Publishing, 1972.
- Alan Martin & Samuel A. Harbison, "An Introduction to Radiation Protection". Chapman and Hall, 3rd edition. 1986.
- Edward Pochin, "Nuclear Radiation: Risks and benefits", Oxford University Press, 1985.

30:1. Therefore, make background readings at the same time as the other test reading.

If the test reading is higher than the background, consider the errors. On each reading, there is 2.5% probability of the error exceeding the limit on one side only. If the background plus error is less than the test reading minus error, the chance of there still being an overlap is 2.5% squared which is 0.625%. So, if the test reading is still greater than the background taking into account errors, then that is a 99.9% probability. If 400 counts are taken and the count rates obtained by dividing each count by the time taken for it, then the test reading rate must be at least 20% higher than the background rate to be clear of the errors. If more counts are taken then the errors can be reduced, and if fewer counts are taken then the errors will be greater.

ETI

Count	95% Error Limits	Error Limits in %
100	$\pm 20$ counts	$\pm 20\%$
400	$\pm 40$ counts	$\pm 10\%$
1000	$\pm 63$ counts	$\pm 6.3\%$
10000	$\pm 200$ counts	$\pm 2\%$

## BUYLINES

Everything here is perfectly straightforward and should be available from almost any electronic components dealer. The Epson display can be obtained from Midwich Computer Company Ltd, Gilray Road, Diss, Norfolk IP22 3EV or from STC Electronic Services, Edinburgh Way, Harlow, Essex CM20 2DF, Tel: (0279) 26777. Similar displays sold by Electrovalue, RS/Electromail and others should be suitable since the pin-out is just about standard, but do make sure you get

one with pins for PCB-mounting. The case isn't critical and any type which is a little larger all round than the PCB should do nicely. Choose one with an aluminium front panel if possible since this will allow everything to be mounted in the same way as on the prototype, simplifying construction and allowing easy access to the circuitry for checking and servicing. The PCB will be available from our PCB Service. See page 62 for details.

# 'S ★ BRAND NEW CATALOGUE ★ p' OMNI ELECTRONICS

We stock a wide range of components:

transformers, switches, pots, ICs, capacitors, resistors, diodes, boxes, triacs, LEDs, cable, connectors, PCBs-

in fact, all you need for your projects.

Send for our new catalogue - 20p + 18p postage or call at our shop Mon-Fri 9am - 6pm, Sat 9am - 5pm.

174 Dalkeith Road  
EDINBURGH EH16 5DX  
031-667-2611

<b>OSCILLOSCOPES</b> TELEQUIPMENT D75 Dual Trace 50MHz Delay Sweep ..... £350 State ..... £350 COSSOR CDU150 Dual Trace 35MHz Solid State Portable 8x10cm display. With Manual ..... £200 GOULD OS255 Dual Trace 15MHz ..... £200 TELEQUIPMENT D61A Dual Trace 10MHz With Manual ..... £175 S.E LABS SM111 Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual ..... £150 TELEQUIPMENT 043 Dual Trace 15MHz With Manual ..... £100 TELEQUIPMENT SS4A Single Trace 10MHz Solid State With Manual ..... £110 Philips PM3230 Dual Beam 10MHz Solid State ..... £100	<b>COMMUNICATION RECEIVERS</b> Racal RA17L 500kHz-30MHz ..... ONLY £140 each with manual. Eddystone 730/4 480kHz-30MHz only £110 each with manual.
<b>MULTIMETERS</b> AVO 9 Mk 4 (Identical to AVO 8 Mk 4 but scaled differently) Complete with Batteries & Leads ..... £55 AVO 8 Mk 2 Complete with Batteries & Leads £45 Above items in GOOD WORKING ORDER - appearance not A1 hence the price AVO TEST SET No 1 (Military version of AVO 8) Complete with batteries, leads & Carrying Case ..... £85 AVO Model 7x Complete with batteries, leads & carrying case ..... £40 AVO Model 73 Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads ..... £18 AVO 72 - Similar to above but no AC current range. With batteries & leads ..... £10	<b>SPECIAL OFFERS</b> B + K Precision CRT Restorer/Analyser Model 467 - Supplied with 2 bases and Manual. (P&P £7) ONLY £125 each LABGEAR Colour Bar Generator KG1 8 Test Patterns. (P&P £4) ..... ONLY £40 each
<b>ADVANCE/GOULD DVMS</b> Auto ranging, max reading 20,000 AC/DC volts - resistance only £50 p&p £5	<b>CROSSMATCH GENERATOR TVTSM</b> Crosshatch/Dots/White RF & Video Outputs. Tuner Control (P&P £4) ..... £10 Degaussing Coils (P&P £4) ..... £20
<b>AVO TRANSISTOR TESTER TT169</b> Handled GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12	<b>ADVANCE AM SIGNAL GENERATOR SG62B</b> 150 KHz-220MHz ..... £45 ADVANCE AM SIGNAL GENERATOR Type 62 150KHz-220MHz ..... £30 METRIX WOBBLATOR Type 210. 5-220MHz ..... £20 PHILIPS WOBBLATOR GM28775 5-220MHz & 440-880MHz ..... £100 LABGEAR COLOUR BAR GENERATOR CM6037 (P&P £4) ..... £60 RACAL 32MHz UNIVERSAL COUNTER TIMER Type 836 ..... £50 MARCONI TF2604 (Later version of TF 1041 VTVM) 20Hz-1500MHz: AC/DC/Ohms AC 300mV-300V FSD ..... £60 MARCONI VALVE VOLTMETER TF2600 10Hz-100MHz: 1mV-300V FSD ..... £40 PHILIPS COLOURBAR GENERATOR type 5501 (P&P £5) ..... £100 PHILIPS COLOURBAR GENERATOR type 5508 Video out. Many Functions ..... £125
<b>ISOLATING TRANSFORMERS</b> 240V INPUT - 230V OUTPUT 500 VA £15ea P&P £5 100 VA £6ea P&P £2	<b>NEW EQUIPMENT</b> HAMEG OSCILLOSCOPE 605 Dual Trace 60MHz Delay Sweep Component Tester ..... £567 HAMEG OSCILLOSCOPE 203 6 Dual Trace 20MHz Component Tester With 2 Probes ..... £298 All Other Models Available
<b>DISK DRIVE PSU 240V 1W: 5V 1.6A &amp; 12V 1.5A out.</b> Size: W125mm, H75mm, D180mm Casad. Un-used. Only £10.00 each (P&P £2) Query keyboard (as in Lynx Micro). Push to make. Cased ..... £5 each (P&P £2) Various 5 1/4" Floppy Disk Drives and Stepping Motors Available	<b>BLACK STAR FREQUENCY COUNTERS P&amp;P £4</b> Meter 100 - 100MHz ..... £99 Meter 600 - 600MHz ..... £126 Meter 100 - 1GHz ..... £175 BLACK STAR JUPITOR 500 FUNCTION GENERATOR Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 £110 HUNG CHANG DMM 7030 3 1/2 digit Hand held 28 ranges including 10 Amp AC/DC 0.1%. Complete with Battery and Leads P&P £4 ..... £39.50 OSCILLOSCOPES PROBES Switched x1, x10 P&P £2 ..... £11
Used equipment - with 30 days guarantee. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK SAE or Telephone for Lists Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage	
<b>STEWART OF READING</b> 110 WYKHAM ROAD, READING, BERKS RG6 1PL Telephone: 0734 68041 Callers welcome 9 am - 5.30 pm Mon.-Fri. (until 8 pm Thurs.)	

## FREE 100 PAGE CATALOGUE

1000's Major & Minor Electronic components  
Audio, Hifi, Car Radios, Amps, Kits, Computer Bits, Meters scopes, Test Gear, Transistors, Disco, Hardware Tools.

write or phone:  
**SMITH ELECTRONICS**  
57 CHAPEL STREET, LEIGH,  
LANCS WN7 2AL Tel: (0942) 606674.

# For KITS & COMPONENTS

## Choose the easy way - with

# TRK

Send 50p & SAE for CATALOGUE (refundable with first order)  
ORDERS: RING (01) 567 8910 - 24 HRS

### NEW POWER STROBE KIT



Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz this kit also includes circuitry to trigger the light from an external voltage source (eg a loudspeaker) via an opto isolator. Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality pcb, components, connectors, 5Ws strobe tube and full assembly instructions. Supply: 240V ac. Size: 75x50x45  
**£12.50**

### DISCO LIGHTING KITS

**DL100K** This value-for-money 4-way chaser features by directional sequence and dimming 1kW per channel ..... £17.50  
**DLZ1000K** - A lower cost uni-directional version of the above. Zero switching to reduce interference ..... £9.95  
 Optional opto input allowing audio 'beat' light response (DLA1) ..... 70p  
**DL3000K** - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. ..... £14.25  
**DL8000**  **NEW**

### HIGH SECURITY LOCK KIT

Designed for use with our lock mechanism (701 150) this kit will operate from a 9V to 15V supply drawing a standby current of only 50uA. There are over 5000 possible 4-digit combinations and the sequence can be easily changed. To make things even more difficult for an unauthorised user an alarm can be sounded after 3 to 9 incorrect entries - selectable by means of a link. The alarm can sound for a few seconds to over 3 minutes during which time the keyboard is disabled preventing further entries. A latched or momentary output is available making the unit ideal for door locks, burglar alarms, car immobilisers, etc. A membrane keyboard or pushbutton switches may be used and a beep sounds when a key is depressed. Kit includes high quality PCB, all components, connectors, high power buzzer and full assembly and user instructions.  
**£15.95**  
**350 118 Set of Keyboard Switches** ..... £4.00  
**KB125 12-Way Membrane Keyboard** ..... £9.98  
**701 150 Electric Lock Mechanism** ..... £16.50

### DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°. The kit has a sensitivity of 200mV for a full-scale reading, automatic polarity and overload indication. Typical battery life of 2 years (PP3). ..... £17.00

### VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits.  
 Supply: 240V AC or 15-24V DC at 10mA  
 Size (excluding transformer) 9 x 4 x 2 cms.  
 The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60m. Two keyboards are available MK9 (4-way) and MK10 (16-way), depending on the number of outputs to be used  
**MK12 IR Receiver (incl. transformer)** ..... £14.85  
**MK18 Transmitter** ..... £7.50  
**MK9 4-Way Keyboard** ..... £2.00  
**MK10 16-Way Keyboard** ..... £5.95  
**601 133 Box for Transmitter** ..... £2.60


### HOME LIGHTING KITS

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300W of lighting  
**TDR300K Remote Control Dimmer** ..... £16.45  
**MK6 Transmitter** ..... £4.95  
 for above ..... £4.95  
**TD300K Touchdimmer** ..... £8.50  
**TS300K Touchswitch** ..... £8.50  
**TDE/K Extension kit for 2-way switching for TD300K** ..... £2.70  
**LD 300K Light Dimmer** ..... £4.35

### PROPORTIONAL TEMPERATURE CONTROLLER KIT



Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, Incubators wine-making, etc. Max load 3kw (240V ac) Temp. range up to 90°C. Size: 7x4x2.5cms.  
**£7.10**



## TRK ELECTRONICS

13 BOSTON RD  
LONDON W7 2SJ  
Tel: 01:567 8910

SEND 9x6" S.A.E. AND 50p FOR CATALOGUE OR CALL AT SHOP MON-FRI 9-5 pm SATURDAY 10-4 pm

ORDERING INFORMATION:  
ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P Europe £2.75 Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No 5293 14002

LOCAL AUTHORITY AND EXPORT ORDERS WELCOME  
GOODS BY RETURN SUBJECT TO AVAILABILITY

# THE ETI CAPACITOMETER

Mind your p's and  $\mu$ 's with Ray Bold's handy bench capacitance meter.

This instrument is designed to accurately measure capacitors from a few picofarads to ten microfarads on a forward reading linear scale. The meter is very sensitive and it incorporates a zero adjustment which is useful for cancelling the effects of stray capacitances on the lower ranges. This means the 0 to 100p range is exactly that and does not call for mental arithmetic.

However, the Capacitometer is simple and inexpensive to build, the most expensive component being the meter M1, although a spare or second hand meter can be used.

There are ten ranges available on the Capacitometer. The ranges are:

- 0 - 100pF
- 0 - 1nF
- 0 - 10nF
- 0 - 100nF
- 0 - 1 $\mu$ F
- 0 - 10 $\mu$ F


## Theory

Figure 1 shows the complete circuit of the Capacitometer. Q1 is a unijunction oscillator producing a narrow pulse at B2 every three milliseconds (if R1 is selected) or every thirty milliseconds (if R2 is selected). The pulses are amplified and inverted by Q2 and used to trigger IC<sup>1</sup>.

IC1 produces a pulse every time it is triggered. The width of the pulse varies according to the formula  $T=1.1CR$ . For example: with SW1 in position three, R1 is selected to produce a pulse every three milliseconds, and R8 is selected. With a 10n capacitor connected to the terminals the pulse width will be:

$$1.1 \times (10 \times 10^{-9}) \times (100 \times 10^3) \\ = 1.1 \times 10^{-3} \text{ seconds}$$

or 1.1 milliseconds every three

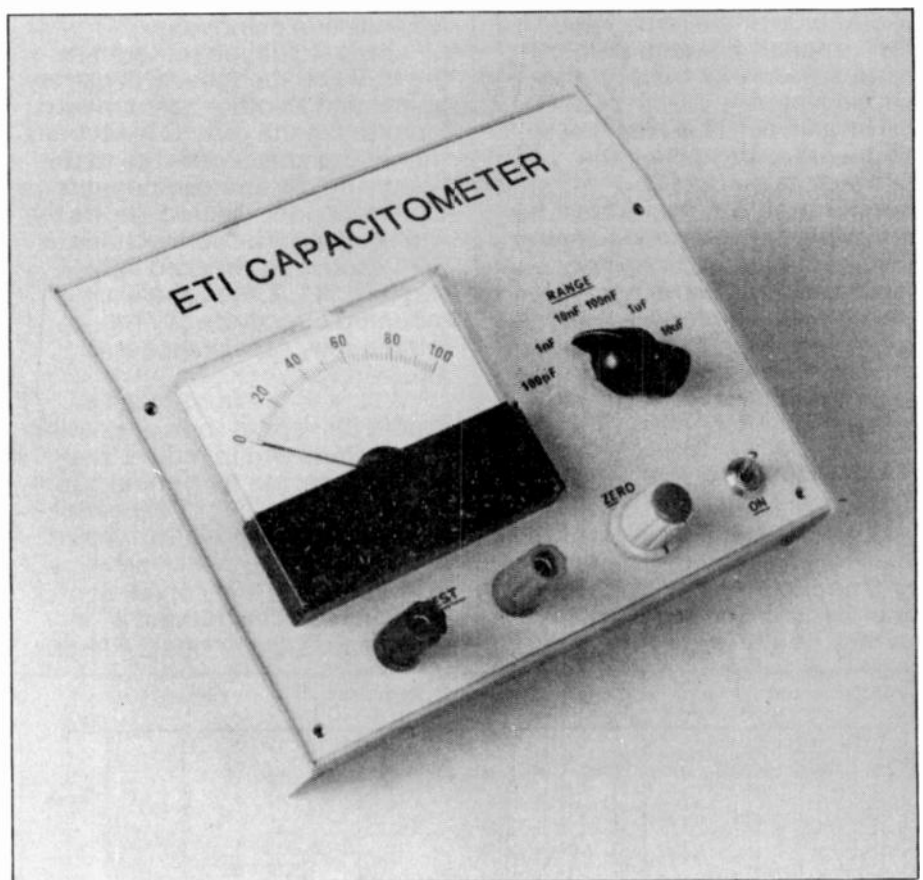

milliseconds. These pulses are averaged to produce full scale deflection on M1.

Now if a capacitor of 100n is connected and SW1 switched to position four, R2 is selected to produce a pulse every thirty milliseconds and R8 is still selected. The pulse width will be:

$$1.1 \times (100 \times 10^{-9}) \times 100 \times 10^3 \\ = 1.1 \times 10^{-2} \text{ seconds}$$

or 11 milliseconds every thirty milliseconds.

It can be seen that the average voltage is the same as in the previous example and full scale deflection is again produced on

M1. Similar calculations apply to the other ranges.

Figure 2 illustrates the advantage of such a low full scale duty cycle. With a test capacitor at the top of the set range the duty cycle is 33% and the meter reads full scale (Fig. 2c). A slightly larger test capacitor produces a greater duty cycle and the meter correctly reads off the scale (Fig. 2d). A much larger capacitor will give overlarge pulse widths causing IC1 to miss alternate trigger pulses so the duty cycle is a little over 50% (Fig. 2e) and the meter still correctly reads off the scale.

If the full scale duty cycle were designed to be, say, 60% the

capacitor with a value at the top of the set range produces the 60% mark-to-space ratio and the meter reads full scale deflection (Fig. 2f). However, if the much larger capacitor is tested, again alternate trigger pulses are missed and a duty cycle of just over 50% is produced (Fig. 2g). This causes the meter to erroneously read a value on the scale.

Designing the Capacitometer with a full scale duty cycle of only 33% increases the margin for error and allows capacitors well over the set range to be shown correctly for what they are.

After being clipped by ZD1 the pulses are applied to C2 which produces a steady voltage proportional to the pulse width. This is applied via calibration preset resistor PR1 to IC2's non-inverting input.

The gain of IC2 is arranged so that for full scale reading the voltage at its output is approximately 5V. Therefore it is impossible to overdrive the meter movement by a factor of more than about 1.8. This technique safeguards the meter without diode protection. In addition, the time constant of the C2 circuit keeps the pointer velocity below overload conditions.

### Construction

The PCB overlay is shown in Fig. 3. Solder in the resistors and capacitors first and the semiconductors last. A suggested panel layout is shown in Fig. 4 but this may be altered as the

dimensions of the meter dictate. However, the centre of the meter is indicated and this should suit the majority of meters.

The front panel of the case used will probably be supplied with a clear protective sheet on. This should be left on and marking carried out in ballpoint pen. Only when all drilling has been completed should the film be removed for lettering to be applied. Before applying lettering clean the surface of the front panel with methylated spirits or similar to remove any grease. Then be careful to handle the panel by its edges only. After lettering, the front panel should be finished with clear lacquer to protect the lettering and paintwork.

Leads should be soldered to the PCB and then the PCB, battery holder and all other components mounted in the case. Connections should then be completed to the battery holder and components on the front panel. Figure 5 shows the wiring layout. The connections to SW1 should be checked very carefully. R1, 2, 7, 8, and 9 are mounted directly on SW1 to reduce stray capacitance and interwiring.

Wiring to the front panel should be kept as short as possible for neatness and to reduce stray capacitance, but long enough to allow easy handling of the panel when assembling the instrument.

After carefully checking all assembly work and connections, make sure the instrument is switched off and connect a nine

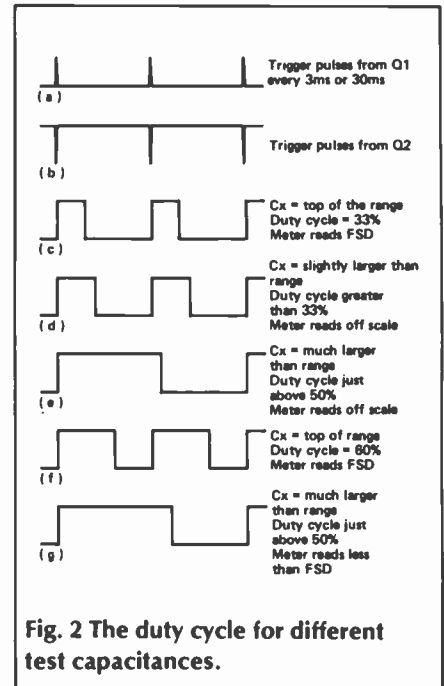


Fig. 2 The duty cycle for different test capacitances.

volt battery via a milliammeter. The prototype took 13mA on the 1μ and 10μ ranges and 5mA on the other ranges. Switch on and if there is a significant difference from these figures the meter should be switched off quickly and the cause investigated.

### Calibration

It is suggested a close tolerance capacitor be obtained for calibration. Alternatively one could be measured on a piece of equipment of known accuracy. This capacitor should be set aside for periodic checks of the

### HOW IT WORKS

Q1 and associated components form a pulse generator generating a narrow pulse every three milliseconds depending on the resistor selected (R1 or R2). These pulses are amplified and inverted by Q2 and are used to trigger IC1, a 7555 CMOS timer connected as a monostable.

IC1 gives out a pulse every time it is triggered, the width of the pulse being dependent on the values of the resistor and capacitor connected to pins 6 and 7. The resistor is selected by SW1b and the capacitor is the capacitor to be measured.

ZD1 is used to chop these pulses to a constant amplitude and C2 acquires a voltage dependent on the pulse width and frequency from IC1. This voltage is fed to IC2 which forms a voltage amplifier with a gain of approximately eight. The amplifier is calibrated for full scale deflection by PR1 and incorporates a zero control, RV1.

M1 is used to indicate the voltage from IC1 pin 6 and therefore the value of capacitor.

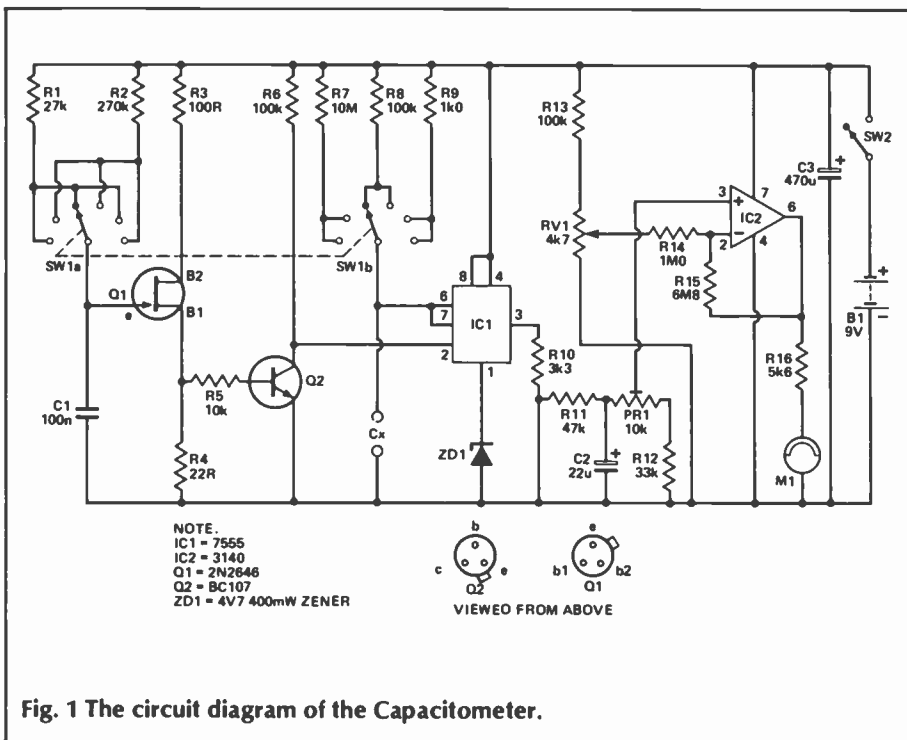


Fig. 1 The circuit diagram of the Capacitometer.

# PROJECT: Capacitometer

instrument's accuracy.

With the instrument switched on and the appropriate range selected, the zero adjustment should be checked. The test capacitor should then be connected and PR1 carefully adjusted to obtain the correct reading. On the prototype it was noted that a change in supply voltage of plus or minus one volt causes a 2% increase or decrease respectively in full scale reading.

On the 0-100p and 0-1n ranges a reading will appear on the meter due to stray capacitances. On these ranges the zero control should be rotated anti-clockwise until the meter just reads zero. Adjusting the control carelessly will cause errors in later readings. It must also be remembered the control needs returning fully clockwise when using the higher ranges. It is advisable to use a marked knob so its position can be checked visually if required during a measurement. It may also be useful to mark the front panel with the correct settings for the 100p and 1n ranges.

The zero control is also useful when measuring short lead capacitors or the sweep of variable capacitors. Flying leads should be connected to the instrument and one of them left disconnected at the capacitor end. The instrument

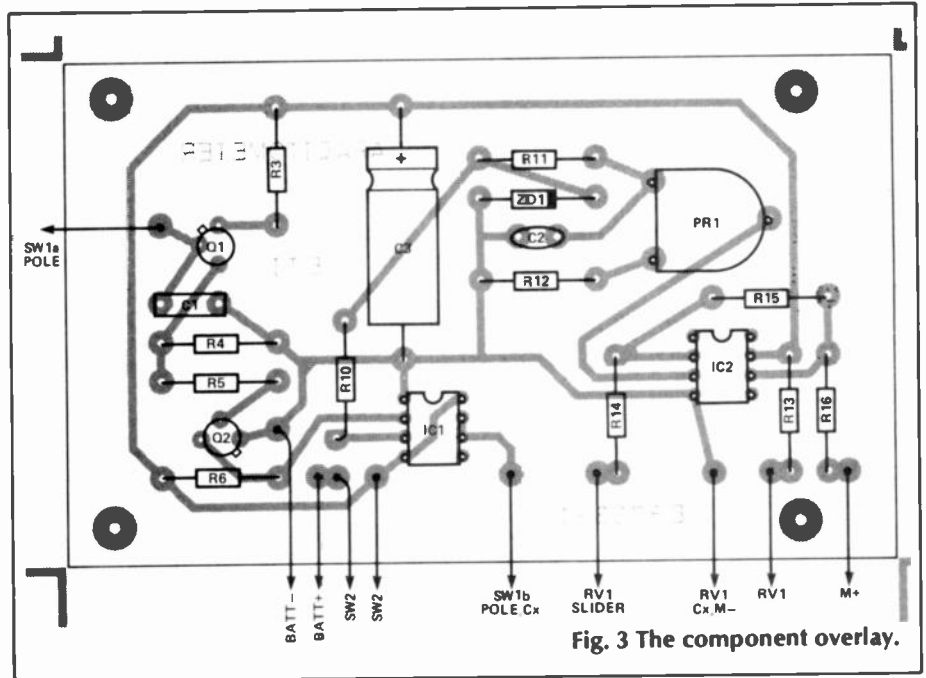


Fig. 3 The component overlay.

should then be zeroed and the lead connected to the other side of the capacitor. Direct readings can then be made.

### Alternative Meters

A wide range of meters can be used in this unit. The value of R16 should be altered to accommodate the meter chosen.

With a capacitor suitable for full scale deflection connected to

the test terminals and PR1 set at its centre point, a voltage of approximately 5V is produced at IC2 pin 6. Using Ohm's law with this voltage and the full scale deflection current of the chosen meter, R16 can be calculated as follows.

Meter sensitivity eg  
100µA FSD  
internal resistance eg 580R

### ETI CAPACITOMETER

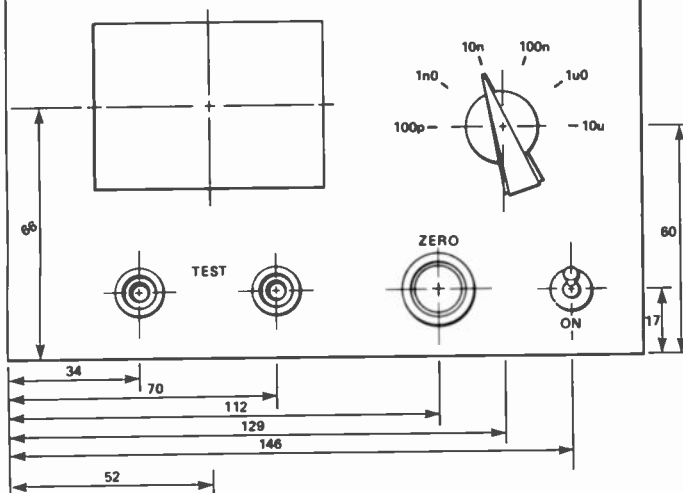


Fig. 4 The suggested front panel design.

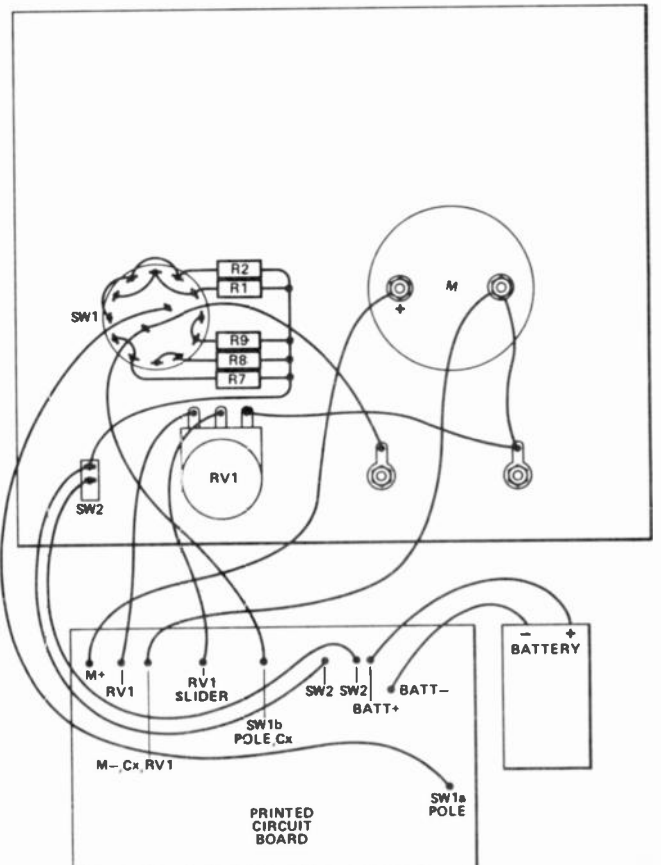


Fig. 5. Wiring of the Capacitometer.

# PROJECT: Capacitometer

total resistance for  $100\mu\text{A} =$

$$\frac{V}{I} = \frac{5}{100 \times 10^{-6}} = 50\text{k}$$

In this case the meter's internal resistance is insignificant and a 51k resistor should be suitable for R16.

It is also possible to calibrate the instrument for use with an existing multimeter in a similar way.

ETI

## BUYLINES

The case can be obtained from MS Components Limited, telephone number 01-670 4466. The catalogue number is 4108.

The battery holder was also from MS Components, as catalogue number 644.

The 10n capacitor with a 1% tolerance can be obtained from Maplin Electronics. All the other components are easily available and should cause no problems. A PCB will be available from the ETI PCB Service in due course.

## PARTS LIST

### RESISTORS All $\frac{1}{4}$ W 5% unless stated

R1	27k 1%
R2	270k 1%
R3	100R
R4	22R
R5	10k
R6, R13	100k
R7	10M 1%
R8	100k 1%
R9	1k0 1%
R10	3k3
R11	47k
R12	33k
R14	1M0
R15	6M8
R16	5k6 (see text)

PR1	10k horizontal preset
RV1	4k7 potentiometer

### CAPACITORS

C1	100n polycarbonate
----	--------------------

C2	22 $\mu$ 16V tantalum
C3	470 $\mu$ 16V electrolytic
	10n 1% polystyrene for calibration

### SEMICONDUCTORS

IC1	7555
IC2	3140
Q1	2N2646
Q2	8C109
ZD1	4V7 400mW zener diode

### MISCELLANEOUS

M1	1mA moving coil meter
SW1	two pole, 6 way rotary switch
SW2	SPST miniature toggle switch
	Red and black 4mm terminals; case; transfers; knobs; PP3 battery and carrier; PCB; connecting wire, screws, nuts and bolts.

# Complete Parts Sets for ETI Projects

## MAINS CONDITIONER

FEATURED IN ETI, SEPTEMBER 1986


It is astonishing how many people buy or build top-flight hi-fi equipment, and then connect it to a noisy, spiky mains supply. Rather than buying a Ferrari and trying to run it on paraffin, you might think, 'Expecting crystal clear sound, the poor music enthusiast ends up with a muddy, confused mush, and feels that he has somehow been cheated. Is this hi-fi? My music centre sounded just as good!'

The domestic mains supply is riddled with RF interference, noise, transient spikes, and goodness knows what else. Computers crash, radios pop and crackle, tape recordings are spoiled and hi-fi sounds 'not quite right'. Why put up with it when the solution is so simple? The ETI mains conditioner is the lowest cost upgrade you will ever buy, and probably the most effective!

Our approved parts set consists of PCB, all components, toroid, enamelled wire, firing lies, fast response VDR\*, and full instructions.

ETI MAINS CONDITIONER PARTS SET ONLY £4.60!

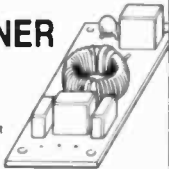\*Note: the toroid and VDR supplied are superior to the types specified in the article.



## TACHOMETER AND DWELL METER

FEATURED IN ETI, JANUARY 1987

### MOTORISTS QUIZ

You are driving along the road one day when the sound of a horn makes you look behind. The driver of a milk float is cursing you for driving so slowly. A while later, an invalid carriage overtakes you, and just as you turn into your drive you hear a tractor driver mutter 'At last I can get out of first gear!'

- Do you:
- Fit a £500 Pie-in-ear in-car stereo with digital flexi-woofers and 24-band ramification?
  - Buy a set of fluffy dice and sticker saying 'My other car is a Maccaroni'?
  - Give your car in part exchange for a milk float/invalid carriage/tractor?
  - Turn your engine.

The combined tachometer and dwell meter parts set contains: case with battery compartments; printed circuit board; all components; switches; plug, socket and test leads; battery connector; full instructions. The answer to the quiz, by the way, is: e) Buy a bright red Lotus Esprit!

### TACHOMETER AND DWELL METER PARTS SET

£12.90 (with terminals for external meter)

£16.40 (with self-contained meter)



## MAINS CONTROLLER

FEATURED IN ETI, JANUARY 1987

Have you ever wondered what people do with all those computer interfaces? Put your computer in control, say the ads. 'The Spectrebeeb has eight TTL outputs. What on earth can you control with a TTL output? A torch bulb?'

The ETI Mains Controller is a logic to mains interface which allows you to control loads of up to 500W from your computer or logic circuits. An opto-coupler gives isolation of at least 2,500V, so the controller can be connected to experimental circuits, computers and control projects in complete safety. Follow your computer interface with a mains controller and you're really in business with automatic control!

The mains controller connects directly to most TTL families without external components, and can be driven by CMOS with the addition of a transistor and two resistors (supplied).

Your mains controller parts set contains: high quality roller tinned PCB; MOC3021 opto-coupler; power triac with heatsink; mounting hardware and heatsink compound; all components, including snubber components for switching inductive loads; transistor and resistors for CMOS interface; full instructions.

### MAINS CONTROLLER PARTS SET

£6.20



## POWERFUL AIR IONISER

FEATURED IN ETI, JULY 1986

Ions have been described as 'vitamins of the air' by the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead air'.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products, was reliable, good to build, and fun! Apart from the serious applications, some of the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller tinned printed circuit board, 65 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs about a third of the price of the individual components. What more can we say?

Instructions are included. **DIRECT ION PARTS SET £9.50**



## MATCH BOX AMPLIFIERS

20W Single IC parts set £6.50

50W Bridge Amplifier parts set £8.90

L165V Power Amplifier IC, with data, £3.90

## LM2917 EXPERIMENTER SET

Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the 'Next Great Little IC' feature (ETI, December 1986).

LM2917 Experimenter Set £5.80

## RUGGED PLASTIC CASE,

suited for mains conditioner and mains controller. ONLY £1.35!



**SPECIAL CHRISTMAS OFFER!**

Until December 31st, our best-selling ioniser set is available with a special white case at the same price as the standard ioniser!

**WHITE IONISER PARTS SET ONLY £9.50!**

Orders should be sent to Specialist Semiconductors at the address below including 60p towards postage and packing. Please allow up to 14 days for delivery. There is no telephone service at the moment, but all letters or requests for lists will be answered (at top speed if you send SAE!)

**Specialist SEMICONDUCTORS**  
FOUNDERS HOUSE REDBROOK MONMOUTH GWENT





# CREDIT CARD CASINO

Paul Chappell risks all with ETI's tiny answer to Las Vegas.

Since the advent of the 1960 Betting and Gaming Act there has been a huge upsurge in the volume of gambling in Britain. It is estimated some 75% of the population now indulge in some regular form of betting, whether it be football pools, bingo, horse racing or casino type games — cards, dice, roulette.

If you include the occasional 10p in an arcade slot machine and your special personal numbers which may already have won you a holiday for two in Acapulco (if you subscribe for seven years to Illiterate Indigestion) then probably everybody who is not an Archbishop or a miser has a flutter at some time or other.

The Credit Card Casino is a pocket gambling machine which will play roulette, craps, and several other games of chance. The case measures only 3in x 2in x 1/2in, so although it may not be quite as slim as a credit card, it's certainly small enough to slip into your pocket.

## Construction

The component overlay for the project is shown in Fig. 2. To allow the switch button to protrude through the front panel, none of the components must be higher than the switch body.

This means mounting the transistors as close as possible to the PCB, and choosing the tantalum capacitors for minimum body length — 16mm or less if possible. Most 6.3V devices will be suitable. If they are a little too tall when standing upright, you can lean them towards R2 and R3. C3 should also be chosen with care. Radial leads with a 5mm pitch and a case that can be mounted flat against the PCB are the main requirements. Ceramic or metallised film types of suitable proportions are both equally suitable.

Don't solder in the LEDs at this stage — wait until the case top has been drilled and you can judge the lead length needed.

The batteries we used were Duracell RM13H mercury cells, sold as hearing aid batteries in most chemists. The PCB is drilled to fit the body of the cells, roughly 8mm in diameter. The positive contacts consist of strips of phosphor-bronze, 5mm x 10mm, cut from a draught excluder strip. These are soldered to the pads on the rear of the PCB on either side of the battery holes (Fig. 3).

A small kink in the middle of each strip helps to keep pressure on the cells to maintain good contact. The negative terminals are made from stiff wire — we used a paper clip bent to shape with long nosed pliers! Be careful when bending the wire. Excessive strain on the soldered end can lift the tracks from the PCB.

## Assembling The Case

Using the fascia as a template, mark out the positions for the LEDs and switch on the lid of the case. The LED holes should be

made with a 5/64in drill. Check the positions after against the fascia — if any holes are not quite central, you can widen them slightly with a larger drill or a reamer. The fascia will disguise any slight errors!

A square hole is needed for the switch button. If you have a 7/16in square punch, or can afford a few pounds to buy one, mark the drilling point by drawing an X between the corners of the square hole, making sure to keep it parallel to the sides of the lid.

If you haven't got a punch the alternative is to mark out the square and drill several holes around the inside. Use a sharp knife to cut out the waste plastic then tidy up the hole by filing it to size or by gradually paring away the remaining waste with a knife.

Insert the LEDs into the PCB, then hold the PCB against the drilled lid so that the switch button is in its hole. Adjust the positions of the LEDs so they all poke through their respective holes with the PCB parallel to the lid. Now solder the LEDs in place and crop the leads.


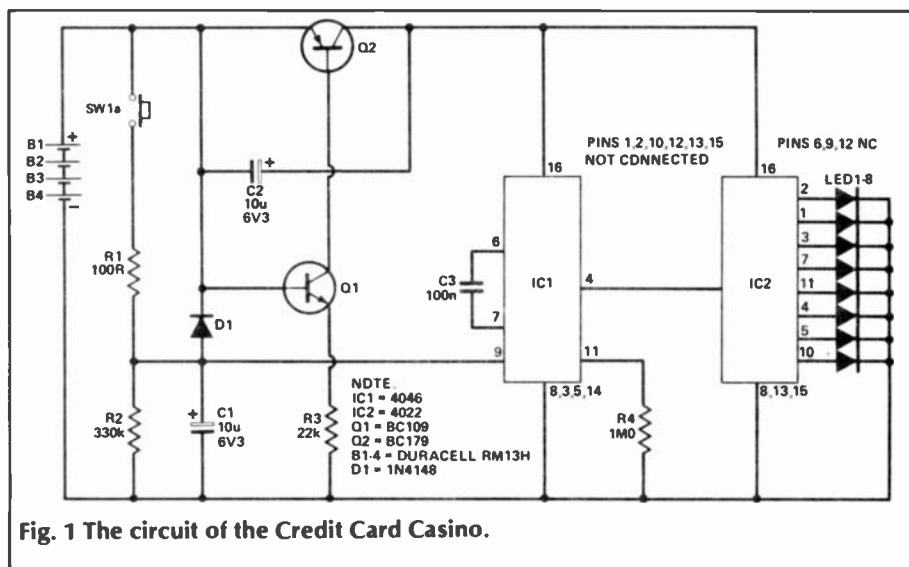


Fig. 1 The circuit of the Credit Card Casino.

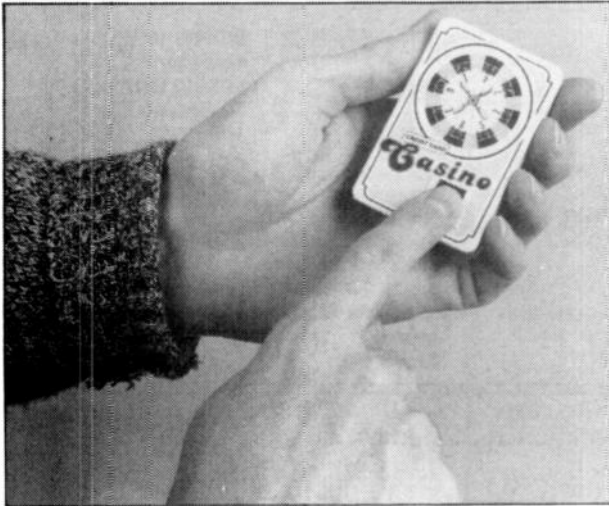

The complete Credit Card Casino. A pocket sized flutter.

At this point you can either finish the casino the easy way or the hard way. The easy way first. Line the bottom of the case with a piece of  $\frac{3}{4}$ in stiff foam plastic. Put on the lid of the case with the foam holding the PCB in place, cover the front with the self-adhesive fascia, and you've finished.

If you prefer the PCB can be held in place by gluing the switch body and LEDs to the lid but in this case you'll have to unsolder the phosphor-bronze strips when you want to change the batteries. The casino finished in this way will be about 1 in deep.

If you are keen to make the slim version, you've still got some work ahead of you. The first thing to do is to mark the body of the case all around,  $\frac{1}{2}$ in from the rim.

By far the easiest way to do this is to spend a few minutes making yourself a simple marking gauge. You'll need a length of  $\frac{1}{4}$ in wood baton, a panel pin and some glue. Cut a 1in length and a 6in length from the baton. Knock the panel pin through one end of the 6in length so that the point just

protrudes through the wood. Fix the 1in piece at right angles to the 6in one,  $\frac{1}{2}$ in from the pin. Now hold the longer baton so that the point is against the side of the case and the short length rests on the rim. Keeping the short piece flat against the top at all times, score a line all the way around the case with the point. If you have a steady hand, the line will be  $\frac{1}{2}$ in from the rim all the way around.

Cut off the top part of the case with a hacksaw, just above the line you have marked, then file down the rough edges. Place a piece of fine grained sandpaper on a flat surface and place the case upside down on it. Rub the case on the sandpaper with a gentle circular motion until it is perfectly smooth and has worn right down to the marked line. Be patient. If you try to rush it, you'll end up with a lopsided case.

Since the case is slightly tapered, you'll now find that the lid won't fit. The raised area on its underside will be too wide. Your next job is to file away the edges of the raised area until the lid fits flush with the top of the case.

## HOW IT WORKS

IC2 is a Johnson counter, which lights each of the LEDs in turn as it is clocked. The clock signal is derived from the VCO section of a phase locked loop, IC1. The output frequency of IC1 is determined by the voltage on pin 9.

When the spin button is pressed, C1 is charged to virtually the full positive supply voltage via R1. When the button is released, the charge leaks away via R2 over a period of several seconds.

The result is that the light spins rapidly around the circle of LEDs while the button is held down then when the button is released it gets slower and slower and eventually comes to rest.

Transistors Q1 and Q2 serve to cut off the supply when the casino is not in use. When the spin button is pressed

Q1 draws current via R3 and turns on Q2, allowing the circuit to operate.

When the button is released the negative end of C2 is at almost the full supply voltage. C2 gradually charges via the base current supplied to Q1 and the voltage across R3 drops.

After a minute or so, Q1 can no longer draw enough current to keep Q2 hard on. The voltage at Q2 collector falls slightly, causing Q1 base voltage to fall, leading to an even lower current from Q1.

This regenerative action causes the current to be shut off almost instantly, and the casino remains in a standby state drawing only Q2's leakage current until the spin button is pressed again.

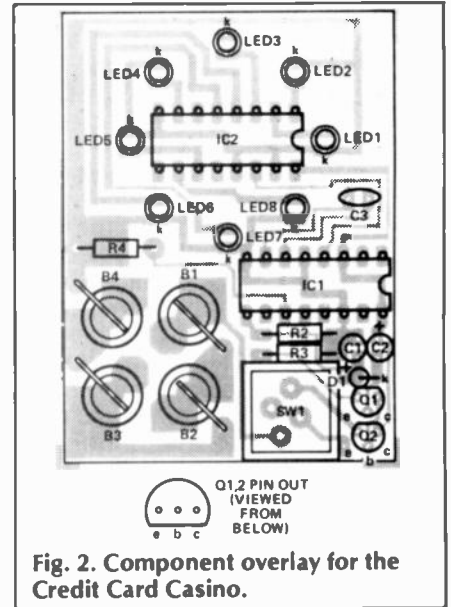


Fig. 2. Component overlay for the Credit Card Casino.

You'll also find that there are no screw holes. You'll have to drill the pillars (carefully!) with a  $5/64$ in drill, using the lid as a template to mark the drilling positions. Now screw the lid in place and gradually pare away the overhanging edges with a sharp knife. Don't use a file or sandpaper, or you'll scratch the sides of the case. It's best to take off the waste plastic a little at a time rather than trying to remove the entire depth with one cut — you'll have more control over the knife.

The final problem is that the PCB will no longer fit. You'll have to widen the case! After some

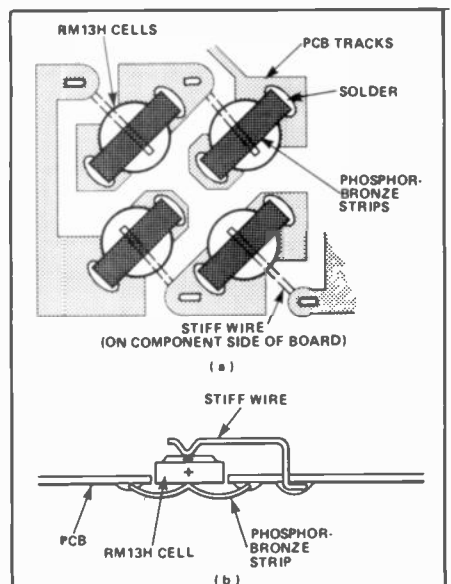


Fig. 3. Some hints on construction. (a) the position of the phosphor bronze strips and the wire for the battery contacts. (b) a side view showing the 'kink' in the phosphor bronze strip and the shape of the wire contact.

experiment, we found that the best way to do this is to use the edge of a file at 45° to the case wall — it takes off the plastic fairly quickly, but it's hard work! You can also file down the edges of the PCB slightly, but be careful not to cut into any of the tracks.

From now on, it's easy! Line the bottom of the case with a layer of 1/4in foam plastic, put the PCB against the front panel so that the switch and LEDs are in their respective holes, then bring the two halves of the case together. You'll probably find it easier to do this upside down — that is, hold the lid face downwards in the palm of one hand with the PCB above it, then lower the body of the case over the top. Then,

## PARTS LIST

### RESISTORS

R1	100R
R2	330k
R3	22k
R4	1M0

### CAPACITORS

C1, 2	10u 6.3V tant.
C3	100n any type. See text

### SEMICONDUCTORS

IC1	4046
IC1	4022

Q1	BC548L or equivalent
Q2	BC558L or equivalent
LED1 to 8	3mm LEDs, 4 red, 4 green.
D1	IN4148

### MISCELLANEOUS

Switch: push-to-make keyboard switch; four Duracell RM13H mercury cells; T3 plastic case (white), self-adhesive fascia; strips of phosphor-bronze; paper clip; printed circuit board.

holding the two halves of the case together, put it on your workbench and put in the screws. Finally, remove the backing from the fascia and stick it to the top of the case.

If you've had the patience and dedication to follow this through, you deserve a little relaxation, so we've put together some games you can play on the Credit Card Casino.

## Roulette

Short of tossing a coin, this must be one of the simplest gambling games in existence. Players bet on numbers or combinations of numbers by placing their betting slips in certain positions on the roulette table. A single spin of the wheel decides the winners and losers. The croupier collects any losing stakes, pays the winners, and the betting begins again ready for the next spin.

Figure 4 shows the layout of the roulette table, which you can make from a sheet of card, and the positions where stakes would be placed to bet on certain combinations of numbers. Table 1 lists the possible bets and the odds that should be paid on them in a fair casino (one with no advantage to the bank). It is conventional in gambling to state odds in terms of the winnings you receive. You also get your stake back again, so if you bet 5 at 7 to 1 you would get back eight pounds;

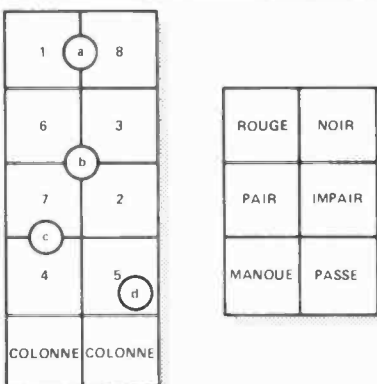


Fig. 4 The markings for the roulette table. Squares should be large enough so that bets can be placed without obscuring the numbers, and so that they can be placed on the border between squares without ambiguity. A *cheval* and *carre* bets only apply to the numbered section. You cannot, for example, place a bet on the border between *pair* and *manque*.

seven pounds winnings and the return of your £1 stake. Next time you put 10p into a fruit machine and get £2 out, you'll know not to say 'I won £2', but 'I won £1.90 and got my 10p stake back again!' The sum of your winnings and the stake money is known as your *returns* from the bet.

The top bet in Fig. 4 will win on either 1 or 8; it is a *cheval* bet and pays 3:1. The next bet down is a *carre* bet on the numbers, 2, 3, 6 and 7. It pays evens. Next comes another a *cheval* bet on 4 and 7, and finally an *en plein* bet on number 5, paying 7 to 1. If the wheel happened to stop on 7, bets 6 and 3 would win. The others would lose.

## Breaking The Bank At Monte Carlo

Every gambler has daydreams about inventing the perfect system to beat the roulette wheel. It's impossible, but then by the laws of aerodynamics a bumble bee can't fly, so just maybe ...

The best known and simplest system is just to double your bet each time you lose. This is how it works. Begin by betting £1 on black. If you win — great! Pocket the winnings and start again with £1 on black. If you lose, bet £2. If you win this time your total stake will have been £3 — £1 on the first go (which you lost) and £2 on the second.

The return will be £4 leaving you with £1 winnings. Start again with £1 on black.

Let's suppose you have some bad luck this time, and get four reds in succession before black comes up. Your total stake will have been £1 + £2 + £4 + £8 + £16 = £31. The returns from the fifth spin of the wheel when black eventually came up (on which you bet £16) will be £32 leaving you with £1 profit. As long as you double your bet each time you lose, you will *always* end up £1 ahead each time black comes up! As soon as it does, you go back to a bet of £1. If the wheel is spun once a minute, and black comes up 50% of the time on average, that makes your earnings £30 an hour! The presence of a zero (in a casino this is the house number: all the stakes go to the bank and nobody wins except the casino!) does not affect the results. You just double your bet as if the outcome had been red.

Of course, such systems have their disadvantages, otherwise casinos would be out of business overnight. With the credit card casino you can try out this system and any others you may dream up without risking your money. If you come up with something good and win a fortune, don't forget to take out a subscription to ETI. We may be able to suggest a few add-ons for your executive jet!

Bet	Meaning	Odds
En plein	Bet on a single number	7 to 1
A cheval	Bet on two adjacent numbers	3 to 1
Pair	Bet on any even number	evens
Impair	Bet on any odd number	evens
Passe	Bet on any number from 5 to 8	evens
Manque	Bet on any number from 1 to 4	evens
Rouge	Bet on any red number	evens
Noir	Bet on any black number	evens
Carre	Bet on any number in a square of 4	evens
Colonne	Bet on any number in a column	evens

Table 1: The types of bets allowed on the credit card casino. These are the same as for a standard roulette wheel, except that *Passe* would represent 19 to 36 and *manque* would be 1 to 18. The odds are different, of course.

## BUYLINES

The only item likely to cause any difficulty is the switch. This is a Preh 75120-008 low profile keyboard switch; you may have to phone a few computer hardware shops to locate a source. The UK distributors for Preh (pronounced 'pray') are Eardley Electronics Ltd, 182-4 Camden Hill Rd, London W8.

The phosphor bronze strip can be obtained from hardware shops. It is sold as draught excluder strip for door frames. As you will probably have to buy it in lengths of several yards, the rest can be used to draught-proof your front door!

The batteries for this project are sold by chemists as hearing aid batteries. The type is not important, but the cell diameter must be about 8mm to fit the

cut-out in the PCB. The cell voltage should be about 1.4V, but the circuit is not fussy about variations in voltage. If you are unable to obtain the specified RM13H, try others from watch or calculator shops. Take a ruler with you!

A complete set of parts for this project including PCB, case, self-adhesive fascia, phosphor bronze strips, and even a paper clip, is available from: Specialist Semiconductors, Founders House, Redbrook, Monmouth, Gwent. The price is £5.90 + 60p postage and packing. The self-adhesive fascia is available separately from the same source for 90p + a stamped, self-addressed envelope.

The PCB will be available from our Readers Services in due course.



## CREDIT CARD GAMES

### Casino Craps

One player is chosen to be the shooter — in this case, the person who presses the button on the Casino. He places his stake on the table, and all other players put down the same amount. The shooter presses the casino button, records the number that turns up, then presses the button again.

If the two numbers total 9 or 15, this is known as a 'natural' and the shooter immediately wins all the money on the table. If they total 2, 3 or 16, this is called 'craps'. The shooter immediately loses and the player on his left takes the casino and becomes the new shooter. If the shooter makes any number other than natural or craps, this number becomes his 'point'.

Now the game becomes a little more complicated. The shooter presses the casino button again and adds the resulting number to the outcome of the previous spin. If the result is a nine, he loses. If he makes his point again, he wins. If neither of these occur, he just keeps spinning until one or the other turns up.

To make this a little clearer Table 3 shows some winning and losing sequences of spins.

Sequence A: The shooter loses because his first two spins add up to three, which is craps.

Sequence B: The shooter wins because his first two spins total nine — a natural. Note that although his first spin is one of the craps numbers, he doesn't lose because it's the total of the first two spins that counts.

	A	B	C	D	E	F
1st spin	2	2	6	6	6	4
2nd spin	1	7	4	4	4	7
3rd spin	-	-	3	3	5	8
4th spin	-	-	2	6	-	3
5th spin	-	-	8	-	-	-

Table 2: Some winning and losing sequences in a game of Casino Craps. See text for explanation.

Sequence C: The first two spins add up to 10. This is neither a natural, nor craps, and so becomes the shooter's point. The fourth and fifth spins also add up to ten. The shooter has made his point and wins.

Sequence D: The shooter's point is again ten but his third and fourth spins add up to nine, which is the losing number.

Sequence E: The shooter loses for the same reason as above. The second and third spins add up to nine.

Sequence F: In this sequence, the shooter's point is 11 and the shooter wins through making his point on spins three and four. Note he does not win through making 15 on spins two and three. You can only have a natural on the first two spins. The other natural (nine) is a winner on the first two spins and a loser thereafter.

If the shooter loses, the casino passes to the player on his left. All stakes remain on the table and another round of betting must take place before the new shooter spins. For every loser, the total pool to be won increases!

### Knock

This is a game of nerves and judgement. Spin the casino and as soon as you think the light has finally come to rest, tap on the table. Anybody who knocks before the light comes to rest loses. The winner is the first person to knock when the light has stopped. This game is usually played for fun — very popular at children's parties! If you wish, it can be played for money. All players put in a fixed stake and the winner takes all.

### The Ultimate Game

A book published in 1972 describes how a disillusioned psychiatrist decided to hand over his entire life to the whim of the Casino. Whenever he had a decision to make, however trivial, he would write down a number of options and then spin the Casino to choose between them.

For some reason, the book refers to the Casino as a die, but we won't let that bother us — it was probably a Casino-inspired decision anyway!

We join the story at the point where our hero, Dr. Rhinehart, has just forged the signature of the director of a mental hospital to take a coach load of loonies to see the rock musical Hair, and has forgotten to bring them back again. Why? Because the Casino told him to, of course. He has admitted everything to the police (you guessed it — because the Casino told him to), but the interview with Inspector Putt is still not going quite the way the detective would wish.

*'Does it not occur to you, Inspector, that in telling you I forged Dr. Mann's signature I may be lying because the Die has told me to?'*

*'What —'*

*'That in fact my original statements of innocence may be the true ones?'*

*'What? What are you suggesting?'*

*'Simply that yesterday when I heard that you wished to question me again, I created three options for the Die to choose from: that I tell you I had nothing to do with the order to go to Hair; that I tell you that I initiated the excursion and forged the orders; and thirdly that I tell you I conspired with Eric Cannon to help him escape. The Die chose the second. But which is the truth seems to me to be still an open question.'*

*'But — What are you saying?'*

*'The Die told me to tell you that the Die told me to take the patients on an excursion to Hair'*

*'But is that story the truth?'* asked Inspector Putt, his face somewhat flushed.

Dr. Rhinehart shook a die onto the little coffee table in front of him. He examined the results.

*'Yes,'* he announced.

Full instructions on how to lead the dice-life, and its advantages when being questioned by the police, can be found in: 'The Dice Man', by Luke Rhinehart, published by Panther Books.

# TECH TIPS

## Auto Battery Charger

Andy Armstrong  
Leighton-Buzzard

This is a car battery charger which can be trusted to charge the battery faster than the standard four amps because it will switch to a low charge rate when the battery is almost fully charged. In addition, it is protected against damage if connected the wrong way round.

Assuming that the battery is connected the right way round, the sensing circuitry is energized via D2. If the battery voltage is below the preset end-of-charge point then the relay switches on and connects the battery directly to the rectified output of the transformer. Charging proceeds at maximum rate.

When the voltage of the battery rises sufficiently, the op-amp switches over and the relay is switched off. The relay will not switch just because the peak of the charging current takes the battery voltage up for a few milliseconds because R7 and C1 average it out. D3 protects C1 in case of reversed polarity.

The battery voltage will then fall to some extent, but the relay should not switch back on because there is about 1V of hysteresis applied to the op-amp (referred to the battery voltage). The voltage is unlikely to fall to this extent because it remains under charge, albeit at a lower rate.

If a 24W car bulb is used in place of R1, the lamp will start to glow

dimly once the relay has switched off. This will serve as a visible reminder that the battery is charged.

It is a wise precaution to switch on after connecting, and switch off before disconnecting the charger, to prevent sparks, and hence the possibility of explosion.

No particular transformer is specified, because constructors can choose what wattage to use. If a tractor or lorry battery is to be charged, then a high current rating is required.


A 50VA transformer would be the minimum useful size. This will not give a particularly fast charge rate. If more than 10A charging current is anticipated, a more substantial bridge rectifier will be required. Also, the relay contacts must be rated for the maximum rated current expected.

The circuitry shown here may, of course, be added to an old, standard-

type battery charger simply to prevent harmful overcharging, or to keep a battery topped up for occasional discharge cycles.

A good way to adjust the cut-off point of the circuit is to connect it to a car battery which is well charged. Adjust RV1 so that the relay switches on for two or three minutes. If the battery is well charged this should be long enough to raise the voltage to its maximum value, without being long enough to damage the battery. Then adjust RV1 so that the relay just switches off. The unit should now work perfectly.

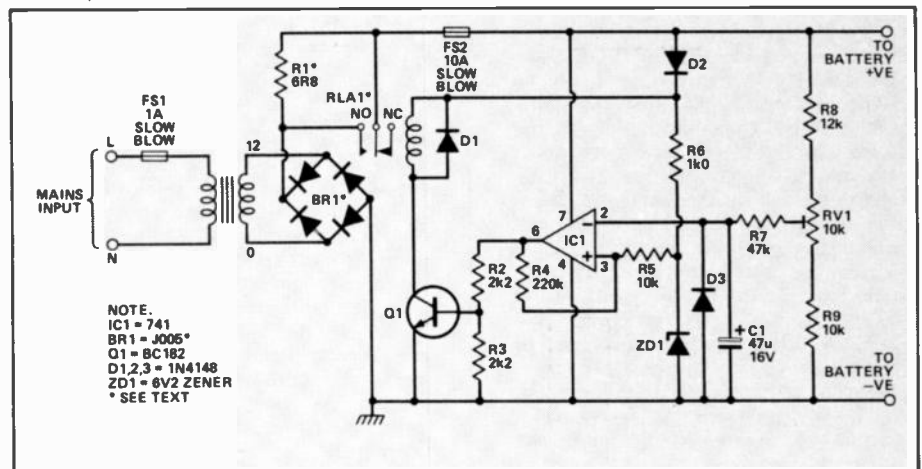If there is any problem with the relay switching back on when the battery is well charged, then the hysteresis can be increased slightly by lowering R4 to 180k or 150k. If it seems necessary to lower it further, suspect the battery of being below standard — maybe it has a high resistance cell.



## Versatile DRAM Interface For The 6502

Keith Howell  
Keele

This interface uses few chips yet is extremely adaptable. It has been tested on a 1MHz Acorn Atom with two 4416-150ns DRAMs without the 33R damping resistors, although these and adequate decoupling capacitors are recommended for fewest errors. I see no reason why it should not work with 6809 processors and with 4164 (1 x 64K) or 41254 (4 x 64K) DRAMs.

The timing diagram shows a single memory access cycle, with the 6502 requiring data valid on the falling edge of 02, the main timing signal.



The refresh row address is enabled in the first half of the cycle (02 high).

The timing signal is exclusive-ORed with a delayed version of itself to produce the Row Address Strobe (RAS) at twice the access rate. The first falling edge of RAS is used to latch in the refresh row address from the 8-bit counter, IC4, and the tristate buffer, IC5. The second falling edge of RAS latches in the CPU row address (A7-A0).

IC2b adds one TTL gate delay to RAS, producing ROW/COL. This signal allows 20ns for the row address to be latched before selecting the CPU column address. IC3b is enabled by ROW/COL low. Input B1 disables the output if 02 is low which prevents a memory access during refresh. Input A1 can be used by a separate device to disable access at


any other time and provide its own data to any memory address. For instance, a boot EPROM can be switched in if its chip select, CS, is tied to dRAMDIS at A1. This will prevent bus contention.

IC1a inverts 02 for the tristate address multiplexers, IC6 and 7. It also drives an RC delay network before IC1b is used to square up the waveform. Because the TTL schmitt trigger thresholds aren't symmetrical about 2.5V, RV2 and D1 have been added to the basic network, RV1 and C1, to give equal delays to rising and falling edges. After trying to calculate values for the delay resistors and finding they didn't work, I gave up and used a couple of presets. If an oscilloscope is unavailable for setting-up, adjusting the presets to the middle of the error-free range should do just as well.

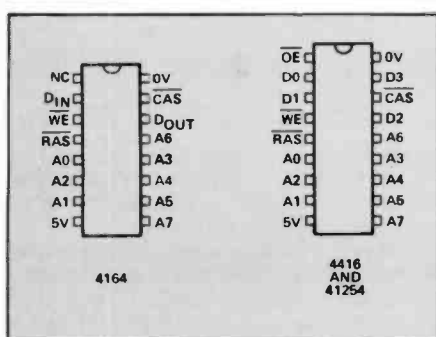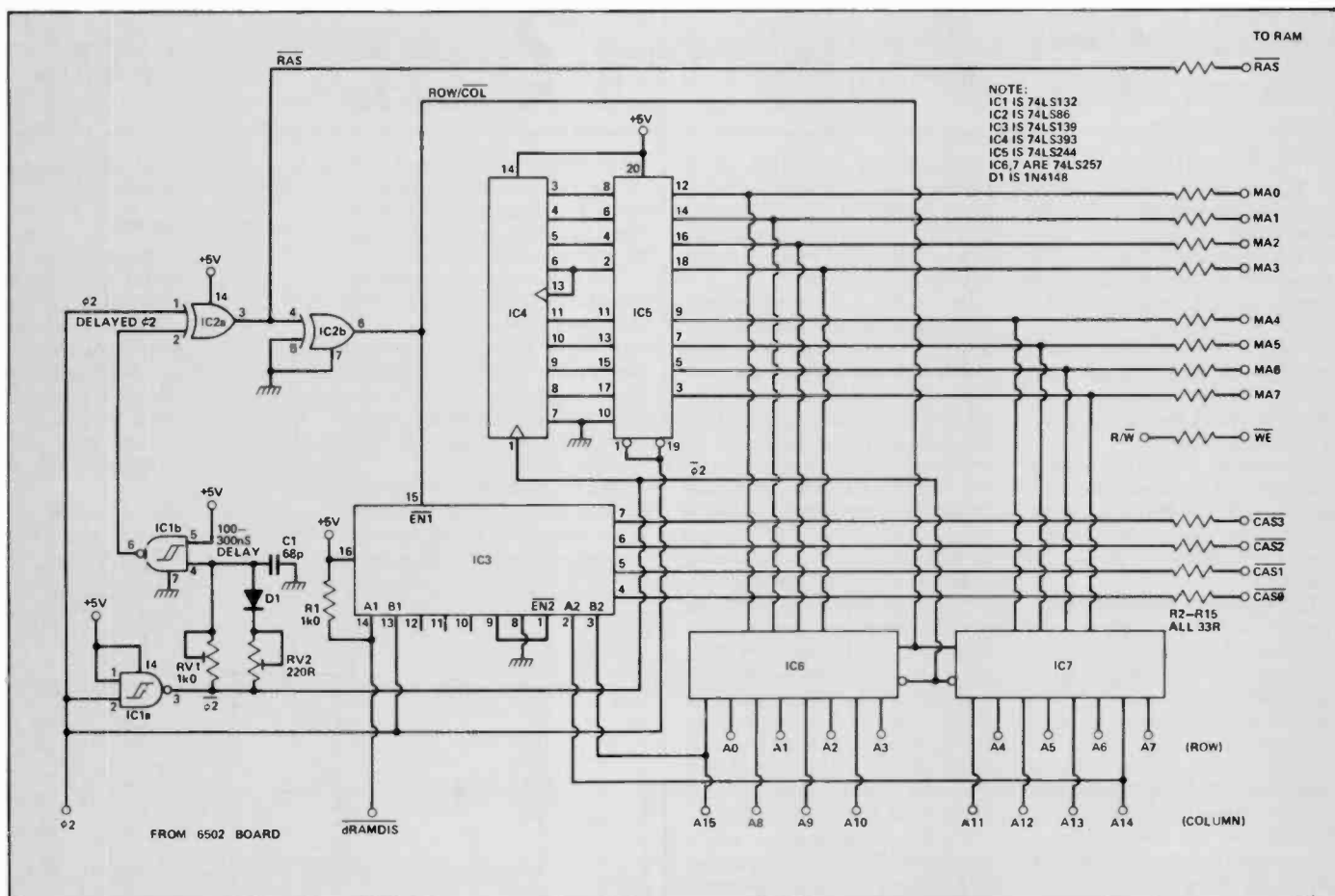


Conventional wisdom says 6502 address lines aren't guaranteed valid until 200ns after the rising edge of φ2. If so, RAS ought not go low until after 200ns. In practice, RAS high times as short as 90ns seem to work.

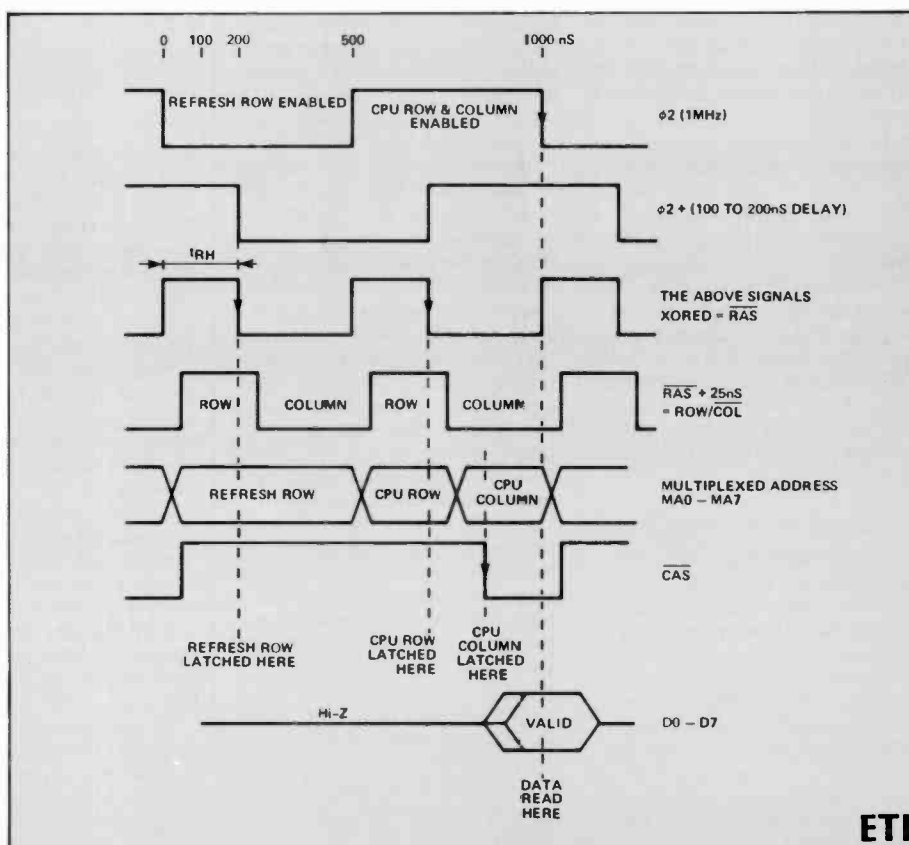A 2MHz clock would allow 500ns for two DRAM cycles. The data sheet for 150ns DRAMs quotes a minimum cycle time of 256ns. The method I have used should not, therefore, work at 2MHz since there is not enough time between CPU accesses to allow refresh. In practice the DRAM may be fast enough for the method to work. Most memories are actually tested at twice their nominal speed.



## OPEN CHANNEL

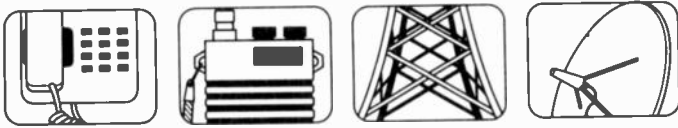

The old Band III 405-line television band, recently re-designated as a mobile radio band, is in the news at the moment. Prospective operators of mobile radio services in the band can't seem to agree on specification to be used.

GEC is proposing a system known as *full off-air call set-up* in which the speech channel is not taken up until the call is completely connected.

Compared with the nearest existing comparative service — cellular radio — this is an enormous benefit to a mobile radio system with a limited number of channels.

Call set-up on the cellular radio system can take anything up to 20 or 30 seconds, and a channel is used throughout this period. In congested areas that means there is one less channel for communications purposes.

GEC is one of two national operators of Band III mobile radio systems. The other national operator, headed by Pye and Racal, does not intend to introduce full off-air call set-up.

This difference wouldn't make equipment on the two services completely incompatible. A GEC mobile phone could be used on lower spec systems, but not vice versa.

Elsewhere on the system, regional operator National Radiofone is joining forces with British Telecom and Motorola to form a company called National Mobile Radio.

It's interesting to note that when applications were first invited for Band III operators last year, the Department of Trade and Industry refused permission for BT to even apply. Also, Motorola had its application turned down by the DTI. If at first you can't succeed ...

### Illegal Cordless Telephones

A large number of the cordless telephones available (those phones which you carry around the house or garden with you so that you can make or take calls without having to return to a fixed point) are actually illegal to use.

Illogically, they are not illegal to import and sell. If you are contemplating buying one soon, you would be wise to ensure that the model of your choice is not in this category.

The general use and operation of illegal and legal types are identical. So what is the difference and why would you want to buy one of the illegal models rather than a legal version?

In terms of user-advantages, legal cordless phones have a typical range of no more than about 100 metres or so, depending on the local environment. The illegal units on the other hand are capable of a range of miles — up to 20 miles or so, depending on the model. To actually obtain distances of this range you might need to mount a loft or roof-top aerial instead of the small aerial supplied with the base station.

This extra distance will obviously make the illegal phones more attractive to potential users. After all, if you stayed within the law and wanted to have a portable phone with such a great range you would need to have a cellular radio phone — at around five times the cost to buy and around three times the call charge rate.

It's the extra distance which these illegal cordless telephones give the user over the legal types which causes the problems. Such high powers of transmissions may cause interference to emergency service transmissions (police, ambulances, fire services, etc). Secondly, the high powers could interfere with legal models.


The situation has deteriorated to the extent that the Department of Trade and Industry is currently in the process of producing legislation against the import and sale of illegal cordless telephones, but there are still a large number of them in service.

If you are worried that your cordless phone is an illegal type, check to make sure it has one of the 'green circle' BT approval labels. If not, or if it has a 'red triangle' unapproved label, don't touch it with a bargepole!

If nothing else, sale of these telephones has highlighted the need for a legal service to do the same job. Opponents of such a legal service use the argument that there is not enough free radio spectrum available. To them I point out my previous story, above and the new part of the radio spectrum which is being re-allocated. Shouldn't we be making a move to use part of this to provide the service?

Keith Brindley

## ALF'S PUZZLE

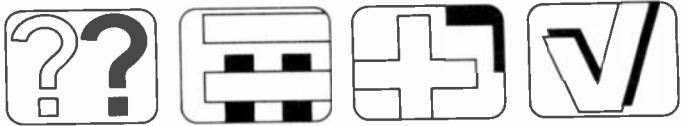

This month Alf has been buying packs of unmarked, untested, unwanted and unloved components. He is very proud of the test rig he built to check out the triacs.

Triacs are basically bi-directional SCRs. They provide a high resistance until a trigger pulse is received at the gate when they can conduct in either direction. Once triggered, a triac will continue to conduct until the current through it is reduced to less than a 'holding' current.

Alf's triacs could be fitted into his test rig and using the patch there something wrong with his


test rig? Will Alf discover the answer by next month?

### January's Answer

The January puzzle was inspired by a circuit in a certain magazine, which shall remain nameless to spare their blushes and to avoid writs for libel!

The author admitted his chosen op-amp only had a gain of  $10^5$  but he claimed that by using the resistor values shown he could force it to have a gain of  $10^8$ !

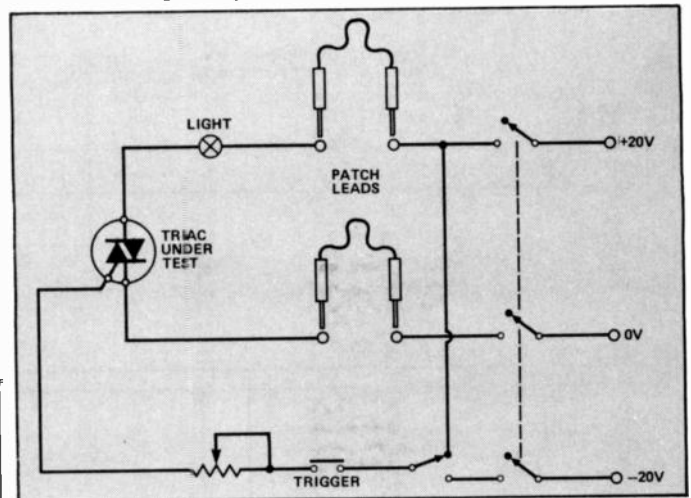By the same reasoning, we could force a piece of wire, which



leads conduction in either direction could be checked. The trigger push button switch provides the trigger pulse and the two way switch enables either positive or negative pulses to be applied to the triac gate. The gate current could be adjusted using the potentiometer.

Alf plugged the first triac into the test socket, taking care to follow the pinout given in his data book, and turned on the power. The light came on immediately, showing the triac was conducting, before he had even thought about pressing the trigger button. 'Short circuit,' said Alf to nobody in particular, and dropped the faulty triac into the bin.

With the next triac, exactly the same thing happened. 'Oh well,' said Alf, 'You've got to expect a few duds.'

By the time the twenty-third triac had failed, Alf was beginning to get a little worried. On the fifty-ninth failure he was certain something was wrong — but what?

Were all Alf's triacs faulty? Is

has an open-loop gain of 1, to have a gain of 1000 simply by connecting suitable feedback resistors across it.

Just think: an amplifier consisting only of wire and resistors!

The answer is that the usual formula for determining the gain of an amplifier with feedback resistors is just a rule of thumb.

It is a very accurate rule of thumb when the closed-loop gain is a small fraction of the open-loop gain, but becomes increasingly inaccurate as the closed loop gain is increased.


Eventually, when the closed loop gain aimed for is comparable with the open loop gain of the amplifier, it becomes a complete nonsense.

This is why Alf's teacher at the evening classes said an op-amp's gain should be as high as possible, to make the feedback formula meaningful (when it is used in the normal way).

Alf's circuit will, in fact, have a marginally worse performance than the unmodified circuit.



## PLAYBACK

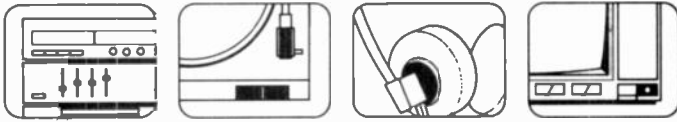


The realism of stereo reproduction from records, tapes and radio is something all hi-fi users now take for granted. Until now, the same effect with TV has only been achievable by simultaneous broadcasts on stereo radio. Soon though, stereo sound on TV looks like becoming a reality.

Both BBC and ITV have agreed on a system called 'Nicom 728' (Near Instantaneous Companion). This augurs well as rivalry between the two organisations has in the past delayed the acceptance of either of their respective technical offerings until they

both sound and vision reproduction is said to be poor as a result.

So what is special about Nicom 728? The main thing is it encodes the signals digitally, eliminating noise, fading, distortion and other transmission ills. This permits another ploy. The existing mono sound signal remains unchanged, spaced at 6 MHz higher than the vision signal, while the additional digital stereo carrier is spaced 0.552 MHz above mono sound.

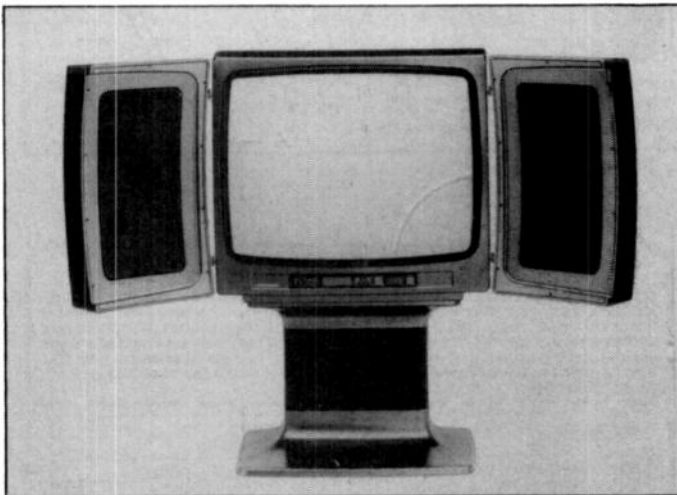The mono sound transmitted power level is one fifth (-7 dB) that of peak vision, but the digital stereo carrier will be -10 dB or



could be thoroughly tested against each other.

However, the Nicom system has been field tested. Transmissions from Weirhoe and Crystal Palace have proved very encouraging. As a result, the system has been approved by the Government and it is expected transmissions could start as early as 1988. Of course we have all heard these over-optimistic predictions before, but the nearness of this one does suggest some certainty.

Other countries have got in first. However, as with colour TV systems, they might live to regret it. Canada is using the 'MTS' system developed by Zenith. This is similar to the ordinary FM stereo radio signal except it is DBX encoded. There are reports of problems such as mono being received from supposedly stereo programmes and some stations using a stereo synthesizer instead of genuine stereo material.

Germany has been transmitting stereo with the 'Zweiton' system for the last two years but

one tenth, half that of the normal mono signal. This low level greatly reduces the possibility of interference or intermodulation with either vision or mono sound carriers, which has been a problem with other systems.

This lowered level is only possible by using a digital signal.

Technically it looks like the UK will have a much superior system to that used elsewhere. It's only a pity it couldn't have been made a world standard.

It is the aesthetic side of the stereo TV that will have to be watched. The present combination of stereo radio and TV throws up many anomalies. When there is a close up shot of an instrument the sound remains the same. So the visual image is probably well to one side of the sound. Should the stereo balance be altered or should close-ups be avoided?

Come to that, as the TV screen width is so small, does stereo image really matter? If not, then why have stereo at all?

Vivian Capel

## BIRD'S EYE VIEW



For some years now my magazine diet has consisted mainly of high protein, low fat trade mags. It was therefore with great interest that I read through the parcel of ETI back issues, kindly supplied by the Editor in preparation for this column.

My first impression was that the standard of features and circuits is generally very high (with a few unfortunate exceptions).

Apart from the lighter approach and the obvious bias towards what is interesting rather than what is necessarily commercially viable, the main difference between ETI and my usual fare can be summed up as: lack of engineering content.

### Engineering

The term 'engineering' is not easy to define. I'll try to clarify what I mean by way of an example. If you take any logic circuit from the pages of ETI (you choose!), the chances are you will find little in it that is essentially 'electronic'.

That is to say, exactly the same result could be achieved by interpreting each IC box in the circuit diagram as an equivalent hydraulic component and each line as a pipe rather than a conductor.

If this sounds unlikely, you have only to remember that any logic system whatsoever can be constructed entirely from NOR gates (although you'll need an awful lot of them to make a microprocessor!)

So, as long as it is possible to make a hydraulic NOR gate (and it is), it is also possible to imitate any electronic logic circuit with hydraulics.

Indeed 'fluidics', as this science is called, is well developed and hydraulic control systems are in use in environments hostile to conventional electronics, such as nuclear power stations.

Naturally there are differences between electronic and fluidic circuits. The electronic implementations are much faster, smaller and usually cheaper, which is the very reason that electronics is used. However, that does not alter the fact that the underlying logical structure is not essentially 'electronic'.

### Lego

This joining together of functional blocks to make a circuit I

call the 'lego' aspect of the design (with a small 'l' to distinguish it from the manufacturer of toy bricks).

This aspect of design is by no means confined to digital circuits. It is quite feasible to cobble together analogue circuits from standard building blocks such as amplifiers, filters and the like. The only difference is that the analogue blocks themselves usually consist of a number of components rather than just a single IC.

Engineering (I've got around to it at last!) is any consideration which goes beyond the functional block approach. It's what makes electronics electronics rather than fluidics.

### Good, Bad and Ugly

If a designer uses a BCD counter and a BCD to one-of-ten decoder where a Johnson counter would do, then that is bad lego. However, if he exceeds the fan-out of a logic gate or builds a VHF radio on Veroboard, that is bad engineering.

The ratio of lego to engineering in ETI (and other similar but unmentionable magazines) varies widely from circuit to circuit. I think it is fair to say that most ETI logic circuits are lego designs — the engineering content is minimal and incidental.

This is in no way to disparage the authors. Some very fine and beautiful structures can be built with lego.


Designing with lego has its own problems, the solutions to which can be elegant or clumsy depending on the skill of the designer. My point is that, admirable though these skills may be, they are not electronics skills.

The means and results of taking logic design beyond the lego stage are being covered by Mike Barwise's excellent series and I have no wish to encroach on his territory here.

Some ETI circuits do have a substantial engineering content. Most of the audio amplifier designs, for instance. Whether or not they embody good engineering principles is an entirely different kettle of pirhanas, and one which I will look into another day.

John Bird

# FROM JAYTEE

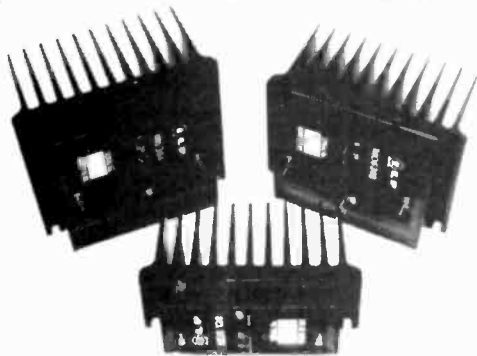

## THE SPECIAL DISTRIBUTOR FOR SPECIAL AMPLIFIERS

ILP have long been recognised as manufacturers of top quality amplifiers.

All ILP products are built to extremely high specification for the ultimate in hi-fi performance. They're unique in being completely encapsulated with integral heatsinks, and can bolt straight onto the chassis. They're also extremely robust, ensuring high levels of reliability as well as performance.

ILP Amplifiers are now available through Jaytee. The UK Distributor with the availability and service to match the quality of the amplifiers.

### POWER BOOSTER AMPLIFIERS

The C15 and C1515 are power booster amplifiers designed to increase the output of your existing car radio or cassette player to 15 watt rms.

C15 ..... 15 watts ..... £10.65  
C1515 ..... 15 + 15 watts ..... £19.78

### ILP LOUDSPEAKER

power ..... 350 watt rms  
size ..... 12 inches  
impedance ..... 8 ohms  
range ..... 20 Hz to 5 KHz

**NEW £78.61**

FOR FREE DATA PACK PLEASE  
WRITE TO OUR SALES DEPT.

### PREAMPLIFIER MODULES

All modules are supplied with in line connectors but require potentiometers, switches, etc. If used with our power amps they are powered from the appropriate Power Supply.

Type	Application	Functions	Price
HY6	Mono Pre Amp	Full Hi Fi facilities	£8.95
HY66	Stereo Pre-Amp	Full Hi Fi facilities	£14.55
HY73	Guitar Pre-Amp	Two Guitars plus Microphone	£14.95
HY78	Stereo Pre-Amp	As HY66 less tone controls	£14.25

NEW! HY83 Guitar and Special Effects Pre-Amp as HY 73 Plus Overdrive and Reverb £18.95

MOUNTING BOARDS: For ease of construction we recommend the B6 for HY6 £0.95. B66 for HY66-83 £1.45.

### MOSFET MODULES

Ideal for Disco's, public address and applications with complex loads (line transformers etc.). Integral Heatsink slow rate 20v/μs distortion less than 0.01%.

Type	Output Power Watts (rms)	Load Impedance Ω	Price
MOS128	60	4 8	£35.95
MOS248	120	4 8	£42.25
MOS364	180	4	£67.45

### BIPOLAR MODULES

Ideal for Hi Fi. Full load protection integral Heatsink, slew rate 15v/μs

Type	Output Power Watts (rms)	Load Impedance Ω	Price
HY30	15	4 8	£10.95
HY60	30	4 8	£10.95
HY6060	30 + 30	4 8	£22.95
HY124	60	4	£17.95
HY128	60	8	£17.95
HY244	120	4	£23.45
HY248	120	8	£23.45
HY364	180	4	£34.95
HY368	180	8	£36.45

Distortion less than 0.01%

### POWER SUPPLY UNIT

Type	For Use With	Price
PSU30	PRE AMP	£9.45
PSU121	1 or 2 HY30	£17.20
PSU412	1 or 2 HY60, 1 HY6060, 1 HY124	£19.35
PSU422	1 HY128	£21.35
PSU432	1 MOS128	£22.35
PSU512	2 HY128, 1 HY244	£23.70
PSU522	2 HY124	£23.70
PSU532	2 MOS128	£24.65
PSU542	1 HY248	£24.65
PSU552	1 MOS248	£26.65
PSU712	2 HY244	£28.35
PSU722	2 HY248	£29.30
PSU732	1 HY364	£29.30
PSU742	1 HY368	£31.25
PSU752	2 MOS248, MOS364	£31.25

All the above are for 240v operation



Jaytee Electronic Services, 143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL Telephone: (0227) 375254  
All Prices include VAT, Post & Packing

# LIGHTING

## THEATRE — BAND — DISCO — CLUB

At MJL we supply a range of stage lighting equipment within everyones budget. With world wide sales we have the backing and expertise to deliver just the system you need to 'Light Up' that Play, Gig or Dance Floor, from Basic 6 channel dimming to 30 channel rock mixing desks. So if you are a lighting engineer, stage manager or rig technician, or simply an amateur Drama group, we're the Professionals.

## FOR FREE COLOUR BROCHURES

Write to:

**MJL (International) LTD.**  
45 Wortley Rd., W. Croydon,  
Surrey, U.K. CR0 3EB

or Phone:

**01-689 4138**

## MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only)

Electronics	<input type="checkbox"/>	Radio, Audio and TV Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds)	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCE over 40 'O' and 'A' level subjects			<input type="checkbox"/>

**ICS** Name \_\_\_\_\_ P. Code \_\_\_\_\_  
Address \_\_\_\_\_  
International Correspondence Schools, 312/314 High St., Sutton,  
Surrey SM1 1PR. Tel: 01-643 9568 or 041-221 2926 (24 hrs) Dept EBS 37

## RACK STYLE CABINET

\* Suitable for instruments, high quality amplifiers and many other purposes \* Black anodised aluminium front panel enhanced with two handles \* Aluminium version, wholly made of black anodised aluminium sheets \* Metal version, rear box is manufactured from steel painted in black with aluminium front panel \* Rack mount or free standing. Customer who requires further details, please send S.A.E.

Panel Size W H (Inch)	Rear Box W H D	Price Steel	AL
19x2.5	17x2x10	22.50	27.50
19x3.5	17x3x10	24.50	29.50
19x5.25	17x5x10	26.50	—
19x3.5	17x3x12	25.50	30.50
19x5.25	17x5x12	27.50	32.50
19x5.75	17x5.5x12	—	33.50
* 17x3.5	15.5x3x9	17.00	—
* 19x3.0	17x2.5x10	—	20.50
* 19x7.0	17x6.5x12	29.95	—




\* Discontinued sizes, special price valid while stock lasts. Please add £3.00 P/P for the first item and £1.50 for each additional item. Quantity discount available. A limited quantity of electronic kits at give away prices. SAE for details. Overseas orders welcome.  
Mail order only. To order send cheque/postal order, please allow up to 7 days despatch for cheque clearance.

**T J A DEVELOPMENTS**  
53 Hartington Road, London E17 8AS.


---

---


# PCB FOIL PATTERNS

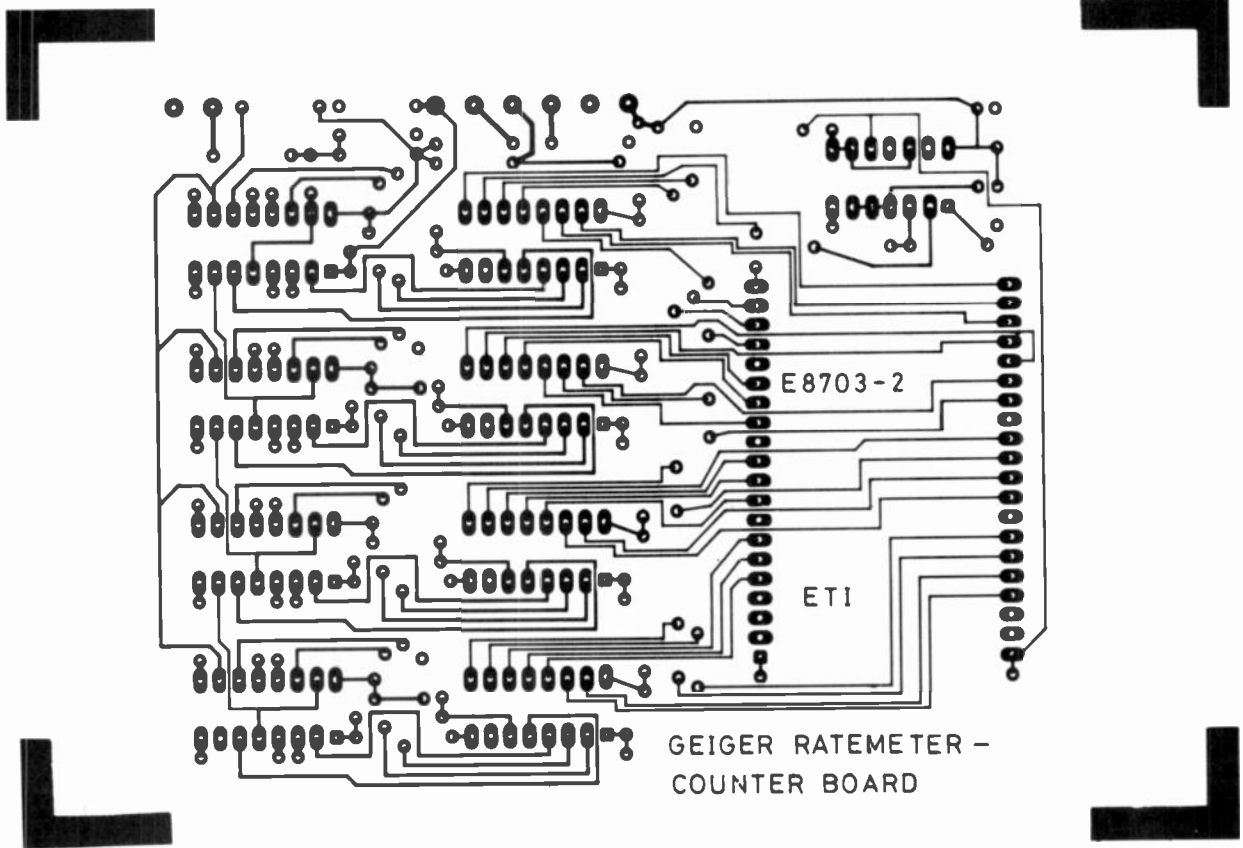


The Geiger Rate meter counter board.

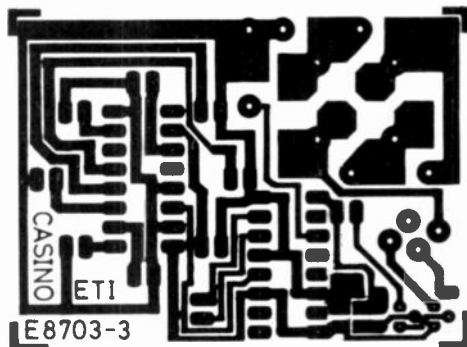

The Casino board foil pattern.

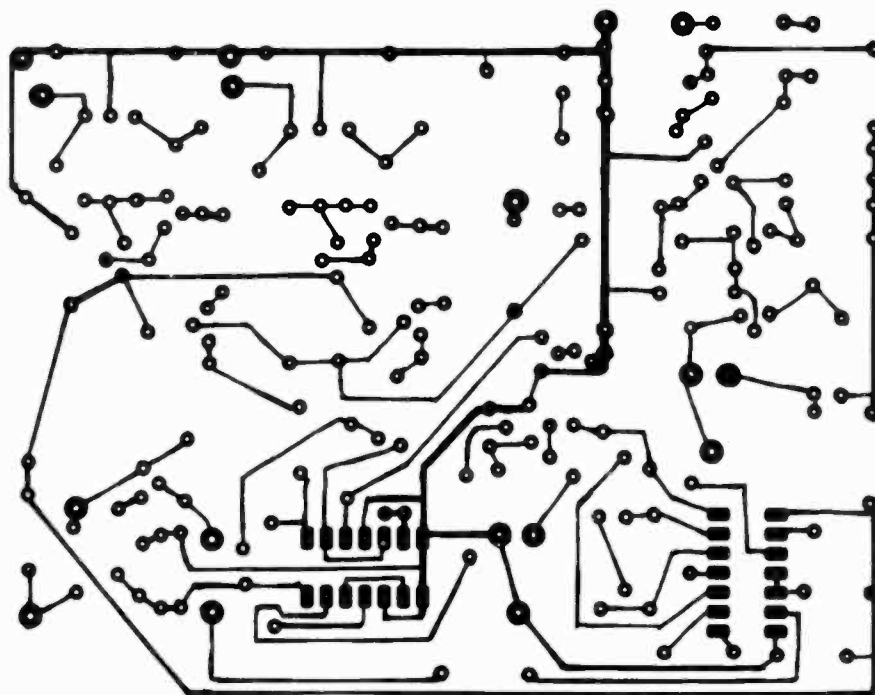

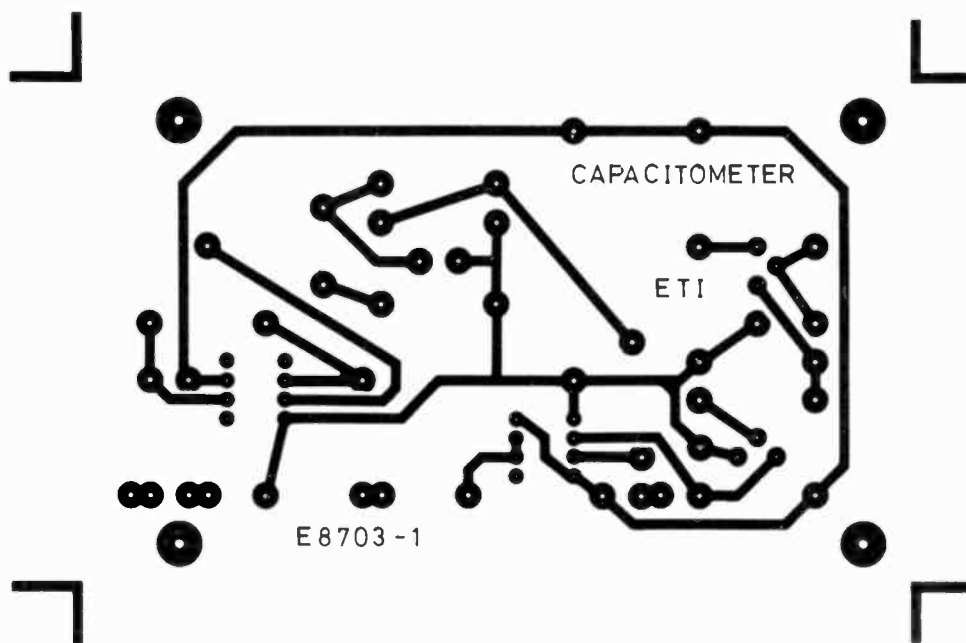The foil pattern for the Stereo Decoder Board, held over from last month.



The foil pattern for the Capacitometer board.

# FREE READERS' ADS

Buy, sell or exchange through our free service to readers

**FLOURESCENT DISPLAY.** Four half inch digits (ITRON FG413D1) data offers £3+ Adrian Bhagat, 10 Meynell Walk, Peterborough PE3 6RR.

**WANTED: CIRCUITS** for pre/post gain guitar preamps. Valve or transistor or ICs. Phone (0827) 53424.

**WANTED CIRCUIT DIAGRAM** for Superfone CT-505. Please contact: Mr Brabrook, 38 Orchard Park, Laugharne, Carmarthen, Dyfed, West Wales.

**CITIZEN MINIATURE DOT-MATRIX PRINTER MECHANISM.** £42. SAE for full practical details. Alan Lee, 8 Compton Rise, Pinner, HA5 5HR. 01-866 4579.

For Sale: **ZX SPECTRUM:** keyboard, interfaces, microdrive, printer, books, software. The lot for £150. 01-278 4013.

**MAGS:** ETI and PE. 1973-1983. Good condition. Offers? R. Houston, 6 East Cres., Snyed Green, Stoke-on-Trent. (0782) 268769.

**SPECTRUM 48K** application or design software wanted by student (Pascal?). Buy/swap original games. 051-527 5276, evenings.

**UNUSED ELECTRONIC COMPONENTS.** Including transformers and plastic drawers. £200. Phone (0604) 68515.

**QL DISC** interface. Centronics port, 256k RAM, RAM Disk, software. £80.00 Money back etc. (060684) 5703.

Clearing quantity parts: test gear, valve radios, amps, gramophones etc. List: SAE to Mr. Bisher, 37 Merchiston Avenue, Edinburgh EH10 4PD.

**BBC 6502 SECOND PROCESSOR.** Unused. Disc Doctor, Printmaster, Revs, Aviator, Chess, Genealogy, etc. cheap. (040 927) 370.

**HITACHI MOTEL V-209 OSCILLOSCOPE.** Portable mains/battery. 20MHz dual trace with manual, probes. VGC. £150. 01-890 3304.

**ETI240.** T1 and feed back winding. Published data faulty. Assitance rewarded. Pensioner Torquay 212091.

4116 200ns, 40p or £25 for 80. Chris Raynor (0539) 87225.

**ILP 400** amplifier modules. New, still in original boxes. £25 each. Tel: (0626) 890085.

**Mixed box** of components and PSU kit. £40 ONO the lot. Tel: 01-677 1475 (evenings).

**Avometer.** DA116 Digital Multimeter. Very good condition. Complete. £70 ONO. Tel: (0785) 643784.

**WANTED:** Audio Design handbook by H.A. Hartley. Tel: Leamington (0926) 315580.

**SELLING UP!** TV test equipment. Dual scope, digital meter, books, stacks. Lot sale only. 01-359 8623.

**GOLFBALL PRINTER.** IBM 3982 complete with details of interface. Dozens of different type-faces possible. £75 ONO. 01-421 2181.

## CONDITIONS

- These ads are only for readers not engaged in buying or selling the same equipment or services on a commercial basis.
- Ads will be inserted as and when space is available. Insertion in a particular issue cannot be guaranteed.
- Ads should be of 20 words or less and in block capitals or typed. Words to appear in bold should be underlined.
- Advertisers should fill in their name, address, and telephone number and sign the form to indicate acceptance of these conditions. Adverts can be on the printed form or a photocopy of it but they must be accompanied by the token at the top of this page.
- ETI reserves the right to refuse or to alter submitted ads wherever this is judged necessary.
- Ads are accepted in good faith. Neither the magazine nor its publishers can be held responsible for any errors in the reproduction of an ad, nor for untruths or misrepresentations, nor for the activities of advertisers or respondents. By acceptance of these conditions the advertisers undertake to indemnify the publisher against any legal action arising from publication of their advertisement.

Enter your advertisement below


Name .....

Address .....

.....

Telephone .....

I accept the conditions set out here.

Signed .....

Send this form to:

**Free Readers' Ads  
Electronics Today International  
1 Golden Square  
London W1R 3AB.**

# ETI PCB SERVICE

Build your projects in style with a properly designed PCB.

Use the form below (or a photocopy) for your order. Please fill in all parts of the form.

The board reference number tells you when the PCB foil was published. The first two numbers are the year and the next two the month. The number after the dash indicates the particular project in that issue.

The terms are strictly cash with order. Make cheques payable to ASP Ltd. We cannot accept official orders but we can supply a proforma invoice if required. Such an order will not be processed until payment is received.

Orders can also be made by telephone on (0442) 211 882 for Access and Visa card holders.

Please allow 28 days for delivery.

Price Code	Price (inc VAT) £
C	1.80
D	2.50
E	3.23
F	4.00
G	4.75
H	5.50
J	6.62
K	7.20
L	8.80
M	10.60
N	13.10
O	15.80
P	17.90
Q	21.80
R	23.90
S	25.90
T	29.00
U	32.20
V	35.80
W	37.90
X	40.70

- E8107-1 System A Disc Input bd MC-MM ..... F
- E8107-2 System A Preamplifier Main ... K
- E8108-1 System A Power Amp ..... L
- E8109-2 System A PSU ..... F
- E8201-2 Infant Guard ..... C
- E8202-5 MM Stage Disc Preamp (Tilsbrook) ..... G
- E8206-5 Logic Lock ..... F
- E8208-1 Playmate Practice Amp 3bds SA1 ..... K
- E8212-1 ELCB ..... F
- E8301-2 Analogue to digital conv (ZX81/Spectrum) ..... E
- E8305-3 Dual Audio Power Supply, Linsley Hood ..... G
- E8305-5 Balanced Input Preamplifier ..... F
- E8307-2 Flash Trigger-sound or FR ..... F
- E8308-1 Graphic Equaliser 1/2 Oct/Chnl ..... M
- E8308-2 Servo Fail-safe ..... C
- E8309-1 NICAD Charger/Regenerator ..... F
- E8310-3 Typewriter Interface - EX42 ... F
- E8311-1 Mini Drum Synth ..... F
- E8311-8 Moving Coil Pre-Preamp ..... F
- E8312-3 Light Chaser EPROM Controlled (2 Boards) ..... K
- E8402-1 Speech Board ..... M
- E8402-2 Modular Pre-amp Disc Input Mono ..... F
- E8402-3 Modular Pre-amp Stereo Output ..... F
- E8402-4 Modular Pre-amp Relay, PSU ..... F
- E8402-5 Modular Pre-amp Tone Main Mono ..... F
- E8402-6 Modular Pre-amp Tone Filter, Stereo ..... F
- E8402-7 Modular Pre-amp Balanced Output ..... F
- E8402-8 Modular Pre-amp Headphone Amp ..... F
- E8404-2 Mains Remote control Receiver ..... F
- E8405-1 Auto Light Switch ..... F
- E8405-2 ZX81 EPROM Programmer ... N
- E8405-3 Mains Remote Control Transmitter ..... H
- E8405-4 Centronics Interface ..... F
- E8405-6 Drum Synth ..... F
- E8406-1 Oric EPROM Board ..... O
- E8406-2 Spectrum Joystick ..... E
- E8406-3 Audio Design RIAA Stage ... G
- E8406-4 AD Buffer/Filter/Tone ..... H
- E8406-5 AD Headphone Amp ..... F
- E8406-6 AD Preamp PSU ..... K
- E8406-7 AD Power Amp ..... H
- E8406-8 AD Power Amp PSU ..... J
- E8406-9 AD Stereo Power Meter ..... F
- E8406-10 AD Input Clamp ..... C
- E8407-1 Warlock Alarm ..... M
- E8408-2 EPROM Emulator ..... N
- E8408-3 Infrared Alarm Transmitter ... E
- E8408-4 Infrared Alarm Receiver ..... F
- E8409-1 EX42 Keyboard Interface ... F
- E8409-2 Banshee Siren Unit ..... F
- E8410-1 Echo Unit ..... F

TO: ETI READERS' SERVICES DEPARTMENT  
Argus Specialist Publications Ltd,  
9 Hall Road, Hemel Hempstead,  
Herts HP2 7BH

Please supply:

No. required per type	Board reference number	Price letter	Price each £	Total for board type £
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p

POSTAGE & PACKING £ 0.75p  
TOTAL ENCLOSED £ . p

ORDER TO BE SENT TO: (BLOCK CAPS PLEASE)

Name .....

Address .....


Postcode .....

(Make cheques payable to ASP Ltd)  
ACCESS and VISA credit card orders can be taken on 0442 211 882 (office hours only).



E8410-2	Digital Cassette Deck	N
E8410-3	Disco Party Strobe	H
E8411-5	Video Vandal (3boards)	N
E8411-6	Temperature Controller	D
E8411-7	Mains Failure Alarm	D
E8411-8	Knite Light	D
E8411-9	Stage Lighting Interface	F
E8411-10	Perpetual Pendulum	E
E8412-1	Spectrum Centronics Interface	F
E8412-4	Active - 8 Protection Unit	F
E8412-5	Active - 8 Crossover	F
E8412-6	Active - 8 LF EQ	F
E8412-7	Active - 8 Equaliser	F
E8501-3	Digital Delay (2 boards)	T
E8502-1	Digital Delay Expander	N
E8502-2	Data Logger	J
E8503-1	Combo Preamplifier	F
E8503-2	THD Meter mV & oscillator bds (2 boards)	K
E8503-3	THD Meter Mains PSU	F
E8504-1	Framestore Memory	M
E8504-3	Framestore Control	N
E8504-4	Buzby Meter	E
E8504-5	CCD Delay	F
E8505-5	Stereo Simulator	F
E8506-1	Audio Mixer Main	J
E8506-2	Audio Mixer PSU	F
E8506-3	Audio Mixer RIAA	D
E8506-4	Audio Mixer Tone Control	D
E8506-5	EPROM Prog MKII	O
E8508-1	RCL Bridge	N
E8508-2	EX42/BBC Interface	E
E8508-3	EPROM Emulator	L
E8509-1	Spectrum	F
E8509-2	Direct Injection Box	E
E8510-9	Sunrise Light Brightener	K
E8511-1	MTE Waveform Generator	H
E8511-2	Milli'aradometer	H
E8511-3	Cymbal Synth	J
E8511-5	Chorus Effect	H
E8511-7	Enlarger Exposure Meter	F
E8511-8	Switching Regulator	E
E8511-9	Seccd Line of Defence	M
E8512-1	Specdram connector	F
E8512-2	MTE Pulse Generator	H
E8511-3	Specdram	L
E8601-2	Walkmate	L
E8601-3	MTE Counter-timer	M
E8602-1	Digi'baro	O
E8603-2	Programmable Logic Evaluation Board	H
E8603-3	Sound Sampler Analogue Board	R
E8604-1	JLLH PA PSU	H
E8604-2	Matchbox Amplifier	C
E8604-3	Matchbox Amp Bridging Version	C
E8604-4	MTE Analogue/Digital Probe	M
E8605-1	Microlight Intercom	E
E8605-2	Baud Rate Converter	M
E8605-3	Baud Rate Converter PSU Board	G
E8605-4	Portable PA	H
E8606-1	Midi-CV Converter Board	H
E8606-2	Midi-CV Converter PSU	D
E8606-3	Troglograph	F
E8606-4	80m Receiver	H

E8606-5	Sound Sampler	R
E8607-1	Directlon	E
E8607-2	Upgradeable Amp, MC stage (Stereo)	G
E8607-3	BBC Motor Controller	F
E8608-1	Digital Panel Meter	G
E8608-2	Upgradeable Amp, MM stage (mono)	H
E8609-1	Mains Conditioner	E
E8609-2	Experimental preamp	F
E8609-3	Upgradeable amp, Tone board (mono)	H
E8609-4	Upgradeable amp, Output board (mono)	F
E8610-1	Audio Analyser Filter Board	L
E8610-2	Audio Analyser Display Driver	K
E8610-3	Audio Analyser Display	H
E8610-4	Audio Analyser Power Supply	F
E8611-1	Audio Switcher (2 bds)	H
E8611-2	PLL Frequency meter (4 bds)	Q
E8611-3	Upgradeable Amp PSU	J
E8611-4	Call meter, main bd	O
E8611-5	Call meter, interface bd	N
E8612-1	Bongo Box	J
E8612-2	Bicfeedback monitor (Free PCB)	E
E8701-1	RGB Converter	F
E8701-2	Mains Controller	D
E8701-3	Flanger	H
E8701-4	Audio Selector main board	M
E8701-5	Audio Selector PSU	H
E8701-6	Tacho-Dwell	F
E8702-1	Ratometer main board	K
E8702-2	Ratometer ranging board	F
E8702-3	Photo Process Controller (3bds)	O
E8702-4	LEDline display board (2 off)	K
E8702-5	LEDline PSU and controller (2 bds)	G
E8703-1	Capacitometer	F
E8703-2	Geiger Counter	L
E8703-3	Credit Card Casino	E

 

#### Microlight Intercom (May, 1986)

In Fig. 1 the link between pins 2 and 3 of PL3 is not shown. C13 is shown as a polarised capacitor. The battery check contact on SK1 should be shown as normally closed. The PCB foil pattern on p.59 is shown as from the component side. It should be reversed. The miniature loudspeakers mentioned in the article cost £2.50 each, not per pair as incorrectly noted in buylines. The author of the article suggests it is advisable to insert a suitable capacitor between R9 and IC3, pin 3.

#### Baud Rate Converter (May, 1986)

In Fig. 4 some confusion has crept in to the ins and outs of the circuit diagram. IC6a and IC5c need to be turned round and pins 20 and 25 of IC2 swapped round. In Fig. 5, D4 and D3 are shown the wrong way round on the overlay. This could of course lead to the destruction of C10 as well as the presence of second +12V rail instead of the required -12V. In Fig. 6, SK4.3 and SK3.3 must be swapped over. In the Parts List, C10 should be 1000µF, not 100µF.

#### RF Oscillators (June, 1986)

Fig. 12 does not, infact, show a working oscillator. For a series fed arrangement, take the 1nk from CV1a,b junction to R3 and Q1 emitter junction and not 0V, remove C1 and move C2 to shunt R2. For a shunt-fed arrangement, break the link between L1 and Vcc and take Q1 collector to Vcc via a 4k7 resistor.

#### Speaking Alarm Clock (August, 1986)

In the circuit diagram, Fig. 2, diode D3 and resistor R14 should be in parallel not series as shown. The link from IC10, pin 1, to battery positive should be removed.

#### Biofeedback Monitor (December, 1986)

The capacitor C4 is shown the wrong way around in the component overlay diagram (Fig. 4).

#### The Intelligent Call Meter (December, 1986)

The hex dump listing of the ROM for this project (Table 3) was badly printed with the byte at location BF missing. This should read 7F.

#### The Better Flanger (January, 1987)

In the circuit diagram (Fig. 2) D1 is not labelled. This is connected to Q1. In the component overlay (Fig. 5) several components are missing. A link should connect the two pads to the left of C1. Q1 is situated next to D1 and connection point P4 is situated between R16 and R33. In addition, the positions of R16 and C11 should be swapped.

#### Aerial Without Holes (In-Car Tech Tips, January, 1987)

Using enamelled wire of only 0.5mm diameter for the bifilar coils could cause overheating problems and even a fire risk with some cars. A much thicker wire (1.5mm should be sufficient) should be used.

# ELECTRONICS TODAY INTERNATIONAL CLASSIFIED

## Lineage:

48p (VAT incl) per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£11.60 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699 Ext 292

Send your requirements to:  
Nicola Baty  
ETI Class. Dept.,  
ASP Ltd.,  
1 Golden Square,  
London W1.

## ALARMS

# ALARMS

**FREE BOOKLET**  
on  
**BURGLAR ALARMS**  
with  
**LOWEST U.K. DIY PUBLISHED PRICES**  
PHONE OR WRITE FOR YOUR COPY  
**051-523 8440**  
**AD ELECTRONICS**  
217 WARBRECK MOOR  
AINTREE, LIVERPOOL L9 0HU

## SPECIAL OFFERS

FREE MEMBERSHIP to a new NATIONAL ELECTRONICS CLUB.

For details and a free gift of components worth over £10 send only £1.00 p&p to  
Woodside, Dowsett Lane,  
Ramsden Heath,  
Essex CM11 1JL.

## PREAMPLIFIERS & CONTROLS

£8.95!! ... MAG/PU ... Selector ... T&B/Vol etc!! ... Ex-equipment 100W/AMP Modules. Tested/£7.50!! ... **Free Offer** ... 40 Radial Polyester Capacitors!! Post - ad + 50p coin (p&p). KIA - 8 Cunliffe Road, Ilkley ... Catalogue 60p.

## ELECTROLYTIC CAPACITORS

from 3p, solder 10 metres - 75p. **OUT NOW!** - I.C. Electronics latest discount catalogue. Send name, address + £1 (refundable). I.C. Electronics, Mail Order Dept. B1, PO Box 130, Aberdeen AB9 8HQ.

## SUPPLIES

**QUALITY WALKIE TALKIES** private, long range satisfaction or refund. £24.95/pair (normally £31.49). Send £3.00 now, pay £21.95 on receipt. 48 hrs delivery. Xenon (Dept ET19) 24 Wharnclyffe Street, Barnsley, Yorkshire.

## SATELLITE

**SATELLITE T.V.** Receiver Kits £155 - £1,800 For Technical How To Build Manual send £3.50 or catalogue only £1 to: C & S T.V. 11, Wensley Gardens, Leeds 7.

## SCOPES

### MENDASCOPE LTD.

REPAIR & RECALIBRATE  
OSCILLOSCOPES.

ALL MAKES ALL MODELS  
NATIONWIDE COLLECTION &  
DELIVERY

FREE ESTIMATES

Phone 069-172-597

**HEATHKIT 10/4530** full-spc 10MHz scope complete kit in original box. Untouched, originally £250, nearest offer £130 secures. Tel: (0732) 354311, evenings.

**OSCILLOSCOPES** Dual-trace, delay sweep. Hameg 70MHz £415, Telequipment D83 50 MHz £325, Tektronix 545B 24 MHz £135, 585A 85 MHz £235, 556 Eight-Trace 50 MHz £495, 561B 875 MHz Sampling £195. Fine condition Tel. 01-868 4221.

## BOOKS

**PARAPHYSICS** Journal (Russian Translation): Psychotronics; Kirlianography, Heliphonic Music, Telekinetics. Computer Software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.

**NOW AVAILABLE** - Bumper Catalogue - 170 pages - for collectors of vintage radio, audio & TV equipment. Price: £3.00 post paid UK, £5.00 post paid overseas. Vintage Wireless Co. Ltd., Cossham Street, Mangotsfield, Bristol BS17 3EN. Phone: 0272 565472.

## COMPONENTS

5.25" disks, bulk RPS, DS 961p £0.46  
Resistors .25W 5% E12 values £0.01  
Caps. .01, .015, .022, .033, .047, .1 £0.06  
Elec. Caps. 1/63, 10/16, 100/16 £0.06  
Eprom 27256-2, 12.5 Vprog £3.95  
25 way D plug, socket or shell £0.74  
DIN plugs & ski's 5, 6, 7 pin £0.20  
LED's 5mm red, grn, amber £0.10  
All prices inc. P&F, please add VAT 15%

**T-systems Ltd** Tel. 0689 22196  
The Signal Cabin,  
61 High Street,  
Orpington, Kent, BR6 0JF

**PROMs - EPROMs - PALs**  
ANY PROGRAMMABLE IC  
SUPPLIED OR BLOWN  
PRICES (Including Programming)

2716	£3.45	2732	£3.60
2764	£2.85	27128	£3.20 etc.

BIPOLAR PROMs from £1.35  
e.g. 82S123, 18S030, 74S288  
PALs, PLDs etc. from £3.26  
e.g. 82S153, 16L8, EP300

Full design and prototyping service  
Any quantity programmed - SAE or phone for details

**P.L.S., 16 Wordworth Drive,**  
Cheam, Surrey, SM3 8HF  
Phone 01-644 8095

I.G.S. Components, No 18 Queensway,  
Shelley, Ongar, Essex, CM5 0BN.  
LEDs 5mm:- red, 1 8p, 25 6p, 1005p/  
green, 1 11p, 25 9p, 100 8p/yellow, 1  
11p, 25 9p, 100 8p/ 1N4148, 1 3p, 25 2p,  
100 1.5p/resistors 1/4W 5% carbon film  
E12, 1 2p, 25 1.5p, 100 1p, quantities  
per single value, 4R7 to 10M, 10 of each  
value 770 resistors £4.40 All prices  
include VAT but 50p must be added to  
orders under £5.00.

## SUPPLIES

**FREE PROTOTYPE** of the finest quality with every P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited, Finsbury House, 31 Head St. Halstead, Essex CO9 2BX. Tel: 0787 477408.

**DESIGN SERVICES**, microprocessor, special interfaces, analogue, digital, signalling, alarm systems, PCB design and artwork. Prototype and small batch production. **ALAB ELECTRONICS**, Grantham (0476) 860089.

**01-437 0699**  
**= RESULTS**

## TRAINING COURSE

### PROFESSIONAL ELECTRONICS TECHNICIANS

Short re-training courses (1-3 weeks)

VCR SERVICING  
MICROCOMPUTER SERVICING

(ONC/OND/HNC also available in modules)

\* MSC GRANT AID to EMPLOYERS/TRAINEEES \*

Television/Video/CCTV/  
MICROELECTRONICS  
Information Technology/  
CAD/CAM/ATE  
MICROPROCESSORS/  
Computers/CONTROL  
**LONDON ELECTRONICS COLLEGE**  
Dept (ETI)  
20 Penywern Road  
LONDON SW5 9SU. 01-373 8721  
Next course starts 6th October and 27th October.

## PLANS & DESIGNS



Design and build your own electronic dashboard  
Plans, instructions, circuits, parts lists  
£4.95 inc p&p

**BURLINGTON MOTOR CO. LTD.,**  
(G2) ARCH 39M, BATH PLACE,  
LEAMINGTON SPA CY3 3AQ.

## PORTABLE WORK STATION

Make your electronic projects and tools portable. Bring them into the warm home from a cold garage. Make table top projects more convenient. Easily constructed from plywood. Plans £3.50 only.

**BOLDELEC,**  
5 Denise Avenue, Penketh,  
Warrington, WA5 2RE.

## VERY COMPETENT ELECTRONIC DESIGNER

of RF, Digital, Computer Circuits, and also Micro-Circuit/s/ry, and possibly flat-screen technology, urgently required. Please ring:

01-659-4098  
After 8.00pm (20.00Hrs)

**ELECTRONIC PLANS**, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet 150 projects. For catalogue, SAE to Plancentre Publications, String Works, Bye St., Ledbury HR8 2AA.



## KITS AND READY BUILT

### LEDScope

A Low Frequency Oscilloscope with High Efficiency LED Display as featured in ETI January 1987.

Kit of Parts.....£49.95  
Case.....£14.95  
Test Probe/Lead Kit .. £7.95  
For Free reprint of article send SAE. All Prices include VAT, Please add £2.50 P&P.

LEFAZ LTD.  
UNIT 6, GENESIS BUSINESS CENTRE, REDKILN WAY, HORSHAM

LEFAZ LTD.  
Unit 6, Genesis Business Centre,  
Redkln Way, Horsham, West Sussex  
RH13 5QH. (0403) 54135

**FM TRANSMITTERS** Same day despatch **MINIATURE MODEL** frequency 60-145 Mhz, range 1 mile. Glass fibre P.C.B. All components. Full instructions 9-12V operation, broadcast reception. Super sensitive microphone. Pick up on **FM/VHF** radio. £6.95 inc or ready built £8.95. Size 57 x 19 x 12mm. **HIGH POWER MODEL.** 3 watts 80-108 MHz. Professional broadcast performance Low drift varicap controlled. Range up to 7 miles. 12V operation. Any input audio/microphone. All components P.C.B. diagrams and instructions. Size 103 x 39 x 29mm. Kit 13.99 inc or ready built £18.99 inc. Send S.A.E. for our DataPack on other products. **ZENITH ELECTRONICS.** 14 Corllandt Business Centre, Hailsham, East Sussex BN27 1AE. Tel: 3323 847973.

**SECURITY LIGHT KIT** mains operated can control up to 600W of additional lighting. Multi-beam passive I.R. people detector triggers light. Kit complete with case. PCB, IR module and all components. For details send SAE to Beeches Security Systems 64, Carrs Way, Harpole, Northampton NN7 4DA.

**ETI KITS** assembled and tested\* by electronic trainees under supervision with a purpose built electronic workshop for as little as £10\* (\* depending on type of kit and complexity) Contact:- A.J. Smith, Dept K.A. Electronics Workshop, Lincoln ITEC, Dean Road, Lincoln LN2 4JZ Tel 0522 43532.

**68008 SINGLE** board computer, contains 80 T/C/S disc interface, colour display, 8K monitor etc Bare P.C.B. or built. Also 6809 micro-set system and tangerine conversions. S.A.E. for details (state which) Ralph Allen Eng Forncett-End Norwich.

**LINSLEY HOOD** Designs Send S.A.E. for details to Teleradio Electronics, 325 Fore Street, London N9 OPE.

## SERVICES

**ASSEMBLY SERVICES:** PCB/Cable/Harness Highest standard workmanship. In-Circuit/Functional testing if required Contact CBA, Dublin (0) 375675

## WANTED

Turn your surplus transistors, IC's etc., into cash. Immediate settlement.

We also welcome the opportunity to quote for complete factory clearance. Contact:

Coles Harding & Co.  
103 South Brink  
Wisbech, Cambs.

ESTABLISHED OVER 10 YRS  
Tel: 0945 584188

**GOOD PRICE** for service and/or operating manuals for Sharp SF-780 and/or SF-825 photocopiers. Contact Mr J R Norman, 40 Inglewood Rd, Bexley Heath, Kent DA7 6JS

## FOR SALE

### 2000!

Ex-Pub amusement PCB's for sale. Containing many caps, resistors, i.c.'s, Diodes, Eproms, 280's, crystals etc. £10.00 each or offers for the lot

RING (0532) 455685

**EX-EQUIPMENT HEATSINKS.** Some with components, eg 2.5° C/W £0.75, 10° C/W £0.20, including p&p over £5 order value. Also ex-equipment electrolytics, eg 5600 micro F/63V £0.75, 23000 micro F/40V £1.50 All have screw terminals. Ideal for power supplies or amplifiers. SAE for list or Telephone (0544) 230853 Portable Power, 37 Church Street, Kington, Herefordshire, HR5 3BE

**AUTOMATIC GARAGE DOOR OPERATORS.** £65.00. S.A.E. for details to Mulberry Ltd, 116 Grosvenor Road, Aldershot, Hants.

**RING NICOLA BATY**  
ON 01-437 0699 FOR  
ADVERTISING DETAILS

## TERMS

### CLASSIFIED ADVERTISING TERMS & CONDITIONS

Our terms for new advertisers (semi-display and lineage) are strictly pro-forma payments until satisfactory reference can be taken up (excluding recognised advertising agencies). Cheques PO's should be crossed and made payable to:

ARGUS SPECIALIST PUBLICATIONS LTD.,

and send together with the advertisement to:

THE CLASSIFIED DEPT., L/H,  
NO: 1 GOLDEN SQUARE, LONDON  
W1R 3AB.

There are no reimbursements for cancellations. Advertisements arriving too late for a particular issue will be inserted in the following issue unless accompanied by instructions to the contrary.

All advertising sales are subject to Government regulations concerning VAT. Advertisers are responsible for complying with the various legal requirements in force eg: The Trade Description Act, Sex Discrimination Act & The Business Advertisements (Disclosure) Order 1977.

FULL TERMS & CONDITIONS OF ADVERTISING AVAILABLE ON REQUEST

## EQUIPMENT

**GEIGER COUNTERS.** Inexpensive gen-purpose portable radiation monitor (Heavy Duty Audiovisual) Kitform (full assembly data) £79.92 Built £89.32 Post incl. Others from £40 send S.A.E. Becker- ET 8 Finucane Drive Orpington 0589 37821

**COMPLETE GEIGER** counter (with Tube) for radiation measurement - Under £50 Send for details: Radiation Detectors 46/47 Pall Mall, London SW1Y 5JG Tel (01) 839 3143.

## POWER SUPPLIES

**220/240v AC** Electricity from 12v batteries Encapsulated modules with screw terminals Microchip design Just connect transformer and 8 heat sinked transistors to terminals 400W/12v £28; 600W/24v £30 p&p £0.75. Detailed assembly instructions provided. Chataigne Products, Green Lane, Great Horkeley, Colchester, Essex, CO6 4HD (Prop. J.A. Richmond).

## REPAIRS

**INSTRUMENT REPAIRS** oscilloscopes, generators, multimeters and more Viking Electronics, Potkins Lane, Orford, Suffolk IP\*2 2SS (0394) 450006

## COMPUTER ADD-ONS

### AMSTRAD OUTPUT PORT

Plugs into printer port and provides seven open-collector outputs. Easy to use from basic or m/c. As detailed in ETI January '87, p9 £14.95 inc. S.A.E. for details  
NCJ Electronics  
13 Binfield Square, Ellis Street,  
Hull, HU5 3AP.

## SWITCHES

**VOICE/SOUND ACTIVATED SWITCHES** easy to follow diagrams and uses only £1.00. Components and P.C.B's available: Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.

## MISCELLANEOUS

**HEATHKIT U.K.** Spares and service centre Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos Tel. 0684 73127

Our next copy  
deadline:  
25th February  
for the  
May Issue

## LANCASHIRE

### ELECTRO SUPPLIES

NORTHERN COMPONENT SPECIALISTS  
Test equipment, Computers, Peripherals

SEND FOR CATALOGUE

also at  
45 Lower Hillgate, Shawclough Road,  
Stockport, Cheshire Waterfoot, Rosendale  
061 497 9272 BB4 9JZ. 0706 - 215556

## LIVERPOOL

### PROGRESSIVE RADIO

87/93 Dale Street Tel: 051 236 0154

47 Whitechapel. Tel: 051 236 5489

Liverpool 2

'THE ELECTRONICS SPECIALISTS'

Open: Tues-Sat 9.30-5.30

## YORKSHIRE

### COMPUTERCARE

Electronic Components \*

Computer Supplies \*

Repairs

12 COMMERCIAL ROAD,

LEEDS, LS5 3AQ.

(Across from Kirkstall leisure centre)

Open: Monday-Friday 9-5.30

(Saturday please phone first)

Phone LEEDS 743356 for stock list

## TYNE AND WEAR

### ELECTRONIC COMPONENTS AND KITS



STATION ROAD, CULLERGOATS,  
NORTH SHIELDS, TYNE & WEAR NE30  
4PG. 091 251 4363.

MON-SAT 9.30 to 5.30  
CLOSED THURS.

E  
L  
E  
C  
T  
R  
O  
M  
A  
R  
T

E  
L  
E  
C  
T  
R  
O  
M  
A  
R  
T

# electronics today

INTERNATIONAL

## CLASSIFIED ADVERTISING COUPON

Post to: **ETI, 1 Golden Square, London W1A 3RB**

Rates:- 48p per word (min. charge £7.20 (VAT incl)). Semi display (min. 2cms) £11.60 (+ VAT) per single column centimetre.

Please debit my Access/Barclaycard No.  Expiry date.....

--	--	--	--	--	--	--	--	--	--

£.....for.....insertions.

Or I enclose my cheque/PO for £.....for.....insertions.


Please use **BLOCK CAPITALS** and include post codes.

Classification .....

Name (Mr/Mrs/Miss/Ms) .....  
(delete accordingly)

Address .....

Signature ..... Date .....

Daytime Tel. No. ....

# ADVERTISERS INDEX

BK Electronics .....	IFC
Boreland .....	12
Cambridge MC Centre .....	49
Cirkit .....	10
Cricklewood .....	8
Crostones Electronics .....	66
Display Electronics .....	IBC
Electromech .....	19
Exchange Resources .....	8
Greenbank Electronics .....	10
Hart Electronics .....	10
Henry's Audio .....	12
ICS .....	59
Jaytee Electronics .....	59
No 1 Systems .....	66
MJL .....	59
NOI Systems .....	66
Omni .....	44
Pineapple Software .....	31
RTVC .....	31
Specialist Semi Conductor Devices .....	48
Stewarts of Reading .....	44
Technomatic .....	4&5
TJA .....	59
TK Electronics .....	44
Turbo .....	12
Vinderen .....	8
VW & E Smith .....	44
Zenith .....	31

CROFTON PM101


**THE VIDEO SPECIALISTS**

(05448) 557

# Crofton

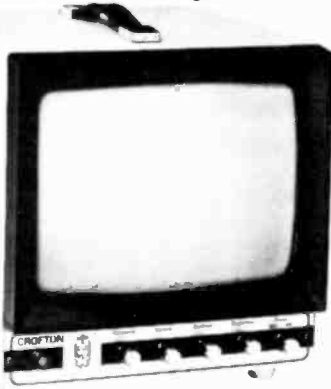**GREEN SCREEN 9" (P31)**

Metal cased monitor only £45.00 + VAT.  
£51.75 incl. carriage.



This 9 inch metal cased, monochrome monitor offers you the chance to obtain a high quality product at a budget price!

Be sure to ask for our various catalogues. We have a full range of products including:

- 1—Discrete listening devices
- 2—Plugs/sockets/connectors/leads
- 3—Television accessories
- 4—Security products
- 5—Computer products
- 6—NEC cased and uncased monitors

Just starting to refurbish CCTV Cameras, and Monitors, Ask For Details. First Come First Serve, these are very popular items and won't last long.

**CCTV camera at attractive prices**

ALL OUR PRICES INCLUDE VAT, CARRIAGE & INSURANCE AND CAN ONLY BE HELD AS LONG AS STOCKS LAST!

**PHONE YOUR ORDER NOW!**

MOST MAJOR CREDIT CARDS ACCEPTED OFFICIAL ORDERS FROM APPROVED INDUSTRIAL OR EDUCATIONAL ESTABLISHMENTS WELCOME

Delivery within 28 days.

If you would like all our catalogues - Please send a 38p 9 x 12 S.A.E.

**THERE'S ALWAYS A SPECIAL DEAL FOR YOU AT CROFTON**

If we haven't listed what you are looking for, please ask, we probably have it in stock.

## SPECIAL OFFERS

BRAND NEW professional board and green tube to make 12" T.T.L./comp open home monitor. **ONLY £30 + VAT** and carriage. ZX81 Full sized keyboard in metal case **£13.80**. COMPUTER DESKS **£20**.

PHILIPS BM7502

Also in stock: PHILIPS BM7522

PHILIPS CT2007

Phone for today's best price

**CROFTON ELECTRONICS**

KINGSHILL, NEXTEND, LYONSHALL,  
Nr KINGTON, HEREFORDSHIRE HR5 3HZ.

LYONSHALL  
(05448) 557

# COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

## THE "ALLADINS" CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HOT LINE DATA BASE

### DISTEL

The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell. 1000's of stock items, spares and one off bargains. Updated daily. ON LINE NOW. CCITT, 8 bit word, no parity. For 300 baud modems call 01-679 1888 For 1200-75 baud modems call 01-679 6183

FREE

Your monitor from its computer! For only £24.95 it becomes a SUPERB HIGH QUALITY COLOUR TV SET

The fabulous TELEBOX, an INVALUABLE MUST for the owner of ANY video monitor with a composite input colour or monochrome. Made by a major UK Co. as a TOP QUALITY, stand alone UHF tuner and costing OVER £75 to manufacture, this opportunity to give your monitor a DUAL FUNCTION must not be missed! The TELEBOX consists of a compact stylish two tone charcoal moulded case, containing ALL electronics tuner, power supply etc to simply plug in and convert your previously dedicated computer monitor into a HIGH QUALITY COLOUR TV SET, giving a real benefit to ALL the family! Don't worry if your monitor doesn't have sound - THE TELEBOX even has an integral watt audio amplifier for driving an external speaker. PLUS an auxiliary output for superb quality television sound via your headphones or HI FI system etc. Other features include: Compact dimensions of only 15.75" w x 7.5" d x 3.5" h, latest technology, BRITISH manufacture, fully tuneable 7 channel push button tuner, Auto AGC circuit, SAW filter, LED status indicator, fully isolated 240v AC power supply for total safety, Mains ON-OFF switch etc. Many other uses.

LIMITED QUANTITY - DON'T MISS THIS OFFER!!!

ONLY £24.95 OR £19.95 if purchased with ANY of our Video monitors. Supplied BRAND NEW with full instructions and 2 YEAR warranty. Post and packing £3.50 \*When used with colour crt.

### COLOUR & MONOCHROME MONITOR SPECIALS

#### 'SYSTEM ALPHA' 14" COLOUR MULTI INPUT MONITOR

Made by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future requirements. Two video inputs: RGB and PAL Composite Video, allow direct connection to BBC/IBM and most other makes of micro computers or VCR's, including our very own TELEBOX. An internal speaker and audio amp may be connected to computer or VCR for superior sound quality. Many other features: PIL tube, Matching BBC case colour, Major controls on front panel, Separate Contrast and Brightness - even in RGB mode. Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc.

This Must Be ONE OF THE YEAR'S BEST BUYS. PC USER Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. ONLY £149.00 as above OR IBM PC Version £165.00 15 Day 'D' sct £1.00. BNC sct 75p BBC interface cable £5.50

DECCA 80 16" COLOUR monitor, RGB input. Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor as yet unheard of! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the DECCA 80 series TV chassis give 80 column definition and quality found only on monitors costing 3 TIMES OUR PRICE. The quality for the price has to be seen to be believed! Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: internal speaker, modular construction, auto degaussing circuit, attractive TEAK CASE, compact dimensions only 52cm W x 34" H x 24" D. 90 day guarantee. Although used, units are supplied in EXCELLENT condition. ONLY £99.00 + Carriage.

DECCA 80 18" COLOUR monitor. Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL use. ONLY £99.00 + Carr.

REDIFFUSION MARK 3, 20" COLOUR monitor. Fitted with standard 75 ohm composite video input and sound amp. This large screen colour display is ideal for SCHOOLS, SHOPS, DISCOS, CLUBS and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition ONLY £145.00 + Carr.

BUDGET RANGE EX EQUIPMENT MONOCHROME video monitors. All units are fully cased and set for 240v standard working with composite video inputs. Units are pre tested and set up for up to 80 column use. Even when MINOR screen burns exist - normal data displays are unaffected 30 day guarantee.

12" KGM 320-1 B/W bandwidth input, will display up to 132 x 25 lines. £32.95  
12" GREEN SCREEN version of KGM 320-1. Only £39.95  
9" KGM 324 GREEN SCREEN fully cased very compact unit. Only £49.00

Carriage and insurance on all monitors £10.00

### DC POWER SUPPLY SPECIALS

GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 55a, +12v @ 0.5a, -12v @ 0.1a and -23v @ 0.02a. Dim 18 x 11 x 6 cm. 110 or 240v input. BRAND NEW only £16.95  
GOULD G6-40A 5v 40 amp switch mode supply NEW £130.00  
AC-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLOY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.6 amps and +24v @ 5 amps. Short circuit and overvoltage protected. 100 or 240v AC input. Dim 28 x 12.5 x 7 cm. NEW £49.94  
Carriage on all PSUs £3.00

### KEYBOARDS

Manufacturer's BRAND NEW surplus.  
DEC LA34 Uncoded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micr conversions etc. £24.95  
AMKEY MPNK-114 Superb word processor chassis keyboard on single PCB with 116 keys. Many features such as On board Micro, Single 5v rail, full ASCII coded character set with 31 function keys, numeric keypad, cursor pad and 9600 baud SERIAL TTL ASCII OUTPUT! Less than half price  
Only £89.00 with data. Carriage on Keyboards £3.50



Double sided 40/80 track disk drives (1Mb per drive), PSU, 4K of memory mapped screen RAM, disk controller, RS232, CENTRONICS and system expansion ports, and if that's not enough a ready to plug into STANDARD 8" DRIVE port for up to FOUR 8" disk drives, either 1M double density or IBM format. The ultra slim 92 key, detachable keyboard features 32 user definable keys, numeric keypad and text editing keys, even its own integral microprocessor which allows the main Z80A to devote ALL its time to USER programs, eliminating "lost character" problems found on other machines. The attractive, detachable 12" monitor combines a green, anti-glare etched screen, with full swivel and tilt movement for maximum user comfort. Supplied BRAND NEW with CPM 2.2, user manuals and full 90 day guarantee. Full data sheet and info on request.

PC2000 System with CPM Etc. COST OVER £1400

NOW only £399

### DON'T MISS THE CPM Deal OF THE CENTURY

### The FABULOUS CPM TATUNG PC2000 Professional Business System

A cancelled export order and months of negotiation enables us to offer this professional PC CPM system, recently on sale at OVER £1400, at a SCOOP price just over the cost of the two internal disk drives! Or less than the price of a dumb terminal!!

Not a toy, the BIG BROTHER of the EINSTIEN computer, the DUAL PROCESSOR PC2000 comprises a modern stylish three piece system with ALL the necessities for the SMALL BUSINESS, INDUSTRIAL, EDUCATIONAL or HOBBYIST USER. Used with the THOUSANDS of proven, tested and available CPM software packages such as WORDSTAR, FAST, DBASE2 etc. the PC2000 specification, at our prices, CANNOT BE BEATEN!

The central processor plinth contains the 84K, Z80A processor, DUAL TEAC 55F 5 1/4" integral modern etc for direct connection to PRESTEL, VIEWDATA etc. Designed to sell to the EXECUTIVE at over £600! Our price BRAND NEW AND BOXED at only £99.00

PC2000 Business System with CPM and Ready to Run FAST Sales and Purchase ledger, supports up to 9000 Accounts, VAT etc. COST OVER £1700

NOW only £499  
Carriage & Insurance £12.00

PC2000 Wordprocessor System with CPM and TEC FP25 daisywheel printer

NOW only £799

### MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets... BRAND NEW State of the art products. DACOM DSL2123 Multi standard 300-300, 1200-75 Auto answer etc. £268.00  
DACOM DSL2123AQ Auto dial, smart modem with multi standard AUTO SPEED detect and data buffer with flow control etc. £365.00  
DACOM DSL2123GT The CREAM of the intelligent modems, auto dial, auto call, index, buffer etc. £498.00  
Stacpack SBI212 V22 1200 baud FULL DUPLEX, sync or async optional auto dial. £485.00  
TRANSDATA 307A Acoustic coupler 300 baud full duplex, originate only, RS232 interface. £49.00

Ex BRITISH TELECOM full spec. CCITT, ruggedised, bargain offers. Sold TESTED with data. Will work on any MICRO or system with RS232 interface. £45.00  
MODEM 13A 300 baud unit only 2" high fits under phone CALL mode only. £45.00  
MODEM 20-1, 75-1200 baud. Compact unit for use as subscriber end to PRESTEL, TELECOM GOLD, MICRONET etc. £39.95 + pp £6.50  
MODEM 20-2 1200-75 baud Same as 20-1 but for computer end. £85.00 + pp £6.50  
DATEL 2412. Made by SE Labs for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc. COST OVER £800. Our price ONLY £199 + pp £8.00  
DATEL 4800, RACAL MP54800 baud modem, EX BT good working order. ONLY £295.00 + pp £8.00

#### SPECIAL OFFER

MODEM TG2393, EX BT, up to 1200 baud, full duplex 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR + pp £10.00

For more information contact our Sales Office.

### MATRIX PRINTERS

SPECIAL BULK PURCHASE of these compact, high speed matrix printers. Built in Japan for the Hazeltine Corporation this unit features quality construction giving 100cps bidirectional, full pin addressable graphics, 6 type fonts, up to 9.5 single sheet or tractor paper handling, RS232 and CENTRONICS parallel interface. Many other features BRAND NEW and BOXED COST £420. Our price ONLY £199.00

### RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa  
A300 07191315 12v 3Ah NEW £13.95  
A300 07191312 6v 3Ah NEW £9.95  
A300 07191202 6-0-6v 1.8Ah TESTED Ex Equip £5.99

### VDU TERMINALS

Standard VDU data entry terminals at give away prices!!

QUME QVT108. Current product, state of the art terminal with detachable keyboard, 12" Green screen, 2 page RAM, TVI 925, Hazeltine, ADMS A emulations, software setup, 25 x 80 Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE ONLY £425.00  
AJ510 - EX REMOTAL, Z80 controlled, 15" green screen 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED complete with manual only £225.00  
ADDS 520 - Dumb terminal, used, 12" b/w screen RS232 interface and printer port TESTED. ONLY £125.00. Carriage on terminals £10.00  
100's of other terminals in stock. CALL for more details.

### SURPLUS SPECIALS ON PRESTEL - VIEWDATA - TELEX

PLESSEY VUTEL, ultra compact unit, slightly larger than a telephone features A STANDARD DTMF TELEPHONE (tone dial) with 5" CRT monitor and integral modem etc for direct connection to PRESTEL, VIEWDATA etc. Designed to sell to the EXECUTIVE at over £600! Our price BRAND NEW AND BOXED at only £99.00  
DECCAFAX VP1 complete Professional PRESTEL system in slimline desk top unit containing Modem, Numeric keypad, CPU, PSU etc. Connects direct to standard RGB colour monitor. Many other features include: Printer output, Full keyboard input, Cassette port etc. BRAND NEW with DATA A FRACTION OF COST only £55.00  
ALPHATANTEL, Very compact unit with integral FULL ALPHA NUMERIC keyboard, just add a domestic TV receiver and you have a superb PRESTEL system and via PRESTEL, the cheapest TELEX service to be found! Many features: CENTRONICS Printer output, Memory dialling etc. Supplied complete with data and DIY mod for RGB or Composite video outputs AS NEW only £125.00  
Post and packing on all PRESTEL units £8.50

### EX-STOCK INTEGRATED CIRCUITS

4164 200 ns D RAMS 9 for £11 4116 ns £150 2112 £1000 2114 £250 2102 £200 6116 £250 EPROMS 2716 £450 2732 £300 2764 £495 2712B £550 6800 £250 6821 £1 68A09 £8 68B09 £10 8085A £550 8086 £15 8088 £8 NEC765 £8 W2793 £28 8202A £22 8251 £7 8748 £15 Z80A DART £650 Z80A CPU £200. Thousands of IC's EX STOCK send SAE for list.

### DISK DRIVES

Japanese 5 1/4" half height, 80 track double sided disk drives by TEAC, CANON, TOSHIBA etc. Sold as NEW with 90 day guarantee ONLY £85.00  
TEC FB-503 Double sided HH 40 TRK NEW £75.00  
SHUGART SA400 SS FH 35 TRK £55.00  
SIEMENS FDD100 SS FH 40 TRK £85.00  
Carriage on 5 1/4" drives £5.50  
Brand NEW metal 5 1/4" DISK CASES with internal PSU  
DSK1 for 2 HH or 1 FH drive £29.95 + pp £4.00  
DSK2 for 1 HH drive £22.95 + pp £3.50  
DKSC 3 As DSK1 LESS PSU £12.95 + pp £2.50  
DSK4 As DSK2 LESS PSU £10.95 + pp £2.00  
B' IBM format TESTED EX EQUIPMENT.  
SHUGART 800/801 SS £175.00 + pp £8.50  
SHUGART 851 DS £250.00 + pp £8.50  
TWIN SHUGART 851\* 2 Mb total capacity in smart case, £595.00 complete with PSU etc.  
MITSUBISHI M2894-63 B DS 1 Mb equiv. to SHUGART SA850R. BRAND NEW at £275.00 + pp £8.50  
DYSAN 8" Alignment disk £29.00 + pp £1.00  
Various disk drive PSUs in Ex Stock SEE PSU section.  
HARD DISK DRIVES  
DRE/DIABLO Series 30 2.5 Mb front load £525.00  
Exchangeable version £295.00. ME3029 PSU £95.00  
DIABLO 44/DRE4000A, B 5 + 5 Mb front £750.00  
CDC HAWK 5 + 5 Mb £795.00. CDC 9762 80 MB RAMC3 etc. £2500.00  
PERTEC D3422 5 + 5 Mb £495.00  
RODIME 5 1/4" Winchesters ex-stock from £150 CALL  
Clearance Items - Sold as seen - No guarantee  
ICL 2314 BRAND NEW 14" Mb Removable pack hard disk drive, cost over £2000 with data ONLY £99.00  
BASF 6172 B 23Mb Winchesters £199.00  
Unless stated all drives are refurbished with 90 day guarantee. Many other drives and spares in stock - call sales office for details.

All prices quoted are for UK Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30, Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

32 Biggin Way, Upper Norwood, London SE19 3XF  
Telephone 01-679 4414 Telex 894502 Data 01-679 1888



# DISPLAY ELECTRONICS

