

ETI ELECTRONICS TODAY INTERNATIONAL

20th ANNIVERSARY

RADIO & ELECTRONICS SHOW '92
28-29th MARCH

HI-FI AUDIO PRE-AMP

A design from **John Linsley Hood**

SOLAR POWERED TECH TIPS

AUTO CARLIGHTS

KEYBOARDS

An alternative to typewriter input

20 YEAR PROJECT INDEX



ARGUS SPECIALIST PUBLICATION



AUTOMATE 20
mixing desk



OMP MOS-FET POWER AMPLIFIERS HIGH POWER. TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN
FEATURES: ★Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
 MXF400 W19" x H5 1/4" (3U) x D12"
 MXF600 W19" x H5 1/4" (3U) x D13"
 MXF900 W19" x H5 1/4" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
 MXF600 £329.00 MXF900 £449.15
 SPECIALIST CARRIER DEL. £12.50 EACH



OMP VARISPEED TURNTABLE CHASSIS



★ Manual arm ★ Steel chassis ★ Electronic speed control 33 & 45 R.P.M. ★ Vari pitch control ★ High torque servo driven DC motor ★ Transit screws ★ 12" die cast platter ★ Neon strobe ★ Calibrated balance weight ★ Removable head shell ★ 1/2" cartridge fixings ★ Cue lever ★ 220/240V 50/60Hz ★ 390x305mm ★ Supplied with mounting cut-out template.


PRICE £61.30 + £3.70 P&P

OPTIONAL MAGNETIC CARTRIDGES STANTON AL500mkII GOLDRING G950
 PRICE £16.95 + 50P P&P PRICE £7.15 + 50P P&P

STEREO DISCO MIXER DJ6500

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with tone control & talk-over switch, 7 Channels with individual faders plus cross fade, Cue Headphone Monitor. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.


Price £134.99 + £5.00 P&P

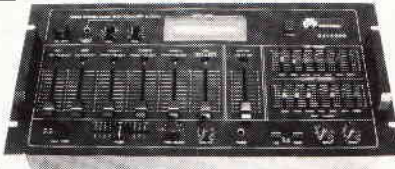

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

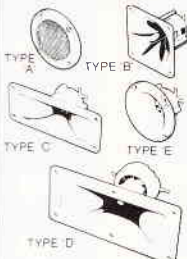Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE

Made especially to suit today's need for compactness with high output sound levels, finished in hard wearing black vinylite with protective corners, grille and carrying handle. Each unit incorporates a 12" driver plus high frequency horn for a full frequency range of 45Hz-20KHz. Both models are 8 Ohm impedance. Size: H20" x W15" x D12".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100WATTS (100dB) PRICE £163.50 PER PAIR
OMP 12-200WATTS (200dB) PRICE £214.55 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR



IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
 150 WATTS (75 + 75) Stereo, 150W Bridged Mono
 250 WATTS (125 + 125) Stereo, 250W Bridged Mono
 400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS

Features:
 ★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms. Frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 220 watts R.M.S. into 4 ohms. Frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms. Frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms. Frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 330 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE - INPUT SENS 775mV, BAND WIDTH 50KHz, ORDER STANDARD OR PEC.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D.s (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control for very fast rise and decay times. Tough moulded plastic case, with acrylic tinted front. Size 64 x 27 x 45mm.
PRICE £8.70 + 50p P&P

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (50p STAMPED) FOR COMPLETE LIST.

P - From McKenzie Professional Series
 S - From McKenzie Studio Series

McKENZIE - INSTRUMENTS, P.A., DISCO, ETC

- ALL McKENZIE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT P C8-100GP GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID. DISCO. RES. FREQ. 80Hz, FREQ. RESP. TO 7KHz, SENS 96dB. PRICE £21.45 + £2.00 P&P
 - 10" 100WATT P C10-100GP GUITAR, VOICE, KEYBOARD, DISCO. EXCELLENT MID. RES. FREQ. 72Hz, FREQ. RESP. TO 6KHz, SENS 97dB. PRICE £28.35 + £2.50 P&P
 - 10" 200WATT P C10-200GP GUITAR, KEYB'D, DISCO, EXCELLENT HIGH POWER. RES. FREQ. 69Hz, FREQ. RESP. TO 5KHz, SENS 97dB. PRICE £52.15 + £2.50 P&P
 - 12" 100WATT P C12-100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 98dB. PRICE £40.15 + £3.50 P&P
 - 12" 100WATT P C12-100TC (TWIN CONE) HIGH POWER, WIDE RESPONSE P.A., VOICE, DISCO. RES. FREQ. 45Hz, FREQ. RESP. TO 12KHz, SENS 97dB. PRICE £41.35 + £3.50 P&P
 - 12" 200WATT P C12-200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES. FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS 99dB. PRICE £71.35 + £3.50 P&P
 - 12" 300WATT P C12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARDS, DISCO ETC. RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 100dB. PRICE £95.50 + £3.50 P&P
 - 15" 100WATT P C15-100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 98dB. PRICE £58.05 + £4.00 P&P
 - 15" 200WATT P C15-200BS VERY HIGH POWER BASS. RES. FREQ. 40Hz, FREQ. RESP. TO 3KHz, SENS 98dB. PRICE £90.57 + £4.00 P&P
 - 15" 250WATT P C15-250BS VERY HIGH POWER BASS. RES. FREQ. 39Hz, FREQ. RESP. TO 4KHz, SENS 99dB. PRICE £90.20 + £4.50 P&P
 - 15" 400WATT P C15-400BS VERY HIGH POWER, LOW FREQUENCY BASS. RES. FREQ. 40Hz, FREQ. RESP. TO 4 KHz, SENS 100dB. PRICE £105.40 + £4.50 P&P
 - 18" 500WATT P C18-500BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES. FREQ. 27Hz, FREQ. RESP. TO 2KHz, SENS. 98dB. PRICE £174.57 + £5.00 P&P

EARBENDERS - HI-FI, STUDIO, IN-CAR, ETC

- ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohms)**
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 8" 50watt EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB. PRICE £8.90 + £2.00 P&P
 - 10" 50WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB. PRICE £13.65 + £2.50 P&P
 - 10" 100WATT EB10-100 BASS, HI-FI, STUDIO. RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB. PRICE £30.39 + £3.50 P&P
 - 12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB. PRICE £42.12 + £3.50 P&P
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 5 1/4" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB. PRICE £9.99 + £1.50 P&P
 - 6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB. PRICE £10.99 + 1.50 P&P
 - 8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB. PRICE £12.99 + £1.50 P&P
 - 10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB. PRICE £16.49 + £2.00 P&P

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz. VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz. VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P




PHOTO: 3W FM TRANSMITTER




POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



It was 20 years ago today ...

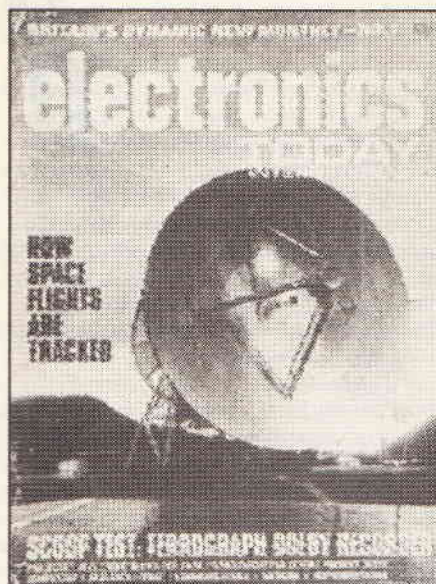

**Volume 21 No 4
April 1992**

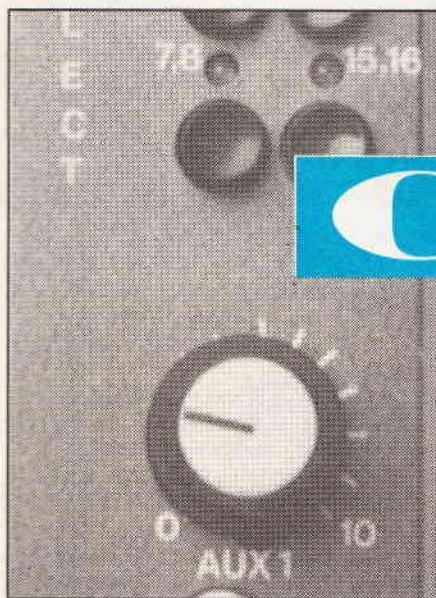

Page 22

Features & Projects

20 Years	4
A look at the past as ETI celebrates twenty years of existence by Paul Freeman and Keith Brindley.	
A High quality Audio Pre-amp	16
John Linsley-Hood provides a semi-conductor designed pre-amp to complement his 80watt power amplifier featured in ETI back in 1989.	
Auto-mate 20 Audio Mixing Desk	22
Mike Meechan begins this major project with a description of the modular features available to the home constructor.	
Keyboards	35
Could the QWERTY keyboard be out of date soon? Stephen Waddington looks at some of the alternatives.	
Auto Car Light Control	38
Colin Meikle provides us with a project to remove the fear of knowing when to turn the car headlights on and off.	
Solar Powered Tech-Tips	42
Robert Penfold presents a series of circuit ideas using solar cells.	
Digital Audio Broadcasting 2	48
James Archer concludes his article on radio broadcasting techniques of the future.	
Earth Charge Recorder 2	52
The second part of our high resolution voltmeter by Kevin Garwell.	
20 Year Index	60
The start of your complete guide to ETI's projects.	

Contents

Regulars

Open Channel	6
News	7
News Stateside	11
Blueprint	12
Photocopy Service	15
PCB Foils	62

Editorial

By Paul Freeman

Twenty years and ETI is still going strong. In this issue we take a brief look back at our history and we also present the beginning of our 20 Year Index to show you the variety of projects covered throughout that period. As will be seen, by far the most popular projects have been in the Audio and Test-gear sections. Judging by your letters, the great Audio debate will remain for some time to come.


But ETI is very much a forward looking magazine always providing new ideas and creations for you to develop and build. We will also continue to bring you the wider aspects of technology even to the point of what such a cumulative effect of mass electronic products has on society and whether such products are

desirable as they become 'semi-intelligent'. So stay with us.

Showtime

As you see from within these pages, ETI will be at the Radio and Electronics Show at Sandown Park over the weekend of 28-29th March. It's a new exhibition covering Ham and CB radio, hobby electronics and home computing. We do hope you can spare the time to pop down and see us.

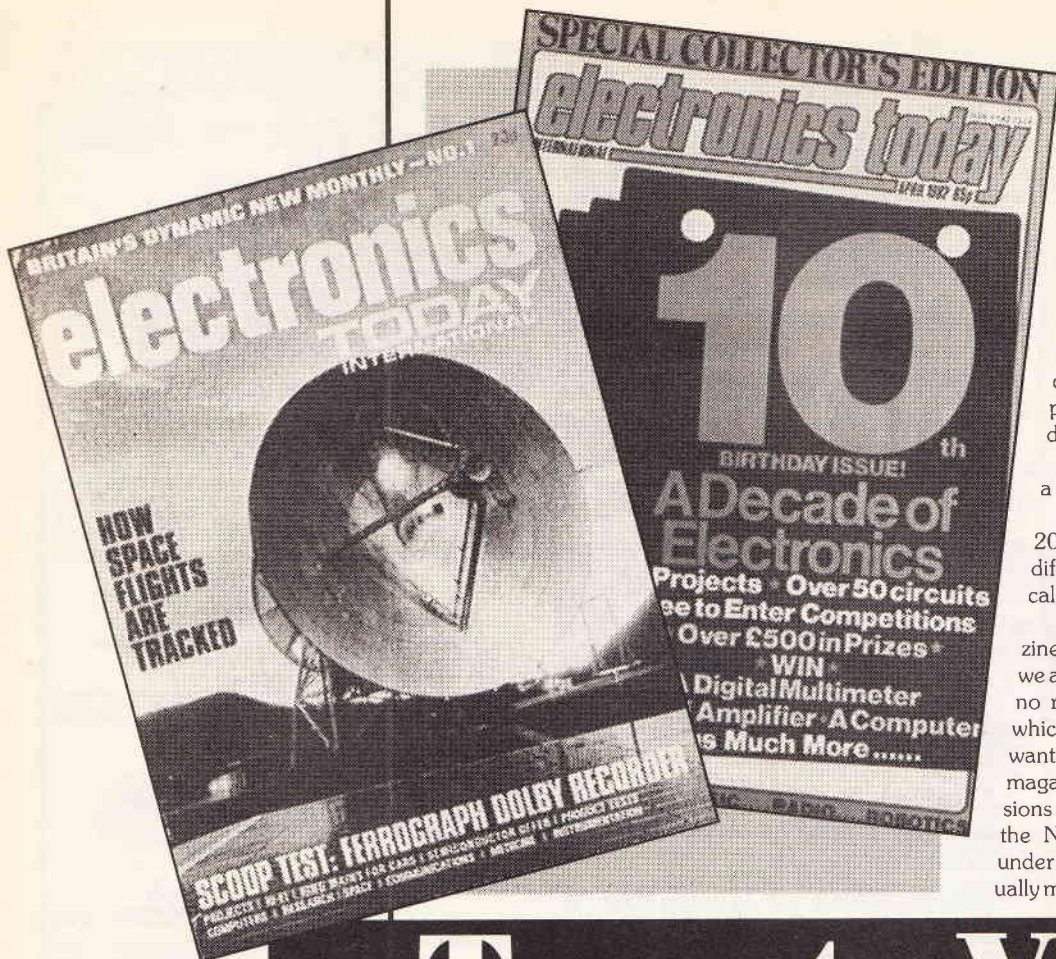Finally, I would like to thank all the advertisers and contributors for supporting us over the years and to you the reader for all your good wishes for the future. Happy Birthday ETI.



ETI. J & N Bull and Electrovalue appeared in the first edition and a little later Maplin Electronics appeared. Do you remember a company by the name of Sinclair Radio-nics? Products like the Z30 & Z50 amplifiers and not forgetting the ZX80 & 81 and Spec-trum computers appeared in the magazine. They have come and gone at a speed which made us all well aware of the pitfalls of devel-opment, marketing and entrepreneurial suc-cess. It taught us all about the risks involved in producing a product with a 'built-in' redun-dancy time. Anyway enough of this!

It's time to hand over to Keith Brindley for a few historical words.

Thanks Paul. Now, a few words for ETI's 20th Birthday issue. There's so much to say, it's difficult to know where to start. Perhaps the logi-cal place is right at the beginning.

ETI was an offshoot of the Australian maga-zine of the same name. ETI Australia, or 'Oz' as we affectionately knew it in the UK office (bearing no relationship to that other Australian import which raised more than a few eyebrows at the time), wanted to branch out by opening editions of the magazine worldwide. These editions included ver-sions in the UK (our own ETI), Canada, France and the Netherlands. Originally, these exports were under editorial direction from Australia, but event-ually most became free-standing. ETI UK was origin-

Twenty Years

Paul Freeman and Keith Brindley take a brief nostalgic look at your favourite mag

Well here we are still after twenty years. The revolution in technology has been unrelenting in its progress and ETI has reflected the trends irres-pective of the varying economic cli-mate.

But let us take a brief nostalgic look at what appeared in the first UK edition of ETI.

The issue contained 88 pages of features, pro-jects, news, reviews and product tests, the features tak-ing front position over constructional articles. The diversity of reported technology certainly made it a magazine to stand above the rest and it has been argued that it is still the case.

Hi-fi was there at the very beginning with outlines on how to put loudspeaker cabinets together including a bass reflex design, tests on Dolby noise reduction, room acoustics and a product test on a Ferrograph tape recorder, to say nothing of LP music reviews.

Projects included an oscilloscope callibrator, wide range voltmeter and a power supply. Tech Tips also appeared in this first issue.

Astronomy and cosmology has been featured very much so in the early days and the first mag cover led us into the subject with an article on space tracking stations.

The most striking change over the years must surely be the way we see women portrayed in what still appears to be a male dominated subject. Beautiful girls appeared to sell products or presented themselves to brighten up a very dull picture. Could we get away with it these days without a tirade of abuse? I wonder what Halvor Moorshead and Ron Harris, past editors of ETI would think about it now!

Some advertisers have maintained a loyalty to

ally owned by Modern Magazine Holdings, later to become Modmags, from there being bought by the Argus Press Group and forming the figurehead maga-zine published by Argus Specialist Publications. All that's historical fact — but what of the underlying per-sonality of ETI?

In the UK at least, ETI was a new type of electro-nics magazine altogether. It eschewed the boring, tex-tual styles of the already established magazines such as Practical Electronics and the like, instead offering readers a whole new insight into modern methods and practices of electronics. As a schoolboy when ETI appeared, I was immediately attracted to its openness and clarity. Now I didn't have to read what stuffy old magazines gave me — at last I was getting what I really wanted. Projects I could use (with no valves!) integrated circuits I could experiment with, features which were up-to-date, and a style and format pleasing to the eye.

Most projects and features in the first issues were simple reprints of Oz issues. As such, ETI worked from a strong base, with only a small financial outlay. Much more could be packed into a single issue of ETI than in the rest of the competition's offerings put together. As I write this I'm looking at issue number one of ETI — I had to delve deep into my archives up in the attic to find it, but it was worth the time and proves my point. There are a dozen features on all sorts of topics, four projects, two product tests, reviews and news, together with lots of other information. Issue number one's cover, featur-ing a photograph of a space flight tracking station's dish antenna, is a sight to behold - even after all this time. All those other electronics magazines of the day must have rued that day back in April 1972, when ETI first hit the news-stands. I don't think they've really ever recovered.

From there, ETI simply got even better. After a number of editors had their turn, Halvor Moorshead took the helm and from there things began to rocket. Halvor realised that the competition was beginning to include the same sorts of things ETI had pioneered. He knew that to forge ahead and keep its position as the best, ETI's projects had to be manifold and varying, and its features had to be even more dynamic and topical. He set up a four-man project team to design, build and test most of the projects ETI published — a fact which allowed ETI to present projects of a consistent quality every month. He trained up a youthful editorial team to research and write exceptionally readable features — just the features readers wanted. These were brilliant and progressive ideas which soon made ETI the nation's number one electronics magazine.

It was at this time I first became associated with ETI. I joined the project team as the fourth man, early in 1979. The team, under the lead of Ray Marston, had the brief to fill ETI's pages with excellent projects, as well as those of two sister magazines Hobby Electronics and Computing Today. It was hard work, but great fun. I consider myself most fortunate to have been involved with ETI at this stage. Things I learned then have stood me well in my freelance days since.

At the height of ETI's popularity back in 1980 Halvor left to run Canada's ETI, and he's there still I think. I know that magazines are occasionally swapped between international offices, so if you're reading this Halvor — thanks! Thanks for knowing what would make ETI the best electronics magazine, thanks for making ETI the best, and thanks for being the best boss I've ever had.

After Halvor, ETI has had a succession of editors: Ron Harris, Dave Bradshaw, Gary Herman, Geoff Bains, Jez Ford and now Paul Freeman. I don't think

I've missed any out, if I have I'm sorry. Each editor has given to ETI his bit of personal style, adding many excellent new ideas, but the legacy of Halvor's original purpose has run throughout — it's an electronics magazine which the rest strive hard (but fail) to follow. ETI has the best projects, the best features, the best electronics information, the best contributors and the best style of any.

As for the future, Paul has smashing ideas for ETI. He has maintained the ETI standard throughout the newstrade recession and knows what ETI has to do to keep its position in the marketplace when the recession ends. ETI's still in the best of hands, and looks destined to set new records and break even more new ground. There's no let-up for the competition, yet!

So — Happy 20th Birthday ETI — I'm proud to be associated with you. May you lead the field for (at least) the next 20 years, too.

Thank you Keith. Now, back to the future, Ron Harris asked in the tenth birthday issue what ETI would include at the grand old age of 21. Although a year away, I would say ETI will very much reflect the digital world, presenting features on the latest developments in digital disc recording of data, video and audio, the combined interactive media experience, forming standards for digital television and the decline of the cathode ray tube. I am sure we will also be reporting further on the communication revolution and the reduction in the need for business travel. We have not reported yet on man-made growth of computer memory, but I'm sure we will — All in good time.

So to end, I am pleased to be associated with this anniversary of the magazine. Although ETI has many plans for the future, one thing is certain, the spirit of the magazine's initial concept will remain, that of technological diversity.

Congratulations

ETI

on your
anniversary

From another 20 year old.



**Toroid Transformers
Amplifier Modules**

Congratulations

ETI

**Your readers have supported us ever since
OUR advert in YOUR first issue. Obviously
they know a good thing when they see it**

Electro/alue

129 page A4 Catalogue
Send £1.50, refundable

28 (BP) St Jude's Road, Englefield
Green, Egham, Surrey TW20 0HB

Phone 0784 433603

Fax 0784 435216

CIRKIT DISTRIBUTION LTD

PARK LANE, BROXBORNE, HERTS EN10 7NQ

TEL. (0992) 444111 FAX. (0992) 464457

*Cirkit would like to wish
ETI a very happy 20th anniversary
and look forward to enjoying a
mutually successful 1992!*

OPEN CHANNEL



ETSI is an acronym we'd all better be learning. It stands for European Telecommunications Standards Institute. Note the wording here: telecommunications standards, not television standards, not consumer electronics standards. But plain and simple telecommunications standards! This is pretty important, which is why I've stressed it and laboured the point.

Now let me explain. ETSI wants to make a standard which defines satellite television dish size as a minimum of 80 cm. Hmm, think about it. If ETSI gets its way new services will have to be designed around an 80 cm dish. Old services like Astra, naturally, won't have to force its users to have 80 cm dishes, so on the face of it there's no concern to the millions of viewers watching Sky TV and the rest of the Astra programmes.



But, when you look deeper, what the 80 cm standard will mean is that more directional dishes are being used. An 80 cm dish has a beamwidth of about 20, while a 60 cm dish beamwidth is around 30. So, if a more directional dish is used, satellites can be more closely spaced around the geostationary orbit. Currently, they're about 30 apart, but future satellites could (and most certainly will) be placed a lot closer. Result is potential interference between satellites if a dish with too high a beamwidth is in use.

So, all these millions of Astra viewers may very well end up with interference on their systems, and so be forced to install a larger dish! Can you just imagine this. Within a year there's probably going to be over 4 million Astra watchers — most with 60 cm dishes. In two years there's likely to be double this, if current rates of sales keep going. What are we going to tell all those viewers when satellites positioned too close to Astra start transmitting and causing chaos to current picture quality? We're sorry, but this daft French organization said 80 cm dishes have to be used?

The whole problem is getting out of hand. ETSI is a pressure group on the European telecommunications scene. Its standards are by no means legally bind-

ing on any manufacturer, broadcaster or user. But ETSI aims to get this standard incorporated into national laws throughout Europe.

ETSI, however, is just a telecommunications institute. As I pointed out earlier, it is neither a consumer electronics institute nor a television institute. So what it seems ETSI is trying to do is get a standard which affects all satellite users made into law effectively by a backdoor route. So what are Soci t  Europ ene des Satellites (SES — the owners of Astra satellites) and broadcasters such as B Sky B doing about trying to stop ETSI? Well, there's nothing they can do. Because ETSI is a telecommunications institute, and they're television and consumer electronics companies, they have no say over what ETSI decides about telecommunications issues. Apart from being a little strange, this is downright underhand. ETSI is an organization which has proved itself to be obviously either unaware of television and consumer electronics issues, or maybe wanting to do something specifically for one type of satellite owner and not for another.

You see, the problem is really only a problem because Eutelsat (the European telecommunications satellite organization) wants to setup a network of satellites spaced around the geostationary orbital arc. The problem has been recently highlighted by Eutelsat's positioning of a high-powered satellite at 16 East of South. Astra is positioned at 19.2 East of South, so there should be little problem for dishes of even 30 beamwidth (ie, 60cm). Actually, six of Astra's transponders are affected, but as they're not currently used don't create many headlines — Astra just can't use them!

But Eutelsat wants to position a high-powered satellite at 21.5 East of South, too — which will definitely cause interference problems. Now we're beginning to get the picture — ETSI's desire for an 80cm standard seems to fall neatly into Eutelsat's requirements, doesn't it?

There is a far better method of using satellites, which SES itself has pioneered — that of co-locating satellites at the same orbital position. SES already has two satellites located at 19.2 East of South, and plans at least another two. Why, oh why, oh why then does Eutelsat need to go gallumping around the sky, putting up satellites in different orbital slots, using up valuable airspace and interfering with existing satellite transmissions?

If Eutelsat was judicious and fair about the process it could co-locate as many satellites as it wants at, say, 160 East of South or (better still) 130 East of South. Alternatively it could use transmission frequencies which did not interfere with Astra transmissions. There'd then be no interference problem.

If ETSI was judicious and fair about television and consumer electronics' use of satellites (and remember they do not have a voice in the ETSI institute!) there'd also then be no problem.

ETSI is to have decided on the proposed standard by the time you read this. Let's hope it sees sense. Let's hope its decision does not appear to give an unfair advantage to Eutelsat. Let's hope we don't all have to strip out our 60 cm dishes and replace them with larger ones.

I'll keep you posted.

Keith Brindley

WORLD'S FIRST 16.5-INCH WIDE VISION AND MULTIMEDIA COLOUR LCD



Sharp Corporation, the major Japanese electronics manufacturer, has developed the world's first wide-vision and multimedia compatible 16.5" colour TFT liquid crystal display. This new big-screen LCD is also compatible with VGA computer software.

The display offers crisp, clear imaging on a high-density, high-resolution screen incorporating more than 1,228,000 pixels. Colour reproduction is exceptional across a range of 16.7 million tones. The new LCD provides the substantial advantage of multimedia compatibility, an important technological advance. The first in the world to offer this capability, it can reproduce not only clear colour computerised graphics, but the animation and natural colours of A/V images. This achievement is due in part to the development of:

- a new high-speed digital driver
- high-speed digital processing technology for video images and computer signals

- new thin-film construction technology for even reproduction over a large area

- lower resistance source and gate-bus lines


As the world's leading manufacturer of LCDs, Sharp continues to develop and commercialise advanced LCD products. The

company produced the world's first 14" TFT LCD in 1988 and has since led the field in large-scale LCD imaging, including such innovations as an HDTV LCD projection system and true wall-mount 8.6" televisions. From the first mass production of LCDs 19 years ago, the Sharp LCD busi-

ness has now grown to annual sales of over £500 million.

Basic Specifications: Screen size 16.5", wide aspect; Pixel structure 853 x R,G,B x 480; Number of pixels 1,228,320; Pixel configuration RGB stripe; Display mode Normally white

16-BIT MICROCONTROLLERS FOR PORTABLES

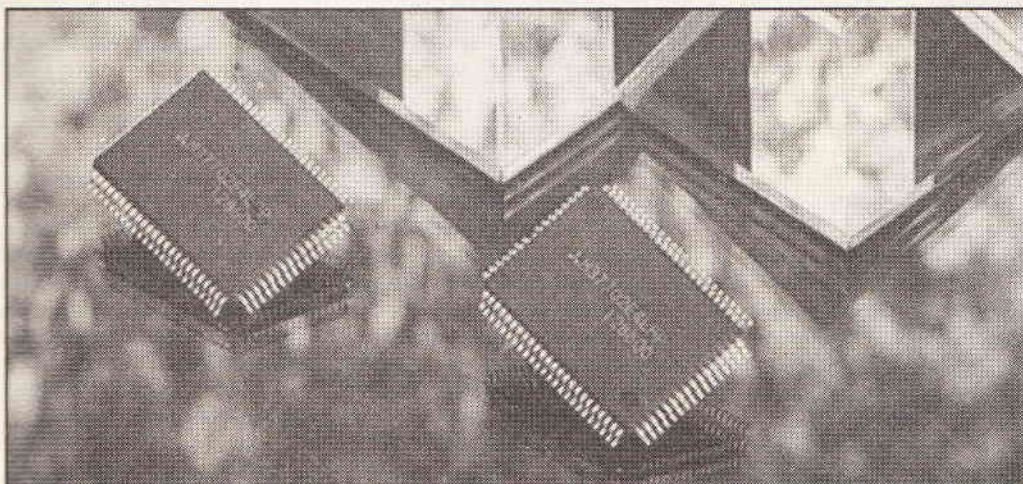

Mitsubishi Electric is announcing the launch of a new series of 16-bit, 7700 single chip microcontrollers which provide processing solutions with low battery requirements for portable applications. Included particularly are telecomms, such as CT2 and

GSM, as well as portable computing and office automation equipment such as palm top, laptop and notebook PCs.

The high performance CMOS devices operate over a wide temperature range of -40 to 85°C as standard, from power supplies

ranging from 2.7 to 5.5V. Typical consumption is just 12mW at 3V and 30mW at 5V. Instruction execution time is a fast 500ns and the chip operates at 8MHz.

The low power microcontrollers come in 80 pin quad flat packaging with 68 programmable

I/Os. Features include 16Mbytes of addressable memory together with three instruction queue buffers and two data buffers for high speed operation. The 16-bit central processor is easily switched for 8bit processing to provide speed optimisation and memory savings.

A basic instruction set of 103 is provided with 19 interrupts at seven levels. Also on-board are a multiple function 16-bit timer and two UARTs which can operate either synchronously or asynchronously.

An 8bit analogue to digital converter provides eight channel inputs and up to 68 I/Os are user programmable. A 12-bit watchdog time is also provided.

For further information, please contact either Christine Warren or Chris Marnoch at Mitsubishi Electric UK Ltd, Tel: 0707-276 100.

CAMCORDERS RECORD IMPRESSIVE GROWTH

Although the market for electronic goods may be depressed at present, one product which seems to have escaped the worst effects of the recession is the Camcorder.

A recent report shows how demand for camcorders has grown. In 1985 the market was worth just £64 million. 1991 saw this figure grow to £378 million

and it is predicted that just under £600 million of camcorders will be sold in 1995.

Because of its restricted consumer base, (65% of owners are ABC1 social groupings), the camcorder market has escaped the worst effects of the recession.

Product developments, price reductions, and the user friendly feel of the camcorder are all help-

ing to expand ownership. And with household penetration standing at only 5% there is plenty of scope for expansion, the report states.

Innovations such as the 'palm' corder and the new compact 8mm format not only attract new buyers but also mean that existing owners trade up. It is thought that 20% of all purchases are now replace-

ments.

Elsewhere in the electronics market new developments are helping to pull the sector out of the doldrums. Radio sales have been boosted by the BBC's change in programme frequencies.

HARD COPIES FROM VIDEO


The TP6490 Video Printer from Thurlby Thandar offers 64 tone gray scale printing and has a built in frame buffer which allows multiple copies to be printed.

It incorporates a programmable control panel with a 32 character LCD readout making selection of the printer facilities easy.

The TP6490 includes a Universal Video Interface which will accept most video signals including PAL, SECAM, CCIR, NTSC and RS170.

Unlike most dot matrix printers the TP6490 will print exactly what is showing on the CRT without the need for complex interfaces or special software. The print time is very fast.

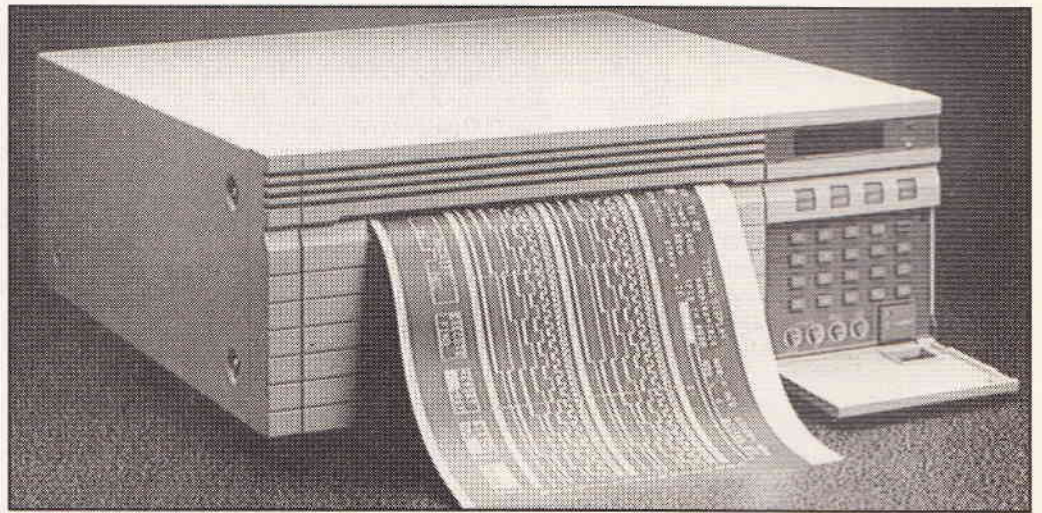One of the major advantages of the printer is that it can be connected with high frequency dot



clocks up to 90MHz as used on computer workstations.

Applications for the product are broad and include medical,

military, computer and video industries. In fact wherever there is a need to take hard copies from a display or at video level.

For further information please contact: Thurlby-Thandar Ltd, Tel: 0480 412451



POCKET-SIZED TONE DIALLER PAD

A universal key tone pad which emits audible Dual-Tone Multi-Frequency (DTMF) encoded signals has been added to the Maplin Electronics fast expanding range of communication products. The pad serves a growing number of products and services which are steadily coming on-stream in the UK, and which require the use of tone signalling over the telephone line. These items include answering machines, home banking facilities, home shopping and computer based services.

The pocket sized key tone pad allows the user to enter the DTMF tone codes required by many such services. Having accessed the service by dialling a line in the conventional manner, the speaker of the tone pad is placed over the microphone of the telephone handset and then the DTMF encoded numbers are transmitted to the receiving device. The unit is powered by two AG13 type button cells supplied. The tone dialler pad (order code ZB19V) costs £8.95 (to incl vat).

ELECTRONIC WATCH-DOG

The Maplin Electronics new Velleman Kit, electronic watchdog is designed to scare away intruders from your household and the surrounding area. The circuit unit generates a realis-

tic barking sound, with a sensitive ear to what's happening around. The sentinel never sleeps, and doesn't ask for much: only a 2x8V transformer or an (unstablied) 9-12V DC power supply.

One may disagree about the best deterrent against burglars, but one fact is true; a frightfully barking dog brings most villains to

their senses. However the kit doesn't need walking, feeding or even a licence.

It features a choice out of two

different dogs with realistic sound using a random generator. It has an adjustable sensitivity control for noisy environments.

The Velleman Kit (K2655) costs £29.95. (including VAT)

DATA DISCMAN 'ELECTRONIC BOOK' FROM SONY

This spring sees the appearance in UK high streets of the first in a new generation of multi-media communications products. Thanks to the Sony Data Discman, both the British business community and the public at large will be able to equip themselves with a revolutionary means of accessing and presenting information, while the publishing world will gain a powerful new 'paperless' communications medium.

A hand-held electronic 'book' (weighing just 705 grams) capable of displaying text, graphics and replaying audio, the Sony DD-1EX Data Discman offers rapid access to the right information whenever and wherever it is needed — and with over

can be confident that their Data Discman can accommodate the additional 85 plus EB titles available from the US, Japan and mainland Europe. Such is the enthusiasm of the publishing community, Sony is confident that around fifty discs sourced from Britain will be on the market within twelve months of the launch.

Data Discman reads CD-ROM discs adhering to the globally-recognized Electronic Book (EB) Standard. With an impressive 200 Mb data capacity, it provides the equivalent of 100,000 pages of A4 text or 32,000 visual images (or any combination of the two). A single 8cm CD-ROM can accommodate the same amount of in-

multi-media systems, CD-I (Compact Disc Interactive) the recording Mini-Disc and even satellite-based 'GPS' Geo-Positioning Systems. For both publishers and those buying the new EB standard software, one thing is certain — EB titles available for first generation Data Discman products are set to be compatible with all of the exciting future hardware developments that Sony and other hardware signatories may have in the pipeline.

Data Discman's 'human interface' consists of a QWERTY keyboard, cursor and function keys, while information is displayed as 10 lines of 30 characters or graphics via a 3.4" diagonal backlit LCD screen. Information can be

Discman's true international portability, and the command functions of the DD-1EX can be selected in any one of twelve languages.

Data Discman's prodigious information capacity lends it to a wide spectrum of business and professional users who need access to either 'off-the-shelf' information (such as dictionaries, maps and business directories) or their own customized data-bases. While Data Discman's UK launch is bolstered by a large international catalogue, Sony is particularly keen to assist corporate users who wish to create their own tailor-made 'books'. Typical custom packages might include stock inventories, price lists, corporate profiles or reports as well as 'expert systems' for legal, engineering and medical practitioners.

Sony's Data Discman product specialists were joined at the Design Museum press launch of Data Discman by Haydn Abbott, Managing Director of Sony UK. He said: "While the Sony name is intimately associated with the concept of personal products such as Walkman and Watchman, the significance of our 1992 Data Discman introduction in the UK is two-fold. As well as representing a breakthrough in personal information technology, it also heralds a radical challenge to the British publishing industry."

"The printed word's role in society is more potent than ever before, and it is now augmented by a complementary medium that unites text, graphics and audio in situations where words on paper alone can not suffice. As we all face the implications of a truly multi-media based future, publishers now have control over another dimension in the presentation and marketing of information. I look forward to the industry's response to this new and exciting opportunity for the Nineties."

The Sony DD-1EX Data Discman comes supplied with three EB titles as standard, plus a NiCad rechargeable battery pack, dry cell battery pack, AC adaptor and video cable. The unit is expected to retail at around £350 from April 1992. UK software prices are as yet unfinalised.



100,000 systems (plus more than 200,000 software discs) in daily use in Japan, Data Discman has already captured the imagination of both consumer and business professional alike.

EB (Electronic Book) software titles are many and varied and they include maps, business directories, reports on the world's top companies and even the complete works of Shakespeare. In April, over a dozen UK titles will be available, three of which will be 'bundled' with each Data Discman sold. However, given the international compatibility of the software, early British purchasers

information that on the printed page would occupy around two hundred telephone books. For extra versatility, the DD-1EX Data Discman can also play standard 8cm audio CD singles.

While the capabilities of its new baby are already remarkable, Sony is quick to underline that, the £350 DD-1EX represents just the first stage in the emergence of a new generation of Data Discman products. Well before the end of the decade, the Electronic Book standard will be just one strand within an interactive personal communications network incorporating advanced

accessed in any of seven ways via either individual words, keywords or word parts — or via a choice of other simple menu-based, cross-referencing and graphic search techniques.

The format's international compatibility is an important aspect of Data Discman: not only will EB software sourced from all over the world perform in any unit, but a multi-standard composite video output enables the device to be connected directly to a monitor or video projector of any television standard for large screen presentation. A multi-lingual capability is central to Data

FIRST EUROPEAN MINI DISC PRODUCTION WILL START IN AUTUMN 1992

Sony have announced that production of pre-recorded Mini Discs (MD) will start at their Austrian plant, in Autumn 1992.

29 years after the launch of analogue compact cassette tape and 10 years after the market introduction of the Compact Disc, the Mini Disc is a revolutionary

record/playback audio system that combines the portability and shock-resistance of analogue, compact cassettes with the sound quality, quick random access and easy operation of CD.

The Mini Disc system offers more than one hour of digital audio playback and recording on

a 64-millimetre (diameter) disc.

Sony believes that the Mini Disc will meet the consumers demand for portability, recordability, quick random access and high quality digital sound, thereby creating a new portable, personal stereo market for both hardware and record industries.

Sony will start to manufacture pre-recorded Mini Discs worldwide in facilities in Japan, America and Europe with a starting capacity of approximately 1.5 million units per month in the second half of 1992.


FLEXIBLE EPROM PROGRAMMING

UK programmer manufacturers Ice Technology are able to offer very flexible solutions to many different gang programming requirements. Their systems are based around the Speedmaster 8000 programmer, which can operate either linked to a PC or in stand-alone mode. The base unit can programme EPROMS up to 32 pins, while systems can be built around this unit to programme Micro-controllers,

Programmable Logic Devices and PLCC devices.

The Speedmaster 8000 is one of the fastest, if not the fastest gang programmer around. Using manufacturers approved algorithms, it can programme eight 27C256 Eeproms in around 5 seconds. Set programming is also a feature.

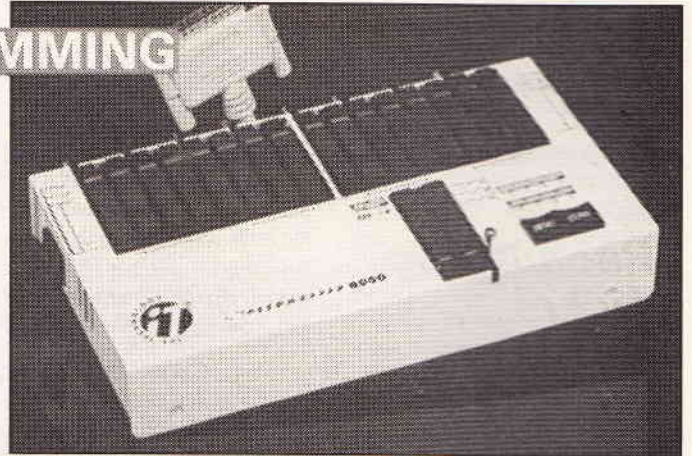For more details contact Ice Technology Ltd on 0226 767404.



MORE HI-TECH IN THE HOME

Personal fax machines will soon be seen in homes and cars across Europe — and they will be manufactured in the North of England.

The Korean giant Samsung Electronics has set up the first manufacturing plant in the North to produce personal fax machines for the European market. The

£4.5 million investment is being made at Samsung's Billingham factory in Cleveland, which was set up in 1987 to manufacture microwave ovens and video recorders. It is the third investment at the Cleveland site to be made by the company.

Samsung's UK Managing Director, Mr Chan Bae said: "The

home fax machine will help improve communications for the businessman or woman, ensuring that no opportunities are missed in the competitive business world of the nineties. Samsung are ensuring that they are leaders in the field."

Support in bringing the investment to the North of England was

given by Northern Development Company — both in England and Korea — and by Cleveland County Council who provided financial assistance towards the project. Regional Selective Assistance has been approved for the project by the Department of Trade and Industry.

ACCELERATOR CARD FOR WINDOWS 3 NEURAL NETWORK PROGRAMS

Neural Computer Sciences has released a plug-in accelerator card for PC AT-compatible computers which provides a more than 100-times increase in performance of its Windows 3 neural network package, Neural Desk. The card provides the means to speed dramatically the 'training' of neural network artificial intelligence programs. It will also improve the performance and response time of installed programs dealing with particularly complex problems. Neural Computer Sciences believes that the £1500 card — working with the Neural Desk provides industry and commerce with one of the most cost-effective approaches to artificial intelligence in the world today.

Based on a 32-bit digital signal processor, the 25Mflop accelerator card implements the algorithms required for Neural Desk to

make over 300,000 neural connections/second; this is more than 100 times the performance of the package when running on a typical 386/387- or i486-based PC. The board plugs into any ISA/PC AT-compatible expansion slot.

This means that the training of a neural network — the process whereby the package learns the correct responses to input data by running real-life examples and optimizing its responses — can be accomplished very rapidly. Training time can be significant when a network is developed to deal with a large number of input variables. Examples of applications involving many inputs include intelligent process control systems and speech recognition; both training and the response times of the program in use would benefit from the installation of the accelerator card — as would defence-oriented applications such as pattern rec-

ognition. Another key application area is where a neural network needs to be regularly re-trained in a short space of time — for example, the accelerator card could allow a network used to predict stock exchange movements to be re-trained overnight using large volumes of the latest trading data.

Until now, neural networks have largely been the preserve of scientists, because of the substantial programming effort and computer power required to implement and run them. Neural Computer Sciences realised that modern PCs, such as those with 386 processors and the new graphical user interfaces, provided the basis for making the technology available to non-specialist users, and developed Neural Desk. This provides artificial intelligence support in the form of a Windows 3-based package for PCs.

The software's unpreceden-

tly simple graphical user interface allows it to be applied quickly and easily to assist with many daily tasks, providing fast, intelligent help for complex and problematic situations. Released in late 1991, Neural Desk is the first complete neural network package for Windows 3, and offers everything required to develop, train, and run applications, including the availability of a low-cost run-time module for embedded applications. The result is a highly powerful neural network tool which can be applied to problems without conventional programming skills. The new accelerator card substantially extends the application range for Neural Desk, taking it into the topmost layers of artificial intelligence applications.

For further details please contact Brian Kett, Neural Computer Sciences, Tel: (0703) 667775.

BLUEPRINT

Blueprint is a column intended to provide suggested answers to readers' electronics design problems. Designs are only carried out for items to be published, and will not be prototyped by the columnist. Circuits published in Blueprint are believed to work, but may need minor alteration by the reader after prototype. Individual correspondence will not be entered into, save as necessary to prepare items for publication.

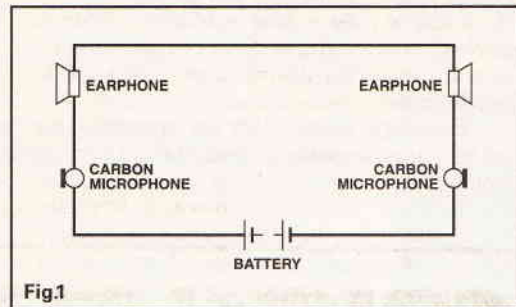


Fig.1

Dear Blueprint,

I have been trying to design a cheap intercom for use in concert situations between the sound desk and a stage assistant. It is difficult because only three cores are available to connect the two stations. My amplifier design uses a 9-0-9 power supply, so that at first glance five cores appear necessary.

One idea I have is to modulate the -9V supply with one signal, and the +9V with the other. Would this work, and is there a better way to do it.

Jamie Ogden
Hemel Hempstead
Herts.

This is a problem which was addressed in the early days of the telephone. Figure 1 shows a simple telephone type intercom which will work effectively. Unfortunately it suffers from the problem that when you speak into the microphone your voice is very loud in your own earphone. This gives rise to a tendency to speak too quietly for the person the other end to hear properly.

The design of the old style of telephone, in use for a long time, incorporated a circuit of the type shown in Figure 2. This uses the primary winding of the transformer to balance out most of the signal passing from local microphone to earphone, without reducing the signal from the other end. The correct amount of sidetone, as it is called, balances the tendencies to shout because one cannot hear one's own voice in the earphone, or to whisper because the sound in the earphone is too loud.

The way this works may not be immediately obvious, so consider what would happen if the centre tap of the transformer were connected directly to

ground. In this case, V2 would be of the same amplitude as V1, but inverted. If the centre tap were not connected at all, then V2 would be in phase with V1. At a particular value of R, the two effects balance and no signal is passed from V1 to V2. In practice the circuit is not balanced exactly because a little sidetone is beneficial.

Active Cancelling

Modern telephones achieve the same effect by using low power active circuitry. We can do the same to make an intercom.

To minimise the complexity, I have not attempted to make this work with only two cores in the way that telephones function; I have used the three cores stated to be available. The connections between the two intercom stations are then: positive power supply, 0V, and bi-directional signal.

Figure 3 shows the signal splitting circuitry. Considering the case of a signal travelling from left to right,

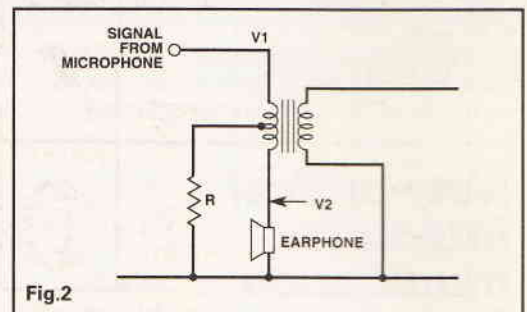


Fig.2

what happens is as follows: the signal from the microphone is amplified by IC1a. The gain of this stage may need to be varied to match whatever microphone is in use. To increase the gain, increase the value of R4; to reduce the gain, reduce the value of R4.

The signal from IC1a is fed to the bi-directional signal line via R5. The signal on the line is half the amplitude of the signal on pin 1 of IC1, because it is potted down by R9 and R5. This is true whether or not a completely separate signal is travelling in the other direction.

The half-amplitude signal on the bi-directional line is fed to IC1b, where a proportion of the output from IC1a is subtracted from it. If the values of R6 and

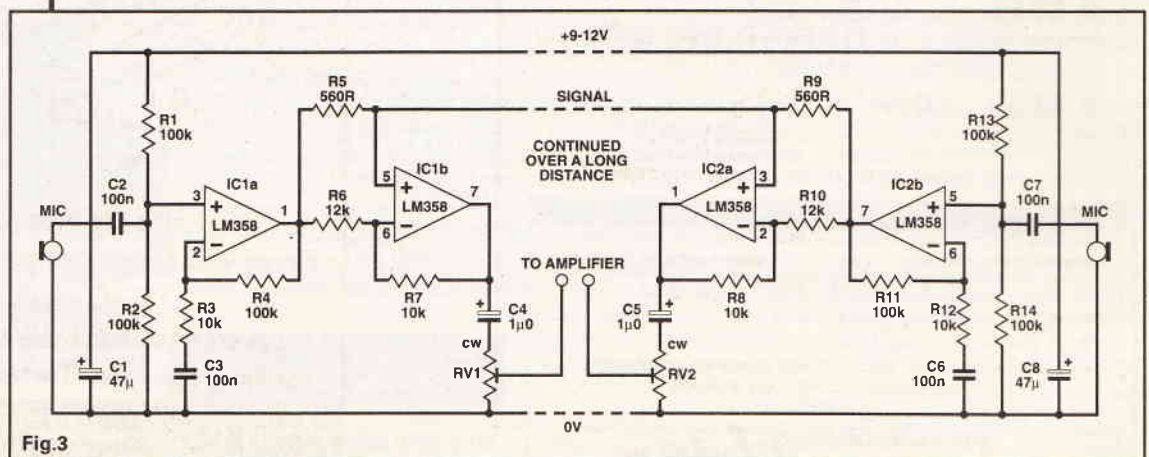


Fig.3

R7 were the same, then cancellation of the signal would be almost complete (with leakage only due to imperfections in the components). As it is, the output from IC1b consists of a small signal in phase with the output of IC1a, plus a much larger replica of any signal travelling in the opposite direction.

Exactly the same reasoning applies to signals travelling in the opposite direction, so that at each intercom station the dominant sound in the earphones is the signal from the other station. Just enough of the station's own signal is fed to the headphones, so you can hear what you are saying in a noisy environment. If extra sidetone is required, then the value of R6 should be increased.

The audio amplifier itself is not relevant to the understanding of how the unwanted signal cancellation takes place. For this reason, the amplifier circuit is shown separately in Figure 4. The LM386 connected

as shown in Figure 4 has a gain of 20dB which should be more than enough to amplify the signal sufficiently for even the noisiest environments. It is likely that, in practice, the volume controls will need to be turned well down.

Because the microphone signal is amplified before being fed into the cable, some extra immunity to the effects of noise is built in. However, if the cable carrying the intercom signal is to be run anywhere near to phase controlled lighting cables, then screen lead may be found to be necessary.

In common with all Blueprint designs, this is believed to be workable as drawn, but it has not been prototyped.

Andrew Armstrong

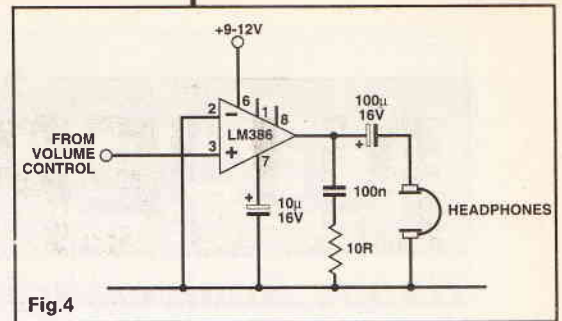


Fig.4

NEW 1992 CATALOGUE
FREE TO THE PROFESSION. PLEASE SUPPLY
COMPLIMENT SLIP/LETTER HEAD

CRICKLEWOOD ELECTRONICS

CRICKLEWOOD ELECTRONICS LTD, 40 CRICKLEWOOD BROADWAY, LONDON NW 2 3ET
Tel: 081 452 0161 Fax: 081 208 1441


BOOKS 	BOXES & CASES 	CABLE & WIRE 	CAPACITORS 	CONNECTORS 	KITS
RESISTORS 	SEMI-CONDUCTORS 	SPEAKERS 	VIDEO HEADS 	SWITCHES 	TOOLS & BENCHMARK

SEND NOW FOR THE **CRICKLEWOOD ELECTRONICS** COMPONENT CATALOGUE
ONE OF THE BEST RANGES AVAILABLE

Name

Address

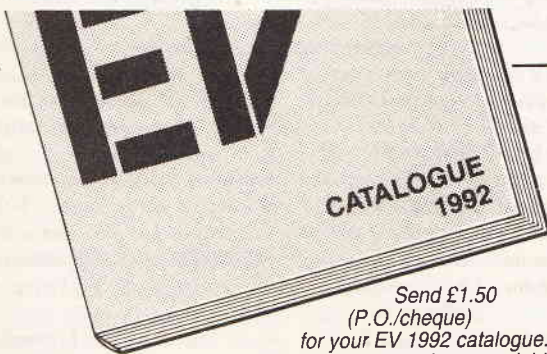Please send copies of Cricklewood Electronics Catalogue at £2.00 each. Cheque's payable to: Cricklewood Electronics Co.



Send £1.50 (P.O./cheque) for your EV 1992 catalogue. Includes £1.50 voucher spendable on orders upwards of £10.

The CATALOGUE
120 pages, A4. Expertly presented and illustrated. Easily referred to. Packed with valuable information.

The COMPONENTS
As wide a choice as you could wish — semiconductors, surface mounting, opto-electronics, Rs & Cs, etc. etc. Top quality; fairly priced.

The SUPPLIERS
Siemens, Boss, Cliff, Omeg, Lorlin, R.S, Uniross — to our top quality standards.

The SERVICE
Prompt, personal with customer satisfaction guaranteed. Access/Visa facilities


Electro/alue

28 (B) St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB
Phone - 0784 433603 Fax - 0784 435216

PICO ADC-10

8-bit Analog to Digital Convertor for IBM PCs & compatibles
• 10-25 kHz typical sampling speed
• 0-5 v input range

£49
+ VAT
(including p+p)

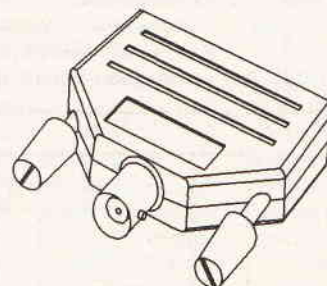

- Plugs directly into parallel printer port
- Requires no external power or expansion slots
- BNC input connector
- Supplied with software to use as a voltmeter & oscilloscope, plus Turbo C and Pascal drivers

Pico Technology Limited
Broadway House, 149-151 St. Neots Road,
Hardwick, Cambridge CB3 7QJ
Tel. 0954 211716 Fax. 0954 211880

Happy Anniversary

In response to your Editorial in the January issue I send my greetings in readiness for the 20th anniversary, and best wishes for another twenty years of your excellent magazine.

As author of the Digital Scoreboard and the ETI Digibaro (and numerous Tech Tips of course — keep them coming everyone!), I have played but a small part in the history of this illustrious publication, surely the best of its kind. (To think that I nearly published in another magazine when ETI turned me down first time — smack hand!). I'm afraid I cannot claim to have every issue, I started around year 5, and I have had to consign them to the basement of my local electronics shop for reasons of

space.

On the subject of the Digibaro, I had a letter quite recently requesting the program for the EPROM, so I know ETI projects get made, even some years after publication. Technology moves on a pace, of course, as does the public perception of what it should be able to do. A revised Digibaro, maybe battery powered LCD and easier to calibrate, might be of interest if ever I can find the time to design it.

To look into the future, the trend in semiconductors, and hence projects, is greater sophistication for little increase in price. We might expect to see some dramatic changes in the level of technology available to the amateur in

the next 20 years, just as we have in the last 20 (or even the last 15 — check out the 5th anniversary issue if you have it!).

There are going to be problems, though. More powerful ICs require special handling — you should see the lengths I go to to get heat off their mainframe PCBs. On a more basic level, more and more devices will only be available in surface mount packages, which are terribly difficult to deal with even for small to medium sized companies, let alone the amateur. One thing I am sure about is that the enthusiasts won't give up, and somebody somewhere will come up with a solution.

Finally, a word in reply to Mr

Henning (Read/Write, January issue). I too have considered the problem of detecting whether a door is secure, not just closed, and it seems remarkable to me that nobody I am aware of has implemented a solution. The idea I came up with is to embed a microswitch in the door frame, so that when the door is locked (or just latched), the bolt actuates the switch. This would detect doors that are not locked, or could be made to sound the alarm if someone even tries the handle.

So, Happy Birthday ETI, and long may you live.

**Ken Wood,
Ipswich.**

Many thanks for your kind words Ken — Ed.

MIDI Origins

Regarding the article by Mike Meechan, on Digital audio mixing consoles.

So MIDI is proprietary to Yamaha, is it? This will come as a bit of a shock to the hundred or so other manufacturers who have merrily been building it into their products for the last nine years. Yamaha should clean up on royalties if they decide to apply them retrospectively.

Runs at 19.2kBaud does it? Yet another blow for the design boffins who have unanimously been running it at 31.25kBaud.

One wonders where Mr. Meechan has been hiding since October 1982 (the date the MIDI specification was made public), that these basic facts have eluded him.

Well yes, it is similar to RS232 but then so is almost every other serial data protocol run through cable. This is as useful as saying a car is a box with a wheel at each corner, (so is a shopping trolley) it's a factual statement that conveys very little information.

To be frank, I am surprised this stuff survived the editorial knife, but it does rather cast doubt on the veracity of other statements in this apparently informative article.

More vigilance, more fact checking, less misinformation please, (I educate people in Technology of Music and my job is easier if I don't have to 'deprogram' those students who believe

everything they read in a magazine).

G Wilkie, London.

Mike Meechan replies:

Taking your points in the order they were made.

After I received your letter, I contacted Yamaha (K) Research and Development in London. The Japanese chap to whom I spoke explained to me that Yamaha had indeed pioneered the original MIDI interface code back in the early eighties. Subsequently, there was a meeting of other major musical instrument manufacturers— Oberheim and Roland among them — and the first MIDI specification was created. Each manufacturer present then developed different parts of the specification. The MIDI 1.0 spec is formulated by joint agreement of the different manufacturers involved and ratified by the International Association and the Japanese MIDI Association (JMSc).

With regards to the 19.2kBaud statement, meâ culpâ, although it was more of an old truth than an untruth. Not being of a musical instrument-playing disposition, my only contact with the word and concept of MIDI apart from when I was researching and designing the AutoMate mixer for the anniversary issue of the ETI was in music equipment manufacturers' literature. The 19.2kBaud figure

mentioned was part of the original and quickly superseded specification. I later found that the up-to-date spec showed 31.25kBaud and informed the Editor of this fact but it was unfortunately past the copy deadline for the issue in which this erroneous statement was issued and it had to remain. Finally, on the point of associating the MIDI protocol with that of RS232, I have to say that I beg to differ. I maintain that the statement referred to is only of very little significance to someone who would most probably find the whole article very simplistic and of little relevance when compared to their own breadth of knowledge in the subject. I should like to point out that the series was entitled Introduction to Audio Mixers, with great emphasis on the elemental and rudimentary nature of the text. It was not pitched at Music Technology lecturer level. If I had said the that MIDI was similar to the Rascal SCORE method for machine interface (Serial Control Of Rascal Equipment) which is also an asynchronous, serial but little-known data protocol, I think that the criticism might have been justified.

However, many people who know little of musical instruments or MIDI but who are interested in mixing consoles and audio in general and who know that RS232 is a medium speed, serial, and asynchronous protocol (like

myself) and may have heard of MIDI mentioned in a music context would, I hope, have been able to easily associate with this statement.

I could have proven the veracity of other statements in the article by including some complicated Fourier Analysis, transforms and convolutions. I refrain from doing so in the interests of keeping the text in a manner that I thought would be interesting and available to a much wider section of the readership of ETI. The Automate Mixer project which I have developed for ETI and which is featured in this issue goes into this sort of depth. In any case, I am sure that you would have been more than willing to highlight any further gaffes on my part. It is a sad fact of life that all of the magazine contributors are human and therefore fallible and prone to the odd mistake.

Hiding? For nine years, Mr Wilkie? Indeed not. I have been busy formulating a fiendishly cunning ten-year plan for world domination. It entails programming individuals with the word "MIDI — 19.2kBaud" whereupon they become mindless zombies completely under my control... Now, Paul, pass the dark glasses and false beard so that I can slip quietly away... click... slip quietly away... click... slip quietly away.

ETI Provides Circuits For Development

I have been a reader of ETI since I went to University to study electronics in the mid 1970s. I found ETI a valuable counterbalance to lecturers whose idea of electronics was sheets of complex maths ending with the throwaway remark that "if the first function had represented the input signal and the second the transfer function of the circuit, then the answer would represent the output".

I rarely built ETI projects as published, but took pieces of circuitry or sometimes just ideas to help design gadgets tailored to my own needs. So did my friends. It was the assumption that others might like to do the same thing which gave me the idea for the Blueprint column.

In the early days of ETI electronics was a younger and more widespread hobby, and there was

more scope to build for oneself things which were not available commercially, or which were much more expensive to buy than to build.

Nowadays that is less true, with many imported Japanese products costing less than the price the amateur would pay for the parts. However, there still are, and will be for the foreseeable future, areas in which personal construc-

tion scores: in audiophile equipment, in interesting gadgets which are not commercial, and in areas too specific for a commercial product to fit the bill.

I hope that ETI will continue to provide interesting projects and technology articles for the next twenty years.

**Andrew Armstrong
Leighton Buzzard**

24V Power Supply For Generator

In the Republic of Ireland, the Electricity Supply Board is a government monopoly. Nevertheless, the workers are permitted to go on strike, which usually leads to five days or more of IPS (Interruptible Power Supply). The management of our little software firm has forethoughtedly outfitted us with a 4kW diesel generator. It has two 12V starting batteries in series. At the moment we charge the batteries one by one from a 12V automotive-type charger, which means a lot of clipping and unclipping giving general irritation. The generator supplier has quoted us a ridicu-

lous price for a 24V charger (can you believe £953.85 plus VAT, installed?).

My question is: is there any reason why we can't use two identical 12V automotive chargers with their outputs connected in series to charge the two series-connected batteries simultaneously? I think that the answer to this might be of interest to a number of readers, but if you can consider putting us out of our misery with a yes/no answer, we would be very appreciative. Alternatively, a charger design for 12/24 volts that can be left on lead-acid cells full time and built for less than

£953.85?

**Frank Chambers,
Co. Mayo, Ireland.**

I see no reason why not. On the other hand, you could modify our battery chargers that ETI has featured over the years to give +24V out by changing the transformer and checking the voltage ratings of other components. — Ed.

Wizard of Oz

From one of the old-timers, best wishes to ETI and all who sail in her as she heads off into her third decade. It just goes to show that not everything washed up on these shores from Australia is duff, despite Paul Hogan, Neighbours, Barry Humphries, Home and Away, XXXX lager, and Kylie Minogue.

All the best.

Dave Bradshaw, London.

20 YEARS OF PHOTOCOPIES

ETI has been published for 20 years and in this time a great many interesting and valuable projects and features have graced its pages. Although backnumbers are available for only the past 12 months issues we can supply photocopies of any individual article ever published in ETI.

Photocopies cost £1.50 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £1.50.

Please supply photocopies of the following articles from ETI (complete in block capitals):

Month Year Page (if known)

Title

Month Year Page (if known)

Title

Month Year Page (if known)

Title

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.50 per photocopy ordered.

Total remittance £ Date

Name

Address

..... Postcode

Send the completed form and your remittance to:

ETI Photocopy Service

**Argus House
Boundary Way
Hemel Hempstead
Herts HP2 7ST**



WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY	
TEKTRONIX 2445B Four Channel 150MHz	£2000
TEKTRONIX 2445A Four Channel 150MHz	£1900
TEKTRONIX 465 Dual Trace 350MHz Delay Sweep	£600
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£550
SCHLIMBERGER/ENERTEC S218 Three Trace 200MHz Delay Sweep	£500
HI-TACHI V550F Dual Trace 60MHz Delay Sweep	£450
TEKTRONIX 2225 Dual Trace 60 MHz Delay Sweep	£500
TEKTRONIX 465 Dual Trace 100 MHz Delay Sweep	£400
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£450
TEKTRONIX 453 Dual Trace 50MHz Delay Sweep	£200
TELEQUIPMENT D75 Dual Trace 50MHz Delay Sweep (with V4 & S24)	£350
TELEQUIPMENT V3 Differential Amplifier for above	£40
HAMEG 605 Dual Trace 60 MHz Delay Sweep	£400
HAMEG 705 Dual Trace 70 MHz Delay Sweep	£300
GOLD OS300 Dual Trace 20MHz	£200
HI-TACHI V212 Dual Trace 20MHz	£250
TRIO CS1022 Dual Trace 20Hz	£225
H.P. 1980B Measuring System 100MHz	£750
THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE	
ELECTRON MICROSCOPES	
A.E.I. Cynos 500 - Transmission	
ISI Super A - Scanning	
RACAL DANA Wideband Level Meier 5002	£1000
H.P. 8620C with 8620C Special Generator 2-18.6GHz	£3000
TEKTRONIX 577 Curve Trace with 177 feature	£2250
WAYNE KERR LCR 4250 with Binning Option	£1250
RACAL/DANA (AIM) LCR Databridge 9341	£350
WAYNE KERR LCR Meier 4210	£600
WAYNE KERR Automatic Component Bridge 8605	£450
WAYNE KERR Universal RF Bridge 8602	£150
FARNELL Synthesised Oscillator DSG1-0-0001Hz-99.99kHz	£275
MARCONI TF2008 AM/FM 10kHz-510kHz Sig Gen	£300
MARCONI TF2015 AM/FM 10-250MHz Sig Gen with TF2171	£400
MARCONI TF2015 without Synchroniser TF2171	£250
MARCONI TF2016 AM/FM 10kHz-120MHz with TF2173	£350
MARCONI TF2016 without Synchroniser TF2173	£175
MARCONI TF2356/2357 Level Osc/Meier 20MHz the pair	£950
MARCONI SANDERS Sig Sources. Various models Covering 400MHz-0.5GHz	from £300
RACAL 9003 Mod Meier 10MHz-15GHz	£350
TEKTRONIX Waveform Monitor type 526	£300
RACAL Instrumentation Recorders Store 4D and Store 7D	from £500
KEITHLEY 224 Programmable Current Source	£1000
FERRISGRAPH RTS2 Recorder Test Set	£160
SPECTRUM ANALYSERS	
TEKTRONIX 491 Spectrum Analyser 15-12.4GHz	£750
H.P. 141T 8555A & IF Plug-in 10MHz-18GHz	£3000
H.P. 140 Series with 8554 IF Plug-in 500kHz-1250MHz	£1500
H.P. 140 Series with 8553 & IF Plug-in 1kHz-110MHz	£800
H.P. 160 Series with 8558B D1-1500MHz	from £2000
PHILIPSD1 trace 8411 1.0kHz-18GHz	£3000
Used equipment — with 30 days guarantee. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage	
STEWART OF READING	
110 WYKEHAM ROAD, READING, BERKS RG6 1PL	
Tel: 0734 268041. Fax: 0734 351696. Callers welcome 9am-5.30pm Mon-Fri (until 8pm Thurs)	

PHILIPS PM2525 Multi Function DMM 4.5-5.5 digit with GPIB IEEE-488 only £300
THURLBY PL3207 GP Bench PSU 0-30V 2 AMP Twice with GPIB only £350
HAND HELD MULTIMETERS 3.5 digit DM105-14 Ranges DC 2AMP M2355-32 ranges AC/DC 10 Amps Diode/Transistor Tester Probe Counter etc. £32.50

MARCONI 2440 20GHz microwave Counter £1500
MARCONI TF2610 True RMS Voltmeter £800
FARNELL SSG1000 Sig Gen 10MHz-1GHz Synthesised £1750
RACAL 1998 13GHz Freq Counter with IEEE £700
SOLARTRON/SCH 7151 Computing Multimeter £750
PHILIPS PMS131 Function Gen 0.1Hz-2MHz from £200
FARNELL PSU L30-5 30V 5amp £150

MARCONI DIGITAL FREQUENCY METERS
Type 2430A 10MHz-80MHz £125
Type 2431A 10MHz-200MHz £150
MARCONI UNIVERSAL COUNTER TIMERS
Type 2437 DC-100MHz £175
Type 2438 DC-500MHz £225

THORN PSU 0-40V 0-50Amps Metered £300
FARNELL PSU H30/100 30V 100Amps £750
FARNELL PSU H60/25 60V 25A £400
TELEQUIPMENT CT71 Curve Tracer from £125
MARCONI TF2700 Universal LCR Bridge, Battery £175
MARCONI TF2337A Auto Distortion Meter 400Hz/1KHz 0.01% £150
RACAL 9915 Freq Counter 10-520MHz Crystal Oven £150
MANNESMAN TALLY Pixy 3XY Plotter RS232 £100

AVO MULTIMETERS
MODEL 8 or 9 (what's available) £40 each
Test Set No1, 6X, 8X, 8Mk 5 with Carrying Case from £65
8 Mk 6 with Carrying Case £90
All Models Supplied with Postcards & Leads £120

NEW EQUIPMENT
HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase £792
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Sweep £810
HAMEG OSCILLOSCOPE HM2037 Dual Trace 20MHz Compensated £338
HAMEG OSCILLOSCOPE HM2553 Dual Trace 20MHz Digital Storage £610
All other models available — all oscilloscopes supplied with 2 probes

BLACK STAR EQUIPMENT (p&p all units £5)
APOLLO 10 — 100MHz Counter Timer Ratio/Period/Time Interval etc £222
APOLLO 10 — 100MHz (as above with more functions) £285
METEOR 100 FREQUENCY COUNTER 100MHz £189
METEOR 600 FREQUENCY COUNTER 600MHz £178
METEOR 1000 FREQUENCY COUNTER 1GHz £135
JUPITOR 500 FUNCTION GENERATOR 0.1Hz-500kHz Sine/Sqr Tri. £110
ORION COLOUR BAR GENERATOR Pst/TV/Video £229
All other Black Star Equipment available

OSCILLOSCOPE PROBES Switchable x4 x10 (p&p £3) £11

A High Quality Mod

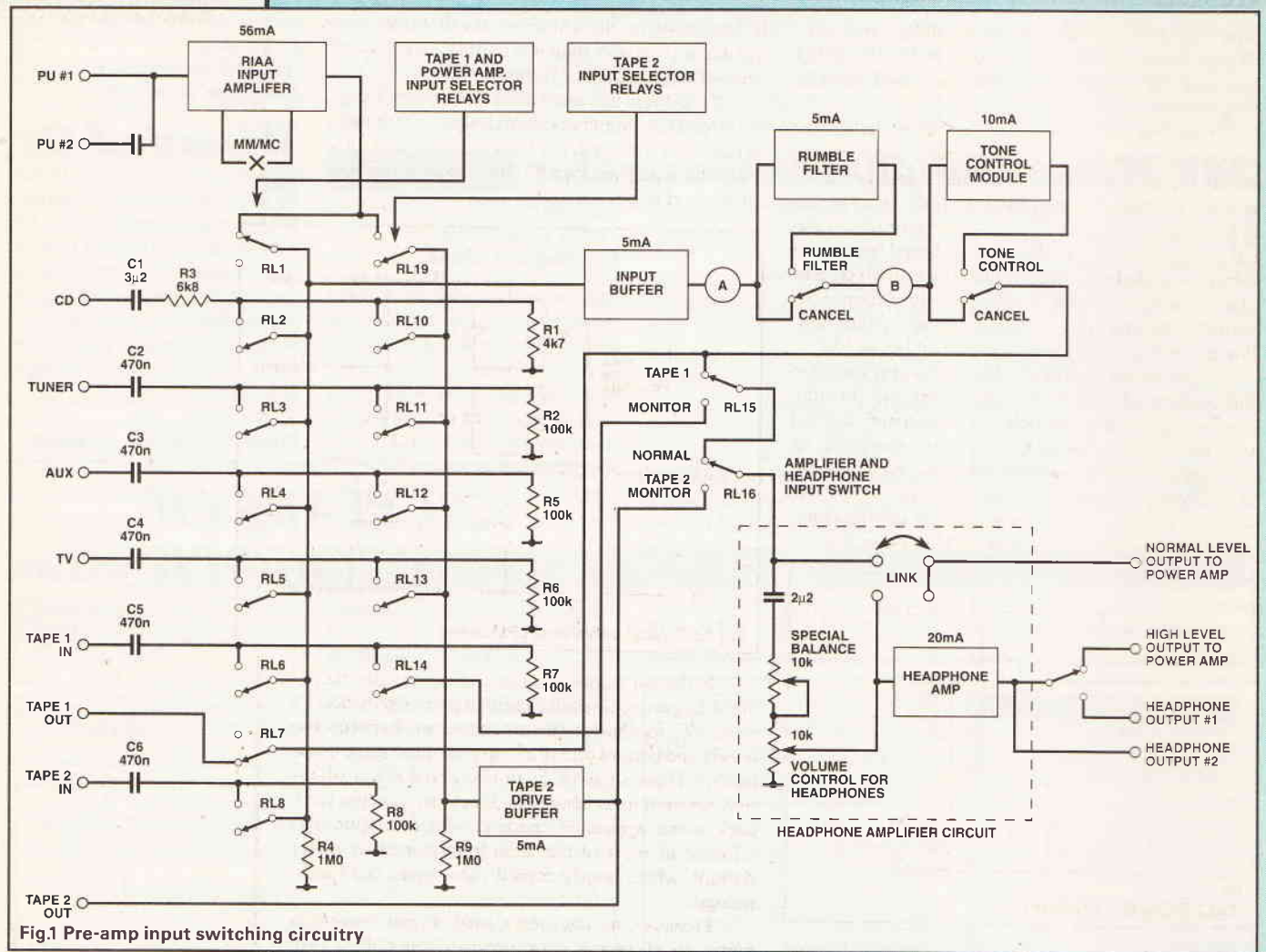


Fig.1 Pre-amp input switching circuitry

John Linsley Hood presents the first part of this audio project to complement the 80 watt power amp featured in ETI.

PROJECT

Basic philosophy

An intentional feature of the 'Audio Design' 80 watt amplifier was that the two separate halves of this system — the preamp. and the power amp. — should be usable, on their own, as separate, self-contained units. The preamp. as a unit which could be used with any existing power amp., or as a very high quality headphone amplifier, with a good range of input facilities, and the power amp., with its input gain and balance controls, capable of use as a flat frequency response system for those whose normal input is from radio, tape or compact disc.

An oversight in the power amp. layout was my failure to provide a separate input selector switch, and I have now remedied this omission.

Preamp Organisation

In order to allow as much flexibility as possible in construction and use, I have based the preamp. design on a series of functional modules which operate from a $\pm 15V$ DC power supply. All of these modules have a high input impedance and a low output impedance, so

that they can be joined together without any difficulty, and the 'tone control' and 'rumble filter' stages can be switched completely out of circuit when the quality of the input programme material makes their presence unnecessary. Similarly, at the discretion of the constructor, unwanted modules could be omitted entirely, without problems.

The circuit interconnection layout of the complete preamp. system is shown in schematic form in Figure 1. This is similar to the layout of the design described in 'ETI' in June/September 1980, except that — at the suggestion of Hart Electronic Kits, who have put together a kit of parts for this design — I have allowed for more signal channel inputs, and have made the layout of the tape monitoring facilities more feedback-proof.

I have also organised the layout, at Hart's suggestion, to provide two entirely separate and isolated signal channels within the preamp., together with an additional pair of output sockets, ('Tape 2'), which makes it possible to record some programme other than that to which one is currently listening, and to simplify tape-to-

ular Pre-Amplifier



tape recording. It would also be possible, if one were wealthy enough to own two tape recorders, to record two separate signals at the same time, and monitor these at will!

Hart Electronics were also keen to use relays for switching the various signal channels, because this would simplify their PCB and front panel layout. It would also avoid the need to route input signal wiring to the front panel, allowing shorter and more direct signal paths. The type of relay they preferred was of the miniature sealed and vacuum 'filled' type, in which gold plated contacts and an inherent freedom from dust, contact contamination or corrosion, will ensure both low contact resistance and a long trouble free life.

To eliminate switching 'clicks', by greatly reducing the amount of current flowing across the preamp. 'mother' board and through the front panel channel selector switch, the relay coils are energised as demanded by a low-powered transistor switching circuit, shown in Figure 2. This also reduces the rise and fall times of the turn-on current pulse. In use this channel selector switching system is entirely noise free.

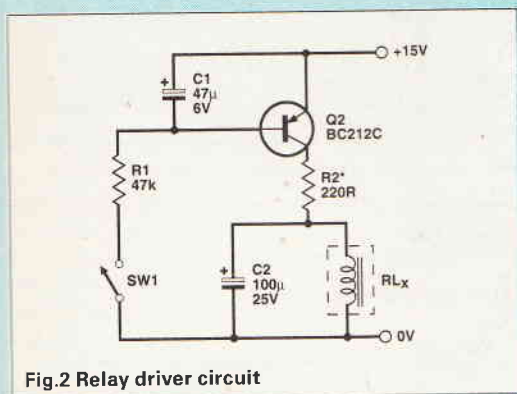


Fig.2 Relay driver circuit

If this preamp is used with the 'Audio Design' power amplifier, which has a high input sensitivity, and also has gain and channel balance controls on its input, it will not be necessary to duplicate these controls in the preamp., except on the input to the headphone amp.

However, the headphone amp. is an extremely high quality 'class A' design, and makes an excellent output driver to more conventional direct input power amps., where its low output impedance and its ability to drive capacitive loads will allow long connecting cables, (up to 50 metres of standard low-loss 'TV' type coaxial cable, or 20 metres of normal twin screened audio cable), to be used without any loss of quality in wiring between the preamp. and any following power amp., as for example, in a 'tri-amped' LS system.

The RIAA stage.

By and large, the design of high quality preamplifiers is easier than comparable quality power amplifiers because they will usually only be required to drive a resistive load, typically 10k or so, in parallel with, perhaps, a few hundred picofarad. The normal output voltage requirement will only be 1.2V RMS, at the most.

On the other hand, preamps will be required in 'tone controls' or 'RIAA type' input frequency response correction stages, to introduce deliberate modifications to the overall frequency response of the system,

is less easy to do either of these in an entirely satisfactory manner than it is to devise a circuit with a ruler-straight frequency response.

It is in these two areas that I have made changes to my original preamplifier circuit design, (ETI June/September 1980), though the basic circuit layout remains much the same, and I would like to explain my reasons for these changes.

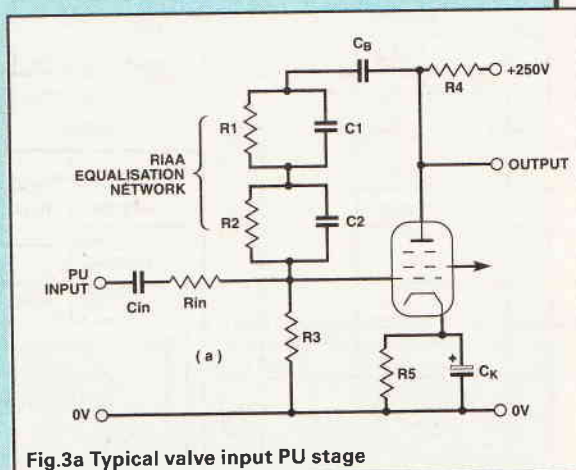


Fig.3a Typical valve input PU stage

In the early days of valve 'hi-fi', gramophone PU input frequency response correction was provided by some RC feedback network connected between the anode and control grid of a high gain input stage in the manner I have shown in Figure 3a, and this type of system; referred to as 'shunt' feedback because the feedback signal appears in parallel with the input; was adopted in most of the early transistor preamplifier designs, which largely copied valve type circuit technology.

However, as low noise small signal transistors began to allow the construction of amplifiers with exceedingly quiet noise and hum backgrounds, designers began to realise that such 'shunt feedback'

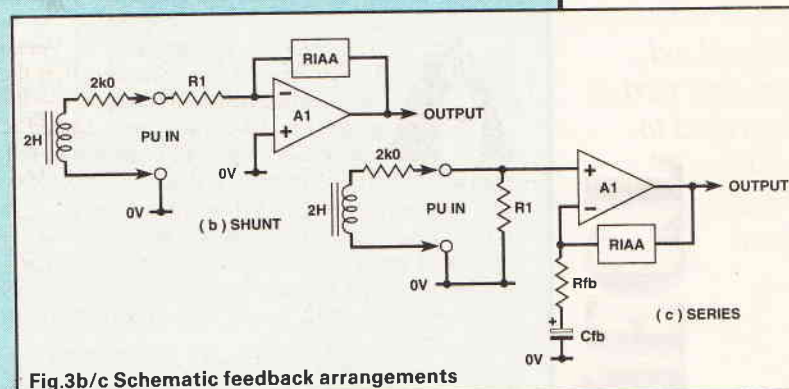


Fig.3b/c Schematic feedback arrangements

systems, shown schematically in Figure 3b, had a higher intrinsic noise level, because of the thermal noise generated in the input (PU load) resistor R1, than the equivalent 'series feedback' system, shown in Figure 3c, in which this resistor was shunted by the DC resistance of the PU coil itself, which might be only 1.2k ohms in value.

In consequence, nearly all designers of commer-



cial hi-fi equipment changed over to series f/b systems, to avoid adverse comment in the 'Hi-Fi' press about their PU input S/N ratios - usually measured at 1kHz with the PU inputs short-circuited.

Shunt vs Series Feedback

As ever, input 'noise figure' is only part of the problem, and there is a host of other ways in which the types of circuit shown in Figure 3 differ in their characteristics. Of these, the most immediately obvious is that when the impedance of the RIAA feedback network falls to zero - as it will do at very high frequencies - the gain of the 'shunt' f/b layout will also fall to zero, (required by the RIAA equalisation specification, shown for reference in Figure 4), whereas the 'series' f/b system simply becomes a unity gain voltage follower.

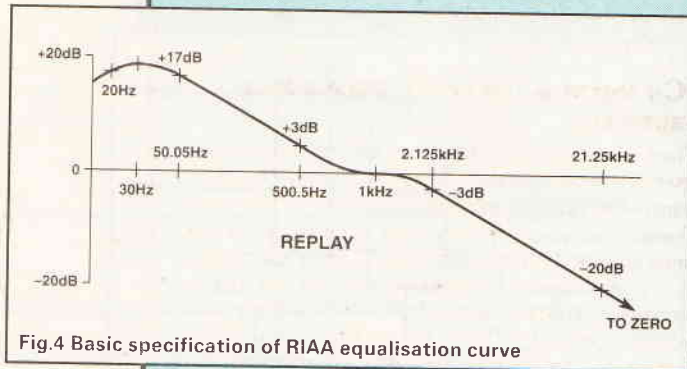


Fig.4 Basic specification of RIAA equalisation curve

There is a 'Catch 22' type of problem hidden in this effect, in that if the designer tries to improve the distortion characteristics of the stage by having a lot of negative f/b, (a feedback network which has a low impedance in relation to Rfb), a flattening-off in the frequency response will occur at a lower frequency. This is closer to the top of the audio band and makes this frequency response error more prominent. On the other hand, having a higher impedance feedback network, that pushes the gain error up towards a higher frequency, may cause the stage to run out of gain at the LF end, resulting in poorer distortion and bass response.

The ear may not notice one or two dBs of error at the top end of the audio band owing to incorrect RIAA equalisation, because of this failure of the series f/b system, but I am sure that most people can hear the phase error associated with this, and in the days when I used to do a lot of 'Hi-Fi' talks, I would frequently invite the audience to do an 'A' vs. 'B' comparison between these systems in the reproduction of a gramophone record.

This would be done by means of a pair of anonymous 'black boxes', simply labelled 'A' and 'B'. These contained RIAA equalising stages based on either shunt or series f/b systems, and, to allay any doubts, I would demonstrate - before the test - that the gain and frequency response given by both of these units was identical, to 0.5dB or so, within the audio band.

Typically about three quarters of the audience - and this would be far from ideal listening conditions - believed that they could hear a difference between 'A' and 'B', and a similar proportion of those who thought that the sound was different, would express a preference for reproduction via the box which contained the 'shunt' f/b arrangement.

I am not surprised at this outcome since, as can be seen from the respective gain/phase curves vs. fre-

quency, for 'passive', 'shunt f/b' and 'series f/b' equalisation systems, shown in Figure 5, the passive and the shunt f/b systems are identical in their characteristics - apart from differences in gain - whereas the series f/b system is the odd man out.

Distortion, 'clicks', and background noise, in RIAA stages

A further difference in performance for the shunt f/b system is due to the fact that, the signal from the (PU) input is applied to the same point as the feedback, whereas it is applied to a different input in the series f/b circuit. So a sudden transient input signal, such as might arise from a dust particle or a nick in the groove of a vinyl disc, can more easily cause a sudden brief input overload in the series f/b system, as both inputs try simultaneously to follow the input signal voltage transient.

Certainly in my experience, shunt f/b systems seem to be less plagued by record surface 'clicks' than the equivalent series f/b ones, which makes for more restful listening.

Another difference between the two systems comes about from the actuality of the input circuit impedance. A typical moving magnet or variable reluctance PU coil may have a DC resistance of 1k5 ohms, coupled with an inductance which can be as high as 2H, (though, in fairness, some of the better modern units have achieved an adequate output voltage with a somewhat lower value of coil inductance). At the bottom end of the audio band, say 100Hz, this will provide a total PU input impedance of about 2k.

However at 15kHz, this has increased, because of the inductance of the PU coil, perhaps to some 180k, with a much higher input noise figure.

Assuming an input load resistance of 47k, a typi-

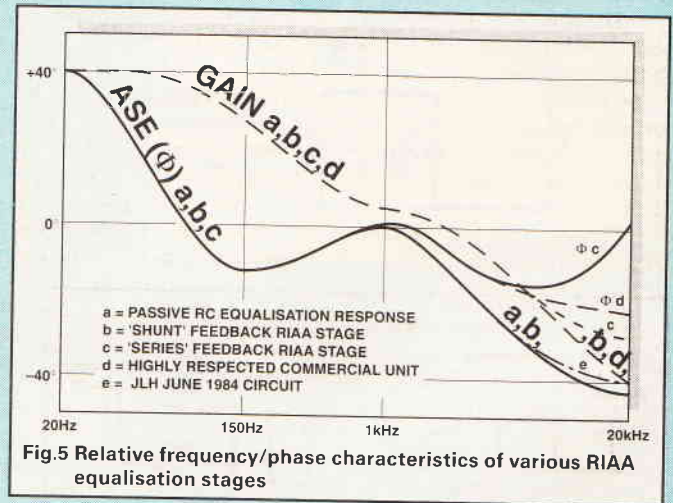


Fig.5 Relative frequency/phase characteristics of various RIAA equalisation stages

cal value, the two systems described will have the same spot frequency noise figure at about 3.8kHz, with the series f/b system being worse than the shunt one above this frequency. This gives rise to a clear difference in the sound of the background noise too, with the series f/b system having a high pitched background 'hiss', while the shunt f/b one is more of a 'rustle'.

As a matter of personal preference I do not like the sound given by simple series f/b RIAA equalisation stages, which was why, in designing equipment which was mainly for my own use, I persisted in the use of shunt f/b designs long after they had been abandoned by my peers, and I am not at all contrite over my obstinacy.

Alternative RIAA equalisation systems

The main circuit options which are available to the

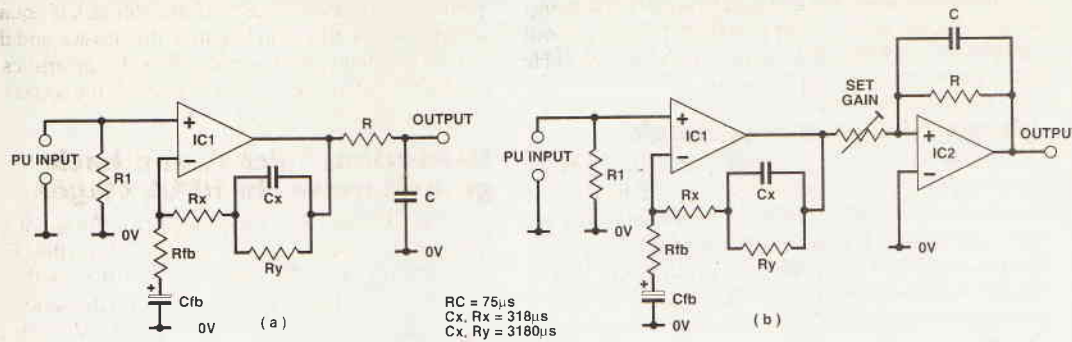


Fig. 6 two stage RIAA equalisation circuits

designer of input RIAA equalisation circuitry are: passive networks, much beloved by the purists; shunt or series f/b layouts, or combinations of all three. Moreover, since the RIAA curve can be divided into two separate parts; that from 20Hz – 1kHz, and that between 1kHz – 20kHz; one can use one type of equalisation for one half and another for the other, giving six possible combinations.

In the circuit I described in ETI in June 1984, I used a series f/b system for the lower part of this frequency band, and a passive RC network to deal with the upper, as shown in Figure 6a. This requires an output buffer stage to prevent the load impedance of any succeeding circuitry from altering the time constant of the output RC network, which should be as close as possible to 75µs.

Having decided to use a two-stage equalisation circuit, I chose this particular layout because it did not introduce any phase inversion in the input signal path, which would have been the case if I had used the electronically equivalent active stage shown in Figure 6b.

The penalty is that the input gain stage must be able to deliver a ten times greater output swing, at 20kHz, in the case of Figure 6a, than would be required for the circuit of Figure 6b, because it must compensate for the signal attenuation introduced by the output network. Unfortunately, the phase characteristics of this circuit, shown in Figure 5e, still differ slightly from the ideal.

This need for high output voltage swing capability, (and consequently more limited 'headroom'), in

allows a low impedance drive to the shunt f/b circuit, so that its impedances (and consequent thermal noise level) can be kept low.

ICs versus discrete transistor layouts.

There are some very good low-distortion, low noise level, ICs around, and the question of how these compare in their audible performance to one another, and to equivalent discrete component circuits, is one which must engage the minds of all audio circuit designers.

I must declare, at this point, that I do not accept, because I cannot hear, the bulk of the audible phenomena claimed by the 'golden eared' fraternity for component types or constructional niceties – like super grade non-polar capacitors or 'single crystal copper' printed circuit boards, whatever that may be.

However, I do believe there can be some small audible differences between different design approaches, and it is up to the designer, if he is conscientious, to try to establish through the verdict of his own ears and of many friends as he can prevail upon to listen, whether these differences are real, noticeable, and closest to the original.

On the subject of linear ('op-amp' type) ICs, I think there are some small differences in sound from similarly specified devices of different types. These only become noticeable when the ICs are caused to give gains in excess of 5×, or when they are asked to drive awkward load impedances.

At unity gain levels, and modest drive voltages into resistive loads in excess of 2k, I confess that my own ears are not good enough to distinguish between a good quality op-amp. IC, used as a voltage follower, and a direct wire connection, on switching trials between one and the other.

I think there are also some small differences in sound between discrete component voltage amplifier designs and op. amp. ICs, especially at higher gain levels, even though they may have impeccable performance specifications. Where low cost and circuit simplicity are not major requirements, I prefer to use discrete component

circuits where gains in excess of 2× are required.

The MM/MC input stage.

As shown in Figure 8, the input signal from the PU cartridge is taken directly to a switched gain stage, shown in simplified form in Figure 9a. This is a fully symmetrical layout of two 'push-pull' two-transistor amplifiers connected in parallel, which halves the input noise impedance presented by Q1 and Q2. These are a pair of TO126-type small power transistors, and makes for a very quiet background noise, even on low output M-C Pins.

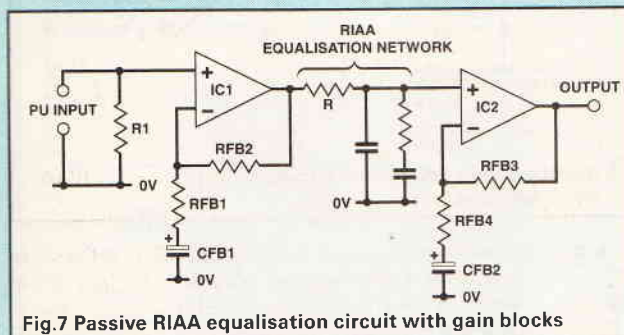


Fig. 7 Passive RIAA equalisation circuit with gain blocks

the line amplifiers, is the principal drawback with all purely passive RIAA equalisation systems of the kind shown in Figure 7.

An idea which has been around for a long time, and has recently begun to be regarded with greater favour, is the layout shown schematically in Figure 8, in which a straightforward gain stage, (IC1), is used as a buffer stage between the PU input and a shunt f/b equalisation stage, and this is the arrangement which I have now chosen.

This allows a simple gain switching facility to cope with pick-up cartridges of greatly different output levels, e.g., moving magnet or moving coil, and also



This circuit has an input noise impedance of about 15R, and a flat frequency response from less than 20Hz up to the MHz range, coupled with a clean square wave response, and a very low harmonic distortion. I also like the sound of this layout better than any of the others which I have tried.

Because the base bias currents of the two input transistors blow from one to the other, the DC input resistance is high, while the use of negative feedback to the input transistor emitter circuits also ensures a high dynamic input impedance, so it will also work well with a higher input impedance moving magnet or variable reluctance PU cartridge.

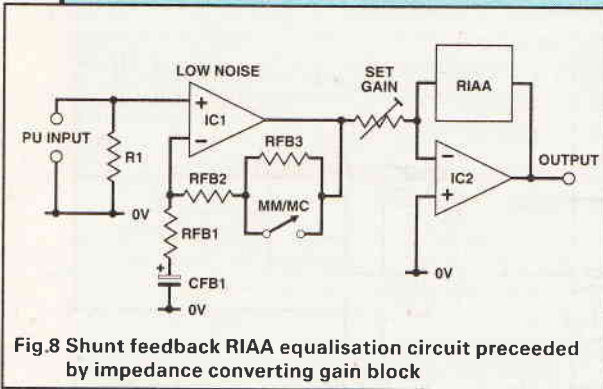


Fig.8 Shunt feedback RIAA equalisation circuit preceded by impedance converting gain block

The gain options chosen are 14.6X for high input signal level cartridges, and 150X for the low output (moving coil) types.

The second, shunt feedback, equalisation stage, shown in schematic form in Figure 9b, is a very high gain, (around the 100,000X mark), symmetrical two-stage amplifier circuit with a closed loop gain, at 1kHz, of 18X. Because the RIAA equalisation network presents a capacitive load to the output stage, it is essential that the output drive capability should be symmetrical - with the output transistor, (Q8), load provided by the current mirror CM1 - and that its output imped-

ance, with feedback applied, should be very low, to prevent any slew-rate limiting.

The complete circuit of the combined input and RIAA stages is shown in Figure 10. The DC supply to the input stage is provided by a pair of on-board 5VDC voltage regulators, and the whole unit should be well screened, and situated away from AC 'hum' fields.

The output voltage swing capability of the complete stage is 10V RMS, over the range 20-20kHz, and its distortion is below 0.005% at 1V RMS output, at 1kHz. The output impedance, at the collectors of Q13 and Q14, is less than 25R, so the effective output impedance is determined largely by the 120R output resistor, R25.

This should allow the unit to drive up to 50 metres of standard low-noise screened connector cable without HF loss, if the user prefers to mount this module, as a separate unit, on the gramophone turntable housing, where this is situated at some distance from the amplifier.

Although I think the sound quality given by CDs is already very good, and likely to improve still further as developments take place in player systems and the disks themselves; nevertheless there are still a lot of vinyl disks around, and a lot of money has been invested in turntables and cartridges for the reproduction of these, so there is clearly a continuing need for good vinyl disc reproduction systems.

Speaking for myself, I have accumulated, over the years, some 2000 LPs, and I wish to be able to enjoy these for a long time to come, so I am very pleased to find that the performance given by this new RIAA stage offers a small but noticeable step forward, in terms of clarity and transparency, by comparison with some earlier designs of my own, which I had, indeed, thought to be quite good when I did them.

In the next part of this article, I will describe the remainder of the preamp. circuit, and explain my changed intentions with respect to the 'tone control' stage.

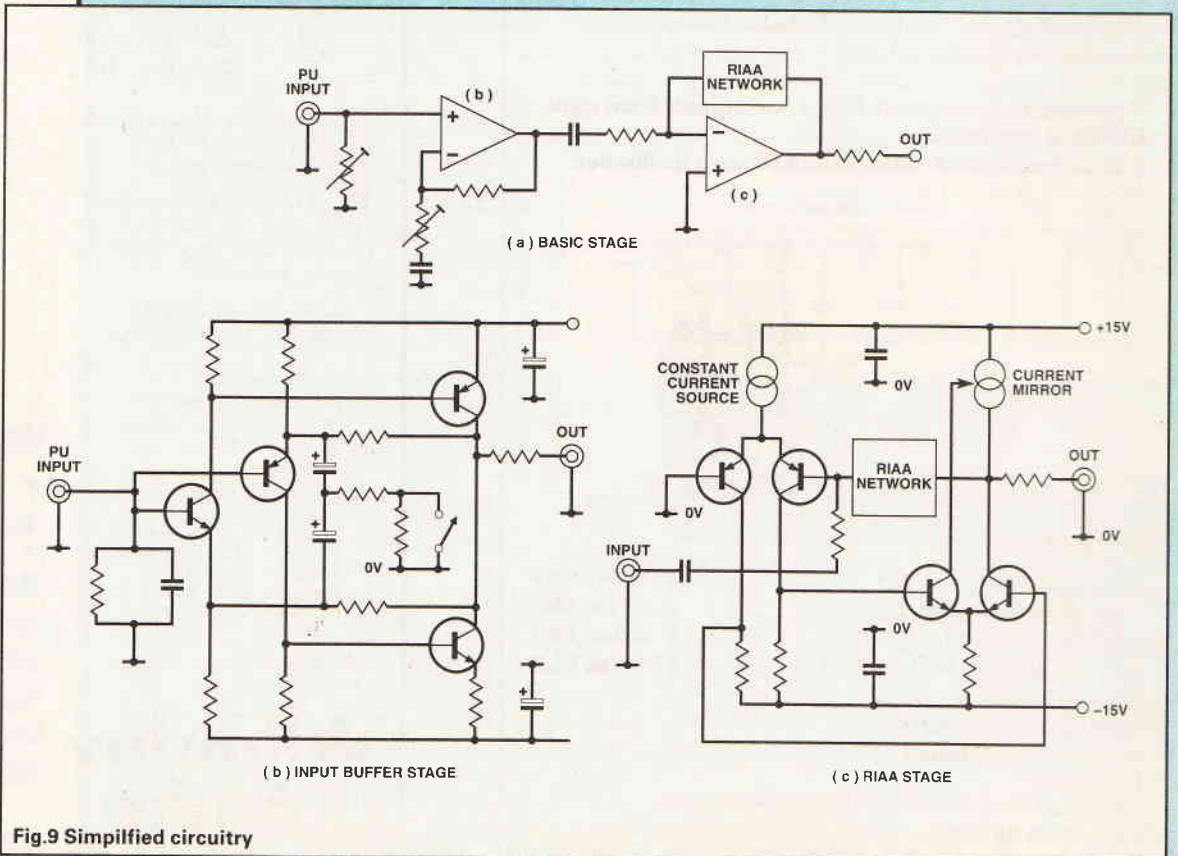


Fig.9 Simplified circuitry


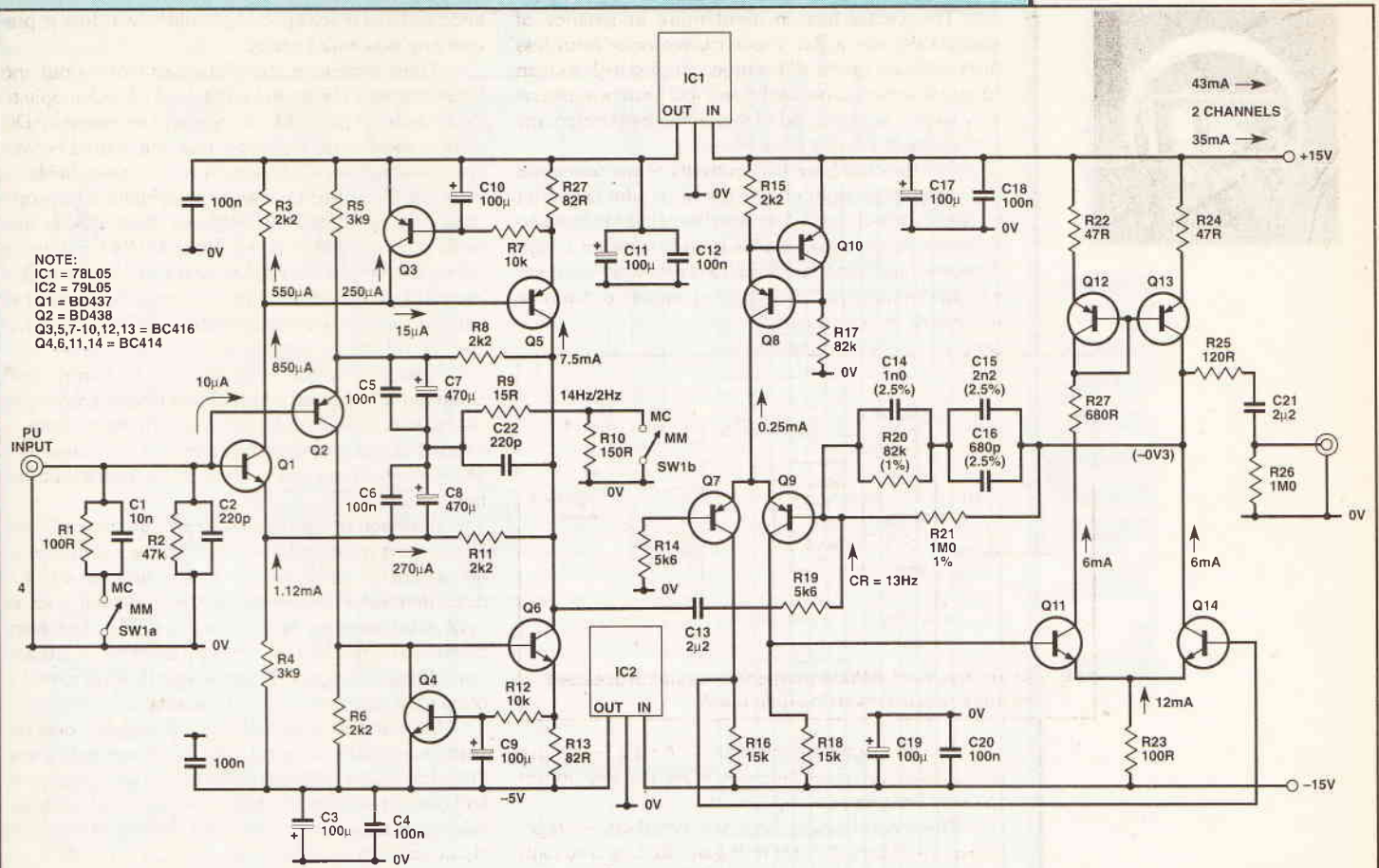


Fig.10 Buffered shunt-feedback RIAA equalisation stage

8031 CPU BASED CONTROL CARD

Why not give your next project computer control!

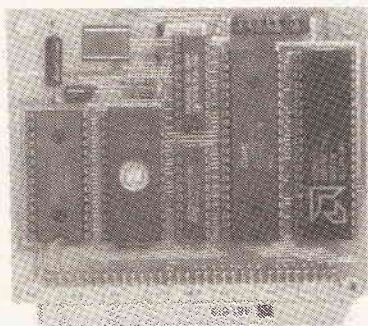- ★ Small Physical Size (HALF EUROCARD)
- ★ 32 Bidirectional I/O Lines
- ★ High Speed (CPU RUNNING @ 16MHz)
- ★ Full Expansion with all important signals from mini DIN41612 connector
- ★ Supplied with 8K RAM, 32K ROM with hexloader, Manual & Diagrams.



- | | |
|-------------------------|--------------|
| ★ 8031 CONTROL CARD | £ 39 inc P&P |
| ★ QASM51 ASSEMBLER | £ 39 inc P&P |
| ★ APRIL 8 ROM EMULATOR | £ 65 inc P&P |
| ★ APRIL 16 ROM EMULATOR | £140 inc P&P |

For more information:
MEC MICROSYSTEMS
 Mountbatten House
 Fairacres
 Windsor
 Berkshire SL4 4LE
 Tel: 0753 857181 • Fax: 0753 860696

Peerless CC FORCE




Wilmslow Audio's NEW range of speaker kits from Peerless.

This new range of four kits utilise CC technology drive units for optimum performance.

The kit contains all the cabinet components (accurately machined from smooth MDF for easy assembly).

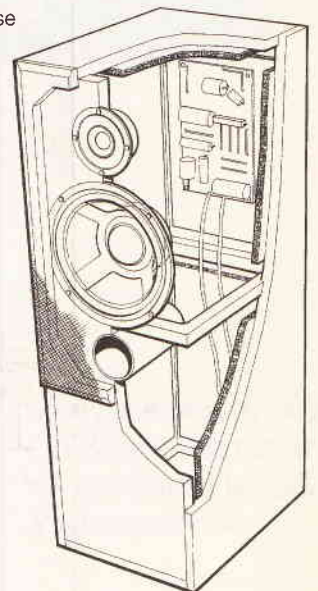Pictured here the Force 6, a large floor standing design.



Dimensions:
 800 x 275 x 335 mm
 Response:
 32 HZ - 20 KHZ
 AMP Suitability: 30 - 120w
 Impedance: 8 ohms

Price	carr./ins
Force 2	£167 £15 pr.
Force 4	£190 £15 pr.
Force 6	£210 £18 pr.
Force 8	£265 £18 pr.

All kits are available in Plus and Basic forms.

Wilmslow Audio

Wellington Close,
 Parkgate Trading Estate
 Knutsford, Cheshire
 WA16 8DX
 Tel: (0565) 650605
 Fax: (0565) 650080

DIY Speaker catalogue £1.50
 post free (export £3.50)



Telephone credit card
 • orders welcome



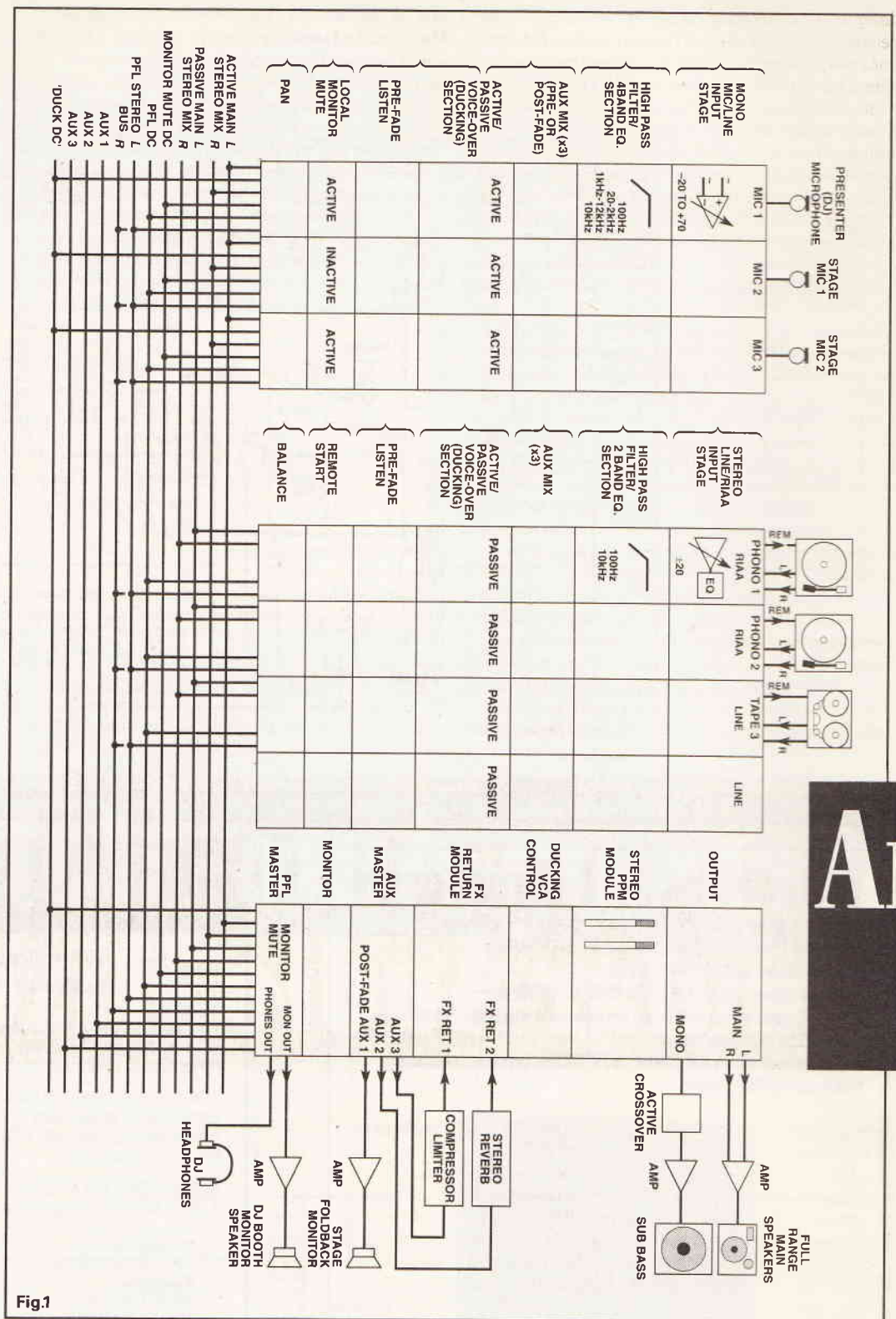


Fig.1

Mike Meechan begins a major series on ETI's biggest project ever for our Anniversary.

If the reader has been following the recently published two part introductory feature on the 'why's and wherefore's' of mixing desks, and wondering just why the magazine doesn't produce something tangible to put all of the high faltering theories into practise, well, fret no more. By burning the candle at both ends, and exhausting extensive stocks of the old midnight oil, I've managed to create a mixer project which will do for your ears what the Nightfighter Lighting Control System did for your eyes and all in time for the magazine's 20th anniversary, hence the name. I have been given strict orders to cease and desist from my usual awful puns so there shall be no mention whatsoever of waltzing through the many

features of the mixer or maintaining the status quo, and contrary to unsubstantiated rumours, my next series of articles will not feature projects for the nose and throat and neither is this an April fool! We hope to follow up this series with a series of projects of studio-quality effects units, starting with a 1/3rd octave, tamper-proof equaliser.

The Mixing Console articles mentioned covered some of the problems which have to be surmounted in the design of a mixing console, and we discussed some of the aspects and problems which the design engineer has to contend with. In this series of constructional articles, we shall delve slightly more deeply and at a more mathematical level into how the circuitry can be

An
T

designed to minimise noise, crosstalk, distortion and general signal degradation. Having said this, the equations will be kept to an absolute minimum here (well almost) and used only to illustrate why certain components, component values or circuit topologies were chosen in this design in preference to others — the author is always open to criticisms and suggestions (but only of the constructors sort). Let me know if the featured circuits could be made to work either with less components or with higher performance. With due deference to the excellent series of articles by my compatriot, Mike Barwise, I hope that the series interests both the technically trained and the scientifically educated! What I wanted — and what I hoped that the readership of ETI would want — was a console which ostensibly could be configured in one of three ways:

As a Disco Mixing Console (albeit with many more inputs and with much greater facilities and flexibility than the usual consoles of this genre). The ability to be used in circumstances such as hospital radio would be an asset. Obviously some sort of voice-over facility would be desirable in this situation.

As a live music mixer for use at small concerts. A good range of auxiliary sends for use in foldback or monitoring purposes was a major prerequisite in this instance.

As a mixing console for use in a multitrack recording situation. This would require a flexible group routing system, in addition to other facilities already mentioned. Also, some sort of console automation — memory retention of group routing switch settings, fader levels and perhaps an option of motorised pots — might be a possibility here. Also, with the present-day

one or two for the Auxiliaries and another for the Master, joined umbilically by a wiring bus system, the mixer is generally constructed as one complete unit, each individual PCB being bolted to and sharing a single front panel. This makes tailoring the console to individual needs a very difficult task to implement, the mixer either having to be bought in a size where there is inbuilt redundancy of unused modules or facilities, or conversely, continually upgraded or superseded if used in an environment where needs are constantly changing. This is not necessarily a bad state of affairs nor is it intended as a criticism or indictment of manufacturer's of these type of consoles, Soundcraft, Soundtech etc — indeed it makes good performance and reasonable facilities affordable and available to a much wider range of musicians and to those within the music industry, particularly struggling, poverty-stricken young bands waiting for their first break.

The afore-mentioned is good news to us as it is in this region that the electronics magazines such as ETI can score, since all of the reasons which make this philosophy of easy upgrade and individual packaging undesirable to the commercial fraternity — cost, intensity of labour and the like — actually make it very attractive to the hobbyist constructor. He or she can spend such time on the project as is necessary to tailor it exactly to one's personal requirements, time which in a commercial environment would spell financial disaster.

Money Matters

Alas, one aspect of mixing console construction in which we are unable to successfully compete with the



PROJECT

Anniversary Auto-Mate 20 Modular Audio Mixer

prerequisite needed for MIDI on anything remotely to do with music, the possible inclusion of the MIDI interface for controlling channel mutes and the like. This would use the continuous controller, note on/note off or system exclusive messages within MIDI to implement these functions. There could also be another Expansion port to allow connection to a PC or external disk drive which would mean that complete mixes and all automated switch settings would be able to be downloaded from the console and then replayed at a later date or perhaps even modified in software.

Figures 1 to 4 show four possible configurations for this console.

Mixing consoles in the commercial market place are generally designed for one of these categories although some can be configured in different ways, such examples marketed as being able to handle two of the three tasks listed.

The major shortcoming is in commercially-produced mixers falling into the budget price range, 'budget' being relative in this instance and meaning that the unit may retail in a region up to about four or five thousand pounds. Although all but the lowest priced use one PCB assembly per Channel, possibly

big boys is in the bulk buying component stakes. If a given console manufacturer orders 10,000 control knobs from the component supplier, a corresponding bulk order discount is applied. This saving in material costs — in a smaller form otherwise the mixing console retailing business would be a profitless one — is then passed on to the consumer. If, on the face of it, this sounds somewhat off-tangent, I should explain why I have mentioned it.

It has to be said that there are available some excellent and competitively-priced mixers. To build these same consoles at home using the component supply channels available to the home constructor would, in material costs alone, probably be priced at least as much as the ready-built version, and most probably more.

This project faces identical problems in that the component cost is high and a similar-looking, commercially produced (though non-modular) example might cost in the same order of magnitude.

All is not lost, though, since an increase in the size of the mixer above about 8 channels or so brings increased savings, as does the fitting of any of the bolt-on extras, owing to development costs to you the

I



reader being negligible — the cover cost of the magazine, in fact. I shall mention a guide cost for each module as and when these are featured.

All Mod Cons

Now, back to the matter in hand. What we were talking about before being so rudely interrupted by the vulgar topic of money is, of course, a modular design philosophy wherein each module is able to be configured in a variety of ways (using sub-modules). The overall size and shape, in a metaphoric sense, is dictated by the

operator and the use to which the console will be put, NOT as is often the case in commercially-produced consumer durables, of the supplier deciding what is average and ideal for the customer.

This modular philosophy also means that the whole desk could be re-configured and completely different from when first constructed, simply by retrofitting some of the specialised add-on modules.

Now that we have a very rough design brief of the requirements of the console, the question now is, how best to implement the design? Why not imitate the better features of the more upmarket desks whilst

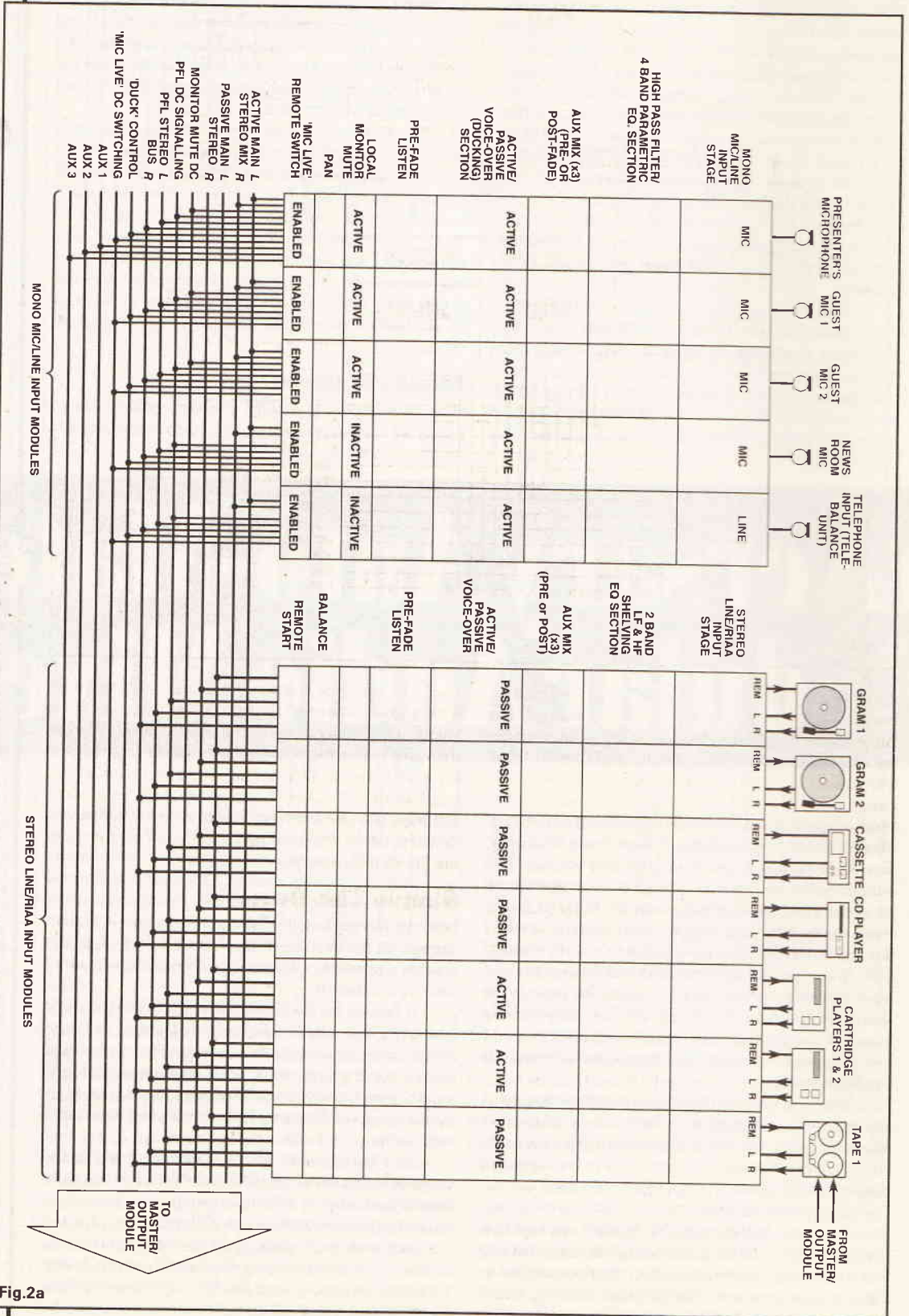


Fig.2a



PROJECT

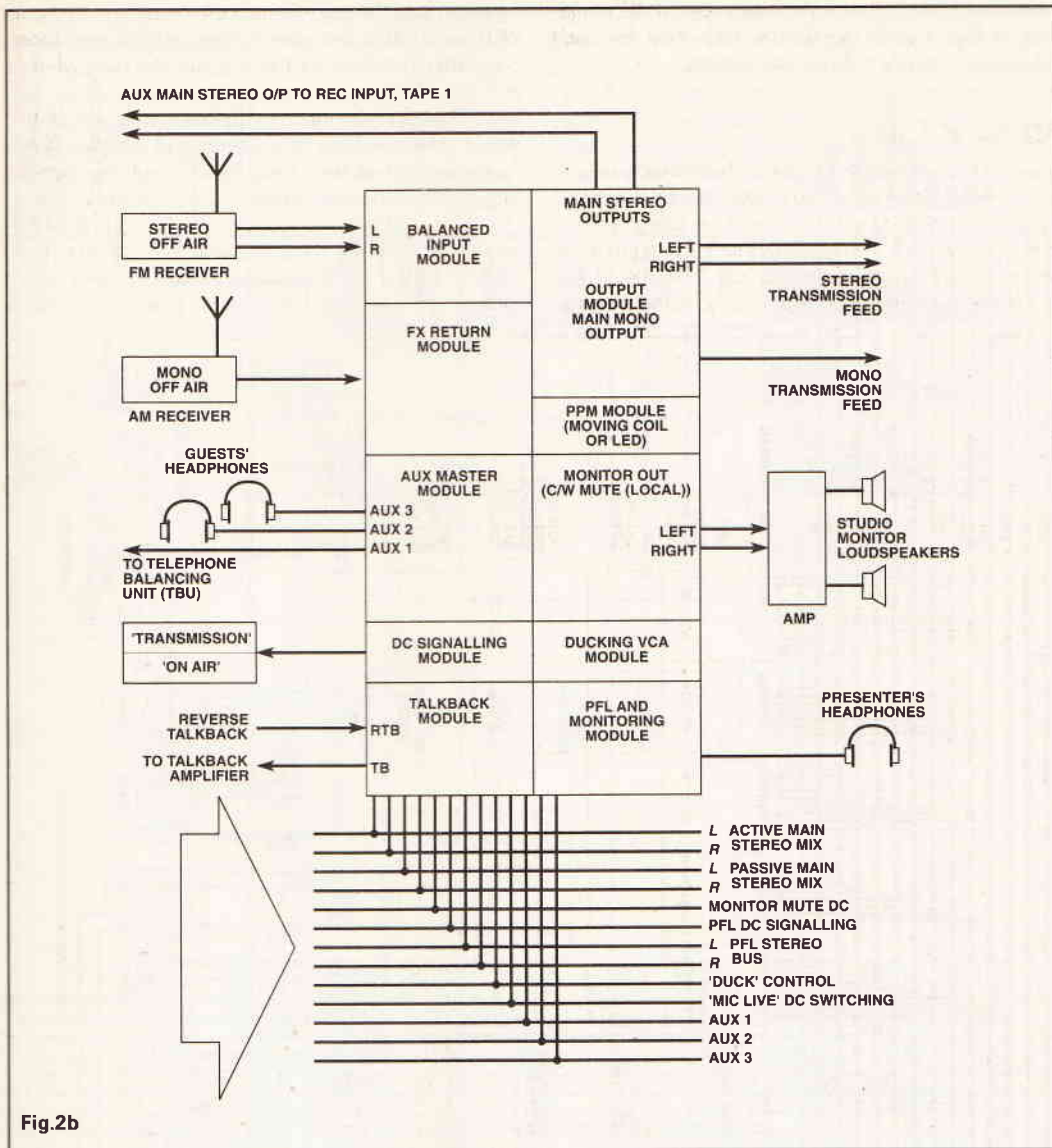


Fig.2b

minimising cost by utilising the commodities which we have in abundance, namely time and energy? The Anniversary AutoMate Mixer uses separate modules for each Channel, Monitor/Group and Output 'card' with each module having its own metalwork. The only component common to all of the modules is the Motherboard 'frame' which houses all of the modules. This can be as small or as large as required, up to certain practical limits which we will discuss later. It is entirely passive and serves only to support and house all of the modules which are inter-connected using a daisy-chained ribbon wire/IDC connector bus system. I did not entertain the idea of using a motherboard/edge connector system for a variety of reasons. The primary one was that the idea of a motherboard system would have somewhat ruled out any infinitely variable modular philosophy, since motherboard PCB's could only be manufactured in a very finite number of sizes. It would also have meant that the PCB for this board on a 36 input desk, say, would have been rather large and expensive, a real mother, in fact. edge connector/mother board systems can also prove to be unreliable unless gold-plating is used on the edge connectors and expensive and good quality sockets are used on the motherboard frame.

The number of different PCB's has been kept to a minimum so that facilities can be supplemented at any time after initial construction. This is important if any future re-configuration of the console is envisaged and since a complicated PCB costs no more to produce

than one which is sparsely populated with tracks, it makes good financial sense to create one standard layout which encompasses all eventualities. We are then able to use this as a standard module. Capital outlay in the first instance is thus minimised as much as possible. Each module has a number of corresponding sub-modules which can be used to alter the configuration of it, either when it is first built or at a later stage in the life of the console.

Simply The Best

I should also say that throughout the design and development of the circuitry, I tried always (and quite successfully, I think to use those techniques which would not be considered amiss in the very best, ultra-fi preamplifiers. It is sadly true that many mixer manufacturers' take what best can be described as liberties in circuit design, with configurations guaranteed to cause weeping and wailing and gnashing of teeth amongst hardened audiophiles, and all seemingly justified as cost-saving exercises. Many such sonic blunders have been avoided here, and with no increase in cost to the constructor. One example of this is in the scaling of the resistors in the Parametric EQ section (yet to be published) such that polystyrene capacitors, which are more aurally-friendly than polycarbonate or polyester, but much bulkier at values more than about 15n, could be used . . . I also went to great pains to return to first principles and design a low-noise, high current power supply to run the whole thing.

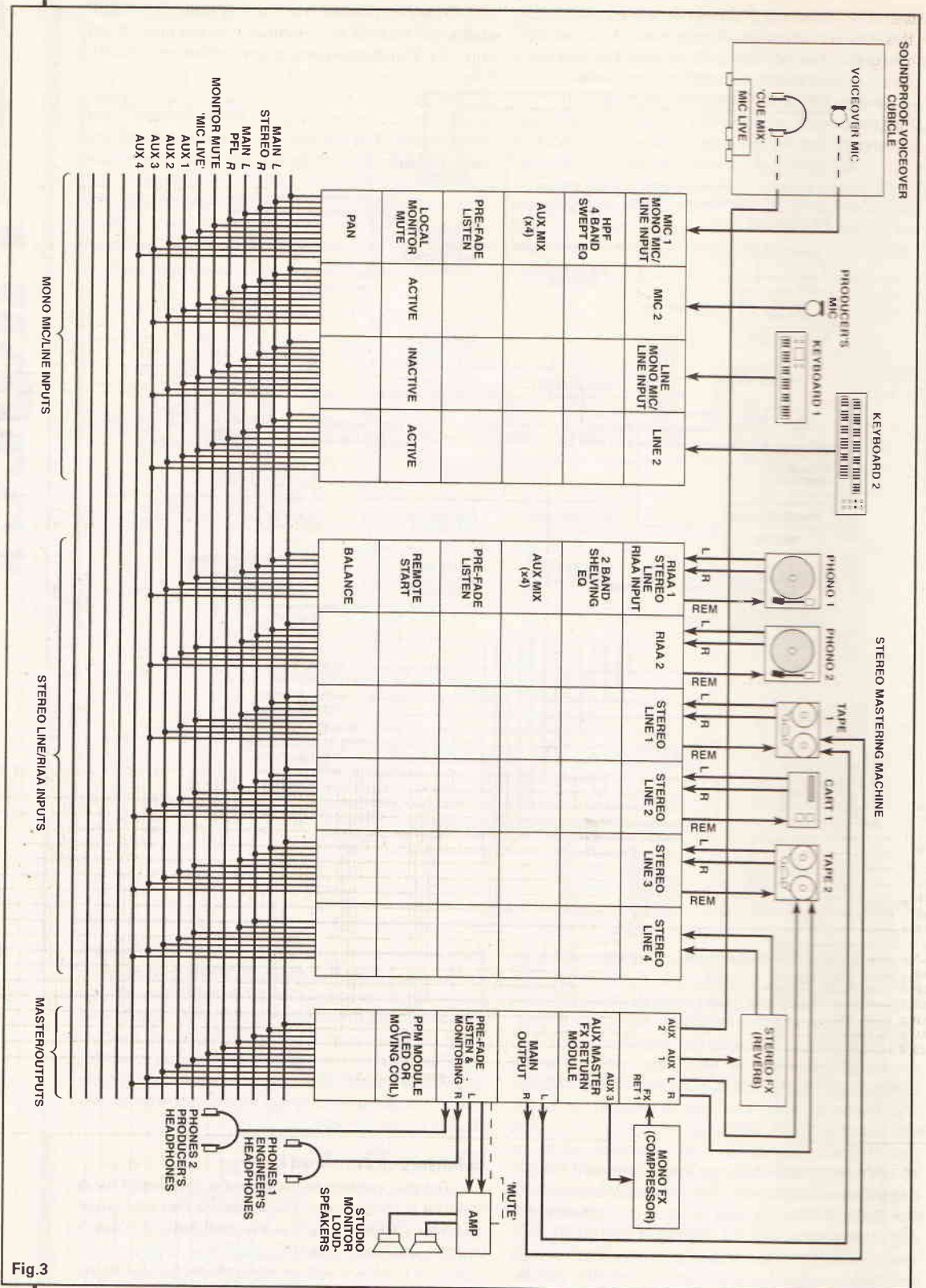


Fig.3

The 'sub-modules' include :
 Mic/Balanced Line Input. 48V Phantom powering for the Mic input and electronic unbalancing of both.

Stereo Line Input/Stereo RIAA Input. Both unbalanced and unbalanced.

Module for the Electronic Muting of inputs – 'ducking' – for use in a DJ or presentation situation.

Presentation module with voice-over masters and enhanced monitoring system more suited to a DJ style console

Remote Start module for use with turntable, cartridge or tape machines.

Electronic Group Routing Matrix module using FET switching – for use in a multi-track recording situation.

Clean-feed module for the generation of PA, fold-back, monitor and cue mixes.

Central Digital Control Module with battery-backed up RAM for memorising of Group Selection and Fader setting.

MIDI and External interface module to be used with all of the automation facilities.

It should be said at this early stage that with a con-
 structional project of this scope and magnitude, it is prudent, and in fact should be considered imperative,

to wait until all parts of the series have been published. In this way, a comprehensive overview of the system can be gained before the idea of any major capital outlay is entertained.

As we said earlier, with the great repetition of components such as jack, XLR and multipole connectors, pots, switches and pushbuttons, op-amps and control knobs, LED's etc, serious financial savings can

Construction-wise, or more specifically, metal-work-wise, each of the modules is constructed from strips of 1.5" angle aluminium (or its metric equivalent). If we refer to the colour shot on the front cover, we can see that these are finished in a rather nice, in-vogue metallic grey colour although who cares about fashion — personally, I'm waiting for the return to haute couture of drip-dry polyester shirts, crimpolene slacks

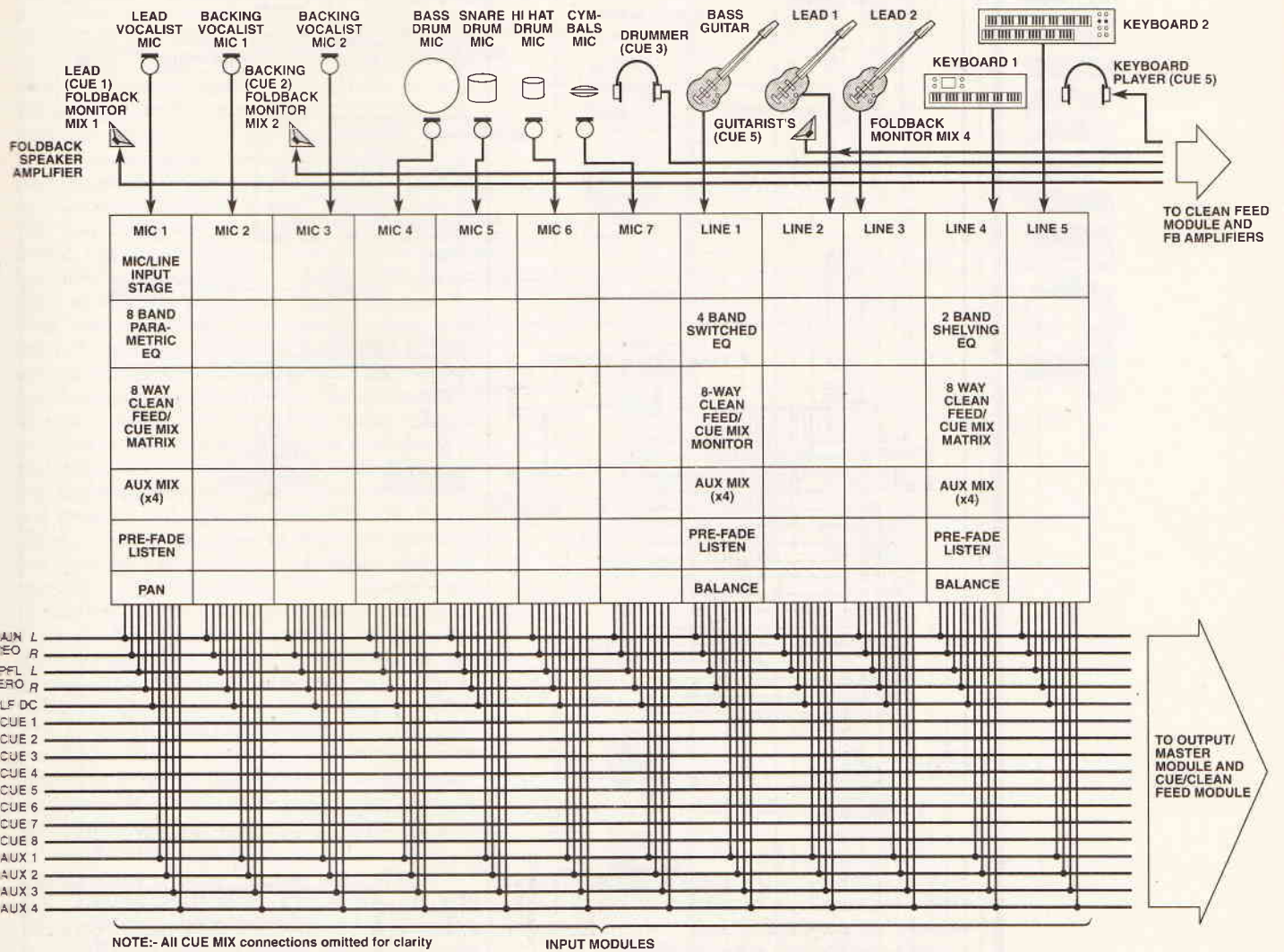


Fig. 4a

be made if all components are bought at one time and in bulk packs. The final prototype — which we'll show in its entirety at the earliest possible date — used some 325 pushbuttons, 333 control knobs, 320 pots, 600 LED's, 52 XLR's, 30 faders, 60 jack sockets and 350 odd switches. Finally, and most importantly for the home constructor, the prototype shown on the front cover was built using tools available to those with a reasonably equipped workshop, the only power tools utilised being an orbital sander (for the woodwork) and a pillar drill for all of the holes. I say this only to demonstrate that it is possible to build it at home using everyday tools, although had I been able to use a milling machine at the local technical college (useful for fader slots and in-line holes), I would have.

All of the modules feature PCB-mounted input and output connectors, switches and pots where at all possible, so minimising the opportunity for hum loops or instability to be introduced because of pickup in the wiring.

and champagne-coloured hi-fi separates. Yes indeed!

A wise investment before any metalworking is undertaken might be a set of needle files and some Q-MAX punches, in view of the multitude of holes in the panels of each module.

The modules will be featured in the following order:

- Power Supply Unit
- Input Channel Modules (and associated plug-in daughter boards)
- Group/Monitor Module (and associated Electronic Switching Matrix)
- Auxiliary and Communication Module
- Output Module
- Meter Pod and optional Digital Group Routing Module
- Fader Automation, Digital Control and MIDI/External Control Module
- Motherboard, Wiring Harness, Casing design and Final Construction

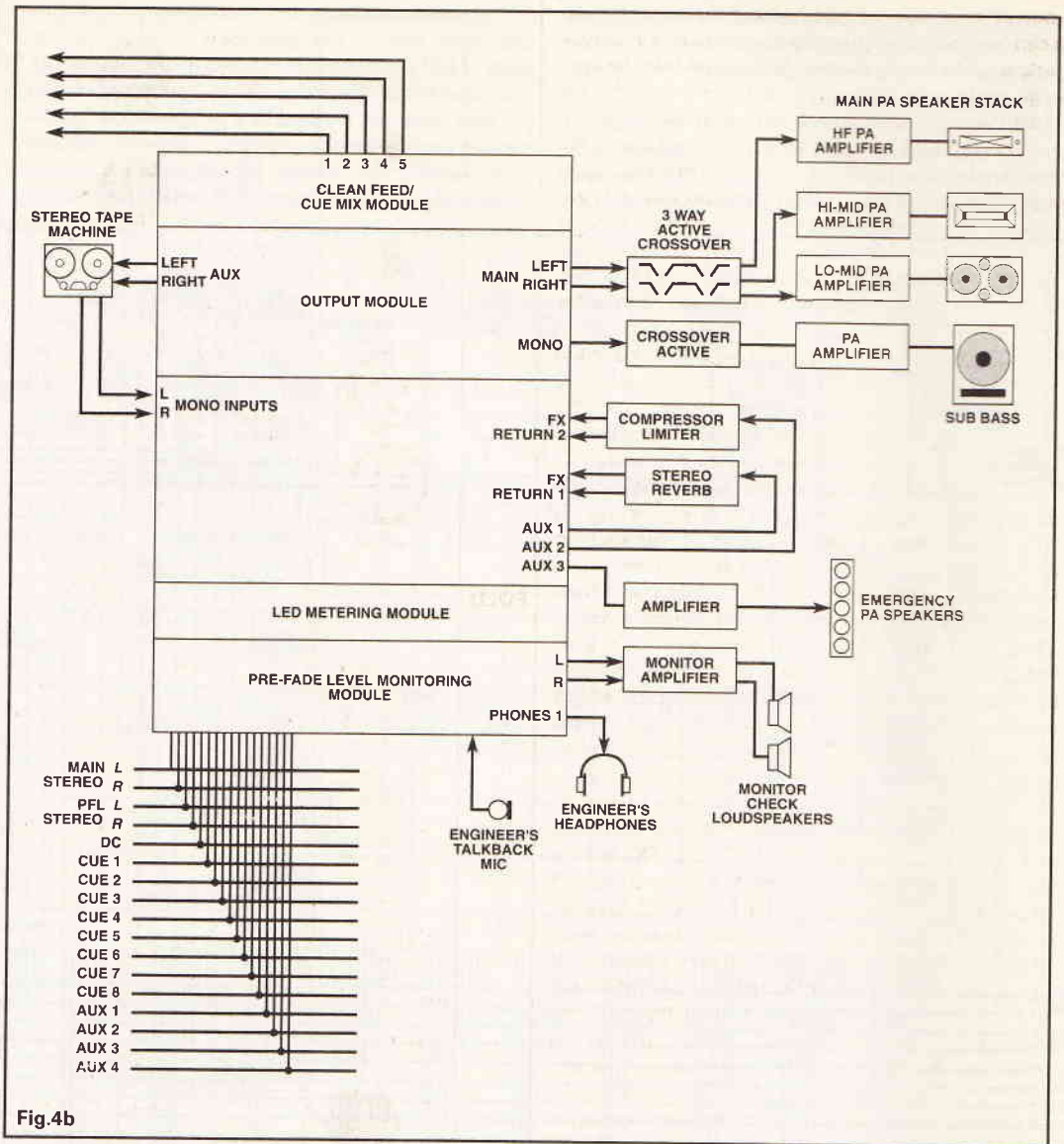


Fig.4b

Use of the console in each of its three intended environments

Please note that this is a listing merely of the order in which each will appear, and either because of space constraints, complexity of certain modules or simply because it is more logical, some of the parts may be featured over a period of two issues.

Component Parts

Mono Mic/Line Input Module

The input modules are fairly self-explanatory, allowing either Mic or Line Inputs on the mono input module with up to 80dB of gain for microphones and 20dB of gain or attenuation for line inputs whilst both inputs may be balanced or unbalanced although ultimate performance is gained when the modules are used with balanced inputs. A 48V supply is available for the phantom powering of microphones which require it, this being switched on or off via a fascia-mounted push-button. Inputs are via XLR chassis-mounting connectors for both Mic and Line inputs with an additional 1/4" 3-pole mono switched jack socket as a parallel input for line level signals — more of the reasoning behind this later — and a socket of the same type for the channel insert point.

There is a 100Hz high pass filter and a 4 band equalisation section, with high and low pass shelving filters offering ± 20 dB of control at 100Hz and 10kHz respectively and two, swept, full parametric mid sections with boost or cut, Q and centre frequency all

independently variable.

The EQ section may be switched in or out as required.

Post EQ but pre-fader, there is a CHANNEL INSERT socket which is wired in the 'normal' way, that is, with no jack inserted, any signal present passes in, through and out of the socket's switch contacts unimpeded. Inserting a stereo jack socket breaks the signal away, it passing out from the channel via the 'tip' contact, where it may, for example, be inputted to an external FX unit such as reverb. It is processed and can then re-enter the channel circuitry via the ring contact of the socket. In this way, effects units can be patched to individual channels in isolation.

There can also be fitted up to four separate Auxiliary Mixes, each independently switchable either PRE or POST FADE. In disco or presentation type situations, AUX 1 and its associated PRE/POST switch can be re-configured as an ACTIVE/PASSIVE MIX, the setting of the PRE/POST switch in this instance determining whether this channel is active in ducking other channels when live or whether it is one of the channels which itself is 'ducked' or attenuated when an ACTIVE channel is live. The level pot in this instance controls the amount of 'ducking' or attenuation.

The first of the input module options is the Group Routing Switch Matrix, which will be of most use to those who envisage constructing the console for a Multitrack recording situation. This can be a passive switching matrix ie direct mechanical switching of

sources or for those who wish to automate the console, it can be made active using logic control and analogue switches. The Group Routing Matrix could also be used to generate up to eight foldback, PA or monitor mixes when the unit is used as a live music mixer.

The second of the input module options is the clean feed matrix, which can be used to originate up to eight clean feed mixes. A clean feed mix is one where the mix contains all channels but one so for instance on an eight channel desk, clean feed mix 1 would contain inputs from channels 2 to 8 inclusive and might be used to send cue programme to the telephone contributor on channel 1. In this way, he would here everything but his own contribution — hearing one's own voice in the telephone earpiece, especially after EQ etc, can be a most disconcerting experience. Also on this channel, there is a Pan pot used to position the source in the stereo image and finally, and most importantly, the Channel Fader. Options in this area of the module include Fader or pushbutton control of remote units eg 'Mic Live' lamps or fader control of loudspeaker muting. The channel fader can control channel signal level directly or it can control a VCA, which then allows fitting of the fader automation unit. There is also a 'Peak' LED fitted which lights when the signal level within the module is 5dB below clipping and the very important PREFADE LISTEN button which allows monitoring in isolation (via headphones, loudspeakers or console metering) of that channel. It also operates as a SOLO button when the console is operated in multi-track Mixdown mode, SOLO in effect being an exclusive AFL (After Fader Level) monitor of that point and channel. The optional CHANNEL ON button allows manual or automated muting of the channel if and when this is required and the UPDATE LED's are connected with this same facility, showing local channel write of the new fader or group position or status. An eleven element bargraph adjacent to the channel fader shows the gain setting through that channel — this may or may not be equal to that shown visibly by the channel fader depending on which WRITE mode has been selected on the master module. The display changes from bar to dot after any fader movement or when the VCA is no longer under machine control. In this way there is an immediate and highly visible marker of both the control status and gain settings of individual channels.

Stereo Line Input Module

This is similar in many respects to the Mono input module apart from the obvious difference, of course, in that it allows the connection of two stereo sources, one balanced and one unbalanced as channel inputs. The unbalanced input may have an optional high quality RIAA phono equalisation module fitted.

Provision is also made for the 'monoiing' of inputs, either using an input on left, right or both channel input connectors.

Again, there is a switchable 100Hz high pass filter and an EQ IN/OUT pushbutton. A two band high and low shelving equaliser is fitted as standard although full parametric EQ may be fitted as an option. This parametric equaliser differs from that fitted on the Mic/Line module in that centre frequency is variable in only discrete steps and boost/cut and Q are the only parameters available as fully variable although both, of necessity, operate over a much more restricted range than those fitted to the mono channels.

There is also the facility for the fitting of up to four AUX MIXes, all able to be switched PRE or POST FADE. A Group Routing matrix may also be fitted if required. A BALANCE pot replaces the PAN control and allows minor errors in the stereo balance of the channel to be corrected.

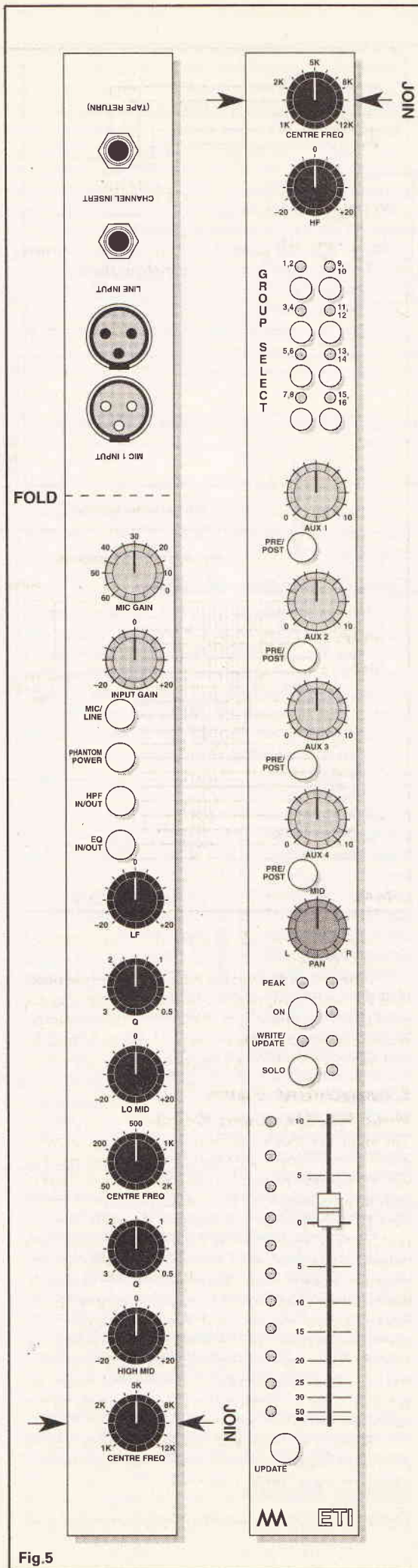


Fig.5



PROJECT

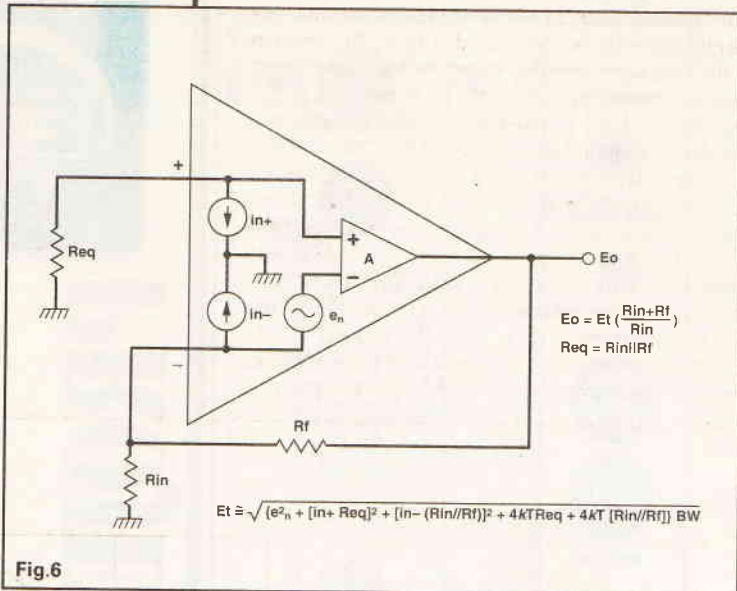


Fig.6

The PFL, CHANNEL ON, remote switching and fader automation/muting are as on the mono input channel, as is the CHANNEL INSERT socket.

Group/Monitor Module

The Group Module is the first of the optional MODULES as opposed to sub-modules and as with the Group Routing Switch Matrix, is of most use — mandatory — in a multitrack recording situation. Each module houses controls for two separate Group/Monitor sections which are entirely independent. The console therefore uses the Split — as opposed to In-line — method of monitoring, so-called because these are modules separate or split from the input modules. An In-line configuration would mean that the controls for the group and monitor functions were included and in-line with those of the channel input controls. This split desk topology allows for expansion far more easily and cost effectively than the In-line method, although this layout has advantages in its own right (not least of which is the fact that monitor channels have all of the facilities — full EQ etc -available to the input channel) and so is preferred by some.

Controls for Group signals (which are, of course, normally outgoing from the desk and destined for one track on a multi-track recording) include a Group Fader, Peak LED, PFL button and optional fader automation/mute facilities. In the associated monitor section, there is a high and low band shelving EQ section, MON. LEVEL control, GROUP PAN control and two switchable AUX MIX send level pots. There are also two buttons labelled RET and SUB, these switching between group output (source) or tape as Monitoring inputs and controlling the sub-grouping of the module. A GROUP INSERT socket is also provided.

Master Module

This is the main output module and has two LEFT and

RIGHT MASTER LEVEL faders, an AUX MIX MASTER section, test oscillator and rudimentary talk-back system controls. It also houses the PFL and other monitoring circuitry as well as controlling the desk metering, loudspeaker muting and headphone driving circuitry. Other outputs are provided, their levels being controlled by the respective LEVEL controls and each able to be mono-ed if so desired. Master Insert sockets are provided. This is the most basic form of this module and is the simplest required for correct operation of the console. It can be fitted with additional sub-modules (these sharing the same metalwork) or in some instances, it may be preferable for these units to become proper 'full' modules in their own right — indeed, this may prove necessary for some as there is not enough room physically in the Master module 'strip' to accommodate all of the sub-modules.

Figure 5 shows the front panel marking of the input module fitted to the prototype.

The 'hybrid' modules include the Meter Bridge, Communications module, Automation module and MIDI/Group Routing module.

A fuller explanation of the facilities available to the user in each of the different configurations would be somewhat pointless at present, since a detailed description of each of the modules is necessary before any full understanding of the ancillary parts can be gained. Suffice to say that it will be worth the wait!

Mic Input Amplifier

As we said more than once in the feature on mixing consoles, the noise performance of the unit as a whole is dictated by two main factors generally, these being the design of the input channel (mic input) and the design of the mixing bus. There are, of course, other areas where bad or marginal design will impair the

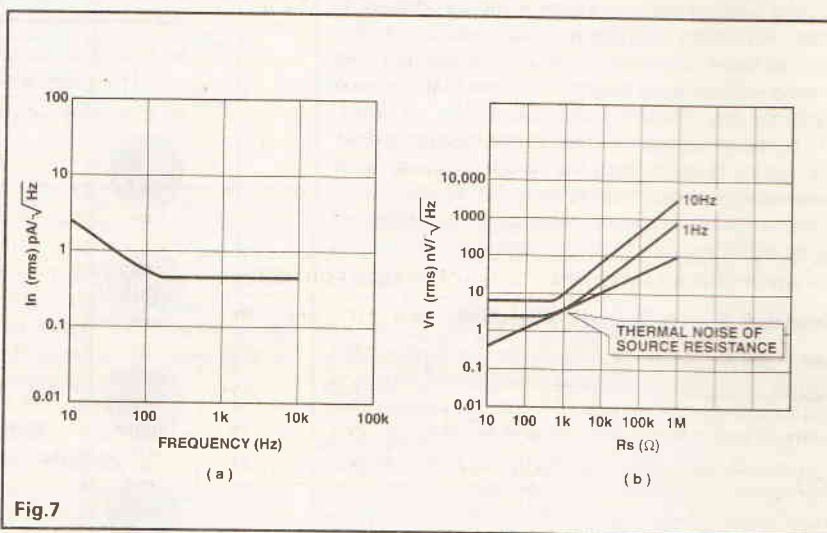


Fig.7

ultimate noise performance but none more seriously than those just mentioned.

Microphones — Taking The Hiss

I said in the opening paragraphs that we would discuss at greater length both the options open to us at each stage in the design and evolution of a particular function and the pros and cons of each and all available. There are obviously certain areas where our choice is limited by complexity, cost or any number of different reasons and where this is the case, I shall endeavour to explain why I have chosen a particular avenue of thought or design. In this way, I hope that I can both educate those who know less than myself on the subject and also stimulate the design-orientated thought processes of those who know more. It should be an interesting eight months or so...

Mic/Line First Input Stage

Microphones used in professional applications encounter an extremely wide dynamic range of sound pressure levels, ranging from about 30dB SPL (ambient noise in a very quiet room) to over 130dB SPL. (Anyone who has miked up something like a dance or swing band will know to the deciBel just exactly how wide. The output voltage of a typical low impedance (200R) microphone over this range of SPL's will vary from 20μV to 2V RMS, while its self-generated output noise would be in the order of 0.25μV over a 20kHz bandwidth. Since the dynamic range of the output of the microphone is so large, any preamplifier intended for use with a microphone should have adjustable gain so that it can be optimised for the signal levels that will be present in a given situation. Large signals should be handled without clipping or excessive distortion whilst small signals should not be degraded by amplifier noise. In a conservative low noise design, the preamplifier should contribute no more noise to the output signal than does the resistive portion of the source impedance. In practical applications, however, it is often reasonable to allow a higher level of input noise since ambient room noise will usually cause a noise voltage at the microphone output terminals that is in the order of 30dB greater than the intrinsic noise floor (due to source resistance) of the microphone.

When long cables are used with a microphone, its output signal is susceptible to contamination by external magnetic fields (especially mains hum). In order to minimise this problem, the outputs of most professional microphones are balanced, driving a twisted pair of wires with signals in opposite phase. In an ideal situation, magnetic fields will induce equal voltages on each of the two wires, which can then be cancelled out if the signals are applied to a transformer or differential amplifier at the preamp input.

Operational amplifier noise is nearly random in nature and determines the ultimate lower limit of signal handling capability.

It is specified as Equivalent Input Noise (or EIN for short) and is increased by the noise gain of the stage. A circuit model is shown in Figure 6.

IMPORTANT AC ELECTRICAL CHARACTERISTICS FOR NE5534					
PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
INPUT NOISE VOLTAGE	f _o = 30Hz f _o = 1kHz		7.0 4.0		nV/√Hz
INPUT NOISE CURRENT	f _o = 30Hz f _o = 1kHz		2.5 0.6		pA/√Hz
BROADBAND NOISE FIGURE	f = 10Hz-20kHz, R _s = 5kΩ		0.9		dB
GAIN BANDWIDTH PRODUCT	C _c = 22pF, C _L = 100pF		10		MHz

Fig.9

The noise generators are modelled as a series voltage noise generator, e_n , and as shunt circuit noise generators, i_{n+} and i_{n-} . These generators represent the mean values of voltage and current noise referred to the input of the amplifier and are specified in terms of noise density in volts-squared or amperes-squared per Hertz of bandwidth. To these noise generators we must add two other noise sources — the thermal noise of the source resistances, R_s , seen by the amplifier, which is Req and R_{in}/R_t .

Thus, an amplifier in a real life situation — a mixing console mic. amp, for example — has five potential sources of noise to be considered for minimising. First, there is the thermal noise of the two source resistances seen by the inputs, which is an irreducible minimum, existing even in an ideal, noiseless amplifier. Next, there are the noise current and noise voltage gener-

ators. For low values of source resistance, the effect of i_n is a minimum. Under these conditions, e_n will dominate as the source of amplifier noise. As the source resistance is increased, the effect of i_n increases until at high source resistances, i_{n+} (Req) and i_{n-} (R_{in}/Req) are the dominant components of amplifier input noise. Thus, in op-amp specifications, these two parameters are detailed separately, with e_n specified at low source resistance and specified at high source resistance. Both e_n and i_n are specified in terms of spectral density, measured with a narrow-bandwidth filter at a series of points across the useful spectrum of the amplifier. Data is given in terms of e_n (or e_n^2) or (or i_n^2). Graphs of the important parameters of a typical low noise op-amp, the audio industry standard NE5534, are given in

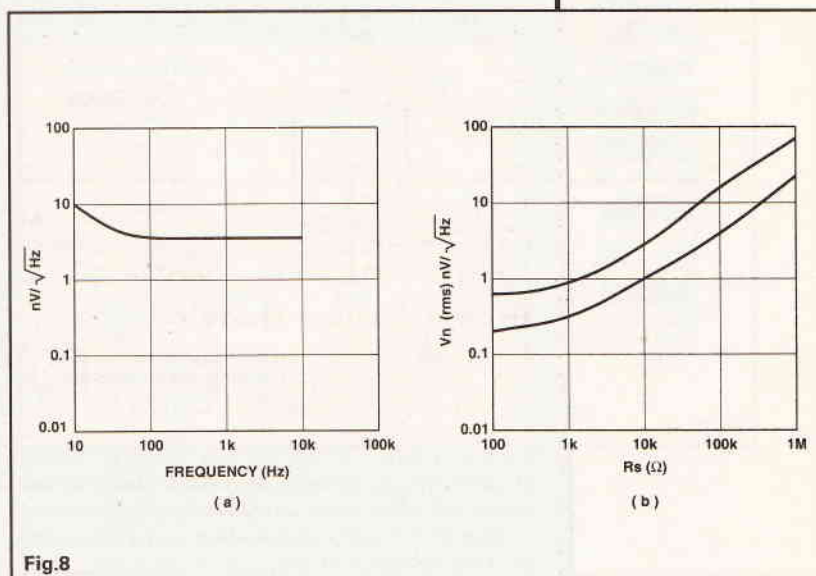


Fig.8

Figures 7, 8 and 9. These curves are given in terms of $e_n/\sqrt{\text{Hz}}$ and $i_n/\sqrt{\text{Hz}}$, but conversion can be obtained by squaring or extracting the root of the given parameter as appropriate.

Although the spectral densities of both e_n and i_n are obviously not flat, it is not unreasonable to select a mean value for e_n and i_n , if their total variation is within the same order of magnitude. Accurate calculation of total RMS noise would involve integration across the bandwidth of the amplifier, but the simplified (simplified?) approach given here yields order of magnitude estimates of noise performance and is more than adequate for the purposes of comparing different products. It follows, therefore, that given values for e_n , i_n and bandwidth, the total noise of the circuit can be approximated

as follows

$$E_t = \sqrt{(e_n^2 + [i_{n+} + \text{Req}]^2 + [i_{n-}(R_{in}/R_f)]^2 + 4kT\text{Req} + 4kT[R_{in}/R_f])BW}$$

where E_t = Total circuit noise

e_n is the amplifier noise voltage $V/\sqrt{\text{Hz}}$

i_n is the amplifier noise current $A/\sqrt{\text{Hz}}$ (i_{n+} or i_{n-})

Req and R_{in}/R_t are the source resistances ($\text{Req} = R_{in}/R_f$)

K is Boltzmann's constant (1.38×10^{-23} J/K)

T is the absolute temperature

BW is the noise bandwidth in Hertz

From the expression, it is obvious that as e_n and i_n are reduced, the total noise approaches the thermal noise of R_s . In choosing an amplifier, requirements (such as those for a microphone pre-amp) will often dictate a certain R_s from which the amplifier must work. This will dictate which of the noise generators is

dominant and therefore, which specification must be minimised — e_n or i_n . In general, low bias current bipolar types or FET input types will have lower current noise and tend to be quieter with R_s above 10k. Below 10k, bipolar types (because of lower voltage noise) have the advantage. In any instance, an absolute minimum of R_s must be used so that R_s is composed largely

optimum turns ratio to match a given source resistance, R_s , to the characteristic noise resistance, R_n , of the op-amp in the circuit, R_n must be first calculated from the specified data for e and i as follows:

$$R_n = e_n / i_n$$

where e_n is in $V/\sqrt{\text{Hz}}$ and i_n is in $A/\sqrt{\text{Hz}}$. The turns ratio for T1 may be calculated as:

$$N_s/N_p = \sqrt{R_n/R_s}$$

For the NE5534, the values for e_n and i_n are $4.0\text{nV}/\sqrt{\text{Hz}}$ and $0.4\text{pA}/\sqrt{\text{Hz}}$ respectively; therefore, $R_n = e_n/i_n = 4.0 \times 10^{-9}/0.4 \times 10^{-12} = 10\text{k}$

Since both e_n and i_n will change with frequency, R_n will also change with frequency. Therefore, an approximate value for R_n can be used with little error for calculation purposes in broadband amplifiers. In this example, if R_s is 200R, then the turns ratio for T1 will be:

$$N_s/N_p = \sqrt{R_n/R_s} = \sqrt{10000/200} = 7$$

A transformer which fulfils this requirement would then be selected for T1 — the transformer, of necessity, would be a shielded type and one suitable for operation in a low-level environment.

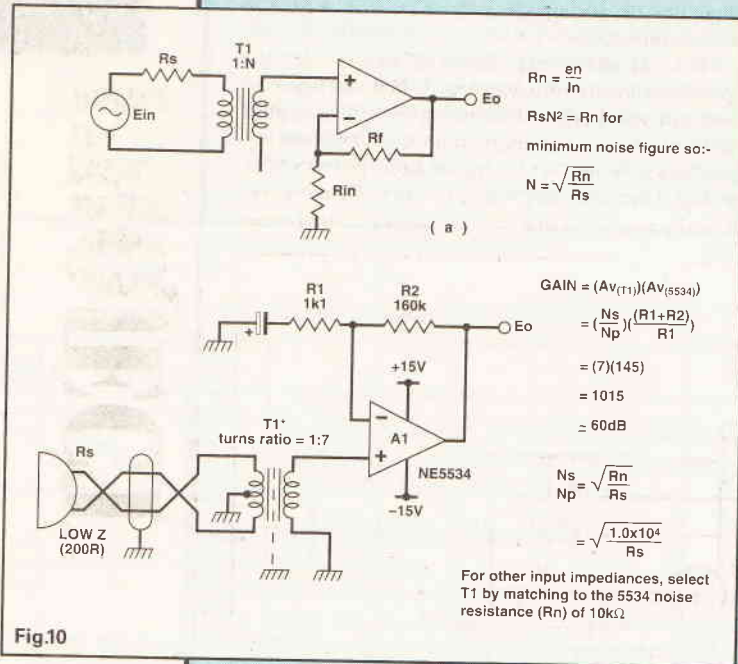


Fig.10

of generator resistance. This means that feedback resistances must be low in relation to the generator resistance. Another consideration is that the non-inverting configuration has only half the noise gain of the inverting configuration for equal signal gains, thus offering a distinct advantage in signal to noise ratio.

In circumstances where it is possible to control source impedance, the characteristic noise resistance, R_n , of the amplifier may be used to advantage; best noise performance for a given IC is obtained when the source resistance is equal to R_n . Thus, in AC applications, optimum performance may be obtained by using a transformer with a turns ratio selected to transform the actual source impedance to the noise resistance of the amplifier. I said in previous issues that designs using transformer inputs had lost vogue somewhat in recent years — this was a slight generalisation as we can see from the above that they can be very useful. They are still used extensively in mixers designed for broadcast purposes where the isolation they afford is completely unsurpassed by any electronic balanced input stages. Other shortcomings listed included cost, linearity at low frequencies and distortion. Cost becomes less of a deciding factor when a manufacturer can place an order for 2000 of the devices and so negotiate bulk discounts, and the linearity problem can be minimised by good design. A typical transformer Mic Input is shown in Figure 10.

The transformer must fulfil certain important requirements. It should:

Transform the impedance of the mic capsule (typically in the order of 150-200R) to the impedance required of the input channel (typically 1k Ω).

Provide good rejection of common-mode signals.

Match the source resistance to the characteristic noise resistance of the op-amp so that the best noise performance is attained. This is the case when $R_s = R_n$.

Provide some degree of voltage gain for the mic input signal.

Refer to Figure 10 and part of the op-amp specification. We have shown that in order to determine an

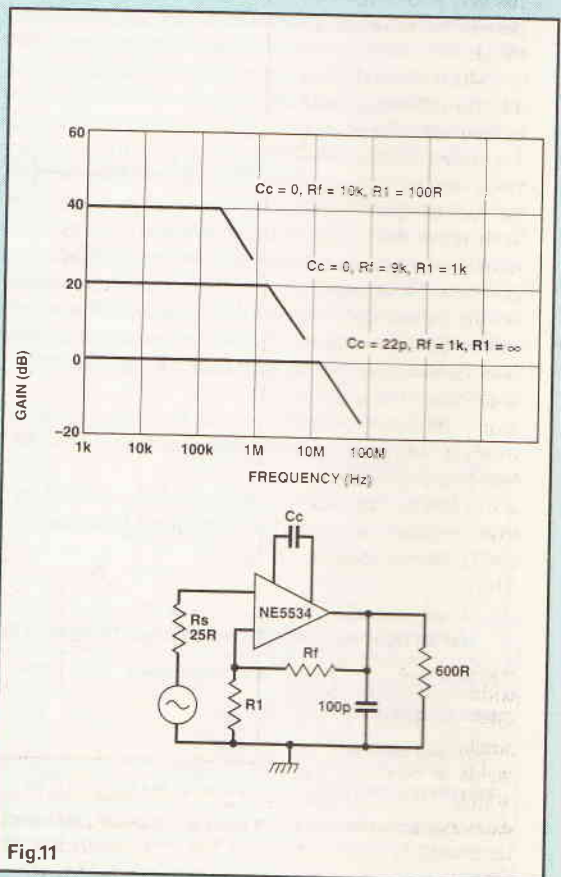


Fig.11

Input Impedance (R_{eq}) = $N^2 \times R = 7^2 \times 200$

The use of a transformer allows the input stage to achieve an equivalent input noise (referred to T1 input) that is only a few dB above the theoretical limit ie very close indeed to the thermal noise of the source resistance. As an example, the thermal noise of a 200R resistor in a 20kHz bandwidth at room temperature (normal operating conditions) is:

$$E_n = \sqrt{4kT(200)(2 \times 10^4)} = \sqrt{4 \times 1.38 \times 10^{-23} \times 298 \times 200 \times 20 \times 10^3} = 260\text{nV}$$

Thus, using the noise figure of 0.9dB taken from the manufacturer's data, the circuit shown in the figure can be expected to have an input referred noise of 260nV or less with a 200R source.

One of the other requirements which we specified, that of gain, is also provided for by the turns ratio of the transformer. This gain is advantageous in that it

is 'noiseless'. For a given circuit gain, A_v , this reduces the gain required of the op-amp, A , to;

$$A = A_v / N_s : N_p$$

It follows that the composite gain is the product of the transformer gain ($N_s : N_p$) and $(R_1 + R_2) : R_1$. This is advantageous in that it allows more loop gain and so greater accuracy and lower distortion since in practice, almost all of the full unloaded voltage gain of the transformer is realised as it looks into the bootstrapped non-inverting input of the op-amp, which has an impedance of many Megohms.

In Figure 10, the source resistance seen by the op-amp is relatively high (10k) and so feedback resistances can be higher without affecting noise performance.

We must remember that a real operational amplifier has neither infinite gain nor infinite bandwidth. Open loop bandwidth begins to roll off from the full DC value at some low frequency (usually about 10Hz in general purpose amplifiers).

As shown in Figure 11, the roll-off is 6dB/octave with increasing frequency until the unity gain frequency, f_1 is reached. In a curve such as this, the product of gain and frequency is constant for any point on the curve. Thus the unity gain frequency also defines the available gain at any point along the curve. The product of gain and bandwidth (Gain Bandwidth Product or GBP) in an amplifier response such as this is constant. Thus;

$$GBP = A_v BW$$

As an example, for a gain of 100, the bandwidth is 100kHz, (for a GBP of 10MHz), and similarly, a gain of 60dB yields a bandwidth of 10kHz. Thus, the rationing of gain and bandwidth is an exchange process – if more gain is necessary, reduced bandwidth is the consequence. We must ensure that all amplifier circuits have the necessary bandwidth when configured for high gain.

And so to the other type of mic input stage, that of the electronic balancing circuitry. From the previous transformer example, we can see that for optimum noise performance, it is imperative that we match as best we can the source resistance and the characteristic noise resistance of the op-amp. From the spec. of the op-amp and because of the internal design of the IC, we can see that the best performance is realised with source resistances much higher than the 1k Ω of a normal direct-coupled Mic Input. This means, of course, that unless we can tolerate a serious compromise in the front-end noise performance, the use of the op-amp for direct low noise amplification of microphone signals is strictly verboten.

Instead, we put to good use the superior noise performance at lower source resistances of the transistor. Figure 12 shows a typical example of this input

stage. Q1 and Q2 are a super-matched beta pair operated in differential, long-tailed pair configuration. They provide source impedance matching and initial amplification of the mic signal. Using a supermatched pair, close-tolerance resistors and a differential-style output to the op-amp means that noise and common-mode rejection are excellent. The op-amp provides the remainder of the amplification necessary and also gives an unbalanced output.

Now, which type of circuitry shall we use as the Mic Input stage for the Anniversary 20 Mixer? Until next month, in true 'Perils of Pauline' style, we'll leave all of you to muse over the information thus far presented and deduce from it what kind of circuitry HAS been employed in the Input Channel circuitry. Next month, I'll briefly recap and then go on to explain why I chose

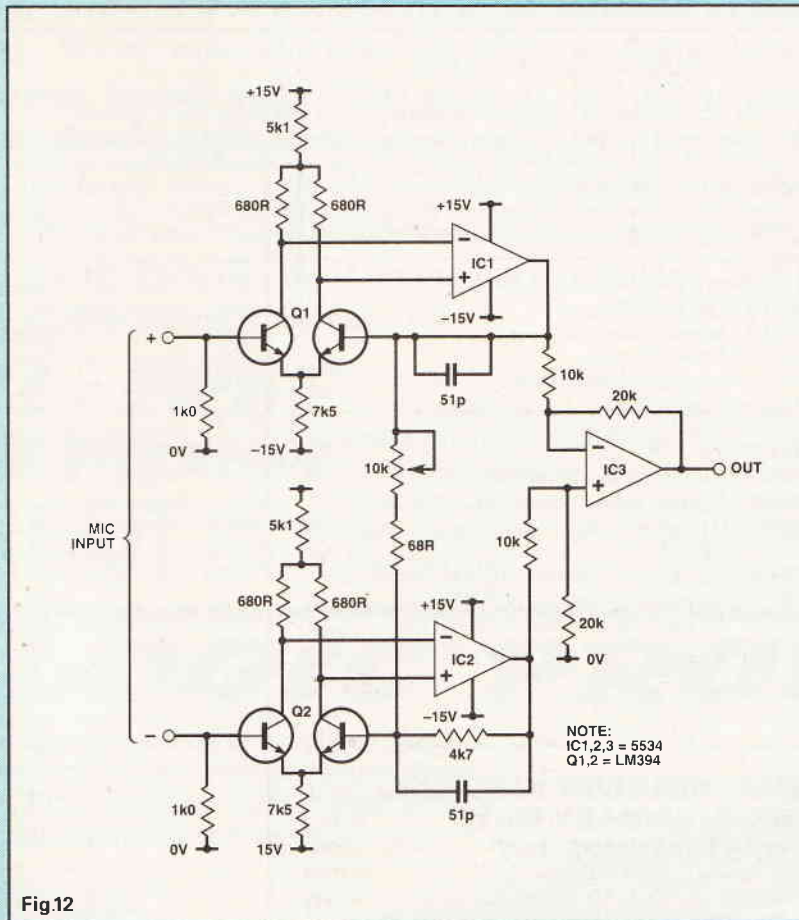


Fig.12

what I chose. Circuit diagrams etc will then be published. We'll also discuss the merits of good power supplies.

As a footnote, I should like to say that I have approached a number of companies who I thought might be interested in marketing a kit of this project. Thus far, there has been a resounding lack of success. If there are any directors of small metalworking companies out there who would be interested in producing the metalwork for this project, I would be delighted to hear from them . . .

References

Horowitz and Hill The Art of Electronics – Low noise design

Walter Jung : IC Op-amp Cookbook – Miscellaneous Audio Circuits

National Semiconductor Linear Applications Handbook : Application Notes AN20 (Applications Guide for Op-amps) AN346 (High Performance Audio Applications of the LM833)



PROJECT

**TELEPHONE
ORDERS**
may be made on
**(0442
66551)**
ACCESS or VISA



**ELECTRONICS
TODAY INTERNATIONAL**

**PCB
SERVICE**

April

**Price
code** **Price
(inc.
VAT)**

C **£1.80**
D **£2.50**
E **£3.25**
F **£4.00**
G **£4.75**
H **£5.50**
J **£6.62**
K **£7.20**
L **£8.80**
M **£10.60**
N **£13.10**
O **£15.80**
P **£17.90**
Q **£21.80**
R **£23.90**
S **£25.90**
T **£29.00**
U **£32.20**
V **£35.80**
W **£37.90**
X **£40.70**

E9204-1 Auto Car Lights **F**

PCBs for the remaining projects are available from the companies lists in Buylines.

Use the form or a photocopy for your order. Please fill our all parts of the form. Make sure you use the board reference numbers. This not only identifies the board but also tells you when the project was published. The first two numbers are the year, the next two are the month.

Terms are strictly payment with order. We cannot accept official orders but we can supply a proforma invoice if required. Such orders will not be processed until payment is received.

E9103-2	64K EPROM Emulator	N	E9107-4	The Consort Loudspeaker	H
E9103-3	SSB Radio Receiver	G	E9108-1	Pulsed Width Train Controller	E
E9103-4	Active Loudspeaker board	H	E9108-2	Model Speed Controller - Main Board	F
E9104-1	Testmeter Volts	E	E9108-3	Model Speed Controller - Power Supply	F
E9104-2	Active Direct Injection Box	F	E9109-1	Geiger Counter	E
E9104-3	EPROM Eraser	F	E9109-2	Hemisync Waveform Generator Board	G
E9104-4	Digital Tachometer	F	E9109-3	Hemisync Pulse Generator Board	F
E9104-5	Radio Calibrator	F	E9109-4	Hemisync Power Supply Board	C
E9105-1	Modulator Laser (2 boards)	H	E9109-5	Nightfighter Main Processor Board	O
E9105-2	Thyristor Tester	F	E9110-1	Freeze Alarm	E
E9105-3	Frequency Plotter	K	E9110-2	Document Saver	E
E9106-1	Laser Receiver	F	E9110-3	Proto-type Designer	J
E9106-2	Temperature Controller - Power Supply	G	E9110-4	Nightfighter - Sound to Light (double sided)	L
E9107-1	Temperature Controller - Main Board	K	E9110-5	Nightfighter - Ramp Generator Board	F
E9107-2	Temperature Controller - Probe PCB	F	E9110-6	Nightfighter - Cyclic Crossfade (double sided)	M
E9107-3	The Foot Tapper - Volume Control (double sided)	J	E9110-7	Nightfighter - Strobe Board (double sided)	J
			E9110-8	Nightfighter - 8 Channel Triac Board	N
			E9111-1	Digital Code Lock	L
			E9111-2	Switched Mode Power Supply	E
			E9111-3	Nightfighter Mode Selection (double sided)	J
			E9111-4	Nightfighter - Display Board (double sided)	M
			E9111-5	Nightfighter - Bass Beat Trigger (double sided)	L
			E9111-6	Nightfighter - Sequence Select (double sided)	H
			E9111-7	Nightfighter - Master Controller PSU	K
			E9111-8	Nightfighter - Output Switch (double sided)	M
			E9112-1	Nightfighter Sensor Switch Master Control (double sided)	L
			E9112-2	Nightfighter Sensor Switch Channel Control (double sided)	L
			E9112-3	Nightfighter Sensor Switch Sound Trigger	H
			E9112-4	Nightfighter Connector Board	F
			E9112-5	Nightfighter Sensor Switch PSU	K
			E9112-6	Nightfighter 8-Channel Input Interface (double sided)	P
			E9112-7	Power On and Overload Regulator	P
			E9201-1	Laboratory Power Supply	F
			E9201-2	Test Card Generator Board	M
			E9201-3	LED Star (double sided)	L
			E9201-4	Enlarger Timer Main PCB (double sided)	N
			E9201-5	Enlarger Timer Selector Board (double sided)	K
			E9201-6	Enlarger Timer Switch PCB	E
			E9202-1	Timer - Counter Driver (double sided)	F
			E9202-2	Timer - Time Base (double sided)	F
			E9202-3	Timer - Power Supply	C
			E9203-1	MIDI Switcher - Main Board	L
			E9203-2	MIDI Switcher - Power Supply	E
			E9203-3	Sine Wave Generator (surface mount)	F

**TO: ETI PCB SERVICE, READERS' SERVICES,
ARGUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD HP2 7ST**

Please supply:

Quantity	Ref. no.	Price Code	Price	Total Price
-----------------	-----------------	-------------------	--------------	--------------------

Post and packing

£0.75

Total enclosed

£

Please send my PCBs to: (BLOCK CAPITALS PLEASE)

Name

Address

Postcode

CHEQUES SHOULD BE MADE PAYABLE TO ASP Ltd.

GREENWELD

1992 SPRING SUPPLEMENT

Welcome to our 1992 Spring Supplement - free with our compliments with your favourite monthly magazine! Inside its 32 pages you'll find the usual mix of new and surplus items, together with a preview of a new category to be included in future Catalogues - Graphic Design Products. We're now stocking Staedtler and Kuretake pens, pencils, markers, drawing instruments, boards and cutting mats, as well as Humbrol airbrushes and a wider selection of paper, labels, staplers etc. Every constructor has to write and draw circuits from time to time, so we hope these additions prove useful to you. There's a wide range of new surplus lines all offering exceptional value for money, and don't miss the remarkable offer of a Hitachi scope with 25% discount on the back page! We look forward to receiving your order soon - the Order Form is on Page 29.

NEWSLINE weekly update on new stock. Call 0891 505121 (48p per min. peak, 34p off peak)

LOOK!! FREE
WITH ORDERS OVER £20.00
EASIWIRE KIT Retail Price
£15

The easy to use no-soldering wiring tool which makes construction of small electronic projects so simple!! All included in the kit are: wiring pen, utility tool, punched wiring board, self adhesive sheet, spring loaded terminals and jacks, spare spool of wire, excellent instruction book

You **MUST** stick this coupon to the Order Form for your **FREE** Easiwire

LOGIC PROBE

Suitable for displaying the logic state of each gate of TTL, CMOS etc. Logic state displayed in light and sound. Pulse enlargement capability allows pulse detection down to 25ns. Supplied with comprehensive instruction manual


Order Code Y132

SPECIAL PRICE

£8.88



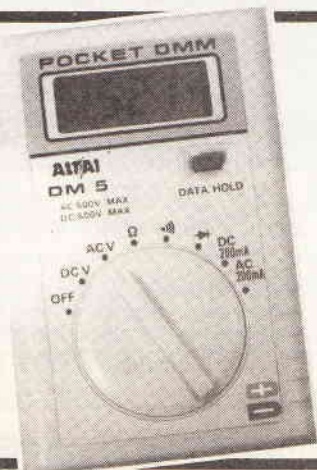Working voltage: 4-16V
 Thresholds: Hi 70% Vcc; Lo 30% Vcc
 Input Z: 1M. Max input freq: 20MHz



POCKET PERSONAL DMM

HC32 This neat little autoranging digital multimeter with built in test leads has a big range of features for such a handy instrument - up to 500V ac/dc, 6 resistance ranges to 20M, continuity tester, diode checker and both ac/dc current up to 200mA! Size 100x67x14mm

PERFECT PRICE

£15.00



**LIGHT
ACTIVATED**

F606 £13.95 6+ 9.92

LIGHT ACTIVATED SWITCH

Plug-in light activated switch, ideal for switching on lights automatically. When the ambient light level falls to a preset point power will be switched on to the built-in socket for a preset period of time. Light level and time-on period are fully adjustable. Controls: Light level, time

Power.....220/240Vac 50Hz
Max. load.....500W



AUTOMATIC

F608 £11.95 6+ 7.84

AUTOMATIC LIGHT SWITCH

Plug-in light switch which turn on table lamps, radios or other low power appliances (up to 500W) when the ambient light level falls below a preset level, switching off again when the light level rises.

Power.....220/240Vac 50Hz
Max. load.....500W
Dims.....145 x 65 x 42mm



PROGRAMMABLE

F607 £21.95 6+ 14.67

PLUG-IN TIMER

Plug-in timer capable of up to 56 programmable switching operations per week. The programming structure consists of 4 timed events occurring on each day, Monday to Friday and 4 timed events on both Saturday and Sunday (one event is an on/off cycle). The timer is simple to use and comes with full instructions.

Power.....220/240Vac 50Hz
Max. load.....3000W
Dims.....145 x 65 x 42mm



F653 £47.95 3+ 31.89

PIR ALARM KIT

A compact PIR alarm kit, ideal for small home installations, garages, caravans, trailers, trucks, boats, etc. The kit contains a combined PIR and alarm box, 3 magnetic reed switches, compact siren and power supply. Instruction manual and fixing screws included. An alkaline PP3 can be added for power failure protection.

PIR coverage.....100m²
Exit delay.....2.5 minutes
Entry delay.....15 seconds
Alarm reset time.....60 seconds
Power.....12Vdc or AC adaptor
Dims.....140 x 90 x 56mm (alarm panel/PIR)



**SUITABLE FOR PORCHES,
GARAGES, ETC.**

L134 £34.95 4+ 23.72

PIR GLOBE LIGHT

A stylish globe shaped lamp with built-in PIR detector which reacts to body heat, switching on the lamp whenever somebody is within the detection zone. A photo detector built into the unit prevents daylight operation. The sensitivity (detection range) is adjustable. Power: 220/240Vac 50Hz.

T072A £29.95 4+ 19.70



MESSAGE RECORD AND PLAYBACK

T072A ANNUNCIATOR
 A stand alone PIR message annunciator on which your own message, up to 20 secs long can be recorded on a microchip and played back every time someone is detected by the PIR. The recorded message can be speeded up or slowed down by a rotary control on the side. The message can be over-written at any time. Note: The message will be lost when the power is switched off.
Dims: 92x136x46
Power: 4xAA cells or external 6V .




F650 £95.00 5+ 60.30
VOLUMETRIC ALARM

A self-contained burglar alarm which requires nothing more of the user than to plug it in and switch it on, no further wiring is necessary. The alarm works by monitoring the air pressure around it, any change such as opening a door or window in the building will trigger the alarm 80 seconds later, unless the alarm is switched off by the key. An additional external alarm box is available (F651). Built-in back-up batteries prevent the alarm from being switched off by unplugging.

Exit delay time 40 seconds
 Entry delay time 20 seconds
 Power 220/240Vac 50Hz
 Dims 174 x 60 x 190mm


WITH BUILT-IN CONTROLLER

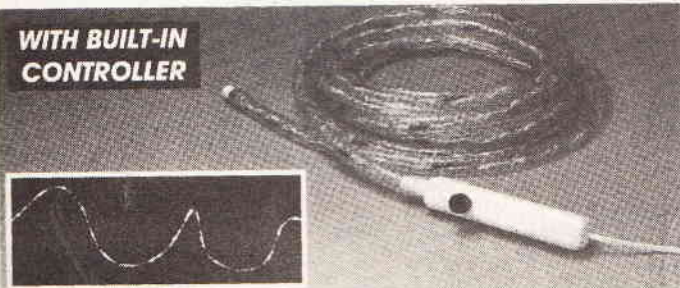

G008S £39.95 3+ 26.13
ROPE LIGHT

Self contained 3-colour rope light with built-in speed controller. 3 circuits of 20 lamps within a tough, blister effect 6m tube.


Length: 6m
 Power: 220/240Vac 50Hz

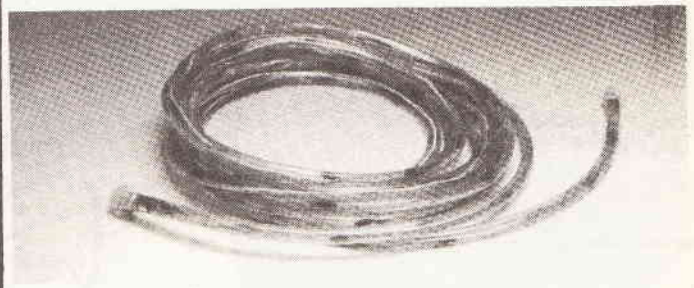

G008RA £21.95 3+ 14.67
ROPE LIGHT

5m tough but flexible plastic tube rope light. 4 circuits of 20 coloured bulbs. May be connected end to end to increase length. Suitable controller: G006M.


Length 5m

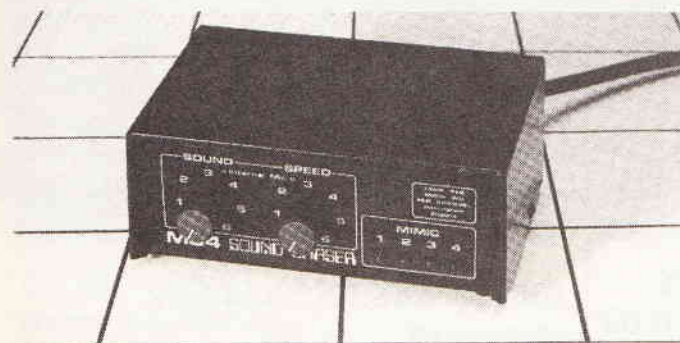

G006P £39.95 3+ 26.73
4-CHANNEL CONTROLLER

4-channel lighting controller with built-in mic, sensitivity control and speed control. Four front panel LEDs mimic the lighting effect. Output via 8-pin Bulgin socket

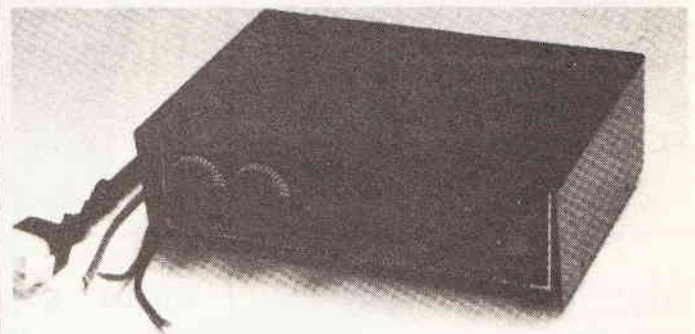Max output 1000W/channel resistive
 600W/channel inductive
 2500W total
 Power 220/240Vac 50Hz
 Dims 184 x 100 x 55mm



G006M £49.95 3+ 32.83
4-CHANNEL CONTROLLER


4 channel lighting controller with five built-in sound activated effects: 1 on/3 off, 2 on/2 off, 3 on/1 off, 4 on/0 off plus random, forward and reverse for all four sequences. Outputs via Bulgin socket and short lead with connector for rope lights.

Max output 1000W/channel
 2500W total
 Power 220/240Vac 50Hz
 Dims 184 x 100 x 55mm

PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT

VIDEO/AUDIO BARGAINS!

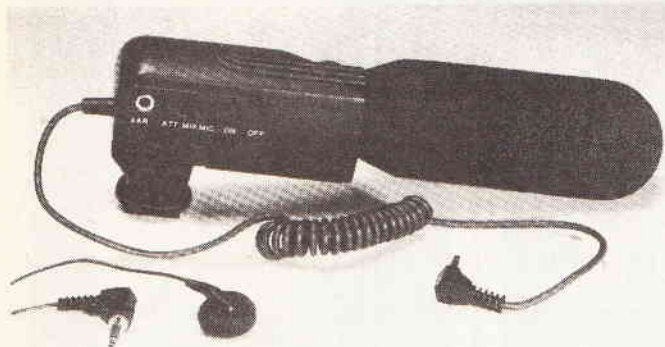
ENHANCE YOUR HOME VIDEOS WITH THESE PRODUCTS!!



G164G £32.95 3+ 22.11
CAMCORDER DUBBING MIC

A unique mic designed for direct dubbing of an external soundtrack, voice-over, etc. at source, whilst the camcorder is recording. A stereo 3.5mm input is provided in the side of the mic for insertion of the soundtrack and a rotary control provides balance between mic and soundtrack. An earphone jack is provided for monitoring the mix. Supplied with a mono in-ear phone.

Type	Super uni-directional electret condenser
Impedance	1kΩ
Response	30-15000Hz
Sensitivity	-45dB (@ mix max.)
Length	185mm

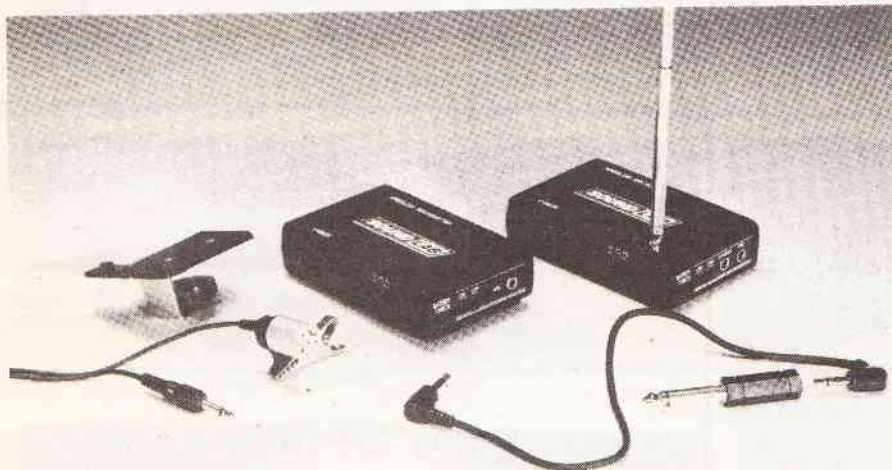

G211 £49.95 2+ 35.52
WIRELESS MICROPHONE

A 3-channel 2-part wireless microphone system designed for use with video cameras. The tie-clip mic has a remote belt clip transmitter with on/off switch. The receiver has a hot shoe for mounting on the video camera. The system allows greater mobility with a microphone than can be achieved with the camcorder mic.

WITH VINYL CARRYING CASE



T081 £47.95 3+ 32.09
VIDEO LIGHT

30W halogen video light with 6V 1700mAh battery pack. The video light is provided with a synchronisation lead which, when the light is switched to "remote", allows the light to switch on when the camcorder is switched on (Sony and Panasonic camcorder). The on/off/remote switch has a lock button to prevent accidental movement.

Packed: BOX

T081AA
Spare bulb **£4.95 5+ 3.28**




T081A £15.95
VIDEO LIGHT 4+ 10.63

30W video camera light with hot shoe fitting and power on/off switch. Accepts 6V 1700mAh battery pack (Sony NP55 and NP77 typically)

Packed: BOX

T081AA
Spare bulb **£4.95**

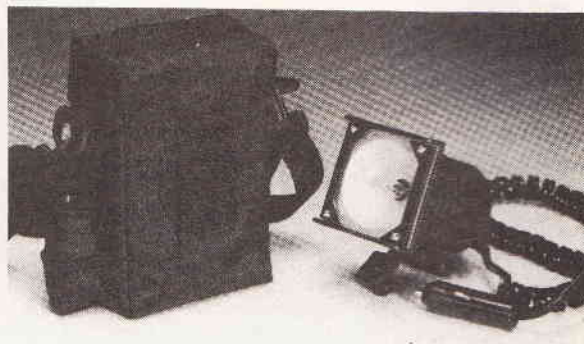


T081B £66.95 3+44.89
VIDEO LIGHT KIT

A semi-professional video light kit comprising 100W halogen lamp, remote 12Vdc 7Ah sealed lead acid battery in carrying case with shoulder strap, 220/240Vac operated battery charger and camcorder power supply adaptor.

Packed: BOX

T081BA Spare bulb **£3.75 5+ 2.80**

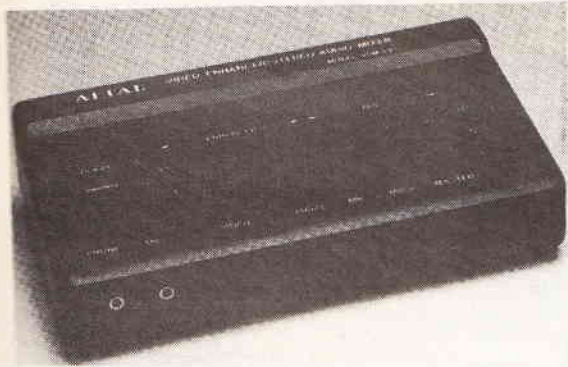
PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT



T128D £36.95 5+ 24.79

VIDEO ENHANCER/AUDIO MIXER

A 3-channel stereo video sound mixer with a built-in video enhancer, specifically designed for video dubbing. The audio input from the camera/VCR, mic and music sources can be mixed at will, with overall output controlled by a master slider. The video enhancer will clean up the picture on older recordings. Powered by an external 12Vdc power supply (not supplied). Complete with all connecting leads and adaptors.

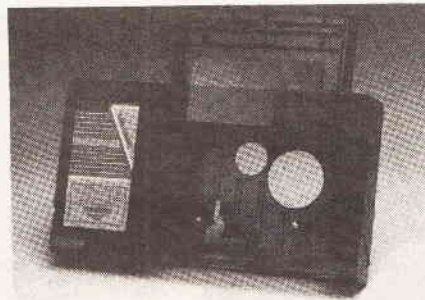

T122D £12.95 10+ 8.56

VHS-C TO VHS ADAPTOR

All mechanical adapter cassette allowing the playback of VHS-C tapes on VHS video players. The action of closing the door moves the tape into position.




T122K £6.95 10+ 4.80

45 minute tape.



T122J £6.95 10+ 4.80

30 minute tape.

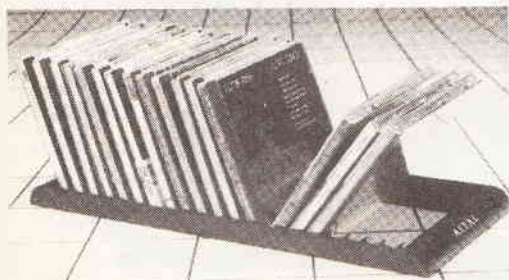

A163A £2.95 40+ 1.03
CD RACK

A unique CD storage system which will hold up to 20 CD's, in their cases, allowing them to flip back and forth as you search for the CD you want. Free standing and interlocking.

GAFFA TAPE

50m rolls of 2" wide self adhesive Gaffa tape

L099R Silver £6.50 10+ 4.36

L099S Black £6.50 10+ 4.36

DC POWER LEAD

Useful universal lead - reversible socket on the end of a DC power lead with 4 interchangeable plugs - 1.3, 2.1, 2.5DC & 3.5mm mono jack. 1.8m long.

A133A £1.25 50+ 0.75




A005A £27.95 5+ 19.03

STEREO PRE-AMP

Mains powered stereo pre-amp suitable for insertion between turntables, mics and other low level sources and aux/line inputs on mixers, amps, stack systems etc.

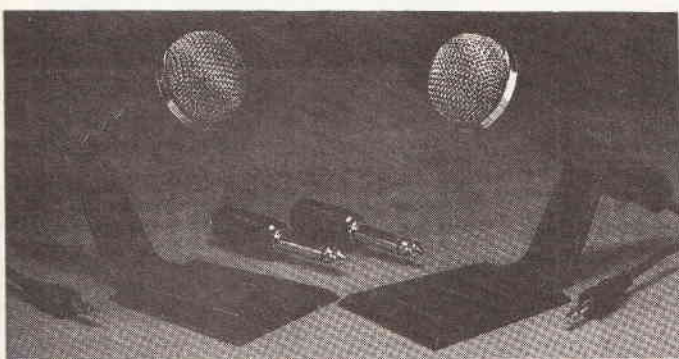Input impedance.....50kΩ
 Max. input level.....33mV (@ 1kHz)
 Max output level.....3.8V (@ 47kΩ load)
 S/N ratio.....more than 50Hz
 Input sensitivity.....2.5mV (output 300mV)
 Frequency response.....30 - 15kHz (RIAA)
 Power.....220/240Vac 50Hz
 Dims.....140 x 75 x 40mm




G170C £5.95 10+ 3.35

DYNAMIC MIC 200Ω

Pair of matched dynamic microphones. Black plastic body with chrome metal grille and chrome trim. On/off switch. Independent 1.2m leads terminating in 3.5mm jack plugs. Mic stands and 6.35mm adaptors included.

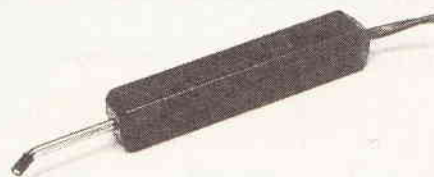Type.....Omni-directional dynamic
 Impedance.....200Ω
 Response.....90-10000Hz
 Sensitivity.....-76dB @ 1kHz
 Dia: Head.....32mm.
 Body.....17mm
 Length.....120mm



A170A £2.95
10+ 1.88

TAPE HEAD DEMAGNETIZER

A compact and easy to use tape head demagnetizer. Simply plug the demagnetizer in, press the red button and place the tip gently in contact with the tape head. Rotate the tip across the surface and withdraw slowly. Demagnetizing every 50 hours of play time improves playback and record quality.


Power: 220/240Vac 50Hz

B003C £39.95 5+ 26.40

GRAPHIC EQUALIZER

11-band graphic equalizer with sub-woofer output and CD input. The sub-woofer output has an adjustable cut-off frequency and level control. The case is standard DIN width for in-dash or under-dash mounting. Low level inputs and outputs only, via phono sockets.

Frequency response	20 - 25000Hz
Total harmonic distortion	Less than 0.05%
S/N ratio	85dB
Separation	65dB
Control frequencies	60, 120, 250, 380, 500, 750, 1k, 2k, 4k, 8k and 16kHz
Control range	12dB boost or cut
Power	12 - 14Vdc
Dims	178 x 25 x 140mm

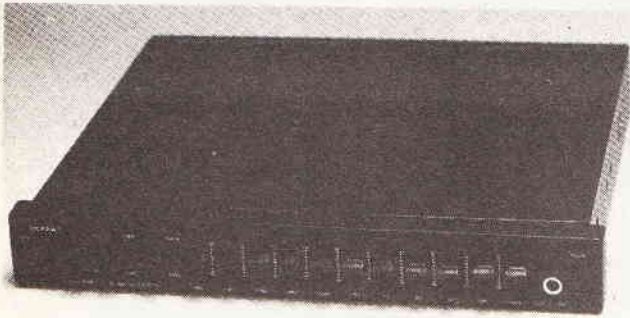

A085 £99.95 2+ 73.70

RADIO HEADPHONE SYSTEM



A radio headphone system comprising a radio transmitter, a belt-clip receiver and a pair of high quality headphones. The transmitter will accept inputs from three separate sources: CD, DAT, tape etc and additionally has a built-in mic with talk button for contacting the headphone wearer. The system allows complete freedom of movement within a range of approximately 100 feet of the transmitter.

Transmitter:

Input sensitivity	Source 1 & 2: 10kΩ/100m
.....	Source 3: 22kΩ/100m
Power	12Vdc 150mA

Receiver:

Frequency response	48 - 16000Hz
Power output	30mW/channel
Range	100ft (36m)
Power supply	PP3 battery
Battery life	8hrs nominal

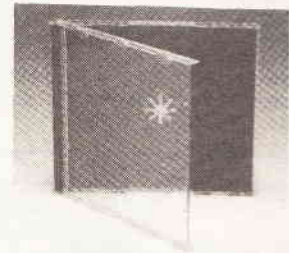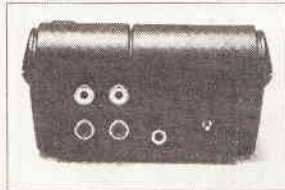

A162B £1.20
50+ 0.66

REPLACEMENT CD CASES

Replacement CD storage cases designed to be direct replacements for the originals supplied with compact discs. Two cases per pack.



A087F £8.95 10+ 5.15

STEREO HEADPHONES WITH BOOM MIC

Lightweight stereo headphones with adjustable dynamic boom mic. Tough plastic headband with stainless steel adjusters. Foam padded earpieces containing high quality samarium cobalt transducers for clear sound reproduction. High sensitivity miniature dynamic mic cartridge with foam windshield. Straight screened lead terminates in 6.35mm stereo plug for headphones and a 3.5mm mono plug for mic.

Headphones:

Type	Mylar transducer
Impedance	32Ω
Response	20 - 20000Hz
Power	150mW

Microphone:

Type	Omni-directional dynamic
Impedance	250Ω
Sensitivity	-78dB @ 1kHz

General:

Lead	2.5m straight screened
Plugs	6.35mm stereo and 3.5mm mono
Weight	80g





B049A **£12.95** 6+ 7.50
12Vdc TRAVEL KETTLE


12Vdc kettle complete with mounting stand, cup and cup holder with a self-adhesive base. Plugs directly into a car cigar lighter socket for power. A power-on light is provided at the base of the kettle. Ideal for cars, vans, campers etc.

Capacity.....0.5 pints (0.3lts)
 Power.....12Vdc 9A, 14Vdc 11A
 Dims.....143 x 125 x 112mm (approx)



B200Z **£1.95** 20+ 1.14
PLUG-IN FLASHING LED

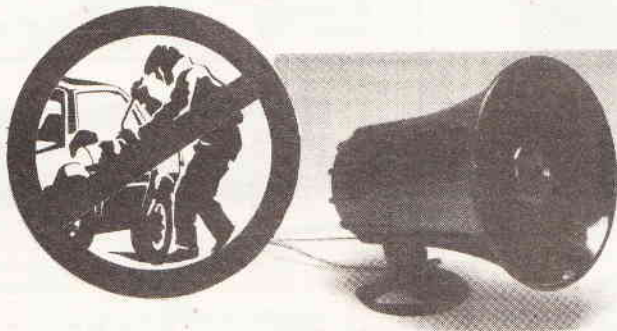A flashing LED built into a car cigar lighter plug to give visual warning that an alarm is activated (whether or not an alarm is fitted). Simply plugs into the car's cigar lighter socket.



B201 **£17.95** 10+ 11.93
CAR ALARM

Keyless, self-contained car alarm with simple, three wire connection into the car's wiring harness. The alarm is self arming one minute after the ignition is switched off. The alarm is current sensing and will operate 10 seconds after a door is opened. Once triggered the alarm will sound for 30 seconds before re-setting.

Operation.....Current sensing
 Reset time.....45 seconds
 Power.....12 - 14Vdc



B047D **£12.95** 10+ 8.84
AIR PURIFIER AND IONIZER

A compact, stylish ionizer and air purifier with a coverage volume of 14m³. Ideal for in car use with the DC lead provided or as a room purifier with the AC adaptor provided. Removes unpleasant smells, airborne dust, bacteria, tobacco smoke etc.

Power.....9-15Vdc or 220/240Vac via adaptor
 Dims.....160 x 95 x 43mm



B047E **£9.95** 10+ 6.50
AIR PURIFIER AND IONIZER

A compact, stylish ionizer and air purifier designed specifically for car, truck and bus use with a coverage volume of 14m³. Removes unpleasant smells, airborne dust, bacteria, tobacco smoke etc. Supplied with a double sided self adhesive pad.

Power.....12Vdc 1.8W
 Dims.....110 x 110 x 65mm

CLEANS AND REFRESHES THE AIR AROUND YOU

PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT



COMPUTER INTERFACING

Y122HR £99.95 2+ 66.73
10MΩ

The Y122HR (M365OCR) multimeter is capable of communicating either the current LCD readout or up to 5 stored measurement values direct to data acquisition systems, PC's, pen plotter, printer, etc. via its MT/RS232C interface cable. Interface cable and program disc included with meter.

- ★ 3.5 digit 17mm LCD display
- ★ 30 ranges including 20A ac/dc
- ★ Data hold
- ★ Max/min value capture
- ★ 40 point analog bargraph
- ★ Frequency counter
- ★ Logic test with auto level
- ★ Capacitance test
- ★ Continuity test with buzzer
- ★ Transistor and diode test
- ★ Built and tested to IEC 348
- ★ Fully shrouded test leads

AC volts	0-200m-2-20-200-750Vac ± 0.8%
DC volts	0-200m-2-20-200-1000Vdc ± 0.3%
AC current	0-2m-200m-20Aac ± 1.8%
DC current	0-200μ-2m-200m-20Adc ± 0.5%
Resistance	0-200-2k-20k-200k-2M-20MΩ ± 0.5%
Capacitance	0-2000pf-200n-20μF ± 2.0%
Frequency	0-20k-200kHz ± 2.0%
Transistor hFE	0-1000 NPN/PNP
Dims	176 x 90 x 36mm

Battery, instruction manual and carrying case included.


Packed: BOX



Y137M £8.95 5+ 6.03
DIGITAL THERMOMETER

A dual sensor digital thermometer designed for comparative temperature measurement, for example inside/outside temperature. The thermometer can be free standing or mounted with the Velcro strips provided. The remote sensor is fitted with a 3m lead and mounted with double sided tape. A digital clock is built in.


Temperature range.....	-20 0 to +70OC ± 1OC
Resolution.....	0.1OC
Power	P009H button cell

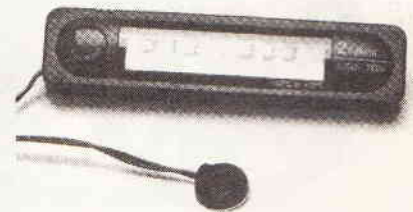

Y137N £11.95 5+ 7.50
DIGITAL THERMOMETER

Dual channel inside/outside comparative temperature thermometer with dual readout display. Dual thermocouple, one internal and one on a 3m extension lead. Free standing or double sided tape attachment.


Temperature range	-50 to +70°C
Power	1 x P009H battery
Dims.....	107 x 25 x 13mm

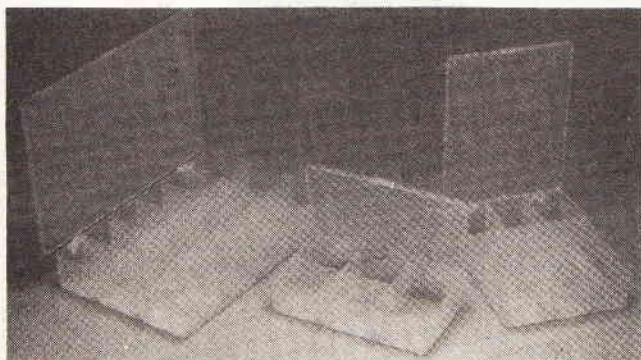

COMPARTMENT BOXES

A range of three strongly constructed polypropylene compartment storage boxes with hinged lids. Semi-transparent finish.

F662	180 x 97 x 43mm	5 compartments	£1.20	40+ 0.74
F662A	185 x 142 x 42mm	9 compartments	£1.60	40+ 1.03
F662B	275 x 180 x 42mm	18 compartments	£1.99	40+ 1.33

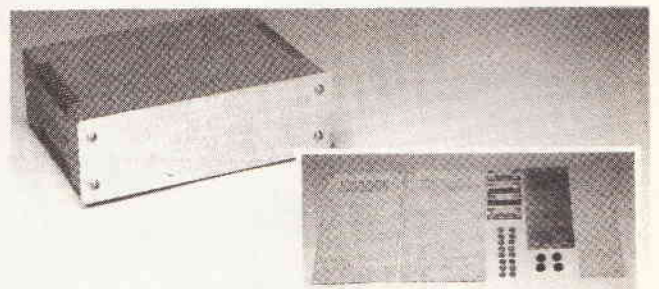


METAL CASES

A range of flat pack steel cases with aluminium front and rear panels. Rust proof finish, ready for painting.

Ref:	Size		
F660	80 x 46 x 85mm	£3.96	10+ 2.65
F660A	110 x 50 x 80mm	£4.78	10+ 3.20
F660B	140 x 56 x 110mm	£5.96	10+ 3.99
F660C	180 x 56 x 130mm	£7.90	10+ 5.29
F660D	230 x 56 x 190mm	£10.99	10+ 7.37

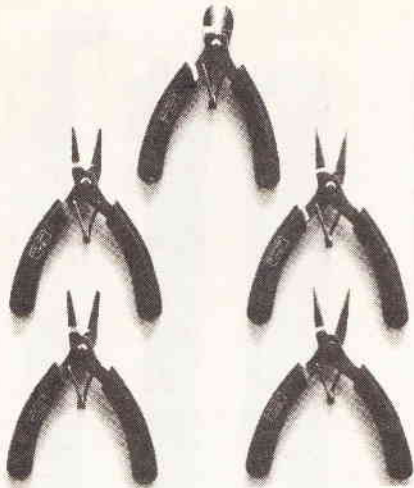PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT



Y030B **£12.95**
 5+ 8.01

PRECISION TOOL SET

5-piece precision, pressed stainless steel tool set with precision ground blades. The set comprises side cutters, bent nose pliers, round nose pliers, long nose pliers and flat nose pliers. Sprung, insulated handles. Length4" (100mm)



Y060S **£6.95** 10+ 4.42
PORTABLE SOLDERING IRON

Battery operated portable soldering iron. Powered by 4 'C' cells in the handle (not supplied). Tip heats up in seconds from operation of the biased off slide switch. Tip retracts into the body for safety. Supplied with one spare tip and 300mm of solder.

Power6Vdc (4 x C cells)
 Dims190 x 66 x 30mm



A150B **£6.95**
MINI VACUUM CLEANER 10+ 3.95

A battery powered mini vacuum cleaner which is ideal for removing the dust from turntables, cameras, video recorders, computer keyboards etc. 5 piece kit. Powered by four AA alkaline batteries (not supplied).

Power4 x AA alkaline batteries

Y006E **£6.95**
 10+ 4.29

PRECISION

PRECISION MAGNIFIER

Precision made magnifier with a fixed focus. The lens fits directly over a graduated scale for magnified measurement. Metric and imperial scales. All metal construction. Folds down for storage in the vinyl wallet provided.


Dims.....53 x 48 x 39 (in use)
47 x 39 x 14 (folded)



Y012C **£9.95**
 10+ 6.67

40-PIECE TOOL KIT

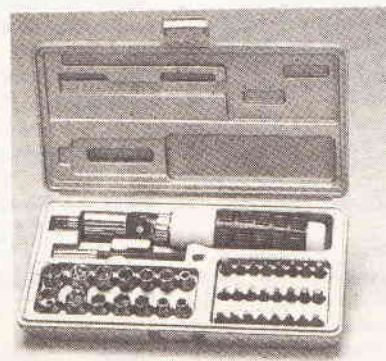A 40-piece tool kit comprising a ratchet driver handle with a lockable knuckle, 100mm extension bar, 7 torque driver tips, 8 hex key tips, 6 screwdriver tips, 2 square drive tips, 1 hex to square drive adaptor, 7 metric sockets and 7 imperial sockets in a hinged plastic case.



POCKET



Y006C **35p**
 100+ 0.19

PRISMATIC MAGNIFIER

Credit card size prismatic magnifier. All plastic.

Y006D **£7.95**
 10+ 5.29


GOOSENECK MAGNIFIER

2X magnification 3" diameter on a flexible 13" gooseneck with heavy base. Useful for close, precise work.

BENCH



Graphic Supplies by Staedler

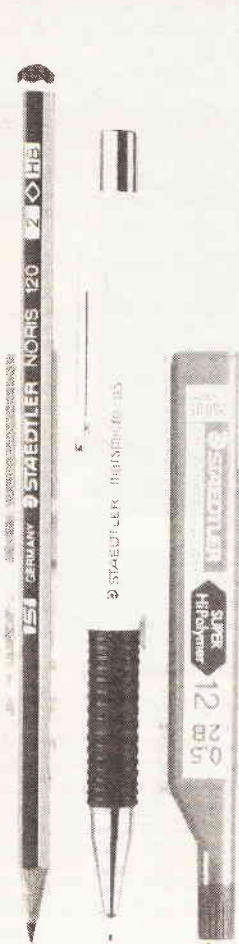

(a) Pencils

The Noris school and office pencil available in 5 colour coded degrees:

Code	Description	1-11	12+	144
S120-2B	2B Pencil	24p	0.17	0.14
S120-B	B Pencil	24p	0.17	0.14
S120-HB	HB Pencil	24p	0.17	0.14
S120-H	H Pencil	24p	0.17	0.14
S120-2H	2H Pencil	24p	0.17	0.14

(b) Propelling Pencils

Fineline propelling pencils. Available in 4 sizes for technical applications. Contoured slip-proof finger grip. Perfectly balanced for convenience and precision. Has 3mm retractable safety sleeve. Replaceable eraser with cleaning pin under push button.

Code	Description	1-9	10+	30+
S775-03	0.3mm lead	£2.75	1.95	1.56
S775-05	0.5mm lead	£2.75	1.95	1.56
S775-07	0.7mm lead	£2.75	1.95	1.56
S775-09	0.9mm lead	£2.75	1.95	1.56

Replacement leads. Fineline black leads with extraordinary point strength, slow wear and opacity. Supplied in tubes of 12.

Code	Description	1-9	10+	30+
S250-03	0.3mm HB lead	£1.70	1.20	0.97
S250-05	0.5mm HB lead	£1.05	0.74	0.60
S250-07	0.7mm HB lead	65p	0.46	0.37
S250-09	0.9mm HB lead	65p	0.46	0.37

(Available in different degrees of hardness to order)



(c) Lead Holders

The MARS Technico lead holder with sliding pocket clip. Lead sharpener built into the push button. For all 2mm leads.

Code	Description	1-9	10+	30+
S780CCA	Mars holder	£3.25	2.30	1.84

Lightweight plastic model for 2mm leads

Code	Description	1-9	10+	30+
S789OOC	Noris holder	£1.85	1.31	1.05

Lumograph 2mm leads for above holders, sold in boxes of 12:

Code	Description	1-5	6-11	12+
S2002B	2B leads	£3.85	2.72	2.18
S200B	B leads	£3.85	2.72	2.18
S200HB	HB leads	£3.85	2.72	2.18
S200H	H leads	£3.85	2.72	2.18
S2002H	2H leads	£3.85	2.72	2.18

(Other degrees from EB to 9H available to order)

Lumochrom Coloured 2mm drawing leads for use on paper or film. Pack of 12 assorted colours

S204S12	12 colours	£4.10	2.91	2.33
----------------	------------	--------------	------	------



(d) Ball point pens

Ventilated caps. Fine point.

Code	Description	1-9	10+	30+
S430F-9	Black	16p	0.11	0.09
S430F-2	Red	16p	0.11	0.09
S430F-5	Green	16p	0.11	0.09
S430F-3	Blue	16p	0.11	0.09

(e) Fibre Pens


Low cost fibre tipped pens - 0.8mm robust point, ventilated cap. Available in a range of colours:

Code	Description	1-9	10+	30+
S333-9	Black	25p	0.17	0.14
S333-2	Red	25p	0.17	0.14
S333-5	Green	25p	0.17	0.14
S333-3	Blue	25p	0.17	0.14
S333-1	Yellow	25p	0.17	0.14
S333-W1	Pack of 10 assorted colours	£2.50	1.70	1.40
S333-W2	Pack of 20 assorted colours	£5.00	3.40	2.80

(f) Graphic Liners

Pigment liner, multipurpose fibre tip pen. Fade proof black pigment ink. Excellent reproduction qualities. In 4 line widths:

Code	Description	1-9	10+	30+
S308-01	0.1mm liner	£1.45	1.02	0.82
S308-03	0.3mm liner	£1.45	1.02	0.82
S308-05	0.5mm liner	£1.45	1.02	0.82
S308-07	0.7mm liner	£1.45	1.02	0.82
S308WP4	Plastic wallet with one each of the above 4 pens	£5.80	4.11	3.29

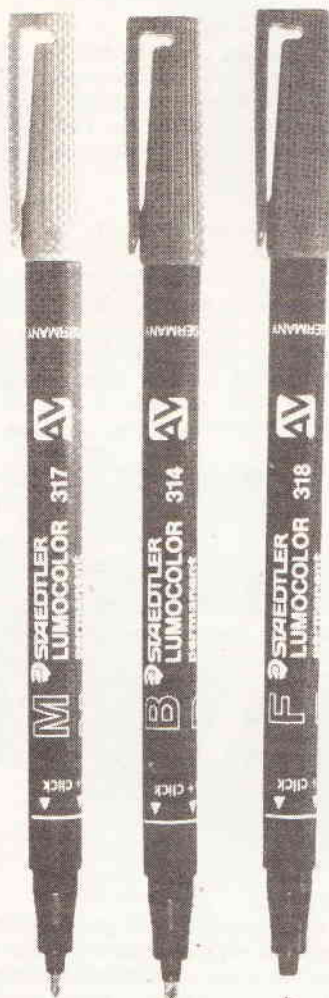

(g) AV Pens & Markers

A range of high quality Lumocolor markers with permanent waterproof ink that will write on all smooth surfaces. Fadeproof. Ideal for OHP - available in 8 colours. Ventilated caps.

Fine Points 0.4mm

Code	Description	1-9	10+	30+
S318-9	Black	72p	0.51	0.41
S318-2	Red	72p	0.51	0.41
S318-5	Green	72p	0.51	0.41
S318-3	Blue	72p	0.51	0.41
S318-W8	Pack of 8; one each black, red, green, blue, yellow, brown, orange and purple	£5.76	4.10	3.30

Medium Points 0.8-1mm

Code	Description	1-9	10+	30+
S317-9	Black	72p	0.51	0.41
S317-2	Red	72p	0.51	0.41
S317-5	Green	72p	0.51	0.41
S317-3	Blue	72p	0.51	0.41
S317-W8	Pack of 8; one of each as S318-W8	£5.76	4.10	3.30

Broad Points 1-2.5mm


Code	Description	1-9	10+	30+
S314-9	Black	£1.00	0.71	0.57
S314-2	Red	£1.00	0.71	0.57
S314-5	Green	£1.00	0.71	0.57
S314-3	Blue	£1.00	0.71	0.57
S314-W8	Pack of 8; one of each as S318-W8	£8.00	5.67	4.54



(h) Highlighters

In 3 popular colours. Universal pigment ink, lightfast for all types of paper including fax, telex and carbonless copy paper. Chisel point.

Code	Description	1-9	10+	30+
S364-1	Yellow	£1.10	0.77	0.62
S364-23	Pink	£1.10	0.77	0.62
S364-5	Green	£1.10	0.77	0.62

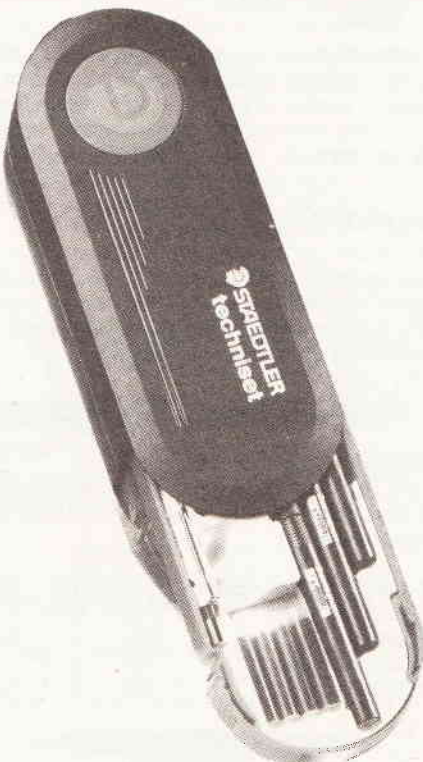

Marsmatic Techniset

S700C7 Compact desktop set with 2 slide out trays. Upper tray contains 3 Marsmatic 700 technical pens (0.25, 0.35, 0.5mm), 4 ink cartridges, an eraser, fineline pencil and tube of leads, and a compass attachment for technical pens. The lower tray is empty.

£29.30 5+ 20.79



Erasers


Code	Description	1-9	10+	30+
S526-B20	Rasoplast Soft white vinyl eraser 58x22x12mm	23p	0.16	0.13
S526BT30	Duoplast dual eraser. Removes ink and graphite	35p	0.25	0.20



S526-61 Razor eraser pencil with brush **75p** 0.53 0.42

Drawing Sets

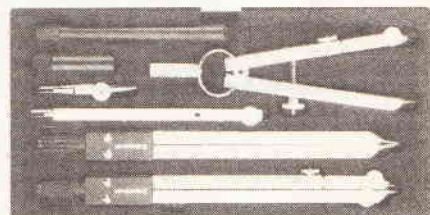High quality student compass sets. The Arco range is sturdy and robust, and incorporates features normally only found on more professional models.



S559-09 Arco drawing set - compass, dividers, extn bar, springbow and lead box. **£9.95** 5+ 6.66



S559-50 Low cost school compasses and lead box **£1.35** 10+ 0.96



Rolling Ruler

Versatile instrument for drawing parallel lines both vertically and horizontally; drawing angles, circles, curves and arcs. Comes with full instructions.

Code	Description	1-9	10+	30+
S962-31	6" model	£4.50	3.19	2.55
S962-30	12" model	£6.25	4.43	3.55



S569-22 Set of 45° and 60° set squares, 6" ruler and protractor **75p** 0.51 0.41




S971-12 Flexible Curve **£2.60** 1.92 1.63



S571-40 French curve set - set of 3 in plastic wallet **£3.75** 2.66 2.13


Drawing Boards

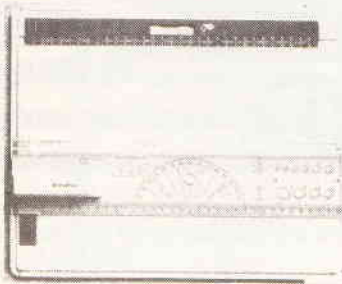Portable drawing boards suitable for student and technical draftsman alike. Advanced features make these quality products excellent value for money. They are made of especially break resistant plastic



S661A4 DIN A4 size has perimeter guide grooves, a recessed sheet clamp with locking key, paper alignment edges and reduction scales. Fixmatic drafting arm has 2 guide grooves for a drafting head. **£24.95** 5+ 14.18

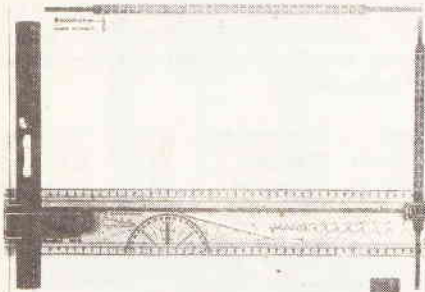
S661A3 DIN A3 size with fixmatic drafting arm **£34.95** 5+ 19.86




S660A3 DIN A3 Mars Technico drawing board with additional features as shown for the professional. **£46.50** 5+ 26.38

Accessories

All suitable for above boards

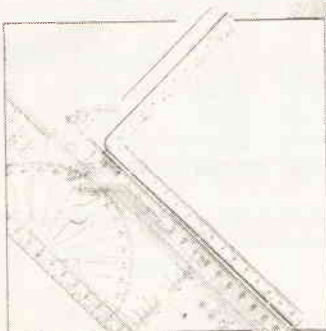

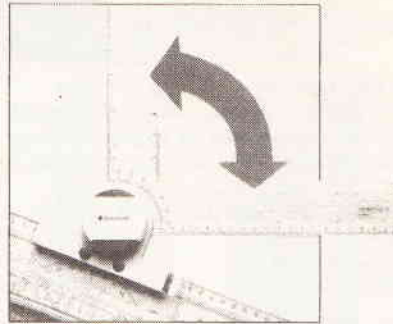S660-15 The quickmatic drafting head. Quickset angle can be set in the guide grooves and moved along the entire length of the drafting arm for hatching. Locks at 15° intervals. **£4.25** 5+ 3.62



S660-20 Variomatic drafting head - fits the guide grooves of the parallel drafting arm. It allows instant drawing of 90° angles, has opposing scales 0-90° and automatic locking at 15° intervals **£14.50** 5+ 8.23

Kuratake

A range of top quality supplies from a company established in 1902. Kuratake has been established in the UK for 5 years, providing graphic markers and equipment to education, industry and commerce.



Ceramic Rollerball Pen

The Zig ball 200 is a low cost high quality 0.3mm rollerball pen, available in 4 colours. Waterbased ink.

Code	Description	1+	12+	96+
KCB220K	Black	70p	0.43	0.34
KCB220R	Red	70p	0.43	0.34
KCB220G	Green	70p	0.43	0.34
KCB220B	Blue	70p	0.43	0.34



Textile Markers

Double ended pens to give a hard line (2mm) and a brush effect. Waterbased pigment ink exclusively for marking on cloth and fabric that once dry will not wash out. Available in a range of colours and packs as shown:

Code	Description	1+	12+	48+
KTC4000K	Black	£2.23	1.34	1.08
KTC4000R	Red	£2.23	1.34	1.08
KTC4000G	Green	£2.23	1.34	1.08
KTC4000B	Blue	£2.23	1.34	1.08
KTC4000Y	Yellow	£2.23	1.34	1.08
KTC4000A	Pack of 12 assorted colours: Black, Red, Green, Blue, Yellow, Brown, Orange, Violet, Grey, Pink, Light blue, Light Green.	£16.92	10.13	8.10



Gold & Silver Pen

Double ended pen 210mm long with valve action and fine tip - Gold one end, Silver the other. Instant drying, high opacity.

Code	Description	1+	12+	48+
KFMP20	Gold & Silver	£3.80	2.28	1.83




Whiteboard & Markers

A revolutionary new product - a flexible whiteboard! The Flexiwipe needs no fixing, just peel off backing sheet and smooth on to any non-absorbent surface. Easily removable for storage in tube supplied. Available in 3 sizes as shown:

Code	Description	1+	3+
FWA2P	A2 (594x420mm)	£27.23	15.73
FWA1P	A1 (840x594mm)	£55.46	31.15
FW2M	2m x 930mm	£126.12	70.85

Markers for above and other whiteboards. Alcohol based ink that simply wipes away when dry. Sold in packs of 4 bullet tipped markers - Black, Red, Green and Blue.

Code	Description	1+	12+	48+
KOMW35	Pack of 4 pens	£4.51	3.17	2.54

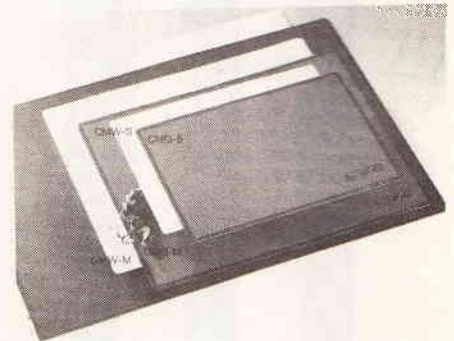

Cutting Mats

High quality double sided green cutting mats with high durability and elasticity. Self healing surface on both sides. Printed with a 2mm grid.


Code	Description	1+	12+
CMG/ES	220x300mm	£7.47	4.20
CMG/S	300x450mm	£14.95	8.40
CMG/M	450x600mm	£29.68	16.67



Changin' Glue

Instant adhesive for paper and card - on application the glue is blue, but dries clear. Non-toxic emulsion based. Can be used as permanent (stick while blue) or temporary (wait till clear - can be repositioned as required). Available in 2 sizes:

Code	Description	1+	12+	96+
KMSB15	10gm, 6mm tip	£1.69	1.02	0.81
KMSB30	25gm 15mm tip	£3.37	2.03	1.63

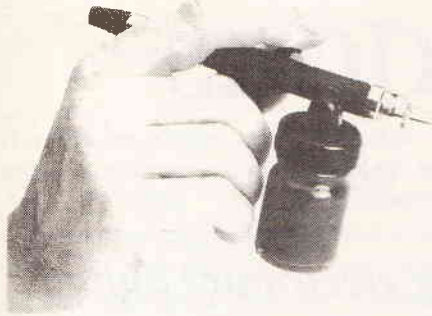

Airbrushes

The Humbrol range of airbrushes and spray guns is designed to offer both modellers and graphic artists an inexpensive introduction to this medium.



H30003 Modellers airbrush designed to give a cost effective method of applying paint. Features include adjustable air jet pattern, air volume and paint flow volume adjustments. The set includes an aerosol power pack and three additional storage jars. **£19.95** 3+ 13.58



H30006 Hobbicraft airbrush set. This offers greater precision and finer atomisation than the above model. It features a dual action control trigger, controlling both paint volume and airflow, with an additional air supply volume control for attachment to aerosol power packs. Included in this set are an aerosol power pack and three spare storage jars. **£46.50** 3+ 31.66

Aerosol Power Packs

H30201 Standard size **£2.95** 12+ 2.00
H30202 Large size **£4.99** 12+ 3.40



OHP Film

Clear acetate film for overhead projection, also ideal for PCB layouts. Available in A4 size only, 0.1mm thick. Supplied in packs of 10 sheets

Code	Description	1-9	10+	30
S632-1021		£1.60	1.06	0.71

Other Stationary Products

(a) Paper & Labels


80gsm high grade copier paper, sold in reams (500 sheets)

Code	Description	1+	10+
A701	A3 size 420x297mm	£9.95	5.73
A702	A4 size 297x210mm	£3.70	2.31

Laser Copier Paper

A high quality paper giving excellent results with all laser printers. Price per ream.

A703	A4 size 297x210mm	£4.50	3.30
-------------	-------------------	--------------	------

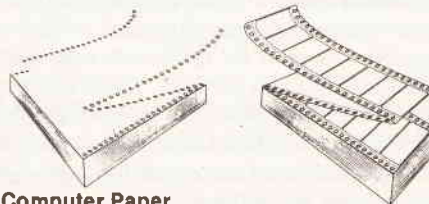

Computer Paper

A458 Computer Listing Paper 11x9 1/2" plain, 60gsm wood free, microperf. Sold in cases of 2000 sheets. **£15.00** 11.06

CL01 Continuous labels 3 1/2 x 1.7/16". One label across sheet. Vertical spacing 0.2" **Pack of 1000 £6.95**; 8000 32.00+VAT

CL02 Continuous labels 4x1.7/16". Three labels across sheet. Vertical spacing 0.2" **Pack of 1000 £6.95**; 12000 51.00+VAT



3M Post-it notes.

The original removable self-stick notes, available in 3 sizes:

Code	Description	1+	12+	144+
S16	1 1/2 x 2"	36p	0.28	0.23
S17	3 x 3"	75p	0.59	0.48
S18	5 x 3"	110p	0.88	0.70




(b) Envelopes

White DL, size 220x110mm (takes A4 folded in 3) Self-seal. Sold in packs of 100

Code	Description	1+	10+
A711	80gsm opaqued, plain	£2.00	1.15
A712	80gsm opaqued, window	£2.20	1.29

Brown C4, size 325x230mm (takes A4 unfolded). Sold in packs of 100

Code	Description	1+	10+
A716	80gsm gummed	£4.20	2.27
A717	80gsm self seal	£4.60	3.09

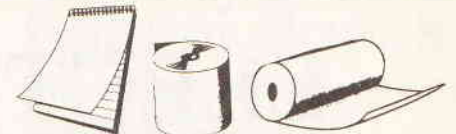

(c) Pads and Rolls

A721 Shorthand notepad, spiral bound 8x5". 80 sheets (160 pages)

1+ 40p; 12+ 0.22; 144+ 0.18

A725 Adding machine rolls. Standard 2 1/4 x 2 1/4". Sold in cases of 20 rolls.

1+ £4.75; 5+ 3.36 25+ 2.68

A721 Fax Roll. Standard for most makes of machine. 210mm wide x 30m long (equivalent to 100 A4 sheets) 12.5mm tube. **Reduced Price:**

£2.95; 12+ 1.80; 72+ 1.68.



Stapler and Staples

R2 Office 26/6 metal stapler in black. **£4.50**; 10+ 3.43

R3 Office 26/6 staples in boxes of 5000 **75p**; 10+ 0.56



Paper Clips

R4 Large lipped in boxes of 1000 **1 box £1.50**; 10+ 0.86

Tippex

S7 The popular white opaquing fluid in 30ml bottles. **83p**; 10+ 0.58

A4 Transparent Pockets

Open at the top and multipunched to fit most files.

Pack of 100 £4.40; 10+ 2.81



Adhesive Tape

A731 1" wide clear adhesive tape, polypropylene 30 micron **60p**; 12+ 0.36; 72+ 0.29

A735 2" wide buff packaging tape, polypropylene 30 micron. **£1.30**; 12+ 0.83; 36+ 0.66



Ballpoint Pens

Low cost ball pens with ventilated caps, in 3 popular colours:

Code	Description	10 for £1	100+ 0.06
HPE01	Black	10 for £1	100+ 0.06
HPE02	Blue	10 for £1	100+ 0.06
HPE03	Red	10 for £1	100+ 0.06
HPE50	Box of 50, any assortment		£3.95

ELECTRONICS BOOKS

Reference Tools written for you!

Three books from a well-known and best-selling electronics author!

The Laser Cookbook Gordon McComb

A hands-on introduction to laser theory and operation, with over 80 practical and easy-to-follow projects. These projects range from simple acoustic modulation of laser beam to super-accurate interferometers that precisely measure the speed of light, light wave-lengths, and light frequencies. Readers wanting to increase their knowledge of this subject should look no further than "The Laser Cookbook". *"...provides a fascinating tour through the world of lasers. It is well written, amply illustrated, and lots of fun."*

(Modern Electronics)

404 pages Size 190 x 235mm
ISBN: 0830693904 £18.15 (SC)

The Robot Builders Bonanza Gordon McComb

A collection of almost 100 tried and tested project modules that can be mixed and matched to create a range of intelligent and workable robot creatures. Clearly illustrated and fun to use, this is a must for electronics enthusiasts interested in the area of robots. The 99 different robot components described in this ingenious guide can be combined in an almost endless variety of intelligent and workable robots of all shapes, sizes, and abilities.

326 pages Size 190 x 235mm
ISBN: 0830628002 £14.45 (SC)

Compact Disc Player Maintenance and Repair Manual Gordon McComb

Specific guidelines for maintaining and repairing more than 100 brands of CD players. Packed with quick and reliable answers to the problems of maintaining and repairing CD players, this illustrated do-it-yourself guide takes the apprehension out of first-time repairs. *"A valuable accompaniment to a CD purchase...should be in the reference library of anyone who owns or is planning to own a CD player."*

(Midwest Book Review)

244 pages Size 190 x 235mm
ISBN: 0830627901 £11.95 (SC)

The Complete Shortwave Listener's Handbook, 3rd edition Bennett

The bible of shortwave for over a decade, revised and updated for today's electronics market. It has been expanded to include all the very latest equipment, procedures, and operating practices. This book will be a useful reference for all those interested in shortwave radio. All the basics of SWL are covered - receivers, antennas, frequencies, radio-wave propagation, how to keep a logbook, and prepare and send reception reports. *"...a comprehensive guide to the basics of shortwave listening."*

(New Technical Books)

294 pages Size 130 x 210mm
ISBN: 0830626557 £13.55 (SC)

Designing, Building and Testing Your Own Speaker System Weems

For those who would like to be able to build a durable, low-cost speaker system that is as good as or better than the most expensive units on the market, now they can, with this completely revised edition of David Weem's best-selling book. There is no better source of clear, step-by-step construction techniques and project plans than Designing, Building and Testing Your Own Speaker System.

224 pages Size 190 x 235mm
ISBN: 083063374X £14.95 (SC)

Solid-State Electronics Theory with Experiments Sanfilippo

Pragmatic rather than mathematic in approach, this book is a comprehensive introduction to solid-state technology. There are a number of interesting projects at the end of each chapter which reinforce concepts and allow readers to experiment with the solid-state applications described in the text by actually building circuits. Careful attention is given to how to test solid-state devices and how to design circuits using them.

330 pages Size 130 x 210mm
ISBN: 0830629262 £16.30 (SC)

How to Build a Small Budget Recording Studio from Scratch - 2nd edition Everest

This is an excellent book about small studios: how to build them and treat them acoustically, with emphasis on budget studios suited to the efficient day-to-day production of radio, audio-visual, film, and television recording. No special skills or training are required to use this book - it is of interest to anyone planning to build or remodel a small recording studio. The author has been involved with TV broadcasting since 1936.

295 pages Size 190 x 235mm
ISBN: 0830629661 £14.45 (SC)



**The Encyclopedia of Electronic
Circuits - Volumes 1 - 3
Graf**

This fully comprehensive best-selling series includes coverage of all aspects of the electronics world. There are fascinating insights into schematics for the latest available alarm and security circuits; smoke, moisture and metal detectors; computer, fiber optic and laser circuits; and hundreds of other areas.

Size 190 x 235mm
 Volume 1 - 0830619380 £28.15 (SC) 760 pages
 Volume 2 - 0830631380 £28.15 (SC) 732 pages
 Volume 3 - 0830633480 £26.95 (SC) 837 pages

**The GIANT Book of Easy-to-Build
Electronic Projects
Editor of Elementary Electronics**

Here's a giant collection of useful, low-cost electronic projects for both the beginner and experienced hobbyist. Ranging from simple circuits to state-of-the-art electronic gadgets, there are dozens of fascinating projects that simply aren't available elsewhere. There are construction and assembly details, and printed circuit board templates reproduced in actual size

352 pages Size 190 x 235mm
 ISBN: 0830601996 £19.95 (HC)

**Homemade Holograms: The Complete
Guide to Inexpensive,
Do-It-Yourself Holography
John Iovine**

This is an ideal 'first-step' into the fascinating world of holograms. The author describes new procedures - using equipment readers can make themselves - that take the complexity out of producing simple white-light reflection and transmission holograms of people, as well as computer graphics, and solid objects.

230 pages Size 190 x 235mm
 ISBN: 0830634606 £11.95 (SC)

**500 Electronic IC Circuits with
Practical Applications
Whitson**

Comprehensive and detailed coverage of 500 electronic IC circuits. Electronics enthusiasts will value the easy-to-follow practical circuit applications and will learn from the basic theory behind each one. A handy tool for anyone working with IC circuits.

340 pages Size 190 x 235mm
 ISBN: 0830629203 £19.05 (SC)

**The Illustrated Dictionary of
Electronics - 5th Edition
Turner**

Featuring more than 27,000 entries, an exhaustive list of abbreviations, and appendices packed with schematic symbols and conversion tables, this is by far *the* most comprehensive dictionary of practical electronics and computer terms available today.

723 pages Size 190 x 235mm
 ISBN: 0830633456 £23.95 (SC)

**The Thyristor Book - With 49 Projects
Delton Horn**

With this new collection of 49 projects, the author simply and clearly demystifies these useful components. He explains in simple terms thyristor construction and operation and uses dozens of designs to illustrate the many practical application of thyristors.

205 pages Size 190 x 235mm
 ISBN: 0830633073 £16.95 (SC)

**Physics for Kids: 49 Easy Experiments
with Electricity and Magnetism
Robert Wood**

An outstanding guide for young scientists to the phenomena of electricity and magnetism. There are exciting experiments such as: tracing a magnetic field with a bar magnet, tracing lines of force with a compass, making a battery, making a motor, and many more.

125 pages Size 190 x 235mm
 ISBN: 0830634126 £9.95 (SC)


**Homemade Lightning:
Classical Experiments in Electrostatics
R A Ford**

The electronics enthusiast's guide to designing, building, and using classic high-voltage generators and associated equipment. There is a fascinating collection of experiments that reveal the wide-ranging impact of electrostatics on such topics as motor design, aerodynamics, gravity, photography, and meteorology.

194 pages Size 190 x 235mm
 ISBN: 0830635796 £11.95 (SC)


Babani Books

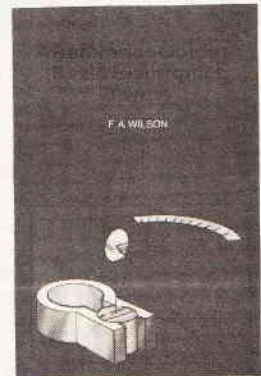2 new titles from this popular publisher:



**A REFERENCE GUIDE TO BASIC
ELECTRONIC TERMS
BP286
£5.95 F.A.WILSON**

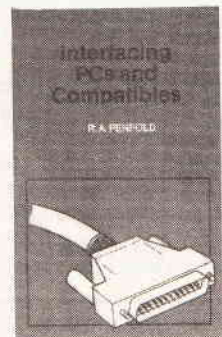Over 700 fundamental terms explained in depth and backed up by a list of other relevant entries. Published in the popular larger format, this useful tome should be on every enthusiasts bookshelf.
 0 85934 231 X 1992 198x135mm
 480 pages




**INTERFACING PC's AND COMPATIBLES
BP272
£3.95 R.A.PENFOLD**

Utilizing the expansion slots for do-it-yourself projects is quite straightforward, and this book gives you detailed descriptions of the relevant parts of the PC. There are practical circuits for a number of projects including address decoder, simple TTL 8 bit input and output ports, 8255 PIA, D-A and A-D converter circuits etc. In fact, all you need in order to produce successful PC add-ons.
 0 85934 217 4 1992 178x111mm
 120 pages

If you like what you see in this supplement make sure you don't miss future bargains - only £2 (UK/BFPO; £4 O'seas) for the next 6 issues - see order form for details.

16 SPRING SUPPLEMENT

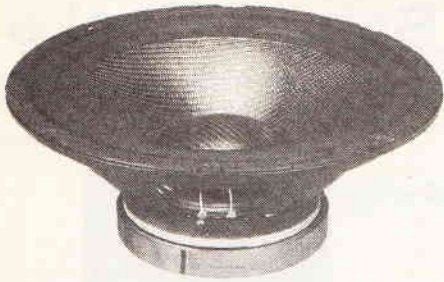

LS037B - Great offer on 12" bass speaker! High efficiency woofer with rubber surround - will handle 150W music power. Freq. response 20-3500Hz. Magnet weight 100oz, Overall weight 4.4kg. 8R impedance. Normally cost over £60 - **Our Offer Price £75 per pair**



F217G Metal stereo combination plug assembly. 3.5mm plug with metal spring outlet with adaptor to give 6.35mm plug. Assembly screws together to give compact solid unit. Would normally sell for over £1.00 each - **Our Low Price 2 for £1.00**; 100+ 0.25

FANTASY DECO ROPE

FDR1 9 meter long tube with 120 lights and special effects controller and power supply. Uses cool and long lasting LED's. 8 different programs on controller - chasing back and forwards at various rates. **£49.95**

SUPER HEADPHONE DEAL!

HB Excellent quality Adastra stereo headphones with boom microphone. Freq. response 20-20,000Hz, 32R impedance. Microphone 600R. 2m leads fitted with 3.5mm plug for mic, and 3.5mm plug + adaptor for headphones. Padded earpieces and leatherette headband. **ONLY £9.95**

QUICKSHOT MOUSE

High quality optomechanical mouse by Bondwell

- * Microsoft compatible
- * IBM PC XT or AT compatible
- * Hardware selectable mouse standard
- * Programmable resolution 29-1450 DPI
- * High tracking speed 500 mm/s
- * Silicone rubber coated tracking ball

Includes


- * Universal mouse driver
- * Performance Test Programme
- * D9-D25 connector adaptor

ORDER CODE QS158
PRICE £24.95 6+ 16.10



TRICOLOUR LED BARGAIN

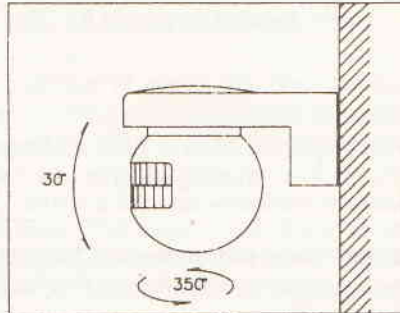F166T Chrome holder needs 10mm hole. LED has 3 leads - common, red and green, when used together produce yellow. These normally sell for around 80p each - **Our special offer price 4 for £1.00**; 100+ 0.12; 1000+ 0.09



SECURITY SENSOR

BPW1 Outdoor light control motion sensor. This automatic sensor is powered from the mains and will handle up to 1000watts. It has 110° elliptical view field, 9 meters on each side and 12m forward. Automatic turn on and off of lights.

Features:

- Security - instantly reacts to intruders by turning light on
- Sensing motion, turns on/off lights automatically in daylight
- Adjustable light sensitivity and shut off time

Manual override
Easy installation

For both incandescent and fluorescent lights.

Ideal for outdoor areas:

- Front or back porch
- Deck or patio
- Secluded walkway
- Garage and driveway
- Cluttered areas

The globe shape makes adjustment exceptionally simple - just rotate to direction and angle required.. Overall size 110mmx100x75mm.

Price: £29.95 5+ 21.30


D90 TDK low noise high output cassette tape, normal bias **£1.20 10+ 0.80**

Goods sent in error

We have received a batch of leads which are not normally stocked - so we'd like to clear them at a Bargain Price!

Z5273 AV lead - 4 pin mini DIN plug both ends. 2m long **£1.95**

MULTIBAND RADIOS!

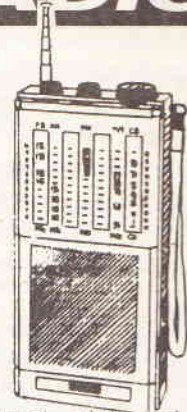


This compact piece of equipment 200x95x50mm comes in an attractive metallic grey case with controls on top - timing, on/off and volume, squelch. The telescopic aerial extends to 500mm and can be rotated in any direction. The 3 wavebands are:

- 1) CB, channels, 1-80
- 2) TV1 54-87 MHz & FM 88-108 MHz
- 3) AIR 108-145 MHz & PB 145-176 MHz.

The large 3" full range speaker delivers 280mW of undistorted power. There is an earphone jack and DC adaptor jack. The unit is powered by 4x AA cells. All this technology for just **£17.95**


Order Code

MB100

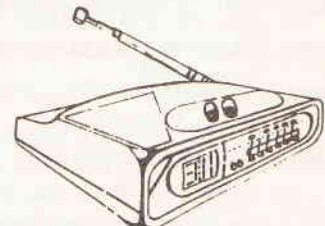

Z4357 Clock Radio by Ross. Extremely neat unit measuring 140x80x35mm. MW/FM bands, telescopic aerial, stand, carrying pouch and strap. Clock has LCD display and can be used in 12 or 24 hr mode. Alarm. Light. Earphone socket. Takes 2x AA cells.

Great value at £13.95

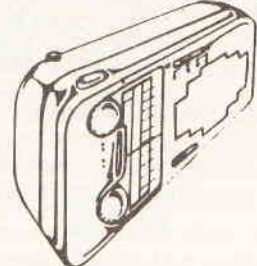

Z8891 Superb 4 waveband radio by Ross, model RR5. Covers FM 88-108MHz, MW 518-1610kHz, LW 150-275kHz SW 5.7-18.1MHz (16.5-52.6m). Nicely styled case measuring 210x145x70mm with clear scale markings. Telescopic aerial, headphone socket. Volume, tone and tuning controls. ON/OFF switch/waveband selector switch and AFC switch. Mains/battery. (Takes 4x C cells). Originally retailed at £19.95

Our Price £14.95

BARGAIN LIST 78

March 1992

Greenweld Electronics Ltd
 27 Park Road
 Southampton
 SO1 3TB

Tel (0703) 236363
 Fax (0703) 236307

The next few pages feature goods that have arrived recently - some are available only in small quantities, so don't delay, order today!!

Changes to Bargain Lists.

We're making a few improvements to our Bargain Lists to make them even more interesting reading!

Quite soon, you'll find included a few circuit ideas for the surplus parts we sell - maybe even a complete project or two. We know our customers' range of knowledge, ability and interests is extremely varied - from the novice who has problems identifying a resistor to eminently qualified experts engaged in design and research of leading edge technology - so we'll try and include a wide variety of ideas. Contributions are welcome, and any published will be paid for.

We're aware that some of our surplus comes without any information, and that this can be very frustrating, but the cost reflects this - the quantities involved are usually too small to justify chasing data. In future, those items that do include data will have a 'D' suffix to the Z number: i.e. **Z8963D**. If the info runs to several pages, there will be a separate charge quoted.

Data can be supplied separately at 20p per item + SAE if not ordering any goods

SWITCHES

The parts listed below have come from a manufacturer of aids for the physically handicapped. There's a lot more hardware to sort out, but below is a selection from this parcel. As you would expect, there are quite a few switches and relays:

(a) Microswitches

Z2486 Burgess type V12K 41x14x18mm, short lever SPCO, probably 15A rating. **2 for £1.00.**

Z2487 Honeywell heavy duty with brass screw terminals and brass threaded plunger. SPCO rated 15A 380V ac. **£1.50**

Z2488 Std 5A microswitch with roller lever on steel bracket with steel plunger. **£1.20**

Z2489 Std 5A microswitch with plastic assembly enabling operation by blowing down tube. **£1.50**

Z2490 2 std 5A microswitches on plastic bracket with lever arrangement. Operate each switch by blowing or sucking. **£3.50**

(b) Other Switches

Z2491 Single pole heavy duty push switch with screw terminals made by Burgess, type KB5-A2 **2 for £1.00; 100+ 0.30**

Z2492 The above switch mounted in a plastic box 49x54x18mm with plunger assembly **£1.60**

Z2493 Very large light action rocker switch, SPCO. Lever is 43mm square. Clip fix mounting. **£2.00**

Z2494 Ceiling switch with pull cord DP on/off rated 30A 250V ac. Red bezel, but no neon fitted. **£2.50**

Z5258 Air operated indicator(?) Plastic box 83x40x34mm with rocker type top. 2m length of twin tubing - and by blowing or sucking the rocker moves. **£2.50**

Z5259 Twin version of above **£3.50**

Z5260 AEG LS07 contactor rated 600V 16A. 4 pole and subsidiary circuit **£3.50.**

Z2495 Small suppressor 28mm long x 12mm dia by LCR. Rated 250V ac **2 for £1.00**

Z2498 Unimax high quality illuminated push switch, DP contacts. Needs 16mm dia fixing hole and takes wedge lamps. Available with green (**Z2498G**), orange (**Z2498R**) or black (**Z2498B**) bezel. **£1.00**

Z8970 Lift control panel. Self contained metal box 265x90x60mm with fascia plate 292x100mm and 5 heavy duty double pole push switches fitted with 12V MBC lamps inside. **£15.00**

Z2387 PC mounting push switch - 1 pr make and 1 pr break contacts. Right angle plunger is 5mm long x 2mm dia. With protective cover. Again, very high quality. **2 for £1.00**

Z2499 Neat limit switch with lever and microswitch action, 1 pr make and 1 pr break contacts. 18.5 x 10 x 7.8mm. Lever is 30mm long. **4 for £1.00** 100+ 0.14 1000+ 0.10

Z2485 PCB mntg keyboard click switch, low profile, only 3.8mm thick. 10mm sq. SP make. **12 for £1; 100+ 0.04**

K591 Pack of 25 miniature toggle switches from page 125 of the 1991 catalogue **£4.00**

K592 Pack of 25 miniature rocker and lever switches from page 125 of the 1991 catalogue **£4.00**

K593 Pack of 25 push and slide switches from page 125 of the 1991 catalogue **£3.50**

FUSES

Thermal Fuse Offer

A job lot of thermal fuses allows us to offer these at much less than our normal selling price (60p each). Available in the following values:

Z2525 104°C short leads - 12.5mm long. **5 for £1.00** 100+ 0.10

Z2526 109°C full length leads. **3 for £1.00;** 100+ 0.15

Z2527 121°C one lead cut to 17mm. **4 for £1.00;** 100+ 0.12

Z2528 152°C full length leads **3 for £1.00;** 100+ 0.15

K834 Pack of 20 assorted thermal fuses (4 values), some with cropped leads. **£2.95**

Thermal circuit breakers. Voltage rating 32V dc, 250V ac. Right angle PCB mounting with manual off/reset button and aux contact. Size 20x6x10. DP 4.33

Z5191 2A rating **£1.00** 100+ 0.40

Z5192 3A rating **£1.00** 100+ 0.40

Z439 Wire ended fuse. 20mm 1.5A antisurge. **Pack of 20 £1.00**

Z2440 Miniature circuit breaker (MCB) rated 250V ac 1.5A. Size 51x40x19mm. Made by Heinemann. **Only £2.00**

Z2444 Protector 14A. This surge arrestor made by Beswick is designed to protect equipment from voltage surges. DP 5.27. Our prices: **£1.00 each,** 100+ 0.60, 1k+ 0.40

Z8962 8 way industrial fusebank, 32A 415V ac. Totally shrouded incoming terminal will accept conductors up to 120mm². DP(1987) 30.55. **Our clearance price £10.00**

HARDWARE

More Hardware - seems to be very popular, especially the smaller sizes for modelmakers. However, most of this lot is a bit on the large side - you don't really need M16 nuts to hold bit of veroboard in a case!!

K830 M8 screws/bolts. Good assortment from 16-90mm long c/s, hex, pozi, some hi-tensile. All steel! **Pack of 50 £3.80.**

K831 M10 Bolts - mostly high tensile hex head, lengths from 16-90mm. **Pack of 20 £3.20**

K832 M12 Bolts-mostly high tensile hex head, lengths from 40-150mm. **Pack of 10 £2.40**

K833 M6 pack. Excellent value - contains screws in various lengths and head. Mostly steel, some hi-tensile. **Pack of 100 £4.50**

K553 2BA screws - c/s, cheese, hex, pan heads, slot and pozi in lengths from 7-63mm. **Pack of 100 £2.60.**

Z7001 M16 Full nut-you really shouldn't be with out some of these! **Pack of 12 £1.00.**

Z7002 Threaded hoop overall length 490mm. Ends are threaded. M10 to a length of 75mm. They are 125 mm apart. **Pack of 3 for £1.00**

Z7003 M18 nut and hex bolt 30mm long. **3 pairs £1.00**

Z7004 M10 Masonry anchor. Drill 12.5 mm hole 40mm deep and insert. Use M10 screw to force anchor into brickwork. **Pack of 8 £1.00**

Z7005 Screw and nut pack- 1/4" Whit: 25 each of 38mm C/S, 25mm C/S, 63mm (threaded 14mm) hex bolts and 25 mm (threaded 14mm) hex bolts +100 steel nuts. **Pack of 200 parts £5.00**

Z7006 Supertwin tufscrow, 8x1.25" combination pozi/straight pan head. Zinc plated. Great as woodscrews. **Boxes of 250 £3.00**

Z7007 M3 x 50 mm csk pozi steel screws. **Boxes of 250 £4.00**

Z9029 M4 x 50mm pan head pozi steel screws **50/£1.00; box of 200 £3.00**

Z9030 M6 x 50mm csk slot steel screws **16/£1.00; box of 100 £3.00**

Z9031 M8 x 60mm (23mm threaded hex head steel bolt **8/£1.00; box of 200 £12.00**

Z9032 M10 x 35mm hex head bolt HT steel **8/£1.00; box of 100 £6.00**

Z9033 M10 x 90mm hex head bolt HT steel **4/£1.00; box of 100 £12.00**

Z2373 M16 Full nuts, steel - **pack of 6 £1.00**

Z2374 M16 Half nuts, steel - **pack of 8 £1.00**

Z2371 5/16"x1" UNC hex head bolts. **A pack of 10 costs £1.00**

Z2372 3/8 x 1.25" set screws, hex head, **pack of 6 for £1.00**

Z2365 M6x16 Hex head set screws, pack of 25 for £1. **Box of 200 is £4.00**

Z2366 M6x1/4 as above. **Pack of 50 for £1.00**

Z2367 5/8" UNC half nut, **pack of 10 £1.00**

Z2368 5/8" UNC thin nut, **pack of 20 £1.50**

Z2369 1/4"x1.5" UNF hex head high tensile steel screws, **Pack of 25 for £1.50.** Box of 200, £8.50

Z2370 1/2"x1/2" as above, **pack of 10 for £2 or a box of 50 for £8**

K552 4BA Screw mix **200 £2.75**

K812 M6 Screw mix **100 for £2.50**

K596 Pack of 200 assorted nuts, believed to be all BA, from 2BA to 8BA. Mostly steel. **£2.40**

K595 Big mix of screws - very few BA, mostly metric, BSF, Whitworth, DZU etc. Tremendous variety of heads - cheese, cs, pan, hex, allan, round etc, etc. As for size, well we've seen some as small as 3mm and a few as long as 80mm. There's even some 12.5mm dia in this pack! You'll probably also find a few odd clips, washers, nuts etc, too. **500gm pack £2.70**

K812 Pack of 100 assorted rivets **£1.80**

K813 Pack of 100 self tapping screws, sizes 4-8, lengths to 20mm most with pozi head **£1.50**

Z2378 T03 Silicone impregnated insulated washers. **Pack of 25, £1.00**

Z5175 High quality heavy duty ball type castor 63mm dia, chromed steel with brass insert with 9.3mm threaded insert. DP 6.25 **Our price £4.00**

Z5176 Smaller brown ball type castor 50mm dia made by Kenrick. Steel insert with 8mm threaded insert. DP 3.15 **Our price £2.50**

Z2429 Black plastic foot 19mm dia x 5mm thick with 4.5mm dia hole. **Pack of 20 £1.00** 100+ .03

Z2375 High quality Sifam 1/4" collet knob S150, 15.5 dia x 14 high black knob, cap, and nut cover. **Pack of 10 of each £4.20**

Z5269 Olivetti cartridge ribbon - correctable carbon type 16.5mm wide x 120mm long, lexicart 90/92 Type No. 568N **£1.00 each**

Z5270 Black nylon ribbon type NCR 499 12.4 mm wide by Caribonum. Box of 4 **£2.00**

Z2502 Olivetti Summa Add ribbon. Twin spools, black **£1.00.**

Z23154 Nylon printer ribbon type N465, ref KSR430. Boxed. **£1.50**

NEWSLINE weekly update on new stock. Call 0891 505121 (48p per min. peak 34p off peak)

Z2437 Nylon stand off 2.5mm high. OD 5.8mm ID 3.2mm. **Pack of 1000 £3.00**

Z2438 White plastic oblong stand off (for 7 seg LED's) 19.5x10.2x12.2mm high. **Pack of 100 £2.00**

Z5261 Orange ABS case by boss, type 2002. 100x50x25mm. Threaded brass inserts and PC slots. 2 BIMdaptors included. DP 1.56. **Our price 80p**

Z9028 Strong compression spring 125mm long x 31mm dia. **£1.00**

Z2431 Compression spring 62mm long x 12 mm dia. **Pack of 6 £1.00**

Z5177 Self adhesive grey cable clip 38mm long. Will take up to 6mm dia cable. DP 3.48. **Pack of 20 £1.00** 10+ packs 0.60

Z2391 Cable gland in black nylon for 8-13mm dia cable. **Pack of 5 £1.50**

Z2392 As above best for 7-10.5mm cable. **Pack of 5 (DP 2.22) £1.20**

Z5152 Plastic Bits. 100 assorted stand offs etc. **£1.00**

Z635 Digital multimeter case DP2010, 110x80x20mm with cut outs for switches and terminals. Aluminium fascia plate. **2 for £1.00**


Z343 Ceramic insulating beads. **Pack of 100 £1.00**

Z1669 Veropins, wirewrap 18-0226. **Pack of 500 £2.00**

Z2443 TO3 heatsink - bolts on top of transistor using same fixing screws. Diecast ally 25x41x27mm. 7.3°C/W.DP 1.93. **Our price 75p**

Z2381 Small heatsink, 25 x 7 x 6mm, for sticking on top of DIL IC's. **Pack of 5 £1.00**

INSTRUMENT CASE

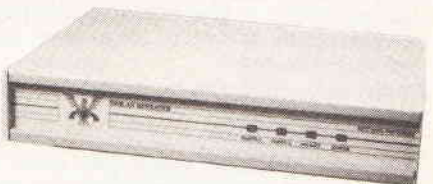

Z8969 Superb heavy duty steel instrument case finished in light grey 426x290x78mm with 4 plastic screw on feet. This was an Isolan repeater for use on a data network, and although the contents have been removed (before being used), the front and back panel remain, the former having 4 oblong red LED's and the latter a fused, suppressed IEC mains inlet, on/off DP rocker switch and 2 x 15 way D sockets joined to 16 way IDC skts with a short length of ribbon cable. There's a 60mm circular cut-out for a speaker on one side and mounting pillars in the base. Just look around and see the price this type of high quality case normally costs! - somewhere around the £30-£40 mark - then compare it to our low, low price - **just £9.95**

SEMICONDUCTORS

MICROPROCESSOR CHIPS

P8035AHL Intel 8 bit CPU, 11MHz **Our Price £3.00**

8051AH Phillips 8 bit CPU **Our Price £1.00**

M80C31F OKI 8 bit CPU 16MHz **Our Price £2.00**

N8097-90 Intel 16 bit H-MOS CPU 12MHz PLCC 68 pin. DP 13.86. **Our Price £6.00**

R80C186-12 Intel 16 bit CMOS CPU. 12MHz clock. PLCC 64 pin. DP 28.37 **Our Price £12.00**

CP82C59A CMOS programmable interrupt controller. DP 3.00 **Our Price £1.50**

P8256AH UART. DP 7.00 **Our Price £2.50**

Z2507 L4962 1.5A switching regulator, 16DIL. 5.1-40V. DP 2.50 **Our Price £1.50**

Z2513 L4960 2.5A switching regulator, 7 pin TO220. 5.1-40V. DP 2.64 **Our Price £1.80**

Z2508 LF13331 quad SPST J-FET analogue switch. 16DIL. DP 7.58 **Our Price £3.00**

Z2509 OPA27 low noise precision op-amp 8DIL. DP 1.86 **Our Price £1.00**

Z2510 SL670C gain controlled pre-amp. 8DIL DP 2.31 **Our Price £1.50**

Z2511 TCA785 16DIL chip by Siemens **£1.50**

Z2512 LF398N sample and hold amp 8DIL. DP 2.64 **Our Price £1.50**

Z2514 ZTX751 PNP TO92 transistor rated 80V, 2A, 1W. DP 0.48 **Our Price 5 for £1.00**; 100+ 0.14; 1k+ 0.10

Z2524 2N3703 PNP TO92 transistor rated 50V 0.2A 360mW. Our normal price is 12p. Surplus stock offered at **15 for £1.00**; 100+ 0.04; 1k+ 0.025

Few SGS Chips:

Z2481 M491BB1 List 11.10. **Our price £4.50**

Z2482 M293B1 List 7.40. **Our price £3.00 and an ITT chip:**

Z2483 SAA1293-02 List 7.64. **Our price £3.00**

Z2484 2N3903 TO92 transistor. **12 for £1.00**; 100+ 0.04

Z2112 Ceramic filter 5.5MHz by Murata. **5 for £1.00**

Z2515 VN2410L TO92 N-channel MOSFET. 1A 0.4W. DP 1.08 **Our Price 3 for £1.00**; 100+ 0.18; 1k+ 0.14

Z2516 AD517JH TO99 converter **£3.00**

Z2517 LM350K steel variable voltage regulator, 1.2 to 33V at 3A. DP 7.20 **Our Price £3.50**

Z2523 TICP106D TO92 SCR rated 400V 100mA. DP 0.56. **Our Price 6 for £1.00**; 100+ 0.09; 1k+ 0.06

Z2518 BYT13-1000 fast recovery diode rated 3A 1000V. Plastic body, axial leads. DP 0.35 **Our Price 5 for £1.00**; 100+ 0.13; 1k+ 0.09

Z2519 AD667JN 28DIL D/A converter, 12 bit uP compatible. Extremely flexible. DP £28.18 **Our Price £10.00**

Z2520 SN75372 8 pin dual MOSFET driver. DP 1.74 **Our Price £1.00**

Z2521 Crystal, HC60 20.000MHz. **Only 50p** 100+ 0.25

Z2522 Watch crystal 32.768kHz, case 2.7mm dia x 8mm. **Pack of 3 £1.00** 100+ 0.15

OPTO

Z2498 Toshiba TLC501 LCD. 24 x 2 line display with standard connexions (supplied). V. similar to our **Z2171 £9.95**

A couple of small matching rectangular LED's, 3.8 x 1.75 mm :

Z2500 Green **Pack of 12 £1** 100+ .05
1k+ .04

Z2501 Red **Pack of 12 £1** 100+ .05
1k+ .04

Z2505 HCPL2531 dual optocoupler, 7% CTR. DP 3.52 **Our Price £1.00**

Z2506 HCPL2630 dual optically coupled high speed logic gate. DP 5.24 **Our price £2.00**

Z1935 LED clip for right angle mounting to PC board. Plastic holder for 5mm LED has 2.3mm dia spigot. Great value at **40 for £1.00**; 1000+ 0.015

PANELS

Z5264 Handy black plastic panel 102 x 22mm with 5 pin 180° DIN skt, 2 phono skts and a single wire aerial/earth socket. Pack of 10 **£1.00** 100+ 0.05 1K+ 0.035

Z5263 Panel 80x60mm with FPT100A phototransistor, LM324 quad op amp, 24v SPCO heavy duty relay, BC546, diodes, R's and C's, Smashing little board - **only £1.00**

Z5262 Panel in the Z5089 etc. series as listed in main Bargain List. This one has 8 x 2764 in sockets + 10 74LS chips. **Only £4.00**

Z2529 Thick film circuit - small PCB 51x12mm with 13 surface mount transistors. R's are etched into substrate. **Pack of 5 £1.00**

Z4252 Seat belt alarm kit. Just a few of these remaining at **£3 each**

Z5271 Some more Currah Microspeech returns, for the Spectrum. No tape or handbook, sold for spare parts only. The 67 x 65 x 18 mm case has a 28w edge socket, phono lead, 3.5 mm jack plug lead and phono socket. Inside is 78M05 reg, SP0256 speech chip and 2 support chips, trimming cap, transistor etc **Only £1.50 each to clear.**

Z5272 PCB 71x64 with SP0256 speech chip, 2 support chips and few other bits and 5 pin DIN plug. 22way edge connector. These are returns and may be faulty - but they are only 50p each!!

SOFTWARE

COMMS SOFTWARE

A few odds and ends delivered with a parcel. As far as we can see, all are new and complete as described below:

Z6003 Multicom - handbook + 5.25" disk for Epson QX10/4.1A

Z6004 Multicom - handbook + 3.5" disk for Apricot PC/XI 4.24

Z6005 Multicom + handbook + 3.5" disk version 4.16

Z6006 Vicom - handbook + 5.25" disk for Apple

Z6007 Sage Chit-Chat - Handbook + 3.5" disk for Apricot V2.2

Z6008 Dial-Up Educational - handbook + 5.25" disk + dongle for RML480Z

Z6010 Dial-Up Educational - handbook + 5.25" disk for RML Nimbus

Z6011 Dial-Up Personal - handbook + 5.25" 80 track disk for BBC B, B+ & Master

Z6013 Dial up Personal - handbook + 3" disk for Amstrad PCW

All the above are at the same price - now reduced to just **£10.00 each** - please give 2nd/3rd choice as numbers are very limited.

Z4266 Software tape for Spectrum - "Mountains of Ket". Returns - may not work. **4 for £1.00**

SOUNDERS

Z2376 Sub-min buzzer 12 dia x 8mm high. PC mounting by Star QMB111P. **Only £1.00**

Z2377 Star CMB 6V buzzer 22.5 x 15.8 x 14.4 mm. PCB mounting. High quality, low cost - **only £1.00**

Z1771 Sounder QMB06 by Star. **3 for £1.00**

CONNECTORS

Z042 2 pin DIN speaker sockets, PC mtng. **Pack of 25 £1.20**

Z4350 A set of 3 different pairs of test leads, offering great value! - a) 67mm long, 2mm probes both ends; b) 110mm long, 2mm probes one end, 4mm plugs the other; and c) 90mm long silicon rubber, 2mm probes one end, shrouded 3mm sockets the other. All are red and black pairs. **All three for just £2.00**

Z739 40 way DIL header plug, gold plated. **3 for £1.00**

Z1485 RC4200-8S 8 way gold plated socket - matches McMurdo red range, but blue **£1.50**

Edge Connectors

Z1828 31 way double sided 0.1" pitch gold plated PC mtng **£1.00**

Z1668 38 way single sided 0.1" pitch solder tags. **40p**

Z5117 19 way single sided 0.1" pitch - takes flexible wiring and locks into place. Sample free. **20/£1.00**; 100+ 0.03; 1k+ 0.02

Z2504 PS2 Keyboard adaptor 6 pin mini -DIN plug to 5 pin 180° socket. Carded. **£2.00**

Z2504 Useful battery holder - 3AA side by side with lead and attached. Supplied with double sided sticky pad. Bagged. **25p**

Z5265 9 way ribbon cable just under 1m long with 10 pin DIL plug (0.1 pitch) one end and 9 way header skt the other. Pack of 10 leads **£2.00**

POWER SUPPLY CAPACITORS

Incredible value - these two jumbo electrolytics are offered at a fraction of their normal price!!

Screw top cans made by Siemens, type B41455

Z5146 10,000µF 100V 105x64mm dia **£4.00**;

Box of 20 £60.00; 100+ 2.00; 1k+ 1.70

Z5147 4700µF 100V 105x51mm dia **£3.00**; **Box of 35 £70.00**; 100+ 1.50; 1k+ 1.20

STOP PRESS -STOP PRESS-STOP PRESS-STOP PRESS-STOP PRESS

Z5292D 'Power one' power supply. Conventional unit, 120/240V input, output 15V @ 1.5A fully stabilized. Part enclosed size 123x102x54mm. Comprehensive data supplied **£10.00**

Z5293D 'Power One' power supply. Conventional unit, 120/240V input, outputs +5V @ 2A; + or -12V @ 0.4A; -5V @ 0.4A. Each output uses a 723 regulator and has a preset for adjusting voltage. With data **£14.50**

Z5289 Push button bank - 11 switches, all DPCO interlocking. **£1.00**

Z5290 Push button bank - 6 switches, 4 interlocking DPCO and a further 2 DPCO interlocking **60p**

Z5291 Push button bank - 6 switches, 4 interlocking DPCO and a further 2, one non-locking DPCO, the other locking 4 pole changeover. **60p**

RESISTORS

Z320 1 Watt wirewound pots - 2 additional values, 250R and 1k.

Z761 0R056 wirewound resistors 10% type HWR21. 0.5W **10 for £1.00**

Z1983 Thermistor, pack of 20, type VA1040. **£2.00**

Z414 30M 10% resistors. **Pack of 10 £1.00** 100+ .06

K446 Bourns mini cermet trimpot type 3362. 200R. **3 for £1.00**

SIL networks in original packing. 9 pin, 8 resistors. DP 38p. Available in these values, all the same price: **Pack of 10 £1.00**; 100+ .05; 1k+ .04

Z5195 330R

Z5196 10k

Z5197 47k

Z2394 TO5 case cermet trimpots type 81E. Value 50R. **Pack of 6 £1.00**. Plastic case of 50 **£4.00**. 10+ cases **£3.00**

Z2359 miniature pot 17mm diameter with 6.75mm bush and splined spindle, PC mounting. 1k lin. **Pack of 4 for £1.00**.

Z2388 Plastic stand-off for 3/4" trimpots (our 75CER type) **Pack of 50 £1.00**

Z5208 PR52 2.5W wirewound resistors, 10k. **In boxes of 500 £5.00**

Z5209 As above but 1k2. **Box of 500 £5.00**

Some more Diplohmatic trimmers, to go with those on page 35 of B/L75



Type156 (like 146)

Values available:


200R 500R 10k 20k 50k 100k 500k 2M

Prices (any mix) **1+ 56p** 100+ 0.28

Type 382

Value available: 500R

Price **1+ 44p** 100+ 0.22

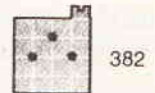

Type 386: (like 383)


Values available:

1k 10k 50k 100k

Prices: **1+ 44p** 100+ 0.22



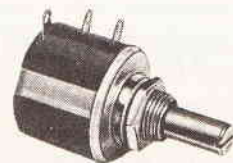Z2447 Siemens dual thermistor type P6350. **Pack of 10 £1.00** 100+ 0.05



Z2530 Precision helical pot by Spectrol, model 534. 3Watt 10 turn, linearity ±0.25%. Value 100R ±5%. DP 4.23 Our Price **£1.00**

PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT

THE POW-POW-POWER PAGE!!!

Some great value power supplies - both conventional and switched mode - all offered at a fraction of their original cost!!


Z5278 Plug in wall type, 24V ac 100mA output on 2m lead. **£1.75** 100+ 1.10

Z5279 Plug in wall type switchable non-regulated 3-6-9V 100mA. Comes complete with multiway reversible spider lead (worth 99p on it's own!). **Special Price £2.00** 100+ 1.25



Z5224 Jupiter Ace mains adaptor (there's a bit of history!) plug in type 240V, output 9V 800mA on 2m lead with 3.5mm plug. **£3.20**

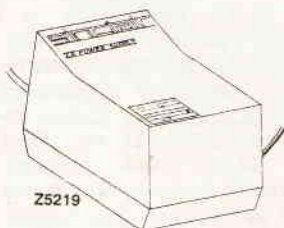
Z5227 Plug in 240V ac Beautronix power supply. Output 9V 333mA on 2m lead with 2.5 power socket. **£2.00**



Z5219 Sinclair ZX powers supply model UK700. 240V ac in, 9V 0.7A DC out. 2 core mains lead. 3.5mm jack lead output. **£2.50**


Z5220 Sinclair ZX powers supply model Euro1200. 220V ac in, 9V 1.2A DC out. 2 core mains lead. 3.5mm jack lead output. **£3.00**

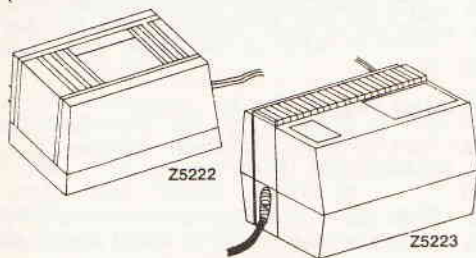Z5221 Sinclair ZX powers supply model Euro1400. 220V ac in, 9V 1.4A DC out. 2 core mains lead with 2 pin Euro plug. 2.1mm power socket lead output. **£3.50**



Z5222 Psion Organiser power supply. Plug in type, 220/240V ac. Output 10.4V 175mA on 2m lead with 2.5 power plug **£2.00**

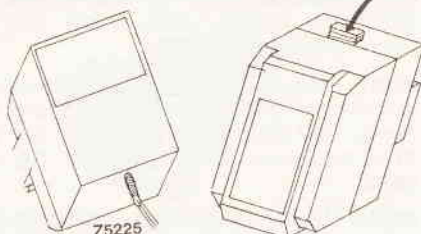Z5223 Psion printer power supply, input 220/240V ac via lead and 2 pin Euro plug. 10.4V 600mA DC output on 2m lead with 2.5mm power plug. **£3.00**




Z5225 Universal mains adaptor, plug in type 240V ac. Output switchable 3-6-9V @ 300mA on end of short lead with 2 pin socket **£2.00**

Z5226 Plug in 240V ac unlabelled power supply with short lead and 5 pin DIN socket. Outputs: 18V @ 250mA ac and 10V @ 500mA ac. **£3.00**


Z5276 Plug-in-wall power supply with 2m lead fitted with 2.5mm power socket. Output 12V 0.2A DC. Fitted with thermal fuse. **£2.00**

SWITCH MODE PSU'S

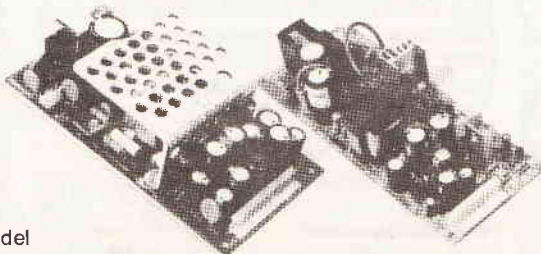

Z5256 Switch mode PSU made by Tamura Corporation. Board 195x100mm with outputs on PCB pins. Input 120/240V ac; Outputs: +5V @ 7.5A; +12V @ 1.25A (2A peak); -12V @ 0.1A. **All this for just £12.95**

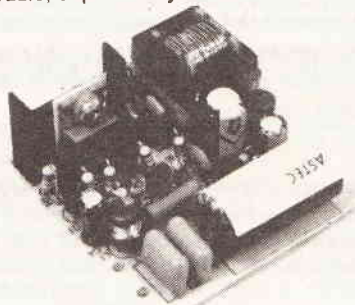
Z5257 Switch mode PSU on PCB 190x78mm. 120/240V ac input. Outputs: +5V @ 3A; +12V @ 1.2A; -12V @ 0.1A. Made by Tamradio, Japan. **Only £7.95**



Z660 Astec switched mode PSU type AA7271. This small PCB, just 50 x 50mm will accept 8-24V input and give a stable 5V dc at up to 2A output. The 6 transistor circuit provides current overload protection, thermal cut-out and excellent filtering. Offered at a remarkably low price.

Price £5.00

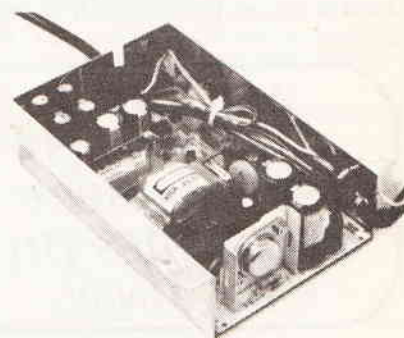Z5280 Neat switch mode PSU on panel 120x100mm and only 32mm high. Mains input via skt supplied, 3 outputs on socket are +5V @ 2A; +12V @ 0.3A; -12V @ 0.2A. These have been removed from equipment, but are clean and in full working order. **£7.50**



AA12531 Switch mode PSU by Astec partially cased. 160x104x45mm overall with 160x100mm Eurocard PCB. Inputs and outputs are on colour coded flying leads. Input 115/230V 50/60Hz. Outputs: +5V @ 5A; +12V @ 0.15A. Total wattage 50W. **£6.95; 25+ 5.43; 100+ 4.53**

Conversion Kit


K725 This kit converts the AA12531 PSU into a much more versatile supply, giving +5V @ 2.5A; +12V @ 2A; -12V @ 0.1A and -5V @ 0.55A. Complete set of parts and full instructions **£3.50** Instructions only (**K726**) **£1.00**



BM41012 Superb switch mode PSU made by Astec. Enclosed case 175x136x65mm with switched and fused IEC mains inlet. 160x80mm PCB with output pins extended to external connector. Input 115/230V 50/60Hz. Outputs: +5V @ 3.75A; +12V @ 1.5A; -12V @ 0.4A. Total wattage 65W **£14.95; 25+ 11.70; 100+ 9.75**

PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT

MOTORS

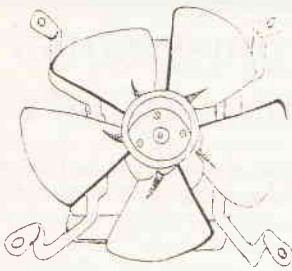

Z5171 Open construction mains fan. Five blade plastic blade 110mm dia (easily removable). Ex-equip in good condition, **£2.50.**

Z5246 Mains synchronous motor with easily accessible gearbox giving a final speed to the 5.5mm dia 12 toothed gearwheel of 0.2RPM (12 revs per hour). **Only £3.95; 100+ 2.50**

**ARE YOU A
BARGAIN LIST
SUBSCRIBER?
DON'T MISS THE
BARGAINS!!**

CAPACITORS



Z5218 22,000µF 16V electrolytic can 35mm dia x 102mm long. Tag ends. Silly price - **only £1.00 each**

K265 4700µF 40V Phillips can, PC mntg 47x35 dia. **2 for £1.00**

Z5180 1000µF 10V radial electrolytic by Nippon 13 dia x 25mm. **Pack of 10 £1.00** 100+ 0.05

Z5181 330µF 16V radial electrolytic by ITT. 13dia x 21mm. **Pack of 14 £1.00** 100+ 0.035

Z5274 40 µF 2.5kV capacitor by Bosch. Size 155x100mm dia. Superb quality **£3.50.**

Z1529 0.22µF ceramic cap. 5mm pitch. **Pack of 30 £1.00**

Z1965 0.01µF disc ceramic 6mm dia. **Pack of 40 £1.00**



Solid dielectric trimmer caps in 3 values, all PC mounting:

Z2454 5.5pF Phillips 808 series, polyethylene film DP 36p **8 for £1.00; 100+ 0.06**

Z2455 10pF Phillips 809.05 series PTFE film. DP 1.66 **3 for £1.00; 100+ 0.15**

Z2456 18pF As above, **3 for £1.00; 100+ 0.15**

PANELS

Z5203 Relay panel - some panel, this! 50, yes 50 DPCO 24V DC min relays, Omron type G2V (our type W834) on PCB 230x160mm with 2xDIN41612 64 way plugs. At 1 off prices, this would cost around £100, but you can have a complete panel at just 20p per relay - **that's only £10.00!**

Z5217 Relay panel - Eurocard 160x100mm with 64 pin DIN41612 plug, containing 8 x Omron G2V 24V min DPCO, LS00, 125 and 14 all in sockets, 4 red LED's, R's, C's, etc. **£2.00**

Z5244 Mosfet panel: 56 x VN0808M (DP 1.01 each!) 80V N-channel 1W 2A device in TO237 case + 28 x ILCT6 8 pin opto isolators, also 30+ CMOS, 74SC etc; 26 SIL networks, 56 0.1µF caps and a few other odd bits. **Super value - only £7.50**

Z5231 Memory panel, contains 208 4164 64k RAM chips all in sockets. **£30.00**

Z5232 As above, but chips are soldered in. **£20.00**

Along with the panels **Z5231/2** mentioned on page 12 (which are here now) there are a great many packed with hi-tech chips - not just 74LS, but Z80 and other processor chips, EPROM's etc. The boards are 430x320mm and mostly contain over 250 chips, date coded '84. **Order Code Z8967** - clearing at **£5 per panel** - but to get a good mix, you'll need 2 or 3 boards.

More GEC Cablevision units - these were the rack mounted distribution panels. 2 types available as below:

Z5204 Diecast housing 252x140x25mm (subscriber module) contains PCB with lots of nice high frequency bits, much of which is contained within 2 diecast boxes bolted on to the board. Most of the transistors (there are 17 of them) are BF980, BFR90A/91A BFW92 etc. Single output socket, 2 DIN41612 plugs. **Great value at £4.50**

Z5205 Larger diecast housing 252x140x57mm with 2 PCB's each containing a number of HF parts, pot cores, crystals, etc. These are input modules - 1 traffic and 1 data panel **£4.40**


Z4295 Although listed in our main Bargain List, we have large stocks of this panel, and it's not selling very quickly - although it contains a number of interesting and useful parts. There's a 27C64 Eprom in a socket, 80C85A microprocessor, 2x82C51A support chips + 5864 RAM, as well as 8x74HCT chips. There's a small length of ribbon cable to a small sub-panel with 2xMC1488 and 1489, and 3 DIL header plugs. These error correction cards by Tulsedata originally cost over £70 each - they were in last year's catalogue at £10, reduced this year to £5. Will you buy them at **£2.50?**

Z1641 PCB. Printer driver board by Teijin. Contains M5L8041A, 8x74 series, 3.579545MHz xtal etc **£2.00**

Z5167 'S' module-like Z492/3. 11 pin plug in module 80x50x50mm with a small PCB inside containing 2xBC184L, R's, C's, etc. **4 for £1**

Z5210 Power supply panel - PCB 150x65mm that has been partially assembled but nit soldered. Contains 79M05, 741, BDX339, FRC730, 4x1N4001, 10,000µF 10V cap + R's, C@s etc. (No transformer) **Only £1.00**

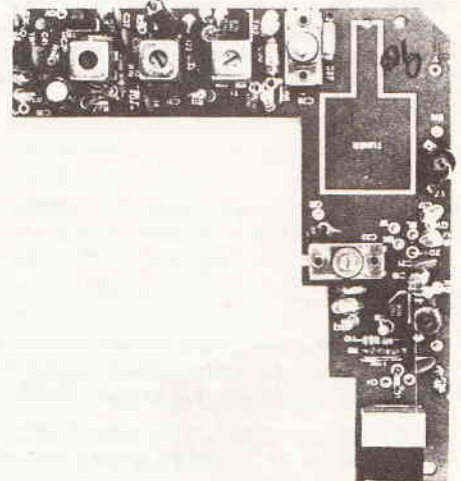Z5211 Another smaller PSU panel 97x55mm, again not soldered. Each board contains 9x1N4001, 121C thermal fuse etc. **8 panels (72 rectx) for just £1.00**



Z911 Found some more of this useful 135x135 L shaped panel - nearly a complete radio front end. Although the tuning cap is missing, there are 2 trimmers, IFT's, lots of R's and C's, 2xBF241 FET, BF194, BC208A, 2xBC148C, 2xBC149C etc. Best of all, the board hasn't been soldered, so the components are easily removeable. All this for just **£1.00**

OPTO



Z2434 Dual 7 seg LED, type TDDR5250 by TFK. Red common anode 13mm digit height. DP 1.14. Our special low price (we have 10000 to clear) **2 for £1.00; 100+ 0.25; 1k+0.18**

Z2435 Single 7 seg LED 10mm high digit. Type LN514RK. Common cathode. **4 for £1.00; 100+ 0.15; 1k+ 0.10**

Z2362 MS463M 0.6" common cathode 4 digit multiplexed display on PCB 70x30 with 15 way connector. Intended for digital clock use. Supplied with pin out. **ONLY £1.50**


2 more LCD's in small quantities, both fitted with pins:

Z2357 6 digit 0.5" 50 pin device **£2**

Z2358 2 digit 0.5" 18 pin device **£1**

Z2432 LCD 8 digit 10mm high. Single sided 36 way edge connector. **Only £2.00** 100+ 1.00 1k+ 0.80

LED BAR MODULES

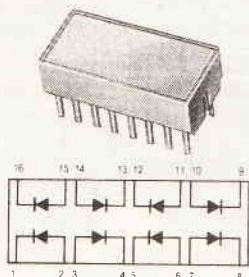

A couple of large LED light bars in 16 DIL package, 10mm high. Made by HP.

Z2462 HLMP2685 HE red 80mcd @ 20mA. DP 2.19. **Our price £1.00**; 20+ 0.70

Z2463 HLMP2785 Yellow 70mcd @ 20mA. DP 2.19. **Our price £1.00**; 20+ 0.70

Using these, you could build up a massive 7 seg display – each module being 1 element. (In practise, to maintain proportions, you'll need 10 displays for each 70mm high digit – details on request)




Z1854 7 seg LED 81720R – giant 1" digit, red. Common anode. **£1.00 each**
Z1855 As above but common cathode **£1.00**


Z1857 Single 7 seg LED LA6480, matches above – green 0.56" **4 for £1.00**
Z1858 7 seg LED LA301MA green 0.3", CA. **4 for £1.00**
Z1859 7 seg LED LA301MK green 0.3" CK **4 for £1.00**

Z2436 3mm red LED's with preformed cropped leads 7.5mm long. Super buy for quantity user – **pack of 100 £3.00** 1000+ 0.02
Z2461 PC mntg packaged red LED – mounts at right angles to PCB. 10.5x8x3.9mm. LED is 3mm. Ore type 9301A. **Pack of 10 £1.00** 100+ 0.05; 1k+ 0.04

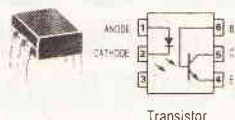Z1934 Stackable red LED – white casing round 6x3.5mm. **Pack of 10 for £1.00**
Z1932 Red square LED with rounded corners, 5mm. **Pack of 15 for £1.00**
Z1933 Thin rect. red LED – 5x1.5mm. **Pack of 20 £1.00**




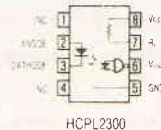Z2467 4N25 optocoupler – transistor output. DP 0.80. **Our price 3 for £1.00**
Z2469 CNY17-1B optocoupler, transistor output 6DIL. DP 0.67. **3 for £1.00**



Z2470 HCPL2300 optocoupler by HP. Logic gate output. DP is astaggering 6.33 – **our price £2.00**

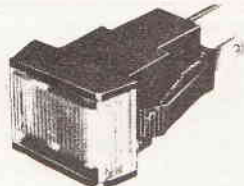Z2466 ILQ1 16 pin DIL device, probably quad opto isolator, but no info. **2 for £1.00**



Lampholders – rectangular snap in type that take LES bulb. Needs 16.1x11.6mm cut-out. DP (1978) 92p

Z5193 Red **3/£1.00** 100+0.15
Z5194 Green **3/£1.00** 100+ 0.15
Z2385 6V 5W SBC bulb. **Box of 10, £1.50**
Z2459 Neon bulbs 5.5mm dia x 15mm long – wire ended 90V neons at a great saving over normal prices! Made by VCH International. **In packs of 100 at £4.00** 10+ 3.00

ARE YOU A BARGAIN LIST SUBSCRIBER? DON'T MISS THE BARGAINS!!

Fibre Optic Cable

Z5245 Fibre optic cable, multistrand sheathed, 2.28mm od, 0.095mm² sq. Type A181. **Approx 5m length £4.00**

Z2476 Similar to above, but 3.6mm od. **£2/metre**

Z2477 Single strand 1mm dia. **Approx 5m length £2.00**

Z2478 Single strand 0.2mm dia. Approx 10m (may not be in one length) **£2.00**

SEMICONDUCTORS

(a) Diodes

Z2439 BZY88C36. 36V 400mW zener diodes. **Pack of 100 £2.00.** 1000 £10.00
Z2465 Dual fast recovery diode BYW51-150A 150V 20A. TO220 case. DP 0.99. **Our price 2 for £1.00**
K129 8 AA113 diodes **£1.00**
K197 50 AA139 diodes preformed for horiz. mntg **£1.00**
K237 200 SD3 diodes, 2 joined back-to-back, preformed **£1.00**
K242 10 S2AR2 rects, 200V 1A **£1.00**
K283 100 1N922 silicon diodes preformed **£1.00**
K285 25 CV8790 signal diodes **£1.00**
K286 10 Germanium signal diode **£1.00**

Z2454 MPS5010 1.2V voltage ref. 2 pin TO92. **3 for £1.00** 100+ 0.15

Bridge Rectifier Clearance

Z2347 4A 200V in line **6 for £1.** 100+0.99 1k+.06

(b) Transistors

Z2383 2N6027 P.U.T DP 49p, **Our price 6 for £1.00**; 100+.08 1k+ .05

Z2384 MPSA13 30V Darlington TO92 transistor. Hfe 10,000 @ 0.1A DP 32p. **Pack of 8 for £1.00.** 100+ .06 1k+ .04

Z2453 TIPL762 NPN 6A 120W 350V transistor. DP 4.02 **£2.00**

K448 12 MPSA92 **£1.00**
K449 20 BC258A **£1.00**
K447 10 BF419 **£1.00**

(c) Voltage Regs

Z2460 78M12 500mA 12V voltage regulator at a super price – **6 for £1.00** 100+ 0.09 1k+ 0.06
Z2455 7805 riveted to small ally heatsink (unused) **5 for £1.00**
Z950 LAS1510 voltage regulator. 10V 1.5A TO3 case. **2 for £1.00**

(d) Digital IC's

Z2452 74HCT164 **4 for £1.00**

(e) Linear IC's

Z2456 CA3161E BCD-7 seg decoder driver, with pin out **£1.00**
Z2457 CA3162E A-D converter, 3 digit display, with data. **£2.50**
Z4160 TDA1035. Versatile audio amp chip, with IF amp and demodulator. Electronic volume control. Max output 4 watts into 8R. Supplied with cct and data. **Only £1.00**

LOW COST SOUND CHIPS

A new range of sound effect chips is now being stocked. Supplied with typical circuit.
UM34811A Melody generator **£1.20** 100+ 0.75
UM3562 3 gun sound generator **75p** 100+ 0.38
UM66 3 Christmas carol medley **75p** 100+ 0.38

Z2471 SN75372 interface chip **50p**

Z2472 LF398N sample and hold amp. 8DIL DP 3.94 **Only £2.00**

Z2473 OP27 low noise precision op amp. 8DIL. DP 1.70. **Only £1.00**

Z722 TDA2653A vertical deflection chip. 13 lead SIL package, with comprehensive data **£1.00**

(f) Crystals


Z2464 8.000MHz crystal HC16 case **50p**

Data sheets giving pin-outs and brief spec are available on all above items at 10p each

TRANSFORMERS

Z5207 Torroidal transformer rated 75VA. Mains primary, 3 secondaries: 7V @ 7A, 8V @ 1.5A, 14V @ 1.5A. Useful voltages at a low price - **£4.50**

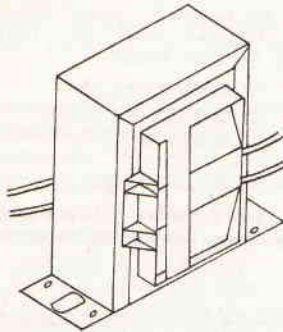Z5202 Torroidal transformer. This is the same series as our Z4290 type by Belclere - 75mm dia x 33mm thick. Fixing by means of a tapped bush. Mains primary, secondary 14-7.5-0-7.5-14V @ 1.25A **Excellent value at £2.95 each** 100+ 1.50



Z5206 Super transformer for railway and other modellers. Mains primary, secondary 16V 3A. Size 50x55x60mm high. 61mm FC. Great value for money, **only £3.00** 100+2.00 1k+1.50

Some new mains transformers, ideally suited for PSU's:

Z5212 21V 1A Clamp, wires
60x45x50mm **£1.50**

Z5214 11V 0.5A PC mntg 53x40x4
4mm **£1.00**

Z5215 15V 0.25A PC mntg 43x33x3
6mm **75p**

All the following are mains transformers, and have secondaries as shown. Current rating is estimated from size of transformer.

Z5233 17V 1A 56x67x53mm **£1.50**

Z5234 14V 0.5A 45x54x41mm **£1.00**

Z5235 9V + 10.5V 15VA max. 56x67x50mm **£2.00**

Z5236 21V 500mA 50x60x45mm **£1.50**

Z568 Transformer, large auto rated 8.3A **£12.00**

Z8971 Transformer rated 100VA - 0-120, 0-120V primary and 0-20, 0-20V secondary (5A total). Size 89x75x68mm. DP 19.06. Our price **£9.50**


Z8972 Transformer rated 100VA by Majestic, 0-240V pri, 25V 4A sec. 100x85x70mm. **£6.50**

Z1773 DC-DC Converter - 5V in, 15-0-15V 10-34mA (1W) Size 34x26x10. **Only £3.00**

FINISHED GOODS




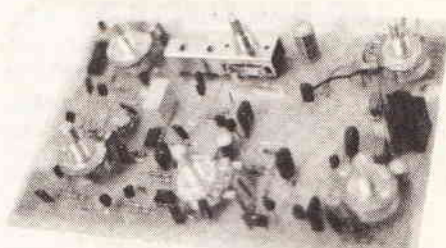Z5285 Oscillator /amplifier type RT5001 by GEC, housed in an aluminium and bakelite case 180x52x50mm. The PCB has on it a small transformer, 3x100µF 16V tant bead caps, 2xBCY40 etc. **Only £1.50**




Z5286D Metal detector panel 185x115mm. This is the complete PCB from an expensive (£80+) "treasure detector" - just add wire coil and meter to make a working unit. Circuit uses 15 transistors and 3 IC's. There are 5 pots and a rotary switch. Detailed info inc. cct diagram and coil windings supplied. **£12.95**

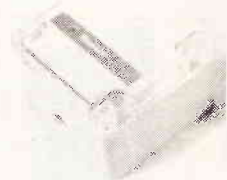Z5201 Ingenious level indicator for LPG tanks. Magnetic strip attaches to exterior of tank and works by pouring hot water down gauge. Colour change will indicate level of gas left. 220mm long. Supplied on card with full instructions. **Only £1.00**



Z5288 Polycarbonate grey sealed box 82x80x55mm with clear lid (DP 9.111). Inside is a steel panel with loud 12V buzzer and a PCB with push button (operates when lid is removed) a green LED and 1N4005. There's a 12mm hole in the side of the box and a cable gland to fit. **Exceptional value at £4.00**

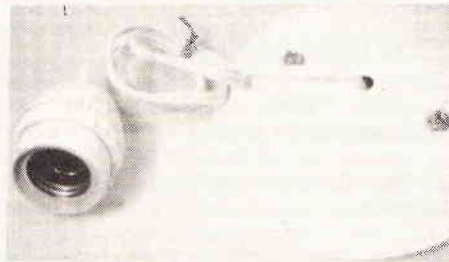Z5287 Here's an oldie - we had a batch of these some time ago - the "Tyrometer" - used to indicate tyre pressures on HGV's, this is the pod that fitted into the drivers cab. On the front panel are two small push and a toggle switch. Inside is a PCB with 11 miniature wire ended bulbs, a choke, 2 caps and a buzzer. There's a short length of 14 way ribbon cable, too. **£3.95**



Z5268 Boxed suspension cord set. White painted steel domed ceiling plate 137mm dia with 0.5m twin lead terminated to ES plastic hanging socket, also white. (250V 500W max rating). **£2.50** 25+ 1.75

Z2109 Dynamic microphone with lead by Adastra, model M8. **£3.50**

We buy surplus stock - send details to the Managing Director, Greenweld Electronics, 27 Park Road, Southampton, SO1 3TB

LIGHT UP YOUR LAYOUT

K692 Super deal for modellers - we supply a mains power supply, 100 miniature lamps for wiring into your railway layout or dolls house, and 100m of flex. Circuits and details of how to wire up the lamps in series/parallel are provided. Everything for just **£19.95**

CONNECTORS

Extra special price on gold plated DIL sockets - a parcel of Vero DIL sockets has arrived:



(a) PCB mntg, std profile:

Z5237 28 way £1/10 100+ .06
 Z5238 40 way £1.50/10 100+ .08

(b) Wirewrap

Z5239 18 way **£3.80/10** 100+ 0.20
 Z5240 20 way **£4.30/10** 100+ 0.25
 Z5241 28 way **£7.00/10** 100+ 0.40
 Z5242 40 way **£10.00/10** 100+ 0.65

Z2360 Turned pin DIL socket - 24 pin, but 0.3" pitch not 0.6". Pack of 5 for £1. 100+ 0.10

ARE YOU A BARGAIN LIST SUBSCRIBER? DON'T MISS THE BARGAINS!!

P5430 14 pin DIL header plug, gold plated solder type. As listed in our cat at 65p - special purchase price **3 for £1.00**; 100+ 0.16; 1k+ 0.12

Z739 40 way DIL header plug, gold plated. **3 for £1.00**

P9016 16 way IDC header socket. Pack of 5 **£1.00**; 100+ .10

Z2379 IDC 16 pin DIL socket. Pack of 5 **£1.00**

Z2382 Double row 0.1 socket PCB/chassis mounting 16 way x 2, but only 1 row of pins. Pack of 5 **£1.00**



High quality 3.5mm mono jack plugs with coloured plastic sleeves made by Cliff:

Z2457 Red **10/£1.00** 100+0.06
 Z2458 Green **10/£1.00** 100+ 0.06
 Z2479 White **10/£1.00** 100+ 0.06
 Z2480 Cream **10/£1.00** 100+ 0.06

Z1485 RC4200-8S 8 way gold plated socket - matches McMurdo red range, but blue **£1.50**

Z1768 Numicator/CRT base 13 pin PC mntg by Cinch. Pack of 4 **£1.00**

Z042 2 pin DIN speaker sockets, PC mntg. Pack of 25 **£1.20**

Z2448 Phono plug. Black plastic cover. We have a large quantity of these to dispose of, so are clearing them at **25 for £1.00**, 100+ 0.03, 1000+ 0.02

The 1992 GREENWELD Catalogue is out now! 132 pages of electronic and modellers supplies.

Only **£2 (UK/ BFPO; £4 O'seas)**

ORDER NOW!
 See order form for details



Z2397 25 way 'D' type shells. Can be used as either plugs or sockets, according to pins fitted. (No pins available) Pack of 6 **£1.00**



Z2395 Right angle 50 way 'D' plug, PCB mounting, plastic housing. **£2.00**

Z2396 Right angle 9 way 'D' socket. **40p**



Z2430 37 way 'D' type plug, IDC type **£2.00** 100+ 1.00



Z2429 15 way 'D' connector sliding lock retainer by ITT type DA51220-1 DP **£3.45**, Only **£1.00** 100+ 0.40



Z2445 Data connector - like BT skt - 6 way PCB mntg for right hand plug. DP 1.74 Our price **2 for £1.00**, 100+ 0.30

Z2398 DIN 41612 IDC socket, C body, rows A and C only. List **£6.65**. Our price **£2.50**

Z2399 20 way card edge IDC socket. DP 2.47. Our price **£1.00**

Z2426 25 way double sided 0.1" pitch edge connector, gold plated, solder tags. **£1.00**

Z2427 50 way double sided 0.125" pitch edge connector, gold plated, wirewrap terminals. **£2.00**

Z2428 PC mounting edge connector, 13 way double sided 0.15" pitch. Gold plated. Pack of 2 **£1.00** 100 + 0.25

NEED A LEAD?

Here's a selection from a recent parcel:

Z5247 1.1m long twin thick flex, 2x3mm wander plugs one end, 3.5mm mono jack plug the other. Assorted colours. Pack of 3 **£1.00**; 100+ 0.18

Z5248 1.8m long twin flex, 3.5mm mono jack plug to open end. Fitted with sleeved square grommet. Pack of 5 **£1.00**; 100+ 0.10

Z5249 2m long twin flex, 2 pin socket to open end. Fitted with sleeved round grommet. Pack of 5 **£1.00**; 100+0.10

Z5250 1.1m long 3 core sheathed cable with odd socket one end, yellow 5mm LED in plastic housing the other. Pack of 8 **£1.00**; 100+ 0.06

Z5251 1m long twin flex, 2.5mm power socket to open end. Fitted with sleeved square grommet. Pack of 3 **£1.00**; 100+0.18

Z5252 Super heavy duty extra long (2.7m) twin sheathed cable with moulded on 2.5mm power socket to open end. 2 for **£1.00**; 100+0.25

Z5254 2m long 4 core sheathed cable fitted with a sleeved grommet. 4 pin DIN socket to open end. 4 for **£1.00**; 100+ 0.12

Z5255 2m long 2 core black sheathed mains cable (3A). Moulded 2 pin Euro plug one end, 0.25 tags the other. 3 for **£1.00**; 100+ 0.18

BATTERIES




Z2452 Lithium battery - inorganic type by Tadiran, type TL5104. AA size, 3.6V PC tabs. Date code 06/88 **£1.70**

Z2453 As above, but type SL360, date code 4/87. **£1.50**

Z2450 Tadiran AA size battery 3.6V PC mounting. Date code 6/89. DP on these is 5.17. Our price **£2.00** 25+ 1.50 100+ 1.20



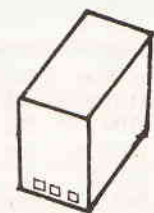Z2451 Tadiran 0.5AA size battery, 3.6V PC mntg. Date code 8/86. DP 4.58 Our price **£1.75** 25+ 1.35 100+ 1.05



Z2415 AA Ni-cads at a price never before seen! Pack of 8 in a tough plastic case 56x63x33mm - either use as a 10V battery pack or remove and use cells individually. Special low price **£1.60 each**; 25+ 1.10 100+ 0.80

PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT


RELAYS

Code	Mnfr	Type	Coil V	Coil R	Contacts	Base	Type	Size l.w.h	Qty	Pic	Price	
Z2423	VARLEY	VP4	48V	5800R	4PCO	1A	ST	C	29.18.29	93	A	1.00
Z2414	SIEMENS	V23154	12V	800R	4PCO	1A	PC	C	29.18.29	96	A	2.00
Z2421	ITT	A2825	24V	1000R	6PCO	1A	PC	C	33.30.29	57	B	1.00
Z2424	ITT	A2446	48V	3000R	DPCO	1A	PC	C	29.16.13	59	C	1.00
Z2425	FEME	RCP11	110V	10K	3PCO	10A	11PIN	C	35.35.56	84	D	2.00
Z2420	AMF	KUP14D	24V	450R	3PCO	10A	ST	C	37.34.51	82	E	2.00
Z2419	NATIONAL	AE1324	24V	2000R	DPCO	1A	PC	C	30.20.10	218	F	1.00
Z2413*	AX	481F	12V	1500R	SPCO	1A	PC	M	32.10.10	533	G	1.00
Z2408*	CLARE	HGR2M	5V	500R	DPCO	1A	PC	M	40.25.10	117	H	1.00
Z2418	OUB	SS124D	24V	1200R	SPCO	5A	PC	C	21.17.15	118	I	1.00
Z2412	OUB	SS-224D	24V	1200R	DPCO	2A	PC	C	18.10.12	20	J	1.00
Z2417	OUB	SS-224D	24V	1200R	DPCO	2A	PC	C	18.10.12	196	J	1.00
Z2422	GENTECH	AZ153D-04Y	36V	4300R	SPCO	2A	PC	C	26.14.11	648	K	1.00
Z2400*	GENTECH	G42F	3V	130R	SPB	1A	PC	C	33.16.11	127	L	1.00
Z2416	HAMLIN	HE221A4860	24V	11K	SPM	1A	PC	R	32.10.09	799	M	1.00
Z2411	HAMLIN	HE221A7080	12V	800R	SPM	1A	PC	R	32.10.09	1501	M	1.00
Z2407	HAMLIN	HE262A7780	5V	470R	DPM	1A	PC	R	32.12.09	135	N	1.00
Z2406*	ELLIOTT	36876/5	5V	130R	SPB	1A	PC	R	32.15.10	345	O	1.00
Z2410	ALMA	CPR3	12V	1100R	3PM	1A	PC	R	38.23.12	38	P	1.00
Z2405*	CLARE	PRME15005AB	5V	470R	SPM	500MA	DIL	R	20.07.05	354	O	1.00
Z2404*	HAMLIN	HE721A5262	5V	520R	SPM	500MA	DIL	R	20.07.07	51	O	1.00
Z2415	AX	132A-1	12V	180R	SPM	500MA	DIL	R	20.07.07	31	O	1.00
Z2403*	AX	132A-4	5V	520R	SPM	500MA	DIL	R	20.07.07	65	O	1.00
Z2402*	CLARE	CUPV10201	5V	170R	SPB	1A	PC	R	25.10.9.5	50	N	1.00
Z2409*	CLARE	CUPV10302	12V	370R	SPB/SPM	1A	PC	R	31.12.04	27	O	1.00
Z2401*	AX	175A-4	5V	500R	SPM	1A	PC	R	32.15.9.5	47	R	1.00



Discounts for larger purchases: 100+ (any mix) less 40% 1000C+ less 60%

Type: C= conventional M= mercury R= reed
 Contacts: 4PCO Four Pole Changeover Base: ST Solder Tags
 DPCO Double Pole Changeover PC PCB mntg
 SPCO Single Pole Changeover DIL 0.3" pitch dual in line
 SPM Single Pole Make
 SPB Single Pole Break
 3PM Three Pole Make

*Internal diode protection

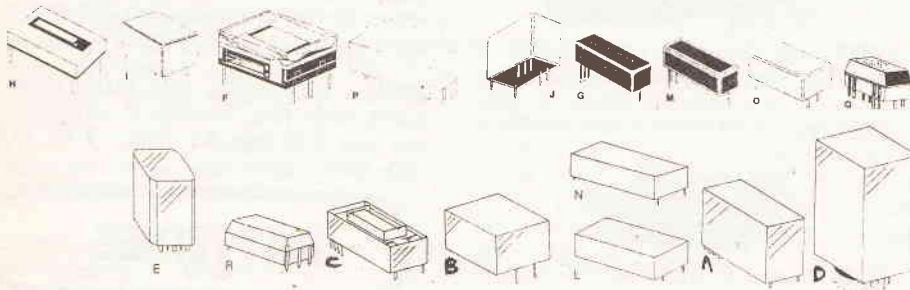

TIME DELAY RELAYS

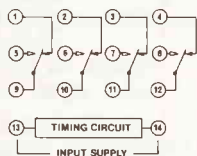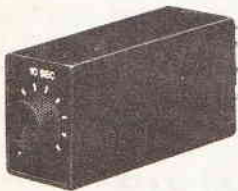

These all originate from the largest component distributor in the UK and are in original packing. Sub min 4 pole changeover plug in type, delay before energize. Same as Omron H3Y4 series

Code	Volts	Time	DP	Price
Z5186	240V ac	5s	25.83	£5.00
Z5198	240V ac	10s	25.83	£5.00
Z5190	240V ac	10m	25.83	£5.00
Z5183	110V ac	5s	25.83	£4.00
Z5184	110V ac	10s	25.83	£4.00
Z5185	110V ac	60s	25.83	£4.00
Z5186	110V ac	5m	25.83	£4.00
Z5187	24V DC	5s	24.19	£5.00
Z5188	24V DC	10s	24.19	£5.00
Z5189	24V DC	60s	24.19	£5.00
Z5190	24V DC	5m	24.19	£5.00

Z2350. Open construction 12V relay with 0.25 tabs. Ideal for car use. Single pole make contact rated 15A. £1

Z2496 Omron MY4 relay. 48V ac coil, 4PCO contacts rated 5A **£1.00**

Z2497 IMO 60.32 relay. 12V DC coil, DPCO contacts rated 10A **£2.50**

Z5178 Ex-equip PCB mntg 12V heavy duty rela - DPCO contacts rated 10A 250V. IMO model 60.42. **£1,50**


Z5179 As above but 3 pole changeover IMO 60.43. **£2.00**

Z2442 PCB mounting relay 30x24x10mm. 4PCO. 1150R coil, operates from 15-30V. **£1.50**



Z2433 Hermetically sealed mains relay, miniature plug in type with 4PCO contacts. Size 22.5x29x32mm. DP (1987) 17.75. Our special low price **£4.75**

SWITCHES

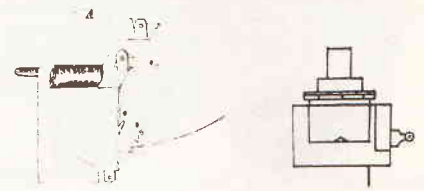

Z5174 Timer switch by Diehl of Germany. Superb geared mains motor, (1 rev per 12 hours) operates a cam that switches 2 change over contacts with centre - off positions rated 16A 250V. Size 60x54x43mm. Spindle is 14x6mm dia. **Only £3.00 100+ £1.50.**

Z2361 Heavy duty push switch - push to change over, locking. Needs 12mm hole. Plunger is 8mm dia x 9mm high, **3 for £1.00**

Z2387 PC mounting push switch - 1 pr make and 1 pr break contracts. Right angle plunger is 5mm long x 2mm dia. With protective cover. Again, very high quality. **2 for £1.00**

POINTS LEVER SWITCHES



Great switch bargains for railway modellers - these small switches 18mm wide and 12mm high (excluding lever) and just 4mm thick with 14mm FC come in two versions:

Z2363 2 position, 2 pairs make and 2 pairs break. **Pack of 5 £1.00 100+ 0.10**

Z2364 3 position, 6 pairs contacts (2 pole 3 way). **Pack of 5 for £1.00 100+ 0.10**

TRANSDUCERS

Z5266 Miniature 15R speaker 45mm(1.75") dia. **3 for £1.00; 100+ 0.16; 1k+ 0.10**


Z5267 75R miniature speaker 57mm dia. **3 for £1.00**

Z5275 57mm 8R speaker with 0.5m twin flex and socket attached. **3 for £1.00**

Z2503 Sub-min 8R speaker with mylar cone. 30mm dia with short lead fitted. **2 for £1.00**


We are always looking for new lines to add to our lists. Send details/samples of goods available to: **The Managing Director Greenweld Electronics Ltd 27 Park Road Southampton SO1 3TB**

Viewdata Terminal/Modem

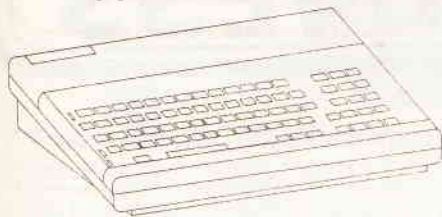

Tandata TD1100 alphanumeric Viewdata/Prestel Adaptor.


These units were used with a home banking system. The console was hooked up to your TV and telephone line, and by using the standard qwerty keyboard with separate numeric keypad, you could access your account. The well styled black and grey case 300x180x75/40 has a 75 key keyboard connected inside by a DIL plug to the main PCB. This has mounted on it the modem sub-panel + 3 relays, UM1286 Astec colour modulator with sound, + SAA5020, 5050, 5070, SY6504, 68B10, MCM51101P45, 2x2114 & 2732 EPROM all in sockets, as well as over 20 other LS and linear chips, transistors etc. There's a back up nicad battery and a regulated power supply. On the rear panel is an on/off rocker switch, UHF output socket, printer skt(15 way D), and cassette DIN socket for recording data. There are 3 leads attached; 4m long mains lead with 13A plug, 4m long BT lead with old-style plug, and a 3m long TV co-ax lead. All in all, a versatile, useful compact unit either to use as it is or for the parts within. The component value alone is over £60, so you can see what a bargain this is - it even comes with a photocopied handbook!!
Order Code Z8963. The whole unit as described for just **£12.95**
 Also available brand new and boxed, **Z8964 £16.95**

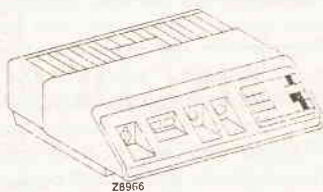


Z8966 Prestel set less monitor. This cased unit 420x430x100mm made by Phillips, model HU01 contains all the logic and control circuitry for Prestel - the monitor (not supplied) sits on top. On the back panel there is an 8 pin DIN socket for text output to monitor, mains outlet to monitor and an 8 pin DIN printer socket. There's also a mains lead and old type lead to telephone socket. On the front panel there is a detachable (on curly lead) keypad (20 keys) on/off keyswitch, tape and keyboard sockets and indicator lamps. Inside there's a large transformer and power supply and 4 PCB's - one is a modem panel; one has 8048 and SBB2626 in sockets + 15 other chips, transistors etc; the third has SAA5030/5042/5020/5050, a bit of memory (2x2114) + a few other chips. The fourth panel has SAA5010 in socket, 9xBSX20, 4xBC548/558. All boards are interconnected with plugs and sockets. These units are complete but not new and may well be in working order - but we're selling them for the parts value only - just **£16.00**



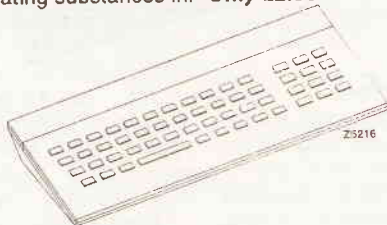Z5200 Spirit Burner. Very useful in science labs or for the home experimenter. Chromed steel container 93mm diax48mm high has absorbent material covered in wire mesh. Adjusting lever allows variations in temperature. Complete with 70mm dia dish for heating substances in. **Only £2.50**




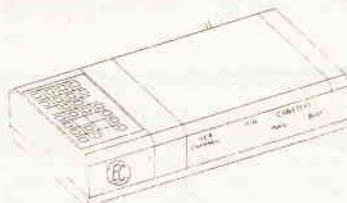Z5216 Tandata "Homedeck". These are later versions of Z8963 and are (a) smaller and (b) remote controlled. The two tone grey case is 270x110x28mm and has a full qwerty keyboard and separate numeric keypad. Inside, on the PCB are a few components to transmit the data via 2 IR LED's to the receiver. The unit is powered by a PP3 battery. Super value at just **£3.00**




Z8970 Remote control cable TV unit made by GEC. Attractive black plastic case 205x120x40mm with membrane pushbutton keypad (22 keys). Front panel has 4x5mm red LED's to indicate status and a dual 7 seg display to show channel. On the 195x102mm PCB is a small regulated power supply (12V & 5V) derived from **Z5226** plug in PSU (not supplied). The main chip is a KS49429 and there are also TBA120T, ULN2003B, 4049 + 4.000MHz crystal & 3 small signal transistors as well as the IR detector diode. 2 screened cases contain (a) a PCB with some filter circuitry utilizing surface mount technology, few small chokes, couple of trimmer caps and input and output sockets; and (b) the infra red decoding circuitry using a TDA3047 chip. Regrettably, we don't have any remote controllers, but these units offer great value for money - just **£5.95 each**

MONSTER SCREWDRIVER BARGAIN !!!

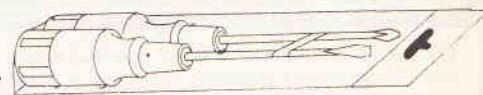

Tremendous value - 2x200mm screwdrivers, 1 pozi, 1 straight blade in plastic pouch. Wooden handles. Overall length 340mm. **ONLY £1.50.** Order code **Z5172**

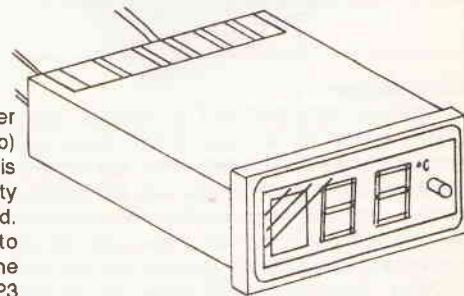A nice parcel of digital thermostats has just been delivered - these are high quality units badged BIRCH and manufactured by Wyrnech.




Z5228 Complete unit in panel mounting clip-fix case (requires 60x27mm cut out). 2 digit display. Range 40-99°C. Independent on/off set points. Uses LM35CZ sensor, supplied on a 3m long lead (DP 5.93). Has 5V relay on board with 240V 8A c/o contact. Exceptional value for money **£14.95**

Z5229 Case for above unit with red bezel and front clip. Overall dimensions 57.5x25x70mm deep. **Only £1.50 each** 100+ 0.80

Z5230 Complete panel to fit in above case (no probe) **£9.95**

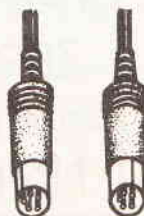Greenweld
27 Park Road
Southampton
SO1 3TB
Tel (0703) 236363
Fax (0703) 236307
We are open to callers
from 9-5.30 Mon-Sat



DRAGON INTERFACE

SB9 £1.00

Interface unit to convert digital input (as obtained from Atari-compatible joysticks) to the correct analogue level for use with such home computers as Dragon, Tandy Colour, Radio Shack etc. Two separate channels for competitive games. Two 5-pin 240° DIN plugs to compact case with two 9-pin plugs, with internal circuitry and connections for Atari-type joysticks. Black plastic.
 Dims: (Body) 116 x 62 x 29mm


MODEM MADNESS

This parcel consists of several hundred brand new BT approved modems - but we are not allowed to say who makes them. They do, however, offer extremely good value for money, as they are being sold for a fraction of their true worth




Z8973 Modem.

A compact V21/V23 300 or 1200/75 baud modem made for a major British telephone company. The units are new, boxed and complete with power supply but are without the official instruction manual, and have had the manufacturers label removed. Some instructions have been worked out by our technical department and these will enable you to use it as a working modem - further information gratefully received. Plugs directly into a standard BT 600 series socket and a RS232 port on any computer. Tone/auto dialling + last number re-dial. Dimensions 205mm x 195 mm x 30mm. Front panel has reset button, and 5 status LED's. Excellent value for money - **£49.95**

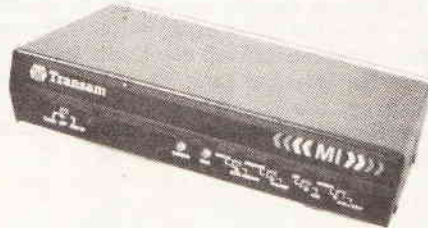


Z8974D Transam M1 mobile/mains intelligent modem. New and boxed with mains plug in power supply (9.5V 800mA). Auto dial and answer, V21/23, buffered terminal interface from 75-9600 baud, password access. Black steel case 230x150x50mm. Rear panel has lead with BT plug, 15 way D skt for radio interface, S5/8 serial data socket (use our **Z4284 S5/8-RS232 converter**, price **£6.00** if required), and 12V input socket. On the front panel there's an ext/batt/off switch; auto/manual answer switch; originate/answer switch; 300/1200 switch; normal/intelligent switch. Comprehensive 36 page user manual. (photocopied for £1.50). **Our Price £50.00**

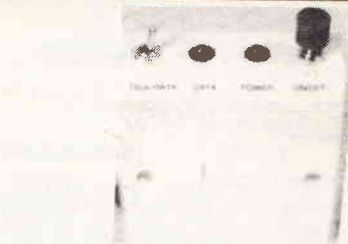

Z5284 Modified BT socket.

Unusual item believed to be used in conjunction with the above modem. It consists of a standard BT socket that has 6 way flat type cable wired into it; this probably plugged into a special outlet that could provide power as the centre pair (blue and green wires) are connected to a switch which links to a 6 pin DIN wired as per above modem power supply. A second switch enables selection between the modem and 'phone plugged into the socket. Power and Data LED's indicate the state of the junction box. **£3.00**

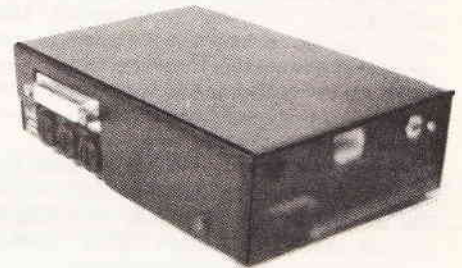

Z8975 Data Switch

Another item from this package of data communication hardware. Powered from a modified RS232 connector that has a 12V supply on line 5 it is believed that the above telephone socket plugged into this device to provide power for the modem and enabled selection between speech and data communication by both the switch on the unit and the "remote" socket switch. Steel case 170x102x45mm has main PCB with 2 relays, pot cores, chips etc, and a small power supply sub panel with an Astec voltage converter, 7805 etc. **All for £4.50**

Z8976 This is the above two items - they are boxed together. (Z5284 + Z8975). **£6.95**

Z8958 Modem returns - model 21/231AD (Same as our Z8937-see P7 of B/L 75). No idea what's wrong with them - some have fault labels on them. Supplied complete with plug in PSU. **£15**

ORDERING INFORMATION

Prices in bold include VAT at 17 1/2% - quantity prices in light type do not include VAT which should be added at the current rate. We accept cheques, PO's, Money orders, Bank drafts, cash including foreign currency bank notes, book tokens, Access and Visa. We are happy to process Official Orders from Education and other government funded sources. Don't forget to include your name and address. Send the completed order form to:

Greenweld Electronics Ltd
27 Park Road
Southampton
SO1 3TB
United Kingdom

Most orders are despatched within a day or two but some may be delayed because of temporary non-availability of goods.

HOW TO CONTACT US:

By Post: Use the address above
By Phone: (0703) 236363
(Ansaphone out of business hours)
By Fax: (0703) 236307
By EMail (Compuserve): 100014.1463

We are happy to despatch orders to anywhere in the world. The most convenient way to order is by Fax, and the best way to pay is by credit card. Our International Telefax number is +44 703 236307, although you may of course telephone us on +44 703 236363, or write to us. Overseas orders are exempt from VAT, and 15% should be deducted from prices shown, except books, which are zero rated.

Cellular Mobile Aerials

A few different types, all new in original packing.

Z5281 Antiference TAP9036 1/4 + 1/2 wave 3dB. Frq 890-960MHz VSWR 1.5:1. Includes 3/4" claw mount with 5m of RG58 cable. Complete with fitting instructions. **Only £3.00**

Z5282 ZS Electroniques ZS914-09 claw mount with 4m cable and fitting instructions **£3.00**

Z5283 Jaybeam MU904-ZG/h with 4m of cable attached. **£3.00**

SPECIAL OFFER - SAVE £10!!

Z8973 Modem + Z8953 Maximiser
Details of maximiser on Page 7 of B/L 75 or Page 5 of B/L 75A
Normally £69.95 - Offer Price £59.95

ORDER FORM

SS92 1 2 3 4 5 6 7 8

Send your order to:



27 Park Road, Southampton, SO1 3TB

(A different postcode is correctly shown on reply paid envelopes)

Customer No: Date:

Name:

Address:

Post code

OFFICE USE	ORDER CODE	QTY	No of Packs	Description	Price	£	p
	Z9999			Bargain List Subscription Service	UK/BFPO inc Post	2.00	
				Our next 6 Lists with reply paid envelope	O'SEAS inc Post	4.00	
	B/ L 75			1992 48 page Bargain List Supplement	UK/BFPO inc Post	0.40	
				(Free if requested with order)	O'SEAS inc Post	1.00	
	C1992			1992 Catalogue	UK/BFPO inc Post	2.00	
					O'SEAS inc Post	4.00	

Tick which required

IMPORTANT: Please fill in the following information. Thank you

1. Did you receive this Catalogue (Tick all that apply):

- with your previous order Unsolicited As a Bargain list subscriber
- with Everyday Electronics With ETI
- with Television Other (Please state how)

2. Please let us know if you want this order:

- Sent as soon as possible with a credit note for any parts out of stock;
- Sent as soon as possible with any out of stock items to follow: (only if value over £10);
- Held for expected deliveries for up to days (state how long);
- Other (please specify)

3. Have you ordered from us before? YES NO Are you already a Bargain List Subscriber? YES NO

4. Please tick method of payment: Cheque PO Cash Credit Card Other

Credit Card No (Visa/Access/Connect): Ex Date

(If ordering by credit card, only goods supplied will be charged, on the date of despatch)

SIGNED

Standard Postage*	£2 50
OR Next day delivery †	£9 00

Sub-Total	
Deduct Cr	
TOTAL	

* UK/BFPO only. O'Seas extra † Mainland UK only


CQ/PO:	EX?:	C/N	C/C	CASH	B/T	G/V	ST
CO:	CH:	P:	D:				

TWO STUNNING DIGITAL MULTIMETER OFFERS!!


- ★ 3½ digit 8mm LCD display
- ★ Fully autoranging
- ★ Display hold facility
- ★ Diode and continuity test
- ★ Probe styling
- ★ Automatic polarity and zero
- ★ Protective carrying case

**A £39.95
AUTORANGING
MULTIMETER
(1991 Catalogue)
LESS THAN
½ PRICE!!
YOURS FOR
JUST**

£19.95

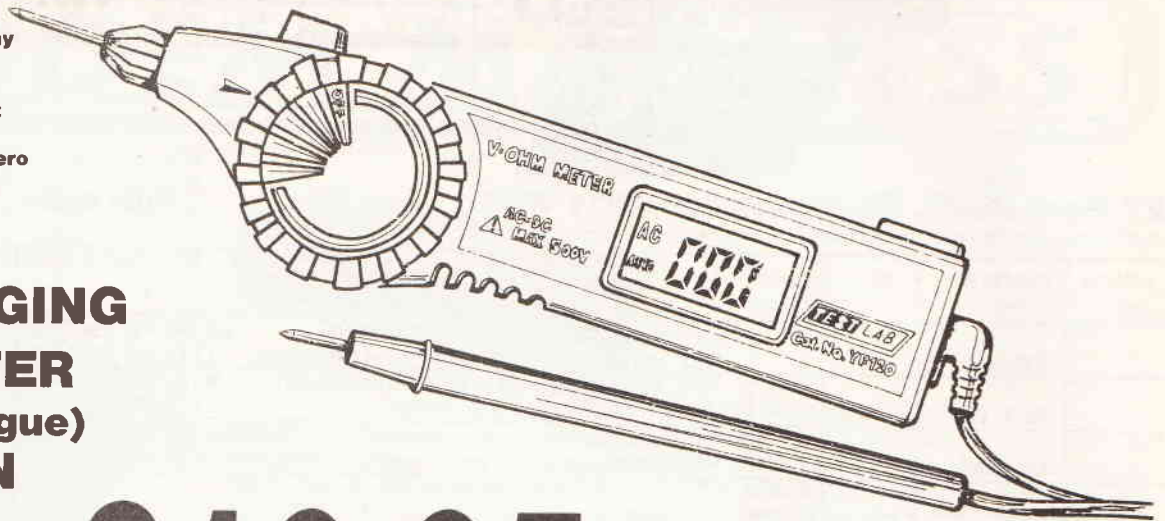

Order Code	DM1360
AC volts	0-2-20-200-500 Vac ± 2.3%
DC volts	0-200m-2-20-200-500 Vdc ± 1.3%
Resistance	0-200-2k-20k-2M-20MΩ ± 2%
Dims	133 × 29 × 17mm

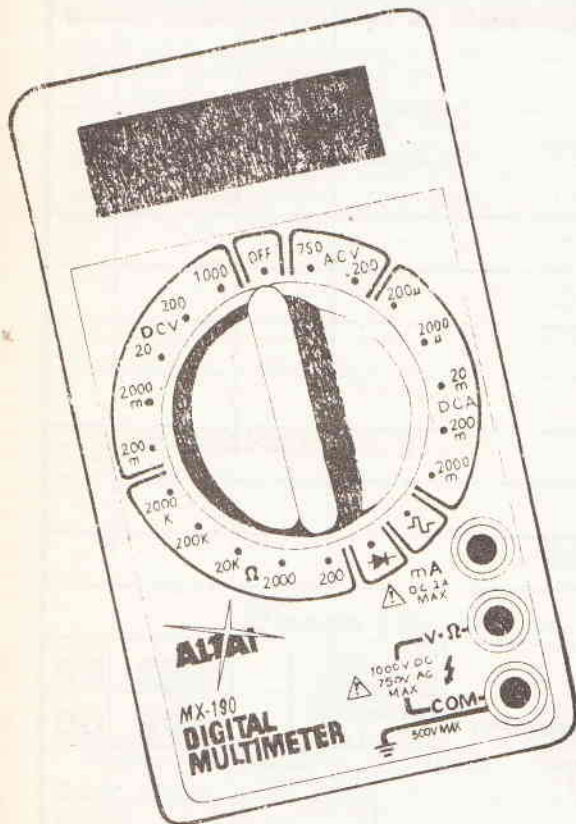

- ★ 19 ranges
- ★ 3½ digit 12mm LCD display
- ★ Signal injector function
- ★ Diode test
- ★ Fuse protection
- ★ Automatic polarity and zero
- ★ Test leads with 4mm plugs
- ★ Battery and instruction manual included

Specification

AC volts	0-200-750Vac ± 1.2%
DC volts	0-200m-2-20-200-1000Vdc ± 0.8%
DC current	0-200μ-2m-20m-200m-2Adc ± 1.0%
Resistance	0-200-2k-20k-200k-2mΩ ± 0.8%
Signal Injector	50Hz square wave

5V peak to peak
Dims


126 × 70 × 24mm
Order Code

MX190

PRICE

£14.95

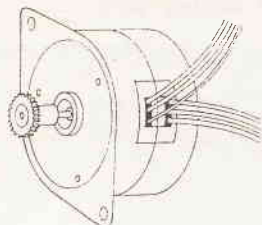PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT



Z5045D Superb little 12V stepper motor by Airpax. 35mm dia x 21mm deep with a 16 tooth 9.5mm dia gear wheel mounted on the 2mm dia spindle. Fixing centres 42mm. 7.5° 48 step. Supplied with data. 100+ DP 9.04; **Our Price £3.00**; 100+ 2.00



AC MILLIVOLTMETER
Y134A MV3002A

A highly sensitive and precise AC millivoltmeter used for measuring AC voltages in the range of 300µV to 100V between 5Hz and 1MHz. The output terminals allow this unit to be used as a wide-band high gain amplifier or pre-amplifier. Calibrated with AC volts and two decibel scales.

Voltmeter:
 Voltage range 300µ to 100Vac ±3%
 Frequency range 5Hz to 1MHz
 Input resistance 10MΩ
 Input capacitance Below 50pF

Amplifier:
 Output voltage 1V no load
 Frequency range 10Hz to 500kHz
 Output impedance 600Ω ±20%

Power 240Vac 50Hz
 Dims 142 x 195 x 205

PRICE £60.00

SURPLUS STRIPBOARD

Factory reject stripboard at approx half price!. Very minor blemishes - almost all totally usable. In sheets or packs as listed:

Z5294 Large sheet 390x205mm **£4.00**

Z5295 4 or 5 pieces, total approx 800 sq cms **£3.50**

Z5296 4 long strips, total approx 1800 sq cms **£7.95**


CABLEVISION CALAMITY !!!

Seems like Visionhire became a bit overstocked on their cablevision consoles - we've just purchased a quantity of these superb brand new units which contain some great electronics and as ever can offer them at an absolute BargainPrice!!

Two tone brown case (dimensions as shown) contains PCB 192x195mm with easily removed UHF modulator made by Labgear (Sound and Vision); video pre-amp; stabilized power supply and all the decoding circuitry (9 transistors and TBA673 chip).

On the front of the case is a cable/off air switch and 5 push buttons (4 channels and on/off mains switch). There are 4 cables coming from the rear (these alone are worth what we are asking for the whole thing!) - 2m mains lead, 1.5m 8 core screened cable with 9 pin plug, 2m video in lead with coax plug and 2m video out lead with coax socket. As you would expect from a company like Visionhire, everything is top quality. The case can easily be utilised for other purposes - the dark brown inserts on the front are both easily removable, if required. Please note the low price we are asking in no way reflects their true worth - they're taking up a lot of space, so we need to shift them quickly!!

Z8939 £6.95 100+ 3.50 1k+ 2.50.

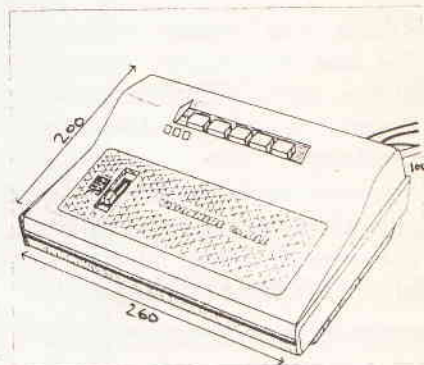


Z2171 24 character x 2 lines LCD by Optrex. High quality display with 192 character ROM; other characters can be displayed by generation in RAM. Other features include: EL type back light (details of high voltage generator supplied); cursor with control, blink character, scroll display, read and write display data, +5V and -7V supply with 150V AC required for backlight, data and power inputs by solder contacts on board, pin outs standard and compatible with other Optrex displays, extended temperature range (253 to 343°K), easily interfaced with either 4 or 8 bit uP's. Supplied complete with data. Characters are 5 x 7 dot arrays with separate cursor. 1 Character measures 3.2 x 6.0 mm. Display size 93 x 16mm. Module size 118 x 35mm. DP around £30.00. **Our Price £10.00**



Z8852D Keyboard. Superb brand new high quality keyboard with LCD displaying 1 line of 10 characters and a further line with various symbols. 100 keys, inc separate numeric keypad. Chips on board are 2x74HC05, 80C48. LCD + driver chip are easily removed. **Amazing low price - only £10.00**

HIGH QUALITY NICAD CHARGER

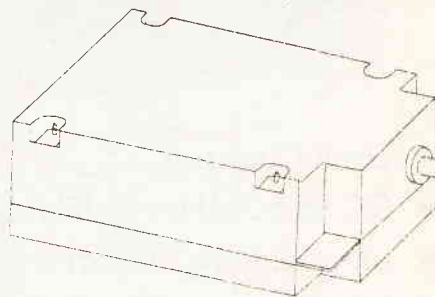

Z5136 Nicad switched mode battery charger for charging 6 x AA, C or D cells. 70mA 16 hour rate, 700mA 1.5 hour rate, 25mA float charge automatically switched in when battery reaches correct charge level. Outputs for fast and slow charging simultaneously if necessary, both on timers to prevent over charging. Fast charge set at 700mA, but internally adjustable. Slow charge set to 70mA. Both outputs switch to 25mA trickle charging after their respective periods of 1.5 hours and 16 hours. Supplied new with instructions and circuit diagram. Was originally supplied for charging cellphone batteries. **Price £12.95**

Optical Shaft Encoder



Z345 Optical Shaft Encoder. Made by sharp. Ideal wherever the position or speed of a rotating shaft needs to be known - ie machine tool control, robotics etc. Supplied with comprehensive data sheet. Size of module 46 x 33.5 x 20mm; size of disc 28mm dia. Bush with grub screw will take a 4mm dia shaft. Disc has 96 slots. DP £48.18. **Our Price £8.50**
 Data sheet available separately **30p**

Cadillac Coupe de Ville


Z8976 1967 model, white with blue interior. 2 door. 7¼ litre V8 engine. Auto gearbox, Power steering, brakes, seats, windows and aerial! Tilt and tele column. Original working AM/FM radio with front and rear speakers. Air conditioning. Original/Import documentation. Excellent chrome. Tinted glass. Recent new whitewall tyres and exhaust. Superb bodywork and low mileage. A true full size American car - all 19ft 4ins of it! **Our Price (1 only) £6995**



EASY-TO-USE

HITACHI

50MHz SCOPES

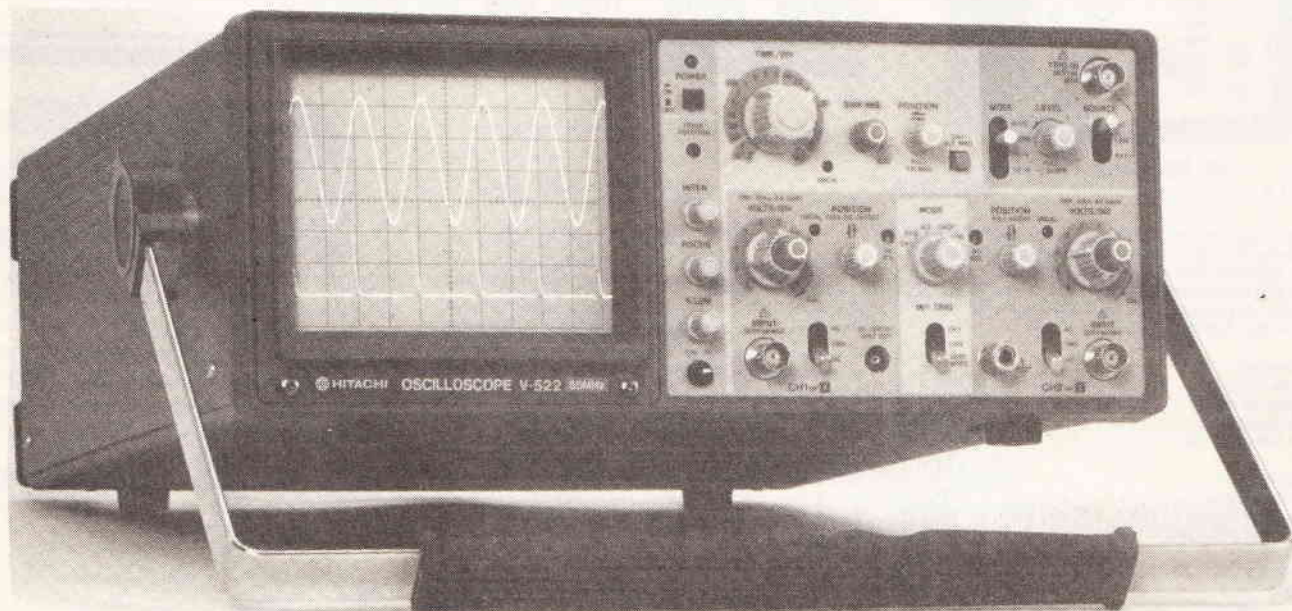

- ★ Dual Channel
- ★ DC to 50MHz - 3dB Bandwidth
- ★ Large 6 inch Screen with Internal Gratical
- ★ 1mV Vertical Sensitivity
- ★ Slim, Compact & Lightweight Design
- ★ DC Offset Function
- ★ Alternate Magnification
- ★ Vertical Trigger Mode
- ★ TV Sync Trigger Circuit

V522 DC-50MHz, 1mV/div, Dual Channel, DC offset function, Alternate Magnifier Function **£745.00**

25% OFF


and FREE next day delivery!

Limited Offer - Order Now!

£555.55

Price Includes VAT-free delivery UK mainland only

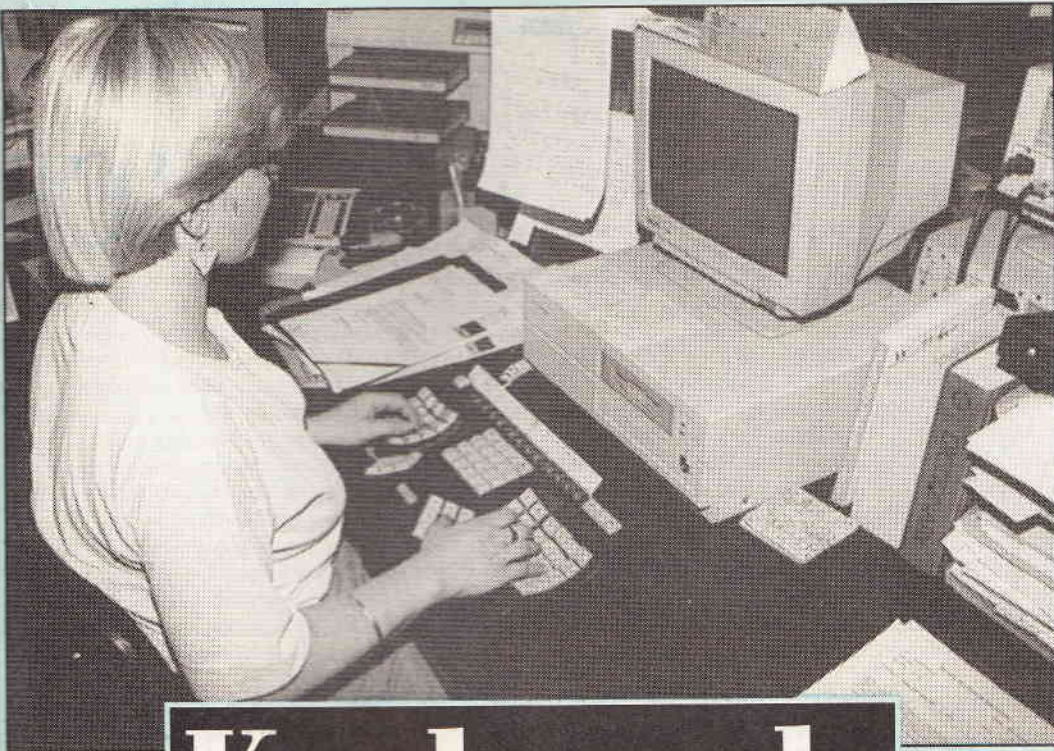PRICES IN BOLD TYPE INCLUDE VAT: PRICES IN LIGHT DO NOT



Keyboards

Speed, size and cost, the three dimensions of computing design become ever closer to their respective limits as years go by: the advent of the 80486 microprocessor conveys the reality that the limiting boundaries of computing power have almost been attained. New machines are favourably reviewed and it is assumed that each new device employs the height of technology and that the manufacturer has laboured intensively to ensure that it works efficiently. Most computer users are happy to continue regardless, knowing little of the insides of the machines which they operate. It would probably come as a shock therefore if they were to be told that the very instrument by which they communicate and command has been deliberately designed to be slow and to make progress difficult for the operator.

To discover the reasoning, a history lesson is required. Returning to the end of the last century when everyone was getting excited about the invention of the electric light bulb, American Christopher Scholes found that his innovative writing machine jammed and was frequently having to be repaired because the typewriter operators who used them were too good. His initial keyboard simply had the keys arranged in a purely alphabetical order. It was soon discovered that once the operator became familiar with the device the machine could not cope. In early manual typewriter machines, the typebar did not simply strike the ribbon and then bounce back instantly into position — instead it lingered somewhat and often became jammed by the next bar on its return. The result is familiar to anyone who has used a very old manual machine. The typebars became locked very tightly and inky fingers resulted after unjamming them. In his solution to the problem, Scholes separated the most commonly used letters so that they became more awkward to reach. The delay thus introduced gave sufficient time for the previous

letter to return and the new arrangement overcame the typebar jamming problem sufficiently for the typewriter to achieve commercial success.

The Qwerty format, inherited to this day, has never been successfully challenged because of the huge investment in typing skills. Outbreaks of operator stress problems, which only occasionally occurred with mechanical typewriters have in recent years demanded reflection. These problems, broadly grouped under the

An alternative to the typewriter keyboard by Stephen Waddington.

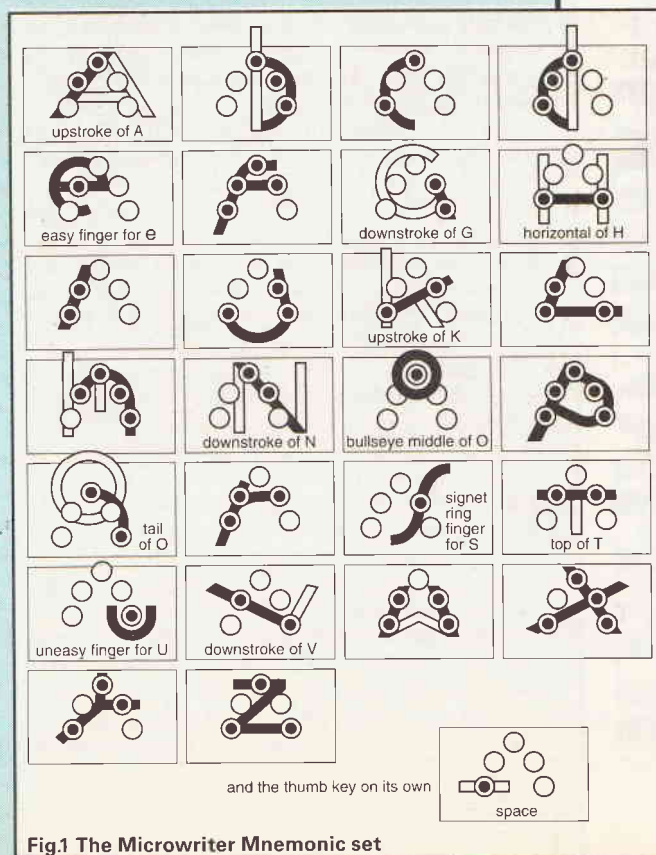


Fig.1 The Microwriter Mnemonic set

heading Repetitive Strain Injury (RSI), are associated with the over use of particular muscle groups and are to be found in a number of occupations. Writers' Cramp and Tennis Elbow are two of the names associated with this type of injury. The problem of RSI is faced by numerous professions according to Catherine Blinman of the Department of Medicine, at the University of Bristol. "Whenever the hand is placed under continual pressure or strain there is danger of injury. Such impairments occur in meat cutting and assembly line work, to hair dressers and concert pianists."

Technology has been blamed for an encyclopedia of medical problems varying from headaches to every kind of muscular ache and pain. The various ills experienced by computer operators are probably due to a wide variety of causes, including bad posture, poor lighting and occupational stress. Increasingly however keyboard operators discover that they are suffering continual aches, twinges and in some cases complete immobilisation of the hands.

Repetitive Strain Injury is now a recognised work disorder but that is of little consolation to anyone who is suffering from it. Numerous strains of RSI exist

bringing the most common used letters under the best fingers. When first launched, the keyboard caused great excitement and was thought to be a real threat to Qwerty with a number of manufactures considering its adoption.

The Meir keyboard splits the key array down the middle, spacing them somewhat, and angling the two halves so that the fingers extend in a straight line from the hand. Endeavouring to assist the transition from Qwerty to Meir, the Qwerty layout is retained so that the typist does not have to be retrained.

Perhaps more drastic are the keyboards with only five or ten keys arranged in a halo beneath the fingers of one of both hands. Pressing keys together in a chord provides the desired character. The established chord keyboard is the Microwriter developed by American Cy Enfield and marketed by Microwriter of Mitcham, Surrey. Though not produced as a personal computer or wordprocessor keyboard, the Microwriter has been adopted in a number of systems and boasts a distinguished but yet diminutive following. Specialised software allows for the serial connection to a PC compatible where upon the user can employ the Micro-

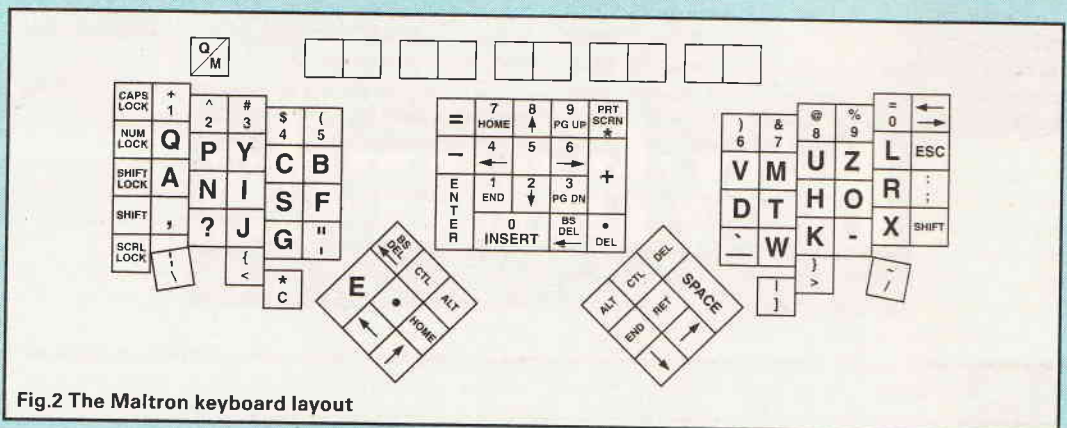


Fig.2 The Maltron keyboard layout

dependant on the suffers occupation. The classical form is called Tenosynovitis and is apparent by a sheathing of the tendons in the wrists and hands. It is caused by fast, small repetitious movements. No convincing cure has been found and much medical doubt surrounds the best mode of treatment. Prolonged rest seems to be the only effective answer. Symptoms when presented should be regarded seriously, prompting immediate action to change work patterns if permanent damage is to be avoided.

The major problem with Qwerty is that the use of common letters requires awkward finger movement. Attempt to type 'Electronics Today International' and you will see that a cross country assault of the keyboard results. The letter E requires the attention of the middle finger of the left hand, a wide sweep of the little finger of the right hand and the flexibility of a gymnast is then demanded to attend to the letter L and so the onslaught continues.

Keyface layout aside, consider for a moment the actual physical design of a keyboard — it has been proved on numerous occasions that simply swapping letters around is not enough to prevent RSI. Every flat keyboard breaks fundamental rules of ergonomic design by insisting that the user sits arms pointing inwards, palms outstretched, encouraging a hunched posture. The touch typist must then stretch his or her fingers to the near limits of movement to encompass the whole keyboard.

Since the turn of the century, a number of curious bids have been made in an effort to break the edge established by Qwerty. The first challenge was made in 1932, by an American professor, Dr August Dvorak. A complete arrangement of the keys was designed to

replace the Qwerty standard. The latest gadget from Microwriter is the Agenda, an electronic Filofax which includes an address book, a diary, a clock, numerous note pads, filing systems and a keyboard. A powerful wordprocessor allows the compilation of text documents and connection to a printer or a personal computer furthers its plausibility as a truly personal organiser.

The machine has never made the mass market — a small four line liquid crystal screen, an additional pad of keys covering every letter and number, together with the characteristic Microwriter chord keyboard result in a device which is small enough to slip inside a pocket. Surprisingly, the chord keyboard is incredibly easy to learn according to Engineering Consultant and Agenda user Alastair Wiggins, "It took a mere ten minutes to master the chord keyboard, the matter is assisted by the fact that the key mnemonics required to log an alphanumeric character coincide in form with the physical outline of the number or letter. Since there is no need to move the fingers to the keys, high speeds can be developed." Figure 1 provides illustration of the key arrangements and character mnemonics — such a design can only assist in the reduction of RSI problems.

Probably the most exciting and revolutionary new keyboard design is the Maltron, a creation of Systems Design Consultant Lillian Malt and Electronic Engineer Stephen Hobday. A split design, moulded in a three dimensional semi-circular bowl form, the Maltron comes as something of a culture shock to the previously unacquainted. Its functions are diverse, both left and right single handed boards cater for disabled people, whilst a two handed version seeks to replace the Qwerty keyboard in an effort to reduce problems of

RSI. The Maltron can be configured to suit any keyface format dependent on the wishes of the user, indeed many opt for the existing Qwerty layout. Lilian Malt has devised a standard format illustrated in Figure 2, a product of extensive research and analysis. The rudimentary concept of the Maltron is to minimise the extension of the fingers as they reach for keys in the upper and lower rows. The thumbs are allocated more work which Malt justifies with investigative work proving that the thumbs are apportioned more brain power than the fingers and should consequently be made to work harder.

Manufactured by husband and wife team Stephen and Pamela Hobday from the confines of their own home in East Molesley, Surrey the keyboards are made to order and cost between two and four hundred pounds. Customers are predominantly disabled or sufferers of RSI, though many newcomers to computing have opted for Maltron keyboards with great delight. A fellow colleague who took such an inverse vantage after being persuaded to replace her antique typewriter, now has a typing speed twice that of myself, a seasoned proponent of Qwerty.

Recommendations come from numerous sources and although the Maltron is a preventative measure and not a cure for RSI, sufferers have found their problems greatly reduced. So why has the Maltron never been adopted as a standard keyboard and why do we insist on continuing the finger calisthenics of Qwerty. Pamela Hobday provides explanation, "Current developments tend towards membrane keyboards which are very cheap and durable. To base the Maltron upon a membrane is impossible purely because of the dish formation. The moulding and casing is complex and therefore expensive to manufacture."

Potential manufacturers are apprehensive to take

up new ideas fearing user rejection of anything other than the standard Qwerty form. Apprehension and keyboard retraining will always be a problem, yet the benefits of increased productivity and fewer keyboard related injuries make the adoption of an alternative keyboard format essential.

Are You Sitting Comfortably?

For those with specific back problems ergonomically designed chairs are available which encourage the spine to remain in its natural position.

The operator's chair should be set so that the thighs are horizontal and feet are flat on the floor.

If the chair is too high to allow the feet to rest on the floor, the use of a foot rest is recommended.

The chair back rest should be adjusted to fit the natural curvature of the spine thus encouraging an upright posture.

The top of the screen should be slightly below eye level so preventing awkward neck movement.

The display should be adjusted to an angle which minimises glare from artificial light.

Set Contrast and Brightness controls to a comfortable level, adjusting several times during the day to account for changes in light level.

Break off from the keyboard and screen for a few minutes every hour if using intensively.

The use of vertical paper holders and Polaroid filters are beneficial to those who continuously use computers.

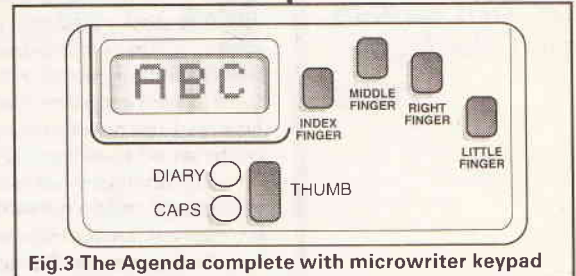


Fig.3 The Agenda complete with microwriter keypad

JUST LOOK AT WHAT'S AVAILABLE FROM BONEX

Balance Mixers

Batteries

Button Cells, Ni-cads, Battery Holders, Battery Eliminators, Ni-cad Chargers, Boxes
ABS Plastic, Die-cast, Hand-Held Enclosures, Bridge Rectifiers
Bulbs
Cables
Audio, BBC, Camcorder, Cassette/Calculator, Mains, Computer, IBM PC/AT, Serial, Monitor Extension, Parallel, Patch/Video Leads, Scart Cables, Serial Printer, Video/Audio Dubbing Kit,
Cable Ties
Capacitors

Ceramic Discs
Ceramic Feedthroughs, Chip, Electrolytics, Monolithics, Mylars, Polycarbonates, Polyethylene, Polyesters, Tantalum Beads,
Capacitors Variable
Film Dielectric Trimmers, Ceramic Trimmers,

CMOS Devices

Computer Accessories

Adaptors 9W to 25W, Data Switch Boxes, Gender Changers, RS232 - Patch Boxes, Null Modems, Plug in Testers, Surge Protectors, Surge Protector Plugs,
Connectors
Audio Adaptor/Plugs, Banana Connectors, Binding Posts BNCs, Centronics, D, D High Density, DC Power, DIL IC, DINs, IDCs, Edge, F, Jack 2.5mm, 3.5mm, 6.3mm, Mains, Microphones, Molex, N-Type, Phono, PL259, RF Adaptors, Scart, TNC, Terminal Strips, TV, XLR,
Crocodile Clips
Crystals
Desolder Pumps
Diodes
Plastic IN4000 / IN5400, Toko Varicaps
Signal Diodes, Zener, BZYs and BZXs,

Drills

Bits and Burrs, Expo, Pin Chucks, Power Supplies, Saws and Slitting Discs,

Fans

Feet, Rubber

Ferrites

Filters

FM Ceramics, Mechanical IFs, Ceramic Resonators, Crystal, Helicals, NTSC / PAL, Pilot Tone, Quadrature Detector, Satellite TV, Video,

Fuses

Grommets

Howes Kits

Heatsinks

Inductors Fixed

Inductors Moulded

Inductors Surface Mount

Inductors Variable

Infra-red Source Sensor

Insulating Tape

Integrated Circuits

CMOS, Epmos, Linears, Memory, TTL,

Kits and Modules

L.E.D.s, 3mm and 5mm

Light Dep Resistors

Loudspeakers

Microphone Inserts

Multimeters

Neon Indicators

Nuts and Bolts

Opto Switches

Optoisolators

P.C.B.s

Copper Clad, Etch Resist

Transfers, Photo Resist,

Pins, Proto-type,

Polishing Mops

Potentiometers

Control Pots, 16mm, 24mm,

Pre-sets, Horizontal/Vertical

Trimmer Pots,

Power Supplies

Relays

Resistors

Carbon Film, Metal Oxide,

Wirewound,

Screening Cans

Semi's Mount Kits

Solder

Soldering Irons

Switches

DIL, Key, Microswitches,

Push, Rotary, Slide, Toggles,

Test Leads

Test Probes

Tools

Crimping, Cutters,

Files, Insertion,

Reamers,

Screwdrivers,

Strip Board, Trimtools,

Toroid Cores

Thyristors

Transformers, Mains

Transistors

Audio Power,

Darlington, F.E.T.s

GaAsFETs,

Low Power RF,

Microwave,

MosFETs,

Power RF,

Small Signal,

VMOS,

Trace

TTL

Video Modulators

Voltage Regulators

Wire

Enamelled Copper,

Tin Plated,

Silver Plated,

Zero Insert Force

Sockets



12 Elder way
Langley Business Park
Slough
Berkshire SL3 6EP. Telephone : 0753 549502 Fax : 0753 543812

VISIT OUR STAND 21- 22 AT
SANDOWN RALLY 28TH- 29TH MARCH

Auto Car Lights Controller

Take away the worry of forgotten lights with this project by Colin Meikle.

Electronic gadgets are becoming very popular in modern cars. Many of these gadgets are of little practical use, however some are designed to give added safety or to make driving more convenient. One such device which would do both is automatic lights, but as far as I am aware there are no such devices available. This is somewhat surprising since it would greatly add to road safety.

The circuit described here, does not replace the conventional light switch but works in parallel with it, therefore allowing the conventional switch to be used if desired. The circuit was originally designed to be a back-up but worked so well the conventional switch is never really required. The completed unit is reasonably small and only requires a few connections to the cars existing wiring. The light sensing is done by a Light Dependent Resistor (LDR), this can be mounted either inside or outside the car, e.g., in the corner of the windscreen or in-between the front grill. There are also connections for a switch to disable the circuit if this is required.

The circuit has two (variable) predefined levels a 'light' threshold and a 'dark' threshold. When the ambient light level falls below the 'dark' threshold the car's dipped headlights are turned on (if properly set-up, the circuit will turn the lights on during foggy or rainy conditions). When the ambient light level increases above the 'light'

threshold the car's lights are turned off. If the circuit is allowed to control the lights they cannot be left on since the unit works from the ignition. One of the most important requirements of this circuit is that it does not respond to false conditions e.g., overhead lights, oncoming traffic or passing under bridges.

The circuit's ability to reject false signals is achieved in various ways. By using two threshold levels (i.e., the 'dark' and 'light' thresholds) rather than a single threshold, the light level must change a significant amount before the circuit will change state. This stops small fluctuations in the light level affecting the circuit. However during normal driving conditions there are many instances where the light level will vary by a large amount over short periods of time, for example passing under a bridge or past a bright overhead light. These conditions do not affect the circuit because when one of the thresholds is crossed (e.g., when it has become dark) the light level must remain almost constant (i.e. it must remain dark) for a period of time (approximately 10 seconds), before the circuit will change state. Hence changes in light level over short periods in time do not affect the unit.

Differences Between Lighting Circuits

The circuit diagram shows two possible ways to connect

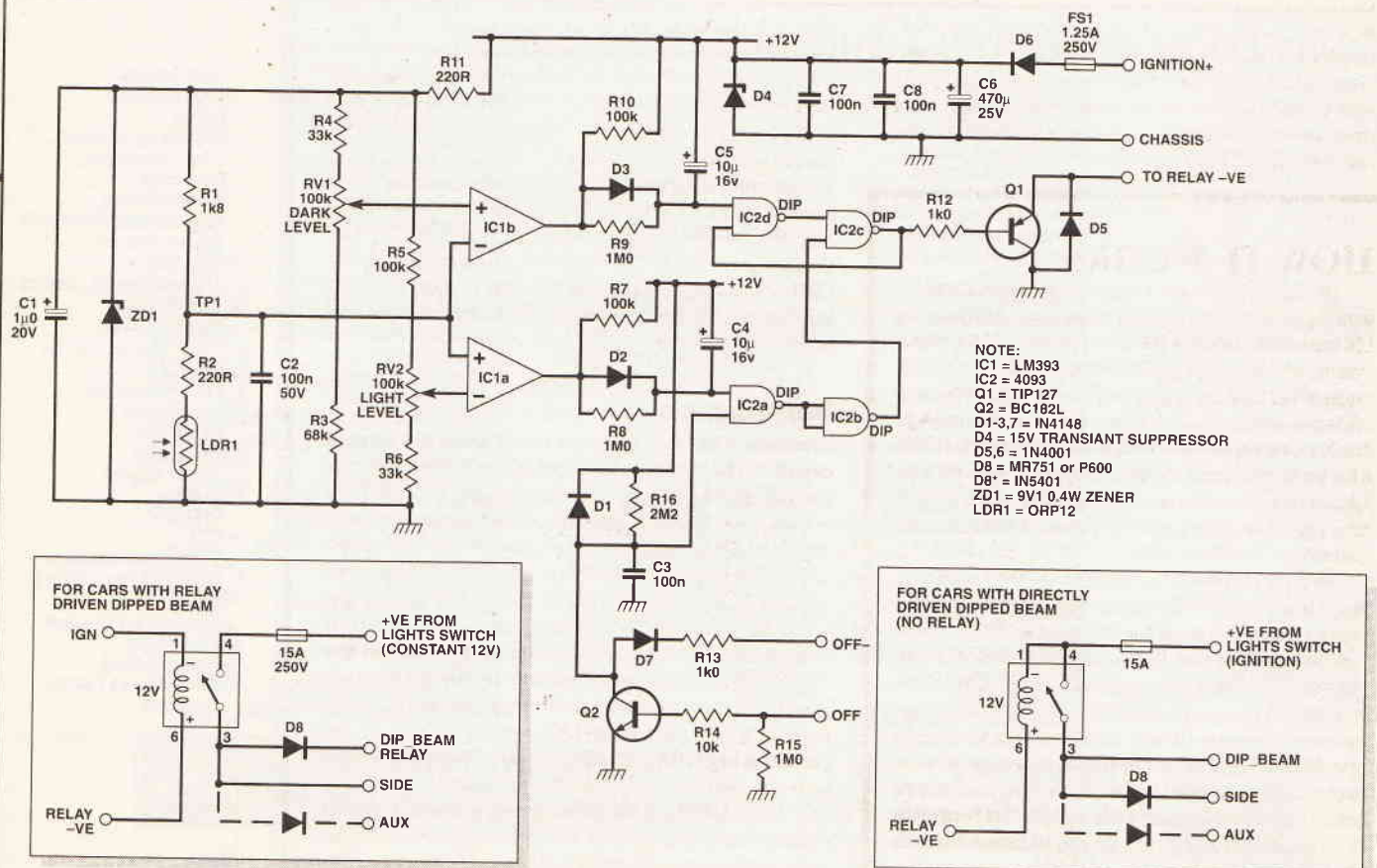


Fig.1 Circuit of Auto-lights controller

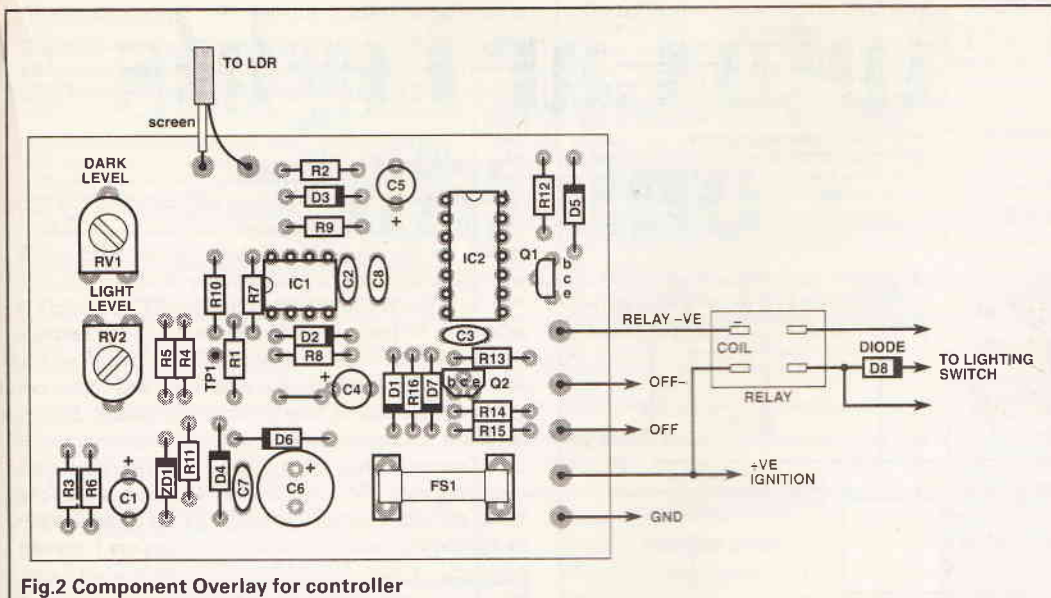


Fig.2 Component Overlay for controller

the circuit to the car wiring. For cars with directly driven lights (i.e. the car's lighting switch switches the dipped beam directly and does not switch a relay), the relay RLY1 drives the dipped beam and diode D8 drives the side and auxiliary lights via the relay. The diode is required to keep the car's side light and dipped beam circuits separate (otherwise the dipped beam would come on when the side lights were activated manually). However some cars dipped beam lights are not driven directly but are driven via a relay. In this case, although the previous set up would work, it would be better to use the diode to drive the car's dipped beam relay and use the circuit's relay to drive the side lights. (If this is the case a smaller relay and diode could be used as the current through each is much smaller). A second diode is shown in the circuit diagram (dotted), this may be required where the auxiliary lights are on a separate circuit. If this is the case this diode should be connected to the auxiliary circuit. This diode could also be used to drive an additional indicator lamp to show the circuit has turned the lights on.

HOW IT WORKS

The circuit diagram is given in Figure 1 - its operation is straight forward. The LDR and R1 form a potential divider; as the light falling on the LDR decreases the voltage at TP1 increases (since the LDR resistance increases with decreasing light). This voltage is compared, by IC1, with two predefined thresholds set by RV1 and RV2. When it is light the output of IC1a is low which causes out-of-the-latch, formed by IC2d&c to be high, thus Q1 and the relay are in the off state. When it is dark the output of IC1b is low and the latch is reset, causing Q1, and the relay which drives the lights to turn on. When the ambient light level is in-between these levels both outputs of the comparator are high and the latch remains in its previous state.

The circuitry in-between the comparator and the latch, ensures that the light level is constant for approximately 10 seconds before the latch is triggered. Assume it is light going on dark, when the threshold level set by RV1 is crossed, the output of IC1b will go low. This will cause C5 to discharge via R9, if it remains dark the input of IC2d will go low after 10 seconds and hence the latch will be triggered. However if there are any interruptions in the 'darkness' C5 will be charged rapidly via R10 hence the input of IC2d will not go low until the darkness has remained above the dark threshold for 10 seconds. When the circuit is initially powered up the latch is reset by R16 and C3 (hence the relay is turned off), so the car can be started with the lights off. (If it is dark, the lights will come on 10 seconds after the ignition is turned on).

Construction And Testing

The layout for the PCB is shown in Figure 2. There should be no problems constructing the PCB, just be careful that all the polarized components are correctly orientated. If IC sockets are used, good quality ones should be used, as poor quality sockets may give problems in years to come with the harsh environment of the car. Testing and initial setting up is best done on the bench rather than in the car. Firstly connect temporary wires to the LDR and relay, next connect up a 12V supply.

With the LDR positioned under a light or in daylight the voltage at TP1 should be approximately 2.0V (it will be slightly higher under artificial light), adjust RV2 so it is just above the voltage at TP1. Now put the LDR in the shade and measure the voltage at TP1, it should be a few volts higher. Adjust RV1 so the voltage at its wiper is slightly below the voltage at TP1. Now position the LDR in the light and allow to settle for 30 seconds, the relay should now be off. Put the LDR in the dark, the relay should turn on after 10-15 seconds. When returned to the light, the relay should take 10-15 seconds to turn back off. Two off lines are provided - one positively and one negatively activated. To test these, cover the LDR so the relay comes on. Touch the OFF wire to ground or the OFF wire to 12V, the relay should go off. Before final fitting to the car give the board a good coat of PCB lacquer to protect it.

Installation

Installation will vary from car to car since the lighting circuit will be different from car to car. Figure 3 shows the two most common lighting circuits and the connections necessary to the completed circuit. The best way to establish the exact wiring layout is to consult the relevant manual. However, it is normally quite easy to determine how the car's lights are connected using a meter to 'buzz out' the lighting switch connections. If you are unsure if a relay is being used to switch the dipped beam, check by measuring the current through the dipped beam contacts of the lighting switch, if the current is low (less than 1A), a relay is used. If the current is high (8A), no relay is used. The gauge of the wire will also give you a good indication.

If diode D8 is driving the dipped beam (cars with a dipped beam relay) sleeve all the connections so there is no chance of short circuits. If diode D8 is driving the side lights, it will have to be mounted on a heatsink. The heatsink can be made from a piece of PCB as

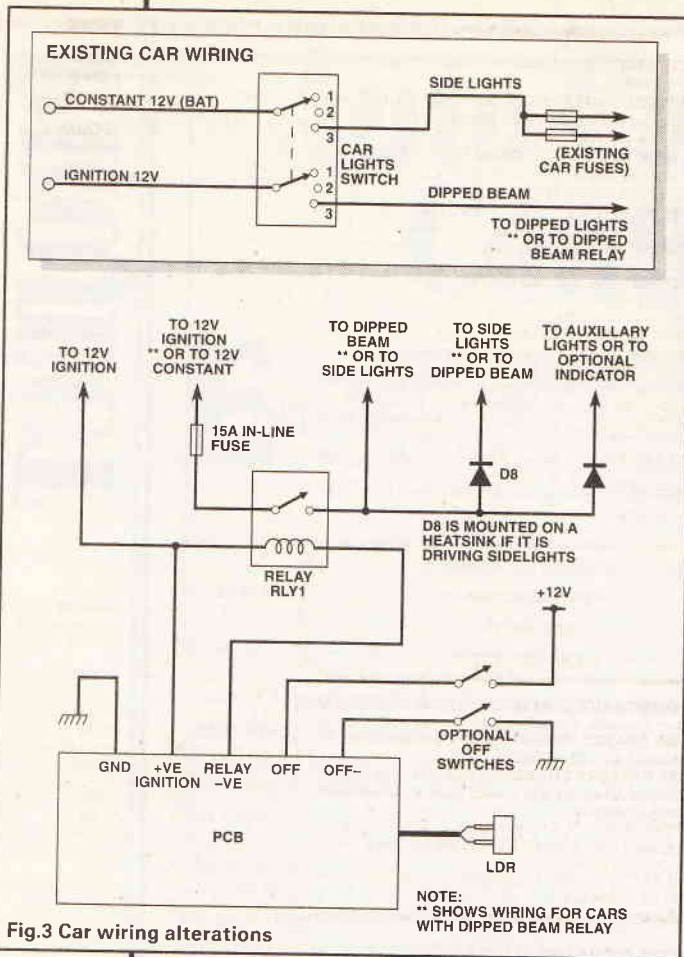


Fig.3 Car wiring alterations

shown in Figure 4, this can then be mounted inside the box, ensuring nothing will short out against the heatsink. When you have established which wire is which connect up the circuit as shown in Figure 2, 'snap-lock' type connectors make connections to existing wiring simple and neat. Ensuring you position the box where you are able to adjust the pots — if necessary put it in a temporary position until the settings are final. I found the best place to position the LDR was in the corner of the windscreen, when connecting the LDR use screened cable to limit any noise pick-up. If mounting the LDR outside the car, e.g. in between the grill, ensure the connections are protected

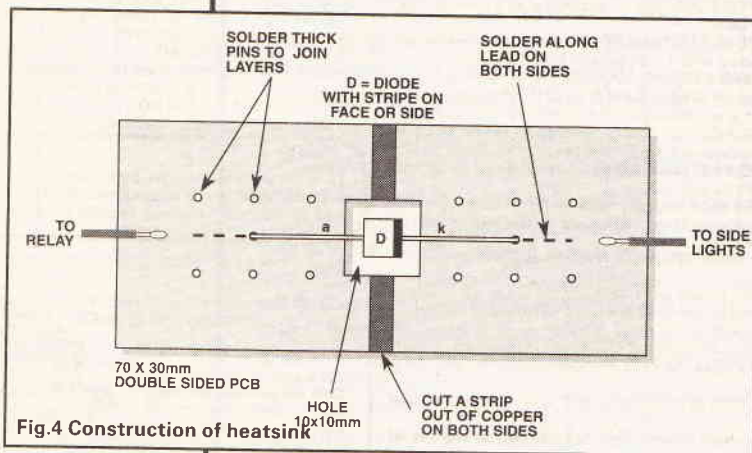


Fig.4 Construction of heatsink

from moisture. (One way is put the LDR in a piece of plastic tubing and fill the end with the wire with silicon or epoxy resin.)

With the LDR in place the light and dark thresholds can be set in the same way as done during testing. When it is just light the voltage at the wiper of RV2 should be set to the voltage at TP1. When it is just getting dark (not dark!) the voltage at the wiper of RV1

should be set to the voltage at TP1. The connections to the Off switch(es) is optional, there is no real need for an off switch. (Both polarities of signal were provided for convenience, only one is required to turn the lights off.)

Possible Problems

D8 will get warm during normal operation but if it gets very hot or disintegrates, the chances are you have mixed up the dipped and sidelight connections or wrongly assumed that a relay drives the dipped beam.

If, when setting the light threshold, you find the voltage at TP1 is higher than the maximum obtainable from RV2 then increase the value of R1. When setting the dark threshold, if you find that the minimum voltage from RV1 is greater than the voltage at TP1 decrease the value of R1. If you find that the dipped beam stays on when the full beam lights are turned on connect a wire from one of the full beam connections to the off signal of the unit. (note : it is normal for the dipped beam to stay on when the lights are flashed).

PARTS LIST

RESISTORS (all 0.25W 5%)

R1	1.8k
R2	220R
R3	68k
R4	33k
R5	100k
R6	33k
R7	100k
R8	1M
R9	1M
R10	100k
R11	220R
R12	1k
R13	1k
R14	10k
R15	1M
R16	2M2
RV1	100k
RV2	100k

CAPACITORS

C1	1 μ 16V Electrolytic or Tantalum
C2,3,7,8	100n 50V Ceramic (5mm pitch)
C4,5	10 μ 25V Electrolytic (radial)
C6	470 μ 25V Electrolytic (radial)

SEMICONDUCTORS

IC1	LM393 Dual Comparator
IC2	4093 CMOS Schmitt Trigger
Q1	TIP127 PNP Darlington
Q2	BC182L NPN G.P.

TRANSISTOR

D1,2,3,7	1N4148 G.P. Silicon Diode
D4	15V Transient Suppressor
D8	MR751 or 6A Power Diode P600
*D8	1N5401 3A Diode (cars with dipped beam relay)
D5,6	1N4001 1A Diode
ZD1	9V1 0.4W Zener Diode

MISCELLANEOUS

LDR	ORP12 Light Dependent Resistor
RLY1	15A (or Greater) SPST Relay (Automotive Type)
F1	1A 20MM Fuse

Set of 20mm Fuseclips
15A In-line Fuse with Holder
Suitable box 80x60x50mm (Maplin YN37S)

* See text



AMSTRAD PORTABLE PC'S FROM £149 (PPC1512SD), £179 (PPC1512DD), £179 (PPC1640SD), £209 (PPC1640DD). MODEMS £30 EXTRA. NO MANUALS OR PSU.

HIGH POWER CAR SPEAKERS. Stereo pair output 100w each. 4ohm impedance and consisting of 6 1/2" woofer 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00 Order ref 30P7R.

2KV 500 WATT TRANSFORMERS Suitable for high voltage experiments or as a spare for a microwave oven etc. 250v AC input. Now only £4.00 ref 4P157

MICROWAVE CONTROL PANEL. Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. Now only £4.00 ref 4P151.

FIBRE OPTIC CABLE. Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R

12V SOLAR CELL. 200mA output ideal for trickle charging etc. 300 mm square. Our price £15.00 ref 15P42R

PASSIVE INFRA-RED MOTION SENSOR. Complete with daylight sensor, adjustable lights on timer (8 secs -15 mins), 50' range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. Now only £19.00 ref 19P29

Pack of two PAR38 bulbs for above unit £12.00 ref 12P43R

VIDEO SENDER UNIT Transmit both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range! (tune TV to a spare channel). 12V DC op. £15.00 ref 15P39R Suitable mains adaptor £5.00 ref 5P191R

FM TRANSMITTER housed in a standard working 13A adapter (bug is mains driven). £26.00 ref 26P2R

MINATURE RADIO TRANSCEIVERS A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x155mm. Complete with cases. £30.00 ref 30P12R

FM CORDLESS MICROPHONE. Small hand held unit with a 500' range! 2 transmit power levels reqs PP3 battery. Tuneable to any FM receiver. Our price £15 ref 15P42AR

12 BAND COMMUNICATIONS RECEIVER. 9 short bands, FM, AM and LW DX/locals with, tuning 'eye' mains or battery. Complete with shoulder strap and mains lead. Now only £19.00!! REF 19P14R.

CAR STEREO AND FM RADIO Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than wow and flutter less than .35%. Neg earth. £25.00 ref 25P21R.

LOW COST WALKIE TALKIES. Pair of battery operated units with a range of about 200'. Our price £8.00 a pair ref 8P50R

7 CHANNEL GRAPHIC EQUALIZER plus a 60 watt power amp! 20-21KHz 4-8R 12-14V DC negative earth. Cased £25 ref 25P14R

NICAD BATTERIES. Brand new top quality. 4 x AA's £4.00 ref 4P44R. 2 x C's £4.00 ref 4P73R, 4 x D's £9.00 ref 5P12R, 1 x PP3 £6.00 ref 6P35R

TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE. The ultimate equivalents book. Latest edition £20.00 ref 20P32R.

CABLE TIES. 142mm x 3.2mm white nylon pack of 100 £3.00 ref 3P104R. Bumper pack of 1,000 ties £14.00 ref 14P6R

1992 CATALOGUE AVAILABLE NOW
IF YOU DO NOT HAVE A COPY PLEASE REQUEST ONE WHEN ORDERING OR SEND US A "X9" SAE FOR A FREE COPY.

GEIGER COUNTER KIT. Complete with tube PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R

FM BUG KIT. New design with PCB embedded coil. Transmits to any FM radio. 9v battery req'd. £5.00 ref 5P158R

FM BUG Built and tested superior 9v operation. £14.00 ref 14P3R

COMPOSITE VIDEO KITS. These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R.

SINCLAIR C5 MOTORS 12v 29A (full load) 3300 rpm 6"x4" 1/4" O/P shaft. New. £20.00 ref 20P22R.

As above but with fitted 4 to 1 inline reduction box (800rpm) and toothed nylon belt drive cog £40.00 ref 40P8R.

SINCLAIR C5 WHEELS 13" or 16" dia including treaded tyre and inner tube. Wheels are black, spoked one piece poly carbonate. 13" wheel £6.00 ref 6P20R, 16" wheel £6.00 ref 6P21R.

ELECTRONIC SPEED CONTROL KIT for c5 motor. PCB and all components to build a speed controller (0-95% of speed). Uses pulse width modulation. £17.00 ref 17P3R.

SOLAR POWERED NICAD CHARGER. Charges 4 AA nicads in 8 hours. Brand new and cased £6.00 ref 6P3R.

12 VOLT BRUSHLESS FAN 1/2" square brand new ideal for boat, car, caravan etc. £5.00 ref 5P20B.

ACORN DATA RECORDER ALF503 Made for BBC computer but suitable for others. Includes mains adaptor, leads and book. £15.00 ref 15P43R

VIDEO TAPES. Three hour superior quality tapes made under licence from the famous JVC company. Pack of 5 tapes New low price £8.00 ref 8P161

PHILIPS LASER. 2MW HELIUM NEON LASER TUBE. BRAND NEW FULL SPEC £40.00. REF 40P10R. MAINS POWER SUPPLY KIT £20.00. REF 20P33R. READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4R.

12 TO 220V INVERTER KIT As supplied it will handle up to about 15w at 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17R. Larger transformer £12.00 ref 12P41R.

VERO EASI WIRE PROTOTYPING SYSTEM Ideal for designing projects on etc. Complete with tools, wire and reusable board. New low bargain price only £2.00 ref 82P1

HIGH RESOLUTION 12" AMBER MONITOR 12v 1.5A Hercules compatible (TTL input) new and cased £22.00 ref 22P2R

VGA PAPER WHITE MONO monitors new and cased 240v AC. £59.00 ref 59P4R

25 WATT STEREO AMPLIFIER. c. STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P89R (Circuit dia included).

BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10 £4.00 REF 4P92R, PACK OF 100 £30.00 REF 30P16R

FRESNEL MAGNIFYING LENS 83 x 52mm £1.00 ref BD827R.

ALARM TRANSMITTERS. No data available but nicely made complex radio transmitters 9v operation. £4.00 each ref 4P81R.

12V 19A TRANSFORMER. Ex equipment but otherwise ok. Our price £20.00

GX4000 COMPUTERS. Customer returned games machines complete with plug in game, joysticks and power supply. Retail price is almost £100. Ours is £12.00 ref B12P1

ULTRASONIC ALARM SYSTEM. Once again in stock these units consist of a detector that plugs into a 13A socket in the area to protect. The receiver plugs into a 13A socket anywhere else on the same supply. Ideal for protecting garages, sheds etc. Complete system £25.00 ref B25P1 additional detectors £11.00 ref B11P1

IBM XT KEYBOARDS. Brand new 86 key keyboards £5.00 ref 5P612

IBM AT KEYBOARDS Brand new 86 key keyboards £15.00 ref 15P612

386 MOTHER BOARDS. Customer returned units without a cpu fitted. £22.00 ref A22P1

COLOUR MONITORS

AMSTRAD CTM644

RGB INPUT

£75.00 REF A75P1

286 MOTHER BOARDS. Brand new but customer returns so may need attention. Complete with technical manual £20.00 ref A20P2

286 MOTHER BOARDS. Brand new and tested complete with technical manual. £49.00 ref A49P1

UNIVERSAL BATTERY CHARGER. Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £6.00 ref 6P36R.

IN CAR POWER SUPPLY. Plugs into cigar socket and gives 3.4, 5, 6, 7, 5.9, and 12v outputs at 800mA. Complete with universal solder plug. £5.00 ref 5P167R.

RESISTOR PACK. 10 x 50 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170R.

CAPACITOR PACK. 10 x 100 values (100 capacitors) all 100V 5% tolerance. £5.00 ref 5P170R.

MIRACOM WS4000 MODEMS

V21/23

AT COMAND SET

AUTODIAL/AUTOANSWER

FULL SOFTWARE CONTROL

-tone AND PULSE DIALLING

£29

WASHING MACHINE PUMP. Mains operated new pump. Not self priming. £5.00 ref 5P18R.

IBM PRINTER LEAD. (D25 to centronics plug) 2 metre parallel. £5.00 ref 5P186R.

COPPER CLAD STRIP BOARD 17" x 4" of .1" pitch "vero" board. £4.00 a sheet ref 4P62R or 2 sheets for £7.00 ref 7P22R.

STRIP BOARD CUTTING TOOL. £2.00 ref 2P352R.

50 METRES OF MAINS CABLE £3.00 2 core black precut in convenient 2 m lengths. Ideal for repairs and projects. ref 3P91R

4 CORE SCREENED AUDIO CABLE 24 METRES £2.00. Precut into convenient 1.2 m lengths. Ref 2P365R

TWEETERS 2 1/4" DIA 8 ohm mounted on a smart metal plate for easy fixing £2.00 ref 2P366R

COMPUTER MICE Originally made for Future PC's but can be adapted for other machines. Swiss made £8.00 ref 8P57R. Atari ST conversion kit £2.00 ref 2P362R.

6 1/2" 20 WATT SPEAKER Built in tweeter 4 ohm £5.00 ref 5P205R

ADJUSTABLE SPEAKER BRACKETS Ideal for mounting speakers on internal or external corners, uneven surfaces etc. 2 for £5.00 ref 5P207R

WINDUP SOLAR POWERED RADIO! FM/AM radio takes rechargeable batteries complete with hand charger and solar panel 14P200R

240 WATT RMS AMP KIT Stereo 30-0-30 psu required £40.00 ref 40P200R

300 WATT RMS MONO AMP KIT £55.00 Psu required ref 55P200

ALARM PIR SENSORS Standard 12v alarm type sensor will interface to most alarm panels. £16.00 ref 16P200

ALARM PANELS 2 zone cased keypad entry, entry exit time delay etc. £18.00 ref 18P200

MODEMS FOR THREE POUNDS!!
Fully cased UK modems designed for dial up system (PSTN) no data or info but only £3.00 ref 3P145R

TELEPHONE HANDSETS
Bargain pack of 10 brand new handsets with mic and speaker only £3.00 ref 3P146R

BARGAIN STRIPPERS
Computer keyboards. Loads of switches and components excellent value at £1.00 ref CD40R

DATA RECORDERS
Customer returned mains battery units built in mic ideal for Computer or general purpose audio use. Price is £4.00 ref 4P100R

SPECTRUM JOYSTICK INTERFACE
Plugs into 48K Joystick to provide a standard Atari type joystick port. Our price £4.00 ref 4P101R

ATARI JOYSTICKS
Ok for use with the above interface, our price £4.00 ref 4P102R

BENCH POWER SUPPLIES
Superbly made fully cased (metal) giving 12v at 2A plus a 6V supply. Fused and short circuit protected. For sale at less than the cost of the case! Our price is £4.00 ref 4P103R

SPEAKER WIRE
Brown twin core insulated cable 100 feet for £2.00 REF 2P79R

MAINS FANS
Brand new 5" x 3" complete with mounting plate quite powerful and quite. Our price £1.00 ref CD41R

DISC DRIVES
Customer returned units mixed capacities (up to 1.44M) We have not sorted these so you just get the next one on the shelf. Price is only £7.00 ref 7P1R (worth it even as a stripper)

HEX KEYBOARDS
Brand new units approx 5" x 3" only £1.00 each ref CD42R

PROJECT BOX
51/2" x 31/2" x 1" black ABS with screw on lid. £1.00 ref CD43R

SCART TO SCART LEADS
Bargain price leads at 2 for £3.00 ref 3P147R

SCART TO D TYPE LEADS
Standard Scart on one end, Hi density D type on the other. Pack of ten leads only £7.00 ref 7P2R

OZONE FRIENDLY LATEX
250ml bottle of liquid rubber sets in 2 hours. Ideal for mounting PCB's fixing wires etc. £2.00 each ref 2P379R

QUICK SHOTS
Standard Atari compatible hand controller (same as joysticks) our price is 2 for £2.00 ref 2P380R

VIEWDATA SYSTEMS
Brand new units made by TANDATA complete with 1200/75 built in modem infra red remote controlled qwerty keyboard BT approved Prestel compatible, Centronics printer port RGB colour and composite output (works with ordinary television) complete with power supply and fully cased. Our price is only £20.00 ref 20P1R

AC STEPDOWN CONVERTOR
Cased units that convert 240v to 110v 3" x 2" with mains input lead and 2 pin American output socket (suitable for resistive loads only) our price £2.00 ref 2P381R

SPECTRUM +3 LIGHT GUN PACK
complete with software and instructions £8.00 ref 8P58R

CURLY CABLE
Extends from 8" to 6 feet! D connector on one end, spade connectors on the other ideal for joysticks etc (6 core) £1.00 each ref CD44R

COMPUTER JOYSTICK BARGAIN
Pack of 2 joysticks only £2.00 ref 2P382R

BUGGING TAPE RECORDER
Small hand held cassette recorders that only operate when there is sound then turn off 6 seconds after so you could leave it in a room all day and just record any thing that was said. Price is £20.00 ref 20P3R

IEC MAINS LEADS
Complete with 13A plug our price is only £3.00 for TWO! ref 3P148R

COMPUTER SOFTWARE BARGAIN
10 cassettes with games for commodore 64, Spectrum etc. Our bargain price one pound! ref CD44R

NEW SOLAR ENERGY KIT
Contains 8 solar cells, motor, tools, fan etc plus educational booklet. Ideal for the budding enthusiast! Price is £12.00 ref 12P2R

POTENTIOMETER PACK NO 1
30 pots for £3.00! ideal for projects etc. Ref CD45R

286 AT PC
286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139 REF 139P1 (no i/o cards or drives included) Some metal work req'd phone for details.

35MM CAMERAS Customer returned units with built in flash and 28mm lens 2 for £8.00 ref 8P200

STEAM ENGINE Standard Mamod 1332 engine complete with boiler piston etc £30 ref 30P200

TALKING CLOCK
LCD display, alarm, battery operated. Clock will announce the time at the push of a button and when the alarm is due. The alarm is switcheable from voice to a cock crowing £14.00 ref 14P200R

HANDHELD TONE DIALLERS
Small units that are designed to hold over the mouth piece of a telephone to send MF dialling tones. Ideal for the remote control of answer machines. £5.00 ref 5P209R

COMMODORE 64 MICRODRIVE SYSTEM
Complete cased brand new drives with cartridge and software 10 times faster than tape machines works with any Commodore 64 setup. The original price for these was £49.00 but we can offer them to you at only £25.00! Ref 25P1R

USED SCART PLUGS
Pack of 10 plugs suitable for making up leads only £5.00 ref 5P209R

C CELL SOLAR CHARGER
Same style as our 4 x AA charger but holds 2 C cells. Fully cased with flip top lid. Our price £6.00 ref 6P79R



BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX
BN3 5QT TELEPHONE 0273 203500
MAIL ORDER TERMS: CASH PO OR CHEQUE
WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY

NEXT DAY DELIVERY £5.00

FX 0273 23077



IN SUSSEX? CALL IN AND SEE US!

Solar Powered Tech-Tips

A selection of easy-to-build 'sunshine' circuits by Robert Penfold.

Solar cells can be based on something as basic as two sheets of dissimilar metal, or something more high-tech such as silicon junctions. Either way, it is important to realise that the power provided by solar cells is pretty small. At least, it is unless you are going to use a large array of cells and will always be blessed with strong sunlight. Although you may find some fairly small cells advertised as having quite impressive output powers, it is important to realise that these output powers will almost certainly assume a light level that is roughly equivalent to strong sunlight. The power available on a dull day will only be a small fraction of this. The maximum output under normal artificial lighting (which tends to be much weaker than you might think) tends to be very low indeed. In fact with some cells their output level under typical artificial lighting is such that you need a sensitive multimeter in order to measure it.

In my experience, the ideal circuit for solar operation is one that requires no current, or something very close to it! A solar cell can be regarded as a voltage source in series with a resistor. If the light level is varied, the voltage source provides an almost constant output

All the circuits described here are designed for use with the Solems solar panel type 14/096/048. This measures 96mm × 48mm, and has a rating of 8V at 100µA. This is a good compromise between small physical size and reasonably high output power. Note that these output ratings do not assume that the cell is used at the equator on a cloudless day, and at midday! Under bright conditions this cell can actually produce appreciably higher output currents at this voltage. These cells work well under artificial lighting incidentally, although much lighting of this type is inadequate to produce the full rated output. The circuits may well work satisfactorily with other solar cell arrays which offer similar output figures, but I have not tried any other cells, and obviously can not guarantee that satisfactory results will be obtained using an alternative.

The sensitive surface of the solar panel is the purple coloured one. The connections are made to the underside (the green side), and there are metal electrodes running the full width of the panel, one at each end. The polarity is clearly marked with '+' and '-' signs. I found no difficulty in making soldered connections to the electrodes, but it is probably best to ensure that the joints are completed speedily. This will avoid any damage to the panel caused by excessive heating from the soldering iron. The panel is based on a sheet of glass, and it should therefore be treated with due care. In use it should be mounted on a panel of the case so that it is physically well supported.

Solar Powered Radio

A radio receiver is an obvious candidate for solar operation, but the power required by an average 'tranny', is rather more than can be supplied by a small solar cell array. There are actually solar batteries that can do the job, but only with the aid of reflectors to increase the effective cell size, and only under reasonably bright sunlight. However, a small radio driving an earphone can run on quite low voltages and currents, and will work well enough even on dull days, or under most artificial lighting. A well known radio magazine featured a project of this type about twenty five years ago and suggested that it might make a good pocket radio — the idea was later withdrawn!

The circuit of the solar powered radio is shown in Figure 1, and is basically just a conventional ZN414 design. L1 is a medium wave ferrite aerial. I used an aerial coil and ferrite rod from Cirkit, but any commercial ferrite aerial should be satisfactory. Most aerials have a small coupling winding, but this is not required in this case. Either remove the coupling winding or just ignore it (leaving it in place does not seem to have an adverse affect on performance). A home constructed aerial can consist of 70 turns of about 32 swg tinned copper wire wound well towards one end of a 10mm diameter ferrite rod about 100mm or more in length. The winding should be reasonably neat with closely spaced turns in a single layer, and all running in the same direction. CV1 is the tuning capacitor, and any value from 200p to about 350p should be satisfactory.

D1 to D3 act as a simple shunt regulator to keep supply voltage at no more than about 1.5 volts. It is

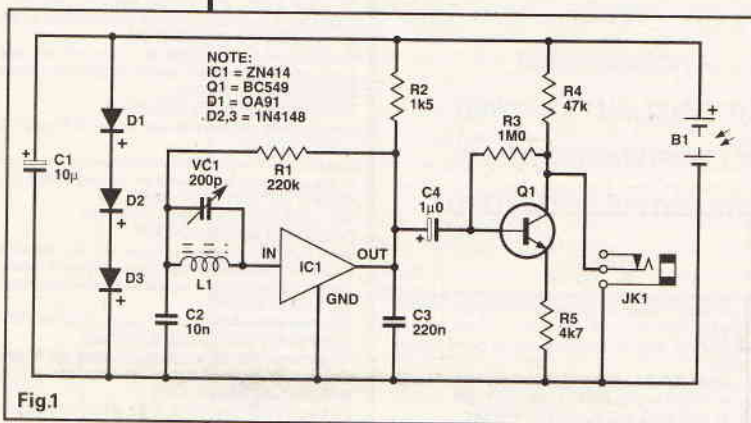


Fig.1

level. The series resistance, on the other hand, varies greatly with changes in light intensity. If the output voltage of a solar cell is measured using a high impedance voltmeter, it therefore remains fairly constant regardless of the light level. This contrasts with the results obtained if the output voltage is measured with a modest load current being taken. The output voltage is then roughly proportional to the light intensity.

This obviously makes life difficult for the circuit designer. Provided circuits consume microamps rather than milliamps, the supply voltage will remain close to the rated voltage of the solar cell and there should be no problem. Producing practical circuits that use really low output powers is not easy, and is impossible in many applications. What is often a more practical approach is to use circuits that require somewhat higher supply currents, but which will operate at quite low voltages. If the supply voltage should then happen to sag under loading, it should still leave a high enough supply voltage. Where the circuit is voltage-conscious, a simple shunt stabiliser circuit should ensure satisfactory results.

TECH-TIPS

possible that the circuit will become unstable, and if this should happen the supply voltage should be reduced slightly by replacing D1 with a shorting link.

The demodulated audio output from the ZN414 is at too low a level to drive an earphone at good volume. It is therefore followed by a common emitter stage having a voltage gain of about 20dB (ten times). This has a fairly high collector load resistor value in order to keep the current consumption of the circuit down to an acceptable level. This gives the circuit a fairly high output impedance, but it is able to drive a crystal earphone satisfactorily. Note though, that it will not drive any other type of earphone.

If the set uses a ready made ferrite aerial it will be necessary to adjust the position of the coil on the rod so as to give full coverage of the medium waveband. A little trial and error should soon produce a suitable setting, which will almost certainly be with the aerial coil almost right at one end of the ferrite rod.

Although the performance of the set should be quite good, remember that it is a simple TRF receiver and not a superhet type. When using the set remember that the ferrite rod is directional. If there is a problem with interference from an unwanted station, try rotating the set to null the unwanted signal. Bear in mind that the solar cell will only operate efficiently if it is aimed roughly in the direction of the light source. The receiver will work quite well under dull daylight and most artificial lighting, but with any solar powered device there is inevitably a minimum light level below which it will not function properly. No solar powered device can run on power which is simply not there.

When the receiver is used under artificial lighting there is a risk of problems with mains 'hum', due to the 100Hz signal amplitude modulated onto the light. In practice this does not seem to be a problem. C1 provides a certain amount of supply smoothing, but the slow response time of the solar cells seems to result in a minimal amount of 'hum' on their output anyway.

Solar Radio - 2

This is similar to the previous circuit, but it is based on the ZN415E rather than the ZN414. The ZN415E is basically just a ZN414 plus a simple audio amplifier and output stage. It is designed to drive medium impedance headphones of the type sold as replacements for personal stereo units. The headphones are driven direct from the output of the amplifier, and should be connected in series in order to obtain good efficiency.


This circuit in Figure 2 consumes somewhat more current than the original circuit. It will work quite well from a single solar panel, but results under low light levels are much better if two solar panels are used. Nothing drastic seems to happen if two panels are simply wired in parallel, but connecting any two power sources directly in parallel has to be considered a bad practise. Therefore, diodes D4 and D5 are used to ensure that one solar panel can not force a current through the other one. However, they can both feed their output to the radio circuit.

Signal Tracer

A signal tracer is a very simple but useful piece of audio test equipment. It is basically just a high gain audio amplifier feeding an earphone or a loudspeaker. You first check that the input signal to the faulty equipment is present. Then checks are made at various points in the circuit, working from the input towards the output. At some stage the signal will be absent, or be at a grossly inadequate level, and the fault should then be at or just prior to this test point. Most signal tracers, including the one featured here, are also capable of detecting amplitude modulated radio signals. This


enables them to be used for checking ordinary MW/LW radio receivers as well as audio equipment. Sometimes the demodulation is provided by a separate probe assembly, but in this case the demodulation is built into the main circuit.

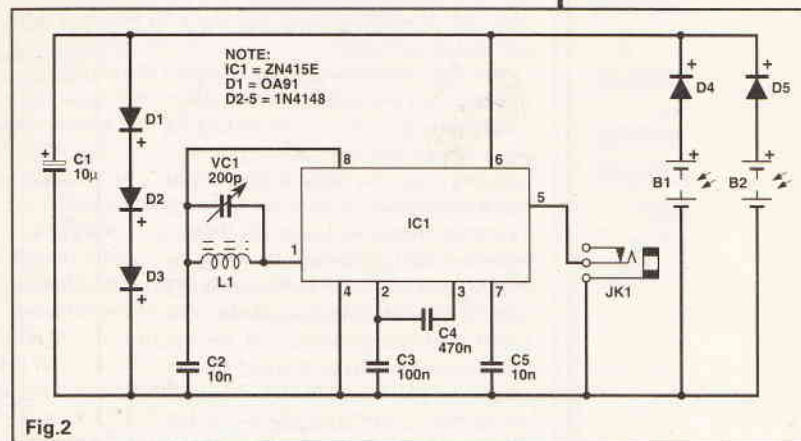The signal tracer circuit is shown in Figure 3, and it really consists of little more than two common emitter amplifiers with capacitive coupling. In order to keep the current consumption down to a very low level the



collector load resistors for both stages have been made quite high. A unit of this type should have a fairly high input impedance, but there is no need for a high impedance buffer stage at the input. Running the transistors at low currents produces a suitably high input impedance.

RV1 is the volume control. After some experience has been gained using the unit, the approximate input level can be gauged from the setting of this control and the volume from the earphone. Roughly gauging signal levels is important when using this type of equipment, since you will often be searching for a lack of gain somewhere in the faulty unit, rather looking for a total break in the signal path.

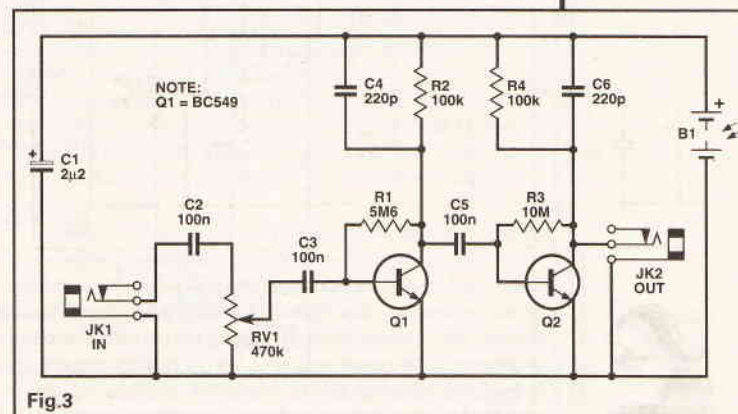

Demodulation of AM signals is provided due to the non-linearity of the transistors. They tend to amplify more on negative half cycles than on positive ones. This is simply because the gain of a transistor tends to rise with increases in the collector current, and the collector current is higher on negative half cycles than on positive ones. This gives a rather crude and inefficient form of rectification, but it is adequate for simple AM demodulation. C4 and C6 are the filter capacitors in the demodulator circuit. They also provide high frequency attenuation which helps to avoid instability.

The output of the unit will drive a crystal earphone at good volume, but it is unlikely to drive anything else satisfactorily. The current consumption of the circuit is only around 100µA, and it will therefore operate quite

well even under fairly dim conditions. The circuit can detect extremely small signals with RV1 set at maximum volume, but this high sensitivity makes it essential to keep the input wiring well screened from mains 'hum' etc. An oscilloscope style test lead is the best type to use with a unit of this type.

Remember when using a signal tracer that it can be used to check for a signal where there should be none. In particular, it can be used to check for a signal across a decoupling capacitor. If a signal is detected, then the decoupling capacitor must be faulty or not connected correctly.

It is possible to get the circuit to operate with a loudspeaker (of sorts). R3 must be decreased to 2M Ω , and R4 must be reduced in value to 15k. The output will then be capable of driving a Maplin Piezo sounder type 41/2.05. The sound output level will not be very high, and will be practically zero unless the sounder is firmly fixed in a suitable case. It should be adequate for this application though, where high volume levels are not normally required. Unfortunately, this modification greatly boosts the current consumption of the circuit, and it will only function under fairly bright conditions unless the unit is powered from several solar panels wired in parallel.

Transistor Checker

This transistor checker is a simple go/no-go type for small signal NPN and PNP devices. If the test component is basically functioning (i.e. is has reasonably high gain and low leakage) a 'buzzing' sound is produced from the unit.

Silence indicates that the test device is almost certainly a 'dud'. Due to the small test current used this checker can not be guaranteed to give satisfactory results with power transistors.

The circuit (Figure 4) is based on a conventional

at all.

Rather than using NPN/PNP switching, separate test sockets are used for these two types of transistor. With a PNP transistor connected to the unit it still functions as a form of astable circuit. R5 provides the base biasing and R6 acts as the collector load resistor. There is no need to switch R3 and R4 out of circuit as the currents that flow through them are too small to prevent the circuit from functioning correctly. Neither does the fact that one section of the circuit is based on an NPN transistor while the other is based on a PNP

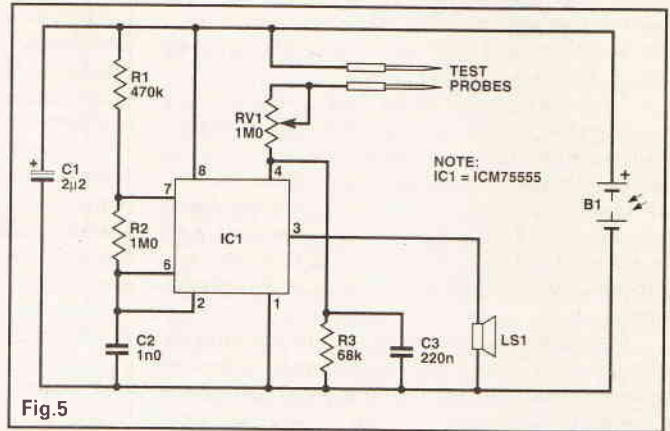


Fig.5

device prevent proper operation of the unit.

The current consumption of the circuit is low enough to ensure that it will function under fairly dim conditions. The test sockets can be sets of three 1 millimetre sockets grouped closely together. Most small transistors will then plug straight into these without any difficulties. However, it is probably worthwhile making up a set of crocodile clip test leads to enable any awkward transistors to be easily connected to the unit. The unit should work properly using any cased ceramic resonator (I used the Maplin wire-ended type). The peak frequency of the resonator is not important in this instance. The unit must simply produce a series of

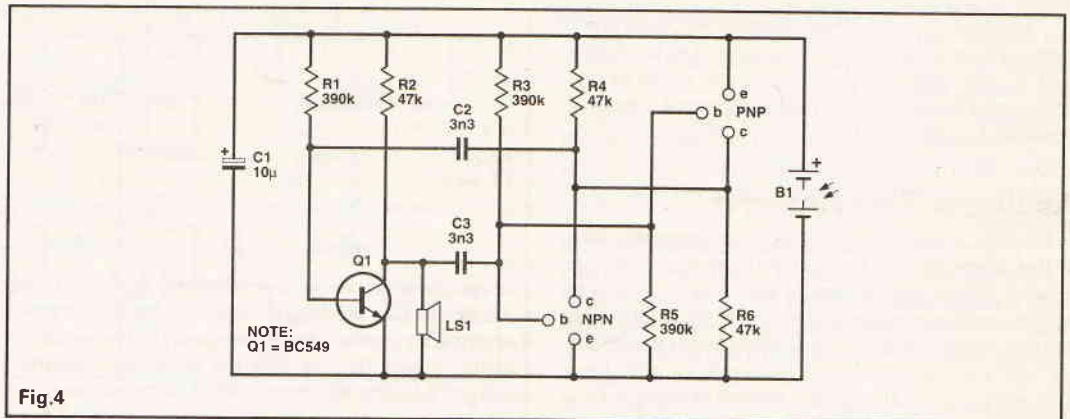


Fig.4

astable multivibrator. In fact, if an NPN test transistor is connected to the unit, the circuit is then a conventional astable circuit. R4 acts as the collector load for the test device, while R3 provides base biasing. R5 and R6 are connected into the circuit, and will pass small currents. However, their effect on the circuit is negligible, and they can be ignored.

If the component under test is serviceable, the multivibrator will function, and oscillation at a low audio frequency will be produced. This will be confirmed by a 'buzzing' sound from loudspeaker LS1. Note that LS1 is a cased ceramic resonator, and not an ordinary moving coil loudspeaker. The output power of the circuit is too low to drive even a high impedance moving coil loudspeaker, and trying to use a speaker of this type will simply prevent the circuit from operating

'clicks', and no attempt is made to generate a piercing tone (which would obviously be undesirable in this application). A non-cased resonator should also be suitable, provided the tester is built-up as a properly cased unit with the resonator mounted on the case in a suitable manner.

Continuity Tester

Producing a solar powered continuity tester seems easy enough, but it is not quite as straightforward as you might think. Firstly, the audio oscillator must produce a reasonably loud tone from some sort of loudspeaker, but it must draw a very low supply current. A low current audio oscillator is not difficult to produce, and as we have seen in previous projects, a ceramic resonator will produce a reasonably loud tone from a very

small drive signal.

In this circuit (Figure 5) the oscillator is built around a low power version of the NE555 timer chip. Some low power 555s seem to be better than others with regard to their current consumptions. Of the devices I tried, the ICM7555 seemed to have the lowest current consumption of all. It does have lower maximum drive currents than most other low power 555s, but in this application high drive currents are clearly not required. The circuit will operate using other low power 555s such as the L555, but operation at low light levels will be more reliable if the ICM7555 is used. The timing resistors have been made high in value so that the current drain in this part of the circuit does not greatly add to the current consumption of IC1.

The second problem is that having designed a circuit which will operate from a current of only 100 to 200 μ A, placing quite a high resistance in series with the supply will not prevent the circuit from oscillating. This can cause misleading results, with continuity being indicated when there is actually tens of kilohms across the test prods. In order to avoid this, the circuit is not controlled by having the test prods in series with the supply.

Instead, it is controlled via pin 4 which is normally taken low by R3. This blocks oscillation, but if the test prods are short circuited, the potential divider action across RV1 and R3 produces a high enough voltage at pin 4 to enable oscillation, RV1 must be correctly adjusted in order to obtain proper operation of the circuit. To set up RV1 correctly, simply short the test prods together and adjust RV1 for the highest resistance that does not cause the output to cease. Provided RV1 is set up correctly, quite small resistances across the test prods should be sufficient to block oscillation. It is certainly adequate in this respect for a simple continuity tester. It will not be 'fooled' by semiconductor junctions, which is more than can be said for most units of this type. Of course, if you want the unit to respond to semiconductor junctions and higher resistances, then all you have to do is adjust RV1 for something close to minimum resistance.

LS1 can be any cased ceramic resonator, or a plain type mounted on the project case in a suitable fashion. Although IC1 is a CMOS type, it has built-in protection circuitry which renders any special handling precautions unnecessary.

Analogue Thermometer

In the past, ordinary silicon diodes have been popular as the sensors for electronic thermometers. If they are forward biased they act rather like zener diodes, but with an avalanche voltage of only about 0.6 volts. This voltage varies to some extent with changes in current, and with changes in temperature. If a diode is fed from a constant current source, the voltage across it is then dependent only on temperature. The change in voltage is very small, being around two to three millivolts per degree Celcius for most diodes, but the linearity is quite good. If necessary, the change in output voltage can easily be boosted using an operational amplifier, and the voltage offset of around 0.6 volts can easily be removed as well.

Most modern electronic thermometers are based on one of the specialist temperature sensing integrated circuits. In essence these are not really much different to the discrete circuits of years gone by. The basic temperature sensing element is still a forward biased semiconductor junction, but it is usually accompanied by some on-chip amplification and other signal processing. This idea is taken to its ultimate in the LM35 series of temperature sensors, which provide an accurate output of 10 millivolts per degree Celcius, with no off-

sets to remove. The device used in this unit is the LM35DZ, which operates from 0 to 100° Celcius. The linearity is guaranteed to be no worse than $\pm 0.8^\circ$ Celcius over the full 0 to 100° temperature range, and would typically be much better than this.

The circuit (Figure 6) requires very few discrete components due to the signal conditioning circuits included in IC1. The LM35DZ is primarily designed for use with a digital voltmeter — in particular as a temperature probe for a digital multimeter. However, it will work perfectly well with lower impedance loads, such as the analogue meter circuit used in this case. R1, RV1, and ME1 form a voltmeter having a full scale deflection sensitivity of 0.5 volts. With an output of 10 millivolts per Celcius from IC1, this gives a full scale temperature of 50° Celcius. If a full scale value of 100° Celcius is required, use a 100 μ A meter for ME1.

This circuit does not utilize a negative supply, and as a result of this it can not be guaranteed to operate properly below 2° Celcius. However, after trying several LM35DZs in this type of circuit I have always found them to operate quite well right down to 0° Celcius.

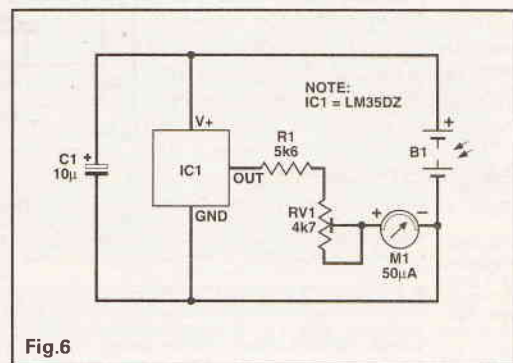


Fig.6

The LM35DZ only consumes about 56 μ A plus the output current. This means that it provides very little self heating, and also that it is well suited to an application such as this where very little supply current might be available. It is also largely impervious to changes in supply voltage, and it will work quite happily on any supply potential in the range 4V to 30 volts. In this application, where large variations in the supply voltage are to be expected, the LM35DZ will therefore work perfectly without the aid of an external voltage stabiliser circuit.

RV1 must be adjusted to accurately calibrate the unit. A good quality thermometer is needed in order to give an accurately known temperature against which the unit can be calibrated. Simply use the calibration thermometer to measure the air temperature, and then carefully adjust RV1 to give the same temperature reading. Of course, IC1 does not have to be mounted in the main unit. It can be fitted in a probe of some kind and connected to the main unit via a three way cable. This should ideally be a twin screened type, with the outer braiding carrying the 0 volt supply rail. This should eliminate any problems with noise pick up even if quite a long connecting cable is used. It is essential that IC1 is mounted in a waterproof probe of some kind if the unit is used to measure the temperature of liquids.

The Solems 14/096/048 8V 100 μ A solar cell is available from:

Chartland Electronics Ltd.,
27 The Glade,
Fetcham, Surrey,
KT22 9TQ.
Tel: 0372 45 0236
Fax: 0372 45 0622

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

Surplus always wanted for cash!

BBC Model B APM Board

£100 CASH FOR THE MOST NOVEL DEMONSTRABLE APPLICATION!

WIN £100 CASH!


BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board! It is supplied complete with a connector panel which brings all the I/O to 'D' and BNC type connectors - all you have to do is provide +5 and ±12V DC. The APM consists of a single PCB with most major IC's socketed. The IC's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Approx. dims: main board 13" x 10". I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only £29.95 or 2 for £53 (B)

MONITORS

MONOCHROME MONITORS

THIS MONTH'S SPECIAL!

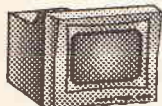

There has never been a deal like this one! Brand spanking new & boxed monitors from NEC, normally selling at about £140! These are over-engineered for ultra reliability. 9" green screen composite input with etched non-glare screen plus switchable high/low impedance input and output for daisy-chaining. 3 front controls and 6 at rear. Standard BNC sockets. Beautiful high contrast screen and attractive case with carrying ledge. Perfect as a main or backup monitor and for quantity users!

£39.95 each (D) or 5 for £185 (G)

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!

COLOUR MONITORS

Decca 16" 80 budget range colour monitor. Features a PIL tube, beautiful teak style case and guaranteed 80 column resolution, features usually seen only on colour monitors costing 3 times our price! Ready to connect to most computers or video outputs. 75Ω composite input with integral audio amp & speaker. Fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee. Ideal for use with video recorder or our Telex ST, and other audio visual uses. £99 (E) 3/£275 (G)

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee.

20".....£135 22".....£155 26".....£185 (F)

CALL FOR PRICING ON NTSC VERSIONS!

HI-DEFINITION COLOUR MONITORS

Brand new 12" multitap high definition colour monitors by Microvitec. Nice tight 0.31" dot pitch for superb clarity and modern metal black box styling. Operates from any 15.625 khz sync RGB video source, with either individual H & V syncs such as CGA IBM PC's or RGB analog with composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 14" x 12" square. Free data sheet including connection information. Will also function as quality TV with our RGB Telexbox.



Only £145 (E)

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee.

Only £129 (E)

NEC CGA IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15"L x 13"W x 12"H. A terrific purchase enables us to pass these on at only.... £79 (E)

V22 1200 BAUD MODEMS

Master Systems 2/12 microprocessor controlled V22 full duplex 1200 baud modem. Fully BT approved unit, provides standard V22 high speed data comm, which at 120 cps, can save your phone bill and connect time by a staggering 75% Ultra slim 4.5 mm high. Full featured with LED status indicators and remote error diagnostics. Sync or Async use; speech or data switching; built in 240v mains supply and 2 wire connection to BT. Units are in used but good condition. Fully tested prior despatch, with data and a full 90 day guarantee. What more can you ask for - and at this price!!

ONLY £69 (D)

IBM KEYBOARD DEALS

A replacement or backup keyboard, switchable for IBM PC, PC-XT or PC-AT. LED's for Caps, Scroll & Num Locks. Standard 84 keyboard layout. Made by NCR for the English & US markets. Absolutely standard. Brand new & boxed with manual and key template for user slogans on the function keys. Attractive beige, grey and cream finish, with the usual retractable legs underneath. A generous length of curly cord, terminating in the standard 5 pin DIN plug. A beautiful clean piece of manufacturers surplus. What a deal!

£39 (B) 5/£175 (D)

Brand new and boxed 84 key PC/XT type keyboards in standard IBM grey with very attractive mottled finish and "clacky" solid feel keys. 10 function keys on slide. English layout and £ sign. Green LEDs for Caps, Scroll & Num locks.

£29.95 (B) 5/£135 (D)

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!

FLOPPY DISK DRIVES BARGAINS GALORE!

NEW 5 1/4 inch from £29.95!

Massive purchases of standard 5 1/4" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from +5 & +12vdc, are of standard size and accept the standard 34 way connector.

TANDON TM100-2A IBM compatible DS £39.95 (C)
CANON, TEC etc. DS half height. State 40 or 80T £79.00 (C)
TEAC FD-55-F. 40-80 DS half height. BRAND NEW £79.00 (C)

Specials!
TEAC FD-55 half height series in your choice of 40 track double sided 360k or 80 track double sided 720k. Ex-equipment fully tested in excellent condition with 90 day warranty. Order TE-36 for 360k £29.95 (C) or TE-72 for 720k £39.95 (C)

CHOOSE YOUR 8 INCH!

Shugart 800/801 SS refurbished & tested £150.00 (E)
Shugart 851 double sided refurbished & tested £225.00 (E)
Mitsubishi M2894-63 double sided switchable hard or soft sectors - BRAND NEW £250.00 (E)

SPECIAL OFFERS!!

Dual 8" drives with 2 megabyte capacity housed in a smart case with built in power supply! Ideal as exterior drives! Only £499.00 (F)

End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only.....£399 (E)

AFFORDABLE 10 Mb WINCHESTERS

A fantastic deal - 10mb (formatted) Winchester for £39.95! Tandon TMS02 full height ST506 interface. Use it as a second hard drive on your present driver card or as a starter into Winchester land - see the driver card listed below. In excellent used condition, guaranteed for 90 days.....£39.95 (C) Hard disk driver card, complete with cables ready to plug into your PC or compatible. Supports two Winchesters.....£29.95 (A)

No Break Uninterruptable PSU's

Brand new and boxed 230 volts uninterruptable power supplies from Densel. Model MUK 0565-AUAF is 0.5 kva and MUD 1085-AHBH is 1 kva. Both have sealed lead acid batteries. MUK are internal, MUD has them in a matching case. Times from interrupt are 5 and 15 minutes respectively. Complete with full operation manuals.....MUK.....£249 (F) MUD.....£525 (G)

RECHARGEABLE BATTERIES

LEAD ACID


Maintenance free sealed long life. Type A300.
12 volts 12 volts 3 amp/hours £13.95 (A)
6 volts 6 volts 3 amp/hours £9.95 (A)
12 volts Centre tapped 1.8 amp hours. RFE. £ 5.95 (A)
12 volts 12 volts 38 amp hours. 7-1/2"L x 6"S. RFE £35.00 (B)

EXTRA HI-CAPACITY NICKEL CADMIUM

Super high capacity Chloride Alcad 12 volts refillable type XL1.5. Electrolyte is readily available Potassium Hydroxide. In banks of 10 cells per 8"H x 24"L x 5.5"D wooden case. Each cell measures 8"H x 1.75"L x 4"D. Can be easily separated. Ideal for all standby power applications. Ex MoD, like new.....£49.95 (E)

SPECIAL INTEREST

Newton Derby frequency changer 3 phase 50hz to 3 phase 400hz. 15kva output. As new. £2900
Trio 0-18 vdc bench PSU, 30 amps. New £470
Fujitsu M3041 600 LPM band printer £2950
DEC LS/02 CPU board £150
Rhode & Schwarz SBUF TV test transmitter 25-1000mhz. Complete with SBT72 Modulator £6500
Calcomp 1036 large drum 3 pen plotter £650
Thurley LA 160B logic analyser £375
1.5kw 115v 60hz power source £950
Tektronix R140 NTSC TV test signal standard. £675
Sony KTX 1000 Videotex system - brand new £2000
ADDS 2020 VDU terminals - brand new £225
Sekonic SD 150H 18 channel Hybrid recorder £2000
Trend 1-9-1 Data transmission test set £525
Kenwood DA-3501 CD tester, laser pickup simulator £350

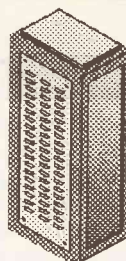

Superb Quality 6 foot 40u

19" Rack Cabinets

Massive Reductions
Virtually New, Ultra Smart!
Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready

punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2"H x 32-1/2"D x 22"W. Order as:

Rack 1 Complete with removable side panels.....£275.00 (G)
Rack 2 Less side panels.....£145.00 (G)

POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. £85.00 (B)

Power One SPL130. 130 watts. Selectable for 12v (4A) or 24v (2A). 5v @ 20A. ±12v @ 1.5A. Switch mode. New. £59.95 (B)
Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a, +12v @ 2a, -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". New £19.95 (B)
Greendale 19AB0E 60 watts switch mode. +5v @ 6a, +12v @ 1a, +15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cms. £24.95 (C)
Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a, -5v @ 1a, +12v @ 6a, 27 x 12.5 x 6.5cms. New. £49.95 (C)
Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a, +12v @ 2.5a, -12v @ 0.5a, -5v @ 0.5a. £29.95 (B)
Farnell G6/40A. Switch mode. 5v @ 40a. Encased £95.00 (C)

COOLING FANS

Please specify 110 or 240 volts for AC fans.

3 inch AC. 11/2" thick £ 8.50 (B)
3 1/2 inch AC ETRI slimline. Only 1" thick. £ 9.95 (B)
3 1/2 inch AC 230 v 8 watts. Only 3/4" thick £12.95 (A)
4 inch AC 110/240v 11/2" thick. £10.95 (B)
10 inch AC round. 3 1/2" thick. Rotron 110v £10.95 (B)
10 inch As above but 230 volts £24.95 (B)
60 mm DC 1" thick. No. 812 for 6/12v. 814 24v. £15.95 (A)
80 mm DC 5 v. Papst 8105G 4w. 38mm. RFE. £19.95 (A)
92 mm DC 12v. 18 mm thick. £14.95 (A)
4 inch DC 12v. 12w 11/2" thick £12.50 (B)
4 inch DC 24v 8w. 1" thick. £14.50 (B)

THE AMAZING TELEBOX!

Converts your colour monitor into a

QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and colour video monitor turning same into a fabulous colour TV. Don't worry if your monitor doesn't have sound, the TELEBOX even has an integral audio amp for driving a speaker plus an auxiliary output for headphones or Hi Fi system etc. Many other features: LED Status indicator, Smart moulded case, Mains powered, Built to BS safety specs. Many other uses for TV sound or video etc. Supplied BRAND NEW with full 1 year guarantee.

Telexbox ST for composite video input monitors.....£32.95 (B)
Telexbox STL as ST but with integral speaker.....£36.50 (B)
Telexbox RGB for analogue RGB monitors.....£68.95 (B)
RGB Telexbox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM / NTSC not available.

BRAND NEW PRINTERS

TEC Starwriter Model FP1500-25 daisywheel printer renowned for its reliability. Diablo type print mechanism gives superb registration and quality. On board microprocessor gives full Diablo/Qume command capability. Serial RS-232C with full handshake. Bidirectional 25 cps, switchable 10 or 12 pitch, 136 cpl in Pica, 163 in Elite. Friction or tractor feed. Full ASCII including £ sign. Font and ribbon Diablo compatible.....£199 (E)
DED DPG21 miniature ball point pen printer plotter mechanism with full 40 characters per line. Complete with data sheet which includes circuit diagrams for simple driver electronics.....£49 (B)
Centronics 150 series. Always known for their reliability in continuous use - real workhorses in any environment. Fast 150 cps with 4 fonts and choice of interfaces at a fantastic price!
£ 159-4 Serial up to 9.5" paper, fan fold tractor.....£ 99.00 (E)
£ 675 150-4 Serial up to 9.5" paper, tractor, roll or s/sheet.....£129.00 (E)
£ 150 152-2 parallel up to 14.5" paper, tractor or s/sheet.....£149.00 (E)

CALL FOR THE MANY OTHERS IN STOCK.

VISIT OUR SHOP FOR BARGAINS

LARGE QUANTITIES OF OSCILLOSCOPES AND TEST GEAR ALWAYS AVAILABLE - CALL NOW!

DISPLAY

MAIL ORDER & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET, 32 Biggin Way,
Upper Norwood,
London SE19 3XF.

LONDON SHOP
100's of bargains!
Open Mon-Sat 9-5.30
215 Whitehorse Lane,
South Norwood,
London, SE25.

DISTEL © The Original
Free dial-up database!
1000's of items + info On Line
V21, V22 & V22 bis
081-679-1888

ALL ENQUIRIES
081-679-4414
Fax: 081-679-1927
Telex: 894502



-ELECTRONICS-

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome - minimum account order £25. Carriage charges (A)=£2.00, (B)=£5.50, (C)=£8.50, (D)=£11.50, (E)=£14.00, (F)=£18.00, (G)=Call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. We reserve the right to change prices & specifications without prior notice. Orders accepted subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always required for cash.



velleman-kit




NEW




K6001 TEMPERATURE SENSOR

NEW

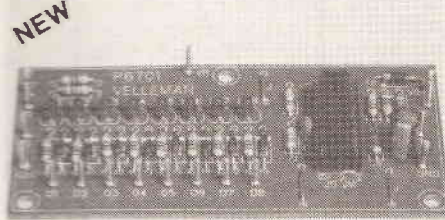

K6700: WIRE COMMUNICATION TRANSMITTER
K6701: WIRE COMMUNICATION RECEIVER

NEW

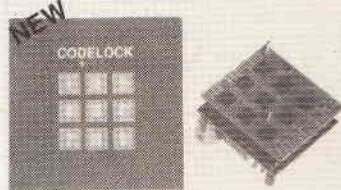


K6400 KEY CODE LOCK


NEW



K6002 uP TEMPERATURE CONTROLLER

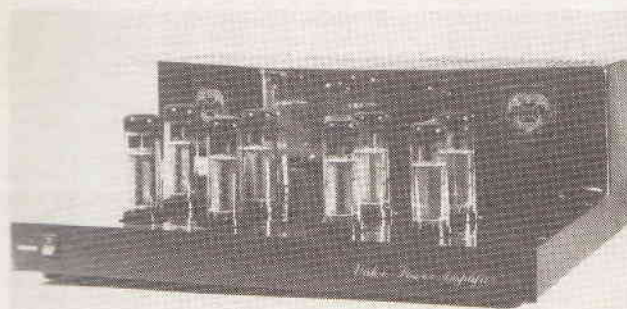

K4000 STEREO TUBE AMPLIFIER

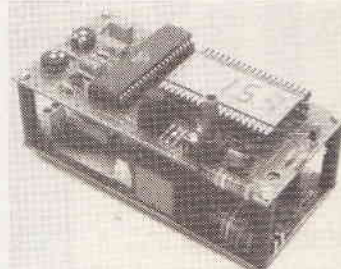


K2649 THERMOSTAT

NEW




K2668 DUAL STEREO VU METER MODULE

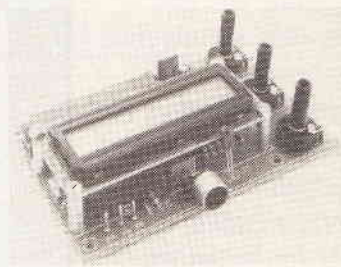


K2659 MORSE DECODER

NEW

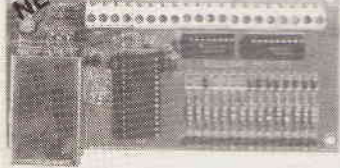

15 CHANNEL INFRARED RECEIVER

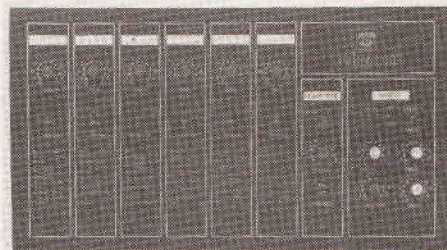


Professional mixing panel



INFRARED TRANSMITTER



K4010 300W MOSFET AMPLIFIER

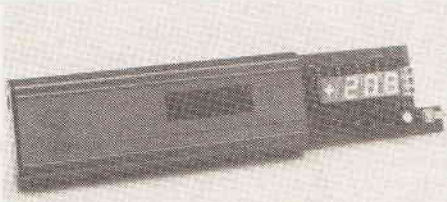

TEMPERATURE SENSOR WITH LED DISPLAY



K4020 600W MOSFET MONO/STEREO

NEW NEW NEW

LOWER PRICES for 1992 LOWER PRICES

Send £1.00 UK or £2.50 overseas for your copy of our NEW 1992 catalogue & price list.

160 kits to choose from — all in stock — it's a must for all electronic enthusiasts.

HIGH-Q-ELECTRONICS LTD.

(SOLE UK DISTRIBUTORS FOR VELLEMAN KITS)
Distributors for high quality electronic components
PO Box 142, Hatfield, Herts AL9 7HJ.
Tel: 0707-263562 Fax: 0707-276746



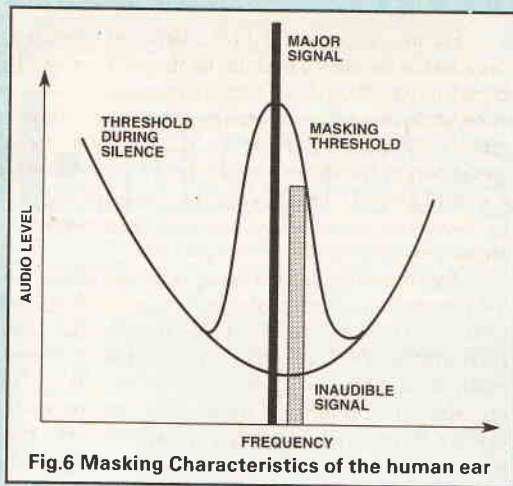


Fig.6 Masking Characteristics of the human ear

the signal which is contained in a particular sub-band, whereas systems using normal PCM (Pulse Coded Modulation) coding can produce disastrous results when errors occur in the most significant bit of a signal. Any individual radio frequency carrier will need to carry only a low bit-rate signal, so that relatively long bit-periods, or symbol times, can be used. Any noise produced by quantisation errors will be distributed over the whole of the available frequency band. This should minimise sensitivity to errors picked up along the transmission path.

The overall effect of using MASCAM plus differential coding is that it is possible to use only about 110Kbit/sec for a mono sound channel, about a third of the 350Kbit/s usually needed. The MASCAM technique for sub-band coding was originally used in the 1988 tests, but since then the idea has been considerably refined, and the latest tests have used an opti-

Digital Audio Broad

This month James Archer explains how DAB signals are put together, and shows that the latest in signal processing techniques can result in virtually perfect radio reception anywhere, whether at home, or on the move.

RADIO

The first step in constructing a DAB signal takes place prior to modulation; a digital signal processing technique called MASCAM is used, primarily to reduce the data rate needed to carry the digital audio signal.

MASCAM

- Masking Pattern
- Adapted
- Sub-band
- Coding
- And
- Multiplexing

This divides the audio frequency signal into 24 discrete frequency bands, each of which is separately quantised. Very little information is actually carried in any one of the sub-bands, which means that a great reduction can be made in the number of bits used for each band. 'Masking' refers to a particular characteristic of the human hearing system which reduces the amount of information that needs to be sent to represent an instantaneous audio signal. The human ear is insensitive to quiet sounds which occur in close proximity to loud sounds, when both sounds are reasonably close in frequency. We say the quieter sound is 'masked' by the louder one. If such a sound is completely masked there is no point in transmitting it, so that we can end up transmitting less data in total. The normal threshold of hearing is shown in the diagram, together with the shifted threshold that exists when a loud sound is present.

Each sub-band is individually coded, and the use of 'dynamic bit allocation', allocating different numbers of bits to the parts of the sound signal where errors would be most noticeable at any given time, is actually taken to the extreme that where the amount of information in any sub-band is below the level that the ear can hear, no bits at all are transmitted. In more technical terms, this bit-rate reduction technique actually works by optimising the matching of the source coding to the characteristics of the human ear.

Another advantage of the scheme is that if any errors do occur they will affect only that small part of

the signal, whereas systems using normal PCM (Pulse Coded Modulation) coding can produce disastrous results when errors occur in the most significant bit of a signal. Any individual radio frequency carrier will need to carry only a low bit-rate signal, so that relatively long bit-periods, or symbol times, can be used. Any noise produced by quantisation errors will be distributed over the whole of the available frequency band. This should minimise sensitivity to errors picked up along the transmission path.

These reduced data rate signals are then transmitted using a form of modulation with the magnificent name of COFDM, although some unenlightened users use just OFDM.

COFDM

- Coded
- Orthogonal
- Frequency
- Division
- Multiplexing

We are all familiar with the idea of FDM, frequency division multiplexing where several different signals are modulated onto a group of adjacent carrier frequencies which are then sent along a common channel. COFDM takes this a stage further, and the figure illustrates what happens.

The COFDM technique breaks the data stream of a single audio channel or multiple audio signals into a large number of simple carriers, and it is the total of all these modulated carriers that makes up the COFDM signal. The individual carriers are derived from the Discrete Fourier Transform of the original signal.

The essential feature of the COFDM technique is that the frequency spectrum of each modulated carrier is allowed to overlap its neighbour, and careful selection of the carrier frequencies, of the phasing of each of the signals, and of the digital coding system that is used, allows the individual carriers to be separated out again by the application of a complex mathematical technique called the Fast Fourier Transform as the signal is demodulated. The same circuitry that can distin-

guish between the individual carriers is able to take account of out of phase reflected signals, such as those that are produced by multipath interference.

The spectrum produced by the tightly packed overlapping spectra of each of the individual carriers gives an effect like that shown on the bottom of the diagram. We can see the system makes very efficient use of the available radio-frequency bandwidth.

In practice there is some intersymbol interference, i.e. interference between one data pulse and the neighbouring ones, caused by the inevitable multipath interference, but the problem is reduced or eliminated by leaving a guard band interval between each symbol; provided that this is long enough to exceed the delay suffered by any of the reflected signals, all the orthogonal carriers (i.e. carriers which are ninety degrees apart in phase) can be demodulated without difficulty.

As mentioned previously, during 1988 and 1989

Broadcasting

a terrestrial transmitter operating at 834MHz in Geneva was used to provide demonstrations of how 16 stereo sound programmes could be transmitted using the MASCAM/COFDM system; these demonstrations were given to members of the European EUREKA project 147, a consortium studying DAB, as well as to many other broadcasting engineers. Excellent results were obtained with a mobile receiver throughout the Geneva area, even in road tunnels and in other areas where reflected signals caused severe multipath interference.

Following this, in 1990 the BBC carried out similar trials using the Crystal Palace transmitter, and excellent results were once again obtained. Just to give you some idea of the numbers involved, the Crystal Palace tests used 448 overlapping carriers which were squeezed into a total bandwidth of 7MHz. The effective data rate achieved was about 5.5 Mbit/sec, which could allow perhaps twenty separate stereo audio programme channels to be broadcast at once. Further developments of the OFDM technique are likely to lead to more than 2000 separate but overlapping carriers being used. This can reduce the data rate required on each one even further, making the system even more immune to multipath interference effects.

DAB terrestrial transmissions for the UK?

Although these new techniques were originally developed with satellite broadcasting in mind, we have seen from the various tests that they need not be restricted to satellites, and it is reasonable to foresee that digital sound broadcasting from terrestrial transmitters could be practicable. During the 1991 Radio Festival in Birmingham the BBC gave some excellent demonstrations to highlight just what could be done using DAB terrestrially, if only a suitable frequency band could be used.

DAB (Digital Audio Broadcasting)

- BBC test and demonstrations
- Terrestrial
- Used VHF Band 3 - 215 MHz
- Lower power - 11 watts
- DAB compared with standard FM

For the purpose of the DAB demonstration tests they used a frequency in Band III, the old 405-line TV band that was taken from broadcasters some time ago in order to provide more channels for private mobile radio. Although not normally available for actual broadcasting, the frequency band just above 200 MHz is actually usable for broadcast ancillary services, i.e. for broadcasters in-house use, such as communications between outside broadcast units.

Two transmitters were set up on a building in central Birmingham, both radiating the remarkably small power of 11 watts, one using standard FM, the other DAB (MASCAM/COFDM). To get some idea of how small this transmitter power is, it is worth noting that the BBC's Radio WM FM transmitter that covers the greater Birmingham area has an effective radiated power of no less than 11,000 watts, although a fairer comparison might be to say that normally a transmitter of about 1kW would be needed to give comparable coverage to the 11 watt DAB test transmitter.

The BBC provided a coach fitted with both FM and DAB receivers, and arranged for each passenger to have headphones and a switchbox so that instant comparisons between FM and DAB reception could be made as the coach travelled around Birmingham.

DAB/FM Comparisons

12 programmes in 4MHz	1 programme in 2.2MHz
Test range 25km	Test range 10km
11 watts power	11 watts power
No Hiss	Hiss when signal weak
No multipath distortion	Multipath - flutter/pops

It was fascinating to hear how the FM signals, which the BBC is currently promoting heavily in its advertising, stressing the quality of reception that is possible, were frequently ruined by the snap crackle and pops caused by electrical interference and multipath. Switching over to DAB always provided perfect reception, and only when the bus passed deep under the bowels of Birmingham into a long underpass did the DAB signal disappear, quickly

and without fuss, as the receiver decided that it really couldn't make anything out of the heavily corrupted digits that it was receiving. As a further test, the bus was driven away from the city centre to see how far the low power transmissions would actually reach. At about seven miles from the city centre the 11 watt FM signals were unusable, but the 11 watt DAB transmissions could still be heard perfectly at a distance of over 15 miles, before failing completely a mile or so later.

Such good coverage from such low power transmitters shows that the DAB system is extremely efficient in its use of the radio frequency spectrum. The BBC estimates that if broadcasters could be given an 8MHz slice of the VHF band, which would only carry one 625-line TV programme, 24 different stereo radio programmes could be radiated, including a selection of commercial ones, and the same frequencies could be used over and over again throughout the UK.

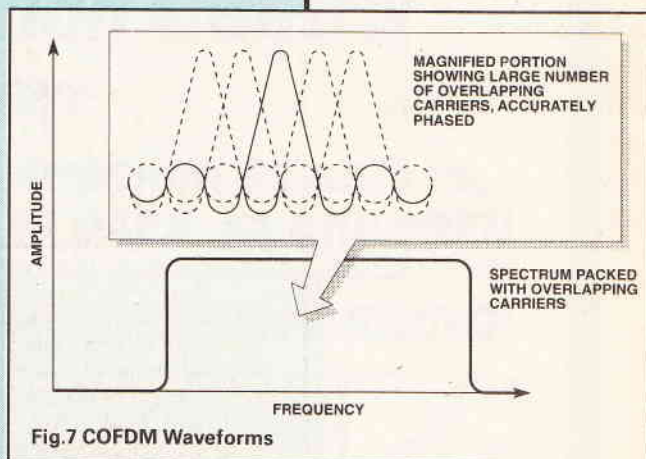


Fig.7 COFDM Waveforms

DAB (Digital Audio Broadcasting)

- Digital stereo sound
- Satellite or terrestrial
- No interference
- No fading
- No retuning

Single frequency network

One of the major problems with a conventional analogue broadcasting network, whether it uses AM or FM, is that a very large protection ratio is required between the wanted signal and other signals on the same frequency arriving at the receiver after a delay. This situation would occur all the time if there were several transmitters broadcasting the same programme in adjacent areas using the same frequency; notice the parallels with the multipath interference that we discussed earlier. This is the reason why conventional analogue broadcast networks need to use many channels, and conventional networks use carefully planned lattices of transmitters using different groups of frequencies. A disadvantage of this technique is that if it becomes necessary to build a 'fill-in' transmitter to serve a new town, perhaps, it is often very difficult to find a frequency channel that can be used without causing interference to listeners in adjacent areas.

If DAB is used, however, the situation is fundamentally different. We have seen that digital radio signals containing the same programme material that

with fill-in stations in built-up areas providing reception in places where the satellite signals cannot reach, with the same receiver being capable of receiving signals from either source, on the same frequency. Care would have to be taken in designing such a system that the signals from the fill-in stations did not compete for reception with the signals from the satellite, since this could give the effect of a large delay being introduced between the two signals, which, if it exceeded the maximum guard interval allowed by the DAB system, could prevent satisfactory reception. A way around this problem might be to have two complementary DAB systems, with the terrestrial system and the satellite system working on different frequencies. Although this would solve the problem, at the expense of more spectrum space, it would also lead to more expensive receivers, because these would need to switch between the satellite and the terrestrial transmissions.

DAB Receivers

DAB receivers are likely to be based on computer technology, with calculator type keyboards allowing for instant selection of any of the available programmes,

without the user having to know anything about the frequency or frequencies being used. After the radio frequency input signal has been received by the aerial and appropriately filtered, the multiplex of digital signals will need to be processed, and it seems that Fast Fourier Transform processing will be required. This is

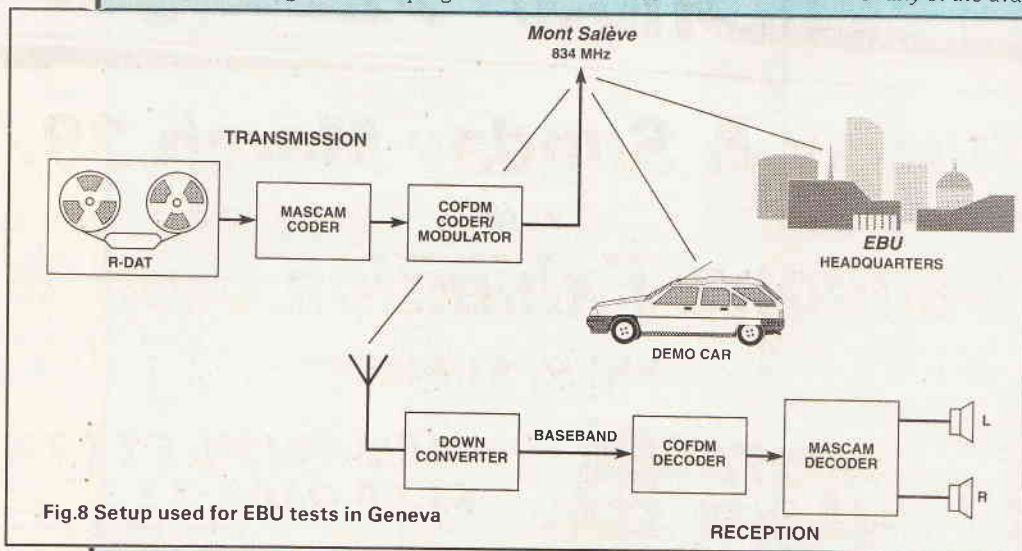


Fig.8 Setup used for EBU tests in Geneva

arrive at the receiver with a delay can be distinguished from the direct signal, so long as the delay is less than that of the guard band interval that has been left between the bits of the COFDM modulated digital signals. It thus becomes possible to envisage a network of transmitters covering the country, all of which use the same frequency. As well as using less of the precious radio frequency spectrum than conventional systems, such a system has the further advantage that it allows for any gaps in coverage to be filled by building low power transmitters on the same frequency, since the digital modulation system will ensure that any interference can be rejected; such fill-in transmitters could even be built in tunnels. This single frequency network would obviously make very efficient use of the spectrum, but some means will need to be found of synchronously feeding each of the transmitters in the network with the same modulating signals. This probably implies that all the different radio programmes that are to be transmitted will be pre-assembled at some central location into a single digital multiplex signal, which can then be distributed to the transmitters.

Hybrid DAB – satellite and terrestrial broadcasting

We began this article by considering the use of satellites for broadcasting high quality audio. If the DAB system were used from satellites it could be possible to provide the major coverage of countries by satellite,

currently a fairly complex affair requiring a good deal of exotic integrated circuitry, and if a single world standard for DAB can be achieved it will mean that large scale production of Very Large Scale Integrated Circuits can get underway, and this will lead to very low cost receivers.

Since we cannot introduce DAB on a broadcast band currently used for AM or FM broadcasts, as existing services would be interfered with, DAB needs to begin by operating in parallel with existing services. This means that it needs its own modest but exclusive chunk of the frequency spectrum. There currently appears to be a good deal of interest world-wide in DAB, and it is reasonable to foresee that digital sound broadcasting from satellite and terrestrial transmitters could be practicable within a very few years - if only a frequency allocation can be found! Further demonstrations of DAB will no doubt show members of the public that DAB really can provide perfect quality reception virtually anywhere, but before getting too carried away by this technological marvel it is sobering to remember that it took something over thirty years to convince the majority of the British public of the benefits of switching to FM radio. We will just have to hope that the immediate benefits that DAB can bring will persuade people to make the change much more quickly than this, and it may well be that it is the CD sound quality that does tip the balance in favour of digital radio, and will persuade people to go out and buy a new DAB receiver. I can't wait!



invites you to make a date with the

Radio and Electronics Show '92

Saturday & Sunday March 28/29

at the

Sandown Exhibition Centre

ESHER, SURREY

FEATURING

**AMATEUR
RADIO**

**CITIZENS
BAND**


**HOBBY
ELECTRONICS**

**HOME
COMPUTING**

and much more!

**ADMISSION: £2 ADULTS,
£1.50 OAPS, £1 CHILDREN**
(Children under 12 free when accompanied by an adult)

FREE & EASY PARKING!

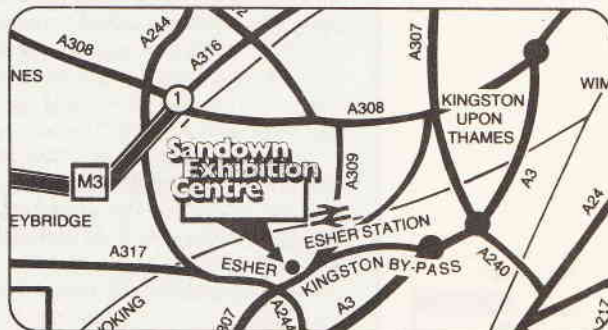

Exhibition sponsored by the following magazines:

Ham Radio Today

Citizens Band

Electronics Today International

Archimedes World

and organised by



ARGUS HOUSE, BOUNDARY WAY, HEMEL HEMPSTEAD,
TELEPHONE: 0442 66551 FAX: 0442 66998

2 Earth Charge Re

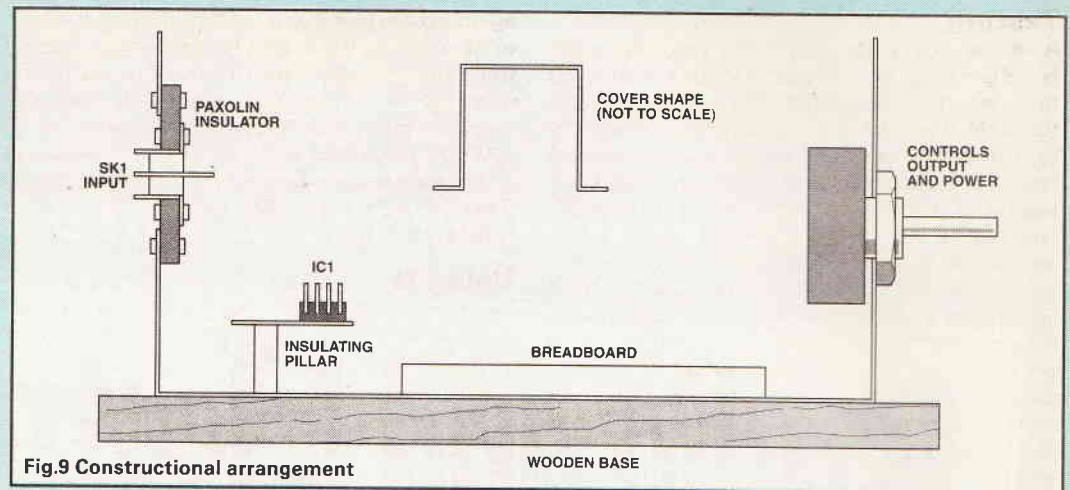


Fig.9 Constructional arrangement

The Power Supply

Kevin Garwell continues with his high resistance voltmeter.

The power supply can be quite conventional. Two rails are required, positive and negative. If either of the supplies are used as references the supply or supplies must be regulated. For example referring back to Figure 8 last month, R6 connects the input of IC2 to the +12 volt supply and as a consequence that supply must be regulated. In practice the regulation adds so little to the cost that the regulators might as well be fitted.

The simplest arrangement is shown in Figure 11. For the small currents involved (about 10 milli-amps) half-wave rectification is sufficient, and there are no special requirements for the components. The most important point is that the 0v rail is connected to a local earth, i.e. not the mains earth.

For the purpose of the ECR almost anything in contact with the earth will do because the currents involved are minute. However there are two most important side effects because the mains electricity is used to power the equipment. The first is safety. Because the mains is involved the earth connection must be a good one. The second is concerned with the capacity between primary and secondary windings. The earth must be sufficiently good to prevent any AC component appearing at the earth. I use a metre length of copper pipe driven into the ground and keep it moist. If you are not happy with the quality of the earth from the safety angle use an RCB in the live and neutral supplies. The RCB is preferable to the earth leakage trip in this instance as the latter employs a relay in series with the earth connection giving the effect we are trying to avoid—a high impedance earth connection.

If the ECR is to be used for experiments in static electricity and the like then batteries can be used. Remember there is less overhead available at the positive rail. Using the ICs suggested the output will only rise to within 2.5 volts of the positive supply, although it will fall to equal the negative supply.

The Probe

The atmospheric probe consists of a flat aluminium

plate, 12 inches square, with its edges turned down at 45° to give a little stiffness and stop any tendency to flutter in the wind. Mounted on plastic supports and fitted with a guard-ring to reduce any leakage. I found the method of construction shown in Figure 12 to be effective and fairly simple to make. The aluminium plate is fitted to the top (lid) of a plastic pill box using a couple of small screws and nuts. The pill box, approximately 3 inches in diameter and 5 inches deep, can be obtained empty from a friendly chemist. Cut a hole in the bottom of the pill-box so that it is a snug fit on the plastic tube, 1.5 inch plastic waste pipe as used by plumbers is just the job. Now comes perhaps the most difficult bit. Fastening the pill box to the tube. A hot melt glue gun is ideal for making this joint as it will weld the two together. The joint doesn't actually have to be watertight but hot melt glue is very handy for welding plastic bits and pieces together. With the aluminium plate fastened to the lid and the pipe fastened to the base of the pill box the next step is fitting the coax. There must be no question of water getting into the coax and the arrangement shown seems to be effective. With the ends of the coax prepared for connection it should be bent over into the shape of a walking stick and attached to the wall of the box (I haven't shown this fastening so that I don't obscure the connection details). A 'P' clip and screw is about the simplest so long as the coax is securely anchored and cannot straighten out. Next wrap a length of bare wire round the pill-box to act as a guard ring. Pass the end through a hole in the side of the pill box and connect to the screen of the coax. Add a length of flexible plastic coated wire to the centre conductor and connect the other end of this to one of the screws holding the aluminium plate to the lid. Ensure that there is a loop in both connections so that any moisture would run down the wires and drip off before reaching the coax. Finally fit the lid and the probe is complete. Support it on a length of wood so that the aluminium plate is about 4 metres above the ground. In my case I have to admit to having pinched one of my wife's clothes props. Softwood just over one and a quarter inches square.

PROJECT

Testing

After assembling the components onto the breadboard give the layout a visual check, don't forget to link the case to the 0v/ground line. Then set R1 to 5K and R2 to 1M. If a meter measuring ohms is not available set R1 to half-way and R2 to maximum. And there's the first pitfall. Remember R2 will have 3 connections only two of which are used, the centre and one of the outside ones. But be sure you have turned the pot the correct way for maximum value. Turning it the wrong way i.e. to zero will do no damage, it just leaves you with a 100M input resistance meter! For R1 the same applies but as the trimmer is turned half-way it doesn't matter. It will, if you experiment with changing the value. Connect to the power supply or batteries and with NOTHING connected to the input check the output at pin 6 of IC2 is approximately 6 volts, and at the output terminals is 3 volts. With 9 volt batteries the corresponding voltages

Recorder

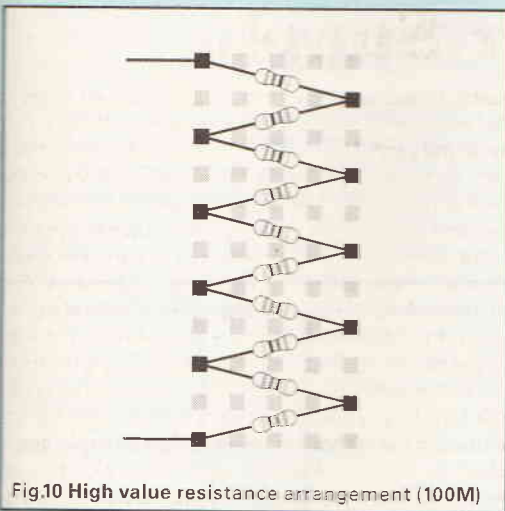


Fig.10 High value resistance arrangement (100M)

would be 4.5 and 2.25. If the voltage tends to wander about as you move your hands that reinforces the idea that it is working. Fashion a piece of bar copper wire (about 6 inches long) at the end so that it will nicely fit the centre input connector. With power on and a meter connected to the output rub a piece of plastic with a piece of dry cloth. A pen and handkerchief are ideal given that the qualifications apply! Move it towards the wire at the input. The output should rise or fall. Which it does depends on the type of plastic. Try also with a piece of glass. The rise/fall will only occur when the test item is moving. If all this happens then put the lid on and start experimenting. If you want to measure the input resistance it can only be done by experiment. This involves charging a capacitor to a known voltage and then connecting it between the centre input connector and the case (which is connected to the 0v/ground line). Determine the time taken for the voltage to fall to 2/3rds of its start value. This gives the approximate time constant CR where C is the capacitance and R is the input resistance. The experiment is most easily done if a single pole change-over switch is used to connect the capacitor first to the test voltage and then to the input. The other legs of the battery and capacitor being connected to the case of the device. The test volt-

age must be at least 2 volts less than the supply voltage to the device. eg. 9 volts for a 12 volt supply, or 6 volts if you are using 9 volt batteries. The switch and capacitor must be beyond reproach, the switch preferably ceramic or plastic and the capacitor polystyrene (about 1000p to 4700p) and all dry with it. It only remains to do the arithmetic and here the problem will be getting the indices right because otherwise there will be a lot of noughts sculling about!

Using It


The voltmeter allows the investigation of static charges in general by fitting a 6 inch length of wire directly to the socket on the device and connecting a suitable conventional voltmeter to the output. As shown in Figure 8 the meter should be connected to the output of IC2 op-amp rather than the junction of R9 and R10. This will enable full use to be made of the low resistance output of the IC. A simple moving coil meter of 5mA or less FSD with an appropriate series resistor is fine. There is no need to tie up an expensive multi-range meter. If the meter plus resistor has a full scale reading of 10V then the equivalent input voltages are, 0 is equivalent to -12V in, 6 to 0 in, and 10 to +8 in. These conversions can be used to determine the voltage at the probe. Alternative ranges can be achieved by changing R5 and R6 but the input can only be measured between -12 and +10V. Knowing the voltage at the probe is not the same as the actual voltage because of the voltage drop across the intervening atmosphere. The situation is equivalent to measuring the voltage of a battery with a resistor in series with the voltmeter. A number of effects can be observed. Charges generated by TV sets, or by friction between various materials. There is no need to touch these things with it, getting anywhere near will show that an electric field is present. One effect which puzzled me for some time was observed whilst building and testing the first one. Without the cover on, the output kept changing by a small amount. The movement seemed quite erratic there being no apparent reason. Eventually I cottoned on to the solution. It was all due to movement of my feet on the floor. I realised that such movement changed the capacity between myself and earth (ground). Such a change produced a corresponding change in my potential with respect to earth. Remember $CV=Q$. Halving the capacity will double the voltage if the quantity of electricity is constant. It must be remembered that the meter does require a current for its operation however small ($FSD = 4 \times 10^{-10}$ Amperes) so that it will always cause any charge to leak away, unlike the gold-leaf electroscope.

The Atmosphere Charge

In this case the device will be under cover preferably in an atmosphere which is reasonably dry. My workshop, which is not attached to the house, isn't centrally heated, but is brick built seems to be perfectly OK. The probe shown in Figure 12 should be mounted outside and preferably 10 metres or more from anything higher than itself. (4 metres).

Use ordinary TV co-ax to make the connection between probe and the electronics. If

any couplings are used be careful to keep them dry as any moisture in them will defeat the insulation and be very difficult to dry out. The meter referred to above, reading 0-10V is suitable for reading the output as an indication of the atmospheric situation. Clear summer skies usually give just above 6V on the meter ie. the voltage at the probe is just fractionally above zero. On the other hand cloud cover will give values approaching zero and indeed may be so negative that the meter just indicates zero, the input IC being cut off. If a meter is connected you may be lucky and see it kick up with one of the spikes under study. However a more certain way is to provide some sort of recording device. A chart recorder running at 1/2 inch an hour will do fine. However the ones which produce a trace by making dots on

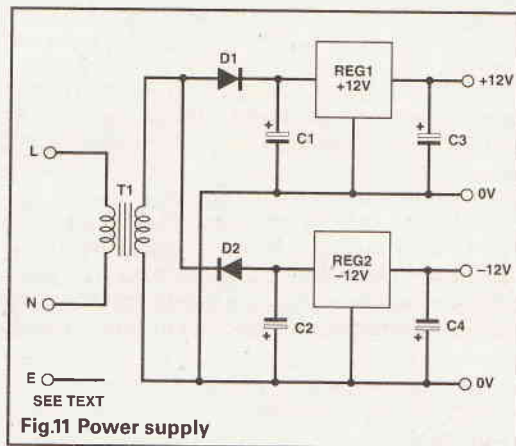

the paper will NOT do for the very simple reason that the spikes last so short a period they can so easily be missed on this type of recorder. Between dots as it were. Failing a chart recorder one can resort to our old friend the computer. The requirements are fairly simple. A method of reading (digitising) an analogue input, a timing device, and some form of media for recording the data. The timing device must be fairly accurate eg. not more than a minute of error per week. The digitiser need not be very special. The machine I use only digitises to 6 bits (ie 0 to 63) and that is quite sufficient. Finally for recording, a disc is ideal, but tape is acceptable. The only drawback to tape being the time taken to read the results. In an ideal world a second computer to interpret the results is available! As it happens I have both a Dragon micro with a disc and an Amstrad PC with twin discs. As one might expect the disc format is different so one cannot take discs from the Dragon and read them in the PC. Well you can because both machines are able to read specific tracks, sectors etc, but doing so would become a real exercise in programming which would be fine for the enthusiast but would take time. In the event I was able to avoid the issue because I have a device which will take the output from the printer port (on the Dragon - practically every machine will have a parallel printer output port) and convert it to RS232 serial form which is available on a PC. See Figure 1. The BBC machine would do nicely because if my memory serves me correctly it has an analogue input, a timer and will write to disc or tape. Another possibility is a PC with a digitising board fitted in a vacant slot. Since there are so many ways of achieving the required effect perhaps the best thing is to describe how my system works to illustrate the various points.

What Do We Do With The Data?

The data generated by the ECR/DRAGON recording system is saved minute by minute along with the day number, hour and minute numbers. A typical line might look like this:

7 6 48 30 28 1

Which translates to-day 7, hour 6, minute 48, max 30, min 28 and maximum difference during 1 second is 1. This was taken from an actual record in file T0906.ECR ie. 1991 September 6th. The following 4 records were:

7 6 49 30 28 1
7 6 50 36 28 7
7 6 51 31 29 1
7 6 52 32 30 1

One can see clearly that at the 50th minute there was a blip of magnitude 7. These values are on a scale 0 to 63 the range which the analogue inputs on the Dragon give. Primarily it is the occurrence of the blip which is of interest and not its absolute magnitude. However we can easily calculate the real values.

It looks as though it may be easier to derive an expression by starting at the front rather than work backwards.

Let the input voltage be X

Let the recorded value be V

Also the gain of IC1 and IC2 is unity so their output voltages will be the same as their input voltages.

Hence the output of IC1 is X

The input to IC2 is $(X+12)/2$

Output at the junction of R8 and R9 = $(X+12)/4$

A scale of 0-64 represents 0-5V

Scaling the output by 64/5 gives:

$$V = (X+12)/4 * 64/5$$

$$V * 5/64 = (X+12)/4$$

$$V * 20/64 = X+12$$

$$X = V * 20/64 - 12$$

or

$$X = V * 0.3125 - 12$$

And for the difference:

$$X = V * 0.3125$$

The line above for the 50th minute therefore is:

7 6 50 36 28 7

7 6 50 -0.75 -3.25 2.1

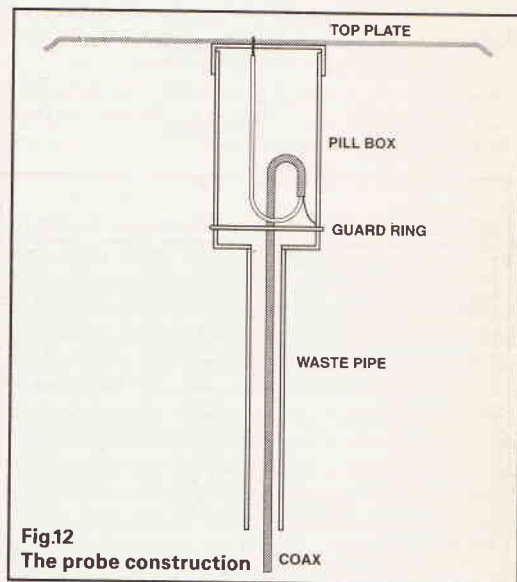


Fig.12
The probe construction

A word of caution here. Remember these are the voltages at the probe and because the input resistance is less than the atmospheric resistance they do not indicate the true voltage. As a very rough and ready guide the true voltages would be about ten times as much.

Having discussed the data we still haven't answered the opening question what to do with it. The answer is fairly simple. Look for the blips. This is more difficult to do because there is a lot of it. The average size of a daily file seems to be about 11 Kbytes. The search for, must be performed by computer would you believe and after much trial and error the currently

most suitable seems to be to classify the 1 minute differences on an hourly by amplitude basis.

Figure 13 shows one such chart. The figures on the left are the hour (GMT or UTC is best. It confuses the issue somewhat if BST is used. It is also important that GMT is also sun-time ie time 0000 coincides with being furthest from the sun).

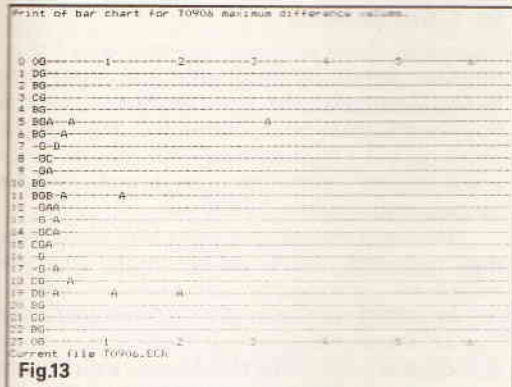


Fig.13

To the right of the hour figures are 64 dashes representing the value from the Dragon digitiser 0 to 63. For each hour the number of occurrences of each value are inserted by using code letters: A is one occurrence, B two or three, C four to seven and so on. Thus for 0000 hours there were 64 or more occurrences of a difference of 1 and no others. For 0100 hours there were 8 or more differences of 0 and 64 or more of 1. At 0500 hours 2 or more 0s, 64 or more 1s, 1 of 2, 1 of 5 and 1 blip of 32.

1900 hours is interesting. A comment in the data file reads "Was it me at 1900" the story is this. At my home where these readings are taken the probe is at the side of the garden not very far from one of these garden swing things. I make a practice of putting the seat cushions in plastic bags when not in use and at 1908 on the evening of 6th September that is just what I was doing. We all know (or we will when we've played with the ECR) that any friction between man-made fibres produces some strong electric charges. So I repeat my comment - was it me? Those three As at 1900 are an odd coincidence if not!

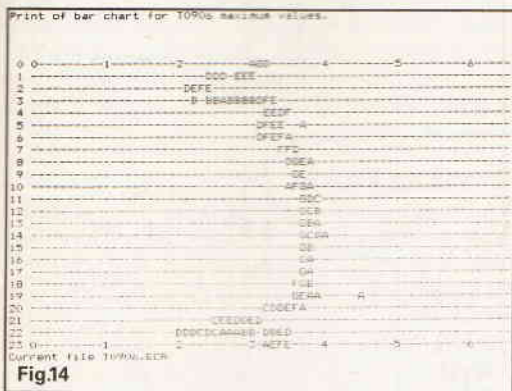


Fig.14

To make a comparison the equivalent chart plotting maximum values is shown in Figure 14. Just to reiterate the distinction Figure 14 shows maximum real values whilst Figure 13 shows maximum differences. The plot in Figure 14 can be converted to real values at the probe by using the formula discussed previously, and which is approximately, probe voltage = $0.3V \cdot 12$. The highest voltage recorded on the 6th September was (would you believe) at 1900 hours and was $45 \cdot 0.3 - 12 = +1.5$ volts. The letters have the same significance as before ie they indicate the number of occurrences.

The day in question (6/9/91) was one of Septem-

bers gorgeous sunny days. The highest voltage reached (ignoring the blip at 1900) being after 1400 hours, at 40 on the chart ie. 0 volts. I have no cohesive explanation of the shape of the chart. It may be reasonable to suggest that the 1400 hours figure is due to the fact that the sun's effect will have produced the lowest humidity. This will give the highest atmospheric resistance and with no strong charges around this would give zero volts input. That seems believable but what about the two dips at 0200 and 2200 with voltages of -5.7 and 6.0 respectively? The evening one might be the effect of a sharp fall in temperature after a very hot day producing condensation which would lower the humidity and hence the atmosphere becomes more conductive, but where did the negative charge come from? As far as I'm aware there were no clouds about.

How Is The Data Analysed?

The data analysis is done by transferring the data from the Dragon to an Amstrad PC1640DD (an IBM PC look-alike), and then using a program I wrote especially for the purpose.

As the Dragon has no RS232 interface I use a convertor fitted to the printer output. This converts to 2400 Baud, no parity, 8 data bits, and one stop bit. Because we have several Dragons in use here and at the Sciences Centre I have produced a board which has an RS 232 interface which converts to 8 bits plus strobe and busy in, and to 8 bits plus strobe out. These are useful for interfacing logic to RS232 in either or both directions and in this case giving Dragons an RS232 capability.

The fact that the Dragon is in the garage (where else would I keep it?) and the PC is in our small bedroom (which is not what my wife calls it) is of no great consequence as one of the chief reasons for choosing RS232 as our 'standard interface' was the fact that only three wires are required, transmit, receive and common. Any low voltage 3 core cable is good enough, or mains cable, whichever is the cheaper. The required PC commands are encapsulated into a batch file call GETCD.BAT which stands for get comms data.

The batch file is:

```
echo off
echo Setting up coms link
mode com1:
2400,n,8,1,p
echo Waiting for file(s)
b:
for %%n in(A1,A2,A3,A4,A5) do copy com1
%%n.GCD
```

In action I just give the command getcd on the PC. It gives the messages "Setting up comms link" followed by "Waiting for file(s)". Then a trip downstairs to the Dragon to print the appropriate data file(s). Each file must be terminated with decimal 26 which is the PC end of file character. On the Dragon this appears in BASIC as:

```
print#-2,chr$(26);
```

As the PC batch file expects 5 files (no magic just a convenient number), if less than five files are sent the end of file characters must still be sent. In fact I have a little program on the Dragon which sends up to 5 named files, each sending ending with chr\$(26). If there are less than 5 named files the end of file characters are still sent. After the end of file character a delay of 5 seconds is inserted to give the PC time to action the closure and get ready for the next file.

Done this way its all fairly straightforward. Just initiate the batch file on the PC and then run the Dragon program giving the named files. Then back to the PC to rename the files as appropriate. That is according to the first line of the file which carries the date.

The Dragon program is as follows:

```

Identity, copyright and declare array
5 DATA TRANSMIT FILE TO COMMS V1.00
8 DATA COPYRIGHT K GARWELL 1991
20 CLEAR500:DIMNFS(4)
Clear screen and put up headers
1000 READHDS:READCR$:CLS:PRINT@32,HDS:PRINTCR$

```

```

Read up to 5 file names. A null entry will terminate the loop by setting I=5
1010 PRINT:FORI=0TO4
1020 INPUT"FILE NAME",NFS(I)
1030 IFNFS(I)=""THENI=5
1040 NEXT

```

```

Print however many files were specified
Giving the file number and line count as they are sent
1100 FORI=0TO4:LC=0:PRINT@320,"FILE";I+1:PRINT
1110 IFNFS(I)=""THEN1160
1120 IFEOF(NFS(I))THEN1150
1130 FLREADNFS(I);FDS:PRINT#-2,FDS
1140 LC=LC+1:PRINT@352,LC," ";GOTO1120
Close the file and send the terminating character, then wait 5 seconds
1150 CLOSE
1160 PRINT#-2,CHR$(26);:WAIT5000
1170 NEXT

```

The program for analysing the data is written in BASIC and then compiled. This gives a faster running program. Interpreted BASIC can be used eg. GWBASIC but be prepared to wait for the results. The following synopsis has been extracted from the source code. The compiler doesn't use line numbers. Data Earth Charge Recorder data Scanner V2.01 data Copyright K Garwell 1991

```

'History
'V1.00 14/6/91 Derived from ECS Mk1 to print bar charts
'V2.01 07/09/91 Used to replace ECS and provided with write '
bar charts to file facility.
'Synopsis
'Enter list of files, ie. dates for charts
'Select variable to be charted, default %maxdif
'Load data from files to charts, merging all in "accumchart" "View results in
any order on request or write them direct
' to file
'Set order of printing results
'Set draft or letter quality
'Print results accordingly 2 per page
The accumchart referred to is an abbreviation for accumulation chart which
gives the totals for all the other files processed in the run. Usually a weeks
worth. This chart is useful for the overview it gives and helps to decide
whether the is any pattern to the blips.
The important bit is "load data from files to charts" and involves taking each
line of data, separating each value and assigning it to the appropriate chart.
The synopsis for this is:
for each entry in the file
if its a line of data then for each item of data
' (day, hour, minute, max value, min value, max dif)
get its value and store in an array of item values eg. items(5)
increment an array of values depending on chartnumber, hour, item
increment the accumchart
next
else
'its a comment
save comment in a string array
end if
next

```

Having loaded the chart array with the total counts there just remains the question of showing/printing the figures in a form which is easy to assimilate. The form chosen is a horizontal bar chart with a line for each hour. The counts are then encoded into letters, A representing 1, B 2, C up to 4, D up to 8, and so on. A typical pair of charts are shown in Figures 13 and 14.

The two charts are for the 6th Sept. 91. Figure 13 shows the maximum differences. Significant blips occurring at 5am with lesser ones at 1100 and 1900 hours. Figure 14 shows the maximum values for the

same day.

As the source for the analysis program is lengthy, about 400 lines, I hesitate to include it here because it would just be hard graft copying it. For anyone who doesn't like the idea of writing it I can provide a copy of mine with a few notes on driving it, for the sake of the price of a disc plus p&p. Send via ETI office.

In Conclusion

Three areas of use have been suggested so far. Experiments into static electricity for instance as generated by friction. Detection of blips, that is short term changes in the potential existing at an external probe a few metres above ground. Observation of daily changes in the actual potential existing at an external probe, possibly with associated weather conditions.

In my case the detection of the blips which, it has been suggested, may be caused by the advent of meteors into our atmosphere is the prime concern. So far only one rig is available which has certainly shown blips at all times during the day. This is contrary to my expectations which would have been to expect a bias towards the hours (midnight to midday sun time) when the portion of the earth containing the observation point is facing (overhead) the direction of the earth's travel. Just how this expectation would be modified if (as I also suspect) the area of perception is local ie. within a 40 km circle I'm not yet sure.

To help to resolve these hypotheses the next step must be to have two rigs a few miles apart and compare the results. If the blips occur at identical times then it is most likely that they are of natural origin and for the timing to be similar the source must be the same distance from the two probes. This could really only be the case if the source were overhead and fairly distant compared with the distance apart. This would really strengthen the meteor theory. If the timing were similar but not the same it would suggest some natural source for example rapid changes due to cloud motion. If the blips don't match time wise then the origin is likely to be man-made.

The most important factor in this experiment is that the two rigs are identical in every respect. For this reason we are going to adopt a height of 4 metres above ground for the probe and 10 metres of coax connecting the probe to the equipment, even if the full 10 metres is not necessary. The circuitry can easily be made identical, and in my case two Dragons are available. If this were not so the important thing would be to sample the probe potential at similar intervals. Currently one second.

Further Work

One disadvantage of the arrangement as described is that the probe or rather the electronics does require a current to provide the measurement. That is it is not a true electrostatic voltmeter and hence the circuit is not strictly as shown in the early Figures. To be accurate the ECR must be represented as having series resistance. This means that the potential at the probe is not the same as the atmospheric potential surrounding it, except in the special case when the input current is zero. However the input resistance of the system can easily be changed by changing the value of R2 in Figure 8. This could be done under program control given a suitable interface. There is therefore the opportunity to take measurements at various input resistances. This lends itself to the idea of solving simultaneous equations with two unknowns. The true potential and the resistance of the atmosphere.


Another change which can be made is to alter the interval at which measurements are taken. Recording each event rather than a minute by minute summary. The amount of data produced by such a change could

be reduced by only recording events in which the change is greater than a certain value. As yet I have had no use for the minimum value so there is the possibility of omitting it as a further reduction in the data captured.

Currently the negative excursions at the input are disproportionately large. The output frequently appearing as zero ie: -12V at the probe. A logarithmic scale would be useful here. As an alternative to a logarithmic scale there is the possibility of a series capacitor in the probe so that the device differentiates the probe potential. Given a time constant of a few seconds IC1 would not be cut off. The problem here may be the capacitor since its insulation resistance needs to be an order of magnitude greater than the input resistance. The capacitance would need to be something like 4700p with an insulation resistance of 2×10^{11} ohms. The only readily available and reasonably priced

capacitors in this range are polystyrene which claim the insulation resistance to be $> 10^{11}$. Alternatively a two gang air-spaced 500p might be worth a try, but they are definitely expensive. Undoubtedly polystyrene would be the first to try.

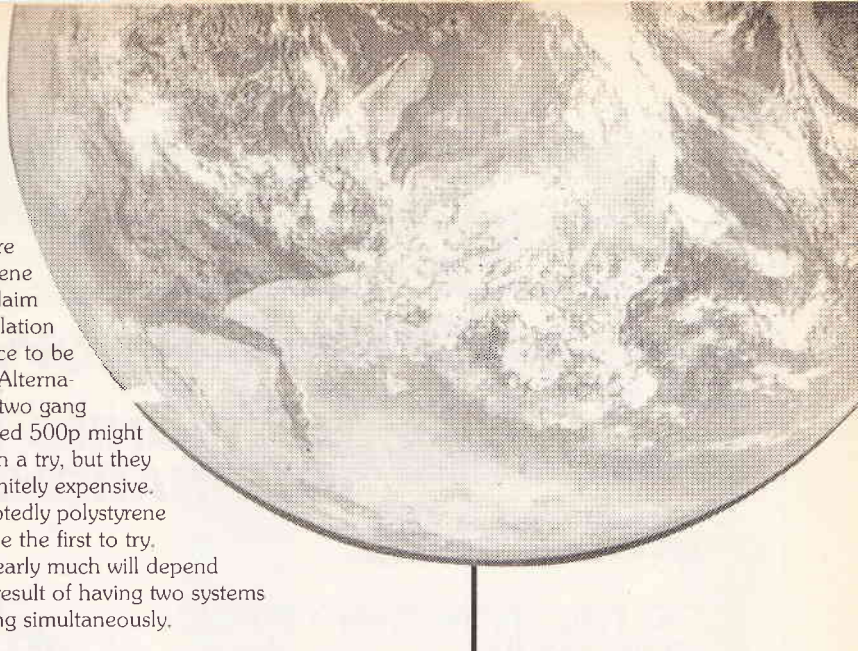Clearly much will depend on the result of having two systems operating simultaneously.



TEST EQUIPMENT MAINTENANCE AND TECHNICAL CONSULTANCY

- Service manuals
 - Spare parts
 - Comprehensive repair service including complete instrument refurbishment at highly competitive rates for radio amateurs.
- Distributors for:
WAUGH INSTRUMENTS
RAMTEST LTD
KRENZ ELECTRONICS

- We support scientific, commercial and industrial equipment manufactured by over 100 different companies.
- New and second-hand test equipment also available at competitive prices.
- Components, valves and miscellaneous items.

Hesing Technology



Cromwell Chambers, 8 St Johns Street, Huntingdon, Cambs PE18 6DD
Telephone and fax: 0450-433156

VISA SERVICE MANUALS

Available for most equipment. TV, Video, Audio, Test, Amateur Radio, Military Surplus, Kitchen, etc. Any Video Recorder, Video Camera or Oscilloscope Manual £15.00 (subject to stock).

All other Manuals £10.00 (subject to stock).
Over 100,000 manuals available for equipment from 1930's to the present.

Circuit sections supplied on full size sheets up to A1 size (33" x 24") if applicable.

Originals or photostats supplied as available.
FREE Repair and Date Guide Catalogue with all orders or send SAE for your copy today.

MAURITRON (ETI),

8 Cherry Tree Road, Chinnor, Oxfordshire OX9 4QY
Tel: (0844) 51694 Fax: (0844) 52554

WE BUY MANUFACTURER'S SURPLUS STOCK HENCE THESE LOW PRICES FOR PRIME COMPONENTS

	PRICE
PAPST FAN - 12V DC 1W 80mm ² 32mm deep.....	£8.50
ETRI FAN - 240V. 14W. - 120mm ² 38mm deep	£8.50
RELAY - SIEMENS - 12V 2 pole c/o. Low Profile. Gold contact, high quality	£1.00
MAINS FILTER - Bulgin or similar 5r 'quality' make/I.E.C./3A. 250V	£1.00
TORROID TRANSFORMER + complete wiring diag. - 240V in. Outputs 12V 4A, 12V 0.4A, 12.0-12 1A + 2A, 9-0-9 2A	£4.00
THERMAL PRINTER PAPER - Rolls 80mm wide 25m long	£1.00
Box of 40 rolls.....	£23.00
BARGAIN PACKS - Approx 3 lbs. of quality NEW mixed components. No rubbish! We deal mainly in bulk to the trade. All smaller qty. parts go in the packs together regardless of value.....	£7.00
HEAT SHRINK TUBING - Pack approx 15 x 16 inch lengths. Different diameters & colours.....	£3.00
HARDWARE PACKS - Same quality & quantity as the packs we do at all the major radio rallies - small nuts & bolts. £3.50; small self tapping screws, £3.50; ring & spade crimp terminals - Insulated	£3.50
3M STICKY PROTECTIVE FEET - grey rubber - sheet of 50.....	£3.00
COPPER CLAD P.C. BOARD - double sided 18in x 10.6in sheet, easy to cut - on thin and flexible fibre glass	£2.00
RESETABLE COUNTERS - 6 digit panel mount inc. catalogue data; 12V DC.....	£6.00; 240V DC
TA-XI CMOS SAFE CONTINUITY PROBE - detects & locates short circuits with variable audio tone, easy to use. S.T.C. price £22.00.....	Our Price £9.00
Needs PP3 battery (state if required)	£0.80

ALL THESE PRICES WILL HAVE BETWEEN 33% TO 50% OFF FOR THE SANDOWN EXHIBITION, 28/29 MARCH

POSTAL CHARGES: Orders £1 to £10 - £2.00; £10 to £20 - £4.00
LARGER ORDERS RING FOR CARRIAGE COST

PLEASE ADD 17½% VAT TO TOTAL COST INCLUSIVE OF POSTAL CHARGES

SEND TODAY — YOU'LL BE BACK FOR MORE!

PHONE
0222 831547

RICH ELECTRONICS
Dept ETI, The Warehouse, Windsor Place, Senghenydd
Mid-Glam, S. Wales CF8 2GD

FAX
0222 830022

HALCYON ELECTRONICS

Test equipment, video monitors, amateur radio gear, printers, power supplies, communications, disk drives, multimeters, oscilloscopes, scientific instruments, connectors, component bridges, frequency counters, signal generators, computers.

IBM POLAROID PALETTE, CG4	£295	WVC COMPENS LCR COMPONENT COMPARATOR	£75
COMMUNICATION RECEIVERS, VARIOUS	POA	QUALITICAL BALANCES WITH WEIGHTS	£69
H.P. 1340A XY CRT DISPLAYS	£145	WAVEMOM TF2001 DISTN FACTOR METER	£175
H.P. 1610A/B/1615A LOGIC ANALYSERS	£39	LIGHT BONES 250V 10"12" area	£49
TEK 2210 DIGITAL STGE SCOPE, LIKE NEW	£395	RECYCLE R/C/V BORES	From £15
VALRADIO FCB230/200 50Hz TO 60Hz 200W	£175	WAVE DEE PNEUMO UV EXP UNIT 390x260mm	£175
WANDAL/GOLTERMAN SPM-2 SEL LEVEL METER	£95	WAVELAMP PUMPS TYP 100MBAR (28L/MIN)	£95
GAUGE BLOCKS (SLIP GAUGES), VARIOUS	POA	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
SCR LEAD PTFE 19/15 SILVER PLATED RING REEL	£175	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
WAYNE KERR RA200+ADSI DISP STORE	£195	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
HONEYWELL 612 HUMIDITY/TEMP RECORDER	£165	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
TEK 5L4N 100kHz SPECT ANAL 510MM P ETC	£130	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
SIEMENS XTC1012 2-PEN CHART RECORDER	POA	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
GOULD BRUSH 260 6-PEN CHART RECORDER	POA	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
RUSH RT2 EN CU W/STRIPPER 38-43MM	£249	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95
RUSH DCF4+VAR SPEED CONT 2-25MM	£249	WINDUW PUMPS TYP 100MBAR (28L/MIN)	£95

Visit our bargain corner in shop
Many valuable items at knock-down prices

B&K 1013 BFO, 2305 LEVEL RECORDER	£295	WINDSHILL NS1540 15V 40A PSU CASED	£295
DATALAB DL912 TRANSIENT RECORDER	£35 each	HP 9861 618C, 620B, 626A, 628A SIG GEN	£35 each
BBC-B & MASTER COMPUTERS	POA	TEKTRONIK 7403N, DF1, 7D01 LOGIC ANAL	POA
RECHARGEABLE SEALED LEAD ACID BATTERIES	From £110	OSCILOSCOPES DUAL TRACE S/STATE	From £110
6V 10AH LONG LIFE, EX NEW EQUIPT	£245	WAVICOM TF2303 AM/FM MOD METER 520MHz	£245
HAMEG HM408 40MHz DIGITAL STORAGE SCOPE	£75	ROBIN 412 PHASE EARTH LOOP TESTER	£75
2 TRACE WITH HM8148-2 GRAPHIC PRINTER	£195	ROBIN 5400 DIGITAL RCOB (ELCB) TESTER	£195
FARNELL E350 PSU's 0-350V 100mA 20W	£150	BET LAB OVENS 12"x13"x14 INTERNAL 210"	£150
MARCONI TF2300 FM/AM MODULATION METER	£495	REDPOINT 6E-1 H/SINKS 1.5°C/W (QTY POA)	£495
TEK 545A, 545B, 565, 535A, PLUG-ING	£150	STAD PR41 EPROM PROGRAMMER	£150
TEKTRONIK 834 PROG DATA/CMS TESTER	£125	WAVICOM TF2330 WAVE ANALYSER	£125
VARIABLE OUTPUT PSU's HV & LV	£249	COHU 301 0-500V DC VOLTAGE STD INT REF	£249
TEKTRONIK 520 621A PAL V-SCOPIES	From £475	LEADER LEO-9C ALIGNMENT SCOPE	From £15
WAYNE KERR CT492 UNIV LCR BRIDGES	£15	SIGNAL GENERATORS AF TO 21GHz	From £15

LIST AVAILABLE, BUT 1000'S OF UNLISTED BARGAINS FOR CALLERS
QUALITY ELECTRONIC EQUIPMENT BOUGHT ALL PRICE EXC. OF P&P AND VAT

423 KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383

JOBSEARCH UK

The nationwide careers guide



NEW!

Select your next job from
the region of your choice!

Looking for a job?

Whether out of work

or wanting a

change - don't

give up or lose hope

JOBSEARCH UK - thousands of

jobs and career opportunities

updated every fortnight

classified by job type and UK region

FORTNIGHTLY AT LEADING NEWSAGENTS 95p



Cirkit TESTING



TM SERIES MULTIMETERS

D-MM Good Value!

The TM series of low cost meters, with 3 1/2 digit LCDs, full overload protection, strong ABS case and packed with features. Supplied with test leads, battery and manual.




TM 5315	DC current (10A) continuity and diode test	56-05315	£19.99
TM 5365	Capacitance and frequency (200kHz) ranges	56-05365	£36.50
TM 5375	Frequency range (20MHz) and HFE test	56-05375	£36.95
TM 115	AC & DC current (10A), HFE and continuity test	56-00115	£32.50
TM 135	Capacitance and temp. ranges (inc. probe)	56-00135	£45.95
TM 175	Frequency (15MHz), capacitance ranges with HFE, diode, continuity and LED test.	56-00175	£53.60
TM8020	3 1/2 digit display, frequency (4MHz), capacitance (40µF), AC + DC current to 20A	56-08020	£54.76
TM8030	3 1/2 digit display, frequency (4MHz), temperature (inc. probe), AC + DC current to 20A	56-18030	£59.96
7705	Capacitance meter, 1pF to 20,000µF	56-07705	£39.82

BLACK STAR

Top quality, UK made, frequency counters and generators.



Jupiter 2010	2MHz function generator plus 20MHz freq. counter	56-12010	£233.00
Orion	PAL TV pattern generator	56-01600	£269.00
1410	Video Monitor Tester	56-01410	£527.00
Meteor 100	100MHz counter	56-00100	£128.08
Meteor 600	600MHz counter	56-00600	£158.63
Meteor 1000	1000MHz counter	56-01000	£209.15
Apollo 100	100MHz counter/timer	56-10100	£381.88
Neva 2400	2.4GHz counter	56-02000	£351.33
Jupiter 500	500kHz function generator	56-00500	£129.25
Jupiter 2000	2MHz function generator	56-02001	£175.05

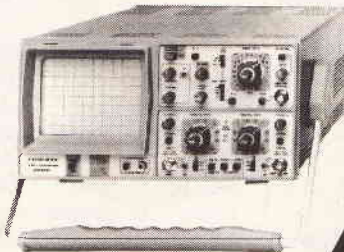

HAMEG 'SCOPES

All Hameg scopes are supplied with two x 10 probes, mains lead, manual and 2 year warranty.



HM203-7	Dual channel, 20MHz	56-52037	£397.15
HM205-3	Digital storage, 20MHz sampling	56-52053	£716.75
HM604	Dual channel, 60MHz	56-56040	£716.75
HM1005	Triple channel, 100MHz	56-01005	£930.60

Full details of all the above are included in our comprehensive catalogue, £1.70 (inc. P&P).

All the above are currently in stock and available for immediate delivery. Standard P&P £1.20, next day delivery £4.60.

Cirkit

All prices include VAT (at 17.5%)



Cirkit Distribution Ltd.
Park Lane, Broxbourne, Herts EN10 7NQ.
Telephone (0992) 444111.


PROJECT INDEX 1972-1992

AUDIO


	Mth	Yr	Pg		Mth	Yr	Pg		
2W power amplifier	Nov	1980	72	Amplifier, guitar effects	part 1	Aug	1982	28	
50-50 watt power amplifier module	Jan	1976	33		part 2	Sep	1982	16	
50/100W amplifier modules	Mar	1977	18	Amplifier, guitar practice		Apr	1982	12	
100W disco mixer/amplifier	Feb	1979	64	Amplifier, guitar practice		Jul	1990	39	
100W guitar amplifier	Feb	1973	52		Errata	Jul	1990	60	
	Errata	Apr	1973	90	Amplifier miniature (ETI Matchbox)		Apr	1986	40
100W MOSFET power amplifier	Aug	1980	64	Amplifier module, 50+50 watt		Jan	1976	33	
	Errata	Sep	1980	11	Amplifier module, 300W		Apr	1980	58
100W stereo disco console	part 1	Sep	1976	42	Amplifier modules, 50/100W		Mar	1977	18
	part 2	Oct	1976	51	Amplifier portable PA	part 1	Apr	1986	19
	part 3	Nov	1976	63		part 2	May	1986	43
	Errata	Nov	1976	8	Amplifier portable PA		Sep	1987	31
150W MOSFET Amplifier	Jun	1982	48	Amplifier Power (Virtuoso)	part 1	Apr	1988	26	
200W power amplifier	Apr	1978	43		part 2	May	1988	36	
300W amplifier module	Apr	1980	58		part 3	Jun	1988	49	
2040 11 active loudspeaker	Sep	1982	46	Amplifier (Virtuoso) MOSFET Upgrade		Nov	1989	36	
	Errata	Nov	1982	75	Amplifier simple 1.5W		Sep	1974	32
Active-8 loudspeaker	part 1	Sep	1984	45	Amplifier, simple stereo		Mar	1975	26
	part 2	Oct	1984	56	Amplifier (Small Fry)		Dec	1988	44
	part 3	Nov	1984	36	Amplifier, stereo, 5 w.p.c.		Jan	1977	10
	part 4	Dec	1984	24			Apr	1977	7
Active bass loudspeaker	Jan	1985	15	Amplifier, stereo (ETI Microamp)		Feb	1986	38	
Active crossover, two or three way	part 1	Dec	1975	11	Amplifier, stereo, International'25				
	part 2	Jan	1976	38		part 1	Oct	1975	26
Active loudspeaker	Nov	1983	68		part 2	Nov	1975	54	
	Errata	May	1984	69	Amplifier, stereo, 'Sweet Sixteen'	Errata	Dec	1975	76
Active loudspeaker, 2040 11	Sep	1982	46	Amplifier, System A	part 1	Jul	1976	38	
	Errata	Nov	1982	75		part 2	Jul	1981	52
Amplifier, 2W power	Nov	1980	72		part 3	Aug	1981	40	
Amplifier, 15 wpc, SQ quadrophonic	Apr	1974	16		Errata	Sep	1981	66	
Amplifier, 50 wpc stereo	part 1	Aug	1974	23		Errata	Oct	1981	13
	part 2	Sep	1974	60	Amplifier, the Audiophile		Feb	1986	54
Amplifier, 100W disco mixer	Feb	1979	64		Errata	Oct	1979	55	
Amplifier, 100W guitar	Feb	1973	52	Amplifiers, phono, high quality		Oct	1980	11	
	Errata	Apr	1973	90	Attenuator, variable 0-59dB		Feb	1982	45
Amplifier, 100W MOSFET	Aug	1980	64	Audio analyser		May	1973	53	
	Errata	Sep	1980	11	Audio buffer		Oct	1986	43
Amplifier, 150W MOSFET	Jun	1982	48	Audio Design amplifier	part 1	Jan	1980	82	
Amplifier, 200W	Apr	1978	43		part 2	Jun	1984	24	
Amplifier, 12V DC portable radio booster	May	1975	55		part 3	July	1984	44	
Amplifier, acousdix bridge 20W	Feb	1992	51		part 4	Aug	1984	30	
Amplifier, (JLH) Audio Design	part 1	Jun	1984	24		part 4	Sep	1984	59
	part 2	Jul	1984	44		Errata	Oct	1985	58
	part 3	Aug	1984	30	Audio frequency meter, 50Hz-10kHz		Jul	1973	66
	part 4	Sep	1984	59	Audio level meter		Mar	1976	17
	Errata	Oct	1985	58	Audio limiter		Dec	1976	58
Audio Design update	May	1989	25	Audio noise generator		Apr	1976	22	
	Errata	Nov	1989	60	Audio mlllvoltmeter, 'A' weighted		Apr	1976	26
Amplifier, bench (Short Circuit)	Feb	1977	52	Audiophile amplifier system		Oct	1979	55	
Amplifier, bench	Aug	1979	67		Errata	Oct	1980	11	
Amplifier, bench	Dec	1980	74	Audiophile FM tuner		Jan	1981	62	
Amplifier, (The Business)				Audiophile moving-coil preamplifier		Jan	1980	29	
Bass amp	part 1	Mar	1990	14		Errata	Feb	1980	17
	part 2	Apr	1990	42	Audio power meter	Errata	Apr	1980	15
	part 3	May	1990	42	Audio power meter		Jun	1976	29
Amplifier, combo (ETI Sonneti)	Mar	1985	22	Audio power meter		Mar	1979	67	
	Errata	Jul	1985	27	Audio source selector, digital	part 1	Mar	1984	35
Amplifier for personal hifi systems (ETI Walkmate)	Jan	1986	41	Audio spectrum analyser	part 1	Nov	1986	26	
Amplifier for record players (Using the LM380)	Dec	1974	34	Audio test oscillator, 30Hz-60kHz	part 2	Dec	1986	47	
	Errata	Jan	1975	70	Audio wattmeter, direct reading 0-50W	part 3	Jan	1987	52
Amplifier for stereo testing	Jul	1977	30	Auto-amp 12V DC portable radio booster		Jun	1978	27	
						Nov	1980	27	
						Oct	1973	46	
						May	1975	55	

	Mth	Yr	Pg		Mth	Yr	Pg
Auto volume control	Sep	1982	63	FM Decoder (update)	Jul	1988	32
Balanced line preamplifier	May	1983	38	FM mains distributor	Jun	1980	15
Bass booster	Mar	1973	44	FM tuner, the audiophile	Jan	1981	62
Bass enhancer for small loudspeakers	Jun	1977	53	FM tuner, the International	part 1	Sep 1975	26
Bench amplifier (Short Circuit)	Feb	1977	52		part 2	Oct 1975	32
Bench amplifier	Aug	1979	67		Errata	Nov 1975	77
Bench amplifier	Dec	1980	74	FM tuner with digital frequency display		Sep 1978	21
Better sound for £2	Feb	1973	58				
Bias optimiser for tape recorders	Jun	1980	44	FM tuner, PLL	part 1	Feb 1987	46
Boosting amplifier output	Feb	1976	51		part 2	Mar 1987	34
Bridging adaptor for the Series 5000 amplifier	Jul	1982	85	Four input mixer	part 3	Apr 1987	33
Bridging amplifier inverter	Oct	1978	41	Four track cassette recorder		Dec 1980	19
Bridging two ETI 100w guitar amplifiers	Nov	1975	30		part 1	Nov 1990	56
CCD phaser	May	1978	57	Frequency meter, audio, 50Hz-10kHz	part 2	Dec 1990	45
	Errata	Jul 1978	7	Frequency shifter		Jul 1973	66
Ceramic cartridge preamplifier	Sep	1975	41	General purpose pneamplifier		Mar 1978	40
Click eliminator	part 1	Jan 1979	73	Graphic equaliser, 1 octave filters		Nov 1976	26
	part 2	Apr 1979	41		Errata	Jan 1975	23
Clipping indicator for power amplifiers	Nov	1973	56	Graphic equaliser, 1 octave filters		Feb 1975	71
Combo amplifier (ETI Sonnet)	Mar	1985	22	Graphic equaliser, 1/3 octave filters		Sep 1977	27
	Errata	Jul 1985	27		part 1	Aug 1983	18
Compander (compressor/expander)	Nov	1977	11		part 2	Sep 1983	41
Compressor gate direct injection	Dec	1985	46		Errata	Nov 1983	96
Compressor/limiter	May	1983	32	Graphic/parametric equaliser		Feb 1985	31
	Errata	Jun 1983	11		part 1	Mar 1985	49
Digital audio selector	part 1	Nov 1986	26	Guitar practice amplifier	part 2	Apr 1982	12
	part 2	Dec 1986	47	Guitar volume pedal		Jul 1991	47
	part 3	Jan 1987	52	Headphone adaptor		Mar 1976	53
Digital cassette deck	part 1	Sep 1984	27	Headphone amplifier		May 1979	77
	part 2	Oct 1984	28		Errata	Nov 1979	13
Direct injection box	Sep	1985	43	High quality phono amplifiers		Feb 1982	45
Direct injection box, Passive	Mar	1991	47	Hi-lo pass filter, variable		Feb 1980	39
Active	Apr	1991	15	Hi-fi Power meter		Jun 1987	29
Direct inject compression gate	Dec	1985	46	Hum filter (50Hz notch filter)		Dec 1979	46
Disco console, 100W stereo	part 1	Sep 1976	42	Hybrid audio pre-amp		Nov 1991	32
	part 2	Oct 1976	51	Improving the response of economy loudspeakers		Feb 1973	58
	part 3	Nov 1976	63	Induction loop portable		Jul 1983	52
	Errata	Nov 1976	8	International 25 stereo amplifier	part 1	Oct 1975	26
Disco mixer	part 1	Jul 1981	39		part 2	Nov 1975	54
	part 2	Aug 1981	76		Errata	Dec 1975	76
	part 3	Sep 1981	42	International FM tuner	part 1	Sep 1975	26
Disco mixer, 4 into 2	Feb	1977	16		part 2	Oct 1975	32
Discrete SQ decoder for quadrophonic systems	Jun	1974	60		Errata	Nov 1975	77
Distortion meter	part 1	Jan 1985	55	LED VU meter		May 1980	78
	part 2	Feb 1985	37	Limiter, audio		Dec 1976	58
	part 3	Mar 1985	43	Line amplifier for microphones		Jul 1975	24
Double Quad ESLs in parallel	May	1975	44	Loudhailer (Short Circuit)		Sep 1977	56
Dummy load for audio testing	Jan	1982	71	Loudhailer, simple		Oct 1973	70
Dynamic noise reducer	Sep	1979	35	Loudness control		Aug 1975	25
Dynamic record noise filter	part 1	Feb 1976	37	Loudspeaker, active		Nov 1983	68
	part 2	Mar 1976	62	Loudspeaker, Active-8	Errata	May 1984	69
Equaliser, combined graphic/parametric (ETI Paragraph)	part 1	Feb 1985	31		part 1	Sep 1984	45
	part 2	Mar 1985	49		part 2	Oct 1984	56
ETI 422 stereo amplifier 50 w.p.c	part 1	Aug 1974	23		part 3	Nov 1984	36
	part 2	Sep 1974	60	Loudspeaker, active, 2040 II	part 4	Dec 1984	24
ETI ER II loudspeakers	May	1977	31			Sep 1982	46
	Errata	Jun 1977	9	Loudspeaker, active bass	Errata	Nov 1982	75
ETI Master Mixer	part 1	Apr 1973	66	Loudspeaker crossover, active, two or three way		Jan 1985	15
	part 2	May 1973	30		part 1	Dec 1975	11
	part 3	Jun 1973	56		part 2	Jan 1976	38
	part 4	Jul 1973	63	Loudspeaker Active (The Flatmate)		May 1990	50
	Errata	Oct 1973	52	Loudspeaker Active (The Consort)		Jul 1991	29
Expander/compressor	May	1976	29	Loudspeaker, ETI ER II		May 1977	31
Experimental preamplifier	Sep	1986	45		Errata	Jun 1977	9
FET four-input mixer	Jul	1972	66	Loudspeaker K2 kit		Feb 1991	57
	Errata	Aug 1972	9	Loudspeaker Micro monitors		Aug 1989	56
Five watt stereo amplifier	Jan	1977	10	Bi-amping micro-monitors		Sep 1989	57
	Errata	Apr 1977	7	Loudspeaker, novel		Jun 1984	57

PCB Foils

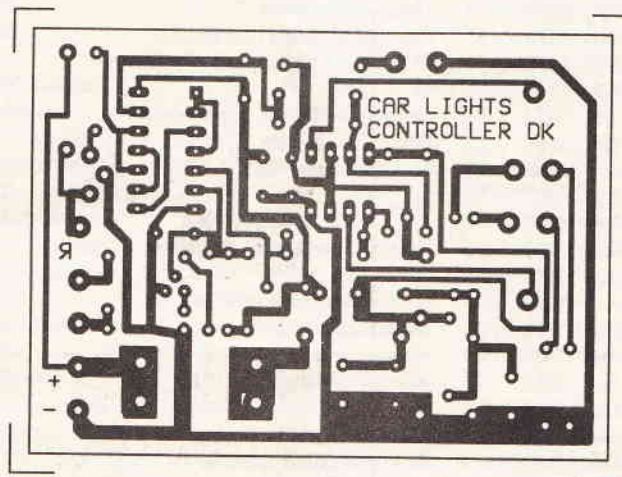

Auto Car Lights Controller board

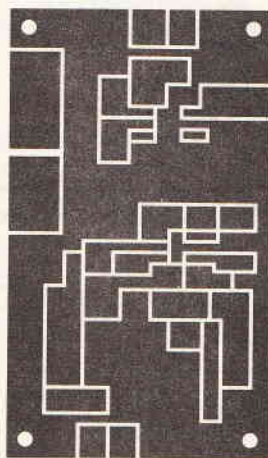

Single Span Audio sine-wave generator — copper uppermost. (Reprinted from last month at correct size.)

ETI

ELECTRONICS TODAY INTERNATIONAL



CLASSIFIED

Rebecca Daborn
0442 66551 Ext 313

Send your requirements to:
ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST.

Lineage: 60p per word (+VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£15.00 per single column centimetre (+VAT) per
Electromart £24.00 per Insertion (+VAT) insertion

Ring for information on series bookings/discounts.
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

- Metal detector boards with data, has tuner, mode, discriminate, headphone jack, on/off/volume and push button facilities £7.95 ea
- Dictaphone cassette, mechanical erase playback heads, 2V solenoid motor half effect switch £2.00 ea
- TV/Printer stands £3.95 ea
- Bico-Vero Easiwire construction kit £4.95 ea*
- TTL/CMOS short circuit snopper £4.95*
- Dot matrix LCD 10x2 lines £3.75 ea*
- Dot matrix LCD 16x1 lines with Dots £4.95*
- 40 character x 1 line dot matrix display with data £14.95 ea
- 20 character x 2 line dot matrix display with data £7.95 ea
- 2 digit 16 segment VF display with data £2.95 ea
- 4 digit intelligent dot matrix display segment VF display with driver £6.00*
- board and data £2.99 ea*
- 8 digit liquid crystal display £1.75 ea*
- 4 digit LCD with 7211 driver chip £3.50 ea*
- Digital clock display £2.50*
- 11 key membrane keypad £1.50 ea*
- Keyboard 392mm x 180mm/100 keys on board + LCD + 74HC05/80C49 easily removable £4.95
- 19" 3U sub rack enclosures £8.95
- 12V stepped motor, 48 steps per rev, 7.3" step angle £3.95 ea*
- Stepped motor board with slotted opto+2 mercury tilt switches £3.95 ea*
- 1000 mixed 1/4 watt 1% resistors £4.95 ea
- 250 electrolytic axial/radial caps £4.95 ea
- 200 off mixed polyester caps £7.95
- 100 Mixed trimmer caps popular values £4.95*
- 50 off MC 78M12CT Volt Regs £2.95*
- 20 off W02M Volt Regs £1.50*
- 25 off mixed buzzers and sounders £4.95
- Cable box UHF modular/video preamp transformer/R's + C's/leads £6.95
- 1000 off mixed Multilayer Ceramic Caps £7.95
- Solar cell modules 0.45V 700mA £2.95 ea*
- BBC Micro to disc drive lead £1.50*
- Car Burglar alarm vibration auto entry exit delay £5.95 ea*
- Single zone alarm panel auto entry exit delay housed in domestic light socket £3.95 ea

- PC, PS U, 50 watt 115-230V input/5V 4A+12V 2.5A output with built-in fan IEC inlet-on off £9.95 ea
 - STC PS U, 240V input 5V 6A output (converts to 12V 3A details available) £5.95 ea
 - 240V input 5V 10A output (converts to 12V 5A no details) £5.95 ea
 - 6000Ω line output transformers £1.25 ea
 - 240V in 0-12V 0.75A out transformer £2.75
 - 240V in 0-28V 62VA out transformer £2.75
 - Transformer+PCB gives 2x7.5V 32VA with skt for 5 or 12V regulator, will power floppy drive £3.75 ea
 - Ultrasonic transducer (transmit+receive) £1.50 pair
 - 3 to 16V Piezoelectric sounders 50p*
 - 9V DC electromechanical sounder 50p*
 - 24V DC electromechanical sounder 50p*
 - 2A 250V keyswitch 3 position key removable in two positions £1.50*
 - DIL switches PCB MT 3/4/6 way 35p*
 - 5V SPCO SILL read relay 40p*
 - 5V 2PCO DIL miniature relay 60p*
 - 12V 2PCO or 4PCO continental relay 60p*
 - 12V 10A PCB MT (to make contact) relay 95p*
 - 3 to 12V electro magnetic acoustic transducer with data 75p*
 - 2.4576, 3.5328, 21.10 MHz crystals 50p ea*
 - Bridges 25A 200V £1.00*
 - 2A 100V 50p*
 - 316 Mixed components pack £4.95
 - 25 off mixed relays £5.95
 - 40 off mixed toggle switches £9.95
 - 50 off mixed switches, toggle, rocker, micro, slide £9.95
 - miniature axial chokes, 0.1, 0.18, 0.12, 0.33, 0.39, 0.15, 1, 3.30H 10p ea 100 for £7.50
 - 50 Mixed terminal blocks £2.95
 - 250 off 16, 22/24/40 way IC Skts £4.95*
 - 100 off Phono plugs (red/blk/grey) £3.50*
- QUANTITY DISCOUNTS AVAILABLE - PLEASE RING**

**ALL PRICES INCLUDE V.A.T.
PLEASE ADD £2.00 p&p EXCEPT ITEMS
MARKED * WHICH ARE 50p
SAE FOR BULK BUYING LIST
PAYMENT WITH ORDER TO:
Dept ETI, COMPELEC,
14 Constable Road, St Ives,
Huntingdon, Cambs PE17 6EQ
Tel/Fax: 0480 300819**

PRINTED CIRCUIT BOARDS

Prototype boards made from your own design packages send your disc with HPGAL file for plotting and a quote for prototypes for multiple runs. Accept 5" and 3" high density or low. Plotting service from £2.00 per plot. Film work produced and PCB's to requirements. Artwork design service. We can produce a design from your schematic. Some designs are not practical. Minimum basic charge for 1 off PCB, £15.00. This would depend entirely on the complexity of the board, from your artwork. Artwork preferably looking from component or solder side needed. At 2-1 or 1-1. Kits and boards from stock for many projects. Send S.A.E. for new catalogue out Sept 1st. Ring 021-366 6047 for further information.

Sadger Boards, 1180
(near of Queslett Moral Co)
Aldridge Road, Great Barr
Birmingham B44 6PE.
magazine advert
contact.

MANUFACTURERS ORIGINAL SPARES

COMPONENTS for TV · Video · Audio · Computer

WE CAN SUPPLY A VAST RANGE FOR MANY MAKES — WRITE (send SAE please) OR
PHONE 0452 526883 FOR A 'PRICE & AVAILABILITY' ON YOUR REQUIREMENTS.

AMSTRAD/SINCLAIR	COMMODORE	OTHER MAKES
#0010 G Array £20.63	6526 CIA £11.11	Sanyo/Fisher VCR Belt Kit £2.23
CPC464 Serv Manual £4.49	8520 (Amiga) £11.22	VTC6500/VBS3500 £2.23
Spec 48K Membrane £4.73	8701 Clock Gen £8.95	Hitachi VT1114/33/34/83 Replacement Video Head £26.10
+128K Membrane £8.39	901225 Char ROM £6.55	Toshiba SH-U2/U2L Power Transformer £9.99
TEA2000 £4.49	C64 User Manual £4.25	TBA530 £1.74
ULALC001 £16.77	C64 ROM (XE/1) £4.49	TBA810P £1.16
ZX 8302 (OL) £10.75	Basic ROM (STE-PSU) £2.94	UPC1378H £2.45
ZX 8401 (Spec) £7.94	PC713V (STE-PSU) £2.94	LM733CN £2.27
PHILIPS CM8633 Serv Manual £3.80	EPSON C78010BD031 CPU £30.24	

This just a small sample of our stock — We are also holding Tools, Connectors, Aerial & Telephone Accessories and much more. For our catalogue please send 50p stamps/chg. MAIL ORDER ONLY. Please add 95p (UK) P&p not VAT. All items subject to availability. Price can change without notice.

MARAPET (TD), 1 HORNBEAM MEWS, GLOUCESTER GL2 0UE

WANTED

TURN YOUR SURPLUS TRANSISTORS, ICs ETC INTO CASH immediate settlement. We also welcome the opportunity to quote for complete factory clearance. Contact: **COLES-HARDING & CO.** 103 South Brink Wisbech, Cambs. PE14 0RJ BUYERS OF SURPLUS INVENTORY ESTABLISHED OVER 15 YEARS Tel: 0945 584188 Fax: 0945 475216

SPECIAL OFFERS

CATALOGUE £1.00 + 25p P&P

- LEDs 3mm or 5mm led or green 6p each yellow 11p each
- 7 segment common anode led display 12mm 30p each
- High intensity red, green or yellow 5mm 30p each
- Cable ties 1p each £5.95 per 1000 £49.50 per 10,000
- Stepping motor 4 phase 12v 7.5 step 50 ohms £8.95
- SA11027 stepping motor driver chip £3.95
- FM Transmitter Kc good quality sound £6.00
- High quality photo resist copper clad epoxy glass boards
- Dimensions: single sided double sided
- 3x3 inches £1.07
- 4x8 inches £2.40
- 6x12 inches £5.37
- 12x12 inches £10.66
- Special Offers
- Computer grade capacitors with screw terminals 38000uf 20v £2.50
- 87000uf 10v £1.95, 88000uf 15v £2.95, 100000uf 16v £1.50
- 7 segment common anode led display 12mm £1.45
- LM551AT5 0 low drop out 5v regulator TO220 package £1.85
- BS250 P channel mosfet 50 A5, BC555B transistor £3.95 per 100
- 74LS05 hex inverter £1.00 per 100, used 8748 Microcontroller £3.50
- TV Mains switch 4A double pole with momentary contacts for remote control pack of 10 £3.95 box of 60 £19.95
- DC-DC converter Reliability model V12PE 12v in 5v 200ma out 300v input to output isolation with data £4.95 each or pack of 10 £39.50
- Hour counter uses 7 digit 24v ac 50Hz £1.45
- Resistor pack 2500 resistors 1R-2W 50 different values £8.95
- QWERTY keyboard 58 key good quality switches new £5.00
- QWERTY keyboard with serial output no data (used) £5.00
- Wide range of CMOS TTL 74HC 74C Linear Transistors kits rechargeable batteries capacitors tools etc always in stock. Please add 95p towards P&p val included

JPG ELECTRONICS
276-278 Chatsworth Road, Chesterfield S40 2BH
Access/Visa Orders (0245) 211202 callers welcome

Technical Information Services
76 Church Street, LARKHALL, NED. IRE
Tel: (0698) 884585 Mon-Fri 9.30am - 5.00pm
Tel: (0698) 883334 Outwith business hours

Write now with an SAE for your
FAST, FREE QUOTE and FREE CATALOGUE
Remember, not only do we have EVERY service sheet ever produced, but we also have
THE WORLD'S LARGEST COLLECTION OF SERVICE MANUALS

WE ARE SOLE SUPPLIES OF FACTORY FACET-FINDING GUIDES, REPAIR MANUALS & TECHNICAL MANUALS
DATA REFERENCE MANUAL - essential for the serious electrician. FREE updating and a 10% discount voucher only £5.95. Incorporates Unique Model Identification and Chassis Data.

LASER Diode Modules, 2mw, 670nm, water and shock resistant, reverse polarity protected, dimensions 14.7mm x 28.5mm, £179.95. A. McKeever, 6 Grange Farm, Kirkcaldy, Fife, Scotland KY2 5UH.

SOLAR PANELS 100mm x 60mm 2.5V 0.2Wp £1.40. 6 for £8. 12" x 6" 12V or 6V 1.4Wp £8.50. 12" x 12" 12V 3Wp £15.00. 36" x 12" 12V 5-6Wp £23.50. Prices include U.K. P&P. Larger / mounted panels available. Orders to Bob Keyes GW4 IED, 4 Glanmor Crescent, Newport, Gwent, NP9 8AX.

100 ELECTRONIC components + cassette £1.50pp. Audio modules parcel £5.00. Rack, 60w/240W, £15.00. 1 Regent Road, Ilkley LS29 9EA.

TRANSFORMERS



New for 1992

- ★ **New MOSFET Amplifiers**
improved range of SMOS modules
30W, 30+30W, 60W, 120W
 - ★ **20 watt Class A Amplifier**
 - ★ **Low profile PCB Transformers**
a range of encapsulated transformers
4VA, 6VA, 10VA, 18VA, 24VA, 30VA
- Write or phone for data and prices...**
which include details of standard range of toroidal transformers and audio modules.

No price increase for 1992

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL
Telephone: (0227) 375254. Fax: (0227) 365104

KITS

NEW VHF MICROTRANSMITTER KIT tuneable 80-135MHz, 500 metre range sensitive electret microphone, high quality PCB. **SPECIAL OFFER** complete kit **ONLY £5.95** assembled and ready to use £9.95 post free. Access/Visa order telephone 021-411 1821. Cheques/POs to: Quantek Electronics Ltd, Kits Dept (ETI), 3 Houndley Road, West Heath, Birmingham B31 3AL. Tel: 0214 599647. For details on this and other kits. Shop now open — callers welcome.

KITS. VHF/FM Microtransmitter, 15x25mm, £5.95, built £9.95. "Stinger" Shocker, uses PP31, £12.99, built £19.99. Loads of plans, kits, units, surveillance, protection. See list. Cheque/PO: Ace(ti), 53 Woodland Way, Burntwood, Staffs WS7 8UP. Tel: 0543 676477 (24 hrs).

MISCELLANEOUS

HEATHKIT UK educational, products, distributors — service centre. Cedar Electronics, Cedar House, 12 Isbourne Way, Broadway Road, Winchcombe, Cheltenham, Glos. Tel 0242 602402.

LOUDSPEAKERS

Falcon DIY SPEAKERS

Send for our **FREE** price list PL20. All we ask for is a large SAE (34p stamp) or \$2 bill (air) overseas. (Europe — 3 international reply coupons)

SYSTEM DESIGNS (Total Kits):
Focal, KEF Constructor, Seas, etc.

DRIVE UNITS:
FOCAL, KEF, Audax, Coles, Peerless, Seas, Slare, Elac Metal Dome, Scanspeak, etc.
Also Group/Disco Units.

CROSSOVER NETWORKS:
Active & Passive Components, Accessories, Polypropylene Caps

AUDIO AMATEUR PUBLICATIONS

BACK ISSUES:
Speaker Builder, Audio Amateur & Glass Audio & lots of books
Full details from

FALCON ELECTRONICS
(Dept ETI) Tabor House, Mulbarton, Norfolk NR14 8JT (0508) 78272
(Proprietors: Falcon Acoustics Ltd)

MAIL ELECTRONICS

UNIT 6 FORBES COURT
BILLINGTON ROAD
BURNLEY, LANCs, BB11 5UB
Telephone / Fax: 0282 26670
Vat No. 562 7002 61

WANTED — WANTED

WE BUY ALL TYPES OF ELECTRICAL/ELECTRONIC PRODUCTS FOR "CASH"
IC's, DIODES, TRANSISTORS, CAPS, CABLE, COMPUTER SCRAP
"FACTORY CLEARANCE"
LET US QUOTE
CALL/FAX ANDE NOW!!
ON 0282 26670

SEND YOUR LISTS TO: MAIL ELECTRONICS
OR FOR FREE UNIT 5, FORBES COURT
CATALOGUE! BILLINGTON RD, BURNLEY
LANCS. BB11 5UB

❖ Catalogues to companies only

ELECTROMART

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street Tel: 051 236 0982
051 236 0154

47 Whitechapel Tel: 051 236 5489
Liverpool 2

'THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30

**To advertise in
Electromart
Tel: 0442-66551
for details of rates**

COMPONENTS

Fuselodge Ltd

267 Acton Lane, Chiswick,
London W4 5DD
Telephone/Fax: 081-994 6275

We stock a large range of Electronic components, semiconductors, switches, resistors, capacitors, transformers, fans, cables, leads, boxes, tools, etc. Power supplies, test equipment. Custom made S.M. power supplies.
Mail Order & Credit Cards accepted

SPECIAL OFFERS

SERVICE MANUALS

Available for most equipment
TV's, Video's, Test, Audio etc

Write or phone for quote
MAURITRON (ETI),

8 CHERRY TREE ROAD,
CHINNOR, OXON OX9 4QY
TEL (0844) 51694 FAX (0844) 52554

COURSES

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on 0626 779398





ETI/4/92


Name _____

- Telecomms Tech C&G 271
- Radio Amateur Licence C&G
- Micro-processor
- Introduction to Television

Radio & Telecommunications Correspondence School
12 Moor View Drive, Teignmouth, Devon TQ14 9UN

**To advertise in ETI
Tel: 0442-66551**

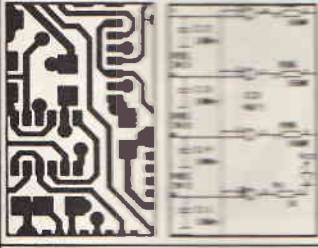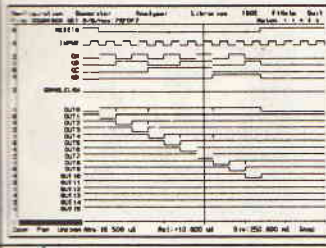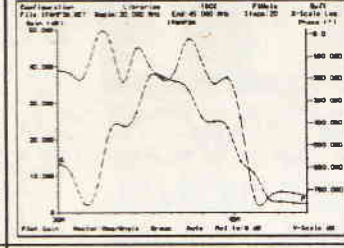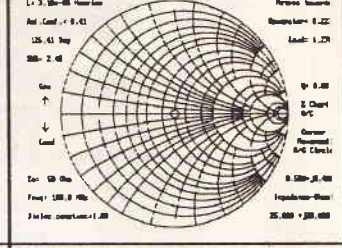PCB & SCHEMATIC CAD	DIGITAL SIMULATION	ANALOGUE SIMULATION	SMITH CHART CAD
EASY-PC £98	PULSAR £195	ANALYSER III £195	Z-MATCH II £195
			
<ul style="list-style-type: none"> • Design Single sided, Double sided and Multilayer boards. • One software package for Schematics and PCB's. • Standard output includes Dot Matrix / Laser / Image printers, Pen Plotters, Photo-plotters and NC Drill. • Award Winning EASY-PC is in use in over 10,000 installations in 70 Countries World-Wide. • Runs on PC/XT/AT/286/386 with Hero, CGA, EGA, VGA. • Optional libraries include S.M. Components etc. etc. 	<ul style="list-style-type: none"> • At last! A full featured Digital Circuit Simulator for less than £1000! • Pulsar allows you to test your logic designs without the need for expensive test equipment. • Catch glitches down to a pico second per week! • Includes 4000 Series CMOS and 74LS Libraries. • Runs on PC/XT/AT/286/386/486 with EGA or VGA. Hard disk recommended. • 74HC / HCT Libraries optional at £48.00 each. 	<ul style="list-style-type: none"> • NEW powerful ANALYSER III has full graphical output. • Handles R's, L's, C's, Bipolar transistors, FET's, Op-Amp's, Tapped and Untapped Transformers, and Microstrip and Co-axial Transmission Lines. • Plots Input and Output Impedances, Gain, Phase and Group Delay. • Covers 0.001 Hz to >10GHz • Runs on PC/XT/AT/286/386/486 with EGA or VGA displays. • Very fast computation. 	<ul style="list-style-type: none"> • Z-MATCH II takes the drudgery out of RF matching problems and includes many more features than the standard Smith Chart. • Provides quick accurate solutions to many matching problems using transmission line transformers, stubs, discrete components etc.etc.. • Supplied with comprehensive user instructions including many worked examples. • Runs on PC/XT/AT/386/486, CGA, EGA, VGA. • Ideal for both education and industry.
For full info' Phone, Fax or Write to:		Number One Systems Ltd. I The Electronics CAD Specialists	
REF: ETI, HARDING WAY, SOMERSHAM ROAD, ST. IVES, HUNTINGDON, CAMBS, PE17 4WR, ENGLAND. Telephone: 0480 61778 (7 lines) Fax: 0480 494042 International: +44-480-61778 Fax: +44-480-494042 ACCESS, AMEX, MASTERCARD, VISA Welcome.			



ELECTRONICS TODAY INTERNATIONAL

CLASSIFIED ADVERTISEMENT DEPARTMENT

ARGUS HOUSE, BOUNDARY WAY, HEMEL HEMPSTEAD HP2 7ST

Rates: Lineage 55p per word + VAT minimum 15 words.
 Semi-display £14.00 per single column cm plus VAT. No reimbursement for cancellations. All ads must be pre-paid.

Name

Address

..... Daytime Tel. No:

Signature

PLEASE DEBIT MY ACCESS/BARCLAYCARD No. Expiry Date

FOR SALE COMPONENTS PLANS OTHERS STATE

ETI

ELECTRONICS TODAY INTERNATIONAL

EDITORIAL

Editor Paul Freeman

CREATIVE

Art Editor Peter Kirby

Designer Iain Houston

Technical Illustration Jerry Fowler

Photography Manny Cefai

ADVERTISEMENT SALES

Advertisement Manager

Mark Linacre

Advertisement Sales

Michele Donovan

Advertisement Copy Control

Marie Quilter

MANAGEMENT

Managing Director

Terry Pattison

Circulation & Promotions Manager

Debra Stuppel

Production Manager

Tony Dowdeswell

Group Editor

Stuart Cooke

ISSN
0142-7229

ABC

Member of the
Audit Bureau
of Circulation

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and any reproduction requires the prior written consent of the Company © 1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

● Subscription rates — UK £19.20. Europe £24.90. Sterling Overseas £26.80. US Dollars Overseas \$49.00.

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST. Tel: (0442) 66551. UK newstrade distribution by SM Distribution Ltd., 6 Leigham Court Road, London SW16 2PG. Tel: 081-677 8111. Overseas and non-news-trade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST. Tel: (0442) 66551. Subscriptions by Argus Subscription Services, ETI, Queensway House, 2 Queensway, Redhill, Surrey RH1 1QS. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. Tel: (213) 3756258. Typesetting and origination by Ashford Scanning, Whitstable. Printed by Wiltshire Ltd, Bristol.



Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Tel: (0442) 66551 Fax: (0442) 66998

NEXT MONTH

Future issues of ETI will give you extra value! ETI will contain more projects and more pages. In the extra pages we can bring you more of those interesting project ideas for you to experiment with. From a beginners level to advanced old hands we will try to satisfy every ability in the creation of electronic aids and to keep you informed of commercial and academic developments.

Our projects include, a neat little device for the detection of Bats (the flying kind), a pond or water level control system, a Xenon flash trigger and a scanner for our surface-mount signal generator featured in the March issue. We must not forget our major project, the Automate 20 mixing desk. It continues with a look at the features available in this huge project. John Linsley-Hood also continues with his high quality pre-amp. This exciting world of electronics will be available in your shops on 3rd April, don't miss out!

The above articles are in preparation but circumstances may prevent publication

LAST MONTH

Projects and articles featured in the March issue were:

MIDI Switch
Earth Charge Recorder 1
Audio Sine-Wave Generator
Digital Audio Broadcasting 1
UV Radiation
High Energy Discharge Systems
Attenuators 1

A supply of back issues are available from Argus Subscription Services. Address in column to left.

ADVERTISERS' INDEX

BK ELECTRONICS	IFC	MAPLIN ELECTRONICS	OBC
BONEX	37	MAURITRON	57
CIRKIT HOLDINGS	5, 21	MEC MICRO	59
CRICKLEWOOD ELECTRONICS .	13	NUMBER ONE SYSTEMS	65
DISPLAY ELECTRONICS	46	OMNI ELECTRONICS	11
ELECTROVALUE	5, 13	PICO TECHNOLOGY	13
HALCYON ELECTRONICS	59	RICH ELECTRONICS	57
HESING TECHNOLOGY	57	REED ELECTRONICS	11
HIGH Q ELECTRONICS	47	STEWARTS	15
ILP ELECTRONICS	5	WILMSLOW AUDIO	59
J&N BULL	41		



ESR ELECTRONIC COMPONENTS
Station Road, Cullercoats,
Tyne & Wear NE30 4PQ
Tel: 091 251 4363 Fax: 091 252 2296

TOOLS




- drop forged 12 carbon steel alloy
- hardened case hardened
- lock-in gear
- polished black heads
- red PVC coated handles (not insulating)
- SOLENOID CUTTERS (10mm)
One head (not listed) **£8.81**
- SOLENOID CUTTERS (10mm)
Slim head (not listed) **£10.34**
- TOP CUTTERS (10mm)
For confined spaces **£9.58**
- SNAP-WIRE PLIERS (10mm)
Smooth jaws **£6.81**
- ROUND NICKEL PLIERS (10mm)
Smooth jaws **£7.27**
- FLAT NICKEL PLIERS (10mm)
Smooth jaws **£6.81**

SWITCHES	
Miniature Toggle Switches 3amp 250v 6.4mm ø mounting	RRP £13.53
SPST Toggle	£0.58
SPDT Toggle	£0.54
SPDT CO Toggle	£0.62
DPDT Toggle	£0.68
DPDT CO Toggle	£0.74
DPDT CO Toggle (biased)	£1.20
DPDT CO Toggle (biased 1 way)	£1.20
DPDT mini slide	£0.16
ROTARY SWITCHES	
1 POLE 12 WAY	£0.76
2 POLE 6 WAY	£0.76
3 POLE 4 WAY	£0.76
4 POLE 3 WAY	£0.76
Key Switch SPST	RRP £10.98
Push to make	£0.25
Push to break	£0.24
Latching Push Sw	RRP £11.49
PCB Tact 6 x 8mm	£0.23

LINEAR ICs	74LS-SERIES	4000 Series	TRANSISTORS
TL071CP	£0.32	74LS00	£0.14
TL072CP	£0.34	74LS01	£0.17
TL074CN	£0.48	74LS02	£0.18
TL081	£0.29	74LS03	£0.17
TL082CP	£0.34	74LS04	£0.14
TL084CN	£0.46	74LS05	£0.17
TBA120S	£0.60	74LS08	£0.17
LM301A	£0.25	74LS09	£0.17
CA311E	£0.28	74LS10	£0.17
CA324	£0.23	74LS11	£0.16
LM348N	£0.31	74LS12	£0.16
LF351N	£0.36	74LS21	£0.16
LM358N	£0.27	74LS30	£0.16
LM377	£2.57	74LS32	£0.17
LM380N	£1.12	74LS37	£0.16
LM381	£2.70	74LS42	£0.25
LM386	£0.48	74LS51	£0.19
LM387	£1.60	74LS86	£0.20
LM392N	£0.79	74LS92	£0.40
LM393N	£0.28	74LS93	£0.25
CA555	£0.22	74LS107	£0.30
NE556N	£0.36	74LS109	£0.21
NE567N	£0.36	74LS123	£0.40
UA733	£0.64	74LS125	£0.21
CA741CE	£0.18	74LS133	£0.22
LM748CN	£0.31	74LS138	£0.24
TBA810S	£0.68	74LS153	£0.25
TBA820M	£0.39	74LS154	£0.90
LM1458	£0.26	74LS157	£0.25
UJN2004	£0.48	74LS164	£0.26
TDA2003	£1.35	74LS165	£0.53
CA3046	£0.37	74LS175	£0.24
CA3080	£0.72	74LS191	£0.24
CA1310	£0.98	74LS193	£0.24
CA3140	£0.44	74LS199	£0.21
CA3240	£1.22	74LS367	£0.21
LM3900	£0.72	74LS374	£0.32
LM3914	£2.70		
LM3915	£2.70		
MC4558	£0.36		
NE5532	£0.80		
ICL7621	£1.70		

TEST AND MEASUREMENT

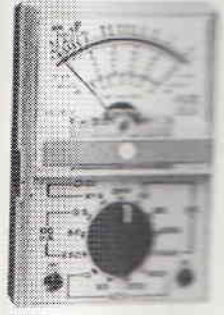

HC213 ANALOGUE METER
12 ranges, diode protection,
mirrored scale, 3mm leads, Pocket
sized, supplied with battery and
instructions.
Dim. 90 x 60 x 20mm **£5.58**

HM103S ANALOGUE METER
19 ranges (inc 10A dc), fuse and
diode protection, battery, 15mm shock
resistant titted case, mirrored scale,
supplied with battery, leads and
instructions.
Dim. 154 x 77 x 45mm **£21.47**

HC2020S ANALOGUE METER
20 Ranges (inc 10A dc), fuse and
diode protection, resistor and
diode testing, polarity reverse switch,
high impact shock resistant case.
Supplied with battery, leads and
instructions.
Dim. 150 x 100 x 45mm **£18.45**

W0930 DIGITAL METER
10 ranges, 3.5 digit 12mm LCD, signal
injector, diode test, fuse protection, auto
zero, supplied with battery, leads and
instruction manual,
Dim. 126 x 70 x 24mm **£14.73**

W0107B DIGITAL METER
17 ranges (inc 10A dc), 3.5 digit 12mm
LCD, diode test, buzzer, auto polarity and
polarity over-range ad low battery indication,
supplied with battery, leads and
instructions.
Dim. 130 x 72 x 33mm **£23.40**

TL34 DIGITAL METER
30 ranges (inc 20A ac/dc) PTC and fuse
protection, 5 capacitance ranges,
resistor test, 3.5 digit large 24mm
display. Heavy duty case with tilt stand.
Supplied with battery, leads and
instructions.
Dim. 191 x 88 x 36mm **£27.59**

RF CONNECTORS

BNC Solder Plug	£0.85
BNC Crimp Plug	£0.88
BNC Solder Skt	£1.06
BNC Chassis Skt	£0.78
PL259 5.0mm	£0.58
PL259 11mm	£0.58
RND UHF socket	£0.48
SOR UHF socket	£0.40
F Plug P258	£0.27
F Plug P26	£0.27
N Plug P26	£1.64

BRIDGE RECTIFIERS

W005 1.5A 30V	£0.19
W02 1.5A 200V	£0.20
W10 1.5A 1000V	£0.24
BR32 3.0A 200V	£0.36
BR62 6.0A 200V	£0.64
100A 10.0A 400V	£1.39

D CONNECTORS

REG'S	DIODES
78L05	£0.24
78L12	£0.24
78L15	£0.24
79L05	£0.24
79L12	£0.28
79L15	£0.28
LM3914	£2.70
LM3915	£2.70
MC4558	£0.36
NE5532	£0.80
ICL7621	£1.70



SOLDER BUCKET TERMINALS	REG'S	DIODES
9 Pin Plug	£0.28	IN4001
15 Pin Socket	£0.30	IN4002
15 Pin H.D.	£0.81	IN4003
23 Pin Plug	£0.40	IN4004
9 Way plastic cover	£0.48	IN4005
15 Way plastic cover	£0.50	IN4006
23 Way plastic cover	£0.30	IN4007
35 Way plastic cover	£0.33	IN5400
	£0.36	IN5401
	£0.36	IN5402
	£0.36	IN5404
	£0.36	IN5406
	£0.44	IN5407
	£0.29	IN5408
		IN914
		IN916
		IN4148
		BY127
		OA47
		OA90
		OA91
		OA202

RESISTORS

0.25W 5% CF E12 Series	£0.60/100
0.5W 5% CF E12 Series	£0.95/100
0.25W 1% MF E12 Series	£1.72/100
POTS Log or Lin 470R — 1MO 25mm dia	£0.40
0.25 shaft	£0.15
PRESETS Enclosed Horz or Vert 100R —	£0.15
1MO 0.15W	£0.15
PRESETS Skeleton Horz or Vert 100R —	£0.11
1MO 0.1w	£0.11

VELLEMAN KITS

Stockists of the full range of Velleman Kits. Catalogue available upon request.

OPTO DEVICES

5mm Red LED	£0.09
5mm Green LED	£0.10
5mm Yellow LED	£0.10
5mm Orange LED	£0.10
3mm Red LED	£0.08
3mm Green LED	£0.12
3mm Yellow LED	£0.13
3mm Orange LED	£0.13
5mm Flashing Red	£0.50
5mm Flashing Green	£0.54
5mm Bi Colour	£0.36
5mm Tri Colour	£0.48
5mm Plastic Bezel	£0.04
5mm Plastic Bezel	£0.05
0.3" 7-Segment Display Red common anode	£1.14
common cathode	£1.14

CAPACITORS

Ceramic Disc 100V 10pf to 100nF	
10, 22, 100, 150, 220, 330, 470, 680pf	£0.07
1, 2n2, 3n3, 4n7, 10, 15, 22, 33, 47, 100nF	£0.07
Ceramic Plate 100V and 63V 1.0pf to 12nf	
1pf-1nf	£0.06
1n2-2n7	£0.12
10nf and 12hp	£0.12
Polystyrene 160V 47pf to 10nf	£0.12
47pf-2n2	£0.09

ORDERING INFORMATION

All prices exclude VAT.
Please add 85p carriage to all orders and VAT (17.5%)
No minimum order charge
Please send payment with your order
PO/Cheques made payable to
ESR Electronic Components
Access and Visa cards accepted
Official orders from schools and colleges welcome.

ELECTROLYTIC AXIAL CAPACITORS

µF	16V	25V	63V	100V
0.47	—	—	£0.05	£0.07
1.0	—	—	£0.05	£0.06
2.2	—	—	£0.05	£0.06
4.7	—	—	£0.05	£0.08
10	£0.05	£0.05	£0.06	£0.08
22	£0.05	£0.05	£0.09	—
47	£0.05	£0.06	£0.11	—
100	£0.06	£0.09	£0.11	—
220	£0.06	£0.12	£0.13	—
470	£0.15	£0.19	£0.17	—
1000	£0.20	£0.29	—	—
2200	£0.27	£0.37	—	—
4700	—	£1.11	—	—

ELECTROLYTIC AXIAL CAPACITORS

µF	16V	25V	63V	100V
0.47	—	—	—	£0.15
1.0	—	—	£0.10	£0.10
2.2	—	—	£0.10	£0.10
4.7	—	£0.09	£0.10	£0.10
10	—	£0.12	£0.12	£0.12
22	—	£0.09	£0.13	£0.17
47	£0.10	£0.11	£0.16	£0.20
100	£0.10	£0.13	£0.21	—
220	£0.13	£0.18	£0.42	—
470	£0.21	£0.20	£0.69	—
1000	£0.33	£0.40	£1.05	—
2200	£0.52	£0.54	—	—
4700	£0.90	—	—	—

CALL IN — OPEN: MON-FRI 8.30-5.00 SAT 10.00-5.00

1992 BUYER'S GUIDE TO ELECTRONIC COMPONENTS

Maplin



Order your copy of the New MAPLIN Catalogue on sale NOW!
Pick up a copy from any WHSMITH for just £2.75 or post this coupon now to receive your copy for just £2.75 + 20p p&p. If you live outside the U.K. send £4.85 or 14 International Reply Coupons. I enclose £2.95.

Name

Address

Post Code

Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex SS6 8LR.
E192

Over 600 product packed pages with
more than 600 brand new products.
On sale now, only £2.75

Available from all branches of WHSMITH and
Maplin shops nationwide. Hundreds of new products
at super low prices!