


ETI
ELECTRONICS
TODAY INTERNATIONAL

SAVE MONEY
Battery
quick-checker

SERENADE YOURSELF
MIDI-controlled
voice harmoniser

Free!
 Discount Voucher
 EdWin NC PCB software

WAY
TO GO,
CAR!

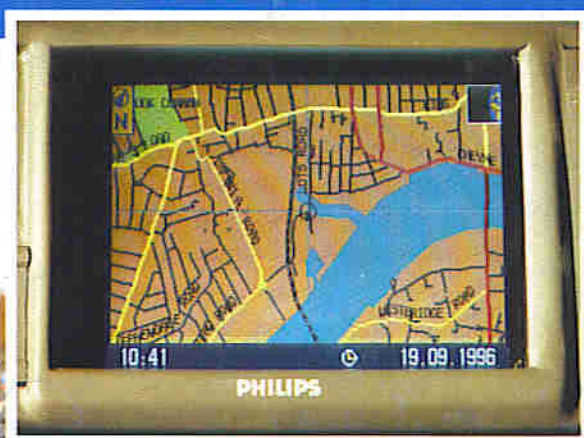

Bin It!

10% off

and

EDWIN NC EDA PCB Design Software

Special ...
 from Swift Designs
 and ETL.
 See Advert for Details

Pay More!

The new
generation of
GPS auto-nav
systems

DON'T MELT DOWN
Household
Freezer Alarm

PLUS

- **New! Fast Fivers**
- **Value! High Impedance Multimeter Amplifier**
- **PIC-controlled! Video Line Trigger**

APR 97 04 >



FOR ENTHUSIASTS
 BY ENTHUSIASTS
NEXUS

VOLUME 26 No. 4 £2.35 USA \$4.95



"extremely good value for money for such a comprehensive package"

Practical Wireless July 96

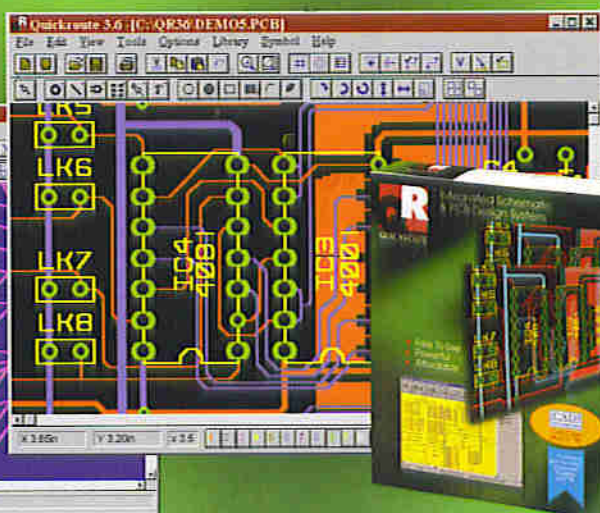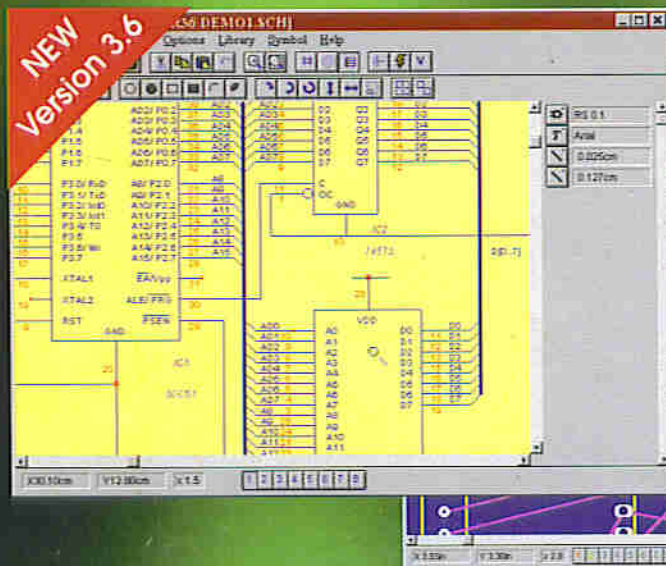

Schematic capture, Autorouting & Design Checking for just £149*

NEW
Quickroute 3.6 Designer £149*


Take a look at Quickroute 3.6 Designer and you might be surprised! For just £149* you get easy to use schematic design (automatic junction placement, parts-bin, etc), "one click" schematic capture, autorouting on 1 or 2 layers, design rule & connectivity checking and a starter pack of over 260 symbols.

NEW
Quickroute 3.6 PRO+ £399*

For those needing more power & more features there is Quickroute 3.6 PRO+. For just £399 you get multi-sheet schematic capture, 1 to 8 layer autorouting, net-list import/export, links to simulators, CAD/CAM file export, Gerber import/viewing, DXF WMF & SPICE file export, copper fill, advanced connectivity checking with automatic updating of a PCB from a schematic, the basic set of over 260 symbols and library pack 1 which includes a further 184 symbols. More symbols are available in additional library packs available separately.

Prices are Quickroute 3.6 Designer £149, Quickroute 3.6 PRO+ £399, SMARTRoute 1.0 £149.00, Library Packs £39 each. *Post & Packing per item is £6 (UK), £8 (Europe) and £12 (World). V.A.T must be added to the total.

NEW PLUG IN AUTOROUTER

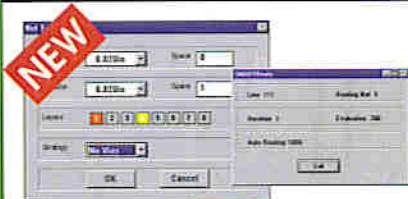

SMARTRoute is a new 32-bit autorouter from Quickroute Systems rated in 'category A' by Electronics World (Nov 96). SMARTRoute plugs straight into Quickroute 3.6, automatically updating Quickroute's menus with new features and tools.

SMARTRoute 1.0 uses an iterative goal seeking algorithm which works hard to find the best route even on single sided PCB's. SMARTRoute allows you to assign different algorithms, design rules, track & via sizes, layers used, etc to groups of nets for total flexibility. SMARTRoute 1.0 costs just £149*.



Tel 0161 476 0202 Fax 0161 476 0505

Quickroute Systems Ltd. Regent House Heaton Lane Stockport SK4 1BS U.K.


WWW: www.quickroute.co.uk EMail: info@quicksys.demon.co.uk



Contents

Volume 26 No.4

& Features & Projects

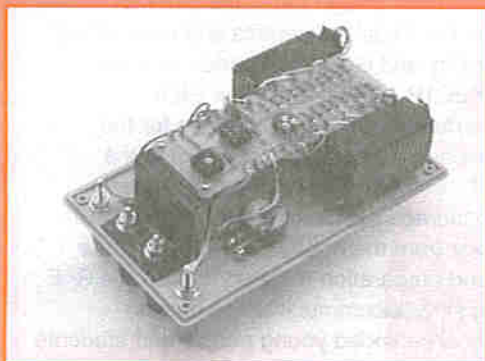

Way to Go, Car!

9

'Carin' is one of the new generation of auto-direction finders, with an extraordinary sense of direction to bring driver and destination together. Graham Whyte reports.

ETI Household Freezer Alarm

23

Don't get cold feet! Robert Penfold's freezer defrost alarm is the watchdog you need to guard your winter stores from premature thaw.

MIDI Controlled Voice Harmoniser

28

Singing in harmony with yourself doubles the voice power of pros and bathroom vocalists alike. Tom Scarff's design, based on the MSM6322 real-time audio controller, allows pitch-shift via a MIDI interface.

Experimenting with Video (Part 4) - A Video Line Trigger

36

The fourth part of our Video series by Robin Abbot is a video line trigger able to isolate a specific line of video for examination by oscilloscope, using a low-cost PIC microcontroller.

High Impedance Multimeter Amplifier and AF/RF Probe

45

You can give moving-coil multimeters a new lease of life, with Raymond Haigh's inexpensive accessory that gives you more accurate high impedance and signal measurements.

Fast Fivers - A Warbling Door Alert

53

The first in a series of low-cost, quick-to-build projects by Owen Bishop, useful around the home or in the workshop, and for teaching and learning as well. Each project has at least one interesting circuit point to aid in discovering electronics.

Battery Quick-Check

57

Do you have lonesome batteries rolling around on the bench, or want to know whether there's still life in a partly-used cell? Terry Balbinie's neat little battery checker health-checks AAs and PP3s.

Review: Electronics Principles 3.00

65

Educational software that introduces the principles of electronics, from basic to intermediate, with change-as-you-go circuit examples.

Regulars

News

4, 5, 7

PCB foils

68, 70

Round the Corner

74



SUBSCRIPTIONS
& BACK ISSUES HOTLINE:

01858 435344

ORDERS:
ENQUIRIES:

01858 435322

Lines Open Mon - 6.30pm

Subscribe & Save

Phone the
hotline and take
advantage of
our special offer
detailed on
page 44

High-powered, modern supply at a good price

Van Draper have brought out a new dual output power supply with full current-foldback overload and short circuit protection and a solid range of features.

The ADPS305 is a dual-output 0 - 30 volt, 0 - 5 amp regulated DC linear bench power supply, capable of operating in constant voltage and constant current modes, with isolated, serial or parallel operation switchable from the front panel: 0 - 30 volts/0 - 5 amps, 0 - 30 volts/0 - 10 amps or dual 0 - 30 volts/0 to 5 amps can be selected. In serial or parallel modes, the unit operates as a master/slave.

Output voltages can be tuned by both coarse and fine controls, with output voltage and current monitored by four 3.5-digit LCDs. Load regulation is better than 0.2 percent, and ripple is less than 5 mV. The steel-cased 350 x 320 x 150 mm unit is priced at £289.

For further information please contact Van Draper Electronics Ltd., Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL. Tel: 0116 277 1400 Fax: 0116 277 3945.



Radio Amateurs Exam: lower costs and quicker results from May 1998

The RA has proposed to simplify the format of the Radio Amateurs' Examination (RAE) so that results can be released more speedily and fees reduced. The RAE currently costs £19.40 per paper for each of two parts. Following an appeal from the Radio Society of Great Britain, the two papers will be amalgamated into one paper of 80 questions at a single cost of £26 from May 1998.

Candidates who already have a pass in one part of the RAE will be able to carry over that pass until May 1998, when they will need to re-sit for full new examination. Other changes agreed are a reduction in the one-off centre approval fee from £250 to £200 for centres running the examination.

80-channel CB sets fair

The Radiocommunications Agency has announced that 80-channel Citizens' Band sets will soon be available for UK users. This is in response to a questionnaire sent out to all CB licence-holders in 1995 and to meetings held by the RA for CB user groups - a demand for sets that would cover both UK and the European CEPT services was clearly indicated.

The UK CB type approval Specification (MPT 1382) has been revised to allow both these services in one set.

The RA and the RSGB hope that these rationalisations will encourage more people to take up amateur radio.

An RAE pass is required to obtain a Class B amateur radio licence, while a further pass in Morse Code at 12 words per minute is required to obtain a Class A licence. The RAE is held in examination centres around the country in May and December each year. For details of centres and examination procedures, contact City and Guilds of London Institute, 1 Giltspur St., London EC1B 1JP. Tel 0171 294 2468.

The decline in the number of new candidates for the amateur radio licence has been causing concern to the RSGB and other radio authorities for a number of years, despite efforts to encourage people to enter by stages with Novice licences. Aside from the hobby benefit of amateur radio, the practice and preparation required to pass the RAE is a valuable training in radiocommunications basics, particularly for practically-minded young people and students hoping to go into engineering and IT.

Manufacturers will still be able to produce sets incorporating any combination of the UK or CEPT channels, however, the Agency stresses that such sets may only be used in the UK.

The UK only service is in the 27.60215 - 27.99125 MHz band and the CEPT service in the 26.965 - 27.405 MHz band. A UK service between 934.0125 - 934.9625 MHz will be withdrawn on 31 December 1998. The Specification for that service was withdrawn in 1998.

Public enquiry line in the UK: 0171 211 0211.

Don't chew do it

Things Electronics Hasn't Fixed Yet - Don't try this at home! Apparently an electrician in Australia turned to his work to help take his mind off a ban on smoking on site - in (to say the least) a somewhat unusual way - we hope. Troubled by internal pains, he was taken to hospital, where tests showed that he had three times the standard safety level of lead in his bloodstream. You will be glad to hear that this was not the result of working in too-close proximity to gently curling solder fumes, much though ingestion of the Constructor's Best Friend should be avoided - this was more solid fare. The dedicated worker had been chewing nearly a yard (1m for the youngsters) of cable a day during his stints on building sites where smoking was not allowed - for 10 years.

Wind up

Britain's wind farms produced a record 505,000,000 units of electricity in 1996, a 49 percent rise over 1995, and bringing the total output over the last five years to over a (UK) billion units. Figures released in February show that the 34 wind farms now operating in the UK are outputting sufficient to meet the average power demand of around 120,000 households.

Underneath the lamplight ...

A couple promenading in the streets of Paris were shocked when their normally mild-mannered dog suddenly leapt into air, bit her owner, and ran off howling into the darkness. The unfortunate dog had received a far worse shock - investigation showed that electricity escaping from a damaged street lamp in the damp street had put a several thousand volts onto a metal pavement grille. At the time of reporting, she was still missing. It's tough when you can't go for a breath of air without strapping on rubber boots and a multimeter.

Fish in power sauce?

US explorer John Lundberg of the University of Arizona and a team of Brazilian researchers have been surveying fish in the rivers of the Amazon basin for the last four years and have come up with a number of new species - including a new genus of electric fish, now called *Magosternarchus*. These will not be gracing the shack fishtank, nor, we calculate, will the blind, pink electric *Orthosternarchus tamandua* - much better that they should stay rarely seen in their riverine habitats. But as pharmacists trawl the rainforests for new medicines and wonder drugs, how long before battery scientists start showing more than a culinary interest in fish?


Web-page authoring software

Users of the industry-wide page-design and publishing software QuarkXPress(tm) can now move onto the Internet with QuarkImmedia(tm), the new comprehensive Internet and multimedia authoring and viewing application from Quark Inc. For use in conjunction with QuarkXPress or QuarkXPress Passport(tm) 3.32 or later, combines the power, ease of use and typographic control for which Quark is famous with the interactive requirements of multimedia, and can be obtained for Danish, Dutch, French, German, Italian, Norwegian, Spanish and Swedish as well as International English. Both components - the QuarkImmedia design software and QuarkImmedia Viewer, are now available for Macintosh and Power Macintosh computers. A Windows version is planned for a later date. QuarkImmedia Viewer is a stand-alone multimedia delivery applications that allows users who don't own QuarkXPress or QuarkImmedia view and interact with QuarkImmedia projects

For more information, contact Adriaan Roosen, Quark Media House BV, tel Netherlands +31 318 693300 or the Quark Internet home page at <http://www.quark.com>.

Crop planning with precision GPS

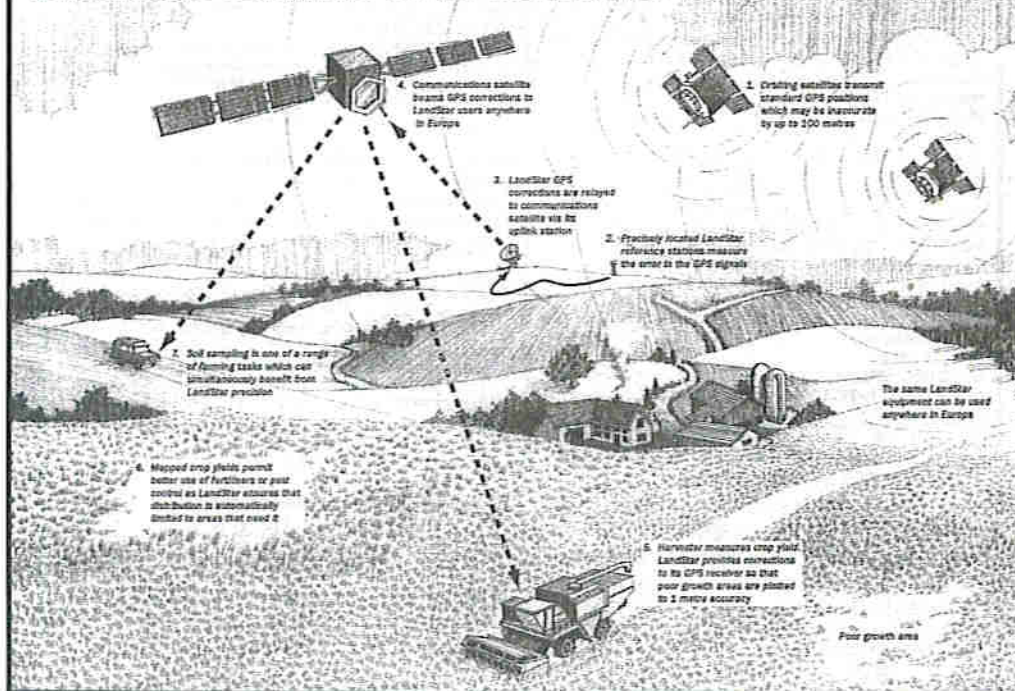PRECISION FARMING WITH LANDSTAR DGPS POSITIONING



Following the launch of the Italsat F2 comms satellite, Racal Survey has introduced a high-accuracy positioning service for precision farming techniques.

The Racal Landstar Europe differential GPS can now provide farmers and agricultural contractors with positioning accurate to 1 metre anywhere in Europe 24 hours a day in any weather conditions. The new service removes the need for local reference stations and comms links which some users had found impractical and unreliable. The LandStar will provide a precise location anywhere from the Western Atlantic to east of Moscow, and from the Straits of Gibraltar to Scandinavia. A 24-hour monitoring station at Aberdeen maintains the quality and accuracy of the differential GPS corrections continuously.

There is some more background to differential GPS in "What a difference a 'd' makes" in our leading feature this month.

RUSSIAN BORDER GUARD BINOCULARS £1799

Probably the best binoculars in the world! ring for brochure

VEGARUSSIAN MULTIBAND World communications receiver, 9 wave bands, (5 short, 1 LW, 1 MW, 1 MW) internal ferrite and external telescopic aerials, mains or battery. Large, typically Russian radio £45 ref VEGA**NEW LASER POINTERS** <5mw, 75 metre range, hand held unit runs on two AA batteries (supplied) £70m £29 ref DEC49**MULTIBAND RADIO** Compact general purpose radio receiver covering air, pb, tv, cb etc. Squelch vol and tuning £24 ref MB1**DIVING RODS** £3.99 a pair! ref EF111**MOONSHINE BIBLE** 270 page book covering the production of alcohol from potatoes, rice, grains etc Drawings of simple home made stills right through to commercial systems. £12 ref M53**NEW HIGH POWER MINI BUG** With a range of 800 metres or more and up to 100 hours use from a PP3 this will be popular! Bug measures less than 1" square! £28 ref LOT102**BUILD YOUR OWN WINDFARM FROM SCRAP** New publication gives step by step guide to building wind generators. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81**PC KEYBOARDS** PS2 connector, top quality suitable for all 286/386/486 etc £10 ref PCKB. 10 for £85.**TRACKING TRANSMITTER** range 1.5-5 miles, 5,000 hours on AA batteries, also transmits info on car direction and motion/Works with any FM radio. 1.5" square. £65 ref LOT101**ELECTRIC DOOR LOCKS** Complete lock with both Yale lock and 12v operated deadlock (keys included) £10 ref LOT99**SURVEILLANCE TELESCOPE** Superb Russian zoom telescope adjustable from 15x to 60x complete with metal tripod (impossible to use without this on the higher settings) 65mm lens, leather carrying case £149 ref BAR69**WIRELESS VIDEO BUG KIT** Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP79 (probably not licensable!)**GPS SATELLITE NAVIGATION SYSTEM** Made by Garmin, the GPS38 is hand held, pocket sized, 255, position, altitude, graphic compass, map builder etc £179 ref GPS1**CCTV CAMERA MODULES** 46x70x29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, COIR, 512x492 pixels, video output is 1v p-p (75 ohm) Works directly into a scan or video input on a tv or video. IR sensitive. £79.95 ref EF137**IR LAMP KIT** Suitable for the above camera, enables the camera to be used in total darkness! £6 ref EF138**INFRA RED POWERBEAM** Handheld battery powered lamp, 4 inch reflector, krypton bulb, gives out powerful infrared light! 4 D cells required. £29 ref PB1**MONO VGA MONITORS**, Perfect condition. Compaq, 14", 3 months warranty £29 ref MVGA**SUPER WIDEBAND RADAR DETECTOR** Detects both radar and laser. X, K and KA bands, 360 degree coverage, front and rear wave guides, may be illegal to use! 1.1x2.7x4.6" £149 ref RD2**9 WATT CHEFTAN TANK LASERS**

Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, no circuit diagrams due to MOD, new price £50, 0007 us? £199. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. £199 for one. Ref LOT4

TWO WAY MIRROR KIT Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) includes full instructions. £12 ref TW1**NEW LOW PRICED COMPUTER/WORKSHOP/HI-FI RCB UNITS** Complete protection from faulty equipment for everybody! Inline unit fits in standard IEC lead (extends it by 750mm), filtered in less than 10 seconds, reset/test button, 10A rating. £6.99 each ref LOT5. Or a pack of 10 at £49.90 ref LOT6. If you want a box of 100 you can have one for £250!**WIND UP FLYING PARROT!** Genuine parrot that flaps its wings and flies for up to 50 meters £6 ref EF2**RADIO CONTROLLED CARS FROM £6 EACH!!!!** All returns from famous manufacturer, single channel (left, right, forwards, backwards) £6 ref LOT1. Two channel with more features £12 ref LOT2**THOUSANDS AVAILABLE RING/FAX FOR DETAILS!****MAGNETIC CARD READERS** (Swipes) £9.95 Cased with fileleads, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well? complete with control electronics PCB. just £9.95 ref BAR31**WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA?** We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74**COIN OPERATED TIMER KIT** Complete with coin slot mechanism, adjustable time delay, relay output, put a coin slot on anything you like! TV's, videos, fridges, drinks outboards, HiFi. takes 50p's and £1 coins. DC operated, price just £7.99 ref BAR27**ZENITH 900 X MAGNIFICATION MICROSCOPE** Zoom, metal construction, built in light, shrimp farm, group viewing screen, lots of accessories. £29 ref ANAYLT**AA NICAD PACK** Pack of 4 tagged AA nicads £2.99 ref BAR34**NIGHTSIGHTS** Model TZS4 with infra red illuminator, views up to 75 metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty**LIQUID CRYSTAL DISPLAYS** Bargain prices, 16 character 2 line, 99x24mm £2.99 ref SM1623A

20 character 2 line, 83x19mm £3.99 ref SM2020A

16 character 4 line, 62x25mm £5.99 ref SMC1640A

TAL-1, 110MM NEWTONIAN REFLECTOR TELESCOPE

Russian Superb astronomical scope, everything you need for some serious star gazing! up to 169x magnification. Send or fax for further information ref TAL-1, £249

SOLAR ENERGY/GENERATOR PLANS For your home, loads of info on designing systems etc £7 ref PV1**SOLAR COOKERS** Comprehensive guide to building solar powered cookers, includes plans, recipes, cooking times etc £7 ref SBC1**WOLVERHAMPTON ELECTRONICS STORE NOW OPEN IN WORCESTER ST TEL 01902 22039****CENTRAL POINT PC TOOLS** Award winning software, 1,300 virus checker, memory optimiser, disc optimiser, file compression, low level formatting, backup scheduler, disk defragmenter, undelete, 4 calculators, D base, disc editor, over 40 viewers, remote computing, password protection, encryption, comprehensive manual supplied etc £8 ref lot 97 3.5" disks**COLOUR CCTV VIDEO CAMERAS, BRAND NEW AND, CASED, £119.****PERFECT FOR SURVEILLANCE, INTERNET, VIDEOCONFERENCING, SECURITY, DOMESTIC VIDEO****Works with most modern video's, TV's, Composite monitors, video grabber cards etc****Pal, 1v P-P, composite, 75ohm, 1/3" CCD, 4mm F2.8, 500x582, 12vdc, mounting bracket, auto shutter, 100x50x180mm, 3 months warranty, 10 or more £99 ea****MICRO RADIO** It's tiny, just 3/8" thick, auto tuning, complete with headphones. FM £9.99 ref EP35**HANDHELD SCANNERS** 10 channel, built in charger, LCD display £119 ref B110B, 100 channel model £229 ref B110E**SMOKE MACHINE** 42.3 cubic metres a min from this mains operated machine £299 ref G002B, smoke fluid £25 (5 litres) gives about 2.5 hours use. ref: G002AA**Check out our WEB SITE****full colour interactive 1997 catalogue**<http://www.pavilion.co.uk/bull-electrical>**IBM PS2 MODEL 150Z CASE AND POWER SUPPLY**

Complete with fan etc and 200 watt power supply. £9.95 ref EP67

1.44 DISC DRIVES Standard PC 3.5" drives but returns so they will need attention **SALE PRICE £4.99** ref EP68**1.2 DISC DRIVES** Standard 5.25" drives but returns so they will need attention **SALE PRICE NOW ONLY £3.50** ref EP69**PP3 NICADS** Unused but some storage marks. £4.99 ref EP52**GAS HOBS AND OVENS** Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob £19 ref BAR316. Basic small built in oven **SALE PRICE £59** ref EP73**ENERGY BANK KIT** 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc £99 ref EF112**PASTEL ACCOUNTS SOFTWARE**, does everything for all sizes of businesses, includes wordprocessor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual. 90 days free technical support (01342-326009 try before you buy!) **SALE PRICE £9.95** ref SA12. SAVE £120!!!**PC PAL VGA TO TV CONVERTER** Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. **SALE PRICE £25** REF SA34**YUASHA SEALED LEAD ACID BATTERIES** Two sizes currently available this month. 12v 15AH at £18 ref LOT8 and 6v 10AH at just £6 ref LOT7.**ELECTRIC CAR WINDOW DE-ICERS** Complete with cable, plug etc **SALE PRICE JUST £4.99** REF SA28**AUTO SUNCHARGER** 155x300mm solar panel with diode and 3

metre lead fitted with a cigar plug 12v 2watt. £12.99 REF AUG10P3

PROJECT STRIPPERS Small cased UNITS ideal for stripping, lots of useful goodies including a smart case 120X150X50mm with feet etc. and lots of components. **SALE PRICE JUST £10 FIVE REF MD1** or a pack of 20 for £19.95 ref MD2.**SOLAR POWER LAB SPECIAL** You get TWO 6"x6" 6v 130mA solar cells, 4 LEDs, wire, buzzer, switch plus 1 relay or motor Superb value kit **SALE PRICE JUST £4.99** REF SA27**13.8V 1.9A PSU** cased with leads. Just £9.99 REF MAG10P3**UNIVERSAL SPEED CONTROLLER KIT** Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17**SOLAR NICAD CHARGERS** 4 x AA size £9.99 ref 6P476, 2 x C size £9.99 ref 6P477**VIEWDATA SYSTEMS** made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. **SALE PRICE £12.99** REF SA18**MEGA POWER BINOCULARS** Made by Helios, 20 x magnification, precision ground fully coated optics, 60mm objectives, shock resistant caged prisms, case and neck strap. £89 ref HPH1**GIANT HOT AIR BALLOON KIT** Build a 4.5m circumference, 1.8m high fully functioning balloon, can be launched with home made burner etc. Reusable (until you loose it!) £12.90 ref HA1**AIR RIFLES .22** As used by the Chinese army for training purposes, so there is a lot about! £39.95 REF EF78. 500 pellets £4.50 ref EF80.**VIDEO SENDER UNIT.** Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £25 REF: MAG15 12v psu is £5 extra REF: MAG5P2***MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range up to 2 km in open country. Units measure 22x2x155mm. Including cases and earpieces 2xPP3 req'd £37.00 pr REF: MAG30***FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever! why pay £700? or price is £18 REF: EF62 (kit) Transmits to any FM radio Built and tested version now available of the above unit at £45 ref EXM34***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd £14 REF: MAG14**GAT AIR PISTOL PACK** Complete with pistol, darts and pellets £14.95 REF EP82B extra pellets (500) £4.50 ref EF80.**6"x12" AMORPHOUS SOLAR PANEL** 12v 155x110mm 130mA. **SALE PRICE £4.99** REF SA24**FIBRE OPTIC CABLE BUMPER PACK** 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

SHORTS

A study by market research consultancy Frost & Sullivan has predicted that the European printed circuit board industry will stabilise and grow steadily, rather than swiftly, in the years leading up to 2002. Badly hit during the recession, the industry lost around 1600 manufacturers since the early 1990s. As with many industries, the trend during the recession has been towards fewer and larger companies, still under "extreme pressure" on profit margins, despite increased sales overall. Put simply, this means that companies are being forced to sell greater amounts for lower prices pro rata. Structural trends for the future include greater use of surface mount technology, use of even larger scale integration on chips, and higher wiring densities, including multi-layer boards of more than 12 layers, with buried vias. Telecommunications looks set to be the biggest market for the most advanced boards.

National Semiconductor have produced a low-voltage CD-quality 'Boomer' audio amplifier chip, the LM4863, designed mainly with laptop and desktop computers in mind, but also suitable for powered loudspeakers and portable video games. The device can alternately power stereo headphones or stereo speakers, at up to 1.5W per channel as a speaker-driver. This is a single-chip solution replacing two mono power amps, a headphone amp, and load switching circuitry between headphone and speaker modes, reducing board space, design


time and cost. The device comes in 16-pin small surface mount or 16-pin dual in line packaging ...

Northrop Grumman Naval Systems, developing advanced thermal batteries for the US Navy and McDonnell Douglas, has joined forces with specialist ceramics manufacturer ART to work on commercialising energy cells based on lithium-metal sulphide (LiMS) technology and aluminium nitride battery separators. LiMS is one of the technologies involved in high temperature battery research over the last two decades. The developers believe that the use of AlN separators, while costing more per unit than current magnesium oxide separator powder, will give a "much higher" battery cycle life, reducing costs overall. Electrically powered vehicles are one of the likely commercial applications in the fullness of time ...

In Washington, USA, an Internet International Ad Hoc Committee (IAHC) has been named to resolve issues arising from a proposal to establish further global registries and international Top Level Domains (iTLDs). New iTLDs would add to the current three-letter tags (.com, .net, .org and so on) that end many Internet e-mail and World Wide Web addresses. The committee will, among other things, be charged with looking at issues including trademark and infringement, administration of registry operations, fees, etc. and may report in January 1997. The web site <http://www/iahc.org> will carry documents for public comment.

Fast microcontroller development kits

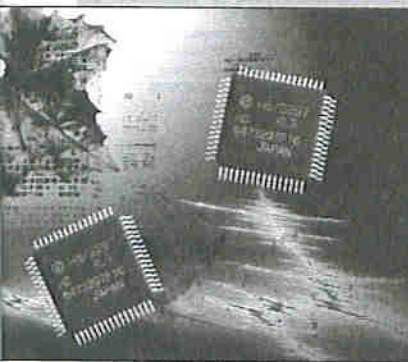The Hitachi H8/300 have been announced as the world's fastest microcontrollers yet. The H8/3297 series of 8/16-bit microcontrollers gives a minimum instruction cycle time of 125ns within a powerful general register architecture, memory options up to 69 Kbytes of rom and 2 kbytes of ram in mask rom and one-time programmable eprom. The device has 51 I/Os and includes 64-pin Shrink dip packaging.



The microcontrollers are supported by a number of development tools, including a low-cost evaluation kit EVB3334Y including the H8/300 evaluation board and

compiler, and the PCE3297 in-circuit emulator. The EVB3334Y also includes an evaluation copy of IAR's C compiler and C-Spy source level debugger, and all documentation and cables. The PCE emulator provides a debugging tool with multi-level break point logic, providing program execution and data value breaks as well as a pass counter. It also has a real-time trace facility.

Hitachi also supply CIDE, a Windows 3.1-based C source level debugger, allowing real time debugging of C code in a point and click screen environment, with single step at C level, breakpoints on C statements, C level real-time trace, monitoring and modifying of complex C structures and variables within a watch window, access to all the features of the emulated device, and I/O and memory-dump windows. The aim is to provide an efficient solution for engineers developing embedded applications in C, including automotive airbags, air conditioning, cordless phones and process control applications. The S5 PCE emulator package includes the emulator, IAR C compiler and CIDE source level debugger.

For information contact Mr. Vince Pitt, Hitachi Europe Ltd., Whitebrook Road, Lower Cookham Road, Maidenhead, Berks SL6 8YA. Tel 01628 585163 Fax 01628 585160.

MODSMODSMODSMODSMODS

PCB Shake'n'Etch ETI February 1997

If you are unable to obtain the LM 3911 temperature controller ic, please write to ETI Shake'n'Etch Worksheet (address on page 74) for an alternative. The LM 3911 has apparently been withdrawn.

Overseas Readers

To call UK telephone numbers, replace the initial 0 with your local overseas access code plus the digits 44.

DIFFERENTIAL THERMOSTAT KIT Perfect for heat recovery, solar systems, boiler efficiency etc. Two sensors will operate a relay when a temp difference (adjustable) is detected. All components and pcb. £29 ref LOT63

MAGNETIC RUBBER TAPE Selfadhesive 10 metre reel, 8mm wide perfect for all sorts of applications! £15 ref LOT67

RADIO METERS - REMEMBER THESE? Glass bulb on a display stand that contains four vanes that rotate when exposed to sunlight, scientific novelty for £8.99 ref SC120

MAINS POWER SAVER UK made plug in unit, fitted in seconds, can reduce your energy consumption by 15%. Works with fridges, soldering irons, conventional bulbs etc. Max 2A rating. £9 each ref LOT71, pack of 10 £69 ref LOT72

YUASHA SEALED LEAD ACID Batteries, ex equipment but ok bargain price just £5.99 each ref YA1. 100 or more £3.50 each.

DC TO DC CONVERTERS

DRM52 input 10-40vdc output 5v 8A £15 DRM129 input 17-40vdc output 12v 8A £18 DRM158 input 20-40vdc output 15v 8A £18 DRM248 input 29-40vdc output 24v 8A £12 DRS123 input 17-40vdc output 12v 3A £10 DRS153 input 20-40vdc output 15v 3A £20 DRS243 input 29-40vdc output 24v 3A £8

INSTALL A COINBOX FOR LESS THAN £20 Convert any standard phone into a coinbox with this kit, some mods required plus hinges and a lock. £19 ref CBT1

HITACHI LM225X LCD SCREENS 270x150mm, standard 12 way connector, 640x200 dots, tec spec sheet. £15 each ref LM2

VARIABLE CAPACITORS Dual gang, 60x33x45mm, reduction gearing, unknown capacity but probably good quality (military spec) general purpose radio tuner. £9 ref VC1

ELECTRONIC FLASH PCB Small pcb fitted with components including a flash tube, just connect 12vdc and it flashes, variable speed potentiometer. £6 ref FLS1

THIEF PROOF PEN! Amazing new ball point pen fitted with a combination lock on the end that only you know! £2.49 ref TP2

JUMBO BI COLOUR LEDS PCB with 15 fitted also 5 giant seven segment displays (55mm) £8 ref JUM1

HOME DECK CLEARANCE These units must be cleared! leads, a n infra red remote query keyboard and receiver, a standard UHF modulator, a standard 1200/75 BT approved modem and loads of chips, capacitors, diodes, resistors etc all for just £10 ref BAR33.

6.8MW HELIUM NEON LASERS New units, £65 ref LOT33

COINSLOT TOKENS You may have a use for these? mixed bag of 100 tokens £5 ref LOT20

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £65 ref FOX1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon.

£45 ref FITKE1

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15 ref FIEH2.

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means- cause it to levitate. £10 ref FIGRA1.

WORLDS SMALLEST TESLA COIL/LIGHTNING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, "Plasma in a jar", St Elmo's fire, Corona, excellent science project or conversation piece. £5 ref FIBTC1/LG5.

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10 ref FICVL1.

VOICE SCRAMBLER PLANS Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6 ref FNV59.

PULSED TV JOKER PLANS Little hand held device utilizes pulse techniques that will completely disrupt TV picture and sound! works on FM too! DISCRETION ADVISED. £8 ref FJTJ5.

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £8 ref FIBHT1.

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc £12 ref FALC7.

MYSTERY ANTI GRAVITY DEVIANCE PLANS Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £6 ref FIAHT1K.

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PCB boards, jewellery, coins, small parts etc. £6 ref FAULB1.

ULTRA HIGH GAIN AMP/STETHOSCOPIC MIKE/ SOUND

AND VIBRATION DETECTOR PLANS Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £6 ref FRIHGA7

WOLVERHAMPTON ELECTRONICS STORE NOW OPEN IN WORCESTER ST TEL 01902 22039

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate £6 ref FIDOG2

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £12 ref F/LLIST1

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 ref FILL51

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £6 ref FIPSP4

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 ref F/TELEGRAB.

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £5 ref F/BD1.

ELECTROMAGNETIC GUN PLANS Projects a metal object a considerable distance-requires adult supervision £5 ref F/EML2.

ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £5 ref F/EMA1.

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in hard to get or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £8 ref F/PMS5

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 ref F/HVMT/TC14.

MEGA LED DISPLAYS PCB fitted with 5 seven segment displays each measuring 55 x 38mm. £5 ref LED5

MOD TRANSMITTING VALVES 6J180E £80 ref LOT112
SWITCHED MODE PSU'S 244 watt, +5 32A, +12 6A, -5 0.2A, -12 0.2A. There is also an optional 3.3v 25A rail available. 120/240V V.P. Cased, 175x90x145mm. IEC inlet. Suitable for PC use. (S drive connectors 1 mboard). £15 ref LOT135.

**Check out our
WEB SITE
full colour interactive
1997 catalogue
http://www.pavilion.co.uk/bull-electrical**

VIDEO PROCESSOR UNITS?/6v 10AH BATTERIES/24V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2x 6v 10AH sealed lead acid batts, pcb's and a BA? 24v toroidal transformer (mains in), sold as seen, may have one or two broken knobs etc due to poor storage. £15.99 ref VP2

RETRON NIGHT SIGHT Recognition of a standing man at 300m in 1/4 moonlight, hermetically sealed, runs on 2 AA batteries, 80mm F1.5 lens, 20mw infrared laser included. £325 ref RETRON

MAKE YOUR OWN CHEWING GUM KIT Everything you need to make real chewing gum, even the bowl and tree sap from the Sapodilla tree £7.99 ref SC190

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 Mhz but easily changed to cover 63-150 Mhz. Works with a common 9v (PP3) battery. 0.2W RF. £9 ref 1001.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £15 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob your self but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £15 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob your self but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM.

BUILT IN 5 watt amplifier, inc speaker. £18 ref 1013.

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1.200 w power handling, microphone included. £17 ref 1014.

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3RF stages, microphone and audio preamp included. £24 ref 1028.

STROBE LIGHT KIT Adjustable from 1-60 Hz (a lot faster than conventional strobes). Mains operated. £17 ref 1037.

COMBINATION LOCK KIT 9 key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £13 ref 1114.

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £9 ref 1130.

ROBOT VOICE KIT Interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! 12vdc £9 ref 1131.

TELEPHONE BUG KIT Small bug powered by the phone line, starts transmitting as soon as the phone is picked up! £12 ref 1135.

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction controls supplied with 12 LEDs (you can fit triacs instead to make kit mains, not supplied) 9-12vdc £17 ref 1026.

12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2A transformer also required. £8 ref 1069.

HELPING HANDS Perfect for those fiddly jobs that need six hands, 6 ball and socket joints, magnifier. £7.99 ref YO67A

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recorders etc, adjustable sensitivity. £10 ref 1073.

PREAMP MIXER KIT 3 input mono mixer, sep bass and treble controls plus individual level controls. 18vdc, input sens 100mA. £15 ref 1052.

SOUND EFFECTS GENERATOR KIT Produces sounds ranging from bird chirps to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045.

15 WATT FM TRANSMITTER (BUILT) 4 stage high power, preamp required 12-15vdc, can use ground plane, yagi or open dipole. £69 ref 1021.

HUMIDITY METER KIT Builds into a precision LCD humidity meter, 9ic design, pcb, lcd display and all components included. £29

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1.640k, serial port, hard drive with min 100k free. £24.99

MAGNETIC MARBLES They have been around for a number of years but still give rise to curiosity and amazement. A pack of 12 is just £3.99 ref GVR20

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £45 ref NIK39

Miniature adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12vDC adjustable from 0-30 secs. £4.99

HY1260M, 12vDC adjustable from 0-60 mins. £4.99

HY2405S, 240v adjustable from 0-5 secs. £4.99

HY24060m, 240v adjustable from 0-60 mins. £6.99

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

POWER SUPPLY fully cased with mains and o/p leads. 17v DC 900mA output. Bargain price £5.99 ref MAG59P

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £12.00 REF: MAG8P2.

FUTURE PC POWER SUPPLIES These are 295x135x50mm, 4 drive connectors 1 mother board connector. 150watt, 12v fan, iec inlet and on/off switch. £12 ref EP6.

VENUS FLY TRAP KIT Grow your own carnivorous plant with this simple kit. £3 ref EP4.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together! believed to cause rain! £3 a pair REF EF29

3' by 1' AMORPHOUS SOLAR PANELS 14.5v, 700mA 10 watts, aluminium frame, screw terminals. £55 ref MAG45.

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needles! good to experiment with. £9 ref 7P30

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £9 ref 7P38.

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 miles per hour! Range of over 200 metres! £8.99 ref R9.

COMPAQ POWER SUPPLIES WITH 12V DC FANS Ex equipment psu's, some ok some not but worth it for the fan alone! probably about 300 watt PC unit with IEC input. £3.50 each ref CQ1

BALLON MANUFACTURING KIT British made, small blob blows into a large longlasting balloon, hours of fun! £3.99 ref GVE99R

9-0-9V 4A TRANSFORMERS, chassis mount. £7 ref LOT19A.

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb for just £4.99 ref LOT16 or a bumper pack of 50 displays for just £29 ref LOT17.

SOLID STATE RELAYS
CMP-DC-200P 3-32vdc operation, 0-200vdc 1A £2.50
SMT2000/3 3-24vdc operation, 28-280vac 3A £4.50

**SAE FOR FREE
COLOUR CATALOGUE**

**WE BUY SURPLUS STOCK
FOR CASH
SURPLUS STOCK LINE 0802 660377**

Way to go, Car!

Carin is part of the new generation of GPS-based in-car get-you-to-your-destination aids. Now the car really does know the way ... Graham Whyte reports.

What do you get when you cross a Wheatstone bridge with a sidereal satellite, with a CD-I, with the highways department? Only so far ... but add a fluxgate compass and several layers of digital mapping, and you arrive at Carin, the new in-car navigation and information system from Philips. The system is controlled from a "Man-Machine Interface" (MMI) front-end, though calling Carin a 'machine' is an impressive understatement.

Conceived early in the 1980s, Carin is one of several in-car navigation systems to reach the public in mainland Europe and America in recent years. In the UK, however, it appears to have stolen the march, at least inside the M25 "London bypass", where I suspect it has been fully operational for longer than Philips have yet admitted - like most new, complicated digital systems, it has not been without its share of teething troubles. But the £3,000 after-market (retro-fit) price-tag will not remain exclusively "capital" expenditure - by the end of 1997 most major conurbations should be looking at the sky to find out where on earth they are - and motorway guidance will provide the missing links for the bits in between.

Why do we need this technology? What's wrong with using the good old A-Z? Quite a bit, if you're driving a car - until someone comes up with a way to convert an entire map-book into a head-up display, stopping to look is the only safe option. And what do you do when you don't know quite where you are - and then you find your destination is on the page join?

Ever since the ancient mariners' race for a positional fix inspired the Harrison chronometers, man has had a passion (a fixation?) to know his exact whereabouts. When all you had to do was find the New World, near enough was often good enough, but nowadays, when we want to get to B to A, we don't mean A+ or A-. If you know the approximate bearing, most scouts could get you to B from A with nothing much more than a watch (even a digital one), as long as the sun is out (and how often is that?). But how do you find your way when you (a) don't know the distance and bearing to your destination, and (b) are enclosed in a dynamic environment constantly re-positioning itself in time and space - like a car?

Take one passenger, add one disc

When Martin Thoone addressed the topic in the *Philips Technical Review*, December 1987, he pointed out that the most reliable in-car navigational aid available at that time was called a "passenger". Note that he said "in-car" - electronic and radio nav has been around in boats since Decca first criss-crossed the English Channel when Marconi was a brand-leader. By the mid-1980s avionics navigation was taken for granted. But none of this spawned an electronic automotive guidance system that needed neither specialised training or a massive support infrastructure such as range-finding beacons.

And - significantly - there was no low-cost means of storing the huge amounts of data in a detailed electronic map of even the smallest town.

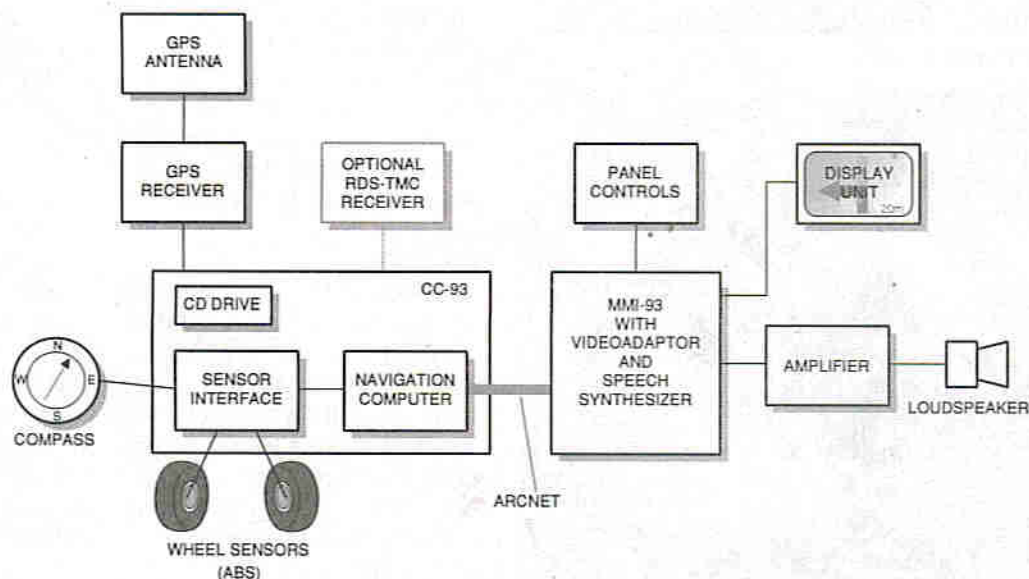


Figure 1: the Carin system schematic

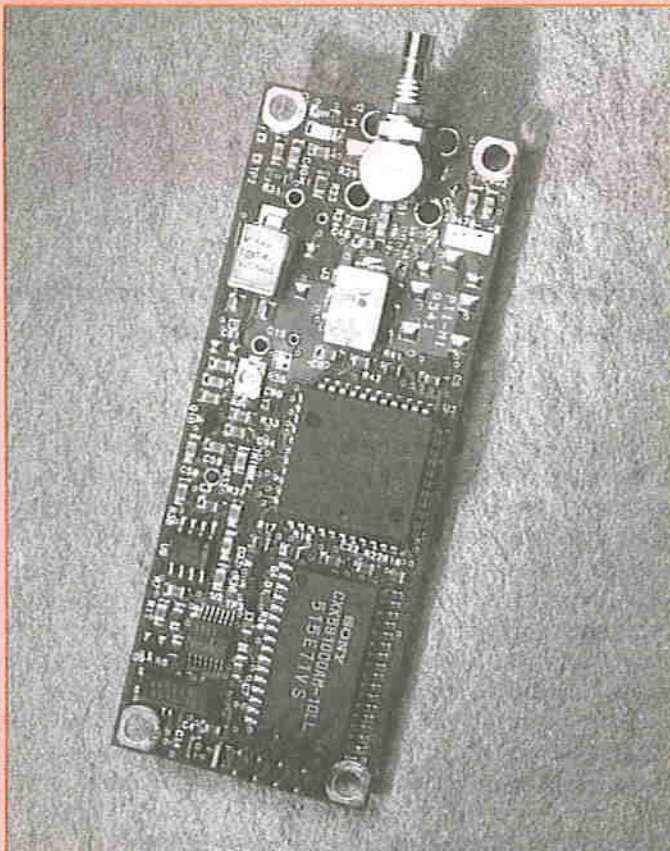


Figure 2: a Trimble GPS engine high integration circuit board
Trimble engine: photograph courtesy of Trimble.



Figure 3: the LCD panel *in situ*

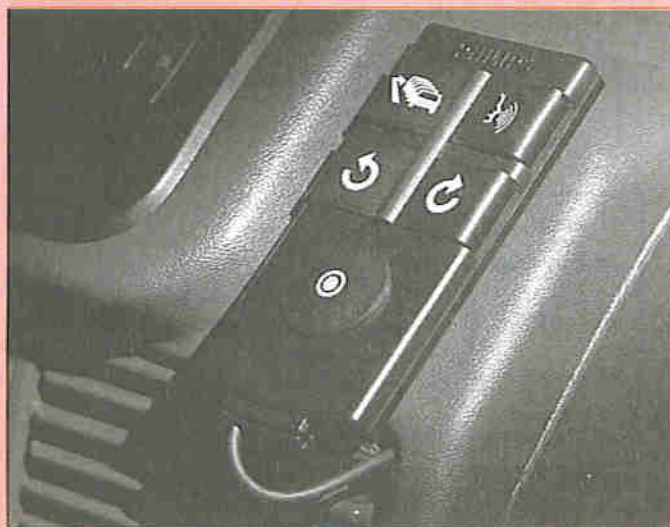


Figure 4: the selection keypad

That was in 1987 - but enter a technological revolution that allowed manufacturers to put Carin and its rivals on the map: CD-I (Compact Disc Interactive), easily portable and able to store up to 700 Mbytes of data, the perfect medium for storing the digitised map data that interacts with Carin's sense of direction. To put it into perspective, the whole of Germany now fits onto one disc.

Clearly, CD-I is only part of the story (figure 1). Long before the digitised map is consulted, the CC-93 navigation computer system gathers positional information from three other sources: wheel sensors, compass and a GPS engine, currently supplied by Trimble (figure 2). The processed data is delivered to the driver via a full-colour LCD panel (figure 3) mounted on or in the vehicle fascia, and a speech synthesiser. Designated the MMI-93, this unit has a small, separate key pad (figure 4) that allows the driver to select command options from multiple-choice displays.

Billed as "the car of the not-too-distant future", the prototype British vehicle fitted with the forerunner of the present system (and a full qwerty keyboard) was designed by I.A.D (Industrial Automotive Design) of Worthing. The CD-I unit and CC-93 computer share a DIN enclosure accessible for changing discs. An Arcnet local area bus on coaxial cable hooks the CC-93 to the MMI-93.

Vehicle Location Probability Area (VLPA) is the Holy Grail of vehicle guidance system designers: we've all heard about the diminutive African tribe whose misfortune was to dwell in a land where the grass was taller than they were - well, the same sort of agonising goes on inside CC-93, as the components of the location system track the vehicle's VLPA. It uses three sources to contribute to a dead-reckoned position at any given moment (strictly speaking, at any given stretch of road within a few metres).

The first of these sources is a pair of sensors that measure the revolutions of the non-driven wheels and the distance each has travelled. As the differential action of their common axle will cause the wheels to travel at different speeds through bends and corners, so the two wheels will also travel different distances. This constantly-changing relationship provides the processor with enough data to calculate changes of direction as well as distance travelled.


Here comes the U.S. ... Navy

The second source is a fairly straightforward fluxgate compass that monitors the vehicle's bearing in relation to the earth's magnetic field. For a while, these two were considered sufficient to give reliable dead-reckoning - which is just as well, because that's all that they had. Then along came the US Navy with around 24 navigation satellites in sidereal orbit, to which they sold the key of the door. (The side door, anyway - only the Top Guns get to play with the real McCoy.)

Suddenly, Philips were able to add (sky)hooks to their belt and braces, and from 11,000 miles away Global Positioning System (GPS) satellites uprated the reliability (if not the accuracy) of the VLPA, and Carin came of age. Yet despite these detailed computations, all the system could know *for sure* was that the vehicle had travelled a certain distance, performed *n* changes of direction, was on some particular bearing, and that the GPS was indicating that the vehicle was either at a given point on the earth's surface (or somewhere in space ...)

So we have arrived at a point (if you'll excuse the pun) where the system can predict with almost cast-iron certainty

Figure 6: a "block diagram" of the navigation process

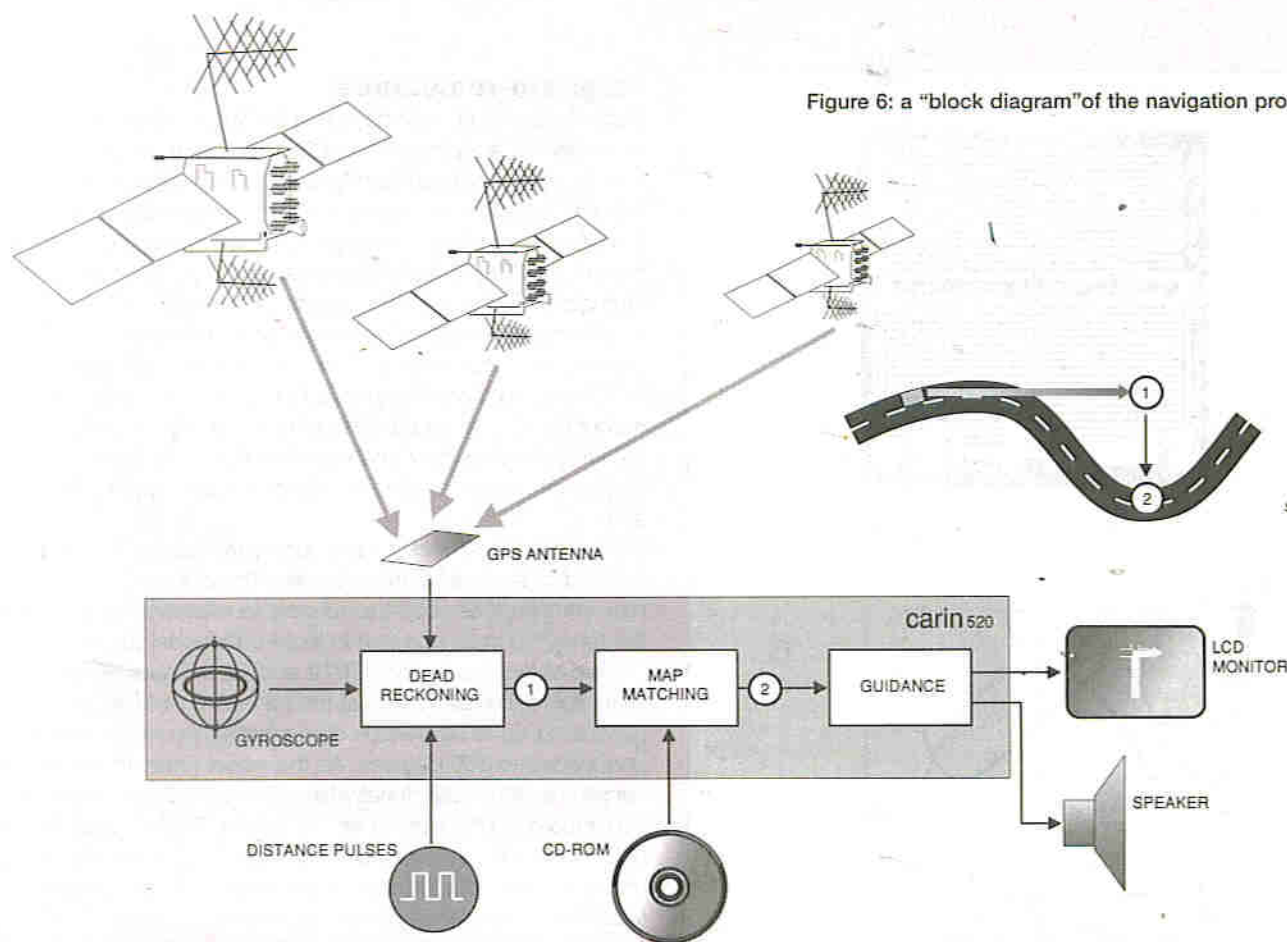

a VLPA within 50 metres or so either way. To turn all this relativity into facts, Carin uses the CC-93 processor to compare the VLPA with the topographical data retrieved from the CD-I, to generate a fix - that appears at last as a street name at the bottom of the MMI screen (figure 5).

But this is not just a location system: its ultimate function is to guide you to your chosen destination. It might be enlightening to discover you are at The Barbican, but suppose you really want to be in Holborn Viaduct?

The clever bit is the dynamic guidance system that updates itself as the vehicle heads towards your destination. You know the one about the driver who asked for directions and was told "you don't want to start from here, mate." Well, Carin follows that advice. Imagine an invisible fishing line, with the hook attached to your car and the rod located at your destination. In principle, that's Carin. It pin-points your destination, works backwards to your current position, and then reels you in with audio/visual directions generated via the MMI. We can use figure 6, which is a schematic of the Series 2 positioning and guidance process, as a block diagram to examine the functions and system components (figure 7) in more detail.

On the left of the diagram is the dead-reckoning function: the wheel sensors and compass have gone, replaced by a gyroscope and "distance pulses". The former combination is still used in some of the "original equipment" arrays factory-fitted by vehicle manufacturers such as BMW. On the aftermarket Series 2 version, Philips have discarded the wheel sensors and compass in favour of a pcb-mounted piezo-electrical vibration gyroscope, which functions as an angular rate sensor, with a feed from the vehicle's own electronic speedometer to provide a linear distance input. Although marginally less accurate, the gyroscope is easier to fit and requires no specialist calibration.



Figure 5: the Carin MMI display



Figure 7: the external hardware of the Carin system

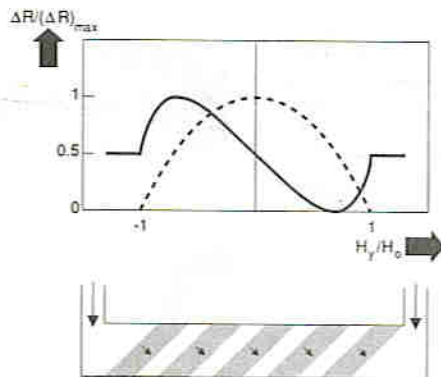
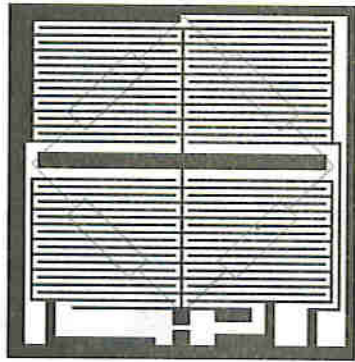


Figure 8: (a) (Top): Inside a KMZ10 magnetic transducer: the transducer is composed of ferromagnetic strips connected to form a Wheatstone bridge, and uses the magneto-resistance effect to measure magnetic fields. (b) shows the principle of a magneto-resistive transducer

Magneto-resistance

Both the electronic compass and the wheel sensors, which in later vehicles are part of the ABS mechanism, employ transducers to convert a magnetic flux into voltage, utilising the magneto-resistance effect in which the resistance of certain materials depends on the angle between the direction of the current and that of the magnetisation. Because the effect is strongest in ferromagnetic material, the transducer is made from multiple strips of a nickel-iron alloy. These strips are connected in four groups to form a Wheatstone bridge (figure 8). When the external magnetic field is zero, the direction of magnetisation will be parallel to the x axis. The angle between the direction of current and magnetisation, and hence the resistance, changes when a magnetic field is applied in the y axis.

The maximum sensitivity of such a transducer is about 0.1mV per ampere/metre at 5 volts. The electronic compass may contain three such transducers to measure the strength of the terrestrial magnetic field in three orthogonal directions.

Two similar transducers (Tr12 and Tr2 in figure 9) are used to measure the revolutions of the non-driven wheels by generating up to 50 periods of magnetisation which together correspond to 360 degrees. As the wheel turns, the transducer supplies a sinusoidal signal which is amplified and converted into square-wave voltages which, in turn, are converted into a pulse train. Binary numbers are also generated to indicate separately the angular rotation of the left and right wheels relative to the previous dead-reckoned fix.

Several calibrations follow installation. To begin with, the vehicle is driven around a closed loop to enable the compass to be calibrated (after which the effect of the car's magnetic field can be largely eliminated), and the wheel-sensor transducers matched to each other by comparing their output with a computer-generated regression circle. The odometric function is calibrated by driving the vehicle in a straight line

along a measured distance and comparing the output with the known distance.

The remaining, non-correctable, errors are collectively treated as random, the magnitude of which can be estimated, since their standard deviation can be calculated with a fair probability from repeated measurements. These standard deviations of the random errors in the measurement of heading and distance can be obtained from comparing a large sample of dead-reckoning fixes with correct, map-matched fixes. The magnitude of the random errors contributes to the size of the VLPA which is, in theory, bounded by an ellipse whose area is determined by rules for the propagation of random errors.

Both the compass and wheel sensors provide a quantifiable heading, in the former case an absolute heading, and in the latter relative to an initial value.

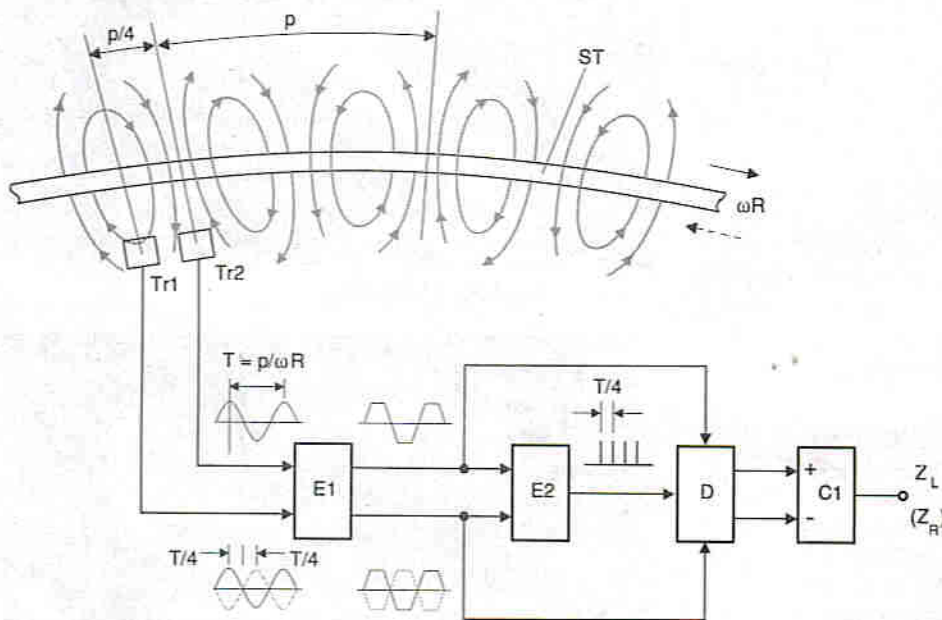


Figure 9: the principle of a wheel sensor. ST is a permanently magnetised strip; p is the period of the radial magnetisation; ωR is the peripheral velocity of the strip where ω is the angular velocity and R is the radius; Tr1 and Tr2 are magnetic transducers. The output signal is approximately sinusoidal with a period $T = p/\omega R$.

Radio Bygones



The leading vintage wireless magazine
INCLUDED IN THE CURRENT ISSUE...

- RAF transmitter T.77 • Early Cossor 'Tin-hat' valves •
- John J. Dunster - cabinet manufacturer •
- SW radio telecommunications after 1945 •

PLUS all the regular features


Annual subscription (6 issues) £18.50 in the UK,
£19.50 to Europe; £23.75 the rest of the world, by
airmail, or send £3.25 or a US\$5 Bill for a sample

Also from the publishers of *Radio Bygones*,
books for the vintage collector
and enthusiast ...

Watchers of the Waves by Brian Faulkner

A history of Maritime Coast Radio
Stations in Britain over the past 100
years. 128 A4 pages with over
80 photos and 24 drawings.

Price £13.50 to UK, £14.20 elsewhere.

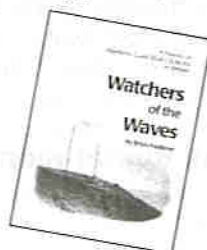

Wireless for the Warrior - Vol. 1 by Louis Meulstee

A technical history of radio communication equipment in the
British Army from Wireless Set No. 1 to No. 88. 360 A4 pages
with over 150 photos and 300 drawings.

Price £27.75 to UK, £28.65 elsewhere.

The Racal Handbook by Rinus Jansen

A review of Racal communications equipment - receivers,
transmitters and ancillaries - from 1956 to 1975, mainly
based on Racal technical sales literature. 102 A4 pages,
with 59 photos and 24 drawings, plus specifications.

Price £13.00 to UK, £13.75 elsewhere.

Comprehensive Radio Valve Guides

Facsimile reprints of books published by Bernard/Babani in
the 1950s and '60s. Among the most comprehensive and
user-friendly valve data ever published, the five books deal
respectively with valves produced during 1934/51, 1951/54,
1954/56, 1956/60 and 1960/63. English, European,
American, USSR and Japanese types are covered.

Each book contains between 40 and 56 A5 pages.
Price £2.95 each to UK, £3.25 elsewhere, or the
complete set of five for £14 to UK, £15.50 elsewhere.

Handbook of Radio, TV, Industrial & Transmitting Tube & Valve Equivalents

A companion to the above Valve Guides, listing
commercial and military equivalents and comparables from
both sides of the Atlantic. 60 A5 pages.

Price £2.95 to UK, £3.25 elsewhere.

The Story of the Key by Louise R. Moreau

A reprint of a popular and profusely illustrated series from
Morsum Magnificat magazine, describing the development
of telegraph keys from Morse's original 'Correspondent' to
the bugs of the post-WWII period. 60 A5 pages.

Price £3.95 to UK, £4.25 elsewhere.

All book prices include postage. Overseas prices are for
airmail despatch to Europe, surface mail elsewhere.
Airmail rates to the rest of the world available on request.

Please make all cheques payable to G C Arnold Partners
G C Arnold Partners (E3), 9 Wetherby Close, Broadstone
Dorset BH18 8JB, England. Telephone/FAX: 01202 658474

NEW SPECIAL OFFERS

New mini waterproof TV camera 40x40x15mm
requires 10 to 20 volts at 120mA with composite video
output (to feed into a video or a TV with a SCART
plug) it has a high resolution of 450 TV lines Vertical
and 380 TV lines horizontal, electronic auto iris for
nearly dark (1 LUX) to bright sunlight operation and a
pinhole lens with a 92 degree field of view. It focuses
down to a few CM. It is fitted with a 3 wire lead (12v
in gnd and video out).

£93.57 + VAT = £109.95 or 10+ £89.32 + VAT = £104.95.
High quality stepping motor kits (all including stepping
motors) 'Comstep' independent control of 2 stepping
motors by PC (Via the parallel port) with 2 motors and
software.

Kit £67.00 ready built £99.00
Software support and 4 digital inputs kit £27.00
power interface 4A kit £36.00
power interface 8A kit £46.00
Stepper kit 4 (manual control) includes 250 step
stepping motor and control circuit £23.00
Hand held transistor analyser it tells you which lead is
the base, the collector and emitter and if it is NPN or
PNP or faulty £33.45
LEDs 3mm or 5mm red or green 7p each
yellow 11p each
table ties 1p each £5.95 per 1000
£49.50 per 10,000

Rechargeable Batteries
AA (HP7) 500 mA £0.99
AA 500mAh with solder tags £1.55
AA 750 mA £2.20
C (HP 11) 1.2AH £2.20
C 2AH with solder tags £3.60
D (HP2) 1.2AH £2.60
D 4AH with solder tags £4.95
PP3 6.4V 1100mAh £4.95
1.2AA with solder tags £1.55
Sub C with solder tags £2.50
AAA (HP1E) 180mAh £1.75
1/3 AA with tags (philips CTV) £1.95

Standard charger charges 4 AA cells in 5 hours or
4Cs or 4Ds in 12-14 hours - 1xPP3 (1, 2, 3 or 4 cells
may be charged at a time) £5.95
High power charger as above but charges the Cs and
Ds in 5 hours AAs Cs and Ds must be charged in 2s
or 4s £10.95

Nickel Metal Hydroxyde AA cells high capacity with no
memory. If charged at 100mA and discharged at
250mA or less 1100mAh capacity (lower capacity for
high discharge rates) £3.75

Special offers please check for availability
stick of 4 42 x 16mm nicad batteries 171mmx16mm
dia with red & black leads 4.8v £5.99
6 button cell 6V 280mAh battery with wires (Varia
EX250DK) £2.45
Shaded pole motor 240Vac 5mm x 20mm shaft 80 x
60 x 55mm excluding the shaft £4.95 each
115v ac 80v dc motor 4mm x 22mm shaft 50mm dia x
60 long body (excluding the shaft) it has replaceable
thermal fuse and brushes £4.95 each £2.95 100+
7 segment common anode led display 12mm £0.45
LM337x T03 case variable regulator £1.95
£1.44 100+
GaAs FET low leakage current S8873 £12.95 each
£2.95 10+ £7.95 100+
BS250 P channel mosfet £0.45, BC559 transistor
..... £3.95 per 100
BC547A transistor 20 for £1.00
74LS05 hex inverter £10.00 per 100, used 8748
Microcontroller £3.50
SL552 UHF limiting amplifier LD 16 surface mounting

package with data sheet £1.95
DC-DC converter Reliability model V12P5 12v in 5v
200ma out 300v input to output isolation with data
£4.95 each or pack of 10 £39.50
Hour counter used 7 digit 240v ac 50Hz £1.45
QWERTY keyboard 58 key good quality switches new
£6.00

Alrax A82903-C large stepping motor 14v 7.5 step
270mm 68mm dia body 6.3mm shaft £8.95 or £200.00
for a box of 30

Polyester capacitors box type 22.5mm lead pitch
0.9uf 250vdc 18p each 14p 100+ 5p 1000+
1uf 250vdc 20p each, 15p 100+, 10p 1000+
1uf 50v bipolar electrolytic axial leads 15p each, 7.5p 100+
0.22uf 250v polyester axial leads 15p each, 7.5p 100+
Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm
pitch 50x28x17mm case 75p each 60p 100+
Philips 123 series solid aluminium axial leads
33uf 10v & 2.2uf 40p each, 25p 100+
Philips 108 series long life 22uf 63v axial 30p each
15p 1000+

Multilayer AVX ceramic capacitors all 5mm pitch 100v
100pf, 150pf, 220pf, 10,000pf (10n) 10p each, 5p
100+, 3.5p 1000+
500pf compression trimmer 60p

40 uf 370vdc motor start capacitor (dielectric type
containing no PCB) £5.95 or £49.50 for 10
Solid carbon resistors very low inductance ideal for
RF circuits

270ohm 2W, 68ohm 2W 25p each 15p each 100+ we
have a range of 0.25w 0.5w 1w and 2w solid carbon
resistors please send SAE for list

4 400V PSU (instal part 20105-001) with standard
motherboard and 5 disk drive connectors, fan and
main inlet/outlet connectors on back and switch on
the side (top for lower case) dims
212x49x145mm excluding switch £26.00 each
£138.00 for 8

MX150 Digital multimeter 17 ranges 1000vdc 750vac
2Mohm 200mA transistor Hfe 9v and 1.5v battery test
£9.95

AMD 27256-3 Eproms £2.00 each, £1.25 100+
DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each
50p 100+

Disk drive boxes for 5.25 disk drive with room for a
power supply light grey plastic 87x265x247mm £7.95
or £49.50 for 10

Hand held ultrasonic remote control £3.95
CV2458 gas relay 30 x 10mm dia with 3 wire
terminals will also work as a neon light 20p each or
£7.50 per 100

Varbatim R300NH Streamer tape commonly used on
nc machines and printing presses etc. it looks like a
normal cassette with a slot cut out of the top £4.95
each (£3.75 100+)

Heatshink compound tube
HV3-2405-E5 5.24v 50mA regulator ic 18-254vac
input 8 pin DIL package £3.49 each (100+ £2.25)
LM 555 timer ic 16p, 8 pin DIL socket 6p

All products advertised as new and unused unless
otherwise stated. Wide range of CMOS TTL 74HC,
74F Linear Transistors kits, rechargeable batteries
capacitors tools etc. always in stock.

Please add £1.95 towards P&P, vat inc. in all prices

JPG ELECTRONICS

ETI 276-278 Cratmoth Road,

(Dorchester) SA0 2BH

Address Vaux Dorey (01246) 211202 fax 550959
Callers Welcome 9.30am-3.30pm Monday-Saturday

Exclusive 10% off all visionics products to all ETI readers

Swift Designs Ltd. are the UK sole agents for all Visionics
products, and following the successful recent release of
EDWinNC are giving all ETI readers a chance to save even
more on all versions of the package. Once you have
purchased (making sure you enclose the voucher from the
front cover of this issue) we will continue to give 10% off any
further updates or software enhancements you buy in the
future. As an ETI special offer buyer your name will remain
on our files and you will need to do nothing more. See the
advertisement in this issue for details of the savings this
offer can make for you.

All software backup is free, and can be accessed via our
phone hotline on 01438 310133 or via eMail
designs@swiftdesigns.co.uk. Also access our web site for all
the latest news about Visionics products and 'Freebies',
www.swiftdesigns.co.uk.

Swift Designs Ltd. is principally a printed circuit design
house, and as such uses this software in the daily running of
our own business, any problems encountered are therefore
shared problems, and we have a commitment to the
advancement of EDWin, in both the single user and
commercial marketplaces. All queries are dealt with
promptly, and hopefully, to all users' satisfaction.
We look forward to giving all ETI readers the chance to own a
really powerful EDA package at a price that has no equal!

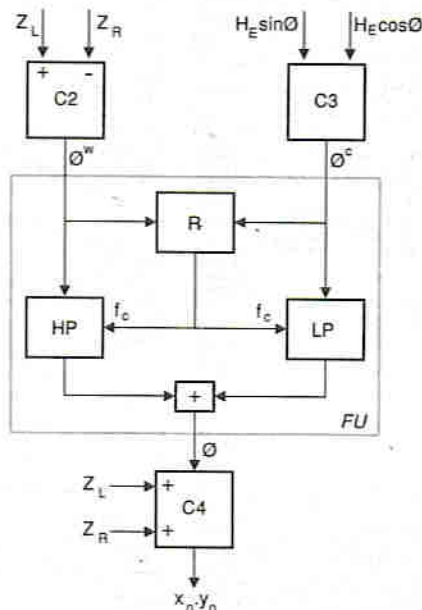


Figure 10: the reconciliation schematic: processing the signals Z_L and Z_R from the wheel sensors and $H_E \sin \theta$ and $H_E \cos \theta$ from the electronic compass. C2, C3, C4 are computing units; FU is the filter unit. In C2 the signals Z_L and Z_R are converted into a signal θ^w for the heading. In C3 the compass signals are converted into a signal θ^c comparable with θ^w . HP is a highpass filter; LP a lowpass filter; f_c the cutoff frequency of the two filters; R is the control unit that continuously controls the magnitude of f_c by measuring the rms value of the interfering components in θ^w and θ^c . After addition, the resultant signal θ is periodically converted into values x_n and y_n for the coordinates of position, with the aid of the sum signal from the wheel sensors.

They are both subject to interference because of the signal source: the wheel sensors are subject to slow drift due to changes in tyre pressure, tyre wear, and so on, while the compass is subject to very fast fluctuations caused by the magnetic fields of other vehicles, steel bridges and other masses along the road. And, of course, there is a small but constant error due to the magnetic field generated by the host vehicle.

These disparate signals must be reconciled and corrected. A schematic and description of this process is given in figure 10.

Getting it right

Having ironed out as many of the disturbances as possible, a complex dead-reckoning algorithm factors in the random errors and calculates the instantaneous VLPA. But despite the cleaning-up process, random errors will always remain within the VLPA which will, in consequence, grow continuously. Under difficult circumstances the VLPA can grow very quickly, and this is where the addition of a GPS fix will limit that growth and so improve the reliability of the positioning system. (*A description of how GPS functions appeared in ETI August 1994.*)

Of course, we know that VLPA positioning, even at the point of update, serves little real purpose unless it can be expressed in terms of a street location. Knowing your whereabouts to a six-figure fix is great if you normally navigate your way round London with a Pathfinder map ...

At this point it is only the GPS element that is providing anything like a navigational fix - the rest is a length of electronic string that has charted the course but not the position. To find your precise whereabouts in the real world, turn to the

NavTech digitised map on the CD-I. The dead-reckoning process generates a pattern of calculated positions which are compared the topographical map. A match fixes the part of the road network where the car is, and resets the VLPA at that instant in time and space to its smallest, or most accurate, area - which immediately begins to grow again as the car continues to move. Whenever a dead-reckoning is made, the computer detects the segments of the digitised map contained in the VLPA rectangle and holds them in memory as 'trees' of possible routes. If a segment is found to lie beyond the VLPA in the next dead-reckoning, it is discarded from the tree. A position correction takes place if the computer can decide with a good degree of certainty which of the possible routes has been followed.

Dead-reckoning, map matching, VLPA update, VLPA growth continue in a merry-go-round of estimate, correction and counter-correction repeated every five metres or so with sufficient accuracy for the system to know, and tell the driver via a message on the MMI, the exact location of the vehicle at any moment. As the name of the road changes, so does the display. It is immediate and, in my experience, always correct and quite uncanny.

The digital map

So far we have looked only at the positioning part of the system; the so-called PVH components - position, velocity and heading relative to polar north. On input of a destination via the MMI, using the keypad to highlight and select the required function on the display screen, Carin starts planning a route. But before that, it is worth considering how the map has been created, bearing in mind that it is much more than an electronic road atlas.

The digital map is divided into a large number of uniform areas, each containing several levels or networks, all covering the same area but with more or less detail. For example, the area that covers part of Wandsworth (in south London) may contain on its highest level only the South Circular and A3 - major routes between, say, Southwark and Kingston. The next layer down would include both these roads plus a number of secondary through routes, and would be used by the system on a more localised journey, say, from Fulham to Clapham Junction. The lowest level would contain all the information on its two superior networks, plus the entire tertiary network of local residential roads as on a printed town plan, and would be used for local journeys, such as might be made by doctors or delivery drivers and, of course, visitors whose destination was in that immediate area.

NavTech, and their only serious rival Tele Atlas (aka Etak), use OSCAR (Ordnance Survey Centre-line Alignment of Roads), which details every public driveable road and most private roads in a digitised format using the vector method, in which the axes of the roads are closely approximated by straight-line segments. This requires less memory than the alternative raster scanning method, and has proved entirely adequate for all the pan-European and American databases already in use. Figure 11 shows how a road network is translated into a series of points each connected by straight lines - the sharper the bend, the shorter the lines. The position of each point can be expressed as either an xy co-ordinate on a conventional grid system, or as a geodetic co-ordinate. NavTech manipulate this geometry to meet the required specification for in-car systems and, as an example of the end result, figure 12 shows how the area around Greenwich Observatory appears on one of NavTech's computers.

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

LOW COST PC's -

SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640K + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!
Order as HIGRADE 286 **ONLY £129.00 (E)**

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£19.95
Wordperfect 6.0 for DOS - when 3 1/2" FDD option ordered	£22.50
NE2000 Ethernet (thick, thin or twisted) network card	£29.00

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition.
Tilt & Swivel Base £475
VGA cable for IBM PC included.
External cables for other types of computers CALL

As New - Used on film set for 1 week only!!
15" 0.28 SVGA 1024 x 768 res. colour monitors.
Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just in - Microvitec 20" VGA (800 x 600 res.) colour monitors.
Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed fan controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 1/2" x 15 1/2" D.
Only £95 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional stereo input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

SPECIAL INTEREST ITEMS

- MITTS. FA3445ETKL 14" Industrial spec SVGA monitors 2Kw to 400 kw - 400 Hz 3 phase power sources - ex stock **£245**
- EPOA **£950**
- IBM 8230 Type 1, Token ring base unit driver **£750**
- IBM 53F5501 Token Ring ICS 20 port lobe modules **£95**
- IBM MAU Token ring distribution panel 8228-23-5050N **£750**
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE **£550**
- Trend DSA 274 Data Analyser with 6703(2M) 64 Vc **£6500**
- Marconi 6310 Programmable 2 to 22 GHz sweep generator **£3750**
- HP1650B Logic Analyser **£950**
- HP3761A Pattern generator & HP3782A Error Detector **£1800**
- HP APOLLO RX760 system units **£175**
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts **£675**
- HP3081A Industria workstation 4 Bc Barcode swipe reader **£1650**
- HP54121A DC to 22 GHz four channel test set **£650**
- HP7580A A1 8 pen HPLG high speed drum platter **£1200**
- EG-G Brookdale 95035C Precision lock in mount **£1425**
- View Eng. Mod 1200 computerised inspection system **£1200**
- Ling Dynamics 2Kw programmable vibration test system **£1200**
- Computer controller 1056 x 560 mm X Y table & controller **£1200**
- Keithley 590 CV capacitor / voltage analyser **£1150**
- Racal ICR40 dual 40 channel voice recorder system **£3750**
- Fiskers 45KVA 3 ph On Line UPS - New batts Dec.1995 **£9500**
- ICI R5030UV34 Cleanline ultrasonic cleaning system **£2200**
- Mann Tally MT645 High speed line printer **£1200**
- Intel SBC 486/133SE Multibus 486 system: 8Mb Ram **£1150**
- Sata 3220-05 A0 4 pen HPLG fast drum plotters **£1450**
- Nikon HF-X11 (Ephiphot) exposure control unit **£550**
- Motorola VME Bus Boards & Components List. SAE / CALL **£1950**
- Trlo 0-18 vdc linear, metered 30 amp bench PSU. New **£1250**
- Fujitsu M3041R 600 LPM band printer **£1250**
- Fujitsu M3041D 600 LPM printer with network interface **£1250**
- Perkin Elmer 2998 Infrared spectrophotometer **£3750**
- VG Electronics 1035 TELETEXT Decoding Margin Meter **£950**
- Andrews LARGE 3.1 m Satellite Dish + mount (For Voyager) **£1995**
- Sekonic SD 150H 18 channel digital Hybrid chart recorder **£750**
- TAYLOR HOBSON Tallysurf amplifier / recorder **£485**
- System Video 1152 PAL waveform monitor **£200**
- Test Lab - 2 mtr square quietised acoustic test cabinets **£650**
- Kenwood 9601 PAL Vectorscope - NEW **£650**

Please call for further details on the above items

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels	£335.00 (G)
OPT Rack 2 Rack, Less side panels	£225.00 (G)

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)
Sold at LESS than a third of makers price !!

A superb buy at only £195.00 (G)

Over 1000 racks - 19" 22" & 24" wide
3 to 44 U high. Available from stock !!
Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives a simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc. Imagine using your finger with 'Windows', instead of a mouse !! (a driver is indeed available !!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: **£145.00 (B)**
Full MICROTOUCH software support pack and manuals for IBM compatible PC's £29.95 RFE - Tested

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. **£59.95 (A1)**
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256K or 512K in 64k steps. May also be used to fill in RAM above 640K DOS limit. Complete with data.
Order as: XT RAM UG. 256K. £34.95 or 512K £39.95 (A1)

SIMM SPECIALS		
1 MB x 9 SIMM 9 chip 120ns	Only	£16.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns	£19.50 or 70ns	£22.95 (A1)
1 MB x 9 SIMM 9 chip 80 ns	£21.50 or 70ns	£23.75 (A1)
4 MB 70 ns 72 pin SIMM. -with parity-	Only	£95.00 (A1)
INTEL 486-DX33 CPU	£55.00	INTEL 486-DX66 CPU £69.00 (A1)

FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR LIST

FANS & BLOWERS

EPSON D0412 40x40x20 mm 12v DC	£7.95 / £65
PAPST TYPE 612 60x60x25 mm 12v DC	£8.95 / £75
MITSUBISHI MMF-D6D12DL 80x60x25 mm 12v DC	£4.95 / £42
MITSUBISHI MMF-08C12DM 80x80x25 mm 12v DC	£5.25 / £49
MITSUBISHI MMF-09B12DH 92x92x25 mm 12v DC	£5.95 / £53
PANCAKE 12-3.5 92x92x18 mm 12v DC	£7.95 / £69
EX-EQUIP AC fans. ALL TESTED 120 x 120 x 38 mm specify 110 or 240 V £6.95. 80 x 80 x 38 mm - specify 110 or 240 V £5.95	
IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240v New	£79.95

Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd user, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256K cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable
Only **£399.00 (E)**
Many other options available - call for details.

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" or 3 1/2" from only £18.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent RFE	£24.95 (B)
3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only	£25.95 (B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£18.95 (B)
5 1/4" Teac FD-55FR 1.2 Meg for IBM pc's etc	£18.95 (B)
5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's RFE)	£29.95 (B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95 (B)
Table top case with integral PSU for HH 5 1/4" Flopp or HD	£29.95 (B)
8" Shugart 800/801 8" SS refurbished & tested	£195.00 (E)
8" Shugart 810 8" SS HH Brand New	£195.00 (E)
8" Shugart 851 8" double sided refurbished & tested	£250.00 (E)
Mitsubishi M2894-63 8" double sided NEW	£275.00 (E)
Mitsubishi M2896-63-02U 8" DS slimline NEW	£285.00 (E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00 (E)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only **£299.00 or 2 for £525.00 (E)**

3 1/2" FUJII FK-309-26 20mb MFM I/F RFE	£59.95 (C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE	£59.95 (C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv) RFE	£69.00 (C)
3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn)	£69.00 (C)
3 1/2" WESTERN DIGITAL 850mb IDE I/F Brand New	£185.00 (C)
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv) RFE	£49.95 (C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95 (C)
5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested	£69.95 (C)
5 1/4" HP 9754B 850 Mb SCSI RFE tested	£89.00 (C)
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00 (E)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00 (E)

Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£36.95
TELEBOX STL as ST but fitted with integral speaker	£39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner	£69.95

For overseas PAL versions state 5.5 or 6 MHz sound specification. *For cable / hyperband reception TELEBOX MB should be connected to a cable type service. Shipping code on all Teleboxes is (B)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call for info / list.

Issue 13 of Display News now available - send large SAE - PACKED with bargains!



ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET. 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9:00 - 5:30
215 Whitehorse Lane
South Norwood
On 65A Bus Route
14 Thornton Heath &
Selhurst Park SR Rail Stations

NEW DISTEL©
The Original
FREE On line Database
Info on 20,000+ stock items!
RETURNING SOON!

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927



All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996. E & O E. 066

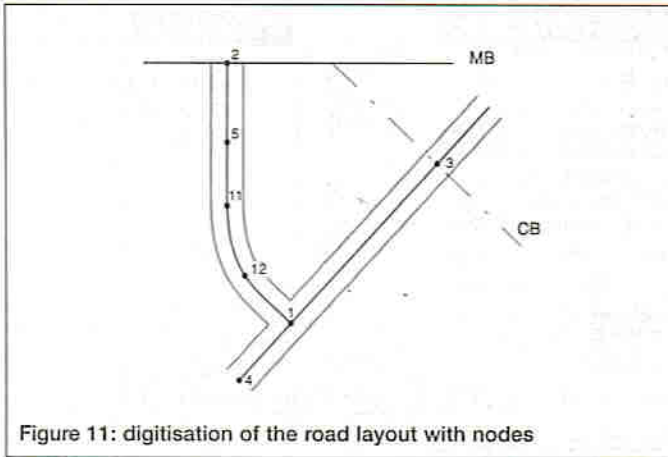


Figure 11: digitisation of the road layout with nodes

Points may be either a node or a shape point. In figure 11, points 1, 2, 3 and 4 are all nodes (where more than one component exists); points 11 and 12, used to plot curvature, are typical shape points. Point 5 marks a change in road name and is therefore upgraded to a node. A succession of points that starts and ends with a node is called a chain, or links. To this skeleton can be added navigable attributes such as directions of one-way streets, restricted turns, road dividers, timed road closures and so on.

Sorting the parcels

At this point NavTech "massage" the data so that it corresponds with drivers' perceptions of junctions "on the ground", rather than being simply a strict geometric interpretation that could occasionally give misleading guidance. NavTech say that the secret of their success is the application of "art, not science". Using County Council (or London Borough) Transport Policies and Programmes (TPP) strategic networks as a starting point, NavTech define the so-called "arterial network" which determines the "weighting" applied to routes, the first steps to which are distinctly hands-on (figure 13). This process is very much qualitative, and includes systematic behind-the-wheel driving of the roads by NavTech's own surveyors, as well as consultation with highway authorities and other interested organisations. This is an ongoing process that has to take account of changes to road layouts and so on, and must include "temporary" long-term road closures (such as Hammersmith Bridge). Regular updates are issued as replacement discs which can be ordered by subscription.

All the information is divided into parcels, stored as discrete blocks on the CD-I and distributed over a number of sectors. The CD also contains addresses of the first sector where each block is stored, its size in blocks, and the co-ordinates of the lines that delineate the corresponding map parcel. Access can be kept to a minimum if the parcels are not too large and are stored logically to minimise pick-up movement. The first requirement dictates that each parcel should contain a similar data value, so that its blocks do not occupy too much space in the RAM. Conversely, there should not be so many blocks that the address directory becomes unwieldy.

The second requirement demands that adjacent parcels on the map should correspond to blocks close to each other on the disc. To achieve similar block characteristics, the map data for each parcel must likewise be similar. From this it follows that parcels in rural areas will be larger than those in towns. The partitioning algorithm is known as the "region quad tree", in which the map is successively subdivided into four rectangles until the data content per parcel is less than a preset value (figure 14).



Figure 12: a digitised map of a NavTech computer



Figure 13: the hands-on approach to weighting

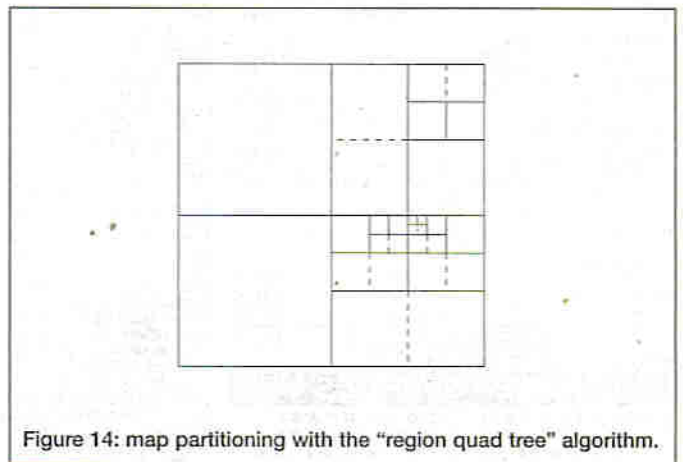


Figure 14: map partitioning with the "region quad tree" algorithm.

Occasionally adjacent parcels are joined again, provided the combined data value barely exceeds the preset. Logical arrangement of the data blocks for accessibility is achieved by the application of Peano space-filling curves, where the curve passes through each point in a given space once only.

POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

PRICES INCLUDE V.A.T. PROMPT DELIVERY FRIENDLY SERVICE + LARGE (A4) S.A.E. 60p STAMPED FOR CATALOGUE

**OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK**

**THOUSANDS PURCHASED
BY PROFESSIONAL USERS**



**THE RENOWNED MXF SERIES OF POWER AMPLIFIERS
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)**

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: *Independent power supplies with two toroidal transformers * Twin L.E.D. Vu meters * Level controls * Illuminated on/off switch * XLR connectors * Standard 775mV inputs * Open and short circuit proof * Latest Mos-Fets for stress free power delivery into virtually any load * High slew rate * Very low distortion * Aluminium cases * MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
MXF400 W19" x H5 1/2" (3U) x D12"
MXF600 W19" x H5 1/2" (3U) x D13"
MXF900 W19" x H5 1/2" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH

OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE * ECHO & SOUND EFFECTS *

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fader, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.




Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

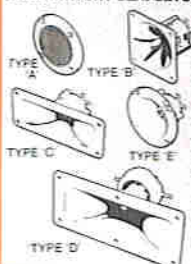Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/4" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

**POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET
FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz**

ibi FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR

ibi FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair



IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

**THREE SUPERB HIGH POWER
CAR STEREO BOOSTER AMPLIFIERS**
150 WATTS (75 + 75) Stereo, 150W
Bridged Mono
250 WATTS (125 + 125) Stereo, 250W
Bridged Mono
400 WATTS (200 + 200) Stereo, 400W
Bridged Mono
ALL POWERS INTO 4 OHMS

Features:
* Stereo, bridgable mono * Choice of high & low level inputs * L & R level controls * Remote on-off * Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £6.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor > 300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC

ALL EMINENCE UNITS 8 OHMS IMPEDANCE
8" 100 WATT R.M.S. MEB-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB. PRICE £32.71 + £2.00 P&P
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB. PRICE £33.74 + £2.50 P&P
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB. PRICE £43.47 + £2.50 P&P
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB. PRICE £35.64 + £3.50 P&P
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.67 + £3.50 P&P
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB. PRICE £46.71 + £3.50 P&P
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB. PRICE £70.19 + £3.50 P&P
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB. PRICE £50.72 + £4.00 P&P
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB. PRICE £73.34 + £4.00 P&P

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB5-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB. PRICE £8.90 + £2.00 P&P
10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 99dB. PRICE £13.65 + £2.50 P&P
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB. PRICE £30.39 + £3.50 P&P
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB. PRICE £42.12 + £3.50 P&P
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB. PRICE £9.99 + £1.50 P&P
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB. PRICE £10.99 + 1.50 P&P
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB. PRICE £12.99 + £1.50 P&P
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB. PRICE £16.49 + £2.00 P&P

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS
3W TRANSMITTER 80-100MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 98 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P
FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 58 x 48mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHDOWN SEA,
ESSEX, SS2 6TR
Tel. 01702 - 527572 Fax 01702-420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.

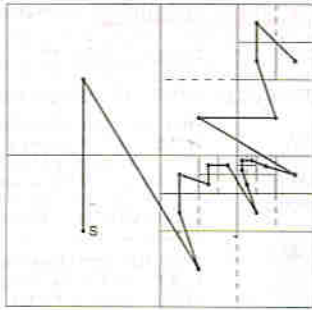


Figure 15: The Peano N-curve that connects the parcels of figure 14 and starts at S. In the case of a parcel formed from a summation, the centre of the first original parcel is taken: the other parcel is then ignored.

A Peano curve is particularly suitable for arranging the parcels generated by region quad tree partitioning. It can be seen from figure 15 that the smaller the parcel, the shorter the Peano curve that joins it to its neighbour. Think of the curves as expressing the physical proximity of one CD sector to another, and it's easy to see how the curve can represent relative pick-up movements.

Because the destination is fixed and the vehicle dynamic, Carin performs the route-planning backwards, based on the algorithms of Dijkstra and Dial. Starting at the destination, many possible routes, all in the general direction of the vehicle, are simultaneously assembled and investigated. The driver will have indicated via the MMI a preference for major or minor roads and whether time or distance is of the essence. To distinguish the optimum route, Carin introduces a "cost" element that reflects the physical characteristics of the route, and also takes account of the "weighting" of particular routes as preferred by the relevant Local Authority. The latter caused some teething problems for NavTech who, by diplomacy as much as technology, were obliged to overcome "edge mapping" problems associated with adjacent authorities preferring different routes.

To the cost function is added a heuristic routine (trial and error) which estimates the cost of the route to the current position of the car. Together, the cost and heuristic functions generate an optimum selection and reject the remainder. Planning time is critical and, as CD-I access times are conventionally too slow, an algorithm has been developed to improve access times by anticipating the map areas and consequent disc sectors likely to be needed and loading them into the system RAM. Expressed in the form of a histogram, typical planning times for the German database are shown in figure 16.

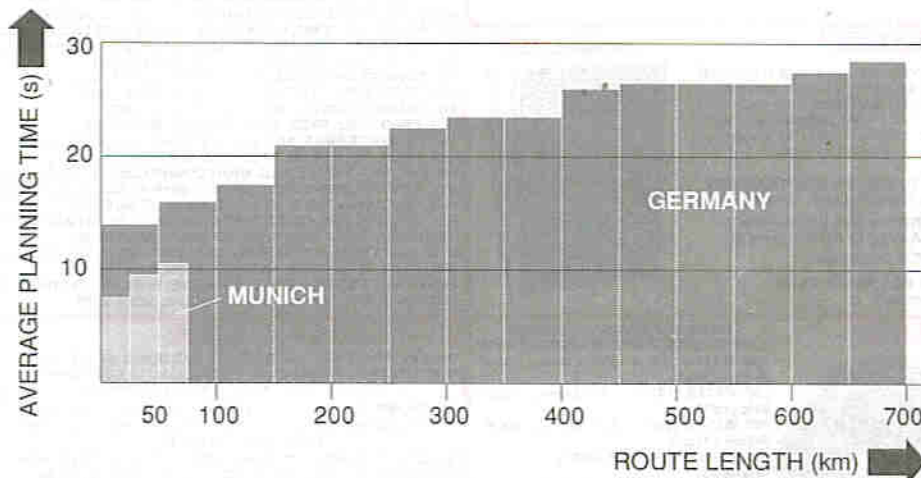


Figure 16: the histogram for Germany

SOCRATES - A philosophy for the future

Within a few years, "getting there" will be even easier as navigational systems begin to interact with traffic status networks via GSM up- and down-links. Philips, in conjunction with a number of other European partners including Volvo and British Telecom, is participating in the so-called SOCRATES programme which will integrate road and traffic information using the cellular network.

In this system, vehicles act as information-sources as well as recipients via the down-link. In the test areas of Gothenburg (Germany) and Eindhoven (the Netherlands) only a few percent of cars are fitted with interactive Carin, yet the system computers are able to detect traffic hold-ups and accidents and relay this information back down to vehicles in the area. It is obvious that Carin will soon be automatically generating its own detours in response to such inputs. SOCRATES will also provide information on available parking spaces, and drivers may reserve places via the system. According to the Transport and Road Research Laboratory, if SOCRATES were to be fully operational in London savings, of up to 100 million pounds per year could be achieved - and no doubt the atmosphere would be a lot more breathable. As the evaluation of the Gothenburg trials are coming to a close, larger trials are planned for Frankfurt and London with 100 and 200 cars respectively.

As the SOCRATES tests continue we can also look forward to RDSTMC, the snappy title for Radio Data System Traffic Message Channel. RDS we already know and hate, particularly when the aliens from Grunt FM interrupt the non-RDS Radio 4 with news of a snarl-up at the War Memorial. Lurking on the sub-carrier of Classic FM (amongst others), RDS is also used to carry the differential correction signals for dGPS - the ultra-accurate GPS system used by farmers and surveyors (see 'What a difference a d makes'). But the Carin-integrated RDS will make it possible to store the transmissions and replay them selectively. Pilot schemes are already operating in the Dutch Rhine-Corridor project and the Paris Ile de France project. As with SOCRATES, RDSTMC also offers the possibility of intelligent re-routing via the Carin guidance system, but only if the computer calculates that the obstruction will still be there when the Carin-equipped vehicle reaches the locality.



Figure 17: Carin in a Mitsubishi Shogun



Figure 18: a pictogram in operation



Figure 19: a scaleable map display

See me, hear me

Everything we have so far encountered, apart from the street name displayed at the base of the screen, occurs without any visual indication to the driver. What makes Carin effective is its public face, the guidance system. The Carin guidance system is of course audible as well as visual, but I will deal with the latter first.

What a difference a d makes

When Uncle Sam launched all that military, sorry, communications hardware that made GPS possible, he introduced something called "selective availability" to ensure that no hostile force could turn it round on him. SA introduces "noise" into the atomic clocks, which reduces their accuracy. The military authorities also feed the satellites slightly erroneous orbital data, transmitted back to earth as a slight wobble which, of course, reduces the accuracy in navigational functions. If a time-period plot of the position solutions of a stationary GPS receiver is taken, the fix can be seen to wander around with a 100-metre circle to a surprising degree. Military receivers have a decrypting key that tells them what errors have been introduced, so that they can be removed and accuracies in the order of 15 metres can be achieved.

Differential GPS receivers are able to improve the accuracy to around 1 metre or less. dGPS not only takes care of SA, it also filters out most of the inaccuracies caused by atmospheric distortion and multipath errors caused by signal reflections (as in TV ghosting).

So how do they do that? Normal GPS navigation is dynamic in the sense that the receiver is usually on the move, and so the fix is dependent upon the inherent trigonometry of the system. dGPS, however, introduces a second receiver which is situated on a point that has been very carefully surveyed. This reference receiver detects errors transmitted from the satellites and applies a correction based on its fixed parameters. A commercial differential correction service is available on subscription from companies like Focus FM, who use the Classic FM sub-carrier, and Racal who have recently launched LandStar Europe differential correction for farmers.

The corrections are transmitted to the mobile GPS receiver which, is relatively close at hand, so the incoming signals from the satellite and the reference receiver are effectively simultaneous. The reference receiver measures the incoming errors using its known position (and therefore distance) to calculate timing discrepancies - the reverse of the mobile receiver, which uses timing to calculate distance.

Having measured and corrected any timing errors for all satellites above the horizon, the reference receiver encodes the information into a standard format and transmits it to the mobiles, which decode and use only those bits of information applying to satellites "visible" to them.

There are a couple of variations which have no need for a continuous radio link. In "post processing", for example, in surveying, the mobile receiver records the time it made each measurement; the correction data can later be downloaded from the reference receiver to clean up raw real-time data. "Inverted" dGPS is sometimes used in vehicle tracking applications: a base station collects location information and applies differential correction. The driver's display may show he's up and down the City Road, but the dispatcher will know when he's in and out the Eagle.

The LCD screen (figure 17) is built into the fascia on some factory-fitted versions, or attached to the top or front of the fascia in aftermarket versions. It offers two modes - junction schematics (pictograms) (figure 18) or a scaleable map (figure 19), which can be viewed head-up or north-up, on which the vehicle's position is tracked. With practice it is possible to

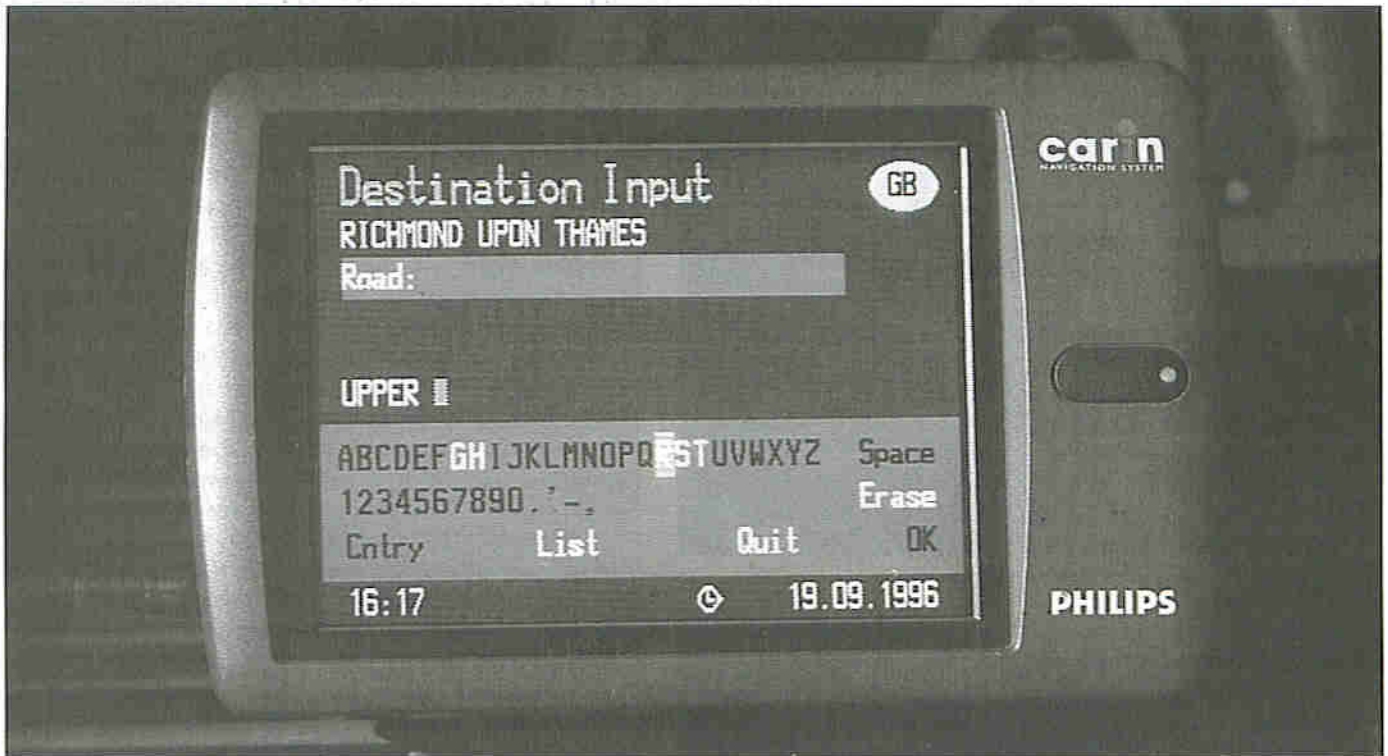


Figure 20: the set-up screens in multiple-choice format

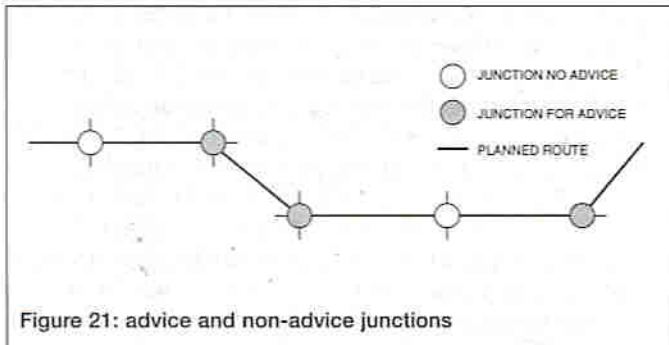


Figure 21: advice and non-advice junctions

toggle deftly between the two, but I have found it much safer and easier to use the pictograms, as they can be understood at a glance and correspond with the spoken guide. As well as the pictogram, the screen shows date and time, distance to destination and the approximate heading (indicated by means of a small rotating arrow-head). The set-up screens (figure 20) offer multiple-choice options in a straightforward text format.

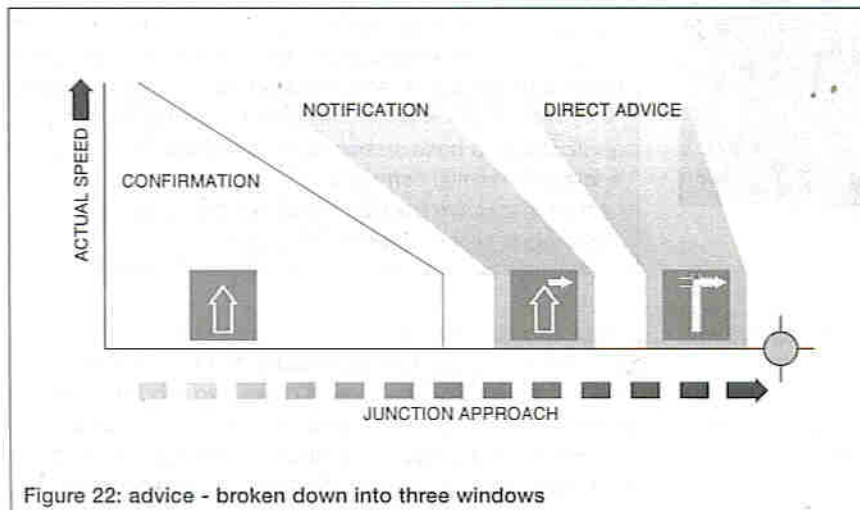


Figure 22: advice - broken down into three windows

Having selected a destination, the driver can set off and within 15-20 seconds the screen fills and voice guidance begins. If, at a simple intersection, no change of direction is required the schematic arrow of the pictogram simply indicates straight ahead, and no audio guidance is provided. Examples of advice and non-advice junctions are shown in figure 21. The approach to junctions where advice will be given is broken down into three windows (figure 22). The first, or confirmation, window is visual only and means "continue straight ahead". This is the same display that would be seen for non-advice junctions. The actual distance to the next 'advice' junction is counted down in metres on the screen display. When the vehicle reaches a point prior to the junction, determined by speed, a visual and audible warning is given of the approaching junction. This is called the notification window. The final instructions occur in the final advice window, in both media, at a point dependent on the vehicle approach speed. The voice messages are divided into three groups: prefix advice, such as 'At the next junction'; main messages such as 'Turn right'; and suffix advice such as 'To join the motorway' - which together offer up to 10,000 possible permutations. If the driver decides to deviate from the route, Carin will detect

the new route, re-calculate from the destination back to the new position, and provide guidance either to return to the original route or for a new route. Philips do not claim that Carin will always take the route that a human with local knowledge would choose, but they are quite bullish that it will always get you to where you want to go, which, in fairness, was the objective. When you reach your destination, which may be a street or a point of local interest like the British Museum, a dot appears above the confirmation arrow on the pictogram and a butler-like voice announces "You have arrived".

Technical diagrams by kind permission of Philips Car Systems.


22nd SANDOWN MODEL SHOW

in association with the Elmbridge Model Club

Europe's
Modelling
Showcase



Welcome to the 1997 Sandown Model Show, a must for ALL modelling enthusiasts. Sandown '97 offers an unmissable combination of superb outdoor flying demonstrations and displays, a stunning model boat pool, spectacular outdoor model car racing together with a vast number of clubs and societies. Of course, this show would not be complete without a vast range of top quality trade stands - and we offer these in abundance! All the UK's leading manufacturers, suppliers, distributors and retailers are there - we guarantee you will be able to see and buy all the latest products.

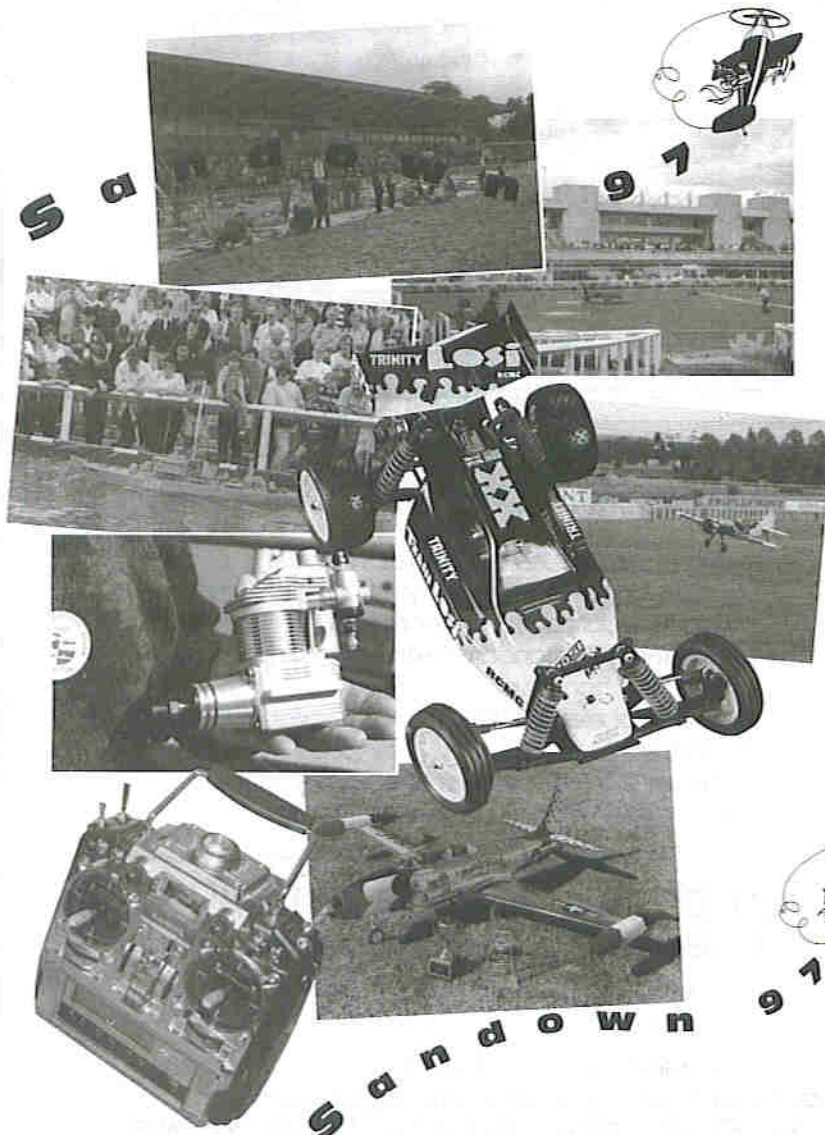

World Class Flying Displays

Europe's Largest Shop Window!

Model Boat Pool

R/C Model Car Racing

The Best Expert Advice

**Sandown Park
Exhibition Centre,
Sandown Park
Racecourse, Esher, Surrey**

**Saturday 10th -
Sunday 11th May 1997
9.30 am - 6.00 pm daily**

Entrance Prices:

Adults £7.50 (£6.00 Advance)

Senior Citizens £5.50 (£4.00 Advance)

Children £4.00 (£3.00 Advance)

Family Ticket £20.00 (£16.00 Advance)

Advance Ticket Hotline 01442 244321

Fax order line: 01442 66998 Closing date: 02/05/97

9am - 5pm
Mon. - Fri.


REMEMBER, SANDOWN HAS FREE CAR PARKING FOR OVER 5,000 VEHICLES.

Electronics Principles 3.0

For Windows 3.1, '95 & NT.

If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.

Electronics Principles 3.0 now contains fifty-eight Windows and an extended range of nearly 300 fully interactive analogue and digital electronics topics. Currently used in hundreds of UK and overseas schools & colleges to support GCSE, A-level, BTEC, City & Guilds and university foundation courses. Also NVQ's and GNVQ's where students are required to have an understanding of electronics principles.

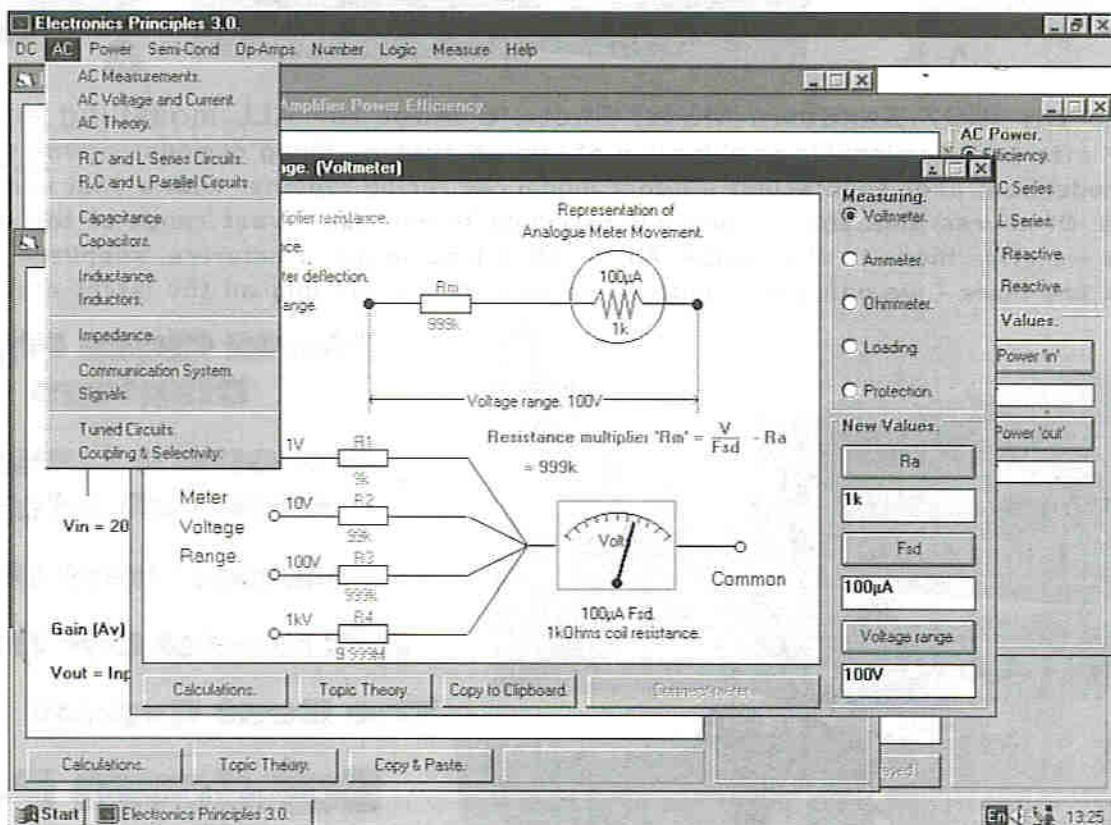

Other titles available.

Electronics Toolbox 3.0 £19.95*

Presents commonly used electronics formulae and routines in a way that makes calculations easy. Just select the topic, 'pop' in your values and find the result.

Mathematics Principles 3.0 £49.95*

Study or revise mathematics in what we believe is an interesting and enjoyable way. Nearly two hundred topics, including the GCSE syllabus with interactive, full colour graphics to enable 'learning through doing'.

Electronics Principles 4.0 £99.95*

Contains all of the extended version 3 and many more digital and analogue topics. Plus: Microprocessor & microcomputer operation, registers, arithmetic and logic unit, ROM, RAM etc. Addressing modes and full instruction set can be executed on the screen.


Inputs & outputs use electronics symbols. Scientific notation avoided where possible to make numbers & calculations meaningful. Experiment with standard textbook examples, even check your homework! Hundreds of electronics formulae available for circuit investigation. Multi-user site licence for schools & colleges. Produce OHP slides & student handouts.

Complete Package just £49.95*

For more information, upgrades or software by return.
Telephone (01376) 514008.

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex, UK. CM8 2BJ. Tel/Fax: 01376 514008.
E-Mail sales@eptsoft.demon.co.uk Web pages <http://www.octacon.co.uk/ext/ept/software.htm>

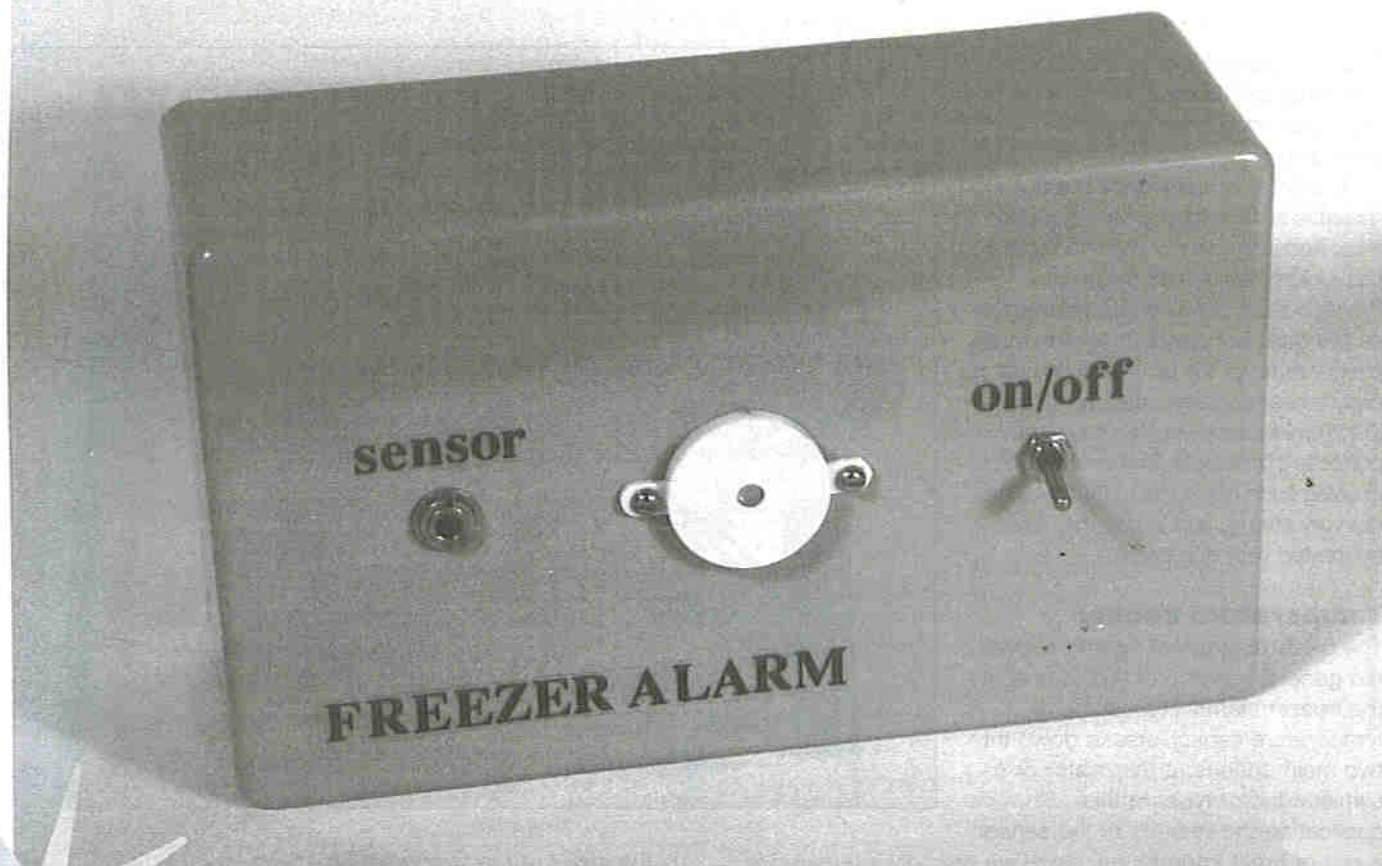* UK Please Add £2 per order for post & packing + VAT. Make cheques payable to EPT Educational Software. Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date.
OVERSEAS ORDERS: Add £2.50 postage for countries in the EEC. Outside EEC add £3.50 for airmail postage.



ETI Freezer Alarm

The kitchen is flooding, your heart is sinking, supper's off - the freezer has gone down again! Time to reach for Robert Penfold's freezer defrost alarm.

O am sure I'm not the only person to have had that sinking feeling on discovering that the freezer door has been left slightly open. The usual cause is a freezer over-stuffed with the latest supermarket bargains, making the door reluctant to close properly - because of the flexible rubber seal, the door can be left so slightly ajar that it appears to have closed. It is the ease with which the door opens the next time you visit the freezer that alerts you. The thick layer of frost on everything inside the freezer also gives you a clue! Having to defrost the freezer prematurely is inconvenient, but there is also the question of whether or not the food in the freezer is fit to eat. The food may not have actually defrosted (unless you have had one of those "someone pulled the wrong plug out when they plugged the electric drill in" events that make a certain editorial team shiver ...) but it is unlikely to have been kept at a suitably low temperature either. Many people prefer to take the safe option and throw it all away "just in case."

Either way, it is the kind of waste and inconvenience - not to mention potential flood - that we would all like to avoid.

One way of providing an electronic alarm to guard against the dreaded defrost is to use a micro-switch to operate an indicator light or a simple audio alarm generator when the door is not fully closed - in other words, an arrangement much like an ordinary refrigerator light, but with the light on the outside. However, it is difficult to add this type of thing to an existing piece of equipment.

The obvious alternative is to use a temperature-operated alarm. This method has the advantage of detecting any problem that causes the temperature inside the freezer to rise above its normal level. Whether the door has been left slightly ajar, the freezer has developed a fault, or the mains supply has failed, the alarm will detect the temperature rise and be activated. This method is also problematic, since the sensor must be inside the freezer with the rest of the unit on the outside. Drilling holes through the side of the freezer is obviously not an option!

The only alternative is to use very fine wires that can be taken out through the door seal without rendering it ineffective.

The finest insulated wire readily available is 44 swg enamelled copper wire. According to my data book, this has a diameter of 0.08 millimetres. Practical tests showed that wire as thin as this does not significantly reduce the effectiveness of the door seal. In fact, a slightly heavier gauge such as 40 swg (0.125 millimetre) wire seems to be perfectly acceptable. The only problem in using such fine wires is that they are not very strong, and in use they must be treated with due care.

Temperature sensor

The block diagram of figure 1 shows the general scheme of things used in the freezer alarm. The choice of temperature sensor breaks down into two main options: a thermistor or a semiconductor type. In this application the linearity of the sensor is not of great importance, since we are only interested in detecting a particular threshold temperature. A thermistor is therefore perfectly adequate. The temperature inside a freezer is well below zero, at around -18 to -20 degrees Celsius. This is outside the scope of some semiconductor temperature sensors, but most of the thermistors currently available will work perfectly well down to about -40 degrees Celsius. A thermistor was therefore selected as the temperature sensor.

A thermistor is effectively a resistor with very poor temperature stability. Normal thermistors have a negative temperature coefficient, which means the component's resistance falls as its temperature is increased. The thermistor is used in a simple potential divider circuit connected across the supply rails. If the temperature of the thermistor rises, its resistance falls, and the output voltage from the potential divider circuit falls as well.

The output from the potential divider is compared with a reference voltage by a voltage comparator circuit. If the output potential from the potential divider is higher than the reference level, the output of the comparator goes high. Conversely, if the output voltage from the potential divider

is the lower of the two voltages, the output of the comparator goes low. In practice the reference voltage is set at a level which results in the output from the potential divider normally being the higher of the two voltages. Under standby conditions the output of the comparator is therefore high. If the thermistor is taken above its normal temperature, its resistance decreases, and the output potential from the potential divider decreases. If the temperature rise is high enough, the output voltage from the potential divider will go below the reference voltage, and the output of the comparator will then go low.

The output of the comparator drives an electronic switch, and this controls the supply to the other stages of the unit. These stages generate a simple frequency modulated alarm sound. The switch and alarm generator are switched off under standby conditions when the output of the comparator is high. When the output of the comparator goes low, it turns on the electronic switch, which in turn supplies power to the alarm generator circuit. The basic alarm sound is produced by a vco (voltage controlled oscillator) which has a centre frequency of around 4kHz or so.

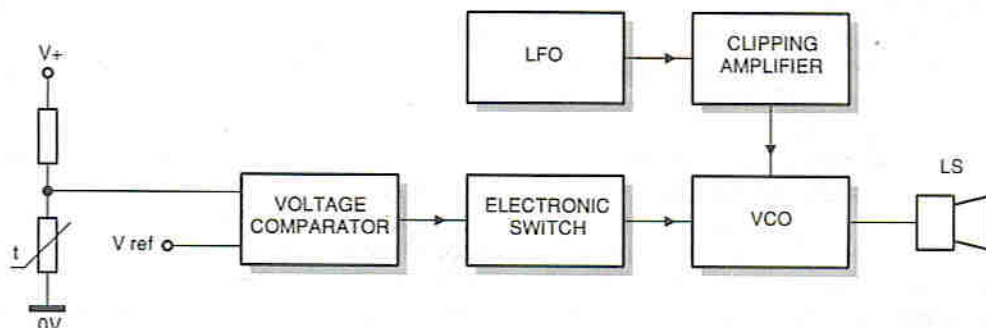
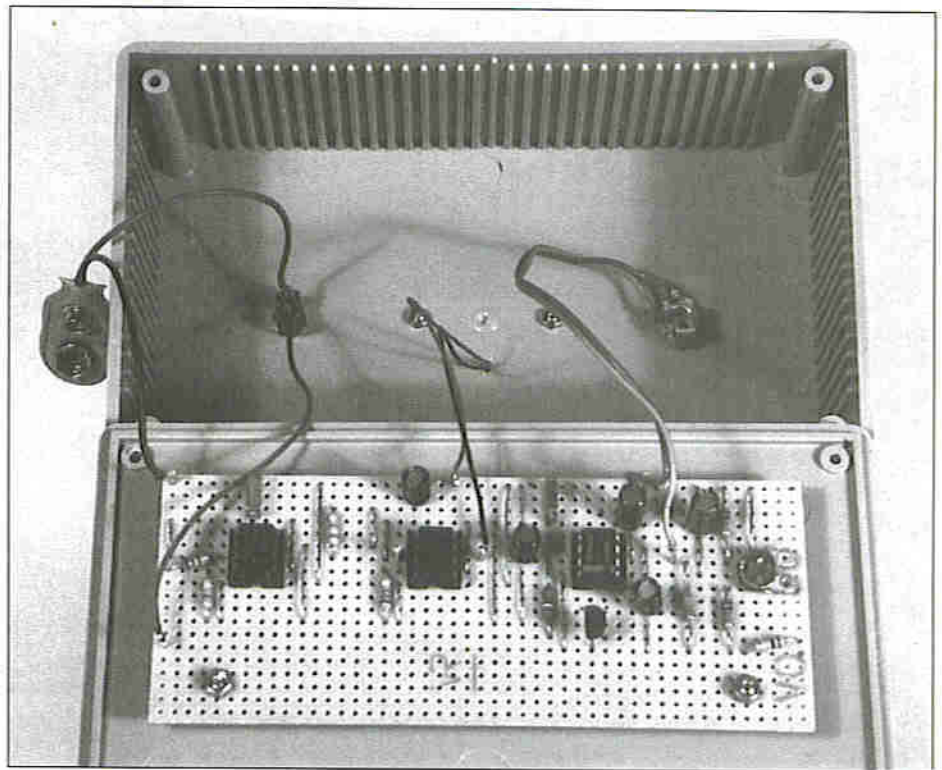


Figure 1: The block diagram of the freezer alarm

An lfo (low frequency oscillator) provides the control signal to the vco, and the roughly squarewave output from the vco would normally result in the vco being switched between two tones. In this case a lowpass filter is used between the lfo and the vco, and this attenuates the harmonics in the squarewave signal to produce a roughly triangular modulation signal. This varies the vco between two frequencies, rather than switching it between the two. The result is an excellent and highly effective alarm sound.

Circuit Operation

The circuit diagram for the freezer alarm appears in figure 2. IC1 is an operational amplifier, but it operates here as the voltage comparator. VR1 provides an adjustable reference voltage to IC1's inverting input, and the potential divider circuit which contains the thermistor (Th1) drives the non-inverting input of IC1. This gives what is really just a basic bridge circuit. An advantage of this simple arrangement is that it does not require a stable supply voltage. If the supply voltage changes, so will the output potential from R3 and Th1. However, the output potential from VR1 will change as well. The temperature at which two sides of the bridge provide the same voltage, and the alarm is activated, is always the same, regardless of the supply voltage. Th1 is a "47k bead" thermistor, but the value of 47k refers to its resistance at 25 degrees Celsius. Its typical resistance is 155.6k at 0 degrees Celsius, and around 220k at the typical operating temperature in this application. VR1 is therefore adjusted for an output potential of about half the supply voltage. A variable reference voltage is needed so that it can be adjusted to compensate for component tolerances, and the exact threshold temperature required. C2 and C3 filter out any "hum" or other noise picked up in the wiring at the inputs to IC1. The circuit lacks any hysteresis, and in theory it is possible for the output of IC1 to go to an intermediate voltage. In reality, the gain of the circuit is so high that this does not seem to happen, although there might be a small amount of "jitter" as the alarm switches on. In practice it seems to be better to tolerate this than to add triggering, which could impair the circuit's ability to respond to small temperature changes. TR1 is the electronic switch, and this is a simple pnp common emitter switching stage. When the output of IC1 goes low, TR1 is switched on and it connects the battery supply through to the alarm generator. The vco uses IC2 in

what is basically just a standard 555 astable (oscillator) circuit. The output of IC2 directly drives IC3, which is a ceramic resonator and not a moving coil loudspeaker. The circuit might operate properly using a high impedance (40 ohm or more) loudspeaker, but a ceramic resonator requires a far lower drive current and is a safer option. The output frequency range of IC2 is quite high, but it is a frequencies of a few kilohertz that a ceramic resonator provides peak efficiency.

The low frequency modulation signal is generated by IC3, which is another 555 astable. The higher timing component values give it a low operating frequency of around 3Hz. IC3's output is coupled to the lowpass filter, which is a simple passive type (R8 - C6). The modulation is applied to pin 5 of IC2. Without the modulation, C5 is first charged to two thirds of the supply potential via R6 and R7, and then discharged to one third of the supply voltage via R7 and an internal switching transistor of IC2. The circuit oscillates indefinitely, with C5 being repeatedly charged and discharged in this manner. The output at pin 3 goes high while C5 is being charged, and low while it is being discharged.

It is possible to vary the upper threshold voltage by applying a voltage pin 5 of IC2. Pulling the threshold voltage higher increases the charge and discharge times of C5, and reduces the output frequency. Taking the threshold voltage lower reduces the charge and discharge times, giving a higher output frequency. This gives a rather crude form of frequency modulation, but it gives good results in an undemanding application of this type.

It is important that the circuit has a very low standby current, so that it can operate continuously for months without exhausting the battery. The high values used in the bridge circuit help in this respect, and the current is further reduced by using a low power device for IC1. The current consumption of the alarm generator circuit is not important, as it is switched off under standby conditions. A leakage current will flow through TR1, but this is too low to be of any significance.

Under quiescent conditions the prototype had a measured current consumption of 120 microamps. The capacity of a PP3 size battery is typically about 0.35 to 0.55 amp/hours, but is effectively higher with the minute current drain involved here. This gives a battery life which is typically about six months to one year. The current consumption is about 12 milliamps when the alarm generator is switched on.


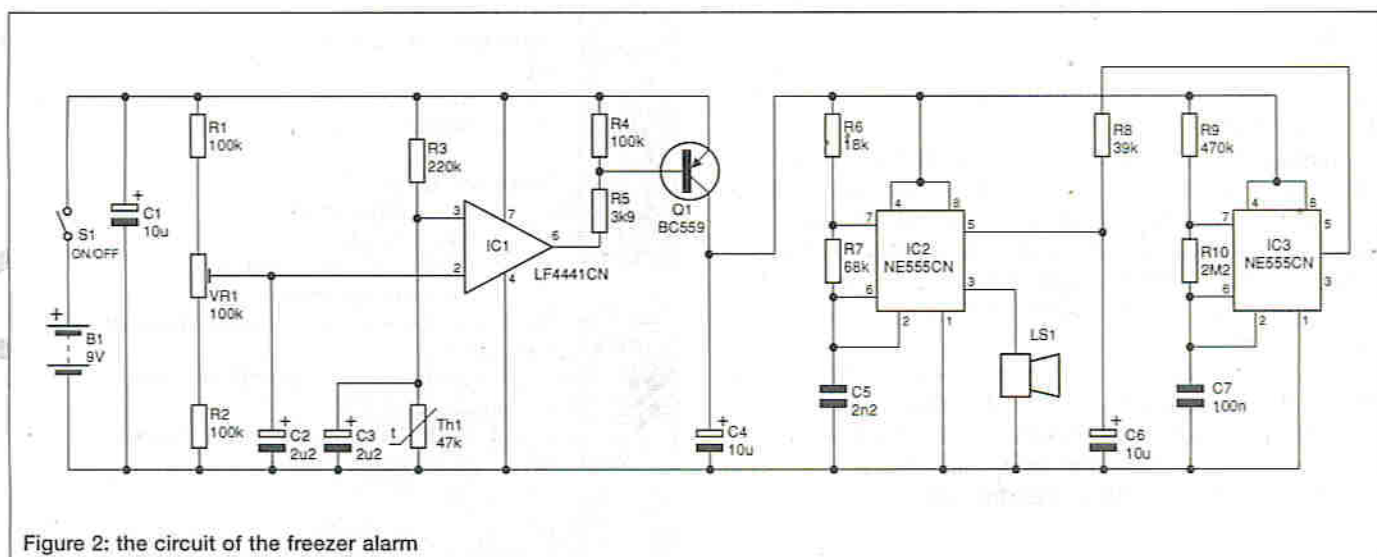


Figure 2: the circuit of the freezer alarm

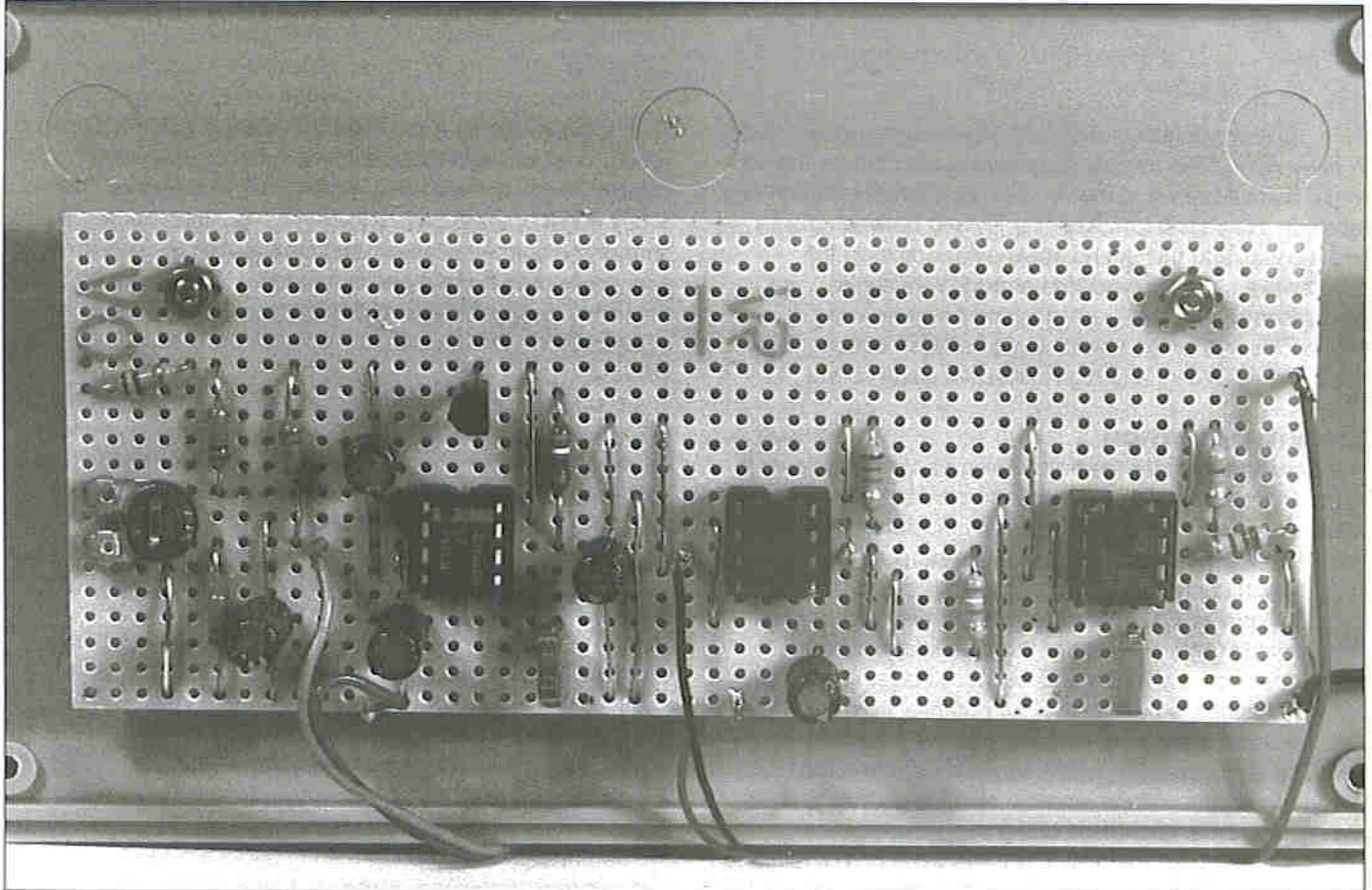

Construction

The circuit is assembled on a 0.1 inch pitch stripboard panel which measures 47 holes by 19 copper strips, using the component layout shown in figure 3. The underside view of the board appears in figure 4. Start by trimming a board to the correct size using a hacksaw, and then drill the two 3.2 millimetre diameter mounting holes. To complete the preparation of the board make the breaks in the copper strips. A special strip cutting tool is available, but a hand held twist drill bit of about five millimetres in diameter also does the job quite well. Modern stripboard is quite thin and brittle, so try not to cut any deeper into the board than is really necessary in order to fully break each strip. Cutting too deeply can seriously weaken the board.

Next the components and link-wires are added. None of the integrated circuits are static sensitive, but I would still recommend using holders for all three. The link-wires can be made from tinned copper wire of about 0.56 millimetres in diameter (24 swg), or the trimmings from the resistor and capacitor lead-out wires might suffice. C5 and C7 must be printed circuit mounting types having 7.5 millimetre (0.3 inch) lead spacing if they are to fit neatly into this layout. Fit single-sided solder-pins at the points where connections to Th1, LS1, etc. will be made.

This project will fit into practically any small to medium size plastic box. The removable lid becomes the rear panel, and the circuit board is mounted on this panel. In general, plastic stand-offs do not seem to work very reliable with stripboard, and it is probably best to use 6BA or metric M3 nuts and screws to fix the board in place. On/off switch S1 and LS1 are mounted on the front panel.

Cased ceramic resonators normally have provision for two small (8BA or M2) mounting bolts. The easiest way of mounting LS1 is to bolt it in place on the front surface of the panel. A small hole must then be drilled at the appropriate point in the panel to permit the two "flying" leads to pass through to the interior of the case.

PARTS LIST for the Freezer Alarm

Resistors (all 0.25 watt 5% carbon film)

R1,2,4	100k (3 off)
R3	220k
R5	3k9
R6	18k
R7	68k
R8	39k
R9	470k
R10	2M2

Potentiometer

VR1	220k min hor preset
-----	---------------------

Capacitors

C1,4,6	10u 25V radial elect (3 off)
C2,3	2u2 50V radial elect (2 off)
C5	2n2 polyester (7.5mm lead spacing)
C7	100n polyester (7.5mm lead spacing)

Semiconductors

IC1	LF441CN
IC2,3	NE555CN (2 off)
Q1	BC559

Miscellaneous

S1	spst toggle switch
B1	9 volt (PP3 size)
LS1	cased ceramic resonator
Th1	47k bead thermistor

Plastic box, 0.1 inch pitch stripboard measuring 47 holes by 19 copper strips, 8-pin dil holder (3 off), battery connector, 40 swg enamelled copper wire, multi-strand connecting wire, solder, etc.

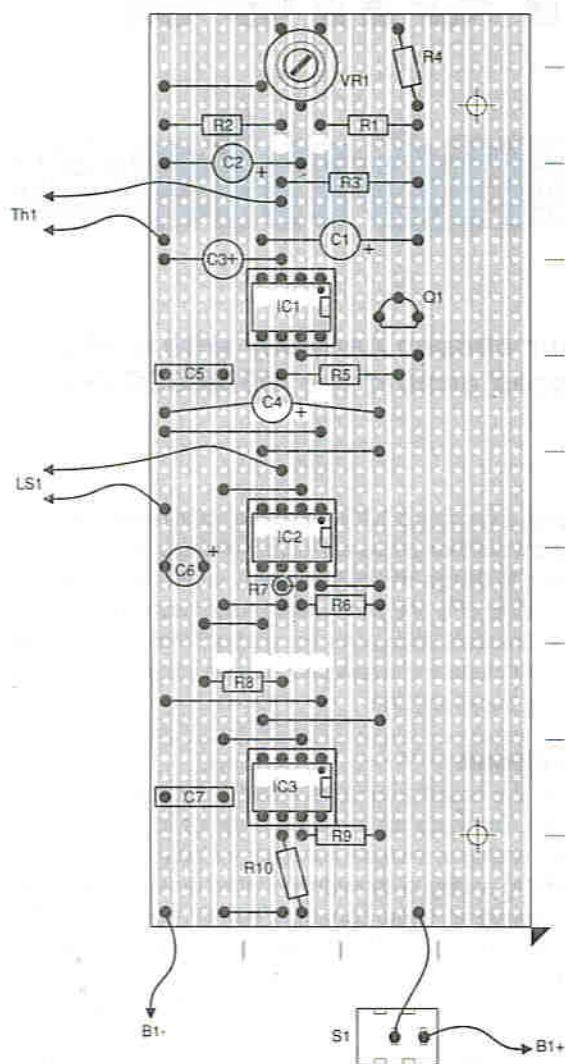


Figure 3: the stripboard layout and wiring

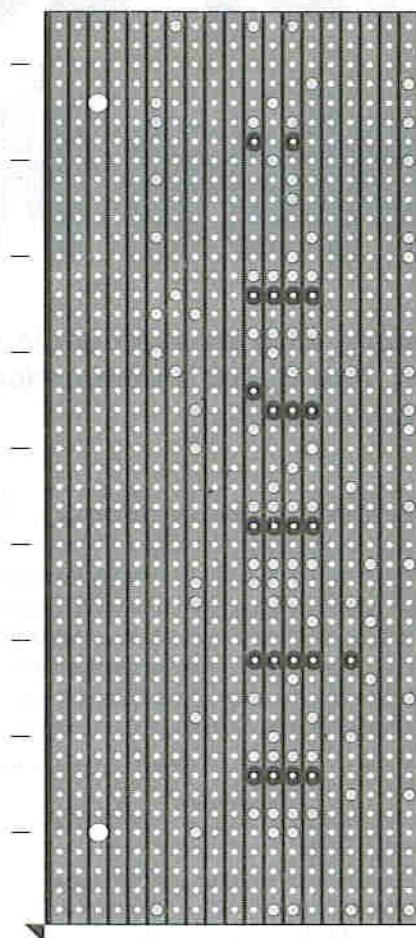


Figure 4: the underside of the stripboard panel

The alternative is to mount LS1 on the rear surface of the panel. A large cutout will then be needed to accommodate the main body of the component. Most ceramic resonators seem to have one black lead and one red one. This is presumably to indicate the phasing, since these components are not polarised, and can be connected either way round.

Th1 can be wired direct to the circuit board, and a small entrance hole for the two leads must then be drilled somewhere in the case. On the prototype Th1 is connected to the circuit board via a 3.5 millimetre jack socket mounted on the front panel, and a matching jack plug fitted to the extension wires from Th1. The enamel insulation is easily removed from the connecting wires using the blade of a penknife, but go very gently or the wire may be damaged and have a tendency to break. Use pvc sleeving over the leads of the thermistor to prevent any accidental short circuits. The connecting wires can be a few metres long if necessary.

In Use

It is best if the thermistor is positioned near the front of the freezer, where it will respond rapidly if the door is not

closed properly. The exact positioning will have to be chosen to suit your particular freezer, but it will probably be necessary to tape the extension leads to the outside of the freezer to help keep everything in place. These leads are very thin and easily broken, so the alarm must be positioned somewhere that enables the leads to be tucked away out of harms way.

Give the thermistor a couple of minutes or so to adjust to the temperature inside the freezer before switching on the alarm and testing it. By adjusting VR1 it should be possible to switch the alarm generator on and off. The optimum adjustment for VR1 is the most counter-clockwise setting that does not result in the alarm sounding. Having given VR1 a suitable setting, try touching the thermistor to warm it up. If all is well, this should result in the alarm being activated within a few seconds. In use the alarm might tend to sound when new food is stored in the freezer, or possibly even if the door is opened for more than a few seconds. Fractionally backing off VR1 in a clockwise direction will make the unit a little less sensitive, and should avoid false alarms.

The circuit is set to operate in binary mode by connecting the mode select (MS) pin to the supply voltage. This enables the ic to be controlled by the binary code that is fed to input pins 5,2,1 and 3, according to the pitch conversion table in Table 2. From the table, it can be seen that both the sampling frequency and the low pass filters are variable relative to the pitch changes - this reduces the chances of aliasing occurring.

The binary code presented to the voice harmoniser IC3 is derived from the output of IC2, a PIC microcontroller which takes the MIDI note-on data, via opto-coupler IC1, and converts it into the required 4-bit binary number to operate the pitch controller IC3. Since no pitch change occurs with the binary input equal to 1000, this is output to the I/O port for the notes that have no corresponding pitch change available. The eight selections from 0000 to 0111 produce corresponding downward pitch changes, whereas a binary output ranging from 1000 up to 1111 produces upward pitch changes.

Analogue section

The microphone input is fed to two pre-amplifiers - one contained in IC3 whose mid-band gain is set by R2/R1, and a direct feed based around IC5A whose mid-band gain is set by $(1+R3/R4)$ - and used in the non-inverting mode to allow in-phase mixing of the direct and effect voices. A summing amplifier IC5B combines three inputs, direct voice, effect voice and external source and feeds them to the line output.

In order to improve the signal-to-noise ratio, the audio signal is routed through a compander consisting of compression via IC4B and expansion via IC4A. The mic amplifier output from IC3 is fed to the compressor IC4B and then to a line amplifier in IC3 whose mid-band gain is set by R14/R13. The analogue output, Aout, from IC3 is fed via expander IC4A to the summing amplifier IC5B.

Compression involves reducing the dynamic range of the input signal being processed so that with a 2:1 compression ratio if the input increases by 12dB then the output increases by only 6dB.

Conversely, expansion increases the dynamic range, so when the input to the expander increases by 6dB the output will increase by 12dB which is a 1:2 expansion ratio, or alternatively, if the input falls by 6dB, the output drops 12dB. At the same time the noise introduced in the system will be reduced on expansion, since it was not subject to the initial compression treatment and is therefore expanded downwards below the lowest dynamics of the audio signal. This process is illustrated in figure 3.

Software operation

The software initialises port A to be inputs and port B to be outputs. On power-up, the switches SW1-4 are read through port pins RA0 to RA3 and decide the MIDI channel which the harmoniser will operate on, from binary 0000 (0) to 1111 (15). The software then waits to detect a note-on in the range mid C (60) to B (71) above it. Outside this range a note-on is ignored. This decides the musical key in which the harmoniser will operate. This allows relative pitch shifting in any key. So in the key of C, the note E would be four semitones up. Whereas in the key of D, the note F# would be four semitones up.

The software then checks for MIDI status and correct channel and, when these match, checks for note-on or note-off and carries out these routines if selected. Both routines allow for MIDI running status. Also, the harmoniser can be switched off if a correct note-off or a note-on with a velocity of zero are received. When a note-on is received, it is checked to see if it is in the correct range relative to the musical key previously selected, plus or minus an octave. Notes outside this range are ignored.

So when a song is being sung, the harmony at the output can be changed by the MIDI keyboard selection at any part in the song. However, since there are only 16 possible pitch changes, not every semitone of the keyboard is operational. The pitch changes that are available are shown in Table 2.

The harmoniser can be controlled in real-time via a MIDI keyboard, or the MIDI data can be recorded onto a track of a MIDI sequencer allowing automatic changing of harmonies as a song progresses. The relative levels of the direct and harmonised voices can be controlled via the built in mixer controls VR2 and VR3. Also the external input, controlled via VR1, can be fed from a previously recorded mix of voices thus allowing the building of multi-part harmonies.

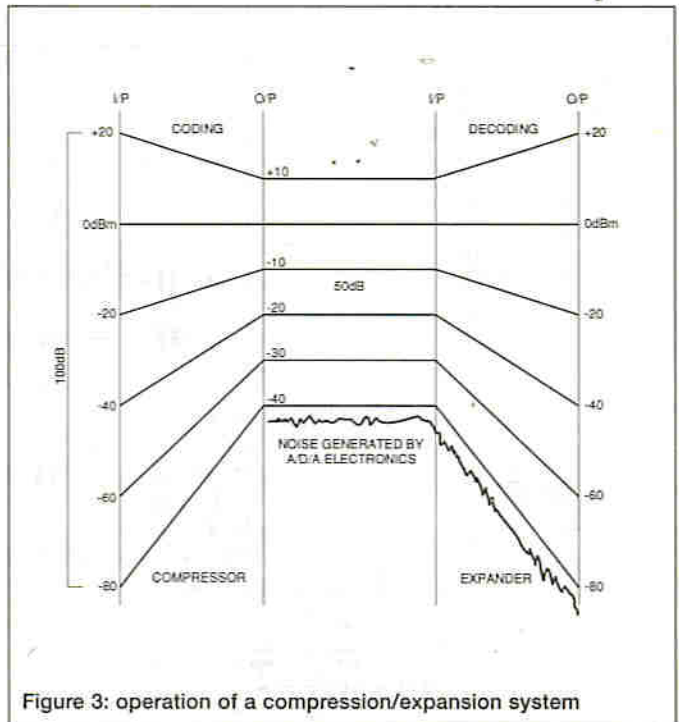


Figure 3: operation of a compression/expansion system

PIN NAME	PIN NUMBER	D/I/A/O	FUNCTION
MICIN	16	AI	INPUT TO MIC. PREAMP MUST BE CAPACITIVELY COUPLED
LOUT	15	AO	OUTPUT OF MIC PREAMP
LIN	14	AI	INPUT TO LINE AMP. MUST BE CAPACITIVELY COUPLED TO EITHER LOUT OR THE LINE OUT SIGNAL FROM AUDIO SOURCES
FIN1	13	AO	SETS THE INPUT AUDIO SIGNAL AMPLITUDE IN COMBINATION WITH THE LIN PIN
STB/ACT	4	DI	CHIP SELECT PIN. THE PROCESSING IS INTERRUPTED BY STOPPING CLOCKS OTHER THAN THE OSCILLATOR WHEN THE CHIP SELECT PIN IS AT THE H LEVEL
TEST 1	7	DI	MANUFACTURERS TEST PINS
TEST 2	8	DI	MUST BE CONNECTED TO 0V
XT,XT	22,23		EXTERNAL CAPACITORS ARE CONNECTED HERE TO STABILISE THE INTERNAL ANALOGUE VOLTAGE REFERENCES OF $\frac{1}{2} AV_{DD}$
DAO	9	AO	OUTPUT FROM THE DIGITAL TO ANALOGUE CONVERTER
FIN2	10	AI	INPUT PIN FOR INTERNAL LOW PASS FILTER (FOR OUTPUT)
AOUT	11	AO	OUTPUT OF LOW PASS FILTER (FOR OUTPUT)
D _{DD}	21		DIGITAL POWER SUPPLY PINS
DV _{DD}	24		
A _{GND}	18		ANALOGUE POWER SUPPLY PINS
AV _{DD}	12		
			NOTE: DI DIGITAL INPUT AI ANALOGUE INPUT AO ANALOGUE OUTPUT

Table 1: Pin functions

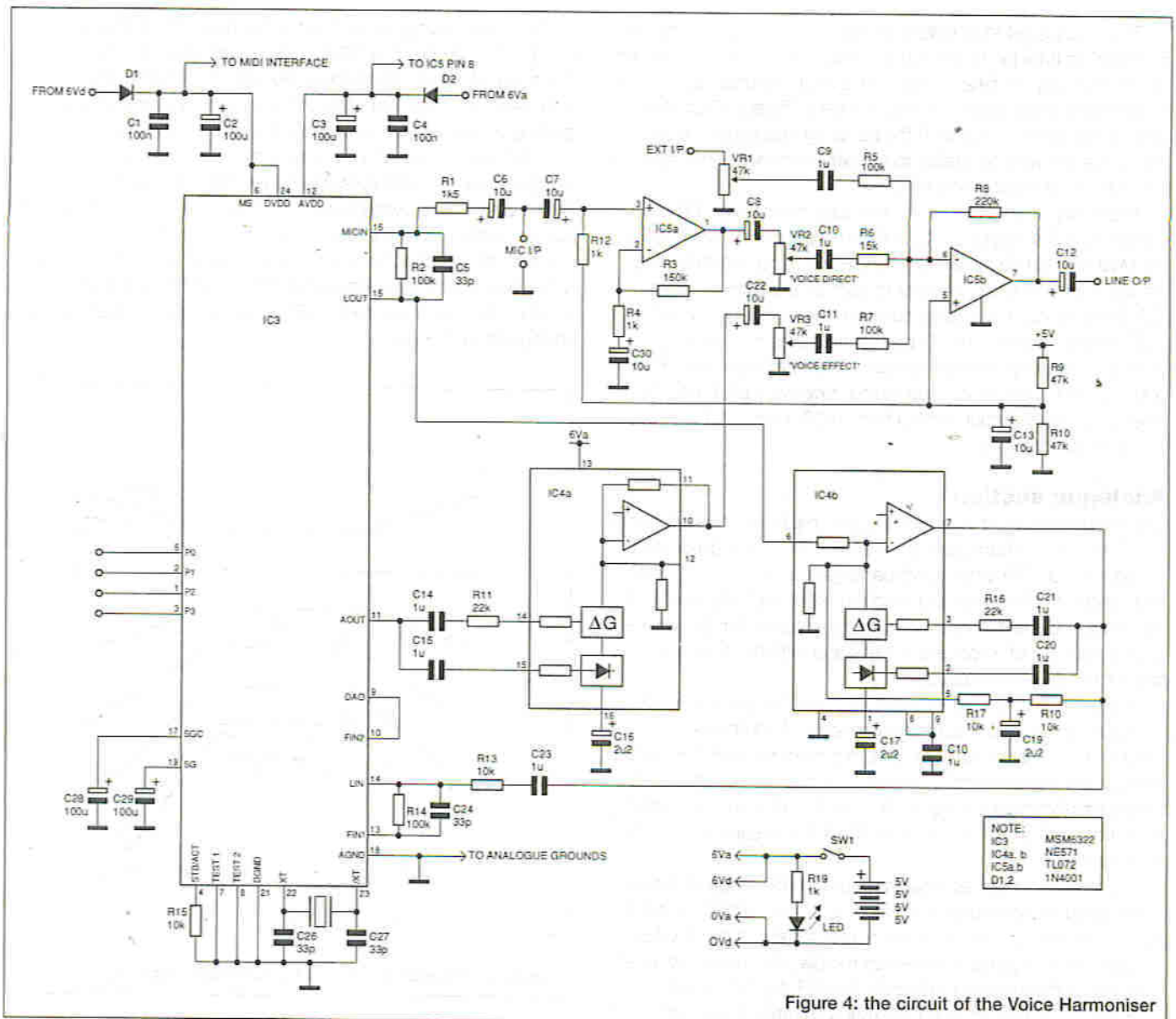


Figure 4: the circuit of the Voice Harmoniser

BIN MODE SETTINGS P3 P2 P1 P0	SCALE STAGE	DA SAMPLING CYCLE (μS) FREQUENCY (kHz)	LPF CUT-OFF FREQUENCY (kHz)	PITCH CHANGE
NOT AVAILABLE	16	60/16.6	7.6	1 octave up
1 1 1 1	15	71/14.0	7.6	9 semitones up
1 1 1 0	14	76/13.1	5.7	8 semitones up
1 1 0 1	13	80/12.5	5.7	7 semitones up
1 1 0 0	12	90/11.1	5.7	5 semitones up
1 0 1 1	11	95/10.5	5.7	4 semitones up
1 0 1 0	10	101/9.9	4.56	3 semitones up
1 0 0 1	9	113/8.84	4.56	1 semitone up
1 0 0 0	8	120/8.33	3.8	no pitch change
0 1 1 1	7	127/7.87	3.8	1 semitone down
0 1 1 0	6	143/6.99	3.26	3 semitones down
0 1 0 1	5	151/6.22	3.26	4 semitones down
0 1 0 0	4	160/6.25	3.26	5 semitones down
0 0 1 1	3	180/5.55	2.85	7 semitones down
0 0 1 0	2	190/5.26	2.53	8 semitones down
0 0 0 1	1	202/4.95	2.53	9 semitones down
0 0 0 0	0	227/4.4	2.07	1 octave down

Table 2: Pitch conversion table

The power supply

The circuit is designed for battery operation using four 1.5V type AA batteries and the current consumption is 20mA.

The analogue and digital power supplies need to be kept isolated to reduce the chance of digital noise introducing itself into the analogue signal path. So the 6 volts from the batteries is fed via D1 to the digital supply inputs of IC1, IC2, IC3, and via D2 to the audio dc supply input of IC3, IC4 and IC5. The diodes prevent damage to the ics if the batteries are fitted incorrectly. The pcb earth tracks for the digital and audio circuits are kept separate, and joined only at the battery terminals.

Construction

The components should be mounted in the following order: links, resistors, diodes, diode sockets, capacitors and finally electrolytic capacitors. You will need to check your leds in circuit to see which way round your type needs to be mounted. The 4MHz

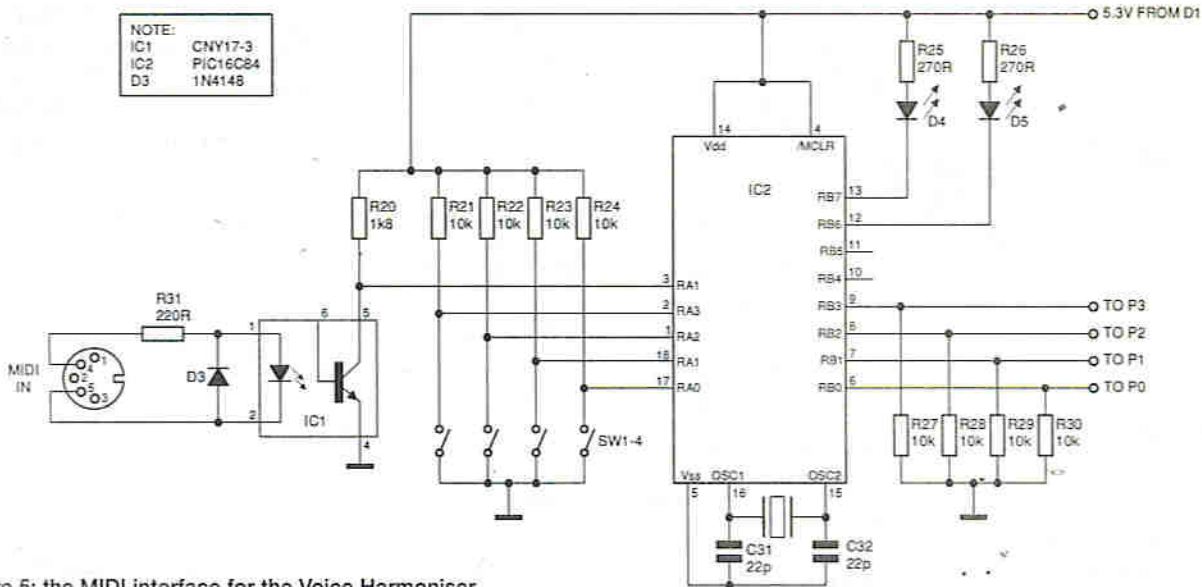


Figure 5: the MIDI interface for the Voice Harmoniser

crystal should be mounted flat on the pcb with its legs connected at 90 degrees into the pcb. The microphone input should be connected to the jack-socket via screened cable to reduce the chances of noise and hum pickup.

The MSM6322 IC3 is a surface mounted device and is soldered to the underside of the pcb. When mounting this component, the smallest possible size soldering bit should be used (less than 1mm), with 22 swg solder. Place the ic squarely on all 24 pins, and solder the opposite diagonal pins first, then solder the remaining pins allowing several seconds between each joint to allow the ic to cool down. The other ics are mounted in dill sockets to allow ease of changing for test or fault-finding purposes. Also, the correct orientation of IC3 is achieved by noting pin 1 being marked on the pcb.

Finally the connectors and controls need to be wired to the PCBs, and the pcbs connected together. Inspection of the pcb overlay diagrams shows the off-board connections, whose names are, for the most part, self explanatory.

Control connections P0, P1, P2, P3 run between the boards and you should take care to connect them in the right order. The midi interface pcb is powered from the pitch shift pcb where there are diodes to protect against reverse polarity. Note that it is powered from the digital supply. The 0V connection for the interface is from the battery.

Make sure to connect the midi connector the right way round, by checking the schematic against the pcb overlay.

The microphone input should be connected using screened cable, unless a metal case is used and the connection is only about an inch long.

On the interface board, switches 1 to 4 are each connected to opposite pairs of pads - with a separate ground connection being available for each one.

The potentiometer connections to the main board should be kept as short as practical, though the signal levels here are greater than microphone level. Pot wires should not be run next to the other wiring to avoid introducing noise. Note that the wiper connection for the voice effect pot is separated from its other two connections. Again, it is necessary to check the layout connections against the schematic to ensure that the pots are connected correctly.

A case has not been specified for this project. The choice of case is left to the reader.

Operation

It is difficult to sing in tune while listening to a pitch-shifted harmony of your own voice, so it is easier to just listen to your input voice while recording the mixture of voices onto tape. One of the limitations of the circuit is the fact that the digital converters in IC3 are only 8-bit, which reduces the quality of the overall sound.

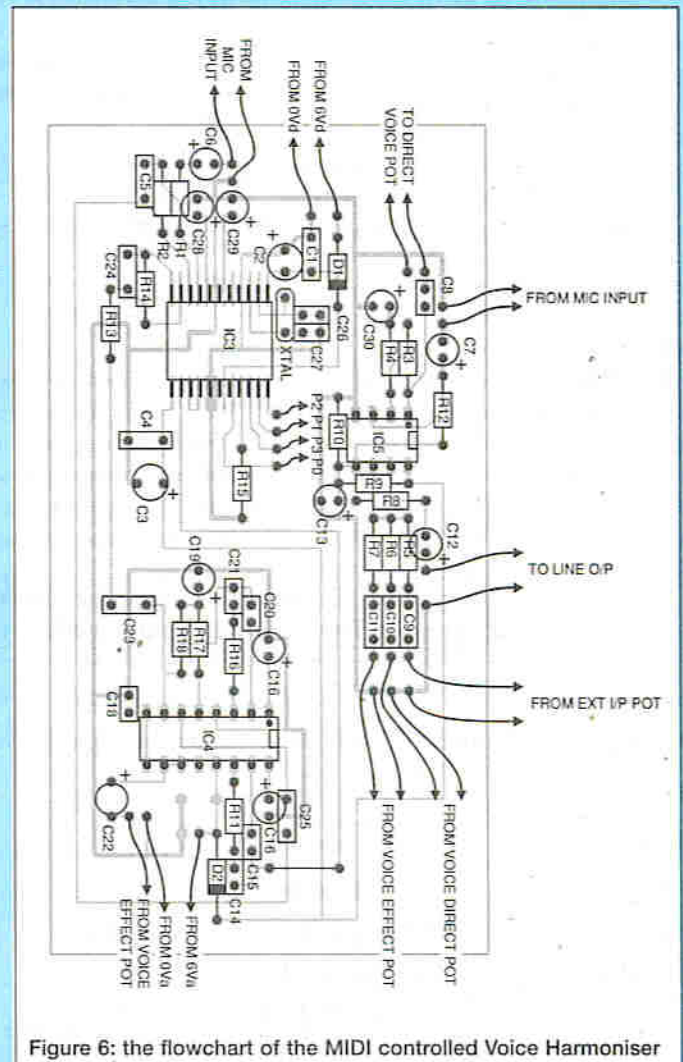


Figure 6: the flowchart of the MIDI controlled Voice Harmoniser

TEACHERS - STUDENTS -
HOME USERS, ETC.

attention Even More!

Your opportunity to save £££££'s

With this non commercial version of our software produced for single users, this is your dream come true!

Software as you are probably aware has no real material value, but is priced to recover the enormous costs of development. The software house tries to evaluate how many units will sell at a specific price to generate the amount needed and produce a healthy profit.

As the electronics marketplace shrinks, due to expanding competition, it means that, in reality, powerful user friendly software, such as EDWin, must be very highly priced and therefore remains inaccessible to the individual and small businesses.

Until today Norlinvest, one of the biggest software houses in the electronics sector, has decided to put onto the market a "Non Commercial" version of their EDWin software, which is known worldwide.

This is the first truly seamlessly integrated suite of software running in all Windows formats simulation, schematics and PCB design. At last allowing amateurs, teachers, students, in a word any "individual" to take advantage of *current technology*, without any restriction.

To avoid misunderstanding - there is no difference between the industrial software at £3,515.25 VAT inc. and the "NC Deluxe 3" normally at £114.00 VAT inc. - the difference rests solely in the licence. In other words, industry is subsidising the development costs and the individual can now take full advantage of this.


Computer Compatibility

To run the program you will need:

- Windows 3.x, Win95 or Win NT,
- a min. 386 processor
- 8mb of RAM • CD-ROM Drive



All Major Credit Cards Accepted

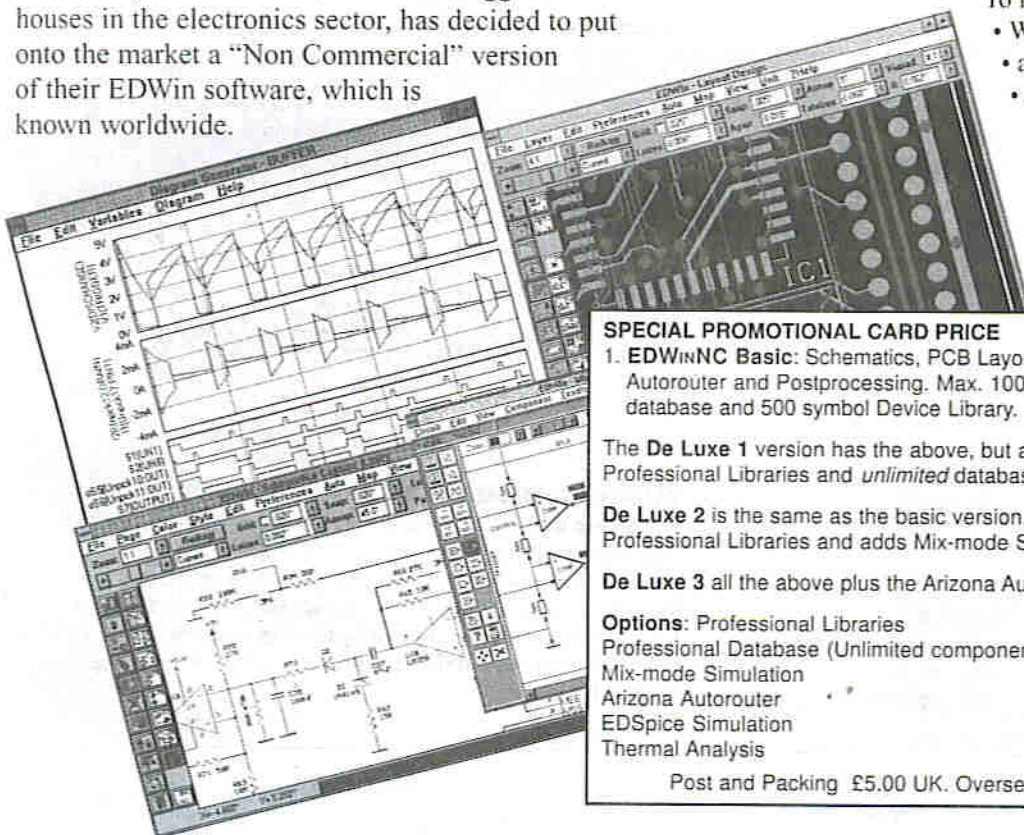

SPECIAL PROMOTIONAL CARD PRICE		Normal Price	Promotional Card Price
1. EDWinNC Basic: Schematics, PCB Layout with Basic Autorouter and Postprocessing. Max. 100 component database and 500 symbol Device Library.		£49.00	* £44.10
The De Luxe 1 version has the above, but also includes Professional Libraries and unlimited database components.		£79.00	£71.10
De Luxe 2 is the same as the basic version, but with Professional Libraries and adds Mix-mode Simulation.		£79.00	£71.10
De Luxe 3 all the above plus the Arizona Autorouter.		£114.00	£102.60
Options: Professional Libraries		£24.00	£21.60
Professional Database (Unlimited components)		£24.00	£21.60
Mix-mode Simulation		£24.00	£21.60
Arizona Autorouter		£24.00	£21.60
EDSpice Simulation		£49.00	£44.10
Thermal Analysis		£19.00	£17.10
Post and Packing £5.00 UK. Overseas £10.00 Prices include VAT			

EDWIN NC
ELECTRONIC DESIGN FOR WINDOWS NON COMMERCIAL

This offer also applies to all academic institutions - minimum order two systems.

Swift Designs Ltd., Business & Technology Centre, Bessemer Drive, Stevenage, Herts. SG1 2DX.

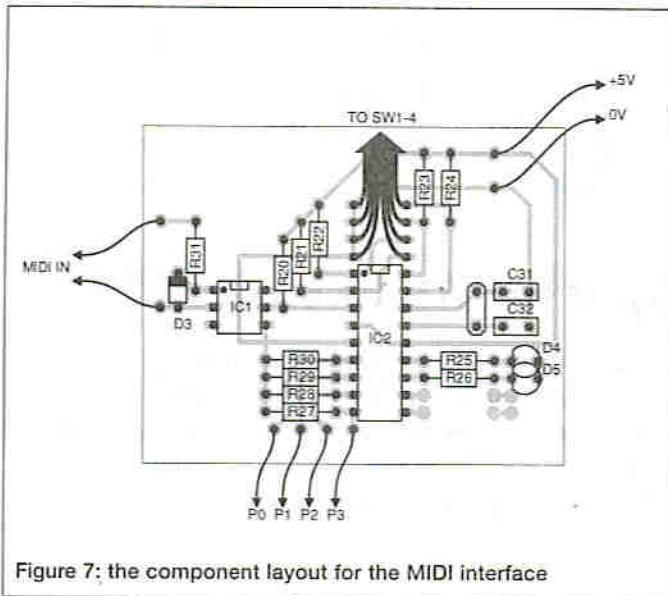


Figure 7: the component layout for the MIDI interface

Further development

To allow further development, the MIDI keyboard decoder and voice harmonizer are built on separate pcbs. More than one pitch controller could then be used to produce up to four or five-part harmonies, controlled via the output ports of a microcontroller.

The pads on the MIDI interface board next to R25 and 26 and D4 and 5 (leds) are empty.

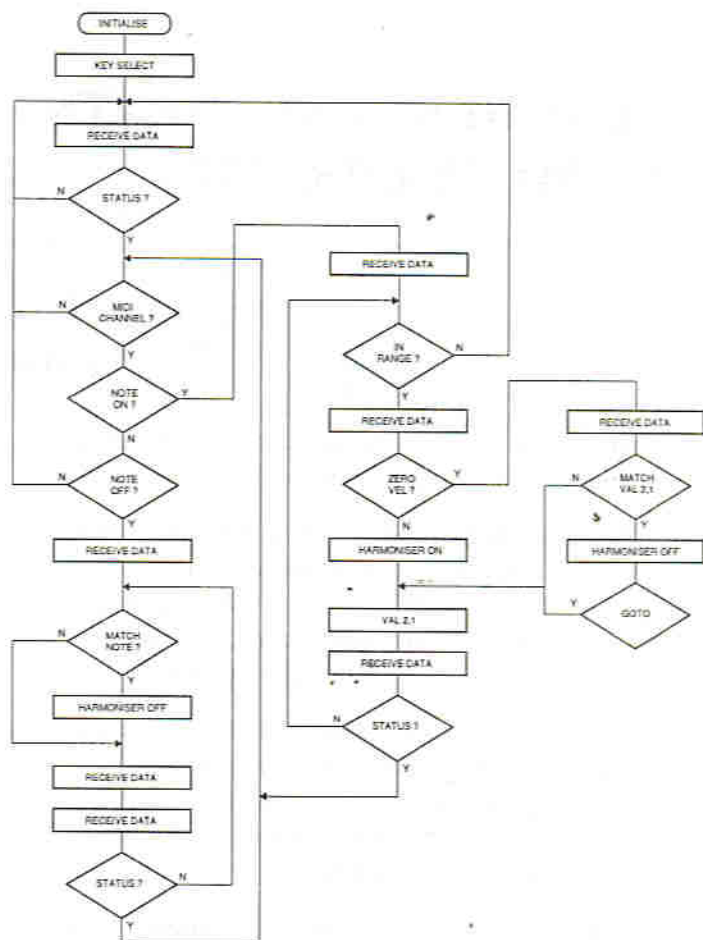


Figure 8: the component layout for the Voice Harmoniser

PARTS LIST for the MIDI Voice Harmoniser

Resistors:

(All 0.25W metal film)

R1	1k5
R2,5,7,14	100k (4 off)
R6	15k
R3	150k
R8	220k
R9,10	47k
R11,16	22k
R13,15,17,18,19	10k (5 off)
R21 to R24, R27 to R30	10k
R4,19,12	1k
R31	220R
R20	1k5
R25,26	270R
VR1,2,3	47k Log.

Capacitors

C1,4	100nF 16V mini disc
C2,3	220uF 10V min elect.
C28,29	100uF 10V min elect.
C5,24,26,27	33pF ceramic
C6,7,8,12,13,22,30	10uF 16V min elect
C9,10,11,14,15,18,20,21 ...	

... 23,25	1uF (non-electrolytic)
C16,17,19	2u2F 16V min elect.
C31,32	22pF ceramic

Semiconductors

IC1	CNY17-3
IC2	PIC16C84
IC3	MSM6322
IC4A,B	NE571
IC5A,B	TL072
D1,2	IN4001
D3	IN4148
D4,5	Leds

Miscellaneous

IC holders 6-pin (1 off), 8-pin (1 off), 16-pin (1 off), 18-pin (1 off), crystals 4MHz and 10MHz, SPST switch, leds, 6mm jack sockets (3 off), 4 x 1.5V battery holder and enclosure of suitable size. A pre-programmed PIC 16C84 is available for £15.00. The program software by itself is available on disk for £4.00 from the author at, 1 Martello Court, Portmarnock, Dublin, Ireland.

```
list P=PIC16C84

;Program to RX. MIDI data
with 10Mhz clock
;MIDI controlled voice
harmoniser
;Filename: Harmidl.asm
;Date: 23/01/1997

;*****
; Variable Assignment Addresses
;*****
dlyregequ 0C
```

```
rcountequ 0D
rcvregequ 0E
offsetreg equ 0F
notevall equ 10
noteval2 equ 11
midichequ 12
note equ 13

;*****
; Constant Assignments
;*****
CARRY equ 00
MSB equ 07
```

```
BORROWequ 00
LED equ 07
W equ 00
F equ 01
Z equ 02
C equ 00
dx equ 05

;*****
; Port Assignments
;*****
PCL equ 02
STATUS equ 03
```

```

PORTA equ 05
PORTB equ 06

;*****
; PROGRAMME Reset Point
;*****
org 0
goto INIT

;*****
; Subroutines
;*****

delay1 movlw .27
movwf dlyreg
dly1 nop
decfsz dlyreg
goto dly1
nop
return

delay2 movlw .17
movwf dlyreg
dly2 nop
decfsz dlyreg
goto dly2
nop
return

rxdata btfsc PORTA,4
goto rxdata
movlw .8
movwf rcount
clrf rcvreg
call delay1

rnext bcf STATUS,CARRY
rrf rcvreg
btfsc PORTA,4
bsf rcvreg,MSB
call delay2
decfsz rcount
goto rnext
return

keysel call rxddata
movf rcvreg,W
andlw #$F0
sublw #$90
btfss STATUS,Z
goto keysel
call rxddata
movlw .184
addwf rcvreg,W
btfsc STATUS,CARRY
goto keysel
movlw .60
subwf rcvreg,W
btfss STATUS,BORROW
goto keysel
movwf offsetreg

bcf PORTB,LED
return

;*****
; Initialise Software
;*****
INIT clrf PORTB
movlw 00H
TRIS PORTB ;MAKE
PORTB ALL 0/Ps

```

```

movlw #$F8
movwf PORTB

clrf PORTA
movlw 0FFH
TRIS PORTA ;make
PORTA all 1/Ps

clrf noteval1
clrf noteval2

movf PORTA,W ;read
midich switches
andlw #$0F
movwf midich

;*****
; Main Program Start
;*****

main call keysel

start call rxddata ;is it
status?
movf rcvreg,W
andlw #$80
sublw #$80
btfss STATUS,Z
goto start

midich? movf rcvreg,W ;cor
rect MIDI Ch?
andlw #$0F
subwf midich,W
btfss STATUS,Z
goto start

noteon? movf rcvreg,W
andlw #$F0
sublw #$90
btfsc STATUS,Z
goto noteon
movf rcvreg,W
andlw #$F0
sublw #$80
btfsc STATUS,Z
goto noteoff

goto start

noteon call rxddata ;check
note range
nrange movf rcvreg,W
movwf noteval2
movf offsetreg,W
sublw .184
addwf noteval2,W
btfsc STATUS,C
goto start
movf offsetreg,W
addlw .48
subwf noteval2,W
btfss STATUS,BOR

ROW goto start
movwf note

vel call rxddata
movf rcvreg,F
btfsc STATUS,Z
goto zerovel
movf note,W
call convert
movwf PORTB

```

```

val2tol movf noteval2,W
movwf noteval1

call rxddata ;sta
tus or note?
movf rcvreg,W
andlw #$80
sublw #$80
btfss STATUS,Z
goto nrange
goto midich?

zerovel movf noteval2,W
subwf noteval1,F
btfss STATUS,Z
goto val2tol
movlw #$08 ; harm
off

movwf PORTB
goto val2tol

noteoff call rxddata ; note
value?
match movf rcvreg,W
subwf noteval2,W
btfss STATUS,Z
goto offvel

movlw #$08 ; harm
off

movwf PORTB

offvel call rxddata ;vel-off
value

call rxddata ;stat
us or note-off
movf rcvreg,W
andlw #$80
sublw #$80
btfss STATUS,Z
goto match
goto midich?

convert addwf PCL
retlw 00
retlw #$08
retlw #$08
retlw #$01
retlw #$02
retlw #$03
retlw #$08
retlw #$04
retlw #$05
retlw #$06
retlw #$08
retlw #$07
retlw #$08
retlw #$09
retlw #$08
retlw #$0A
retlw #$0B
retlw #$0C
retlw #$08
retlw #$0D
retlw #$0E
retlw #$0F
retlw #$08
retlw #$08
retlw #$08
retlw #$08
end


```

Experimenting with Video

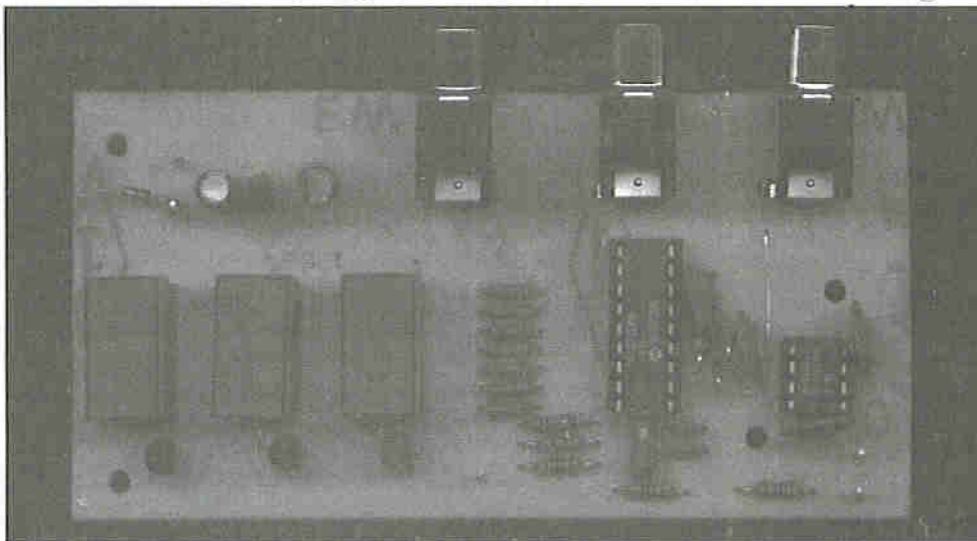PART 4

A Video Line Trigger

For the experimenter or developer of video projects, Robin Abbott's video line trigger allows the examination of a specific line in the video frame.



Over the last couple of months we have looked at the structure of the video signal, and built a sync separator which was used for a video mixer/fader. In the next two articles we will have a look at building test equipment of use for the experimenter or developer of video projects.

This month's project is a video line trigger suitable for an oscilloscope.

An oscilloscope is virtually essential for serious work with video signals, and it is very useful to be able to look a specific line in the video frame. Although it is possible to trigger the oscilloscope from the frame signal, and then use the delay facility to examine a specific line, it is not easy to identify a specific line in each frame. This project allows the user to select a line, and it then produces a trigger signal suitable for the external trigger input of an oscilloscope. This enables a specific line to be examined in each frame, considerably simplifying circuit debugging.

This circuit makes use of a cheap PIC microcontroller to implement a video line trigger device which is considerably less complex and less expensive than commercially available units.

Operation

In operation the line trigger consists of a small unit with a three-digit, seven-segment display, and two pushbuttons for up and down. The unit is powered from an external 9 to 30V supply rail. The video signal is supplied to the unit on a standard phono socket, and provides a phono output, so that the unit can be placed in line with a video signal under test.

There is also an output on a phono socket for the trigger signal of the oscilloscope. The push buttons select the line which is to be examined. If one is pressed briefly, then the line count increases or decreases by one. If one is held down, then the count runs more rapidly. If the unit is left powered up, and the line selection is not changed for more than five minutes, then the unit automatically writes the current line into internal eeprom, and will use this value next time the unit is powered up. This makes the unit considerably easier to use on a day by day basis on a project.

The display will flash, and the unit will not allow keypresses when there is no video signal present.

The output of the unit is a single low-going pulse of about 4 μ s, which is approximately coincident with the colour burst on the selected line. This may be connected directly to the external trigger input of the 'scope.

In practice it is probably better to trigger from the line immediately prior to the required line. The first synchronisation pulse shown on the 'scope will be at the start of the required line.

The circuit

Figure 1 shows the circuit diagram. The main work of the unit is performed using a PIC - a 16C84 in this case. The 16C84 is used because it has an internal eeprom data store, which is employed to store the line set by the user and ensure that, on power-up, the same line is displayed as was previously used.

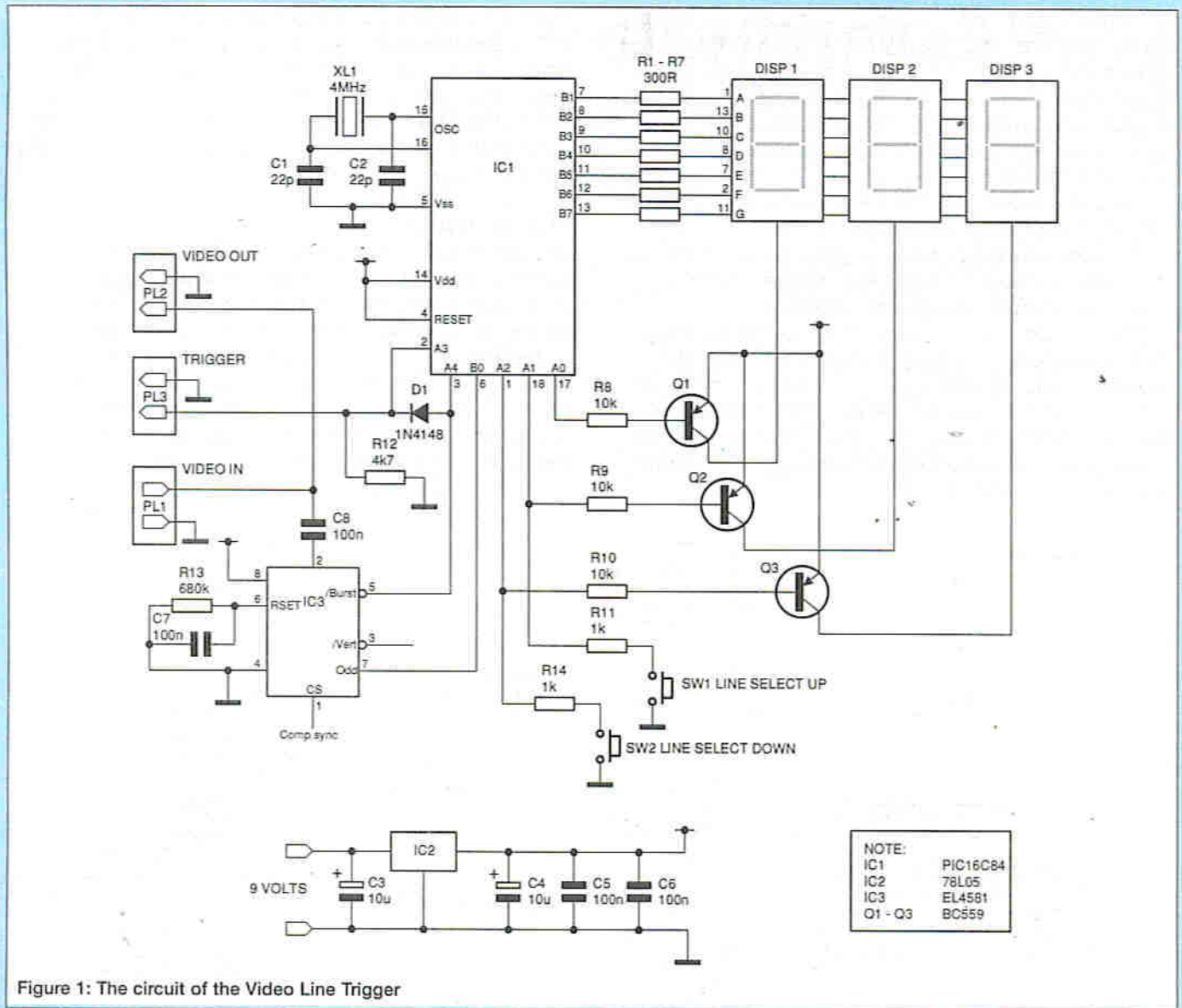


Figure 1: The circuit of the Video Line Trigger

The incoming video signal is not terminated, as the unit is expected to be used in line with other equipment. However it will operate successfully without requiring connection to other equipment with termination.


The video signal is supplied to the EL4581 sync separator. This ic provides detection of the frame signals in the incoming video signal. It also provides a colour burst output - a short pulse following the horizontal synchronisation pulse, which is approximately coincident with the colour burst in the line. The odd/even frame output is a signal which is high during the first field of the frame (the odd field), and is low during the second field of the frame (the even field).

The odd/even frame output is used to drive the interrupt input of the PIC, and causes an interrupt at the start of the first field.

The colour burst output is used to drive the counter input of the PIC, and it is this signal which is used to count the lines internally to the PIC.

The trigger output of the PIC (on pin RA3) must be retimed with the video signal. This is because the PIC has a resolution of 1us per internal instruction, and a latency of 3 or 4us to respond to an interrupt. This results in an error of up to 2us in the position of the trigger pulse output, which results in jittering of the oscilloscope trace.

Traditionally retiming would be achieved with D-type latch, such as an HC74; however, to simplify the circuit, the trigger signal from the PIC is wire OR'd with the colour burst signal. During normal operation the output of the PIC is driven high holding the trigger output high. Approximately 25us before the start of the desired line, the PIC places its output into a high impedance state. The trigger signal is then held high by the

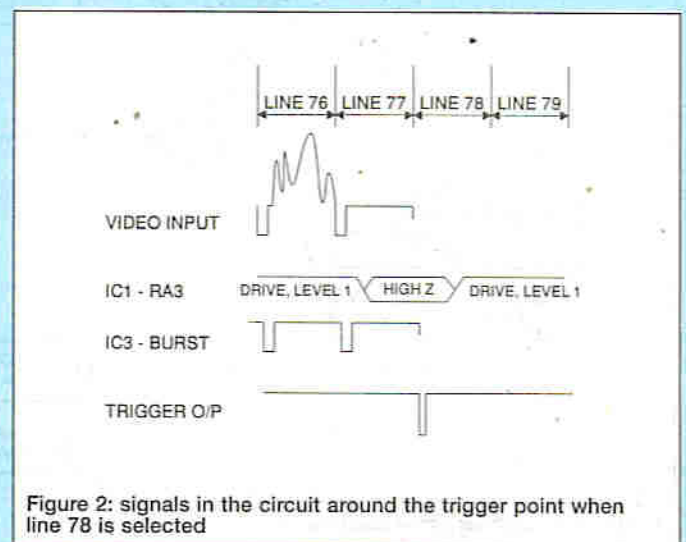

colour burst output. During the colour burst signal of the desired line the colour burst output also goes low, and the trigger output is pulled low by resistor R12. About 20µs after this, the PIC trigger output returns to driving a high level signal. This results in a trigger output which is synchronous with the video frame signals, and avoids jitter due to software operation. This is illustrated in figure 2.

The display is driven in a multiplexed fashion. The PIC has sufficient drive capability on its output port pins to drive small (0.3in) 7 segment displays directly, however, the common anode of the displays is driven through a PNP drive transistor. The displays are driven on a 5ms multiplexing cycle.

The push buttons are connected to the base of the display drive transistors using 1k resistors, as shown in the circuit. This is necessary due to the lack of I/O pins on the PIC. Normally the PIC drives the transistor bases through the 10k base resistor and drives them high or low, overriding the push buttons. When the PIC reads the push buttons, it sets the display outputs all high


which disconnects the seven-segment displays, and tri-states the PNP transistor base drive signals. Now the push button inputs are pulled high by the 10k resistors through the transistors base/emitter junction. However, if the push button is pressed then it will pull the input to around 0.5V, which is well below the PIC's low level input threshold, and the PIC will read a low logic level from the pin.

The software

The software operation of the unit is straightforward, but is of interest to other constructors of real time systems operating using microcontrollers. Figure 3 shows a block diagram of the main modules of the software, and the way in which they are called.

The main loop checks to see if a frame interrupt has occurred, and whether it is time to call the multiplexing routine to shift on to the next display digit. The main loop also maintains a counter which checks the time since the count was last changed. After about 5 minutes the value is written to the eeprom.

MAIN LOOP

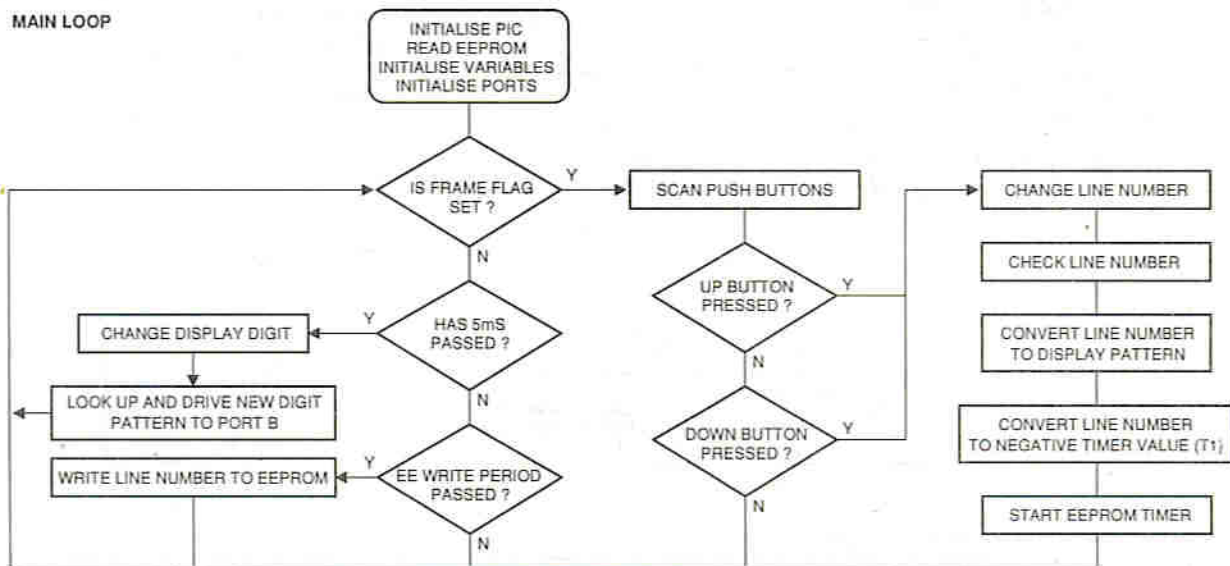

INTERRUPT ROUTINE

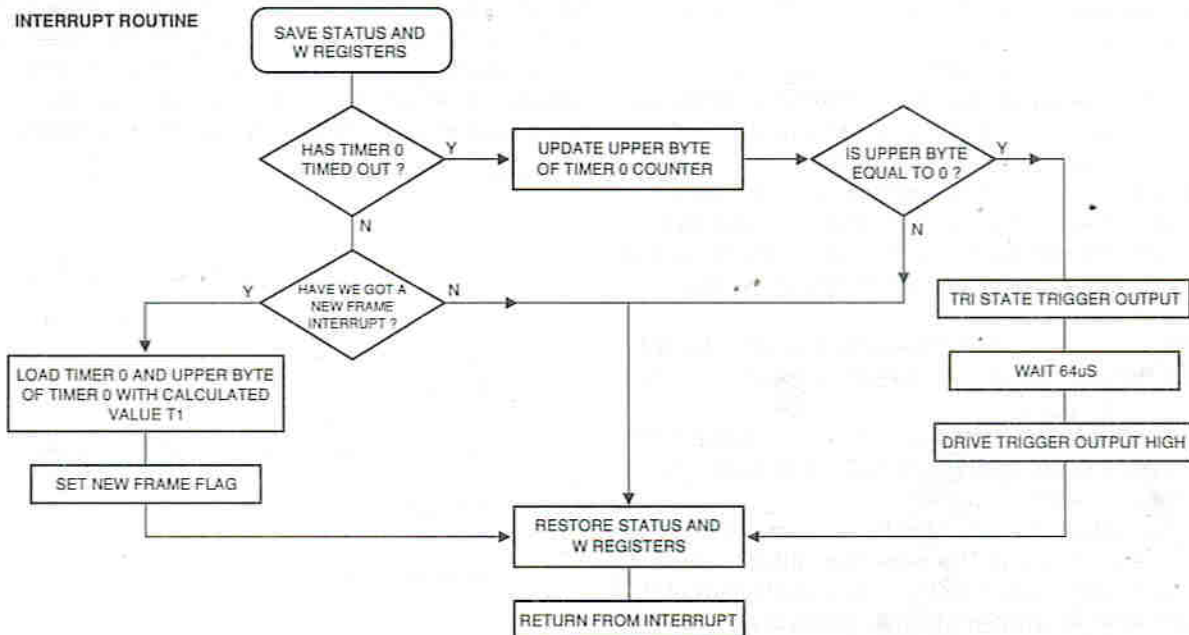


Figure 3: the software flow diagram

Electronics Components
 Station Road, Cullercoats,
 Tyne & Wear
 NE30 4PQ
 U.K.

4000 Series	74HC Series	74LS Series	74ALS Series
4000	74HC00	74LS00	74ALS00
4001	74HC02	74LS02	74ALS02
4002	74HC03	74LS03	74ALS03
4006	74HC04	74LS04	74ALS04
4008	74HC08	74LS08	74ALS08
4009	74HC10	74LS10	74ALS10
4010	74HC11	74LS11	74ALS11
4011	74HC12	74LS12	74ALS12
4098	74HC99	74LS99	74ALS99
4099	74HC00	74LS00	74ALS00
4100	74HC01	74LS01	74ALS01
4101	74HC02	74LS02	74ALS02
4102	74HC03	74LS03	74ALS03
4103	74HC04	74LS04	74ALS04
4104	74HC05	74LS05	74ALS05
4105	74HC06	74LS06	74ALS06
4106	74HC07	74LS07	74ALS07
4107	74HC08	74LS08	74ALS08
4108	74HC09	74LS09	74ALS09
4109	74HC10	74LS10	74ALS10
4110	74HC11	74LS11	74ALS11
4111	74HC12	74LS12	74ALS12
4198	74HC99	74LS99	74ALS99
4199	74HC00	74LS00	74ALS00
4200	74HC01	74LS01	74ALS01

ADM232AA	£3.55	TDA2611A	£1.88	BA158	£0.10	ZSBS48	£0.30	BC328	£0.10	BD807	£0.80
ADM485JN	£2.97	TDA2822A	£1.68	BA159	£0.10	BD1730	£1.44	BC328-16	£0.10	BDX22	£1.78
ADM690AN	£5.13	TED3718DP	£1.11	BY127	£0.13	AC136	£0.44	BC337	£0.10	BDX33C	£0.56
ADM691AN	£6.25	TEA5115	£3.07	BY127	£0.18	AC127	£0.50	BC337-25	£0.12	BDX34C	£0.50
ADM699AN	£6.48	TL061CP	£0.35	BY133	£0.10	AC128	£0.40	BC338	£0.10	BDX53C	£0.47
CA741CE	£0.26	TL062CP	£0.60	OAY47	£0.28	AC187	£0.48	BC338-25	£0.10	BDX54C	£0.50
CA747CE	£0.39	TL064CN	£0.72	OA90	£0.07	AC188	£0.48	BC348B	£0.14	BF180	£0.31
CA3046	£0.37	TL071CP	£0.48	OA91	£0.10	AC17	£0.48	BC357	£0.25	BF182	£0.31
CA3059	£1.16	TL072CP	£0.40	OA200	£0.56	AD149	£1.67	BC393	£0.73	BF185	£0.58
CA3080E	£0.73	TL074CN	£0.50	OA202	£0.29	AD161	£0.92	BC414C	£0.16	BF194	£0.31
CA3130E	£0.98	TL081	£0.33	Zeners 2.7 to 33V	£0.12	AD162	£0.92	BC441	£0.46	BF195	£0.19
CA3140E	£0.98	TL082CP	£0.54	400mW	£0.08	BC107	£0.16	BC461	£0.29	BF244	£0.35
CA3189E	£1.22	TL084CN	£0.40	1.3W	£0.14	BC107B	£0.17	BC463	£0.29	BF244C	£0.40
CA3240E	£1.12	TL12705ACT	£1.46	Bridge Rectifiers	£1.62	BC108	£0.16	BC478	£0.32	BF244C	£0.40
DG211CJ	£1.55	TL271	£0.54								



**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Cosson 3102 - 60MHz Dual Channel	£250
Gould OS 255 - 15MHz Dual Channel	£150
Gould OS 3351 - 40MHz Dual Channel	£220
Gould 1602 - 20 MHz D.S.O. with printer (cursors)	£1150
Hewlett Packard 1740A, 1741A, 1744A, 100MHz dual ch	from £350
Hewlett Packard 1707A, 1707B - 75MHz 2ch	from £275
Hewlett Packard 54100D - 1GHz Digitizing	£2995
Hewlett Packard 54200A - 50MHz - 2 Ch Digitizing	£1000
Hewlett Packard 54201A - 300MHz Digitizing	£1750
Hewlett Packard 54501A - 100MHz - Digitizing 4 channel	£1950
Hewlett Packard 54602A - 150MHz - 4 channel	£2000
Hewlett Packard 182C - 4 channel - 100 MHz	£350
Hitachi V650F - 60 MHz Dual Channel	£350
Hitachi VC6265 - 100 MHz Digital Storage (AS NEW) GPIB	£2250
Intron 2020 - 20 MHz Digital Storage (NEW)	£750
Kikusui COS 6100 - 100MHz, 5 Channel, 12 Trace	£475
Meguro - MSO 1270A - 20 MHz Digital Storage (NEW)	£750
Nicolet 3091 - LF D.S.O.	£1100
Panasonic VP5741A - 100 MHz D.S.O. with digital readout - waveform analysis - TV Signal Analysis Function - GPIB	£1995
Phillips 3211, 3217, 3240, 3243, 3244, 3261, 3262 (2ch + 4ch)	from £125
Phillips 3219 - 50MHz with analogue storage	£400
Phillips PM 3295A - 400MHz Dual Channel	£1750
Phillips PM 3295 - 350MHz Dual Channel	£1500
Phillips 3263 - 100MHz Dual Channel with Microprocessor Controlled Timing	£400
Phillips 3540 - Logic Scope (25MHz Scope & Logic Analyser)	£350
Tektronix 434 - 25MHz - 2 Channel Analogue Storage	£250
Tektronix 454 - 150MHz - 2 Channel	£400
Tektronix 468 - 100MHz - D.S.O.	£400
Tektronix 2213 - 60MHz Dual Channel	£750
Tektronix 2215 60MHz dual trace	£425
Tektronix 2235 - 100MHz-Dual trace	£450
Tektronix 2236 - 100MHz Dual Channel with Counter/Timer	£500
Tektronix 2335 Dual trace 100MHz (portable)	£750
Tektronix 2445 150 MHz - 4 Channel	£1250
Tektronix 2445A - 150MHz - 4 Channel	£1650
Tektronix 2465 - 350MHz - 4 channels	£2300
Tektronix 2225 - 50MHz dual ch	£450
Tektronix 455 - 50MHz Dual Channel	£350
Tektronix 464/466 - 100MHz An storage	from £350
Tektronix 465/465B - 100MHz dual ch	from £350
Tektronix 475/475A - 200MHz/250MHz Dual Channel	from £475
Tektronix 485 - 350MHz - 2 channel	£900
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch	from £300
Tektronix 7704 - 250MHz 4 ch	from £650
Tektronix 7904 - 500MHz	from £850
Tektronix 7934 500MHz with storage	from £1000
Tequipment D93 - 50MHz Dual Channel	£200
Tequipment DM63 - 20MHz - 4 Channel	£150

Other scopes available too

SPECIAL OFFER

HITACHI V212 - 20 MHz DUAL TRACE	£180
HITACHI V222 - 20 MHz DUAL TRACE - ALTERNATE MAGNIFY	£200

SPECTRUM ANALYSERS

Ando AC8211 - Spectrum Analyser 1.7GHz	£3000
Eaton/Alitech 757 - 10KHz - 22 GHz	£2750
Hewlett Packard 3580A - -5KHz-50KHz	£995
Hewlett Packard 3709B - Constellation Analyser with 15709A High Impedance Interface (As New)	£5750
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
HP 3582A - 25KHz Analyser, dual channel	£2500
Hewlett Packard 35801A - Spectrum Analyser Interface	£1000
Hewlett Packard 3582A - 40MHz Spectrum Analyser	£5000
Hewlett Packard 141T - 8552B + 8555A - (10MHz - 18GHz)	£1600
Hewlett Packard 3582A Dual Channel Dynamic Sig. Analyser	£7500
Hewlett Packard 8505A - Network Analyser 500KHz - 1300MHz	£3950
Hewlett Packard 8565A - 0.01-22GHz	£3750
Hewlett Packard 8591E - 10KHz-1.6GHz	£5000
Hewlett Packard 8754A - Network Analyser 4-1300MHz	£2750
Marconi 2370 - 110MHz	£995
Marconi 2371 - 30KHz - 200MHz	£1250
Meguro MSA 4901 - 1-300 GHz (AS NEW)	£1995
Meguro MSA 4912 - 1-1 GHz (AS NEW)	£3000
Polrad 641-1 - 10MHz - 18GHz	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz	£2500
Takeda Riken 4132 - 1.7GHz Spectrum Analyser	£3000
Tektronix 2710 9 KHz - 1.8 GHz	£4250
Tektronix 7L18 with 7603 mainframe (1.5-60GHz with external mixers)	£2000

MISCELLANEOUS

Adret 740A - 100KHz-1120MHz Synthesised Signal Generator	£2000
AVO RM215 - L2 - AC/DC Breakdown, Leakage - Ionisation Tester	£400
ANRITSU ME 462B DF3 Transmission Analyser	£3000
Danbridge JP30A - 30KV Insulation Tester	£1500
Anritsu MGS42A Pulse Pattern Generator	£1500
Dransatz 626 - AC/DC - Multifunction Analyser	£850
Dyanpert TP20 Intelliplace - Tape peel Tester - immaculate condition	£1750
BiP 331 - Frequency counter 160KHz	£700
Farnell AP70-30 Power Supply (0-70V/30A) Auto Ranging	£750
Farnell TSV 70 MxI Power Supply (70V-5A or 35V-10A)	£200
Flure 5100A - Calibrator	£3500
Flure 5101B - Calibrator with Tape Deck	£5000
Flure 5106B - Calibrator	£4500
Guidline 9152 - T12 Battery Standard Cell	£550
Heiden 1107 - 30V-10A Programmable Power Supply (IEEE)	£650
Hewlett Packard 331A - Distortion Analyser	£300
Hewlett Packard 333A - Distortion Analyser	£300
Hewlett Packard 3336C - Synthesised Signal Generator (10Hz-21MHz)	£1000
Hewlett Packard 3437A System Voltmeter	£350
Hewlett Packard 3435A Digital Voltmeter	£850
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser	£2250
Hewlett Packard 3776A - PCM Terminal Test Set	£POA
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen	£1500
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available)	£650
Hewlett Packard 334A - Distortion Analyser	£300
Hewlett Packard 339A - Distortion Measuring Set	£1500
Hewlett Packard 3455A 61/2 Digit M/Meter (Autocal)	£750
Hewlett Packard 3478A - Multimeter (5 1/2 Digit) + HP-1B	£550
Hewlett Packard 3776A - PCM Terminal Test Set	EP.O.A.
Hewlett Packard 3779A/3779C - Primary Multi Analyser	from £600
Hewlett Packard 4275A - LCR Meter (Multi-Frequency)	£395
Hewlett Packard 4338A - Milliohmeter (As New)	£2000

Hewlett Packard 4342A - 'Q' Meter	£995
Hewlett Packard 4952A - Protocol Analyser (with interfaces)	£2500
Hewlett Packard 4954A - Protocol Analyser	£2995
Hewlett Packard 4953A - Protocol Analyser	£2750
Hewlett Packard 432A - Power Meter (with 478A Sensor)	£275
Hewlett Packard 435A or B Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 4271B - L.C.R. Meter (Digital)	£900
Hewlett Packard 4278A - 1MHz, C-V Meter	£6500
Hewlett Packard 4548A - (TMS) Transmission Impairment M/Set	£2000
Hewlett Packard 4972A - Lan Protocol Analyser	£2000
Hewlett Packard 5420A Digital Signal Analyser	£350
Hewlett Packard 5335A - 200MHz High Performance Systems Counter	£600
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter	£250
Hewlett Packard 5163 - Waveform Recorder	£2250
Hewlett Packard 5238A Frequency Counter 100MHz	£250
Hewlett Packard 5370A - 100MHz Universal Timer/Counter	£450
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 6010/3000/005	£995
Hewlett Packard 6034 - 60V-10A System Power Supply	£1500
Hewlett Packard 6253A Power Supply 20V-3A Twin	£200
Hewlett Packard 6181C D.C. current source	£150
Hewlett Packard 6255A Power Supply 40V - 1.5A Twin	£220
Hewlett Packard 6266B Power Supply 40V-5A	£225
Hewlett Packard 6271B Power Supply 60V-3A	£1500
Hewlett Packard 6034A - 0-80V-10A System P.S.U.	£250
Hewlett Packard 7475A - 8 Pen Plotter	£450
Hewlett Packard 7550A - 8 Pen Plotter A3/A4	£450

HEWLETT PACKARD 6261B Power Supply 20v-50A £450 Discount for Quantities

Hewlett Packard 8015A - 50MHz Pulse Generator	£750
Hewlett Packard 8403A - Modulator	£500
Hewlett Packard 8405A - Vector Voltmeter	£500
Hewlett Packard 8165A - 50 MHz Programmable Signal Source	£1650
Hewlett Packard 8150B - Sweep Oscillator Mainframe (various Plug-ins available) extra	£2650
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011)	£1250
Hewlett Packard 83554A - Wave Source Module 25 to 40 GHz	£1100
Hewlett Packard 8620C Sweep oscillator mainframe	£3500
Hewlett Packard 8684A 5.4GHz to 12.5GHz Sig-Gen	£2750
Hewlett Packard 8620C Sweep oscillator mainframe	from £250
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 8903A - Audio Analyser (20Hz - 100KHz)	£2600
Hewlett Packard 8958A - Cellular Radio Interface	£4000
Hewlett Packard 8901A - Modulator Analyser	£3400
Hewlett Packard P382A Variable Attenuator	£250
Hewlett Packard 1630D - Logic Analyser (43 Channels)	£650
Hewlett Packard 16500A - Fitted with 16510A/16515A/16530A/16531A - Logic Analyser	£4000
Hewlett Packard 11729B - Carrier Noise Test Set	£2000
Krohn-Hite 2200 Lin/Log Sweep Generator	£995
Krohn-Hite 4024A Oscillator	£250
Krohn-Hite 6500 Phase Meter	£250
Marconi 2018 - 80KHz - 520MHz Synthesised AM/FM Signal Generator	£850
Marconi 2019 - 80KHz - 1040MHz Synthesised Sig. Gen	£1850
Marconi 2019A - 80KHz - 1040MHz - Synthesised Signal Generator	£1950
Marconi 2022A - 10KHz-1GHz AM/FM Signal Generator	£2000
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2610 - True RMS Voltmeter	£350
Marconi 2850BS - Digital Transmission Analyser (As New)	£2250
Marconi 2871 Data Comms Analyser	£2000
Phillips PM 167 10MHz function gen.	£400
Phillips 5190 L.F. Synthesiser (G.P.I.B.)	£800
Phillips PM5515 - TV Pattern Generator	£350
Phillips PM5567 - Vectorscope	£500
Phillips PM6552 - 1.5GHz Programmable High Resolution Timer/Counter	£900
Phillips PM6570 - 120MHz High Resolution Universal Counter	£350
Phillips PM6573 - 120MHz High Resolution Universal Counter	£350
Prima 4000 - 6 1/2 Digit Multimeter (NEW)	£450
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9245S Programmable PSU 25V-10A	£400
Racal Dana 3100 40-130MHz synthesiser	£750
Racal Dana 1992 - 1.3GHz Frequency Counter	£800
Racal Dana 9081 Synth sig. gen. 520MHz	£550
Racal Dana 9084 Synth sig. gen. 104MHz	£450
Racal Dana 9303 R/F Level Meter & Head	£950
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9302A R/F millivoltmeter (new version)	£375
Racal Dana 9082 Synthesised am/fm sig gen (520MHz)	£500
Racal 9085 Low Distortion Oscillator	£POA
Racal 9301A - True RMS R/F Millivoltmeter	£300
Racal 9921 - 3GHz Frequency Counter	£450
Rohde & Schwarz AMF 2 - TV Demodulator	£1250
Rohde & Schwarz LFM 2 - 60 Mhz Group Delay Sweep Gen	£1600
Rohde & Schwarz SMFP2 - 1GHz Radio Comms T/Set	£2500
Rohde & Schwarz UPSF 2 - Video Noise Meter	£1400
Rohde & Schwarz URE - RMS Voltmeter (10Hz-25MHz)	£500
Rohde & Schwarz - Scud Radio Code Test Set	£500
Rohde & Schwarz SUF 2 Noise Generator	£300
Rohde & Schwarz UPGS - Psophometer	£150
Schaffner NSG 203A Line Voltage Variation Simulator	£1250
Schaffner NSG 222A Interference Simulator	£850
Schaffner NSG 223 Interference Simulator	£850
Schlumberger 4015 - 1GHz Radio Comms Test Set	£6000
Schlumberger 4923 Radio Code Test Set	£1500
Schlumberger 4031 - 1GHz Radio Comms Test Set	£2000
Schlumberger 2720 1250 MHz Frequency Counter	£2500
Solartron 1250 - Freq. Response Analyser	£2500
Stanford Research DS 340 - 15 MHz Synthesized Function (NEW) and arbitrary waveform generator	£1200
Syatron Donner 6030 - Microwave Frequency Counter (26.5 GHz)	£2750
Tequipment GT71 Curve Tracer	£250
Tektronix TMS503 - AFG 5101 Arbitrary Function Gen.	£1750
Tektronix 1240 Logic Analyser	£750
Tektronix 651 HR Monitor	£POA
Tektronix DAS9100 - Series Logic Analyser	£500
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PG508, FG504, FG503, TG501, TR503 + many more	£POA
Tektronix 577 Curve Tracer	£1150
Tektronix AM503 + TM501 + P6302 - Current Probe Amplifier	£395
Tektronix PG506 - TG501 - SG503 + TM503 - Oscilloscope Calibrator	£1995
Tektronix AA501 & TM 5006 M/P - Programmable Distortion Analyser	£2500
Tektronix 577 - Curve Tracer	£1150
Time 9811 Programmable Resistance	£600
Time 9814 Voltage Calibrator	£750
Toellner 7720 - Programmable 10 MHz Function Gen (AS NEW)	£700
Valhalla Scientific - 272A Programmable Resistance Standard	£POA
Wayne Kerr 3245 - Precision Inductance Analyser	£3250
Wayne Kerr 4210 - LCR Meter	£600
Wayne Kerr 4225 - LCR Bridge	£600
Wayne Kerr 6425 - Precision Component Analyser	£275
Wayne Kerr 8905 - Precision LCR Meter	£850
Wavetek 172B Programmable Sig Source (0.001Hz-13MHz)	EP.O.A.
Wavetek 184 - Sweep Generator - 5MHz	£250
Wavetek 3010 - 1-1GHz Signal Generator	£1250
Wiltron 6620S - Programmable Sweep Generator (3.6 - 6.5GMZ)	£650

**MANY MORE ITEMS AVAILABLE -
SEND LARGE S.A.E. FOR LIST OF EQUIPMENT
ALL EQUIPMENT IS USED -
WITH 30 DAYS GUARANTEE.
PLEASE CHECK FOR AVAILABILITY BEFORE
ORDERING - CARRIAGE & VAT TO BE ADDED
TO ALL GOODS**

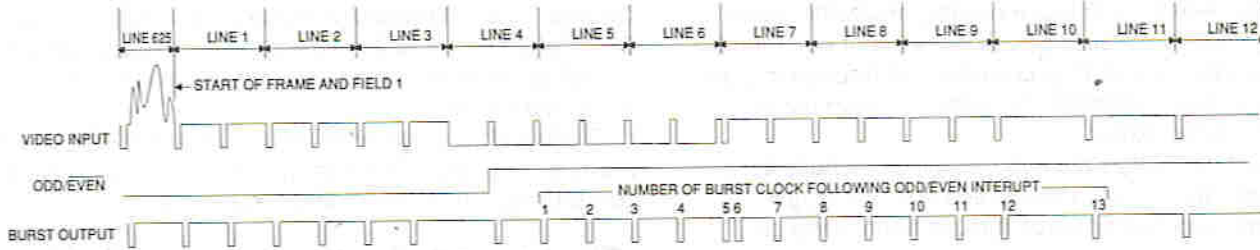


Figure 4: the burst count at the start of field 1 following Odd/Even frame interrupt

The user-selected line number is converted into a negative number, and the lower 8 bits are loaded into the internal (8-bit) timer. The internal timer increases its count on every colour burst signal. When it overflows it causes an interrupt. This is used to increment an internal register which keeps count of the upper 8 bits of the line counter. When the 16 bit line counter reaches 0, the required line has been reached, and the trigger output is generated.

Figure 4 shows a timing diagram of the signals produced by the EL4581. Note that the equalising pulses which occur during the vertical frame interval are detected by the chip and cause colour burst signals to be generated at twice the normal frequency during the vertical frame interval.

The frame interrupt occurs half way through line 4 of field 1, and is clocked out by the colour burst signal produced by the equalising pulse in the middle of line 4. To avoid problems with this late signal then the first line which may be selected as a trigger is line 10 of the field. Note (from figure 4) that to trigger on line 10 of the field requires the PIC to tri-state the trigger output (RA3) during line 9, and that this is the twelfth colour burst pulse of the signal following the odd/even frame change. Therefore a count of 2 is added internally to the user-selected count.

During the entire frame, there will be another field synchronisation pulse between field 1 and field 2. During this field the colour burst signals will again be at double the correct rate. To correct for this the software in the PIC adds 2 to the count for each line during the field synchronisation pulse, and adds a total of seven extra pulses to the count for any line in the second field of the frame.

The frame interrupt routine causes the negative value for the line counter to be loaded into the internal counter, and into the upper 8-bit counter register. This is achieved within 20µs of the frame interrupt - plenty of time for the first colour burst signal following the frame interrupt. The frame interrupt routine also sets a flag which is used by the main loop to scan the push buttons.

The push button scanning routine checks to see if the push button is pressed. If so the count is moved up or down appropriately. If the button remains pressed then no action is taken until approximately 250ms passes. Then the count is changed by five on each frame interrupt, while the button remains pressed.

On each change of the count the following actions are undertaken :

The count is checked to make sure that it is in range (from 10 to 620).

The count is converted into decimal, into a 3-digit BCD form to be used by the multiplexing routine for the display.

The count is converted into the correct negative number for loading into the counter registers. This involves checking the range of the count, adding on the appropriate offset to compensate for the equalising pulses, and then negating the count. This result is stored for immediate use by the frame interrupt routine.

Finally when the counter overflows to 0, the trigger output is placed in a high impedance state for 60µs.

The code

The hex code for the program can be manually entered into a text file. As the file is checksummed, errors should be easy to find. Save the file with the name "LINETRIG.HEX"; most programmers accept this hex file format. The PIC should be programmed with the Watchdog disabled, and Power Up timer enabled. The XT fuse type should be selected. Alternatively, ready-programmed 16C84 devices are available (see the end of the article).

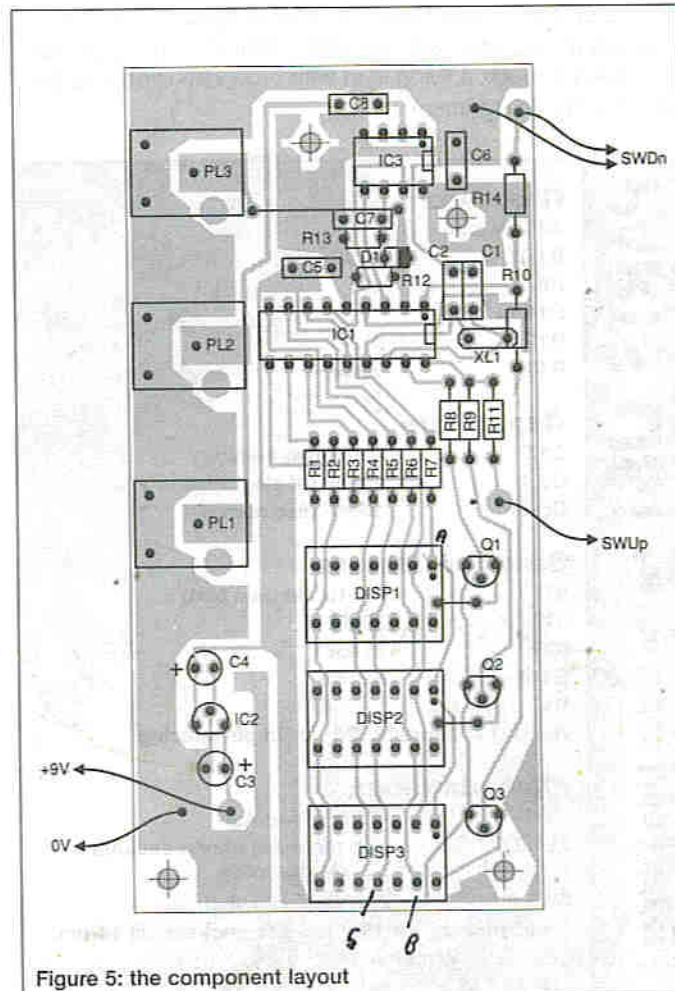


Figure 5: the component layout



Construction and testing

The circuit is built on a single small pcb. The overlay is shown in figure 5. Note that a ceramic resonator should be used for the PIC because it uses the smallest board profile. (they are also cheaper than crystals). The displays may be any 0.3 in, seven-segment, CA types, as they nearly all have the correct pinout.

The phono sockets are pcb-mounting components. There are three in total: video in and out, and trigger out. The power supply is provided through flexible wire on Veropins.

The board has three wire links which should be fitted first. Horizontally mounted resistors should be fitted next. The displays and both diodes should be mounted in sockets. Finish construction with the capacitors and phono sockets. It may be worthwhile connecting a diode in series with the input positive power supply pin to protect against wrong polarity connection.

Initially do not fit the ics or the displays. Apply a power supply of 9V or greater, and check that the power pins of IC1 and IC3 are at +5V. If you wish to check the operation of the displays then insert them now and use short wire links on the socket of IC1 to short each digit driver transistor to ground and then each segment.

Finally, power down, fit ics and displays, and then power up again. The display should show "010" and will be flashing if there is no video signal. Connect a video signal and then check the operation of the push buttons. Connect the trigger output to an oscilloscope and check that the expected line is correctly displayed (trigger at the start of field 2 - line 310 onwards - to see the even field synchronisation pulse).

The prototype was fitted into a small plastic box. The displays are covered with red filter material, and the power is applied through a flying lead with crocodile clips to allow use in a lab environment.

Obtaining components

A pre-programmed 16C84 is available from Forest Electronic Developments (10 Holmhurst Avenue, Christchurch, Dorset, BH23 5PQ) for £12.00. Please enclose a cheque payable to "Forest Electronic Developments", and a stamped, self addressed envelope.

The EL4581 is available from Maplin, as are the PCB mounted phono sockets used in the prototype. All other components are standard and can be obtained from most suppliers.

The hex code for the Video Line Trigger

```

:02000000528D1
:100008003C29A8208316F830810010308500013083
:10001800860083125A21B4200A21D0200830850096
:10002800FF30860006308E00B0308B000A30970013
:100038001016901836282F208F0B1D282521A50A69
:10004800A40BA503A508031D1D28101A1D28901E22
:100058001D286D211D2803309A009A0B31280800AD
:10006800133030280608A3000508A2009010831654
:10007800073085048312FF3086004C208B178316C7
:10008800F8308505831222088500230886001D287C
:10009800851C5528051D6928F33090050A309700FE
:1000A80008008B130130101D5F28970803195E287C
:1000B800970308000530622010157D289A008D0AE4
:1000C8008C0F8D039A0B632808008B130130901D49
:1000D80071289708031D5C280530742090157D2829
:1000E8009A008C03FF300C0203198D039A0B7528B4
:1000F800080090161012A401EA30A500B4200A21C5
:10010800D020080010101A088002840A03189028CA
:1001180001308002031C10141B088002031C1014F9
:100128000310101803148403080010101A0880071D
:10013800840A031CA32801308007031810141B0825
:10014800800703181014942822308C000E308D007C
:100158000D08840080018D0A8C0BAC288D010800E5
:100168008D08031DBE280C08093C031C08000A3032
:100178008C00080071309A0002309B000C089C002B
:100188000D089D001C30840086200318080071307B
:100198008C0002308D00080037309C0001309D00033
:1001A8003D309E0001309F000730A000EA20023059
:1001B8009C009D011C30840099201C089A001D0891
:1001C8009B00950196011530840086280C089A003A
:1001D8000D089B001E3084008620031801291C305E
:1001E80084008620031C08009C099C0A9D01992014
:1001F8001C089A001D089B00080020308400A101FB
:10020800992020089A0021089B0008000C089C00EF
:100218000D089D009B0164309A001A2191000A3054
:100228009A001A2192001C0893000800FF309E00D3
:100238001C30840086209E0A031C1E2999201E0853
:1002480008000730850403148E0D0E080739073C93
:10025800031D2F290E1011088E1C12080E1D1308DD
:100268008A239A001A0D86000E08F83885050800BA
:100278009800030E990083128B184F290B194529F2
:1002880055290B11940F552985158316851534208A
:100298008511831255298B101508810016089400C2
:1002A8009014190E8300980E180E09008901682110
:1002B8008C00890A68218D000D0A031D08000A3088
:1002C8008C0000308D00080083160814831208087B
:1002D800080089010C087621890A0D087621101674
:1002E8009012080088008B13831608155530890072
:1002F800AA308900881488187F2983128B17080070
:10070000C034F934A434B034993492348234F83497
:10071000803490349A0003308A001A08803E8200A8
:00000001FF
    
```

PARTS LIST for the Video Line Trigger

Resistors

All 1 percent, 0.25 watt

R1-7	300R
R8-10	10k
R11,14	1k
R12	4k7
R13	680k

Capacitors

C1,2	22pF disc ceramic
C3,4	10uF 10V electrolytic radial
C5-8	100nF disc ceramic

Semiconductors

IC1	PIC16C84 (See text)
IC2	78L05
IC3	EL4581 <i>468 MS 389 K</i>
Q1-3	BC559
D1	1N4148
Disp1-3	7-segment, CA, 0.3in pin spacing

Miscellaneous

XL1	4MHz resonator
PL1,2,3	pcb mounted phono sockets (eg Maplin HF99)
SW1,2	pushbutton switch
1 x ic sockets, dil 18-pin, 3 x ic sockets, dil 14-pin; pcb; case; Veropins.	

RS 191-336

LM1881N
CPC 2-25


AN5521	1.35	STK73410/2	5.95	TEA2026C	4.50
AN5732	1.40	STK73605	4.50	TEA5170	1.40
AN6327	9.85	STR441	18.99	TJA2000-4	4.25
AN6677	8.50	STR451	29.99	U884B	2.35
BA5114	1.55	STR3125	5.50	UAA1008	3.00
BA6218	1.85	STR4211	5.50	UPC1178	1.05
BA6219	1.20	STR4090	11.15	UPC1182H	5.15
HA11423	1.65	STR20005	5.00	UPC1278H	2.20
HA13119	2.50	STR40090	4.00	UPC1420	4.50
KA6210	4.99	STR50103A	3.85	UPD1937	3.00
LA3220	0.60	STR54041	3.75	25A814	0.71
LA4183	1.35	STR58041	3.75	25A839	1.40
LA4445	1.90	STR80001	6.00	25A1052	1.00
LA4495	1.40	STR1706	4.75		
LA4588	2.55	STRD1806	4.50		
LA7835	2.35	STRD6008	10.00		
LB1415	2.25	TA227	1.85	ELECTROLYTIC CAPACITORS	
LM301	0.25	TA7271	2.50	250V Working	
LM317T	1.50	TA7280	2.25	1UF (5/pack)	1.00
M4918BI	4.75	TA7281	2.20	4.7UF (5/pack)	1.50
M498BI	6.75	TA7698	5.00	10UF (5/pack)	1.70
MS1393	5.95	TAB200	3.50	22UF (each)	0.40
MS8655	3.30	TAB210	3.00	33UF (each)	0.56
MB3730	1.70	TAB214	3.00	47UF (each)	0.65
MB3756	8.00	TAB215	3.00	100UF (each)	1.28
STK078	6.00	TAB205	3.95	400V Working	
STK435	4.00	TAB659	13.00	1UF (5/pack)	1.10
STK461	10.50	TA75339	**	4.7UF (5/pack)	1.50
STK2250	7.45	TDA3500	4.99	10UF (each)	0.70
STK4121/2	7.00	TDA3645	8.00	22UF (each)	0.75
STK4141/2	5.50	TDA3650	8.99	4.7UF (each)	1.40
STK4142/2	6.50	TDA3850	18.99		
STK4162/2	6.25	TDA4400	1.75	IC-DATABASE ON FLOPPY DISK	
STK4171/2	8.10	TDA4500	3.50	The most important technical data & functions of 48000 semi (20k IC's + 25k Transistors / Trank on floppy disk only	£14.99+ p+p & Vat
STK4191/2	8.50	TDA4505A	4.10	TEST CD2	
STK4352	6.20	TDA4505B	4.10	This CD can be used to control CD player - 71 different test signals - Planning time 30 min - Sinus/Rectangle/white & pink noise - Complete with instruction book	£12.99 each
STK4372	5.65	TDA4505M	5.25	TEST CD3	
STK4803	7.05	TDA4505K	6.15	With this CD a technician can control & adjust the electrical data of CD players in a minimum of time will improve the repair results in adjusting cd player after changing the laser unit.	£20.99 each
STK4843	7.05	TDA4680	4.50		
STK5315	5.85	TDA4950	1.40		
STK5332	1.80	TDA5660P	2.50		
STK5338	3.25	TDA7072	3.99		
STK5361	4.15	TDA8370	14.00		
STK5372	2.85	TDA8405	8.00		
STK5372H	4.15	TDA8732	5.95		
STK5412	3.75	TEA2018A	1.50		
STK5471	3.85				
STK6732	14.00				
STK7226	7.50				
STK7308	4.05				
STK7308	4.05				
STK7348	4.05				
STK7356	4.75				
STK7004	6.50				
STK73410	5.15				

Please phone us for the types not listed. Please add 60p post & packing and lines add 17.5% VAT to the total. Callers by appointment only.

J.J. COMPONENTS
63 THE CHASE, EDGEWARE, MIDDIX, HA8 5DN, ENGLAND
Hotlines No 081 381 1700/081 952 4641
Free Fax order Line only: 0800 318 498
General Fax 081 381 1700

PIC16C84 and BIM Transceiver Development Platform in one !

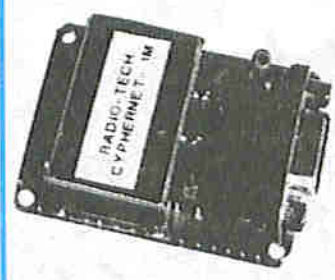A hardware development platform for exploring high speed, PC-PC, half duplex, two way Radio Data Communications !



Radio-Tech Limited CYPHERNET -1M
Measures only: 39 x 59mm x 17mm

- INCLUDES:-**
- 10MHz PIC16C84
 - BIM-418-F Transceiver
 - 9-Pin D-Type Connector
 - 2-Wire RS232 Interface
 - Transmitter On LED
 - Receiver On LED
 - 1/4 Wave Wire Antenna

Supplied with a free firmware driver the Cyphernet transceiver will permit you to link PC's and transfer data using Windows terminal mode. Only 79.95 each

Combined power and RS232 data cable. Only 6.95 each.



Dedicated PIC16C84 programming tool for re-programming the internal control firmware, permitting the user to explore and develop applications of their own. Only £ 94.95 each.

Unit featured above is Licence Exempt to MPT1340 within the UK. Export Versions on 433.92MHz to ETS300-220 available with 1 and 10mW output power. Prices exclude VAT and Carriage.

Radio - Tech Limited, Overbridge House, Weald Hall Lane
Thornwood Common, Epping, Essex CM16 6NB.
Sales +44 (0) 1992 57 6107 (4-lines) Fax +44 (0) 1992 56 1994
<http://www.radio-tech.co.uk> E-mail radtec@radtec.demon.co.uk

NEW & HARDLY USED TEST EQUIPMENT

DUAL TRACE 20MHz OSCILLOSCOPE MODEL HC3502
5MV - 20V/DIV, 0.2µ Secs to 0.55µSec/Div, X - Y, X5 Magnifier, TV Sync etc.
Used £180 Un-used £220

KENWOOD FL10A WOW/FLUTTER METER
0.003% - 10% Frequency 5KHZ/3.15KHZ, RMS/AVERAGE/PEAK, Weighted Filters, Digital Display of rms; 4 digit Frequency Counter (0.01KHZ-9.9999KHZ-55KHZ)
Used £400 Un-used £500

PANASONIC VP8177A FM/AM SIGNAL GENERATOR
100KHZ-110MHz, Output -19dB to 99dB; FM 0.100KHZ, AM 0-60%; 32 PreSet Memory; Digital Display Frequency & Output
Used £450 Un-used £750

POWER SUPPLY MODEL HSP3010
0-30 Volts, 0-10Amps, Current Limiting, 2 metres
Used £235 Un-used £275

PANASONIC VP7037A STEREO SIGNAL GENERATOR
Generates Broadcast FM - RDS/RRI PreSet Memory, GP8
Used £400 Un-used £700

GOODWILL GFC 8010G FREQUENCY COUNTER
Range 1Hz-120MHz, 8 Digit Display, 15mVrms Sensitivity
Un-used £95

ANALOGUE MULTIMETER Model HC260TR
AC/DC Volts, DC Current, 10 Amps, 17 Ranges, Continuity Buzzer, Transistor Tester
Un-used £15

GOODWILL GVT 427 DUAL CHANNEL AC MILLIVOLTMETER
10µV - 300V in 12 ranges; Frequency 10Hz-1MHz
Used £100 Un-used £125

GOODWILL GAS 8086 AUDIO GENERATOR
Sine/Square 10Hz-1MHz in 5 ranges; 0.1% Low Distortion; 5 steps Output Attenuator.
Used £60 Un-used £80

New Free 1997 Catalogue !

Fourth International Edition

Radio - Tech Limited

Helping Mankind With Affordable Wire-Free Radio Data Communications Solutions!

Monitoring, EPOS, Agriculture, Irrigation, Environmental

<http://www.radio-tech.co.uk>

Tel +44 (0) 1992 576107 (4-lines) Fax +44 (0) 1992 561994
Overbridge House, Weald Hall Lane, Thornwood, Epping.

- EPOS
- Telemetry
- Security
- Metering
- Spread
- Spectrum
- Frequency
- Agile
- Modems
- Antenna
- Dev. Tools
- EMC

To Request a Copy of the Radio - Tech, Fourth Edition Radio Data Module Catalogue Contact:

Overbridge House, Weald Hall Lane
Thornwood Common, Epping, Essex CM16 6NB.
Central Office +44 (0) 1992 57 6107 (4-lines)
Fax +44 (0) 1992 56 1994
Technical Support + 44 (0) 1992 57 6114

E-Mail radtec@radtec.demon.co.uk


STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 01734 268041 Fax: 01734 351696 Callers Welcome 9am - 5.30pm MON-FRI

High Impedance Multimeter Amplifier and AF/RF Probe

An inexpensive multimeter accessory to give you more accuracy on high impedance and signal measurements. By Raymond Haigh.

This simple and inexpensive unit will greatly enhance the performance of moving-coil multimeters by permitting the measurement of low DC and signal voltages with a minimum of disturbance to the circuit under test.

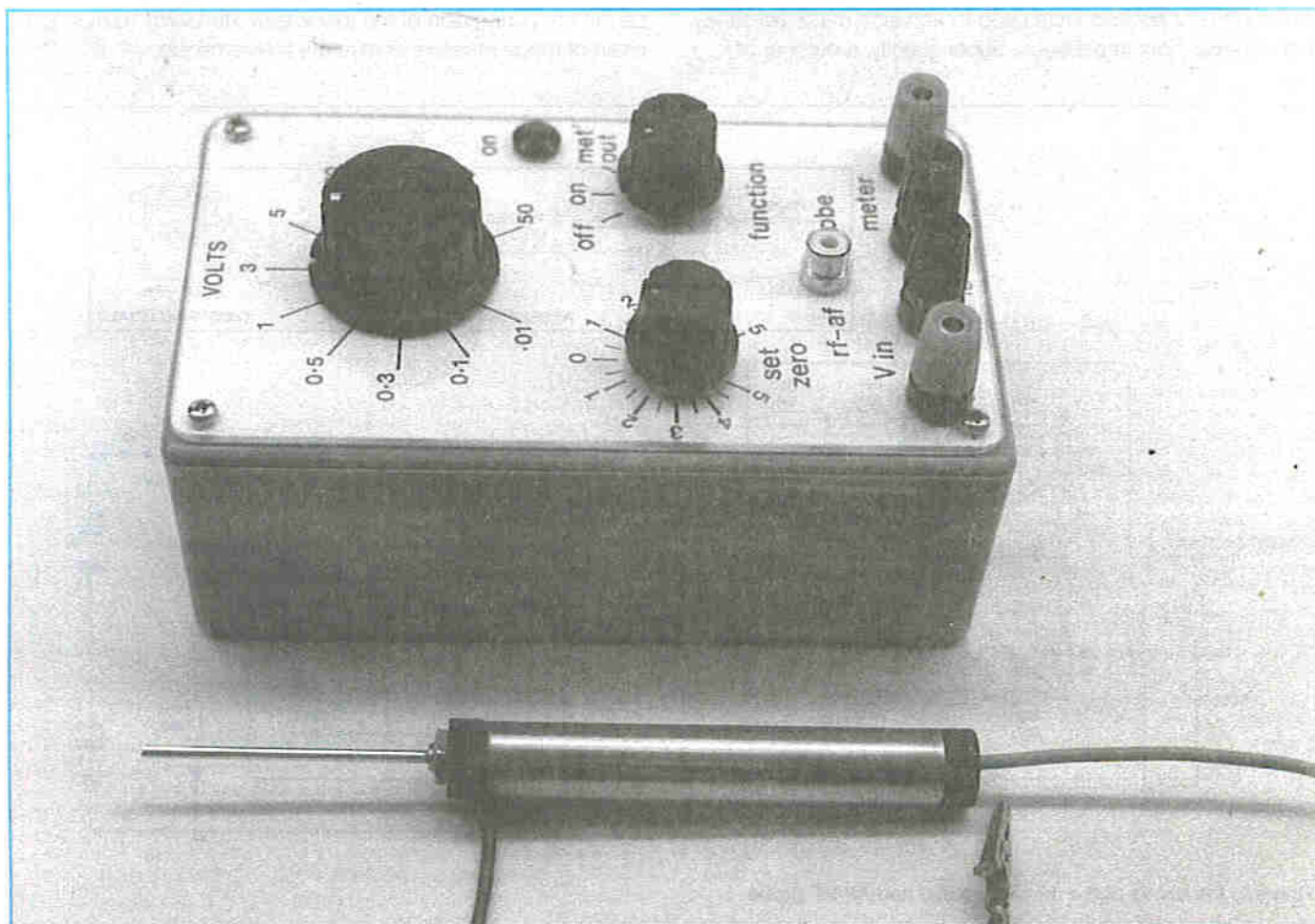Many constructors rely on moving-coil multimeters to check voltage levels in equipment under development or repair. However, even the best meters present a comparatively low resistance to the circuit under test, especially when small DC voltages are being measured, and this can cause inaccuracies.



The situation is even worse when a meter of this kind is used to measure AC voltages. The impedance on these ranges is even lower, and sensitivity falls off rapidly above a few hundred Hertz.


Warning: Mains project - constructors without experience of safe mains handling should seek the assistance of someone more experienced.

Digital multimeters present a much higher impedance on both AC and DC ranges, and low voltage readings taken with these instruments can be relied upon. Again, however, the accurate measurement of AC voltages is restricted to the lower audio frequencies, and most manufacturers indicate reliable AC readings only within a frequency range of 50 to 500Hz.

The inexpensive unit described here will greatly increase the sensitivity of a moving-coil multimeter, and give it an input resistance of 10 megohms when DC voltages are being checked, even on the lowest (0.01V or 10mV) range. A simple probe enables low AC voltages to be measured, from 20Hz to around 200MHz. This last facility can be particularly useful as a signal tracing aid. Voltage ranges have been chosen to accommodate the scale calibrations of most moving-coil multimeters. Constructors who prefer stand-alone equipment could install the amplifier unit along with its own moving-coil meter into a larger case.

The circuit

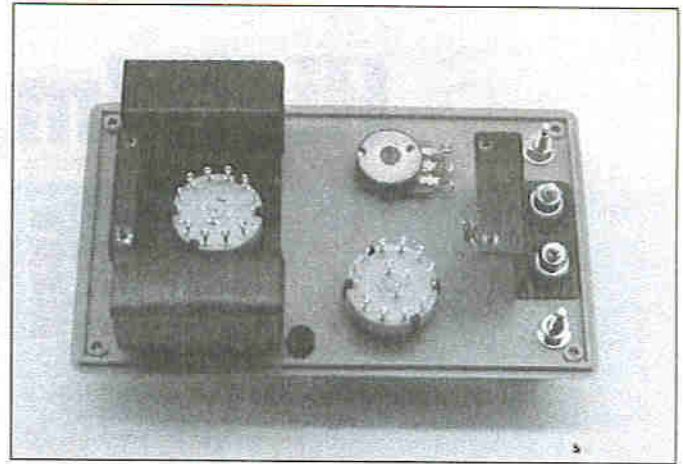No originality is claimed for the basic design, which has been around in one form or another since the invention of the triode valve. With the development of the transistor, discrete semiconductor devices were used to enhance meter sensitivity and increase input impedance. Subsequently, a number of



meter amplifier designs based on the ubiquitous 741 op-amp were published. These represented an improvement on many of the circuits incorporating bipolar transistors, but the one megohm input resistance of the 741 meant that performance still fell short of earlier laboratory instruments. It was the introduction of the field-effect transistor (fet) that made possible the achievement, with solid-state devices, of standards of performance formerly associated only with valves. The incorporation of fets into op-amps, and the availability of close-tolerance resistors at low cost, has since made the construction of high-performance meter amplifiers a comparatively simple and inexpensive matter.

The meter amplifier

The unit is designed around the widely available CA3140E fet-input op-amp. This device has an input resistance of 1T5 ohms (yes - 1.5 million, million ohms), more than high enough to permit the connection of the (once fairly standard) 10 megohm chain of range resistors across the test terminals.

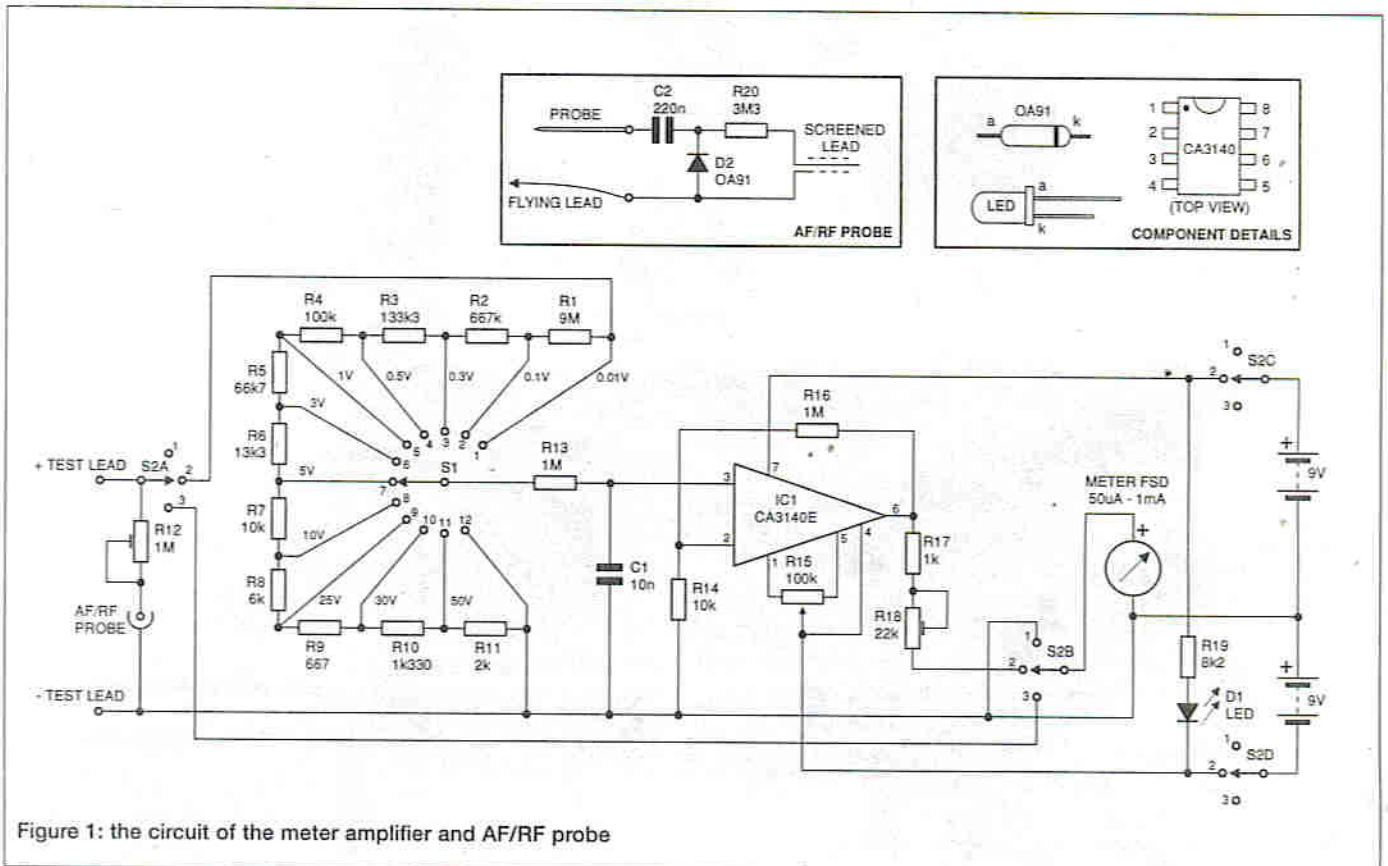


Figure 1: the circuit of the meter amplifier and AF/RF probe

The full circuit of the unit is given in figure 1, where the CA3140E op-amp is connected in the non-inverting mode with feedback resistors, R14 and R16, setting the gain of device at x 100. An input of 10mV will, therefore, produce an output of 1V. Potentiometer R15 is connected to the amplifier's offset-nulling circuitry, and functions as a set-zero control for the meter. R17, and pre-set potentiometer R18, set the meter to read 1V FSD. The non-inverting input of the op-amp (pin 3) is connected by range switch, S1, to the appropriate point on the potential divider chain formed by R1 to R11. The resistor values have been chosen to accommodate classic British multimeters with 0-10 and 0-30 ranges (the AVO meters, for example), and imported instruments with scales calibrated in multiples of 0-10, 0-25, and 0-50. The full chain of resistors is presented to the circuit under test, and the input resistance of the unit is, therefore, 10 megohms on all ranges.

R13 and C1 filter the input to the op-amp and ensure the stability of the circuit. The value of R13 may, at first sight, seem a little high, but it has a negligible effect on DC voltage levels because of the extremely high input resistance of the device. If, despite this measure, random movements of the meter pointer are encountered (no problems of this kind have been displayed by several prototypes), fit 100nF ceramic capacitors close to pins 4 and 7 of the op-amp in order to decouple the supply lines.

When the amplifier unit is connected to the workshop multimeter, it is sometimes necessary to switch the meter directly into the circuit under test in order to measure current and resistance, and S2a and S2b facilitate this. Always remember to set the multimeter to an appropriate range before switching it through, or damage may result. The unit is powered by two PP3 batteries, connected into circuit by S2c and S2d. Equipment of this kind is often inadvertently left switched on. The low current led, D1, gives a visual indication that the amplifier is drawing current, and helps to prevent this.

The AF/RF probe

The AF/RF probe could hardly be simpler. It comprises a DC blocking capacitor, C2, which couples the voltage being measured to rectifier diode D2. Resistor R20 isolates the probe tip from the connecting cable and, together with pre-set resistor R12, sets the probe output to a true RMS value.

The diode has to be connected shunt fashion across the circuit under test. If it were to be series connected the load resistance of 14 megohms or so would greatly exceed its own reverse resistance, and the rectifying action would be disastrously impaired. The arrangement is, of course, the same as the DC restorer circuit used in TV receivers to shift the level of the vision signal, and a little less than twice the peak value of the applied AC voltage appears across the diode. More is said about the implications of this later.


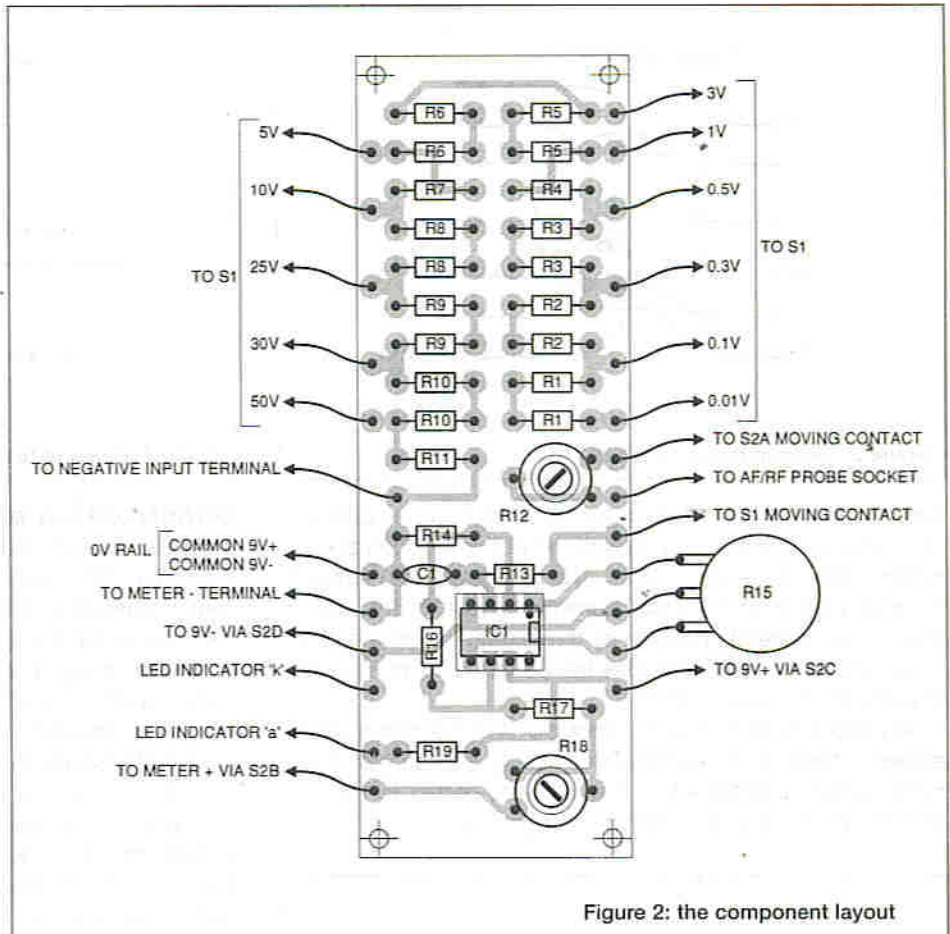


Figure 2: the component layout

Constructing the amplifier

Most of the components for the meter amplifier are mounted on a small pcb. Details of the component layout and the off-board wiring are shown in figure 2. The switch connections are given in figures 3 and 4. The use of a holder for the ic facilitates substitution-checking of the device, and Vero pins, inserted at the lead-out points, simplify the task of off-board wiring. Provision is made on the pcb for the recommended chain of close-tolerance resistors (see the Parts List), but it should be possible to adapt the layout, and use the land areas, for other resistor combinations in order to produce a different set of voltage ranges, should this be desired. Two photographs show the switches, terminals, battery holders

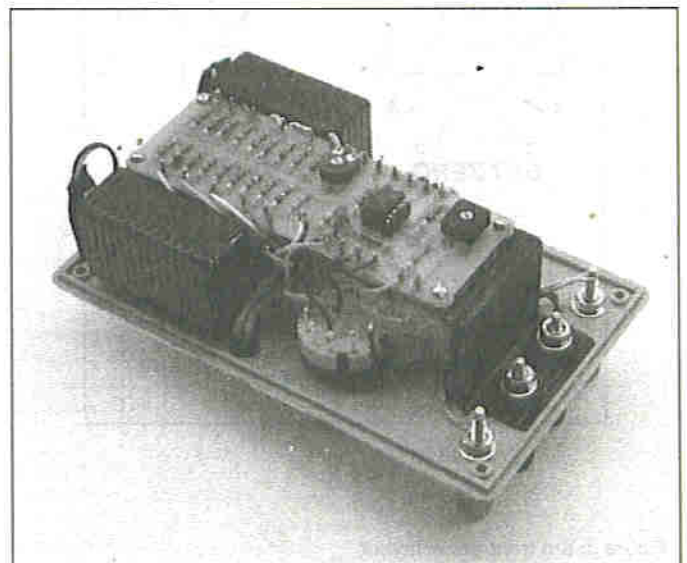

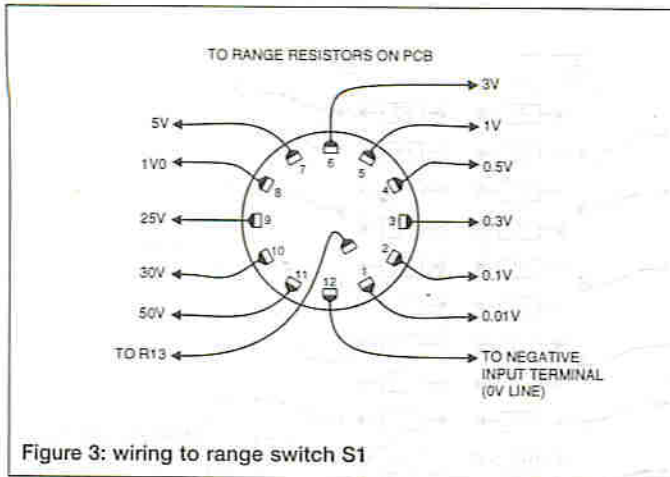


Figure 3: wiring to range switch S1

and pcb mounting brackets mounted on the lid of a plastic box, and the completed unit, with the pcb in position and wired to the other components. The brackets which support the pcb are formed from thin aluminium sheet. The smaller bracket is secured in position by the negative terminals. The larger assembly, which includes the battery holders, is held in place by the range switch.

A suggested layout for the front panel of the instrument is shown in figure 6. The original was simply marked out on white card and protected by a small piece of thin acrylic sheet of the kind sold for DIY double-glazing.

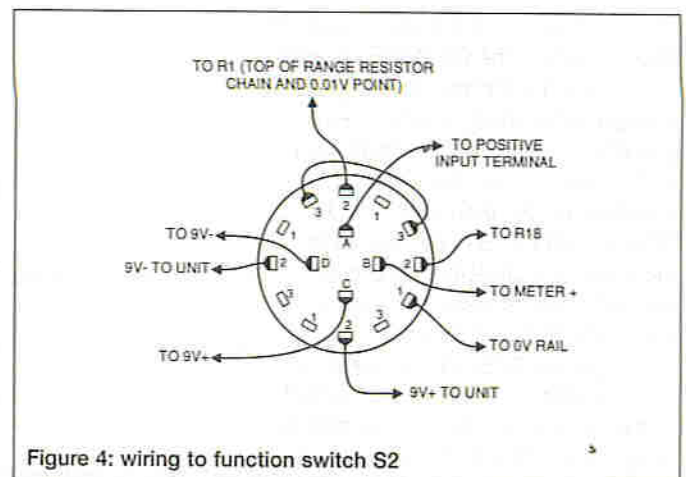


Figure 4: wiring to function switch S2

Construction of the probe

A section through the probe unit is given in figure 6. The case is formed from a short length of brass tubing (copper central heating piping would do just as well), and some scrap plastic terminals which are a tight push fit into the tube ends. Most constructors will have something suitable for the end pieces in their spares boxes but, if all else fails, they can be made from hard, dry wood. If wood is used, it is a good idea to insulate the probe tip where it passes through the plug.

Keep the leads of capacitor C2, diode D2 and resistor R20 as short as possible. These components are self supporting: just soldered together, to the probe tip, and to the thin strip of brass which connects the probe to the 0V rail via the cable screen. It is a wise precaution to use a small crocodile clip as a heat shunt when soldering the diode into circuit after its leads have been cropped in this way. The connecting cable is retained by the brass strip, which is held in place by sandwiching it between the probe tube and the end plug. Terminate the flying test lead with a small crocodile clip, and solder it to the projecting end of the brass strip. Screened audio cable and a phono plug can be used to connect the probe to the amplifier unit. See the photographs for the show the completed probe.

Components

No difficulty should be encountered in obtaining any of the components. Low cost, close-tolerance resistors, in a wide range of values, are retailed by Maplin. (Some suppliers stock a more restricted range and they may not be able to supply some of the values quoted in the Parts List). Lower tolerance resistors can, of course, be used if a reduced standard of accuracy is acceptable.

Inexpensive, plastic-cased, Lorlin rotary switches are one type that is suitable for S1 and S2, and low-current 2mA leds are available from Maplin. If a standard led is fitted, the value of R19 should be reduced to 1k5 (the current drawn by the indicator will then be of the order of 10mA, which exceeds the 8mA drawn by the meter amplifier). Brass tube and strip, in a wide range of sizes, is available from most model shops. Constructors who would prefer to combine meter and amplifier in a stand-alone unit will require a moving coil meter with a full-scale deflection of between 50uA and 1mA. A larger case will, of course, be also required.

Setting up and testing

Check the pcb for poor soldered joints and bridged copper tracks, and check the off-board wiring and connections. Check the orientation of the ic and diodes and, if

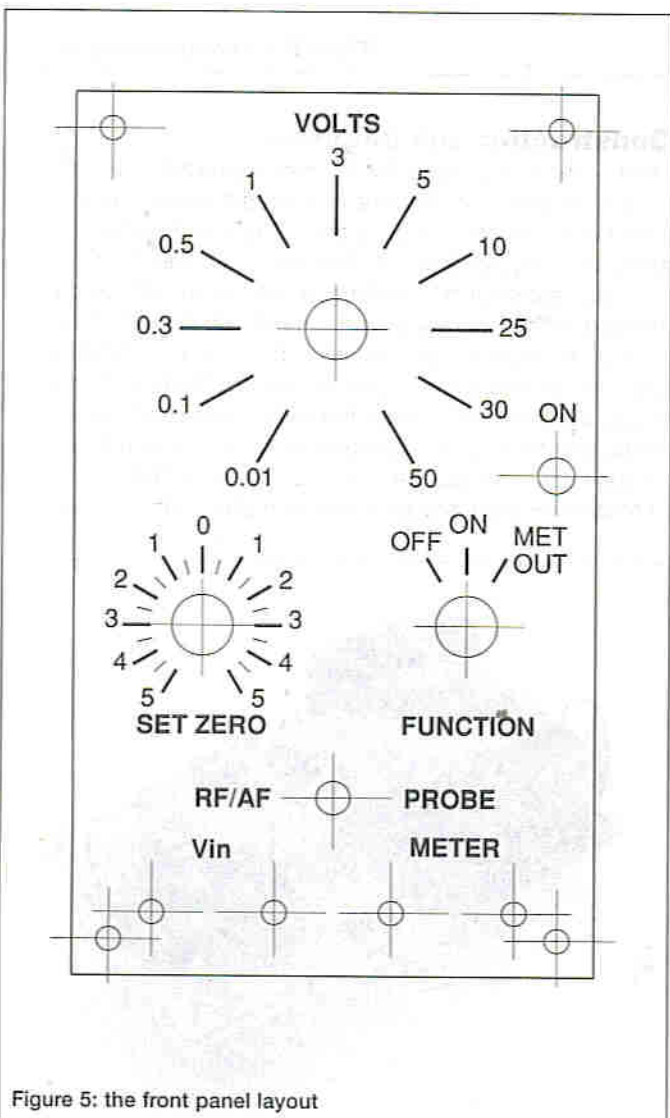


Figure 5: the front panel layout

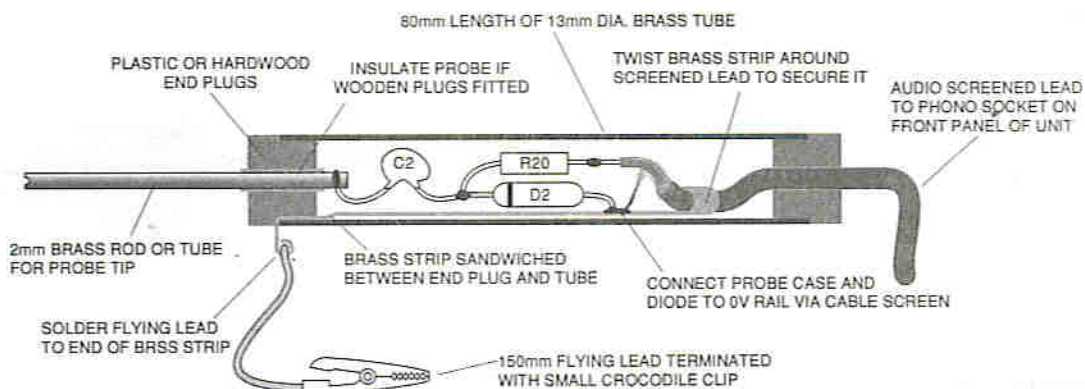


Figure 6: details of the AF/RF probe assembly

everything is in order, connect up the PP3 batteries and switch on. The current in each supply rail should be of the order of 4mA.

Set R15 to mid travel, set R18 to maximum resistance, switch the multimeter to its 3mA or 5mA current range, and connect it to the amplifier unit. Operating R15 should swing the meter pointer either side of zero. Switch the multimeter to a current range of 1mA or less, and, if necessary, refine the adjustment of R15 to bring the pointer back to zero. If the multimeter does not have a sufficiently low current range but has a voltage range of less than 1V (unusual but not unknown) this can be used instead.

Calibration

Switch the meter amplifier to the 10V range, apply its test leads to a fresh PP3 or similar battery, and set R18 so that the meter reads the correct voltage. (Check the battery voltage by direct measurement with the multimeter.) Switch the meter amplifier through the higher voltage ranges to check for consistency and the accuracy of the input divider chain. The correct voltage should continue to be displayed on the multimeter (very slight variations will probably be due to non-linearity in the meter movement as the pointer has to traverse less and less of the scale). The DC calibration of the instrument is now complete.

Connect a power transformer, with a secondary in the 5-10V range, to the mains supply, and check the output voltage by direct measurement with the multimeter.

Readers who have no experience of constructing mains-powered equipment should note that the voltages involved are LETHAL and should seek the help of someone with the necessary experience, particularly if the wiring or terminals at the mains primary side of the transformer are exposed.

Reconnect the multimeter to the amplifier unit (remember to reset it to the low current range), plug in the probe, and set the amplifier to 0-10V. Apply the probe and its flying lead to the mains transformer secondary, and adjust R12 until the reading coincides with the one given directly by the multimeter. The AC calibration of the instrument is now complete. The quoted component values are best suited to meters with FSDs in the μA range. If a less sensitive meter with a 1mA FSD is used with the amplifier, calibration adjustments will be easier if the current limiting resistor R17 is shorted out and the value of pre-set R18 is reduced to 1k.

Use and limitations: DC measurements

The basic accuracy of the unit will, of course, only be as great as the accuracy of the multimeter used to check the calibration voltages. However, with a constant input resistance of 10 megohms on all ranges, disturbance of the circuit under test is minimal, and this will result in the more accurate measurement of voltages in high impedance circuits. The amplifier greatly increases meter sensitivity, and potentials below 1mV can be measured, still with the very high instrument resistance of 10 megohms. Although there is seldom need to measure DC voltages as low as this, the facility can be useful for checking dubious earth returns and switch contacts. The maximum voltage range is 50V, and this should accommodate the needs of most constructors who work with transistorised equipment. At voltages greater than this, even fairly inexpensive multimeters present a reasonably high resistance to the circuit under test, and there is not so much to be gained by using the meter amplifier. Constructors who have decided to build a stand-alone unit may, however, wish to incorporate higher voltage ranges, and this can be done by sub-dividing R11 (the range resistor at the bottom of the chain). Those who wish to do this, or to modify the range switching in some other way, may find figure 7 useful. From that diagram:

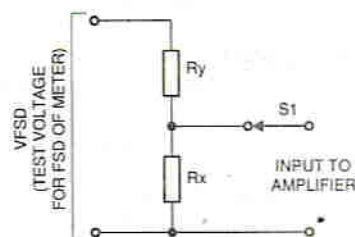


Figure 7: sub-dividing R11 to incorporate higher voltage ranges

$$R_x = (0.01 \times 10^7) / \text{VFSD}$$

and:

$$R_y = 10^7 - R_x$$

(The total value of the chain is maintained at 10 megohms)

For a 100V range:


$$R_x = (0.01 \times 10^7) / 100 = 1\text{k}$$

So R11 would have to be sub-divided into two 1k resistors, and connecting the amplifier input to their junction would give a 100V range.

Random meter pointer fluctuations have not been experienced with any of the amplifiers constructed to this design, and the set-zero control, R15, is smooth and easy to operate. Some readjustment may be necessary after the first reading has been taken (this is commonplace with op-amp designs of this kind), but otherwise the zero setting will be found to be completely stable. R15 can be used to set the pointer at centre scale, and this facility is useful for some test work.

AC measurements

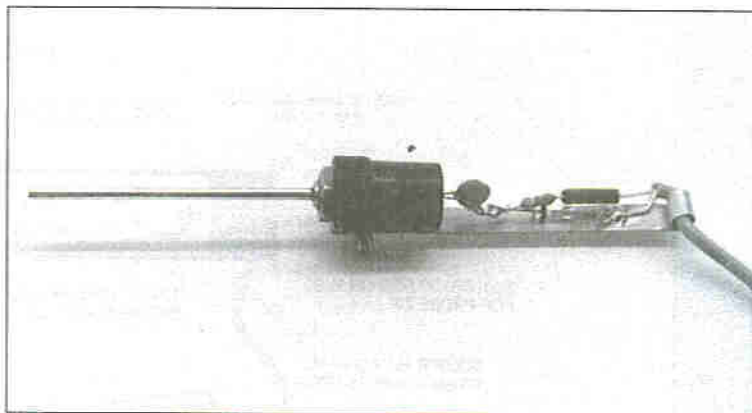From 0.5V upwards, and from 20Hz to 20kHz, the probe will enable AC voltages to be measured accurately. (The readings should, of course, be taken from the multimeter's DC scales: its AC scale is modified to suit its own rectifier circuitry). Below



0.5V and, more particularly, below the knee of the diode characteristic (around 0.3V for a germanium diode), deteriorating rectifier performance results in progressively low readings. At 0.1V (100mV), the reading is approximately 25% low, and around 0.05V (50mV) the readings should be doubled to give a more accurate RMS value.

The voltage developed across the probe diode is a little less than twice the peak value of the AC voltage being measured, that is, almost 2.82 times the RMS value. Different manufacturers quote PIV ratings of between 100 and 115 volts for the OA91 diode, and the probe should not, therefore, be used to measure RMS voltages in excess of 30V. This ceiling could be extended by using a silicon diode with a higher PIV rating, or by using germanium diodes in series (voltage equalising resistors would have to be placed in parallel with the diodes). This would, however, detract from the performance of the probe at low voltages and at RF, and the arrangement suggested here is probably the best compromise.

The value of the blocking capacitor C2 is given as 220nF in order to ensure a uniform response down to 20Hz. This can be reduced to 100nF, or even 10nF, if an extended LF response is not required. Probe impedance is, of course, frequency dependent, and designers of probes of this kind have quoted impedances of the order of 6kohms shunted by around 2pF at 200MHz.

A rough check on the impedance presented by this probe was carried out by progressively increasing a resistance placed in series with its tip until the meter reading was halved. The value of the resistance was then taken as an approximation of the impedance of the probe. This revealed that, from 20Hz to 20kHz, (ie the entire AF range) the impedance presented by the probe is approximately 0.5 megohms. At 1MHz this falls to 25k, at 10MHz 2k5, until, at 40MHz, the impedance is of the order of 700 ohms. As frequency increases, probe impedance becomes increasingly dependent upon its capacitance. Constructors wishing to maximise performance at RF should, therefore, take care with this aspect of the design. A larger diameter probe case, a shorter probe tip, ceramic or other high performance insulation, lowering the value of C2 to 10 or even 1nF in order to reduce its physical size, will all help to keep capacitance low and impedance as high as possible.

Notwithstanding the limitations outlined above, the performance of the unit at audio and radio frequencies is very acceptable, and should meet the needs of most experimenters and hobbyists. The RMS values of sine waves can be measured with reasonable accuracy throughout the AF spectrum, and the probe will provide an indication of AF and RF signal levels down into the low mV region.

PARTS LIST for the Multimeter Amplifier

Resistors

(All 0.25 Watt, 1% tolerance unless otherwise stated.)

R1	9M (6M8 and 2M2)
R2	667k (620k and 47k)
R3	133k3 (130k and 3k3)
R4	100k
R5	66k7 (62k and 4k7)
R6	13k3 (10k and 3k3)
R7	10k
R8	6k (3k3 and 2k7)
R9	667 (620R and 47R)
R10	1k330 (1k and 330R)
R11	2k
R12	1M pre-set variable
R13	1M 5% tolerance
R14	10k
R15	100k linear potentiometer
R16	1M
R17	1k 5% tolerance
R18	22k pre-set potentiometer (see text)
R19	8k2 5% (see text)
R20	3M3 5% tolerance

Capacitors

C1	10nF (.01uF) ceramic
C2	220nF (.22uF) ceramic, 100V working (see text)


Semiconductors

IC1	CA3140E FET input op-amp
D1	Low current, 2mA LED
D2	OA91 germanium diode

Miscellaneous

S1 1 pole, 12 way switch; S2 4 poles, 3 way switch; PCB making materials, Vero pins and ic holder; hook-up wire, audio screened lead and flexible test-meter leads; one large and two small control knobs and 5mm led holder; battery connectors, two red and two black terminals, phono plug and socket, and one red and one black test probe; scrap aluminium sheet for brackets and battery holders; brass tube and strip for AC probe; nuts, bolts and washers; thin acetate sheet to protect panel markings; plastic box, 90 x 150 x 52mm externally; PP3 batteries.

THE Autorouter for EASY-PC Pro' XM!

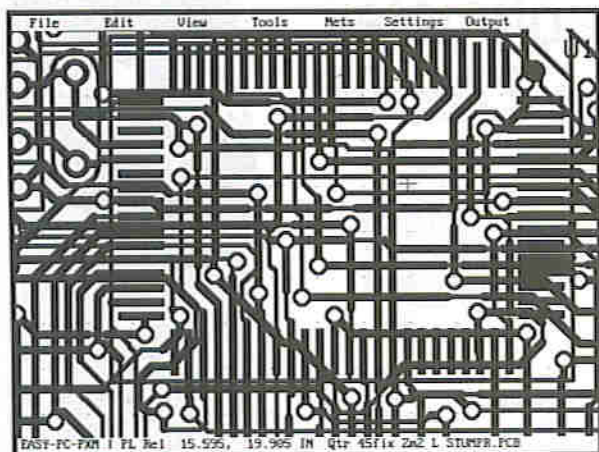


"The Best Autorouter that I have seen costing less than £10,000!" R.H. - (Willingham, UK)

- Uses the latest 32 Bit, Shape Based, Multi-pass, Shove-aside and Rip-up and Re-try Technology
- AutoRoute very large and complex boards
- User Controllable, User Configurable
- 100% Completion where other autorouters fail
- 100% Autorouted 140 Components on a 210mm x 150mm board in less than 10 minutes! (75MHz Pentium)
- **Could Easily Pay For Itself On The First Project**

MultiRouter - only £295/\$475!

Integrated Electronics CAD

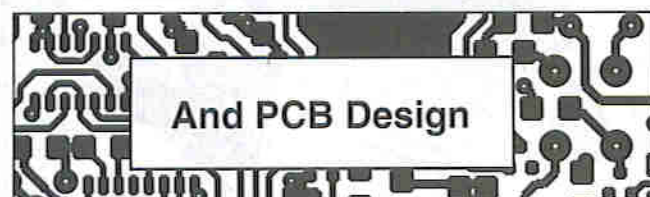

Prices from UK£75 / US\$145

Affordable Electronics CAD

EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III, LAYAN and PULSAR.	From \$275	£145
MultiRouter: 32bit Multi-pass Autorouter for EASY-PC Professional XM	\$475	£295
LAYAN: Electro-Magnetic Layout Simulator. Include board parasitics in your Analogue simulations. Links with and requires EASY-PC Professional XM and ANALYSER III Professional	\$950	£495
PULSAR: Digital Circuit Simulator	From \$195	£98
ANALYSER III: Analogue Linear Circuit Simulator	From \$195	£98
FILTECH: Active and Passive Filter Design program	From \$275	£145
STOCKIT: New comprehensive Stock control program for the small or medium sized business	\$275	£145
EASY-PC: Award Winning PCB and Schematic CAD.	\$145	£75
Z-MATCH: Award Winning Smith-Chart based program for RF Engineers.	From \$275	£145

We operate a no penalty upgrade policy. US\$ prices include Post and Packing Sterling Prices exclude P&P and VAT.

For Full Information and Demo' Disk, please write, phone, email or fax:-

Number One Systems

UK/EEC: Ref: ETI, Harding Way, St.Ives, Cambridgeshire, ENGLAND, PE17 4WR.
Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042
USA: Ref: ETI, 126 Smith Creek Drive, Los Gatos, CA 95030
Telephone/Fax: (408) 395-0249

Email: sales@numberone.com
International +44 1480 461778

- TECHNICAL SUPPORT FREE FOR LIFE
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

<http://www.numberone.com>



Transform your PC

into a digital oscilloscope, spectrum analyser, frequency meter, voltmeter, data logger . . for as little as £49.00

Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement instruments or as an advanced data logger.

Hardware and software are supplied together as a package - no more worries about incompatibility and no programming required.

Pico Technology specialises only in the development of PC based data acquisition instrumentation. We have the product range and experience to help solve your test and measurement problem.

Call for your guide on 'Virtual Instrumentation'. We are here to help you.



The ADC-10 supplied with PicoScope gives your computer a single channel of analog input.

ADC-10 £49
with PicoLog £59

Data Logging

Pico's range of PC based data logging products enable you to easily measure, display and record temperature, pressure and voltage signals.

TC-08 Thermocouple to PC Converter

- Supplied with PicoLog data logging software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs
- No power supply required.

TC-08 £199 TC-08 £224 with cal. Cert. complete with serial cable & adaptor. Thermocouple probes available.



Virtual Instrumentation

Pico's PC based oscilloscopes simply plug into the parallel port turning your PC into a fully featured oscilloscope, spectrum analyser and meter. Windows and DOS software supplied.

ADC-100 Dual Channel 12 bit resolution

The ADC-100 offers both a high sampling rate 100kHz and a high resolution. Flexible input ranges ($\pm 50\text{mV}$ to $\pm 20\text{V}$) make the unit ideal for audio, automotive and education use.

ADC-100 £199 ADC-100 with PicoLog £219

ADC-200 Digital Storage Oscilloscope

- 50 MSPS Dual Channel Digital Storage Scope
- 25 MHz Spectrum Analyser
- Windows or DOS environment
- $\pm 50\text{mV}$ to $\pm 20\text{V}$
- Multimeter
- 20 MSPS also available

ADC 200-20 £359.00
ADC 200-50 £499.00

Both units are supplied with cables, power supply and manuals.



Call for free demo disk and product range catalogue

Post & Packing UK £3.50, Export customers add £9 for carriage & insurance.

Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ UK Tel: + 44 (0)1954 211716 Fax: + 44 (0)1954 211880
E-mail: post@picotech.co.uk Web site: <http://www.picotech.co.uk/>

Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT

releasing PC potential

releasing PC potential

PICO Technology Limited

Fast Fivers

Adaptable, affordable - handy circuits for around £5. By Owen Bishop.

1. Warbling Door Alert

This is the first of a series of simple low-cost, quick-to-build projects that will be useful around the home or in the workshop. Each project has at least one interesting point about the circuit that will help you discover a little more about electronics. The target cost of the circuit is £5, including VAT. Suppliers' prices vary and you may sometimes need to shop around for the more expensive items when the budget is tight. The loudspeaker in this month's project is an example, for some suppliers charge about 50% more than others for virtually the same thing. Or you can get one free from an old radio set.

There are numerous electronic buzzers on the market but most of them produce either a rather dreary sound or one that is too aggressive for many domestic situations. Like the more expensive telephones, this one produces a more relaxed warbling note. Better still, you can program the warble over a wide range of pitch and warble-rate. If you need more than one alert in your home you can tune each one to give a distinctive tone.

How it works

The circuit in figure 1 is based on two voltage controlled oscillators, one to make the basic tone and the other to produce the warbling effect. The VCOs (voltage controlled oscillators) are provided by a pair of CMOS 4046 ICs. In the catalogues the 4046 is described as a Phase Locked Loop, which it certainly is. A PLL is a circuit that locks on to a signal of given frequency, even when the signal is faint against a lot of background noise. The 4046 contains all the parts necessary to build a PLL, among them a VCO. It needs so few extra components that a 4046 is an inexpensive and easy way to build a VCO, and we can (with a clear conscience) just forget about the other bits of the IC that we do not use.

The basic tone is provided by IC2. Its output is a square wave from pin 4, driving a loudspeaker by way of a mosfet to produce a sound amply loud to rouse the average household. The central frequency (f_c) of the tone is decided by the values of capacitor C2 and resistor R2, where:

$$f_c = 1/(R2 \times C2)$$

With the values shown in figure 1, f_c is about 15kHz. This is the frequency when the control voltage at pin 9 of IC2 is at half the supply voltage (4.5V in this circuit). As the control voltage is reduced below 4.5V, the frequency gradually falls to zero. As the voltage is increased, the frequency rises to $2f_c$, about 30kHz. So the tone frequency can be set anywhere in the audio range simply by adjusting VR2.

The warbling effect is provided by IC1. This VCO has a central frequency of $1/(R1 \times C1) = 37\text{Hz}$ and can be varied from zero up to 74Hz by adjusting VR1. When the push-button at the front door (S1) is pressed, both ICs begin to oscillate. The oscillations of IC1 provide a pulsed control voltage to IC2, so that its basic tone is frequency-modulated, and gives the warbling effect. By adjusting VR1 and VR2 you can produce an almost unlimited variety of sounds, some harsh, some urgent, and some pleasantly restful.

Construction

The power supply is intended to be a 9V PP3 battery. Since current is supplied only when the button is pressed, the battery lasts a long time. The circuit is built on a piece of 0.1in-matrix stripboard, 16 (or only 14) strips wide and 35 holes long. First use a spot face cutter to cut the strips beneath the board at C10 to K10, C17 to K17, C23 to K23, J29, K 29 and P13. When you solder in the IC sockets, solder blobs beneath the board join points B12 to C12, B25 to C25, K9 to L9 and K22 to L22.

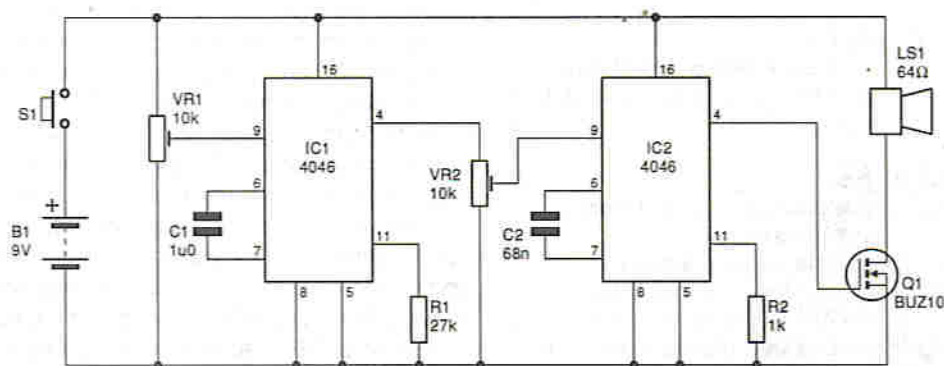


Figure 1: the circuit of the Warbling Door Alert

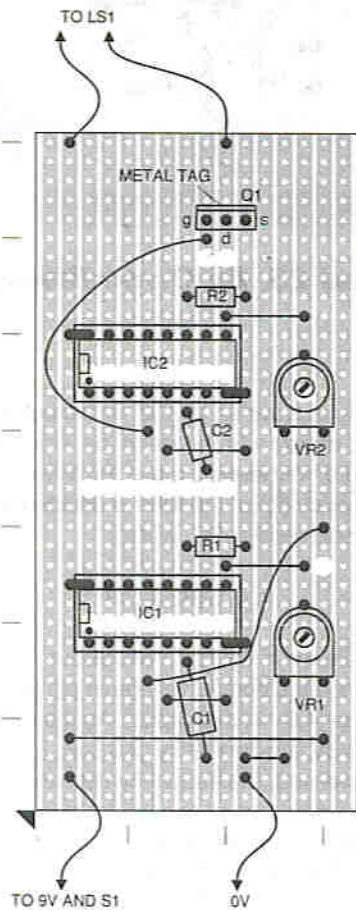


Figure 2: the stripboard layout

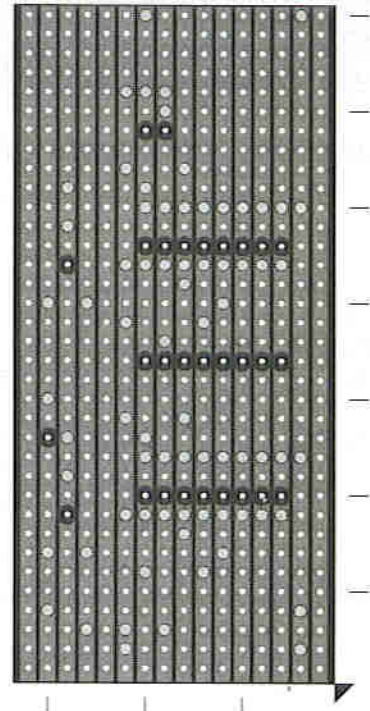


Figure 3: the underside of the stripboard layout

PARTS LIST for the Warbling Door Alert

(Capacitor and fixed resistor values can be amended to suit your requirements)

Resistors (5% tolerance or better)

- R1 27k Ω
- R2 1k Ω
- VR1, VR2 Miniature horizontal preset potentiometer, 10k Ω

Capacitors (polyester layer)

- C1 1 μ F
- C2 68nF

Semiconductors

- IC1, IC2 4046 cmos phase locked loop
- Q1 BUZ10 n-channel enhancement power mosfet

Miscellaneous

- S1 push-switch (door-bell type)
- LS1 64W loudspeaker
- Clip for PP3 battery; 0.1in stripboard approx 40mm (16 strips) wide by 80mm (35 holes) long, 1mm terminal pins (4 off), 16-pin dill sockets for the ics (2 off), connecting wire, including twin lead from door to site of alert.

Assemble the whole circuit before testing it. At this stage, the loudspeaker need not be mounted in its enclosure; just connect it temporarily. Before testing compare the circuit with figure 2 to make sure that all components and particularly the wire links go to the correct holes. Check beneath the board (use a hand-lens) to make sure that all tracks have actually been cut where required and also that there are no unwanted solder bridges between adjacent tracks. Set VR1 and VR2 to about half way along their tracks and press S1. When all is working properly, adjust VR1 and VR2 to obtain the sound you prefer.

The £5 costing in this series does not include a case. Often a project will run just as usefully without one. But a loudspeaker really needs an enclosure if full volume and tone quality is to be obtained. You may have a small wooden or plastic box that can be adapted for this purpose, otherwise, the cheapest solution is to buy an ABS project box. You do not need a box with slots for mounting the circuit-board; use a lump of Blu-tack or a piece of double-sided tape to fix it to the bottom of the box. Cut a circular aperture in the lid of the box for the speaker and glue it in place. Of course, if you happen to have a spare speaker with enclosure from an old radio set, tape player, or stereo system, you can use this: strip out the old circuit board, and mount the project circuit-board inside the case. Figure 1 shows a 64R speaker being used, but the BUZ10 can take up to 20A, so an 8R speaker can be used instead. You may want to reduce volume by wiring a 2 watt (or more) wire-wound resistor of a few ohms in series with the speaker.

From the Microcontroller Professionals:

Program PIC Microcontrollers:

We now have 3 programmers for PIC's !

Original - This is our original programmer for 16C5X, 16C55X, 16C6X, 16C7x, 16C8x, 16F8X devices.

Price : £40 for the kit, or £50 ready built.

Serial - This programmer programs the newest PIC devices in a single 40 pin multi-width ZIF socket. Will program: 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, PIC 14000. Also In-Circuit programming.

Price : £40 for the kit, or £50 ready built.

Introductory - This programmer is intended for the smaller user, or newcomer to PIC's. Will program 8 pin and 18 pin devices : 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508, and 12C509.

Price £22 for the kit (not available ready built).

Note : All our programmers operate on a PC, using a standard RS232 serial interface (COM1, 2, 3, or 4). No hard to handle parallel cable swapping ! All programmers are supplied with full instructions, Windows programming software, MPASM, MPSIM and PICDE - the Windows based PIC assembler environment. (offers all features of PICDESIM below without the simulator).

PIC BASIC

FED's PIC BASIC products - straightforward, capable, powerful, rapid development.

In a Windows Development Environment our modules need no assembler or UV eraser to program your PIC's, and operate from a serial link to your PC.

The 16C74 module features - 8k EEPROM, up to 2000 lines of BASIC, 27 lines of programmable I/O, 8 A/D inputs, Interrupt driven serial RS232 interface, Peripheral I²C bus interface, LCD display driver routines, up to 178 bytes for variables and stack, extendible with optional external ram and all the standard 16C74 features.

Compiler - The FED PIC BASIC compiler for the 16C74. It produces hex code to program your 16C74 directly with no need for external EEPROM. Compatible with the EEPROM versions of PIC 16C74 BASIC modules - develop on an EEPROM based module then compile and program your PIC chips directly.

16C57 Module Kit (8k EEPROM, 4MHz) £27.00, Pre-built £33.00
16C57 Module Kit (8k EEPROM, 10MHz) £31.00, Pre-built £37.00
16C74 Module Kit (8k EEPROM, 4MHz) £35.00, Pre-built £42.00
16C74 Module Kit (8k EEPROM, 20MHz) £40.00, Pre-built £46.00
16C84 chip programmed with BASIC - £25.00
Compiler - £60.00, or £50.00 when ordered with a module



Forest Electronic Developments

10 Holmhurst Avenue, Christchurch,
Dorset, BH23 5PQ. <http://www.ibmpcug.uk/~gmwarner/fed.htm>
01425-270191 (Voice/Fax)

Prices are inclusive, please add £3.00 for P&P and handling to each order.

Cheques/POs payable to Forest Electronic Developments, or phone with credit card details. Serial Cables - £7.50.



Windows Based PIC Development: PICDESIM - the Windows based development environment.

PICDESIM allows you to develop your PIC projects in one Windows program.

Incorporate multiple files, view help file information directly from the code, edit within the project, build, and track errors directly in the source, then simulate.

Simulator allows addressed, conditional and timed breakpoints, follow your code in the source editor window, set a breakpoint directly in the code. Run your program, or single step, or step over subroutines. Track variable values and trace them for display on the Trace Analyser. Input stimuli include clocks, direct values and asynchronous serial data. Profile your program - examine frequently called routines which are timed and use the information to optimise out bottle necks.

Trace Analyser allows any register or port value to be examined in analogue (graphical), waveform, or numeric values, check your program directly against your predicted waveforms.

Runs up to 50 times faster than MPSIM !

NEW ! - 32 bit version allows full use of Windows '95 and Windows NT 4.0 facilities.

Cost £30.00, or £25.00 for existing and new purchasers of any of our programmers. Please specify Windows 3.1, or Windows '95 (32 bit) versions of PICDESIM.

PIC's

PIC16C74/JW Erasable 20MHz	£24.00	PIC16C556 (14 bit versn 16C56)	£4.50
PIC16C74-04POTP 4MHz	£8.00	PIC16C74-20P OTP 20MHz	£11.00
PIC16C57-04POTP 4MHz	£5.00	PIC16C57-10P OTP 10MHz	£6.00
PIC16C84-04P 4MHz	£6.00	PIC16C84-10P 10MHz	£8.00
PIC16F84-04P 4MHz	£7.00	PIC12C508-04P OTP 4MHz	£2.20
PIC14000-04P OTP 4MHz	£10.00	PIC14000/JW Erasable	£23.00
PIC12C508-04P OTP 4MHz	£2.70	Ask about other chips!	

PIC Training

Our new training course introduces PIC's painlessly with a practical emphasis.

Our training package includes

- Full introductory manual to the PIC series including use of assembler, peripherals and interrupts for the 12 bit and 14 bit controllers.
- Video introducing the PIC, and showing use of PICDESIM
- Development board with PIC16F84, and all components required to develop 3 practical projects, including LED driving, handling delays and serial communications to a PC.
- PICDESIM - the Windows based Simulator (see left)
- Microchip MPSIM and MPASM programs

Training Course £80.00

Training Course with pre-built Introductory PIC programmer £99.00

Development Boards

Development boards allow simple prototyping of projects.

Our 18 pin development board includes a simple serial interface to a PC, 18 pin socket for any 18 pin device, 4MHz resonator and power regulator components. All instructions components, and circuits supplied. Includes a 16F84 - 10MHz version of 16C84 with an additional 32 bytes of RAM for programs.

Development board with all components for serial interface, power supply, oscillator and 16F84 device £20.00.

Coming soon...


Look out over the next few months as we expand our PIC BASIC range and extend our microcontroller support to another major manufacturer.



CHELMER VALVE COMPANY

If you need Valves/Tubes or RF Power Transistors etc. ...then try us!

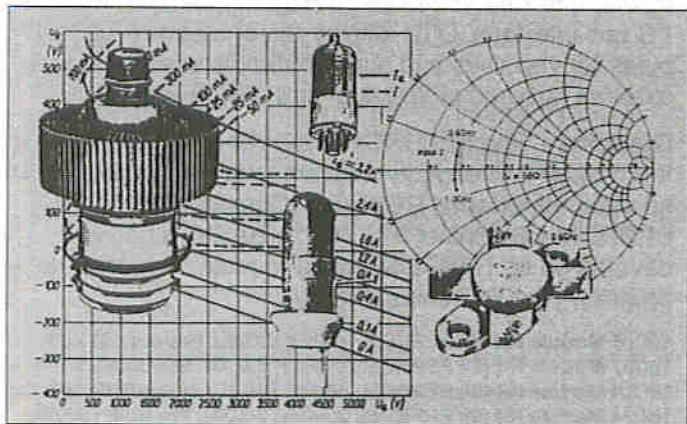We have vast stocks, widespread sources and 35 years specialist experience in meeting our customers requirements.



Tuned to the needs of the Radio Amateur


Chelmer Valve Company, 130 New London Road,
Chelmsford, Essex CM2 0RG, England.

Tel: 44-01245-355296/265865

Fax: 44-01245-490064

ROBOTICS!

NEW!
from the USA

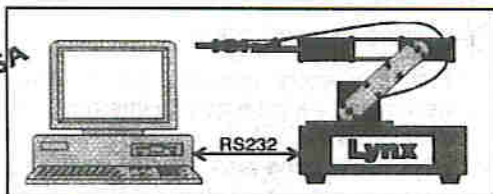


LYNX ARM

ROBOTIC ARM Kit, five axis motion with gripper. Control from any serial port. Uses R/C servos for good repeatability and accuracy. Kit includes pre-cut arm components, electronics controller board, PC software (inc source listing) and detailed construction manual. 40x30x20cm

STAMP BUG

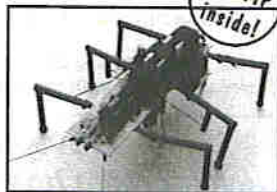"STAMP" based insect kit illustrates basic walking mechanisms. Tactile feelers detect objects causing back-up and turn. Pre-programmed but with the option to re-programme (needs Stamp programming pack). Powerful 3 servo construction carries payloads up to 250gms and up to 3 hours motion from the on-board NiCad. 20x15x5cm



STAMP
inside!

MUSCLE WIRES

Fascinating wires that CONTRACT WHEN ELECTRICALLY HEATED producing a useful amount of force (Up to 0.9kgf for 250um wire). Require 0.3V/cm and currents from 100ma to 1Amp. Choose from four gauges of wire (50, 100, 150 and 250 um dia). Detailed Data and Project Book (128 pages) also available separately and with Deluxe Wire kit suitable for 13 projects.

SERVO - IR - LCD CONTROLLERS

A range of low cost controller kits: R/C servos (up to 8 servos per board - simple RS232 commands from your PC hold servo in position until updated etc).
LCD display drivers (All standard Hitachi controller types up to 4x20 characters - RS232 input)
IR programmable receivers (7 output channels - accept any TV/IRF controller - up to 25mA output per channel - programmable toggle/momentary switching action)

Please call to receive further details on any of the above products

MILFORD INSTRUMENTS

Creative Products for Enquiring Minds
01977 683665, Fax 01977 681465

Calling all Radio enthusiasts



Ham Radio TODAY

The magazine for amateur radio

New equipment, scanners, packet radio, construction,
club news, views and much more.

This month in HRT:

Full Technical Review

The new Kenwood TS-570 DSP HF Transceiver
reviewed by G4HCL

Build an Audio Test Meter

An HRT construction project

High tech review

Realistic PRO-2045 base receiver

Scanner Review

Realistic handheld PRO-70

"Yes, it's Radio, but is it enough?"

Ham Radio and the Internet

All in a Day's Work

Radio repair "Insider's tips"

Packet radio -

and the latest data modes

Ask your newsagent for Ham Radio Today

PLUS

Radio Today, Scanners for listeners, free radio Software

Offers, free readers' ads, band reports and more.

OUT NOW!

All contents are currently planned but may alter.

Battery Quick-Check

Terry Balbirnie's battery "health-checker" will tell you instantly whether those loose AA cells and PP3s are still in service, or ready for the bin.

The modern home is filled with battery-operated devices. These include toys, photographic equipment, TV remote controls, Walkman-type personal stereos, games and radios. Batteries are also used as back-up supplies for clocks and videos. Most of these batteries fall into two categories: the 9V PP3 type and the 1.5V "AA" (HP7) size cell. Note that, strictly speaking, a *cell* is a single unit and a *battery* consists of several cells connected in series. However, the word 'battery' is often used for single cells and this is how it will be used here.

All mixed up

It often happens that batteries are left lying around the house, or new ones get mixed up with the old. It is then necessary to test them to find out which are fit for use, which may be

used for some other purpose and which should be thrown away. Sometimes a cell that shows up as unsuitable for the most demanding purposes may be used to operate a clock or other very low-current device for a few months. *Note, however, that smoke detectors must always be fitted with new batteries.*


This tester circuit will give a good indication of the "state of health" of the types of battery mentioned above. It is very simple to use, making it ideal where children or the non-technically minded are involved.


Fit for service

The unit is housed in a small plastic box which has an "AA" size cell holder and a PP3 connector mounted on top. There is also a small slide switch and an LED. To make the test, the slide switch is set to "9V" or "1.5V" as appropriate; the battery is then connected and the LED observed. If there are bright flashes given about once every second, the battery is in good condition and fit for further service. If the flashes are somewhat dimmer and the rate is markedly slower, the battery may be suitable for use in a low-current appliance such as a clock. If the LED remains off or flashes very feebly and slowly, the battery is "flat" and should be discarded.

If a battery is connected to the tester with incorrect polarity, no harm will result but, of course, the circuit will not work and the LED will remain off.

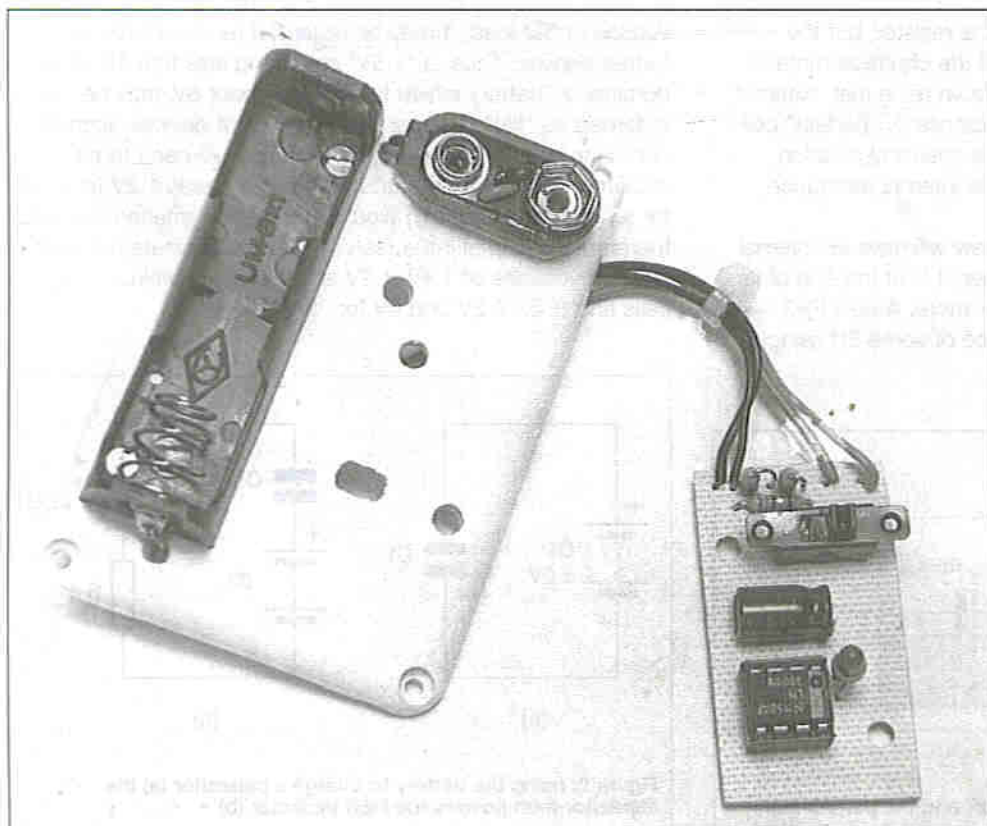Note that the LED is powered by the battery being tested, so there is no problem caused by having a battery in the checking circuit itself (how do you check the battery that checks the battery?).



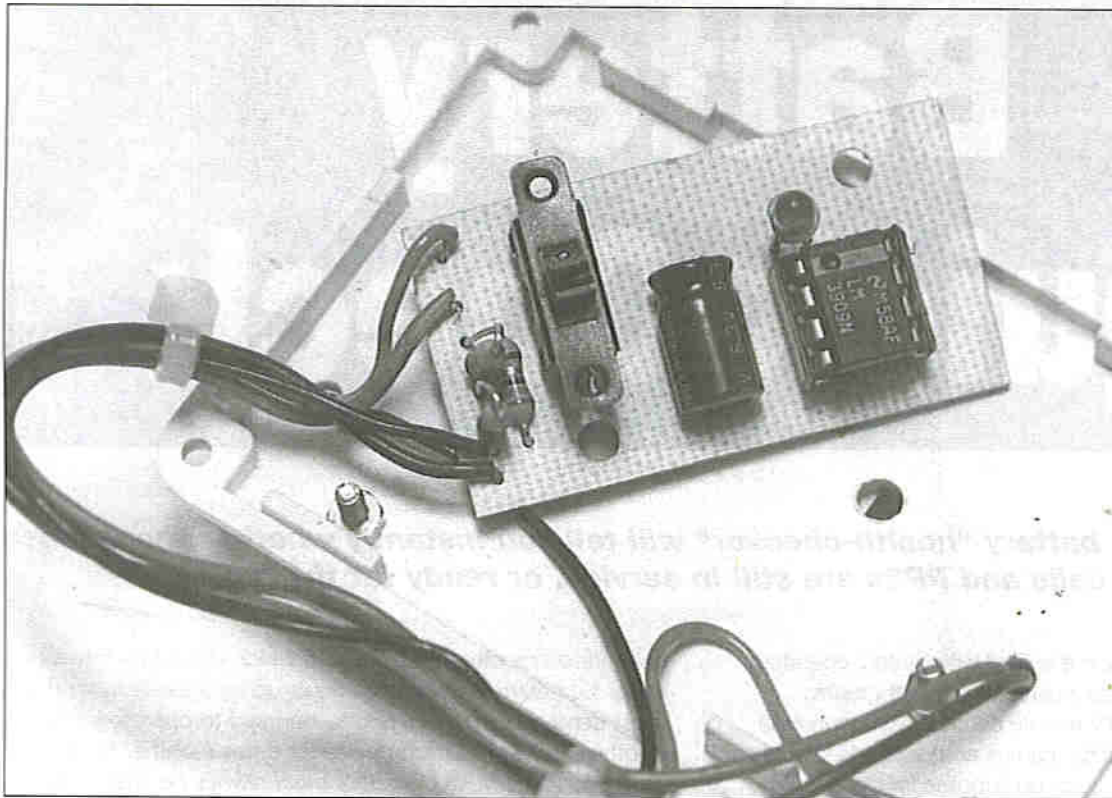

When current flows through the internal resistance, a voltage is developed across it (as Ohm's Law dictates). This voltage is "lost" as far as the external circuit is concerned. To take a practical example, suppose a bulb is connected to a battery. The same current flowing through the lamp's filament also passes through the internal resistance. The greater the voltage developed across the internal resistance, the less will appear across the bulb. To put it another way, the bulb loses out and becomes dimmer as the battery ages.

A bit of theory

To test a battery, it is necessary to use a circuit which responds to the voltage between the terminals. This voltage tends to fall as the battery ages. Some inexpensive units perform the test with the battery off-load (that is, while not delivering significant current). This is not very satisfactory, because the voltage does not fall very much under such circumstances. In use, the battery will be delivering current, and it is then that the reduction in terminal voltage is more pronounced. This is due to the voltage drop which occurs when current flows through the internal resistance of the cell. The internal resistance is not a physical resistor, but the undesirable effect of the resistance of the chemical material inside. It may be imagined as, and drawn as, a real external resistor connected in series with a supposedly "perfect" cell (see figure 1). As the battery ages, the chemical reaction taking place within it clogs up, and the internal resistance rises.

A typical "AA" alkaline cell when new will have an internal resistance of less than 0.5 ohms. When it is at the end of its useful life, it may have risen to 10R or more. A new PP3 battery may have an internal resistance of some 3R rising to 60R or thereabouts when "flat".

Under working conditions, a brand new "1.5V" cell may develop some 1.45V across the load. A 9V PP3 type battery operating, say, a small radio may develop some 8.6V. Appliances always allow for some voltage drop, so that they will continue to work properly (up to a point) as the battery ages. The rated voltage of a cycle light bulb, for example, may be 2.4V when the supply is derived from two cells (nominally 3V). When the battery is new, the bulb may be somewhat overloaded. However, for most of the time it will operate correctly or with only slight dimming.

When a battery provides less than 66% of its nominal voltage under load, it may be regarded as unsuitable for further service. Thus, a "1.5V" cell giving less than 1V, or a nominal 9V battery which falls below about 6V, may be regarded as "flat". To operate high-current devices such as certain toys and flashguns, the batteries will need to be discarded long before that, and in those cases 1.2V (or 7.2V for a nominal 9V battery) would be a better criterion. It would therefore be helpful if the tester could discriminate between on-load voltages of 1.4V, 1.2V and 1.0V for nominal "1.5V" cells and 8.4V, 7.2V and 6V for "9V" batteries.

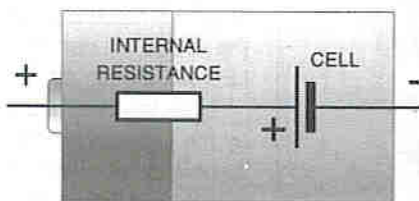


Figure 1: in theory: the "external resistor and the perfect cell"


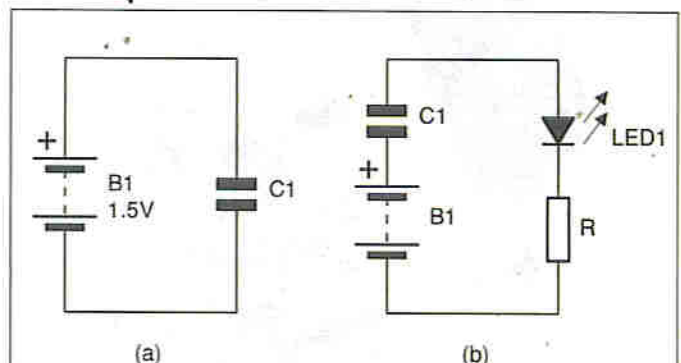


Figure 2: using the battery to charge a capacitor (a) the capacitor then powers the PED indicator (b)

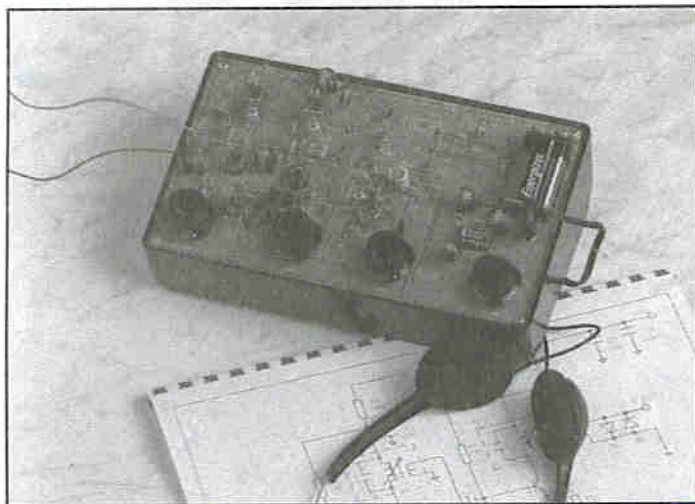

Radio Receiver Trainer

An Invaluable Learning and Design Tool for all Experimenters



The manual contains complete schematics and theory of operation of all the building blocks. Use this trainer to receive frequencies from 500KHz to 110 MHz!

A set of proven alternate building block designs are included in the manual for you to get started with your own designs. There is no need to get your complete receiver design working all at once. Build and test each block one at a time.

The Radio Receiver Trainer contains nine receiver building blocks and a comprehensive training manual.

Simply connect the building blocks to build AM, SW, Superhet and Direct Conversion receivers. Decode SSB, CW and FM! Use proven building blocks to develop and test your own designs.

Full technical support and advice given

Pricing: Complete £129.00
Kit £89.00
(Kit excludes case & headphones)

P&P is £5 (UK), £8 (EC), £12 (World)
Add 17.5% Vat to Total Price

Building Blocks: RF Input Tuner
RF Oscillator
Mixer
IF Filter
IF Amplifier
AM Detector
Beat Frequency Oscillator
Audio Filter
Audio Amplifier

Mail Order To: **Pyramid Electronics LTD.**

204 Ferndale Road, Brixton, London SW9 8AG

Phone (0171) 738 4044 Fax (0171) 274 7997

Out of office hours ordering by answering machine.



GREENWELD
ELECTRONIC
COMPONENTS

Greenweld has been established for 23 years specialising in buying surplus job lots of Electronic Components and Finished Goods

We also keep a wide range of new stock regular lines. Why not request our 1997 Catalogue and latest Supplement - both absolutely FREE!

BECOME A BARGAIN LIST SUBSCRIBER TO SEE WHAT'S ON OFFER BEFORE IT'S ADVERTISED GENERALLY

Standard Bargain List Subscription

For just £6.00 a year UK/BFPO (£10.00 overseas), we'll send you **The Greenweld Guardian** every month. With this newsletter comes our latest **Bargain List** giving details of new surplus products available and details of new lines being stocked. Each issue is supplied with a personalised **Order Form** and details of exclusive offers available to Subscribers only.

Gold Bargain List Subscription

For just £12.00 a year (£20.00 overseas) the **GOLD** Subscriber category offers the following advantages:

- The **Greenweld Guardian** and latest **Bargain List** every month, together with any brochures or fliers from our suppliers
- A **REDUCED POSTAGE RATE** of £1.50 (normally £3.00) for all orders (UK only) and a reply paid envelope
- 5% DISCOUNT** on all regular Catalogue and Bargain List items

So Don't Miss Out - Subscribe Today!



1997 CATALOGUE OUT NOW!

**Greenweld · 27E Park Road
Southampton · SO15 3UQ
TELEPHONE: 01703 236363
FAX: 01703 236307**

INTERNET: <http://www.herald.co.uk/clients/G/Greenweld/greenweld.html>

Our stores (over 10,000 sq. ft.) have enormous stocks. We are open 8.00 am - 5.30 pm Monday to Saturday. Come and see us!



The Low Cost Controller That's Easy To Use

Features

The K-307 Module provides the features required for most embedded applications

- Analogue** • 4 Channels in 1 Channel out
- Digital** • 36 Digital in or out & Timers
- Serial** • RS-232 or RS-485 plus I2C
- Display** • LCD both text and graphics
- Keyboard** • Upto 8 x 8 matrix keyboard
- Memory** • > 2Mbytes available on board
- Low Power** • Many modes to choose from

Development

The PC Starter Pack provides the quickest method to get your application up & running

- Operating System** • Real Time Multi Tasking
- Languages** • 'C', Modula-2 and Assembler
- Expansion** • Easy to expand to a wide range of peripheral cards

Other Features

Real Time Calendar Clock, Battery Back Up, Watch Dog, Power Fail Detect, STE I/O Bus, 8051 interface, 68000 and PC Interface

Cambridge Microprocessor Systems Limited



Units 17 - 18 Zone 'D'
Chelmsford Road Ind Est
Great Dunmow Essex CM6 1XG
E-mail cms@dial.pipex.com

Phone 01 371 875 644



Visible Sound Ltd.

The following features apply to all of our PC control cards:

Standard 8 bit ISA, base address fully selectable via dip switches. Installation instructions, application notes, circuit schematic and software examples in 'C', BASIC and assembler (on 3.5" floppy disk). All connections to the cards made via a standard 25 way female D-type connector on the end plate.

H134A 24 Digital I/O's: Fully programmable TTL level digital I/O's based around the 8255. Kit available K134A £27 **£29**

H130A 8 Channel Relay: Completely isolated programmable relay output card. 3 contacts available per channel, NO, NC and C. Contacts rated 1A @ 30v DC. (Readback Feature!) Kit available K130A £32 **£35**

Isolated I/O: For ultimate protection this virtually indestructible card offers 8 opto isolated inputs and 4 relay outputs. 5v H131A, 12v H132A, 24v H133A. Kits available 5v K131A, 12v K132A and 24v K133A £32 **£35**

25 Way terminal board: This board allows simple screw terminal access for all of the above cards. Kit available K135A £12 **£14**

A057A M/M 25 way or A058A M/F 25 way cables available **£6**

151-s, The Exchange Building, Mount Stuart Square, Cardiff, CF1 6EB.
Tel (01222)458417 Fax (01222)625797 www.vstec.demon.co.uk
ALL Prices INCLUSIVE of vat and delivery (UK Only) Same day dispatch

10% DISCOUNT TO ALL ETI READERS

0-12" (300mm) Digital LCD Calipers ~~£99.95~~ £89.95 inc

0-6" (150mm) Digital LCD Calipers ~~£49.95~~ £44.95 inc

AUTO TURN OFF
MEASURE INSIDE, OUTSIDE AND DEPTH.
ZERO ANYWHERE ON THE SCALE, CONVERTS METRIC TO IMPERIAL AND VICE VERSA

BOTH THESE CALIPERS MEASURE TO A RESOLUTION AND REPEATABILITY OF 0.01mm/0.0005" AND ARE POWERED BY ONE STANDARD 1.5v SILVER OXIDE BATTERY. THE PRICES INCLUDE A FOAM LINED CARRY CASE, VAT, POST AND PACKING (IF YOU ARE NOT COMPLETELY SATISFIED WITH YOUR PURCHASE SIMPLY RETURN IT TO US WITHIN 30 DAYS FOR AN IMMEDIATE NO DOUBT REFUND. THIS OFFER DOES NOT AFFECT YOUR STATUTORY RIGHTS)

From: **KPL, 226 WHITEHORSE ROAD, CROYDON, SURREY, CR0 2LB**
OR CALL TO ORDER **0181 665 1041**
FOR MORE DETAILS AND OTHER SPECIAL OFFERS.



TEST EQUIPMENT SPECIAL OFFER

10MHz Function Generator

(offer valid while stocks lasts)

- Δ Sine, square, triangle, pulse & sawtooth
- Δ 20mV to 20Vpp output
- Δ 50Ω and TTL outputs
- Δ External frequency modulation & sweep
- Δ Pulse width modulation
- Δ Offset and duty cycle adjustment

H6000 0.1Hz - 10MHz £198.58 £149.00
All equipment is supplied new, complete with mains lead, operating manual and 1 year guarantee. Prices include VAT and free delivery, phone for complete list.

- MX180** 3½ digit, 20 range, digital multimeter ~~£23.00~~ £14.95
- DM9092** 3½ digit, auto range, digital multimeter ~~£81.08~~ £49.00
- DM9023** 3½ digit, capacitance meter 200pF-20mF ~~£81.08~~ £49.00
- FC1300** 1.3GHz hand held 8 dig LCD freq counter ~~£139.83~~ £89.00
- AF2000** Audio signal generator 10Hz - 1MHz ~~£154.58~~ £129.00
- PR363A** Kenwood 0-36V 0-3A psu with 2 displays ~~£352.20~~ £149.00
- CS4125** Kenwood 20MHz 2 channel oscilloscope ~~£468.83~~ £379.00

VANN DRAPER ELECTRONICS LTD Tel (0116) 2771400 Fax (0116) 2773945
Unit 5, Premier Works, Canal Street, South Wigston, Leicester LE18 2PL

COLOUR VIDEO CAMERAS

LIMITED SPECIAL OFFER
JVC GR-S505 ONLY £79

Ideal for image capture, home videos, security, digital photography and much more. Excellent image quality from 1/2" CCD, 410,000 pixels. Has 8x zoom lens, shutter speed to 1/10,000 second, manual aperture override for precise exposure, and digital effects controls. These are brand new camcorders but the cassette mechanism has been removed. These are the same model as we sold a year ago but the output is S-VHS NTSC. These will give a colour picture with a multi-standard TV or most frame grabbers but a B&W picture with PAL type. Some assembly work required.

Also available is a viewfinder which has standard video input. Has high resolution 0.6" B&W CRT. Ideal for virtual reality and 3-D vision when used in pairs. Requires only 8Vdc at 90mA (eg 9V battery). Not many left. Only £39.

Matching mains power supply and charger unit £12. NiCad 9.6V 1Ah battery £12. UHF modulator £6. All the above & camera only £99. Please add 17.5% VAT to all prices.



LASERTECH Telephone 01284 788108 Fax 01284 788135
Mill Road, Great Barton, Bury St. Edmunds, Suffolk, IP31 2RU

Cheap and easy


In this circuit, an LED is used to indicate, by its brightness and rate of flashing, a good idea of the terminal voltage. However, there is a problem. An LED needs approximately 2V before it will operate. A single cell, even when new, would therefore not be sufficient.

One way of overcoming this would be to use the cell, B1, to charge a capacitor, C1 (see figure 2a). After a short while, a voltage equal to that of the cell would appear across its ends. If the capacitor were now connected in series with the cell (figure 2b), the voltage across the pair would be about 3V (that is, there would be a doubling of the voltage) and it would then be sufficient to operate the LED. Resistor R limits the current flowing to prevent damage to the LED. The LED would give a burst of light until the capacitor discharged to a voltage less than about 0.5V (that is, until the total falls below 2V). If this whole process were repeated quickly, the LED would emit a series of flashes. The repeated action could be carried out automatically. To design and construct such a circuit would not be difficult, but it would involve several components that would raise the cost above that which seemed reasonable for a device of this type.

Fortunately, there is an inexpensive ic that does the work with very few external components. It is designed to flash an LED brightly with a supply of 1.5 to 1.4V. Tests show that it will flash the LED less brightly and more slowly between 1.4V and 1.2V. At 0.9V approximately, the flashing stops altogether. This makes it ideal for the present purpose. The internal structure of this ic is fairly complex and will not be explained in detail here. However, it works in a similar way to the process shown in figure 2. A capacitor connected externally gives the voltage doubling effect; there is an internal oscillator (a pulse generator to provide the "repeating" aspect of the circuit) and this also needs a capacitor to make it work. Here, the two functions are combined so that one capacitor does both jobs. With the value specified, and with a 1.5V supply, there will be one pulse per second approximately. At 1.2V it will be much dimmer and the flash rate will be roughly once every 1.2 seconds. At 1V, the LED will be very dim and it will flash every 1.5 seconds approximately.

How it works

Figure 3 shows the circuit of the Battery Quick-Check. IC1 is the integrated circuit LED flasher. C1 (referred to above) is connected to pins 1 and 8 on one hand and pin 2 on the other. The LED is connected between pin 6 (anode) and pins 1 and 8 (cathode). Note that no conventional series resistor is

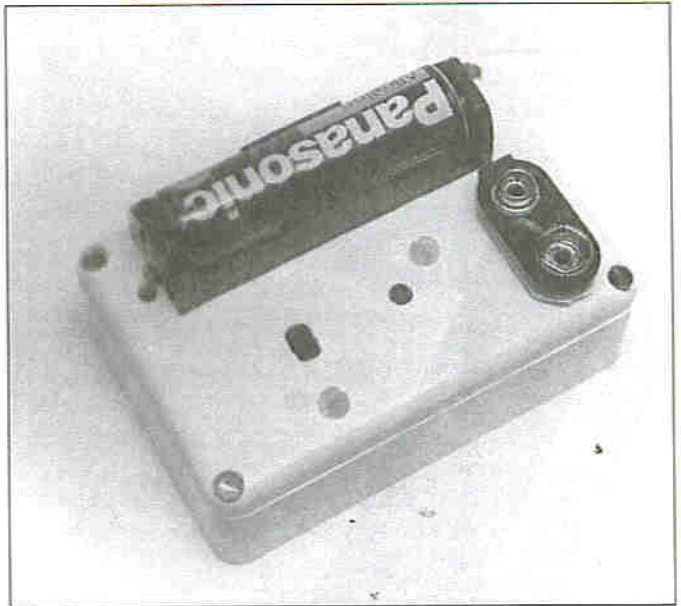

needed for the LED, because current control takes place on the chip. The nominal 1.5V input is made to pin 5. The two-way switch, S1, selects between the 1.5V cell or 9V battery to be tested. For the 9V battery, the voltage will need to be scaled down to make it appear like a 1.5V supply to the circuit so that the ic will respond correctly.

For the 1.5V cell, R3 is connected directly across its terminals, and provides the load. With the value specified, and with the battery in average condition, the current drain will be about 100mA on average. It will be somewhat higher with a new battery and less when it is nearly flat. When a 9V battery is being tested, resistors R1 and R2 connected in series provide the load. By using comparatively low values, there will be a moderate current flowing through the pair - some 40mA - with a battery in average condition. This is a suitable load for the PP3 type. The resistors also form a potential divider which scales down the voltage. The value of R1 is five times greater than R2. The effect is that the voltage appearing across R2 is one sixth of that across the pair (since the resistance of R2 is one sixth of the total). Thus, when the "9V" battery is connected across R1 and R2 a nominal 1.5V appears across resistor R2. The result is then applied to IC1 pin 5 via the "9V" switch contacts.

(Figure 3b is a little extra for experimenters from the Office - configuring the circuit this way means that no switch is necessary - but you will have to adapt the pcb layout, and test to make sure the circuit still works as the author describes it.)



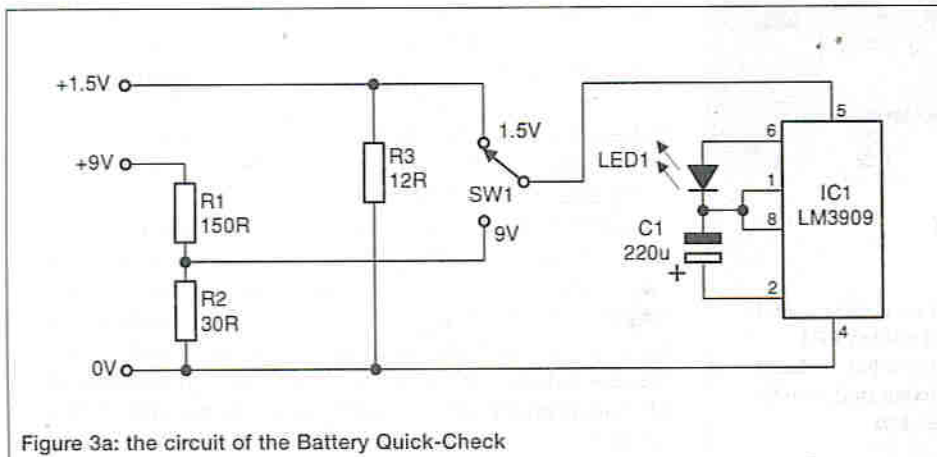


Figure 3b: experimenter's circuit: adding an extra resistor to the potential divider chain is a way of removing the need for a switch

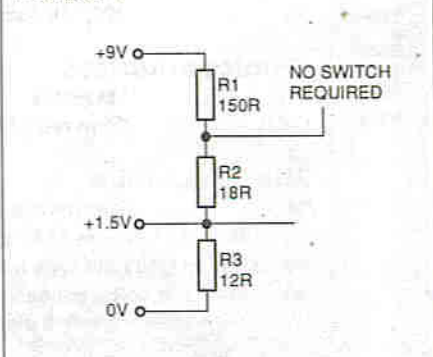

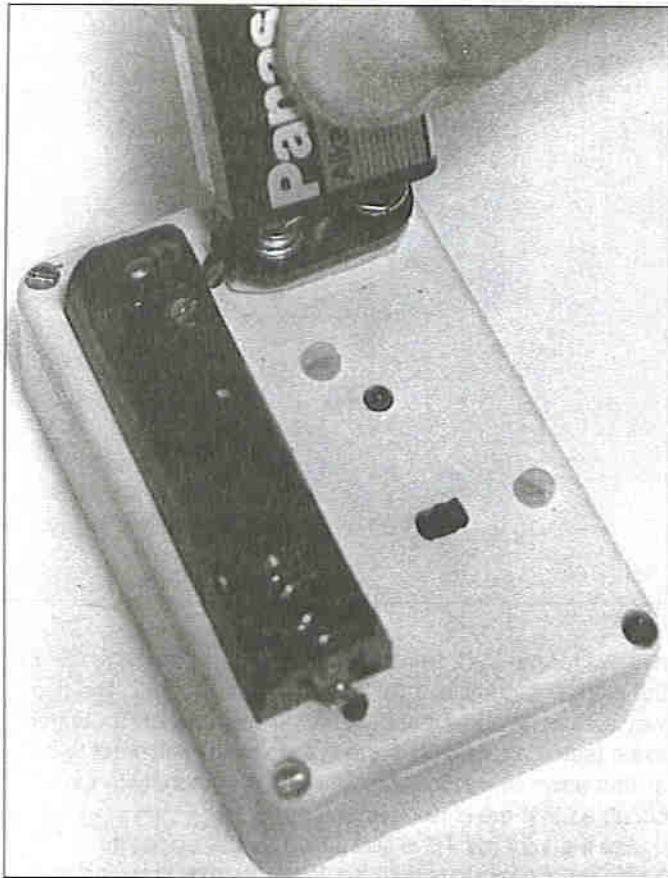

Construction

Figure 4 shows the topside pcb layout of the circuit. Drill the two mounting holes, and solder S1 in position. Use the minimum length of tags pushed through the holes (about 1mm) to make good soldered joints - do not push the body right down on to the surface of the pcb. The switch should stand clear of the pcb by about 2mm. Solder the ic socket in place, and then the other components, noting the polarity of the capacitor. Bend the capacitor's end leads so that it flat against the pcb. Solder the LED so that it stands with its tip about 12mm above the circuit panel - the slightly shorter end lead is the negative (k) one. Solder 10cm pieces of light-duty stranded wire to the point labelled "+1.5V" and one of the "0V" pads.

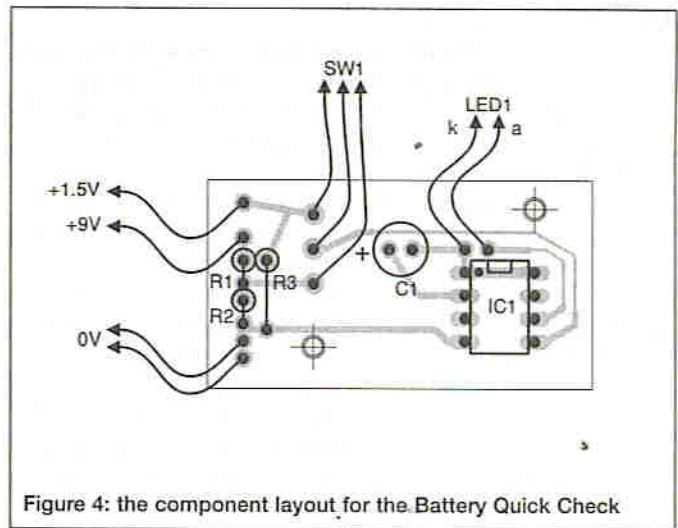


Figure 4: the component layout for the Battery Quick Check

Carefully measure the position of the switch and LED on the pcb, and make holes in the lid to correspond. Mount the pcb temporarily, using 6mm long plastic stand-off insulators on the bolt shanks. This should allow the tang of the switch to protrude through its hole sufficiently to operate it. Check that the switch can be used easily and make any adjustments as necessary. Remove the pcb again.

Place the cell holder on the lid and mark the positions of the mounting holes. Drill these through and attach it. Drill a small hole near each end for the wires passing through the lid from the pcb. Attach the PP3-type connector using an adhesive fixing pad (the type available from stationer's shops), and make a small hole nearby for the wires. Note that the rigid type of connector with a flat surface can be attached much more securely than the soft variety. Pass the connecting wires through the hole. Solder the red and black to the "+9V" and unused "0V" pad respectively on the circuit panel. Attach the pcb. Pass the 1.5V cell wires already soldered to the pcb through their holes and solder them to the cell holder tags taking care over the polarity. All the wires may be grouped together and held neatly using small cable ties.

Testing

Testing is simply a matter of checking for correct operation. Find a few "AA" cells in various states from new to practically "flat". Set the switch to "1.5V" and place them one by one in the holder taking care to put them in the right way round. With a fresh cell, the LED should flash brightly at about once per second. Compare the effect of cells in poor condition. It should be found easy to distinguish between them. Set the switch to "9V" and conduct a similar test using some PP3 batteries. If all is well, the unit may be put into service. Note that a PP3 battery should be simply *touched* on the connector (see photograph). Engaging it properly will probably detach the fixing pad when it is removed.

When making a test, observe the LED over a period of ten seconds or so. This will distinguish between batteries which really are in good condition and those which have simply "picked up" temporarily - this often happens when a battery has been left standing for a while. However, do not leave a battery connected for longer than necessary, as it is still being drained by the load resistor in the unit while it is on test.

PARTS LIST

Resistors

All 0.6W 1%

R1	150R
R2	30R
R3	12R

Capacitor

C1	220 μ 6V radial electrolytic
----	----------------------------------

Semiconductors

IC1	LM3909N
LED1	3mm red LED

Miscellaneous


S1	Sub-miniature spdt slide switch
8-pin dil socket. Single "AA" cell holder, PP3 battery snap (the rigid type having a flat surface). Small nuts and bolts, adhesive fixing pad, plastic stand-off insulators, small plastic box.	

PROTEUS

For DOS and Windows 3.1, 95 & NT

The Complete Electronics Design System - Now With RIP-UP & RETRY!

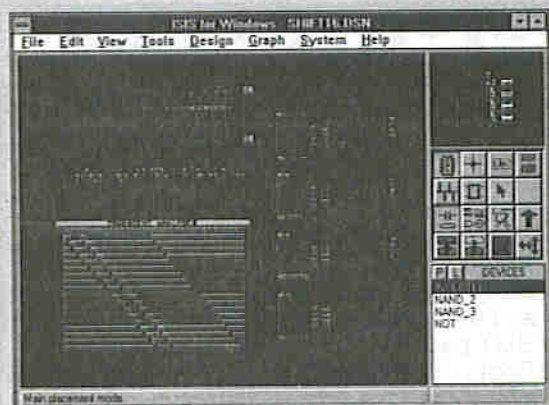NEW LOW PRICE OPTIONS AVAILABLE
Level 1 (500 pins) from £250
Level 2 (1000 pins) from £495
Level 3 (unlimited) from £995




Schematic Capture

- Easy to Use Graphical Interface under both DOS and Windows.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and



Simulation

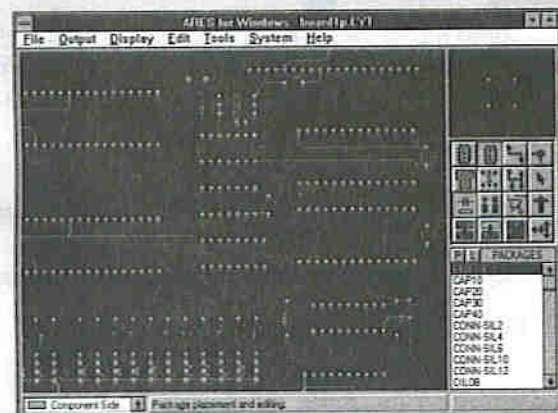- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



PCB Design

- 32 bit high resolution database.
- Multi-Layer and SMT support.
- Full DRC and Connectivity Checking.
- RIP-UP & RETRY Autorouter.
- Shape based gridless power planes.
- Output to printers, plotters, Postscript, Gerber, DXF and clipboard.
- Gerber and DXF Import capability.

labcenter
Electronics

Call now for your free demo disk
or ask about the full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857.
53-55 Main St, Grassington. BD23 5AA.

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.


EMAIL: info@labcenter.co.uk
WWW: <http://www.labcenter.co.uk>

PCB Designer

For Windows 3.1, '95 or NT



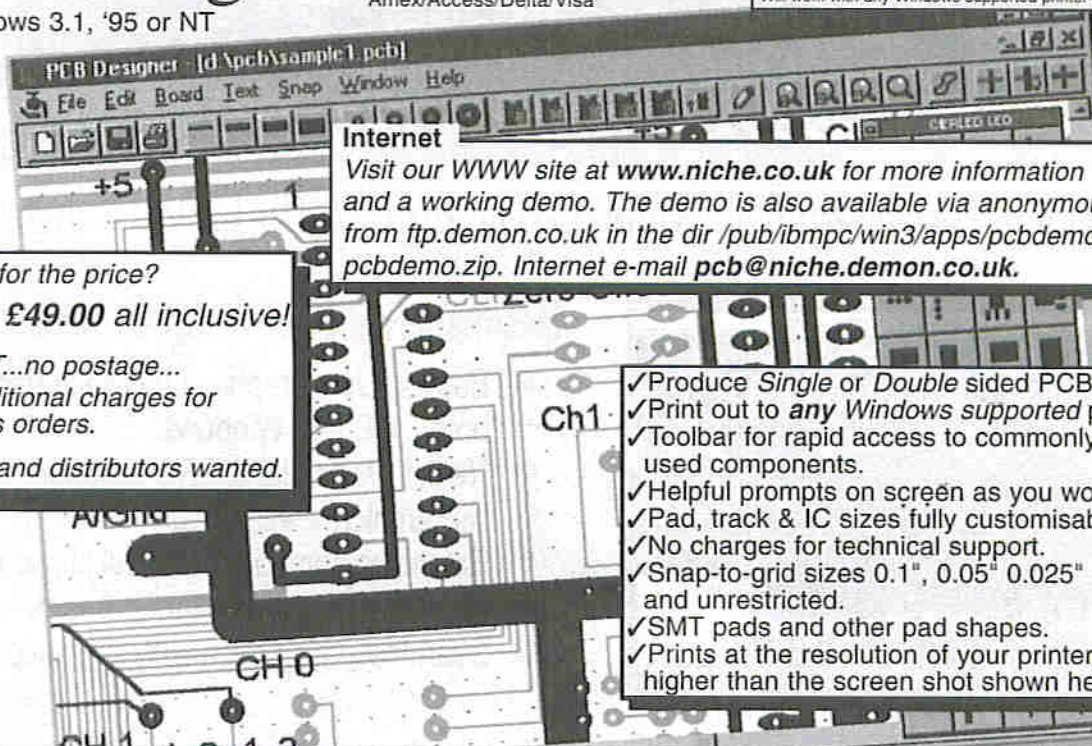Runs on any PC running Windows 3.1, Windows 95 or Windows NT with a minimum 2MB RAM
Will work with any Windows supported printer and monitor



Looking for the price?

It's just **£49.00** all inclusive!

...no VAT...no postage...

...no additional charges for overseas orders.

Dealers and distributors wanted.

Internet

Visit our WWW site at www.niche.co.uk for more information and a working demo. The demo is also available via anonymous FTP from <ftp:demon.co.uk> in the dir /pub/ibmpc/win3/apps/pcbdemo/ as [pcbdemo.zip](#). Internet e-mail pcb@niche.demon.co.uk.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to-grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Prints at the resolution of your printer, much higher than the screen shot shown here.

Niche Software (UK)

12 Short Hedges Close, Northleach, Cheltenham GL54 3PD Phone (01432) 355 414

Available in South Africa from JANCA Enterprises, PO Box 32131, 9317 Fichardtpark at R299,00

SEETRAX CAE RANGER PCB DESIGN

WITH COOPER & CHYAN AUTOROUTER

RANGER2 + SPECCTRA £400.00

RANGER & SPECCTRA AUTOROUTER
Together giving the most cost effective PCB design system on the market TODAY!
SEETRAX'S ease of use combined with COOPER & CHYAN'S renowned gridless autorouter, at an outstanding price.

R2 Outputs: 8/9 & 24 pin printers, HP Desk & Laser Jet, Cannon Bubble Jet, HP-GL, Gerber, NC Drill, AutoCAD DXF
Demo Disk available at £5.00 +VAT

RANGER2 £150

Upto 8 pages of schematic linked to artwork
Gate & pin swapping - automatic back annotation
Copper flood fill, Power planes, Track necking, Curved tracks, Clearance checking, Simultaneous multi-layer auto-router

RANGER2 UTILITIES £250

COOPER & CHYAN SPECCTRA auto-router (SPI)
Gerber-in Viewer, AutoCAD DXF in & out

UPGRADE YOUR PCB PACKAGE TO RANGER2 £60



TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 0SG
Call 01705 591037 or Fax 01705 599036 + VAT & P.P

All Trademarks Acknowledged

REVIEW

Electronics Principles from EPT Educational Software has been around for several years, gradually expanding and being updated in response feedback from users, particularly teachers. The current version, V3.0 for Windows on the PC, appeared for the first time in 1996. (The DOS version 2.1 is still available.) Installation into Windows should be straightforward so long as other applications are closed down first, but if there is any problem, EPT will give telephone support, always an advantage of the smaller independent company.

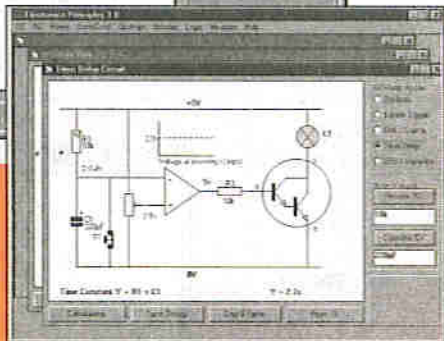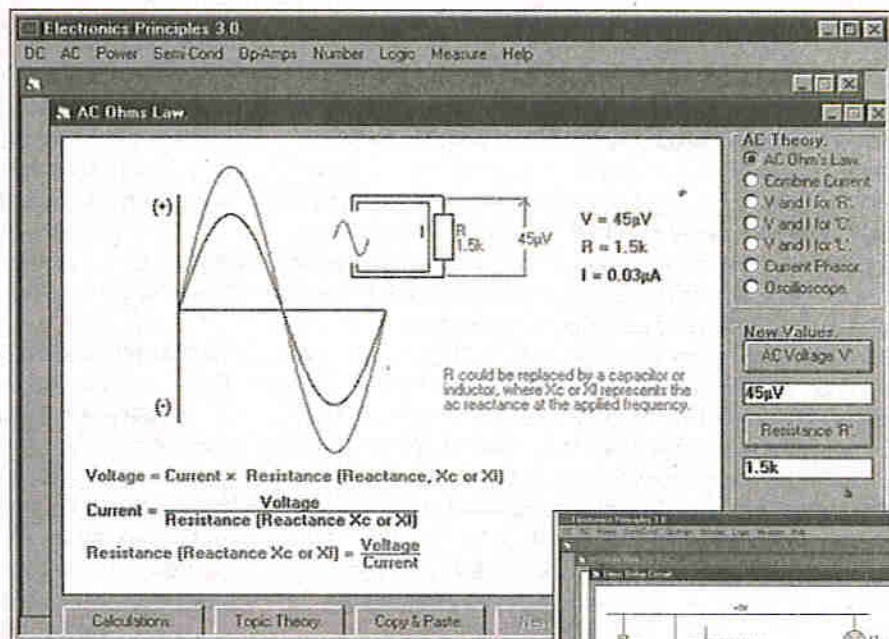

Electronics Principles 3.0

For Windows 3.1, '95 or NT

As the name suggests, *Electronics Principles* concentrates on explaining and demonstrating principles, in a modular form, rather than specific advice about building circuits. Starting with the atomic structure of many of the materials used in electronics (carbon, silicon, copper, germanium), it explains the relationship between the structure and the function of the material, and works through a variety of components and demonstration circuits up to the basic circuits of a Wheatstone bridge and an analogue multimeter. Progress is quite literally from top to bottom and left to right through the pull-down Windows menus.

The current version has 284 topics in 64 windows, many of which can be opened at the same time so that the user can switch between them quickly. If too many windows are open, users may encounter resource low warnings - but as there are only so many topics that a serious student can work with at one time, this may be an advantage rather than a restriction, by providing a motivation to be organised.

Principled

The major attraction of *Electronics Principles* is the demonstration circuits into which you can enter any values, and in most cases see how these affect the outcome of the calculation directly on the circuit diagram, while others have a

calculations box that must be opened separately after the component values have been changed. The actions performed under the screens are adjusted to the subject being demonstrated.

Here is a quick round-up of the Menu headings and some of the topics under them: DC, AC, Power, Semiconductors, Op-Amps, Number, Logic, Measure, Help - topics covered include Ohm's Law, power supplied, transistor configurations, sum and difference amplifiers, complex numbers and logic interfacing.

All the screens have the important details picked out in different colours, which has the effect of drawing the user's eye to the important areas. The colours also provide a cross-reference with tables on the screen - for instance, in the Voltage Divider screen, all values relating to V_{in} and V_{out} are in brown, all values relating to I are in blue, and all values relating to R are in green. The colours are not universal to the whole program, but this is not necessary, and there is enough consistency to be helpful.

The Topic Theory screens, and later in the program the Calculations screens, must be opened separately from the interactive circuit screens, and although this does allow operation from the minimum 8.5 x 6 in window, this is not a great advantage (see below) whereas if everything was displayed on one screen, the window could then be resized

just to show the interactive area if desired. Also, returning to the interactive buttons automatically switches off the Calculation and Topic Theory screens, which I found rather annoying, as the Calculation screen is often the primary display of the changes.

Some circuits - for instance the Timer Delay, in the Op-amp Applications section under the Op-Amps menu - have a "switch" button that runs a waveform display of the voltage at the inverting input when it is operated, plus a numerical display of the changes as they take place. Some circuits may compel you to pay particular attention. For instance, the Schmitt Trigger (under the same menu) only accepts changes up to 12 volts. This should be self-evident from the +12V rail, but if you enter a higher number you do not get an error message - the screen simply sits and waits unblinkingly for you to work out what you have done wrong. The Calculation and Topic Theory screens switch themselves off once you have begun to work with the New Value boxes, as previously remarked, so there are no clues there unless you manually switch them on again, and again you must think through the implications of what they are telling you.

Buttons

Other examples of the variety of screen displays are the windows showing the different logic gates, which have "Input A" and "Input B"

buttons that change the logic levels back and forth within the circuit, as well as an interactive truth table alongside that also displays the changes. Some screen do not have user-definable values, but simply display changes for a series of set values when the right button is pushed - perhaps accompanied by a diagram of a buzzer sounding, switches operating or a relay opening and closing. The only individual chip demonstrated is the 555 timer, "probably the most useful chip available to the hobbyist", according to the Topic Theory, shown in three separate screens.

In terms of versatility and availability, the 555 and its family are indeed old friends, although this does reinforce the fact that EP 3.0 is aimed at a basic level, rather than industry training. One helpful idea is the Resistor Value Test screen under the DC menu, where random four-band patterns are produced and you must work out the value from the colour key given.

I would have liked it if there was some indication which main menu topic each window was operating under - sometimes it took some guesswork to re-locate a window that had been closed among the menu sub-topics if I was not paying attention to which aspect of the demonstration I was supposed to be studying. But I find that this is a shortcoming with many Windows programs, although it would not be difficult to rectify.

As it is designed to be self-explanatory, *Electronics Principles* comes with very little paperwork other than the loading instructions, so you must get used to how it works by trying it out. A minor vexation is that to enter the new values for any screen, you must click on a "New Values" button, and then move to a completely separate box that opens up to type in your values and Enter them. This may be partly for reasons of space in the box, as you may need to select, for instance, volts, microvolts, or millivolts from another menu once you have entered a basic

value. The division of the dialogue box into "actual value" and "formatted value" seems puzzling at first, but you soon get used to the program adjusting your entries to the appropriate number of decimal places and adding scientific notation. Entering simple values is quite quick as you can select from the New Values box with the mouse and the Actual Value box straight from the keyboard. But you must return to New Values for each value change you make in the circuit.

Concentration


Certainly, using the screens and boxes requires a fair amount of concentration to follow and understand everything that is there in the box, but the advantage is that it is all there, and you can change it to see how it works. The Topic Theory boxes tend to be short and to the point.

Once or twice, challenging the boxes to accept odd values, or change quickly, I found that the program got its combinations in a slight twist and refused to accept certain values, or to change the notation. I would not even bother to mention this if this were not an entry-level program, as nearly all software behaves in this way given half a chance. Good practice is to make sure you step through the instructions as intended, and give the program "time to work", and it will not let you down. Also, it is easy to reset screens "back to start" by closing and re-opening, which is not true of all software.

On opening, I found that the main Window occupied the entire screen, but if the main window is reduced using the middle top right icon, you can work with the smaller window, and resize it manually to a minimum practical display of just over 8.5 in wide by 6in deep to be useable with the control panels. In fact, as you open more windows and "cascade" them (from the Help menu) they take up more space. Non-Windows users will see that Windows users quickly become spoiled by being able to run several programs at once and moan about the window sizing! With this in mind, screens from *Electronics Principles* can be easily cut and pasted into a Windows wordprocessor for use in your own documents, which is also useful for teaching staff who wish to make up worksheets or overhead projector slides, as EPT point out.

The level, clearly indicated by the favoured 555 timer and the four-band resistor test, is hobbyist and entry-level educational rather than industrial, although the practice available from a program like this could be helpful to higher levels of study. Indeed, although EPT stress that they are aiming at the hobby market, many of the features of EP 3.0 are described as useful to teachers. EPT also produce a version 4.0 of *Electronics Principles*, which is essentially built on the same lines, but with an extended - roughly doubled - range of screens and topics, and priced at £99.95. On a sheerly practical note, EPT also recommend two low-cost paperbacks, Teach-in No 6 "Design your own circuits" by Mike Tooley (£3.45) and Teach-in No 7 "A complete electronics course" by Alan Winstanley and Keith Dye (£3.95) (Books are VAT-free. Post and packing add £1.50 each or £2.50 for both books) as useful partners to *Electronics Principles*. Software has many virtues, but well-written paperbacks are a great source of information.

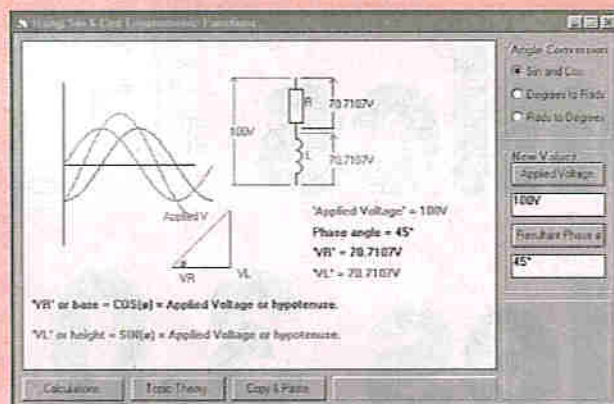EPT also market *Mathematics Principles* at £49.95 and *Electronics Toolbox* formula software at £19.95 (all prices ex VAT - please add VAT plus £2 for UK post and packing). They have a Web page at <http://www.octacon.co.uk/ext/ept/software.htm> or Tel. 01376 514008.





EQT LTD STEVENAGE

Professional Sub-Contract Manufacturing & Suppliers to the Electronics Industry

Do you have a requirement for any of the following services:

PCB Assembly (Conventional and Surface Mount)	Product Design/Consultation
Wave & Hand Soldering	Full Procurement Service
Complete Equipment Manufacture	PCB Test & "Burn in" Facilities
Device Programming from hand written sheets or PC 3 1/2" disc	Enclosure Design & Manufacture
Cable Harness Assembly/loom Manufacture	PCB Artwork Manufacture
Card Cage and Module Wiring	Circuits Drawn Professionally
Full Inspection	Kit Procurement & Supply
	Component Sales
	Refurbishment a speciality
	Top Quality Work at Reasonable Rates

Phone Steve on (01438) 360406 or fax details of your requirements to us on (01438) 352742

EQT LTD, Cromer House, Caxton way, STEVENAGE, HERTS, SG1 2DF

SERVICE MANUALS & Technical Books

Available for most equipment, any make, age or model.

Return the coupon for your **FREE** catalogue

MAURITRON TECHNICAL SERVICES (ETI)

8 Cherry Tree Road, Chinnor, Oxon, OX9 4QY.

Tel: 01844-351694, Fax: 01844 352554 email: mauritron @ dial.pipex.com
Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps, or £4.11 inc. vat for the complete Service Manuals Index on PC Disc plus catalogue.

NAME _____

ADDRESS _____

POSTCODE _____

Photocopy this coupon if you do not wish to cut the magazine

£12.00

Build your own computer

- Features: - 16 Digital I/O's
- 12 Analog inputs
- 16 Timers
- 2 High speed counters 2.5kHz
- Direct LCD control
- RS232 Serial interface
- I²C bus
- One wire bus (touch memory)

Contact: Diamond Chip

Tel: +27 12 803 6287

Fax: +27 12 803 4350

E-mail: stefan@dchip.com

Internet: <http://www.dchip.com>

Free BASIC compiler and circuit diagram



Developers kits available

excl. postage & tax

Laser Pointers

Wavelength 660-680 nm.

Max Output < 3 mW.

Laser Range up to 200 meters.

Uses two AAA batteries (supplied).

Ideal for demonstrations and lecturing.

Only £28
inc. VAT & postage

Also CCD Camera Modules;
b/w Standard, low lux & pinhole, £65
b/w Standard with sound, £70
Colour from £180



Nonuts Ltd.

2 Chase Cottages,
New Road, Aldham,
Essex CO6 3QT Tel. & Fax 01206 213322

Purveyors of Quality
Electronic Things at
Very Friendly Prices

Printed Circuits in Minutes Direct from LaserPrint!

8 1/2" x 11"

* Or Photocopy

**Use standard

household iron

or P-n-P Press.



1. LaserPrint*

2. Press On**

3. Peel Off

4. Etch

Use Standard Copper Clad Board

5 Sheets £12.50, 10 Sheets £25.00 + VAT. Add £2.50 postage

Complete kits to manufacture your own PCB's from £40.00, or individual

items of material, chemicals, etchant etc.

PRESS-N-PEEL ETCHING SUPPLIES

18 Stapleton Road • Orton • Southgate


Peterborough PE2 6TD • Tel: 01733 233043

Top Value, Wide Choice, equipment from Feedback

Oscilloscopes & Hand-Held Meters available NOW!

DUAL TRACE OSCILLOSCOPE OS5020P

LCRMETER ELC-131D

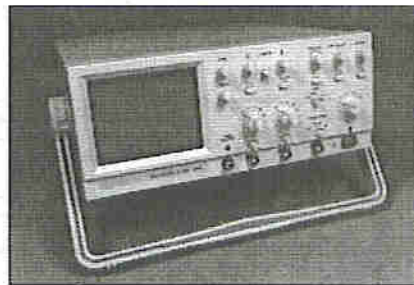

- dc to 20MHz bandwidth.
- 2 channels & Dual Trace, X-Y mode.
- 6" rectangular CRT with internal graticule.
- High sensitivity triggering.
- Sweep magnification, x10 (20ns/div).
- ALT triggering.
- TV sync separator circuit for stable TV signal observation.
- CE mark: EMC (Electromagnetic Compatibility, LVD (Low Voltage Directive).

£299 inc. probes + VAT

- Dual display of L, C or R and D/Q.
- 10,000 counts resolution.
- 0.3% basic accuracy.
- 120Hz & 1kHz test frequency.
- Full auto-ranging or manual ranging.
- 10Ω-10MΩ • 1nF-10mF.
- 1mH to 10,000H.

£137 + VAT

Feedback Park Road, Crowborough, E.Sussex, TN6 2QR.
Telephone: 01892 653322, Fax: 01892 663719,
Feedback Instruments Limited E Mail: feedback@fdbk.demon.co.uk

WANTED TOP PRICES PAID

For all your Test Equipment. Receivers,
Transmitters etc.

Factory Clearance, Prompt Service and Payment.

We buy and sell worldwide.


HTB ELEKTRONIK

Alter Apeler Weg 5


27619 Schiffdorf, Germany

Tel: 0049 4706 7044 Fax: 0049 4706 7049

FOILS FOR THIS ISSUE

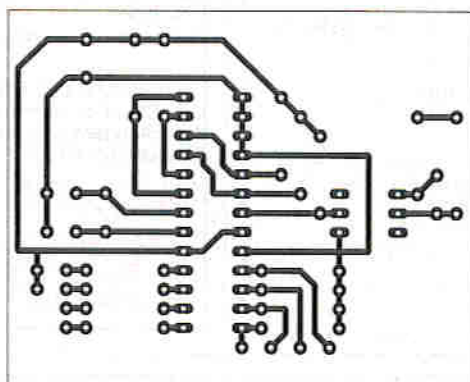

VOICE HARMONISER - MIDI INTERFACE

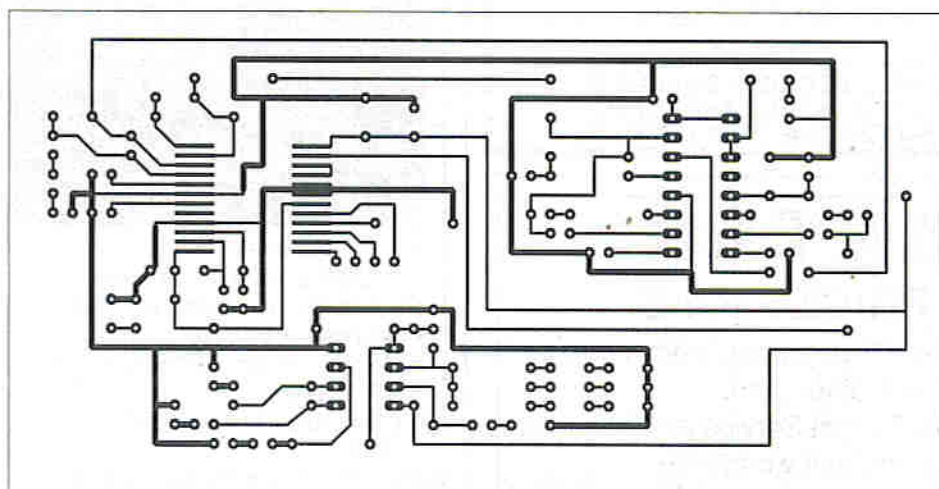

VOICE HARMONISER - MAIN BOARD

TRANSISTORS

FUSES

PART	PRICE	PART	PRICE	PART	PRICE	PART	PRICE
BU105	80P	BU408D	75P	BUT18AF	80P	MJ15024	400P
BU108	100P	BU409	85P	BUT30V	1700P	MJ15025	700P
BU109	80P	BU426A	70P	BUT56A	100P	MJE13004	100P
BU110	90P	BU506DF	120P	IRF450	650P	MJE13005	60P
BU111	100P	BU508APH	80P	IRF520	150P	MJE13007	100P
BU124	60P	BU508AF	95P	IRF530	300P	MJE13009	100P
BU125	100P	BU508APH	80P	IRF540	300P	MJE15028	200P
BU126	65P	BU508D	90P	IRF610	150P	MJE15029	200P
BU133	125P	BU508DF	115P	IRF630	150P	MJE15030	250P
BU137	150P	BU508DR	130P	IRF730	175P	MJE15031	400P
BU180	100P	BU508V	110P	IRF740	400P	MJE18004	125P
BU184	100P	BU508VF	100P	IRF740	400P	OC28	350P
BU204	65P	BU801	70P	IRF820	150P	OC29	250P
BU205	70P	BU806	70P	IRF830	225P	OC35	350P
BU206	100P	BU807	60P	IRF840	200P	OC36	250P
BU207	150P	BU2508A	130P	IRF9530	400P	S2000A3	175P
BU208	70P	BU2508AAF	130P	IRF9540	300P	S2000AF	175P
BU208A	75P	BU2508D	130P	IRF9610	200P	S2055A	175P
BU208AT	200P	BU2508DF	150P	IRF9620	225P	S2055AF	200P
BU208D	130P	BU2520AF	225P	IRF9630	325P	2N3053	18P
BU209	90P	BU2520DF	225P	IRF9640	375P	2N3054	40P
BU225	120P	BU2525AF	325P	IRFBC30	200P	2N3055	38P
BU226	120P	BUH315	200P	IRFC40	400P	2N3055H	50P
BU312	90P	BUH515	200P	MJ2501	100P	2N3440	45P
BU325	55P	BUH517	275P	MJ2955	55P	2N3441	175P
BU326A	75P	BUH715	425P	MJ15003	250P	2N3442	85P
BU406	60P	BUT11AF	55P	MJ15004	300P	2N3771	85P
BU406D	85P	BUT12	80P	MJ15015	250P	2N3772	90P
BU407	55P	BUT13	310P	MJ15016	350P	2N3773	100P
BU407D	75P	BUT18	80P	MJ15022	250P		
BU408	60P			MJ15023	400P		

CURRENT RATING	TIME LAG (20mm)		QUICK BLOW (20mm)	
	ORDER CODE	PRICE	ORDER CODE	PRICE
100mA	FUSE36	75P	FUSE37	60P
160mA	FUSE01	75P	FUSE17	60P
250mA	FUSE02	75P	FUSE18	60P
315mA	FUSE 03	75P	FUSE19	60P
400mA	FUSE04	75P	FUSE20	60P
500mA	FUSE05	75P	FUSE21	60P
630mA	FUSE06	75P	FUSE22	60P
800mA	FUSE07	60P	FUSE23	60P
1A	FUSE08	60P	FUSE24	60P
1.25A	FUSE09	60P	FUSE25	60P
1.6A	FUSE10	60P	FUSE26	60P
2A	FUSE11	50P	FUSE27	60P
2.5A	FUSE12	50P	FUSE28	60P
3.15A	FUSE13	55P	FUSE29	50P
4A	FUSE14	55P	FUSE30	50P
5A	FUSE15	60P	FUSE31	50P
6.3A	FUSE16	60P	FUSE32	50P

CERAMIC PLUG TOP

CURRENT RATING	ORDER CODE	PRICE
3A	FUSE33	100P
5A	FUSE34	100P
13A	FUSE35	100P

20mm CERAMIC TIME LAG

CURRENT RATING	ORDER CODE	PRICE
6.3A	FUSE38	100P
8A	FUSE39	100P
10A	FUSE40	100P
3.15A	FUSE41	85P
4A	FUSE42	85P
5A	FUSE43	85P

32mm CERAMIC SLOW BLOW

CURRENT RATING	ORDER CODE	PRICE
8A	FUSE44	185P
10A	FUSE45	185P
15A	FUSE46	185P
20A	FUSE47	210P

38mm CERAMIC TIME LAG

CURRENT RATING	ORDER CODE	PRICE
10A	FUSE48	825P

****ALL THE ABOVE PRICES ARE ARE FOR PACKS OF 10 FUSES****

NB. ALL FUSES ARE MADE IN THE UK AND FULLY MEET BS4265 & BS1362 SAFETY STANDARDS AND SHOULD NOT BE COMPARED WITH CHEAP IMPORTED TYPES.

SATELLITE PSU REPAIR KITS

Experience shows that 50% of all receiver power supplies 'bounce' unless the correct precautionary measures are taken when being serviced. A kit of all the recommended parts is supplied for the most popular models, which when fitted should overcome this.

MAKE & MODELS	ORDER CODE	PRICE
PACE PRD800, PRD900	SATPSU1	650P
PACE SS900, 9200, 9010, 9210, 9020, 9220	SATPSU2	650P
AMSTRAD SRD510, SRD520	SATPSU3	650P
AMSTRAD SRD500	SATPSU4	650P
AMSTRAD SRX340, SRX345, SRX350	SATPSU5	650P
PACE D100/150	SATPSU6	650P
CHURCHILL D2MAC	SATPSU7	650P
PACE MSS100	SATPSU8	730P
PACE MSS200/300 APPOLLO	SATPSU9	650P
PACE MSS500/1000	SATPSU10	1230P
FERGUSON SRD4	SATPSU11	835P
ECHOSTAR SR5500	SATPSU12	1735P
ECHOSTAR 6500/7700/8700	SARPSU13	3125P
AMSTRAD SRD600	SATPSU14	3125P
MIMTEC (Sorensen)	SATPSU15	775P
AMSTRAD SRD700/SR950/SRX100/302		
SRX501/502/1002/2001/SRD2000 SAT250	SATPSU16	730P

PACE 9000 SWITCH MODE TRANSFORMER
ORDER CODE: PACE9000 PRICE 800p

SERVICE AIDS

DESCRIPTION	VOLUME	CODE	PRICE
VIDEO HEAD CLEANER	75 ML	SP01	160P
VIDEO HEAD CLEANER	200 ML	SP27	250P
SWITCH CLEANER	178 ML	SP02	170P
SUPER 40	400 ML	SP15	250P
SILICONE GEASE	200 ML	SP03	210P
FREEZE IT	170 ML	SP04	300P
FREEZE IT	400 ML	SP16	600P
FOAM CLEANER	400 ML	SP05	180P
ANTI STATIC	150 ML	SP06	190P
AEROKLEANE	200 ML	SP07	220P
AERO DUSTER	150 ML	SP08	310P
AERO DUSTER	400 ML	SP17	550P
PLASTIC SEAL	200 ML	SP09	250P
GLASS CLEANER	250 ML	SP10	160P
COLDKLENE	250 ML	SP13	230P
EXCEL POLISH 80	250 ML	SP18	150P
ADHESIVE 120	400 ML	SP19	190P
LABEL REMOVER 130	200 ML	SP20	240P
REFURB 140	400ML	SP21	240P
TUBE SILICON GREASE	50 GRAMMES	SP11	220P
TUBE SILICON SEALANT WHITE	75ML	SP22	280P
TUBE SILICON SEALANT CLEAR	75 ML	SP23	280P
TUBE HEAT SINK COMPOUND	25 GRAMMES	SP12	150P
DRIVE CLEANER	200ML	SP24	150P
SCREEN CLEANER	200 ML	SP25	150P
COMPUTER CARE KIT		SP26	2100P
ANTI STATIC FOAM CLEANER	400 ML	SP28	175P
AIR DUSTER	400 ML	SP29	450P

ALL THE ABOVE ITEMS ARE MANUFACTURED BY SERVISOL

IF YOU PURCHASE MORE THAN ONE SERVISOL PRODUCT POSTAGE & PACKAGE WILL BE CHARGED AS FOLLOWS: 300p FOR 5 CANS 450p FOR MORE THAN 5 CANS

GRANDATA LTD

K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE,
SOUTHWAY, WEMBLY, MIDDLESEX, ENGLAND HA9 0HB
Telephone: 0181-900 2329 Fax: 0181-903 6126
OPEN Monday to Saturday.
Times: Mon-Fri 9.00-5.30 Sat 9.00-2.00

SOLDERING ACCESSORIES

ANTEX SOLDERING IRONS

DESCRIPTION	CODE	PRICE
25 WATT 240 VAC (XS25W 240V)	S101	900P
15 WATT 240 VAC (XS 15W 240V)	S102	900P
25 WATT SPARE ELEMENT	S103	450p
15 WATT SPARE ELEMENT	S104	450p

SOLDERING STAND & SPONGES

DESCRIPTION	CODE	PRICE
SOLDERING STAND (MADE BY ANTEX)	S108	350p
SPARE SPONGE	S109	55p

SOLDER

DESCRIPTION	CODE	PRICE
18 SWG 500 GRAMMES	S110	500P
20 SWG 500 GRAMMES	S111	650P
22 SWG 500 GRAMMES	S112	700P

DESOLDERING AIDS

DESCRIPTION	CODE	PRICE
SOLDER MOP STANDAR GUAGE 1.2mm x 1.5 METRE	S107	80P
SOLDER MOP 1.2mm x 10 METRE	S113	400P
DESOLDERING PUMP	S105	320P
SPARE NOZZLE	S106	60P

8 way PREPROGRAMMED Universal remote Control

A single remote control to operate Televisions, Videos and Satellite Receivers. Plus Auxiliary Options!!
* Replaces up to 8 remotes with one
* Simple 4 digit setup routine
* Controls 1000's of models
* Teletext functions with Fastext
* Clear (large key) layout
* Code Search Facility
* Stylish and easy to operate
* Replace broken or lost remotes
* Original Remote not required

Order Code: 8 WAY Price: 1450P + VAT

8 way PREPROGRAMMED Universal remote Control

The Optimum 8 way universal remote control preprogrammed to operate up to 8 other remote controls for Televisions, Videos and Satellite Receivers. Plus Auxiliary Options!!
* Pre-programmed with learning capability
* Replaces up to 8 remotes with one
* Jog/Shuttle thumb control
* Illuminated key pad
* Clear key layout
* Easy access secondary keypad
* Teletext & Fast text function.
* Stylish and easy to operate
* Replace broken or lost remotes
* Original Remote not required
* Freephone Helpline (UK Only)

Order Code: OPTIMUM 8 Price: 2100P + VAT

PLEASE PHONE US FOR TYPE NOT LISTED HERE AS WE ARE HOLDING 30,000 ITEMS AND QUOTATIONS ARE GIVEN FOR LARGE QUANTITIES

Please send £1 P&P and VAT at 17.5%. Govt. Colleges, etc. Orders accepted. Please allow 7 days for delivery. Prices quoted are subject to stock availability and may be changed without notice.

TV and video parts sold as replacement parts.


Access & Visa Card accepted

WE STOCK TV AND VIDEO SPARES, JAPANESE TRANSISTORS AND TDA SERIES. PLEASE RING US FOR FURTHER INFORMATION.




TOMORROW'S TECHNOLOGY TODAY


FOILS FOR THIS ISSUE

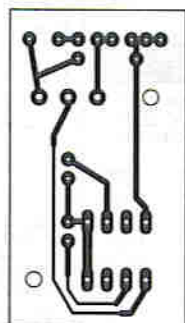

BATTERY QUICK-CHECK

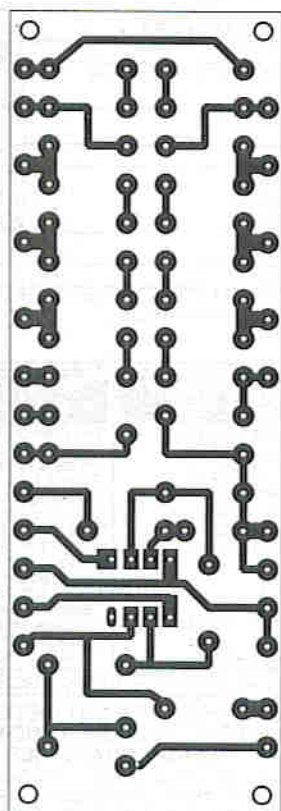


HIGH IMPEDANCE MULTIMETER AMPLIFIER

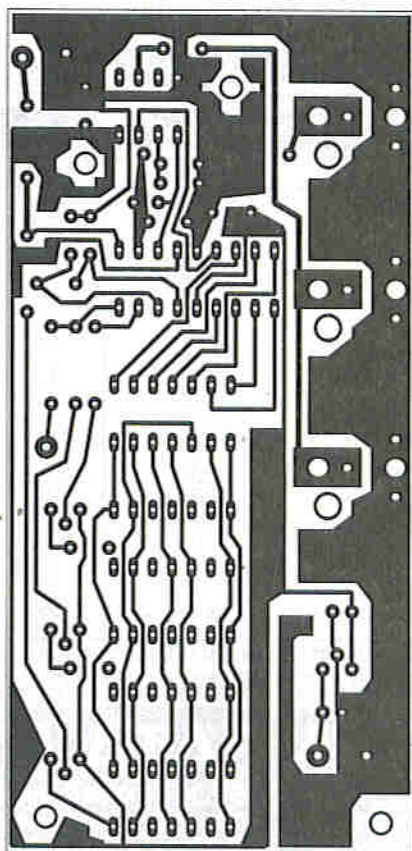

VIDEO LINE TRIGGER



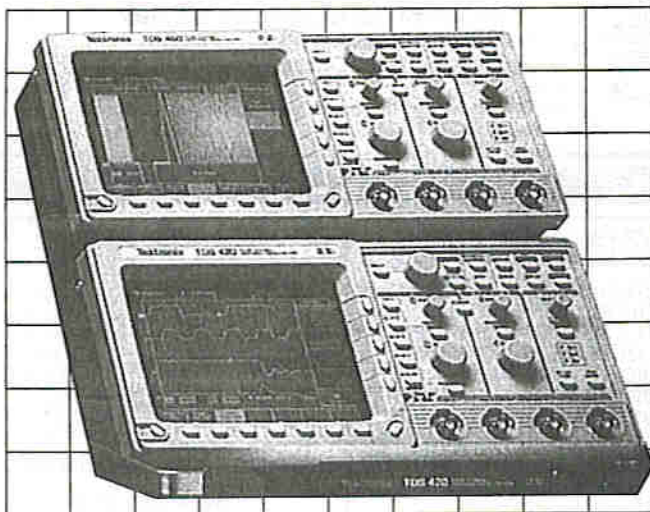SUPPLIER OF QUALITY USED TEST INSTRUMENTS



CONTACT

Cooke International


ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0HD U.K.

Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CATALOGUE AVAILABLE



OPERATING & SERVICE MANUALS

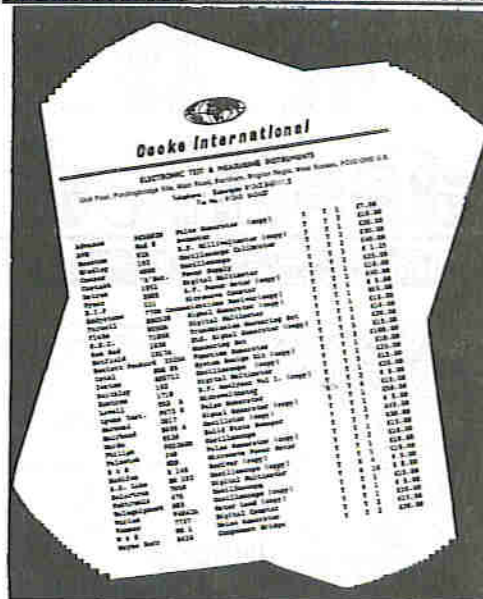

CONTACT

Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham,
Bognor Regis, West Sussex, PO22 0HD U.K.

Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

CATALOGUE NOW ALSO AVAILABLE ON DISK

TRANSMITTERS

NEW

Fully comprehensive guide to building and using short/medium range radio transmitters and receivers. Includes detailed and practical information on all aspects of construction, from simple FM room transmitters to more sophisticated and powerful audio and data transceivers.



Manual includes:

- **AM, FM and UHF Transmitters** from micro power up to 3 Watts. Covers simple 'bugs' as well as circuits operating on 27MHz and 418MHz etc.
- **TRACKING AND SIGNALLING.** How to build micro circuits for finding animals, cars etc.
- **CRYSTAL CONTROLLED TRANSMITTERS.** High stability circuits.
- **RADIO PAGER AND RADIO CONTROL.** How to build coded radio keys, multi-channel remote controls, radio alarms etc.
- **RECEIVER CIRCUITS.** Wide range of receiver projects for building high security audio links and transceivers.
- **EXTENSIVE** assembly information. Includes sections on construction, testing, mics, aerials, coils and miniaturisation.

Over 100 detailed PCB, strip-board and point to point designs. Manual comes with **FREE** micro transmitter PCB.

(Some of the circuits included in the manual may not be used legally in the UK).

Make cheques/POs payable to
JCG ELECTRONICS

P.O. Box 73, York YO2 1YJ

Wide range of Audio/Radio kits available.

Send stamp for list. Mail order only

**FREE
P.C.B.**

£8.95
+ £1 p&p

ADVERTISERS INDEX

BK ELECTRONICS	17	MILFORD INSTRUMENTS	56
BULL ELECTRICAL	6, 8	NICHE SOFTWARE	64
CMS	60	NO1 SYSTEMS	51
CHELMER VALVE	56	NO NUTS	67
COOKE INTERNATIONAL	71	PDSL	73
COLES HARDING AND CO	72	P H HAGAR	72
DIAMOND CHIP COMPUTERS	67	PARTRIDGE ELECTRONICS	72
DISPLAY ELECTRONICS	15	PLANCENTRE PUBLICATIONS	72
EPT EDUCATIONAL SOFTWARE	22	PICO TECHNOLOGY	52
EQT	67	PRESS AND PEEL	67
ESR COMPONENTS	39	PYRAMID	59
FEEDBACK INSTRUMENTS	67	QUICK ROUTE SYSTEMS (POWERWARE)	IFC
FOREST ELECTRONICS	55	RADIO TECH	43
G.C. ARNOLD	13	ROBINSON MARSHALL	IBC
GRANDATA	69	SEETRAX CAE	64
GREENWELD ELECTRONICS	59	SCIENTIFIC WIRE COMPANY	72
HTB	67	SERVICE TRADING CO	72
JJ COMPONENTS	43	STEWART OF READING	43
JPG	13	SWIFT	13, 32, 33
J+N FACTORS	72	TELNET	40
JCG	71	VAN DRAPER	60
KPL	60	VARIABLE VOLTAGE TECHNOLOGY	73
LABCENTRE	63	VERONICA FM	72
LASERTECH	60	VISIBLE SOUND	60
MAPLIN	0BC	WILSON VALVES	72

ETI Classified



Andy Forder
01442 66551

Send your requirements to:
ETI Classified Department, Nexus, Nexus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 75p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£10.50 + VAT per single column centimetre



Ring for information on series bookings/discounts.
All advertisements in this section must be pre-paid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60
OUTPUT 0-260V

Price P&P
PANEL MOUNTING

0.5kVA 2.5 amp max £33.00 £5.00 (£45.83 inc VAT)
1kVA 5 amp max £45.25 £7.00 (£51.39 inc VAT)

SHROUDED

0.5kVA 2.5 amp max £34.00 £5.00 (£47.00 inc VAT)
1kVA 5 amp max £46.25 £7.00 (£52.57 inc VAT)

2kVA 10 amp max £65.00 £8.50 (£86.36 inc VAT)
3kVA 15 amp max £86.50 £3.50 (£111.53 inc VAT)

5kVA 25 amp max £159.00 Plus Carriage & VAT
10kVA 45 amp max £309.00 Plus Carriage & VAT
15kVA 3 PHASE Star £265.00 Plus Carriage & VAT

Buy direct from the Importers. Kineston prices in the country
COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO (110-240V Auto transfer either cased with American socket and main lead of open frame type. Available for immediate delivery.

WIDE RANGE OF XENON FLASH TUBES

Write/Phone your enquiries

ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft 40 watt £14.00 (callers only) (£16.45 inc VAT)
2ft 20 watt £9.00 (callers only) (£10.58 inc VAT)

12in 8 watt £4.95 + 75p p&p (£5.50 inc VAT)
5in 5 watt £3.95 + 50p p&p (£4.24 inc VAT)
5in 4 watt £3.95 + 50p p&p (£4.24 inc VAT)

250V AC BALLAST KIT For either 5in, 9in or 12in tubes £8.05 + £1.40 p&p (£8.75 inc VAT)

The above Tubes are 3500/4000 angstrom, (350-400nm) ideal for detecting security markings, effects lighting & Chemical applications.

Other Wave Lengths of UV TUBES available for Gemological & Photo Sensitive applications. Please telephone your enquiries.

400 WATT BLACK LIGHT BLUE UV LAMP (GES Mercury Vapour lamp suitable for use with a 400W P.F. Ballast)

Only £38.00 + £4.00 p&p. (£49.35 inc VAT)

12V D.C. BILGE PUMPS

500 GPH 15h head 3 amp £19.98
1750 GPH 15h head 3 amp £34.55
Also now available 24V D.C. 1750 GPH 15h head 5 amp £35.55. All designed to be used submerged. PRICES INCLUDE P&P & VAT.

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical uses etc. Approx 10 joules. Adjustable speed £50.00 + £3.00 p&p (£52.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (£21.73 inc VAT)

SAE for further details including Hy-Light and industrial Strobe Kits.

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
TEL 0181-995 1560 FAX 0181-995 0549
ACCOUNT CUSTOMERS MIN. ORDER £10



Ample Parking Space

FAIRS

RADIO AMATEUR ELECTRONICS & COMPUTER FAIR

SUNDAY 6TH APRIL
CHELTENHAM RACECOURSE

GOLD CUP ROOM
Signposted from Junc. 11 M5
10-00am to 4-00pm

TALK IN S22 G5BK
ADMISSION £1-00
Refreshments & Ample Free Parking
Enquiries and Booking
Ian (G4FLN) AUSTIN FAIRS
TEL: 01454 633524 : 0850 389505

5kVA ISOLATION TRANSFORMER

As New Ex-equipment fully shrouded Line Noise Suppression, Ultra Isolation Transformer with terminal covers and Knock-out cable entries. Primary 120/240V Secondary 120/240V 50/60 Hz. .005 pF Capacitance. Size L.37 x W.19 x H.16cm Weight 42 Kilos. PRICE £120.00 +VAT
at warehouse. Carriage on request.

24V DC SIEMENS CONTACTOR
Type 3THS022 DB 2 x NO and 2 x NC 230V AC 10A contacts Screw or Din Rail fixing. Size H 120 x W 45 x 0.75mm. Brand New Price £7.63 incl. P&P and VAT.

240V AC WESTCOOL SOLENOIDS
TT2 Mod 1 flat. 1 Max stroke 1/4 in. Base mounting 1/2 in. stroke 5/16 in pull approx. TT6 Mod 1 Flat. 2 Max stroke 1/8 in. Front mounting 1/2 in. Front mounting 1/2 in. stroke 1/16 in pull approx. Price incl. p&p & VAT. TT2 £5.88. TT6 £6.81. SERIES 400 £7.64.

AXIAL COOLING FAN
230V AC 120mm square x 38mm x 38mm 10 watt Low Noise fan. Price £7.29 incl. P&P and VAT. Other voltages and sizes available from stock. Please telephone your enquiries.

INSTRUMENT CASE
Brand new Manuf. by Imhof L31 x H18 x 15cm deep. Removable front and rear panel for easy assembly of components. Grey finish complete with case fast. PRICE £16.45 incl. P&P & VAT 2 off £28.20 inclusive.

SEWING MACHINE MOTOR
Brand new 220/240V AC/DC SEW-TRIC 2 lead Brush Motor. Size L. 100mm x H. 70mm x W.55mm. Spindle. 1/4 in. dia x 1 in. long. £14.10 incl. P&P & VAT

GEARED MOTORS
71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation.
Price inc VAT & p&p £27.73

SOLID STATE EHT UNIT
Input 230/240V AC. Output approx 15kV. Producing 0.5mA spark. Built-in 10 sec timer. Easily modified for 20sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case.
£8.50 + £2.40 p&p (£12.81 inc VAT) NMS

EPROM ERASURE KIT
Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angstrom Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

WASHING MACHINE WATER PUMP
Brand new 240V AC, fan cooled. Can be used for a variety of purposes. Inlet 1 1/2 in. outlet 1 in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

SWC SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE
TINNED WIRE SILVER
PLATED COPPER WIRE
SOLDER EUREKA WIRE
NICKEL CHROME WIRE
BRASS WIRE LI TZ WIRE
BIFALAR WIRE MANGANIN
WIRE TEFZEL WIRE NICKEL
SAE BRINGS LIST 18 RAVEN
RD LONDON E18 1HW
FAX 0181 559 1114

£50 BT INSTRUMENT FOR ONLY £7.50

We refer to the BT insulation tester and multi-meter with which you can read insulation directly in megohms, AC volts up to 230, 4 ranges of DC volts up to 500, 3 ranges of milliohms and one 5A range and 3 ranges of resistance. These are in perfect condition, have had very little use, if any, tested and fully guaranteed. Complete with leads and probes £7.50. Order Ref 7.5P4. Carrying case which will take small tools as well, £2 extra. Postage £3 unless your order is £25 and over.
J & N Factors
Dept ETI, Pilgrim Works, Stairbridge Lane, Bolney, Sussex, RH17 5PA
Telephone: (01444) 881965



88-108MHz FM TRANSMITTERS

Professional PLL transmitter, Stereo Coder, and Compressor/Limiter kits licensable in the U.K. Also very stable VFO transmitter kits. Prices from under £10 and a 'Ready Built' service is available. Contact us for a free brochure including prices and more detailed information.

18 Victoria St, Queensbury, BRADFORD, BD13 1AR
Tel 01274 816200 Email veronica@legend.co.uk



TURN YOUR SURPLUS TRANSISTORS, ICs ETC INTO CASH immediate settlement.
We also welcome the opportunity to quote for complete factory clearance
Contact:
COLES-HARDING & CO
Unit 58, Queens Road, Wisbech, Cambs PE13 7PQ
BUYERS OF SURPLUS INVENTORY ESTABLISHED OVER 20 YEARS
Tel: 01945 584188 Fax: 01945 475216

ELECTRONIC VALVES

WILSON VALVES
(PROP JIM FISH GAMH)
Over 50,000 valves stocked, 2000 different types, vintage, military, audio, etc. Fast service. Send SAE for list VALVES WANTED FOR CASH
28 Banks Avenue, Golcar, Huddersfield, West Yorks HD7 4LZ
Tel: 01484 654650 Fax: 01484 656699

PRINTED CIRCUIT BOARDS

Try Me!
For PCB's,
One offs and low quantities.
High quality at low cost.
For details send SAE to:
33 Lennox Gardens,
Linlithgow, West Lothian.
EH49 7PZ.

PRINTED CIRCUIT BOARDS
Designed & Manufactured
● Prototype or Production Quantities
● Fast turnaround available
● PCBs Designed from circuit diagrams
● Almost all computer files accepted
Easy PC / Aries / VuTrax / Cadstar Gerber / HPGL / IDraw and many others.
● Fast international service
● Contract Assembly & Test available
TELEPHONE 01232 473533
INTERNATIONAL +44 1232 473533
agar FAX - 01232 473533
Circuits Email - agar@argonet.co.uk
36 WOODCOT AVENUE, BELFAST BT5 5JA

To advertise in the next issue of ETI please call our friendly sales team on 01442 66551

Around the Corner

T With all the concentration on software, the internet, computing power at our fingertips, CAD, CAE, simulations, networking, so on ad infinitum, one sometimes

overlooks the advances in other areas of electronics. For example, last year mosfets (metal oxide field effect transistors) with an improved structure were introduced, and they may soon reach the level of availability that hobbyists and other people who work with electronics in quantities under 10,000 units a time may be able to buy them and build them into their own designs.

The basic improvement is that the gate is buried in the channel, and current flows around it. The capacitance is increased a little, compared with the same gate area on the surface, and the ON-resistance drops by a much larger percentage.

This is significant, because one of the limitations on switching FETs fast is that the gate capacitance must be charged and discharged, which requires significant current to do quickly. In a switched mode power supply, a major part of the dissipation in the power mosfet usually occurs during the switching, because when the device is in an intermediate state its dissipation can be enormous. A moderate power offline switcher might be switching off a mosfet passing a current of 3A. When it is switched half way off, the current will not have declined much by the time that the voltage across the device reaches 200V, which means that the dissipation at this instant is 600W! Clearly you do not want that situation to continue for long.

With the improved FET topology you can switch faster for a given gate drive current and on resistance, or have lower on resistance and therefore less dissipation during conduction for the same switching speed.

Gate drive power can be significant in some circuits, such as micropower dc-to-dc

converters (as in next month's free pcb project). The battery power used in charging and discharging the mosfet gate capacitance in a low power dc-dc converter can noticeably reduce the battery life.

What you will notice on the consumer side is that your lump-in-a-lead switching power supply delivers more watts for the same size, and doesn't even get warm. You'll just have to ask the family for thicker socks next winter. And a couple of extra cups of coffee from the boss.

Another change which has happened quietly has been in television set design. In the old stone age, the IF (intermediate frequency) stages used tuned transformers to give selectivity, separate the sound subcarrier from the video, and so on. Surface acoustic wave devices have been used for this purpose for a long time, resulting in cheaper televisions (because factory adjustment was reduced), and better sound and pictures.

Modern television ics available from Philips have taken the next step - to DSP (digital signal processing). Intermediate frequency bandpass filtering, separation of sound and video, separation of colour subcarrier, all is done digitally. The only tuned circuits in sight are in the UHF tuner.

With lower cost memory, look for average-priced televisions with a frame store to do comb filtering, so that the horizontal resolution can be increased by a factor of perhaps 50% without the moire type patterns which result from crosstalk between luminance and chrominance. Then wide-screen will then not look quite so blurred.

Perhaps you remember the Challenge concerning hifi loudspeakers a few months back? Well, it looks as if the people at Nxt have gone quite a distance towards answering this one (they have been working on the project for years. You may have seen the *Tomorrow's World* feature a few weeks back). Look out for an in-depth review soon.

The Challenge - Things that electronics hasn't fixed yet

Given that Nxt have invented a flat loudspeaker, what we want now is a good flat video display with lots of resolution, with a fast update, but without hundreds of wires to carry signals to each crosspoint. Is this just StarTrek technology?

Send your suggestions to the Editor at the address on the right.

Next Month...

Volume 26 no.5 of Electronics Today International will be in your newspaper on 25th April 1997, with a FREE pcb on the cover - look out for the Little Red Reading Torch - a long-life torch for reading and walking at night, based on red LEDs ... an ingenious multi-function PIC-controlled Lottery and Games Console - plus how to interface to an LCD, and adapt the basic design for other applications ... Don't get caught in the dark - build a car-headlight switch-on warning if you are forgetful (or know someone who is) ... Are power cables an unseen danger? Douglas Clarkeson reports on the safety angle of electro-magnetic radiation around us ... on test: a new system to make your own pcbs at home ... Spiced Circuits ... all the news, and more ...



EDITORIAL

Editor **Helen Armstrong**
Editorial Assistant **Lynn Bugden**
Consultant **Andrew Armstrong**

CREATIVE

Designer **Dan Sturges**
Technical Illustration **John Puczynsk**
Photography **Gary Sinfield**

ADVERTISEMENT SALES

Advertisement Manager
Andrew Forder
Advertisement Copy Control
Marie Quilter

MANAGEMENT

Divisional Director
John Bridges
Production Manager
Mike Burns
Production Administrator
Theresa Davis
Business Manager
Stuart Cook
Marketing Manager
Jason Doran
Copy Sales Manager
David Pagendam



ISSN0142-7229

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Nexus Special Interests. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Nexus Special Interests and reproduction requires the prior written consent of the company © 1997 Nexus Special Interests. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Annual subscription (13 issues): UK £27.00 Europe £40.00 Sterling. Overseas £41.80 US Dollars Overseas \$64.00 (Air £45.00 or \$72.00) Back issues (last 12 months) £3.05 per issue if available. Older issues: photocopies of whole articles often available. Write to The Photocopy Service, Readers Services Department at the address below for details.

Published by Nexus Special Interests, Nexus House, Boundary Way, Hemel Hempstead HP2 7ST, Telephone (01442) 66551. UK newstrade distribution by Comag Magazine Marketing, Tavistock Road, West Drayton, Middlesex, UB77QE. Overseas and non-newstrade sales by Magazine Sales Department, Nexus House, Boundary Way, Hemel Hempstead, HP2 7ST, Telephone (01442) 66551. Facsimile (01442) 66998. Subscriptions by Nexus Subscription Dept, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leicestershire, LE16 9EF.

US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. For Visa/Mastercard orders in USA - Telephone (310) 375 6258 Fax (310) 375 0548. Pacific Time: 9am-5pm Weekdays, 10am-6pm Weekends. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd, Bristol.

Nexus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (01442) 66551
Fax (01442) 66998

The indispensable tool for DIY enthusiasts, hobbyists and students, amateurs and professionals in the world of electronics...

It's all in here!

It's at your local Maplin store

With more than 40 stores nationwide and many new stores on the way, there should be a Maplin store near you.

Same day despatch

Every order is processed on the day of your call. 24 hour ordering - see catalogue for details.

Free technical support

Available on all products. Call 01702 556001

New! Updated twice a year

Now it's produced in March and September, you can be sure the products are right up to date.

Only £3.45

Available at WH Smith, John Menzies or any Maplin store, or you can order your copy direct on 01702 554000 (add 50p for P&P).

If you live outside the UK send £8.45 or 21 IRCs for airmail in Europe or surface mail outside Europe; £16.00 or 37 IRCs for airmail outside Europe to: Maplin MPS, P.O. Box 777, Rayleigh, Essex, England SS6 8LU.

Over 18,000 high quality products

Everything you could want from the fascinating world of electronics, - and all in full colour.

Over £50 in discount vouchers

There's more than £50 in vouchers inside to save you even more money.

Free delivery

There's no delivery charge on orders over £30 (inclusive of VAT) or any size business account order.

MPS
MAPLIN PROFESSIONAL



THE COMPLETE
CATALOGUE FOR
ELECTRONICS

1997
March '97 - August '97

Visit our Web Site
<http://www.maplin.co.uk>



1972-1997

25 years of experience

Britain's best selling electronics catalogue is now in its 25th year. Nobody can match our experience.

Save £50+ Vouchers Inside
FREE DELIVERY*
*see terms for details

MPS
MAPLIN PROFESSIONAL

Priority Reference Code MA014