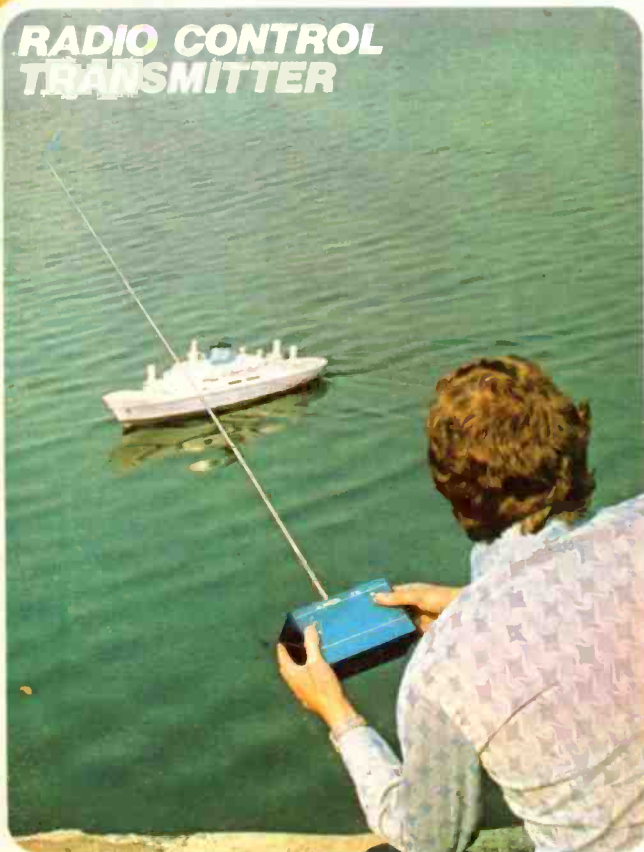


An exciting hobby.... for everyone


# everyday electronics

DEC.72  
15p

## RADIO CONTROL TRANSMITTER



## New Series DEMO CIRCUITS

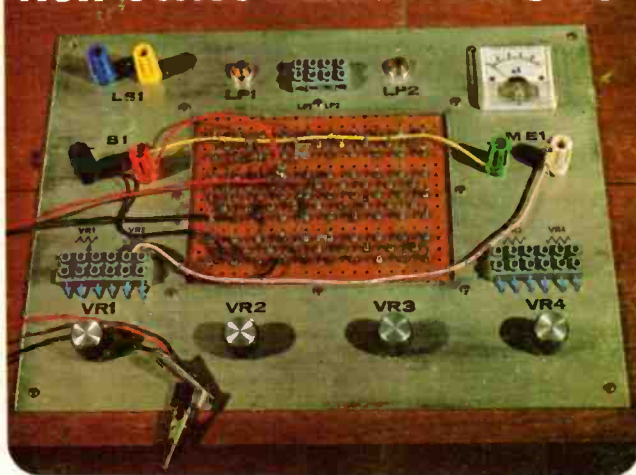

## BIT SAVER



*BETA, Pick-ups and fittings*

# ADCOLA

meet the precision  
**'INVADER' SOLDERING INSTRUMENTS**

Precision instruments supplied with standard detachable copper chisel face bits. Standard temp. 360°C at 19/23/27 watts. Special temps. from 250°C/410°C.



For perfection  
in soldering

**L1076**  
BIT SIZE 1/4"  
6.34 mm Dia.  
27 watts.  
£2.18

**L646**  
BIT SIZE 3/16"  
4.75 mm Dia.  
23 watts.  
£2.12

**L706** →  
BIT SIZE 1/8"  
3.2 mm Dia.  
19 watts.  
£1.96



Don't take chances. We don't. All our ADCOLA Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this production tool. ADCOLA day after day.

Send for **NEW**  
catalogue today

ADCOLA PRODUCTS LTD. ADCOLA HOUSE GAUDEN ROAD LONDON SW4 6LH

Postage, packing paid on orders over £2. under £2, add £0.10

Models required \_\_\_\_\_


Enclosing P/O or cheque for \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

EE6

# Are you alright for Jacks?

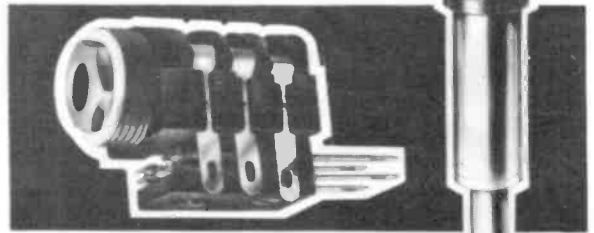

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes... plugs in both screened and unscreened versions... socket bodies in high melting point thermoplastic... several unique features (some protected by UK and US Patents)... Post Office and NATO specifications.

If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!



## RENDAR®

Rendar Instruments Ltd., Victoria Road  
Burgess Hill, Sussex. Tel. Burgess Hill 2642-4  
Cables: Rendar, Burgess Hill

## SOUND BARGAINS




**GIANT POWER MULTI-WAVEBAND BROADCAST RECEIVER**

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM  
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

**OUR PRICE** £10.50  
+40p P. & P.

THIS NEW 1972 RADIO. No less than 3 VHF BANDS. Picks up Aircraft Transmission, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHER-BAND. Frequency ranges: MW540-1600 KHZ, FM88-108MHZ, Airband 108-145 MHz, VHF 145-175MHZ, 23 semi-conductors—12 transistors, 11 diodes and thermistors. Automatic frequency control. 31" telescopic aerial. Runs off mains AC 230/250 volts or off 4 U111 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10 1/2" x 6 1/2" x 3 1/2". Written guarantee. Special magnetic ear-piece for personal listening. dry batteries FREE. HURRY! Limited quantity only from Marktyme. Fully guaranteed.



**OUR PRICE** £28.95  
+50p P. & P.

Tune into the world with this amazing world radio. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; thermistor. External ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350Kcs. Medium 353-1605Kcs. FM/VHF 88-108Mcs. Aircraft 108-135 Mcs. PUBLIC SERVICE BANDS 135-174Mcs. Fully guaranteed.



**8 WAVEBANDS AND WORLD MAP & TIME ZONE SCALE**

Tune into the world with this amazing world radio. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; thermistor. External ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350Kcs. Medium 353-1605Kcs. FM/VHF 88-108Mcs. Aircraft 108-135 Mcs. PUBLIC SERVICE BANDS 135-174Mcs. Fully guaranteed.

*N.B.—The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.*

**SONIC SOUND  
AUDIO LTD.**

(Dept. ED7), 372 EDGWARE ROAD,  
LONDON, W.2. Tel. 01-723 0094.  
Callers welcome Monday to Saturday  
9 a.m.—6 p.m.



## Christmas Presents a Problem!

We can take it for granted that she will be buying you the very thing you've set your heart on, so let's concentrate on that superb present you are so generously thinking of buying her! Simple—as everybody knows, today's finest range of radio and electronic components is to be found in the Home Radio Components Catalogue. You could buy her a copy, so that she can pick out just what she wants. On second thoughts, that might complicate matters. Better make the choice yourself. After all, you want it to be a surprise for her on Christmas morn! Moreover, you'll both have the Home Radio Components Catalogue, and can spend many hours together, browsing through it. The Catalogue is crammed full with details of 8,000 items, of which about 1,500 are illustrated. It costs only 70 pence,

including post and packing, and each copy contains 10 vouchers worth 5p each.

Of course, you can call at our shop (we're open 9 to 5.30 Monday to Saturday, except Wednesday 9 to 1) and get just what you want straight off the shelf. Incidentally, a catalogue bought this way will cost you only 50 pence. Whether you order by post or buy over the counter you should join our Credit Account Service. It's the simple and convenient way of buying all your radio and electronic components. We supply pre-paid envelopes and order forms, and no matter how many orders you send us you make only one payment per month. Full details and entry forms are in the catalogue.



The price of 70p applies only to catalogues purchased by customers in the UK and to BFPO addresses.



**POST THIS COUPON** with your cheque or postal order for 70p

Name .....


Address .....



Please use block capitals

HOME RADIO (Components) LTD.  
Dept. EE, 234-240 London Road, Mitcham CR4 3HD
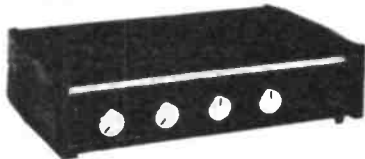
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knob, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response:  $\pm 3\text{dB}$  12-30,000 Hz. Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm 3\text{dB}$  12-15,000 Hz. Bass boost approx. to  $\pm 12\text{dB}$ . Treble cut approx. to  $-16\text{dB}$ . Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size: 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. **AMPLIFIER KIT** £10 50 P. & P. 15p (Magnetic input components 30p extra) **POWER PACK KIT** £3 00 P. & P. 30p **CABINET** £3 00 P. & P. 30p

(Post Free if all units purchased at same time)  
Full after sales service  
Also available ready built and tested £21.00. Post Free.  
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discophone use, etc.

## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts  $\pm 3\text{db}$ . Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, enclosure panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. **PRICE £10 50. P. & P. 25p.**


**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top quality record player amplifier employing heavy duty double wound mains transformer, EXC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. **PRICE £3 95. P. & P. 40p.**  
**ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit into cabinet below. **PRICE £5 25. P. & P. 50p.**  
**DELUXE QUALITY PORTABLE R/P CABINET MK II**  
Uncut motor board size 14 1/2 x 12in., clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE £4 75. P. & P. 50p.**



### SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS  
With large ceramic magnet and plasticised cone surround.  
8 ohms impedance £2 75. P. & P. 25p.

## DE LUXE STEREO AMPLIFIER

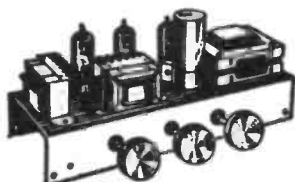

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 x ECL86 Triode Pentodes. 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w. x 4" d. Overall height including valves 5". Ready built & tested to a high standard. **PRICE £8 92 P. & P. 45p.**

**4-SPEED RECORD PLAYER BARGAINS**  
Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £6 97. Carr. 50p. With stereo cartridge £7 97. Carr. 50p.

**SPECIAL BARGAIN OFFER!**  
**PRECISION ENGINEERED PLINTHS**  
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2022TC, 2500, 3000, 3500, 5100, SP25 II and III, SL45B, AT60 etc. or B.S.R. C109, C129, A31 etc. Choice of Black leatherette or Teak grain finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). **ONLY £4 50. P. & P. 35p.**

**CENTRE ZERO MINIATURE MOVING COIL METER.**  
100uA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

## HARVERSON SURPLUS CO. LTD.

(DEPT. EE) 170 HIGH ST., MERTON, LONDON, S.W 19 Tel: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## G. F. MILWARD

# ELECTRONIC COMPONENTS

Wholesale/Retail:

369 Alum Rock Road, Birmingham B8 3DR.

Tel. 021-327 2339

£1	100 1/4 Watt Resistors 100 Ceramic Capacitors 100 Diodes	Pack No. 1	£1	100 Resistors 100 Ceramic Capacitors 100 Polystyrene Capacitors	Pack No. 2
£1	1 Vero-board Cutter 5 2 1/2 in. x 1 in. x 15 Boards 50 sq. ins. "Odd Pieces" Vero	Pack No. 3	£1	100 Resistors 100 Ceramic Capacitors 50 Mullard Polyester Capacitors	Pack No. 4
£1	20 Assorted Unused Marked, Tested Transistors. BC108 Etc.	Pack No. 5	£1	1 Transistorised Signal Tracer Kit 1 Transistorised Signal Injector Kit	Pack No. 6
£1	6 Computer Panels containing masses of Diodes, Transistors, Inductors, Resistors & Capacitors	Pack No. 7	£1	100 Resistors 100 Capacitors (Assorted Types)	Pack No. 8

## INDUSTRIAL USERS!

We have access to some of the largest stocks of transistors and i.c.s in Europe. Some sample prices are given below. Regret that it is not possible to supply less than 100 of any one type at these prices. All marked and to full specification. Please 'phone or write for immediate quote should types you require not be listed.

AD 149 .. .. . 34p each	BD 137/138 .. .. . 46p pair	2N 3055 .. .. . 31p each	741C (T05 or DIL) .. 27p
AD 161/162 .. .. . 35p pair	2N 1613 .. .. . 8p each	2N 3053/4037 .. .. . 34p pair	723C (T05 or DIL) .. 46p
AF 124 .. .. . 12p each	2N 1711 .. .. . 8p each	2N 5179 .. .. . 38p each	
BC 141/161 .. .. . 38p pair	2N 3053 .. .. . 11p each	709C (T05 or DIL) .. 25p	

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p.

**ALMOST UNBELIEVABLE!** Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! \*We challenge you to compare performance and value with that of £80 radios! Test 7 days, we'll refund instantly if you are not astounded! Elegant black & chrome finish fascia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth 24 hours a day including all normal transmissions. VHF, AM, FM, MW, LW, USW, plus local & new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** slide control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 14ins x 10½ins x 4½ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions & circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra) **BOX, POST, ETC. 50p.** \***BUT WAIT**, for only 55p extra you get the sensational "**COMPUTERISED**" **WORLD TUNING GUIDE** (it enables you to time-pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) PLUS Standard 'longlife' batteries PLUS ultra sensitive earphone for personal listening. (Sorry—we cannot change these new radios for any earlier model purchased.) **HURRY!** Send today or call at either store.

**JUST ARRIVED!** THIS YEAR'S NEW \* **COMPUTERISED?**  
**RUSSIAN MIRACLE!**

**BRAND NEW SPACE AGE model**  
—SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!

**THE FABULOUS ASTRAD 17**

THIS OFFER ONLY FROM NOW!

**WORLD WIDE RECEPTION**  
THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!

**PORTABLE RADIO & COMMUNICATIONS RECEIVER**



**28 TRANSISTORS AND DIODES!**  
**WAVEBANDS:**  
STANDARD LONG and MEDIUM  
Plus 5 SHORT WAVEBANDS  
Plus ULTRA SHORT WAVES  
(V.H.F. AM, FM, MW, LW, USW.)

\*COMPARE ITS PERFORMANCE with **£80** RADIOS!

**BATTERY MODEL £20.75**  
**BOX POST ETC. 50p**  
**MAINS/BATTERY ELIMINATOR £1.48 extra**

**FIRST TIME EVER!**  
\*NOW AVAILABLE WITH **"COMPUTERISED"**  
**WORLD TUNING GUIDE!**  
**NO MORE GUESSWORK—**  
INSTANT DATA at your fingertips — enables you to **TUNE IN A FLASH** to transmissions the world over!

**ANOTHER EAST EUROPEAN MIRACLE!**

**FANTASTIC 2-in-1 PERSONAL PORTABLE and CAR RADIO**  
**NOW WORLD WIDE RECEPTION**  
**IN YOUR CAR TOO!** RUNS OFF 12V. CAR BATTERY

Position it for **CAR RADIO**, results will justify! OR detach & use carry handle for **PORTABLE** with its own batteries!

**4 WAVEBAND VHF AM FM LONG & SHORT WAVEBANDS**  
**FANTASTIC PRICE £9.95**  
**TRY AND MATCH IT FOR UNDER £35!**  
**BOX, POST ETC. 45p.**

**FANTASTIC!** Brand spanking new from East Europe we bring you this incredible 2-in-1 Radio! First class makers —because of our crazy price, contract stipulates we must NOT mention name! Beautifully made. 9x5x2½ inches overall approx. Every up-to-date technological improvement. **15 SEMI-CONDUCTORS!** 19 Transistors, 5 Diodes and Stabiliser! **F O U R W A V E - B A N D S!** Yes, VHF model with AM/FM Long and Short wavebands! Will get stations

around the world, including Standard Long, Medium and Short Wave, also local and new stations not yet operational! Built-in internal ferrite aerial plus 5 section 26in. swivel telescopic aerial. On/off/volume and tone controls. Clear Station Selector Dial. Waveband selector! Equally wonderful in CAR or HOME! **TWO Tuning Dials** for flat or upright use as illustrated. **RUNS OFF 12 VOLT BATTERY!** (AS A **PORTABLE** it runs on standard batteries). **PLUG IN 12 VOLT ADAPTOR JACK PROVIDED** and automatically cut out internal batteries, using car battery only! Don't you think it's miraculous! Span the Oceans and pull in hundreds of transmissions day and night, including short wave—even in car! **BUT WAIT**—simply remove Radio from car, "snap on" optional carry handle **AND YOU HAVE A DE-LUXE PORTABLE**, with additional upright tuning dial. **WRITTEN GUARANTEE.** Only £9.95 box, post 45p. \*Sprung all metal matching detachable carry handle (as illus.), and batteries only 25p ex. if required. Match with sets costing £35 or more. Send and Test 7 days. Refund if not delighted or call. Order by post to Uxbridge Road address, or call at either store.

**COMMERCIAL TRAVELLERS NOTE:** Merchandising office at Holborn Store.

**SHOPERTUNITIES LTD.**

**FIRST TIME EVER! SAVE £14.48!**  
**BRAND NEW AC/DC BATTERY/MAINS**

**Cassette TAPE RECORDER & PLAYER**  
**FIRST CLASS MAKERS**  
With remote control microphone.  
**WE COULD CHARGE UP TO £26.97!**  
**OUR PRICE £12.49**  
**POST ETC. 31p**

**THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW** a superb deluxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £12.49!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "**FLYING KEYBOARD**" **CONTROL PANEL** (or latest **MASTER SWITCH** control) **AND AUTOMATIC LEVEL CONTROL**. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on standard batteries **AND 220/240v. AC** mains. Separate jacks for remote control microphone, etc. Size 9½in. x 5in. x 2½in. approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. **ONLY £12.49 post, etc., 31p.** \*Refund if you don't agree we could charge up to £26.97! **BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries, **AND microphone stand** all for 50p extra, if req. Send quickly. Test 7 days—refund if not delighted or call. Also super deluxe model fitted with VHF AM/FM, radio **ONLY £23.75** carr. extra 35p. (Standard batteries and cassette tape 25p extra if required).

Dept. EE/13, 164 UXBIDGE ROAD (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) **BOTH STORES OPEN FROM MONDAY TO SATURDAY FROM 9 A.M. UNTIL 6 P.M.**



# HI-FI EQUIPMENT

SAVE UP TO  
**33 1/3% OR MORE**  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!

## RECORD DECKS

BBR	
CL29 Mono	£6.50
CL37	£8.35
MP60	£9.75
610	£12.65
610	£31.25
MP60/	
G800*	£12.95
MP60 TPD1	£18.06
MP60/TPD1	
G800*	£19.50
MP60 TPD2	£14.35
610 TPD1	£18.95
610 TPD1	£17.95
201/TPD3	£8.75
HT 70	£13.99
HT70/	
G800*	£17.25
HT 70 Pack	£20.35
HT70/Pack/	
G800*	£23.90

GARRARD	
2025 T/C*	£8.50
408*	£9.25
8P25 III	£10.25
RL56B	£13.76
AP76	£17.95
RL72B	£21.95
RL95B	£32.25
401	£25.95
ZERO 100A	£38.95
ZERO 100B	£38.95

GOLDRING	
GL69/2	£18.50
GL69/2/P	£24.20
GL72	£23.50
GL72/P	£27.50
GL75	£26.95
GL75P	£35.25
LID75	£3.60
LID73	£3.25
G99	£19.95
GL85P/C	£56.95
LID85	£4.95
G101P/C	£20.50

PIONEER	
PL12AD	£33.95
PL15C	£51.35
PLA35	£32.65
THORENS	
TD124/11	£66.50
TD125AB/11	
TX35	£69.95
TD1800	£56.95
TD150	£28.50
TD150A II	£35.95
TD150AB II	£39.95
TD150 Plinth	£3.80
TX11	£3.60

### \* Stereo Cartridge

All other models less Cartridge  
Carriage 50p extra any model.

## RECORD DECK PACKAGES

Decks supplied with  
cartridge ready  
wired in teak ven-  
eered plinth with  
cover.

Garrard 2025TC/9TAHCD	£12.76
Garrard 8P25 III/9TAHCD	£15.95
Garrard 8P25 III/G800	£17.95
Garrard 8P25 III/M44-E	£19.76
Garrard 8P25 III/M44-E	£20.95
Garrard 8P25 III/M55-E	£22.40
Garrard AP76/G800	£27.95
Garrard AP76/M75-E	£30.25
Garrard AP76/M55E	£30.50
Garrard AP76/M75EJ	£32.50
Garrard AP76/G800E	£30.75
Garrard AP76/M44-E	£30.50
Garrard AP76/M75ED	£38.95
BSR McDonald MP60/G800	£17.50
BSR McDonald MP60/M44-E	£19.50
BSR McDonald MP60/M44-E	£20.25
Goldring GL72/G800	£34.50
Goldring GL75/G800	£38.95
Goldring GL75/G800E	£41.95

## EA-41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverbation control. Beautiful walnut cabinet. 7 1/2 x 3 x 4 1/2 in. £5.97. P. & P. 15p.



## LATEST CATALOGUE

Our 7th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS

VALUE 50p  
320 pages,  
fully illustrated and  
detailing  
thousands of  
bargains.

SEND NOW

ONLY  
40p  
P & P  
10p



## TELETON SAQ-206B STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal, aux. tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls.

OUR PRICE £22.95 Carr. 37p.

## SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-450 KHz and 55 to 30 MHz. Illuminated slide rms. dial. Bandspread. Aerial tuning. B.F.O. AVC. ANL. 'B' meter. AM/CW/88 B. Integrated speaker and phone socket. Operation 220/240 V AC or 12v DC. Size 325 x 266 x 150 mm. Complete with instructions and circuit. £30.00. Carr. 50p

## HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5MU/100MU. Output 50mW. £5.97. P. & P. 15p.

**TAPE CASSETTES**  
Top quality Hi Fi Low Noise in Philips Library cases.  
C90 3 for 75p 10 for £2.35 P. & P.  
C90 3 for £1.05 10 for £3.30 10p  
C120 3 for £1.35 10 for £4.20 extra  
Tap: Head Cleaner 30p each

## \* TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER, 812E ONLY 6 x 4 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £8.37. P. & P. 12p. Stereo multiplex adaptors £4.97.

## U43E MULTIMETER

Extremely sturdy instrument for general electrical use. 667 o.p.v.  
0/3/1-5/7-5/30/60/150/300/600/900 VDC and 75mV.  
0/3/1-5/7-5/30/60/150/300/600/900VAC.  
0/300uA/1/5/6/50/60/150/600mA/1/5/6 AMP. A.C.  
0/200 0/3/3K/30K 0.  
Accuracy DC 1%, AC 1.5%.  
Knife, edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9.50 plus P. & P. 25p.

## MCA. 220 AUTOMATIC VOLTAGE STABILISER

Input 98-125 VAC or 176-250VAC. Output 120VAC or 240VAC. 200VA rating. £11.97. Carr. 50p.

# SINCLAIR IC-12



## HOMER INTERCOMS



Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

- 2 Station £2.97. P. & P. 15p.
- 3 Station £5.25. P. & P. 15p.
- 4 Station £6.62. P. & P. 17p.



## EMT LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 16 ohms. £7.25 each. P. & P. 37p.  
Model 450. 13" x 8" with twin tweeters/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3.62 each. P. & P. 25p.



## TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1.97. P. & P. 15p.

## MP7 MIXER PREAMPLIFIER


5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3".
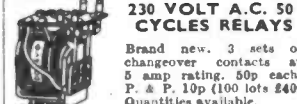
## 1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2.25. P. & P. 15p.



**LB4 TRANSISTOR TESTER**  
Tests PNP or NPN transistors. Audio indication. Operates on two 1.5v batteries. Complete with all instructions etc. £4.50. P. & P. 20p



## 230 VOLT A.C. 50 CYCLES RELAYS


Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40) Quantities available.

# SPECIAL OFFER!



**PHILIPS GA308 TRANSCRIPTION TURNTABLE**  
2 speeds 33 1/3 and 45 rpm. Lightweight tubular counter-balanced arm. Belt driven low speed synchronous motor. Viscous damped pick up lift/lower device. Complete with teak plinth and hinged cover. GA308 less cartridge (List £26.55).  
OUR PRICE £24.50. P. & P. 50p.  
GA308 PU with GP400 stereo magnetic cartridge (List £47.65)  
OUR PRICE £29.95. P. & P. 50p.

## SINCLAIR EQUIPMENT

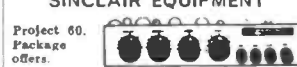

Project 60. Package offers:  
2 x Z30 amplifier, stereo 60 pre-amp, P25 power supply. £15.95 Carr. 37p. Or with P26 power supply £18.00 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, P28 power supply. £20.25 Carr. 37p.  
Transformer for P28. £2.97 extra.  
Add to any of the above £4.4b for active filter unit and £18.00 for pair of Q16 speakers. All other Sinclair products in stock.  
2000 Amp £21.95 Carr. 37p.; 3000 Amp £28.50 Carr. 37p.; Neoteric Amp £43.95 Carr. 37p. IC12 £1.80 Post 10p.  
PROJECT 605 — £20.87, Carr. 37p.

## WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5" dia. Impedance 4/8 ohms. High dust ceramic magnet, 20 watts rms. Brand new £1.50. Carr. 37p.



## UNR-30 RECEIVER

4 Bands covering 550kc/s-30 Mc/s. B.F.O. Built-in Speaker 220/240v. A.C. Brand new with instructions. £15.75. Carr. 37p.



## LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s. 550 kc/s-30mc/s. PET front end. 3 mech. filters, product detector, variable B.F.O., noise limiter, B. Meter, Bandspread. RF Gain. 16" x 9 1/2" x 8 1/2". 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £50. Carr. 50p.

## TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500v. A.C. volts 1.5-1,500v. Resistance up to 1,000 megohms. 200/240v. A.C. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional probes available. R.F. £2.12; H.V. £2.50.

# POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. Tin, dia. snatts. Bulk quantities available.  
25 WATT 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 90p. P. & P. 7 1/2p.  
50 WATT 10/25/50/100/250/500/1000/1500 or 5000 ohms, £1.15 P. & P. 7 1/2p.  
100 WATT 1/5/10/25/50/100/250/500/1000 or 2500 ohms, £1.45 P. & P. 7 1/2p.

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery	
S-260 General Purpose Bench Mounting	S-260B Panel Mounting
1 Amp £7.00	1 Amp £7.00
2.5 Amp £8.05	2.5 Amp £8.05
5 Amp £11.75	
8 Amp £15.90	
10 Amp £22.50	
12 Amp £23.60	
20 Amp £49.00	
25 Amp £58.00	
40 Amp £82.50	

Please add postage ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES. OUTPUT VARIABLE 0-260 VOLTS. Special discounts for quantity

# G.W. SMITH & CO. (RADIO) LTD

10 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-637 2232  
27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
257/258 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-580 0670  
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

# gspk (sales)

## MICROSCOPE

An extremely modestly priced yet efficient microscope capable of magnification up to 750 times with clear, sharp images. This model is of the self-illuminating type and incorporates an easily rotatable four-position turret magnifying lens selector with rack and pinion focusing. The crackle black metal body houses the batteries for adjustable light illumination. Sample slide also provided. Price each £4.95



## G.1111 STEREO HEADPHONE

A particularly well designed stereo headphone with smooth response throughout its frequency range 23-13,000 Hz. The rubber padded earpieces are adjustable for personal fitting. Model G.1111 is presented in two-tone grey with 4' matching lead and fitted plug. Impedance is 8 ohms. Price each £2.90



## AUTO BURGLAR ALARM

Designed for easy installation on any car (whether 6 or 12V) this device activates the horn when a theft is attempted of expensive equipment or personal belongings. This neat unit only 5 1/4" x 2 1/2" x 1" deep on fixing backplate, reacts when the vehicle is disturbed or rocked and continues its warning for 15 seconds after tampering. The sensitivity of the device is adjustable and controlled by a separate On/Off panel which can be located wherever convenient. Supplied with connecting wires and screws, installation instructions and diagrams. Price each 89p



Single push-pull 4 pole switches **0.28p**  
3 button 2 pole 6 way interlocking, interchange switches suitable for car radios, D.I.Y. stereo and many other uses **0.49p**

## NUMEROUS OTHER ITEMS AVAILABLE INCLUDE:

Switches. Comprehensive range of N.S.F. Toggle switches and Rotary Wafer switch kits (to enable you to make your own switch to your own specification).  
Copper laminate and all materials available to make your own printed circuit boards.  
Lamps and lampholders for every requirement. Ready Built Circuits and Modules.  
Freezer and Cleaner aerosol sprays.  
Jack plugs and sockets.  
Variety of speciality products.  
Resistors, Capacitors.

All orders value £2 or over post free. Other orders please add 10p P. & P. We only sell new products—do not confuse with "seconds" or surplus stock. Because of our keen prices we regret the prices apply to U.K. and B.F.P.O. addresses only.

To GSPK (Sales) Limited  
Dept. E.E., Head Office, Hookstone Park, Harrogate, Yorks., HG2 7BU

ALL CALLERS  
WELCOME  
MON. to FRI.  
9-3.00

Please fill in the coupon and send with 10p (refundable on ordering) for catalogue

Name .....

Address .....

E.E.

# DISCOUNTS P.T.O.

## 60%

## Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

## GARRARD SP25 Mk. III SPECIAL OFFER £17.45

Garrard SP25 Mk. III Goldring G800 Teak plinth and tinted cover. All leads supplied. Please add £1.25 for P. & P.

## TUNERTABLES

Please add 75p for P. & P.

Garrard SP25 Mk. III	£9.95
Garrard AP76	£17.45
Garrard SL65B	£13.95
Garrard 401	£28.95
Garrard Zero 100 (Auto)	£36.95
Garrard Zero 100 (Single)	£35.95
Garrard 3000	£10.00
Garrard 2025TC with Sonotone 9TAHC	£9.75
BSR MP60	£9.40
Goldring GL72	£21.60
Goldring GL72/P	£28.35
Goldring GL75	£26.90
Goldring GL75/P	£33.90
Goldring 101 PC	£20.00
Wharfedale Linton & cart. Thorens TD125 AB Mk. II	£26.50
New Product	£91.75
Thorens TD150 Mk. II	£26.95
Thorens TD150A Mk. II	£32.95

## AMPLIFIERS

Please add 75p P. & P.

Amstrad 8000 Mk. II	£13.95
Amstrad IC2000	£26.90
Amstrad Integra 4000	£21.95
Armstrong 521 (teak cased)	£44.40
Alpha Highgate 212	£24.95
Alpha Highgate FA300	£30.95
Alpha Highgate FA400	£34.50
Keltron 700 new prod.	£19.50
Leak Delta 30	£44.85
Leak Delta 70	£54.95
Metrosound 5T20E	£24.50
Metrosound 5T60	£45.50
Pioneer SA600	£57.00
Pioneer SA500A	£34.25
Pioneer SA900	£85.00
Pioneer SA1000	£93.00
Rogers R/brook (Chassis)	£35.80
Rogers R/brook (Cased)	£38.00
Rogers R/bourne (Chassis)	£41.80
Rogers R/bourne (Cased)	£48.95
Sinclair PRO60 2 x Z30/PZ5	£14.70
Sinclair PRO60 2 x Z30/PZ6	£16.70
Sinclair PRO60 2 x Z50/PZ8/Trans	£20.95
Sinclair AFU (Filter Unit)	£4.20
Sinclair 605	£17.90
Sinclair 2000	£20.95
Sinclair 3000	£28.20
Wharfedale Linton	£42.75
Teleton SAQ206B	£20.50
Teleton SAQ307	£22.50
Rotel RA 310	£33.75
Rotel RA 610	£50.75

## TUNERS

Please add 75p P. & P.

Amstrad Multiplex 3000	£28.65
Armstrong 523	£39.50
Armstrong 524	£31.45
Rogers Ravensbrook FET4 (Chassis)	£31.00
Rogers Ravensbrook FET4 (Cased)	£34.95
Rogers Ravensbourne FET4 (Chassis)	£43.00
Rogers Ravensbourne FET4 (Cased)	£47.50
Sinclair PRO60 (Module)	£15.75
Sinclair 2000/3000 Tuner	£31.00
Philips RH690	£33.00
Leak Delta FM (Cased)	£53.75
Leak Delta AM/FM (Cased)	£60.75
Alpha Highgate FT 150	£34.95

## TUNER/AMPLIFIERS

Please add 75p for P. & P.

Alpha Highgate 150	£44.25
Armstrong 525 (Teak cased)	£69.45
Armstrong 526 AM/FM (Teak cased)	£77.75
Leak Delta 75	£120.95
Philips RH781	£50.00
Philips RH702	£82.50
Teleton 2100	£29.45
Goodmans One Ten	£98.00
Rogers R/brook (Teak)	£77.50
Rogers R/brook (Chassis)	£72.00
Alpha FR 3000 New Prod.	£66.00

## SPEAKERS

Please add £1.25 P. & P. per pair

Amstrad 138	£14.70
Wharfedale Denton 2	£28.50
Wharfedale Linton 2	£35.75
Wharfedale Melton 2	£47.45
Wharfedale Dovedale 3	£59.90
Celestion Ditton 120	£38.50
Celestion Ditton 15	£52.00
Celestion Ditton 25	£85.50
Celestion County New Prod	£35.50
Goodmans Double Maxim	£47.85
Goodmans Mezzo 3	£46.95
Goodmans Magister	£76.95

£3.20\*



Plus 35p p. & p. Finished in teak veneer with tinted dust cover fully assembled. For Garrard SP25 2025TC, 3000, AT60, 2005, 2500, 3500, 5100, 1025, SL65B. Also for BSR McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B; £4.20 plus 55p P. & P. Also finished in walnut to match Japanese equipment—at no extra. CARTRIDGES. Please add 10p for P. & P.

Goldring G850	£3.25
Goldring G800	£5.50
Goldring G800E	£7.50
Goldring G800 Super E	£14.15
Shure M3D	£3.85
Shure M447	£4.95
Shure M55E	£5.60
Shure M75E Type 2	£10.00
Sonotone 9TAHC	£1.65



All prices correct at time of press E. & O.E. and are subject to alterations

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (E13)174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country




# SAXON ENTERTAINMENTS.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT  
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN  
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.
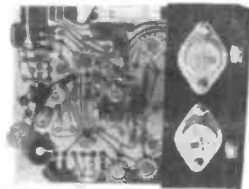
## SA25-SA35-SA100

LOW-PRICED AUDIO MODULES  
FOR DOMESTIC & COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

**SA25 £2.95** carr. free

25 WATTS RMS. 7 transistors 7 diodes

**SA35 £4.45** carr. free

35 WATTS RMS. 7 transistors 7 diodes

**SA100 £10.90** carr. free

100 WATTS RMS. 11 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

### BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000 Hz $\pm$ 1dB
Distortion	0.2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	25-45 volts SA25/35 40-70 volts SA100
Size	4 1/2" x 4" x 1" (SA100) 4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

### POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

Stab PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
PU70	Unstabilized supply for one or two SA100	£7.75 carr. 40p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON  
GLASS FIBRE P.C. BOARD  
AND ARE SUPPLIED FULLY TESTED

## OTHER SAXON PRODUCTS. . .

120 WATT HEAVY DUTY MODULE £13.90 + 20p carr. or with supply  
£18.95 + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

### SPECIFICATION

Power output 120 watts into 8 ohms  
Freq. response 20-20,000 Hz  $\pm$  2dB  
Input sensitivity 200 mV into 10K  
Construction Fibreglass board  
Size 8" x 4" x 4" (5" with supply)  
Low distortion parallel push-pull output stage.



**NEW**  
160 watt version & supply **£27.90**

### SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 8p.



SPOT BANKS INCLUDING 3 SPOTS  
STATE COLOURS: RED, BLUE, GREEN.  
£10.25 complete, carr. 40p.

**£8.90** carr. free

### THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue steelvite hooded cover. Fully guaranteed.

**£19.75** carr. 30p


MONO VERSION £6.50 carr. 20p (As illustrated left S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



**£15.80** carr. 30p
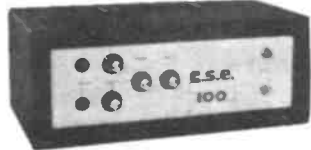
### SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE. (N.B.—Stereo only has mic input.)



### COMPLETE AMPLIFIERS

The CSE 100. £34.90 carr. free

This versatile unit is now available in a black vynlide case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.

The SAXON 100 £48.50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

### LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £8.95 carr. 30p. 15" 50W.8/15 ohm £14.50 carr. 50p.  
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.  
A.K.G. MICROPHONES suitable for disco, group or general P.A. use.  
D11DHL rrp £11.00 our price £9.45 post free  
D190C High Z rrp £21.50 our price £17.45 post free  
D1000C 24 ct gold plate rrp £37.00 our price £32.00 post free

SEND SAE FOR OUR AKG PRICE LIST, DISCOUNTS ON ALL MICS.

### CALLERS & MAIL ORDER:

327-331 Whitehorse Rd.,  
West Croydon, Surrey.  
CRO 2HS 01-684 6345

### CALLERS ONLY:

OUR NEW  
DISTRIBUTORS

CIRCLE SOUND,  
328-330 The Banks, Rochester.  
Medway 404199

### BUSINESS HOURS:

9.30 a.m.  
to 5.30 p.m.

### TERMS OF BUSINESS:

C.W.O. or C.O.D. (35p extra)  
All cash in regd. envelopes please!  
Telephone orders to our CROYDON BRANCH.  
TRADE & EXPORT enquiries invited.

# CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL

## COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N-9 803 1685

### 7" x 4" LOUDSPEAKER



A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in. x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.

### ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL

5 Section Extended Length 100cm Length under Fender 40cm Cable Length 120cm complete with Fixing Bracket and Control Switch. £5.75 plus 5p P. & P.

### S.G. BROWN HEADPHONES

Used! But in good working condition. These Type "P" phones are 4,000 Ohm, and a bargain at

50p Plus 10p. P. & P. per pair

### LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.

### "CRESCENT" DIGITAL CLOCK KIT

24 Hour Brite Digital Clock Kit We Supply:  
★ A complete set of components to follow instructions  
★ Printed circuits made to make construction as simple as possible  
★ A cabinet and front panel to give a professional finish.  
All for the price of the components: £22.50 + 50p. P. & P. Please send S.A.E. for more information.

### MINIATURE RELAY

6 volt 70 ohm. Single Pole Changeover. Approx. size - 1 1/2" x 1" x 1".

40p plus 5p P. & P.



### TRI-VOLT BATTERY ELIMINATOR

Enables you to work your transistor radio, amplifier, or cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug you can select the voltage you require - 6v, 7 1/2v or 9 volts. This means all your transistor power pack applications can be handled by this one unit. Approx. size: 2 1/2" x 2 1/2" x 3 1/2". OUR PRICE - £2.75p + 10p. P. & P. Same model suitably wired for the Philips Cassette - £3.00 + 10p. P. & P.

### ALUMINIUM CHASSIS

Made from 18 gauge aluminium 4 sided chassis with corner brackets. All are 2 1/2" depth.

6x3-41p	12x3-53p	14x3-94p
6x4-45p	12x5-61p	16x6-80p
8x6-53p	12x8-83p	16x10-108p
10x7-83p	14x8-80p	

Please send 10p per chassis P. & P.

### POWER TRANSISTOR HEAT SINKS

Extruded aluminium. Approx. size: 6" x 4 1/2" x 1 1/2". A few only at this low price - 40p each + 5p P. & P.

### INTEGRATED CIRCUIT SOCKETS

A must for the experimenter interested in I.C.s. 14 pin, 20p each. 16 pin, 20p each. Please include 5p P. & P. per 3 sockets.

### EA1000 3 WATT AUDIO AMPLIFIER MODULE

An Audio Amplifier designed around the TAA821 Linear I.C.:-  
Supply Voltage ... 9-24V  
Speaker Imp. ... 8-16 ohm  
Frequency ... 50Hz-26kHz  
Overall Size ... 2in x 3in x 1 1/2in  
Ideal Amplifier for radios, record players, stereo units, etc.  
Full technical data and diagrams with each module. All guaranteed and a bargain at

### TRI-VOLT CAR CONVERTER

Enables you to work your Transistor Radio, Amplifier or Cassette etc. from the 12 volt car supply positive or neg. earth. This converter supplies 6, 7 1/2 or 9 volts and is transistor regulated. Approx. size 2 1/2" x 3 1/2" x 2". Very easy to fit and a real money saving device for £2.50 + 10p. P. & P.

### WAFER SWITCHES

1 pole 12 way  
2 pole 2 way  
2 pole 3 way  
2 pole 4 way  
2 pole 6 way  
3 pole 4 way  
4 pole 3 way  
18p each. Please inc. 5p P. & P. Up to 3 switches.



### POTENTIOMETERS

All types 1" and less diameter.  
SINGLES DUAL  
5K Log or 5K  
10K Lin Less 10K  
25K Switch 25K Less  
50K 50K Switch  
100K 12p ea, 100K 40p.  
250K Double 250K  
500K Pole 500K each  
1M Switch 1M  
2M 2M  
24p ea.

Up to 3 Pots. Please add 5p P. & P.




MINIATURE RELAYS  
Brand new range of British made Relays.  
Size - 1 1/2" x 1" x 1"  
All two changovers with 250V, 1.5A contacts and suitable for fitting on 1m Veroboard.  
Type Volts Current Ohms.  
27/A 12v 17M/A 700 Ohm  
21/A 12v 28M/A 430 Ohm  
12/A 6v 33M/A 185 Ohm  
80p each.  
Please include 5p P. & P. up to 3 delays.
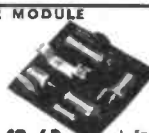
### BARGAIN BOARDS

Components galore for the experimenter. Ex computer boards with: Resistors, Capacitors and useful Transistors.




Now at this unbeatable price: 15p each. 7 Boards £1. 10p P. & P.



£2.63 + 5p P. & P.

# VEROBOARD

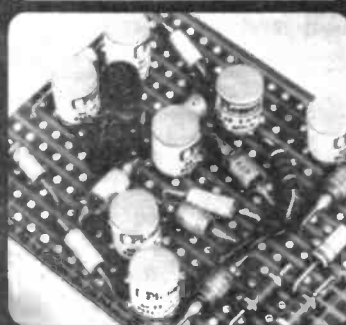

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK


0.1" and 0.15" pitch, plain and copper clad universal circuit boards. AVAILABLE FROM YOUR LOCAL RETAILER.

TRADE DISTRIBUTOR: N. Rose (Electrical) Ltd., London, W.C.1.



VERO ELECTRONICS LTD.  
Industrial Estate, Chandlers Ford,  
SO1 3ER Tel: Chandlers Ford 2952
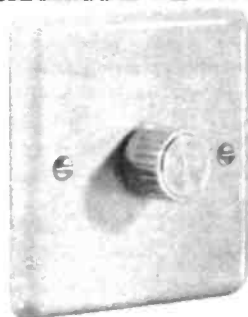
## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:  
600 Watt £3.20. Kit Form £3.70  
300 Watt-£2.70. Kit Form £2.20

All plus 10p post and packing. Please send C.V.O. to:-

**DEXTER & COMPANY**  
5 ULVER HOUSE, 19 KING STREET,  
CHESTER CH1 2AH Tel: 0244-25883

As supplied to H.M. Government Departments.

## INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £2.60 post paid.

MAIL ORDER ONLY.  
S.A.E. ALL ENQUIRIES.

**DABAR ELECTRONIC PRODUCTS**

99a, LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ

**FOR  
RAPID  
SERVICE**

# GARLAND BROS. LTD.

## DEPTFORD BROADWAY, LONDON, SE8 4QN

### TRANSFORMERS

all with 0-250 Volt primaries  
**Miniature**  
MM6 6V, 500mA + 6V, 500mA  
MM12 12V, 250mA + 12V, 250mA  
MM20 20V, 150mA + 20V, 150mA  
£1.29 plus 13p p. & p.

**L.T.**  
LT1 6-3V, 1.5A—75p plus 18p p. & p.  
LT2 6-3V, 3A—87p plus 26p p. & p.  
LT3 12V, 1.5A—87p plus 26p p. & p.  
LT4 12V, 3A—£1.32 plus 30p p. & p.  
**LTS** 9-0-9V, 0.5A—75p plus 21p p. & p.  
LT6 12-0-12V, 1A—95p plus 26p p. & p.  
LT7 30-0-30V, 1A—£1.87 plus 30p p. & p.

**Multi-tapped**  
MT30/2 0-12-15-20-24-30V, 2A—  
£1.95 plus 30p p. & p.  
MT60/1 0.5-20-30-40-60V, 1A—  
£2.10 plus 30p p. & p.  
MT60/2 0.5-20-30-40-60V, 2A—  
£2.95 plus 34p p. & p.

**Charger**  
CT/01 1A—£1.05 plus 26p p. & p.  
CT/02 2A—£1.30 plus 30p p. & p.  
CT/03 4A—£1.60 plus 30p p. & p.  
Secondaries—0.5-11-17V.

### SEMICONDUCTORS, etc.

Zeners—400mW, 15p; 1.5W, 22p  
L.D.R.—ORP12, 56p  
S.C.R.—400 P.I.V., 3-0A, 57p  
Bridge rectifier—40 P.I.V., 1.5A,  
50p  
Bridge rectifier—200 P.I.V., 2-0A,  
50p  
Transistor sockets—7p  
D.I.L. I.C. sockets—14 pin, 20p;  
16 pin, 20p  
IN4001—50 P.I.V., 1-0A, 6p  
IN4002—100 P.I.V., 1-0A, 7p  
IN4003—200 P.I.V., 1-0A, 8p  
IN4004—400 P.I.V., 1-0A, 9p  
IN4005—600 P.I.V., 1-0A, 12p

### ALUMINIUM BOXES

with lids and screws  
**Type** L. W. D. Price p. & p.  
GB7 5 1/2in 2 1/2in 1 1/2in 38p 15p  
GB8 6 1/2in 4in 1 1/2in 38p 15p  
GB9 8 1/2in 4in 2 1/2in 38p 13p  
GB10 10 1/2in 4in 3 1/2in 44p 18p  
GB11 4in 2 1/2in 2in 38p 13p  
GB12 3in 2in 1in 33p 13p  
GB13 6in 4in 2in 52p 18p  
GB14 7in 5in 2 1/2in 63p 19p  
GB15 8in 6in 3in 81p 26p  
GB16 10in 7in 3in 92p 26p  
\* These sizes fit standard veroboards

### EQUIPMENT CASES

in plain aluminium with sloping front panel.  
**Type** H. W. D. Price p. & p.  
SF1 2in 5 1/2in 2 1/2in 45p 12p  
SF2 2in 7in 3 1/2in 60p 16p  
SF3 2in 9 1/2in 4 1/2in 75p 19p  
Stove - enamelled silver-grey hammer finished, 25p extra.

### CONSOLE CASES

in plain aluminium, ideal for mixers, instruments, etc.  
**Type** W. A B C D Price p. & p.  
in in in in in  
GB20 8 9 3 1/2 3 £1.42 30p  
GB21 10 9 3 1/2 3 £1.58 30p  
GB22 12 9 3 1/2 3 £1.72 30p



### PRE-AMPLIFIER

for microphones or guitars. Mounted on printed circuit panel and complete with 1/2 inch jack socket. Requires 9V battery. Input 50kΩ. Complete with connection data. 65p.

### ELECTROLYTICS

1µF 450V 19p	1,000µF 25V 27p
2µF 450V 20p	1,000µF 50V 43p
4µF 450V 17p	2,000µF 25V 39p
16µF 450V 18p	2,500µF 25V 45p
25µF 25V 7p	2,500µF 50V 60p
25µF 50V 10p	3,000µF 25V 48p
32µF 450V 27p	5,000µF 25V 60p
50µF 50V 10p	5,000µF 50V £1.10
100µF 25V 10p	8-8µF 450V 18p
100µF 50V 11p	8-16µF 450V 20p
250µF 25V 14p	16-16µF 450V 27p
250µF 50V 17p	16-32µF 450V 63p
500µF 25V 18p	32-32µF 450V 49p
500µF 50V 25p	50-50µF 350V 38p

### MINIATURE ELECTROLYTICS

1µF 63V 6p	47µF 16V 7p
2.2µF 63V 6p	47µF 25V 6p
3.3µF 63V 6p	68µF 16V 6p
4.7µF 63V 6p	100µF 10V 6p
8µF 40V 7p	220µF 16V 7p
10µF 25V 6p	330µF 16V 11p
10µF 64V 7p	470µF 10V 11p
16µF 40V 7p	1,000µF 16V 11p
33µF 16V 6p	1,500µF 16V 23p

### CASSETTE OWNERS!

For Philips and similar cassette recorders.  
PU12 Power unit for connection to 12V or - E car electrical systems, giving 7 1/2V, stabilised output. **£3.25**  
PU1-A as above but switched for 6V, 7 1/2V or 9V output. **£5.10**  
PP75 Mains power supply, output 7 1/2V d.c. **£1.95**  
All units are complete with cable and plug.

### CASSETTES

Top quality British made, low noise, complete with transparent library cases—  
C60—40p; C90—55p; C120—70p

### BATTERY ELIMINATORS

suitable for transistor radios and similar light current equipment  
PB6 Input 240V a.c. Output 6V d.c.  
PP9 Input 240V a.c. Output 9V d.c.  
Price £1.50 plus 12p p. & p.

## ILLUSTRATED CATALOGUE

Post Free **15p**

### CONTROLS, Log. or Lin.

Single, less switch, 15p  
Single, D.P. switch, 24p  
Tandem, less switch, 40p  
5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ

### SLIDER CONTROLS, 87mm.

complete with knobs.  
Single, 44p; Tandem, 55p, 10kΩ, 25kΩ, 50kΩ, 100kΩ, log. or lin.

### RESISTORS

Carbon  
All 5%, high-stability, E12 values. 1/2W, 1p; 1/4W, 1 1/2p; 1W, 4p; 2W, 6p  
Wire-wound  
5W, 10p; 10W, 12p

### VEROBOARD

Size	0-1 Matrix	0-15 Matrix
2 1/2in x 3 1/2in	22p	16p
2 1/2in x 5in	24p	25p
3 1/2in x 3 1/2in	24p	25p
3 1/2in x 5in	27p	29p
1 7/8in x 2 1/2in	75p	57p
1 7/8in x 3 1/2in	£1	75p

Spot face cutter—39p  
Pins—either size, packet of 36 18p

### Edge connectors:


24 way, 0-1 (2 1/2in)—34p
36 way, 0-1 (3 1/2in)—24p
16 way, 0-15 (2 1/2in)—23p
24 way, 0-15 (3 1/2in)—34p

### BONDED ACRYLIC FIBRE

B.A.F. wadding, 18in wide, 1in thick. The ideal lining for speaker enclosures. 30p per yard. p. & p. one yard 12p; each extra yard 4p.
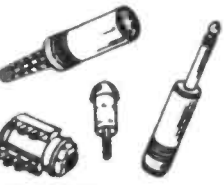
### PLUGS

Car aerial 14p  
Co-axial 9p  
D.I.N. 2 pin (speaker) 10p  
D.I.N. 3 pin 13p  
D.I.N. 4 pin 14p  
D.I.N. 5 pin, 180° 13p  
D.I.N. 5 pin, 240° 15p  
D.I.N. 6 pin 15p  
Jack, 2 1/2mm unscreened 10p  
Jack, 3 1/2mm screened 8p  
Jack, 3 1/2mm unscreened 12p  
Jack, 4 1/2mm screened 20p  
Jack, 4 1/2mm unscreened 20p  
Jack, 4 1/2mm screened 20p  
Jack, stereo, unscreened 20p  
Jack, stereo, screened 35p  
Phono, plastic top 12p  
Phono, plated metal 12p  
Wander, red or black 3p  
Banana 4mm, red or black 6p



### CAR SOCKETS

Car aerial 8p  
Co-axial, surface 8p  
Co-axial, flush 9p  
D.I.N. 2 pin (speaker) 10p  
D.I.N. 3 pin 9p  
D.I.N. 5 pin, 180° 9p  
D.I.N. 5 pin, 240° 9p  
Jack, 2 1/2mm 10p  
Jack, 3 1/2mm 10p  
Jack, 4 1/2mm 10p  
Jack, 4 1/2mm unscreened 15p  
Jack, 4 1/2mm screened 17p  
Phono, single 5p  
Phono, 2 on a strip 7p  
Phono, 3 on a strip 9p  
Phono, 4 on a strip 10p  
Wander, single, red or black 5p  
Wander, twin strip 7p  
Banana 4mm red, or black 6p

### LINE SOCKETS

Car aerial 14p  
Co-axial 9p  
D.I.N. 2 pin (speaker) 10p  
D.I.N. 3 pin 13p  
D.I.N. 5 pin, 180° 14p  
D.I.N. 5 pin, 240° 16p  
Jack, 3 1/2mm 10p  
Jack, 4 1/2mm screened 20p  
Jack, stereo, screened 34p  
Phono, plated metal 14p

### CAPACITORS

2.2pF 500V S/M 71p	0.0027µF 500V S/M 15p
3.3pF 500V S/M 71p	0.003µF 500V Cer. 3p
5pF 500V S/M 71p	0.0033µF 125V P.S. 6p
10pF 125V P.S. 5p	0.0033µF 1,000V MDC 6p
10pF 500V S/M 71p	0.0036µF 500V S/M 15p
15pF 125V P.S. 5p	0.0047µF 125V P.S. 9p
15pF 500V Cer. 4p	0.0047µF 500V Poly. 6p
18pF 500V S/M 71p	0.0047µF 1,000V MDC 6p
22pF 125V P.S. 5p	0.005µF 100V Mylar 3p
22pF 500V S/M 71p	0.005µF 500V Cer. 5p
25pF 500V S/M 71p	0.0068µF 125V P.S. 10p
27pF 500V Cer. 4p	0.0068µF 500V S/M 30p
33pF 125V P.S. 5p	0.0068µF 500V Poly. 6p
33pF 500V S/M 71p	0.0082µF 125V P.S. 10p
39pF 500V S/M 71p	0.0082µF 500V S/M 30p
47pF 125V P.S. 5p	0.01µF 18V Disc 4p
47pF 500V Cer. 4p	0.01µF 125V P.S. 10p
50pF 500V S/M 71p	0.01µF 160V Poly. 4p
56pF 500V S/M 71p	0.01µF 250V M.F. 3p
68pF 125V P.S. 5p	0.01µF 400V Poly. 5p
68pF 500V S/M 71p	0.01µF 500V Cer. 5p
75pF 500V S/M 71p	0.01µF 500V S/M 30p
82pF 500V S/M 71p	0.01µF 600V MDC 7p
100pF 125V P.S. 5p	0.01µF 1,000V MDC 9p
100pF 500V S/M 71p	0.015µF 160V Poly. 3p
100pF 500V Cer. 5p	0.015µF 400V Poly. 3p
120pF 500V S/M 71p	0.02µF 100V Mylar 3p
150pF 125V P.S. 5p	0.022µF 18V Disc 5p
150pF 500V S/M 71p	0.022µF 250V M.F. 3p
180pF 500V Cer. 5p	0.022µF 400V Poly. 3p
200pF 500V S/M 71p	0.022µF 600V MDC 7p
220pF 125V P.S. 5p	0.022µF 1,000V MDC 10p
220pF 500V S/M 71p	0.033µF 250V M.F. 4p
250pF 500V S/M 71p	0.033µF 400V Poly. 4p
270pF 500V S/M 71p	0.047µF 12V Disc 6p
300pF 500V Cer. 5p	0.047µF 160V Poly. 3p
330pF 125V P.S. 5p	0.047µF 250V M.F. 3p
330pF 500V S/M 71p	0.047µF 400V Poly. 4p
390pF 500V S/M 71p	0.047µF 600V MDC 8p
470pF 125V P.S. 5p	0.047µF 1,000V MDC 10p
470pF 500V S/M 71p	0.1µF 30V Disc 6p
500pF 500V S/M 71p	0.1µF 250V M.F. 4p
560pF 500V S/M 71p	0.1µF 400V Poly. 5p
680pF 125V P.S. 5p	0.1µF 600V MDC 10p
680pF 500V S/M 71p	0.1µF 1,000V MDC 14p
820pF 500V S/M 71p	0.15µF 250V M.F. 5p
0.001µF 100V Mylar 3p	0.22µF 160V Poly. 6p
0.001µF 125V P.S. 6p	0.22µF 250V M.F. 5p
0.001µF 400V Poly. 3p	0.22µF 400V Foil 10p
0.001µF 500V S/M 10p	0.22µF 1,000V MDC 15p
0.001µF 500V S/M 10p	0.33µF 250V M.F. 8p
0.001µF 500V S/M 10p	0.47µF 250V M.F. 8p
0.001µF 1,000V MDC 6p	0.47µF 1,000V MDC 15p
0.0015µF 400V Poly. 3p	0.47µF 250V M.F. 5p
0.0015µF 500V S/M 10p	1.0µF 250V M.F. 15p
0.0015µF 500V Cer. 5p	
0.0018µF 500V S/M 10p	
0.002µF 100V Mylar 3p	
0.002µF 500V Cer. 5p	
0.0022µF 125V P.S. 6p	
0.0022µF 500V S/M 10p	
0.0022µF 1,000V MDC 6p	

Note:  
S/M=silver mica 1% tol.  
P.S.=polystyrene 2 1/2% tol.  
MDC—a.c. rating = 300V.  
M.F.—Mullard min. foil.  
Cer.=ceramic.

MAIL ORDERS: Some items have a post and packing charge shown against them. Where p. & p. is not shown the charge is 12p for any selection. When both classes of goods are ordered the charge is 12p plus any p. & p. charges shown. (Overseas extra.) Telephone 01-692 4412

## now YOU can CATCH SHOALS OF BIG FISH with new electronic miracle

special introductory offer £2.50

First time marketed in England, this exciting electronic instrument the "Decoytronic" is the one responsible for starting the electronic fishing craze in the U.S.A. just recently. Uses ingenious double-action method of attracting all kinds of fish from hundreds and hundreds of feet away... saltwater or freshwater. Why this device is so fantastically successful is because it actually imitates the sound of wet insects milling about the surface. These sound waves spread out hundreds of feet in all directions. Although this peculiar sonic frequency won't sound like much to you—to all the fish in the area it's their dinner bell! But that's not all... electroluminescence neon tubes continually flicker intermittently, penetrating the area for hundreds of feet around, at a frequency fish are unable to resist. The fish mistake this flickering glimmer for soft phosphorescence glow given off by Plankton... a favourite delicacy of most fish! All you do is switch on, lower into the water (it's completely water resistant) allow around 5 minutes—then start reeling 'em in. We'll bet you won't be able to reel 'em in fast enough. Self-contained batteries last ages—cost pennies. Kit of all parts including special step by step a.b.c. directions only £2.50 + 25p. P. & P. (Parts available separately).

## BUILD 5 RADIO AND ELECTRONIC PROJECTS

ONLY £2.45



Amazing Radio Construction Set! Become a radio expert for £2.45. A complete Home Radio Course. No experience needed. Parts including simple instructions for design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. Send £2.45 + 20p p. & p.

## SOOTHE YOUR NERVES RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION

SOOTHS YOUR NERVES!

THE RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HATE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones. Components: nuts, screws, wire, etc. no soldering. £2.75 + 25p p. & p. Parts available separately.



ONLY £2.75

## UNIQUE RADIO FOR BEDROOM OR OFFICE

No batteries, no electricity, ONLY £1.70 never wears out

Tune in your favourite programmes or the news, or sports in the Office or in your bedroom. Uses sensitive, germanium diode originally evolved from Wartime radar. Never buy a battery. Never use electricity. Never replace. Covers all medium waves. Clear beautiful tone. Size 4 1/2" x 11" in beautiful case. ONLY 7 CONNECTIONS AND IT'S WORKING. No soldering necessary. CAN BE BUILT ALMOST BLINDFOLD IN UNDER 15 MINUTES! Ideal for absolute beginner from 8 years of age upwards. SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS, ONLY £1.70 + 20p. P. & P. for all parts including beautiful case. Germanium semi-conductor, tuning condenser, personal phone, wire, nuts, screws. SIMPLE AS A.B.C. INSTRUCTIONS (Parts available separately).

WORKING. No soldering necessary. CAN BE BUILT ALMOST BLINDFOLD IN UNDER 15 MINUTES! Ideal for absolute beginner from 8 years of age upwards. SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS, ONLY £1.70 + 20p. P. & P. for all parts including beautiful case. Germanium semi-conductor, tuning condenser, personal phone, wire, nuts, screws. SIMPLE AS A.B.C. INSTRUCTIONS (Parts available separately).

## "READ PEOPLE'S MINDS"—TEST THEIR NERVES—BEAT THEM AT CARDS, ETC. WITH THIS ASTONISHING ELECTRONIC BRAIN BOX only £2.87

With this "Brain-box" you will be able to perform mind-boggling feats. THE MIND READING DEVICE will make people swear you have "telepathic" powers. THE AMAZING CARD TRICK UNIT completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. THE ELECTRONIC NERVES TESTER puts your friends to a very lively test. It gives out fall and finish signals (the winner is the person with lowest number of fall signals). Can be adjusted from the weakest to strongest person. THE ELECTRONIC MAZE tests the mental ability of the player because it uses psychology with an electronic twist to it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof. Size 18" x 12" x 6" (Max.). You can play all these games and more beside after building the "Brain box". No soldering, you get pictorial, easy as a.b.c. step-by-step simple instructions. ONLY £2.87 + 33p. p. & p. for all parts including chassis, switches, styms, signalling lights, wire, nuts, screws, etc. etc. Uses standard battery. Presentation Box 33p. extra as illus. if reqd. (PARTS AVAILABLE SEPARATELY) FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.



## the amazing "Phototron" SOUND OPERATED FLASH

Take flash pictures at the exact instant of the bursting of a balloon. A champagne cork leaving the bottle. The split second a hammer strikes a light bulb. The mind boggles at the possibilities of the "Phototron" ... the only limit is your imagination. Now that inexpensive flash guns

ONLY £4.50

are on the market in quantity, it has made possible, with the help of effects, only strictly limited to the professionals. The duration of an electronically produced flash is extremely brief and normally measured in Millionths. Now, providing the camera shutter is left open in a dark or subdued light, it is the timing of the flash that determines what is imprinted on the film—not necessarily anything done by the camera. As electronic flash guns are fired by making a switched connection then it becomes obvious that one of the latest Silicon Controlled Rectifier's can be used. If we make this S.C.R. operate by sound effects can be captured forever on film. Easily built in a couple of hours or so, the "Phototron" is fully solid state, uses self contained PP3 battery. No soldering necessary using our special printed circuit terminal board (pat. Applied for). All parts including special pictorial step-by-step plans, transistors, microphone, S.C.R., potentiometers, switches, test lamp, case, nuts, screws, etc. etc. ONLY £4.50 + 25p. P. & P. Made up must be worth at least £10. (parts available separately).

## ELECTRONIC ORGAN

ONLY £3.25



Don't confuse with ordinary electronic organs that simply blow air over mouth organ type reeds etc.

Fully transistorised. SELF-CONTAINED LOUDSPEAKER. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live portable electronic organ. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED. No soldering, simple as ABC to make. Anyone over nine years can build it easily in one hour following the fully illustrated, step-by-step, simple instructions. ONLY £3.25 + 25p. p. & p. for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

## READY BUILT AND TESTED

### TREASURE LOCATOR MODULE

ONLY £4.95

FULLY TRANSISTORISED PRINTED CIRCUIT BOARD MODULE. Ready built and tested—just plug in a PP3 battery and phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR. EASILY PENETRATES THROUGH EARTH, SAND, ROCK, WATER, ETC.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN £4.95 + 30p cart. signal.



## Eavesdrop on the exciting world of Aircraft Communications—

### V.H.F. AIRCRAFT BAND CONVERTER ONLY £2.85



Listen in to AIRLINES, PRIVATE PLANES, JET-PLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness of talk domes. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHERBROW, GATWICK, LUTON, RINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portable). NO CONNECTIONS! WHATEVER RECD. ETC. SEND ONLY £2.85 + 20p. p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

### INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY £3.25

Do you wake up in the night and can't get off to sleep again? Would you like to be gently soothed off to satisfying sleep every night? Then build this ingenious electronic sleep inducer. It even steps by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated, but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. All transistor. No knowledge of electronics or radio needed. Step-by-step instructions included. No soldering necessary. Kit includes case, nuts, wire, screws, etc. SEND £3.25 + 25p p. & p. (parts available separately).



## FIND BURIED TREASURE!

### Transistorised Treasure Locator



This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC. Extremely sensitive will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one shot evening by anybody from nine years of age upwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. etc. p. & p. (Sections handle as illustrated 95p. extra). Parts available separately. Made up looks worth £15.

ONLY £2.85

### SHORTWAVE TRANSISTOR RADIO

ONLY £2.75

Anyone from 9 years up can follow the step by step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins.—RUSSIA, AFRICA, USA, SWITZERLAND, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4" x 11" ONLY £2.75 + 20p p. & p. Kit includes cabinet, screws, instructions. etc. (Parts available separately).



## AMAZING MAGIC MUSIC BOX

make electronic music waving your hands about only £2.75

Everyone's heard the weird, wonderful, but beautiful music used in Science Fiction Films, Horror Films etc., also on Radio and Television. This unearthly, eerie music is almost always produced by a little known electronic device measuring only a few inches... called a Theremin. All you have to do is switch on your radio (almost any type will do) and place the Theremin close by. Switch on the Theremin and proceed to wave your hands mysteriously in the air like a magician. The most fantastic musical sounds are then produced, and with a little practice people can learn to play all the well known tunes. Apart from it's musical value, it's small size allows it to be used to best advantage at parties, gatherings of friends etc., where it attracts tremendous interest. Provides hours and hours of pleasure to young and old. Uses standard PP3 battery which lasts ages. The 3 Transistor Circuit, though fairly advanced is simple to build with our pictorial step-by-step plans. No soldering necessary. Easily built in an hour or so using our special printed circuit terminal board (Pat. Applied For). All parts including nuts, bolts, case etc. ONLY £2.75 + 25p. P. & P. (Parts available separately).



## INGENIOUS ELECTRONIC SINGING & WARBLING CANARY only £4.50

Actually whistles & warbles like a real live Canary! Amazing circuitry faithfully reproduces the Canary's magnificent song. Just switch on and it will warble, then several seconds later shutting off for a second or two—only to start automatically again in a few seconds. People listen to the delightful song all day and never get bored! Relax, as the sweetest nerve-soothing bird-song takes you to leafy woods and glades. Provides countless hours of joy to young and old alike. Standard self-contained battery lasts ages. Easily built in an hour printed circuit terminal board (pat. applied for) transformers, loudspeaker, transistors, nuts, screws, wire, etc. + case (which fits under cage—cage and toy bird not supplied) ONLY £4.50 + 25p. P. & P. (parts available separately).



# Solder a friendship! Give Antex this Christmas

**Model X25** \*

220-240 Volts or 100-120 Volts  
The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".  
Tested at 1500v. A.C.  
This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16" Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be removed. **PRICE: £1.75 (rec. retail)**  
Suitable for production work and as a general purpose iron.

**Model CCN** \*

220 volts or 240 volts  
The 15 watt miniature model CCN, also has negligible leakage.  
Test voltage 4000v. A.C.  
Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"  
4 other bits available, 1/8", 3/16", 1/4" and 1/16"  
**PRICE: £1.80 (rec. retail)**  
OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8" **£1.95 (rec. retail)**

**Model CN** \*

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 1/16" to 3/16"  
Voltages 240, 220, 110. 50 or 24  
**PRICE £1.70 (rec. retail)**

**Model SK.1 Kit**  
contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.  
**PRICE £2.75 (rec. retail)**

**Model MES Kit**  
Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder". **PRICE £1.95 (rec. retail) \***

**Model SK.2 Kit**  
contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, and "How to Solder" booklet.  
**PRICE £2.40 (rec. retail)**



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from:—  
**ANTEX LIMITED FREEPOST**  
(no stamp required) **PLYMOUTH,**  
**PL1 1BR** Tel: 0752 67377

- Please send the ANTEX colour catalogue.  
 Please send the following

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I enclose cheque/P.O./Cash (Giro No. 258 1000)

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

EE12



# everyday electronics

PROJECTS...  
THEORY.....

## IN ASSOCIATION

Quite a number of leisure activities rely upon electronics—to some greater or lesser degree. And the number seems to be steadily increasing. There are also certain activities which are entirely inseparable from electronics, since they depend upon some branch of this technology for their very existence.

Radio control of models is one such example. This very popular hobby brings the model maker with his particular skills and often artistic, even romantic, eye for points of detail, into association with the electronics enthusiast.

## RADIO CONTROL

The subject *Radio Control of Models* was introduced in a general feature last month. We now present in this issue a detailed constructional design for a single-channel model control transmitter. This will be complemented by a second article next month describing a simple model control receiver.

These designs are necessarily of a fairly basic character, within the scope of this magazine's declared policy. Thus the functions they permit are of a somewhat limited nature, but will provide reward and pleasure to the builder and operator.

No doubt these projects will launch many a reader into this associated field of radio control, where the possibilities for the use of more advanced electronics are quite wide and extensive. We hope these articles may also induce a number of model enthusiasts to take-up elec-

tronics generally, and thus discover an even wider range of applications.

## BBC JUBILEE

Mention headphones to our senior readers and this will surely conjure up memories of listening-in to the wireless in those pioneer days of broadcasting. The faint, thin-sounding voices and orchestras borne over the mysterious ether were far, far removed from hi fi. Yet no present day audiophile with the very latest in four-channel headphones clamped on his head listening to quadraphonic or surround sound will have a more immense and unforgettable thrill than those early listeners experienced during the first broadcasts half a century ago.

The ancestor of today's all important transistor was also in at the start of radio. Reference to twiddling the cat's whisker will be incomprehensible to our younger readers, and certainly will cause some to believe we are as old as Methuselah; so we will desist.

We wish the BBC, or "Auntie" if you prefer, hearty congratulations. To say "we don't know what we would do without you" is just the plain truth—very few could say in all honesty that they are immune from the blandishments of the loudspeaker or TV tube.



Our January issue will be published on Friday, December 15

EDITOR F. E. BENNETT ● ASSISTANT EDITOR M. KENWARD ● B. W. TERRELL B.Sc.  
ART EDITOR J. D. POUNTNEY ● P. A. LOATES ● S. W. R. LLOYD  
ADVERTISEMENT MANAGER D. W. B. TILLEARD

© IPC Magazines Limited 1972. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.  
All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.  
Subscription Rates including postage for one year, to any part of the world, £2.35.  
Everyday Electronics, Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.

**EASY TO CONSTRUCT  
SIMPLY EXPLAINED**



VOL. 1 NO. 14

DECEMBER 1972

## CONSTRUCTIONAL PROJECTS

<b>RADIO CONTROL TRANSMITTER</b> <i>Simple single channel transmitter</i> by D. Bollen	750
<b>BIT SAVER</b> <i>Prevents pitting of a soldering iron bit</i> by T. P. Manning	761
<b>ELECTRONIC GUITAR</b> <i>Pick-ups and fittings for the Beta</i> by Brian W. Terrell	766

## GENERAL FEATURES

<b>EDITORIAL</b>	748
<b>FIFTY YEARS</b> <i>An exhibition to mark the anniversary of the BBC</i>	755
<b>ELECTRONICS AT SEA</b> <i>Fishing Vessels and Coasters</i> by W. Machonachie	756
<b>SHOP TALK</b> <i>Component buying and new products</i> by Mike Kenward	760
<b>GUIDE TO CIRCUIT SYMBOLS</b> <i>Part 6—Crystal, Semiconductors, Block Symbols</i>	764
<b>BASIC ELECTRICITY</b> <i>Part 2—Current Flow in Liquids</i> by Maureen Birch	771
<b>RUMINATIONS</b> <i>London Calling</i> by Sensor	774
<b>DEMO CIRCUITS</b> <i>I The Emitter Follower</i> by Mike Hughes	777
<b>THEY MADE THEIR MARK</b> <i>No. 7 Henry</i> by J. E. Gregory	782



## Demo Deck Reprint

A reprint of the Demo Deck article, including one experiment from *Teach-in*, is now available price 15p, postage and packing 3p. To receive a reprint send a postal order or cheque for 18p, made payable to IPC Magazines Ltd., to: The Receiving Cashier (E.E. Demo Deck), IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2.

## A simple single channel transmitter for radio control of a boat or aeroplane.

**T**HIS single channel model control equipment for novices is probably the simplest that can be devised while still satisfying the range requirements of model aeroplane enthusiasts and the requirements of the Post Office.

The transmitter and receiver are both assembled on Veroboard, for ease of construction, and the receiver offers direct, relayless operation of a rubber or clockwork driven escapement, or a motorised actuator. Maximum ground range in open country with the prototype equipment was one mile.

Due to the small size of the receiver (detailed next month) we do not advise anybody who has not yet constructed any equipment to embark on the building of this project.

### WORKING PRINCIPLE

The transmitter supplies 27MHz radio frequency energy (carrier) which is switched on and off (modulated) by an audio frequency tone of 500Hz. If modulation was not used, it would be much more difficult to amplify the received signal and obtain a useful working range. The receiver detects the modulated carrier and converts this into a d.c. current whenever the transmitter key is pressed.

The crystal, X1, used in the prototype transmitter (and receiver next month) had a third harmonic frequency of 27.145MHz but any frequency in the range 26.970-27.270MHz may be used. There are 13 frequency bands within this range, each separated by 25kHz. The 27MHz frequency band is allocated by the Post Office for this and similarly operated transmitters; see the *Radio Control* article in the November issue of *EVERYDAY ELECTRONICS*. (This issue is no longer available from the publishers).

The block diagram of the complete control system is shown in Fig. 1. The transmitter carrier is generated by a low power, crystal controlled oscillator, which does not need to be calibrated to function at the correct frequency.

A second oscillator in the transmitter delivers a square wave tone of 500Hz to a diode gate via a keying switch. The diode gate is situated between the crystal controlled oscillator and the power amplifier and is opened and closed 500 times per second whenever the keying switch is pressed.

With the keying switch off, virtually no radio frequency energy reaches the power amplifier, but when the keying switch is held on short bursts of 27MHz energy are passed to the power






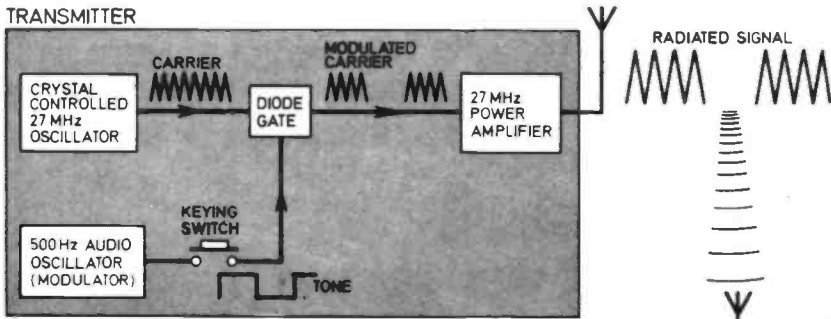


Fig. 1. Shows the block diagram of the complete control system.

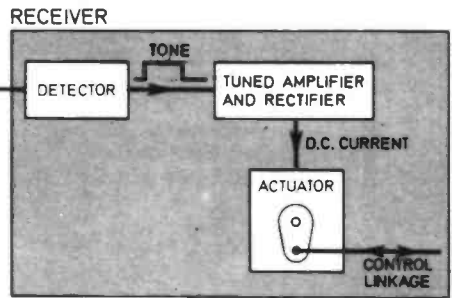

amplifier and thence to the aerial.

**RECEIVER BASICS**

In the receiver section of Fig. 1, a highly sensitive single transistor detector first amplifies the weak signal from the aerial and then extracts the 500Hz tone from the carrier. Following the detector stage is a tuned amplifier, which rejects frequencies above and below 500Hz, thus reducing interference from electric motor brushes and other sources.

Finally, the 500Hz a.c. output from the tuned amplifier is converted into a steady d.c. current (rectified) of sufficient power to operate an electromechanical device.


**TRANSMITTER CIRCUIT**

The complete transmitter circuit is shown in Fig. 2. Modulator transistors TR1 and TR2 form a multivibrator oscillator which functions at a frequency determined by the values of C1, C2, R2, and R3. When S1 is keyed, this switches on the modulator and operates the diode gate.

It will be noticed that the collector load of TR2 is made up of the combined resistance of R4 and R8, and thus the diode gate switching voltage appears at the junction of these two resistors.

Looking next at the crystal controlled oscillator TR3, this is broadly tuned by C3 and L1 to approximately 27MHz. Crystal X1 serves the dual role of providing a positive feedback path to make TR3 oscillate, and constrains the circuit to oscillate only at a fixed frequency, which is marked on the crystal.

Fig. 2. The complete circuit diagram of the transmitter.

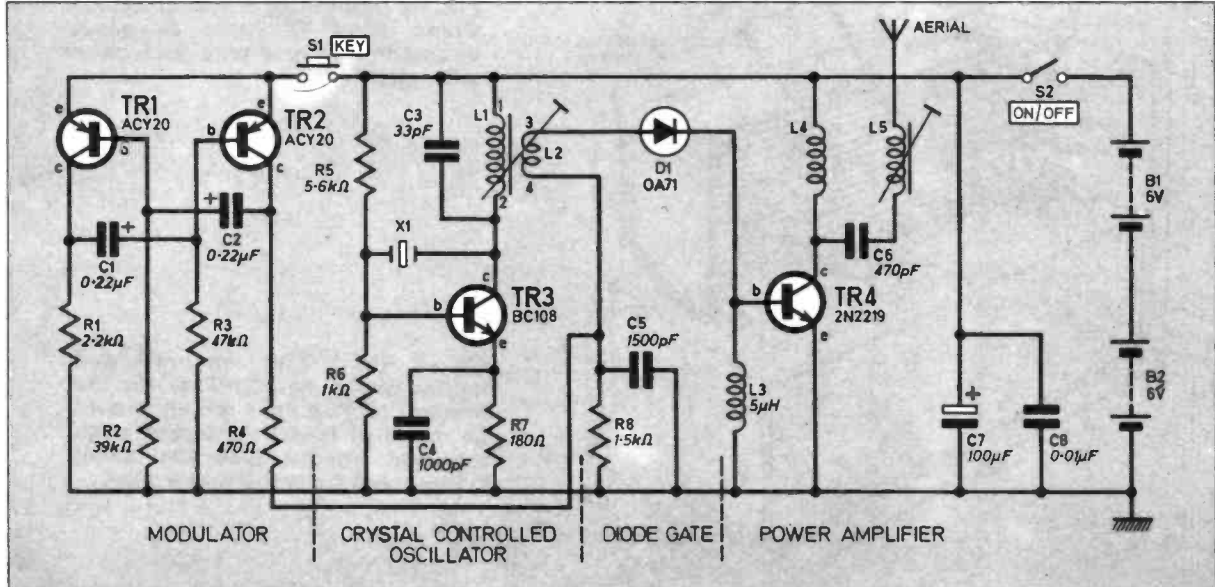

# RADIO CONTROL TRANSMITTER

Fig. 3a. (right) L1 and L2 coil winding details. (1) Close wind 20 turns 28 s.w.g. enamelled copper wire. (2) Cover with plastic insulating tape. (3) Close wind 5 turns 28 s.w.g. enamelled copper wire and then solder the finish of L1 to pin 2.

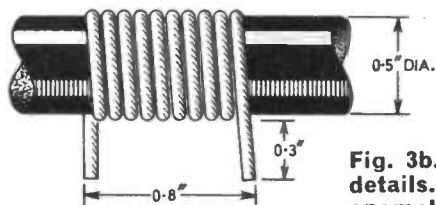
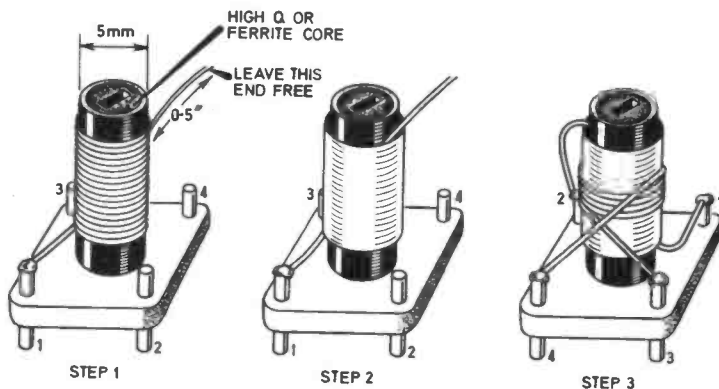


Fig. 3b. (left) L4 winding details. 10 turns 16 s.w.g. enamelled copper wire on 0.5in. mandrel.

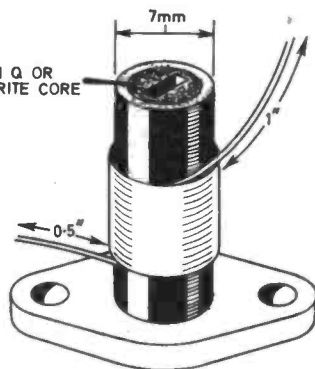


Fig. 3c. (above) L5 winding details. Close wind 12 turns 28 s.w.g. enamelled copper wire and cover with plastic tape.

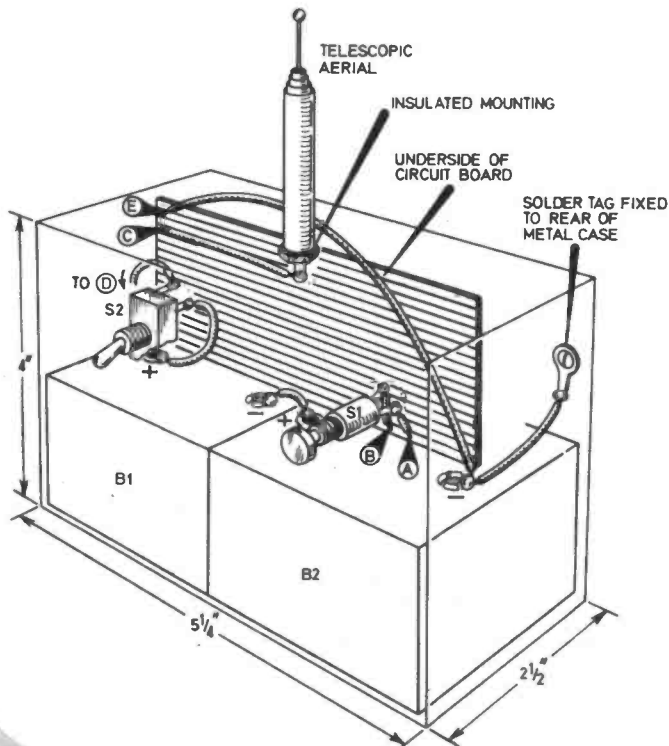


Fig. 5. (left) The recommended layout of the components for the transmitter in a case which should be made of metal. Note the earth tag and ensure that the aerial is insulated from the metal case.

The ferrite or high 'Q' dust slug in L1 coil former therefore serves only to bring L1 to resonance with the crystal frequency, so that maximum output is developed across the secondary winding L2.

Radio frequency energy from L2 is taken via diode D1 to the base of TR4, with a return path provided by capacitor C5.

The coil L3 prevents the low frequency modulator output from reaching the base of TR1, while allowing the high frequency carrier to pass unhindered. For maximum efficiency, TR4 is operated in the "class C" mode, that is to say, with collector current flowing during less than one half of an a.c. cycle, hence the absence of base biasing resistors.

The action of the modulator is to forward bias the diode D1 whenever TR2 conducts, and to allow D2 to become reverse biased by the output from L2 when TR2 is off. When reverse biased, D1 blocks the input to TR4 base.

Power amplifier TR4 steps up the output from the crystal oscillator and feeds this energy to the aerial via C6 and L5. The purpose of L5 is to match the aerial impedance to the impedance of TR4 collector. L4 merely serves as a broadly tuned collector load.

Capacitors C7 with C8 in parallel are necessary to prevent instability by providing a low impedance path to audio and radio frequency energy across the relatively high impedance batteries.

## COIL CONSTRUCTION

Commence construction by winding 10 turns of 16 s.w.g. enamelled copper wire for L4 on a 0.5in. diameter mandrel, see Fig. 3b. A piece of wood dowel or metal tubing would serve. The spacing between L4 turns can be adjusted after removal of the mandrel.

With sandpaper or a razor blade, remove the enamel coating from the ends of L3 and carefully tin the bare copper with solder.

For L5, close-wind 12 turns of 28 s.w.g. enamelled copper wire on a 7mm diameter former, and anchor the winding with a wrapping of plastic insulating tape. Remove enamel from the ends of L5 leads and tin with solder (Fig. 3c).

After practise with L4 and L5, sufficient confidence will have been gained for a start to be made on the more complicated L1 and L2 coils.

First, bare and tin the end of a reel of 28 s.w.g. enamelled wire and solder this to pin 1 on the coil former, see Fig. 3a. Close-wind 20 turns, as neatly as possible on the 5mm former and secure the windings with a layer of plastic insulating tape. The 0.5in. end of L1 should be left free while winding L2.

For L2, clean and tin the end of the wire on the reel, and solder this to pin 3, then close wind five turns over the insulating tape covering L1, approximately in the middle of the 5mm former, and then anchor the end of L2 to pin 4. To complete the coil, clean and tin the free end of L1 and solder to pin 2.

## Components . . . .

### Resistors

R1	2.2k $\Omega$
R2	39k $\Omega$
R3	47k $\Omega$
R4	470 $\Omega$
R5	5.6k $\Omega$
R6	1k $\Omega$
R7	180 $\Omega$
R8	1.5k $\Omega$

All  $\frac{1}{2}$  watt  $\pm 10\%$  carbon

### Capacitors

C1	0.22 $\mu$ F tantalum bead
C2	0.22 $\mu$ F tantalum bead
C3	33pF polystyrene
C4	1,000pF polystyrene
C5	1,500pF polystyrene
C6	470pF polystyrene
C7	100 $\mu$ F elect. 15V
C8	0.01 $\mu$ F polyester

### Semiconductors

TR1	ACY20 germanium <i>pnp</i>
TR2	ACY20 germanium <i>pnp</i>
TR3	BC 108 silicon <i>npn</i>
TR4	2N2219 silicon <i>npn</i>
D1	OA71

SEE  
**SHOP  
TALK**

### Switches

S1	Single-pole push to make release to break
S2	Single-pole toggle

### Miscellaneous


X1	Subminiature third overtone 27MHz crystal with socket (see note 1)
L3	Radio frequency choke 5 $\mu$ H—1A TV type choke

B1, B2 PP1 6V (2 off)

Coil formers: for L1, L2, 5mm diameter, length 16 mm, printed circuit mounting with ferrite or high Q core (see note 2); for L5, 7mm diameter, length  $\frac{3}{8}$ in.,  $\frac{1}{2}$ in. fixing centres with ferrite or high Q core (see note 3); Veroboard 4.7in. x 1.7in. x 0.1in. matrix; terminal pins; 16 s.w.g. enamelled copper wire; 28 s.w.g. enamelled copper wire; metal box 5in. x 4in. x  $2\frac{1}{2}$ in. minimum dimensions; telescopic aerial 3 $\frac{1}{2}$  to 4 feet extended; m.e.s. bulb holder; 6V 60mA m.e.s. bulb; TO5 heat sink.

Note 1. Henry's Radio type 2mm with socket  
Note 2. Henry's Radio type 1 with 1f ferrite core

Note 3. Home Radio CR4 with Z81B core

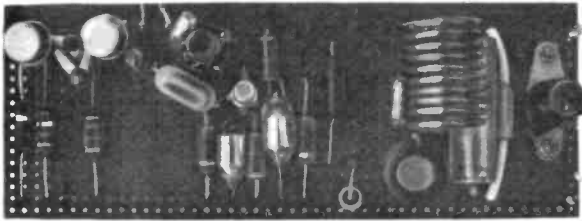

## ASSEMBLY OF TRANSMITTER COMPONENTS

Transmitter components are assembled on a piece of 0.1in. matrix Veroboard measuring 4.7in. x 1.7in., see Fig. 4. Terminal pins are used to mount L1, L2, the crystal holder, and L4, and also as anchor points for circuit board leads (labelled A-E).

Cut the circuit board to size and drill two holes for the L5 mounting screws. Break the copper strips on the underside of the board with a spot-face cutter as detailed in Fig. 4. The extra cutaways around the collector of TR4 and the connection to L5 are to minimise stray capaci-

tance. Insert and solder all terminal pins, and then proceed to mount all components, starting at the R1 end, but solder the semiconductors in position last of all.


The following important points should be observed during assembly: make sure that the polarity of C1, C2, D1, and C7 is correct; the crystal should not be in its holder when this is soldered to the terminal pins; avoid prolonged contact with the soldering iron when mounting semiconductors and use a heatshunt; fit TR4 heat sink prior to mounting; check that stray blobs of solder do not bridge any of the copper strips on the underside of the circuit board.

Thoroughly check-out all connections before proceeding. The layout should not be altered in any way.

## ALIGNING THE TRANSMITTER

A Model Control Licence should be obtained before operating the transmitter. An application form is available from the Ministry of Posts and Telecommunications, Radio Regulatory Division

Fig. 4. Layout and wiring of the transmitter circuit board. The layout should be carefully followed and not altered in any way.

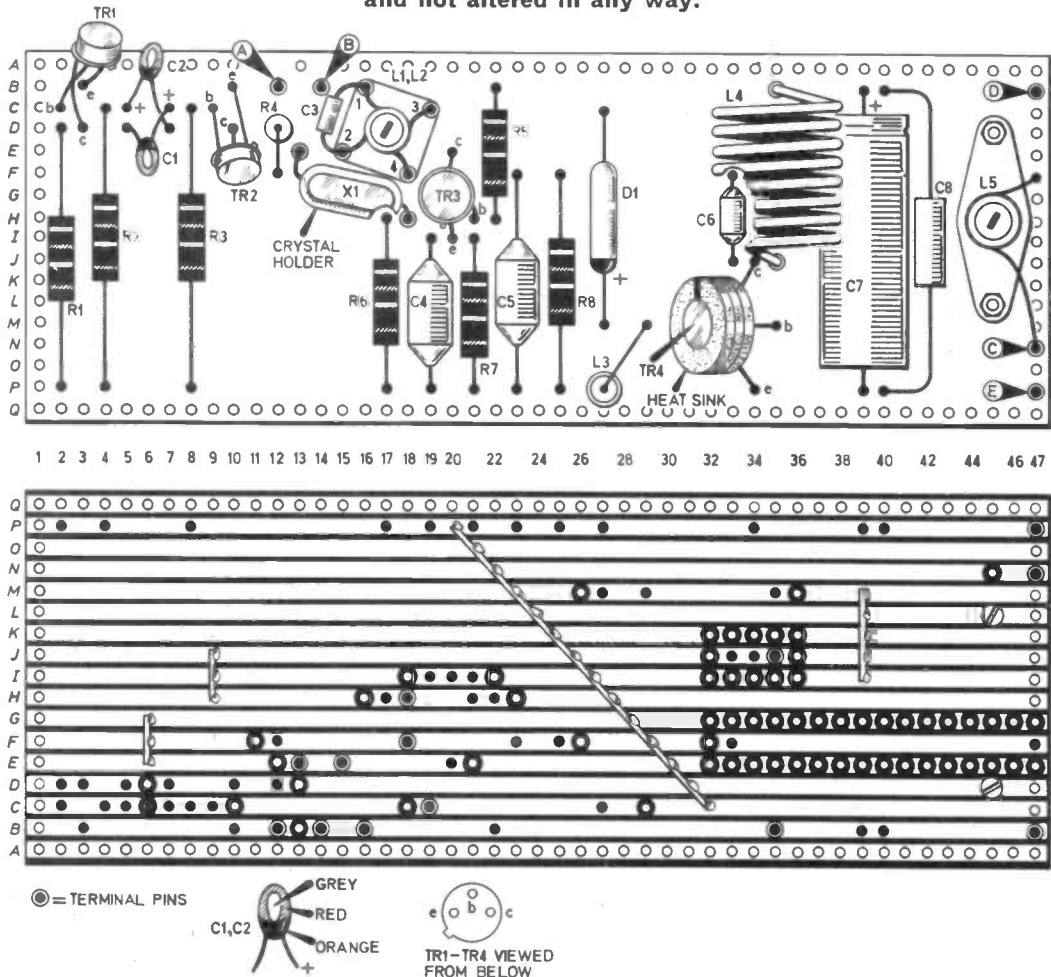

(Amateur and Special Licencing Branch), Waterloo Bridge House, Waterloo Road, London S.E.1. The licence costs £1.50 for a five year period.

Solder a temporary shorting link across terminal pins A and B on the transmitter circuit board, and attach insulated battery leads to pins D and E. Connect one terminal of an m.e.s. bulb holder to pin C with a short length of insulated wire.

Place the transmitter circuit board on an insulated surface, preferably on a floor, and hook up a three or four foot vertical length of insulated wire as a temporary aerial to the remaining terminal of the m.e.s. holder. Insert a 6V 60mA bulb in the holder to monitor aerial current. If a 0-100mA meter is available, this could usefully be employed to measure battery consumption, in series with the positive battery lead, but this is not essential. Adjust both coil slugs so that they are flush with the top of their formers.

Connect the negative end of battery B1 to the positive terminal of B2 and the negative terminal of B2 to pin E and dab the wire from pin D on the positive terminal of B1 while adjusting L4 slug for aerial bulb glow; this technique will prevent the destruction of TR4 in the event of a circuit fault.

If the bulb glows and TR4 runs just warm, the positive battery lead can be left in position. Now trim L5 and L1, L2 slugs for the brightest bulb glow. When the wire link between pins A and B is cut the bulb should cease to glow. Current consumption is shown in Table 1.

In the event of no bulb glow, overheating of

**Table 1: Specifications**

Transmitter	
Idling current	20mA
With modulation	70mA
Approximate aerial input power	250mW
Power supply	12V
Modulation frequency	500Hz
Receiver	
Weight with leads	1oz
Size	2½in. x 7in. x ¾in.
Approximate output	3V at 0.5A
Power supply	4.8V
Idling current	15mA

TR4, or abnormal current consumption, check the circuit board for faults.

### FINAL ASSEMBLY

The transmitter circuit board is now ready for installation in a metal box, complete with S1, S2, batteries and a telescopic aerial (Fig. 5).

For final adjustment, place a bulb in series with the aerial as before, and trim L5 for maximum output with the aerial held well away from buildings or trees. The bulb is then replaced by a short wire link straight from pin C to the aerial. Secure tuning slugs with a dab of paint.

Part 2 next month deals with the receiver.

*The model boat shown in the front cover photograph was kindly loaned by Beatties of London (Models), 112 High Holborn, W.C.1.*

## Fifty Years

**B**.B.C. 50—The Technical Story is the title of a two-month exhibition staged at Mullard House, Torrington Place, London, W.C.1., jointly by Mullard and the B.B.C. It was opened by Lord Hill, chairman of the B.B.C., on Thursday November 2 and will run until December 21.

The exhibition, which has the full support and co-operation of the Post Office, is complementary to that organised by the B.B.C. at the Langham, near Broadcasting House, and its aim is four-fold: to show how technical innovation has contributed to the growth of broadcasting, to stress the pioneering effort that has gone into it, to give the public a better idea of the technical side of broadcasting and to show how research and development are continuing for the future.

The Mullard House exhibition is open to the public from 12 noon to 9 p.m. on Mondays, Thursdays

and Fridays and 12 noon to 6 p.m. on Tuesdays, Wednesdays and Saturdays. Admission is free.

The company's role in colour television is illustrated by a feature called Colour TV Look-In. Housed in a separate room, this is a six-minute presentation—using film, video tape, recorded sound, programmed lighting and television itself—which tells the story of colour television and Mullard's contribution in simple everyday terms.

A major exhibit in the section dealing with current sound and vision broadcasting techniques is a working demonstration—in which the public can take part—of colour separation overlay. This technique enables the image of a person appearing on the TV screen to be superimposed on a variety of pictorial backgrounds. He can be shown, for example, on the moon or in the depths of the jungle, without ever leaving the studio.


A demonstration of three dimensional television, broadcasting from satellites, cameras that can see in the dark and Post Office plans for future transmission techniques are among

exhibits that give visitors a peep into the future. There is also a viewing lounge where they can relax and watch colour programmes.

A programme of talks and films is being presented in the Mullard House Theatre throughout the run of the exhibition. A total of 23 films will be shown, covering a variety of subjects. They range from a behind-the-scenes story of the Post Office Tower to the operation of a colour TV camera. Thirty-three talks will be given by BBC, Mullard and other specialists on topics ranging from satellite TV broadcasting to digital techniques and, in a more general vein, from running a local radio station to organising TV sports coverage.

A detailed programme of talks and films, together with a timetable, is available; tickets for particular films/talks on specific days can be applied for. All requests regarding programmes and tickets should be made to Mrs. Doreen Smith, Mullard Ltd., Mullard House, Torrington Place, London, WC1E 7HD. No tickets are required for admission to the exhibition itself.

# Electronics

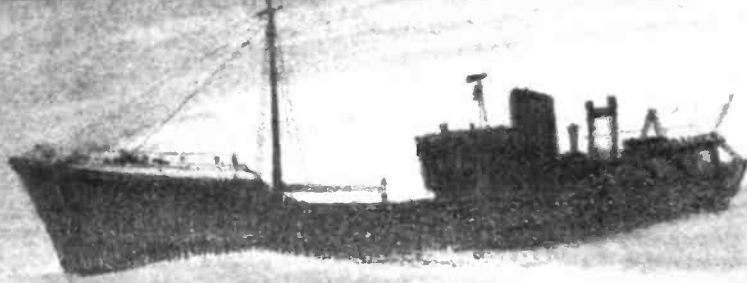

## at Sea

### **Fishing Vessels and Coasters** By **W. Machonachie**

**A** PREVIOUS article in this magazine dealt with the ways in which electronic equipment is employed on board merchant ships of 1,600 tons or more—most of them, in fact, ocean-going vessels much greater in size than this, and only passing mention was made of smaller ships in Class III (500 tons or more but less than 1,600 tons) and Class IV (300 tons or more but less than 500 tons) and of fishing vessels.

#### **MINIMUM REQUIREMENTS**

So far as the requirements of the Merchant Shipping (Radio) Rules are concerned ships in Classes III and IV, are, broadly speaking, treated alike in that they must be fitted with approved radio-telephone (R/T) installations capable of reception on 2182 kHz and at least 20 other spot frequencies between 1605 and 3800 kHz, and of transmission on 2182 kHz and at least eight other spot frequencies, while a device capable of generating the R/T two-tone alarm signal must also be fitted. As an alternative they may, if their owners so desire, have an approved radio telegraph installation, in which case the crew must include a qualified radio officer.

These are, it must be emphasised, the minimum requirements to comply with the law. In practice relatively few small ships do have telegraphy installations and radio officers, with the exception of some passenger-carrying craft, but on the other hand a great many of them—one might almost say the majority—do fit electronic equipment well in excess of the mandatory minimum.

Radar is, as might be expected, an almost universally chosen "extra", possibly because little ships sailing in busy coastal waters like to see the big fellows in case the big fellows fail to see them. Decca Navigator receivers are also

widely used in coastal waters, as are echo sounders, while v.h.f. radio-telephones are invaluable for short range communication, since such ships are on short voyages between ports.

Also, because these ships are seldom out of range of shore TV transmissions for very long, a television receiver may usually be found on board. Increasing use is made nowadays of relatively simple intercom. systems, even though it might seem that the man on the bridge has only to shout to be heard all over the ship.

#### **FISHING FLEET**

Fishing vessels have a separate set of radio rules of their own and the statutory require-

**A trawlerman making a radio-telephone call with his s.s.b. h.f. and m.f. equipment.**



ments for their electronic installations are very different and much less stringent, although the Holland-Martin Report on safety of fishing vessels made a number of recommendations which may have the effect of tightening the regulations in a number of ways.

So far as British-flag fishing boats are concerned compulsion to carry specific minima applies in general only to those over 140 feet long, except for portable survival craft radio, which must be carried by all boats over 80 feet in length, and by those between 60 and 80 feet long when fishing alone and not in company with other vessels. Apart from this requirement for battery-powered survival craft radio, there is at present no radio legislation affecting fishing vessels less than 140 feet long, of which there are many in the British fishing fleets.

The regulations applying to trawlers of 140 feet and upwards demand that each must have either a radio-telegraph installation, consisting of approved transmitter and receiver, automatic keying device, auto-alarm receiver, and a loud-speaker watch receiver (which may be part of the auto-alarm) covering 500 kHz, or an approved radio-telephone installation with a loud-speaker watch receiver covering 2182 kHz and a two-tone alarm generator operating on the same frequency. She must also carry either two portable battery-powered survival craft radios or one set powered by a hand-driven generator.

## COMPLEX OF EQUIPMENT

As was clearly apparent from the Holland-Martin Report, the regulations do not go far enough and even the full radio telegraphy installation specified does not meet the needs of a trawler battling with Arctic conditions off Bear Island in winter.

Trawlermen and trawler owners have long recognised this obvious fact and as a result the use of electronics in British commercial fishing craft, even the smaller ones, far exceeds the mandatory minimum. In fact, the majority of distant-water trawlers—those which fish the far grounds—are fitted with a complex of equipment more numerous in units and wider in scope than that to be found on many a foreign-going cargo vessel, supertanker, or passenger liner.

These trawlers fish far afield nowadays, a number of them are "factory ships" which even freeze and package their catch at sea, and their requirements are highly specialised. They are continually on the air with communications to their owners' offices and to other vessels in their fleet; their skippers indulge in a sort of radio espionage to the extent that they try to listen in on other trawlers' radio traffic to find out if they are making good hauls; and they all use electronics as an aid to fishing as well as to navigation and safety.

## TRAWLER COMMUNICATION

While even a small North Sea herring drifter will have not only the statutory survival craft radio and a voluntarily-fitted radio-telephone installation, she will almost certainly have in addition a Decca Navigator, an echo sounder (perhaps two), radar, and a direction-finder, as well as TV for crew entertainment. The electronics usage graph climbs steeply in the larger boats fishing the White Sea and other distant grounds.

A trawler of this type will have—and use to the full under extremely arduous conditions—a high-power s.s.b. (single side-band) transmitter providing both telegraphy and telephony communication over long distances on h.f., and with this two or perhaps three main receivers.

A secondary radiotelephone installation operating in what used to be called the intermediate frequency band around 2182 kHz will also be fitted and used principally for inter-ship speaking over shorter distances, while her skipper will use v.h.f. for close-range work when he does not want rivals to know that he is "on a good living" and getting full hauls.

An interesting sidelight on this, and one that most trawlermen will strenuously refute, is the frequent use of a direction finder unit with the receiver of the 2182 kHz R/T to take snap bearings on the transmissions of a rival who is rash enough to go on the air and boast that he is fishing well. The skipper who manages to obtain such a bearing will then stem straight down it until he meets the careless talker when he, too, streams his nets among the shoal.

## POSITION FIXING

Most trawler skippers know the banks and contours of the seabed as well as many of us know the streets of our home town. Position-fixing in conditions of poor visibility is therefore vital to the trawlerman, for he can only identify the ground he seeks by its geographical position, aided by echo sounding as a cross-check. To help him in this he makes use of direction-finding, radar, echo sounding, and usually one of the hyperbolic systems such as Loran or Decca.

His electronics installation in the wheelhouse, in addition to that in the radio room, will therefore include at least one instrument for each of these facilities, and he will most probably have two direction-finders, one of them automatic and capable of taking bearings on 2182 kHz as well as the other medium frequencies; at least two, perhaps three or even four echo sounders; two radars with interswitching; and possibly both Loran and Decca receivers.

The trawler skipper is, in this respect at least, a belt-and-braces man, with a couple of safety pins for good measure. His time at sea is too precious for him to risk wasting any of it because of equipment failures.



The "fishing cockpit" at the starboard side of a modern trawler's bridge. From the left the units are: crew call controls, Decca navigator, a radar set, four recording and one cathode ray tube echosounders, and propeller pitch adjustment for fine speed control.

### **ECHO-FISHING**

Echo-fishing is one of the fisherman's most valuable electronic tools, helping him to identify the contours of the undersea hills and valleys where he knows from experience he will be most likely to find fish; showing him the nature of the sea bed over which he will trawl; and above all letting him "see" whether fish are indeed there in justifiable quantity and, so far as discernible, what kind of fish they are. All these things the modern echo sounder, coupled with his own skill and experience and knowledge of the grounds, will tell him.

His belt-and-braces philosophy, therefore, demands at least two recording sounders, frequently reinforced by a cathode-ray tube presentation set which, once he has observed fish on the recorder instrument, gives him a "close-up" view of the stratum of water in which they are swimming, and thus a supporting indication of their density and type.

### **RADAR AND FISHING LIMITS**

National extensions of territorial fishing limits, underlined by Mr Rippon's recent Common Market negotiations and the Icelandic "Cod War", together with the heavy penalties imposed for encroachment on territorial waters, have made radar more important than ever to the trawlerman. Limits are not defined by a line drawn on the water and in bad weather or poor visibility it is only too easy to steam inside them. With accurate radar ranging a trawler can fish close up to the limit line without actually crossing it while, needles to say, radar observation will also show the skipper if a patrol vessel is nearby, should he be inside the limit.

He also uses radar to keep station on a good fishing area. It has long been practice, once a

good haul has been taken, to mark the spot with a dhan buoy and then fish round it. The dhan is traditionally no more than a pole buoy with a small identity flag on it and, in poor visibility which so often exists in Arctic waters, it is difficult to keep in sight. With a radar reflector on top of the pole, dhan observation is made easy in darkness or fog.

The fisherman therefore looks on radar as much more than a navigational and anti-collision aid. Nevertheless, its value for anti-collision purposes cannot be underestimated, particularly on busy grounds cluttered with trawlers, all with nets streamed, and a dual installation with inter-switching of units is not regarded as an expensive form of insurance.

### **WEATHER CHARTS**

Advance warning of imminent adverse weather conditions is even more vital to the trawler in northern waters than to the big merchantman plodding across the Atlantic, and here the facsimile weather chart receiver can be of tremendous value, even if only from the safety point of view. It can also help in fish-finding, for the World Meteorological Organisation service also broadcasts water temperature and ice formation charts and since fish, like people, like to be in the temperatures they are used to, warm or cold layers in the sea can affect fish movements.

### **INBOARD COMMUNICATIONS**

Distant-water trawlers make great and constant use of internal communications systems. Unlike the average merchant ship on passage, with all her cargo safely stowed and therefore relatively little work going on on deck, a trawler, once she has reached the fishing grounds, is catching, cleaning, processing and stowing her cargo and

An automatic direction finder in use in the chart room of a distant water trawler.



*Everyday Electronics, December 1972*



the crew are at work round the clock every day and night—on deck, in the fish holds, in the engine room—in what are for most of the time the most difficult and dangerous conditions.

The skipper on the bridge must therefore be in constant touch with all working positions and be able to speak to, and receive an immediate reply from, any working point in his vessel and even the messrooms and cabins.

For this he must have a robust and comprehensive sound distribution network with full crew-call and talk-back facilities. Special glass-fibre waterproof loudspeakers are fitted in all open-deck locations, with waterproof talk-back switches. Often as many as four separate and independent systems are installed—belt-and-braces again—with master over-ride control so that urgent orders and announcements can break into any circuit, including the entertainment speakers in messrooms and cabins.

### QUART IN A PINT POT

It will be clear that the modern commercial fisherman is highly conscious of the help that electronics techniques can provide in what is a highly competitive business as well as a dangerous occupation, and he uses them to the full. With the sheer amount of electronic equipment carried by a distant water trawler, which is not really a very big vessel, every cubic inch of available space is at a premium, a wide assortment of units and instruments must be crammed into the smallest possible space and yet be installed in such a way that everything is instantly accessible and easily operable, even by fingers often numbed with cold and swollen with salt water. Even planning the layout of a trawler installation is a task not to be lightly contemplated.

### OUTLINES

Within the limits of an article such as this it is difficult to draw anything more specific than an outline sketch of the many ways in which electronics work to help the seaman and the fisherman. Detailed description of any one of these ways has therefore been impossible.

It is to be hoped, however, that these outlines have given some indication of the general picture and have served to show that marine electronics is much more than a man sitting tapping on a Morse key and to illustrate the extent to which the shipowner and the men who sail his ships rely upon the electronics industry to help them in their business "upon the great waters".

Could Marconi, one wonders, have dreamed what might develop within a mere 75 years as he stood on the shore of the Bristol Channel that May day in 1897? And what limits would we dare to set, today, on what might be achieved tomorrow? □



With the winter coming it is often necessary or useful to know when the temperature falls to freezing point. This device can be set to indicate "ice" conditions or similar temperature levels.

## Radio Control receiver

A receiver to match the single-channel transmitter described in this issue.

## BETA treble boost & fuzz

The effects units used in the Beta guitar

## Basic electricity magnetism

Part 3 of the series for beginners deals with magnetism and describes the construction of an electric buzzer.

All in the January  
On sale Friday, December 15.



It occurs to us that since this is our December issue, Christmas will only be about five weeks away when you read this—less if you only read it as an after thought! So now is the time to start dropping a few hints like “my pen would write better if it was solid gold” or “these cheap cuff links are staining my shirt—silver ones might be better.” If, however, like the rest of us, you cannot number Onasis among your personal friends, perhaps “this old soldering iron is coming to the end of its life” might be more fruitful and more to the point—by all means try the others first and watch for a reaction!



Assuming the last hint is greeted with signs of delight at having solved the annual problem, then perhaps one of the two irons described below might just be suitable.

Although the Antex X25 soldering iron has been on sale for some months now we have recently received one for testing. The iron is easy to use and looks very smart with its red and black handle. The low leakage current and high insulation (tested at 1500V a.c.) make this iron very safe, even when used on “live” semiconductor circuits.

One thing we particularly like about this iron is the ease with which the bit can be changed. The X25 is fitted with a  $\frac{1}{8}$  inch iron coated bit when purchased and this should prove excellent for most constructors’ needs;  $\frac{3}{32}$  and  $\frac{3}{16}$  inch bits are also available. The cost of the iron is £1.75.

The second soldering iron item consists of an iron, an iron stand (both previously mentioned in this page), a box of solder, two spare bits and some hints on soldering all for £3.99 from Adcola Products, who advertise in our pages. The cost of the iron and stand alone is £3.83, so for 16p you get two bits, a box of solder and some hints, in a very smart presentation pack; just the thing if you are starting in the electronics construction hobby. The soldering iron is the 23 watt Invader with stand to match.

### Radio Control Transmitter

With all the notes and information provided in the *Radio Control Transmitter* article, by the author, concerning the supply of the “more difficult” components it is hard to give any more information. However, the case to be used may present some problems. The one shown on the front cover was specially made up for the project but one of the Veroboxes mentioned last month should be suitable and, with a coat of paint on the plain panels, would make a very smart, light-weight case.

Both the aerial and the crystals used should be available from some of the larger shops specializing in the supply of radio control equipment and models. We advise readers to take heed of the warning to constructors printed at the beginning of the transmitter article. Although the transmitter is reasonably easy to construct, the receiver (to be described next month is rather more compact and may prove difficult for a complete beginner.

### Bit Saver

Small metal cases such as those used for the *Bit Saver* are available from a number of retail components shops or one could be made up using 18 s.w.g. aluminium. The mains indicator neons used in this project are normally sold with the series resistor incorporated—if you get the neons on their own, place a 270 kilohm  $\frac{1}{4}W \pm 10$  per cent resistor in series with each neon.

We have quoted the diode ratings necessary, any diode with at least the required voltage and current ratings will be suitable, the type numbers we have given are for the diodes

shown in Fig. 3. Other types may vary in size and shape.

### Beta Pick-Ups and Fittings

In order to make the construction of the *Beta Electronic Guitar* more simple, one or two components are rather special. The matching transformer is a good example of this, to save you winding about 5,000 turns of very fine wire on each pick-up the guitar uses a special transformer, designed and wound by Zeta Windings specially for the Beta.

The transformer is therefore only available from a few firms. It can be purchased for £1.70 (including post and packaging from Zeta Windings Ltd., 26 All Saints Road, London W.11., H. L. Smith and Co., (not G. W. Smith note) 287-289 Edgware Road, London W.C.2. and Tidman Mail Order Co., 236 Sandycombe Road, Richmond, Surrey.

Two other components that are rather special are the pick-up changeover switch and the jack output socket, these are produced by Re-An Products and are available from them at Burnham Road, Dartford, Kent. The button magnets used for the pick-ups are made by Eclipse and are available from most hardware shops.

### Demo Circuits

There should be no trouble buying the components to make up the simple voltmeter described in the first part of *Demo Circuits*. However, for those people who are going to build a *Demo Deck* from the reprint now available (price 15p), a word or two about the components used in its construction.

All the potentiometers are linear, the meter is available from G. W. Smiths, the circuit board and loudspeaker from Home Radio who can also supply the bulbs if you have any difficulty.

Please note (once again) that R. S. Components do not sell direct to the general public but any component supplier or radio and T.V. repair shop can order from them and delivery is usually fairly quick. There are also one or two firms who specialise in the supply of R. S. Components parts; they sometimes advertise on our pages.



# BIT SAVER

**A useful project for all constructors. Prevents pitting of a soldering iron bit between making joints** By T. P. Manning

IT is a great source of annoyance when using a soldering iron to find that the once clean and smooth bit has become badly pitted due to being left on for long periods between making soldered joints.

This article describes how the power supplied to the iron may be halved when the iron is not in use. Thus the iron will keep warm and heat up quickly when required but will not get hot enough to damage the bit.

## THEORY


The theory behind the unit to be constructed is concerned with half wave rectification; this means that the alternating current taken from the mains is fed through a diode before being passed to the load—in this case the soldering iron.

Fig. 1a shows the 250 volts a.c. taken from the mains, when this is passed through a diode (D1) only the positive half cycles of the waveform can pass (Fig. 1b). Thus only half of the total mains voltage is applied to the load.


## CIRCUIT

The complete circuit diagram is shown in Fig. 2. Switch S1 is the change over switch that selects half or full power and D1 is the rectifier diode that feeds the load. When S1 is in the half power position D1 conducts the positive half cycles only, supplying approximately 125 volts to the load. D2 will also conduct in a similar manner and supply 125 volts to the neon LP1. Diode D3 does not conduct as only a positive

**Fig. 1. The sine wave and half wave rectification.**

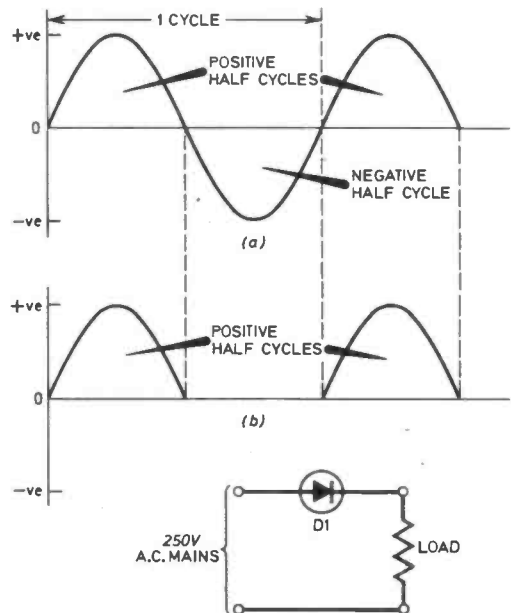


**Approximate cost of components**  
**£1.50 plus case**

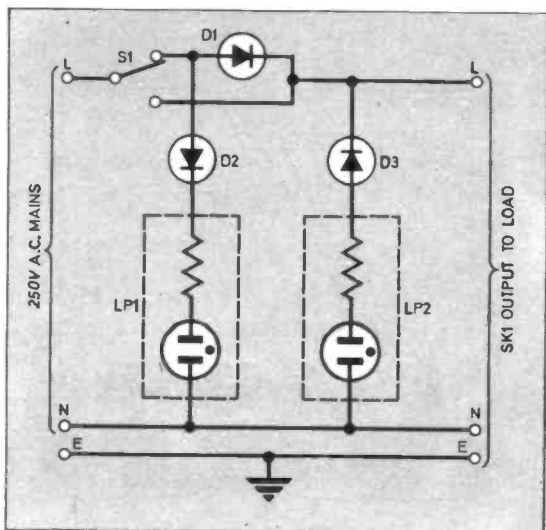

**Fig. 2. Complete circuit diagram of the Bit Saver.**

voltage is present from D1 and this cannot pass through D3 to light LP2.

When switch S1 is in the full power position the 250 volts a.c. is applied to the junction of D3 and D1 and directly to the load. The positive half cycles are not able to pass through either diode (D3 or D1) but the negative half cycles may pass through both, thus 125 volts is applied to LP2 which lights. The negative pulses which pass through D1 are unable to pass D2 and LP1 is prevented from lighting.

The neons used for LP1 and LP2 are mains indicators, incorporating series resistors as shown in Fig. 2, but have been found to work satisfactorily on 125 volts.

### CONSTRUCTION

The unit can be constructed in two ways—the first incorporating a toggle switch for S1 so that the unit is manually changed from half to full power and back; the second incorporating a micro-switch actuated by the iron when it is not in use. Thus the unit “automatically” changes from one state to the other when the iron is rested on a lever connected to the micro-switch.

The construction of the manually operated unit is shown in Fig. 3 while Fig. 4 shows the modification for “automatic” operation—the toggle switch is not included with this arrangement. The prototype unit was housed in an aluminium case measuring 4in x 2½in, plastic cases are not recommended for this application as they are easily damaged by a hot soldering iron. The case should be earthed using a solder tag under the tag strip mounting as shown, and the tag strip should be mounted on stand-off pillars to prevent the tags or diodes from touching the case.

The approximate cost of components shown for this project was calculated for the automatic unit and includes all items except the case and lever arm.

## Components . . . . **SEE SHOP TALK**

### Diodes

- D1 IS103 or any 300V 1A silicon rectifier
- D2 IS103 or any 300V 100mA silicon rectifier
- D3 IS103 or any 300V 100mA silicon rectifier

### Neons

- LP1, LP2 mains indicator neons incorporating series resistors (2 off)

### Switch

- S1 Single pole 2 way toggle or micro-switch (see text)

### Socket

- SK1 3 way miniature mains socket and plug to suit

### Miscellaneous


- Case 4 in x 2½ in x 2 in aluminium, 4 way tag strip, stand off pillars (2 off), 4BA fixings, earth tag, grommet, 3 core mains lead, connecting wire, metal for micro-switch lever if used (¼ in aluminium or brass strip 4 in x ½ in).

### USE

The iron is connected to the unit by way of SK1 and allowed to warm up as required. Between soldering operations it should be switched to half power and returned to full power when needed. If the micro-switch in the automatic unit fails to operate with lightweight irons the operating lever can be lengthened or a weight affixed to its outer end.

At half power the iron was found to stay hot enough to keep any solder on the bit molten but not hot enough for successful soldering. On full power the normal working temperature is quickly regained and the iron is ready for use. ■
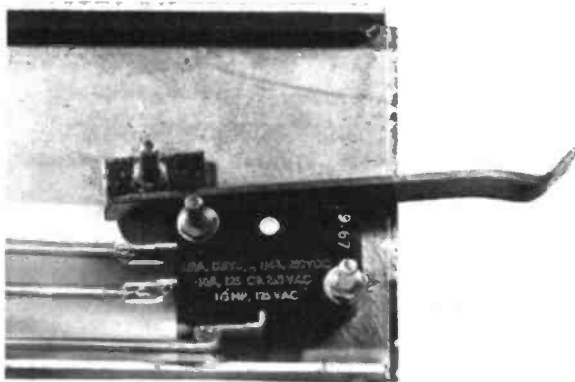
### Microswitch assembly for the automatic units.



*Advert missing*




# guide to circuit

## Crystal



1 Two electrode piezoelectric crystal

## Semiconductors

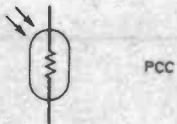

2 Photoconductive cell with symmetrical conductivity, e.g. light dependent resistor



3 Photo transistor *pn*p




4 Photo diode *pn*




5 Photo voltaic cell



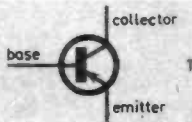6 Light generating semiconductor diode, e.g. gallium arsenide diode







7 Transistor, *pn*p

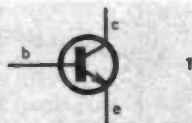







7 Transistor, *np*n (note: if collector is connected to envelope, dot joint at c)



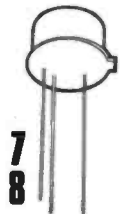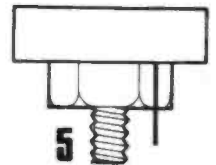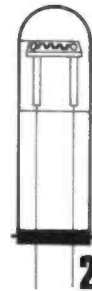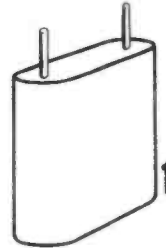
8 Unijunction transistor with *p* type base




# symbols . . . part 6

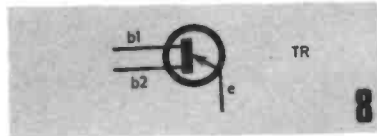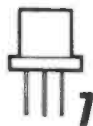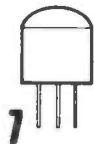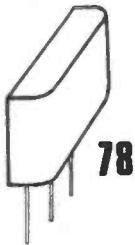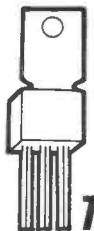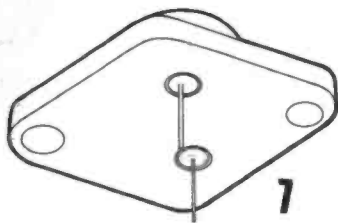

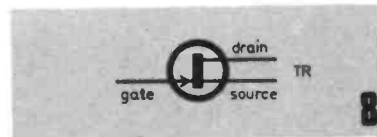Unijunction transistor with *n* type base



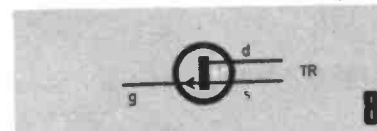Junction gate field effect transistor, *n* channel



Junction gate field effect transistor, *p* channel

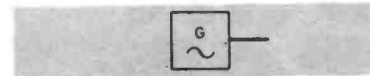
## Block Symbols




Equipment



Signal path, arrow to signify flow direction



Non-rotating sine-wave generator

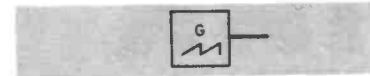


Non-rotating saw tooth generator




Non-rotating pulse generator



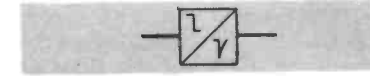
Non-rotating variable frequency sinewave generator



Differentiator

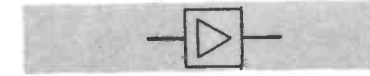

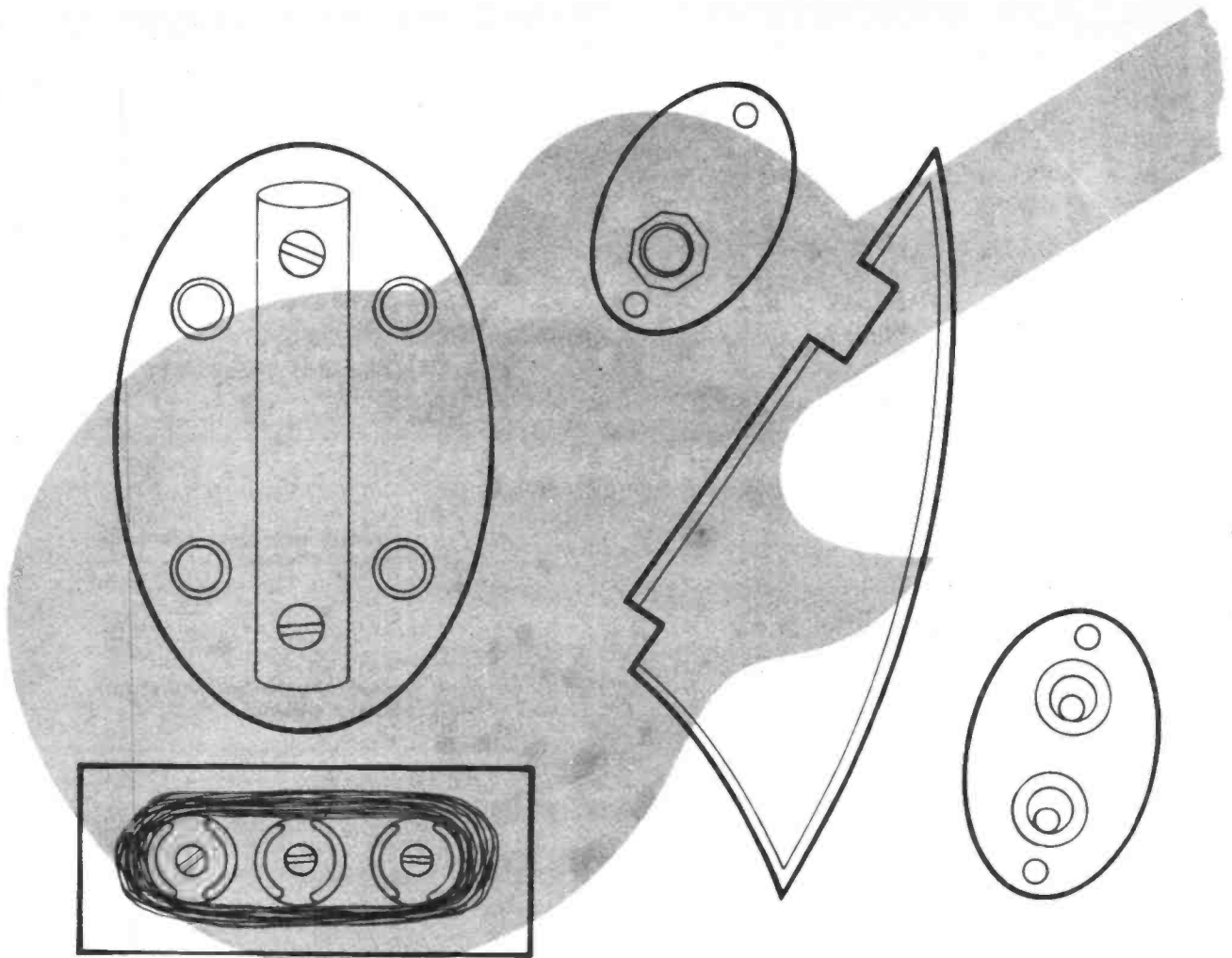Amplifier, the triangle points in the direction of transmission



# ELECTRONIC GUITAR

PICK-UPS & FITTINGS by Brian W. Terrell B.Sc.

**L**AST month we saw how the Beta body, neck and fretboard were constructed with details of the cut-outs and recesses to be made to house the fittings.

This month deals with the making of all these fittings including the two pick-ups and the wiring-up of a temporary circuit. This temporary wiring-up will enable the guitar to be played until the January issue of *EVERYDAY ELECTRONICS* when the "electronics" will be installed.

## TAILPLATE

The tailplate assembly is shown in Fig. 5 and is drawn full size. It consists of an elliptical base plate made from  $\frac{1}{4}$ in. aluminium which is

screwed to the body in the recess already made by means of four 1in. countersunk screws.

Bolted on top of the base plate is an aluminium tube of about  $\frac{1}{2}$ in. diameter to take the strings. This tube can be either solid or hollow (as shown).

The tube is bolted to the base plate by means of two 6BA round headed bolts. Araldite is then used to securely fix the tube to the plate. This is done by putting a line of Araldite on either side of the tube where it meets the plate. In the prototype the base plate was tapped to take the bolts; if a suitable tap is not available two nuts may be used to secure the tube to the base plate. Drill the necessary sized clearance holes for these securing bolts into the body.



Six  $\frac{1}{8}$ in. diameter holes are drilled through the tube, parallel to the base plate (not shown in Fig. 5). They should be countersunk and equispaced and span  $2\frac{3}{8}$ in. about the centre line through the guitar body.

If care is taken in preparing this fitment and it is filed smooth, polished with a fine grade of emery cloth and then polished with a metal polish such as Solvol Autosol, the finish can be brought up to sheen like chrome plate. A thin layer of clear varnish will preserve this sheen.



Photograph of some of the fitments: scratch plate, tailplate assembly, bridge and machine heads.

### OTHER METAL FITMENTS

There are two other metallic fitments, the jack socket cover, Fig. 10, and the stem support plate, Fig. 3.

First the jack socket cover—this is to be made from  $\frac{1}{16}$ in. aluminium to the dimensions given in Fig. 10. The curvature of this piece should be made identical to that on the body edge where it is to be fitted. It should be polished and protected in a similar way to that described in the tailplate section.

Screw the jack socket into the cover plate and fit into position and secure with two small  $\frac{1}{2}$ in. chrome screws.

The stem support plate is to be made from  $\frac{1}{16}$ in. steel plate to the dimensions given in Fig. 3. When made this should be polished and given a layer of clear varnish for protection against rusting.

### OTHER FITMENTS

The other fitments are shown in Figs. 6, 7, 8 and 9, and a recommended material is  $\frac{1}{8}$ in. thick Perspex as was used in the prototype.

Perspex is normally sold with a protective paper covering so tracing the shapes of these parts is a fairly easy matter using the carbon paper method described last month. Perspex can be cut with an ordinary hacksaw blade and filed smooth with a fine file.


In the prototype, the scratch plate (Fig. 6) and the switch covers (Figs. 8 and 9) had their edges chamfered with a smooth file, and polished with fine emery paper and Solvol Autosol.

When drilling be careful not to press too hard else the Perspex may split. An ordinary metal drill will do the job adequately.

The final positions of these fitments is clearly shown by cross-hatched regions in Fig. 1. Secure these pieces in position with small round-headed chrome screws.
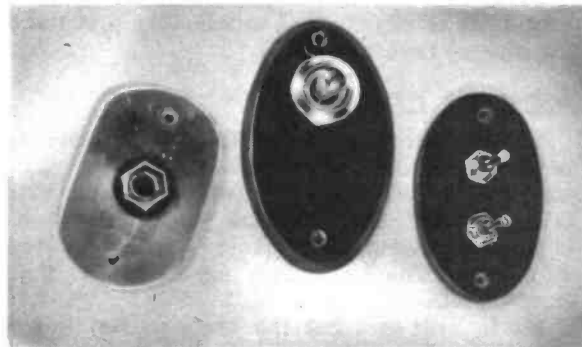
### BRIDGE

No details have been given for the construction of a bridge since a lot of mechanical work would be involved and besides, these are usually available from suppliers of guitars and other stringed instruments, and are inexpensive. It is recommended that an adjustable type is obtained.



Photograph showing the Perspex switch covers and jack socket cover.

### PICK-UPS

The Beta guitar uses two identically wound low impedance pick-ups which are matched to commercial amplifier inputs by means of a small matching transformer T1 (5 ohm to 50 kilohm).

Full details of the pick-ups and covers are shown in Figs. 11, 12, 13 and 14.

Begin making one of the pick-ups by cutting a piece of Veroboard to the dimensions shown in Fig. 13 and make the cut-outs along the copper strips and the magnet fixing holes as indicated.

Using 6BA nuts and bolts secure the three button magnets (Eclipse 821) in position as indicated ensuring that the magnet polarities agree with those of Fig. 13. This can easily be done by remembering that unlike poles attract one another and that each button has one north pole and one south.

A blob of solder placed on the copper strip either side of the fixing nut will ensure a permanent fixing.

## COIL WINDING

Approximately 20 yards of 30 s.w.g. enamelled copper wire is needed for each coil (pick-up).

Cut a piece of cardboard size 1 $\frac{1}{4}$ in. by 2 $\frac{1}{2}$ in. approx. and glue centrally on top of the three magnets. In the prototype double-sided Sellotape was used.

Clean one end of the enamelled wire by scraping off the enamel, tin this and solder in location F3 on the Veroboard. Now wind on 100 turns in a clockwise direction around the three magnets as a whole. Try to make the turns as neat as possible, although this is not very critical. Clean and tin the other end of the coil winding, and solder in location E2 on the Veroboard.

A dab of paint, nail varnish or lacquer should now be applied to the coil winding to prevent it coming unravelled. Solder on a piece of screened lead as shown in Fig. 13. Do not use the television aerial type of cable. Repeat the above procedure for the second pick-up.

Using an ohmmeter or battery and bulb, test for continuity of the coils. If satisfactory proceed to the pick-up covers.

## PICK-UP COVERS

These covers must be made from a non-magnetic metallic material that can be easily soldered. For these reasons copper or brass plate is recommended. Aluminium would be suitable if aluminium solder is available but this is rather expensive. The prototype used 1/16in. thick copper plate.

Mark, drill and cut the plate as detailed in Fig. 11 (one for each pick-up) and then bend to shape as illustrated in Fig. 13. Now solder the internal joints so that the cover is rigid and leak-proof. It will be necessary to use a large soldering iron for this job, 60 watts or more. If this is not available, the soldering can be carried out using the kitchen gas stove as follows: with the cover bent to final and accurate shape, grip with a pair of nose pliers and hold one joint over the hotplate on the stove. Heat until the solder freely flows in the joint. Dip in cold water to cool and then dry. Repeat for the other three joints.

When satisfied with your soldering, the sharp edges and corners should be filed smooth and then cleaned with emery cloth.


With reference to Fig. 14, assemble the pick-up, pushing the magnet/coil assembly in as far as possible as shown. Now solder the copper strips of the Veroboard (pick-up baseplate) to the cleaned inside faces of the covers as shown. Use a soldering iron for this job and not the gas stove otherwise damage may result to the pick-up coil. Repeat for the second pick-up and assemble similarly.

When finished, both pick-up covers can be brought to a high sheen with fine emery paper and metal polish. To preserve the sheen a coat of

clear varnish or polyurethane may be applied. If so desired the covers may be painted—this will not affect pick-up performance.
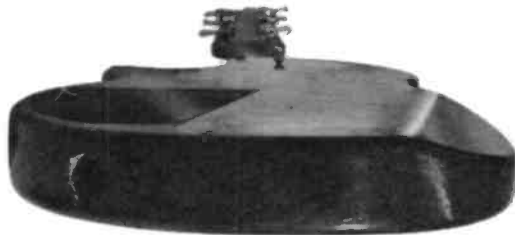
## ASSEMBLY


Before complete assembly to check out the instrument, clean up all the woodwork and carry out any refinements you may desire. On the prototype all the edges on the body were rounded off and a large slope was put on one side of the back of the body to make holding and playing a little more comfortable.



View showing sloping cutaway for more comfortable handling whilst playing.

Attach the machine heads to the head and place the nut in position for inspection. Affix all the fitments to the body of the guitar with the exception of the control section back plate. Start with the pick-ups; screw these in position and thread the cables through to the control section.

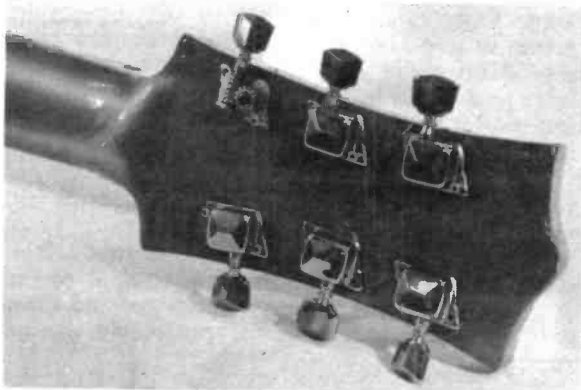Screw in position the tailplate assembly, scratch plate and switch covers, jack socket cover with socket attached, and the tailplate assembly.



Fixing the machine heads in place.

Now attach the neck to the body with the six 2in. screws through the stem support (Fig. 3) and tighten fully.

Thread the strings through the tube on the tailplate from the front end such that the strings will pass over the tube on their way to the machine heads over the bridge and nut.

Position the bridge so that the distance between the bridge and 12th fret is the same as

# ELECTRONIC

# GUITAR

Fig. 11 (below). Marking and cutting details of the pick-up cover. Dotted lines represent bending lines.

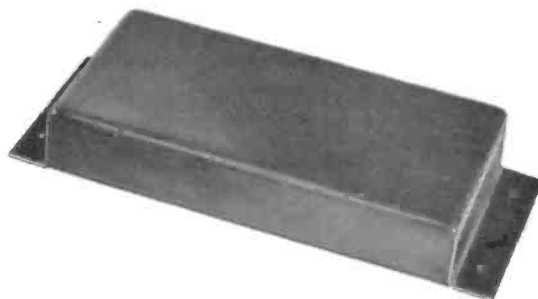
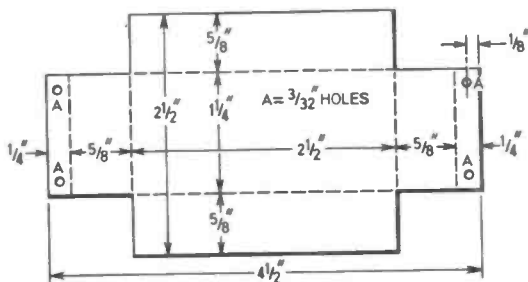


Fig. 12 (above). Photograph of a completed pick-up cover with rounded edges and corners.


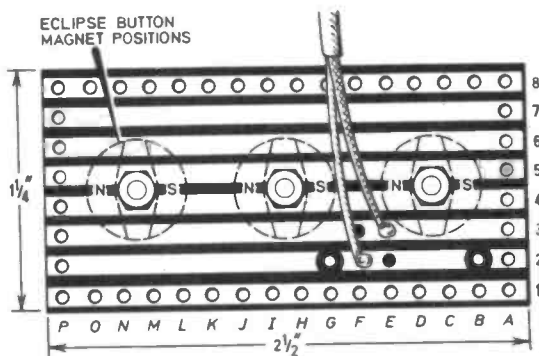


Fig. 13 (above). Underside view of the pick-up baseplate made from a 0.15in. matrix Veroboard. Shown dotted are the button magnets mounted on the top side of the Veroboard.

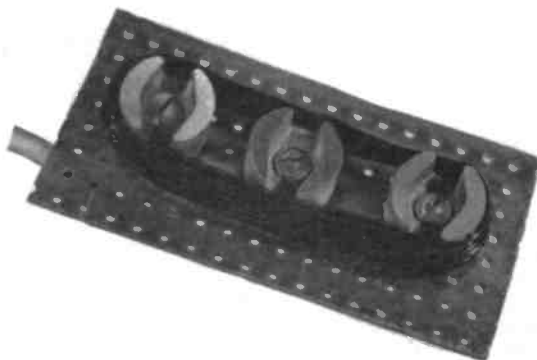

Photograph (above) of the coil wound on the magnets with insulated top removed.

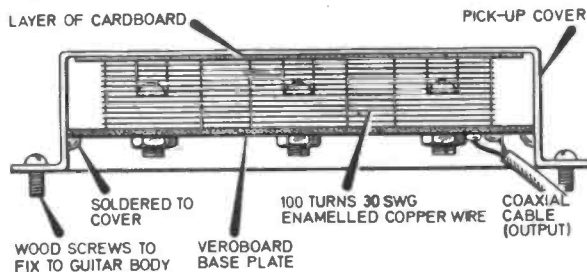


Fig. 14 (left). Details of assembling the pick-up coil into its metallic case. Note the cardboard layer between magnets and cover.

that from the nut to the 12th fret.

If the depth of the nut slots are satisfactory, loosen the strings and glue the nut securely in position. If not, correct and then glue.

Thoroughly check the performance of the fretboard at every position for each of the six strings and remedy if not completely satisfactory by filing down any high frets.

## TEMPORARY CIRCUIT

The circuit used is a temporary one until next month when the effects units—fuzz and treble boost—will be fully described. This circuit enables the guitar to be played through a commercially available amplifier with normal input impedances until the January issue.

As can be seen from Fig. 15 the two pick-ups, PU1 and PU2 are connected in parallel, and are inputted to the transformer on the Veroboard. The output is then taken direct to the jack socket SK1.

## VEROBOARD—WIRING UP

The size of the Veroboard to be used is 23×12 holes by 0.15in. matrix and this will be used next month to install the effects units.

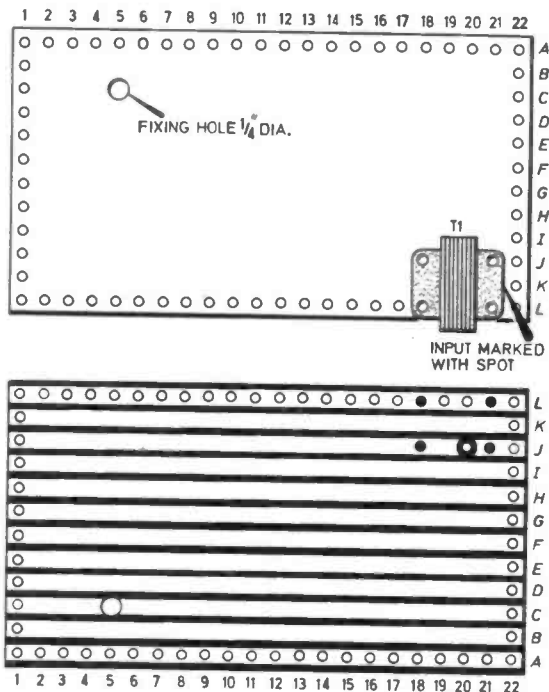


Fig. 15. Shows the transformer T1 mounted in position on the Veroboard and regions of copper strip to be removed from underside.

Make the cut-outs as shown in Fig. 15 and mount the transformer T1 as shown. The transformer is marked with a spot between its input terminals—ensure that this is correctly observed. The transformer is a very delicate component so

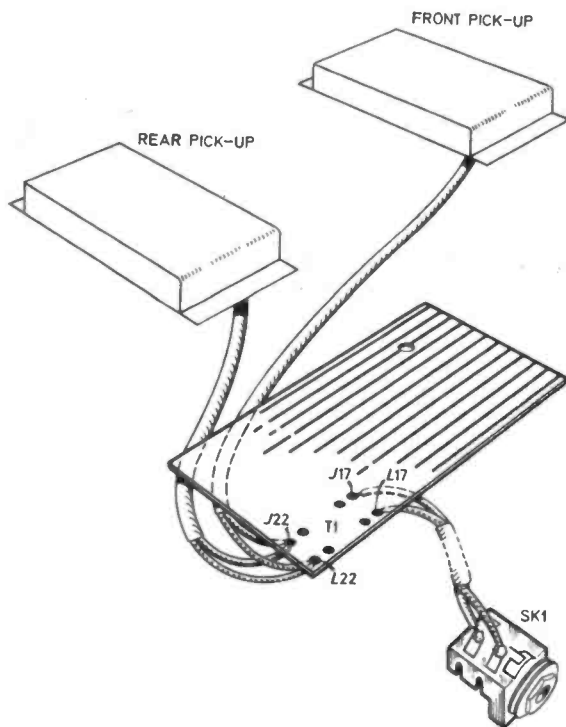


Fig. 16. The wiring up of the two pick-ups and Veroboard panel to the output socket. The pick-ups are in parallel.

extra care should be taken when placing and soldering in position. Do not apply too much heat or the transformer may become damaged. It has been designed to sit comfortably in 0.15in. matrix Veroboard.

Now wire up as detailed in Fig. 16 using co-axial cable for all connections. If co-axial cable is not used, considerable noise and interference may be experienced.

The Veroboard should now be fixed to the base of the control recess with a small wood screw located at position C5 as indicated in Fig. 16. Screw on the control recess back plate and the guitar is ready to play through an amplifier.

Next month: adding the fuzz and treble boost effects units

## Components....

**T1** matching transformer type M218 5Ω to 50KΩ (Zeta Windings Ltd.)

**SK1** jack socket type R26/I (Re-an Products Ltd.). Toggle changeover switch for pick-up selection for use next month is also available from Re-an Products Ltd.

### Miscellaneous

Eclipse button magnets type 821 (6 off); 30 s.w.g. enamelled copper wire; brass or copper plate size 4½in x 2½in. (2 off); Veroboard 0.15in. matrix: 2½in. x 1½in. (2 off), 3.3in. x 1.8in.; co-axial cable (12in.).

# BASIC

## 2

# Electricity

## Current flow through liquids

By Maureen Birch

**L**AST month we considered how a chemical action inside a dry cell produces an electric current. Now we can set up a very simple experiment to show the reverse effect; i.e. how the passing of a current can cause a chemical reaction.

### CURRENT THROUGH A LIQUID

Connect a wire to the positive terminal of a battery and another wire to the negative terminal. Cover the bared free ends of the wires with aluminium cooking foil ensuring that the foil makes contact with bare wire ends. Place the foils into a glass of water making sure that they do not touch each other and that only the foil is under the surface of the water (none of the wire) Fig. 2.1.



Fig. 2.1. Electrolysis of water. You should see tiny bubbles at both electrodes.

Everyday Electronics, December 1972

If you look closely you should see a stream of bubbles coming from each piece. These are bubbles of hydrogen and oxygen—the elements from which water is made.

The bubbles of hydrogen are coming from the wire connected to the negative terminal of the battery and this we call the **cathode**. The oxygen bubbles come from the end connected to the positive terminal—or **anode**. The two pieces of aluminium foil are collectively called **electrodes**. Thus as the electric current passes between the anode and cathode it breaks the water down to its two elements.

### ADDITION OF SALT

To make a success of this experiment a teaspoonful of salt should be added to the water to increase the conductivity since water by itself is not a very good conductor of electricity.

Now set up the experiment shown in Fig. 2.2. Putting a bulb in series with our basic circuit we can investigate the effect of adding more salt to the water. You should immediately see that



Fig. 2.2. Adding table salt increases current flow and the bulb glows more brightly.

adding more salt has the effect of increasing the number of bubbles evolved at the anode and cathode and at the same time the bulb glows more brightly.

It must be that the salt is helping the current to flow and the larger the current, the more bubbles there are produced. Now why should this be?

We must remember that an electric current is a flow of negatively charged particles called electrons. Since the bulb in Fig. 2.2 continues to glow, the current must be flowing around a complete circuit and therefore it must be flowing through the salt solution between the anode and cathode. To differentiate between current flow in solids and liquids we say that the liquid conductor is an electrolyte and the process of conduction that leads to the chemical breakdown of the electrolyte is called electrolysis.

### CHEMICAL THEORY

We will now try to understand exactly why the current flows in the electrolyte. When the salt is dissolved in water both the salt and the water break up into charged particles called ions. The salt, which is sodium chloride, (chemical formula NaCl) breaks up into positively charged sodium ions (abbreviated as  $\text{Na}^+$ ) and negatively charged chloride ions ( $\text{Cl}^-$ ). Water, which has the chemical formula  $\text{H}_2\text{O}$  breaks up into positively charged hydrogen ions ( $\text{H}^+$ ) and negatively charged hydroxyl ions ( $\text{OH}^-$ ).

The solution remains electrically neutral because the total numbers of positive and negative charges are the same.

These charged ions migrate to the electrode of

the opposite charge (Fig. 2.3) under the influence of the electrical pressure (voltage). Thus the chloride and hydroxyl ions migrate to the anode (positive) carrying electrons with them; these electrons are given up by the hydroxyl ions, oxygen is released and electrons flow away into the wire connected to the electrode.

At the cathode,  $\text{H}^+$  and  $\text{Na}^+$  ions arrive. The hydrogen ions collect the electrons that the hydroxyl ions had given up at the anode (it has moved round the outside circuit and is available at the cathode for this effect to take place) and hydrogen gas is formed.

There is a chemical law that governs which ions are discharged at the electrodes but we need not concern ourselves with the details of this.

### ELECTROPLATING EXPERIMENT

Thus the ions in the liquid are responsible for transporting the current between the electrodes. Let's see what happens if we replace the salt solution with another liquid—copper sulphate solution.

You should be able to get blue copper sulphate crystals from your local chemist but failing this a science teacher at your local school might be able to help.


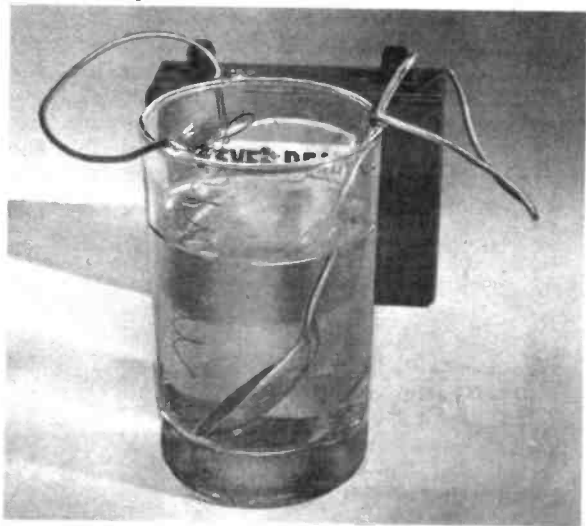


Fig. 2.4. Demonstrates the principle of electroplating. The enamel must be removed from the immersed portion of the wire coil.

Set up the circuit shown in Fig. 2.4 making sure that the metal spoon is connected to the negative terminal of the battery and the copper wire to the positive terminal. After a few minutes you will see that the spoon has been coated with a thin layer of copper.

A very brief explanation of this is that the copper sulphate ( $\text{CuSO}_4$ ) ionises and the positive copper ions ( $\text{Cu}^{++}$ ) travel to the negative electrode (the spoon) where they are deposited as a layer of copper metal. If you examine the

Fig. 2.3. Movement of ions in a salt solution under the influence of an external battery.

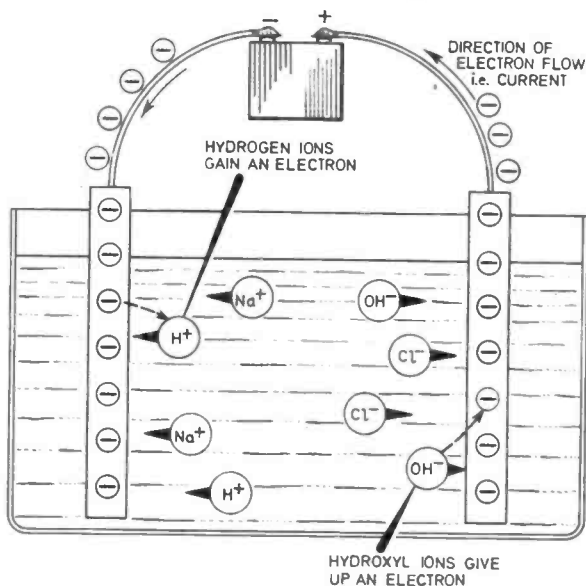

copper wire which you have been using as the anode you may just be able to see that it looks a little "frayed", this is because some of the copper from the anode has been passing into the solution as ions. This has the effect of keeping the concentration of the copper sulphate solution constant. The electrolysis merely transfers copper from anode to cathode and this is the principle of electroplating.

You should be able to clean the spoon using an abrasive.

## INDUSTRIAL TECHNIQUE

A similar process called **electro-typing** is used in the printing industry for making engraved copper plates. An impression of the required plate is made in wax, then the face of the wax is covered with a layer of graphite (to conduct the current) and this wax mould is placed in a copper solution. The graphite/wax mould is made the cathode and a sheet of copper is used for the anode. When a current is passed, a layer of copper is deposited on the wax.

After several hours the mould is taken out and the wax melted off leaving a copper plate with the desired impression on it. Dies for making bank notes, coins and medals and gramophone records can be made this way. In fact this process is used whenever an exact reproduction is required.

## ANODISING

In our first two experiments with water, and salt solution, we saw that oxygen bubbles were given off at the aluminium foil anode. One interesting point to mention here is that using suitable electrolytes this oxygen can be made to react with the aluminium forming a layer of aluminium oxide. This is the principle of a process called **anodising** that is used to produce protective and decorative films on aluminium.

The main difference between anodising and electroplating is that in anodising, the articles are made the anode in a diluted acid solution and not the cathode as in electroplating.

Strangely, the acids used in the anodising process dissolve about half the aluminium oxide as it is formed on the surface of the article and this has the effect of making the anodised layer porous. Because of this it will readily absorb dyes giving the decorative finish we can see on many articles around us eg. saucepan lids, motor car trims and lettered fascia panels etc.


Electrolysis, electroplating and anodising are all examples of what is called "the chemical effect" of an electric current. Another similar effect is the charging of a type of cell called an accumulator.

## ACCUMULATORS

The dry cells mentioned last month have to be thrown away when their chemical energy is

exhausted. Cells which can be re-charged i.e. have their chemical energy restored, are called accumulators or storage batteries. You might also see them referred to as "secondary-cells" to distinguish them from the "throw away" primary cells.

**Fig. 2.5. Shows the arrangement of plates in a lead-acid accumulator.**

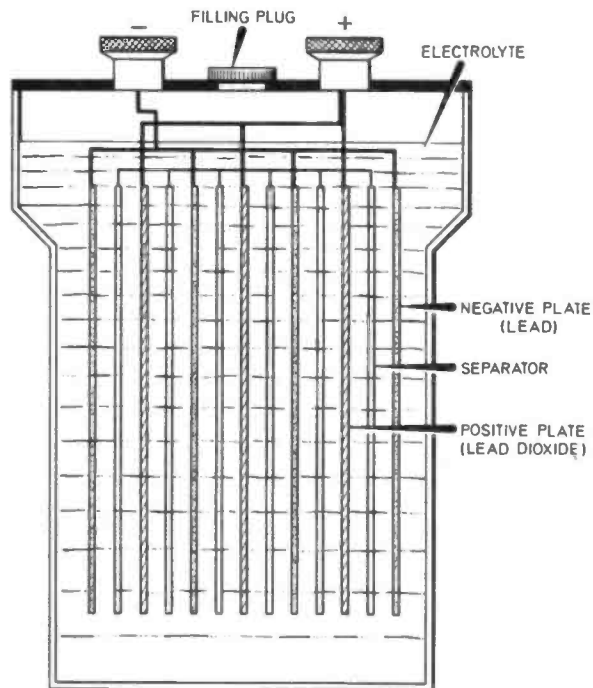

The most common form of accumulator, see Fig 2.5, is the lead acid type found in motor cars and basically it consists of lead plates standing in dilute sulphuric acid. When a cell is first charged by passing an electric current through it, the positive plates become coated with red/brown lead dioxide and the negative plates remain unchanged. When the cell discharges and a current is drawn from it, the lead dioxide becomes lead sulphate, the negative plates also become coated with lead sulphate and the sulphuric acid becomes less dense.

In re-charging, the acid becomes denser again and the plates become lead dioxide and lead once more.


One of the quickest and easiest ways of testing the state of the cell is to check the density of the sulphuric acid using a small float called a hydrometer. There is in fact no "accumulation" or storage of electricity in this cell, charging simply converts electrical energy into chemical energy which is ready to produce electricity again when connected to an external circuit.

**Next month:** the magnetic effect of current.

## LONDON CALLING . . .
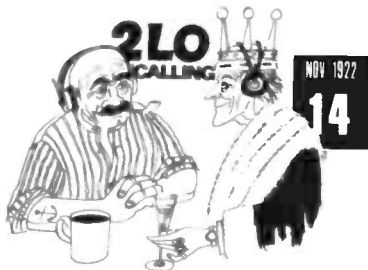
### The BBC

On November 14 1922, the British Broadcasting Company later to receive its charter and become the British Broadcasting Corporation began transmitting from station 2L.O. in London. Listeners throughout the country adjusted the tuning of their receivers and pressed the headphones closer to their ears so that they should not miss any part of the historic moment.



*Dustman and Duke shared the same programmes,*

Few, perhaps of those listeners could foresee how much their lives, and the lives of their children would be affected by this new medium. At the touch of a switch or the tickle of a cat's whisker, a voice, music or laughter came from out of the air to comfort the lonely or to cheer the sad. Dustman and Duke shared the same programmes, the same courteous address; for all listeners are equal, each scarcely aware of the other but each connected by radio waves to a common point.

But what of the material effects? The new industries of radio and radio component manufacturer, given impetus by this novel form of entertainment, were quick to respond with improved equipment. The amateur constructor and experimenter played a large part in the evolution of a scientific "toy" to a reliable simply operated domestic appliance. The use of short waves for telecommunications was pioneered by the "hams" who were forced into the higher frequencies by commercial pressures as the demand for broadcasting stations increased.

### Do it Yourself

The electronics construction hobby had its beginning with the opening of 2L.O. and so November 14 is also the 50th anniversary of our own hobby. Fifty years ago our grandfathers and our fathers drilled ebonite panels, wound honeycomb and basket coils and built variometers. Many mastered the art of soldering with a soldering iron heated in a gas jet (or even in the fire), a stick of solder and a tin of flux—no resin cored solder in those days!

Most components had screwed terminals—even small capacitors, and so those who could not "tin" the soldering iron could still indulge in the hobby. It is interesting to note that in those days, grid leak resistances were often formed by drawing pencil lines on the baseboard—a similar principle to that now used in modern thick film circuits!

Many of these receivers were cunningly designed to look like something else; my wife recalls a crystal set that was built into a flower bowl with terminals for aerial, earth and headphones at the back. In these early days it was thought necessary to disguise the "wireless" so that it would blend in with the home furniture; it must have been difficult to hide a horn loudspeaker, though.

A good outside aerial installation was necessary, except for strictly local reception, and every listener had his inverted "L", complete with "egg" insulators, draped across backyard or garden. The earth connection was little understood and consequently was regarded by many with great awe and a proper sense of respect.

### Radio Times

During the war, the BBC news broadcasts were an essential part of our lives. In order to prevent any attempt by the enemy to hoodwink the British listener, the BBC news readers began to announce their names at the beginning of each news broadcast, so that listeners would be

able to identify them and thus forestall a would-be impersonator. At first, this was quite strange and in my family we used to vie with each other to name the news reader before he announced himself.

### Television

The first public television broadcasting service in the world had been started by the BBC in 1936. The transmissions were intended to serve only the London area and the service was closed down during the war so that enemy aircraft could not use the transmitter for navigational purposes.

I saw television for the first time at the Science Museum, South Kensington, after the war and resolved to build a receiver myself, I wound coils, drilled chassis and worked feverishly at night to try to line up the vision strip on the signal before the transmitter went off the air. What a thrill it was when the modulation on the tube melted into a picture!

Thank you, BBC for that moment, and for the pleasure I got from my first home-built crystal set, as a boy of eleven, lying in bed wearing headphones and using the steel mattress as an aerial.

Many happy returns, BBC, you may not have pleased all of the people all of the time, but you deserve full marks for trying.





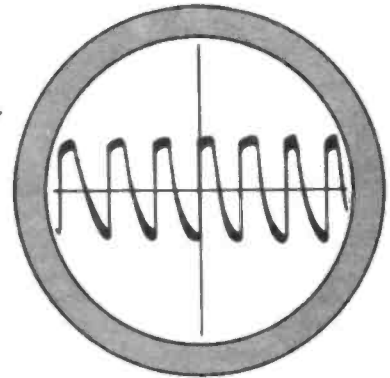
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
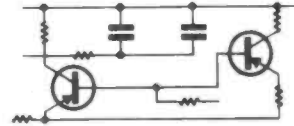
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EEL 12. 2

**special free gift also to all our students**

# YATES ELECTRONICS (FLITWICK) LTD

DEPT. E.E., ELSTOW STORAGE DEPT.  
KEMPSTON HARDWICK,  
BEDFORD.

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2

Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

## RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.  
1/2W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 1/2W 2%  
Electrosil TR5.

Power	Tolerance	Range	Values available	Price
1/2W	5%	4.7Ω-2.2MΩ	E24	1-99 100+
1/2W	10%	3.3MΩ-10MΩ	E12	1 0p 0 8p
1/2W	2%	10Ω-1M	E24	1 0p 0 8p
1/2W	10%	1Ω-3.9Ω	E12	1 0p 0 8p
1/2W	5%	4.7Ω-1MΩ	E12	1 0p 0 8p
1/2W	10%	1Ω-10Ω	E12	6p 5 5p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40, E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0-1 matrix).  
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

## TRANSISTORS

AC107	15p	BC107	10p	BF195	15p	OC81	12p	2N3703	12p
AC126	12p	BC108	10p	BFY50	22p	OC82D	12p	2N3704	13p
AC127	12p	BC109	10p	BFY51	22p	OCF71	40p	2N3705	12p
AC128	12p	BC147	10p	BFY52	22p	ORP12	50p	2N3706	11p
AC131	12p	BC148	13p	BSY56	32p	2N2369	16p	2N3707	12p
AC132	12p	BC149	13p	OC26	45p	2N2646	60p	2N3708	10p
AD140	50p	BC157	13p	OC28	45p	2N2926R	9p	2N3709	11p
AD161	33p	BC158	13p	OC35	45p	2N2926O	9p	2N3710	11p
AD162	36p	BC159	13p	OC42	12p	2N2926Y	9p	2N3711	11p
AF114	20p	BD131	75p	OC44	12p	2N2926G	10p	2N4062	12p
AF115	20p	BD132	75p	OC45	12p	2N3054	58p	ZTX302	15p
AF116	20p	BF179	32p	OC70	12p	2N3055	60p	ZTX500	16p
AF117	20p	BF181	25p	OC71	12p	2N3442	60p	ZTX503	16p
AF118	38p	BF194	15p	OC72	12p	2N3702	13p	40362	58p

## ZENER DIODES

400mW 5% 3-3V to 30V, 15p.

## LINEAR IC's (DIL)

709 50p 741 50p  
710 50p 748 50p

## DIL SOCKET

14 and 16 pin  
16p

## DIODES RECTIFIER

DIODES	RECTIFIER	1250V	1A	12p	SIGNAL	7p
BY127	1250V	1A	12p	OA85	7p	
BZY10	800V	6A	25p	OA90	5p	
BZY13	200V	6A	20p	OA91	5p	
IN4001	50V	1A	7p	OA202	5p	
IN4004	400V	1A	8p	IN4148	5p	
IN4007	1000V	1A	12p	BA114	8p	

## BRUSHED ALUMINIUM PANELS

12in x 6in—25p; 12in x 2in—10p; 9in x 2in—7p.

## SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K log, or lin. 40p

DUAL GANG, 10K + 10K etc. log, or lin. 60p.

KNOB FOR ABOVE 12p.

FRONT PANEL 65p

18 Gauge panel 12" x 4" with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2½p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7½p, 0.33μF, 11p, 0.47μF, 13p.  
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3½p, 0.15μF, 4½p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7½p, 0.68μF, 11p, 1.0μF, 13p.

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF, 3½p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6½p, 0.47μF, 8½p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

## MYLAR FILM CAPACITORS 100V,

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF  
2½p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3½p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

6p each.  
(μF/V) 10/2-5, 40/2-5, 80/2-5, 160/2-5, 320/2-5, 500/2-5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6.4/6-4, 25/6-4, 50/6-4, 100/6-4, 200/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1.6/25, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.64/64, 2.5/64, 5/64, 10/64, 20/64, 32/64.

## MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6.4, 800/4, 1000/2.5, 9p, 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1600/2.5, 12p, 160/64, 250/40, 400/2.5, 64/16, 2000/4, 1000/10, 1600/6.4, 2500/2.5, 15p, 250/64, 400/40, 640/25, 3200/4, 1000/16, 1600/10, 2500/6.4, 4000/2.5, 18p.

## ELECTROLYTIC CAPACITORS Miniature P.C. mounting

5p each.  
(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

## VEROBOARD

0-1	0-15
2½ x 3½	22p
2½ x 5	24p
3½ x 3½	24p
3½ x 5	28p
17 x 2½	75p
17 x 3½	100p
17 x 5 (plain)	82p
17 x 3½ (plain)	60p
17 x 2½ (plain)	42p
2½ x 5 (plain)	12p
2½ x 3½ (plain)	11p
Pin insertion tool	52p
Spot face cutter	42p
Pkt. 50 pins	20p

## JACK PLUGS AND SOCKETS

Standard screened 18p	2.5mm insulated	8p
Standard insulated 12p	3.5mm insulated	8p
Stereo screened 35p	3.5mm screened	13p
Standard socket 15p	2.5mm socket	8p
Stereo socket 18p	3.5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable 15p/metre  
6 way screened cable 22p/metre

## BATTERY ELIMINATOR

£1.50  
9V mains power supply. Same size as PP9 battery

## THERMISTORS

VA10555 15p VA10665 15p VA1077 15p R53 £1.35

## COMPACT CASSETTES—IN PLASTIC LIBRARY BOX

C90 65p C120 85p

## LARGE (CAN) ELECTROLYTICS

1600μF	64V	74p	3200μF	16V	50p
2500μF	40V	74p	4500μF	16V	50p
2500μF	50V	58p	4500μF	25V	£1.68
2500μF	64V	80p	5000μF	50V	£1.10
2800μF	100V	£3.00			

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	10p	0.047μF	13p	0.22μF	20p
0.022μF	12p	0.1μF	16p	0.47μF	22p

## POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series values 4p each.

## FAST-RELIABLE SERVICE

FOR  
ELECTRONIC COMPONENTS  
SEND NOW FOR A  
**CATALOGUE**

5th EDITION  
AND

**DISCOUNT VOUCHERS**

25p POST FREE (UK)

W.E.C. LTD.  
HIGH STREET, RIPLEY, SURREY  
Established 1954

## GREAT TEST METER VALUE !!

New 1 Multimeter MF-9

SENSITIVITY—20kΩ/V D.C. 4kΩ/V A.C.

### RANGES

D.C. current 0-5, 5, 50, 500mA, 10Amp.  
D.C. volts 0-5, 2.5, 10, 50, 250, 500,  
5000Volts.  
A.C. volts 0-2.5, 10, 50, 100, 250, 1000  
Volts.  
Resistance 0-4kΩ, 40kΩ, 4MΩ, 40MΩ.

### ACCURACY

D.C. ranges and resistance  
±2.5%.  
A.C. ranges ±4%


PRICE ONLY **£9.20**

Inclusive of freight and  
customs duty (at 12½%).

**TELEMIX-IMP & EXP**

BOX 75 S-175 22 JARFALLA 1 SWEDEN



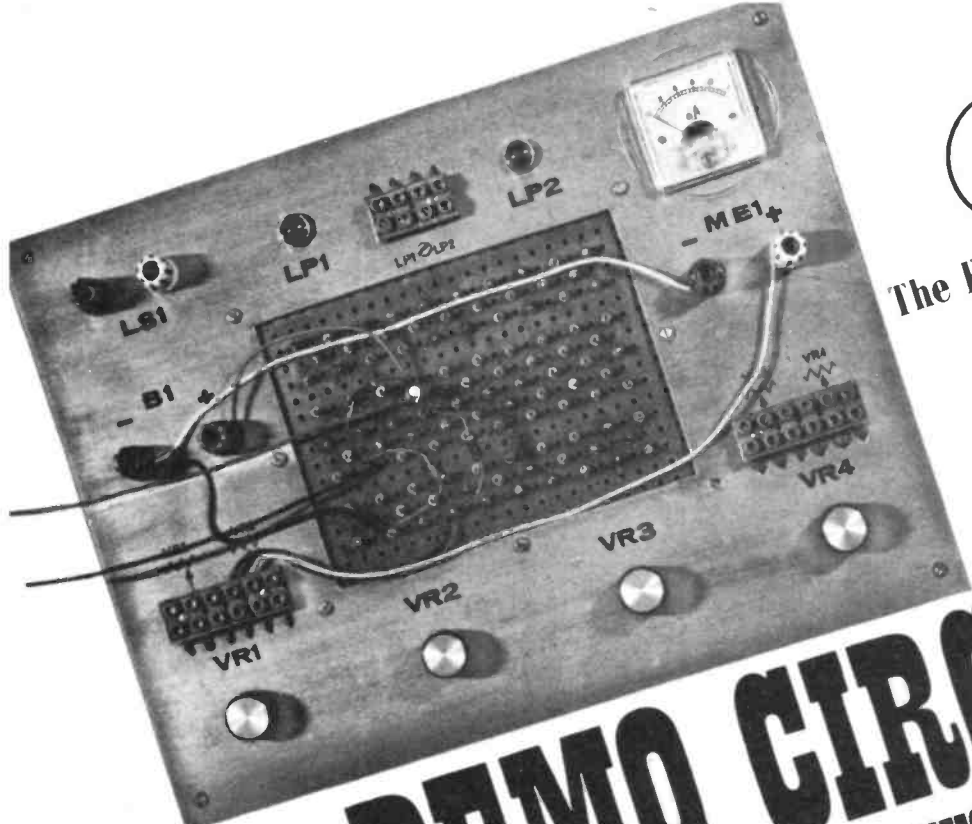

1

The Emitter Follower

# DEMO CIRCUITS

By MIKE HUGHES

IN this series we shall be describing a number of useful circuits. Some of them—such as that described this month—will be functioning pieces of equipment in their own right; others will be basic circuits that are often encountered in larger systems.

We shall describe the workings of each circuit in full detail and give some suggested experiments to verify the way in which they work. It is suggested that the circuits are built and the various measurements carried out, therefore to economise on components—many of which can be used several times over—we shall give layouts that refer to the Demo Deck. (A reprint of the Demo Deck article describing construction is available, price 15p, see page 749.)

Should you wish to, there is no reason why you should not use other forms of construction, e.g. Veroboard, standard pattern printed circuit board or one of the several forms of experimental “breadboards” that are available. Unfortunately we cannot give details that will cover all these other possibilities.

## EMITTER FOLLOWER

This month we look at the workings of the emitter follower stage and use it to make a simple, single range, high resistance voltmeter using the 1mA meter movement of the Demo

Deck as the display. Fig. 1.1 shows the basic configuration of an emitter follower—it is sometimes called a common collector or grounded collector stage because the collector of the transistor goes straight to the power supply rail.

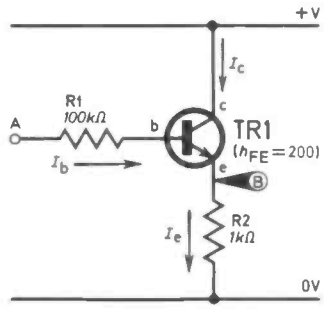


Fig. 1.1. The basic circuit configuration of the emitter follower.

To make TR1 conduct between collector and emitter we have to make the base positive (for an npn device) with respect to the emitter and pass base current ( $I_b$ ). This causes collector current ( $I_c$ ) to flow and the emitter current ( $I_e$ ) will be the sum of base and collector currents.

$$I_e = I_b + I_c$$

But  $I_c$  is controlled by the base current and the d.c. current gain of the transistor ( $h_{FE}$ ) so we can say  $I_c$  is the same as  $I_b \times h_{FE}$ .

$$\begin{aligned} \text{therefore } I_c &= I_b + (I_b \times h_{FE}) \\ &= I_b(1 + h_{FE}) \end{aligned}$$

For a typical *npn* transistor such as the BC108,  $h_{FE}$  is between 150 and 250; let us assume it is 200 as a round figure.  $I_c$  will be  $201 \times I_b$ , i.e. about 0.5 per cent greater than  $I_b$  would be. Because of this we can justifiably say there is very little difference between  $I_c$  and  $I_e$  and, to all intents and purposes (provided the transistor has a high enough gain), the emitter current is directly proportional to the base current—the linking factor being the gain ( $h_{FE}$ ) of the device in question.

### CIRCUIT THEORY

We'll assume that we are using a BC108 for TR1; as it is a silicon device we must make the base at least 600mV positive with respect to the emitter before base current starts to flow. Assume point A is held at +4V and R1 and R2 are 100 kilohm and 1 kilohm respectively.

Initially the transistor is not conducting therefore point B will be zero volts; therefore the current flowing through R1 will be given by the potential difference between A and B minus the forward voltage drop of the base emitter junction

$$\text{divided by R1 i.e. } \frac{3.4}{100,000} = 0.034\text{mA. By}$$

rights this should cause a current of  $0.034 \times h_{FE}$  milliamps to flow through R2, i.e.  $0.034 \times 200 = 6.8\text{mA}$ .

If this were to happen we should get a voltage drop across R2 of  $1,000 \times 0.0068$  volts (6.8V) which would make point B a more positive potential than point A. Obviously this cannot be because as soon as point B reaches a potential 600mV less than point A base current ceases to flow and hence the emitter current is automatically self limiting. What happens is that the potential at point B rises towards A, the effect of this happening reduces the amount of base current which in turn prevents the emitter current rising further. This is a form of negative feedback.

Provided the current needed through R2 (to make point B rise in a positive direction) is not too great we can arrange matters so that whatever voltage we apply at A, the potential at B will be approximately the same (less 600mV) and the transistor will draw whatever base current it needs to do this through R1. We must, of course, make R1 a low enough value so it is the transistor that decides when enough is enough and not the resistance of R1.

In practice R1 can usually be considerably higher in value than R2 therefore we can convert voltage changes in high resistance circuits to similar changes in low resistance circuits. We say the emitter follower has a high input impedance (because it does not draw much current) and a low output impedance.

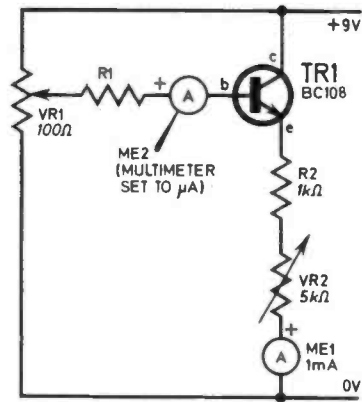


Fig. 1.2. Test circuit for the emitter follower.

### TEST CIRCUIT

You can check some of this for yourselves by using the circuit of Fig. 1.2. First wire up R2, VR2 and ME1 in series and adjust VR2 (with a 4.5V battery connected between the top end of R2 and the negative end of the meter) so you get a reading of 0.9mA. You now have a 5V full scale voltmeter with an internal resistance of approximately 5,000 ohms (1,000 ohms per volt).

Wire up the rest of the circuit and, if you have one, connect a multimeter (set to its lowest current measuring range) in series with R1. Alternatively connect R1 direct to the base of TR1. Start off with R1 being 10 kilohm.

The voltmeter we have made serves two purposes: (a) it enables us to measure the voltage between the emitter and ground by means of the current flowing through it and (b) it is the emitter load. Potentiometer VR1 has very low resistance and hence can be ignored when it comes to calculating current flow in R1.

Set VR1 about a quarter of a turn up from its bottom end (this corresponds to about 2.5V being applied to R1). You should read about 0.4mA on ME1 (this means the emitter voltage has risen to about 2V—roughly 600mV below the input voltage). Now check the base current on ME2—it will be about 2 or 3 microamps (depending on the gain of your transistor).

Leaving everything else as it is remove R1 and substitute another resistor of lower value (say 1 kilohm). You might expect the base current to increase dramatically, but it does not because the transistor draws only what it needs for the emitter voltage to follow the input. As a further experiment try increasing the value of R1 to 100 kilohm and then 1 megohm.

With the 100 kilohm resistor you should not see much change in base current or emitter current (ME1) but when you put in a 1 megohm resistor the base current will fall and there will be an appreciable drop in emitter current because, although the transistor is trying to draw the right amount of base current to keep matters correct, this current is now being limited by R1 and we lose the emitter follower effect.

introducing

**ARROW ELECTRONICS LTD.**

'Service the way it ought to be'

an associate Company of LST ELECTRONIC COMPONENTS LTD.

When it comes to retail distribution we're head and shoulders above the rest!

We're a new Company but our experience and ability in electronic components goes back a long way . . .

Here at Arrow Electronics fast, reliable service is law!

We offer a rapid, same day turn round on all mail received up to 3 p.m. on any given weekday.

What's more, when we promise to clear all orders on receipt, we really mean it!

**A SELECTION FROM OUR CATALOGUE  
COS-MOS-CIRCUITS**

This range of COS-MOS Logic is stocked in DIL plastic encapsulation. This range offers High reliability, high speed operation, high level output compatability with low power TTL and high noise immunity.

Type No.	Description	Price each
CD4001AE	Quad 2 input NOR gate	72p
CD4009AE	Hex. buffer — inverting type	£1.56
CD4011AE	Quad 2 Input NAND gate	72p
CD4012AE	Dual 4 Input NAND gate	£1.16
CD4013AE	Dual "D" Flip-Flop	£1.48
CD4015AE	Dual 4 stage Shift Register	£3.90
CD4017AE	Decade Counter/Divider with Decimal outputs	£3.90
CD4018AE	Presetable divide by "N" Counter	£3.90
CD4020AE	14 Stage Ripple Binary Counter/Divider	£4.34
CD4024AE	7 Stage Counter (Buffered Reset)	£2.78

Order as "COSMOS" + Type No.

**INTEGRATED CIRCUIT SOCKETS**

These low cost sockets are moulded in Makroion with Phosphor Bronze contacts, silver plated.

Type No.	Description	Price
DRD7	14 pin Dual in Line	14p each
DRD8	16 pin Dual in Line	15p each

Order as "DIL Sockets" + Type No.

**LIGHT EMITTING DIODE**

Type No.	Description	Price
TIL209	High brightness visible light source	35p each

**OPTICALLY COUPLED ISOLATOR**

Type No.	Description	Price
TI112	GA source optically coupled to NPN transistor giving high DC transfer ratio with high electrical isolation of 1.5kV.	£2.00 each

**RECTIFIERS — MEDIUM CURRENT**

Plastic cased rectifiers with 3A current capability. Miniature size and axial leads make them particularly useful for Printed circuitry.

Type No.	If (Amps)	PIV	Price
1N5400	3 A	50	14p each
1N5404	3 A	400	18p each
1N5408	3 A	1000	25p each

Shoot me your catalogue

Arrow Electronics Limited

Dept.  
7 Coptfold Road  
Brentwood Essex  
Tel: Brentwood 219435


EE2

Enclose P/O Cheque for 10p.  
Name \_\_\_\_\_  
Address \_\_\_\_\_

# Have fun with electronics...



## Radionic Construction Kits

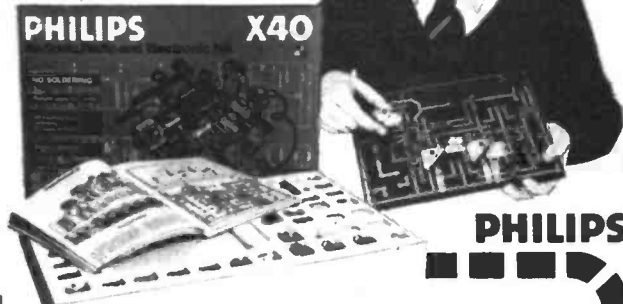

**NO SOLDERING  
BATTERY OPERATED**

Build your own radio receiver and many exciting experiments with the unique printed circuit board and mounted components. Easy to build, no soldering, battery operated, plus a fully illustrated instruction manual giving precise directions for each experiment. Ideally suitable for both the experimenter and beginner.

**Radionic Products Limited**

St. Lawrence House, Broad Street, Bristol BS1 2HF.  
Tel: 0272 25351

Member of the ESL BRISTOL Group of Companies.

**PHILIPS**

Please send me literature on Radionic radio and electronics construction kits.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

EE





## INPUT IMPEDANCE

We say that an emitter follower has an input impedance, but this is not caused by the resistor in series with the base (R1 in Figs. 1.1 and 1.2) the input impedance is an imaginary resistance the value of which we can calculate from the input voltage and the current the transistor wants to draw from it. To a first approximation this impedance is the value of the emitter resistance multiplied by  $h_{FE}$ .

In our experimental circuit of Fig. 1.2 we can say that the input impedance of the transistor is  $200 \times 5,000 = 1,000,000$  ohms. You can see now why adding resistors up to about 100 kilohm had little effect, but as soon as we made R1 1 megohm the potential at the base of TR1 falls by the potential divide effect of R1 (1 megohm) and the input impedance (also 1 megohm).
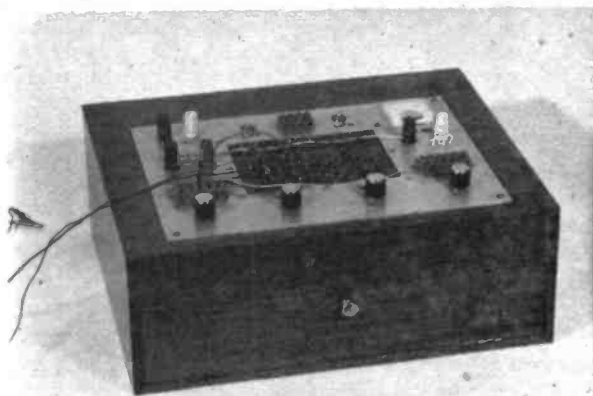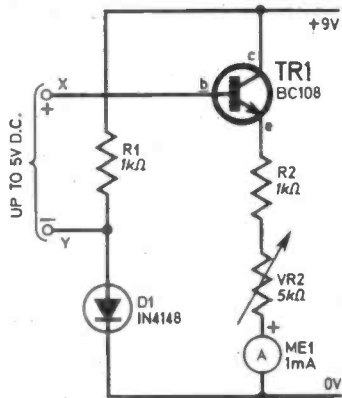
## PRACTICAL CIRCUIT

A practical circuit is shown in Fig. 1.3. This uses the same emitter load as Fig. 1.2 and we



will use the circuit to measure voltages across points X and Y. Point Y is above a forward biased silicon diode so all input voltages at X will be biased up by +600mV. This counteracts the drop between base and emitter of the transistor.


Provided VR2 is set exactly as before we have a 5V range voltmeter monitoring the emitter potential and this, we now know, will be to all intents and purposes the same as the potential difference applied between points X and Y.

The circuit will not draw much current from the voltage source being measured because of the high input impedance of the emitter follower. This being about 1 megohm, corresponds to a sensitivity of around 200,000 ohms per volt.

The circuit of Fig. 1.3 is shown wired up on the Demo Deck in Fig. 1.4.

**Note:** This series of articles is referred to as *Circuit Experiments* in the Demo Deck reprint.

**Next month:** Relaxation Oscillator

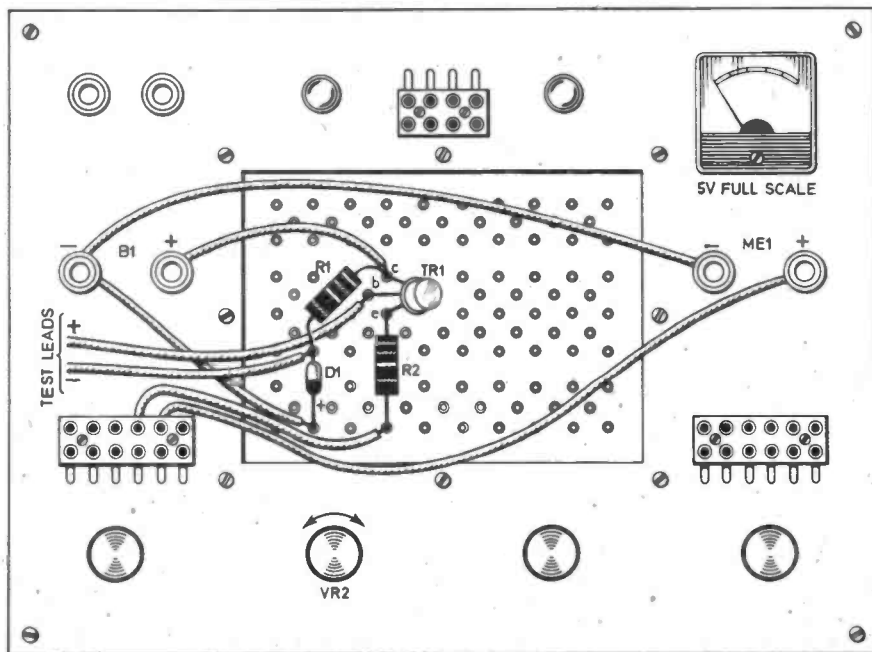

**Fig. 1.3.** (above, left) practical circuit for a 5V d.c. voltmeter.

**Fig. 1.4.** (left) The circuit of Fig. 1.3, wired up on the Demo Deck.



Photograph: IEE library

# THEY MADE THEIR MARK

## NO7 Henry

By J. E. Gregory

IN an earlier article we met Michael Faraday and the dynamo. At about the same time, working independently, 3,000 miles away in America on the problems of induction, was Joseph Henry who gave his name to the unit of inductance.

Henry was born in Albany, New York on December 17 1797, the only son of Scottish immigrant parents. Attending a local country school until the age of 13 he showed "little interest in study". He began his career as a watchmaker's apprentice. At the age of 16 he chanced upon a book, "The Problems of Natural Philosophy". This changed his outlook on life and interests so much that he enrolled as a student at the Albany Academy where he studied Chemistry, Anatomy and Physiology with a view to becoming a doctor. In 1825 he received an unexpected appointment to survey a route for a road across New York State from the Hudson River to Lake Erie, this broadened his interests to engineering.

In 1826 he returned to the Albany Academy to teach mathematics and natural philosophy, and it was here that he started his first experiments in electromagnetism. Henry was the first to insulate wire for the magnetic coil. He also invented the "spool" or "bobbin" winding which allowed electromagnets to be wound with extremely long lengths of wire. The resulting electromagnets were more sensitive than their predecessors and could be used for the detection of electric currents sent over great distances. Electrical dynamos or motors use the electromagnet in practically the form in which it was left by Henry.

Using such a magnet in a mile long electric circuit of copper wire, Henry in 1830, caused a small bell to ring at the end of

Table I: THE HENRY (H)
<p>The unit of self and mutual inductance named in recognition of Joseph Henry's work by the International Electrotechnical Commission at a meeting in Chicago in 1893, who defined it as the inductance of a closed circuit in which an e.m.f. of 1 volt is produced when the electric current in the circuit varies uniformly at the rate of 1 ampere per second.</p>
<p><b>Mutual Induction</b></p> <p>When two coils are coupled by their magnetic fields, a changing current in one coil will produce a changing magnetic flux and induce an e.m.f. in the other coil. The mutual inductance is a measure of the closeness of the coupling between the two coils.</p>
<p><b>Self Induction</b></p> <p>When the current flowing through a coil changes, the accompanying change of magnetic flux will produce an e.m.f. which tends to oppose the current. The self inductance is a measure of the impedance offered to the flow of current.</p>

the line. This is believed to have been the first electrical magnetisation of iron at a remote point, the starting point of the telegraph.

Transferring to the College of New Jersey (later Princeton University) in 1832, Henry startled the Campus by setting up a telegraph line between the laboratory and his house. He added the "relay" to his telegraph machine, and is believed to have been the first to use the earth as a return conductor.

It was also in 1832 that he published his paper on self induction. He found also that a second induced current could induce a third; the third a fourth; and so on, indefinitely, and that these currents could be induced at a distance. Some of his experiments on induction involved the transmission of electric force without wires through the floors and walls of buildings, and in one case he magnetized a needle by the transmission from a lightning flash 8 miles away. This appears to be the earliest record of the action of electromagnetic waves of the type employed in radio telegraphy and telephony today. The discovery of the oscillatory character of the electrical discharge came

in 1842.


Henry has been called the "Father of the Wireless Telegraph". Early in his career Samuel Morse of Morse code fame came to Henry for advice and in 1837 when visiting London, Henry met Cook and Wheatstone who were constructing their telegraph line along the Great Western Railway.

In December 1846 Henry resigned the Professorship of natural Philosophy at Princetown to become the organiser and first secretary of the newly formed Smithsonian Institute. Under his secretaryship, government support for all scientific activity was enlisted, but not content to be known only as an administrator Henry continued, with a wide range of practical experiments in various fields. Experiments ranging from researches in meteorology which laid the foundation for the U.S. Weather Bureau, to the invention of a new method for determining the velocity of projectiles.

Henry died in Washington on May 13 1878. The boy who had "shown little interest in studying" had by general consent become one of America's foremost physicists, and scientific administrators.


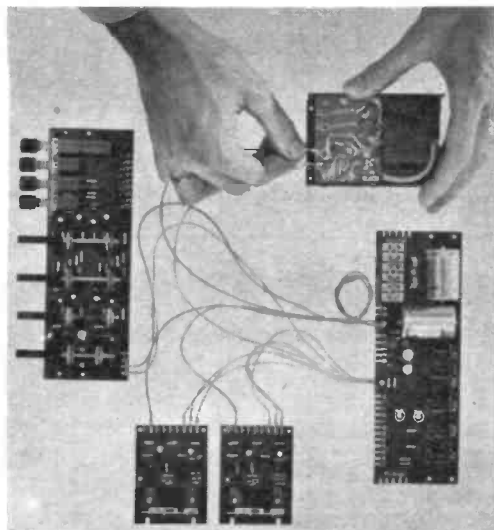
# Project 605 the new simple way to assemble Sinclair high fidelity modules



For several years now you have been able to assemble your own high fidelity system to world beating standards using Sinclair modules. We have progressively improved these technically but hitherto the method of assembly at your end has remained the same – there has been no alternative to a soldering iron. Now for those who prefer not to solder, there is an alternative – Project 605.

In one neat package you can now obtain the four basic Project 60 modules plus a fifth completely new one – Masterlink – which contains all the input sockets and output components you previously bought separately. Also in the Project 605 pack are all the inter-connecting leads, cut to length and fitted at each end with plugs which clip straight onto the modules, eliminating soldering completely. The pack contains everything you need to build a complete 30 watt stereo amplifier together with a clear well illustrated Instruction Book. All you have to do is to arrange your modules in the plinth or case of your choice and then clip them together – the work of a few minutes.

Your hi-fi system will, as we said, match the finest in the world and you can add to it at any time to increase power or extend the facilities. For example a superb stereo FM Tuner unit is obtainable for only £25.

**Guarantee** If within 3 months of purchasing Project 605 directly from us, you are dissatisfied with it, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail, Air-mail charged at cost.

**sinclair**

Sinclair Radionics Ltd., London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Telephone: St. Ives (04806) 4311

## Specifications

Output – 30 watts music power (10 watts per channel R.M.S. into 3 Ω).

Inputs – Mag. P.U. – 3mV correct to R.I.A.A. curve 20–25,000 Hz ± 1dB. Ceramic pick-up – 50mV. Radio – 50 to 150mV. Aux. adjustable between 3mV. and 3V.

Signal to noise ratio – Better than 70dB.

Distortion – better than 0.2% under all conditions.

Controls – Press buttons for on-off, P.U., radio and aux. Treble +15 to –15 dB at 10 kHz. Bass +15 to –15 dB at 100 Hz. Volume. Stereo Balance.

Channel matching within 1dB.

Front panel – brushed aluminium with black knobs.

Project 605 comprises Stereo '60 pre-amp/control unit, two Z-30 power amplifiers, PZ-5 power supply unit, the unique new Masterlink, leads and instructions manual complete in one pack. Post free

**£29.95**

To SINCLAIR RADIONICS LTD., ST. IVES, HUNTINGDONSHIRE PE174HJ

Please send Project 605 post free  Details and list of stockists

Name .....

Address .....

for which I enclose £29.95 cheque/money order/cash.

**E.E.98.**

# C. HADLEY

24, WOODHILL, HARLOW, ESSEX

Add 5p P. & P. Price list S.A.E. No callers please.

All our stocks are brand new with money back guarantee

TRANSISTORS		CAPACITORS	
AC107 15p	AL102 50p	BD116 70p	OC14 13p
AC126 11p	AL103 40p	BD121 50p	OC45 13p
AC127 11p	AL108 85p	BD130 40p	OC71 12p
AC128 11p	AU111 95p	BD131 50p	OC72 12p
AC176 25p	BC107 8p	BF194 15p	OC81 13p
AC141K 20p	BC108 8p	BFY80 15p	OC81D 13p
AC142K 20p	BC109 8p	BFY85A 15p	OC83 20p
AD14 40p	BC164 20p	ME0402 18p	OC200 25p
AD150 44p	BC168 10p	ME0404 14p	OC201 25p
AD161 M/P 55p	BC169 11p	ME4401 10p	OC25 25p
AD162 44p	BC182L 8p	ME4102 12p	OC28 30p
AF114 15p	BC183L 8p	ME9002 14p	OC29 35p
AF115 15p	BC184L 8p	ME8101 14p	OC35 25p
AF116 15p	BC212L 8p	ME8102 15p	OC36 36p
AF117 15p	BC214L 8p	MP8111 32p	TIP29A 48p
		MP8511 34p	TIP30A 55p
		MP8513 45p	TIP31A 58p
		OC41 13p	TIP32A 68p
			2N3710 10p
			2N3711 49p
			2N3712 55p
			2N3713 18p
			2N1171 24p
			2N1304 25p
			2N1305 25p
			2N2646 47p
			2N2926 10p
			2N3053 30p
			2N3055 49p
			2N3702 12p
			2N3703 12p
			2N3704 12p
			2N3705 12p
			2N3706 10p
			2N3707 10p
			2N3708 9p
			2N3709 10p
			2N3710 10p

## MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0-9 and decimals (Data Sheet on request)

ONLY £1.50

for one month only

16 DIL Socket 30p  
Driven by 7447 95p

### SUPER LOW PRICED LINEAR I.C.'S

301A	To99	49p
301A	DIL	45p
709C	To99	28p
709C	DIL	30p
723C	To99	87p
741C	To99	35p
741C	DIL	34p
741C	8p in DIL	34p
747C	DIL	40p
748C	To99	38p

### VOLUME CONTROLS

Potentiometers  
Carbon track 500Ω to 2.2MΩ  
Log or Linear  
Single 12p. Dual gang (stereo) 40p.  
Single type only with D.P. Switch 12p extra.

RESISTORS  
1p each  
4 watt 5% carbon 1p each  
4 watt 10% carbon 1p each  
range 2-7Ω to 10MΩ type TR5  
triple rated 1/4-1/2, tin oxide x 2%  
range 10Ω to 1MΩ. 3p each

SLIDE SWITCH  
8P Three Position 10p each  
12p each

MINIATURE NEON LAMPS  
240v or 110v 1-4 5p, 5 plus 4 1/2 5p each.

### CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only:  
100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7,  
10K, 22K, 47K, 100K, 220K, 470K,  
1M, 2M2, 4M7, 10MΩ. Vertical or  
horizontal mounting, 5p each.

### VEROBOARD

	0-15 Matrix	0-1 Matrix
2 1/2 x 3 1/2 in	17p	23p
2 1/2 x 5 in	25p	23p
3 1/2 x 3 1/2 in	25p	25p
3 1/2 x 5 in	30p	29p
5 x 17 in (Plain)	83p	—
Vero Plus (Bag of 36)	20p.	—
Vero Cutter 45p.	—	—
Pin Insertion Tools (1 and .15 matrix) at 55p.	—	—

### ZENER DIODES

400mW 5% 3.3V to 30V, 15p.

### LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each.  
16 pin type at 16p each.

### TRANSISTOR EQUIVALENTS BOOK

Pack of 20 1N4148	50p	Mix Pack of 20 1N4000 Series Diodes	50p
AC127 & AC128 1-9 10 plus 100 plus	13p 11p 8p	AD161, AD162 M/P 1-9 10 plus	52p 48p
2N3055 1-9 10 plus	40p 18p	BC107-BC108 BC109	8p 7p 6p
Pack of 10 2N2926G unbranded but tested	50p 46p	Pack of 10 Plastic BC109 Unmarked but fully tested	50p
Unmarked but fully tested 2N3055	50p 26p	TBA900 5 watt AF power Amp.	£1.40 each
1-9 10 plus	50p 26p		

MULLARD POLYESTER CAPACITORS C280 SERIES  
250V P.C. mounting: 0-01μF, 0-015μF, 0-022μF, 3p, 0-033μF, 0-047μF, 0-068μF, 3p, 0-1μF, 4p, 0-15μF, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 8p, 0-68μF, 11p, 1-0μF, 13p, 1-5μF, 20p, 2-2μF, 24p.

MULLARD POLYESTER CAPACITORS C296 SERIES  
400V: 0-001μF, 0-0015μF, 0-0022μF, 0-0033μF, 0-0047μF, 2p, 0-0068μF, 0-01μF, 0-015μF, 0-022μF, 0-033μF, 3p, 0-047μF, 0-068μF, 0-1μF, 4p, 0-15μF, 6p, 0-22μF, 7p, 0-33μF, 11p, 0-47μF, 13p.  
160V: 0-01μF, 0-015μF, 0-022μF, 0-033μF, 0-047μF, 0-068μF, 3p, 0-1μF, 3p, 0-15μF, 4p, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 7p, 0-68μF, 11p, 1-0μF, 13p.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES 6p each  
(μF/V) 10/2-5, 20/2-5, 50/2-5, 100/2-5, 320/2-5, 500/2-5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6-4/6-4, 25/6-4, 50/6-4, 100/6-4, 320/6-4, 4/10, 8/10, 32/10, 64/10, 125/10, 200/10, 2-5/10, 10/10, 20/10, 40/10, 80/10, 125/10, 1-5/25, 5-4/25, 12-5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64, 20/64, 32/64.

MULLARD C437 SERIES  
100/40, 160/25, 250/16, 400/10, 640/6-4, 800/4, 1000/2-5, 1p, 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1000/8-4, 1600/2-5, 12p, 160/64, 250/40, 400/2-5, 640/16, 2000/4, 1000/10, 1600/8-4, 2500/2-5, 15p, 250/64, 400/40, 640/25, 3200/4, 1000/16, 1600/10, 2500/8-4, 4000/2-5, 18p.

Miniature Fixed Ceramic Plate, 3p each.  
Preferred values from 1.8p to 10,000p.

## HI-FI BARGAINS

BAKER SPEAKERS  
Group 25, 12" 25 watts ..... 6.70  
Group 35, 12" 35 watts ..... 8.65  
Group 50, 15" 50 watts ..... 17.95  
All types 8 or 15 ohms.



BIB GROOV KLEEN  
with brush and roller  
to keep your records  
in perfect condition.  
£1.80

TRANSISTOR AMPLIFIERS  
Eagle TSA 149 stereo, 7 watts/channel, teak cabinet ..... 24.95  
Eagle TSA 151 stereo, 15 watts/channel, teak cabinet ..... 33.75  
Gem type 304 miniature mono, 3 watts peak ..... 3.95  
Baker 100 watt r.m.s. with Hi-Fi pre-amp. Suitable for guitars, disco, vocal, Hi-Fi, 25Hz-25k Hz ..... 38.50  
Discosound DJ 101 mixer pre-amp, six inputs. Use with tape recorders, most amplifiers, disco etc. .... 13.75  
Discosound DJ 105B, 30 watt r.m.s. amplifier with integral pre-amp. Four inputs, mixing, bass and treble control ..... 37.50

TUNERS AND DECODERS  
A 1005 F.M. Tuner chassis ..... 6.99  
A 1005M Multipler decoder ..... 4.99  
A 1008 F.M. Tuner in cabinet ..... 13.40  
A 1007 A.M. Tuner chassis ..... 4.15  
ST 300C F.M. Tuner chassis ..... 7.85  
VHF 105 Aircraft band converter ..... 4.85

MAGNETIC CARTRIDGES  
Goldring (R80) ..... 6.95  
Goldring G800H ..... 6.55  
Goldring G800E ..... 11.55  
Goldring G800 Super E ..... 18.25  
Goldring G850 ..... 4.95  
Shure M44-7 ..... 6.95  
Shure M55-E ..... 8.85  
Shure M75-6 Shillaline ..... 5.65  
Shure M75-EJ type 2 ..... 12.70  
Shure M75-E type 2 ..... 13.75

PSYCHEDELIC LIGHT CONTROL  
DJ 30L, 3-channel mixing from speaker output. Entertain your friends with this great unit. Total output 3000W. £32.95

SANWA MULTI-TESTERS  
U50 DX 20k o/v | 350 YTR 10k o/v  
28.35 ..... £7.95

RECORDING TAPE—High Quality, Low Noise			
5"		5 1/2"	
L.P.	800 ft	L.P.	1200 ft
D.P.	1200 ft	D.P.	1800 ft
	45p		85p
	92p		1.18
			1.44

TRANSISTORS			
AC 107	28p	AD 140	47p
AC 126	27p	AD 149	47p
AC 127	23p	AF 114	25p
AC 128	20p	AF 118	40p
BC 107	12p	BC 108	12p
BC 108	12p	BC 109	12p
BC 117	8p	OC 171	23p
OC 28	52p	OC 75	22p
OC 75	22p	OC 171	23p
OC 171	23p	OC 171	23p
OC 171	23p	OC 171	23p

ALL R.S. COMPONENTS SUPPLIED, MOSTLY BY RETURN OF POST.  
CATALOGUE only 25p BY RETURN. ALL PRICES POST FREE, U.K.

MAIL ORDER ONLY FROM

## ELECTRON-E

P.O. BOX No. 1, LLANTWIT MAJOR, GLANMORGAN, CF8 9YN.

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME:

ADDRESS:

EEB 12.2  
BLOCK CAPS please



# BI-PRE-PAK

## COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE  
**ONLY 95p**  
 POST & PACKING 35p EACH

TELEPHONE DIALS  
 Standard Post Office type. Guaranteed in working order.  
**ONLY 25p**  
 POST & PACKING 15p

### TESTED AND GUARANTEED PAKS

B3	4	Photo Cells, Sun Batteries. 0-3 to 0-5V. 0-5 to 2mA.	50p
B79	4	1N4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Read Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H39	10	Integrated Circuits. 6 Gates BMC 962, 4 Flip Flops BMC 945	50p
H9	2	OC771 Light Sensitive Photo Transistor	50p
H40	20	BFY50/2, 2N696, 2N1613 NPN Silicon uncodded TO-5	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	50p
H35	100	Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short Lead Transistors. NPN Silicon Planar types.	50p

### UNMARKED UNTESTED PACKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7-Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors. PNP, Germ. NPN Silicon TO-3 Can.	50p

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



## OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
 TYPE "B" NPN Silicon, plastic encapsulation.  
 TYPE "E" PNP Germanium AF or RF.  
 TYPE "F" NPN Silicon plastic encapsulation.

### FULLY TESTED AND MARKED SEMICONDUCTORS

5p		6p	
AC107	0-15	OC139	0-15
AC126	0-15	OC140	0-15
AC127	0-17	OC170	0-23
AC128	0-15	OC171	0-23
AC176	0-20	OC200	0-25
ACY17	0-20	OC201	0-25
AF239	0-30	2N1302-3	0-15
AF186	0-20	2N1304-5	0-17
AF139	0-30	2N1306-7	0-20
BC154	0-20	2N1308-9	0-22
BC107	0-10	2N13819FET	0-40
BC108	0-10	2N4416FET	0-35
BC109	0-10	2N3823EFET	0-30
BC148	0-10	Power Transistors	
BC169	0-12	OC20	0-40
BF194	0-15	OC23	0-25
BF274	0-20	OC25	0-25
BFY50	0-13	OC26	0-25
BSY25	0-13	OC28	0-20
BSY26	0-13	OC35	0-25
BSY27	0-13	OC36	0-37
BSY28	0-13	AD149	0-35
BSY29	0-13	AU110	0-75
BSY95A	0-10	2N3034	0-25
OC44	0-13	2N3055	0-40
OC45	0-10	AA42	0-10
OC71	0-10	OA95	0-07
OC72	0-10	OA79	0-07
OC81	0-13	OA81	0-07
OC81D	0-13	OA95	0-07
OC83	0-18	IN914	0-06

## POWER TRANSISTOR PRICE BREAKTHROUGH!

Plastic cased Silicon Power Transistors of latest design. 40watts and 90watts. PNP & NPN types. All types available at the most shatteringly low prices of all time. All are fully tested, marked and guaranteed!

	1-12	13-25	26-50
40W NPN	20p	18p	16p
40W PNP	21p	19p	17p
90W NPN	24p	23p	20p
90W PNP	25p	23p	21p

PAK PAKS of matched pairs  
 MP40  
 40W + 40W 50p 48p 46p  
 MP90  
 90W + 90W 60p 58p 56p



## A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs **£3.50, post paid.**

A MUST for Colour T.V. Alignment.

## Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p.  
 10p P & P on this Pak.

## FREE CATALOGUE FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS



## 8 RELAYS FOR VARIOUS TYPES P & P 25p £1

### INTEGRATED CIRCUITS

	1-12	13-25	26-50
Clocked Flip Flop	BMC931	20p	18p 16p
Ex. 2/4-input Buffer	BMC932	12p	11p 10p
2/4-input Expander	BMC933	12p	11p 10p
Hex. Inverter	BMC934	12p	11p 10p
Hex. Inverter	BMC935	12p	11p 10p
Hex. Inverter	BMC936	12p	11p 10p
Hex. Inverter	BMC937	12p	11p 10p
Divide Counter	BMC938	25p	23p 21p
Div. by 16 Counter	BMC939	25p	23p 21p
Hex. Inverter	BMC940	12p	11p 10p
Hex. Inverter	BMC941	12p	11p 10p
Type D Flip Flop	BMC942	20p	18p 16p
Ex. 2/4-input Power	BMC944	12p	11p 10p
Clocked Flip Flop	BMC945	20p	18p 16p
4/2 Input	BMC946	11p	10p 9p
Clocked Flip Flop	BMC948	20p	18p 16p
Nand Gate	BMC949	12p	11p 10p
Pulsed Trig. Binary	BMC950	20p	18p 16p
Monostable Multivib.	BMC951	25p	23p 21p
Dual J/K Flip Flop	BMC953	20p	18p 16p
Dual J/K Flip Flop	BMC955	20p	18p 16p
Dual J/K Flip Flop	BMC956	20p	18p 16p
Quad. 2-Input Power	BMC958	12p	11p 10p
2-Input Gate	BMC961	12p	11p 10p
3/3-input NAND Gate	BMC962	11p	10p 9p
3/3-input NAND Gate	BMC963	12p	11p 10p
Audio Amp. 3w. SL403D	£1.50	£1.40	£1.36
Linear Op. Amp 709C	25p	20p	15p
Decade Counter SN7490	65p	60p	55p

### LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile  
 16 pin type at 16p each. } type

### BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

**B.P.I. Transistor Equivalents and Substitutes;** 40p  
 This includes many thousands of British U.S.A., European and C.V. equivalents.

**The Hiffo Radio Valve & Transistor Data Book 9th Edition;** 75p  
 Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Postage and Packing 21p.

Send for lists of these English publications.

Please send me the FREE BI-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

# BI-PRE-PAK LTD

DEPT. E, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF  
 TELEPHONE: SOUTHEND (0702) 46344

## PREMIER 800 STEREO AMPLIFIER



(As used in SYSTEM '800')

A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1%. Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12½" x 6½" x 2½".

ONLY £15.00 Carr. 60p.

Mk. 11 Version available with Teak Finish Cabinet. £16.25. Carr. 50p.


## PREMIER HI-FI STEREO SYSTEMS

### SYSTEM "800"

Consists of the Premier 800 Mk II all transistor stereo amplifier (described left) Garrard auto/manual record player unit fitted stereo/mono cartridge with diamond stylus and mounted in teak finish plinth with cover and two cloth front loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 800 Mk II amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector. Mono/Stereo switch. Headphone socket. Power on/off. Teak finish cabinet with aluminium front panel. Size: 12½in x 6½in x 2½in.

£35.00

Carr. £1.75

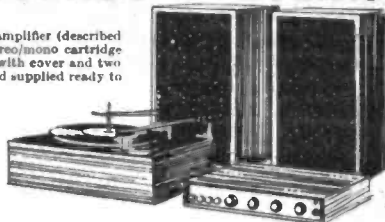

### SYSTEM "TWO"

as above but with slotted front teak finish loudspeakers. Garrard SP25 Mk. III and magnetic cartridge.

£45.00

Carr. £1.75

### SYSTEM "THREE"

This consists of KLINGEE KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and Ceramic pick-up, tuner, tape in and out. Stereo headphone socket. Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of HMF Speakers size 16½" x 10½" x 9" fitted EMI units complete the matching system.

£57.75

**FREE**  
LEADS  
AND PLUGS  
SUPPLIED  
WITH ALL  
SYSTEMS

## PREMIER PARAGON STEREO HI-FI AMPLIFIER



Gives the best possible reproduction of records, radio and tape at a reasonable price.

Fitted with all the controls and facilities you're ever likely to want, the Paragon gives you a degree of sophistication that is usually only found with amplifiers costing twice its price. It has bass and treble slide controls, volume and balance knobs, and eight push-buttons. There's also a standard stereo jack socket on the front panel, plus a ceramic/magnetic cartridge switch and a mains outlet socket on the back panel.

Specifications 10 + 10 watts into 8 ohms. Power/frequency response: 9dB 10 watts into 8 ohms -3dB 20Hz -20KHz. Distortion typically less than 0.25%. Inputs for Magnetic phono (4mV) Ceramic phono (66mV) Radio/Tape (100mV). High and low filters. Teak finish cabinet. Size: 12½" x 5½" x 10½".

£32.00 P. & P. 50p.

Premier Stereo System '69P

Consists of the Premier Paragon Stereo Amplifier, Garrard SP25/III in teak finish plinth with cover and fitted Goldring G800 stereo magnetic cartridge plus a pair of Maruden Hall Annex 100 Loudspeaker Systems.

£69 Carr. & Insurance £1.75

Complete with Free leads and plugs.



**WELLER "EXPERT" SOLDER GUN.** Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 W. P. & P. watt. 240 volt A.C. £3.95 30p

"Litesold" Soldering Iron. Lightweight & pencil bit ideal for regular bench use and around the home. 25 watts. 240 volt A.C. £1.50 P. & P. 16p



**E.M.I. 13 x 8in. HI-FI SPEAKERS**  
Fitted two 2½in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.  
£3.47 P. & P. 50p

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILIBED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth out throughout the entire audio range. Double wrapped—attractively boxed.

TT3 3' 450' POLYESTER 37p	DT6 8½' 1800' POLYESTER £1.18
DT3 3½' 600' POLYESTER 37p	TT8 5½' 2400' POLYESTER £1.87
SP5 5' 500' P.V.C. 42p	ST7 7' 1200' P.V.C. 62p
LP5 5' 900' ACETATE 50p	LP7 7' 1800' ACETATE 75p
DT5 5' 1800' POLYESTER 75p	DT7 7' 2400' POLYESTER £1.25
LP8 5½' 1200' ACETATE 75p	TT7 7' 3600' POLYESTER £2.50

TAPE SPOOLS 3" 5p, 5", 5½", 7" 9p.

Post and Packing 3" 5p, 5", 5½", 8p, 7"-10p (3 reels and over Post Free).



## PREMIER HI-FI OFFERS

- Rogers Ravensbrook II Stereo Amplifier teak £38.50
- Rogers Ravensbourne Stereo Amplifier teak £55.00
- Metrosound ST20E Stereo Amplifier teak £25.50
- Goldring GL72 less cartridge £22.00
- Garrard SP25 III with Goldring G800 cartridge £15.00

P. & P. 60p extra any of above.



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE. COMPLETE IN TEAK PLINTH WITH COVER.  
Total list price over £34.

### PREMIER PRICE

£17.95

P. & P. £1

Garrard AP76 with G800, ready wired to 5 pin Din in plinth with cover £29.50 P. & P. £1

Garrard AP76 less cartridge P. & P. 60p. £18.80

Garrard 401 Transcription Unit P. & P. 60p. £26.60

Garrard 2025 T/C with Stereo Ceramic Cartridge P. & P. 60p. £8.50

Garrard 2025 T/C with Stereo Ceramic Cartridge ready wired in teak plinth with cover P. & P. £1. £12.45

**CARTRIDGE BARGAINS!**  
Goldring G800M £5.00; G800 £5.50; G800E £9.50; P. & P. 10p



### METER BARGAIN

MODEL GT-800 MULTIMETER

A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. R.A.G.P. — DC Voltage: 10, 50, 250, 1,000V (1,000 opV). AC Voltage: 10, 50, 250, 1,000V (1,000 opV). DC Current: 1mA, 100mA. Resistance: 0-150K ohms. Decibel: -10 to +22dB (at AC 10V range) £2.47, P. & P. 25p.




### HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.

£2.47 P. & P. 25p.
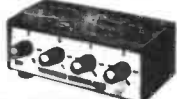
### VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2½in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono plugs output. Attractive teak wood grain finish case.



MONO MODEL £3

STEREO MODEL £3.47 P. & P. 15p

## E.M.I. LOW NOISE CASSETTES in library cases



C60 (List 71p) 45p  
C90 (List 98p) 65p  
C120 (List £1.49) 85p P. & P. 10p

## LOW-NOISE COMPACT CASSETTES

Screw fixing—fully guaranteed. In Library cases.

	EACH	3 for	6 for	10 for
C60	29p	81p	£1.56	£2.50
C90	40p	£1.11	£2.16	£3.50
C120	52p	£1.40	£2.76	£4.50

P. & P. 10p each (3 and over 15p)

# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



### BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p. 50 cycle, 0-38 amp (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/100th h.p. 50 cycle, 0-28 amp.

"As new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. Input. Price, either type £3-50 plus 35p P. & P. or less transformer £2-25 plus 27p P. & P.

### PARVALUX TYPE SD2. 200/250 VOLT A.C. D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch. Illustrated at 3,200 r.p.m. PRICE: £1-75 P. & P. 25p. Other models available on request.

### 600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3inc. P. & P.

### ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3-00. P. & P. 22p.

### 50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7-75. P. & P. 30p.

### CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instruction. £1-75 inc. post.

### RAINBOW STROBE FOUR LIGHT CONTROL MODULE

In response to numerous requests, we now offer a mains operated fully isolated short-circuit proof ready-built module with variable flash rate. It will operate four of our Hy-Light or Super Hy-Light Strobes in either 1, 2, 3, 4 sequence; 2+2; or all together. Fantastic effects with or without colour filters. Modules can be connected together to operate 8 or 12 Strobes. Will work on long runs up to 50 yards, so that your Strobes can be spaced out for maximum effect. Size of module is 5x6x1½in. Easily fitted into your own equipment, or into a separate case. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18-50 plus 25p P. & P. Send S.A.E. for details.

### BIG BLACK LIGHT

400 Watt. Mercury vapour ultra violet lamp. Outer bulb designed to absorb visible light and to transmit u.v. rays. Extremely compact and powerful source of u.v. Ideal for stage, display, disco's etc.

### COLOUR WHEEL PROJECTOR

Complete with oil filled colour wheel. 100 watt lamp. 200/240 V A.C. Features extremely efficient optical system. £18-50 + 35p P. & P.

### VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/140V a.c. 50/60 OUTPUT VARIABLE 0.260V from ½ to 50 amp stock. SHROUDED TYPE

1 amp, £7-00 2-5 amp, £8-05  
5 amp, £11-75  
10 amp, £22-50 20 amp, £49-00  
15 amp, £25-00 25 amp, £58-00  
37-5 amp, £82-00 50 amp, £98-00  
OPEN TYPE (Panel Mounting) 1 amp, £4-75.  
2 ½ amp, £7-00 5 amp, £8-05 All types carriage paid.

### Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT, 1 ohm, 10A; 5 ohm, 4-7A; 10 ohm, 3A 25 ohm, 2A; 50 ohm, 1-4A; 100 ohm, 1A; 250 ohm, 0-7A; 500 ohm, 0-45A; 1 kΩ, 280 mA; 1-5 kΩ, 230mA; 2-5 kΩ, 0-2A; 3-5kΩ, 165mA 5 kΩ, 140mA. Diameter ¾in Shaft length ¾in, dia. ½ in. All at £1-65 each. P. & P. 7p.  
50 WATT, 1/5/10/25/50/100/250/500/1k/1-5k/2-5k/5kΩ. All at £1-15 each. P. & P. 7p.  
25 WATT, 10/25/50/100/250/300/500/1k/1-5k/2-5k/3-5kΩ. All at 90p each. P. & P. 7p.

### RELAYS New SIEMENS PLESSEY, etc. Miniature Relays at competitive prices.

1		2		3		4	
52	3-6	2 c/o	63p*	700	15-35	2 c/o HD	73p*
280	9-12	2 c/o	73p*	700	16-24	6M	65p*
410	10-18	4 c/o	73p*	1,200	24-36	4 c/o	63p*
700	16-24	4 ½ 2B	63p*	2,500	36-45	6M	63p*
700	16-24	4 c/o	78p*	2,400	30-48	4 c/o	50p*
700	12-24	2 c/o	63p*	9,000	40-70	2 c/o	50p*
700	6-12	1 c/o HD	80p*	15k	85-110	6M	50p*
700	22-30	6 c/o	75p				

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. \*Including Base.

### 12 VOLT D.C. RELAY 140 OHM COIL

Type 1: 3 sets c/o contacts 5 amp. 78p incl. P & P (similar to illustration below).  
Type 2: 1 set of c/o contacts 60p incl. P & P.

### 'DIAMOND H' 230 VOLT A.C. RELAYS

Three sets c/o contacts rated at 5 amps. Price: 50p P & P 10p. (100 lots £40-00 incl. P & P.) (UNUSED)

### 'KEY SWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. BOXED. Price: 40p. P & P 5p. (100 lots £32-00 incl. P & P.)

### MINIATURE LATCHING RELAY

Manufactured by Clare-Elliott Ltd. (Type F). 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size ½" high 1" wide, 1" thick. Complete with 3" leads. New 73p incl. P. & P.

### PROGRAMME TIMERS

240V A.C. 5 r.p.m. motor. 2 models available with either 10 cams or 15 cams. Each cam operating a 10 amp c/o micro switch. Cams are individually variable allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW 10 cam £4-75 p. & p. 25p. 15 cam £5-75 p. & p. 25p.

### STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard 5.C.R. Unijunction Xenon Tube and instructions £6-30, plus 25p P. & P.

**NEW INDUSTRIAL KIT**  
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10-50. P. & P. 50p.

**HY-LIGHT STROBE MK III**  
Designed and produced for use in large halls and utilises a silica tube printed circuit. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £2-00. P. & P. 50p.

**SPECIALLY DESIGNED, FULLY VENTILATED METAL CASE.** Including reflector. £4-00 P. & P. 45p. Post paid with kit.

### THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe. Incorporating:

- Variable speed from 1-23 flash per sec.
- Reflector control circuit producing an intense white light. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.

**ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE** specially designed for the Super Hy-Light Kit including reflector £7-00 P. & P. 45p.

**7-inch POLISHED REFLECTOR**  
Ideally suited for above Strobe kits. Price 33p. P. & P. 13p or post paid with kits.

**6 IN COLOUR WHEEL** as used for disco lighting effects etc. £5-75 incl. P. & P. can be operated from our 1 r.p.m. synchronous motor 75p incl. P. & P.

### SINCLAIR PROJECT 60

Z30 £3-50  
Z50 £4-25  
PZ5 £3-97  
P26 £6-26  
Project 60  
tuner £16-80  
AFU £4-50



Stereo 60 £7-80  
Project 605 £19-00

### PROJECT 60 KIT

£2-50

Our extremely popular kit contains the extra capacitor, DIN plugs and sockets, cables and fuse holder needed to complete Project 60.


### S-DECS AND T-DECS

S-DECS £1-40  
T-DECS £2-80  
M-DEC A £3-00  
16 di IC carriers £1-25


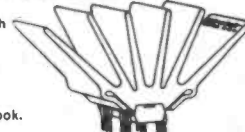
### SINCLAIR SUPER IC12

Complete with free printed circuit board and 44 page instruction book.



Special price if bought with basic or deluxe kits below, only £1-80 plus 10p postage. (£2-00 if purchased separately)

### DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-30. Stereo version with balance control £3-00.

### BASIC KIT FOR THE IC12

Contains components for P.C. board and volume and simple tone controls. Mono version £1-10. Stereo model with balance control £2-00.

### POWER UNITS FOR THE IC12

A set of components to construct a 28V 0.5 amp power supply £2-27. Also suitable Sinclair PZ5 fully constructed £3-87.

### LOUDSPEAKERS FOR THE IC12

Specialty chosen for the IC12. 5" 8 ohm £1-06. 5" x 8" 8 ohm £1-45. 10" x 6" x 15 ohm £2-27.

### PREAMPLIFIER KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1-20. Stereo model £2-20. Type 2 for ceramic or crystal pickups. Mono 48p. Stereo 96p.

### SEND S.A.E. FOR FREE LEAFLET ON KITS

### IC RADIO CHIP TBA651

As featured in July Practical Wireless IC of the month feature. Contains RF Amp, oscillator, mixer, IF Amps, detector, voltage stabilizer and wide range A.G.C. circuitry. Specially developed by SGS for high performance radios and car receivers. Complete with application data £2-00.

### AC/DC CONVERTOR SENSATION

Introducing the most versatile AC/DC convertor yet offered, with a high current output that makes it suitable for operating most battery tape recorders, record players, cassette recorders and shavers. Input 200/240 V. Output voltage selected by front panel switches may be 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500 ma. Housed in a very strong, attractive plastic case and fully guaranteed for 12 months. £4-47.

### SINCLAIR EXECUTIVE CALCULATOR



Weights only 2½oz. Fits the pocket. Runs for 3 months average use on one set of tiny hearing aid batteries. Contains 7000 transistors. Brilliant 8 digit display. Adds, subtracts, multiplies and divides. Constant multiplier facility. Floating point or fixed point with 2, 4 or 6 decimal places. Subject to manufacturer's complete 5 year guarantee. Comprehensive after sales back up is supplied by Sinclair's famous service dept. If any Executive purchased from us fails to give satisfaction and is returned undamaged in 10 days we undertake to refund the whole purchase price.

SAVE £10.  
OUR PRICE ONLY £69 (List Price £79).

**SWANLEY ELECTRONICS**  
32 Goldsel Road, Swanley, Kent

Mail order only. Postage 10p per item. Our Hi-Fi colour catalogue is 10p post free

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
Dept. F.E. 57 Bridgman Road, Chiswick, London, W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.  
9 LITTLE NEWPORT ST.  
LONDON WC2H 7JJ 01-437 0576

### Eliminators



- 9 volt @ 20mA (PP3) £1.25
  - 6 volt @ 50mA £1.50
  - 9 volt @ 50mA £1.50
  - 6 + 6 volt, 50mA £2.50
  - 9 + 9 volt, 50mA £2.50
  - 7 1/2 volt for cassette recorders £2.00
  - 6, 7 1/2 or 9 volt £3.00
  - 3, 4 1/2, 6, 7 1/2, 9, 12 @ 500mA £3.99
  - Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts (illustrated) £4.99
- (p. & p, 15p. on all types)

### DIL Sockets



- 14 and 16 pin  
**16p**  
(including ZIG-ZAG)

# THE TEXAN



Complete Kit (inc. Teak Case) **£28.50** 06p 45p

20 Watts per channel integrated stereo amplifier developed by engineers of 'Texas Instruments Ltd.' This designer approved kit, has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 Hz at -3db. The semiconductor complement of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistors, 4 rectifiers and 2 zeners. Controls include : bass, treble, volume, balance; on/off; 'on' indicator; headphone sockets; scratch filter; rumble filter; inputs for magnetic phono; tuner, aux or tape; tape head etc; input; selector; mono/stereo switch. The construction of this kit was featured in 'Practical Wireless' May - Aug. 1972.

### Veroboard

	Copperclad		Plain
	0.1"	0.15"	
2 1/2" x 1"	6p	6p	-
2 1/2" x 3 1/2"	20p	16p (9)	10p
2 1/2" x 5"	24p	21p (7)	12p
3 1/2" x 3 1/2"	24p	21p (8)	-
3 1/2" x 5"	27p	27p (10)	17p
17" x 2 1/2"	67p	50p	37p
17" x 3 1/2"	90p	70p	52p
17" x 5"	-	-	75p

- Spot-face Cutter 36p
- Pin Insertion Tool 47p
- Terminal Pins 18p per pack of 36

### Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2 1/2"	5 1/2"	1 1/4"	35p	8p
(8)	4"	4"	1 1/4"	35p	8p
(9)	4"	2 1/2"	1 1/4"	35p	8p
(10)	4"	5 1/2"	1 1/4"	40p	8p
11	4"	2 1/2"	2"	35p	8p
12	3"	2"	1"	32p	9p
13	6"	4"	2"	50p	10p
14	7"	5"	2 1/2"	58p	12p
15	8"	6"	3"	75p	18p
16	10"	7"	3"	85p	20p

### Resistors

1/2 watt 5% Carbon Film - low noise Hi-Stabs All E24 values 1p. each plus p. & p. 7p. for up to 50 Resistors and a further 2p for each additional 50. Deduct 33 1/3% for 100 of one type or 25% for mixed orders over £1 in value.

- 1 watt 10% Carbon Composition 3p. each
  - 2 watt 10% Carbon Composition 6p. each
  - 2 1/2 W 5% Wire wound 9p. each
  - 5 W Wire wound 9p. each
  - 10 W Wire wound 10p. each
- plus p. & p. 7p. for up to 25 resistors plus 1p. for each additional 25.

### Semiconductors


AC107	25p	AF239	30p	BF197	15p	2N1304	23p	AA120	9p
AC126	17p	BC107	10p	BU105	£2	2N1893	30p	AA129	9p
AC127	15p	BC108	10p	MPF102	40p	2N2926	10p	BA100	15p
AC128	15p	BC109	10p	MPF103	37p	2N3053	23p	BA154	13p
AC176	20p	BC147	10p	MPF104	37p	2N3055	49p	BA155	14p
AC187	25p	BC148	10p	MPF105	40p	2N3702	12p	BA156	15p
AC187K	25p	BC149	10p	MPF106	45p	2N3704	17p	DA47	10p
AC188	25p	BC157	12p	OC28	40p	2N3819	35p	DA79	9p
AC188K	25p	BC158	10p	OC35	40p	IN914	11p	DA81	7p
AD140	40p	BC159	12p	OC44	15p	IN4148	6p	DA90	7p
AD149	40p	BC169	15p	OC45	15p	IN4001	6p	DA91	7p
AD161	60p	BF180	26p	OC71	11p	IN4002	7p	DA200	10p
AD162	60p	BF181	30p	OC72	17p	IN4003	8p	DA202	10p
AF114	18p	BF184	25p	OC170	23p	IN4004	8p	SL403D	£1.50
AF115	18p	BF185	25p	OC171	30p	IN4005	10p	µA709C	45p
AF116	18p	BF194	15p	2N697	18p	IN4006	12p	µA710	45p
AF117	18p	BF195	15p	2N706	12p	IN4007	15p	µA71C	50p
AF139	28p	BF196	15p	2N708	15p	AA119	9p	µA723C	£1.05

### Thermistors



- RS3 £1.32
- VA1005 13p
- VA1026 13p
- VA1033 13p
- CZ1 15p
- CZ4 15p
- CZ13A 13p
- GL16 £1.00
- GL23 £1.00
- A15B 75p

### Heat Sinks

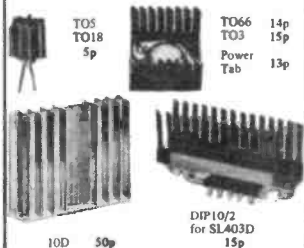

# CHROMASONIC electronics

### Capacitors

#### Mylar

- 100V

Value	2p	0.04µF	3p
1000pf	2p	0.04µF	3p
2000pf	2p	0.05µF	3p
5000pf	2p	0.068µF	4p
0.01µF	3p	0.1µF	4p
0.02µF	3p	0.2µF	5p

#### Polystyrene - 160V

10pf to 10,000pf all 3p. each in multiples of 10, 15, 22, 33, 47 & 68.

#### Mullard C280 - 250V

0.01µF	3p	0.22µF	5p
0.015µF	3p	0.33µF	6 1/2p
0.022µF	3p	0.47µF	8p
0.033µF	3p	0.68µF	11p
0.047µF	3p	1µF	13p
0.068µF	3 1/2p	1.5µF	20p
0.1µF	4p	2.2µF	24p
0.15µF	4p	-	-

#### Mullard C281 - 400V

0.01µF	4 1/2p	0.1µF	7p
0.015µF	4 1/2p	0.15µF	8p
0.022µF	4 1/2p	0.22µF	10p
0.033µF	5 1/2p	0.33µF	14p
0.047µF	6p	0.47µF	15p
0.068µF	6p	-	-

### Mullard C426, 015


£016 all 6p each

Voltage	2.5	4	6.4	10	16	25	40	63
Capacity µF	22	15	10	6.8	1	150	100	10
	47	68	22	47	2.2	100	150	10
	100	150	47	100	47	100	100	10

10	8	6.4	4	2.5	1.6	1	0.64
40	32	25	16	10	6.4	4	2.5
80	64	50	32	20	12.5	8	5
160	125	100	64	40	25	16	10
320	250	200	125	80	50	32	20
500	400	320	200	125	80	50	32

### Mullard C437 & 017

2.5	4	6.4	10	16	25	40	64
1000	800	640	400	250	160	100	64
1600	1250	1000	640	400	250	160	100
2500	2000	1600	1000	640	400	250	160
4000	3200	2500	1600	1000	640	400	250
			470		220		10p
					470		12p
						470	18p

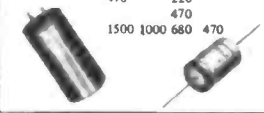

We also hold:  
Mullard C333 ceramics 1.8pf - 330pf 63V. 5p  
Silvered Mica 1%; 500V; 2.2pf - 820pf 7p  
Feedthrough ceramic 1000pf; 350V. 5p  
Disc ceramics, monolithic ceramic, high voltage types; tantalums etc.

### Mullard C431

10	16	25	40	64
2000	1250	800	500	320
3200	2000	1250	800	500
5000	3200	2000	1250	800
10000	6400	4000	2500	1600
16000	10000	6400	4000	2500

### HT Electrolytics

1; 2; 4; 8µF	450V	14p
16µF	450V	15p
32µF	450V	20p
50µF	350V	20p

### TV & Radio Types

8 + 8µF; 450 V.W	18p	32 + 32µF; 350 V.W	25p
8 + 16µF; 450 V.W	20p	32 + 32µF; 450 V.W	43p
16 + 16µF; 450 V.W	25p	50 + 50µF; 350 V.W	35p
16 + 100 + 100 + 300µF; 275 V.W.	£1.23		
32 + 100 + 125 + 200µF; 275 V.W.	£1.23		
32 + 100 + 200 + 200µF; 300 V.W.	£1.23		
100 + 100 + 100 + 150 + 150µF; 320 V.W.	£1.66		
100 + 100 + 200 + 300µF; 275 V.W.	£1.23		
60 + 100 + 200µF; 300 V.W	93p		
100 + 200 + 200µF; 300 V.W	£1		
100 + 200µF; 275 V.W	75p		
100 + 400µF; 275 V.W	£1.15		
200µF; 275 V.W.	50p	300 + 300µF; 300 V.W	£1.90

### Potentiometers



5K Ω	50K Ω	500K Ω
10K Ω	100K Ω	1M Ω
25K Ω	250K Ω	2M Ω

- log or lin less switch 12p
- log or lin with switch 24p
- dual less switch 40p
- dual with switch 10K, 100K & 1M log only 52p
- 10K log + 10K antilog less switch 40p

### Slider Pots

Single	Dual	
10K	10 + 10K	
25K	25 + 25K	log
50K	50 + 50K	or
100K	100 + 100K	lin
30p	50p	
Knobs	10p.	

### Presets

Vertical or Horizontal			
0.1 watt 5p	0.25 watt 7p		
100	1K	10K	100K
250	2.5K	25K	250K
500	5K	50K	500K
			1M

# Everyday Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 10p. extra. Semi-display—£6.00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisements Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

## RECEIVERS and COMPONENTS

Versatile  
**10 in ONE**



### MINI-LAB

Comprising

- AC & DC Voltmeter ● Audio Generator
- Ohm Meter ● Resistance Substitution
- Capacitance Substitution ● DC Ammeter
- Battery Supply ● RF Signal Generator ● RF Field Strength Indicator

This new, unique instrument combines all you need for testing. Guaranteed, money back if not satisfied.

**£11.25**

+25p. p&p

Cash with order or write for illustrated data sheet to:

### RSL COMPONENTS (Dept. EE)

Cricklefield Lane, Bishop's Stortford, Herts.

### SOUND SUPPLIES

(Electronics) Co. Ltd.

P.A. EQUIPMENT, Marshall amps, Instruments and guitars, etc. TOA and Eagle amps and accessories, Reslo mics, etc.

COMPONENTS. Resistors, capacitors, plugs, sockets, cables, audio leads, semiconductors, valves, vero board, etc., for the constructor. Power packs and car droppers for the cassette recorder or radio.

S.A.E. for list and enquiries. P.A. list 15p.

12 Smarts Lane, Loughton, Essex

Tel. 01-508 2715 Closed all day Thursday

FOR ALL YOUR Electronic Component requirements. Send for free list to B.C. Electronic Supplies, 7 Regent Road, Huddersfield HD1 4NR.

COMPUTER PANELS 5BC108, diodes, 4-50p post 10p. PANELS WITH SILICON AND GERM/TRANS. at least 50. £1.00 post 15p. UNIT WITH 4-LA2 POT CORES CAPS 50p post 15p. ICs 7400 SERIES ON PANEL(S) 10-75p post 10p. FALL-OUTS 5-45p. DRP12 on panel ex equip. 35p cp. WIRE ENDED NEONS 10-45p, 20-75p post 8p. SEND LARGE S.A.E. FOR LIST OF PANELS ETC.

7LB ASSORTED COMPONENTS £1.50 cp.

J.W.B. RADIO  
75 HAYFIELD ROAD SALFORD 6 LANCAS  
MAIL ORDER ONLY

## EXPRESS COMPONENTS

17 Albert Square, Stratford,  
London E15 1HJ

### ELECTRONIC KITS FOR E.E. PROJECTS

HAVE you waited weeks (or months) in the past for your electronic components to arrive??? Well you won't have to any more—not if you order from us!! It is our intention to satisfy our customers—quickly and completely!!! This month's bargains are:—

HORSES FOR COURSES £2.00

WASH/WIPE CONTROLLER £2.10

SHAVER INVERTER (20 watt) £3.75

These kits comprise all electronic components to complete the project.

OTHER COMPONENTS Transistors: AD142 (similar characteristics to OC26, OC28, OC29 OC35). .35p each; Relays: 185 Ω 2-pole change-over 5A contacts. £1.00 each; Wafer switches: 1-pole 12-way, 4-pole 3-way, 3-pole 4-way. .20p each; Microswitch: S.P.C.O.. 15p each; Potentiometers: 25k Ω log. .12p each, 250k Ω log with D.P.D.T. switch. .20p each; Mains neons (with resistor). .20p each.

Orders over 50p post free, others add 5p.

MAIL ORDER ONLY

### NEW MODEL V.M.F. KIT Mk 2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 + p. & p. 10p U.K. only.

Illustrated catalogue of selected kits and components. 15p P. & P. free.

Gallison Trading Co., Dept E.E.  
12 Burns Way,  
Corringham,  
Stanford-le-Hope, Essex.

TRANSISTORS: mint, branded top grade AD161/162 c.p.r., 60p; BC107B, 12p; BC169C, 10p; 2N2926G, 12p; 2N3702, 10p; 2N3704, 10p. Diodes: OA90, 6p; IN4002, 5p. Mail order only, UK postage 5p. AMATRONIX LTD., 396 Selsdon Rd., South Croydon, Surrey, CR2 0DE.

## BOOKS

"HOW TO LISTEN TO THE WORLD 1973", £1.90. "World Radio TV Handbook", published December, £2.80, post (first class) 10p each, David McGarva, Box 114J, Edinburgh EH1 1HP.

## EDUCATIONAL

MEN! You can earn £50 p.w. Learn computer operating. Send for FREE brochure—London Computer Operators Training Centre, G22 Oxford House, 9-15 Oxford Street, London, W.1.

**FREE**

### TO ENGINEERS

Whatever your age or experience you must read New Opportunities. It describes the easiest way to pass A.M.S.E., A.M.I.M.I., City & Guilds (all branches), Gen. Cert., etc., and gives details of courses in all branches of engineering Mechanics, Electrical, Civil, Auto, Aero, Radio, TV, Building, etc. You must read this book.

Send for your copy today—FREE!

B.I.E.T. B32, Aldermaston Court,  
Reading, RG7 4PF

Accredited by the Council for the  
Accreditation of Correspondence Colleges

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

## SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide, S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

## WANTED

WANTED. Hire, buy, Everyday Electronics, Nos. 1-7, 49 Shaftesbury Drive, Maidstone, Kent.

## MISCELLANEOUS

EXPERIMENTERS! Hundreds of unusual items cheap, catalogue only 5p. Grimsby Electronics, Lambert Road, Grimsby, Lincs.

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE, LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW

S.A.E. for details

TO: BOFFIN PROJECTS,  
DEPT. KEE,

4 CUNLIFFE ROAD,  
STONELEIGH, EWELL, SURREY

ENCAPSULATE your circuit in crystal clear plastic, cold pouring, quick setting. S.A.E. Westby Products (Dept. PF2), East Keswick, Nr. Leeds.

## 12 VOLT FLUORESCENT LIGHTS

(as illustrated)



Best power cuts, be Independent. Ideal for Caravans, Tent, Emergency Lighting, etc. Works anywhere where 12V is available. Guaranteed for six months, READY TO USE at:-

12ins 8watt £3.60 post paid

21ins 13watt £4.60 post paid

SALOP ELECTRONICS  
23 Wyle Cop  
Shrewsbury,  
Shropshire.

Callers welcome for lists or Enquiries Large S.A.E.

RADIO & TELEVISION AERIAL BOOSTERS £2.95p, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50, carr. £1.50p. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge Street, Ramsbottom, Bury, Lancs.

## MUSICAL MIRACLES

KITS to build quality accessories:—

WAA-WAA all parts, electronic & mech. £2.95


FUZZORAMA quality fuzz box £4.75 P&P 20p.

BASS PEDAL 16" and 8" tones £35

BUILD A SYNTHESIZER OR AUTO RHYTHM from Dewtron professional modules

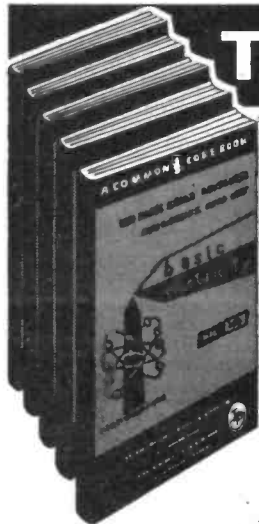Cat. 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AR





# The Pictorial Method

## BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR  
100%  
GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

### WHAT READERS SAY

I find the manuals most enlightening and I am very grateful. *A.C. Stratford.*

By far the easiest and simplest manuals I have ever studied. *L.S. High Wycombe.*

These books make interesting reading of a complicated subject. *A.V. Andover.*

I am delighted with these marvellous manuals, they are so easy to follow: well done. *W.A. Cheltenham.*

**POST NOW FOR THIS OFFER!**

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £4.50

BASIC ELECTRONICS 6 parts £5.40

BASIC TELEVISION 3 parts £3.60

Tick Set(s) required.

Prices Include Postage and Packing.

**YOUR 100% GUARANTEE.** If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME .....

BLOCK LETTERS

FULL POSTAL.....

ADDRESS .....

**EX COMPUTER PRINTED CIRCUIT PANELS**  
2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for \$1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot. Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875—All long leaded on panels 1 1/2in x 4in. 4 for \$1, P. & P. 25p.

**709C OPERATIONAL AMPLIFIER TOS**  
8 lead I.C. 1 off 50p. 50 off 35p. 100 off 20p.

**250 MIXED RESISTORS** 62p  
1/2 and 1/4 watt.

**150 MIXED HI STABS** 62p  
1/2, 1/4 and 1 watt 5% and better.

### QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each, P. & P. 5p.

### GPO EXTENSION TELEPHONES

with dial but without bell. 95p each, P. & P. 30p. \$1.75 for 2, P. & P. 50p.

### BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2-5k  $\Omega$  coil. 8 for 50p, P. & P. 5p.


**KEYTRONICS** mail order only

44 EARLS COURT ROAD

LONDON, W.8

01-478 8499
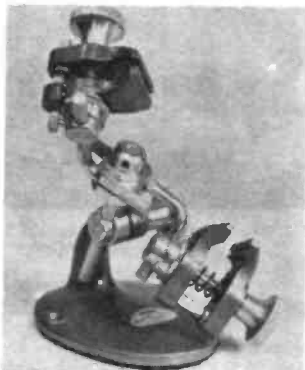
## The New Styled "MULTI-MINI" TWIN-VICES



An extra "Pair of hands" for those tricky jobs  
**ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING—ETC.**

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

**TWIN VICE: £8.95 (25p P. & P.)**

Also available

**SINGLE VICE: £5.45 (21p P. & P.)**

**CANLEY ENGINEERING (SALES) LTD.** DEPT. C/E2  
OSBORNE ROAD, COVENTRY CV5 6EA  
TEL: (0203)-77163/4.

## B.H. COMPONENT FACTORS LIMITED

**MULLARD POLYESTER C280 250V. ( $\mu$ F) 0.01-0.015, 0.022, 0.033, 0.047, 3p. 0.069, 0.1, 0.15, 4p. 0.22, 5p. 0.33, 7p. 0.47, 8p. 0.68, 10p. 1.0, 13p. 1.5, 20p. 2.2, 23p.**

**MULLARD POLYESTER C296: 160V. ( $\mu$ F) 0.01, 0.015, 0.022, 2p. 0.047, 0.068, 3p. 0.15, 0.22, 4p. 0.33, 5p. 0.47, 6p. 0.68, 1.0, 10p. 400V: ( $\mu$ F) 0.001, 0.0015, 0.0022, 0.0033, 0.01, 2p. 0.015, 0.033, 3p.**

**MULLARD ELECTROLYTIC C426, 5p. each. ( $\mu$ F/V) 0.64/64, 1.6/25, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/6.4, 125/16, 125/10.**

**MULLARD C437: 64/64, 160/25, 640/6.4, 9p. 160/40, 11p. 1600/6.4, 14p.**

**LARGE ELECTROLYTIC: 500/25, 10p. 500/50, 12p. 1000/12, 10p. 1000/25, 2000/12, 2500/12, 15p. 1000/50, 35p. 2000/25, 25p. 2500/25, 30p. 3000/50, 65p. 5000/50, 85p. 2500/50, 55p.**

**CERAMIC PLATE. 750V: ( $\mu$ F) 5, 10, 25, 40, 70, 220, 21p. ( $\mu$ F/V) 0.0047/30, 0.01/350, 21p. 0.047/30, 3p. 0.1/30, 4p. 0.1/100, 5p. 22pF-0.01 $\mu$ F, 50V: 2p. (E12 series).**

**CARBON FILM RESISTORS, 1/2W. 5% 100hms-2.2M 1p. each, or 100 for 55p.**

**SPECIAL RESISTOR KITS (1W 5% Carbon Film) 10E12KIT. 10 each E12 value, 100hms-1M**

A total of 510. £2-80 net

25E12KIT. 25 each E12 value, 100hms-1M

A total of 1525. £8-50 net

**VEROBOARD 0.1 0.15**  
2 1/2" x 5" 25p 25p  
2 1/2" x 3 1/2" 23p 17p  
3 1/2" x 5" 29p 30p  
3 1/2" x 3 1/2" 25p 25p  
Pins, Pkt. 25 8p 8p

2 Pin DIN Plug 12p, Socket 10p

3 Pin DIN Plug 13p, Socket 10p

5 Pin DIN Plug 180° 15p, Socket 12p

Red Panel Neon 240V. 15p

EP Chokes ( $\mu$ H) 0.22, 2.2, 12, 22 22p

PVC Wire 7/0078, 5 x 10 yds. 30p

PVC Wire 14/0078, 5 x 10 yds. 20p

Neon Bulb 80V, wire ended 5 for 30p

Min. Push button, push to make 10p

Mains Transformer 32-0-32 at 150mA 5pp

1N4001, 8p. 1N4002, 7p. 1N4003, 8p. 1N4004, 8p

1N914, 6p. 7400N, 15p. 7401-7410-7430, 15p

2N708, 10p. 2N914, 30p. BQ908, 11p. BZY51, 20p

CWO. pp 10p. Discount 10-10%. The above items are only a few taken from our catalogue which is available free. Money back refund.

Dept. PW, 61 CHERDDINGTON RD., FITSTONE LEIGHTON BUZZARD, BEDS., LU7 9AQ.

Tel.: Cheddington 688448 (STD Code 0296)

**TAPE HEADS**  
We are gradually obtaining more information about the Truvox tape heads we have, and are told that these have been wound in a very ingenious way so that winding may be coupled either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and now offer these in pairs. 1 record and 1 erase head. Price of the 2 track 45p per pair. 4 track 75p per pair. Pair mounted on plate 45p extra.

**I.R.P.M. MOTOR**  
Made by the famous Smiths Company. 240v 50 cycle mains working. Ideal motor to drive clock mechanisms. Price £1 each or 10 for £9.

**DRILL CONTROLLER NEW IKW MODEL**  
Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available. £2.25 plus 13p post & p.

**MAINS OPERATED CONTACTOR**  
220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2in. £1.50 each.

**HIGH ACCURACY THERMOSTAT**  
Uses differential comparator I.C. with thermistor as probe. Designer claims temperature control to within 1/17th of a degree. Complete kit with power pack £2-50.

**AUTO-ELECTRIC CAR AERIAL**  
With dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.75 plus 25p post and insurance.

**WATERPROOF HEATING ELEMENT**  
26 yards length 70W. Self-regulating temperature control. 60p post free.

**MULTI-SPEED MOTOR**  
Replacement in many well-known food mixers. Six speeds are available 500, 850 and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixer normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. This drive shaft is 1/2 in. diameter and approximately 1 in. long. A further point about this motor is that being 230/240v. A.C.-DC series wound its speed may be further controlled with the use of our Thyristor controller. This is a very powerful and useful motor size approx. 2 in. dia. x 5 in. long, mains 230/240v. Price 85p plus 23p postage and insurance. 12 or more post free.

**ISA ELECTRICAL PROGRAMMER**  
Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have corn house in cone house on. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch on timer can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £1-95 + 20p p & p with glass front chrome bezel 75p extra.

**0.8 AMMETER**  
2in square full vision for flush mounting. Moving iron instrument. Ideal for charger. Price 60p each. 10 for £5.40.

**NUMICATOR TUBES**  
For digital instruments, counters, timers, clocks, etc. Hi-vac XN. 3. Price £1.45 each. 10 for £13.

**12 WAY SUB-MINIATURE MULTI-CORE CABLE**  
7-0076 copper cores each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 20p per yard.

**LIGHT CELL**  
Almost zero resistance in sunlight increases to 10 K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1in. dia. by 1/2in. thick. Rated at 500 MW, wire ended. 48p with circuit. Also ORP 12 light cell 45p.

**SNAP ACTION SLIDE SWITCH**  
Rated 5a. 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuums, etc. 5p each, 10 for 45p.

# RADIO CONTROL - BETA-DEMO DECK

To receive parts for these and other products featured in this issue send quoted approximate amount and cash adjustment will be made later.

## THYRISTOR LIGHT DIMMER

For any lamp up to 200 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price £2-95 plus 20p post and insurance.



**TANGENTIAL HEATER UNITS**  
This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprise motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £3-50. 2kW. Model as above except 2 kilowatts £2-50. Don't miss this. Control Switch 85p. P. & P. 40p.



## DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 8 feet of flex cable. Wired up ready to work. £2-25 plus 25p P. & I.

**THIS MONTH'S SNIP**  
A bargain parcel of 7 motors for £1. Some not as large as a postage stamp and only 1 1/2" thick, largest is 1 1/2" x 1 1/2" dia. Some work off 1 1/2" some as high as 18v. These motors are used in racing cars, power toys etc. The largest is so powerful that it will drive a Mini drill, model bike, or similar. This is a 4 pole motor, optimum working 16-5v but very powerful even as low as 4 1/2v. Don't miss this wonderful snip.

**TIMAC 24 hour amp Clock Switch.** Self-contained unit for 8x connection to the mains. Clock switches 2 on/off per 24 hours. Operates a 15 amp switch. All neatly made up in an ivory moulded case with outlet socket. The only snag is that the outlet socket is the continental type. Plugs for these can be brought in this country alternatively you could fit a connector strip in place of the outlet socket. Overall size of this unit is approx. 4" x 2 1/2" x 3" and the clock has a clear perspex cover which is easily removable for reprogramming. Ideal for blanket controller, etc. Price £2-75 each.

**STANDARD 1 1/2" WAFER SWITCHES**

Standard size 1 1/2" wafer—silver-plated 5-amp contact, standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
3 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
4 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
5 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
6 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
7 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
8 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
9 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
10 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
11 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p
12 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p

**MULLARD AUDIO AMPLIFIERS.** All in module form, each ready built complete with heat sinks and connection tags, data supplied.  
Model 1153 500m watt power output 75p.  
Model 1172 750m watt power output 85p.  
Model EP1000 4 watt power output £1.45p.  
10% discount if 10 or more ordered.

**13 AMP TWIN GANG SOCKETS**  
Offered at less than wholesale price your opportunity to replace those dangerous adaptors—brown bakelite flush mounting—standard fitting. Unswitched 20p each, separately switched 30p each. Separately switched and with neon on/off indicators 45p each. Less 10% ten or more +20p postage if order under £5.

**50 MICRO AMMETER** Square, panel mounting type. £2

**INTEGRATED CIRCUIT BARGAIN**  
A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade devices, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only £1 post paid.  
**DON'T MISS THIS TERRIFIC BARGAIN.**

**MULLARD I.F. MODULE**  
This is a fully screened intermediate frequency module for amplification and detection of i.m. signals at 10.7MHz and a.m. signals at 470kHz. The first stage is used as an i.f. amplifier for i.m. and a self-oscillating mixer for a.m. operation, in conjunction with an external oscillator coil. 85p each. 10 for £7-85. With connection dig.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Benelux countries add 6p post. Over £1 post free. S.A.E. with enquiries please.

**POCKET CIRCUIT TESTER**  
Test continuity of any low resistance circuit, house wiring, car electric. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied). 30p or 2 for 60p post paid.

**AMPLIFIER IN CASE WITH SPEAKER**  
Marketed by British Rely under the name Lovator. This is a very neat looking cabinet and is ideal around the home or in the workshop for trouble shooting or for testing out a quick lash up. Size approx. 9 1/2" x 6 1/2" x 3 1/2" deep. Input is via a matching transformer and volume control and amplifier may be powered by an internal 8v battery or an external 110v source. Speaker is an R-A elliptical 6 1/2" x 3 1/2" in diameter. The amplifier proper is a Newmarket model ref. P.C.4. Price £2-50 each, 10 for £21-50. Post and insurance 20p.

**BAKELITE INSTRUMENT CASE**  
Size approx. 6 1/2" x 3 1/2" x 2 1/2". Deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price 45p each.

**TELEPHONES**  
Complete as Illustrated. Save your leg, time and temper, simply by putting in some telephones. Ex. G.P.O. not new—but guaranteed in good condition and serviceable. Supplied with diagram and instructions showing how to connect. Price 75p each + 50p post or 2 for £2 post paid.  
Also available separately, dials and handsets 60p each + 20p post.

**ROCKER SWITCH**  
13 amp self-fixing into an oblong hole. Size approximately 1" x 1" 6p each. 10 for 64p.

**SLIDE SWITCHES**  
Slide Switch. 2-pole changeover panel mounting by two 6BA. screws. Size approx. 1in x 1in rated 250V lamp. 6p each. 10 for 64p, 100 for £5-10, 500 for £24. Ditto as above but for printed circuit 5p each 10 for 45p, 100 for £4-25. Sub Miniature Slide Switch. D.F.P.T. 19mm (1in approx.) with fixing centres 18p each or 10 for £1-08. 8P Change over spring return 250v 1 amp. 10p.

**EDUCATIONAL KITS—all with pictorial instructions**  
**THIS BALANCE KIT FREE**  
Fascinating educational kits. Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 40p each post paid. Special price for all 8 kits £3.00 with free balance kit.

**KA2 Lens Kit.** Eleven parts, including candle, one concave lens, one convex lens, stage and slit frame, etc. Watch light rays bend as they pass through different lenses.

**KA3 Water Pump Kit.** Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working. Three types of pump may be made: Lift Pump, Force Pump and Force Pump with reservoir and nozzle.

**KA4 Buzzer Kit.** Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer.

**KA5 2-Pole Motor Kit.** Twenty-four parts including enamel wire, armature and pole pieces, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor.

**KA7 Electro-Magnet Kit.** Fifteen parts. Includes compass. Makes two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.

**KA8 Current and Resistance Kit.** Twenty-nine parts, including bench and light bulb. Conduct interesting and educational projects to learn the application of "OHM'S LAW" and see the difference in current and resistance with different types and lengths of wire.

**KA9 Bell Kit.** Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.

**KA10 Morse Key buzzer and bell kit.** 25 part kit easy to construct, simple to operate.

**J. BULL (ELECTRICAL) LTD.**  
(Dept. E.E.), 7 Park Street, Croydon CRO 1YD  
Callers to: 102/3 Tamworth Road, Croydon.

# Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

## ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated Telescopic Aerial, for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 80p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost

**£8-50**

P. P. & Ins. 50p

(Overseas P. & P. £1)

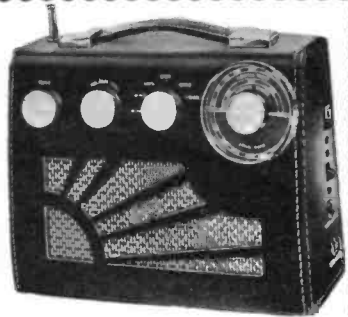

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


Total building cost **£6-98** P. P. & Ins. 45p. (Overseas P. & P. £1)


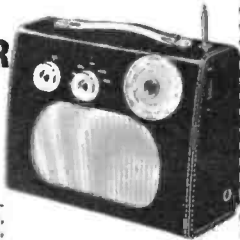
## ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


Total building costs **£5-98** P. P. & Ins. 45p. (Overseas P. & P. £1)


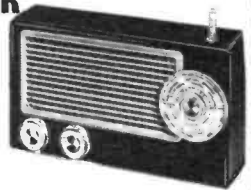
## ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3, Trawler, band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Easy build plans and parts price list 15p (FREE with parts).

Total building costs **£3-98** P. P. & Ins. 30p. (Overseas P. & P. £1)



## POCKET FIVE

8 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5½ x 1½ x 3½in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-29** P. P. & Ins. 25p. (Overseas P. & P. 65p)



## TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-50** P. P. & Ins. 24p. (Overseas P. & P. 65p)




## TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

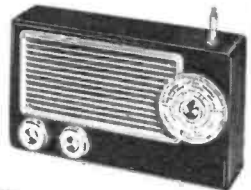Total building costs **£4-48** P. P. & Ins. 32p. (Overseas P. & P. £1)



## NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY TO FOLLOW FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 3 Inch Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 2 Diodes: Resistors: Capacitors: Three ½" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction

All parts including **£5-50** P. P. & Ins. 32p. (Overseas P. & P. £1)

FULL AFTER SALES SERVICE

• Callers side entrance "Lavelle" Shop  
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61a HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

(Dept. E.E.14.)

# U.K.'s LARGEST ELECTRONICS CENTRES!

## HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



**NOW OPEN!**

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381  
 354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736  
 309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963  
 303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1BW

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

## BUILD THE TEXAN

**20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER**

★ **FREE TEAK CABINET** with complete kit!

**FEATURES.** New slim design with 6 - IC's, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. special 'Gardeners' low field slim line transformer. Fibre glass PC panel. Complete chassis work.  
**HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.  
**FACILITIES.** On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).  
 Constructional details Ref. No. 21 30p



(As featured in "Practical Wireless" May to August 1972)

**SPECIAL KIT PRICE**

**£28-50** P & P 45p

★ **SLIM DESIGN WITH SILVER TRIM**

Overall chassis size 14½" x 6" x 2" high

**COMPLETE WITH FREE TEAK CABINET**

Designer approved kits distributed by Henry's!

### RECORD DECKS

- CHASSIS (POST 50p)
- SP25/3E10-25 HT70 £14-50
- MP60 £9-95 MP610 £12-95
- AP76 £17-95 GL75 £28-50
- PLINTH/COVERS (State Model)
- SP25/MP60/610 £3-30 post 40p
- AP76 £4-50 post 40p
- CART/PLINTH/COVER (Post 70p)
- (HL) MP60/G800H/PC £18-50
- MP610/SC5MD/TPD2/PC £15-95
- AP76/M7565M/PC £32-50
- AP76/M7565M/PC £39-95
- (HL) AP76/G800/PC £28-95
- (HL) SP25/G800H/PC £18-95
- HT70/G800/TPD1/PC £24-50
- (HL) 2025/9TAHCD/PC £13-95
- MP60/SC5MD/PC £17-25
- (HL) GL75/G800/PC £41-95
- (HL) GL75/G800/PC £38-95

### ULTRASONIC TRANSDUCERS

Operate at 40Kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.  
 £3-90 per pair. Post 10p

### MARRIOTT TAPE HEADS

- 4 TRACK MONO or 2 TRACK STEREO
- '17' High Impedance £2-00
- '18' Med. Impedance £2-00
- '36' Med.-Low Imp. £3-50
- Erase Heads for above 75p
- '63' 2 track mono—Hi Imp. £1-75
- '43' Erase Head for above 75p

### POWER INTEGRATED CIRCUITS

- Plassey 3L403D—3 watt with 8-pole data layouts and circuits £1-50. P.C. Board 60p. Heat Sink 14p.
- Sinclair IC12—6 watt with data and circuits £1-80.
- TH9013P—20 watt Power Amp Module £4-57.
- TH9014P-IC Preamp £1-50. Data/Circuits for above No. 42 10p

### 7 SEG & NIXIE TUBES

- (Post 15p per 1 to 6)
- XN3, XN13, GN6 0-9 side view with data, 85p.
- GNP-7, GNP-8 0-9 side view with decimal points and data, 95p
- 3015F 7 seg £2 each. £7 per 4 with data.
- 12 and 24 hour clock circuits Ref. No. 31 15p.

### Miniature Amplifier

5 transistor. 300mW o/p. Fitted volume and sensitivity control, 9 volt operated. £1-75 each P/P 15p.

### Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K, 1 meg, Log and Lin. 45p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged. 75p each.

### Hi-Fi & Tape Equipment

Acknowledged as U.K.'s Largest Stockists with Lowest Prices Plus 12 months Guarantee. Write or call for FREE 16 page lists (Ref. N. 17)

Transistors - IC's - SCR'S - Rectifiers - Triacs, etc. LATEST BROCHURE Ref. No. 36 on request, or see our earlier page.

### LOW COST HI-FI SPEAKERS



- E.M.I. Size 13½" x 8½". Large Ceramic Magnet.
- TYPE 150 6 watt, 3, 8 or 15 ohms £2-20. Post 22p.
- TYPE 150 TC Twin cone version £2-75. Post 22p.
- TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3-85. Post 25p.
- TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7-70. Post 28p.



**POLISHED CABINETS** 150, 150TC 450 £4-60. Post 30p. ASSEMBLED IN POLISHED CABINETS (8 ohms) SERIES 6 (Assembled 150 TC) per pair £16-50. Post 70p. SERIES 8 (Assembled 450) per pair £18-95. Post 70p

### ML-3 MW/LW TUNER to BUILD



Uses Mullard Module. Slow motion tuning. Built in battery Ferrite core. Overall size 7" x 2½" x 3½". TOTAL COST TO BUILD £4-85. Post 15p. All parts sold separately. Leaflet No. 6

### "BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard R/F/H Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.  
 TOTAL COST TO BUILD £7-98. p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

### TEST EQUIPMENT

- SE250B Pocket Pencil Signal Injector £1-90
  - SE500 Pocket Pencil Signal Tracer £1-50
  - THL33D Robust 2K/Volt £4-55 with case £4-95
  - TE15 Grid Dip Meter 440 KHz-280 mHz £13-45
  - 500 30 K/V Multimeter £9-25
  - 200H 20K/V Multimeter £4-20. With case £4-95
  - AF105 50K/V Multimeter £8-50. With case £9-50
  - U4341 AC/DC Multimeter with transistor tester with steel case £10-50
  - TE20D RF Generator 120KHz-500MHz £15-95. Carr. 35p
  - TE22D Audio Generator 20Hz-200KHz £17-50. Carr. 35p
  - CI-5 3" Pulse Scope 10Hz-10mHz £39-00. Carr. 50p
  - TE65 Valve Voltmeter 28 ranges £17-50. Carr. 40p
- ALL NOMBREX MODELS IN STOCK




### PA-Disco-Lighting

- UK's Largest Range—Write phone or call in. Details and demonstrations on request.
- DJ30L 3 Channel sound to light unit, 3KW. £29-75
- DJ40L 3 channel Mic (built-in) to light, 3kW £38-75
- DJ705 70 watt Disco amp/mixer, £49-95
- DISCOAMP 100 watt amp/mixer, £66-50
- D1055 30 watt Disco amp/mixer, £32-75
- Anti-Feedback Quality Mic., £11-50
- DJ500 50 watt PA Amplifier GROUP 300 150 watt rms Group Valve Amplifier £86-00
- FIBRE OPTICS LIGHTING, — MICS, EFFECTS, PROJECTORS, SPOTS, DIMMERS — STANDS, MIXERS, SPEAKERS, Everything for PA — Disco — Lighting.
- FREE Stock List Ref. No. 18
- PORTABLE DISCOS — DETAILS ON REQUEST
- CREDIT TERMS FOR CALLERS


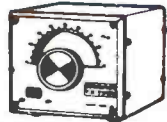
### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO  
 A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6-97, p.p. 20p. Decoder Kit £5-97. Tuning meter unit £1-75  
 Mains unit (optional) Model PS900 £2-47. Post 20p  
 Mains unit for Tuner and Decoder PS6/12 £3-25. Post 20p




### SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!

- Z30 £3-57; Z50 £4-37
- STEREO 60 PZ5 £3-97
- £7-97; PZ8 £4-77
- PZ6 £6-37;



Transformer for PZ8 £2-95  
 Active Filter Unit £4-45  
 Stereo FM Tuner £16-95  
 IC12 £1-80; Q16's £15 pr.  
 Post etc. 20p per item

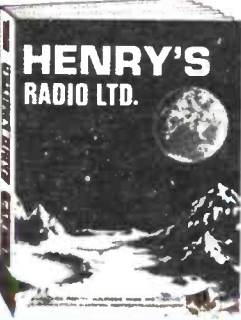**PACKAGE DEALS** Post 25p  
 2xZ30, Stereo 60, PZ5 £15-95  
 2xZ30, Stereo 60, PZ6 £18-00  
 2xZ50, Stereo 60, PZ8 £20-25  
 Transformer for PZ8 £2-95  
 PROJECT 60S KIT £19-95



### CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics— plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid (40p FOR CALLERS)  
**PLUS! FIVE 10p VOUCHERS**

Send to this address— HENRY'S RADIO LTD. (Dept. E.E.) 3 ALBEMARLE WAY, LONDON, E.C.1.— for catalogue by post only. All other mail and callers to "303" see above.

**MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S**  
 All the parts you need plus Data and Circuits — Get a Catalogue — it's all in there!  
 Prices subject to change without notice E. & O.E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

**H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H**