

# EVERYDAY ELECTRONICS and computer PROJECTS

MAY 1984

90p



**EXPERIMENTERS PSU  
VARICAP AM RADIO  
SIMPLE LOOP/BURGLAR ALARM**


Australia \$1.60 New Zealand \$1.75 Malaysia \$4.95

electronize

# AUTO-ELECTRONIC PRODUCTS

KITS OR READY BUILT
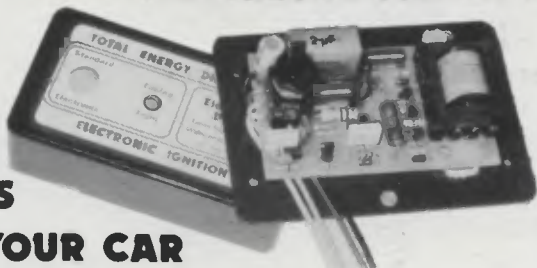
## TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION




IS  
YOUR CAR

### AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and the damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output and maintains it from service to service.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where the ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
- ★ Is the **PERFORMANCE SMOOTH**. The more powerful spark of Total Energy Discharge eliminates the "near misfires" whilst an electronic filter smooths out the effects of contact bounce etc.
- ★ Do the **PLUGS and POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition doesn't affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
- ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3 1/2 times the power of inductive systems - 3 1/2 times the energy and 3 times the duration of ordinary capacitive systems. These are the facts:  
 Performance at only 6 volts (max. supply 16 volts)  
 SPARK POWER — 140W, SPARK ENERGY — 30mJ  
 SPARK DURATION — 500µS, STORED ENERGY — 135mJ  
 LOADED OUTPUT VOLTAGE  
 50pF load — 38kV, 50pF + 500k — 26kV  
 We challenge any manufacturer to publish better performance figures. Before you buy any other make, ask for the facts, its probably only an inductive system. But if an inductive system is what you really want, we'll still give you a good deal.
- ★ **ALL ELECTRONIZE** electronic ignitions feature:  
**EASY FITTING, STANDARD/ELECTRONIC CHANGEOVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee).**
- ★ **IN KIT FORM** it provides a top performance system at less than half the price of comparable ready built units. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2uF discharge capacitor, case, easy to follow instructions, solder and everything needed to build and fit to your car. All you need is a soldering iron and a few basic tools.

Most **NEW CARS** already have electronic ignition. Update **YOUR CAR**

## ELECTRONIZE ELECTRONIC CAR ALARM

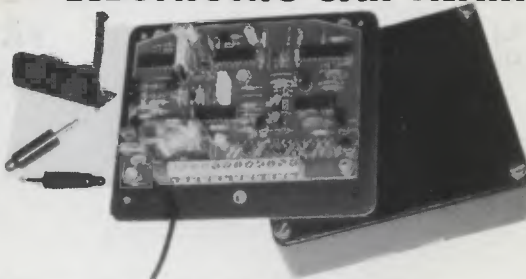

### HOW SAFE IS YOUR CAR ?

More and more cars are stolen each week and even a steering lock seems little help. But a car thief will avoid a car that will cause him trouble and attract attention. If your car has a good alarm system - well there are plenty of other cars to choose from.

#### LOOK AT THE PROTECTION AN ELECTRONIZE ALARM CAN GIVE :

- ★ **MINIATURE KEY PLUG** A miniature jack plug attaches to your key ring and is coded to your particular alarm.
- ★ **2025 INDIVIDUAL COMBINATIONS** The key plug contains two 1% tolerance resistors, both must be the correct value and together give 2025 different combinations.
- ★ **ATTRACTS MAXIMUM ATTENTION** This alarm system not only intermittently sounds the horn, but also flashes the headlight and prevents the engine being started.
- ★ **60 SECOND ALARM PERIOD** Once triggered the alarm will sound for 60 seconds, unless cancelled by the key plug, before resetting ready to be triggered again.
- ★ **30 SECOND EXIT DELAY** The system is armed by pressing a small button on a dashboard mounted control panel. This starts a 30 second delay period during which the owner can open and close doors without triggering the alarm.
- ★ **10 SECOND ENTRY DELAY** When a door is opened a 10 second delay operates to allow the owner to disarm the system with the coded key plug. Latching circuits are used and once triggered the alarm can only be cancelled by the key plug.
- ★ **L.E.D. FUNCTION INDICATOR** An LED is included in the dashboard unit and indicates the systems operating state. The LED lights continuously to show the system is armed and in the exit delay condition. A flashing LED indicates that the alarm has been triggered and is in the entry delay condition.
- ★ **ACCESSORY LOOP - BONNET/BOOT SWITCH - IGNITION TRIGGER** These operate three separate circuits and will trigger the alarm immediately, regardless of entry and exit delays.
- ★ **SAFETY INTERLOCK** The system cannot be armed by accident when the engine is running and the car is in motion.
- ★ **LOW SUPPLY CURRENT** CMOS IC's and low power operational amplifiers achieve a normal operating current of only 2.5 mA.
- ★ **IN KIT FORM** It provides a high level of protection at a really low cost. The kit includes everything needed, the case, fibreglass PCB, random selection resistors to set the code and full set of components etc. In fact everything down to the last washer plus easy to follow instructions.

fill in the coupon and send to:

**ELECTRONIZE DESIGN** Dept C · Magnus Rd · Wilnecote · Tamworth · B77 5BY · tel 0827 281000

Please Supply:

Send More Information

**TOTAL ENERGY DISCHARGE** (6 or 12 volt negative earth)

D.I.Y. parts kit **£15.90** £14.95

Assembled ready to fit **£26.70** £19.95

(positive earth unit) **£22.95**

**TWIN OUTPUT** for cars and motor cycles with dual ignition

Twin, D.I.Y. parts kit **£24.55** £22.95

Twin, Assembled ready to fit **£36.45** £29.95

**CAR ALARM** (12 volt negative earth)

D.I.Y. parts kit **£24.95** £19.95

Assembled ready to fit **£37.95** £29.95

**SPECIAL OFFER.** Buy one electronic ignition kit plus one alarm kit for £30.85 or assembled units for £44.65. Goods must be purchased at the same time.

I enclose cheque/postal order OR debit my Access/Visa card

VISA

Name \_\_\_\_\_

Address \_\_\_\_\_




Code \_\_\_\_\_

Please Add £1.00 P&P(UK) Per Unit Prices Include VAT
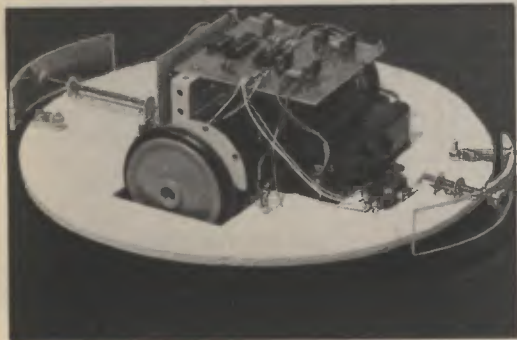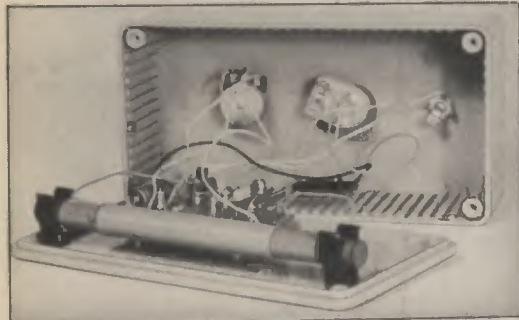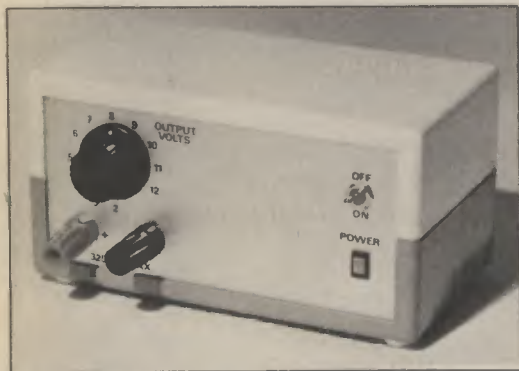
# EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 13 NO. 5 MAY 1984

PROJECTS . . . THEORY . . . NEWS . . .  
COMMENT . . . POPULAR FEATURES . . .



© IPC Magazines Limited 1984. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our June 1984 issue will be published on Friday, May 18. See page 323 for details.

## PROJECTS

### EXPERIMENTER'S POWER SUPPLY

by S. Niewiadomski

298

Switched outputs from 2V to 12V in 1V steps

### VARI-CAP A.M. RADIO

by R. A. Penfold

302

Personal m.w. receiver

### COMPUTER-CONTROLLED BUGGY

by J. Adams and G. M. Feather

317

### EXTRA 1K RAM for the ACORN ATOM

by A. J. Presnail

326

Simple expansion project

### EXTRA UTILITY PROM for the ACORN ATOM

by A. J. Presnail

327

For extra power at switch-on

### MASTERMIND TIMER

by L. A. Privett

330

Black Box Project—Recreates the "black chair" atmosphere

### SIMPLE LOOP BURGLAR ALARM

by C. Lare

338

Battery powered loop protection system

## SERIES

### TEACH-IN 84

by George Hylton Part 8: Power in General

306

### MICROCOMPUTER INTERFACING TECHNIQUES

by J. Adams and G. M. Feather

314

Part 11: Computer control of small vehicles

### WHY NARROW BAND F.M.? by E. A. Rule

334

Modulation systems compared

## FEATURES

### EDITORIAL

Robotics; Shortage

297

### FOR YOUR ENTERTAINMENT

by Barry Fox

312

Holographic Call; Sociable Mic; War Games

### SHOPTALK

by Dave Barrington

313

Product news and component buying

### EVERYDAY NEWS

324

What's happening in the world of electronics

### RADIO WORLD

by Pat Hawker G3VA

329

Finding Directions; Voice from Space; Chatter Box; Shoot Out

### READERS' LETTERS

332

Your news and views

### BOOK REVIEWS

337

A selection of recent releases

### NEW PRODUCTS

342

Facts and photos of instruments, equipments and tools

### PRINTED CIRCUIT BOARD SERVICE

343

SQUARE ONE Beginners' Page: Logic Symbols

344

### CIRCUIT EXCHANGE

345

A forum for readers' ideas

### COUNTER INTELLIGENCE

by Paul Young

346

A retailer comments

Readers' Services • Editorial and Advertisement Departments

297

# MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY  
THIS IS THE AGE — OF ELECTRONICS!  
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.


Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.

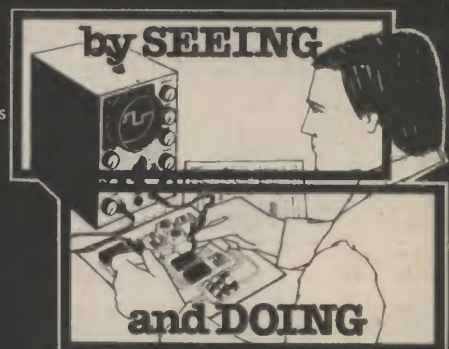

CACC

**British National Radio & Electronics School** Reading, Berks. RG1 1BR

**FREE!**  
COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

BLOCK CAPS PLEASE  
EE/5/841

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

OR TELEPHONE US  
0734 51515 OR  
TELEX 22758  
(24 HR SERVICE)




**British National Radio & Electronics School** Reading, Berks. RG1 1BR


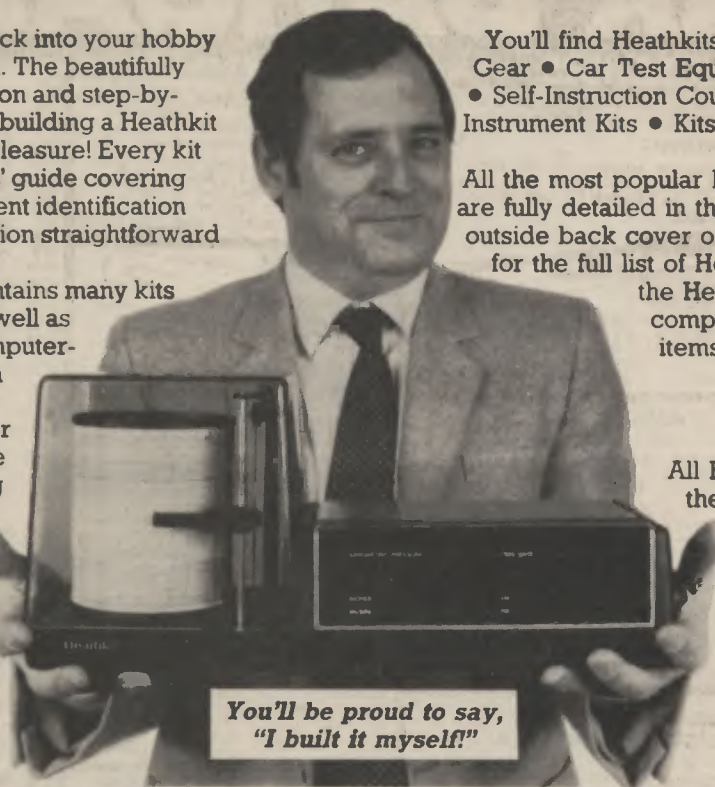
# Heathkit - IT'S A PLEASURE TO BUILD

Bring the enjoyment back into your hobby with a kit from Heathkit. The beautifully illustrated documentation and step-by-step instructions make building a Heathkit a relaxing, absorbing pleasure! Every kit includes a constructors' guide covering soldering and component identification which makes construction straightforward even for a beginner.

The Heathkit range contains many kits ideal for beginners as well as amateur radio kits, computerised weather stations, a highly sophisticated robot, a 16-bit computer kit and a range of home (or classroom) learning courses that have easy-to-understand texts and illustrations, in sections so that you can progress at your own pace, whilst the hands-on experiments ensure long-term retention of the material covered.



You'll be proud to say, "I built it myself!"

You'll find Heathkits available for Amateur Radio Gear • Car Test Equipment • Kits For The Home • Self-Instruction Courses • Computer Kits • Test Instrument Kits • Kits For Weather Measurements.

All the most popular kits and educational products are fully detailed in the 1984 Maplin catalogue (see outside back cover of this magazine for details) or for the full list of Heathkit products send 50p for the Heathkit International Catalogue complete with a UK price list of all items.

All Heathkit products available in the UK from:

**Maplin Electronic Supplies Ltd.**  
P.O. Box 3, Rayleigh,  
Essex, SS6 8LR.  
Tel: (0702) 552911.

(For shop addresses see back cover.)

## BSR P256 TURNTABLE


P256 turntable chassis • S shaped tone arm • Belt driven • Aluminium platter • Precision calibrated counter balance • Anti-skate (bias) device • Damped cueing lever • 240 volt AC operation (Hz) • Cut-out template supplied • Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.  
Price £32.35 each. £2.50 P&P.


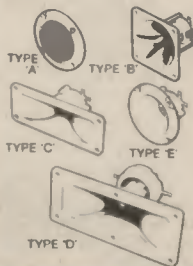
## PIEZO ELECTRIC TWEETERS — MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.


LARGE S.A.E. For details of disco mixers, speakers, kits, amp - modules, buglaf alarms, turntables, etc.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.29 each + 30p P&P.  
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.99 each + 30p P&P.  
TYPE 'C' (KSN8016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.99 each + 30p P&P.  
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £7.99 each + 30p P&P.  
TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.99 each + 30p P&P.

## OMP POWER AMPLIFIER MODULE

READY BUILT

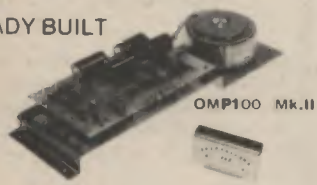

New model.  
Improved specification

NEW OMP100 Mk. II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New Improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications.

**SPECIFICATION**  
Output Power:— 110 watts R.M.S.  
Loads:— Open and short circuit proof 4/16 ohms.  
Frequency Response:— 15Hz - 30KHz - 3dB  
T.H.D.:— 0.01%  
S.N.R. (Unweighted):— 118dB ± 3.5dB.  
Sensitivity for Max Output:— 500mV at 10K.  
Size— 360 x 115 x 72mm Price:— £31.99 + £2.50 P&P. Vu Meter Price:— £8.50 + 50p P&P.

MOS-FET HIGH SPEC. MODULES

MOS-FET VERSIONS AVAILABLE UP TO 300 W. R.M.S.  
100 Watt 300mm x 123mm x 60mm Price: £39.99 + £2.50 P&P  
200 Watt 300mm x 150mm x 100mm Price: £62.99 + £3.50 P&P  
300 Watt 330mm x 147mm x 102mm Price: £79.99 + £4.50 P&P

## PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £7.99 + 75p P&P.

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled, professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £12.49p + 75p P&P.

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £16.49. Transmitter 80 x 50 x 15mm (9/12 volt). Price: £10.29 P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

## LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See 'Photo) Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. Specifications and Prices.

15" 100 watt R.M.S. Impedance 8 ohms 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 20 Hz. Freq. Resp. to 25KHz. Sens. 97dB. Price: £34.00 each + £3.00 P&P.  
12" 100 watt R.M.S. Impedance 8 ohms 50 oz. magnet. 2" aluminium voice coil. Res. Freq. 25Hz. Freq. Resp. to 4 KHz. Sens. 95dB. Price: £24.50 each + £3.00 P&P.  
8" 50 watt R.M.S. Impedance 8 ohms 20 oz. magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz. Freq. Resp. to 6 KHz. Sens. 92dB Black Cone. Price: £9.50 each. Also available with black protective grille. Price: £10.50 each. P&P £1.50.



12" 85 watts R.M.S. McKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB Price £24.99 + £3 carriage.  
12" 85 watt R.M.S. McKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone. 8 ohm imp. Res. Freq. 45Hz. Freq. Resp. to 14KHz. Price £24.99 + £3 carriage.  
15" 150 watt R.M.S. McKENZIE C1518ASS GUITAR, P.A.] 3" aluminium voice coil. Die cast chassis. 8 ohm imp. Res. Freq. 40Hz. Freq. Resp. to 4KHz. Price £49 + £4 carriage. Cabinets fixings in stock S.A.E.

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★

**B. K. ELECTRONICS**

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
ESSEX SS2 6TR TEL 0702-527572



# BI-PAK BARGAINS

## MINIATURE TOOLS FOR HOBBYISTS

Miniature round nose side cutters - insulated handles 4 1/2 inch length. Order No: Y043.

Miniature long nose pliers - insulated handles 5 1/2 inch length. Order No: Y044.

Miniature bend nose pliers - insulated handles 5 1/2 inch length. Order No: Y045.

Miniature end nippers - insulated handles 4 1/2 inch length. Order No: Y046.

Miniature snipe nose pliers with side cutter and serrated jaws - insulated handles 5 1/2 inch length. Order No: Y042.

### FLEXI DRIVER


A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch. Order No: FS-1 Rat blade 4mm FS-2 Cross point no. 1 £1.75 each.

### GRIP DRIVER

8 1/2 inch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No: SD-1 Flat blade 4mm SD-2 Cross point no.0. £95p each.

ALL AT £1.25 each

## 13 PIECE TOOL KIT AND CASE

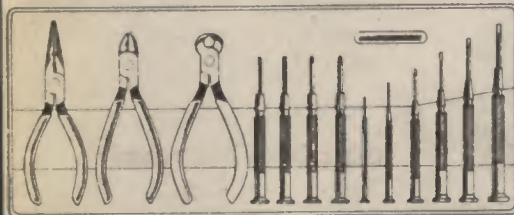

13-piece tool set housed in attractive moulded plastic case with clear sliding cover. Includes:  
 • 1 off 5" snipe nose "radio" pliers with side cutters  
 • 1 off 4 1/2" side cutters  
 • 1 off 4 1/2" end cutters  
 • 2 off hex. "Allen" key drivers 2mm and 2.5mm  
 • 2 off cross-point "Phillips" drivers No. 0 and No. 1 (with tommy bar)  
 • 6 off precision screwdrivers. Sizes from 1mm to 3.5mm.

ONLY £7.50 ORDER No. VP102

## PRECISION JEWELLERS' TOOLS

Rustproof Tempered Handles and Blades. Chrome Plated Handles. Swivel Heads for use on Precision Work.

### 5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2.4, 2.9 and 3.8mm £1.75

### 5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm £1.75

### 5T41 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers - H0 and H1 Hex key wrenches. Sizes - 1.5, 2 and 2.5mm £1.75

### 5T51 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm £1.75

## MULTITESTER


1,000 opv including test leads & Battery  
 AC volts - 0-15-150-500-1,000  
 DC volts - 0-15-150-500-1,000  
 DC currents - 0-1ma-150ma  
 Resistance - 0-25 K ohms 100 K ohms  
 Dims - 90 x 61 x 30mm.  
 O/No. 1322 OUR PRICE £6.50 ONLY

## BRAND NEW LCD DISPLAY MULTITESTER

RE 188m  
 LCD 10 MEGOHM INPUT IMPEDANCE  
 \*3 1/2 digit \*16 ranges plus hFE test facility for PNP and NPN transistors \*Auto zero, auto polarity \*Single-handed, pushbutton operation \*Over range indication \*12.5mm (1/2 inch) large LCD readout \*Diode check \*Fast circuit protection \*Test leads, battery and instructions included.

Max indication 1999 or -1999  
 Polarity indication Negative only  
 Positive readings appear without + sign  
 Input Impedance 10 Megohms  
 Zero adjust Automatic  
 Sampling time 250 milliseconds  
 Temperature range -5°C to 50°C  
 Power Supply 1 x PP3 or equivalent 9V battery  
 Consumption 20mW  
 Size 155x88x31mm

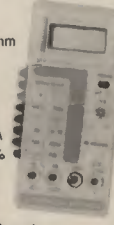RANGES  
 DC Voltage 0-200mV  
 0-2-20-200-1000V. Acc. 0.8%  
 AC Voltage 0-200-1000V  
 Acc. 1.2% DC Current 0-200uA  
 0-2-20-200mA, 0-10A. Acc. 1.2%  
 Resistance 0-2-20-200K ohms  
 0-2 Megohms. Acc. 1%  
 BI-PAK VERY LOWEST PRICE  
**£45.00** each  
 Leather Case for 188m £2.50 EACH



## SIGNAL INJECTOR

Simple push button operation. Oscillates at 700 - 1k Hz with harmonics to 30MHz. 14V p/p output. Impedance 10kΩ. Ideal for trouble shooting with audio equipment. One "AA" penlight battery supplied. O/No VP96 £2.50

## LOGIC PROBE

Automatic levelling. White LED indication. Minimum width of measuring pulse 30 nsecs. Maximum input frequency 10M Hz. Input impedance: 100kΩ  
 40mA maximum  
 4.5 - 18 V d.c.  
 Power consumption:  
 Power supply: ORDER No. VP97 £10.50

## CURRENT/POL CHECKER

Heavy duty test prods with built-in indicators for testing polarity; indicates whether a.c. or d.c. 3.5V to 400V. O/No. VP98 £2.50

## TESTER

Universal tester with ceramic buzzer. Tests diodes, transistors, resistors, capacitors and continuity. One "AA" penlight battery included.  
 Test current: Max 2µA  
 Test voltage: 12V  
 Response range: 100MΩ  
 500V  
 Internal resistance: 390kΩ  
 Length: 135mm  
 £5.00  
 O/No. VP99

## CIRCUIT TESTER

D.C. continuity tester for circuit checking on all low voltage equipment and components. Diode checking also possible. Takes two AA batteries. 90cm lead has crocodile clip. Body length 145mm. O/No. VP100 75p

## ELECTRONIC SIREN 12v DC

Red plastic case with adjustable fixing bracket. Emits high-pitched wailing note of varying pitch - 100 cycles per minute. Dims - 90mm (dia.) 60mm (depth). Power - 12v DC. 0/P 90dBA 1m type.  
 Our Price: £5.50 O/No. VP79

## MINIATURE FM TRANSMITTER

Freq: 95-106MHz. Range: 1/2 mile O/No. VP128  
 Size: 45 x 20mm. AAd: 9v batt. ONLY  
 Not licenced in U.K.  
 Ideal for: 007-MIS-FBI-CIA-KGB etc. £5.50

## POWER SUPPLY OUR PRICE £4.25

Power supply fits directly into 13 amp socket Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug. Input - 240V AC 50HZ. Output - 3, 4, 5, 6, 7.5, 9 & 12V DC Rating - 300 ma VP109.

## RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size. 2 cross point size 4 & 6. 1 Ratchet handle. 5-in-1 Kit. £1.45 each. O/No 329B

## VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1
VP2	300	Carbon Resistors 1/4 Watt Pre-Formed	£1
VP3	200		£1
VP4	150	1/4 Watt Resistors 100 ohm-1M Mixed	£1
VP5	200	Assorted Capacitors All Types	£1
VP6	200	Ceramic Caps Miniature - Mixed	£1
VP7	100	Mixed Ceramic Disc. 1pf - 56pf	£1
VP8	100	Mixed Ceramic Disc. 68pf - 015pf	£1
VP9	100	Assorted Polyester/Polystyrene Caps	£1
VP10	60	C280 Type Caps Metal Foil Mixed	£1
VP11	100	Electrolytics - All Sorts	£1
VP12	60	Bead Type Polystyrene Min Caps	£1
VP13	50	Silver Mica Caps Ass. 56pf - 150pf	£1
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1
VP15	50	High Voltage Disc. Ceramic 750v - 8kv Mixed	£1
VP16	50	Wirewound Res. 9W (avg) Ass. 1 ohm - 12K	£1
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1
VP20	6	Rockers Switches 5 Amp 240v	£1
VP21	20	Pcs. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1
VP22	200	Sq. Inches Total. Copper Clad Board Mixed Sizes	£1
VP23	20	Assorted Slider Pots. Mixed Values	£1
VP24	10	Slider Pots. 40 mm 22K 5 x Log. 5 x Lin	£1
VP25	10	Slider Pots. 40 mm 47K 5 x Log. 5 x Lin	£1
VP26	20	Small 125° Red LED'S	£1
VP27	20	Large 2° Red LED'S	£1
VP28	10	Rectangular 2° Green LED'S	£1
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vts. Coded	£1
VP30	10	Ass. 10W Zener Diodes Mixed Vts. Coded	£1
VP31	10	5 Amp SCR'S TO-66 50-400v Coded	£1
VP32	20	3 Amp SCR'S TO-66 Up To 400v Uncoded	£1
VP33	200	Sil. Diodes Switching Like IN4148 DO-35	£1
VP34	200	Sil. Diodes Gen. Purpose Like OA200/BA1X13/16	£1
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1
VP36	8	Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vts. Coded	£1
VP37	8	Black Instrument Type Knobs With Pointer 1/2 Std	£1
VP42	10	Black Heatsinks To Fit TO-3, TO-220 Ready Drilled	£1
VP45	50	BC107/8 Type NPN Transistors Good Gen. Purpose Uncoded	£1
VP46	50	BC177/8 Type PNP Transistors Good Gen. Purpose Uncoded	£1
VP47	10	Silicon Power Trans. Similar 2N3055 Uncoded	£1.50

## TRANSISTOR CLEARANCE

All Sorts Transistors A mixed Bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes Instructions for Making Simple Transistor Tester. Super Value. Order No. VP80 100 for £1

## REGULATED VARIABLE MODULE Stabilised POWER SUPPLY + KIT

Variable from 2-30 volts and 0-2 Amps. Kits includes -  
 1 - VPS30 Module. 1 - 25 volt 2 amp transformer.  
 1 - 0-50v 2" Panel Meter. 1 - 0-2 amp 2" Panel Meter.  
 1 - 470 ohm potentiometer. 1 - 4K7 ohm potentiometer. Wiring Diagram.  
 included Order No. VPS30 KIT £20

## OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&p to:


## TECASBOTY THE ELECTRONIC COMPONENTS AND SEMICONDUCTOR BARGAIN OF THE YEAR!

This collection of Components & Semiconductors for the hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc. PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for ONLY at BI-PAK. Remember, stocks are limited so hurry! You can call us on 0920-3182/3412 and order with your Barclaycard or Access Card - 24hr Answerphone Service NOV. Order No. V.P. 85. just £6.50

# BI-PAK

Send your orders to Dept EE5 BI-PAK PO BOX 6 WARE, HERTS SHOP AT 3 BALDOCK ST WARE, HERTS. TERMS CASH WITH ORDER. SAME DAY DESPATCH. ACCESS. BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRD 388 7006. ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING

Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your Total order. Postage add 75p per Total order



# IS SOFTWARE YOUR BASIC PROBLEM?

Are you bewildered by the choice of Software Programs on the market?  
Not sure what Program you really need, what it does or where to get it?

**SOFTWARE INDEX**  
Is your answer

The most comprehensive magazine listing of Software programs for the eight leading Microcomputers.

● BBC ● COMMODORE 64 ● DRAGON ● VIC 20  
● ORIC ● ATARI 400/800 ● SPECTRUM ● ZX81

Software Index takes the headache out of choosing the programs suited to your Micro.

For people involved in electronics and specialist programs, Software Index will provide the information you need and be a valuable time-saving guide.

Games, education, business and personal management are also covered.

DON'T LET SOFTWARE GIVE YOU  
A HARD TIME, GET THE USER  
GUIDE TO MICROCOMPUTER  
SOFTWARE—

OVER  
**2,500**  
PROGRAMS  
LISTED

IN YOUR  
NEWSAGENT'S  
NOW

User Guide to Microcomputer Software  
**SOFTWARE  
INDEX**  
1984 No.2 £1.50



**XK113 MW RADIO KIT**

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. IDEAL FOR BEGINNERS. **£5.50**

**HOME LIGHTING KITS**

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting

- TDR300K Remote Control Dimmer **£14.95**
- MKB Transmitter for above **£4.50**
- TD300K Touchdimmer **£7.75**
- TS300K Touchswitch **£7.75**
- TDE/K Extension kit for 2-way switching for TD300K **£2.50**
- LD300K Rotary Controlled Dimmer **£3.95**



**DVM/ULTRA SENSITIVE THERMOMETER KIT**


This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week

Price **£15.50**

**NOW OPEN**

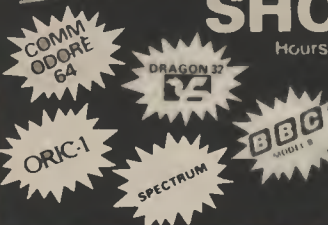**COMPUTER SHOWROOM**

Hours: Mon - Fri 9am - 5pm  
SAT 10am - 4pm



We also stock peripherals and accessories: disc drives, printers, joy sticks etc. together with a wide range of books and the latest software for all the above computers including ZX81

SEND S.A.E. FOR LIST TODAY!

**COMPONENT PACKS**

- PACK 1 650 Resistors 47 ohm to 10 Mohm - 10 per value **£4.00**
- PACK 2 40 x 18V Electrolytic Capacitors 10µF to 1000µF - 5 per value **£3.25**
- PACK 3 60 Polyester Capacitors 0.01 to 1µF/250V - 5 per value **£5.55**
- PACK 4 45 Sub-miniature Presets 100 ohm to 1 Mohm - 5 per value **£2.90**
- PACK 5 30 Low Profile IC Sockets 8, 14 and 16 pin - 10 of each **£2.40**
- PACK 6 25 Red LEDs (5mm dia) **£1.50**

Have you got our

**FREE YELLOW CATALOGUE yet?**

NO! Send S.A.E. 6" x 9" TODAY!! It's packed with details of all our KITS plus large range of SEMICONDUCTORS including CMOS LS TTL linear microprocessors and memories, full range of LEDs, capacitors resistors, hardware, relays, switches etc. We also stock VERO and Antex products as well as books from Texas Instruments Barban and Ektor


ALL AT VERY COMPETITIVE PRICES ORDERING IS EVEN EASIER JUST RING THE NUMBER YOU CAN'T FORGET FOR THE PRICES YOU CAN'T RESIST **5-6-7-8-9-10** and give us your Access or Barclaycard No. or write enclosing cheque or postal order. Official orders accepted from schools, etc. Answering service evngs and wnds

**3-NOTE DOOR CHIME**

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as XK 102. **£5.50**

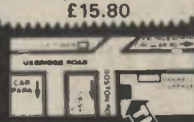**TEACH-IN 84**

Complete kit of top quality components as specified by EE including two EBBO starter packs. **£15.80**



**LCD 3 1/2 DIGIT MULTIMETER**

16 ranges including DC voltage (200 mv-1000 v) and AC voltage, DC current (200 mA-10 A) and resistance (0-2 M) + NPN & PNP transistor gain and diode check input impedance 10M. Size 155x88x31 mm. Requires PP3 9v battery. Test leads included. **ONLY £29.00**

**ELECTRONIC LOCK KIT XK101**

This KIT contains a purpose designed lock IC, 10-way keyboard, PCBs and all components to construct a Digital Lock, requiring a 4-key sequence to open and providing over 5000 different combinations. The open sequence may be easily changed by means of a pre-wired plug. Size: 7 x 6 x 3 cms. Supply: 5V to 15V d.c. at 40mA. Output: 750mA max. Hundreds of uses for doors and garages, car anti-theft device, electronic equipment, etc. Will drive most relays direct. Full instructions supplied. **ONLY £11.50**

Electric lock mechanisms for use with latch locks and above kit **£14.95**

**DL 1000K**

This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers and incorporates a master dimming control. **£15.95**

**DL2100K**

A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **£8.95**

Optional opto input DLA1

Allowing audio ("beat"), -light response. **60p**

**DL3000K**

This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust - simply connect to mains supply & lamps. **£12.95** (1Kw/Channel)

**FAST SERVICE - TOP QUALITY - LOW LOW PRICES**



No circuit is complete without a call to

**ELECTRONICS**

11-13 Boston Road  
London W7 3SJ

Add 50p postage & packing + 15% VAT to total Overseas Customers. Add £2.50 (Europe), £6.00 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability. 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)

**OPEN**

**ALL PRICES EXCLUDE VAT**

TEL: 01-567 8910 ORDERS  
01-579 9794 ENQUIRIES  
01-579 2842 TECHNICAL AFTER 3PM

**KITS FROM £7 TO £60**

**Sparkrite**

Buy Sparkrite Brand Leading Auto Electronics in self-assembly kit form - And save pounds!!

- Electronic Ignition systems - contact triggered and contactless
- Electronic Car Security Systems - including a new ultrasonic unit
- Car Drive Computer - with 12 functions

SEND FOR FREE LITERATURE PACK - TODAY!

8 SOPHISTICATED KITS TO CHOOSE FROM.



To:

SPARKRITE (A Division of Stadium Ltd.), Queensway, Enfield, EN3 4SD. Telephone: 01-804 4343

NAME .....

ADDRESS .....

EE

**FREE CAREER BOOKLET**

**Train for success, for a better job, better pay**

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today - at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

<b>ELECTRONICS ENGINEERING</b>	<input type="checkbox"/>	<b>TV &amp; AUDIO SERVICING</b>	<input type="checkbox"/>
<b>ELECTRICAL ENGINEERING</b>	<input type="checkbox"/>	<b>RUNNING YOUR OWN BUSINESS</b>	<input type="checkbox"/>

Name .....

Address .....



ICS Dept EC144  
160 Stewarts Road,  
London SW8 4UJ



01-622 9911 (all hours)

# T.V. SOUND TUNER

**SERIES II**

**BUILT AND TESTED**

**£26.50** + £2.00 p&p.



Also available with built-in headphone amp. **£32.50** + £2.00 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10½" x 7½" x 2½".

E.T.I. kit version of above without chassis, case and hardware. **£16.20** plus £1.50 p&p.

## PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT



• NOISE REDUCTION SYSTEM • AUTO STOP • TAPE COUNTER - SWITCHABLE E.O. • INDEPENDENT LEVEL CONTROLS • TWIN V.U. METER • WOW & FLUTTER 0.1% • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES. — METAL, CHROME DIOXIDE, ETC.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts. I.e. semiconductors, resistors, capacitors, hardware top cover, printed scale and mains transformer. You only supply solder and hook-up wire.

Featured in April issue P.E. Reprint 50p. Free with kit.

**£34.50** + £2.75 p&p. Complete with case.

## MONO MIXER AMP

Ideal for Church halls & Clubhouses. **£45.00** + £2.00 p&p.

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux. inputs. Size: 13½" x 6½" x 3¾" approx. Power output 50 watts R.M.S. (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.



## 125W HIGH POWER AMP MODULES

**KIT £12.00** + £1.15 p&p  
**BUILT £17.50** + £1.15 p&p

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Stereo mains power supply w/transformer **£10.50** + £2.00 p&p. Mono version, **£7.50** + £2.00 p&p.



### SPECIFICATIONS:

Max. output power (RMS): 125W.  
Operating voltage (DC): 50 - 80 max.  
Loads: 4 - 16 ohms.  
Frequency response measured @ 100 watts: 25Hz - 20KHz.  
Sensitivity for 100 watts: 400mV @ 47K.  
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.  
Dimensions: 205 x 90 and 190 x 36 mm.

## VHF STEREO TUNER KIT



• SPECIAL OFFER! •  
**£13.95** Plus £2.50 p&p.

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July '81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to strict P.E. specification. Front scale size: 10½" x 2½" approx. Complete with diagram and instructions.

## SLEEP SAFELY AT NIGHT

### SMOKE DETECTOR ALARM!

Gamma ionization type smoke detector with built-in audible alarm. Model No. F227. IDEAL FOR HOMES, HOTELS & GUEST HOUSES, CARAVANS, BOATS, ETC. • MICROCHIP technology, no mechanical parts. • Maintenance free. • No wiring needed. • Runs off transistor battery, lasts for a year. • Money back guarantee.



**£4.95** plus 75p p&p. or 2 for **£8.50** plus £1.50 p&p.


## QUALITY SPEAKER SYSTEMS

Made to sell for over £300! Must be heard to be believed. Made in England by World famous British manufacturer. SPECIFICATIONS: Bi-Directional 5 speaker system. Drive units: 2x25mm soft dome tweeters, 2x13cm polymer cone mid range speakers, one 24cm bass unit. Impedance: 8ohms. Rated power 200W peak max. Sensitivity: 87 dB @ 1W. Freq. range: 45 to 20,000 Hz. Finish: Satin walnut veneer, with brown trim. Size: 35½" x 8½" x 15¼". Weight: 27kgs. **£99.95** a stereo pair. Buyer collect only!



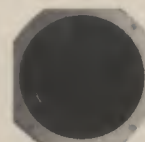
## HI-FI SPEAKER BARGAINS


**AUDAX 8" SPEAKER**  
High quality 40 watts RMS/Mid. Ideal for either HiFi or Disco use this speaker features an aluminium voice coil and a heavy 70mm diameter magnet. Frequency res: 20Hz to 7KHz. **£5.95** + £2.20 p&p. Impedance: 8 ohms.



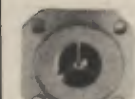**AUDAX 40W FERRO-FLUID HI-FI TWEETER**  
Frequency response: 5kHz - 22kHz. Size: 60mm square. Impedance: 8 ohms. **£5.50** + 60p P&P.



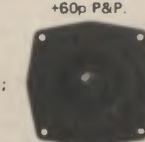
**GOODMANS TWEETERS**  
8 ohm soft dome radiator tweeter (3½"sq.) for use in up to 40W systems; **£3.95** each plus £1.00 p&p, or **£6.95** a pair plus £1.50 p&p.



## BSR RECORD DECKS

3 speed, auto, set-down; with auto return. Fitted with viscous damped cue, tubular aluminium counter-weighted arm, fitted with ADC magnetic head. Ideally suited for home or disco use.

**£25.95** plus £1.75 p&p.

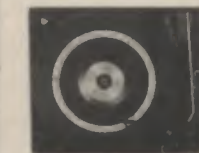

Auto-Changer model - takes up to 6 records with manual override. Supplied with stereo ceramic cartridge. **£12.95** plus £1.75 p&p.

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx. **£14.95** + £1.75 p&p.



**SPECIAL OFFER!** Replacement stereo cassette tape heads - £1.80 ea, add 50p p&p to order. Philips stereo magnetic cartridge. **£3.95** + 60p p&p.

**PLINTH TO SUIT BSR RECORD PLAYER DECK (with cover)** Size: 16½" x 14" x 2½". Cover size: 14½" x 13½" x 3¾". Due to fragile nature of this item, buyer to collect only. **ONLY £8.95.**

All mail to: **21C HIGH ST, ACTON W3 6NG.** Callers Mon - Sat, 9.30 - 5.30. Half day Wednesday. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/11/83 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to up-

date their products without notice. All enquiries send S.A.E. All cheques & P.O.'s payable to RTVC Ltd.

**CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432.** (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include V.A.T.

Mail or 'phone orders by ACCESS. Tel: 01-992 8430.



# EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 13 NO. 5 MAY 1984

## Editor

MIKE KENWARD

## Consultant Editor

FRED BENNETT

## Assistant Editors

DAVE BARRINGTON (Production)  
DAVID SHORTLAND (Technical)

## Technical Editor

MIKE ABBOTT

## Technical Sub-Editors

RICHARD BARRON  
BRIAN BUTLER

## Art Editor

JACK POUNTNEY

## Assistant Art Editor

KEITH WOODRUFF

## Senior Technical Illustrator

JOHN PICKERING

## Technical Illustrator

ISABELLE GREENAWAY

## Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL  
WESTOVER HOUSE  
WEST QUAY ROAD, POOLE, DORSET BH15 1JG  
Phone: Poole (0202) 671191

We regret that lengthy technical enquiries cannot be answered over the telephone

## Advertisement Manager

DAVID TILLEARD 01-261 6676

## Secretary

CHRISTINE POCKNELL 01-261 6676

## Advertisement Sales Executives

ALFRED TONGE 01-261 6819  
RICHARD WILLETT 01-261 6865

## Classified Supervisor

BARBARA BLAKE 01-261 5897

## Advert Make-Up and Copy Department

JULIE FISH 01-261 6615

## Advertisement Offices

EVERYDAY ELECTRONICS ADVERTISEMENTS  
KING'S REACH TOWER  
STAMFORD STREET  
LONDON SE1 9LS  
Telex 915748 MAGDIV-G

## Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

## Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

## ROBOTICS

THIS issue of EE carries our first step into robotics with the "vehicle" in our *Microcomputer Interfacing Techniques* series. This step is a significant one and will lead to other projects in this area. We do not see a big market for expensive androids at the present time but we do expect to see small robotic arms being introduced to schools, colleges and industry for educational and development purposes.

Our buggy is relatively cheap and easy to build and can provide a fascinating involvement in control applications for microcomputers. We believe that many computer users are now tiring of just playing games—great fun though they are—and that this project will extend the fun element while developing new software skills and understanding.

As regular readers will be aware the whole *Microcomputer Interfacing Techniques* series has been designed to provide practical assistance in connecting computers to the outside world. Many computer hobbyists may have read the series with interest but resisted the temptation to actually build any projects and get involved in a practical way: We suggest that this project is the one to take you over the edge. Not only will it be fun to build but should provide hours of entertainment and learning for all the family.


Another project which has always been a must for the novice is a small radio. We are sure many of our more experienced readers remember the thrill of tuning in your first station on a set made with your own hands. Perhaps it is the thrill of capturing radio waves out of the "air", or of being able to listen to distant stations for next to nothing. Maybe familiarity with radio has diminished the excitement for modern youngsters but we still feel such a project would give many novice constructors quite a kick. Why not try it and see?

## SHORTAGE

Recent reports in the industrial electronics press indicate that the consumer industry is about to face a shortage of high technology chips. While this should not affect the constructor whose interest lies in the non-microprocessor projects those with aspirations to building any MPU-based system or add-on would be well advised to buy components as soon as possible.

Many manufacturers have sold their entire production of memory and microprocessor chips for the remainder of 1984 and stories of "black market" prices of up to six times the list price are filtering through from the States. Needless to say we will watch component availability on the products we publish but we cannot promise that chips we use will continue to be available at all times. Delivery time from manufacturers is often 16 weeks and 40-plus weeks is being quoted on some devices now. Plan ahead if you can.

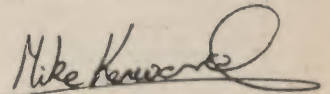We wonder how chip shortages might affect sales of microcomputers next Christmas.



## Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.


## Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.

## Subscriptions

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £13.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

# EXPERIMENTER'S POWER SUPPLY UNIT

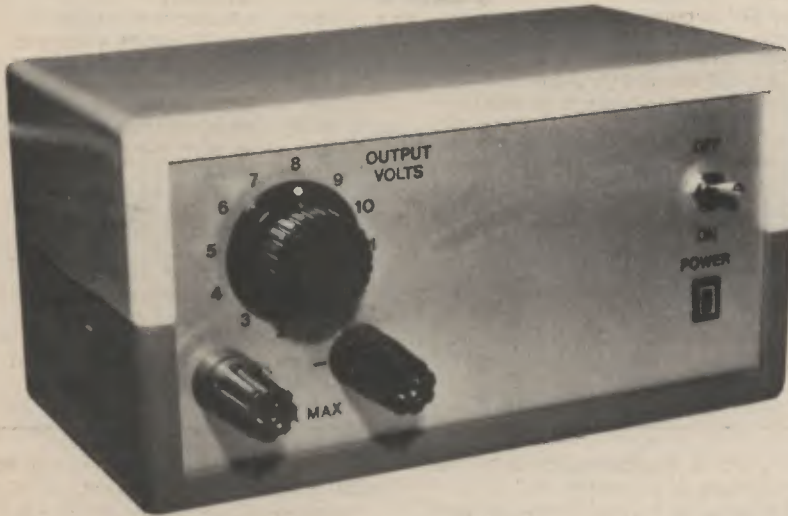

BY S. NIEWIADOMSKI

*An essential piece of laboratory equipment for the experimenter with the output switchable from 2 to 12V in 1V steps thus invalidating the need for an expensive voltmeter. Maximum output current of 325mA.*

ONE of the first things a newcomer to electronics learns is that powering circuits from batteries can be expensive and inconvenient. It is easy to leave a circuit accidentally switched on overnight and find the batteries flat next day.

So a mains powered variable d.c. supply is a must to the serious constructor and experimenter. This Power Supply

provides a cheap and easy solution to this problem and additionally, has educational value in the use of an operational amplifier as an output driver.

The unit has 11 preset voltage settings from 2 to 12V at up to 325mA output current. Its output is short circuit protected and since the voltage is switched, a voltmeter is not required, considerably

reducing the cost of the instrument. A novel feature is the use of a power operational amplifier which provides the output current without the use of an additional device.

On the prototype, the output voltage was found to be within 0.1V of the expected value at all switch positions.

## POWER OP-AMP


The  $\mu A759$  is a power operational amplifier manufactured by Fairchild. It operates like a 741 op-amp, having a very high open loop gain and high input resistance. It also has an output stage capable of supplying up to 325mA. This makes it suitable for many applications such as audio amplifiers, servo amplifiers and power regulators. Like any conventional operational amplifier, its closed loop gain is defined accurately by the ratio of feedback resistors.

The features of the  $\mu A759$  which make it specially suitable for use in a power supply are firstly, its output current capability; secondly, its output is short circuit protected and thirdly, it is internally protected against thermal overload. Care has to be taken to use an adequate heatsink so that the temperature of the device does not rise above that which will cause the thermal shutdown to operate. The dissipation in the device is at its highest at low output voltages and high current.

## CIRCUIT DESCRIPTION

The full circuit diagram of the unit is shown in Fig. 1. T1 is the mains step down and isolation transformer. Its primary is fed from the mains via the anti-surge fuse FS1 and the mains ON/OFF switch, S1. The transformer used on the prototype has split primary windings so that it can be used on 120V mains. In this country, the two windings

Fig. 1. Circuit diagram of the Experimenter's Power Supply Unit.

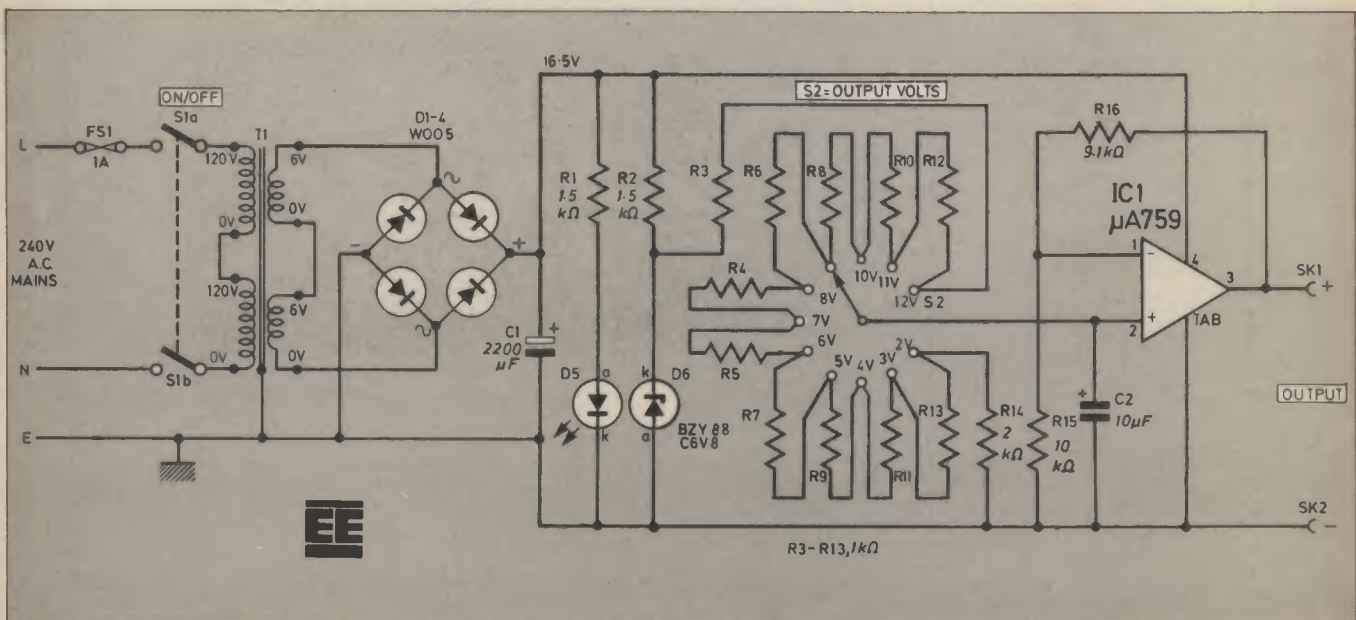

are connected in series. Similarly the secondary consists of two windings each giving 6V r.m.s. which are also connected in series. A transformer with a single 12V r.m.s. secondary is also suitable.

The secondary feeds the bridge rectifier D1 to D4 and smoothing capacitor C1. An unregulated d.c. voltage of 16.5V at no load and 15.5V at 325mA output appears on C1. R1 supplies about 10mA to the front panel mounted light emitting diode D5 which indicates when the unit is switched on.

Current is supplied to the 6.8V Zener diode D6 by R2, allowing about 6.5mA to be split between D1 and the resistor chain R3 to R13. The voltage across the

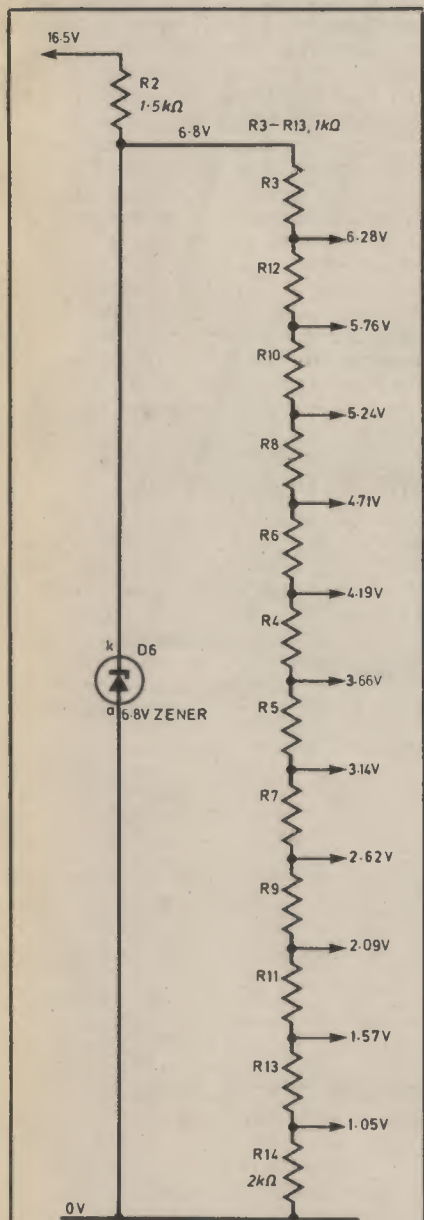


Fig. 2. The potential divider chain around S2. D6 establishes a reference voltage and points along the chain give voltages, that when multiplied by the gain of IC1 (set at 1.91 by R15 and R16), give the output voltages.

## COMPONENTS

See  
**Shop  
Talk**  
page 313

### Resistors

- R1,2 1.5kΩ (2 off)
- R3-13 1kΩ (11 off)
- R14 2kΩ
- R15 10kΩ
- R16 9.1kΩ
- All 1/4W carbon ±5%

### Capacitors

- C1 2200μF 25V elect.
- C2 10μF 16V tantalum bead

### Semiconductors

- D1-4 W005 1A, 50V bridge rectifier
- D5 rectangular red l.e.d. plus mounting bezel
- D6 BZY88 C6V8 6.8V, 500mW Zener
- IC1 μA759 power op-amp

### Miscellaneous

- S1 d.p.d.t. miniature mains toggle

- S2 1-pole, 12-way midget rotary (11 ways used)
  - T1 6VA mains transformer, 12V or 0-6V, 0-6V secondary
  - FS1 1A, 20mm anti-surge fuse plus panel mounting holder
  - SK1 4mm insulated screw terminal, red
  - SK2 4mm insulated screw terminal, black
- Verobox, 155 x 85 x 80mm (type 202-21042L); 0.1in matrix strip-board, 24 strips by 17 holes; knob, 20mm diameter; grommet; P-clip; mains cable; mains plug; 7/0.2mm p.v.c. sleeved wire; p.v.c. sleeving; solder tags (6 off); M3 screws and nuts (to mount T1); M2.5 screw and nut (to mount IC1); stick-on rubber feet (4 off).

resistor chain is maintained stable by D6 despite changes in the supply.

The number of 1-kilohm resistors and the 2-kilohm resistor in the chain mean that voltage steps of 0.52V are tapped off by the rotary switch S2 (see Fig. 2). Capacitor C2 holds the previous voltage level on pin 2 of IC1 when rotating S2 until the new position is reached. This means that a break-before-make component can be used for S2 without the output voltage becoming uncontrolled when being changed.

R15 and R16 are the operational amplifier feedback resistors, defining the voltage gain of the circuit. Their values are chosen to give a gain of 1.91 which

when multiplied by 0.52 (the input step value) gives the output step value of 1V.

The unregulated supply is connected to the power supply pin of IC1. Ripple on this pin is smoothed out by the ripple rejection of the operational amplifier and the stabilising action of D6.

SK1 and SK2 are 4mm screw terminals to which the positive and negative outputs are connected. The negative supply to IC1 is the tab of the package and is bolted directly to the back panel to provide a heatsink. This arrangement means that the negative output is earthed. If a floating output is required the tab of IC1 must be insulated from the case earth.

The completed prototype Power Supply with front panel removed. Note how the cable form permits the withdrawal of the panels without the need for desoldering.



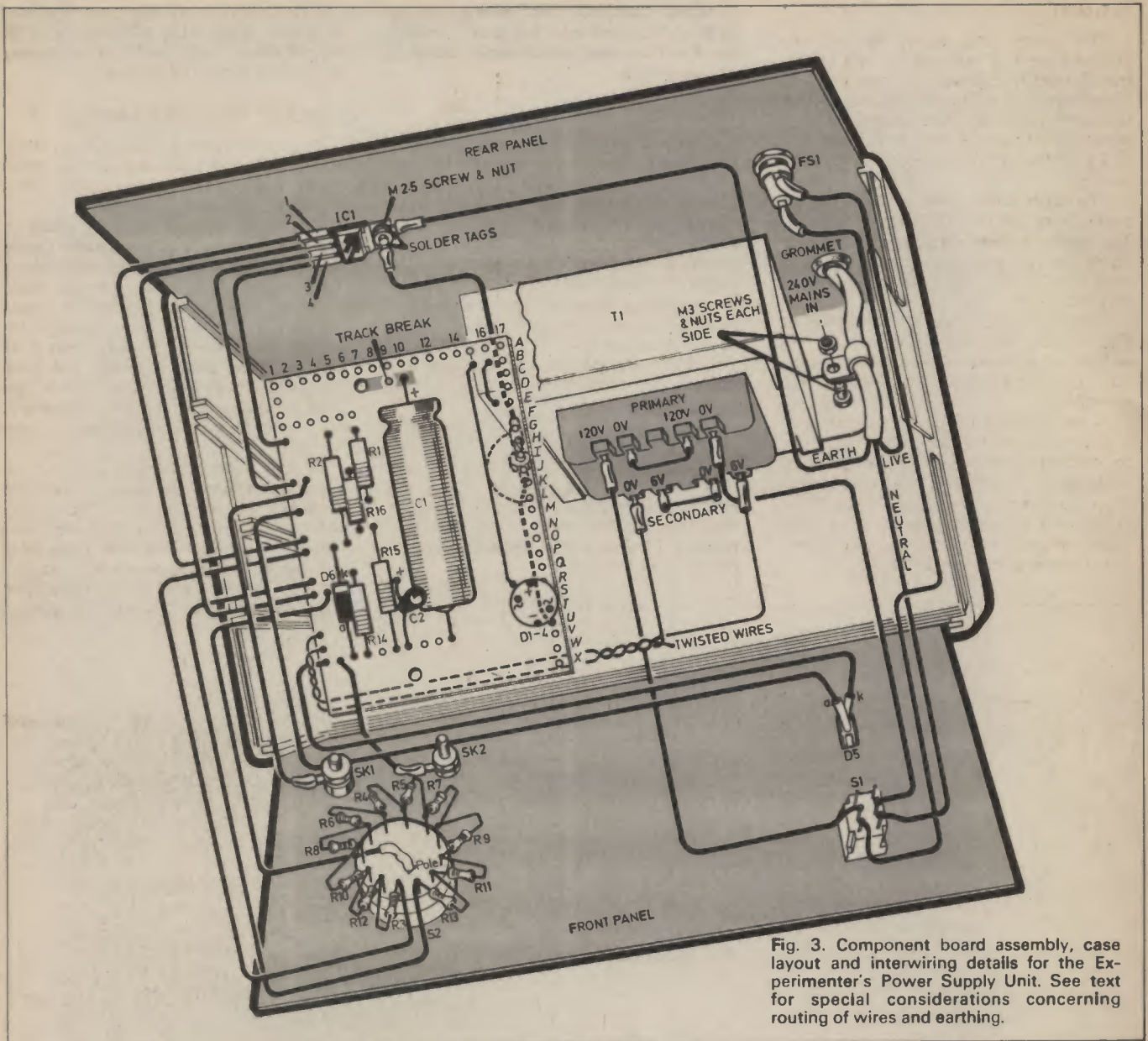


Fig. 3. Component board assembly, case layout and interwiring details for the Experimenter's Power Supply Unit. See text for special considerations concerning routing of wires and earthing.

## CONSTRUCTION

### CIRCUIT BOARD

The prototype unit was constructed on a piece of stripboard (24 strips by 17 holes) mounted in a Verobox, 155 × 85 × 80mm, which also houses the transformer. The layout of the stripboard is shown in Fig. 3. No trackside view is shown as only one break is required at location B9. The two mounting holes are positioned to line up with the moulded bosses in the base of the case.

The leads of the bridge rectifier D1 to D4 have to be preformed to suit the layout and this component must be mounted quite low into the board to avoid it hitting the fixing stud of SK2 when construction is complete.

The transformer is mounted in the other side of the base of the box as shown. It is positioned to the rear to allow for the switch and l.e.d. and also to allow for the fuseholder and mains cable grommet.

### CASE

The drilling details of the front and rear panels are shown in Fig. 4. These are the anodised aluminium panels that are supplied with the Verobox. The rectangular cut-out for the l.e.d. (D5) may be replaced with a hole if a standard l.e.d. and mounting clip is used.

The rotary switch, on/off switch, l.e.d. and terminals SK1 and SK2 are mounted on the front panel. Note that SK1 (the positive) screw terminal is mounted so that it is isolated from the panel (with the bushes supplied) but SK2 (the negative) is

secured so that it makes contact (the plastic bush on the threaded mounting stud is not used). These terminals require a "keyhole" cut-out to prevent them turning.

S2 is a 12-way, break-before-make midget rotary switch of which 11 ways are used. This type of switch has an adjustable stop and to set it, the mounting nut must be removed and the special washer with a tab on it lifted out of the recess. The tab is then inserted into the hole marked "11" and the washer is pushed back into the recess.

Resistors R3 to R13 are soldered directly to the terminals of S2 and note that R3 actually uses terminal "12" as this position is not required.

The back panel carries IC1, the fuseholder and the cable grommet. IC1 is mounted directly to the panel (no isolating kit required) with M2.5 fixings.

## WIRING

The mains cable enters through the grommet and is clamped to one of the transformer fixings with a P-clip. The live wire (brown) is taken to the fuse and then to on/off switch S1. The neutral (blue) is wired directly to the switch. The primary of T1 is then wired to the other side of the switch.

The earth wire (yellow/green) is routed to the fixing screw of IC1 via a solder tag. The earth is then wired to a mounting screw on T1 and onto the component board (ref. U17). The front panel will be earthed via SK2.

All interwiring details are also given in Fig. 3. Note that most joints are sleeved as this not only improves the appearance but also acts as strain relief to aid reliability.

When wiring from the component board to the front panel, the wires should be long enough to allow this panel to be withdrawn if necessary. The connection from the board to the secondary of T1 is made with a twisted pair of wires and these are kept away from all other wires. This helps prevent mains pick-up.

When complete, the wiring can be neatly held together (with the exception of the a.c. side) with spiral cable wrapping or lacing cord.

## TESTING

When construction is complete, check all wiring carefully *particularly* that associated with the mains. If everything is in order, switch on and D5 should light. Check that the voltage across C1 is about 16.5V. Also check that D6 has 6.8V across it. Now connect a voltmeter to the output terminals and rotate S2 through all its settings. If an analogue voltmeter is used the output voltage should appear to be indistinguishable from the nominal voltages expected. A digital voltmeter should show differences of only about 0.1V.

Since the current limiting circuit is built into IC1, no testing of it is really necessary. High power resistors of appropriate values can be connected to the output to draw up to 325mA to check the regulation of the supply. For the 12V range, a 27 ohm, 4 watt resistor will draw the maximum current.

The regulation on the prototype was extremely good; at a nominal 10V, the output fell by only 0.01V on increasing the current from 0 to 325mA.

## CIRCUIT MODIFICATIONS

It is worthwhile to mention some possible modifications to the circuit which might make the power supply more versatile.

An output current ammeter could be included in series with the positive output terminal. This gives a useful indication of the operation of the circuit being powered. If an infinitely variable output voltage is required, then replace the resistor chain of R3 to R13 with a 10 kilohm linear potentiometer. The front panel can still be marked with the output voltages or a moving coil d.c. voltmeter of suitable range could be connected across SK1 and SK2.

Higher output voltages can be obtained by using a transformer with two secondary windings of say 9V r.m.s. connected in series. The maximum allowable supply voltage for IC1 is 36V. Remember that the built-in features of IC1 make it virtually indestructible so if you do blow it up, send it back to where you bought it! □



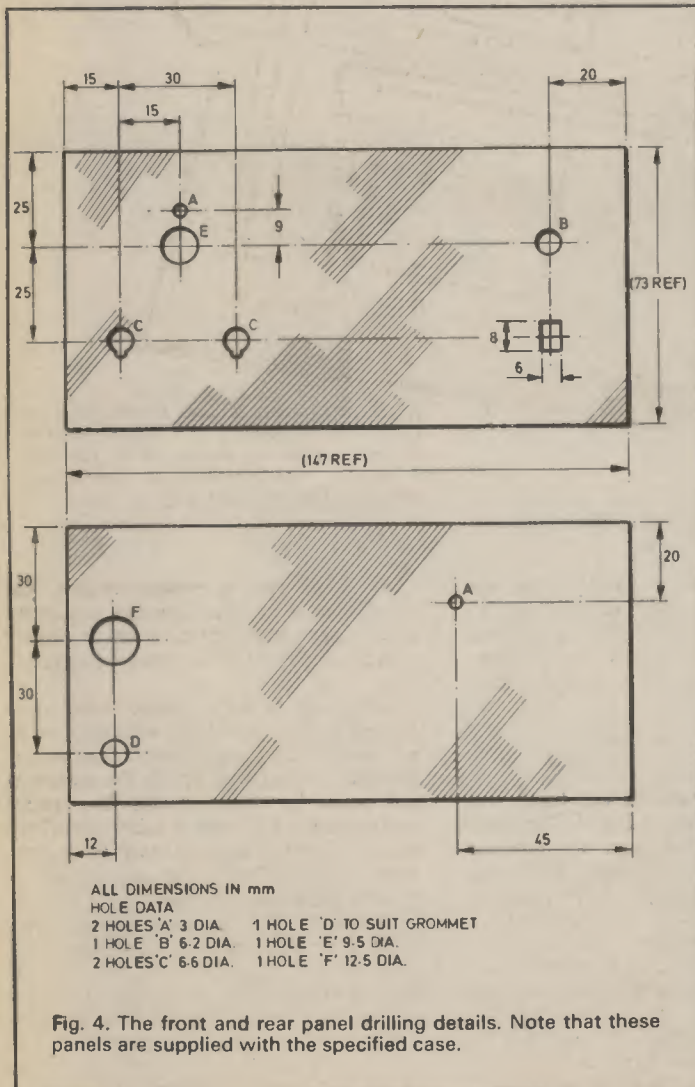



Fig. 4. The front and rear panel drilling details. Note that these panels are supplied with the specified case.

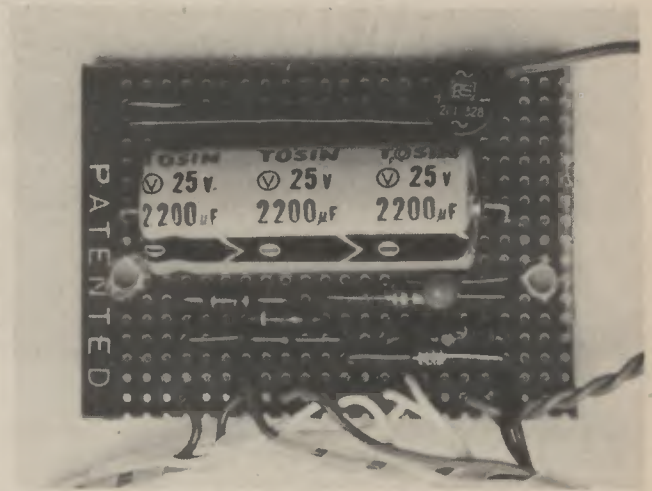

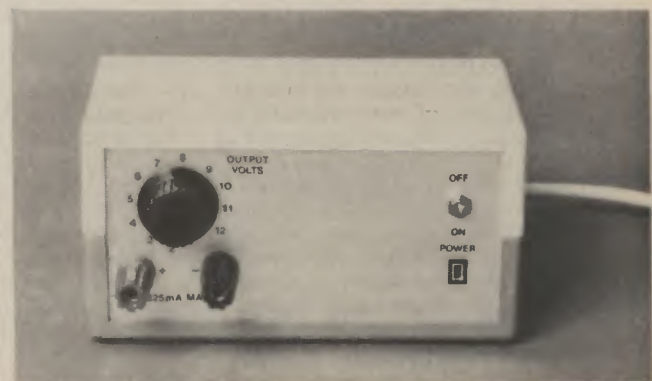The finished component board (above) and the front panel labelling of the Experimenter's Power Supply Unit (below).



# Vari-cap A.M. Radio

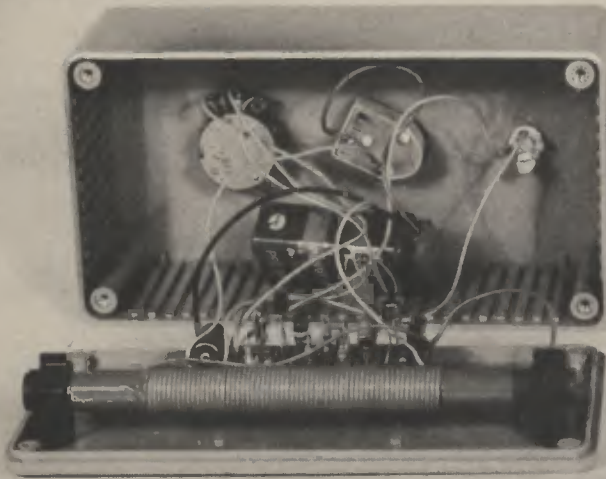

BY R.A. PENFOLD

**V**ARIABLE capacitance (varicap) diodes have been in use for many years now, but they are mainly used in v.h.f. designs. This is partially because varicaps have the advantage, at v.h.f., that they can be positioned close to the tuning coils, with the tuning control situated as far away from the varicaps and coils as one wishes.

## VARI-CAP TUNING

This is simply because varicaps are tuned by a d.c. tuning voltage, and there is no real limitation on the length of a lead carrying a d.c. signal. On the other hand, using an ordinary tuning capacitor necessitates the fitting of the tuning coils close to the tuning gangs, since the leads to the variable capacitor are carrying v.h.f. signals, and the small inductance in even quite short connecting leads could easily cause a malfunction.

This makes the component layout very critical, and it can be a little awkward to achieve a satisfactory layout.

However, even though varicaps do not have this advantage in a.m. (medium and longwave) radios where the lower signal frequencies render lead lengths of relatively little importance, they still represent a neat and attractive alternative to ordinary tuning methods.

The reason for the lack of varicap tuning in a.m. radios is mainly due to the lack of suitable devices. An a.m. receiver requires a much larger maximum tuning capacitance than v.h.f. types, and the ratio of maximum to minimum capacitance is also substantially larger for a.m. sets. Most varicaps give totally inadequate capacitance swings.

## VARI-CAP PERFORMANCE

A few varicaps having adequate performance for a.m. applications were introduced a number of years ago, but they failed to achieve popularity due to their fairly low  $Q$  (magnification factor) values and more importantly, they required inconveniently high maximum tuning voltages of as much as 27 volts in some cases. More recent devices are much better in both respects with  $Q$ s of around 200 to 500 being typical, and a maximum

tuning voltage of only about 7 to 8 volts being adequate.

This enables the tuning voltage to be obtained using a 9-volt battery supply without any voltage step-up circuitry, and a.m. varicap diodes now represent a really viable alternative to conventional tuning methods.

The simple t.r.f. (tuned radio frequency) radio described in this article covers the full medium waveband in a single tuning range. The output is for a crystal earphone, and good volume and sensitivity are obtained by using the popular ZN414 integrated circuit plus a simple high gain audio stage. A simple varicap tuning circuit is used, and the whole receiver is powered from a single PP3 size 9-volt battery.

## CIRCUIT DESCRIPTION

The circuit diagram of the receiver is shown in Fig. 1, and the varicap tuning diodes are D2/3 which are in a single device called the KV1236. These are used in the usual back-to-back arrangement and are connected direct across the ferrite aerial (L1). The latter is tuned over slightly more than the full medium-wave broadcast band by the series capacitance of D2 and D3.

R1 and D1 provide a stabilised 7.5 volt supply, and VR1 gives a continuously variable 0 to 7.5 volt output at its wiper. This voltage is used to tune the set, and VR1 is, of course, the tuning control. R2 couples the output of VR1 to the tuning diodes and prevents VR1 from heavily damping the aerial tuned circuit.

## DEPLETION LAYER

Varicap diodes are basically the same as ordinary silicon diodes, and the tuning voltage reverse biases both diodes so that an insulating *depletion layer* is formed


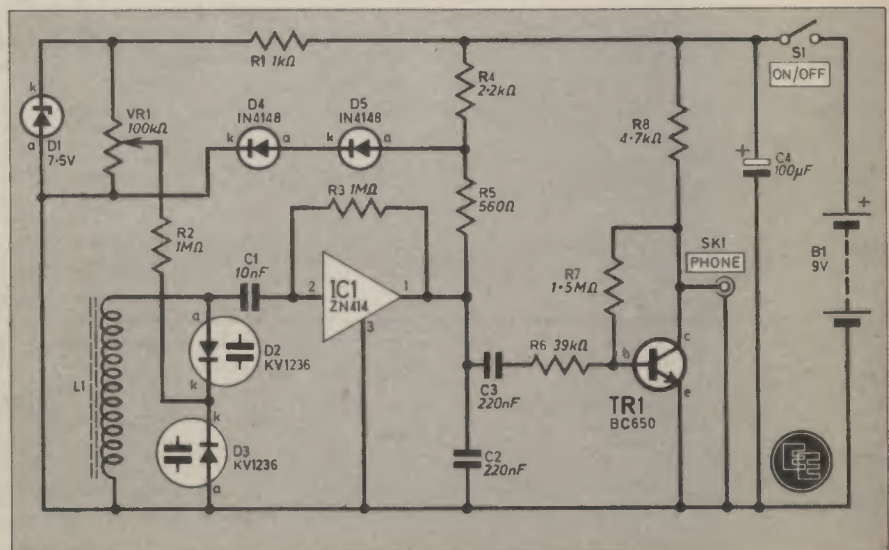


Fig. 1. Complete circuit diagram of the Vari-cap A.M. Radio.

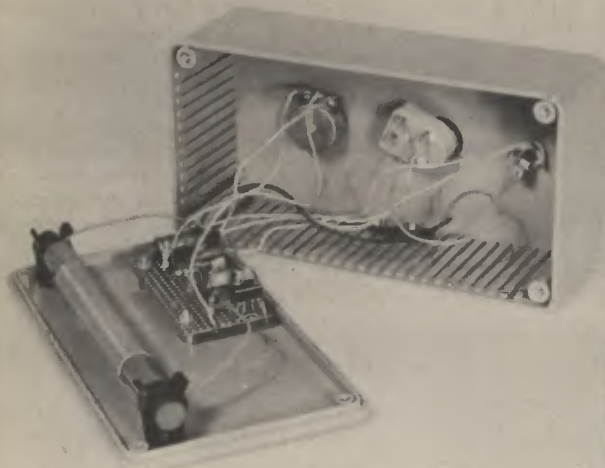



Ferrite aerial and circuit board mounted on rear panel of the case.

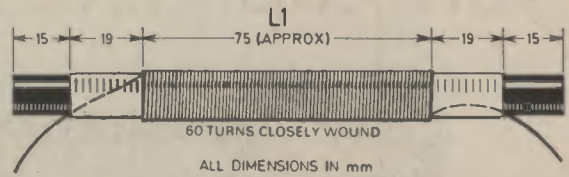


Fig. 2. Diagram showing construction details for the ferrite rod aerial.

**COMPONENTS**  
approximate  
cost £10

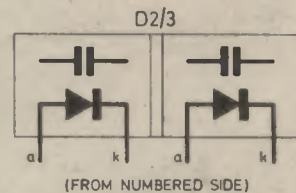


Fig. 4. Pinning details for the varicap device.

## COMPONENTS

### Resistors

R1	1k $\Omega$
R2,3	1M $\Omega$ (2 off)
R4	2.2k $\Omega$
R5	560 $\Omega$
R6	39k $\Omega$
R7	1.5M $\Omega$
R8	4.7k $\Omega$
All $\frac{1}{4}$ W carbon $\pm$ 5%	

See  
**Shop  
Talk**

### Capacitors

C1	10nF ceramic plate
C2,3	220nF polyester (2 off)
C4	100 $\mu$ F 10V elect.

page 313

### Semiconductors

D1	BZY88 C7V5 400mW 7.5V Zener
D2,3	KV1236 dual varicap diode
D4,5	1N4148 (2 off)
IC1	ZN414 a.m. radio
TR1	BC650 npn silicon

### Miscellaneous

VR1	100k $\Omega$ linear carbon potentiometer
S1	rotary on/off switch
SK1	3.5mm jack
B1	9V type PP3

Stripboard: 0.1 inch matrix size  
12 strips by 25 holes; battery con-  
nector; plastic case size 150 x  
100 x 50mm (ABS 2005); 140 x  
9.5mm ferrite rod plus wire; tape  
and mounting clips; crystal  
earphone; control knobs; 6BA fix-  
ings.


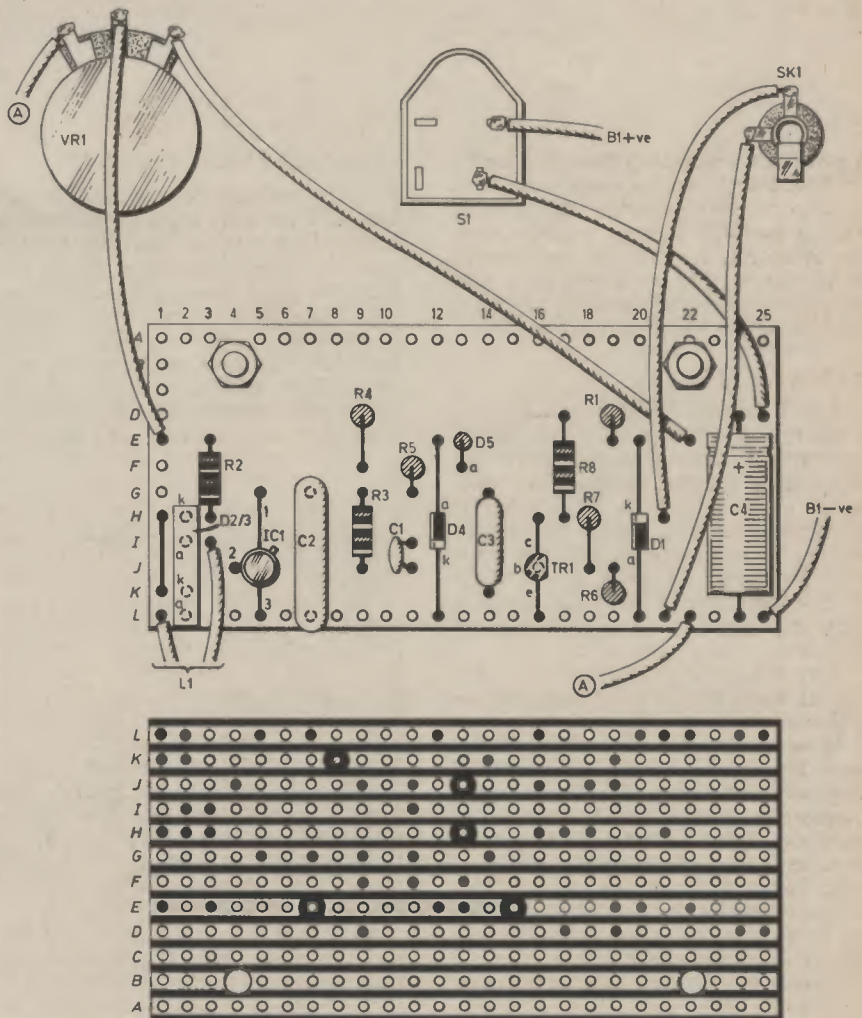


Fig. 3. Stripboard layout and external component wiring diagram.

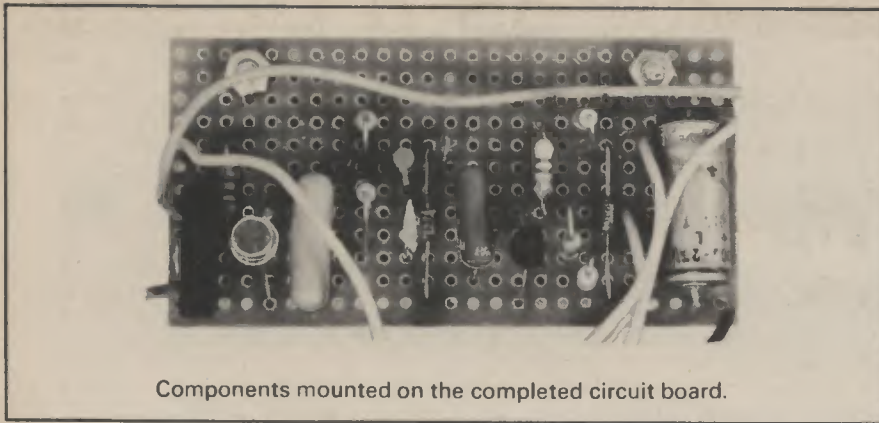

Components mounted on the completed circuit board.

between the two pieces of semiconductor material that form each diode. In effect, the two pieces of semiconductor material are the plates of the capacitor and the depletion layer is the dielectric. The depletion layer increases in thickness as the reverse bias is increased, and the capacitance of the diode is consequently decreased.

It is not possible to simply use any silicon diodes for D2 and D3, since it is necessary for the diodes to provide certain capacitances at various reverse voltages with reasonable accuracy, and for the diodes to give a reasonable  $Q$ . Only a few modern varicaps are capable of giving satisfactory results in respect to this application where a large capacitance swing is required.

Each diode in the KV1236 device has a typical capacitance of 450pF at a reverse potential of 2 volts, falling to a capacitance of only 30pF with an 8.5 volt reverse bias. For series connected diodes both these capacitance figures are halved. The typical  $Q$  of the KV1236 is 200.

### CONVENTIONAL CIRCUIT

Because of the use of varicap tuning, IC1 is used in a circuit which does not quite conform to the normal ZN414 configuration. C1 couples the *non-earthly* end of the ferrite aerial to the input of IC1 and R3 is used to bias IC1. R3 has been made somewhat higher in value than would normally be the case in order to minimise damping of the aerial. The circuit has been tried using several ZN414 i.c.s, and worked well in each case. Apart from the input coupling and biasing this part of the circuit is quite conventional.

The audio output from IC1 is coupled by C3 and R6 to a simple common emitter amplifier based on TR1. R6 is needed to prevent the output from TR1 becoming excessive in amplitude, which would cause clipping and severe distortion. It also introduces a degree of high frequency attenuation in conjunction with the input capacitance of TR1, and this reduces the risk of instability.

A crystal earphone can be driven direct from the collector of TR1 and no coupling capacitor is necessary here. The current consumption of the circuit is only about 5mA, or so, and this gives many hours of use from each PP3 battery.

## CONSTRUCTION starts here

### AERIAL

A home-constructed ferrite aerial is used in this design, although a ready-made type such as the Denco MW5FR can be used if preferred. In common with most ready-made ferrite aerials the Denco MW5FR has a small coupling winding in addition to the main winding, and this should either be removed or just ignored.

Details of the home-constructed aerial are provided in Fig. 2, and this is based on a ferrite rod which measures 140mm long by 9.5mm in diameter. The winding consists of 60 turns of 7/0.2mm p.v.c. insulated connecting wire, or any similar multi-strand connecting wire. Bands of 19mm insulation tape are used to hold the winding in place, and the turns should be as closely wound as possible if the winding is to fit into the available space. Leave leadout wires about 100mm long.

Mount the completed ferrite aerial high up on the rear panel of the case using special mounting clips or P style cable clips of adequate diameter. Make sure that adequate space is left for the component panel to be fitted below the aerial.

Note that the case must be made from plastic or some other non-metallic

material that will not screen the aerial and prevent any significant signal pick up. The simple front panel layout of the set can be seen from the photographs.

### COMPONENT PANEL

A 0.1 inch matrix stripboard measuring 12 strips by 25 holes is used to take most of the components, and Fig. 3 gives details of this board. It is constructed in the standard way with a board of the required size first being cut out using a hacksaw, after which the two 3.3mm diameter mounting holes and the five breaks in the copper strips are made. The latter can be made using a small hand-held twist drill if the special tool is not available.

The components can then be soldered into place with the semiconductor devices being left until the end. Fig. 3 gives details of the wiring of the set. Be careful to connect C4 and the semiconductors the right way round, and make sure that the single link wire (beside D2/3) is not accidentally omitted.

Complete all the point-to-point wiring before finally fitting the component panel onto the rear panel of the case using 6BA fixings. After a final thorough check of all the wiring the set is then ready for use, and no alignment whatever is required if the home constructed aerial described earlier is used.



Finished project with a crystal earphone fitted.

### TRIAL AND ERROR

If a ready-made ferrite aerial is used it will be necessary to position the aerial coil on the rod correctly, in order to obtain full coverage to both ends of the medium-wave band.

This is really just a matter of trial and error, and the correct position will almost certainly be with the coil slid right to one end of the ferrite rod. As the set covers slightly more than the full medium-wave band the positioning of the coil will not be too critical. When the correct setting has been found, glue or tape the coil in place. □

# Are you as fast as a bullet?

WOULD YOU HAVE MADE A FIGHTER PILOT?  
NOW YOU CAN FIND OUT WITH THE NEW

## REACTION TESTER

A FREE PROJECT FROM GSC


Split second timing is essential for this, the latest and fastest game from GSC. Find out how long you could have stayed "upstairs" before you "bought it". Press start switch, after a random time period, a moving light appears. The quicker you press the button, the longer you "stay alive". You can't fool this game though — a "cheat" light will tell everyone that you guessed when the lights would come on.

Speed and concentration are the names of this game — build our kit and "beat the bullet".
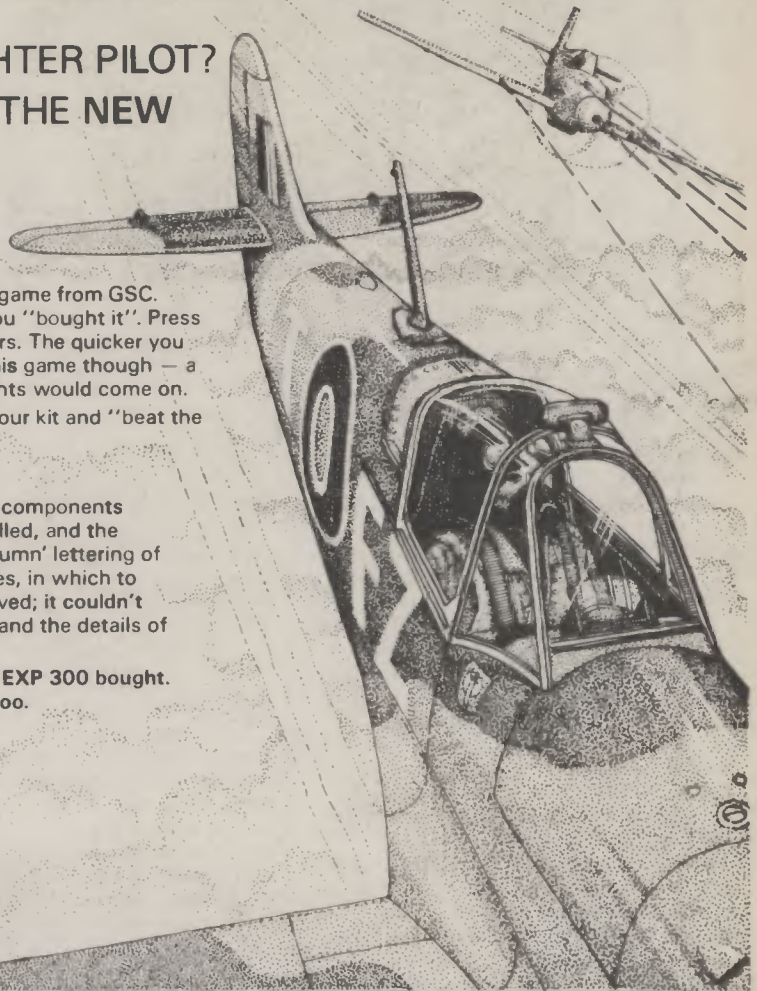
### HOW DO YOU MAKE IT?


Our FREE project sheet gives you a large, clear diagram of the components layed out on an EXP 300 breadboard. Each component is labelled, and the values are given in a component listing. Even the 'row and column' lettering of our EXP 300 is shown to make the location of the correct holes, in which to push the components, easy to find. There's no soldering involved; it couldn't be easier! As an extra bonus, there's a full circuit description, and the details of a regulated power supply on the other side of the sheet.

"Clip the coupon" and get your FREE project sheet with each EXP 300 bought. AND a free catalogue! Just ask about our other free projects too.


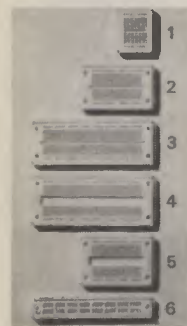
### EXPERIMENTOR BREADBOARDS

The largest range of breadboards from GSC. Each hole is identified by a letter/number system. EACH NICKEL SILVER CONTACT CARRIES A LIFE TIME GUARANTEE. Any Experimentor breadboard can be 'snap-locked' with others to build a breadboard of any size.




1. EXP 325 £2.25 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.
2. EXP 350 £3.80 Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.
3. EXP 300 £6.50 The most widely bought breadboard in the UK. With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.
4. EXP 600 £7.95 Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.
5. EXP 650 £4.75 Has 6" centre spacing so is perfect for MICROPROCESSOR applications.
6. EXP 4B £2.75 Four more bus-bars in "snap-on" unit.

### PROTO-BOARDS

The ultimate in breadboards for the minimum of cost. Two easily assembled kits.

7. PROTO-BOARD 6 KIT £12.00 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

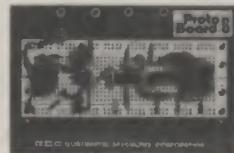
8. PROTO-BOARD 100 KIT Complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with kit economy.



"Clip the coupon" and get your FREE project sheet with each EXP 300 bought. AND a free catalogue! Just ask about our other free projects too.

For further details of our FULL PROTO-BOARD RANGE, please send for our free catalogue.

GLOBAL SPECIALTIES CORPORATION

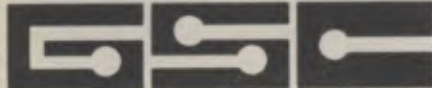

G.S.C. (UK) Ltd. Dept. 4J8,  
Unit 1, SHire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682

G.S.C. (UK) Limited Dept 4J8, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ  
Price include P & P and 15% VAT.


1	QTY.	2	QTY.	3	QTY.	4	QTY.	5	QTY.	6	QTY.	7	QTY.	8	QTY.
	£3.45		£5.23		£8.63		£10.29		£6.33		£4.03		£14.95		£20.07

Name \_\_\_\_\_ Address \_\_\_\_\_

I enclose Cheque/P.O. for £ \_\_\_\_\_ or debit my Barclaycard/Access/American Express card no. \_\_\_\_\_ expiry date \_\_\_\_\_

FOR IMMEDIATE ACTION - The G.S.C. 24 hour, 5 day a week service  
Telephone (0799) 21682 and give us your Barclaycard, Access, American  
Express number and your order will be in the post immediately

For FREE  
catalogue  
tick box

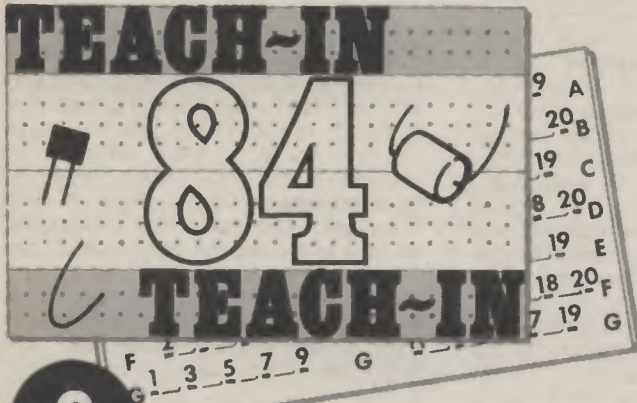

A TWELVE-PART HOME STUDY COURSE IN THE PRINCIPLES AND PRACTICE OF ELECTRONIC CIRCUITS. ESSENTIALLY PRACTICAL, EACH PART INCLUDES EXPERIMENTS TO DEMONSTRATE AND PROVE THE THEORY.

USE OF A PROPRIETARY BREADBOARD ELIMINATES NEED FOR SOLDERING AND MAKES ASSEMBLY OF CIRCUITS SIMPLE.

THE IDEAL INTRODUCTION TO THE SUBJECT FOR NEWCOMERS. ALSO A USEFUL REFRESHER COURSE FOR OTHERS.

By GEORGE HYLTON

## POWER IN GENERAL

**E**LECTRIC POWER, as we saw last time, is the rate at which electrical energy is being transformed into some other form. This can be heat, sound, light, mechanical energy, and other kinds.

The electronic engineer is often also concerned with the transformation of one form of electrical energy into another. In audio amplifiers, for instance, d.c. power from the battery is transformed into a.c. power to drive a loudspeaker. In mains power supply units, a.c. power is turned into d.c.

In d.c.-d.c. converters, d.c. at one voltage is turned into d.c. at another voltage.

### VOLTAGE CHANGING

A.c. power supply circuits are sometimes called a.c.-d.c. converters. Here, a.c. mains power (at 240V, 50Hz in the UK) is turned into d.c., usually at a much lower voltage.

If the mains is 240V a.c. and we need 12V d.c. what do we do about the excess voltage? One possibility would be to "drop" it in a series resistance ( $R_s$  in Fig. 8.2). This would be grossly inefficient: 228V out of the 240V would be thrown away. At a current of 1A, the resistor would burn up 228W and the equipment being powered only 12W.

Power in Watts = Volts  $\times$  Amps. In electronics we are often concerned with volts and milliamps rather than amps. The Power Alignment Chart or *nomograph* (Fig. 8.1) covers a range of common values.

If a rule is placed across Fig. 8.1 so that its edge intersects two known quantities the unknown third quantity is then read directly from where the rule intersects that column.

To return to Fig. 8.2, even if the waste were tolerable there is another snag. The d.c. output voltage varies. In real life the "load",  $R_L$  is not a resistor but a piece of equipment such as an amplifier. If the power demanded by the amplifier varies,

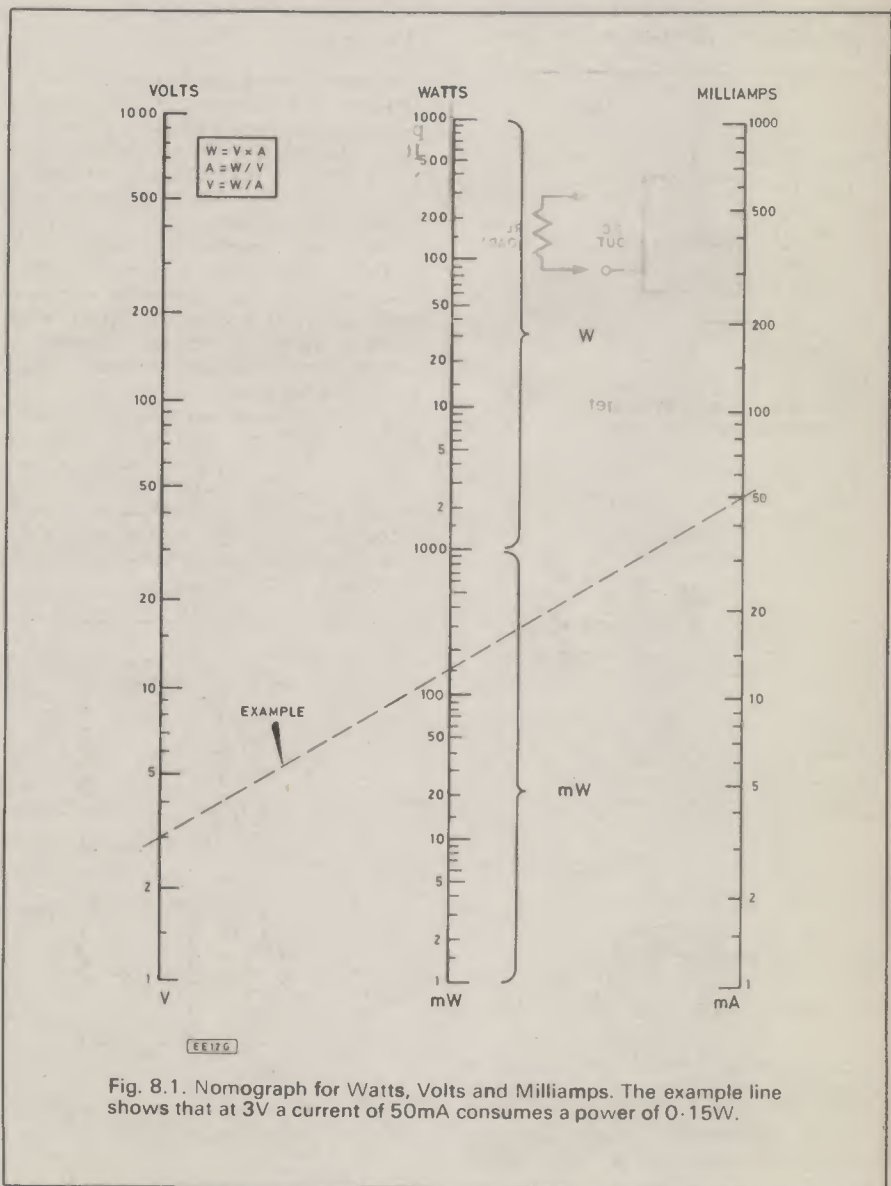


Fig. 8.1. Nomograph for Watts, Volts and Milliamps. The example line shows that at 3V a current of 50mA consumes a power of 0.15W.

then the value of  $R_L$  varies. An amplifier which requires 12V at 1A looks like  $12\Omega$ . But if its current demand falls to 0.5A it looks like  $24\Omega$ .

In the Fig. 8.2 type of circuit,  $R_S$  is so much larger than  $R_L$  that the current is forced to keep nearly constant despite such variations. The result is that the amplifier voltage nearly doubles if its effective resistance is halved.

To avoid this (which may be dangerous) we need a magic box (Fig. 8.3) which always gives out 12V, whatever the load. In other words, we need something which automatically adjusts the current drawn from the mains to suit the needs of the load, keeping the voltage supplied to the load constant.

## TRANSFORMERS

Something like this can be done, for a.c. only, with the aid of an electrical transformer. The first transformer (invented by Michael Faraday in the course

of experiments on electro-magnetism) looked like Fig. 8.4. An iron ring is provided with two "windings" of insulated wire. When an a.c. voltage is applied to the primary winding another a.c. voltage appears at the secondary winding.

The relationship between the two voltages is the same as the relationship between the numbers of "turns" on the windings. If the secondary has only one-tenth of the turns on the primary then the secondary gives out only one-tenth of the voltage.

What about the currents? Well, the secondary current is determined by the load. If the secondary voltage is 10V and the load connected to the secondary is  $10\Omega$ , then the secondary gives out 1A. The primary current is the load current divided by the ratio of primary to secondary turns. In our example, this turns ratio is 10, so when the load draws 1A the primary supplies 0.1A.

## LOSSES

If the voltage applied to the primary is 100V, then a current of 0.1A implies a power at the primary of  $100V \times 0.1A = 10W$ . The power at the secondary is  $10V \times 1A$ , which is also 10W. So a transformer changes the voltage without itself consuming any energy.

Or rather, it would, if it were perfect. Real-life transformers are imperfect. Their windings have resistance so heat is produced (and voltage dropped) when currents flow. A certain amount of current also circulates uselessly round and round the iron core.

There is also a magnetic loss. Transformers work by creating a changing magnetic field in the core. The core's job is to conduct the whole of this field to the secondary, where it operates in reverse, inducing a voltage in the secondary winding. But in real life some of this field escapes. This is waste.

Despite these losses, a well-designed transformer can be very efficient. The small, low-power transformers often used in electronics are not specially efficient, but can still be quite good. The best type (toroidal transformers) use the same shape of core as Fig. 8.4, a "doughnut".

Most mains transformers, however, have rectangular cores made of thin sheets of silicon steel called laminations, stacked to provide the required thickness. (Much less waste current circulates in a laminated core than a solid core.) In a toroidal transformer the core is wound from a long strip of silicon steel tape which has the same loss-reducing effect.

## A.C.—D.C. CONVERSION

We still have to convert the a.c. from the secondary into the d.c. for our equipment. For this we use rectifiers and reservoir capacitors.

A rectifier is an assembly of diodes. A diode is a device which allows current to flow in one direction (anode to cathode) but not in the reverse direction.

The kind of diode used as a power rectifier is able to pass large currents in the easy (or forward) direction and is able to withstand large reverse voltages which try to make it conduct "backwards". (In most rectifier circuits the peak reverse voltage, also called the peak inverse voltage or p.i.v., is twice the peak a.c. voltage at the transformer secondary.)

## HALF-WAVE RECTIFIER

A single diode (Fig. 8.5a) makes a half-wave rectifier. It lets only half of the mains-derived sinewave through to the load. During the alternate half-cycles it is reverse biased and blocks current. So the load receives "humps" of current. This is useless for powering most sorts of electronic equipment. So the humps are smoothed out by adding a reservoir

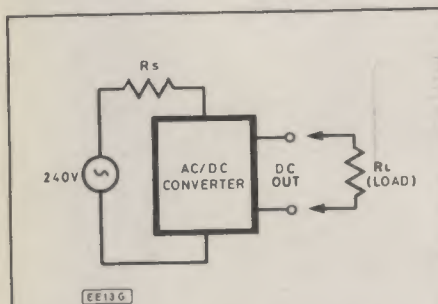


Fig. 8.2. A bad way to get rid of unwanted voltage.

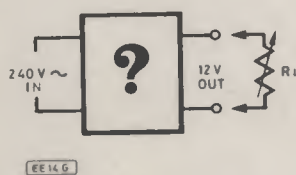


Fig. 8.3. "Magic Box" for voltage changing. The output is always 10V, whatever the size of  $R_L$ .

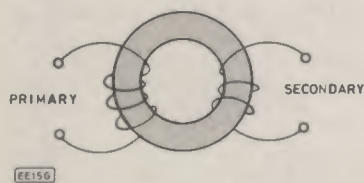


Fig. 8.4. One form of transformer.

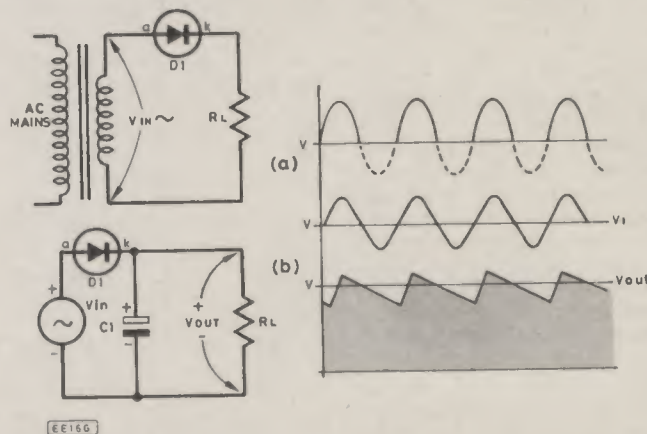


Fig. 8.5(a). Half-wave rectifier circuit, with waveforms. (b) Half-wave rectifier with reservoir capacitor.

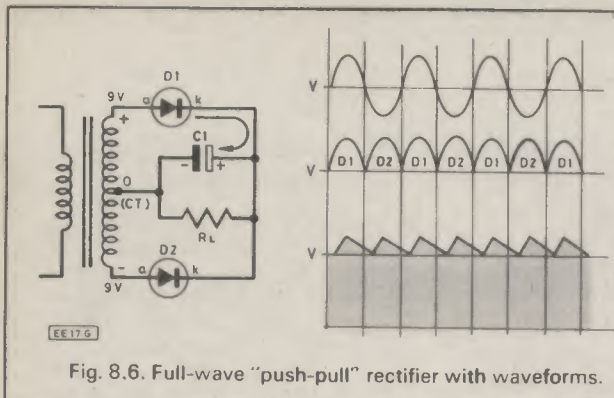


Fig. 8.6. Full-wave "push-pull" rectifier with waveforms.

capacitor C1. This charges up rapidly when the a.c. input  $V_{IN}$  is near its peak, and gives out its charge when D1 is non-conducting.

If C1 is large enough, the fall in voltage which occurs between the times when D1 conducts and tops it up is small. This up and down wobble on the d.c. output is called the ripple voltage. Since it is an a.c. effect and is applied to a capacitor it follows that a.c. must flow through C1. This is the ripple current.

In the circuits commonly used the ripple current is about one-third of the a.c. input current to the rectifier. (For design purposes, call it half and use a reservoir capacitor with at least that ripple current rating.)

The larger the capacitance of C1 the smoother the d.c.; that is, the less the ripple voltage. Reservoir capacitors (sometimes called smoothing capacitors) are usually high-value electrolytics.

## FULL-WAVE

Half-wave rectification is hardly ever used in the sort of power supply units (p.s.u.s) incorporated in mains radios and amplifiers. Full-wave rectification is the norm. Here both half-cycles of the mains are persuaded to produce d.c. of the same polarity.

One way of performing this trick is to use a mains transformer with a centre-tapped secondary (Fig. 8.6). The centre tap (c.t.) is a voltage zero or reference point.

During one mains half-cycle the voltage polarities are as shown. D1 conducts. During the next, the polarities reverse and D2 conducts. And so on. In the absence of C1 the voltage across  $R_L$  would be as in curve 2. With C1 it is as curve 3. C1 gets topped up every half-cycle. Current flows into C1 in short sharp pulses near the peak of each half-cycle.

The need for a centre-tapped winding is avoided if a bridge rectifier is used (Fig. 8.7a). This has four diodes. Only two conduct at any one time. When the mains polarity is as shown, D1 and D4 conduct, topping up C1. On the next half-cycle D3 and D2 conduct, and so on.

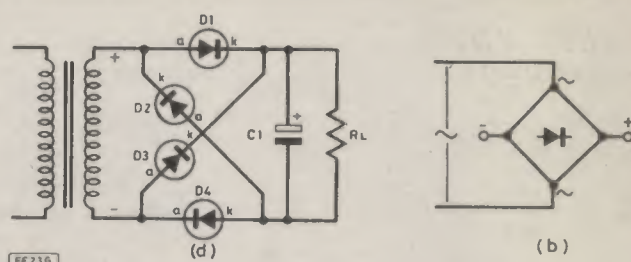


Fig. 8.7(a). Full-wave "bridge" rectifier with (b) an alternative symbol.

## RECTIFIER VOLTAGE DROP

Rectifiers are cheap, so bridge circuits (often drawn in other ways, including the "shorthand" form illustrated in Fig. 8.7b) are common. But for very low voltage outputs they are not so attractive as the Fig. 8.6 arrangement ("push-pull" rectification).

The reason is that some voltage (usually about 1V) is dropped across each diode. In a bridge circuit, where two diodes conduct together, 2V is lost and the d.c. output voltage is 2V less than the peak a.c. input. With the push-pull circuit, only 1V is lost.

On the other hand, in Fig. 8.6 each half of the secondary is idle half the time, while in Fig. 8.7 the whole secondary is used on every half-cycle.

## D.C. OUTPUT VOLTAGE

Since C1 gets topped up to nearly the peak a.c. voltage the d.c. output voltage is higher than you might expect. Transformer secondary voltages are often quoted as "r.m.s. voltage output at full load". Let's look at this.

For starters the peak of a sine wave like the mains voltage is 1.414 times the r.m.s. value. So 10V r.m.s. would yield 14.14V d.c. if there were no drop in the rectifiers. In a push-pull circuit this would fall to about 13V.

Next, the full-load output voltage means what the transformer delivers when it's working flat out, delivering as much current as it can safely do. But then the losses in the winding resistances and the core are greatest and the voltage suffers. The voltage loss can easily be 20 per cent more in the flat-out condition than when "idling". With no load, the d.c. voltage might be 16V instead of the 10V you might expect from the transformer specification.

In practice, much greater differences between full-load and no-load voltages are found in miniature transformers. The variation is called the regulation of the transformer and expressed in specifications ("specs") as a percentage:

$$\text{Regulation} = \left( \frac{\text{No-load } V - \text{Full-load } V}{\text{Full-load } V} \right) \times 100 \text{ per cent}$$

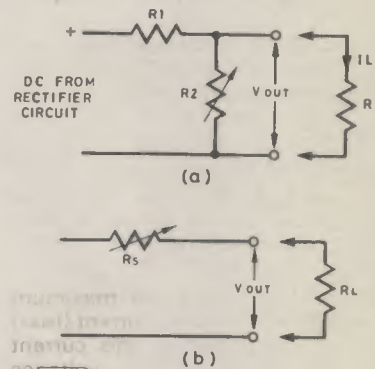


Fig. 8.8(a). Elements of a "shunt" or parallel voltage stabiliser. (b) Elements of a series stabiliser.

In complete power units the regulation is worse than the figure for the transformer alone.

## VOLTAGE STABILISERS

In many applications this variation in voltage can be tolerated. But some equipment, notably computers and most other digital equipment, the voltage must be kept at a constant level (such as 5V d.c.) even when the current demanded by the equipment is varying, and also the mains voltage.

In such cases a voltage stabilising circuit is needed. There are two basic "traditional" ways of stabilising the voltage (Fig. 8.8). In the first (a) a higher than needed voltage is applied to a voltage divider ( $R_1, R_2$ ). If the current demanded by  $R_L$  changes,  $R_2$  is automatically adjusted to compensate.

To make this sort of circuit work it must be operated at full current all the time. If  $R_L$  doesn't need it, the surplus current is absorbed by  $R_2$ . Suppose the current demanded by  $R_L$  varies from 10mA to 100mA. Then when it is 10mA the unwanted 90mA must flow in  $R_2$ . As the load current  $I_L$  rises,  $R_2$  adjusts itself to absorb less and less until, when  $I_L = 100\text{mA}$  no current at all flows in  $R_2$ .

The required automatically varying  $R_2$  is obtained by using, not a resistor, but a Zener diode. A "Zener" behaves like an

## CHECK YOUR PROGRESS

Questions on *Teach-In 84 Part 8*  
Answers next month

- Q8.1 A Zener diode is rated at 10V, 400mW:
- What is the maximum current it can safely pass?
  - When used as R2 in Fig. 8.8a, if the d.c. input is 14V what is the lowest safe value for R1?
  - If the tolerance on the Zener voltage is 10% and your Zener is on the lower limit what power does the Zener then dissipate when no load is connected across it?
  - If R1 is 10% low how much current flows? (Other conditions as in c).

- Q8.2 In Fig. 8.9, if the maximum permissible i.e.d. current ( $I_{MAX}$ ) is 30mA and at this current the combined i.e.d. voltages come to 3.3V, what is:
- The value of R1 which allows  $I_{MAX}$  to flow?
  - The power dissipated in the i.e.d.s when no load is across them?
  - The power in the i.e.d.s when a load across them draws 20mA?

- Q8.3 In a half-wave rectifier circuit like Fig. 8.5b,  $V_{IN} = 10V$  r.m.s. What is:
- The output voltage d.c. when  $R_L$  is infinite?
  - The peak reverse voltage then experienced by D1?

- Q8.4 A mains transformer has a secondary winding rated to deliver 12-0-12V r.m.s. at 100mA maximum.
- What type of rectifier circuit is it intended for?
  - If the regulation of the transformer is 20% what is the likely d.c. output off-load?

(c) What would be a suitable minimum ripple current rating for the reservoir capacitor?

(d) If the 100mA rating is "r.m.s." what is the maximum safe d.c. output current when a reservoir capacitor is used?

(e) If the centre-tap is left unconnected and a bridge rectifier connected across the whole secondary, with a reservoir capacitor, what is:

(1) The likely d.c. output voltage, off-load?

(2) The maximum permissible output current?

- Q8.5 When a reservoir capacitor is used, the rectifier diodes conduct for only a portion of a half-cycle. During this period they must provide enough current to charge the capacitor sufficiently to keep up the d.c. output. In Fig. 8.5, if the d.c. output is 100mA and D1 conducts for 10% of its "on" half-cycle, roughly how much current does it pass when conducting?

## ANSWERS TO PART 7

- Q7.1 (a) 100mA (0.1A). If all  $V_{CC}$  is dropped across the load (leaving nothing across the transistor) the current is  $10V/100\Omega = 0.1A$ .  
(b) 1W ( $10V \times 0.1A$ ).  
(c) Zero ( $0V \times 0.1A = 0W$ ). In practice there is always a small voltage across the transistor but it can be neglected in this kind of calculation.  
(d)  $V_{CC}$  shared equally between load and transistor.  
(e)  $V_{CE} = 5V$ ,  $I_C = 50mA$ . (Dissipation is then 250mW.)  
(f) 0.5mA (500 $\mu$ A).

- Q7.2 (a) 10W. If the case is at 50°C and the junction at 150°C the temperature drop inside the transistor is 100°C. This drop appears across the thermal resistance (10°C/W). For every 10°C the transistor is dissipating 1W, so in our example the dissipation (called "collector dissipation" in data sheets) is 10W.  
(b) 2.5°C/W. The thermal power supplied by the transistor to the heatsink is 10W and the temperature difference between sink and ambient air is 25°C.

- Q7.3 (a) 25W. Peak load current =  $10V/4\Omega = 2.5A$ . Note that peak current =  $(V_{CC}/2)/R_L$ , which is the same as  $V_{CC}/2R_L$ . Peak power is this times the peak voltage  $V_{CC}/2$ . So peak power is  $V_{CC}/2R_L$  times  $V_{CC}/2$  which comes to  $V_{CC}^2/4R_L$ . This formula is a handy rule of thumb for estimating the power obtainable from this type of circuit. In practice it is always an over-estimate because of inadequacies in the transistors and drive circuit.  
(b) 100W. Note that doubling the voltage quadruples the power. (See Part 8).  
(c) If the peak power is  $V_{CC}^2/4R_L$ , half this is  $V_{CC}^2/8R_L$ . This is the rule-of-thumb formula for estimating the r.m.s. sinewave power. In real-life mains-powered amplifiers, however, it may not be possible to obtain a sustained sinewave power output of half the peak power. This is because with sustained sinewave signals of large amplitude the supply voltage  $V_{CC}$  often falls and this limits the output power.

ordinary silicon diode in the "easy" direction, but it is in the reverse-biased state that it is used. Once the reverse voltage reaches a certain breakdown value the Zener conducts very freely.

If the voltage is to be stabilised at say 10V then a "10V Zener" is substituted for R2. If the voltage tries to rise above 10V the Zener conducts and the "surplus" is absorbed by R1.


By the way, all silicon diodes breakdown at some reverse voltage, but for rectifier diodes this is kept as high as possible. Zeners are made with breakdown voltages down to a few volts.

Circuit Fig. 8.8 (b) is less wasteful than (a). With no-load  $R_S$  becomes infinite so it absorbs all the surplus voltage without drawing current. At full-load,  $R_S$  is small and then also wastes little power even

though it is passing all the current.


There is no simple component like a Zener which will do the work required of  $R_S$ . Quite complex combinations of transistors, Zeners and other components are required to make efficient voltage stabilisers. Fortunately they can be obtained in the form of integrated circuits, which you can use without bothering about their inner workings.

## 8.1—SHUNT STABILISER

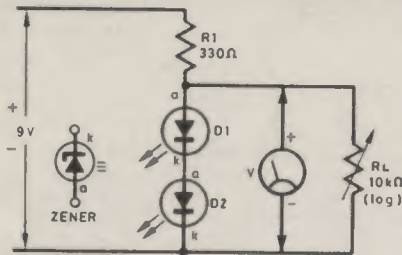

EE19G

Fig. 8.9. Shunt stabiliser experiment. The two l.e.d.s are equivalent to a Zener diode giving 3V approximate.

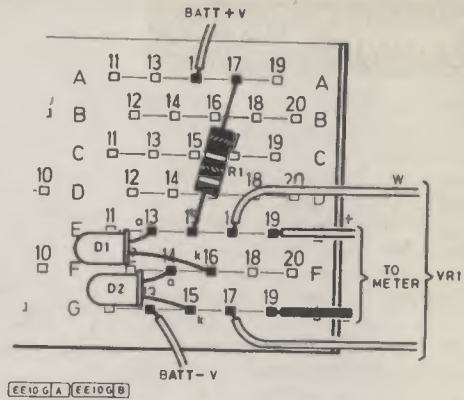

EE10G(A) EE10G(B)

Fig. 8.10. EBBO board layout for Fig. 8.9. The lead to potentiometer VR1 marked "W" should connect to the centre or wiper terminal.

## 8.2—INPUT VARIATIONS


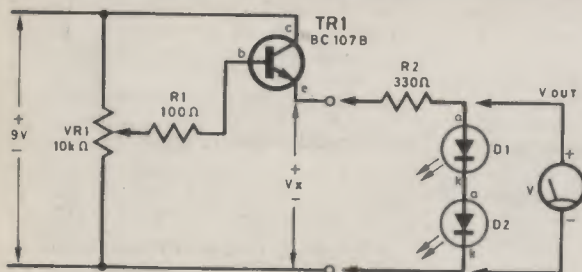



Fig. 8.11. Checking the effect of input-voltage changes.

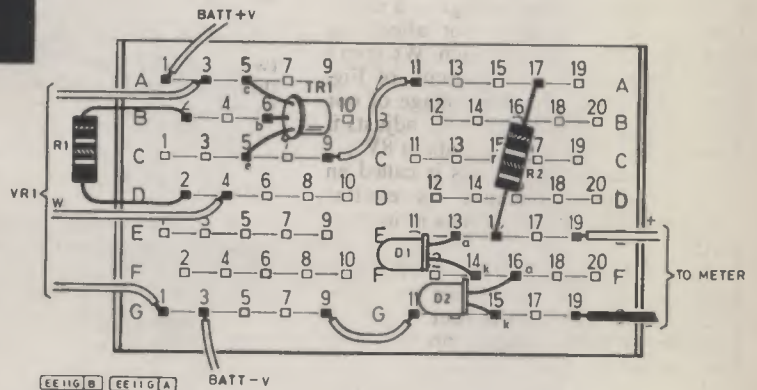

EE11G(B) EE11G(A)


Fig. 8.12. EBBO board layout for Fig. 8.11. The lead marked "W" should connect to the wiper terminal of VR1.

## 8.3—SERIES STABILISER

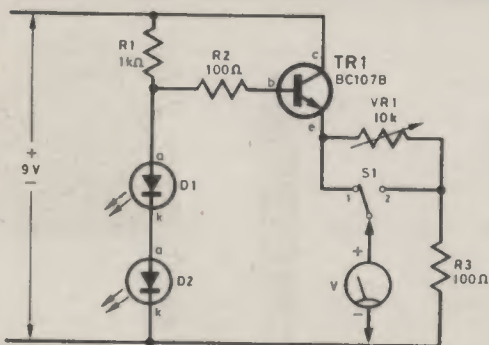

EE21G

Fig. 8.13. Simple series stabiliser.

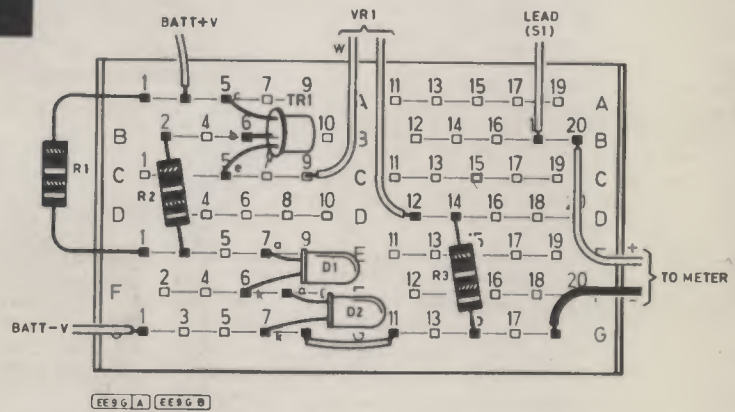

EE9G(A) EE9G(B)

Fig. 8.14. EBBO board layout for Fig. 8.13. The lead marked "W" should connect to the wiper tag of potentiometer VR1.



## EXPERIMENTS 8.1,2,3

A simple test circuit (Fig. 8.9) will demonstrate the working of the first sort of voltage stabiliser.

You haven't got a Zener? Never mind. It so happens that a l.e.d. used in the normal, "easy" direction acts like a low-voltage Zener. We'll use two in series (D1 and D2) to get a higher voltage. Variations in current show as brightness changes.

The "pot" (used here as a two-terminal variable resistance) simulates load variations (RL). At very low settings of RL the diodes are not turned on and have no effect. But at around 3V they start to take current. Increasing RL then has little effect on the output voltage.

The set-up for this experiment is shown in Fig. 8.10.

### INPUT VARIATIONS

In real life the input voltage of a mains p.s.u. varies. This must not affect the stabilised output voltage much. We aren't using the mains, but the circuit of Fig. 8.11 enables the effective voltage of our 9V battery to be reduced. VR1 adjusts it to anything between 0V and about 8V.

A transistor used like this is called an emitter follower because its emitter voltage follows any variations in its base voltage.

You should find that once the l.e.d.s light, turning R1 up further has little effect on the stabilised output. Thus the stabiliser protects against input voltage variations.

The set-up for Fig. 8.11 is given in Fig. 8.12.

### SERIES STABILISER

Your transistor and l.e.d.s can also be used to demonstrate the Fig. 8.8b type of circuit. This is called a series stabiliser because the control element (Rs) is in series with the load RL.

In Fig. 8.13, R1 and the l.e.d.s provide a stable voltage (about 3V). This is applied to the base of TR1 as a reference voltage. The load RL is R3 and VR1, and can be varied between 100Ω and 10kΩ approx. With S1 in position 1 the meter measures the output voltage VOUT. In position 2 it measures the drop (Vi) across R3; this indicates the load current since every 10mA drops 1V.

Plot a rough graph VOUT against Vi. The output voltage is stabilised reasonably well at low and medium currents.

### VARIABLE VOLTAGE

For many purposes a variable-voltage stabilised supply is needed. The essential elements of a variable series stabiliser are shown in Fig. 8.15. The differential (operational) amplifier is used to compare a tapped-off portion (VF) of the output

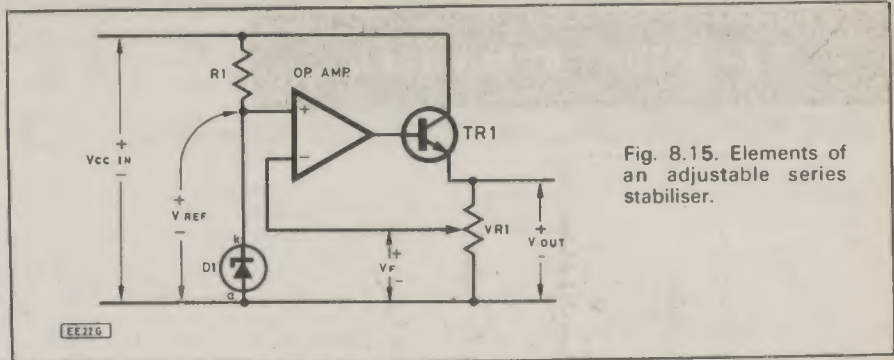


Fig. 8.15. Elements of an adjustable series stabiliser.

voltage with a reference voltage (VREF) derived from the Zener, D1.

If there is any difference the amplifier output drives the "series" transistor, TR1, the right way to reduce the difference. (Negative feedback rides again!) In other words, the circuit forces VF to equal VREF. The output voltage is then greater than VREF by the voltage attenuation factor of the voltage divider VR1.

If VF = 5V and the factor is 3 then VOUT = 15V. The circuit works only between certain limits. VOUT can't be less than VREF, and it can't be quite as high as VCC because a certain voltage is needed to operate TR1.


### SWITCHING STABILISERS

In recent years another kind of stabiliser has come into fashion. The es-


sence of the switching stabiliser, as it is called, is to keep a capacitor across the load charged to the required voltage. To do this the capacitor is "topped up" from time to time by short pulses of current. These pulses come from the unregulated supply via a series transistor. If the load demands more current the series transistor is turned on for longer periods at a time.

In practice switching regulators are rather complex. The capacitor topping-up is usually done indirectly, via an inductance, because this enables the efficiency to be increased. Integrated circuits for switching stabilisers are now available (as indeed they are for series stabilisers).

Next month: Radio Systems

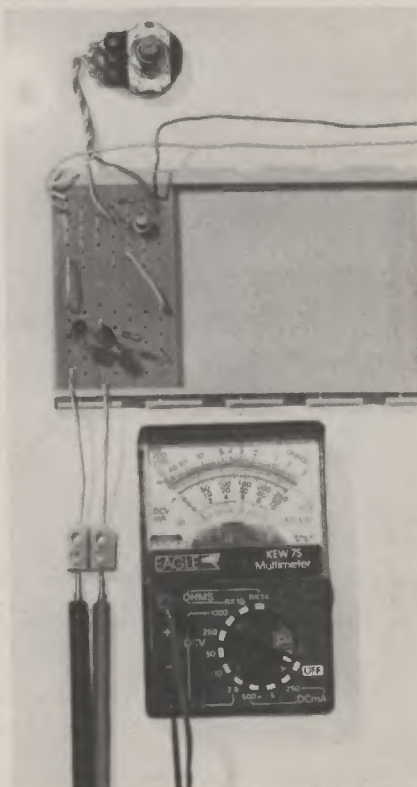

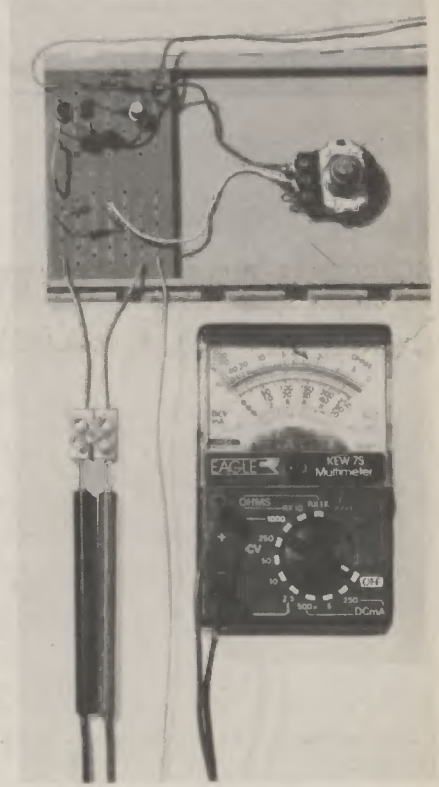The EBBO layout for input-voltage variations—Experiment 8.2.



Layout for Experiment 8.3. The "test" lead S1 is shown between meter and leads.

# FOR YOUR ENTERTAINMENT

BY BARRY FOX

## Holographic Call

Since British Telecom came under threat (now becoming reality) of privatisation, it has been loudly announcing or inaugurating something every day. The snag is that when BT has something really worthwhile to announce or inaugurate, it can pass unnoticed.

The fact that British Telecom's Phone-cards use a holographic optical pattern, rather than a magnetic strip, to control a cashless call box, is a good example. The hot news on holography was buried in a rather boring press release which many people did not read the whole way through. So the clever use of holography was never reported.

Another good example, recently, was inauguration by BT of the world's first 140M bit/s commercial optical fibre link between Luton and Milton Keynes. Although an important achievement, it sounded like old news to many people.

At the British Association's annual meeting in Brighton last August, BT told scientists that it had transmitted light over 100km of optical fibre without amplification and predicted runs of 400km. In October 1983, BT announced "the first single mode optical fibre link", following a successful test of the 27km link between Luton and Milton Keynes.

Then, in November, BT announced the "go-ahead" for a submarine cable using single-mode fibres to carry phone-calls and data under the Atlantic. These will operate at a data rate of 280M bit/s. A month later BT announced that it had signed the contract for what had previously been announced.

Despite the inevitable feeling of *deja vu*, inauguration of the Milton Keynes link bears testimony to the fact that BT made the right decision in 1980. That was when engineers switched from graded index fibre, which carries a wide beam of light prone to undesirable dispersion, to mono-mode or single-mode fibre, which carries a single light ray with no dispersion.

The switch proved far easier than anyone expected. "The problems just tumbled as people put their minds to them," says Dr. John Midwinter, of BT Research Laboratories in Ipswich. "We were astounded when we put pulses in one end and they came out with identical shape after 50 kilometres".

## Future Developments

They have, so far, kept quieter on their long-term research. They are now working on solid-state lasers with a longer wavelength, 1.5 micrometres instead of 1.3 micrometres, and with the laser tuned very tightly to a specific frequency. Longer wavelengths means less absorption by the fibre.

Tighter tuning makes it possible to send a large number of separate channels of information simultaneously down one mono-mode fibre, separated by only a slight shift in light carrier frequency. The use of tightly defined frequencies also makes it possible to use optical boosters in-

stead of converting light into electricity and then back into light again.

Until now light amplifiers have operated on a broad frequency band and introduced too much unwanted noise. With tight frequency tuning the receiver at the far end of the cable can work on the heterodyne principle just like a radio receiver; the incoming light signal beats with a beam of locally generated laser light to produce an intermediate frequency (i.f.) of much longer wavelength.

BT believes it was the first body in the world to recognise the benefits of using lasers tuned to very narrow frequency. The system is still only a laboratory tool. But commercial development would mean that even existing mono-mode fibres, like those now laid under the ground between Milton Keynes and Luton, could carry more information channels than anyone has previously thought possible.

Also the theoretical distance for mono-mode transmission, without any boost along the route, rises to 500 kilometres. In contrast to all this, France is locked into the ten-year-old technology of "Graded Index Fibre" which is not upwards compatible in the same way as the mono-mode technology on which BT has successfully gambled.

The biggest problem in bringing mono-mode fibre technology out of the laboratory and into, quite literally, the field was the difficulty of joining the fibres, every kilometre, by a wet and windy roadside. The microprocessor controlled arc-fusion jointing machine built by BT, welds two fibres, each 125 micrometres in diameter, with a light carrying core of 8 micrometres, to an alignment accuracy of 0.25 micrometres!

## Sociable Mic

Electronics shops often sell f.m. radio microphones, even though it is against the

## War Games

The film *War Games* is now famous for its scary suggestion that anyone with a home computer could gain access by telephone to one of the computers used by the military. Of course, *War Games* goes over the top, but it is true that any computer which is programmed for telephone access cannot be 100 per cent safer from unauthorised connection.

The more complicated the password procedure, the more difficult and time consuming it is for an authorised computer to gain access. So password procedure may not be too complicated. Also the basic idea of the film, that a defence computer will be accidentally triggered into playing war games for real, may not be as absurd as the military apologists have professed.

Take the case of the Thorn-EMI company, Simtec, who recently developed a war game simulator for the navy. The Simtec system is intended for training sonar and radar operators, and crews in charge of weapon systems. It can simulate a war in an area of

over four million square miles, with up to 100 land vehicles, submarine or aeroplanes. Each of the vehicles can be assigned characteristics from a selection of 250 different classes, for instance: bomber, fighter, helicopter and so on.

There is nothing new in this, although the Simtec simulator obviously relies on a bigger and more powerful computer system than most. The sting is in Thorn-EMI's own description of the system. I quote verbatim:

"These trainers inject simulated responses into the actual sensor/weapon system. Operators and command teams are at their "real" battle stations and so train in a situation very close to realistic battle conditions."

In other words the Simtec war game computer actually tells the ship's missile crews how, when and where to fire. Let's hope that the system doesn't develop a fault, and doesn't have telephone inputs that can be accessed by a kid with a home computer.

Obviously I'm not going to recommend that anyone uses an f.m. radio mic. in Britain. But there's no reason why you shouldn't use one abroad and their disadvantage (tendency to interfere with other people's radios) can be turned to your advantage. Here's how.

Imagine you are laying on a sunny beach, on holiday. Quite a few people on the beach are quietly listening to music on headphones from cassette tape. Then along comes an unsociable sunbather with an ordinary portable radio and sits down beside you. There are few worse sounds in the world than a portable radio turned up too loud so that it distorts music that you don't want to hear anyway.

To kill it, all you have to do is quietly switch on an f.m. radio mic. and tweak the tuning screw until its transmission frequency hits the same number as the rogue receiver. There is then either feedback or distortion. Before long the unsociable sunbather either changes stations, in which case you re-tune your mic., or gives up and switches off, in which case you've won.

# SHOP TALK



BY DAVE BARRINGTON

## Catalogues Received

This month only two catalogues, from Marco Trading and Electrovalue, have landed on the "Shoptalk" desk. Also news of the latest **Ambit** components catalogue was delivered, but alas no catalogue accompanied the release!

The TV service repair engineer will find a range of voltage-dependent resistors, TV replacement droppers or resistor networks and valves all included in the 109-page Marco Trading mail order components catalogue.

Also, there's an excellent range of plugs and sockets, including BNC and coaxial types. Aerial amplifiers and a u.h.f./v.h.f. colour bar generator are also listed.

The semiconductor section is spread over 35 pages and covers a comprehensive range of transistors, bridge rectifiers and integrated circuits, including CMOS devices.

Amongst the soldering equipment is an Antex 12V 25 watt soldering iron ideal for car owners. This iron comes with approximately 4 metres of cable terminated with heavy duty clips and is easily clamped on the battery normally fitted to any car, boat or caravan.

All prices of goods are contained on the page of entry but are exclusive of VAT, which must be added to the total order. A 30p credit note is included with each catalogue.

Copies of the Marco Trading catalogue cost 65p each and can be obtained from: Marco Trading, Dept EE, The Maltings, High Street, Wem, Shropshire, SY4 5EN.

Most of our readers will no doubt be familiar with the excellent component service offered by Electrovalue and will need no persuasion to obtain their latest A-Z product list.

If in doubt, we can only point out that this 36-page catalogue lists items ranging from cases and discrete components to meters and printed circuit materials. This is without listing the numerous computer equipment stocks.

Copies of the Electrovalue A-Z product list are available free of charge from: Electrovalue Ltd., Dept EE, 28

St Judes Road, Englefield Green, Surrey, TW20 0HB.

## Ace Buy

Some good news for owners of the Jupiter Ace home computer who felt left out in the cold by the sudden demise of Jupiter Cantab Ltd.

It is now back on sale, by mail order only, from **Boldfield Limited Computing**. Existing owners will be pleased to note that the Jupiter 16K RAM packs and software are also available. Further titles will be added in the near future.

The best news is that the prices have been drastically cut! The Ace, with power supply, 182 page manual, demonstration cassette, leads, and a 12 month guarantee, is only £26. The 16K RAM pack costs £20 and all the software cassettes are £3 each. But add VAT and £3 towards postage and packing.

As a combined deal, you can purchase the Ace with a 16K RAM pack for £44 plus VAT. This would have set you back £124.90 previously.

For more information write to: **Boldfield Limited Computing, Dept EE, Sussex House, Hobson Street, Cambridge.**

## CONSTRUCTIONAL PROJECTS

### Simple Loop Burglar Alarm

The quad 2-input NAND gate i.c., type number 4011, used in the *Simple Loop Burglar Alarm*, carries the designation **B** after the numerals.

The use of this letter signifies that it has a buffered output and this type should be used in this circuit. Some devices may carry the letters **BE**, these types will work quite satisfactory in the circuit.

It is quite possible that an un-buffered type, designated **UBE**, will work, but they have not been tried in the prototype model.

The key switch or lock switch should not cause any buying problems, and is stocked by most component suppliers. However, if readers do experience difficulties in locating a source, it is currently listed by Maplin (code: FH40T), Greenweld, Rapid and Enfield Electronics.

## Experimenter's Power Supply

The operational amplifier, type  $\mu A759$ , used in the *Experimenter's Power Supply* has similar characteristics to the 741 but features a power output stage capable of providing up to 325mA output current into a 50-ohm load. This advice appears to be only available from RS Components, Order code 303-258.

It should be noted that RS will not supply to the general public but must be ordered through a local stockist.

## Microcomputer Interfacing Techniques

The motors and gearbox used in our model for the *Computer Controlled Vehicle* was obtained from Greenweld Electronics.

As the motors and gearbox come as one complete unit, this appears to be the "best buy" at £5.95, and to be recommended. They are also able to supply the wheels (two for £1.30).

These motorised gearboxes, originally used in a mobile model tank, have two 3-volt motors linked by a magnetic clutch. The gearing arrangement reduces the final drive speed to about 50 r.p.m.

Full details of these units can be obtained from: **Greenweld Electronics, Dept EE, 443D Millbrook Road, Southampton SO1 0HX.**

The mains transformer (code 207-199) and the infra-red slotted opto-switches (code 306-061) are available from RS Components. These items must be purchased through a bona fide dealer as RS will not supply components to the general public.

A similarly rated mains transformer could be used, but the printed circuit board layout would probably need to be changed to cater for the different pinning arrangements.

Most of our advertisers stock micro-switches and types with an operating lever should be specified when ordering.

## Vari-cap A.M. Radio

The only component called-up in the *Vari-cap A.M. Radio* which could cause purchasing problems is the Vari-cap diode D2/3.

This is a dual-diode device in a single package and is stocked by **Ambit International**. The Vari-cap type KV1236 should be purchased and carries the stock number 12-12365.

## Mastermind Timer

A suitable "earpiece" called for in this month's "Black Box" project—*Mastermind Timer*, is available from Magenta, Rapid and Enfield Electronics.

We do not expect any component purchasing problems for the *Extra 1K RAM* for the *Acorn Atom* or the *Extra Utility Prom*.

Please mention  
**EVERYDAY ELECTRONICS**  
when replying to  
products mentioned  
on this page  
and to  
**Classified Ads**

# MICROCOMPUTER INTERFACING TECHNIQUES

INCLUDING MANY USEFUL CONSTRUCTIONAL PROJECTS

PART 11: COMPUTER CONTROL OF SMALL VEHICLES

BY J. ADAMS B.Sc., M.Sc. & G. M. FEATHER B.Sc.

THE intrinsic ability of the micro-computer—to execute a specific set of stored instructions—allied with its capability to interface with a wide range of peripheral devices has formed the basis of this series of articles.

In particular the reader will be aware that the microcomputer, in conjunction with external circuitry, is capable of accessing data, corresponding to both digital and analogue quantities. Such information may be used to modify or control the execution of output signals to additional electronic devices.

This month's article will deal with another application of this technique to control small motor driven vehicles.

Such vehicles are widely employed in "Technology" courses and several versions, differing both in general philosophy and mode of operation, are available. This article sets out to describe the underlying principles and construction of a simple "buggy" which will offer at least some of the facilities of its commercial counterparts.

## TRACTION MOTOR CONTROL

In order that reasonable precise positioning of the vehicle can be achieved it is of course essential that the operation of the traction motors is carefully controlled by the microcomputer.

Various techniques have been devised in order to achieve this end and an effective, albeit rather expensive, solution is the employment of stepper motors for this purpose. Readers interested in developing a system along these lines should refer to *M.I.T. Part 5* (November 1983) in which the control of such motors was described.

## FEEDBACK

If it is intended to employ d.c. motors to provide traction for the vehicle, then some form of feedback is essential.

In the system to be described, such information is derived by opto-electronic sensing of the number of revolutions of the driving wheels. Assuming that slipping of the wheels does not occur, this arrangement is capable of providing

reasonable precise information concerning the vehicle's operations. These include forwards, backwards and rotational motions.

## COLLISION DETECTORS

Two other "sensors" are provided; these are collision detectors and will provide signals in the event of the vehicle encountering obstacles in its path whilst moving either forwards or in the reverse direction.

On receipt of such information, appropriate software can output control signals to the traction motors in order that the obstacle might be negotiated.

## CIRCUIT DESCRIPTION

A complete circuit diagram of the Interface/Motor Control and associated circuitry is given in Fig. 11.1 and the reader should consult this.

Output signals from and input signals to the microcomputer user port are buffered by IC1, a 74LS244 octal non-inverting buffer. A pin-out diagram of this is shown in Fig. 11.2, which also shows the internal arrangement of the individual buffers.


Each employs Schmitt trigger circuits (which, insofar as signals from the sensors is concerned, is necessary) and all buffers offer tri-state outputs. Pins 1 and 19 provide control of the tri-state facility and are active low; in this application. The devices are permanently enabled by grounding these control inputs.

Inputs 1A1, 1A2, 1A3, 1A4 to IC1 are used for motor control information from the user port, corresponding respectively to starboard motor forward, starboard motor reverse, port motor reverse and port motor forward.

Associated outputs from IC1, 1Y1, 1Y2, 1Y3 and 1Y4 are routed directly to four of the inputs of IC2, a 7-stage Darlington driver i.c., the collectors of which drive the motor control transistors TR1 to TR8.

## MOTOR OPERATION

Fig. 11.3 shows a simplified version of this section of the circuit for one of the motors, TR1 to TR4 having been

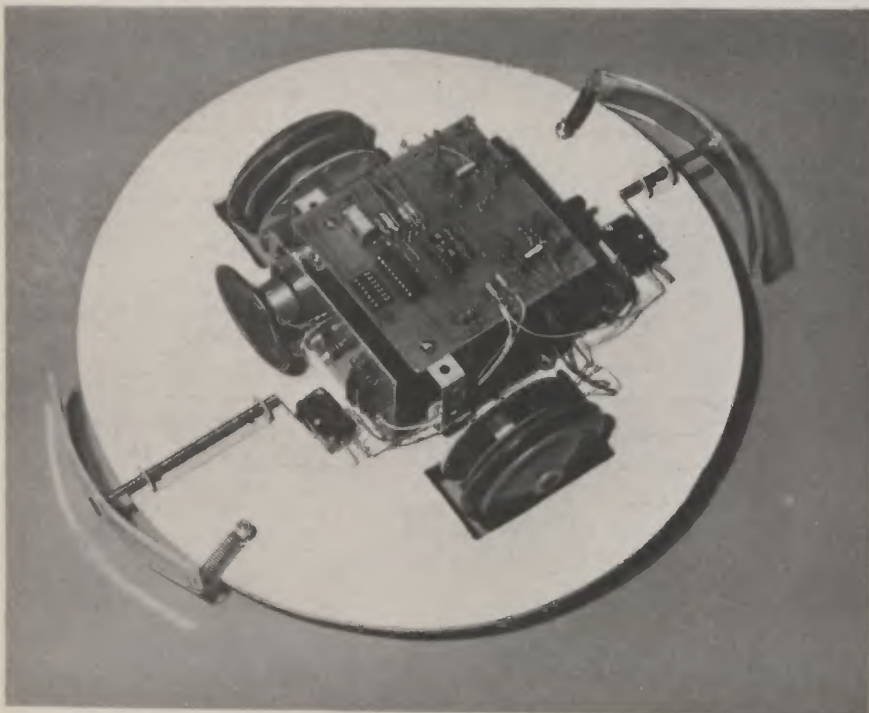

represented as simple switches *S1*, *S2*, *S3*, *S4*.

*S1* and *S4* are closed, then the motor will run in one direction, whilst opening these and closing *S2* and *S3* will reverse the direction of the motor. If either *S1* and *S3*, or *S2* and *S4* are open or closed, then the motor will stop. One motor can thus be controlled by a 2-bit binary number as shown in Table 1.

**Table 1**

Switch State		Result
S1/S3	S2/S4	
0	0	STOP
0	1	FWD
1	0	REV
1	1	STOP

0=open 1=closed

For control of both motors, a 4-bit number is required and this is derived from appropriate user port control lines configured for output. This is discussed later in the software section.

The drive motors are likely to produce some rather spurious pulse on their supply lines and, for this reason, a separate 7.5V supply for them is derived in the power supply section of the circuitry.

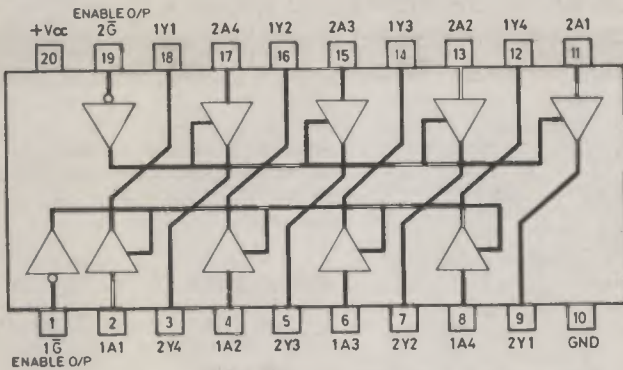


Fig. 11.2. Pin-out details of the 74LS244 tri-state octal buffer.


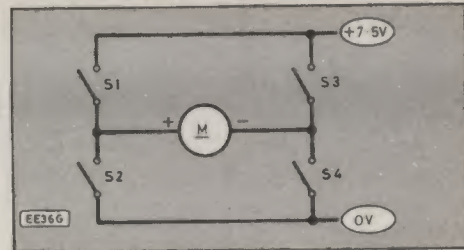


Fig. 11.3. Switch representation of the motor drive circuit.

Fig. 11.1. Circuit diagram of the Interface/Motor Drive section of the Computer Controlled Buggy.

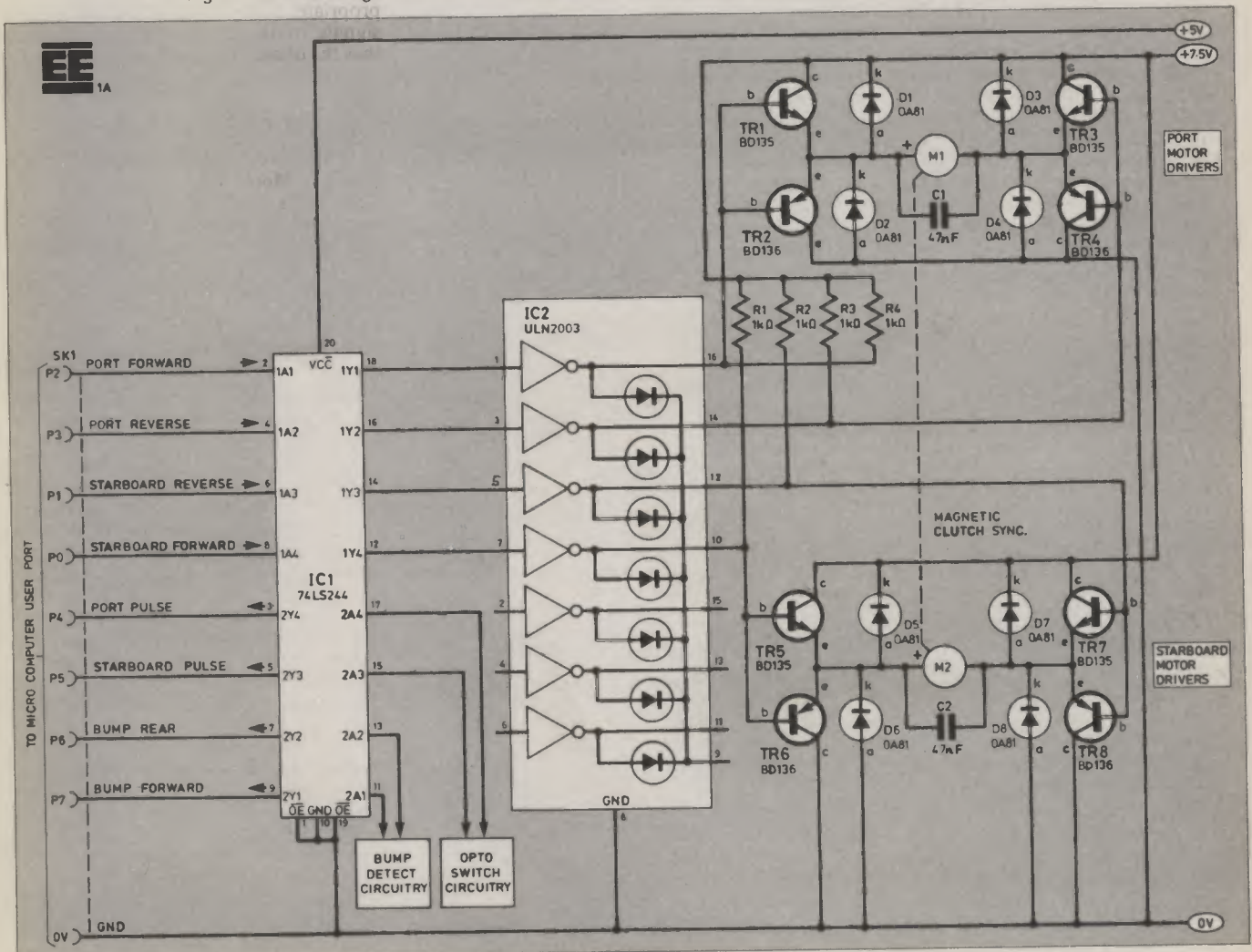

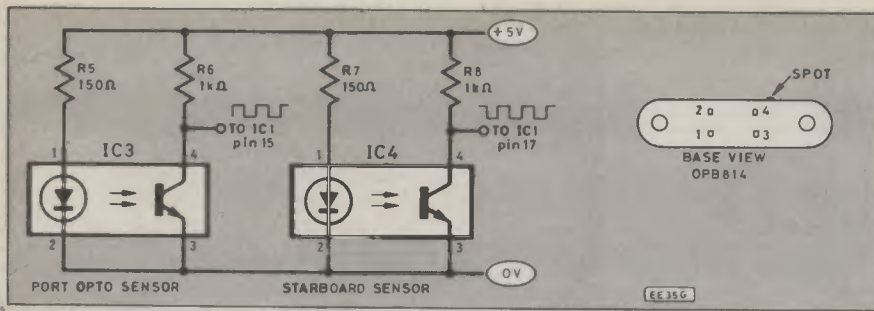


Fig. 11.4. Infra red opto-switch sensing circuit.

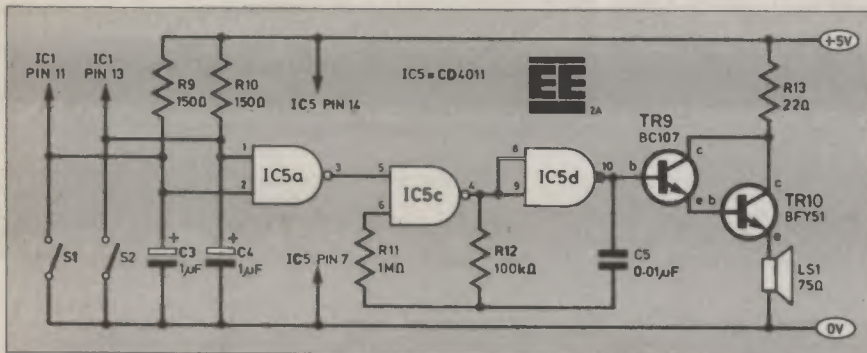


Fig. 11.5. Collision sensing/warning circuit diagram. The switches S1 and S2 are microswitches which form part of the "bumper" mechanism.


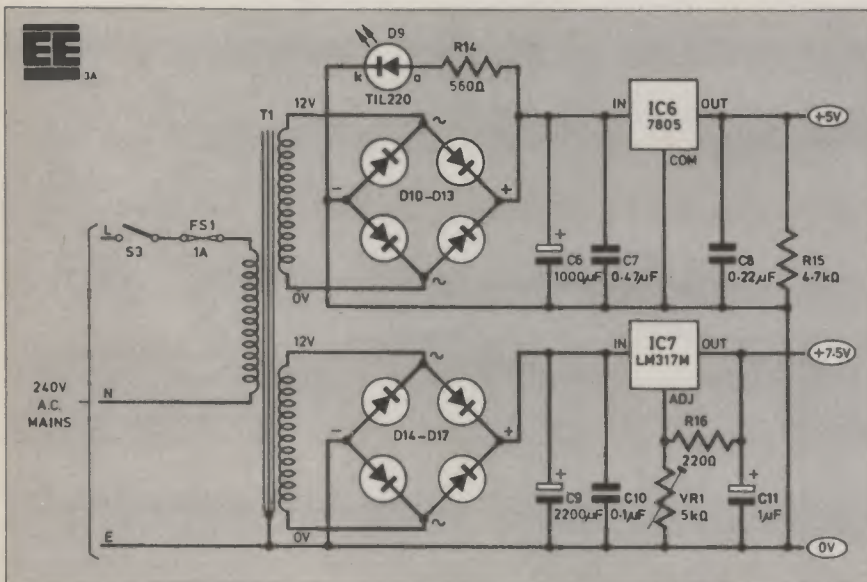


Fig. 11.6. Circuit diagram for a suitable power supply of the "buggy".

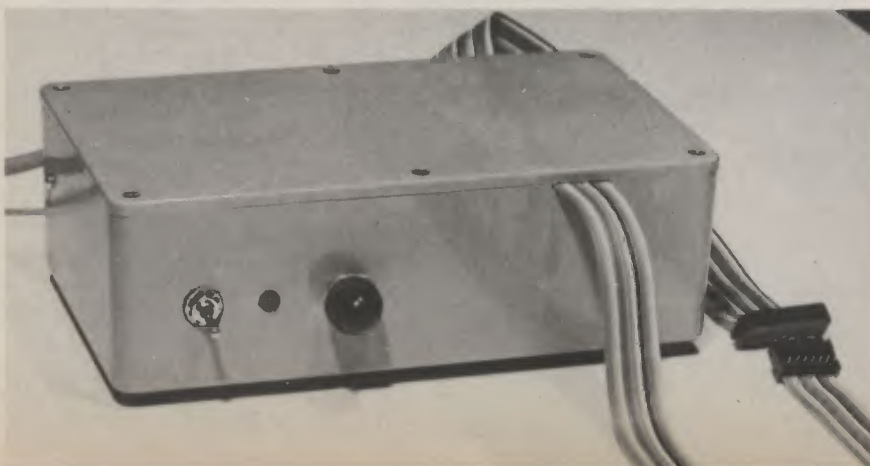Completed prototype power supply showing the "umbilical cord" which connects to the micro user port and the buggy (SK1). Note the slots in the case sides for the ribbon cable.



Diodes D1 to D8 provide protection against switching transients for the drive circuitry.

## ROTATION SENSING

The final drive shafts from the motor/gearbox assembly are provided with rotational sensors. Each shaft carries a slotted disc which rotates in the gap of a slotted opto-switch. The pulse output from the phototransistor section of these devices is applied to two of the inputs of the 74LS244 buffer and the corresponding outputs are routed to the user port P4/P5 lines. Suitable software can provide positional information perhaps to be displayed on the VDU. The l.e.d. sections of the opto-switch derive their power from the +5V supply for the main board. Fig. 11.4 shows the circuitry of this section of the vehicle.

## COLLISION DETECTION

Forward and rear mounted micro-switches, S1 and S2, provide collision signals. The associated circuitry is shown in Fig. 11.5.

Under no collision conditions, these switches, S1 and S2, are open and the associated buffer inputs are pulled up to logic 1 by resistors R9 and R10. A collision pulse pulls either input down to logic 0 and the corresponding buffer output of IC1 also goes low. These signals are applied to user port lines P6 and P7 and IC1.

A subsidiary "on-board" circuit also provides an audible indication of a collision. This consists of IC5 and its associated circuitry. This i.c. is a CD4011 CMOS quad 2-input NAND gate.

One gate, IC5a, is used to detect a collision sensor output going low and reference to the NAND gate truth table given below will reveal that this condition results in the output of that gate going high. Two of the remaining three gates are wired as inverters in an astable circuit, oscillating at approximately 1kHz, the output of the first gate providing a logic 1 to initiate operation of the astable.

Transistors TR9 and TR10 form a conventional Darlington pair circuit to drive the small loudspeaker, LS1.

NAND gate truth table


Inputs		Output
A	B	
0	0	1
0	1	1
1	0	1
1	1	0

## POWER SUPPLIES

Fig. 11.6 shows the circuit diagram of the power supply section.

The power supply circuitry is fairly conventional; fixed and variable voltage regulators IC6 and IC7 providing respectively the +5V TTL and +7.5V motor drive supplies. Preset VR1 gives a measure of speed control for the vehicle and should be adjusted to provide the required voltage up to 7.5V.

# COMPUTER CONTROLLED BUGGY CONSTRUCTION

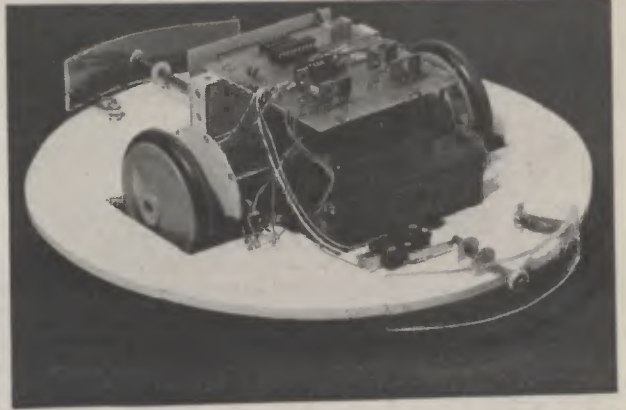

## INTERFACE DRIVER BOARD

The prototype employed three printed circuit boards in its assembly, two in the vehicle and the third in the case containing the power supply circuitry.

The actual-size master p.c.b. pattern for the board containing the interface and motor drive circuitry is shown in Fig. 11.7. This board is available from the *EE PCB Service*, Order code 8405-02.

The layout of the components on the top side of this board is shown in Fig. 11.8. Begin by fixing the Veropins to the board to allow easy interconnection to other boards/components in the system. Next mount the i.c. sockets and link wires followed by the transistors and diodes. Pay special attention to the orientation of these devices when mounting to the board.

There are four resistors required in the circuit and all of these are contained in a single-in-line package (s.i.l.). This package may be mounted either way round.

## COLLISION SENSING/WARNING BOARD

Most of the components forming the collision sensing and warning circuitry of Fig. 11.5 are mounted on a printed circuit board, the actual-size master pattern of which is shown in Fig. 11.9. This board is available from the *EE PCB Service*, Order code 8405-03.

The layout of the components on the top side of this board is shown in Fig. 11.10. Assemble the components as indicated making sure to use a d.i.l. socket to house IC5. Do not insert this device until all construction is complete. Once again use Veropins where indicated to facilitate easy wiring up later.

## POWER SUPPLY

The power supply circuitry is housed in a plastics box measuring 215 x 130 x 85mm. Most of the components are fitted to a printed circuit board and the master pattern (actual-size) for this p.c.b. is

## COMPONENTS

Approx. cost £35 excluding boards  
Guidance only

### Resistors

R1-4	1k $\Omega$ 8-pin s.i.l. package
R5	150 $\Omega$
R6	1k $\Omega$
R7	150 $\Omega$
R8	1k $\Omega$
R9,10	150 $\Omega$
R11,12	100k $\Omega$
R13	22 $\Omega$
R14	560 $\Omega$
R15	4.7k $\Omega$
R16	220 $\Omega$
All $\frac{1}{4}$ W carbon $\pm 5\%$ tolerance unless specified otherwise	

See Shop Talk page 313

### Capacitors

C1,2	0.047 $\mu$ F
C3,4	1 $\mu$ F 10V elect.
C5	0.01 $\mu$ F
C6	1000 $\mu$ F 25V elect.
C7	0.47 $\mu$ F
C8	0.22 $\mu$ F
C9	2200 $\mu$ F 25V elect.
C10	0.1 $\mu$ F
C11	1 $\mu$ F 10V elect.
C12	100nF

### Semiconductors

D1-8	OA81 small signal germanium diode (8 off)
D9	TIL220 5mm red l.e.d.
D10-13	1A Bridge (REC 70)
D14-17	BD135 silicon npn
TR1,3,5,7	BD136 silicon pnp
TR2,4,6,8	BC107 silicon npn
TR9	BFY51 silicon npn
TR10	74LS244 low-power Schottky TTL octal non-inverting buffer with tri-state outputs
IC1	ULN2003 7-stage Darlington driver i.c.
IC2	Slotted Infra-red opto switch (2 off) (RS 306-061)
IC3,4	

### IC5

### IC6

### IC7

### Miscellaneous

#### S1,2

#### S3

#### VR1

#### T1

#### LS1

#### M1/2

#### FS1

CD4011 CMOS quad 2-input NAND gates  
7805 +5V 1A monolithic voltage regulator i.c.  
LM317M adjustable positive 0.5A voltage regulator i.c.

standard lever microswitch (2 off)  
miniature mains on-off toggle  
5k $\Omega$   
mains primary/0-12V, 0-12V 500mA secondaries (RS 207-699)  
miniature moving coil speaker, 75 ohms impedance  
motorised gearbox assembly (Greenweld)  
1A 20mm with panel mounting holder

**Printed circuit boards:** Interface/drive board, single-sided size 115 x 100mm, *EE PCB Service*, Order code 8405-02; Collision sensing/warning board, single-sided size 103 x 69mm, *EE PCB Service*, Order code 8405-03; power supply board, single-sided size 160 x 90mm, *EE PCB Service*, Order code 8405-04; plastics case type, size 215 x 130mm; 85mm diameter, 2mm thick Perspex discs (for position sensing) (2 off); brackets for board support; ribbon cable to connect to micro user port with appropriate SK1; 3-core lightweight mains cable to connect power supply unit to vehicle; 3-core mains cable; material for base of buggy; general-purpose hook-up wire, stranded, various insulation colours.

# INTERFACE AND MOTOR DRIVE BOARD


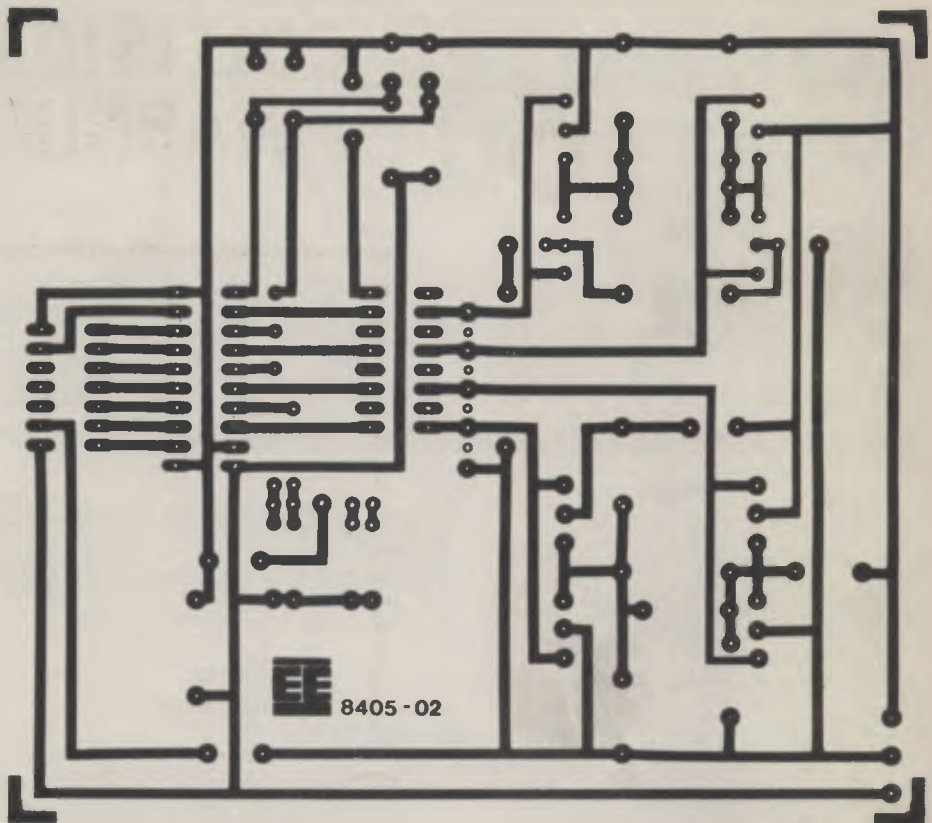



Fig. 11.7. Actual-size master pattern for the Interface/Motor Drive. This board is available from the *EE PCB Service*, Order code 8405-02.

Fig. 11.8. Layout of components on the topside of the Interface/Drive board. The leads terminated in letters G,H,I,K, go to the bumper microswitches S1 and S2. SK1 is the inter-connecting socket for the buggy and micro-computer, via the power supply unit. Refer to the circuit diagram for wiring to the plug.

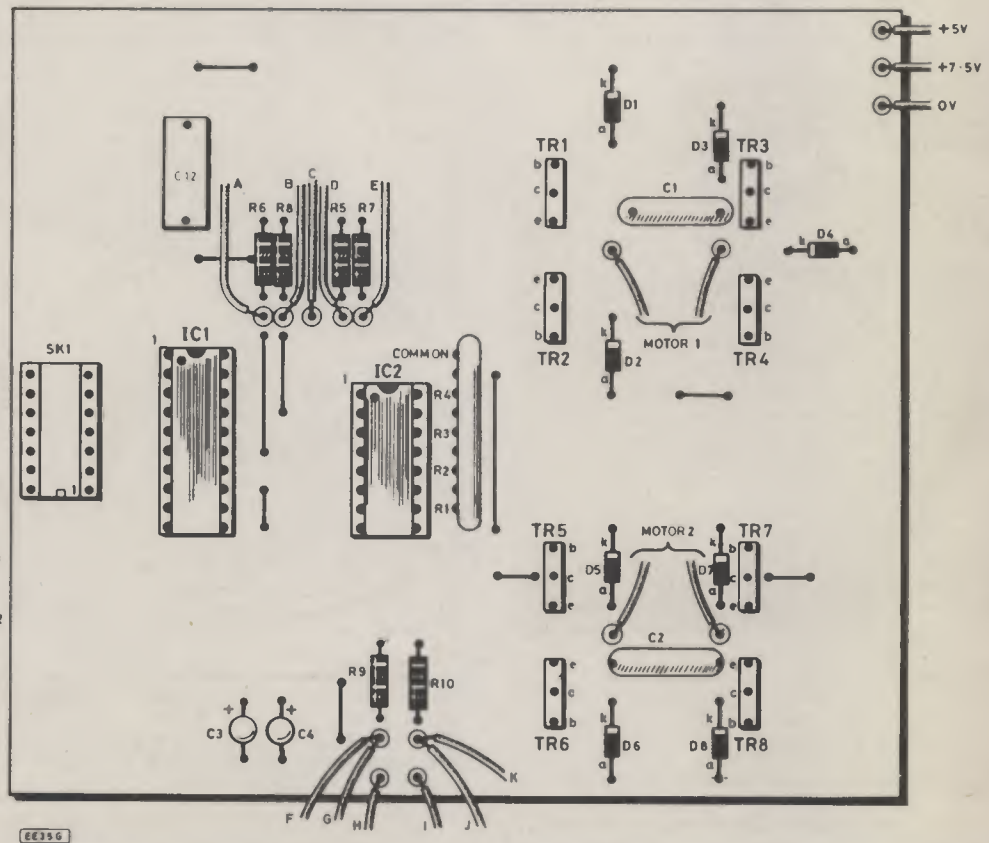



# COLLISION SENSING WARNING BOARD

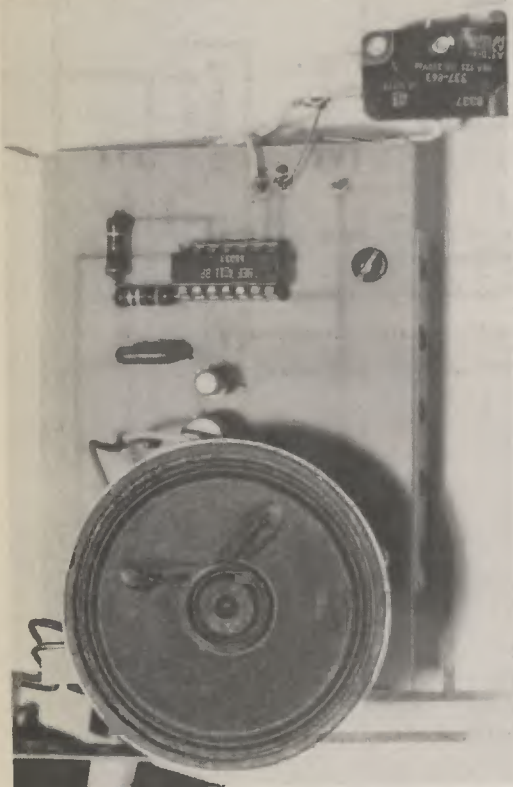

Completed prototype Collision Sensing/Warning board. One microswitch can be seen in the top right.


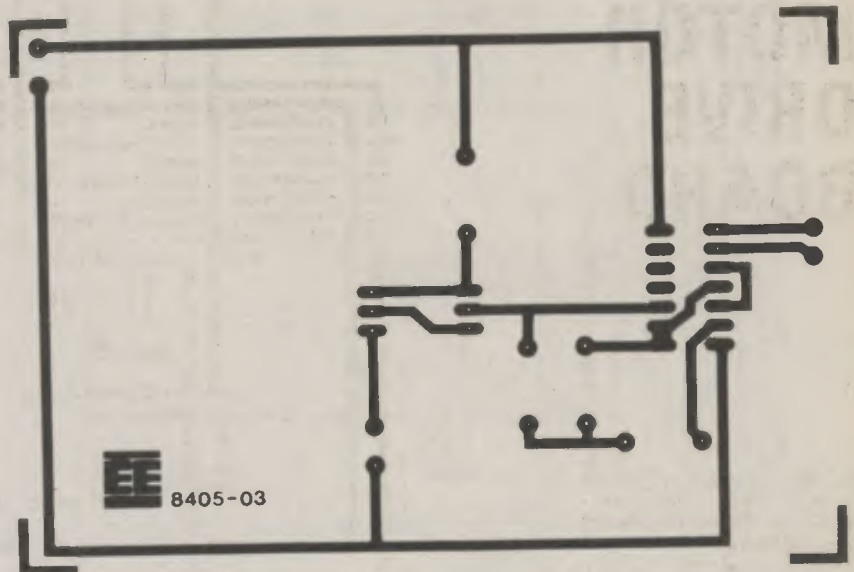


Fig. 11.9. Actual-size master pattern for the Collision/Warning board. This board is available from the EE PCB Service, Order code 8405-03.

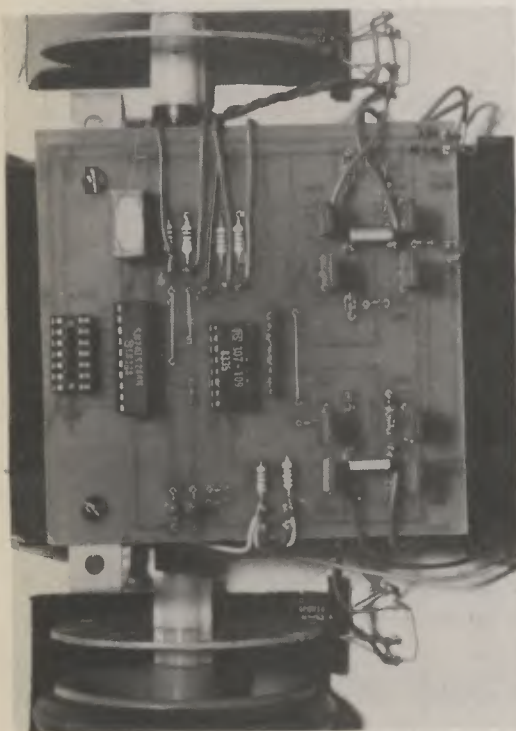

Completed prototype Interface and Motor Drive board.

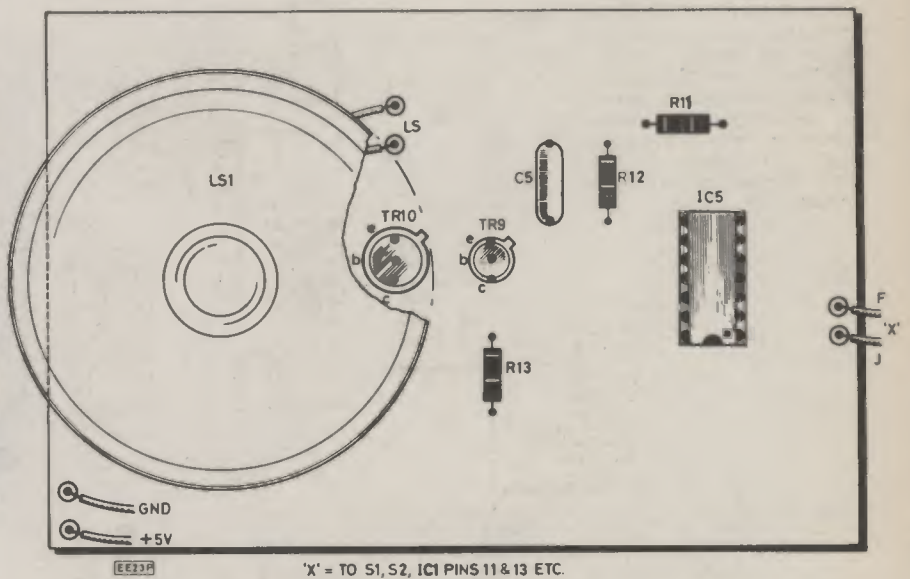


Fig. 11.10. Layout of components on the topside of the Collision/Warning board. The loudspeaker is held in position with impact adhesive.

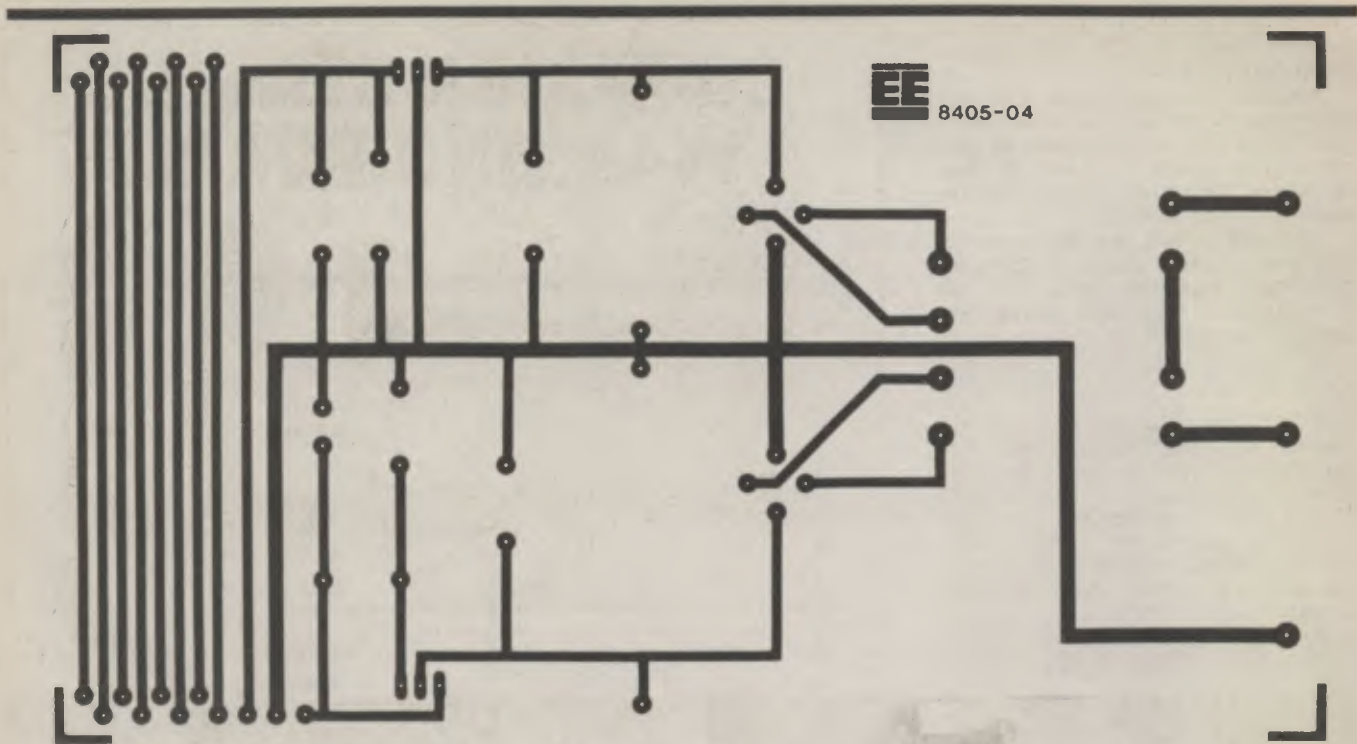


Fig. 11.11. Actual-size master pattern for the power supply board. This board is available from the *EE PCB Service*, Order code 8405-04.

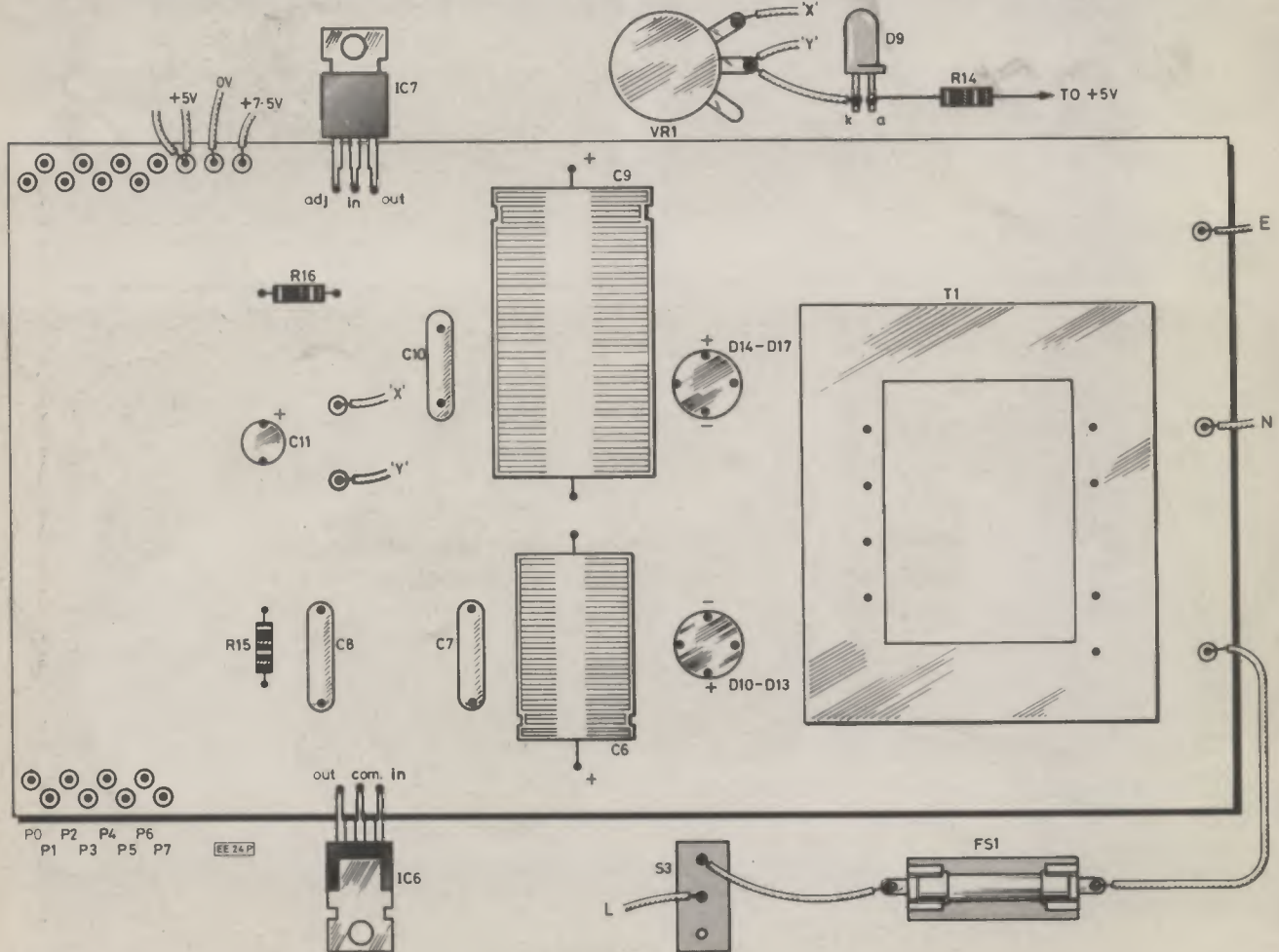


Fig. 11.12. Layout of components on the fopside of the power supply board and interwiring to case mounted components.


shown in Fig. 11.11. This board is available from the *EE PCB Service*, Order code 8405-04.

Assemble the components according to the topside layout given in Fig. 11.12. Next prepare the case to accept the case mounted components and then fit these items. Fix the assemble board into the case and wire up as shown.


Thoroughly check over the assemblies and when satisfied secure these to the mechanical equipment detailed in the photographs or some other arrangement that may be required.
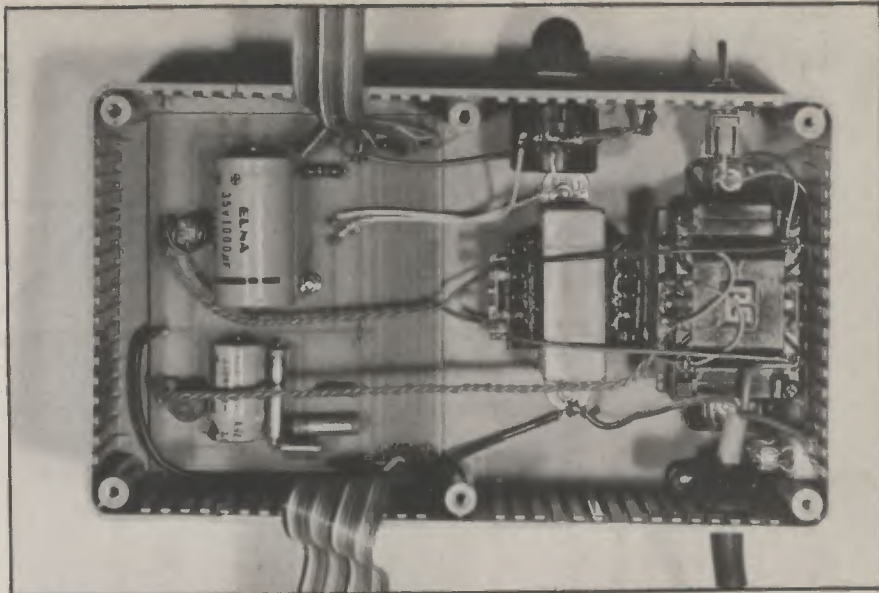
## CABLES

Attach suitable lengths of cable to the vehicle to reach the power supply box and the micro user port outlet. The latter cable should be suitably terminated to mate with the micro user port. Constructors are referred to the pin assignment tables and diagrams for the user ports of the micros catered for in this series which appeared in *M.I.T. Part 1*.



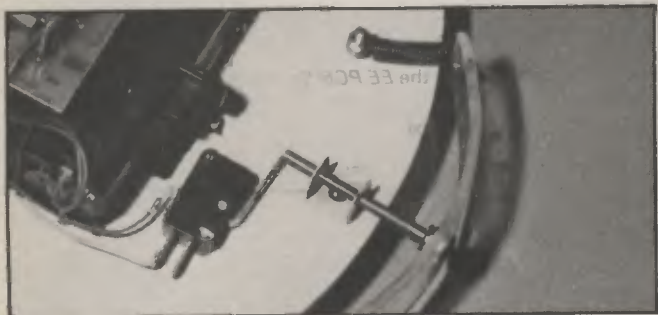Early prototype of the power supply unit. This model shows two mains transformers which have been replaced by a single unit. The pcb has been extended to accept the new transformer.




Close-up view of the bumper mechanism.



Close-up view of the sensor opto-switch and sensor disc.

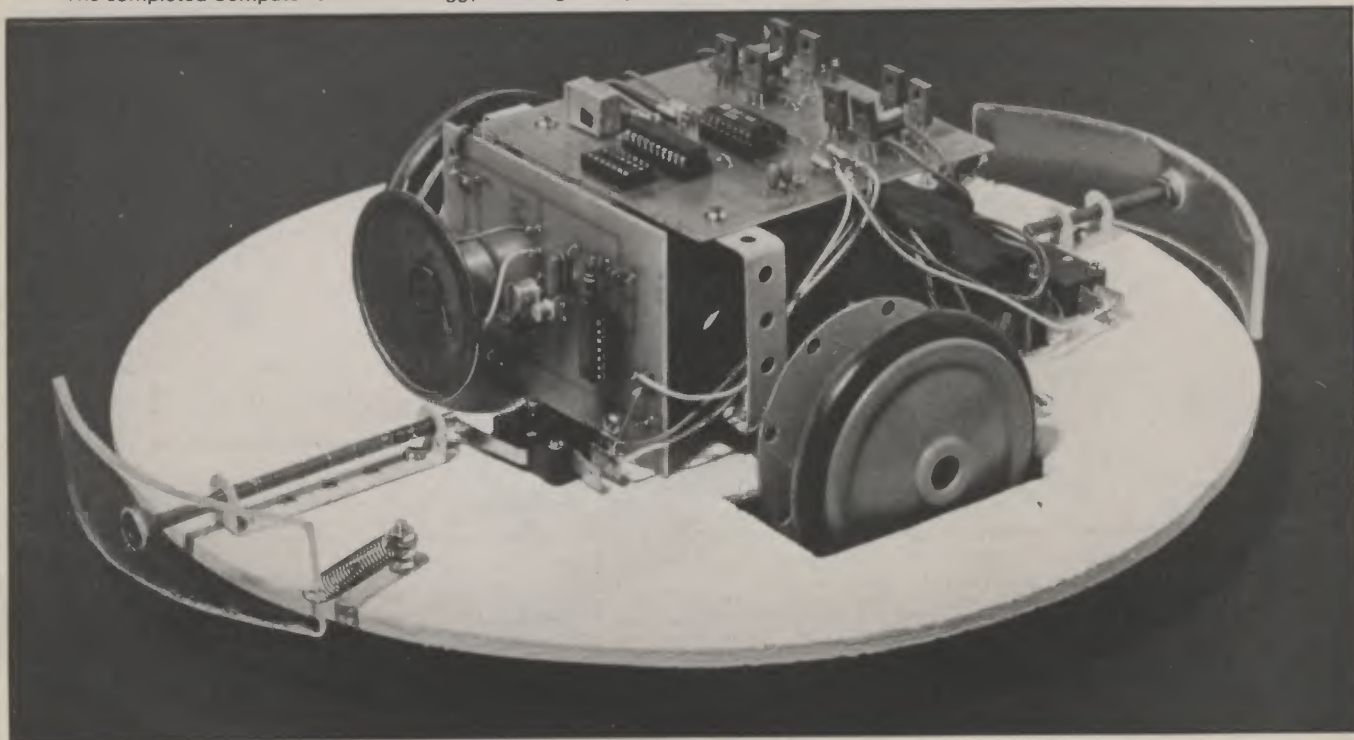The completed Computer Controlled Buggy showing arrangement and positioning of boards, motors and front and rear bumpers.



Insofar as the mechanical side of the construction is concerned the photos give the layout used in the prototype, but clearly much scope exists for the ingenuity of the reader in designing his own version of the vehicle.

## MECHANICAL DESIGN OF THE VEHICLE

The prototype vehicle was designed around the motorised gearbox assembly currently available from Greenweld Ltd. and intending constructors are strongly urged to employ this unit. An interesting feature of the unit is its magnetic clutch arrangement; the purpose of this is to pull both motors into synchronisation with each other and the arrangement appears to be quite effective.

The use of entirely separate port and starboard motors without some arrangement for synchronising the speed of the two would almost certainly lead to problems.

## SOFTWARE

The behaviour of the "buggy" is entirely under the control of the micro-computer. The following software modules should allow the flexibility necessary for the reader to write software appropriate for the particular application.

It should be stressed that in cases where the computer senses a collision, for example, PRINT "FRONT COLLISION", then remedial action should be taken. One obvious step would be to reverse both motors if a front collision is detected. This is particularly important if the vehicle is stationary even though the motors are active. Rotational sensing software would prove useful in this case.

Although this series has dealt exclusively with the use of BASIC for control it is worthwhile to note that machine code software can offer considerable advantages in many control applications.

For example, the rotational sensing software could be written as an interrupt service routine and the position of the vehicle displayed on the VDU. This approach is, unfortunately, beyond the scope of the article.

The BASIC software utilises the same principles that have been used throughout the series. Logical operators are used to test for individual bumper collisions.

In BBC BASIC an EXCLUSIVE-OR operation is first performed to confirm the states of lines P7 and P6 whilst lines P5 to P0 are masked by the AND operator.

This is accomplished in Commodore BASIC by the use of a WAIT statement as outlined in *M.I.T. Part 2*.

A NOT operation and then six shift rights ensures that the nature of the collision will result in an appropriate branching condition.

It should be noted that logical operators follow a strict order of priority with the NOT operator taking the highest precedence.

Next Month: Speech Synthesis

## SOFTWARE MODULES

### INITIALISATION

The least significant four lines (P0 to P3) need to be configured for output whereas the four most significant lines (P4 to P7) must be configured for input. This is achieved using the appropriate data direction register as follows:

BBC	?65122=15
PET	POKE 59459,15
COMMODORE 64	POKE 56579,15
VIC-20	POKE 37138,15

### MOVE THE BUGGY FORWARDS

Linear forward motion can be achieved by rotating both port and starboard motors in the same direction at the same speed as follows:

BBC	?65120=5
PET	POKE 59457,5
COMMODORE 64	POKE 56577,5
VIC-20	POKE 37136,5

### MOVE THE BUGGY BACKWARDS

Linear reverse motion can be achieved by rotating both port and starboard motors both in the opposite direction to that required to move the buggy forwards:

BBC	?65120=10
PET	POKE 59547,10
COMMODORE 64	POKE 56577,10
VIC-20	POKE 37136,10

### TURN THE BUGGY TO THE LEFT

A left turn can be achieved by reversing the port motor whilst the starboard motor rotates in a forward direction:

BBC	?65120=6
PET	POKE 59459,6
COMMODORE 64	POKE 56577,6
VIC-20	POKE 37136,6

### TURN THE BUGGY TO THE RIGHT

A right turn can be achieved by reversing the starboard motor whilst the port motor rotates in a forward direction:

BBC	?65120=9
PET	POKE 59457,9
COMMODORE 64	POKE 56577,9
VIC-20	POKE 37136,9

### STOP THE BUGGY

This can be achieved by turning off both port and starboard motors:

BBC	?65120=255
PET	POKE 59457,255
COMMODORE 64	POKE 56577,255
VIC-20	POKE 37136,255

### TEST FOR BUMPER CONTACT

A front collision will be indicated by a negative transition on P7 whereas a rear collision will be indicated by a negative transition on P6:

#### BBC

```

10 IF (?65120 EOR 192) AND 192
   THEN 20 ELSE 10
20 ON NOT (?65120/64) AND 3 GOSUB
   100,200,300
30 STOP
100 PRINT "REAR COLLISION":RETURN
200 PRINT "FRONT
   COLLISION":RETURN
300 PRINT "BOTH FRONT AND REAR
   COLLISIONS!":RETURN

```

#### PET

```

10 WAIT 59457,192,192
20 ON NOT (PEEK(59457)/64) AND 3
   GOSUB 100,200,300
30 STOP
100 PRINT "REAR COLLISION":RETURN
200 PRINT "FRONT
   COLLISION":RETURN
300 PRINT "BOTH FRONT AND REAR
   COLLISIONS!":RETURN

```

#### COMMODORE 64

```

10 WAIT 56577,192,192
20 ON NOT (PEEK(56577)/64) AND 3
   GOSUB 100,200,300
30 STOP
100 PRINT "REAR COLLISION":RETURN
200 PRINT "FRONT
   COLLISION":RETURN
300 PRINT "BOTH FRONT AND REAR
   COLLISIONS!":RETURN

```

#### VIC-20

```

10 WAIT 37136,192,192
20 ON NOT (PEEK(37136)/64) AND 3
   GOSUB 100,200,300
30 STOP
100 PRINT "REAR COLLISION":RETURN
200 PRINT "FRONT
   COLLISION":RETURN
300 PRINT "BOTH FRONT AND REAR
   COLLISIONS!":RETURN

```

# JUNE FEATURES...

*Electronic*



## SURVEILLANCE SYSTEMS


How can electronics effectively guard property? What are the various surveillance options? This series explains the advantages and disadvantages of relative systems and presents the following three alarm projects:

*Passive Infrared, Ultrasonic, and Microwave.*

All these provide a secure envelope in which any movement is detected, and an alarm sounded.
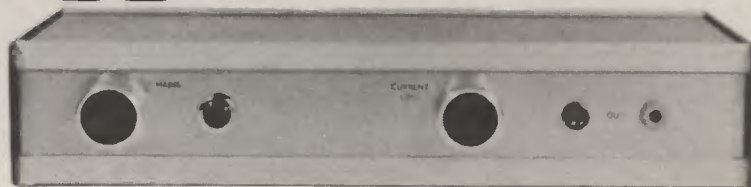
## SPECTRUM PSU

This digitally controlled bench PSU has been designed for use with the ZX Spectrum. It has a maximum output voltage of 24 volts which can be incremented in 0.1 volt steps and is current limited over four switched levels; 50mA, 100mA, 500mA and 1A.



## TRAIN WAIT

This is a must for model train enthusiasts, wanting more realism and automation. This circuit provides automatic wait facility for selected trains at stations and crossings.

**EVERYDAY**  
**ELECTRONICS**  
and computer **PROJECTS**

**JUNE 1984 ISSUE ON SALE FRIDAY, MAY 18**

# EVERYDAY news

... from the world of

## MATCHING UP TO THE FUTURE

**R**EMOTE CONTROL of all the home entertainment facilities such as TV, hi fi, teletext and video are featured in the new Matchline System Television unveiled by Philips.

Made up of separate units, it can, for instance, integrate all the present video possibilities into one system under the command of a single remote "keypad".

Matchline is their answer to the changing role of the domestic television. Video recorders, teletext, home computers, TV games, "stereo" sound and video discs are already with us; satellite and cable broadcasts are just around the corner.


Initially, three TV models will be available, the 20in V6620, 22in V6720 and the 26in V6820. Each model incorporates a 15W stereo tuner/amplifier, with two speakers mounted at the rear of the cabinet behind adjustable, hinged flaps for sound direction. Alternatively, for a better "stereo impression", a pair of separate hi fi speakers are available, or the sound can be replayed through an existing home audio system.

Teletext is standard, along with Philips' "Supertext" facility. This allows 20 page numbers to be stored in the sets memory. Automatic tuning is capable of giving direct access to 99 channels, 50 on pre-selection. Channel selection is indicated by a fluorescent display.
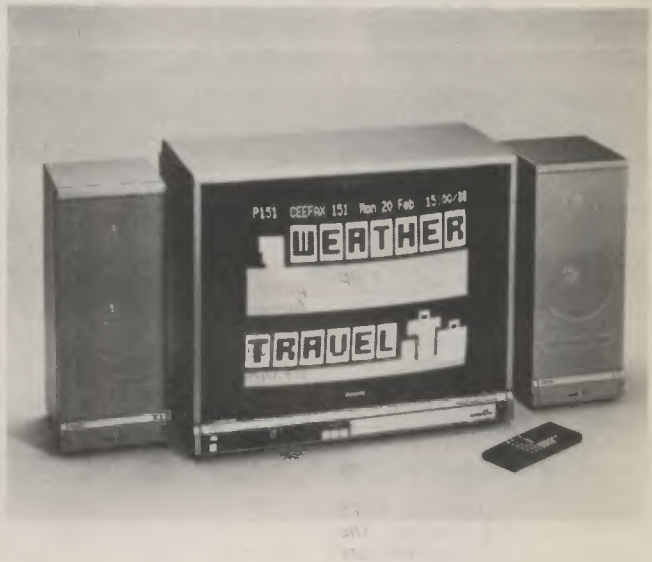
### Euroconnector

The secret to Matchline's flexibility lies in the use of the "Euroconnector", an internationally agreed new standard for connecting video and audio components. The TV receivers each have two Euroconnector sockets, allowing permanent connection of additional equipment. This can take the form of video recorder and computer.

Using the remote control, via the Euroconnector link, it is possible to control and operate the Philips Video 2000 video recorder. Also, it is claimed that in the future control of the Laser-Vision video disc player will be possible, even if it is in a different room.



One of the new Matchline sets with remote control and separate loudspeakers. New video features and services such as Satellite TV and Videotex may be added to the system by plugging in new modules as they become available.

## NEWS . . . ROBOTICS NEWS . . . ROBOTICS NEWS . . . ROBOTICS NEWS . . .

### TRAINING FOR ROBOTS

As more and more firms turn to robots in their drive for efficiency, so the need for experts who understand what these non-human workers can and cannot do increases.

Now a new project under the Open Tech Programme, sponsored by the Manpower Services Commission, aims to meet that need by making training readily available throughout the country.

It will be run by the Organisation for Rehabilitation through Training (ORT), whose Technical Department in London, under the direction of Dr. Dan Sharon, has developed a robot study programme.

This programme is split into 92 two-hour study units under seven "chapters": introductory topics, supporting subjects, electronics, computers, robotics, applications, and social and economic impacts.

The plan is to establish a network of up to 20 countrywide contact points, at which students will be able to receive instructions and access to robotics hardware, or even borrow equipment such as desk-top computers and educational robotic arms to use at home.

You can, of course, start by constructing the Computer Controlled Buggy in this issue, see page 317.

### Training for the Microprocessor

One of the claims for the new Heathkit microprocessor training course being marketed in the UK by Maplin, is that it provides the most comprehensive educational and training programme covering 16/8-bit micros currently available.

The training course provides full-scale understanding of the principals and practice of 16-bit micro technology and the kit has been designed to meet the needs of both beginner and those who may already be familiar with 8-bit techniques.

The self-contained training course will meet the needs of the classroom student or provide individual self-instruction. Basic training units include programming, memory segmentation, data handling and hardware interfacing.

Doug Simmons of Maplin, believes that completion of the total course will take about 100 to 120 hours. Cost of the classroom course, together with experiment parts is approximately £99.

### Micro-Robotics Fair

The "London Computer Fair" is being held at the Central Hall, Westminster over the Easter Bank Holiday weekend from 19 to 23 April. This is the fifth annual fair to be sponsored by the Association of London Computer Clubs.

The "1984 ACC Micro-Robotics Conference" is also to be held at Central Hall, Westminster, on 21 April. This venue is in conjunction with the Association of London Computer Clubs' Easter Fair, and many of the stands will have a Robotics flavour.

## COMPUTER HOLIDAYS for the HANDICAPPED

Last year the first one-week Computer Holiday for the Handicapped was planned to accommodate only 25 persons, but the response was overwhelming with over 400 applicants wanting to take up residence.

This year, from July 23 onwards, it is planned to run three one-week computer holidays for the handicapped at Valence School, Westerham, Kent. Accommodation is limited to 60 persons at a time and will be on a "first come first served" basis.

The holiday will cost £145 for full-board, tuition and the use of the computers. For more information write to Dr. Lionel Wardle, c/o M.A.P.S. Ltd., Dept EE, 37 University Road, Southampton, SO2 1TL.

## TRANS WORLD CALL

The Business Communications Service end of British Telecom has just secured a data transmission contract from Trans World Airlines (TWA) of Kansas City, Missouri, worth £1 million over five years.

Working in close harmony with TWA, they have designed and are to install dedicated equipment to give a 24-hour, year-round communications facility for the airline.

This deal from a major multinational company means that TWA will use London as the hub of all its computer data transmissions between Europe and the United States.

Locations in 12 European capitals and major cities will feed their computer data to London, over private leased circuits, and through equipment in London, to TWA's offices in Kansas City using undersea transatlantic cable links.

## Exhibitionist

The 15th Annual Scottish Electronics Exhibition and Convention, SCOTELEX '84, organised by the Institution of Electronics, will be held during the period 5 to 7 June, inclusive, 1984, in the Royal Highland Exhibition Halls, Ingleston, Edinburgh, EH28 8NF. Admission will be free-of-charge to visitors, via tickets available from the exhibitors, and from the organisers.

The first International Computer Show for Venezuela, "Inforven 84", will be held from 8 to 11 May 1984, in the new Convention Centre at the recently opened Caracas Hilton Hotel in central Caracas.

The exhibition, and the associated conference, will be sponsored by the Ministerio de Fomento, Oficina Central de Estadística (OCEI) and by Petroleos de Venezuela S.A. (PDVSA).

The Offshore Computer's Conference and Exhibition, to be held from 5 to 7 June in Skean Dhu, Altens, Aberdeen, has to date attracted 35 confirmed exhibitors from The Netherlands, Norway and the UK.

## Vote of Confidence

The Organisers of "The All-Electronics/ECIF Show" announced that over four hundred members of the electronics industry voted "yes" to the proposal that "The Show" should move to the new Olympia 2 in 1985.

After detailed discussions with Hudson Soft Co., of Tokyo, Kuma Computers have announced that an agreement has been reached for them to market certain Sharp MZ700 and Spectrum software packages in the UK. The most important of which is Hu-Basic and Hu-Cal.

## RAIL LINK

GEC Computers has been selected to supply hardware for the second phase of British Telecom's Prestel Service.

Avon Direct Mail Services, is to install a Rediffusion R2800 Telecentre system.

Following successful trials of a Westinghouse "Westronic System Two" data link installed between East Finchley station and Cobourg Street control centre, London Transport has ordered a further nine links for installation on the Northern Line between High Barnet and Kennington.

## BIASED REPORT

Recording-tape manufacturers throughout the Common Market are taking a lead from Britain. A UK call for immediate action to stop the European Parliament imposing levies on sales of blank audio and video recording tape has been fully accepted by manufacturers in member states.

At an international conference in Brussels, staged by the UK "Tape Manufacturers' Group" (TMG) last month, delegates from France, Germany, Italy, Belgium, Denmark and the Netherlands all agreed to campaign in their own countries and on a united basis amongst European parliamentarians... just as British manufacturers have been campaigning since May 1981.

Their first task is to expose the "total bias and inadequacy" of a report, requested by the EEC, which could force consumers to pay more than double the present retail costs for recording tape.

Entitled, "The Private Copying of Sound and Audio-Visual Recordings", the report calls for levies of one EEC currency unit (61p Sterling) per playing hour on sales of blank audio tape and three currency units per playing hour on blank video tape. In addition, Value Added Tax would be payable on the costs of the levies as well as on the costs of the recording tape. That would mean that a one-and-a-half-hour C90 audio cassette, at present retailing for 90p, would have an over-the-counter cost of about £1.80. And a three-hour E180 video cassette, currently retailing at around £5.30, would sell for upwards of £10.60.

The report was prepared by the International Federation of Phonogram and Videogram Producers (IFPI)—the very people who would receive the money raised by levies.

Leader of the British initiative, TMG Chairman, Mr. Bill Fulton (MD of Sony UK) said after the conference: "I'm delighted. We came here to make the case for immediate, united action and response has been magnificent. The degree of co-operation here is remarkable. Our mission has been a complete success."

Condemning the controversial report requested by the EEC, Mr. Fulton stressed: "It is a totally biased document, compiled without consulting consumer protection groups or, indeed, anyone except the people who would benefit from the imposition of levies; in other words the music and film industries."

"What is needed is a genuinely impartial analysis of the situation by a totally independent body, experienced in preparing such documents."

As this is a subject of very controversial opinions, our Readers' Letters page is open to all interested parties to record their own personal "soundings".

# EXTRA 1K RAM FOR THE ACORN ATOM

BY A. J. PRESNAIL

THE basic Acorn Atom RAM is made up from 2114 static memory devices. These are 1024 × 4-bit chips and are arranged in pairs in the Atom to yield 1024 × 8-bit blocks.

An extra 1K of RAM can easily be added to the Acorn Atom without a great deal of difficulty. All that is needed is experience with a soldering iron.

This extra 1K of RAM will be located between the maximum on-board memory (at hex 3BFF) and the start of off-board memory (at hex 4000).

This is accomplished by soldering two extra 2114s directly on top of two existing 2114s, IC10 and IC11 of the Atom circuitry; the pins are soldered in parallel with those of the existing chips except for pin 8 of each which connects to other parts of the Atom circuitry.

## CIRCUIT DIAGRAM

The circuit diagram of the expansion is shown in Fig. 1. Pin 8 of IC1 and IC2 (the "chip select" pins,  $\overline{CS}$ ) are connected together and also to IC5 pin 1 and IC6 pin 7. The remainder of the lead-outs are in parallel with the on-board RAM chips.

IC5 pin 1 and IC6 pin 7 must be disconnected from the Atom p.c.b. This is easily achieved by bending up the i.c. pin so that it sits out of its socket.

IC6 selects these new memory chips between locations hex 3C00 and hex 3FFF. Pin 1 of IC5 connects to pin 7 of IC6 to disable the locations from being accessed by the off-card buffers.

## CONSTRUCTION PROCEDURE

(1) Carefully remove IC6 from its socket and bend out pin 7.

(2) Remove IC5 and bend out pin 1.

(3) Remove IC10 and IC11.


(4) Bend out pin 8 on both of the new memory chips and then place these new chips over the two removed 2114s, IC10 and IC11, and carefully, with a small soldering iron, solder the two chips together.

(5) Connect a wire to pin 7 of IC6, another to pin 1 of IC5 and one to each pin 8 of the new memory chips. Cut the wires to a convenient length, strip their ends, twist together and solder. Slide a short length of sleeving over the connection to prevent it shorting on any other part of the circuitry.

(6) Re-insert all the chips into their respective sockets.

(7) Run the Memory Test given below.

Fig. 1. Circuit diagram of the 1K RAM expansion for the Acorn Atom. IC1 and IC2 are the additional 2114 static memories; IC5 and IC6 are part of the existing Atom circuitry.

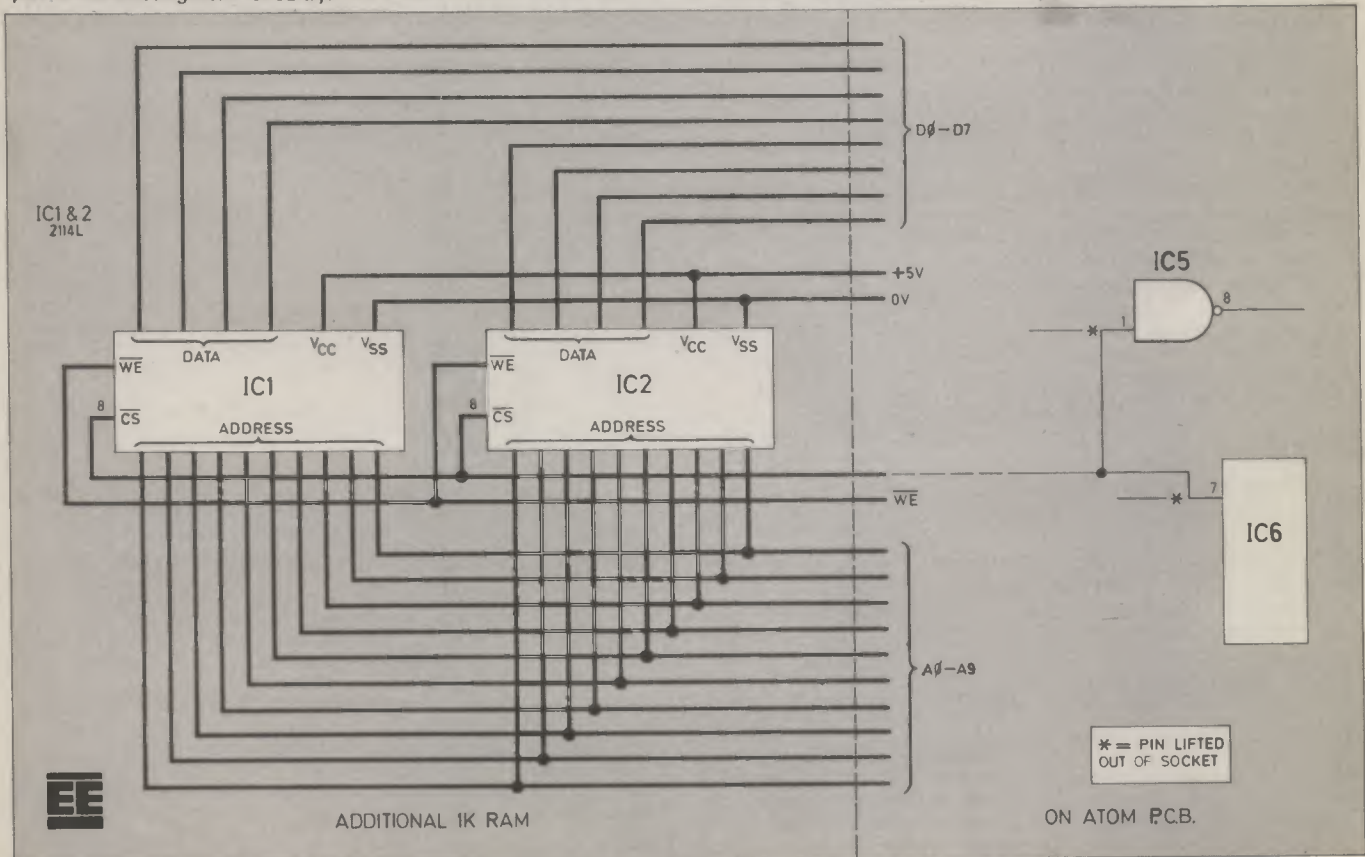



## MEMORY TEST

10 F.A=0 TO 255;F.X=#3C00 TO #3FFF  
 20 ?X=A;N.  
 30 F.X=#3C00 TO #3FFF  
 40 IF?X<>A P.&?X,"AT  
 "&X,"SHOULD BE ",&A'  
 50 N.;N.;E.

If all is well the program should run and end without any errors.

If however errors are printed out, by examining the printout you should be able to tell where the problem is.

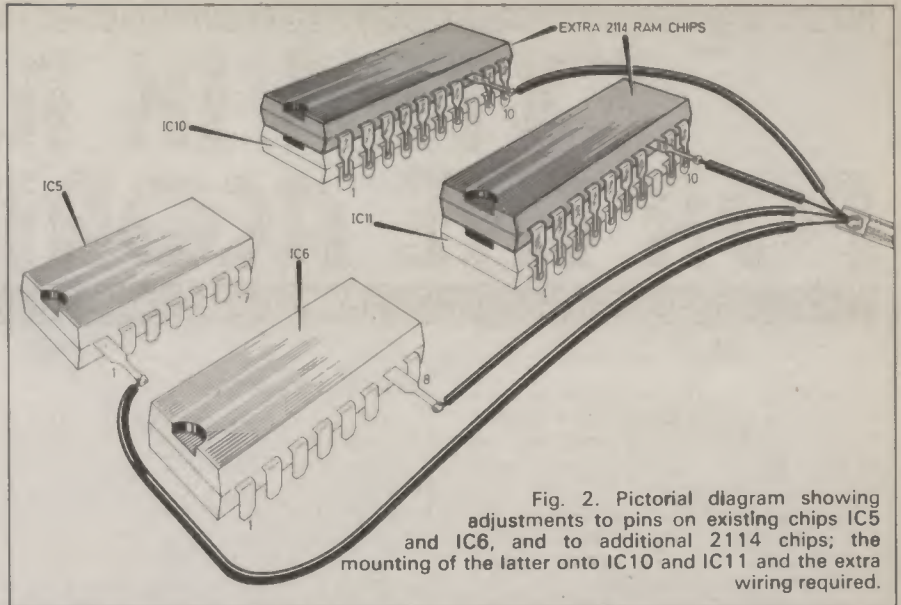
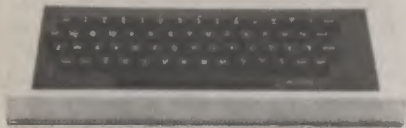


Fig. 2. Pictorial diagram showing adjustments to pins on existing chips IC5 and IC6, and to additional 2114 chips; the mounting of the latter onto IC10 and IC11 and the extra wiring required.

# EXTRA UTILITY PROM FOR THE ACORN ATOM

BY A. J. PRESNAIL

THE Atom only has one EPROM socket for utility PROMS which can be a disadvantage if you have more than one EPROM to go into it, for example, Wordpac, Toolkit, etc., since you have to power off and open the Atom's case to change the EPROM.

A simple solution to this would be to parallel two sockets from the Acorns with a switch on the select lines, but a better way would be to select the PROMS by software or from the keyboard.

The following circuit allows up to eight EPROMS to be selected, or with an additional i.c. it can select 16.

## DESCRIPTION

IC1 pin 14 goes low if an address in the range hex 9000 to 9FFF is written to, or read from.

IC2 pin 8 goes low if an address in the range hex XFF0 to XFFF is selected.

These two lines are NORED together by IC4 which when ANDed with clock 2 (ø2) by IC3 enables the latch IC5. This means that IC5 is enabled in the range 9FF0 to 9FFF, which is not normally used in the Atom.

When IC5 is enabled the address lines A0 to A3 are latched into IC5 to become LA0 to LA3, these outputs will stay at their latched levels until IC5 is again enabled or the power is turned off.

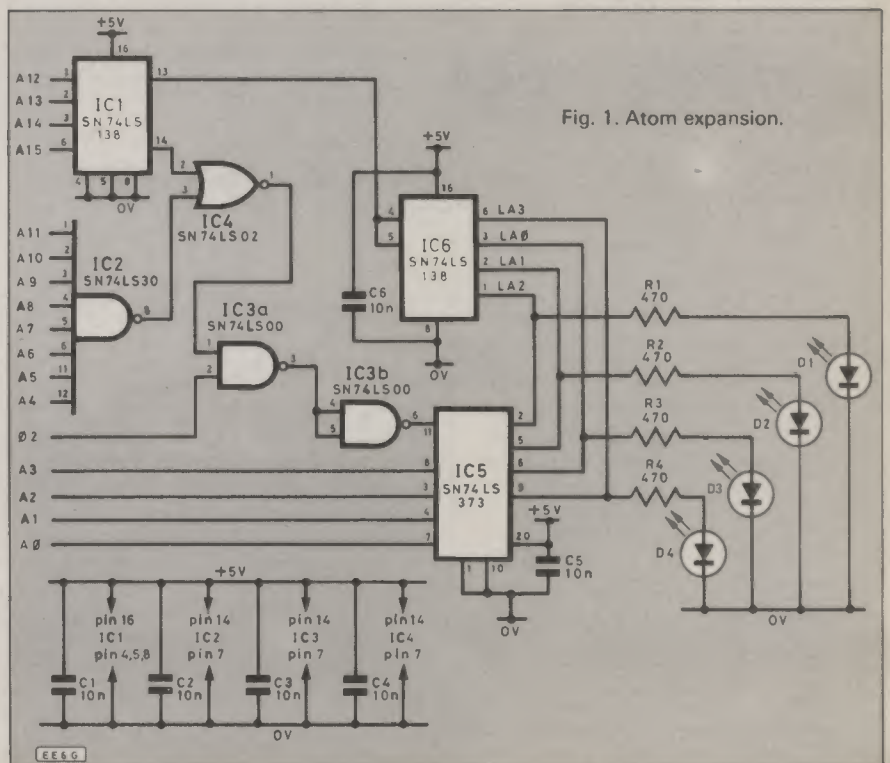


Fig. 1. Atom expansion.

**Table 1. EPROM Socket Pin 20 to IC6 or IC7**

Prom Address	IC6 Pin	Prom Address	IC7 Pin
9FF8	15	9FF0	15
9FF9	14	9FF1	14
9FFA	13	9FF2	13
9FFB	12	9FF3	12
9FFC	11	9FF4	11
9FFD	10	9FF5	10
9FFE	9	9FF6	9
9FFF	7	9FF7	7

**Table 2. Atom Output Bus Connector Pins**

+5V	a1
0V	a32
A0	a15
A1	a14
A2	a13
A3	a12
A4	a11
A5	a10
A6	a9
A7	a8
A8	a7
A9	a28
A10	a27
A11	a26
A12	a25
A13	a24
A14	a3
A15	a2
D0	a23
D1	a22
D2	a21
D3	a20
D4	a19
D5	a18
D6	a17
D7	a16
clock 2(φ2)	a29

## COMPONENTS

### Resistors

R1-4 470Ω (4 off)

### Capacitors

C1-7 10nF (7 off)

### Semiconductors

IC1,6,7\* SN74LS138 (3 off)  
 IC2 SN74LS30  
 IC3 SN74LS00  
 IC4 SN74LS02  
 IC5 SN74LS373  
 D1-4 Any l.e.d.s (4 off)

### Miscellaneous

i.c. or socket  
 24-pin i.c. socket  
 SN74LS08 i.c. for Atom mod.

\*IC7 only necessary if greater than eight EPROMs required.

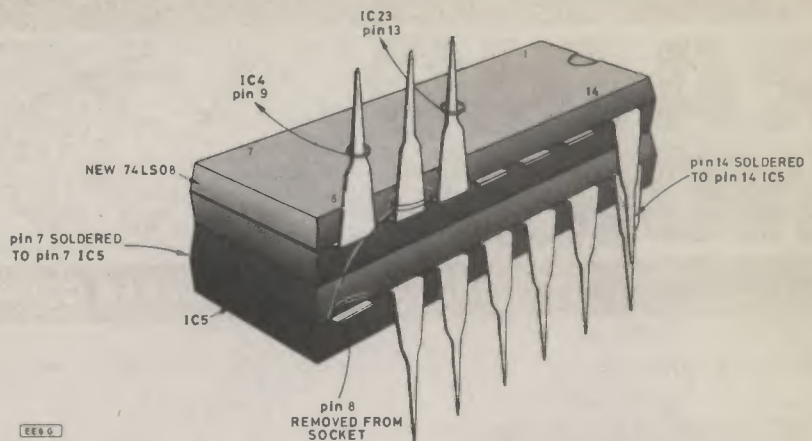


Fig. 2. Pins 1 to 6 and pins 11 to 13 of the new 74LS08 must be bent away from IC5's pins.

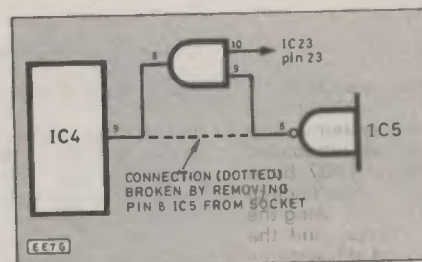


Fig. 3. Modification to allow Utility PROM (address AXXX) to appear on the output bus (i.e. numbers refer to the Atom's main p.c.b. i.c.s).


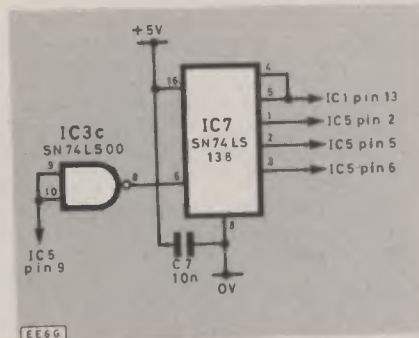


Fig. 4. Modification for 16 EPROM sockets.

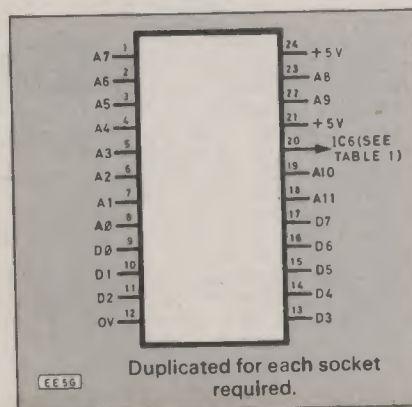

When an address in the range A000 to AFFF is read from, or written to, pin 13 of IC1 goes low and in turn selects one of the outputs of IC6. Which output is selected depends on the binary code on latched lines LA0 to LA3, which must be between 8 and hex F. The l.e.d.s will display the binary code that is latched.

### MODIFICATION FOR 16 EPROMS

By inverting LA3 with one of the spare NAND gates (for example, pins 8, 9, 10 of IC4) and then repeating the wiring as for IC6 an extra eight EPROMs can be selected, their address would be 9FF0 to 9FF7.

### MODIFICATION REQUIRED TO THE ATOM MAIN PCB

Because Addresses A000 to AFFF are normally only present on the main p.c.b. a small modification has to be undertaken. This requires that IC5 of the Atom has to be removed from its holder and pin 8 bent out, a 74LS08 then has to be placed over this chip so that pins 7 and 14 can be soldered. Pin 8 of IC5 has to be connected to pin 9 of the 74LS08 and pin 10 of the 74LS08 has to be connected to pin 13 of IC23. Pin 8 of the new 74LS08 now has to be connected to pin 9 of IC4. Replace IC5 into its socket. □

# RADIO WORLD



BY PAT HAWKER G3VA

## Finding Directions

Radio navigational techniques have come a long way since their early use, now dating back more than 70 years, of the simple loop aerial. This, when combined with triangulation on two or more transmitters, was already in use before the first World War.

One of the first scientists to become interested in the directional properties of radio was Professor Frederick Braun, inventor in 1897 of the "cathode-ray indicator tube", that was later to become such an important component not only for TV but also for many radio-navigational systems. Two Italians, E. Bellini and A. Tosi, introduced the idea of using fixed aeriels in 1907, but it was the wide use of d/f (direction finding) techniques, in World War I, for tracking the movement of warships, airships, and the like, that raised the status of d/f systems and resulted in reliable equipments.

Similarly World War II gave a further impetus to d/f and also saw the development of the pulsed hyperbolic systems such as Gee, Loran and Decca for accurate radio-navigation.

## Bird Sense

But radio navigators have always looked with interest and puzzlement at the natural navigational abilities and compass sense of birds and animals.

Over the past decades many attempts have been made to determine just how some birds are able to navigate so accurately over enormous distances. There is now good evidence that the compass sense of birds is based on a combination of celestial and geomagnetic cues.

The celestial cues are provided by the Sun, sunset, skylight polarisation pattern and stars much as in classic astro-navigation. More puzzling, and for a long time more controversial, are the natural "magnetic compasses", yet there is good and convincing evidence that young birds, particularly before the full development of their celestial compass, do possess a magnetic sense that they use, if only to "calibrate" their Sun compasses.

Further evidence of the role of the geomagnetic field has come from experiments carried out at the University of Lund in Sweden. Scientists deliberately "shifted" the magnetic field at the nesting boxes of Pied Flycatchers and have been able to show that a corresponding shift was still occurring two months later.

This was done using large Helmholtz coils energised from 12-volt batteries throughout the incubation period of the eggs and the subsequent nesting periods (about one month in all). Control birds had no coils attached to their nesting boxes and showed no sign of any anomalies in their

navigation. Fully-grown birds seem to depend much more on their "Sun compass" than on magnetic fields.

## Auto-route

Engineers for several decades have sought to develop navigational systems that would provide guidance to car drivers in urban or rural areas or for cross-country journeys, seeking to replace map-reading or stopping to ask the way.

While various systems of vehicle position location and guidance have been developed most of these have postulated the use of buried inductive loops or radio transmitters, and would be expensive to install. The latest system, "Autoscout" has been developed by Siemens and Volkswagenwerk in West Germany, and is currently undergoing field trials in Wolfsburg.

This uses low-cost infra-red transmitters, basically similar to those used in many TV remote-control units, installed on traffic-lights. They act as beacons providing to the vehicles a stream of data on main roads in the area.

The vehicle has a microprocessor-controlled, dashboard-mounted, control unit with display and keypad, and also a magnetic field sensor mounted under the car roof which acts as a "compass", with circuitry that is claimed to correct errors due to surrounding metal and similar objects. Distance pulses are fed into the control unit from the vehicle's speedometer, providing direction and line-of-sight distance data.

The control unit can operate independently of the infra-red beacons to display distance and direction; however, in conjunction with the local information provided by

## Shoot Out

Some people regard particular TV and radio presenters less than enthusiastically but usually express their dislike by means of a channel switch. But Jerry Dunphy, a 62-year-old TV "news anchor" in Los Angeles for more than 20 years, together with a woman make-up artist, were victims of a shooting incident last Autumn.

Both were shot, Jerry Dunphy seriously, while returning to the studios of KABC-TV, Hollywood, after a meal. The police, however, believe it to have been a random act of violence rather than the action of a TV critic.

However, in nearby Monterey a man first fired several shots over the head of a radio disc jockey and then scattered some 58 shotgun rounds into the equipment, including the record that was being played. When arrested, the suspect claimed that KWAV-FM was "poisoning his mind".

the beacons it can guide a driver to the destination programmed by the keypad into the control unit, including detours or other local routing information. Autoscout can even direct the driver to a specific building, garage, or parking space using information from the local beacons.

The vehicle unit, in volume production, would cost about the same as a good car radio. All traffic lights at a major intersection could be equipped at under £1500.

Sounds good, but how far is it away from a completely "guided" vehicle in which the "driver" becomes merely a passenger?

## Voice from Space

The success of the long-awaited operation of a 144MHz amateur-radio hand-held transceiver by Dr. Garriott, W5LFL, aboard the "Columbia" Space Shuttle early December, focused much media publicity on the hobby.

Whether it added much to anybody's technical knowledge of space communications is more doubtful, though it certainly showed that a low-power v.h.f. rig can easily span over 250km when the curvature of the Earth or the local topography does not get in the way. Dr. Garriott taped the incoming calls from amateurs to sort out on the ground, all a bit like the airborne "Jean-Eleanor" v.h.f. equipment used by the Americans during the closing stages of World War II when they were able to wire-record messages from their agents in Germany.

## Chatter Box

The silicon revolution in the form of ultra large-scale integrated circuits means that it is already possible to put nearly one-million components on a single silicon chip for such purposes as providing large electronic memories. Over the past two decades this represents an increase of some 100,000 times on the first integrated circuits—and equally important a corresponding decrease in terms of "cost per transistor" to the level where this amounts to only about one-thousandth of a penny.

But at a recent Mountbatten lecture of the National Electronics Council, Dr. Ian Ross, president of the famous Bell Laboratories, confidently predicted that we still have a long way to go before we reach the end of this road. After carefully analysing all the ultimate limiting factors, he foresaw development over the next two decades of devices with 1000-million (an American billion) components on a single 1-inch chip, operating from a 1-volt supply, and suitable, because of the minuscule dimensions of the components, of acting at speeds of about 10 picoseconds.

"Micro-electronics is merely at the half-way point," he said, though he seemed a little less certain of what will be done with such complexity. He mentioned computers for language translation, for weather forecasting, for the prediction of the land-fall of hurricanes—and computers that can be programmed just by talking to them. Indeed, he feels there is a need to make computers more "user-friendly" so that ultimately it should be possible to hold a fluent discourse with a computer.

It sounds to me a bit like having a chat with your accountant, wondering all the time what he is really thinking. With individual computer-designed dolls sweeping America I wish I could be as enthusiastic as Dr. Ross about a world in which one is liable to be nagged by a computer!

## A Black Box Project

# MASTERMIND TIMER

As the title suggests, this is a timer which can be used to give the similar conditions to a contestant as in the BBC's Mastermind quiz. After switching on the unit and pressing the reset button, a delay is in effect (variable from one to two minutes), after this time the familiar bleep-bleep will sound signifying the end of the required time. It can also be used for other games such as chess or draughts to give a time limit for each move.

### CIRCUIT DESCRIPTION

The circuit diagram of the Timer is shown in Fig. 1. The first time period is based around IC1, a 555 timer. This is wired up as a resettable monostable multivibrator; this can be stopped in the middle of a cycle and re-started again by pressing S1.

This connects the trigger input and reset pins to ground, creating a negative-going pulse (positive to ground transition) as the pins were previously held high by R1. If a negative-going pulse appears at this input then the timing capacitor C2 will be discharged, resetting the cycle.

The output from this i.c. (pin 3) is connected to pin 12 and pin 13 on IC2a and is inverted by the Schmitt trigger action of this NAND gate. The output pin 11 is connected to input pin 9 on IC2b. The other two gates are made up as two oscillators; one being controlled by the other. The oscillator based around R3, C4 (IC2d) is approximately 0.5Hz; this switches on and off the oscillator based around R4, C3 (IC2c); this has a frequency of about 3kHz approximately.

The output of IC2c goes to the other input of gate IC2b. When the condition arises that IC1 output (pin 3) goes low then IC2a goes high; this makes input pin 9 high and so whatever appears at the input (pin 8), will appear at the output (pin 10); in this case half second bursts of a high frequency squarewave (see Fig. 2). This is then fed to the output speaker via

C1. The sound level is quite adequate for this circuit as long as the earpiece is used. The current drain on the battery is approximately 4.5mA on standby and 18mA to 20mA when beeping.

### CONSTRUCTION

All the components should be mounted on the Veroboard as shown in Fig. 3. It

was found best to solder in the i.c. sockets first as this provides a location to base all the other components and links. IC1 can be soldered in directly if the constructor feels confident enough, otherwise an 8-pin socket should be used.

Note that C1 is fitted lying flat against the board to allow room for all the components and the board to fit into the case.

Fig. 1. Circuit diagram of the Mastermind Timer.


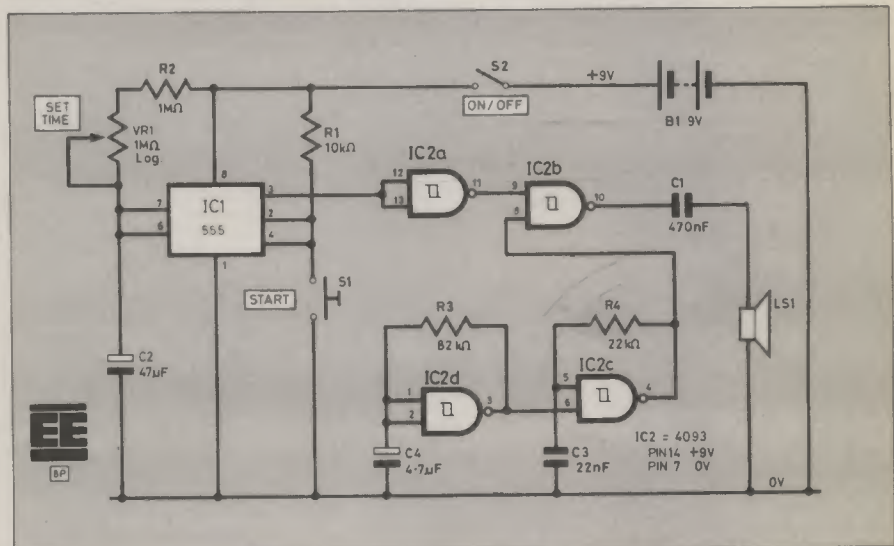



Fig. 3. Veroboard layout.

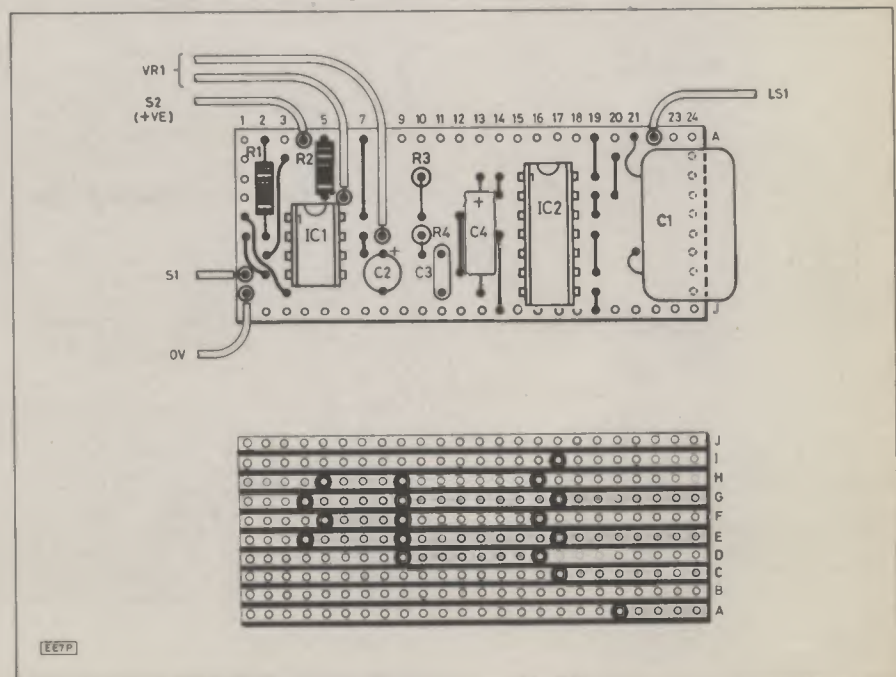

ALL DESIGNS FEATURED IN THE BLACK BOX SERIES WILL USE THE SAME BLACK PLASTICS CASE AND SAME SIZE PIECE OF STRIPBOARD

BY L. A. PRIVETT

Fig. 2. Output waveforms.

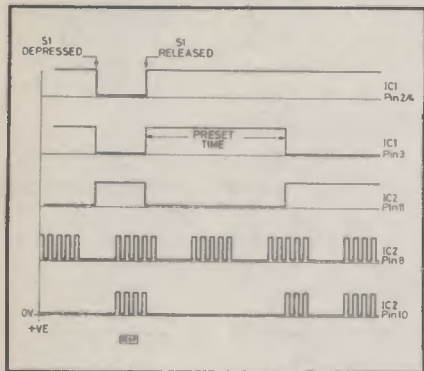


Both switches were fixed to the top of the box (Fig. 4) while the speaker was glued to the front after drilling suitable holes; VR1 is also mounted on the front panel and is held by its own fixing nut. Card-board can be used to insulate the battery from the rest of the circuit. When placing IC2 into its socket normal CMOS precautions should be taken.

### TESTING


Insert battery; switch on; the bleep may sound depending on the condition of C2. Pressing S1 will sound the bleep-bleep and upon releasing, the sound will be extinguished for the time period set by VR1 (between one and two minutes).

Fig. 4. Wiring diagram.

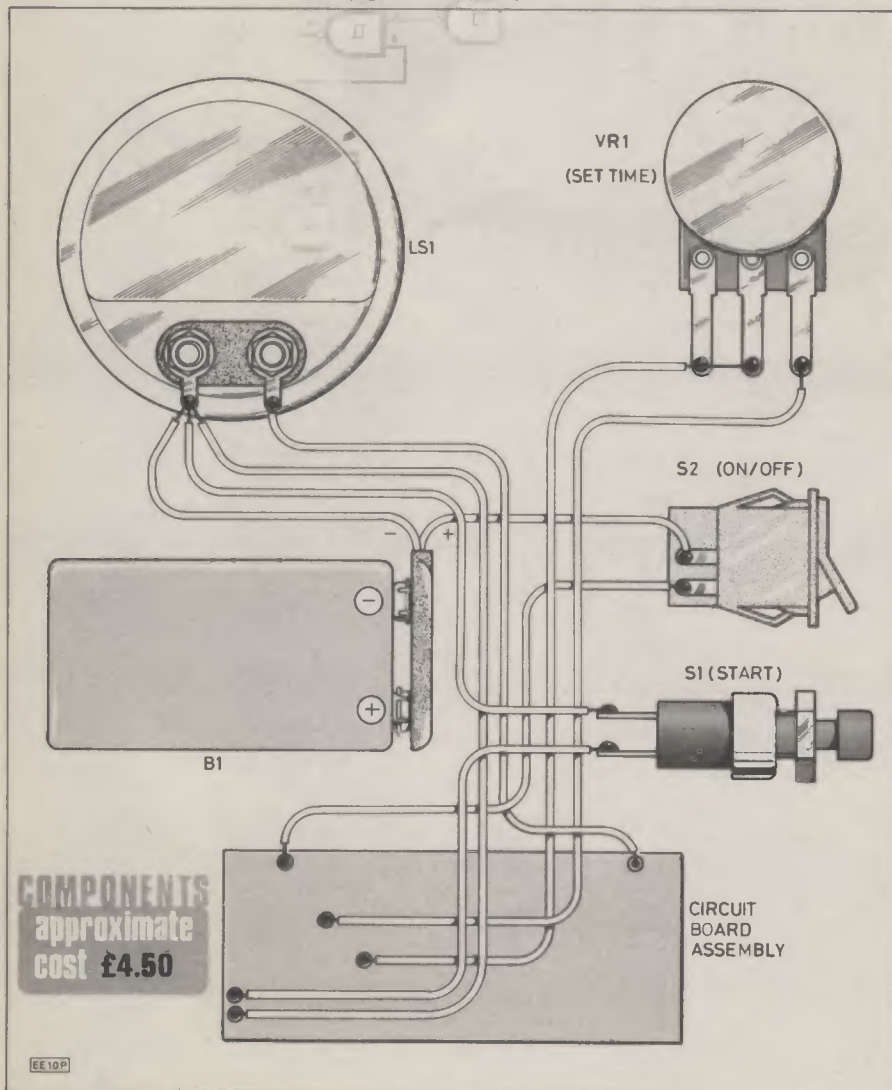

COMPONENTS  
approximate  
cost £4.50

EE10P

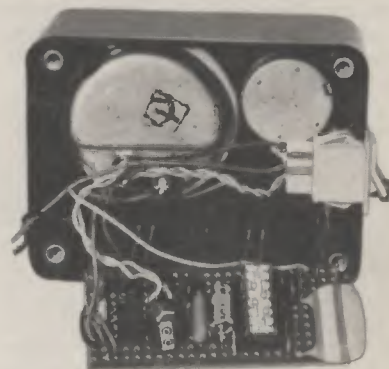

Internal view of the Timer.

After the preset time the familiar sound should be heard and will continue until switched off by S2. For games such as chess then each player has a set time to make his move; after which he then presses S1 and so resetting the time for his or her opponent. As to whether the move has to be made before any sound is heard or within so many bleeps is up to the players making the rules. □

## COMPONENTS

### Resistors

- R1 10kΩ
- R2 1MΩ
- R3 82kΩ
- R4 22kΩ
- VR1 1MΩ log. carbon pot.
- All resistors 1/4W carbon ±5%

### Capacitors

- C1 470nF
- C2 47μF 16V electrolytic radial
- C3 22nF polyester
- C4 4.7μF 25V electrolytic

### Semiconductors

- IC1 555 timer
- IC2 4093 quad 2-input NAND

### Miscellaneous

- S1 push-to-make single pole
- S2 on/off toggle
- Veroboard; case 80 x 61 x 41mm; PP3 battery connector; 14-pin i.c. socket; knob for VR1; wire and cable for on and off board links; (LS1) telephone ear-piece; (B1) PP3 battery.

# LETTERS

## Clearing the Air

Sir—It is to be regretted that your contributor A. Flind was not better informed on the question of ozone generation from ionisers. As a direct consequence he has caused considerable concern to a number of our clients who have purchased ionisers for the treatment of asthma (see *Negative Ion Generator*, February issue.)

We trust that you will make space available to offer the reassurance afforded by the following:

1) Whilst a number of early ionisers (particularly American models) generated considerable quantities of ozone, techniques to overcome this were developed and patented in the UK by Medion some 15 years ago.

2) Since then all Medion ionisers and many other models utilising these design features have been free of ozone. Independent or government tests in the UK, USA, Canada and Australia have all confirmed that, at distances of four or more inches from the ion-emitters, ozone densities do not exceed 1 part in 2000 million. This is less than the natural background level which exists in clean air and is, in fact, less than can be detected by the most sophisticated equipment currently available.

3) Ozone is not produced purely as a function of the voltage applied to a needle tip, but by the employment of too high a field intensity. This would almost certainly be the case with the published design where an earthed lead is positioned only 5mm from needles with voltages of 7kV to 8kV.

4) It should be appreciated that any ioniser can be induced to produce ozone if an earthy object comes close to the needles, and this includes the human nose. Sniffing close to an ioniser gives no indication whatever of ozone emission under normal usage. Perhaps the simplest way to confirm this is to sniff the air when first entering a room with an ioniser. The "electric motor" smell of ozone will be quite apparent if it is present.

5) The author suggests that ozone is linked to output voltage and that it seems to be higher at about 3.5kV and above 8kV. We can assure readers that this simply is not so and wonder how this conclusion was reached.

6) It should be appreciated that research into various therapeutic effects of negative ions has been conducted in many parts of the world since before the last war. Many of the results of controlled trials have been outstanding, particularly with all kinds of respiratory disorders and tension conditions.

Julian P. Laws,  
Manager—Environmental Division,  
Medion Limited,  
Old Oxted,  
Surrey.

Firstly, the disparaging remarks about *some* commercially made ionisers were not intended to apply to the products of Medion, a reputable firm specialising in them. Indeed this company's name is not mentioned anywhere in my article. Nevertheless, I

hope Medion will accept my apologies for any inconvenience that may have been caused unintentionally.

The fact is that for some years it was possible to assemble a transformer with half a dozen diodes and capacitors into a box and sell the result for £80 or more, and this not unnaturally attracted a few "cow-boys". This led to sub-standard ionisers being sold.

Field intensity, and thus ion and ozone production, seems to be related to voltage, area and the proximity of earthy conductive objects. If the voltage is high enough it must exceed a point where ozone is emitted directly into the atmosphere, regardless of the other factors.

The earthed wire in my design is some distance from the needle tips where the field intensity is supposed to be at its highest. Over a long period of use I have never encountered any smells of ozone except, as Medion suggest, when taking a good sniff very close to the needles.

I hope this will set the minds of both Medion's customers and constructors at rest.

A. Flind.

## Vanishing Tardis

Sir—As an ardent viewer of the BBC TV series *Dr. Who*, I am pleased to see that the instrumentation used by so many planets' civilisations rely on meters, lamps and switches of European manufacture.

Obviously our electronic and electrical industries advertising and sales teams have achieved results "out of this world". But why haven't we heard about this from the firms themselves?

Is there a straightforward answer or are my suspicions likely to be proved correct. Have the aliens been secretly stealing our best designs from inside the Tardis!!! Would they dare steal from a British Police Box!

Mind you, rumour has it that the Tardis will "change" in the underwater series. The police box is retiring because "children no longer understand what a police box is!" Viewers in other countries have lived with this problem since the first series in 1963... and have accepted this rare British customised police "vehicle" with the blue flashing light on top warning of its imminent disappearance.

How true. Very few are now visible in the UK. Although a very slim Dr. Who might be able to make use of London's Metropolitan Police call boxes: the door does seem very small though.

Doesn't Dr. Who understand that parents and grandparents remember with pride the old "Tardis" in their village or town and enjoy telling the children what they were for, or is the doctor happy in the knowledge that the generation gap will widen?

Derek Gooding,  
London.

## Help the Handicapped

Sir—I am compiling a catalogue of programs and hardware available to help the handicapped make use of a Micro and would be very glad to hear from anyone who has developed or knows of such "aids".

In particular programs or devices to help the severely handicapped to communicate or to control their environment, for instance, controlling domestic appliances, opening doors, turning book pages and so on.

Dr. Lionel Wardle,  
c/o M.A.P.S. Ltd.,  
37 University Road,  
Southampton, SO2 1TL.

## Mini-Roulette

Sir—I wish to draw readers' attention to my circuit for a "Mini-Roulette" published on the *Circuit Exchange* page in the February 1984 issue.


The wire from pin 13 of IC2 (4017) should run to the cathode of D1 not to battery negative.

The wire from TR1 collector should run to battery negative not to the cathode of D1.

J. Wood,  
West Lothian,  
Scotland.

The BBC assures us that there are no immediate plans to retire the "Tardis" and it will appear throughout 1984-5. Apparently the speculation was sparked off by a comment made by the programme's producer when he suggested the *Dr. Who* team might need to consider the relevance of the police box style in an age when few children see them.—Ed.

"Tardis" photo courtesy of BHI.

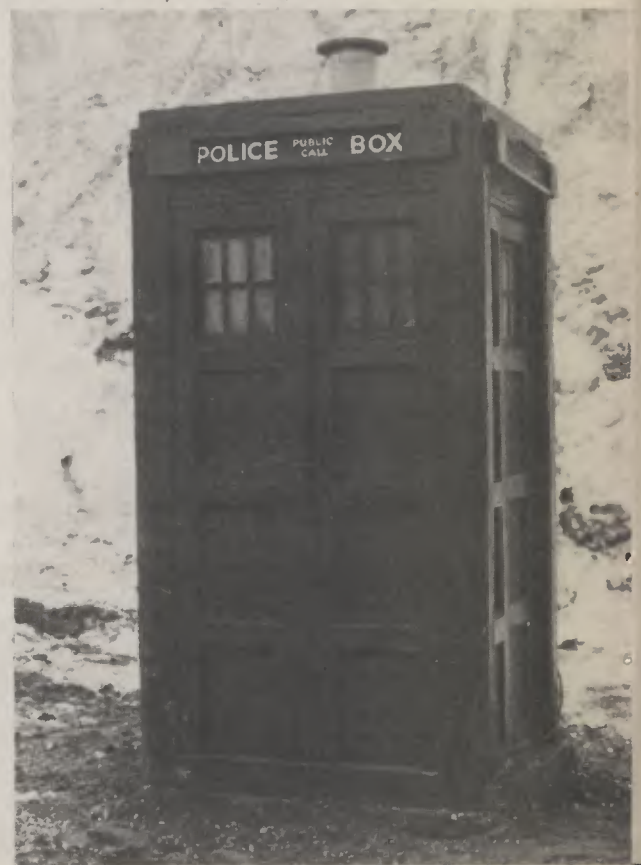



# WHY NARROW BAND F.M. ?

## Part 2

BY E.A. RULE

In the first part of this article we considered the main differences between the f.m. and a.m. systems. We shall now take a closer look at some of these differences.

Taking the receiver first, Fig. 8 shows a typical a.m. detector circuit and Fig. 9, an f.m. discriminator; however these are only two examples of the different types used in each system.

### SIMPLE A.M. DETECTOR

In Fig. 8 we have a simple a.m. detector circuit where T1 is the last i.f. transformer (normally around 455kHz), this feeds D1 (the actual diode detector) and R1, the diode load resistor. Capacitors C1, C2 and R2 form a low-pass filter which removes any residual i.f., and C3 is a d.c. blocking capacitor which passes the recovered audio on to the next stage but prevents any d.c. being passed on. The diode detector D1 acts like any half-wave rectifier and a voltage will develop across R1. The amplitude of this voltage will depend on the amplitude of the signal feeding into D1 from T1.

As the signal increases more voltage will be produced across R1 and this can be fed via R3 back to the earlier stages to control their gain and prevent overloading on strong signals. (Remember that in Part 1 we explained that the amplitude modulation on the signal must be passed on without distortion and that some means of preventing stages from overload must be provided.)

The audio is recovered from the signal by D1 acting as a half-wave rectifier which removes one half of the modulated carrier leaving the other half with the audio signal on it. The low-pass filter removes the remaining carrier and the audio passes via C3 to the next stage. This action is shown in the waveform diagrams in Fig. 8.

### RATIO DETECTOR

Fig. 9 shows an f.m. discriminator circuit and this type is called a "ratio detector". The phasing of the coils which make up T1 are arranged so that at the centre frequency (normally 455kHz or 10.7MHz) the voltage across the two

diodes D1 and D2 is equal and the resultant voltage at the end of L2 is zero.

Now when the incoming frequency shifts due to deviation, the circuit will no longer be balanced, and because of the phase differences between L2 relative to the two halves of L3 there will be unequal voltages applied to the diodes and the difference between these two voltages will appear at the end of L2. As this voltage will be varying at an audio rate due to the modulation of the carrier it will be passed on to the next stage via C5 as the recovered audio signal.

The explanation of how these detectors work has been simplified, as a full description would require considerable space and there are many technical books available for those who wish to pursue the matter in more detail.

Fig. 10 shows the response of the f.m. discriminator regarding its output voltage plotted against input frequency. As the output voltage swings plus and minus in polarity depending on the deviation of the incoming signal it can be used to control an automatic frequency correction circuit

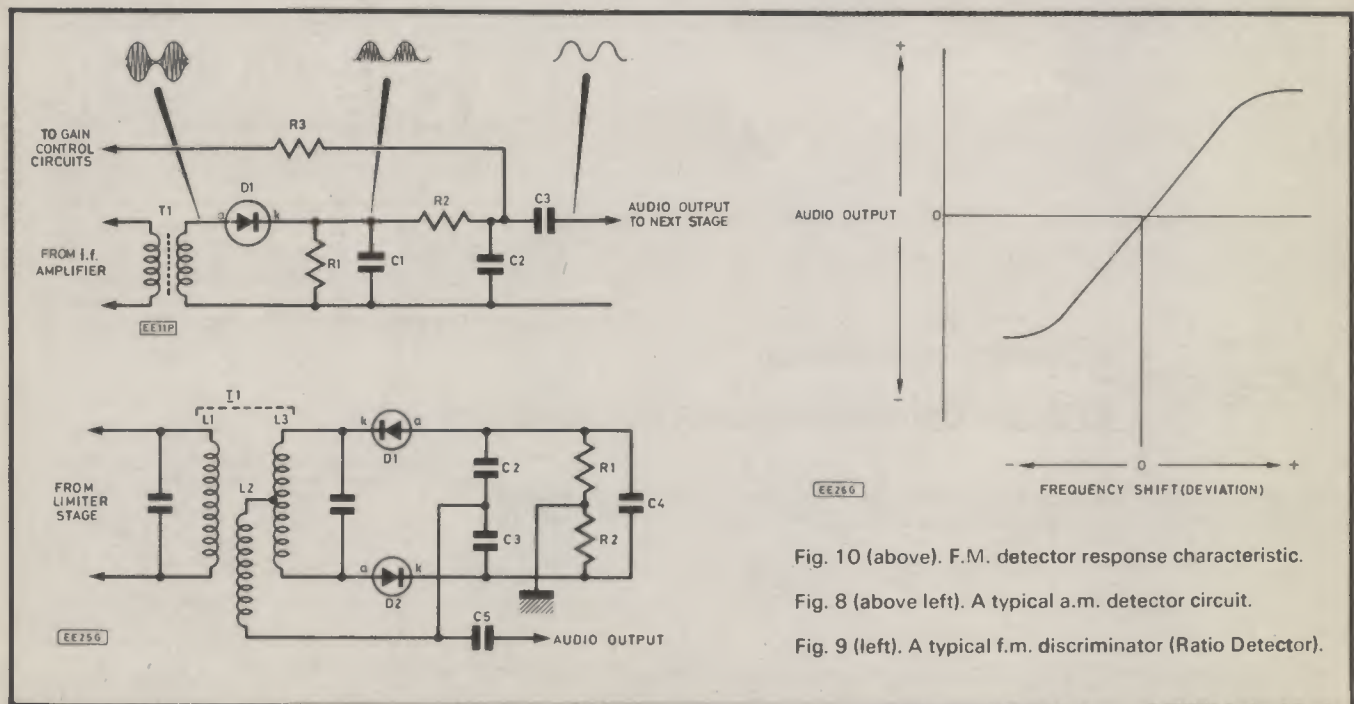


Fig. 10 (above). F.M. detector response characteristic.

Fig. 8 (above left). A typical a.m. detector circuit.

Fig. 9 (left). A typical f.m. discriminator (Ratio Detector).



to maintain the receiver on tune. However with the modern crystal controlled oscillators used today this feature may not be used.

Although amplitude pulses will already have been removed by the limiter stage (to be described later) the f.m. discriminator will also reject any amplitude pulses remaining on the signal, because such pulses will be presented to the diodes in equal amounts, and cancel out in the same way as a carrier at the centre frequency. Many of today's transceivers use a "quadrature" detector. This is normally included into an integrated circuit which also contains the i.f. amplifiers, limiters

and meter drive circuits. Such a circuit is shown in Fig. 11.

### THE I.F. AMPLIFIER

The i.f. amplifier stage is different for the two systems because in the case of the a.m. signal we want to amplify it and pass it on with the minimum of amplitude distortion, and in the f.m. case we want to remove any amplitude variations and only pass on changes in frequency.

Fig. 12 shows a typical a.m. i.f. stage and Fig. 13 one used for f.m. These are simple versions as the modern circuit would almost certainly use integrated cir-

cuits for these. In the case of the a.m. circuit, automatic gain control is applied via R5 so that as the signal gets stronger the gain is reduced to prevent the next stage overloading. The f.m. circuit is allowed to operate at maximum gain all the time so that the next stage is fully saturated. This next stage is the "limiter" and has no counterpart in the a.m. receiver.

Fig. 14 shows a simple limiter. The main difference between this and the i.f. amplifier is that the collector voltage is held down to a low level so that the output is prevented from increasing once a certain level has been reached. The graph in Fig. 15 shows what happens.

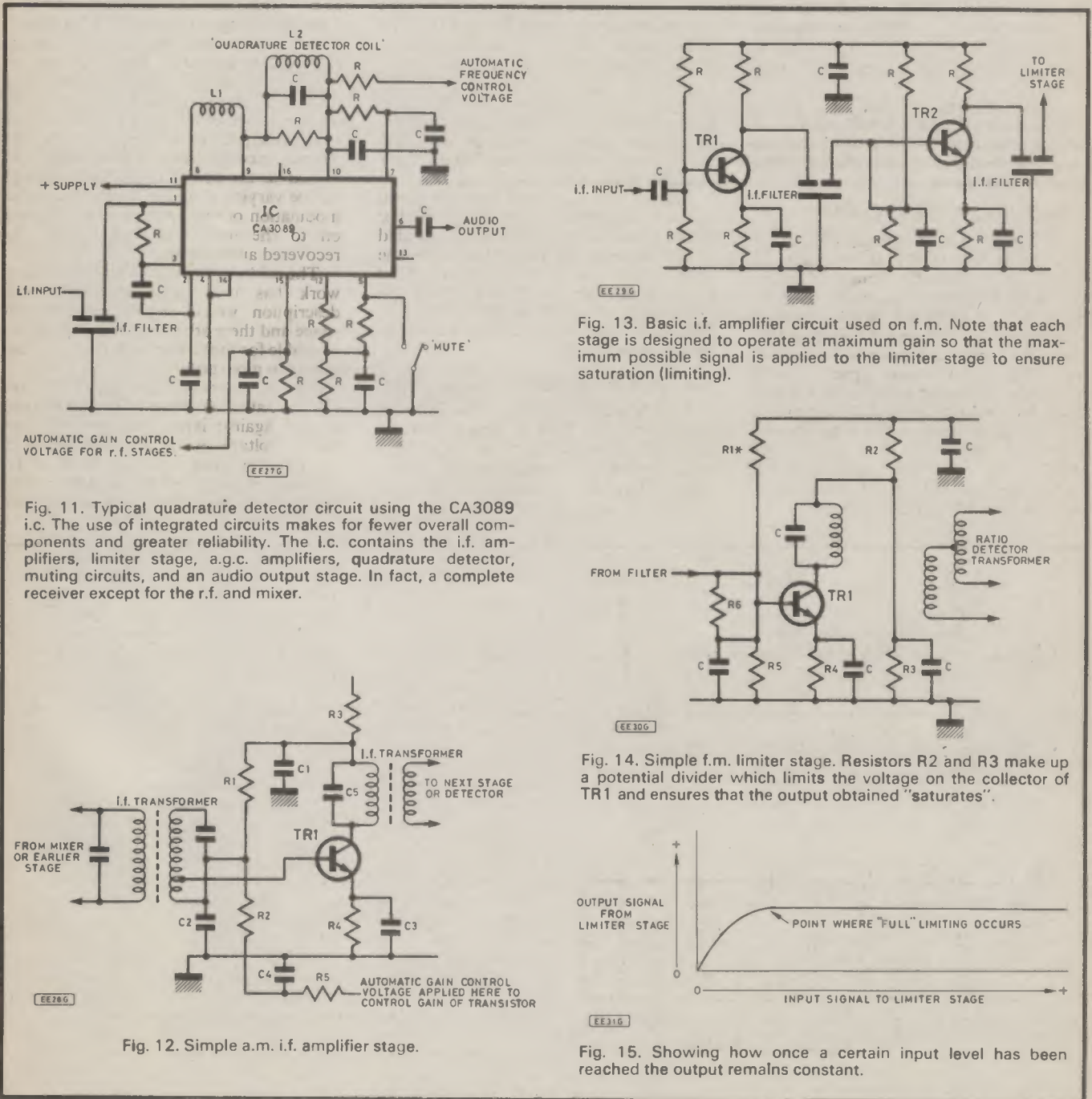


Fig. 11. Typical quadrature detector circuit using the CA3089 i.c. The use of integrated circuits makes for fewer overall components and greater reliability. The i.c. contains the i.f. amplifiers, limiter stage, a.g.c. amplifiers, quadrature detector, muting circuits, and an audio output stage. In fact, a complete receiver except for the r.f. and mixer.

Fig. 12. Simple a.m. i.f. amplifier stage.

Fig. 13. Basic i.f. amplifier circuit used on f.m. Note that each stage is designed to operate at maximum gain so that the maximum possible signal is applied to the limiter stage to ensure saturation (limiting).

Fig. 14. Simple f.m. limiter stage. Resistors R2 and R3 make up a potential divider which limits the voltage on the collector of TR1 and ensures that the output obtained "saturates".

Fig. 15. Showing how once a certain input level has been reached the output remains constant.

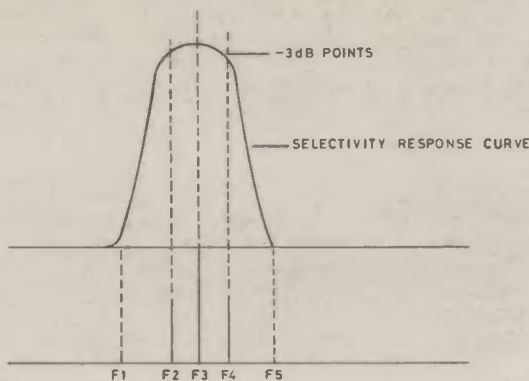


Fig. 16. Points F1 and F5 are the absolute limits of the selectivity curve. F2 and F4 represent the point where the selectivity curve would be about -3dB down on its maximum response. These also represent the two sidebands, one above the carrier, F3, and one below. Any sidebands spaced further out than these would be attenuated by the selectivity curve until at points F1 and F5 there would not be any output at all. From this it can be seen that the higher the selectivity (narrower) the greater the loss of the higher audio frequencies.

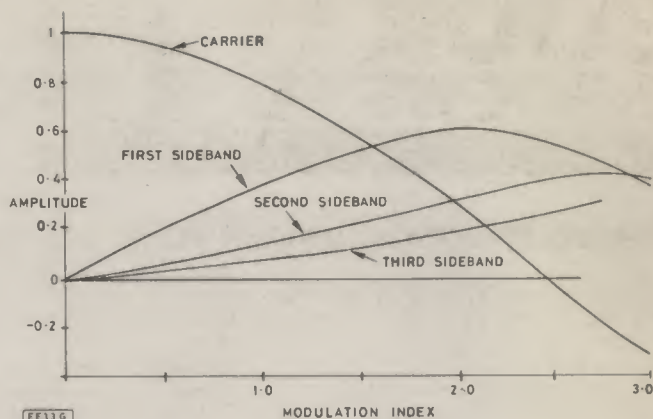


Fig. 17. Showing how the various sidebands vary in amplitude with the modulation index. The carrier would go through zero at a number of points at higher values of modulation index. This also applies to the sidebands.

Once the maximum output has been reached any further increase in input will not cause a corresponding increase in output. Thus any interference pulses on the signal are effectively removed, it also means that all signals irrespective of their strength are passed to the discriminator at the same signal level, effectively removing any need for an r.f. gain control on an f.m. receiver. Some f.m. receivers have a.g.c. applied to their r.f. amplifier stages before the mixer, to prevent overload and cross-modulation, but that is another story and also applies to a.m. Here we are only concerned with the main differences between the two.

## GENERATING THE A.M. OR F.M. SIGNALS

The main difference between the a.m. and f.m. transmitter is in the way the signal is produced. Looking first at the a.m. system, we find that the modulation is mixed with the carrier wave and this results in the amplitude of the carrier varying at the same rate as the modulating signal.

This modulation process also produces "sidebands" adjacent to the main carrier frequency. For example, if the modulation signal was at 1kHz and the main carrier frequency was at 1MHz then the modulation process would also produce frequencies at 1MHz plus 1kHz and 1MHz minus 1kHz, that is, three separate radio frequency signals.

When speech is used to modulate the carrier the sidebands can extend to plus and minus 3kHz, a total bandwidth of 6kHz. The a.m. receiver must be able to accept these in order to reproduce the original audio without distortion. In other words the receiver bandwidth (selectivity) would be a minimum of 6kHz. Fig. 16 shows a typical a.m. receiver selectivity curve and the type of signal it will accept.

With the f.m. transmitter the modulating signal is used to shift either the carrier frequency or the phase; in practice the end result is the same and most so called f.m. transmitters are in fact phase modulated. This modulation process also sets up sidebands but the number of sidebands that occur on f.m. depend on the relationship between the modulating frequency and the amount of deviation used. The relationship between these two is called the "modulation index".

$$\text{Modulation index} = \frac{\text{Carrier frequency deviation}}{\text{Modulating frequency}}$$

for example, if our modulation frequency is 3kHz (same as our a.m. example) and our maximum deviation is 5kHz (the maximum for the UK CB service), we get

$$\frac{5000}{3000} = 1.666$$

For the same deviation the modulation index at 300Hz would be 16.666 and so on. The deviation figure is for a frequency shift on one direction, so a 5kHz deviation means plus and minus 5kHz, that is a total of 10kHz.

A full technical explanation would take up far too much space but a given modulating frequency will produce a number of sidebands whose individual amplitude will depend on the modulation index for the particular system. A rough rule of thumb calculation for f.m. overall bandwidth is:  $2Fd + F_{mod}$ , where  $Fd$  is the maximum deviation and  $F_{mod}$  is the highest modulating frequency used.

In our example, of maximum deviation 5kHz and 3kHz maximum modulating frequency we get,  $2 \times 5 + 3 = 13$ kHz. In other words our bandwidth is 13kHz compared with 6kHz of the a.m. system for the same modulating frequency.

So clearly, the maximum deviation and modulating frequency must be restricted

if a larger number of stations are to operate in a given band of frequencies (channels). Just for interest the BBC stereo system requires a bandwidth of 250kHz and is known as "wide-band f.m." whereas the CB specification calls for a maximum bandwidth of 13kHz and is known as "narrow-band f.m."

## SHIFT OUTSIDE PASSBAND

From the above it can be seen that if the f.m. transmitter is over-deviated or if higher than permitted audio frequencies are used, the signal can shift completely outside the receiver passband, with resulting distortion or even loss of signal.

Fig. 17 shows how the amplitudes of the carrier and sidebands vary with the modulation index. The chart is for a single tone modulation. These sidebands will occur on each side of the carrier. For example, if our modulating frequency is 2kHz and our carrier frequency is 28MHz the first sideband pair will be at 28.002MHz and 27.998MHz, the second pair at 28.004MHz and 27.996MHz, the third pair at 28.006MHz and 27.994MHz, and so on. The amplitude of these sidebands will depend on the modulation index, not the amount of frequency deviation present.

Note also that in Fig. 17 the carrier strength varies with the modulation index, compared to a.m. where the carrier amplitude is constant and only the sideband amplitudes vary. In the f.m. system the energy that appears in the sidebands comes from the carrier, the total power is the same regardless of the modulation index (on a.m. the total power varies with the modulation).

Since the amplitude is constant with an f.m. signal any amplification can be carried out with class "C" biased stages for maximum efficiency (or as mentioned earlier a receiver can use amplitude limiter stages). □

# BOOK REVIEWS



## MACHINE CODE FOR BEGINNERS

**Author** L. Watts & M. Wharton  
**Price** £1.99 limp  
**Size** 240 x 168mm. 48 pages  
**Publisher** Usborne  
**ISBN** 0-86020-735-8

ONE of the most difficult areas of computing is machine code programming, not only is it more difficult to write, but it is less easy to understand than a program in BASIC.

Machine Code For Beginners is a book designed to introduce fun into learning machine code and with the aid of easy text and cartoon drawings it manages to succeed. The book has 48 pages and starts with a basic description of machine code and its advantages and disadvantages. Although the contents of this book are aimed at a fairly low level of computing knowledge, the subject matter becomes progressively more difficult as you delve further.

A particularly useful section are the Decimal/Hex conversion charts, because in machine code programs, numbers and addresses are always written in hexadecimal. Plenty of conversion examples are given, so no difficulties should be encountered.

Mnemonics are short words which represent an instruction to the computer and are much easier to understand than hex. A program in mnemonics is called an assembly language program and is fully explained and example programs are provided.

On the whole the book provides a reasonable introduction to machine code programming and does not try to baffle the reader.

R.A.H.

## ROBOTICS

**Author** T. Potter & I. Guild  
**Price** £1.99 limp  
**Size** 240 x 168mm. 48 pages  
**Publisher** Usborne  
**ISBN** 0-86020-724-2

ROBOTICS is classed as a complete science all on its own, although computing does play an important part in the control of the robot. There are many robots in existence today which are mainly used for industrial processes and doing jobs that would be impossible for people to do.

The text gives the reader a sufficient insight into the uses of robots and the basic technical format that is required to operate one. The book also provides constructional details for a computer-controller micro-robot with step by step instructions on how to make an electronic interface circuit to connect the robot to a computer.

In the Usborne tradition the book is full of colour illustrations which enhance the overall appearance of the pages and help support the text. There are 48 pages contained within and the text touches briefly on the most important areas of robotics. Cybernetics, the science of control and communication in both machines and living organisms is also briefly explained, which is just as well, because this is a highly specialised area.

R.A.H.

**NEXT  
MONTHS  
ISSUE...**

PRACTICAL

# ELECTRONICS

JUNE ISSUE ON SALE FRIDAY, MAY 4

## HYPERCHASER

### LIGHTING EFFECTS UNIT

## Test Gear Buyers Guide

### OSCILLOSCOPES · FUNCTION GENERATORS POWER SUPPLY UNITS

**FREE**  
**LOGIC  
DESIGN  
CARD-N°4**

# Simple LOOP BURGLAR ALARM

Chris Lare

**M**OST designs for alarm units are very flexible and quite expensive. The unit described here is a simple loop alarm which was originally designed to be connected to a wire loop of the sort used in shops to protect small and easily stolen articles such as radios. The design does, however, have many applications since the principle is that the alarm sounds for a preset length of time once the loop is broken. It would be possible to connect the loop to a magnetic reed switch or even foil strips as often used on large windows.

The circuit is designed around CMOS logic components and consumes less than 10 $\mu$ A in its standby condition and so it is well suited to being battery powered. Naturally, the supply current rises dramatically once the alarm sounds. The alarm tone itself is pulsed at half second intervals which not only makes it much more noticeable but cuts down battery consumption by some 50 per cent.

## OSCILLATIONS

It has already been mentioned that the circuit is designed around CMOS logic i.e.s to minimise power consumption. It is important to note that this type of logic will not work reliably when fed with slow moving analogue signals, and therefore the levels supplied to each gate at any time should be close to the supply voltage.

Other voltages, particularly those around the half supply area, are likely to cause the gate to oscillate at a high frequency which will cause the i.c. to overheat and eventually destroy itself, not to mention the apparent spurious action of the circuit involved. It may be of interest to note that TTL logic is much more sensitive to this type of abuse than CMOS parts, and half supply input voltages will almost certainly quickly destroy the gate; although for a different reason.

Consider a typical CMOS gate as shown in Fig. 1. This is an inverting gate so that when the input voltage is close to 0 volts the output is high. As the input voltage is increased the output will eventually go low, but at some time in between the gate may become unstable and several sam-

ples measured oscillated at 2MHz as well as consuming large amounts of current. This oscillation becomes worse with increasing input series resistance but may be reduced by the addition of a 100pF capacitor between the gate input and 0 volts which effectively reduces the source impedance presented to the gate.

## SCHMITT TRIGGERS

The most popular way to clean up a slow moving edge such as this is to employ a Schmitt Trigger which operates by applying feedback across the logic gates. Some logic gates are actually manufactured for this purpose including the CMOS 4093 (quad 2-input NAND). These require no further treatment of the input signals but do tend to be much more expensive than the equivalent standard gate. Fig. 2 illustrates a Schmitt Trigger designed around standard CMOS gates and serves as a suitable example to explain the Schmitt action.

With 0 volts applied to the 330k $\Omega$  input resistor ( $V_{in}$ ) the output of the first gate will be high and naturally the output of the second gate will be low. This means that until the output from the second gate starts to go high the 1M $\Omega$  resistor will act as a potential divider to any input voltage applied, such that the input gate voltage ( $V_{gate}$ ) will be only about two-thirds  $V_{in}$ . Obviously therefore, an input voltage of

some 3 volts will be required before the gate starts to change its output state.


Immediately this happens however, the output of the second gate will rise and the 1M $\Omega$  resistor will no longer act as a potential divider to ground, but to the +ve supply since the gate output will pull it high. Immediately therefore the starting voltage on the gate of some 2 volts becomes 4 volts without any increase in  $V_{in}$ .

This action is very fast and so the final output is a good edge. Once the gate has changed state the 1M $\Omega$  will tend to source current holding  $V_{gate}$  slightly high and so the input voltage has to be reduced considerably to return the system to its original state. This is the most important feature of a Schmitt Trigger: The input voltage at which switching occurs is different depending on whether the input voltage is rising or falling. This action is called hysteresis and is denoted by a symbol which combines the graphs of rising input and falling output into a box with two tag ends. Hysteresis was originally noticed in magnetic circuits when iron cores tended to retain some magnetisation.
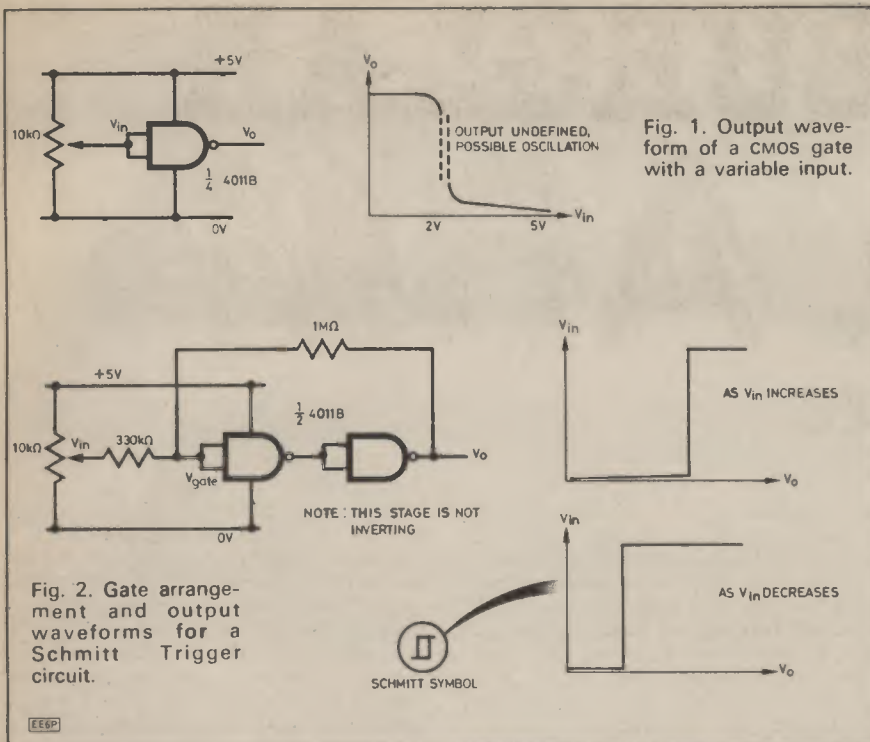
## CIRCUIT DESCRIPTION

The full circuit diagram of the alarm is shown in Fig. 3. In normal non-active conditions the "loop" pins will be joined





together which means that the inputs to gate IC1a are held high by R1.

When the loop is broken R2 pulls these inputs low, but it must be a fairly high value resistor to minimise current flow when the loop is joined. R3 is present to protect the gate inputs from static and mains pick-up when the loop is open.

As soon as the loop is broken the gate output goes high which rapidly charges up C1 by means of R4 and D1. The

voltage across C1 then triggers the Schmitt Trigger formed by the two gates of IC1b and IC1c. When the loop is joined again pin 3 of IC1 will go low which will discharge C1 through R5, R4 having no effect because of the series diode.

The relative high value of R5 ensures that C1 takes a long time to discharge sufficiently to alter the output state of the Schmitt Trigger and so allows the alarm

to go on ringing some time after the loop has been rejoined.

It must be noted that R5 is not solely responsible for this reset delay and that in its high state the Schmitt Trigger sources some current through R6 and R7 helping to increase the reset time.


Obviously some form of manual reset is required since the alarm is not required once someone has been alerted and total reset is obtained by simply removing the power for a brief period. This allows C1 to discharge via D2 and hence resets the circuit.

## OSCILLATORS

The output from the Schmitt is used to gate two oscillators, also built around standard CMOS parts. The first formed by IC1d and IC2b uses a 220pF capacitor and operates at about 700Hz, whilst the second formed by IC2a and IC2d operates at 1.3Hz. Only when the output of the slow oscillator is high will the tone be allowed on the output by virtue of gate IC2c. S1 serves as a test switch and may be omitted if desired, the main advantage of this is the alarm only sounds when the switch is pressed. R8 protects gate IC1c when the switch is pressed.

The tone output on pin 10 of IC2 is buffered by two transistors arranged such that when the alarm is inactive pin 10 is high and no current is consumed. In this state TR1 will be off (since it is *pnp*) and so no current will be available to switch TR2 on. When pin 10 does fall TR1 turns on and sources current to TR2 which drives the speaker at some 700Hz in 0.6 second bursts. Diode D3 blocks any back e.m.f. from the speaker which might damage other parts of the circuit. A 22-

Fig. 3. Circuit diagram of the Loop Alarm.

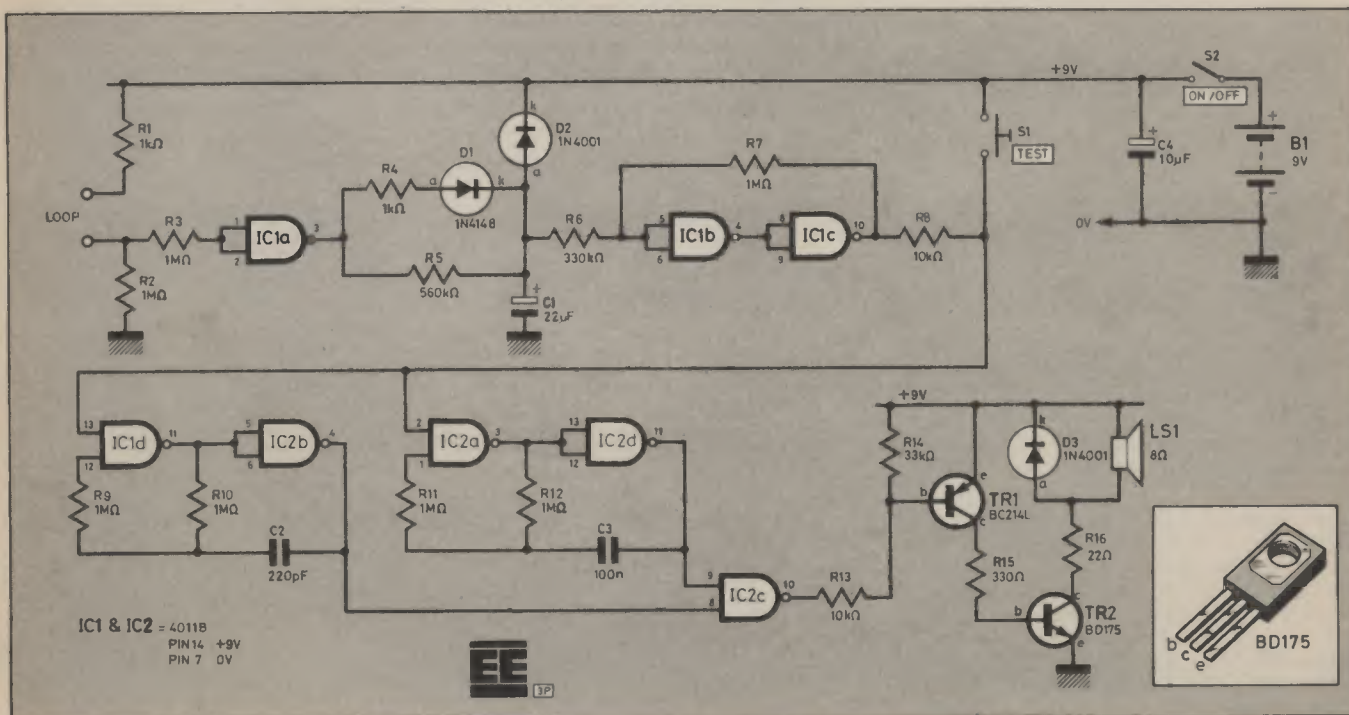

ohm resistor was inserted in series with the prototype speaker to limit the volume slightly since the shop display was always staffed but this may be linked instead if required.

The complete circuit was decoupled with a 10µF electrolytic capacitor.

## CONSTRUCTION

### PRINTED CIRCUIT BOARD

The prototype unit was assembled on a p.c.b. which gives a much neater and more reliable result than circuits built on stripboard. Fig. 4 shows the design of the p.c.b. and the component layout is shown in Fig. 5. The components should be placed into the board in a logical way, i.e., the smallest first, although the 4011s should be left until last. The i.c.s used in the prototype were directly soldered in but sockets may be used if preferred. Pay

## COMPONENTS

### Resistors

R1,4 1kΩ (2 off)  
R2,3,7,9, 1MΩ (7 off)  
10,11,  
12

R5 560kΩ  
R6 330kΩ  
R8,13 10kΩ (2 off)  
R14 33kΩ  
R15 330Ω  
R16 22Ω ½W carbon

All resistors ¼W carbon except where otherwise stated

### Capacitors

C1 22µF 10V tantalum  
C2 220pF polystyrene  
C3 100n polyester C280  
C4 10µF 16V electrolytic

### Semiconductor

D1 1N4148  
D2,3 1N4001 (2 off)  
TR1 BC214L  
TR2 BD175  
IC1,2 4011B quad 2-input NAND gate (2 off)

### Miscellaneous

Printed circuit board: single-sided, size 105 x 42mm; EE PCB Service, Order code 8405-01; terminal pins (8 off); plastic case 190 x 60 x 110mm; S1 press-to-make switch; S2 keyswitch; battery PP9; battery clips for PP9; 8-ohm speaker 85mm square; polystyrene foam; aluminium sheet; loop plugs and sockets (if required); connecting wire; 6BA bolts 25mm (4 off); 6BA nuts (12 off); grommet.

Approx. cost  
Guidance only

**£16**

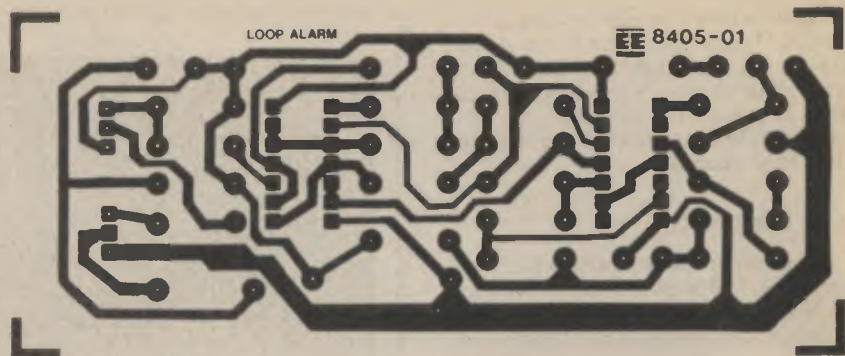


Fig. 4. P.c.b. design.


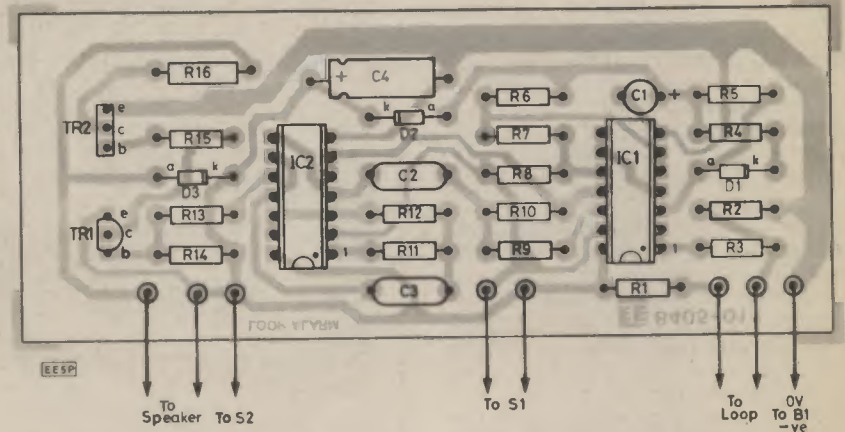


Fig. 5. Component layout.

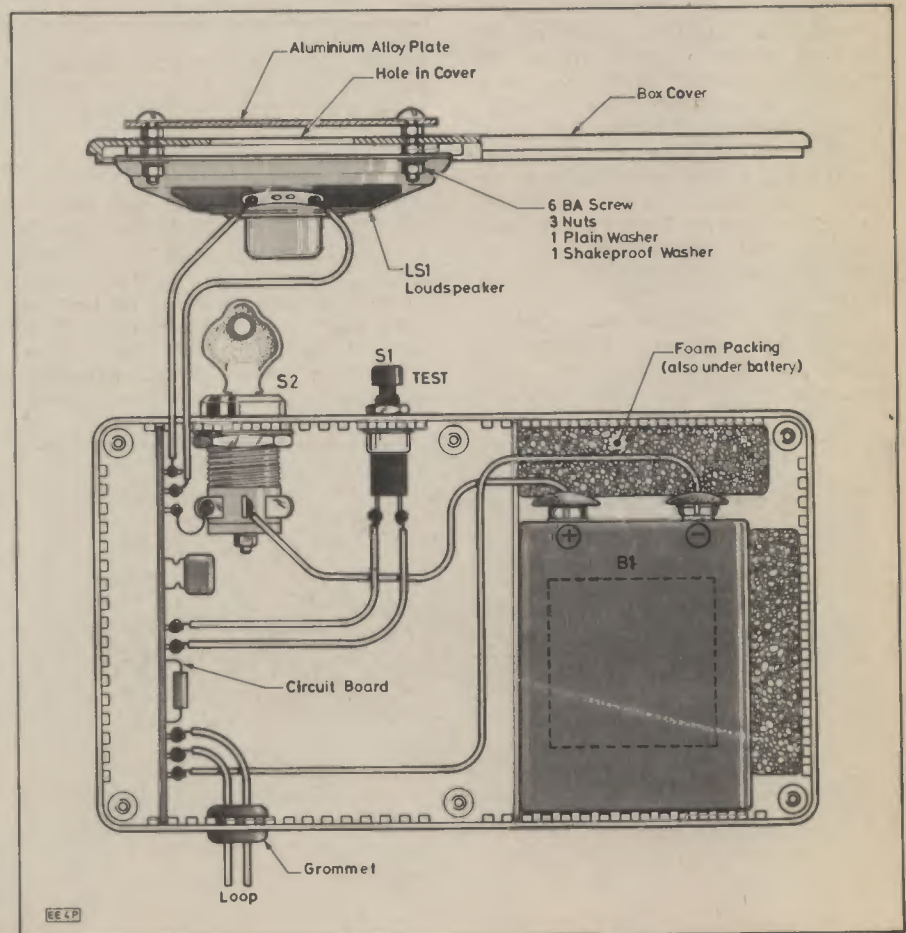

particular attention to the orientation of the BD175 transistor which is not always obvious; the side of the transistor with the metal plate should face the rest of the circuit board (see Fig. 2).

It is best to bench test the circuit board before final assembly.


## CASE ASSEMBLY

The prototype was housed in a black plastic box 190 × 60 × 110mm. The circuit board is exactly the right size to slip into the slots provided in this type of box. It is suggested that the speaker be mounted first into the lid of the box to ensure that suitable clearance is left for all the other major components. Fig. 5 shows the general assembly and the method of mounting the speaker.

A 50mm hole should be cut in the middle of one end of the box lid, and the speaker mounting hole positions marked and drilled. The hole may be covered with an aluminium plate cut slightly larger than the hole with four corner holes corresponding to the speaker mounting holes. This plate was painted matt black for the prototypes. Assemble the speaker as shown in Fig. 5. Note that three nuts are used on each bolt, one to space off the metal plate, one to space the speaker and one to hold the speaker in place. Additional washers may be required if the speaker has unusual mounting holes or none at all, in which case the rim must be clamped.

Position the circuit board at one end and then choose the positions for the other components. Note that if a keyswitch is used care must be taken before assembly to ensure that it does not foul the speaker. Wire up the unit as shown in Fig. 6. Cut a piece of aluminium 105 × 35mm to act as a battery retainer and place it and the battery in the box. Two pieces of polystyrene foam were glued in place to hold the battery secure.

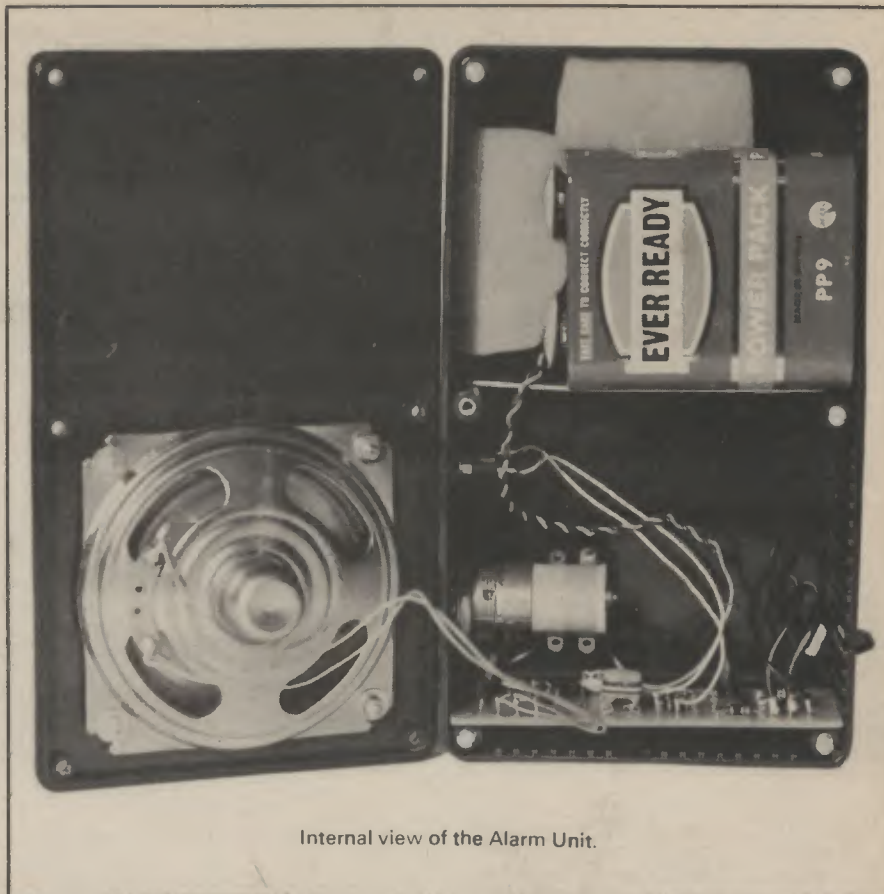Since the prototypes were used as security loops the loop consisted of lengths of black 24/0.2in wire each terminated in a 3.5mm jack plug and



socket. Two lengths were connected to the box itself, again one end terminated with a plug, the other with a socket.

## TESTING

Connect the complete unit with the loop closed to a battery and speaker. Testing may be accomplished by simply opening the loop when the alarm should sound. If it does, reconnect the loop and check that the alarm keeps on for 30–40 seconds. Finally break the loop quickly and remake it which should again sound the alarm but only for the 30–40 seconds.


If these checks are correct measure the current consumption of the board. Firstly connect an ammeter in series with the supply line set to the highest range, switch on and wait for a minute. This is to allow the circuit to settle. Progressively increase the range until the current can be measured; this should be less than 20µA. If it is much greater than this ensure that all the CMOS pins that should be connected together actually are, and that the transistors are fully off.

If the unit does not fully work check each stage in turn, starting at the output of IC1 pin 3, through the voltage on C1, the Schmitt operation, and finally the oscillator and output stages.
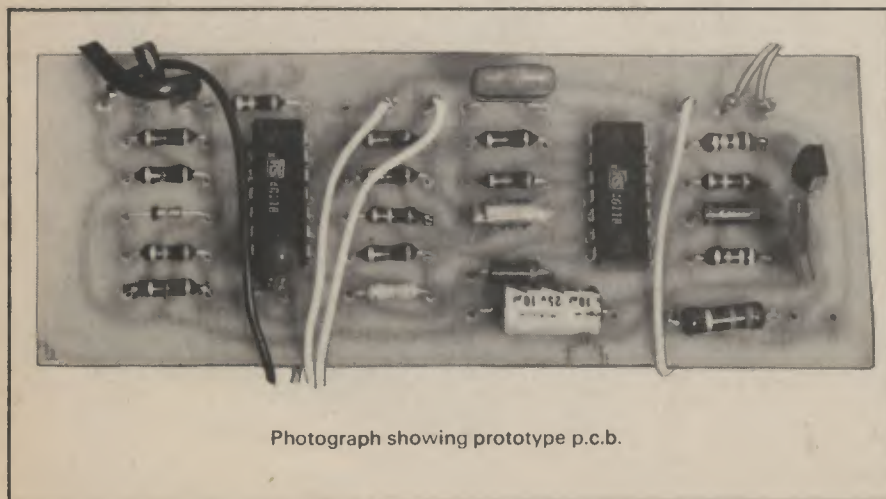
## IN USE

The prototype units were connected to a 10-metre loop split into eight sections and two one-metre lengths attached directly to the alarm unit itself. This loop was then threaded through the handles of the goods to be protected. Other uses where the loop is connected to window foil or even pressure pads under a carpet are not hard to imagine.

Again in a shop situation it would be far nicer to have a pressure mat in front of the counter instead of a bell push marked "press for attention". In this sort of application it would be better to replace the keyswitch with a simple press-to-break switch since it does not really matter who resets it. □



NEW · NEW · NEW · NEW  
**PRODUCTS**  
 NEW · NEW · NEW · NEW



### IN THE PICTURE

**T**HE Bradford-based manufacturer of colour computer monitors, Microvitec, has just announced that it is making available its Cub range of 14in and 20in monitors to home users.

The Cubs are already familiar to schools as they are the only colour monitor to be approved under the Government's "Micros in Schools" programme and over 20,000 primary and secondary schools, not to mention colleges of further education, are claimed to be users.

They claim that the monitors are better than conventional television sets in two ways. First of all, the screens have up to four times as many "dots" as ordinary colour television tubes and so can reproduce much finer detail.

Secondly, because they are "RGB" monitors, the Cubs can accept signals straight from the computer without the necessity for those signals to be encoded on a carrier by the computer and then decoded by the conventional TV circuitry.

Because the coding and decoding have been eliminated, the clarity of the picture or display is claimed to be much sharper. The greater resolution offered by the Cub range is seen by Microvitec as an important feature, particularly as a text-width of 80 characters is becoming an industry standard for the microcomputer.

*Microvitec Ltd.,  
 Dept EE, Futures Way,  
 Bolling Road, Bradford,  
 West Yorkshire BD4 7TU.*

### ACT ONE

**A** COMPLETE analogue training instrument containing all the functions required for studying and experimenting with active filters, operational amplifiers and other analogue circuitry is being marketed by E & L Instruments.

Called the ACT-1 it contains four regulated, short-circuit proof, d.c. power supplies. Two are fixed at  $\pm 12V$  d.c., the third is variable from 0 to  $+7.5V$  d.c. and the fourth is variable from 0 to  $-7.5V$  d.c.

Integral to the front panel is a function generator circuit providing waveform outputs for amplifier experiments. It has outputs of sine, triangle, square and

TTL as well as a.m. and f.m. modulation control lines.

The front panel also contains a number of uncommitted devices, including a  $10k\Omega$  slide potentiometer,  $100k\Omega$  slide potentiometer, two slide switches, two BNC connectors and one uncommitted solderless breadboard.

To support the "trainer" a series of manuals are being produced.

For more details of price and addresses of local stockists contact:

*E & L Instruments Ltd.,  
 Dept EE, Whitegate Industrial  
 Estate, Whitegate Road,  
 Wrexham, Clwyd LL13 8UG.*



### OSCILLOSCOPE AMPLIFIER ADD-ON

**T**HE  $\mu$ Amplifier from Otter Electronics allows signals as minute as  $100\mu V$  from d.c. to 2MHz to be viewed and measured on most oscilloscopes. The amplifier offers sensitivities from  $100\mu V$ /division to 50mV/division with a.c. or d.c. input coupling, and maintains a constant output of 100mV/division.


To make full use of the high sensitivity a differential input is provided so that common mode signals can be minimised. Also to improve the display, a bandwidth limiting switch is provided to

reduce the upper frequency limit to 20kHz or 1kHz.

This amplifier will find many uses in audio and video work enabling monitoring of signals direct from playback heads and measuring ripple. Even physiological signals come within the amplifier's wide performance.


The amplifier is powered from PP3 batteries and further details and addresses are obtainable from:

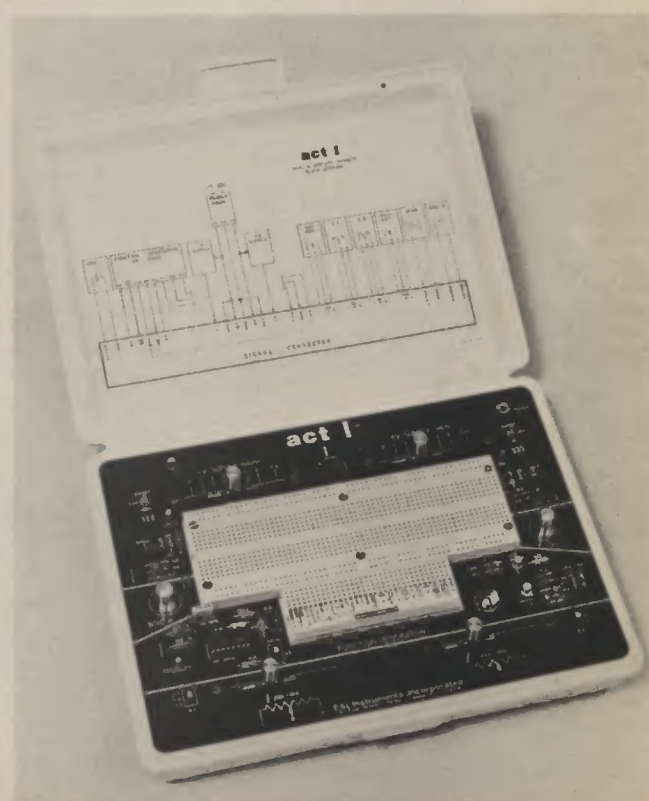*Otter Electronics Ltd.,  
 Dept EE, Otter House,  
 West Underwood,  
 Olney, Bucks MK46 5JS.*




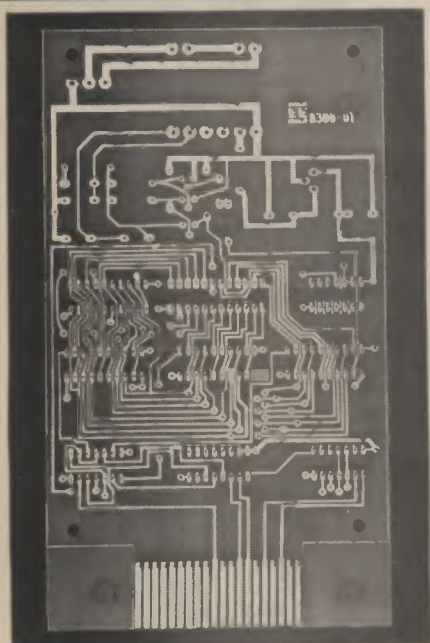
# EVERYDAY ELECTRONICS PRINTED CIRCUIT BOARD SERVICE



Printed circuit boards for certain EE constructional projects are now available from the EE PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Remittances should be sent to: EE PCB Service, Everyday Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Cheques should be crossed and made payable to IPC Magazines Ltd.

We regret that the ordering codes for the August projects have been incorrectly quoted in the Sept-Oct issues. Correct codes are given here.

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps.

Readers ordering both p.c.b.s and software cassettes may send a single cheque/PO for the combined amounts listed.

\*Set of four boards.

\*\*Calibrated with C1, VR1 and IC3 fitted.

M.I.T.—Microcomputer Interfacing Techniques, 12-Part Series.

Readers are advised to check with prices appearing in current issue before ordering.

PROJECT TITLE	Order Code	Cost
Eprom Programmer, TRS-80 (June 83)	8306-01	£9.31
Eprom Programmer, Genie (June 83)	8306-02	£9.31
Eprom Programmer, TRS-80 & Genie (June 83)	8306-03	£1.98
User Port Input/Output M.I.T. Part 1 (July 83)	8307-01	£4.82
User Port Control M.I.T. Part 1 (July 83)	8307-02	£5.17
Storage 'Scope Interface, BBC Micro (Aug 83)	8308-01	£3.20
Car Intruder Alarm (Aug 83)	8308-02	£5.15
High Power Interface M.I.T. Part 2 (Aug 83)	8308-03	£5.08
Pedestrian Crossing Simulation M.I.T. Part 2 (Aug 83)	8308-04	£3.56
Electronic Die (Aug 83)	8308-05	£4.56
High Speed A-to-D Converter M.I.T. Part 3 (Sept 83)	8309-01	£4.53
Signal Conditioning Amplifier M.I.T. Part 3 (Sept 83)	8309-02	£4.48
Stylus Organ (Sept 83)	8309-03	£6.84
Distress Beacon (Sept 83)	*8309-04	£5.36
Distress Beacon Pocket Version (Sept 83)	8309-05	£3.98
D-to-A Converter M.I.T. Part 4 (Oct 83)	8310-01	£5.77
High Power DAC Driver M.I.T. Part 4 (Oct 83)	8310-02	£5.13
Electronic Pendulum (Oct 83)	8310-03	£5.43
TTL/Power Interface for Stepper Motor M.I.T. Part 5 (Nov 83)	8311-01	£5.46
Stepper Motor Manual Controller M.I.T. Part 5 (Nov 83)	8311-02	£5.70
Digital Gauss Meter (Nov 83)	8311-03	£4.45
Speech Synthesiser for BBC Micro (Nov 83)	8311-04	£3.93
Car On/Off Touch Switch (Nov 83)	8311-05	£3.11
4-Channel High Speed ADC (Analogue) M.I.T. Part 6 (Dec 83)	8312-01	£5.72
4-Channel High Speed ADC (Digital) M.I.T. Part 6 (Dec 83)	8312-02	£5.29
TRS-80 Twin Cassette Interface (Dec 83)	8312-03/09	£7.43
Environmental Data Recorder (Dec 83)	8312-04	£7.24
Touch Operated Die (Dot matrix) (Dec 83)	8312-05/06	£4.34
Touch Operated Die (7-segment) (Dec 83)	8312-05/07	£4.34
Continuity Tester (Dec 83)	8312-08	£3.41
Central Heating Pump Delay (Jan 84)	8401-01	£3.33
Biological Amplifier M.I.T. Part 7 (Jan 84)	8401-02	£6.27
Temp. Measurement & Control System for ZX Computers (Jan 84)		
Analogue Thermometer Unit	8401-03	£2.35
Analogue-to-Digital Unit	8401-04	£2.56
Games Scoreboard (Jan 84)	8401-06/07	£9.60
Eprom Programmer/ROM Card for ZX81 (Feb 84)	**8402-01	£7.84
Oric Port Board M.I.T. Part 8 (Feb 84)	8402-02	£9.56
Negative Ion Generator (Feb 84)	*8402-03	£8.95
Temp. Measurement & Control System for ZX Computers (Feb 84)		
Relay Driver Unit	8402-04	£3.52
Latched Output Port M.I.T. Part 9 (Mar 84)	8403-01	£5.30
Buffered Input Port M.I.T. Part 9 (Mar 84)	8403-02	£4.80
VIC-20 Extension Port Connector M.I.T. Part 9 (Mar 84)	8403-03	£4.42
Commodore 64 Extension Port Connector M.I.T. Part 9 (Mar 84)	8403-04	£4.71
Digital Multimeter Add-On for BBC Micro (Mar 84)	8403-05	£4.63
Multipurpose Interface for Computers	8404-01	£5.72
Data Acquisition "Input" M.I.T. Part 10 (Apr 84)	8404-02	£5.20
Data Acquisition "Output" M.I.T. Part 10 (Apr 84)	8404-03	£5.20
Data Acquisition "PSU" M.I.T. Part 10 (Apr 84)	8404-04	£3.09
Timer Module (Apr 84)	8404-05	£3.58
A.F. Sweep Generator (Apr 84)	8404-06	£3.55
Quasi Stereo Adaptor (Apr 84)	8404-07	£3.56
Simple Loop Burglar Alarm (May 84)	8405-01	£2.92
Computer Controlled Buggy M.I.T. Part 11 (May 84)		
Interface/Motor Drive	8405-02	£4.75
Collision Sensing	8405-03	£3.04
Power Supply	8405-04	£4.53



# SQUARE one FOR BEGINNERS

Logic gates are used in many electronic applications to perform a variety of specific functions. The idea of logic is to have only two distinct states known as high or low, on or off, or simply 1 or 0. In electronic circuits these states are determined by voltage levels present at the input or output of the gates. Each gate has two or more inputs, and one output whose logical state can be manipulated by its input condition.

There are several "Logic Families" available, the most common being Transistor-Transistor Logic (TTL) and Complementary Metal-Oxide Semiconductor (CMOS). Their characteristics are quite different but the same logic rules apply to both. These gates are usually contained in dual-in-line (d.i.l.) i.c. packages, a typical example being a quad 2-input NAND gate (TTL-7400), which has 14 pins.
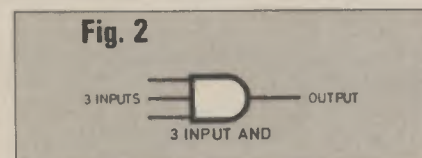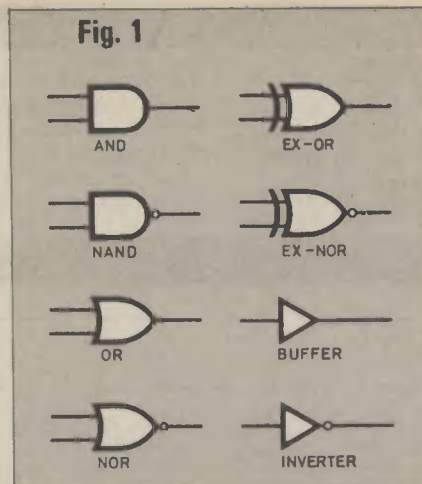
## LOGIC SYMBOLS

The logic symbols used in circuit diagrams are shown in Figs. 1 to 4, and input/output functions are shown in the truth tables. A 0 and 1 represent low and high voltage levels, respectively.





The three basic logic functions can be explained as follows:

The AND function will always give a low output unless all its inputs are high, for example, any 0 in will give a 0 out.

The OR gate will give a low output unless any of its inputs are high, for example, any 1 in will give a 1 out.

The EX-OR gate will give a high output if only one input is high (not both).

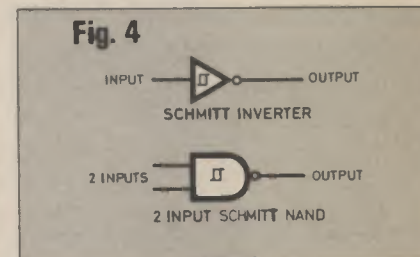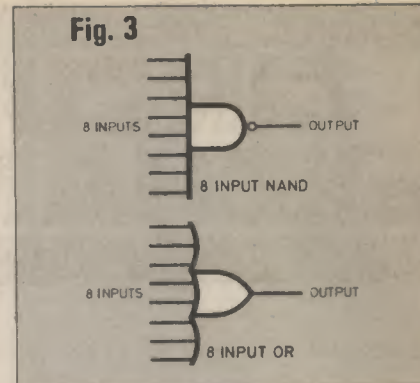Each of the above gates is available with inverted outputs, thus giving: NAND, NOR and EX-NOR functions. An inverted logic level is one that is changed from a high to low, or low to high. For example, any 1 into a NOR gate will give a 0 out. Logic gates are available with up to eight inputs with exception of the EX-OR and EX-NOR which can have only two inputs.



Other gates which are commonly used are the Buffer, Inverter and "Schmitt" triggered gates. Buffers and Inverters are single input devices used to buffer previous outputs. The buffer will give the same logic level at its output, as applied to its input, whereas the inverter will give the inverse. "Schmitt" triggered devices are fast switching inverting gates used in high speed circuits.

There are limitations to the use of these chips which vary from one type of i.c. to another. However, they are all clearly defined in manufacturers' data sheets. Examples of limits are supply voltages, load currents and fan-out capability. Fan-out capability, being the number of gates which can be connected to any one output.

## TRUTH TABLES

### AND

Inputs		Output
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

### OR

Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

### EX-OR

Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

### NAND

Inputs		Output
A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

### NOR

Inputs		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0


### EX-NOR

Inputs		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

# CIRCUIT EXCHANGE

This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised. Payment is made for all circuits published in this feature. Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.

## LEVEL CROSSING LIGHTS FLASHER

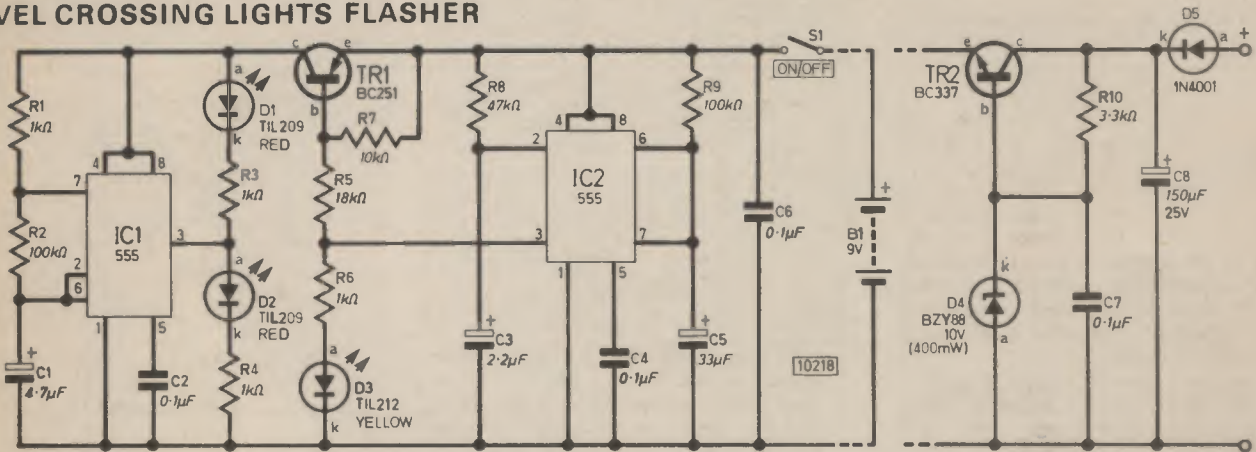

THIS circuit is used to simulate level crossing lights on a model railway. R8 and C3 trigger IC2 as soon as S1 is closed. The yellow l.e.d., D3, lights for about five seconds, after which the output of IC2 goes low. The yellow l.e.d. goes out and TR1 is biased into conduction which starts the red l.e.d.s flashing.

The circuit operates from a 9V battery, but if the railway power controller has a separate fixed voltage d.c. output, then this can be used, although the smoothing and regulator circuit shown above may be required. On an "00" scale layout, 3mm diameter l.e.d.s should be used.

R. Ormston,  
Hythe,  
Hants.


## DIGITAL GAME


THE circuit presented here is a game which uses two l.e.d.s and a large 7-segment display for playing and one of its features is touch operation. To start the game, the player must touch the two touch plates. As soon as these are bridged C1 and C2 will be charged up via D1 and D2. The time constant for these networks will be determined by C1, R2 and C2, R3 respectively, and will change the logical states of two NAND gates from high to low (1 to 0). TR1 and TR2 will switch on for a predetermined time, and thus supply current to the rest of the circuit. Since C1 is smaller than C2, TR1 will switch

off, first causing the oscillator to switch off before the display. The frequency of the oscillator may be adjusted by VR1.

After a certain time, the display will turn off and the power consumption of the whole circuit will be around 1µA or less (because of CMOS i.c.s). Because of the low current drain an on/off switch is not needed. For D3 and D4 a Tri-colour l.e.d. could be used but this device will increase the price of the unit.

Hamid Reza Tajzadeh,  
Tehran,  
Iran.

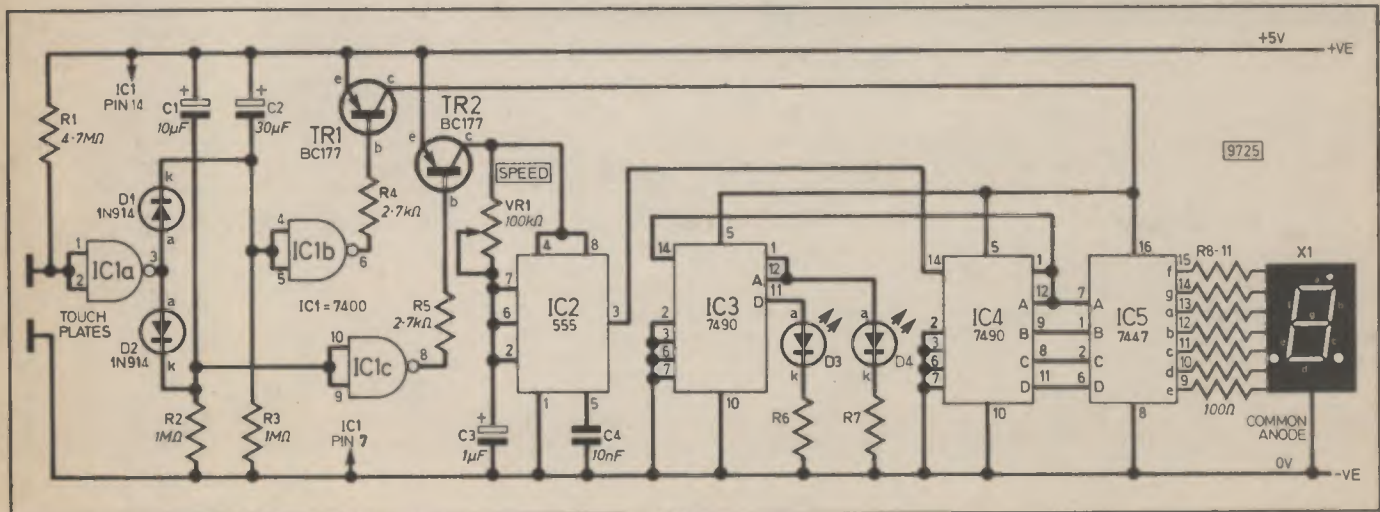

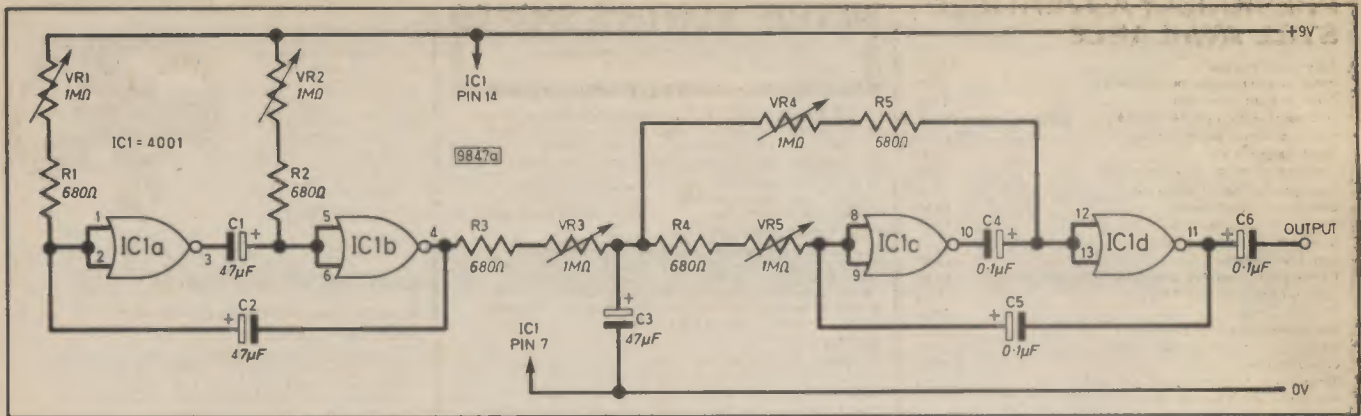

### ELECTRONIC SIREN

THE heart of the electronic siren is a quad two-input NOR gate MC717 integrated circuit or equivalent. The four gates are used in pairs to make two oscillators. One oscillator varies the frequency of the other.


After completing the circuit, setting all pots to mid position should yield a sound much like that of an air-raid siren.

Hamid Reza Nameri, Tehran, Iran.

### ELECTRONIC CANARY

THE Electronic Canary was designed for play sound effects. The circuit is quite simple and is based around an NE 556 timer i.e. Pin 3 is connected to the emitter of TR1 which follows the voltage on C1 to produce a "ramp" waveform. That is the charge/discharge curve of C1. Thus a roughly triangular wave is fed to the audio oscillator causing it to glide between tones.

Shaun Gander, Lewes, Sussex.

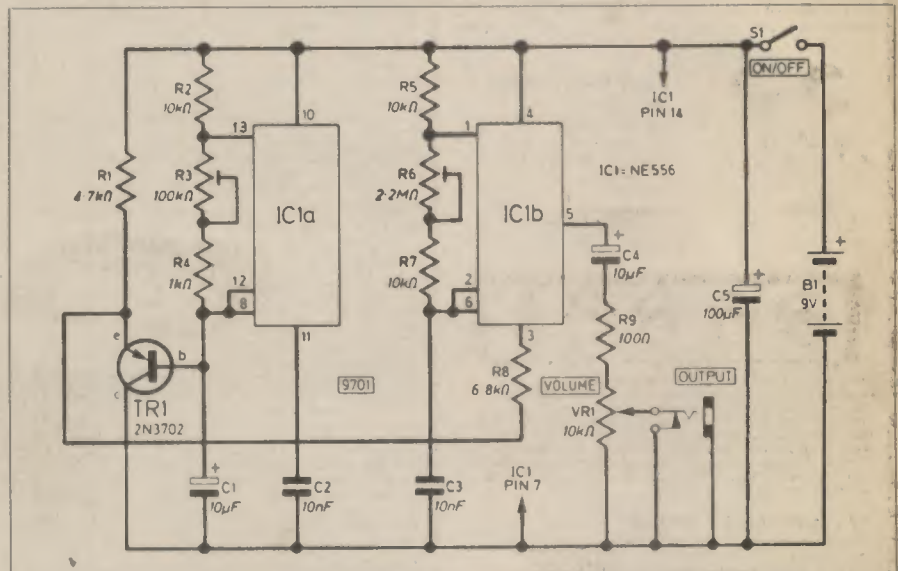

# COUNTER INTELLIGENCE

BY PAUL YOUNG

## Ubiquitous Electronics

A cartoon in the "Nationals" the other day, depicted a little boy being asked by the King what he wanted to be, and he answered, "A jeweller and an electrical engineer". "Why both?" asked the King. "So I can repair watches".

I think I might have used the word, "Electronic" instead of "Electrical" but what impressed me was, that the cartoonist was stating a truth that goes far beyond watches. If the boy in question wanted to be any number of things, Automobile Engineer, Washing Machine Mechanic, Typewriter Repairer, Refrigeration Engineer, the list could be extended almost indefinitely, today, he would still need to have a thorough grounding in electronics.

This can only be good news for the technical schools and the electronics magazines, for what better start can any

youngster have in this field, than reading "Everyday Electronics" and our sister publication, "Practical Electronics".

## Solutions Good and Bad

One thing that pleases all of us is a neat solution to a problem, especially if electronics are involved. Here is a case in point.

High up in the very isolated Ibadin Pass, between France and Spain, telephone engineers wanted to install a coin-operated phone box. Laying cables would have presented a major problem so this is what they did.

The power supply was solved by using solar panels to charge up batteries. It can function up to 15 days without any sunlight and instead of wires carrying the sound, a short-wave radio link connects it to the nearest exchange.

If this earns a bouquet, then a brick bat should go to whoever installed the lighting at Fenchurch Street Station. The lights are arranged to come on automatically when the natural daylight falls below a certain level.

Nothing new in that of course, but here is the rub. The sensors have been placed so that the artificial light falls directly on them. The result being, that they immediately switch all the lights off again.

## Sound Sense

I recently had the misfortune to burst an ear drum, a legacy of my flying days. About a week later I was wandering disconsolately down Middlesex Street, better known as Petticoat Lane, and speculating on whether it would eventually heal, or whether I should need a hearing aid, when I heard a costermonger calling out, "Don't bother with the National Health, Deaf Aids only 10p".

Deciding that I could hardly go wrong, I purchased one. I was given a small cardboard box and inside was a yard (sorry metre) of white tea string with a knot in one end.

"How does it work?" I asked the vendor. "Simple, Guv, put the knot in your ear and the other end in your breast pocket, and people will shout at you like mad!!"

## PREVIOUSLY ADVERTISED STILL AVAILABLE

Tape punch and reader	£22.50
Bench isolating transformer 250 watt	£7.75
BOAC in-flight stereo unit	£1.50
Drill assortment 4 each 25 sizes between .25mm & 2.5mm	£11.50
Battery condition tester, less box	£1.75
Niced chargers, mains	£0.75
Flourescent inventor 13 watt from 12v	£3.50
Ten digit stitch pad-pb phone etc.	£1.95
Uniselecter 2 pole 25 way	£4.60
Water valve mains operated	£2.50
Counter 6 digit mains operated	£1.15
ditto 12v resettable	£3.45
Double glazing clear PVC sheet, 23 1/2" wide-per running ft.	£0.15
Locking mechanism with 2 keys	£1.15
Magnetic Clutch	£4.50
Mouth operated suck or blow switch	£2.30
Solenoid with slug 8-12v battery op.	£1.82
ditto 230v mains	£2.30
Timer Omron STP NH 110v AC Coil	£6.90
Key switch with 2 keys dp mains	£1.75
Air valve mains operated	£3.75
Drying lubric lubr mains operated	£3.50
Leaf film lubricant aerosol can	£0.65
Coin op switch, cased with coin tray	£4.60



### 8 POWERFUL MODEL MOTORS (all different)

for robots, meccanos, drills, remote control planes, boats, etc. £2.95.



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/2" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

### 12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle — Price £3.45. Ditto, but double ended £4.25. Ditto, but permanent magnet £3.75.



### EXTRA POWERFUL 12v MOTOR

Probably develops up to 1/4 h.p. so it could be used to power a go-kart or to drive a compressor, etc. £7.95 + £1.50 post.

### THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

### MINI MONO AMP on p.c.b., size 4" x 2" (app.)

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



### — BARGAIN OF THE YEAR —

#### The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 270 KHz, medium wave band 525 — 1650KHz, FM band 87 — 108MHz, mono, stereo & AFC switchable, tuning meter to give you spot on stereo tuning, optional LED wave band indicator, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or head phones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board.

Offered at a fraction of its cost: **only £6.00** + £1.50 post + insurance.

## THIS MONTH'S SNIP

Hi Fi sound from your Spectrum 1 watt amp — pm speaker & instructions £2.45

**REVERSIBLE MOTOR with control gear** Made by the famous Framco Company this robust motor is approx 7 1/2" long, 3 1/2" dia. 3/8" shaft. Very powerful, almost impossible to stop. Ideal for operating stage curtains, doors, ventilators, etc. Even garage doors if properly balanced. Offered complete with control gear as follows: 1 Framco motor with gear box 1 push to start switch 1 manual reversing & on/off switch 2 limit stop switches 1 circuit diag. of connections **ONLY £19.50 + postage £2.50.**

### FOR SOMEONE SPECIAL

Why not make your greeting card play a tune? It could play "Happy Birthday", "Merry Christmas", "Wedding March", etc. or "Home Sweet Home", etc. Wafer thin 3 part assemblies, for making cards musical. Mini microchip speaker and battery with switch that operates as the card is opened. Please state tune when ordering. Complete, ready to work £1.25.

### JOYSTICK

**WHY PAY £10 OR MORE** — Make yourself a Joystick — full details given in Dec/Jan "Similar Projects". We will supply complete kit for £2.30. Although designed for the Spectrum or ZX81 it is equally suitable for any home computer.

### TELEPHONE ITEMS

Plug and Wall socket — 4 pin or 5 pin	£3.45
Plugs only 4 pin or 5 pin	£1.15
Modern desk telephone	£7.50
Heavy black old type	£5.50
External bell unit	£6.50
Bell ringing power unit	£4.50
Pick up coil	£1.15

### STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) — ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation .1% with input variations up to 20% — load regulation .1% from no load to full load — or full load to no load. Complete in heavy duty case — Models available: 5v - 9A £23. 12v - 1.5A £13.25. 15v - 1.2A £13.25. 24v - 2A £23.

### PRESTEL UNIT

— brand new and complete except for 7 plug in IC's — Price: £19.75

+ £2.00 p&h.

Note: British Telecom may not connect this equipment as there is no manufacturer to guarantee it, however

it is well worth buying for its immense breakdown value — sold originally at over £150.



### 25A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you wake — switch on lights to ward off intruders — have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. Independent 60 minute memory jogger. A beautiful unit at £2.50.



### BELLS & ALARMS

Hooter/Siren 6v - 12v	69p
Loud, med & soft buzzer	75p
Open buzzer exc. G.P.O.	50p
12" Gong cast Iron cased ALARM BELL 12v dc	£19.50
6" Gong 12v dc	£7.50
6" Gong mains	£8.50

## 50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will have hundreds of parts for future projects. Our 10kg parcel contains not less than 1,000 items — panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, multi-turn pots and notes on the 50 projects.

**YOURS FOR ONLY £11.50 plus £3.00 post.**

### TELEPHONE & INTERCOM CABLES

15 conductors colour coded 200mt coil	£59.00
10 conductors colour coded 200mt coil	£39.00
Flex extension lead twin rubber	
5mm Ideal grass cutters etc. 250mtm coil	£25.00
50 meter coil	£6.75

### MAINS TRANSFORMERS

4 volt 4 amp	£1.75	24 volt 4 amp	£4.85
6 volt 1 amp	£1.15	25 volt 1 amp	£2.25
12 volt 1/2 amp	£1.15	35 volt 2 amp	£3.95
12 volt 1/4 amp	£1.55	38 volt 2 1/2 amp	£4.95
12 volt 1 amp	£1.75	26 volt 10 amp	£9.95
15 volt 2 amp	£3.45	50 volt 2 amp	£5.50
15 volt 4 amp	£4.60	25.25 1/2 amp	£3.95
18 volt 1 amp	£1.95	12.0.12 2 amp	£4.95
20 volt 1 amp	£2.30	115v 100w auto	£3.95
24 volt 2 amp	£3.45	115v 250w auto	£5.75

## J. BULL (Electrical) Ltd.

(Dept. EE), 34 - 36 AMERICA LANE, HAYWARDS Heath, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclay orders accepted day or night. Haywards Heath (0444) 454533. Bulk orders you can save yourself a fortune — send for our Sale List, hot for small buyers as minimum order £100.

### STORE CLOSING SALE

All stocks must go from one of our big warehouses. 10,000,000 items, everything from AERIALS to ZENER diodes cleared at fantastically low prices — If you are a manufacturer you can save yourself a fortune — send for our Sale List, hot for small buyers as minimum order £100.

## EXTRACTOR FANS — MAINS OPERATED

Woods extractor	
5" — £5.75, Post £1.25	
6" — £6.95, Post £1.25.	
5" Planinair extractor	
£6.50, Post £1.25.	
4" x 4" Muffin 115v.	£4.50, Post 75p.
4" x 4" Muffin 230v.	£7.50, Post 75p.
4" x 4" Muffin 115v.	£4.50, Post 75p.
All the above ex-computer,	those below are unused.
4" x 4" — £8.50, Post 75p.	
9" American made	£11.50, post £2.00.
Tangential Blower 10x3	air outlet, dual speed
£4.80, Post £1.50.	



## LIGHTING & POWER CABLES

Made by Volex to BRITISH STANDARD SPECIFICATIONS

P.V.C. sheathed outer-copper clad conductors	
1.5mm flat twin 100 metres	£4.50
1.5mm flat 3 core 8E metres	£11.00
6mm flat 3 core metres	£54.00
16mm flat twin 8E metres	£115.00

### MINIATURE WAFER SWITCHES

2 pole, 2 way — 4 pole, 2 way — 3 pole, 3 way — 4 pole, 3 way — 2 pole, 4 way — 3 pole, 4 way — 2 pole, 6 way — 1 pole, 12 way. All at 25p each or 10 for £2.00

OTHER TYPES IN STOCK — PLEASE ENQUIRE

**BLEEP TONE** These work off 12v and have an unusual and pleasant tone. 69p each.

**CONNECTING WIRE PACK** 96 lengths of connecting wire, each 1 metre long and differently colour coded, a must for those difficult interconnecting jobs. 85p the lot.

**RED LEDS** 10 for 69p. 100 for £5.75. 1000 for £52.

**IN LINE SIMMERSTAT** Ideal heat controller for soldering iron and many other hand-held appliances. £2.30. 10 for £17.25.



### VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic case — £1.75 or metal case — £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

### IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included. £11.95 plus £2.00 post.

## OTHER POPULAR PROJECTS

Short Wave Set — covers all the short wave bands using plug-in coils. Kit complete	£14.50
R C Bridge Kit	£9.95
3 Channel Sound to Light — with fully prepared metal case. — made up	£14.95
Big Ear, listen through walls	£25.00
Robot controller — receiver/transmitter	£9.50
Ignition kit — helps starting, saves petrol, improves performance	£13.95
Silent sentinel Ultra Sonic Transmitter and receiver	£9.50
Car Light 'left on' alarm	£3.50
Secret switch — fool friends and enemies alike	£1.95
3 — 30v Variable Power Supply	£13.80
2 Short & Medium wave Crystal Radio	£3.99
3v to 16v Mains Power Supply Kit	£1.95
Light Chaser — three modes	£17.50
Mullard Unilux Hi-Fi stereo amplifier with speakers	£16.75
Radio stethoscope — fault finding aid	£4.80
Mug stop — emits piercing squawk	£2.50
Morse Trainer — complete with key	£2.99
Drill control kit	£3.95
Drill control kit — made up	£6.95
Interrupted beam kit	£2.50
Transmitter surveillance kit	£2.30
Radio Mike	£6.90
FM receiver kit — for surveillance or normal FM	£3.50
Seat Belt reminder	£3.00
Car Starter Charger Kit	£15.50
Soil heater for plants and seeds	£16.50
Insulation Tester — electronic megger	£7.95
Battery shaver or fluorescent from 12v	£6.90
Matchbox Radio — receives Medium Wave	£2.95
Mixer Pre-amp — disco special with case	£16.00
Aerial Rotator — mains operated	£29.50
Aerial direction indicator	£5.50
40 watt amp — hi-fi 20Hz — 20kHz	£9.50
Microvolt multiplier — measure very low currents with ordinary multimeter	£3.95
Pure Sine Wave Generator	£5.75
Linear Power output meter	£11.50
115 Watt Amplifier 5Hz 25kHz	£13.50
Power supply for 115 watt amps	£8.50
Stereo Bass Booster, most items	£8.95

# BIG K

## THE ONLY COMPUTER MAGAZINE YOU'LL EVER NEED.

BIG K IS BURSTING WITH NEW IDEAS TO HELP YOU GET THE MOST OUT OF YOUR MICRO - HARD-HITTING REVIEWS OF NEW EQUIPMENT, INGENUOUS TECHNIQUES TO ADD NEW DIMENSIONS TO YOUR SOFTWARE, IN-DEPTH TESTS OF THE VERY LATEST GAMES, AND IN EVERY ISSUE YOU'LL FIND LISTINGS FOR SOME OF THE VERY BEST ADVENTURE GAMES YOU'LL EVER PLAY.

STAY IN TOUCH WITH BIG K EVERY MONTH.

### THIS ISSUE:

FALKLANDS VICTOR GENERAL SIR JEREMY MOORE REVIEWS THE LATEST WAR GAMES.

COMPUTERS COMPARED - 3 NEW BRITISH MICROS VERSUS 3 AMERICANS.

ADVENTURE X - A SUPERB FULL-SIZE GRAPHIC ADVENTURE FOR THE SPECTRUM.

AMAZING GAMES FOR BBC, VIC 20, SPECTRUM, ATARI, COMMODORE 64.

SPECTRUM GRAPHICS SPECIAL - GREAT 3D ROTATION TECHNIQUES.



### FREE FLEXIDISC

- 3 superb programs to  
add amazing effects  
to your BBC and  
Spectrum games.



SECOND AMAZING ISSUE  
ON SALE 19th APRIL-85p

# ELECTROVALUE



Your **SPECIALIST SUPPLIERS** for **CAPACITORS** of all preferred types



**POLYESTER LAYER** (Siemens) B.32509 5mm PCM 10% tolerance 63V. In 13 values from 0.0047 to 0.47µF  
 B.32510 7.5mm PCM 10% tolerance 100V min. In 7 values from 0.0047 to 0.47µF  
 B.32512 15mm PCM 10% tolerance 100V 1µF, 2.2µF  
 B.32560 7.5mm PCM 26 types 10% tolerance 400V 0.001 to 0.0068µF  
 9% tolerance from 0.0082 to 0.68µF in 400, 250 & 100V

**CERAMIC PLATE**  
 Above 1000pF, in E6 values to 4700pF  
 C.333 100Vdc 18-4700pF - 10 types  
 B.37448 63Vdc 2.5mm PCM 0.01-0.68pF - 5 types  
 B.37449 63Vdc 5mm PCM 0.047, 0.68, 0.1µF  
**CERAMIC DISC**  
 1nF-10nF, 300Vdc  
**ELECTROLYTIC**  
 Axial in 48 values from 1 to 10000µF, 10 to 63Vdc  
 Canned in 9 values from 2000 to 220000µF, voltages to 350

Reversible from 2 to 100µF  
 Low Leak, Almm 0.1-100µF, 17 values, 6-50Vdc  
 Radial 15 values 1-1000µF, 16-63Vdc  
**TANTALUM BEADS**  
 in 18 values from 0.1-100µF, 6.3-35Vdc  
**POLYSTYRENE** (Siemens) 39 values 5pF to 18nF, 160Vdc  
 The above ranges should meet the majority of current requirements. Mention EE when sending for our latest A-Z list showing very many more types.


**BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 32 PAGE A-Z LIST ATTRACTIVE DISCOUNTS-FREE POSTAGE-GOOD SERVICE & DELIVERY**

**ELECTROVALUE LTD**

28 St. Jude's Rd. Englefield Green, Egham, Surrey TW20 0HB, (0784)

33603 Telex 264475 (Callers only) 680 Burnage Lane W/c. (061-432 4945)  
 EV Computing Shop, 700 Burnage Lane, Manchester (061-431 4866).

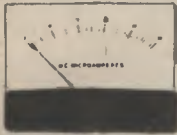**ACCESS AND BARCLAYCARD Phoned Orders Welcome**



**METERS: 110 x 82 x 35mm**  
 30µA, 50µA, 100µA. £6.90  
 Post 50p.

**METERS: 45 x 50 x 34mm**  
 50µA, 100µA, 1mA, 5mA, 10mA, 25v, 1A, 2A, 5A 25V. £3.54. Post 30p.

**METERS: 60 x 47 x 33mm**  
 50µA, 100µA, 1mA, 5mA, 10mA, 100mA, 1A, 2A, 25v, 50v, 50-0-50µA, 100-0-100µA. £6.04.  
 VU meters £6.04.  
 Post on above meters 30p.

**Silicone grease 50g £1.32.**  
 Post 16p.

**NI-CAD BATTERY CHARGER**  
 Led indicators charge-test switch. For PP3, HP7, HP11 & HP2 size batteries.  
 Price £5.85. Post 94p.

**Motorola Piezo Ceramic Tweeter** £5.20 Post 33p

T.V. UHF Aerial Amplifier 300-890MHz £6.03 post 57p  
 Desoldering Pump £4.25 post 27p  
 Resistance Substitution Box £3.97 post 17p  
 Vernier Dial 50mm Dia. £2.31 post 17p  
 Tape Head Demagnetizer £2.60 post 39p  
 Min. Buzzer 6 or 12V 63p post 21p

**TRANSFORMERS**  
**240v Primary**

3-0-3v	100mA	82p
6-0-6v	100mA	£1.20
6-0-6v	250mA	£1.33
12-0-12v	50mA	£1.13
12-0-12v	100mA	£1.21
9-0-9v	75mA	£1.20
9-0-9v	250mA	£1.37

Post on above transformers 48p.

9-0-9v	1A	£2.05
12-0-12v	1A	£2.52
15-0-15v	1A	£3.11
6-0-6v	1½A	£2.20

Post on above transformers 94p.

**Rotary Switches:** 1 Pole 12 Way 2P6W, 3P4Way, 4P3W 42p Post 16p

**Illuminated Rocker Switch** 240V 6A Red 88p Post 16p

All above prices include V.A.T. Send £1 for a new comprehensive 1983/84 fully illustrated catalogue with a new price list. Send S.A.E. with all enquiries. Special prices for quantity on request.

All goods despatched within 3 days from receipt of the order.

## M. DZIUBAS


158 Bradshawgate, Bolton, Lancs. BL2 1BA.

## FIND YOUR WAY THROUGH THE DIGITAL ELECTRONICS MAZE

First there was **SUPERKIT**

and now ... **NEW**

### SUPERKIT II

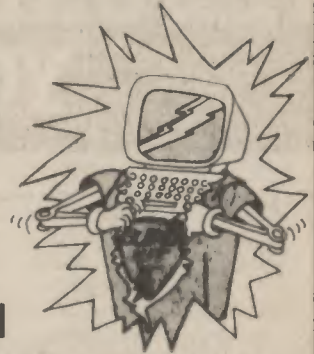

This practical self-instruction kit has been developed to extend the original beginners' SUPERKIT. SUPERKIT II includes an instruction manual and many more components, enabling you to design and use adders, subtractors, counters (ripple, up/down, synchronous, decade and Gray code), registers, pattern recognisers and 7-segment displays. You need the board and components from SUPERKIT to enable you to build the circuits in SUPERKIT II. Together the two kits provide an excellent introduction to digital electronics - what really goes on inside a computer.

**SUPERKIT (SUP) £22.00**      **SUPERKIT II (SUP II) £16.00**  
**Special price £36.00 for both (SUP + II) (inc. VAT and p & p)**

The SUPERKIT series is backed by our theory courses, **DIGITAL COMPUTER LOGIC** (beginners' course), which covers the design of logical circuits, and **DIGITAL COMPUTER DESIGN** (more advanced), which covers the design of digital computers. **MICROPROCESSORS AND MICROELECTRONICS** teaches you what a microprocessor is and what it can do.

**DIGITAL COMPUTER LOGIC (DCL) £7.00**  
**DIGITAL COMPUTER DESIGN (DCD) £9.50**  
**MICROPROCESSORS AND MICROELECTRONICS (MIC) £6.50**

Please send for full information on these and our other courses.  
**GUARANTEE** If you are not completely satisfied, return the item to us within 28 days for a full refund. All prices include worldwide surface postage (ask for prepayment invoice for airmail). Allow 28 days for delivery in UK. Overseas payment by international credit card or by bank draft drawn on a London bank.

**CAMBRIDGE LEARNING LTD, Unit 38, Rivermill Site, FREEPOST, St Ives, Cambs PE17 4BR, England.**

Tel: 0480-67446

VAT No 313026022 Transcash No 2789159 Reg No 1328762  
 Please send me (initial letters used):

..... SUP	@ £22.00	..... DCL	@ £7.00
..... SUP II	@ £16.00	..... DCD	@ £9.50
..... SUP + II	@ £35.00	..... MIC	@ £6.50

I enclose a cheque/PO payable to Cambridge Learning Ltd for £.....  
 Please charge my ..... credit card.

No ..... Expiry date .....

Telephone orders from credit card holders accepted on 0480 67446 (24 hrs)

Name .....

Address .....

.....

..... Signature .....

.....

.....

.....

.....

.....

.....

.....

.....

.....



**CAMBRIDGE LEARNING**

Unit 38, Rivermill Site, FREEPOST, St Ives, Cambs PE17 4BR, England.



## Miscellaneous

**COMPLETE SET EVERYDAY ELECTRONICS**  
Nov '71 to Dec '84 except Sept '84. Offers Box  
No. 13.

### LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Send cheque or P.O. to:  
Roden Products, Dep EE  
High March, Daventry,  
Northants, NN11 4DE.

**£4.99**

including p & p

**ORIC-1 EPROM PROGRAMMER.** Full hardware and software plans of a low-cost unit which programs, simulates and duplicates Eproms on your 48K Oric. Price £2.50 from **HOWELL & COLLINS**, 43 Crossways, Crawley, Sussex RH10 1QT.

#### THE SCIENTIFIC WIRE COMPANY

811 Forest Road, London E17. Telephone 01-531 1568

##### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69

##### SILVER PLATED COPPER WIRE

14 to 30	9.09	5.20	2.93	1.97
----------	------	------	------	------

##### TINNED COPPER WIRE

14 to 30	3.97	2.41	1.39	0.94
----------	------	------	------	------

Fluxcore Solder 5.90 3.25 1.82 0.94

Prices include P&P VAT. Orders under £2 add 20p.  
SAE for list of copper and resistance wire.  
Dealer enquiries welcome.

## For Sale

**WORKING TEST EQUIPMENT.** Signal generators, variable P.S.U.s, meters, isolating transformers and breakdown units etc at give away prices. S.A.E. to S.H.E., 5 St Josephs, Ballycruttle, Downpatrick, BT30 7EN.

## Repairs

**M & S COMPUTER REPAIRS.** Specialising ZX80, ZX81, ZX Spectrum, ZX Printer. Cheap rates, guaranteed. Phone 021-384 1297 1pm-6pm for enquiries.

## Receivers & Components

**500 SMALL COMPONENTS** including TTL transistors £2.50, 7lbs or 10lbs assorted components £5.00/£6.50. Fifty 74 series I.Cs on panel £2.20. Post Paid. J. W. BLANSHARD, 2 Barnfield Crescent, Sale Cheshire, M33 1NL.

# EVERYDAY ELECTRONICS and computer PROJECTS

Reach effectively and economically to-days enthusiasts anxious to know of your products and services through our semi-display and classified pages. Semi-display spaces may be booked at £7.80 per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 33 pence per word (minimum 12 words), box number 60p extra. All cheques, postal orders, etc., to be made payable to

**COMPONENTS & EQUIPMENT** - 1984 Catalogue 70p + 20p P&P. Callers: 18 Victoria Road, TAMWORTH. 369 Alumrock Road, BIRMINGHAM. 103 Coventry Street, KIDDERMINSTER. Express Mail Order Service. **LIGHTNING ELECTRONICS**, PO Box 8, Tamworth, Staffs.

## Security

**BURGLAR ALARM EQUIPMENT.** Free catalogue C.W.A.S. Ltd. 0274 731532 open 9-5 Mon-Sat.

### BUMPER BOX OF BITS

WOW!!! We've got so many components in stock, we can't possibly list them all!!! - So buy a box, in it you'll find resistors, capacitors, displays, switches, panels with transistors, diodes, IC's etc, coils, pots... and so on. All modern parts - guaranteed at least 1000 items, minimum weight 10lbs. **ONLY £8.50.**

### PSU PANEL

Stabilized 5v, variable  $\pm 0.5V$ . Regulation 1% Max. current 2A. Will take AC I/P up to 15V, or DC I/P up to 24V. Panel 140x35mm contains all components except series reg. transistor which is mounted separately. PCB stand-offs, included **ONLY £3.95.** Heatsink 75p; transformer £5.00.

### RESISTOR PACK

All sorts - everything from 1/10th to 10W. Carbon, Film, W/W, Oxide, PCB, etc. 2000 resistors - yes, 2000!!! For only £4.95.

### SWITCH PACK

Slide (up to 9 way), push button banks, push types - a total of 50 switches for only £3.95.

All prices include VAT and Post/Packing.

Send SAE for latest lists.

### ELECTRONICS WORLD

1d Dews Road, Salisbury, Wilts, SP2 7SN

### AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20dbs. Tunable over the complete UHF TV band. **PRICE £8.70.**

AMPLIFIED SET TOP AERIALS, for VHF TV. Trebles the gain. **PRICE £11.70.**

All Boosters we make work off a PP3/006p/6F22 type battery or 8v to 18v DC. **P&P 30p PER ORDER.**

**ELECTRONIC MAIL ORDER**, 62 Bridge St. Ramsbottom,

Lancs BLD 9AG. Tel. (070682) 3036

Access/Visa Cards Welcome SAE Leaflets

**TURN YOUR SURPLUS** capacitors, transistors etc., into cash. Contact Coles Harding & Co., 103 South Brink Wisbech, Cambs. 0945-584188. Immediate settlement.

**WHO CAN PUT A PRICE ON A PEACE OF MIND**

PROFESSIONAL SECURITY EQUIPMENT AT LOW/LOWI PRICES.

**HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES**

ADVANCED SECURITY PRODUCTS LTD

2 Ealing Road, Aintree, Liverpool L9 0HU, Merseyside.

Tel: 051-525 3440

FREE CATALOGUE PHONE OR S.A.E.

**TO ADVERTISE ON THESE PAGES PLEASE RING PAT ON 01-261 5942**

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for .....  
Insertions. I enclose Cheque/P.O for £ .....  
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to **Everyday Electronics**)


**NAME** .....

**ADDRESS** .....

.....

.....

### EVERYDAY ELECTRONICS

Classified Advertisement Dept., Room 2612,  
King's Reach Tower, Stamford Street, London SE1 9LS  
Telephone 01-261 5942

Rate:  
33p per word, minimum 12 words. Box No. 60p extra.



# AT YOUR SERVICE

Everyday Electronics and Computer Projects and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics and Computer Projects, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St, London SE1 9LS. (Telephone 01-261 5942).

## Courses

**CONQUER THE CHIP**—master modern electronics the practical way by seeing and doing in your own home. Write for your free colour brochure now to **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**, Dept C3, Reading, Berks RG1 1BR.

## Service Sheets

**FULL SIZE SERVICE SHEETS £2 + 1sae;** CTV/MusC £3 + 1sae. Repair/circs almost any named TV/VCR £9.50. 1sae free quotations for manuals, sheets — free mag inc. service sheet. T.I.S.E.E. 76 Church Street, Larkhall, Lanarks — Phone 0698 883334.

**BELL'S TELEVISION SERVICE** for service sheets on Radio, TV etc. £1.50 plus S.A.E. Service Manuals on Colour TV and Video Recorders, prices on request. S.A.E. with enquiries to: BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

# NO!

If you see an advertisement in the press, in print, on posters or a cinema commercial which you find unacceptable, write to us at the address below. TV and radio commercials are dealt with by the I.B.A.

The Advertising Standards Authority. ✓

ASA Ltd., Brook House, Torrington Place, London WC1F 7HN

## ★ BAKER ★

### GROUP P.A. DISCO

#### AMPLIFIERS post £2

150 watt Output, 4 input Mixer pre-amp. Illustrated ..... £99  
 150 watt Output, Slave 500 mv. Input 3 Speaker Outputs ..... £80  
 150+150w Stereo, 300w Mono Slave 500 mv. Inputs ..... £125  
 150w P.A. Vocal, 8 inputs, High/Low Mixer Echo Socket ..... £129  
 100 watt Valve Model, 4 inputs, 3 Outputs, Heavy duty ..... £125  
 60 watt Valve Model, 4 inputs, Low imp and 100v line output ..... £69  
 60 watt Mobile 240v AC and 12v DC, 4-8-16 ohm+100v line ..... £89

#### BAKER LOUDSPEAKERS

Type	Model	Size	Watts	Ohms	Price
Disco/P.A.	DG50/10	10	50	8/16	£18.00
Midrange	Mid 100/10	10	100	8	£25.00
Hi-Fi	Major	12in	30	4/8/16	£16.00
Hi-Fi	Superb	12in	30	8/16	£26.00
Disco/P.A.	DG45	12in	45	4/8/16	£16.00
Hi-Fi	Woofer	12in	80	8	£25.00
Hi-Fi	Auditorium	15in	60	8/16	£37.00
Disco/P.A.	DG75	12in	75	4/8/16	£20.00
Disco/P.A.	DG100	12in	100	8/16	£26.00
Disco/P.A.	DG100/15	15in	100	8/16	£35.00

#### BAKER DISCO SYSTEMS

150 Watts twin turntables, twin speakers, headphones, microphone, slide controls. Complete £330 or Console only £105. Carriage £30

#### RCS SOUND TO LIGHT CONTROLLER KIT

Printed circuit, Cabinet, 3 channels, 1,000 watts each. Will operate from home Hi-Fi or Disco. £19. Post £1 or Ready Built £27. Coloured Disco Bulbs 100w ES or BC £2.20 pp £1.50 for 6.

**LOW VOLTAGE MAINS TRANSFORMERS £5.50 post paid**  
 9 volt 3 amp; 12 volt 3 amp; 16 volt 2 amp; 20 volt 1 amp; 30 volt 1 1/2 amp; 30 volt 5 amp + 17-0-17 volt 2 amp; 35 volt 2 amp; 20-0-20 volt 1 amp; 12-0-12 volt 2 amp; 20-0-20 volt 1 amp; 25-0-25 volt 2 amp.

**ALUMINIUM CHASSIS 18 s.w.g.** Un-drilled, 4 sides, riveted corners: 6 x 4 x 2 1/2in. £1.75; 8 x 6 x 2 1/2in. £2.20; 10 x 7 x 2 1/2in. £2.75; 14 x 9 x 2 1/2in. £3.60; 16 x 6 x 2 1/2in. £3; 12 x 3 x 2 1/2in. £1.80; 12 x 8 x 2 1/2in. £3.20; 16 x 10 x 2 1/2in. £3.80.

**ALI ANGLE BRACKET 6 x 1 x 3/8in. 30p.**  
**ALUMINIUM PANELS 18 s.w.g.** 12 x 12in. £1.80; 14 x 9in. £1.75; 6 x 4in. 55p; 12 x 8in. £1.30; 11 x 7in. 90p; 8 x 6in. 90p; 14 x 3in. 72p; 12 x 5in. 90p; 16 x 10in. £2.10; 16 x 6in. £1.30.

**ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.**  
 4 x 2 1/2 x 2in. £1.00; 3 x 2 x 1 1/2in. 80p; 6 x 4 x 2in. £1.60; 8 x 6 x 3 1/2in. £2.50; 12 x 5 x 3 1/2in. £2.75; 6 x 4 x 3 1/2in. £1.80; 10 x 7 x 3 1/2in. £3.

**HIGH VOLTAGE ELECTROLYTICS** 32+32/350V ..... 60p  
 20/500V ..... 75p 8+8/500V ..... £1 32+32+32/450V ..... 95p  
 32/350V ..... 45p 8+16/450V ..... 75p 125/500V ..... £2  
 32/500V ..... 95p 16+16/350V ..... 75p 16+32+32/500V ..... £2

#### SINGLE PLAY DECKS. Post £2.

Make	Model	Cartridge	Price
BSR	P170	Ceramic	£29
GARRARD	6200	Ceramic	£22
BSR	P182	Ceramic	£26
BSR	P232	Magnetic	£28
BSR	P200	Magnetic	£34



#### AUTOCHANGER BSR Ceramic £20

### RADIO COMPONENT SPECIALISTS

Dept 4, 337, WHITEHORSE ROAD, CROYDON SURREY, U.K. TEL: 01-684 1665

ACCESS

Post 5p Minimum. Callers Welcome. Lists 32p. Same day despatch. Closed Wed.

VISA

the leader of the packs

### BIG VALUE RESISTOR PACKS

1/2 WATT CARBON FILM 10-10MΩ ten values. Total 720 resistors. **£5**  
 1/2 WATT METAL FILM 1% 50ppm 10Ω-1MΩ E24 range. Total 960 resistors. **£25**

## FREE CATALOGUE

Sent to every new customer

### AC/DC COMPONENT PACKS

Pack No	Qty	Description	Price
TF11	12	RED 5mm LED	£1.00
TF12	30	500mz ZENERS 5%	£1.00
TF13	100	1N4148 Diode	£1.00
TF14	100	1N4151 Diode	£1.00
TF15	50	1 amp Rect. Diodes In 4000 series	£1.00
TF16	6	1 amp Bridge Rect.	£1.00
TF17	100	Transistor pads	£1.00
TF18	20	A/S Fuses 20mm	£1.00
TF19	10	3A Rect. Diodes	£1.00
TF110	2	ORP 12	£1.00
TF111	5	BR 100 DIAC	£1.00
TF112	10	BC109B	£1.00
TF113	10	IC's all different	£1.00
TF114	50	BFR86	£1.00
TF115	12	8 pin DIL sockets	£1.00
TF116	20	10mm Horiz. Pre set (10 values)	£1.00
TF21	200	47pf 160v Polystone cap	£2.00
TF22	10	LM 3900 N	£2.00
TF23	10	Mixed DTL	£2.00
TF24	5	4700 mf 25v Tag Elect 2" x 1"	£2.00
TF25	10	1000 mf 63v Ax Elect.	£2.00
TF26	50	.022 mf 400v RAD POLY	£2.00
TF27	10	100mf 250v Ax	£2.00
TF28	10	2.2mf 160v Polyester RAD	£2.00
TF51	100	white/red 5mm LED	£5.00
TF52	50	BC 108C	£5.00
TF53	2	10,000mf 63v comp. grade elect.	£5.00
TF54		1/2 kg. reel 22g ersin multicore solder	£5.00
TF55	10	2N3055 H(RCA)	£5.00
TF56	5	0CP71	£5.00

ALL PRICES INCLUDE VAT — ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.

TERMS: Cash with order, POST & PACKING: Please add 75p to total order.

## AC/DC ELECTRONICS COMPONENTS

DEPT E.E. 45 CHURCH STREET, ENFIELD, MIDDLESEX.

### BIMBOXES

2000 Series, ABS. Guides for vertically mounting PCB's, bimductors for horizontal mounting.

Part No.	Size	Grey or Black	White
BIM 2002/12	100 x 50 x 25	1.10	1.21
BIM 2003/13	112 x 62 x 31	1.25	1.37
BIM 2004/14	120 x 65 x 46	1.32	1.45
BIM 2005/15	150 x 80 x 56	1.54	1.69
BIM 2006/16	190 x 110 x 60	2.70	2.97
BIM 2005/25	150 x 80 x 76	Grey Base, Clear Lid	1.91
BIM 2006/26	190 x 110 x 80	Grey Base, Clear Lid	3.20
BIM 2007/17	112 x 62 x 31	Grey Polystyrene, No Guides	0.63

### BIMBOXES

4000 Series, ABS Base, Aluminium recessed lid.

Model	Size	Price	Color
BIM 4003	85 x 56 x 35	1.18	Grey
BIM 4004	111 x 71 x 48	1.46	Grey
BIM 4005	161 x 58 x 96	2.02	Black

### BIMTOOLS

12v Mini Bimdrill inc collets	8.05
Mini Bimdrill Kit inc 20 tools	14.45
Mains Bimdrill inc collets	9.55
Mains Bimdrill Kit inc 20 tools	15.45
Bimiron 17W	6.15
Bimiron 27W	5.75
Bimpump, Desoldering Tool	6.25

### BIMCASES

1000 Series, ABS base, Sloping-Front, Aluminium recessed lid.

Model	Size	Price	Color
BIM 1005	161 x 39 x 57 x 96	1.78	Grey or Black
BIM 1006	215 x 47 x 72 x 130	2.88	Black



All prices inc VAT. Add 60p per order p&sp. S.A.E. for full list. Mail order only.

### BIMSALES

Dept EE5, 48a Station Road, Cheadle Hulme, Cheshire SK8 7AB. Tel: 061 485 6667.

MIT Part 11 in this issue:


## "COMPUTER CONTROL OF SMALL VEHICLES"

Complete set of components (not PCB) + gearbox and wheels (as recommended by the authors) for around £30. Ring for exact price - and place your order by Access at the same time!


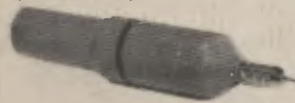
### MOTORIZED GEARBOX

These units are as used in a computerized tank, and offer the experimenter in robotics the opportunity to buy the electro-mechanical parts required in building remote controlled vehicles. The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors etc. £5.95. Suitable wheels also available: 3" Dia plastic with blue tyre, drilled to push-fit on spindle. 2 for £1.30 (limited qty). 3" dia aluminium disc 3mm thick, drilled to push-fit on spindle. 2 for 68p.



### PRECISION PCB DRILL

Small size, 35mm dia x 165mm long. 12V operation. Supplied with collet + 1mm bit 6000RPM. Only £7.50.

### PACKSI PACKSI PACKSI!

K517 Transistor Pack. 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114, 117, 172, 182, 183, 198, 239, 251, 214, 225, 320, 8F198, 255, 394, 2N3904 etc etc. Retail cost £7+. Special low price 275p

K523 Resistor Pack. 1000 - yes, 1000 & 1/2 watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several megohms. Only 250p. 5000 £10; 20,000 £36.

K520 Switch Pack. 20 different assorted switches - rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p

K522 Copper clad board. All pieces too small for our etching kits. Mostly double sided fibreglass. 250g (approx 110 sq ins) for 200p

K541 It's back!! Our most popular pack ever - Vero offcuts. This has been restricted for some time, but we have now built up a reasonable stock and can once again offer 100 sq ins of vero copper clad offcuts, average size 4x3". Offered at around 1/2 the price of new board 320p

K530 100 Assorted polyester caps - all new modern components, radial and axial leads. All values from 0.01 to 1uf at voltages from 63 to 1000V Super value at 395p

# GREENWELD

Goods normally despatched by return of post.

Our shop has enormous stocks of components and is open from 9-5.30 Mon-Sat. Come & see us!!



Minimum Access order £5.00

## TEACH-IN 84

Once again GREENWELD is supplying a complete set of parts for this ever popular series - as we have done for all previous series. Our experience in this field means your kit can be supplied from stock at the best possible price, so order with confidence. Price for complete kit is only £18.95 inc post and VAT.

### SEAT BELT ALARM

Originally for sale at £8.95, these well made units 70x50x25mm provide both audible and visual alarms. Uses 2 IC's, PB2720 transducer, etc. Available ready built, with circuit and instructions for just £3.95. Also available as a kit, PCB + all components, box, wire, etc, together with instructions. Only £2.95.

### RIBBON CABLE

Special purchase of multicoloured 14 way ribbon cable - 40p/metre; 50m £18; 100m £32.00; 250m £65.00.

### TTL PANELS

Panels with assorted TTL inc LS types. Big variety. 20 chips £1.00; 100 chips £4.00; 1000 chips £30.00.

### "THE SENSIBLE 64"

David Highmores new book on the Commodore 64 now available. £5.95.

## THE 1984 GREENWELD CATALOGUE

### NOW AVAILABLE!!

It's Bigger, Brighter, Better, more components than ever before. With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00! Order now for early delivery!

### COMPUTER GAMES

Z901 Can you follow the flashing light/pulsating tone sequence of this famous game? Supplied as a fully working PCB with speaker (no case) plus full instructions. Only £4.95

Z902 Probably the most popular electronic game on the market - based on the old fashioned pencil and paper battleship game, this computerized version has brought it bang up to date! We supply a ready built PCB containing 76477 sound effect chip, TMS1000 micro-processor chip, R's, C's etc. Offered for its component value only (board may be cracked or chipped, it's only £1.95. Instructions and circuit, 30p.

### NICAD CHARGERS

Versatile unit for charging AA, C, D and PP3 batteries. Charge/test switch, LED indicators at each of the 5 charging points. Mains powered. 210 x 100 x 50mm £7.95. Model A124. Unit plugs directly into 13A socket, and will charge up to 4 AA cells at a time. Only £4.80.

### NICAD BATTERIES

AA size 99p each; C size 199p; D size 220p; PP3 size 395p.

# VELLEMAN - KIT THAT'S IT!

## NEW INTERFACE SYSTEM FOR ZX81 and SPECTRUM now available

K2609	DC Output Board .....	£19.01
K2610	A/D Converter .....	£28.26
K2611	Opto Input Board .....	£20.55
K2614	Centronics Interface .....	£30.83
K2615	Spectrum Interface Motherboard .....	£25.69
K2616	ZX81 Interface Motherboard .....	£25.69
K2618	D/A Converter .....	£24.66

(Prices include VAT)

**NEW** K2606 - LED Audio Power Meter  
4 selectable scales, complete with front plate for panel mounting, no power supply required ..... £12.48

**NEW** K2601 - Stroboscope  
Flash frequency 2-20 Hz.  
Power supply: 220-250V AC ..... £10.79

**NEW** K2590 - Light Computer  
New version with 16 programs of max. 128 steps each. Triac outputs, adjustable speed ..... £30.39

SEND FOR NEW FULL COLOUR SHEET  
DETAILING COMPLETE RANGE WITH LIST OF  
STOCKISTS available free from:

## VELLEMAN UK. Ltd

P.O. Box 30, St. Leonards-on-Sea,  
East Sussex TN37 7NL, England.  
Telephone: (0424) 753246



## INDEX TO ADVERTISERS

AC/DC Electronics .....	351
AD Electronics .....	350
Big K .....	348
Bimsales .....	351
Bi-Pak .....	293
BK Electronics .....	292
B.N.R.E.S. ....	290
Bull J. ....	347
Cambridge Learning .....	349
Dziubas M. ....	349
Electronic Mail Order .....	350
Electronics World .....	350
Electronize Design .....	Cover II
Electrovalue .....	349
Enfield Electronics .....	333
Global Specialties Corporation .....	305
Greenweld Electronics .....	352
ICS Intertext .....	295
Magenta Electronics .....	Cover III
Maplin Electronics .....	292 Cover IV
Radio Component Specialists .....	351
R & TVC .....	296
Rapid Electronics .....	291
Roden Products .....	350
Software Index .....	294
Sparkrite .....	295
T.K. Electronics .....	295
Velleman UK .....	352

# E.E. PROJECT KITS MAGENTA TEACH IN 84

## THIS MONTHS KITS PHONE OR WRITE FOR PRICES

Full Kits inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.  
If you do not have the issue of E.E. which includes the project — you will need to order the instruction reprint as an extra — 50p each. Reprints available separately 50p each + p&p 50p.

**DIGITAL MULTIMETER** add on for BBC Micro Mar. 84 £24.98

**NI-CAD BATTERY CHARGER** Mar. 84 £9.95

**REVERSING BLEEPER** Mar. 84 £6.78

**DIN LEAD TESTER** Mar. 84 £8.32

**PIPE FINDER** Mar. 84 £3.60

**LOW POWER STEREO AMP** Mar. 84 £27.68

**IONISER** Feb 84 £23.98

**EPROM PROGRAMMER (ZX81)** Feb 84 £14.48

**SIGNAL TRACER** Feb 84 £13.35

**CAR LIGHTS WARNING** Feb 84 £3.76

**GUITAR TUNER** Jan 84 £17.73

**BIOLOGICAL AMPLIFIER** Jan 84 £19.16

**CONTINUITY TESTER** Dec 83 £9.99

**CHILDREN'S DISCO LIGHTS** Dec 83 £8.42

**NOVEL EGG TIMER** Dec 83 inc case £10.24

**SPEECH SYNTHESIZER FOR THE BBC MICRO** Nov. 83 less cable + sockets £12.98

**MULTIMOD** Nov. 83 £16.98

**LONG RANGE CAMERA/FLASHGUN TRIGGER** Nov. 83 £25.63

**HOME INTERCOM** less link wire Oct. 83 £14.38

**IMMERSION HEATER TELL-TALE** Oct. 83 £9.98

**TEMPERATURE TRANSDUCER AMP** Oct. 83 £14.87

**SHORT WAVE RADIO** less 'phones, Oct. 83 £25.63

Mono headphones extra £3.36

**DIGITAL TO ANALOGUE BOARD** Oct. 83 £19.98

less cable, case & connector

**HIGH POWER DAC DRIVER BOARD** Oct. 83 less case £12.52

**A TO D CONVERTER FOR RM3802** Sept. 83 inc plug £35.98

**HIGH SPEED A TO D CONVERTER** Sept. 83 less cable & connector £27.98

**SIGNAL CONDITIONING AMP** Sept. 83 no case £8.98

**'STORAGE' SCOPE INTERFACE FOR BBC MICRO** Aug. 83 less software £15.38

**PEDESTRIAN CROSSING SIMULATION BOARD** Aug. 83 no case £10.29

**HIGH POWER INTERFACE BOARD** Aug. 83 no case £10.38

**CAR INTRUDER ALARM** Aug. 83 £16.98

**TRI BOOST GUITAR TONE CONTROLLER** July 83 £8.35

**USER PORT I/O BOARD** less cable + plug £10.49

**USER PORT CONTROL BOARD** July 83 less cable + plug £10.49

**BINARY BANDIT GAME** July 83 less case £9.88

**EPROM PROGRAMMER** Jun. 83 less software, TRS80 £44.99 Genie £45.73

**ENVELOPE SHAPER** Jun. 83 less case £12.33

**REAL TIME CLOCK** May 83 less software and cases

Apple II £33.98 BBC £39.59 less power plug

**MODEL TRAIN CONTROLLER** May 83 £27.17

**GUITAR HEADPHONE AMPLIFIER** May 83 £7.62

**MW PERSONAL RADIO** less case. May 83 £7.62

**MOISTURE DETECTOR** May 83 £5.46

**CAR RADIO POWER BOOSTER** April 83 £11.99

**FUNCTION GENERATOR** April 83 £45.98

**FLANGER SOUND EFFECTS** April 83 £24.17

**NOVELTY EGG TIMER** April 83 less case £5.48

**ZX SPECTRUM AMPLIFIER** April 83 £9.87

**DUAL POWER SUPPLY** March 83 £59.38

**BUZZ OFF** March 83 £4.51

**SPEECH PROCESSOR** Feb. 83 £11.66

**PUSH BIKE ALARM** Feb. 83 £11.73

**DOUBLE DICE** Jan. 83 £11.90

**ELECTRONIC V/I METER** Dec. 82 £12.52

**ZX TAPE CONTROL** Nov. 82 £7.13

**SINE WAVE GEN** Oct. 82 £16.11

**G. P. PRE-AMP** Oct. 82 £6.09

**LIGHTS ON ALERT** Oct. 82 £4.68

**CONTINUITY CHECKER** Sept. 82 £5.47

**SOUND SPLITTER** Sept. 82 £17.35

**SOUND RECOMBINER** Sept. 82 £4.97

**SCREEN WASH DELAY** Sept. 82 £4.93

**CB ROGER BLEEPER** Aug. 82 £9.32

**2-WAY INTERCOM** July 82 no case £4.52

**ELECTRONIC PITCH PIPE** July 82 £5.40

**REFLEX TESTER** July 82 £7.77

**SEAT BELT REMINDER** Jun. 82 £4.10

**EGG TIMER** Jun. 82 £5.44

**CAR LED VOLT METER** less case. May 82 £3.18

**V.C.O. SOUND EFFECTS UNIT** Apr. 82 £12.71

**CAMERA OR FLASH GUN TRIGGER** Mar. 82 £13.65 less tripod bushes £4.10

**POCKET TIMER** Mar. 82 £17.19

**GUITAR TUNER** Mar. 82 £17.19

**SIMPLE STABILISED POWER SUPPLY** Jan. 82 £26.98

**MINI EGG TIMER** Jan. 82 £4.40

**SIREN MODULE** Jan. 82 less speaker £6.10

**MODEL TRAIN CHUFFER** Jan. 82 £8.98

**SIMPLE INFRA RED REMOTE CONTROL** Nov. 81 £18.70

**EXPERIMENTER CRYSTAL SET** Nov. 81 less aerial £6.60

Headphones £3.36 extra

**CAPACITANCE METER** Oct. 81 £25.81

**SUSTAIN UNIT** Oct. 81 £13.99

'POPULAR DESIGNS' Oct. 81 £60.00

**TAPE NOISE LIMITER** £4.98

**HEADS AND TAILS GAME** £2.75

**CONTINUITY TESTER** £4.48

**PHOTO FLASH SLAVE** £3.80

**FUZZ BOX** £7.50

**SOIL MOISTURE UNIT** £6.39

**ICE ALARM** £8.70

**0-12V POWER SUPPLY** Sept. 81 £19.48

**CMOS CAR SECURITY ALARM** Sept. 81 £9.95

**CMOS DIE** Sept. 81 £8.80

**CMOS METRONOME** Aug. 81 £9.99

**COMBINATION LOCK** July 81 less case £21.53

**LIGHTS REMINDER AND IGNITION LOCATOR** E.E. May 81 £6.26

**SOIL MOISTURE INDICATOR** E.E. May 81 £4.49

**GUITAR HEADPHONE AMP** E.E. May 81 £4.66

**PHONE BELL REPEATER/BABY ALARM** May 81 £7.35

**INTERCOM** April 81 £24.43

**SIMPLE TRANSISTOR & DIODE TESTERS** Mar. 81 Ohm meter version £2.22

LED version £2.98

**LED DICE** Mar. 81 £9.35

**MODULATED TONE DOORBELL** Mar. 81 £7.35

**2 NOTE DOOR CHIME** Dec. 80 £11.35

**LIVE WIRE GAME** Dec. 80 £12.87

**GUITAR PRACTICE AMPLIFIER** Nov. 80 £14.10 less case, Standard case extra £3.88

**SOUND TO LIGHT** Nov. 80 3 channel £23.40

**TRANSISTOR TESTER** Nov. 80 £12.80

**AUDIO EFFECTS UNIT FOR WEIRD SOUNDS** Oct. 80 £14.40

**IRON HEAT CONTROL** Oct. 80 £6.30

**TTL LOGIC PROBE** Sept. 80 £5.68

**ZENER DIODE TESTER** Jun. 80 £7.30

**LIGHTS WARNING SYSTEM** May 80 £5.15

**BATTERY VOLTAGE MONITOR** May 80 £5.66

**CABLE & PIPE LOCATOR** less coil former Mar. 80 £4.61

**KITCHEN TIMER** Mar. 80 £16.20

**MICRO MUSIC BOX** Feb. 80 £17.86

Case extra £3.50

**SLIDE/TAPE SYNCHRONISER** Feb. 80 £13.50

**MORSE PRACTICE OSCILLATOR** Feb. 80 £4.98

**SPRING LINE REVERB UNIT** Jan. 80 £27.20

**UNIBOARD BURGLAR ALARM** Dec. 79 £6.70

**DARKROOM TIMER** July 79 £3.20

**ELECTRONIC CANARY** Jun. 79 £6.40

**TRANSISTOR TESTER** Apr. 79 £5.38

**MICROCHIME DOORBELL** Feb. 79 £17.48

**SPEECH CHECKER** Sept. 78 £2.54

**SOUND TO LIGHT** Sept. 78 £9.20

**CAR BATTERY STATE INDICATOR** less case Sept. 78 £2.29

**R.F. SIGNAL GENERATOR** Sept. 78 £31.20

**IN SITU TRANSISTOR TESTER** Jun. 78 £7.50

**FLASHMETER** less calc & diffuser May 78 £16.50

**WEIRD SOUND EFFECTS GENERATOR** Mar. 78 £6.20

**AUDIO VISUAL METRONOME** Jan. 78 £6.58

**ELECTRONIC TOUCH SWITCH** Jan. 78 £2.99

**RAPID DIODE CHECK** Jan. 78 £3.15

**PHONE/DOORBELL REPEATER** July 77 £8.20

**ELECTRONIC DICE** Mar. 77 £6.24

**FUN WITH ELECTRONICS**

Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed. 64 full colour pages cover all aspects — soldering — fault finding components (identification and how they work). Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 pages clearly show you how.

**COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.**

Supplied less batteries & cases.

**FUN WITH ELECTRONICS, COMPONENT PACK £16.48**

BOOK EXTRA £1.25.

Book available separately.

**MORE KITS AND COMPONENTS IN OUR LISTS**

FREE PRICE LIST

Price list included with orders or send sae (S x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

**ELECTRONICS CATALOGUE**

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery.

Send 80p in stamps or add 80p to order. Free to Schools/Colleges requested on official letterhead.

**MAGENTA ELECTRONICS LTD.**

EE16, 135 HUNTER ST., BURTON-ON-TRENT STAFFS, DE14 2ST. MAIL ORDER ONLY. 0283 65435, Mon-Fri 9-5. Access/Barclaycard (Visa) by phone or post. 24 hr Answerphone for credit card orders.

Add 50p p&p to all orders. Prices include VAT. See all enquiries. Official orders welcome. OVERSEAS: Payment must be sterling. IRISH REPUBLIC and BFPO. UK PRICES. EUROPE: UK PRICES plus 10%. ELSEWHERE: write for quote.

BARCLAYCARD  
A CARD WITH A LIFE

★ **NEW SERIES — ALL COMPONENTS IN STOCK NOW FOR FAST DELIVERY.** All top quality components as specified by Everyday Electronics. Our kit comes complete with FREE COMPONENT IDENTIFICATION SHEET. Follow this educational series and learn about electronics — Start today.

★ **MAGENTA'S TEACH IN KIT INCLUDES ALL OF THESE TOP QUALITY ITEMS:** resistors, pot, capacitors, semiconductors, varicap diode, leds, ferrite rod, sockets, crystal earpiece, terminal blocks, wire and of course 2 breadboards. **PLUS A FREE COPY OF OUR CATALOGUE & PRICE LIST. AVAILABLE NOW**

★ **— TEACH IN 84 KIT. £18.98 inc VAT. P + P 50p.** Send now for fast delivery. Reprints of previously published parts 50p each.

★ Official school/college orders welcome.

## SOLDERING/TOOLS

<b>ANTEX X5 SOLDERING IRON 25W</b>	£6.29
<b>SOLDERING IRON STAND</b>	£2.18
<b>SPARE BITS.</b> Small, standard, large, each For X5+X25	£1.04
<b>SOLDER.</b> Handy size	£1.38
<b>SOLDER CARTON</b>	£2.50
<b>DESOLDER BRAID</b>	65p
<b>HEAT SINK TWEZERS</b>	35p
<b>DESOLDER PUMP</b>	£6.40
<b>HOW TO SOLDER LEAFLET</b>	13p
<b>LOW COST CUTTERS</b>	£1.69
<b>LOW COST LONG NOSE PLIERS</b>	£1.68
<b>WIRE STRIPPERS &amp; CUTTERS</b>	£2.88

<b>PRECISION PETITE 12V PCB DRILL</b>	£12.80
<b>DRILL STAND</b>	£1.78
<b>VERO SPOT FACE CUTTER</b>	£1.76
<b>PIN INSERTION TOOL</b>	£2.52
<b>VEROPINS (pk of 100 0.1")</b>	65p
<b>MULTIMETER TYPE 1 (1,000 opv)</b>	£5.85
<b>CROCODILE CLIP TEST LEAD SET.</b> 10 leads with 20 clips	£1.15
<b>RESISTOR COLOUR CODE CALCULATOR 23p</b>	£1.15
<b>CONNECTING WIRE PACK TYPE ED. 11</b>	40p
<b>ILLUMINATED MAGNIFIERS</b>	£1.32
Small 2" dia. (5 x mag)	£2.32
Large 3" dia. (1 x mag)	39p
<b>CORE TRIM TOOL</b>	60p
<b>PRESET TRIM TOOL</b>	60p
<b>FREZZER AEROSOL</b>	£1.59
<b>CONTACT CLEANER AEROSOL</b>	£1.45
<b>ELECTROLIT CONDUCTIVE PAINT</b>	£4.99
<b>PVC TAPE (RGB) 3 reels</b>	£3.99
<b>SCREWDRIVER SET</b>	£1.98
<b>POCKET TOOL SET</b>	£3.98
<b>DENTISTS INSPECTION MIRROR</b>	£2.85
<b>JEWELLERS EYEGLASS</b>	£1.50
<b>PLASTIC TWEZERS</b>	69p

**MULTIMETER TYPE 2 (YN360TR) 20K o.p.v.** with transistor tester. £14.99  
AC + DC volts, DC current, 4 very useful resistance ranges. We've used it and we like it.



**HELPING HANDS JIG** £6.65  
Heavy base. Six ball and socket joints — allow infinite variation of clips through 360°. Has 2" diameter 12.5 magnifier attached, used and recommended by our staff.



**PAIR OF PROBES WITH LEADS (cc).** 77p  
**Q MAX PUNCHES** 3/8" £2.98; 1/2" £3.06; 5/8" £3.17; 3/4 3.24.

<b>Speakers</b> Min 8 ohm 87p; 64 ohm 89p; 80 ohm 90p	£6.48
<b>Crystal earpiece</b>	57p
Magnetic earpiece	19p
Stethoscope attachment	89p
Mono headphones	£3.36
Headphones	£5.49
Telephone pickup coil	68p
Min buzzer 6V 75p. 12V 72p.	£6.20
Euro breadboard	£3.98
S Dec breadboard	£6.98
Bimboard breadboard	£5.88
Verobloc breadboard	£5.88

**BOOKS:**

A Practical Introduction to Digital IC's £1.75

How to design and Make Your Own PCB's £1.95

50 Simple L.E.D. Circuits £1.95

How to Make Walkie-Talkies £1.95

Projects in Opto-Electronics £1.95

Electronic Projects for Beginners £1.95

Electronic Security Devices £1.95

50 Circuits Using 7400 Series IC's £1.75

Second Book of CMOS IC Projects £1.75

Electronic Household Projects £1.75

Radio Control for Beginners £1.75

Electronic Synthesiser Projects £1.75

How to Identify Unmarked IC's 65p

International Diode Equivalents Guide £2.25

Handbook of Integrated Circuits (IC's) Equiv. & Substitutes £1.95

Beginners Guide to Building Electronic Projects £1.95

Second Book of Transistor Equivalents and Substitutes £1.75

How to Build Your Own Solid State Oscilloscope £1.95

Semiconductor Data Book Newnes £8.98

Basic Electronics: Theory and practice £8.98

Burglar Alarm Systems £5.55

Electronics, Build and Learn £3.90

Electronic Projects in Music £3.90

Electronic Projects in Photography £3.90

Microprocessors for Hobbyists £4.75

Electronic Test Equipment Construction BP75 £1.75

Electronic Projects for Home Security £2.90

Questions and Answers Electronics £2.70

20 Solid State Projects Car and Garage £4.80

110 Electronic Alarm Projects £5.98

52 Projects using IC741 £1.25

IC555 Projects £1.95

Electronic Music Projects £1.75

Practical Construction of Pre-Amps, Tone Controls, Filters + Atten. £1.95

Radio Control For Beginners £1.75

Mobile Disco Handbook £1.35

More books in our price list

**ADVENTURES WITH MICROELECTRONICS**

Similar to 'Electronics' below. Uses IC's. Includes dice, electronic organ, doorbell, reaction timer, radio etc. Based on Bimboard 1 bread board. Adventures with Microelectronics £3.20 Component pack £34.64 less battery.

**ADVENTURES WITH ELECTRONICS** by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.

Adventures with Electronics £2.85. Component pack £20.98 less battery.

# MAPLIN Massive range of components for your hobby....insist on Maplin quality!

## MAPLIN'S TOP TWENTY KITS

THIS LAST MONTH	DESCRIPTION OF KIT	ORDER CODE	KIT PRICE	DETAILS IN PROJECT BOOK
1. (1)	75W Mosfet Amp Module	LW51F	£12.95	Best of E&MM
2. (3)	Modem	LW99H	£44.95	5 XA05F
<i>Case also available: YK62S Price £9.95.</i>				
3. (5)	ZX81 I/O Port	LW76H	£9.25	4 XA04E
4. (4)	Car Burglar Alarm	LW78K	£6.95	4 XA04E
5. (8)	Partylite	LW93B	£9.45	Best of E&MM
6. (2)	Keyboard for ZX81	LW72P	£23.95	3 XA03D
<i>Case also available: XG17T £4.95. Complete ready-built: XG22Y £32.50</i>				
7. (10)	8W Amp Module	LW36P	£4.45	Catalogue
8. (14)	VIC20/64 RS232 Interface	LK11M	£9.45	7 XA07H
9. (7)	Syntom Drum Synthesiser	LW86T	£11.95	Best of E&MM
10. (12)	Harmony Generator	LW91Y	£17.95	Best of E&MM
11. (17)	Spectrum RS232 Interface	LK21X	£17.95	8 XA08J
12. (6)	VIC20 Speech Synthesiser	LK00A	£22.95	6 XA06G
13. (13)	ZX81 Sounds Generator	LW96E	£10.95	5 XA05F
14. (11)	Ultrasonic Intruder Detector	LW83E	£10.95	4 XA04E
15. (15)	Logic Probe	LK13P	£9.95	8 XA08J
16. (26)	Car Battery Monitor	LK42V	£6.25	Best of E&MM
17. (18)	Hexadrum	LW85G	£19.95	Best of E&MM
18. (21)	Synwave Sounds Synth	LW87U	£10.95	Best of E&MM
19. (25)	Spectrum Keyboard	LK29G	£28.50	9 XA09K
<i>Also required: LK30H £6.50; Case: XG35Q £4.95 — Total £39.95.</i>				
<i>Also available complete ready-built: XG36P £44.95.</i>				
20. (9)	ZX81 Speech Synthesiser	LK01B	£16.95	6 XA06G

Over 80 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.



## MAPLIN'S FASCINATING PROJECTS BOOKS


Full details in our Project Books  
Price 70p each.

In Book 1 (XA01B) 120W rms Mosfet Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • 6 Vero Projects. In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W Mosfet Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to 600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.

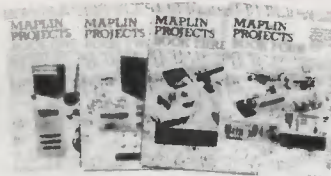In Book 5 (XA05F) 300 Baud Duplex Modem to European Standard • 100W 240VAC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Alarm.



In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 • Module to Bridge two of our Mosfet Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20/Commodore 64 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.

In Book 8 (XA08J) Modem (RS232) Interface for Dragon 32 & Spectrum • Synchime • I/O Ports for Dragon 32 • Electronic Lock • Mnilab Power Supply • Logic Probe • Doorbell for the Deaf.

In Book 9 (XA09K) Keyboard with Electronics for ZX Spectrum • Infra-

Red Intruder Detector • Multimeter to Frequency Meter Converter • FM Radio needs no alignment • Hi-Res Graphics for ZX81 • Speech Synthesiser for Oric 1 • VIC20 ExtendiBoard • ZX81 ExtendiRAM • Dynamic Noise Limiter for Personal Cassette Players • TTL Levels to RS232 Converter • Logic Pulser • Pseudo-Stereo AM Radio • Ni-Cad Charger Timer •

Adder-Subtractor • Syndrum's Interface • Microphone Pre-Amp Limiter. In Book 10 (XA10L) Cassette Easyload for ZX Spectrum • 80m Amateur Receiver • Auto Waa-Waa Effects Unit • Oric 1 Modem Interface • 2.8kW Mains Power Controller • Extendiport for Dragon 32 • 12V Fluorescent Tube Driver • 32-Line Extension for Digi-Tel.

### 1984 CATALOGUE

A massive 480 big pages of description, pictures and data and now with prices on the page. The new Maplin catalogue is the one book no constructor should be without. Now includes new Heathkit section. On sale in all branches of W.H. Smith. Price £1.35 — It's incredible value for money. Or send £1.65 (including p & p) to our mail-order address.

### GREAT PROJECTS FROM E&MM


Our book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first Year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects. Order As XH61R. Price £1.

Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packaging. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65

Name .....

Address .....

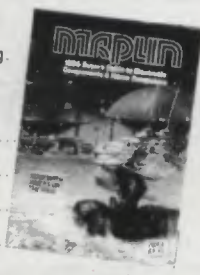

EE/5/84

# MAPLIN

ELECTRONIC SUPPLIES LTD

Mail Order. P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 • Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926. • 8 Oxford Road, Manchester. Tel: 061-236-0281. • Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292. • 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000. • 46-48 Bevois Valley Road, Southampton. Tel: 0703 25831. All shops closed all day Monday.

All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

Despatch by return of post where goods available.