

EVERYDAY

JULY 1990

ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

£1.40

VIDEO CHECK

TOW-TEST

**GRAND
NATIONAL
GAME**

**CHOOSING AND USING
TEST EQUIPMENT—**

THE OSCILLOSCOPE

ISSN 0262-3617



9 770262 361003

The Magazine for Electronic & Computer Projects



ONE POUND PACKS



All packs are £1 each. Note the figure on the extreme left of the pack ref number and the next figure is the quantity of items in the pack, finally a short description.

- BD2 5 13A spurs provide a fused outlet to a ring main where devices such as a clock must not be switched off.
- BD9 2 6V 1A mains transformers upright mounting with fixing clamps.
- BD11 1 6 1/2in speaker cabinet ideal for extensions, takes our speaker. Ref BD137.
- BD13 12 30 watt reed switches, it's surprising what you can make with these—burglar alarms, secret switches, relay, etc., etc.
- BD22 2 25 watt loudspeaker two unit crossovers.
- BD30 2 Nicad constant current chargers adapt to charge almost any nicad battery.
- BD32 2 Humidity switches, as the air becomes damper the membrane stretches and operates a microswitch.
- BD42 5 13A rocker switch three tags so on/off, or change over with centre off.
- BD45 1 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day. original cost £40 each.
- BD49 5 Neon valves, with series resistor, these make good night lights.
- BD56 1 Mini unisector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through one pole.
- BD67 1 Suck or blow operated pressure switch, or it can be operated by any low pressure variation such as water level in water tanks.
- BD103A 1 6V 750mA power supply, nicely cased with mains input and 6V output leads.
- BD120 2 Stripper boards, each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc.
- BD132 2 Plastic boxes approx 3in cube with square hole through top so ideal for interrupted beam switch.
- BD134 10 Motors for model aeroplanes, spin to start so needs no switch.
- BD139 6 Microphone inserts—magnetic 400 ohm also act as speakers.
- BD148 4 Reed relay kits, you get 16 reed switches and 4 coil sets with notes on making c/o relays and other gadgets.
- BD149 6 Safety cover for 13A sockets—prevent those inquisitive little fingers getting nasty shocks.
- BD180 6 Neon indicators in panel mounting holders with lens.
- BD193 6 5 amp 3 pin flush mounting sockets make a low cost disco panel.
- BD199 1 Mains solenoid, very powerful, has 1in pull or could push if modified.
- BD201 8 Keyboard switches—made for computers but have many other applications.
- BD211 1 Electric clock, mains operated, put this in a box and you need never be late.
- BD221 5 12V alarms, make a noise about as loud as a car horn. Slightly soiled but OK.
- BD252 1 Panostat, controls output of boiling ring from simmer up boil.
- BD259 50 Leads with push-on 1/4in tags—a must for hook-ups—mains connections etc.
- BD263 2 Oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted into pattress.
- BD268 1 Mini 1 watt amp for record player. Will also change speed of record player motor.
- BD305 1 Tubular dynamic mic with optional tail rest.
- BD653 2 Miniature driver transformers. Ref. LT44. 20k to 1k centratapped.
- BD548 2 3.5V relays each with 2 pairs changeover contacts.
- BD667 2 4.7 µf non-polarised block capacitors, pcb mounting.

There are over 1,000 items in our Catalogue. If you want a complete copy please request this when ordering.

- FLOPPY DISCS 5 1/4" pack of 10 £5.00. Ref. 5P168. 3 1/2" pack of 10 £10.00. Ref. 10P88.
- TOASTERS 2 slice toasters—may need slight attention. Only £3.00 each. Ref 3P84.
- PERSONAL STEREOS Again customer returns but complete and with stereo head phones. A bargain at only £3.00 each. Our ref 3P83.
- MICROWAVE CONTROL PANEL Mains operated, with touch switches. This unit has a 4 digit display with a built in clock and 2 relay outputs—one for power and one for pulsed power level. Could be used for all sorts of timer control applications. Only £6.00. Our ref 6P18.
- EQUIPMENT WALL MOUNT Multi adjustable metal bracket ideal for speakers, lights, etc. 2 for £5.00. Our ref 5P152.
- NEW MAINS MOTORS 25 watt 3000 rpm made by Framco. Approx 6" x 3" x 4". Priced at only £4.00 each. Our ref 4P54.
- SHADED POLE MOTORS Approx 3" square. Available in 24V and 240V AC. Both with threaded output shaft and 2 fixing bolts. Price is £2.00 each. 24V Ref 2P65, 240V Ref 2P66.
- SUB-MIN TOGGLE SWITCH Body size 8mm x 4mm x 7mm SBDT with chrome dolly fixing nuts. 3 for £1. Order ref BD649.
- COPPER CLAD PANEL for making PCB. Size approx 12in long x 8 1/2in wide. Double-sided on fibreglass middle which is quite thick (about 1.6in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price £1 each. Our ref BD683.

POWERFUL IONISER

Generates approx. 10 times more IONS than the ET1 and similar circuits. Will refresh your home, office, workroom etc. Makes you feel better and work harder—a complete mains operated kit, case included. £18. Our ref 18P2.

REAL POWER AMPLIFIER for your car, it has 150 watts output. Frequency response 20Hz to 20KHz and signal to noise ratio better than 60dB. Has built in short circuit protection and adjustable input level to suit your existing car stereo, so needs no pre-amp. Works into speakers ref. 30P7 described below. A real bargain at only £57.00. Order ref: 57P1.

REAL POWER CAR SPEAKERS. Stereo pair output 100W each. 40hm impedance and consisting of 8 1/2" woofer, 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00. Order ref: 30P7.

STEREO CAR SPEAKERS. Not quite so powerful—70w per channel. 3" woofer, 2" mid range and 1" tweeter. Again, in a super purpose built shelf mounting unit. Price per pair £30.00. Order ref: 30P1.

VIDEO TAPES These are three hour tapes of superior quality, made under licence from the famous JVC Company. Offered at only £3 each. Our ref 3P63. Or 5 for £11. Our ref 11P3. Or for the really big user 10 for £20. Our ref 20P20.



ELECTRONIC SPACESHIP.

Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with really detailed instructions. Ideal present for budding young electrician. A youngster should be able to assemble but you may have to help with the soldering of the components on the pcb. Complete kit £10. Our ref. 10P81

COMPUTER KEYBOARDS Brand new, uncased. £3.00 each. ref 3P89.

12" HIGH RESOLUTION MONITOR Amber screen, beautifully cased for free standing, needs only a 12v 1.5 amp supply. Technical data is on its way but we understand these are TTL input. Brand new in makers' cartons. Price: £22.00. Order ref: 22P2.

SINCLAIR C5 WHEELS

Including inner tubes and tyres. 13" and 16" diameter spoked poly carbonate wheels. Finished in black. Only £6.00 each. 13" Ref 6P10, 16" Ref 6P11

COMPOSITE VIDEO KITS These convert composite video into separate H sync, V sync and video. Price £8.00. Our ref 8P39.

LINEAR POWER SUPPLY Brand new +5v 3A, +/-12v 1A. Complete with circuit diagram. Short circuit protected. Our price £12.00 Ref 12 P21.

3 1/2in FLOPPY DRIVES We still have two models in stock: Single sided, 80 track, by Chinon. This is in the manufacturers metal case with leads and IDC connectors. Price £40, reference 40P1. Also a double sided, 80 track, by NEC. This is uncased. Price £60.00, reference 60P2. Both are brand new.

10 MEMORY PUSHBUTTON TELEPHONES These are customer returns and "sold as seen". They are complete and may need slight attention. Price £6.00. Ref. 6P16 or 2 for £10.00. Ref. 10P77. BT approved.

INDUCTIVE PROXIMITY SWITCHES These will detect ferrous or non-ferrous metals at approx. 10mm and are 10-36V operation. Ideal for alarms position sensors, etc. RS price is £64.00 each! Ours £12.00. Ref. 12P19.

RETROFLECTIVE MODULATED INFRARED 5M BEAMS IR transmitter and receiver housed in the same case. Ideal for beam alarms, counting, etc. RS price is £95.00 each! Ours £25.00. Ref. 25P15.

ASTEC PSU. Mains operated switch mode, so very compact. Outputs +12v 2.5A, +5v 6A, ±5v 5A, ±12v 5A. Size: 7 1/2in x 4 1/2in wide x 2 1/2in high. Cased ready for use. Brand new. Normal price £30+, our price only £13.00. Order ref 13P2.

VERY POWERFUL 12 VOLT MOTORS. 1/2hp Horsepower. Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20. Our ref 20P22. ALSO AVAILABLE WITH GEARBOX A 4:1 reduction giving 800rpm. Our ref 40P8. Price £40.

PHILIPS LASER

This is helium-neon and has a power rating of 2mW. Completely safe as long as you do not look directly into the beam when eye damage could result. Brand new, full spec. £35. Our ref. 35P1. Mains operated power supply for this tube gives 8kv striking and 1.25kv at 5mA running. Complete kit with case £15.

PANEL METERS 270 deg movement. New. £3.00 each. Our ref 3P87.

SURFACE MOUNT KIT Makes a super high gain snoothing amplifier on a PCB less than an inch square! £7.00. Our ref 7P15.

CB CONVERTERS Converts a car radio into an AM CB receiver. £4.00. Our ref 4P48.

GEIGER COUNTER KIT Includes PCB, tube, loudspeaker, and all components to build a 9v battery operated geiger counter. Only £39. Our ref 39P1.

12V TO 220V INVERTER KIT This kit will convert 12v DC to 220v AC. It will supply up to 130 watts by using a larger transformer. As supplied it will handle about 15 watts. Price is £12. Our ref 12P17.

SINCLAIR GEARBOXES These are the original gearboxes and give about 50% reduction in speed and a toothed pulley output. Price for the gearbox AND motor is £40.00. Ref. 40P8.

SPECTRUM AND COMMODORE SOFTWARE Pack of 5 different tapes only £3.00. Ref. 3P96 for Spectrum and 3P97 for Commodore 64.

HIGH RESOLUTION MONITOR 9in black and white, used Philips tube M24360W. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new. £20. Our ref 20P26.

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape (4 1/2in x 4 1/2in x 1 1/2in). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motor do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref 8P26.

MINI MONO AMP on p.c.b. size 4" x 2" (app.) Fitted Volume control. The amplifier has three transistors and we estimate the output to be 2W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.00.



BULL ELECTRICAL

Dept. EE 250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5QT.

MAIL ORDER TERMS: Cash, PO or cheque with order. Monthly account orders accepted from schools and public agencies. Please add £2.50 postage to orders. Minimum order £5. Phone (0273) 203500. Fax No. (0273) 23077.

POPULAR ITEMS — MANY NEW THIS MONTH

MAINS FANS Snail type construction. Approx. 5" x 4" mounted on a metal plate for easy fixing. New. £5.00 each. Our ref 5P166.

MICROWAVE TURNABLE MOTOR Complete with weight sensing electronics that would have varied the cooking time. Ideal for window displays, etc. Only £5.00. Our ref 5P165.

JOYSTICKS for BBC Atari, Dragon Commodore, etc. All £5.00 each. All brand new, state which required.

TELEPHONE TYPE KEYPAD. Really first class rear mounting unit. White lettering on black buttons. Has conductive rubber contacts with soft click operation. Circuit arranged in telephone type array. Requires 70mm by 55mm cutout and has a 10 IDC connector. Price £2.00. Ref. 2P251.

SUB-MIN PUSH SWITCHES Not much bigger than a plastic transistor but double pole PCB mounting. 3 for £1.00. Our ref BD688.

AA CELLS Probably the most popular of the rechargeable NICAD types. 4 for £4.00. Our ref. 4P44.

20 WATT 4 OHM SPEAKER With built in tweeter. Really well made unit which has the power and the quality for hi-fi 6 1/2" dia. Price £5.00. Our ref. 5P155 or 10 for £40.00 ref. 40P7.

MINI RADIO MODULE Only 2in square with ferrite aerial and solid dia. tuner with own knob. It is superhet and operates from a PP3 battery and would drive a crystal headphone. Price £1.00. Our ref. BD716.

BULGIN MAINS PLUG AND SOCKET The old and faithful 3 pin with screw terminals. The plug is panel mounted and the socket is cable mounted. 2 pairs for £1.00 or 4 plugs or 4 sockets for £1.00. Our ref. BD715, BD715P, or BD715S.

MICROPHONE Low cost hand held dynamic microphone with on/off switch in handle. Lead terminates in 1.35mm and 1.25mm plug. Only £1.00. Ref. BD711.

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES 140V 100 watt pair made by Hitachi. Ref. 2S199 and its complement 2SK343. Only £4.00 a pair. Our ref. 4P51.

TIME AND TEMPERATURE LCD MODULE A 12 hour clock a Celsius and Fahrenheit thermometer a too hot alarm and a too cold alarm. Approx 50x20mm with 12.7mm digits. Requires 1AA battery and a few switches. Comes with full data and diagram. Price £9.00. Our ref. 9P5.

REMOTE TEMPERATURE PROBE FOR ABOVE. £3.00. Our ref. 3P60.

PAPST fan 80 x 80mm 230V. Our ref 9P7. Price £9.

PAPST fan 120 x 120mm 230V. Our ref 6P6. Price £6.

600 WATT AIR OR LIQUID MAINS HEATER Small coil heater made for heating air or liquids. Will not corrode, lasts for years. Coil size 3" x 2" mounted on a metal plate for easy fixing. 4 dia. Price £3.00. Ref. 3P78 or 4 for £10.00. Our ref. 10P76.

EX-EQUIPMENT POWER SUPPLIES Various makes and specs. Ideal bench supply. Only £8.00. Our ref. 8P36.

ACORN DATA RECORDER Made for the Electron or BBC computer but suitable for others. Includes mains adaptor, leads and book. £12.00. Ref. 12P15.

PTE COATED SILVER PLATED CABLE 19 strands of .45mm copper will carry up to 30A and is virtually indestructible. Available in red or black. Regular price is over £120 per reel. Our price only £20.00 for 100m reel. Ref. 20P21 or 1 of each for £35.00. Ref. 35P2. Makes absolutely superb speaker cable!

NEW PIR SENSORS Infra red movement sensors will switch up to 500W mains. UK made. 12 months manufacturers warranty. 15-20m range with a 0-10m timer, adjustable wall bracket. Only £20.00. Ref. 20P24. Also available to switch 1000watts. Our ref. 25P16. Price £25.

GEARBOX KITS Ideal for models, etc. Contains 18 gears (2 of each size), 4 x 50mm axles and a powerful adjustable speed motor. 9-12V operation. All the gears, etc. are 2mm push fit. £3.00 for the complete kit. Ref. 3P93.

MINI HI-FI SPEAKERS Made for televisions, etc. Two sizes available. 70mm x 57mm 3W 8 ohm, 2 for £3.00. Ref. 3P99. 127mm x 57mm 5W 8 ohm, 2 for £3.00. Ref. 3P100.

SPECTRUM SOUND BOX Add sound to your Spectrum with this device. Just plug in. Complete with speaker, volume control and nicely boxed. A snip at only £4.00. Our ref. 4P53.

BBC JOYSTICK INTERFACE Converts a BBC joystick port to an Atari type port. Price £2.00. Our ref. 2P261.

TELEPHONE EXTENSION LEAD 5m phone extension lead with plug on one end, socket on the other. White. Price £3.00. Our ref. 3P70 or 10 leads for only £19.00! Ref. 19P2.

LCD DISPLAY 4 1/2" digits supplied with connection data £3.00. Ref. 3P77 or 5 for £10. Ref. 10P78.

CROSS OVER NETWORK 8 Ohm 3 way for tweeter midrange and woofer nicely cased with connections marked. Only £2.00. Our ref. 2P255 or 10 for £15.00. Ref. 15P32.

BASE STATION MICROPHONE Top quality uni-directional electret condenser mic 600 impedance sensitivity 16-18KHz — 68db built in chime complete with mic stand bracket. £15.00. Ref. 15P28.

MICROPHONE STAND Very heavy chromed mic stand, magnetic base 4" high. £3.00 if ordered with above mic. Our ref. 3P80.

SOLAR POWERED NICAD CHARGER 4 Nicad AA battery charger. Charges 4 batteries in 8 hours. Price £6.00. Our ref. 6P3.

SOLDERING IRON STAND Price £3.00. Our ref. 3P66.

INCAR GRAPHIC EQUALIZER/BOOSTER Slimline 7 band with built in 30 watts per channel amplifier. 12V operation, twin 5 LED power indicators, 20-21KHz with front and rear fader plus headphone output! Brand new and guaranteed. Only £25.00. Ref. 25P14.

SHARP PLOTTER PRINTER. New 4 colour printer originally intended for Sharp computers but may be adaptable for other machines. Complete with pens, paper, etc. Price £16.00. Our ref. 16P3.

CENTRONICS ADAPTER KIT Converts the above plotter/printer to Centronics compatible. Price £4.00. Our ref. 4P57.

CAR IONIZER KIT Improve the air in your car, clears smoke and helps prevent fatigue. Case ref. Price £12.00. Our ref. 12P8.

NEW FM BUG KIT New design with PCB embedded coil 9v operation. Priced at £5.00. Our ref. 5P158.

NEW PANEL METERS 50µA movement with three different scales that are brought into view with a lever. Price only £3.00. Ref. 3P81.

STROBE LIGHTS Fit a standard edison screw light fitting 240V 40min. flash rate available in yellow, blue, green and red. Complete with socket. Price £10 each. Ref. 10P80 (state colour required).

ELECTRONIC SPEED CONTROL KIT Suitable for controlling our powerful 12v motors. Price £17.00. Ref. 17P3 (heatsink required).

EXTENSION CABLE WITH A DIFFERENCE It is flat on one side making it easy to fix and look tidy. 4 core, suitable for alarms, phones etc. Our price only £5.00 for 50m reel. Ref. 5P153.

METAL PROJECT BOX Ideal for battery charger, power supply etc. Sprayed grey size 8" x 4" x 4 1/2". Louvered for ventilation. Price £3.00. Ref. 3P75.

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY





ABC

VOL 19 No. 7 JULY 1990

The Magazine for Electronic & Computer Projects

ISBN 0262-3617

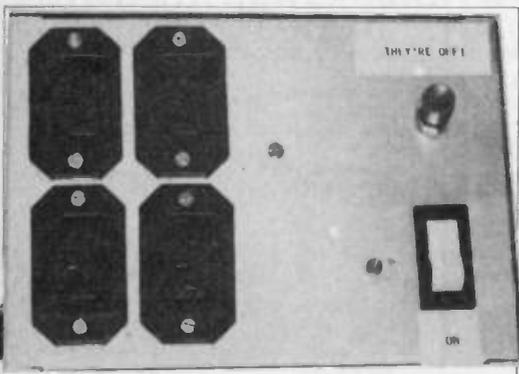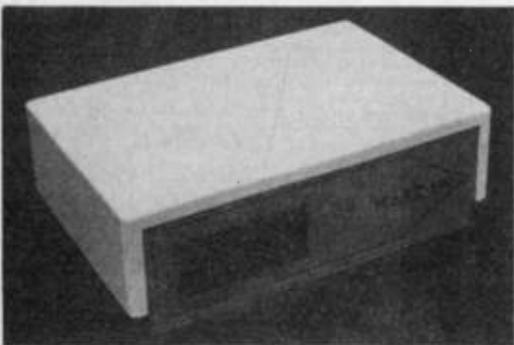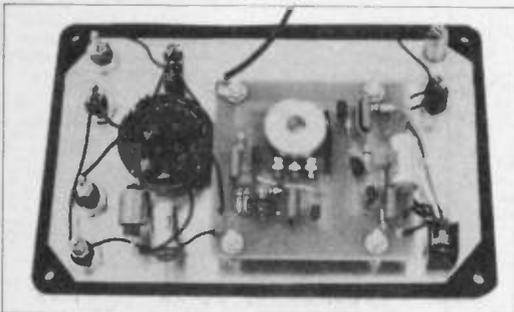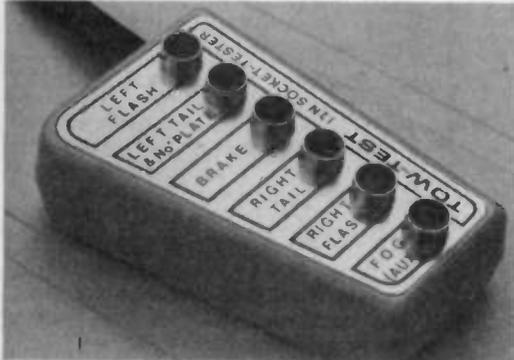PROJECTS . . . THEORY . . . NEWS . . .
COMMENT . . . POPULAR FEATURES . . .



© Wimborne Publishing Ltd 1990. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduced or imitations in whole or in part are expressly forbidden.

Projects

- GRAND NATIONAL GAME** by Ivan Partick Gore 436
A horse racing game with various odds, for fun or fund raising
- VIDEO CHECK** by T. R. de Vaux-Balbirnie 444
Inexpensive light level check for camcorder users
- MAINS APPLIANCE REMOTE CONTROL SYSTEM - 2** by Chris Walker 457
Control household appliances from your armchair or computer
- TOW-TEST** by Peter Rawnsley 466
Checks out the tow socket wiring easily
- THE TESTER** by George Hylton 480
A versatile and unusual item of test gear

Series

- CHOOSING AND USING TEST EQUIPMENT** by Robert Penfold 448
Oscilloscope specifications and uses explained
- ROBOT ROUNDUP** by Nigel Clark 465
investigating the world of robotics
- MICRO IN CONTROL - Part 8** by John Hughes 470
Now we're getting to the microprocessor
- ON SPEC** by Mike Tooley 476
The place for Spectrum and Sam micro owners
- AMATEUR RADIO** by Tony Smith G4FA1 479
Intruder Watch, Esperanto, Novice Licence
- BBC MICRO** by Robert Penfold 484
Communications applications software

Features

- EDITORIAL** 435
- FOR YOUR ENTERTAINMENT** 443
Not British, All That Jazz, Crystal Gazing
- MARKET PLACE** 453, 475
Readers buy, sell and swap spot
- SHOP TALK** with David Barrington 468
Product news and component buying
- EE SPECIAL OFFER** 469
Passive Infra-Red intruder Detector
- DOWN TO EARTH** by George Hylton 486
Interference Filters
- DIRECT BOOK SERVICE** 488
Selected technical books by mail order
- PRINTED CIRCUIT BOARD SERVICE** 492
- ADVERTISERS INDEX** 496

Our August '90 Issue will be published on Friday, 6 July 1990. See page 427 for details.
Everyday Electronics, July 1990

Readers Services • Editorial and Advertisement Departments 435
Cover photograph by Reflections of Bournemouth

425

THE RTC MONITOR II

100 WATT SPEAKER KIT £60.00 + £3.50 P&P (pair)

RESPONSE: 55Hz-20kHz

BASS POLYMER CONE D: 22cm

DOM TWEETER: 14mm

OVERALL SIZE
(HWD): 382,252,204mm

RECOMMENDED AMP POWER:
10-100 watts per channel

The performance standard achieved in this compact design is distinctively superior to anything else available at the price. The drive units used are of sophisticated design and have been carefully integrated with a Complex Crossover. Stereo performance is exceptionally good with a well focussed sound stage and sharp resolution of detail. Distortion throughout the frequency range is low even at quite high power input and this gives a great sense of dynamic range and openness especially when used in bi-wired mode.

Supplied with:— 2 READY CUT BAFFLES, ALL CROSSOVER COMPONENTS, 2 BASS MID-RANGE, 2 DOME TWEETERS, HOOK UP WIRE, GRILLE CLOTH, SCREW TERMINALS AND SCREWS.



ROSS MULTI TESTER

As new condition but have been returned by customers or shops so they may need some attention. Hence the price of £3.50 each plus £1.60 P&P. Order five and get the sixth one free. Postage £5.40.



LCD DIGITAL MULTI TEST METER AC DC Volts resistance and DC Amps. Most of these units are new but have been returned or rejected by the store and sold with all faults at £11.00 each. Postage £1.00. (Made by Ross Electronics).

ROSS PUSH BUTTON RADIO

Mains and battery operated. High quality VHF/FM, Medium and Long Wave reception. 6 pushbutton selected preset stations. Fully retractable telescopic aerial. Headphone/earphone jack socket.



Size 230H x 150W x 65D.
Ref RE-5500.
Brand new.
Listed price over £30.00.

Price £14.95 + £2.80 P&P

SHURE HIFI STEREO MAGNETIC CARTRIDGE Fitted with an elliptical diamond stylus supplied with fitting kit and instructions. A good quality unit made to sell for well over twenty pounds due to scoop purchase, we are able to offer these at a fraction of the manufacturers price. All units are brand new and boxed. £7.20 each. If you order in multiples of five you get one free. Postage £1.30 (Made in U.S.A.)

KOSS STEREO HEADPHONES High quality light weight stereo headphones fitted 3.5mm jack with adaptor to 6.4mm jack. Ideal use Hifi or personal stereos. Made to sell for nine pounds. Our price for this unit £4.25. Postage 60p.

TV SOUND TUNER KIT



In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are quite common and that really is quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact independent TV tuner that connect direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 4 pre-selected tuning controls. All parts including Varicap tuner, mains transformer, PCB with IC's, capacitors and coils etc., to build the unit illustrated above; without case and scale.

£11.50 + £2.30 P&P

Case as illustrated £6.90 + £2.00 P&P

MAIL ORDER £1 BARGAIN PACKS BUY 20 GET 1 FREE

Please state pack(s) required

No.	Qty.	per pack
BP015B	1	30W dome tweeter. Size 90x66mil JAPAN made
BP016	6	2200µf can type Electrolytic 25V d.c. computer grade made in UK by PHILIPS
BP017	3	33000µf 16V d.c. electrolytic high quality computer grade UK made
BP019	20	20 ceramic trimmers
BP020	4	Tuning capacitors, 2 gang dielectric a.m. type
BP021	10	3 position, 8 tag slide switch 3 amp rated 125V a.c. made in USA
BP022	5	Push-button switches, push on push off, 2 pole change over. PC mount JAPAN made
BP023	6	2 pole 2 way rotary switch
BP024	2	Right angle, PCB mounting rotary switch, 4 pole, 3 way rotary switch UK made by LORLIN
BP025	4	3 pole, 3 way miniature rotary switch with one extra position off (open frame YAXLEY type)
BP026	4	4 pole, 2 way rotary switch UK made by LORLIN
BP027	30	Mixed control knobs
BP029	6	Stereo rotary potentiometers
BP030	2	10k wire wound double precision potentiometers UK made
BP031	6	Single 100k multitune pots, ideal for varicap tuners UK made by PHILIPS
BP032	4	UHF varicap tuner heads, unboxed and untested UK made by PHILIPS
BP033	2	FM stereo decoder modules with diagram UK made by PHILIPS
BP033A	4	6"x¼" High grade Ferrite rod. UK made
BP034	3	AM IF modules with diagram PHILIPS UK made
BP034A	2	AM-FM tuner head modules. UK made by Mullard
BP034B	1	Hi-Fi stereo pre-amp module inputs for CD, tuner tape, magnetic cartridge with diagram. UK made by MULLARD
BP035	6	All metal co-axial aerial plugs
BP036	6	Fuse holders, panel mounting 20mm type
BP037	6	In line fuse holders 20mm type UK made by BULGIN
BP038	20	5 pin din, 180° chassis socket
BP039	6	Double phono sockets, Paxolin mounted
BP041	3	2.8m lengths of 3 core 5 amp mains flex
BP042	2	Large VU meters JAPAN made
BP043	30	4V miniature bulbs, wire ended, new untested
BP044	2	Sonotone stereo crystal cartridge with 78 and LP styli JAPAN made
BP045A	2	Mono Cassette Record and play heads
BP046A	2	606 Mains transformers, PCB mounting. Size 42x33x35
BP047	1	24V 0.3VA mains power supply. Brand new boxed UK made by MULLARD
BP047A	1	25V DC 150mA mains adaptor in black plastic case with flying input and output leads new units made for famous sound mixer manufacturer. Size 80x55x47
BP049	10	OC44 transistors. Remove painter from top and it becomes a photo-electric cell (ORP 12) UK made by MULLARD
BP050	30	Low signal transistors n.p.n., p.n.p. types
BP051	6	14 watt output transistors. 3 complimentary pairs In TO66 case (ideal replacement for AD161 and 162s)
BP052A	1	Tape deck pre-amp IC with record/replay switching No LM1818 with diagram
BP053	5	5 watt audio ICs. No TBA800 (ATEZ)
BP054	10	Motor speed control ICs, as used with most cassette and record player motors
BP055	1	Digital DVM meter IC, made by PLESSEY as used by THANDAR with diagram
BP056	4	7 segment 0.3 LED display (red)
BP057	8	Bridge rectifiers, 1 amp, 24V
BP058	200	Assorted carbon resistors
BP059	1	Power supply PCB with 30V 4VA transformer. MC7818CT IC & bridge rectifier: Size 4"x2¼"
BP061	5	6.35mm Mono jack plugs
BP063	5	6.35mm stereo switched jack sockets
BP064	12	Coax chassis mount sockets
BP065	1	3mtr Euro-mains lead with chassis socket

MULTIBAND RADIO

VHF 54-176 MHz + AM CB BANDS 1-80

Listen to: AIR TRAFFIC CONTROL,

AIRCRAFT, RADAR

PUBLIC UTILITIES

RADIO AMATEURS AND

MANY MANY MORE

£17.95

POSTAGE

£2.85

SQUELCH CONTROL

"RUBBER DUCK AERIAL"

HAND HELD WALKIE TALKIES

Ideal for sports or any outdoor activities. Built-in call button and separate volume control. Range 1.2km maximum. 49MHz crystal control superhet circuit with built-in condenser mic. and speaker. Unit supplied with vinyl carrying case and personal earphone.

£32.90 a pair

+ £2.60 P&P

RADIO AND TV COMPONENTS ACTON LTD

21 HIGH STREET, ACTON, LONDON W3 6NG

MAIL ORDER TERMS, POSTAL ORDERS and/or CHEQUES with orders.

Orders under £20 add £3.00 service charge. Nett monthly accounts to Schools, Colleges and P.L.C. only. ACCESS VISA. Phone orders between


9.30 & 12pm please. Overseas readers write for quote on delivery.

Phone: 071-723 8432 or 081-992 8430

Callers 323 Edgware Road, London W2. Closed Sun.

21 High St., Acton, London W3 closed Sun, Mon & Wed

30+30 WATT AMPLIFIER KIT

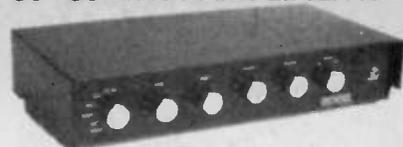

An easy to build amplifier with a good specification. All the components are mounted on the single P.C.B. which is already punched and backprinted.

■ 30W x 2 (DIN 4 ohm)

■ CD/Aux, tape I, tape II, tuner and phono inputs.

■ Separate treble and bass

■ Headphone jack
Size (H.W.D.) 75x400x195mm
Kit enclosed: case, P.C.B., all components, scale and knobs £36.80. post £3.50
(Featured project in *Everyday Electronics* April 1989 issue). Reprint Free with kit.

AMPHONIC 125 + 125 POWER AMPLIFIER



125 watt per channel stereo power amplifier with independent volume controls, professional 19" rack mount and silent running cooling fan for extra reliability.

Output power 125W RMS max. per channel

Output impedance 4 to 16 ohms
(max. power into 4 ohms)

Sensitivity 450V at 22K ohms

Protection Electronic short-circuit and fuses

Power 220-240V a.c. 50Hz

Chassis dim 435x125x280mm

£142 + £7.00 p&p

STEREO MIXER



5-channel stereo disco mixer in racking case which can handle up to a total of 10 phono, line and mic inputs, switchable on front panel. Twin 5-band graphic equalizer with insert/bypass switch. Cross fader between channels 1 and 2. Mic channel with low cut filter and talkover switch. Separate L and R master controls. Output for amp, tape and headphones.

Input Mic 0.3mV 600 ohms

Phono 2.5mV 50K ohms

Outputs: Amp & Tape 1.2V

Headphone 50mV @ 75 ohms

Equalizer control frequencies 60, 250, 1k, 3.5k, 12kHz

Equalizer control range ±12dB boost or cut

Size 350 x 280 x 90mm

£118.90 + £5.80 P&P

BELT-DRIVE QUICKSTART VARISPEED DISCO TURNTABLE

★ Quick start Ideal for scratching

★ Pitch control

★ Pop-up target lamp

★ Strobe lamp

★ Counterweighted tubular tone arm with plug-in headshell

★ Full manual control

★ Remote start/stop

★ 7.5kg



£112.00

+ £7.00 P&P

28.0.28V 4 AMP MAINS TRANSFORMERS

With a 5.5V at 0.5A mains input 110-240. Size 90 x 105 x 75 fitted with copper screening band; made for famous HIFI Co. £6.50 each. Postage £2.80. It's weight is 2.7Kg! Brand new and unused condition.

PRESSURE PAD ALARM



Protect your valuables with this portable anti-theft system. This burglar alarm emits a loud tone when an intruder steps on a pressure pad placed under a window or other likely points of entry. The system is portable with self-contained batteries so could be found useful in many temporary or semi-permanent security applications such as for garden sheds or boats. It can operate a wide variety of 12V audible warning devices including high-powered sirens of up to 3A rating. The pad may be situated any reasonable distance from the main unit – if the interconnecting wire is cut or the plug pulled out, the alarm will sound.

SIMPLE METRONOME

A "flash" and a "tick" for musicians. A linear control with excellent stability from a simple oscillator circuit. Variable from 40 to 200 beats per minute.



GAS RESERVE INDICATOR

Make sure your camping gas supply does not let you down. The gas supply in a caravan is vital to maintain the refrigerator and cooking facilities. Failure is always inconvenient and can be disastrous where no back-up supply is available. Motor caravanners – due to shortage of space – often carry only one small (6lb) butane cylinder. This device will therefore be of particular interest to them. The indicator displays cylinder contents on a five-point scale – thermometer fashion – using a row of l.e.d's.

CHOOSING AND USING TEST EQUIPMENT

POWER SUPPLIES • LOGIC PROBES • DIGITAL FREQUENCY METERS
• R.F. GENERATORS • A.F. GENERATORS • SIGNAL TRACERS
• MILLIVOLTMETERS • COMPONENT TESTERS

EVERYDAY ELECTRONICS

AUGUST ISSUE ON SALE FRIDAY 6 JULY 1990

TRANSISTORS

AA932	9p
AC107	40p
AC125	25p
AC126	25p
AC127	21p
AC128	21p
AC128K	21p
AC141K	30p
AC142K	30p
AC176	22p
AC176K	28p
AC187	21p
AC187K	28p
AC188	21p
AC188K	28p
AC193	48p
AC193K	48p
AD149	60p
AF124	50p
AF125	50p
AF126	50p
AF127	50p
AF139	30p
AF238	30p
AF379	45p
BA145	10p
BA148	10p
BA154	6p
BA157	12p
BB105B	18p
BB205B	24p
BC107	8p
BC108	8p
BC109	8p
BC109C	10p
BC118	10p
BC118	11p
BC140	20p
BC141	20p
BC142	20p
BC143	20p
BC147	8p
BC148	8p
BC149	8p
BC157	8p
BC159	8p
BC160	30p
BC171	10p
BC172	10p
BC177	14p
BC178	14p
BC179	14p
BC182	14p
BC182L	14p
BC183	7p
BC183L	7p
BC184	7p
BC184L	7p
BC212	7p
BC212L	7p
BC213	7p
BC213L	7p
BC214	7p
BC214L	7p
BC237	7p
BC238	7p
BC239	7p
BC300	20p
BC301	20p
BC302	20p
BC303	20p
BC304	25p
BC308	25p
BC327	7p
BC328	7p
BC337	7p
BC338	7p
BC441	28p
BC446	15p
BC449	15p
BC461	28p
BC477	18p
BC478	18p
BC479	18p
BC489	18p
BC490	18p
BC516	22p
BC528	22p
BC537	25p
BC546	8p
BC547	8p
BC548	8p
BC549	8p
BC550	8p
BC556	8p
BC557	7p
BC558	8p
BC559	8p
BC560	8p
BC637	20p
BC638	20p
BC639	20p
BC640	20p
BCY32	200p
BCY33	200p
BCY34	200p
BCY70	16p
BCY71	16p
BCY72	16p
BD115	30p
BD124P	50p
BD124	110p
BD131	25p
BD132	25p
BD133	25p
BD135	20p
BD136	20p
BD137	20p
BD138	20p
BD140	20p
BD142	45p
BD150	30p
BD157	38p
BD158	38p
BD175	30p
BD177	30p
BD179	32p
BD181	45p
BD182	60p
BD187	60p
BD201	33p
BD202	38p
BD203	42p
BD204	42p
BD222	31p
BD225	31p
BD232	31p
BD233	32p
BD234	32p
BD235	32p

BD236	30p
BD237	21p
BD238	24p
BD239	30p
BD240	40p
BD241A	40p
BD243A	50p
BD244	50p
BD245	50p
BD246	50p
BD265	45p
BD267	45p
BD269	45p
BD278	50p
BD311	100p
BD312	100p
BD313	100p
BD314	100p
BD315	150p
BD316	150p
BD317	150p
BD318	150p
BD331	40p
BD332	40p
BD361	60p
BD362	60p
BD370	30p
BD371	30p
BD410	50p
BD433	28p
BD435	31p
BD436	30p
BD437	28p
BD438	36p
BD439	40p
BD440	40p
BD441	40p
BD442	40p
BD520	60p
BD533	60p
BD534	38p
BD535	38p
BD536	38p
BD537	40p
BD538	40p
BD643	50p
BD645	50p
BD647	50p
BD649	50p
BD651	40p
BD675	40p
BD676	40p
BD677	38p
BD678	40p
BD680	40p
BD681	45p
BD682	45p
BD705	50p
BD707	50p
BD711	50p
BD736	85p
BD826	50p
BD828	50p
BD875	50p
BD897	50p
BD899	50p
BD901	50p
BD977	50p
BDX32	100p
BDX33	60p
BDX34	60p
BDX53	60p
BDX65	60p
BDW23	55p
BDW24	55p
BDW93	50p
BDW94	60p
BDY20	100p
BDY92	100p
BF137	35p
BF154	30p
BF167	30p
BF173	40p
BF178	30p
BF180	16p
BF181	18p
BF183	20p
BF194	7p
BF195	7p
BF196	8p
BF197	10p
BF198	10p
BF199	10p
BF200	16p
BF225	30p
BF240	16p
BF245	25p
BF255	25p
BF256	18p
BF257	18p
BF258	18p
BF259	18p
BF262	25p
BF270	18p
BF273	15p
BF311	21p
BF324	25p
BF336	20p
BF337	20p
BF338	20p
BF355	28p
BF362	30p
BF367	13p
BF371	17p
BF392	18p
BF420	16p
BF421	18p
BF422	21p
BF423	25p
BF450	20p
BF455	14p
BF458	19p
BF459	19p
BF481	60p
BF482	62p
BF469	30p
BF470	28p
BF471	28p
BF472	28p
BF473	28p
BF493	115p
BF494	16p
BF495	16p
BF506	25p
BF595	16p
BF596	16p
BF815	30p
BF817	30p
BF818	30p
BF819	30p
BF1000	30p

MP8512	50p
MP8513	50p
MP8514	50p
MP8601	50p
MP8602	50p</

GRAND NATIONAL



Complete set of parts for this months project!

- (a) Battery version inc. case £8.95
- (b) Mains version inc. case £27.95

SONY

DISKS AT UNBEATABLE PRICES!

5 1/4" DS DD	10	£6.20	100	£55.00
5 1/4" DS HD	10	£11.20	100	£99.00
3 1/2" DS DD	10	£9.30	100	£83.00
3 1/2" DS HD	10	£19.30	100	£171.00

VIDEO TAPES

We've sold many thousands of these top quality tapes to satisfied customers!

£180 £2.50 each
5 for £10
Box of 40 £69.00

MOTOR + GEAR PACK K579. This pack contains 10 assorted battery powered motors (mostly 3V) + 90 gears etc, 16-60mm dia + worms and shafts. Amazing value at just £7.95

KEYBOARDS



Z8852 Keyboard: Superb brand new keyboard 392 x 181 with LCD displaying 1 line of 10 characters and a further line with various symbols. 100 keys, inc. separate numeric keypad. Chips on board are 2 x 74HC05, 80C48. LCD + driver chips are easily removable from board. £15.00

Z8857 High quality Alphanumeric keyboard on aluminium frame 314 x 150mm. Contactless keys good for 20 million operations. Originally sold at over £100 each, they were used in a 'Printcom' portable terminal. Fully ASCII encoded output. Power supply +5V and -12V @ 35mA. Supplied with comprehensive data. £14.95

Z8856 Cherry computer keyboard. Very slim model 340 x 130 by only 14mm deep, including keys. Matrix output. 67 keys in pale/dark brown. £4.00

Z8863 Keyboard. High quality unit made by Micro Switch. 69 pale grey and blue keys. 6 red 5mm LED's. 15 various LS chips and socketed DB048 by Intel. Output via 7 way plug and there is a 4 way edge connector too. Keyboard frame is 317 x 128mm. PCB on which it's mounted is 285 x 170mm. Price..... Excellent value at £12.00

DISPLAYS

Z4243 Display panel 152 x 112mm with NEC 8 digit display (Z1731); 8279-5, MC146818, 3 x uPA80C, & a couple of LS chips, crystal, etc. £2.90

Z1731 NEC Vacuum Fluorescent Display FIPBBII. 8 digit multiplexed output 10mm high. Heater voltage 2V. grid/anode voltage 24V. £2.00

Z4115 8 digit 12.7mm high LCD and holder. These are 14 segment devices allowing alphanumeric display. Normally costing over £15.00 we are offering these for just £4.50

Z4148 LCD as Z4115 but 6 digit, 50 pins. Like RS 588-601. Their price 10.86. £3.00

Z1732 Epson LCD 4 digit 8mm high. £2.00

Z1637 LCD Display - Direct drive 3 1/2 digit similar to RS 588-572. 12.7mm high digits. Op voltage 4-12 RMS @ 32Hz typ. Supplied with data. £2.00; 10+ / £1.75; 25+ / £1.50; 100+ / £1.00

Z1560 7 seg display, 20mm high. Common anode. Only 70p! 25+ / 50p; 100+ / 42p

DL1416 Alphanumeric 4 character intelligent display 0.16" £7.00

DL3416 4 digit intelligent alphanumeric display with built-in drive and memory. ASCII ROM and multiplexing circuitry. TTL compatible inputs. +5V. Supplied with data. List price £41.50. £8.00

1990 CATALOGUE

128 PAGES OF ELECTRONIC COMPONENTS AND EQUIPMENT. HUGE RANGE! AMAZING VALUE! DON'T MISS OUT - GET YOUR COPY NOW - ONLY £1.50 POST FREE!!!

HIGH QUALITY TEST EQUIPMENT

HITACHI OSCILLOSCOPES FOR QUALITY AND VALUE



V223 DC-20MHz, dual Channel, single time-base delayed sweep, DC offset, alternate magnifier, 6in screen, 5mV/div vert. sensitivity 0.2µs/div-0.2s/div sweep time. Complete with 2 probes, manual, mains lead. £475
Other models from £339 - full details in catalogue. Ask for colour brochure.

METEX METERS

8 different models in our catalogue!

- ★ 4 1/2 digit 12mm LCD display
- ★ 30 ranges incl 20A ac/dc
- ★ Frequency counter
- ★ Capacitance test with zero adjust
- ★ Data hold switch
- ★ Diode test
- ★ Transistor test
- ★ Continuity test
- ★ Test leads with 4mm plugs
- ★ Rugged yellow case
- ★ Carrying case



M4650

£94.00

Battery and instruction manual included.


AC volts 0-200m-2-20-200-750Vac ±0.5%
DC volts 0-200m-2-20-200-1000Vdc ±0.5%
AC current 0-2m-200m-20Aac ±1.0%
DC current 0-200µ-2m-200m-20Adc ±0.5%
Resist 0-200-2k-20k-200k-2M-20MΩ ±0.15%
Capacitance 0-20p-200n-20µF ±2.0%
Frequency 0-20k-200kHz ±2.0%
Transistor hFE 0-1000 NPN/PPN
Dims 176 x 90 x 36mm

FREQUENCY COUNTER



FC5250 7 digit frequency counter for frequencies between 10Hz and 150MHz. Power on/off, x1/x10 gate time and VHF/HF switches. Inputs via BNC sockets. Supplied complete with instruction manual and test lead. Requires an external 9Vdc nom 200mA power supply. Price..... £65.00

DIGITAL CAPACITANCE METER

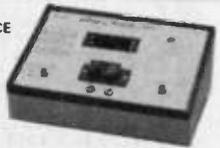

CM3300 High accuracy AUTORANGING 3 digit capacitance meter. High resolution measurement in the range 0.1pF to 99900µF with 10 auto ranges. Range hold switch for batch testing capacitors. Range zero control. Inputs via spring terminals or test leads (supplied). Complete with leads and instruction manual. Price..... £65.00

AF GENERATOR/COUNTER



AG2603AD A combined audio frequency signal generator and frequency counter. A six character LED display allows direct reading of internally generated signal or signals from an external source. The frequency generator has a range of 10Hz to 1MHz with either square or sine waveforms and adjustable output level. The frequency counter has a range of 10Hz to 150MHz. Frequency range controlled by a 5-step selector and fine control. Adjustable output level with 0/20/40dB attenuator.

AUDIO GENERATOR
Frequency range..... 10Hz to 1MHz
Output impedance..... 600Ω unbalanced
Output control..... 0-20-40dB and fine adjuster
Output control:
Sine..... 8V rms max
square..... 10V p-p max

FREQUENCY COUNTER
Frequency range..... 10Hz to 150MHz
Input voltage..... Less than 50mV
Max input voltage..... 3V
Input impedance:
High frequency..... 1MHz
VHF..... 50Ω
Power..... 240Vac 50Hz
Dims..... 215 x 150 x 200mm
Price..... £175.00

RF GENERATOR/COUNTER

Similar in appearance to above with same frequency counter. Spec:

Frequency range..... 100kHz to 150MHz
RF Output..... 100mV rms (up to 35MHz)
Output control..... 0/20dB and fine adj.
Modulation..... Internal 1kHz,
external 50kHz-20kHz
at less than 1V rms
Price..... £179.00


AMSTRAD SPEECH SYNTHESISER

As featured in the May issue!

All components inc. PCB, edge conn., etc., for just £10.95!

+ FREE! An extra SP0256 chip with every kit!!
Suitable Case £3.00
SP0256 Speech Chip £2.50

SIGNAL TRACER/INJECTOR

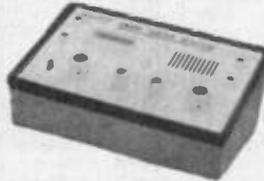

Y133 For fault finding on Audio & RF Equip. VU meter and speaker. Level controls, 0-60dB atten. switch. I/P, O/P, ext spkr, and injector skts on Front panel. Size 200x140x96mm. Uses PP3..... £55.00

GREENWELD ELECTRONIC COMPONENTS

All prices include VAT; P&P £2.00 per order. Min Credit Card £5. No CWO min. Official Orders from Education welcome & min invoice charge £10.00.

Payment is accepted by cheque, postal order, cash inc. foreign currency bank notes/book tokens/Access/Visa/Connect. Our stores have enormous stocks of components and our trade counter is open from 9-5.30 from Mon-Sat. Come and see us!

PLEASE NOTE OUR NEW ADDRESS. PHONE & FAX NUMBERS: Tel: (0703) 236363 (4 lines) Fax: (0703) 236307 EMail: MAG36026 Telex: 9312131093 (GWG)

27D PARK ROAD, SOUTHAMPTON, SO1 3TB.



MSDOS PACK 74305 Epson PCe disk pack


- Contents:
- 1) 364 page MSDOS 3.20 reference manual showing all commands, etc.
 - 2) 100 page book "Everyday with MS-DOS" - an excellent introduction, starting from basics.
 - 3) 95 page book "Setting up and getting started".
 - 4) 61 page book "Diagnostics Users Guide".
 - 5) Pack of 3 5.25" disks - 2 MSDOS 3.20 system/utilities disks and a system dependent utilities disk.

All books are spiral bound. Everything brand new in original carton.

Cost new £55. Our price **£10.00**

POWER SUPPLIES

(a) SWITCH MODE

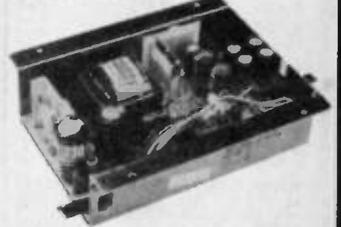

ASTEC Model AA12531
I/P: 115/230V ac 50/60Hz O/P: V1 + 5V 5A; V2 + 12V 0.15A. Size: 160 x 104 x 45mm. Partially enclosed panel with fixing holes in steel case on 120 x 125mm centres. Inputs and Outputs are on colour coded leads; there is also an EEC socket on a flying lead. £6.95

Z660 Astec switched mode PSU Type AA7271.

This small PCB, just 50 x 50mm will accept 8-24V input and give a stable 5V DC at up to 2A output. The 6 transistor circuit provides current overload protection, thermal cut-out and excellent filtering. Offered at the remarkably low price of just..... £5.00

(b) CONVENTIONAL

Z4215 Siliconix mains input, 4.5V DC 150mA output to 3.5mm jack plug on 2m lead. Built-in continental 2-plug. Size 62 x 46 x 35mm £1.50

Z4170 Plug In power supply. Built in 13A plug. Output 6V DC 300mA on 2m long lead terminated in a 3mm power plug. British made to BS415 £1.50

Z4208 Oriac Power Supply. Moulded plastic case with built in 13A plug. Output 9Vdc at 600mA delivered to 2m lead with 2.5mm power plug..... £3.50

BREADBOARDS

FREE, if requested, with every breadboard sold this month! K574 wire link pack with about 250 links for use with breadboard or PCB's!

PROTBLOC 1

G708 Protobloc 1 has a total of 400 tie points consisting of two sets of 30 rows of 5 interconnected sockets plus 4 rows of interconnected sockets running alongside, suitable for use as power supply rails. All contact positions are clearly defined on an alphanumeric grid. ABS polymer board mounted on an adhesive foam base. Will accommodate up to three 16 pin devices. An ideal introduction to solderless circuit development systems. Size 80 x 60mm. £2.50

PROTBLOC 2

G711 Protobloc 2 has a total of 840 tie points. Will accommodate up to seven 16 pin devices. Size 172 x 64mm. £3.95

PROTBLOC 2A

G712 As above, but mounted onto a rigid base plate complete with three 4mm terminals for power connections. A mounting bracket which clips into the base is also provided to accept a variety of components including switches and potentiometers, etc. Price..... £6.95

PROJECT BOARD GL24

G724 2 of type G711 mounted onto a rigid baseplate with 3 coloured terminals, for power connections. Overall size 225 x 150mm. Price..... £13.95

PROJECT BOARD GL36

G736 3 of type G711 and an additional strip of 100 tie points mounted onto a rigid base plate with 4 coloured terminals. Overall size 242 x 195mm. Price..... £19.95

PUBLIC ADDRESS AND DISCO EQUIPMENT

YOU PAY TRADE PRICES!



MIXERS

Choose from 25 models ■ Mixers for home use, disco's, public address and studio use ■ From 4 to 16 channels ■ Also 6 and 8 ch midi systems ■ Equalizer mixers MAT60 and many more.

ECHO'S

■ VC1 analogue ■ 6040 stereo amplifier ■ 8040 digital echo ■ Also mini echo's.

DIGITAL DELAY/REVERB

■ 19" rack systems ■ Digital reverb with 63 user programs ■ Digital delay up to infinite repeat ■ Also multi-effects programmable unit.

GRAPHICS

■ 19" rack systems ■ 31 band single channel ■ 2 x 15 band two channel, and 2 x 31 band two channel.

CHASSIS SPEAKERS/ CABINETS



■ PA speakers 5 1/4" to 12" ■ Twin cone from 40 to 100 Watts ■ Various models disco/group speakers 10" to 18" various types ■ Bass speakers ■ Bass mids and mids ■ Also Rexine cabinets 10", 12" & 15" ■ Plus range of cabinet fittings and portable speaker stands and brackets.

PIEZO TWEETERS

■ 10 models stocked from £2.95 to £7.95 ■ Square piezo £4.95.



PUBLIC ADDRESS SPEAKERS

■ For PA and background music system with and without 100 volt line ■ OUTDOOR. Range of weatherproof systems at various power ratings ■ INDOOR. Columns for speech, columns for music ceiling speakers, suspension speakers, corridor speakers, wall speakers, music speakers - various sizes and types.



DECKS

3 models heavy duty top quality with plinth/cover. ■ DLP1 belt drive quick start. ■ DLP2 direct drive system. ■ DLP3 quartz controlled quickstart direct drive.



POWER AMPLIFIERS

■ Power boosters single channel: 100W, 175W and 2kW. 2-ch/stereo: 135 + 135W, 160 + 160 Watt and 1500 + 1500 Watt.

AMPLIFIERS

■ With preamps ■ 240V AC models and 12V DC/240V AC or 24V DC/240V AC ■ From 15 Watts up to 175 Watts ■ Also background music tape amplifiers and paging amplifiers. ■ Plus range of mixer-amplifiers. ■ Choose from 25 models.

MOBILE AMPLIFIERS

■ Range of 12 volt amplifiers up to 100 Watts ■ Also portable megaphones stocked and 12 volt power boosters.

MICROPHONES/ STANDS

■ XLR/Jack etc ■ Mics for disco, public address and Hi-Fi ■ Good quality at low cost ■ Also stands, booms etc. and wireless microphone systems.

OUTDOOR HORNS



■ Various models up to 12" with or without 100 volt line with drivers ■ Also range of horns with choice of drive units. ■ Accessories: Leads ■ Plugs ■ Adaptors ■ Transformers etc, for all PA requirements.

HORN/ CROSSOVERS

■ 100 Watt midrange and tweeter horns ■ Also matching crossovers and filters up to 300 Watts.

CALL IN OR PHONE FOR BEST PRICES
OPEN 6 DAYS A WEEK



HENRY'S AUDIO ELECTRONICS

404 Edgware Road, London W2 1ED

Telephone: 071-724 3564

Fax: 071 724 0322

Sales Office: 071 258 1831


TRADE/EDUCATION/EXPORT SUPPLIED

PA - DISCO
CATALOGUE
WITH
DISCOUNT
VOUCHERS
Ref PA1

Send A4 SAE
(£1.00 UK)
or £2 UK full
products
catalogue



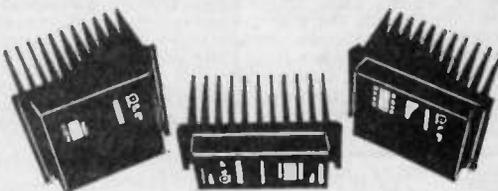The UK Distributor for the complete ILP Audio Range



BIPOLAR AND MOSFET MODULES

The unique range of encapsulated amplifier modules with integral heatsink.

HY30 15W Bipolar amp	£11.50	HY248 120W Bipolar amp (8ohm)	£25.20
HY60 30W Bipolar amp	£11.50	HY364 180W Bipolar amp (4ohm)	£39.25
HY6060 30W Stereo Bipolar amp	£24.45	HY368 180W Bipolar amp (8ohm)	£39.25
HY124 60W Bipolar amp (4ohm)	£19.00	MOS128 60W Mosfet amp	£40.70
HY128 60W Bipolar amp (8ohm)	£19.00	MOS248 120W Mosfet amp	£46.35
HY244 120W Bipolar amp (4ohm)	£25.20	MOS364 180W Mosfet amp	£75.75

PLATE AMPLIFIERS

Bipolar and Mosfet modules with the same electronics as above amplifiers housed in a different extrusion without heatsink.

HY6060P 30W Stereo Bipolar amp.	£20.10	HY364P 180W Bipolar amp (4ohm)	£25.99
HY124P 60W Bipolar amp (4ohm)	£14.85	HY368P 180W Bipolar amp (8ohm)	£25.99
HY128P 60W Bipolar amp (8ohm)	£14.85	MOS128P 60W Mosfet amp	£31.75
HY244P 120W Bipolar amp (4ohm)	£20.10	MOS248P 120W Mosfet amp	£39.95
HY248P 120W Bipolar amp (8ohm)	£20.10	MOS364P 180W Mosfet amp	£66.65

Note: These modules require additional heatsinks

POWER SUPPLIES

Comprising toroidal transformer and DC board to power the ILP amplifier modules.

PSU30 Pre amplifier	£10.80	PSU542 HY248	£27.40
PSU212 1 or 2 HY30	£19.25	PSU552 MOS248	£29.60
PSU412 HY6060, HY124, 1 or 2 HY60	£21.45	PSU712 HY244 (2)	£31.75
PSU422 HY128	£23.70	PSU722 HY248 (2)	£32.80
PSU432 MOS128	£24.75	PSU732 HY364	£32.80
PSU512 HY244, HY128 (2)	£26.35	PSU742 HY368	£34.95
PSU522 HY124 (2)	£26.35	PSU752 MOS364, MOS248 (2)	£34.95
PSU532 MOS128 (2)	£27.40		

PRE-AMP and MIXER MODULES

These encapsulated modules are supplied with in-line connectors but require potentiometers, switches etc.

HY6 Mono pre-amp with bass and treble	£9.30
HY66 Stereo pre-amp with bass and treble	£15.50
HY83 Guitar pre-amp with special effects	£18.95
B6 Mounting board for HY6	£1.15
B66 Mounting board for HY66 or HY83	£1.75

POWER SLAVES

These cased amplifiers are supplied assembled and tested in 60 and 120 watt Bipolar or Mosfet versions.

US12 60 watt Bipolar (4ohm)	£77.50	US32 60 watt Mosfet	£105.95
US22 120 watt Bipolar (4ohm)	£85.95	US42 120 watt Mosfet	£115.95

Prices include VAT and carriage



Quantity prices available on request
Write or phone for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL

Telephone: (0227) 375254 Fax: 0227 365104

HIGHGRADE Summer Sale

LOW PRICES

CHOOSE ANY £100 OF COMPONENTS FROM THIS ADVERT FOR ONLY £48! CHOOSE £300 OF COMPONENTS FOR £98!!!

DISPLAYS

Futaba M40SD02CA 40-character electroluminescent display, with data. All characters are on a 7x5 dot matrix, with a separate cursor or underline. Data gives interface details for six popular ICs, including Z80, 8085 (see IC section), 6809, 8255. Current UK distributor price £95 each. Our price £38! □
Two line LCD module with text and graphics symbols, controlled by D7225 IC. Supplied with data for the controller IC. Our price £6.60! Ten for £54! □
MA1023ZW clock module. Needs only a transformer and time-set switches to make a complete clock. Huge 0.7" digits, 24 hour alarm, snooze control, 59 minute sleep counter, power switch (for adding a radio, tea maker, etc). Supplied with full data and circuits. Our price £4.20! □

BAR GRAPH MODULES with integral driver IC. Ten-LED bar stretches from end to end of the module, so several can be joined to make a bar as long as you like. The modules respond to voltage input: linear, log or VU responses available. With data and circuits.
TSM39146 GGGGGRRRRR Linear £4.80! □
TSM39152 GGGGGGGGGG Log £4.80! □
TSM39153 YYYYYYYYYY Log £4.80! □
TSM39162 GGGGGGGGGG VU £4.80! □
TSM39163 YYYYYYYYYY VU £4.80! □

BAR GRAPH MODULE without drive IC. Eleven-LED bar, green. Our price £1! □

SUPER VALUE

SEVEN-SEGMENT LED DISPLAYS. Three types to meet every need.
0.43" CA single 10 for £2.80! □ 100 for £25! □
0.56" CA dual 10 for £4.80! □ 50 for £22! □
0.50" CC 1½ digit 10 for £3.80! □ 50 for £17! □
If these prices look good, just think: you pay less than half!

INTEGRATED CIRCUITS

8085AC MICROPROCESSOR £2.80! □ 10 for £25! □ 50 for £110! □
8085AC DATA £2.00! □
UDN6128 driver. Allows CMOS to drive relays & other high voltage or current devices. Ten drivers in each IC. With data.
Pack of 4 £1.20! □ 20 for £4.80! □
SAB0600 THREE-TONE CHIME. You've heard them: every supermarket and airport has one! Ideal for PA systems, airport lounges, doorbells. With data & circuit. Our price £1! □ 13 for £10! □
LM3046 TRANSISTOR ARRAY. Five closely matched transistors for the designer who won't take second best. With data. Pack of 4 for £1! □

C912 DISPLAY DRIVER. Has all the drive and multiplexing circuitry for up to six seven-segment LED displays (see displays section). Easy to use. With data & circuit. Our price £1.80! □ 5 for £8! □

OP-AMPS, in TO5 package for the designer who insists on good screening.
301 General purpose op-amp. With data & circuits. 6 for £1! □
101 Military grade version of 301. With data & circuits. 4 for £1! □
308 Precision, low error op-amp. With data and circuits. 2 for £1! □

TEA5570 RADIO IC. Forget the cheap 'n' nasty TRF ICs. This one's the real thing. A full superhet circuit for LW, MW, SW, and the basis for VHF too. With data & circuits. Our price £2.20! □
Ceramic filters for TEA5570, pack of 2 for £1!

MC14412VP MODEM IC. FSK MODEM, compatible with CCITT and USA standards. £2! □
10 for £15! □

BIG SAVINGS

PASSIVES

TOP QUALITY CERMET PRESETS:
100R vertical, 100 for £5! □ 100R horizontal, 100 for £5! □
100k vertical, 100 for £5! □ 47k horizontal, 100 for £5! □
2MΩ vertical, 100 for £5! □ 250k horizontal, 100 for £5! □
BOX POLYESTER CAPS
4n7 400V 200 for £6! □ 470n 63V 100 for £7! □
10n 250V 200 for £6! □ 630n 250V 100 for £7! □
22n 100V 200 for £6! □ 1u0 250V 100 for £8! □
47n 100V 200 for £6! □ 2u2 63V 100 for £12! □
68n 200 for £6! □ 6u8 63V 100 for £12! □
100n 250V 100 for £4! □ 6u8 100V 100 for £35! □
220n 400V 100 for £4! □ 22n Class X2 mains suppression caps, 60 for £5! □

SAVE THE BEST FOR LAST

CB CONVERTER. Plug into your car radio for a ten-ten, why don't you! £4.80! □
MICROPHONES. Dynamic, cassette recorder type, with on-off switch. £1! □
LEVER-OP MICRO SWITCH, Bonnell. 100 for £8! □
DIL SWITCHES, and lots of them.
20 assorted for £6! □ 100 for £25! □
SCARABS. STC's high power DC-DC converters. worth having just to admire the internal circuit: tiny surface-mount ICs, microscopic coils and inductors—it's a joy to behold. Input can be anything from 35V to 63V. STC price £60+.
Scrab 1: Single +5V output at 6A. £3.60! □
Scrab 2: Outputs 5V @ 4WA, 12V @ 1A. £4.20! □
KEYBOARD 1: Full QWERTY keyboard, numeric pad, function keys. £12! □
KEYBOARD 2: Low profile keys, QWERTY, numeric and functions. £12! □
SOLENOID 1: 24V DC, strong pull. A good one for beginners. £1.40! □
SOLENOID 2: 50V AC, this one will have your fingers off soon as look at you. Build yourself a rotweiler. £3.80! □
TUNING CAP: Air spaced, 50pF. £1.60! □
TRIMMER CAP: 2 to 5pF. For anyone needing that last 10p to make £100 on the nose, this is the item for you. 10p! □

OPTO DEVICES

VISIBLE LEDs. Top quality 5mm red LEDs. Our price 100 for £4.80!
INFRA-RED SOURCES AND SENSORS. Professional grade IR components.
TMT1288 880nm emitter, 3mm unfocussed. Pack of 3 £1! □ 50 for £12! □
TMT55 940nm emitter, focussed narrow beam. Pack of 2 £1.20! □
TMT880 880nm emitter, 5mm 24°, medium angle. Pack of 3 £1! □ 50 for £12! □
TMT940 940nm emitter, 5mm 24°, medium angle. Pack of 3 £1! □ 50 for £12! □
TMT941 940nm emitter, 5mm 50°, wide beam. Pack of 3 £1! □ 50 for £12! □
TDET800 Receiver for all emitters. Pack of 2 £1! □
Opto data pack—covers I.R. components, 7-seg displays, opto switches, and more. £1! □

CONNECTORS

DIN41612, 3-row body, 96-way plus and socket for £1.40! □
DIN41612, 3-row, 32-way plug and socket for £1.00! □
DIN41612, 2-row body, 32-way plus and socket for £1.00! □
DIN AUDIO, 5-way 180° chassis socket, single hole mtg. 8 for £1! □ 100 for £10! □
DIN SPEAKER SOCKET, 10 for £1! □ 100 for £8! □
MOLEX ASSORTMENT: a selection of Molex connectors at 100 for £5! □
'D' CONNECTORS, 25-way PCB socket, 6 for £4! □
'D' CONNECTORS, 15-way PCB sockets, 8 for £4! □
'D' CONNECTORS, 9-way PCB plug, 8 for £4! □
'D' CONNECTORS, 25-way straight plug, 6 for £4! □
BNC CONNECTORS, Greenpar, 75R panel sockets, 6 for £4! □
IEC MAINS LEADS with moulded three-pin plug, 6ft lead, IEC socket. £1.40! □
IEC CHASSIS PLUG. Mains inlet, to mate with IEC lead. 2 for £1! □
IEC CHASSIS SOCKET. Mains outlet. 2 for £1! □

FUN TIME

Take a few minutes rest and build yourself a project! BURGLAR ALARM to scare off the baddies. Lots of features. £12.80! □
SOUND SWITCH and camera trigger. Little fishes. £6.90! □
POCKET GAMBLING MACHINE. Pretty naff, but what the hell? £5.90! □
MAINS SWITCH. Put your CMOS circuits in charge of the mains. £6.20! □

VOLTAGE REGULATORS ICs.

79L05 5V 100mA regulator, 5 for £1! □
78L08 8V 100mA regulator IC, 5 for £1! □
LM337LZ ADJUSTABLE 1.2V to 37V 100mA regulator, 3 for £1! □
LM337HV ADJUSTABLE 1.2V to 47V 1.5A regulator, 2 for £1! □
LM342 18V 250mA regulator IC, 3 for £1! □

OTHER SEMICONDUCTORS

BAW62 High speed logic & switching diode 100 for £4! □
M1044 High current rectifier: 6A, 200V. 100 for £7! □
1N5821 Schottky high speed rectifier, 3A, 30V. 20 for £7! □
BZT03 Q10: 10V, 1.3W zener 200 for £7! □
ZTX450 NPN general purpose transistor. 100 for £7! □
ZTX550 PNP general purpose transistor. 100 for £9! □
Transistor Lab Pack, all types. 100 for £5! □
J201 N-channel JFET amplifier. 100 for £6! □
JFET Lab Pack, nice selection. 100 for £5! □
BD681 NPN power Darlingon, 40W, 4A. 20 for £8! □
MV2110 Tuning diode. 30pF @ 4V. 2.5:1 range. 5 for £6! □

Semiconductor data pack—covers these and many hundreds of others. £1! □

ACCESS or VISA VISA orders:
TEL. 0600 3715

Offer ends July 31st 1990

To Highgrade Components Ltd, Unit 11, 8 Woburn Road, Eastville, Bristol BS5 6TT
Please send £100 + VAT worth of components for £48 + £2 postage + VAT = £57.50
 £300 + VAT worth of components for £98 + £2 postage + VAT = £115.00
Overseas orders: do not add VAT. Europe add £5 postage. Outside Europe add £6 surface
I enclose cheque/postal order for £.....
I authorise you to debit my ACCESS or VISA card number
Expiry date: / /
Name: / /
Address: / /
Signed: / /

MAGENTA ELECTRONICS LTD

MAIL ORDER AND SHOP:
EE90 135 Hunter Street,
Burton-on-Trent,
Staffs. DE14 2ST
Tel: 0283 65435
Fax: 0283 46932



All prices include VAT
Shop open 9-5 Mon-Fri;
9-2 Saturday
Official orders welcome

Add £2
p&p to
all orders

SUPERHET BROADCAST RECEIVER


EE MAR '90

At last, an easy to build SUPERHET A.M. radio kit. Covers Long and medium Wave bands. built in loudspeaker with 1 watt output. Excellent sensitivity and selectivity provided by ceramic I.F. filter. Simple alignment and tuning without special equipment. Kit available less case, or with pre-cut and drilled transparent plastic panels and dial for a striking see-through effect.

£16.79

KIT REF 835

D.C. MOTOR GEARBOXES

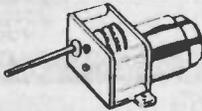

Ideal for Robots and Buggies. A miniature plastic reduction gearbox coupled with a 1.5-4.5 Volt mini motor. Variable gearbox reduction ratios are obtained by fitting from 1 to 6 gearwheels (supplied). Two types available:

SMALL UNIT TYPE MGS £3.99

Speed range 3-2200 rpm. Size 37x43x25mm

LARGE UNIT TYPE MGL £4.55

Speed range 2-1150 rpm. Size 57x43x29mm

**Supplying Electronics
for Education,
Robotics, Music,
Computing and much,
much more!**

Send NOW for our
illustrated
CATALOGUE
Only £1.00!

STEPPING MOTORS

A range of top quality stepping motors suitable for driving a wide range of mechanisms under computer control using simple interfacing techniques.

ID35 PERMANENT MAGNET MOTOR — 48 steps per rev. £16.50

MD200 HYBRID MOTOR — 200 steps per rev. £16.80

MD35 1/4 PERMANENT MAGNET MOTOR — 48 steps per rev. £12.70

MD38 PERMANENT MAGNET MOTOR — 48 steps per rev. £8.95

HAMEG HM 203-6 OSCILLOSCOPE

Special Summer discount price (this is a 10% reduction on the normal retail price). Full two year warranty.
20MHz · 2 channels · 2mV sensitivity
Easy to operate and high performance **£282.60**
+ **£42.39 VAT**

EDUCATIONAL BOOKS & BOOK PROJECTS

ADVENTURES WITH ELECTRONICS

The classic Easy to Follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-DEC breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-DEC breadboard and all the components for the series.

ADVENTURES WITH ELECTRONICS £5.25
COMPONENT PACK (less book) £23.49

FUN WITH ELECTRONICS

From the USBORNE Pocket Scientist series — An enjoyable introduction to electronics. Full of very clear full colour pictures accompanied by easy to follow text. Ideal for all beginners — children and adults. Only basic tools are needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification & how they work). Also full details of how to build 6 projects — burglar alarm, radio, game, etc. Requires soldering — 4 pages clearly show you how.

The components supplied in our pack allows all the projects to be built and kept. The book is available separately.

FUN WITH ELECTRONICS Book £2.50
COMPONENT PACK (less book) £18.45

30 SOLDERLESS BREADBOARD PROJECTS

A book of projects by R. A. Penfold covering a wide range of interests. All projects are built on a Verobloc breadboard. Full layout drawings and component identification diagrams enable the projects to be built by beginners. Each circuit can be dismantled and rebuilt several times using the same components. The component pack allows all projects in the book to be built one at a time. Projects covered include amplifiers, light actuated switches, timers, metronome, touch switch, sound activated switch, moisture detector, M.W. Radio, Fuzz unit, etc.

30 SOLDERLESS BREADBOARD PROJECTS Book 1 £2.95
COMPONENT PACK £28.50

ENJOYING ELECTRONICS

A more advanced book which introduces some arithmetic and calculations to electronic circuits. 48 chapters covering elements of electronics such as current, transistor switches, flip-flops, oscillators, charge, pulses, etc. An excellent follow-up to Teach-in or any other of our series. Extremely well explained by Owen Bishop who has written many excellent beginners' articles in numerous electronics magazines.

ENJOYING ELECTRONICS Book £3.60
COMPONENT PACK £15.05

Note — A simple multimeter is needed to fully follow this book. The M102 BZ is ideal. **£13.98**

A FIRST ELECTRONICS COURSE

A copiously illustrated book that explains the principles of electronics by relating them to everyday objects. At the end of each chapter a set of questions and word puzzles allow progress to be checked in an entertaining way. An S-DEC breadboard is used for this series — soldering is not required.

A FIRST ELECTRONIC COURSE BOOK £3.75
PACK £23.47

EVERYDAY ELECTRONICS KIT PROJECTS

ALL KITS HERE HAVE BEEN FEATURED IN EE. IF YOU DO NOT HAVE THE MAGAZINE WITH THE ORIGINAL ARTICLE, YOU WILL NEED TO ORDER THE REPRINT FOR 80p EXTRA. REPRINTS ALSO AVAILABLE SEPARATELY. KITS INCLUDE CASES, PCB'S HARDWARE AND ALL COMPONENTS (UNLESS STATED OTHERWISE) CASES ARE NOT DRILLED, LABELS ARE NOT SUPPLIED.

Ref	Price	Ref	Price
835	SUPERHET BROADCAST RECEIVER Mar 90	542	PERSONAL RADIO June 86
	With drilled panels and dial		£12.89
	Without above	528	PA AMPLIFIER May 86
	£16.79		£29.95
834	QUICK CAP TESTER Feb 90	523	STEREO REVERB Apr 86
	£10.17		£29.57
833	EE 4 CHANNEL LIGHT CHASER Jan 90	513	BBC MIDI INTERFACE Mar 86
	£31.45		£31.25
815	EE TREASURE HUNTER Aug 89	512	MAINS TESTER & FUSE FINDER Mar 86
	Full Kit £41.95		£9.86
814	BAT DETECTOR June 89	497	MUSICAL DOOR BELL Jan 86
	£20.98		£20.95
812	ULTRASONIC PET SCARER May 89	493	DIGITAL CAPACITANCE METER Dec 85
	£14.49		£46.46
800	SPECTRUM EPROM PROGRAMMER Dec 88	481	SOLDERING IRON CONTROLLER Oct 85
	£29.95		£6.12
796	SEASHELL SYNTHESISER Nov 88	464	STEPPER MOTOR INTERFACE FOR THE BBC
	£27.94		COMPUTER less case Aug 85
790	EPROM ERASER Oct 88		£9.40
	£27.90		1D35 STEPPER MOTOR EXTRA
769	VARIABLE 25V-2A BENCH POWER SUPPLY		£8.95
	Feb 88		OPTIONAL POWER SUPPLY PARTS
	£55.61		£5.74
763	AUDIO SIGNAL GENERATOR Dec 87	461	CONTINUITY TESTER July 85
	£15.66		£8.93
739	ACCENTED BEAT METRONOME Nov 87	455	ELECTRONIC DOORBELL June 85
	£23.43		£8.45
740	ACOUSTIC PROBE Nov 87 (less bolt & probe)	453	GRAPHIC EQUALISER June 85
	£19.58		£29.98
744	VIDEO CONTROLLER Oct 87	444	INSULATION TESTER Apr 85
	£32.58		£21.89
734	AUTOMATIC PORCH LIGHT Oct 87	392	BBC MICRO AUDIO STORAGE SCOPE
	£19.20		INTERFACE Nov 84
728	PERSONAL STEREO AMP Sep 87		£39.95
	£15.99	387	MAINS CABLE DETECTOR Oct 84
730	BURST-FIRE MAINS CONTROLLER Sep 87		£6.18
	£16.17	386	DRILL SPEED CONTROLLER Oct 84
724	SUPER SOUND ADAPTOR Aug 87		£9.70
	£42.93	362	VARICAP AM RADIO May 84
718	3-BAND 1.6-30MHz RADIO Aug 87		£14.70
	£29.66	337	BIOLOGICAL AMPLIFIER Jan 84
719	BUCCANEER I.B. METAL DETECTOR July 87		£27.00
	Inc coils, and case, less handle and hardware	263	BUZZ OFF Mar 83
	£29.58		£6.35
722	FERMOSTAT July 87	242	INTERCOM no case July 82
	£13.58		£6.36
715	MINI DISCO LIGHTS June 87	240	EGG TIMER June 82
	£14.08		£7.68
707	EQUALIZER (IONISER) May 87	108	IN SITU TRANSISTOR TESTER June 78
	£17.37		£10.53
700	ACTIVE I/R BURGLAR ALARM Mar 87	106	WIRED SOUND EFFECTS GEN Mar 78
	£39.87		£8.76
581	VIDEO GUARD Feb 87	101	ELECTRONIC DICE Mar 77
	£9.39		£7.00
584	SPECTRUM SPEECH SYNTH (no case) Feb 87		
	£23.39		
578	SPECTRUM I/O PORT less case Feb 87		
	£10.55		
569	CAR ALARM Dec 86		
	£13.94		
563	200MHz DIG. FREQUENCY METER Nov 86		
	£69.95		
561	LIGHT RIDER LAPEL BADGE Oct 86		
	£11.40		
560	LIGHT RIDER DISCO VERSION		
	£21.93		
559	LIGHT RIDER 16 LED VERSION		
	£15.25		
556	INFRA-RED BEAM ALARM Sep 86		
	£31.70		
544	TILT ALARM July 86		
	£8.76		

TEACH-IN 1 PROJECTS

591	REGULATOR UNIT & SAFE POWER SUPPLY	£29.95
592	UNIVERSAL LCR BRIDGE	£28.89
593	DIODE/TRANSISTOR TESTER	£21.22
594	AUDIO SIGNAL TRACER	£18.73
595	AUDIO SIGNAL GENERATOR	£29.31
596	R.F. SIGNAL GENERATOR	£27.37
597	FET VOLT METER	£24.02
598	DIGITAL PULSE GENERATOR	£18.65

INSULATION TESTER

EE APRIL 85



A reliable electronic tester which checks insulation resistance of wiring appliances etc., at 500 volts. The unit is battery powered simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. One of our own designs and extremely popular.

KIT REF 444

£21.89

PET SCARER

EE MAY 89

Produces high power ultrasound pulses. L.E.D. flashes to indicate power output and level. Battery powered (9V-12V or via Mains Adaptor).

KIT REF 812

Mains Adaptor £1.98

£14.49



DIGITAL CAPACITANCE METER

EE DEC 85

Simple and accurate (1%) measurement of capacitors from a few pF up to 1,000 µF. Clear 5-digit LED display indicates exact value. Three ranges - pF, nF, and µF. Just connect the capacitor, press the button and read the value.

KIT REF 493

£46.46




3 BAND SHORT WAVE RADIO

EE AUG 87

Covers 1.6-30 MHz in 3 bands using modern miniature coils. Audio output is via a built-in loudspeaker. Advanced design gives excellent stability, sensitivity and selectivity. Simple to build.

KIT REF 718

£29.66

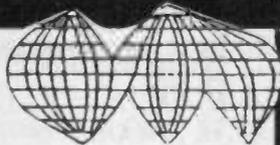

DIGITAL FREQUENCY 200 MHz METER

EE NOV 86

An 8 digit meter reading from AF up to 200 MHz in two ranges. Large 0.5" Red LED display. Ideal for AF and RF measurements. Amateur and C.B. frequencies.

KIT REF 563

£69.95


MOSFET VARIABLE BENCH 25V 2.5A POWER SUPPLY

EE FEB 88

A superb design giving 0.25V and 0-2.5A. Twin panel meters indicate Voltage and Current. Voltage is variable from zero to 25V. A Toroidal transformer MOSFET power output device, and Quad op-amp IC design give excellent performance.

KIT REF 769

£55.61

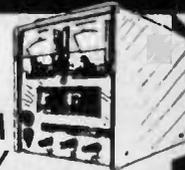

MINI STROBE

EE MAY '86

A hand held stroboscope which uses 6 "ultra bright" LEDs as the light source. Designed to demonstrate the principles of stroboscope examination, the unit is also suitable for measuring the speed of moving shafts etc. The flash rate control covers 170-20,000 RPM in two ranges.

KIT REF 529

£15.50

ACOUSTIC PROBE

EE NOV '87

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers and nosey parkers!

KIT REF 740

£19.58



4 CHANNEL LIGHT CHASER

EE Jan '90

A 1000W per channel chaser with zero volt switching, hard drive, inductive load capability, mic sound sensor and sophisticated 'beat' detector. Chase steps to music or auto when quiet. Variable speed and mic. sens. LED mimic on front panel. Switchable for 3 or 4 channels. P552 output. Ideal for rope lights, pin spots, disco and display lighting.

KIT REF 833

£31.45



EE EQUALISER

EE MAY '87

A mains powered loniser with an output of negative ions that give a refreshing feeling to the surrounding atmosphere. Negligible current consumption and all-insulated construction ensure that the unit is safe and economical in use. Easy to build on a simple PCB.

KIT REF 707

£17.37



MUSICAL DOORBELL

EE JAN '86

This project uses a special I.C. pre-programmed with 25 tunes and 3 chimes. A Magenta design, the circuit is battery powered and only draws current whilst producing sounds. Two rotary switches select the tune required. Provision is made for three bell pushes, each of which sounds a different tune, so that three points of entry can be identified.

KIT REF 497

£20.95

EPROM ERASER

EE OCT '88

Safe low-cost unit capable of erasing up to four EPROM's simultaneously in less than twenty minutes. Operates from a 12V supply. Safety interlock. Convenient and simple to build and use.

KIT REF 790

£27.90



LIGHT RIDERS

EE OCT '86

Three projects under one title - all simulations of the Knight Rider lights from the TV series. The three are a lapel badge using six LEDs, a larger LED unit with 16 LEDs and a mains version capable of driving six main lamps totalling over 500 watts.

KIT REF 559 CHASER LIGHT

£15.25

KIT REF 560 DISCO LIGHTS

£21.93

KIT REF 561 LAPEL BADGE

£11.40

EE TREASURE HUNTER

EE AUG '89

A sensitive pulse induction Metal Detector. Picks up coins and rings etc., up to 20cms deep. Low "ground effect". Can be used with search-head underwater. Easy to use and build, kit includes search-head, handle, case, PCB and all parts as shown.

KIT REF 815

Headphones

£41.95
£1.99



STEPPING MOTOR INTERFACE

EE AUG '85

This interface enables 4 phase unipolar stepping motors to be driven from four output lines of any computer user port. The circuit is especially suitable for the ID35 motor and our MD200 which are commonly used in buggies and robot arms. Supplied complete with ribbon cable and connector for the BBC user port.

KIT REF 464

£9.40


TK FOR KITS

GUARD DOG KIT



One of the best burglar deterrents is a guard dog and this kit provides the barking without the bite! Can be connected to a doorbell, pressure mat or any other intruder detector and produces random threatening barks. Includes mains supply and horn speaker. **XK125** £24.95


DISCO LIGHTING KITS

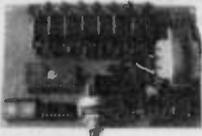

OL8000K 8-way sequencer kit with built-in opto-isolated sound to light input. Only requires a box and control knob to complete ... £39.95
OL1000K 4-way chaser features bi-directional sequence and dimming 1kW per channel ... £23.95
OL21000K Uni-directional version of the above. Zero switching to reduce interference ... £13.95
OLA/1 (for DL & DL21000K) Optional op-to input allowing audio 'beat/light response' ... 95p
OL3000K 3-channel sound to light kit, zero voltage switching, automatic level control and built-in mic. 1kW per channel ... £19.55

POWER STROBE KIT

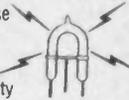Produces an intense light pulse at a variable frequency of 1 to 15Hz. Includes high quality PCB, components, connectors, 5Ws strobe tube and assembly instructions. Supply: 240V ac. Size: 80x50x45. **XK124 STROBOSCOPE KIT.** £17.25




ELECTRONIC WEIGHING SCALE



Kit contains a single chip microprocessor. PCB, displays and all electronics to produce a digital LED readout of weight in Kgs or Sts/Lbs. A PCB link selects the scale-bathroom/two types of kitchen scales. A low cost digital ruler could also be made. **ES1** £8.25

PROGRAMMABLE ELECTRONIC LOCK KIT

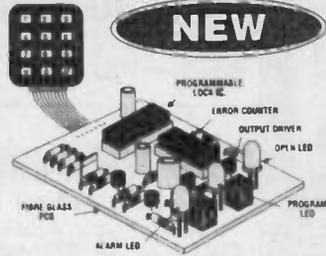

Keys could be a thing of the past with this new high security lock. Secure doors to sheds, garages, even your home or prevent the unauthorised use of computers, burglar alarms or cars. One 4-digit sequence will operate the lock while incorrect entries will sound an alarm. The number of incorrect entries allowed before the alarm is triggered is selected by you. Further entries will be ignored for a time also set by you. Only the correct sequence will open the lock and switch off the alarm. The sequence may easily be changed by entering a special number and code on the supplied keyboard. Kit includes; keyboard, alarm buzzer, high quality PCB and all electronic components. Supply 5-15V DC. Will drive our Latch Mechanism (701 150 @ £18.98) or relay directly. **XK131**


£19.95

SIMPLE KITS FOR BEGINNERS

Especially aimed at the beginner. Have fun with your project even after you have built it and also learn a little from building it. These kits include high quality solder resist printed circuit boards, all electronic components (including speaker where used) and full construction instructions with circuit description.



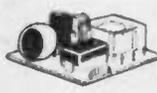SK1 DOOR CHIME plays a tune when activated by a pushbutton £4.50



SK2 WHISTLE SWITCH switches a relay on and off in response to whistle command £4.50



SK3 SOUND GENERATOR produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun £4.50

XK118 TEN EXCITING PROJECTS FOR BEGINNERS this kit contains a solderless breadboard, components and a booklet with instructions to enable the absolute novice to build ten fascinating projects including a light operated switch, intercom, burglar alarm and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section component identification and function is included, enabling the beginner to build the circuits with confidence ... £17.25

SUPER-SENSITIVE MICROBUG



Only 45x25x15mm, including built-in mic. 88-100MHz (standard FM radio). Range approx. 300m depending on terrain. Powered by 9V PP3 (7mA). Ideal for surveillance, baby alarm etc. **XK128** £6.35

NEW

REMOTE CONTROL DIMMER KIT

Imagine controlling the brightness of your lights or switching them on or off from the comfort of your armchair! This kit contains all the components from front panel to the last screw to enable you to do just that and fit the shallowest wall boxes. Max power 300W (not fluorescent). **XK132** £19.95

IR TRANSMITTER KIT

Designed for use with the XK132 and comes complete with a pre-drilled box. A PP3 9 volt battery is required. **MK 6** £4.95




XK136 TOUCH DIMMER KIT £12.95

VERSATILE REMOTE CONTROL SYSTEM

These kits can switch up to 16 pieces of equipment on and off or control 16 functions depending on the keyboard selected for the MK18 transmitter. MK12 receiver has 16 logic outputs and operates from 12 to 24V d.c. or 240V a.c. via the transformer supplied. The MK18 requires a 9V battery and keyboard. Great for controlling lights, TVs, garage doors etc.

MK12 IR Receiver £19.55
MK18 Transmitter £8.95
MK 9 4-way Keyboard £2.75
MK10 18-way Keyboard £7.95
601 133 Box for transmitter £2.95


VOICE RECORD/PLAYBACK KIT

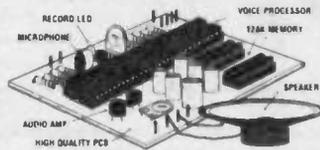

This simple to construct and even simpler to operate kit will record and playback short messages or tunes. It has many uses - seatbelt or light reminder in the car, welcome messages to visitors at home or at work, warning messages in factories and public places. In fact anywhere where a spoken message is announced and which needs to be changed from time to time. Also suitable for toys - why not convert your daughter's £8 doll to an £80 taking doll!!!

Size 76 x 60 x 15mm
 Message time 1-5 secs normal speed, 2-10 secs slow speed
XK129 £25.95

PROPORTIONAL TEMPERATURE CONTROLLER KIT

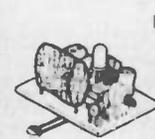

Uses 'burst fire' technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine making, etc.

Maximum load 3kW (240V AC). Temperature range up to 90°C. Size: 7x4x2.5cms. **MK4** £8.95

TK ELECTRONICS

TK ELECTRONICS

13 Boston Road
 London W7 3SJ
 Tel: 081-567 8910
 Fax: 081-566 1916

ORDERING INFORMATION All prices INCLUDE VAT. Free P & P on orders over £60 (UK only), otherwise add £1.15. Overseas Customers divide total order by 1.15 then add P & P: Europe £3.50, elsewhere £10.00. Send cheque/PO/visa/Access No. with order. Giro No. 529314002. Local Authority and educational institutions orders welcome. Shop Open: Tuesday-Thursday 10 am - 5 pm. Saturday 10 am - 4 pm.



ORDERS: 081-567 8910 24 HOURS

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

The Magazine for Electronic & Computer Projects
VOL. 19 No. 7 July '90

Editorial Offices
EVERYDAY ELECTRONICS EDITORIAL,
6 CHURCH STREET, WIMBORNE,
DORSET BH21 1JH
Phone: Wimborne (0202) 881749
FAX: (0202) 841692. DX: Wimborne 45314
See notes on Readers' Enquiries below – we regret
that lengthy technical enquiries cannot be answered over
the telephone

Advertisement Office
EVERYDAY ELECTRONICS ADVERTISEMENTS
HOLLAND WOOD HOUSE, CHURCH LANE,
GREAT HOLLAND, ESSEX CO13 0JS.
Frinton (0255) 850596

UP TO DATE

Although we work on high tech. designs all the time and obviously electronics is our business we have been a little behind the times editorially. By this I mean that our typesetting has been done on rather old equipment. Recently we have come bang up to date with a fantastic new on screen page make-up system.


We now have a "sister" company *The Typesetting Bureau Ltd.*, which specialises in supplying a complete page make-up typesetting software package for just £185 plus VAT. The software provides WYSIWYG (what you see is what you get) page layout with over 200 type fonts, variable in size from 1 to 1000 point, plus output on a 2000 dpi typesetter for £3 per foot (or less). But forget all the jargon – as you can see the quality of the final product is excellent.

All our typesetting needs can now be met by an inexpensive IBM compatible computer and proofed on a simple dot matrix printer. This set up means that for a modest outlay anyone can undertake their own "professional" typesetting and in fact two of our advertisers are already starting to use the system for their promotional material, articles and catalogues.

If you are interested in this product please turn to the "Typefit" advertisement in this issue. Modern technology, and of course some excellent software, is now helping to produce your magazine.

OUT IN FRONT

I am pleased to be able to report that yet again EE is the UK's best selling monthly magazine for the electronics hobbyist. Our latest ABC figures show that we now outsell our nearest competitor by more than 5,000 copies each month. We hope and believe that this excellent trend is because you like what you read in EE and keep coming back for more. As I have said before, we always welcome constructive criticism of EE – so if there is anything you feel we can improve, or any project you would like to see published, just drop us a line – we will do our best to comply.

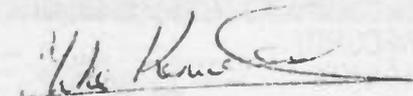

SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £16.00. Overseas: £19.50 (£37 airmail). Cheques or bank drafts (in £ sterling only) payable to Everyday Electronics and sent to EE Subscriptions Dept., 6 Church Street, Wimborne, Dorset

BH21 1JH. Subscriptions can only start with the next available issue. For back numbers see below.

BACK ISSUES

Certain back issues of EVERYDAY ELECTRONICS are available price £1.50 (£2.00 overseas surface mail—£ sterling only please—inclusive of postage and packing per copy. Enquiries with remittance, made payable to Everyday Electronics, should be sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. in the event of non-availability one article can be photostated for the same price. *Normally sent within seven days but please allow 28 days for delivery.* We have sold out of Sept. Oct. & Dec. 85, April, May, Oct. & Dec. 86, Jan., April, May & Nov. 87, Jan., March, April, June & Oct. 88.

BINDERS

Binders to hold one volume (12 issues) are available from the above address for £4.95 (£6.95 to European countries and £9.00 to other countries, surface mail) inclusive of post and packing. *Normally sent within seven days but please allow 28 days for delivery.* Payment in £ sterling only please.

Editor MIKE KENWARD
Secretary PAMELA BROWN
Deputy Editor
DAVID BARRINGTON
Business Manager
DAVID J. LEAVER
Editorial: WIMBORNE (0202) 881749
Advertisement Manager
PETER J. MEW Frinton (0255) 850596.

Classified Advertisements
Wimborne (0202) 881749

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that we cannot provide data or answer queries on projects that are more than five years old.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should address them to the advertiser or should consult a local trading standards office, or a Citizen's Advice Bureau, or a solicitor.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We would like to advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the U.K. Readers should check the law before using any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use. The laws vary from country to country; overseas readers should check local laws.



GRAND NATIONAL GAME

IVAN PATRICK GORE



A grand day at the electronic races!

THIS GAME provides great fun at parties and could be useful as a fund-raiser at school open days and similar events. The original theme was "a day at the races" but the constructor's imagination could turn the basic circuits to many other ideas.

The display consists of pictures or models of four race horses with the odds against them winning clearly displayed. The true odds are 10:1, 5:1, 10:3 and 5:2 but the "bookmaker" will alter these to give an overall profit at the end of the session. For example, they could be marked 8:1, 4:1, 3:1 and 2:1 respectively. On pressing a switch momentarily, the "race" begins and lamps indicating each horse flash rapidly in turn. This continues for several seconds then stops suddenly with just one lamp illuminated - that for the winning horse.

Two versions of the circuit are described. The miniature one is battery-powered and

uses 6V lamps. The alternative system, although using a battery to power the control circuit, operates mains bulbs. This would be more appropriate for village fetes and similar functions where a mains supply is available.

CIRCUIT DESCRIPTION

The two-circuit diagrams for the Grand National Game are shown in Fig. 1. (miniature, battery version) and Fig. 2. (mains version). That part of the circuit up to diodes D2 and D11 is the same for both versions and centres on a CMOS dual integrated circuit timer, IC1, and a CMOS decade counter, IC2.

The first section, IC1a, of IC1 is configured as a monostable and with switch S2 (ON-OFF) switched on, a supply is established from battery, B1. The race is


started by operating push-button switch S1 (THEY'RE OFF!).

Switch S1 has one pair of changeover contacts. The normally-open pair close and make IC1a trigger the input, pin 6, low momentarily. IC1a output, pin 5 then goes high (supply positive voltage) for a preset time then reverts to low.

The time during which the output remains high depends on the values of preset, VR1, fixed resistor, R3 and capacitor, C1. With the values specified this will lie between 5 and 20 seconds approximately depending on VR1 adjustment.

The output from IC1a pin 5 is connected to IC1b reset input, pin 10, and while high allows IC1b and associated components to operate as an astable multivibrator. This then delivers a stream of positive pulses from its output, pin 9, while the race is in progress. When pin 10 reverts to low, IC1b is disabled and the pulses stop. The frequency of the pulses is determined by resistors R4 and R5 in conjunction with capacitors C2 and C3.

Fig. 1. Complete circuit diagram for the miniature battery version of the Grand National Game.

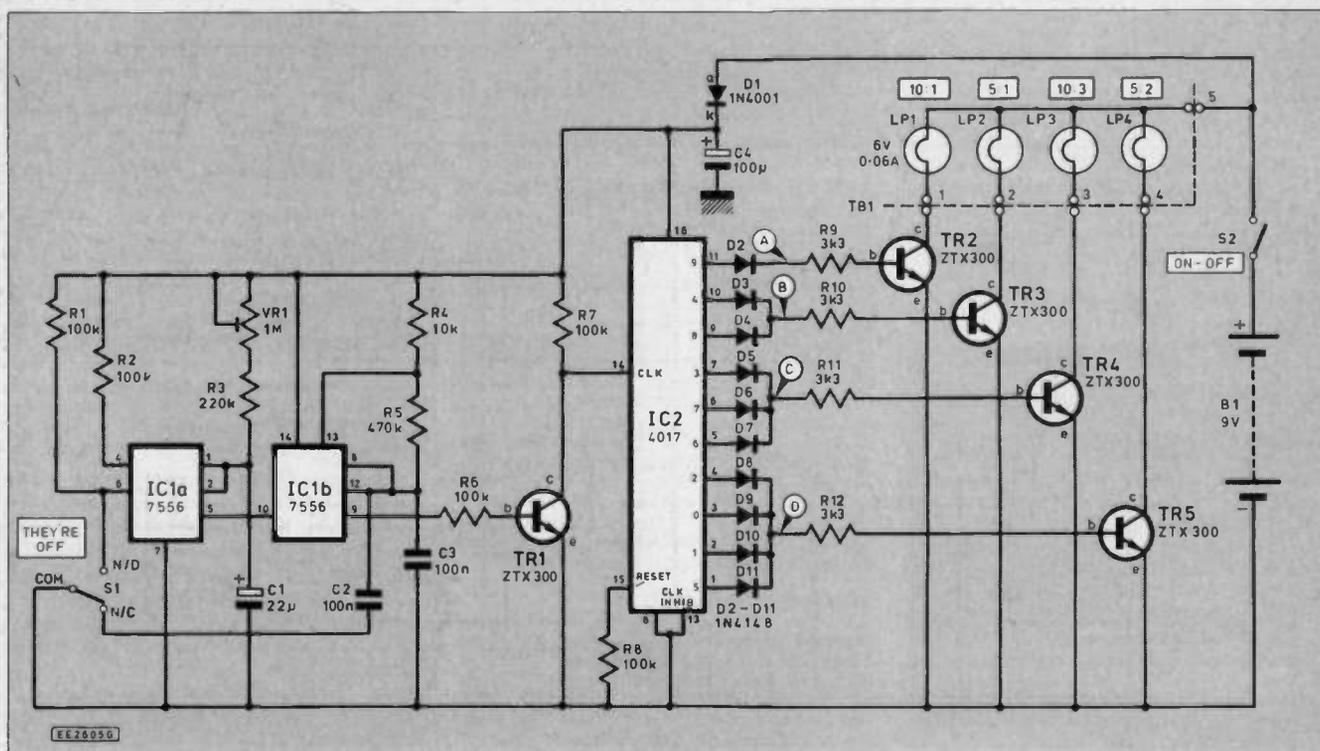

When S1 is released, its normally-closed contacts connect capacitor C2 in parallel with C3 so increasing the capacitance appearing between IC1b pins 8 and 12 and the negative supply line. This reduces the flash repetition frequency.

With the specified component values, pulses will be produced at a rate of 20 per second (20Hz) approximately with S1 pressed and 10Hz when released. The purpose of this will be explained later.

Resistor R2 keeps IC1a reset input (pin 4) normally high. This enables the i.c. ready to receive a trigger pulse. Resistor R1 keeps IC1a trigger input (pin 6) high except while triggering - this prevents false operation due to possible stray pick-up.

COUNTER

Pulses from IC1 pin 9 are applied to transistor TR1 base through resistor, R6, so the collector switches rapidly between high and low states. These are applied to IC2 clock input, pin 14, causing each one of the ten outputs 0 to 9 (pins 3, 2, 4, 7, 10, 1, 5, 6, 9 and 11 respectively) to go high in turn. IC2 then resets to begin a further cycle. This continues until IC1a inhibits IC1b, as previously described, whereupon the clock pulses stop and one output of IC2 will be left high.

There is clearly an equal chance of any particular output being on and this would not make the basis for a successful game. Diodes D2-D11 are therefore used to direct current from various combinations of outputs to the lamps indicating each horse.

Consider point A. This will be high only if pin 11 is high - a 10:1 chance. Point B will be high if either pin 9 or 10 is high - a 5:1 chance. Point C will be high if any of pins 5, 6 or 7 are high and with point D, a high state of any of pins 1, 2, 3 or 4 will make it high. These are 10:3 and 5:2 chances respectively. Of course, the horse which wins a particular race is a matter of chance but odds can be offered which will enable an overall profit to be made.

MINIATURE VERSION

In the miniature circuit of the Grand National Game, Fig. 1, a high state at point A, B, C or D is applied to transistor TR2 to TR5 base as appropriate through current-limiting resistors, R9 to R12.

The collector current then operates the corresponding lamp, LP1 to LP4.

MAINS VERSION

To operate mains lamps, a system of optical-coupling is used (see Fig. 2). This ensures that there is no electrical connection between the battery and high voltage sections of the circuit.

Four optically-coupled triacs, IC3 to IC6 are used for this. Within each of these components is an infra-red l.e.d. and a triac. These two sections are electrically isolated from one another but when the l.e.d. is on, the triac is optically triggered and mains current flows between the main terminals (pins 4 and 6).

Each point A, B, C and D is responsible for one l.e.d. and hence one triac. Only

one l.e.d. current-limiting resistor, R13 is needed since only one l.e.d. is on at a time.

Since the internal triacs cannot supply sufficient current to operate mains lamps of a reasonable power direct, external triacs, CSR1 to CSR4 are used for this purpose. These are triggered when the internal triacs are on by gate current entering through current-limiting resistors R14 to R17 as appropriate.

The external triacs handle sufficient current to operate 60W lamps without the use of heatsinks. In the prototype unit, coloured spotlights, LP5 to LP8, directed onto the horses were used.


RANDOMIZATION

When push switch S1 (THEY'RE OFF!) is operated, IC1a is triggered in the manner already described via the normally-open contacts. At the instant these contacts close, timing of the monostable section begins.

With the release of S1, the normally-closed contacts connect capacitor C2 in parallel with C3 so the frequency of the multivibrator decreases. This introduces a measure of randomization since the time



Fig. 2. Complete circuit diagram for the mains version of the Grand National Game.

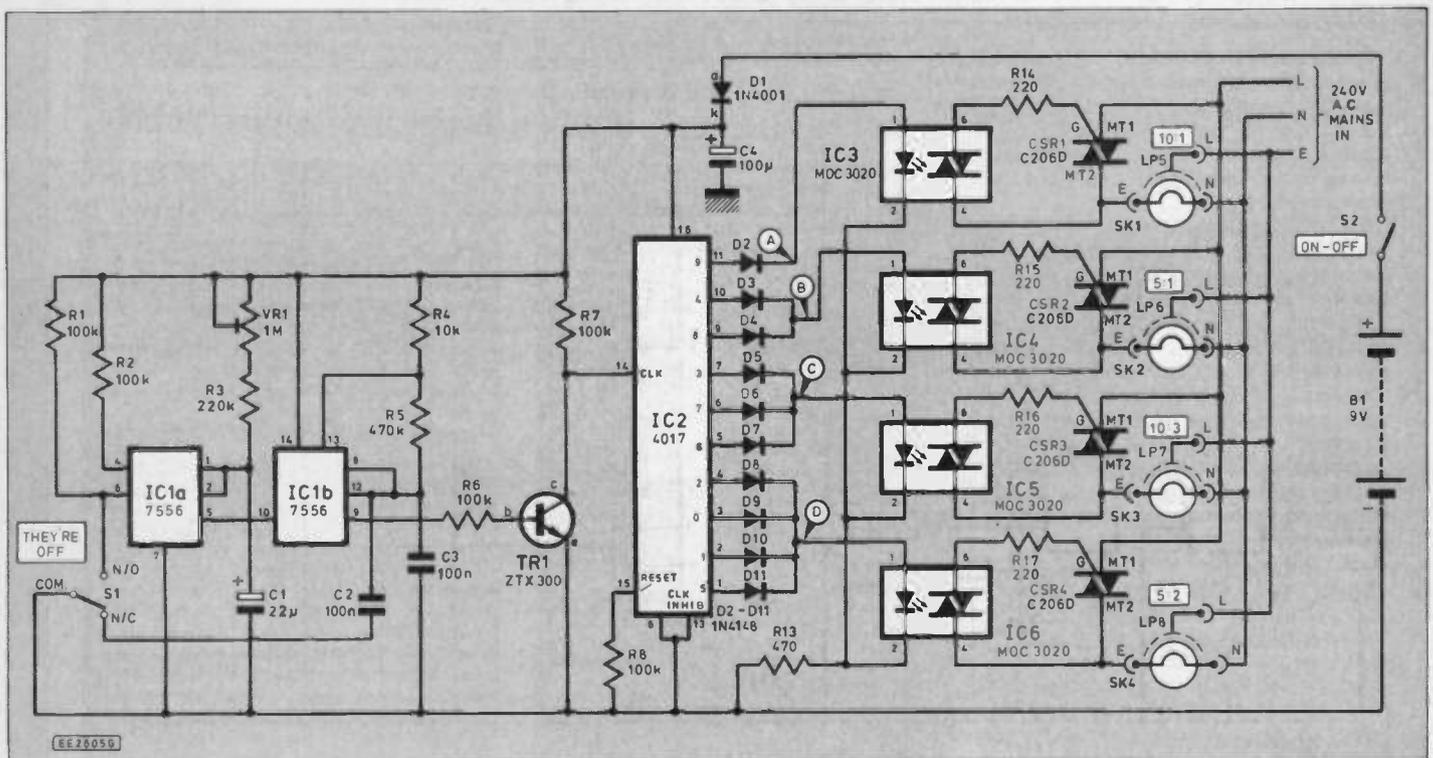

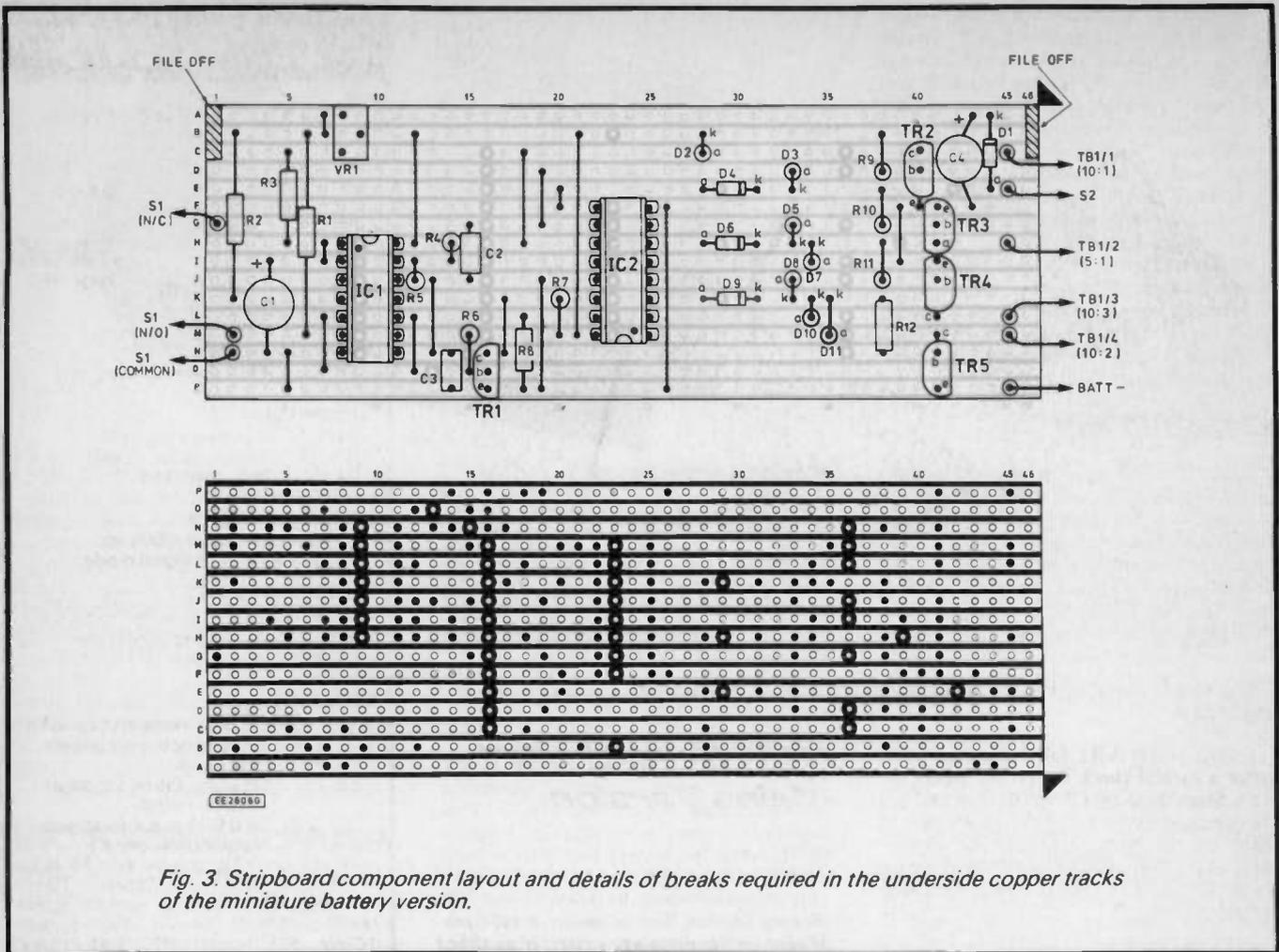


Fig. 3. Stripboard component layout and details of breaks required in the underside copper tracks of the miniature battery version.

during which the button is pressed varies slightly from one "race" to another. This is desirable to prevent any pattern developing - however unlikely - in the order of winning horses.


CONSTRUCTION - Miniature Version

Construction of the Grand National miniature version is based on a circuit panel made from a piece of 0.1in. matrix stripboard, size 46 holes x 16 strips. The topside component layout and details of breaks in the underside copper tracks are shown in Fig. 3.

Begin by cutting the panel to size and checking that it slides into the grooves of the plastic box. Make all inter-strip links and track breaks as indicated. File off the top corners of the circuit board as indicated so that when this is in position the lid will close on the specified plastic box.


Solder the on-board components, including the i.c. holders, into position taking care over the polarities of all diodes and capacitors C1 and C4. Take care also over the orientation of transistors TR2 to TR5. Do not insert the i.c.'s themselves until the end of construction.

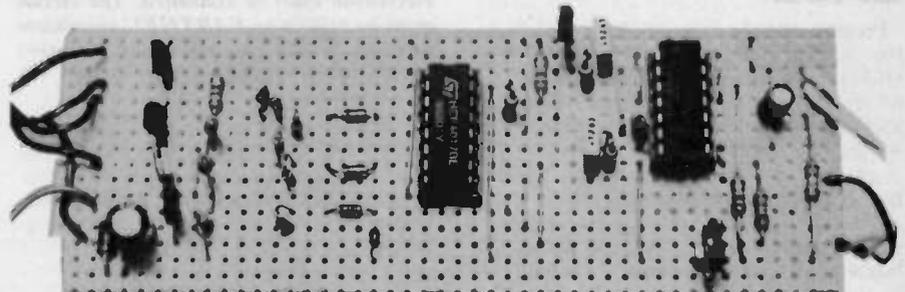
Once the on-board components, excluding the i.c.'s, have been mounted in position, solder 12cm pieces of light-duty stranded connecting wire to strips G, M and N on the left-hand side of the circuit panel. Solder similar wires to strips C, E, H, L and M along the right-hand side. Solder the negative battery connector wire to strip P.



Completed circuit board for the miniature version.

Fig. 4. Interwiring details for the miniature version.

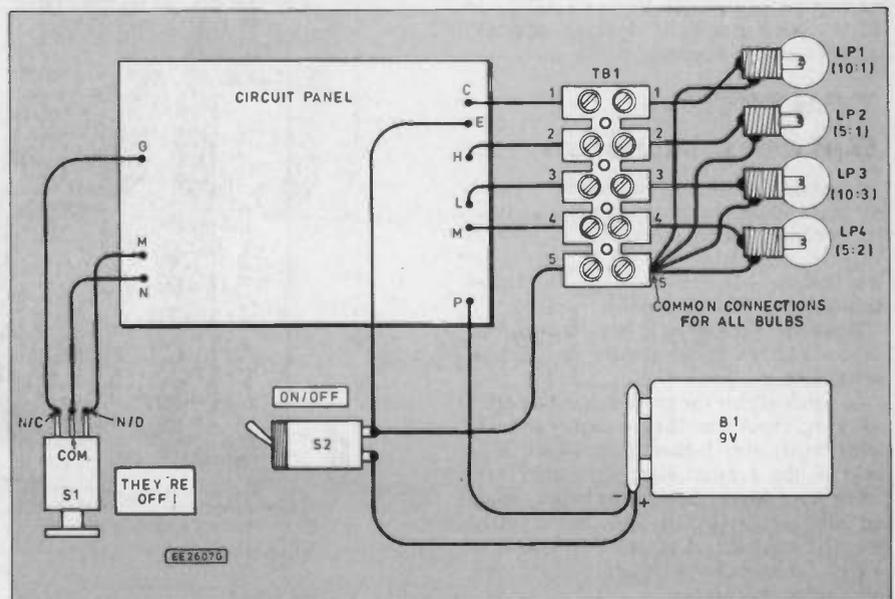

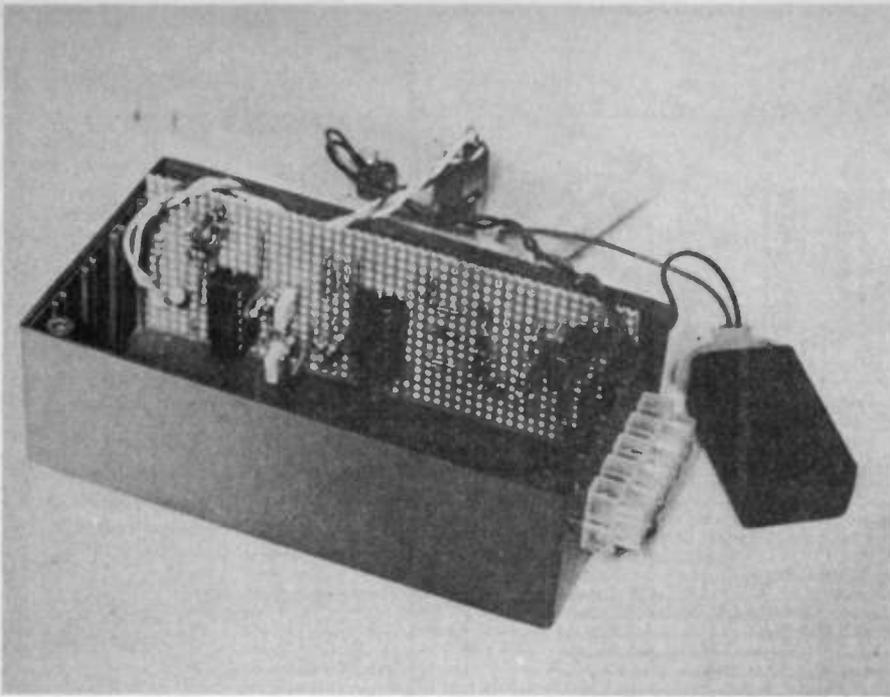

The complete miniature version showing the lamp connecting block mounted on the outside of the case.

Adjust preset VR1 fully clockwise and, after a careful check for errors, insert the i.c.'s. Since these are CMOS devices and can be damaged by the static charge which may exist on the body, take care to unpack and insert them without touching the pins. Note that IC2 is upside down compared with IC1.

CASE

Prepare the box by making holes in the lid for push switch S1 (THEY'RE OFF!) and the toggle switch S2 (ON-OFF). Mount these components. Drill holes for, and mount, the 5-way terminal block TB1, on the side. Drill a 5mm hole below TB1 position to carry the wires passing through the box from the circuit panel.

Refer to Fig. 4 and complete all wiring. It will be found necessary to file off the fixing bushes in the lid of the case to enable this to close when the circuit panel is in position.

Attach the lamp holders to the "horses" and, using light-duty twin-stranded connecting wire, connect these to TB1/1 to TB1/5. Note that TB1/5 forms a common connection for all lamps.

TESTING — Battery Version

Commence testing of the battery version by first sliding the circuit panel into position and connecting the battery. Switch on S2 — usually the circuit self-triggers when this is done — if not, press S1. The lamps should begin flashing rapidly.

When the timing cycle has elapsed, one of the lamps should remain on. Repeat several times.


To confirm that the randomization part is working, check that the frequency of flashing is noticeably higher while switch S1 is held in the pressed state compared with when it is released. Secure the battery using an adhesive fixing pad. The timing period may be adjusted as require by means of VR1 — anti-clockwise rotation of the sliding contact increases it.

CONSTRUCTION — Mains Version

Safety note:

Construction of the mains circuit should only be undertaken by readers who are sure of their ability to make a safe job. Where any uncertainty exists, a qualified electrician must be consulted. The circuit must be built in an EARTHED aluminium box and on no account may a non-earthed mains supply be used.

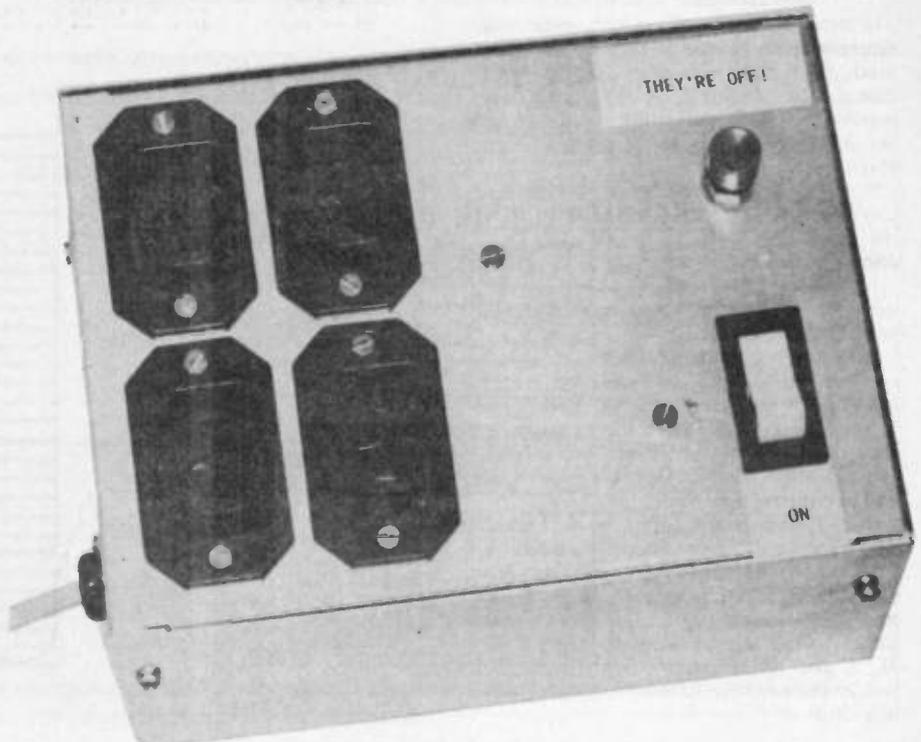Construction of the mains version is based on two circuit panels each made from 0.1in. matrix stripboard. The component layout and details of the underside breaks in the copper tracks is shown in Fig. 5 and Fig. 6.



COMPONENTS

MINIATURE VERSION

Resistors

R1, R2, R6, R7, R8 100k (5 off)
R3 220k
R4 10k
R5 470k
R9-R12 3k3 (4 off)
All 0.25w 5% carbon.

See
SHOP
TALK
Page 468

Potentiometer

VR1 1M sub-min preset, vert.

Capacitors

C1 22 μ axial elec. 10V
C2, C3 100n ceramic (2 off)
C4 100 μ elec. 16V

Semiconductors

D1 1N4001 1A 50V rec.
D2 to D11 1N4148 signal diode (10 off)
TR1-TR5 ZTX300 npn silicon (5 off)
IC1 ICM 7556 dual CMOS timer
IC2 4017B CMOS decade counter

Miscellaneous

S1 Push-to-make switch, with single-pole changeover contacts
S2 SPST miniature toggle or rocker switch
LP1-LP4 6V 0.06A m.e.s. lamp and bulbholder (4 off)
Stripboard 0.1in. matrix, size 16 strips \times 46 holes; case, size 125mm \times 70mm \times 49mm (external); 5-way 3A screw terminal block; 14-pin d.i.l. socket; 16-pin d.i.l. socket; PP3 battery and connector (see text); materials for "horses"; connecting wire; solder etc.

Approx cost
guidance only

£12

The main panel, on which most of the components are mounted, uses a piece of stripboard size 36 holes \times 16 strips. The

COMPONENTS

MAINS VERSION

Resistors

- R1, R2, R6, R7, R8 100k (5 off)
- R3 220k
- R4 10k
- R5 470k
- R13 470
- R14-R17 220 1W (4 off)

See
**SHOP
TALK**
Page 468

All 0.25W 5% carbon except where stated.

Potentiometer

- VR1 1M sub-min preset, vert.

Capacitors

- C1 22 μ axial elec. 10V
- C2, C3 100n ceramic (2 off)
- C4 100 μ elec. 16V

Semiconductors

- D1 1N4001 1A 50V rec.
- D2 to D11 1N4148 signal diode (10 off)
- TR1 ZTX300 *n*pn silicon
- IC1 ICM 7556 dual CMOS timer
- IC2 4017B CMOS decade counter
- IC3-IC6 MOC3020 optically-isolated triacs (4 off)
- CSR1-CSR4 C206D 3A triac (4 off)

Miscellaneous

- S1 Push-to-make switch, with single-pole changeover contacts
 - S2 SPST miniature toggle or rocker switch
 - LP5-LP8 60W coloured spotlight and lamp holder (4 off)
- Stripboard 0.1in. matrix, size 16 strips \times 36 holes (main panel) and 28 strips \times 21 holes (triac panel); aluminium case, size 152mm \times 114mm \times 76mm (AB31 box); 8-pin d.i.l. socket (4 off - see text); 14-pin d.i.l. socket; 16 pin d.i.l. socket; PP3 battery and connector (see text); Euro-type 3-pin chassis socket and plug (4 off); materials for "horses"; plastic feet (4 off); connecting wire; solder tags; solder etc.

Approx cost
guidance only

£29
plus lamps


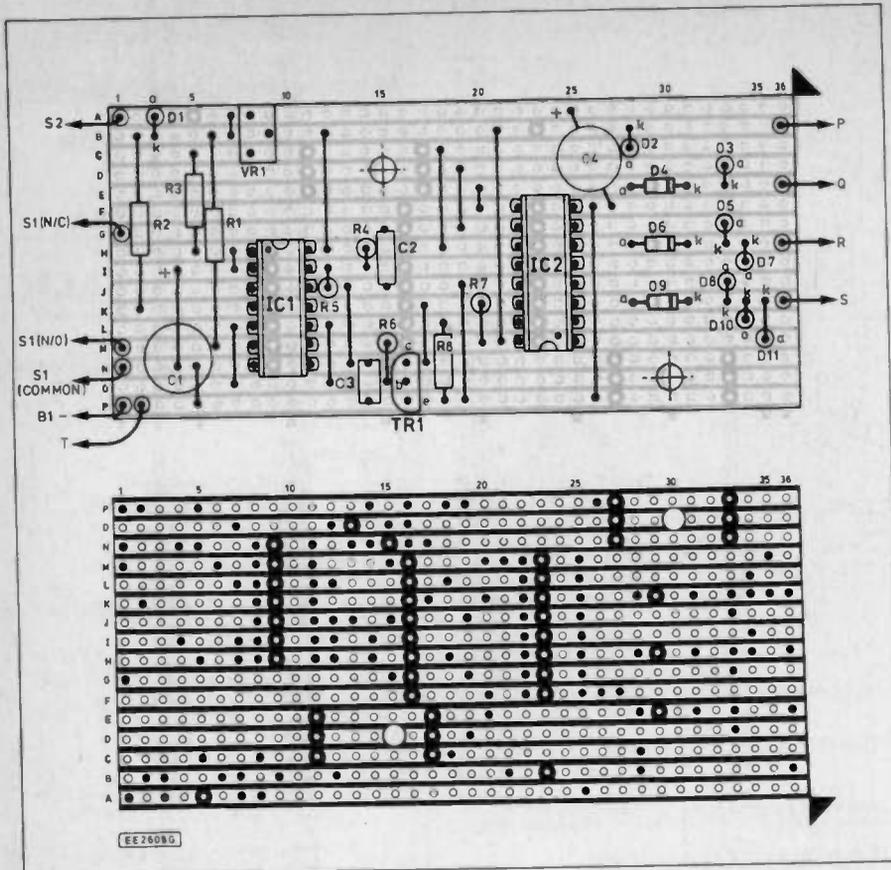


Fig. 5. Mains version main stripboard component layout and details of breaks required in the underside copper tracks.

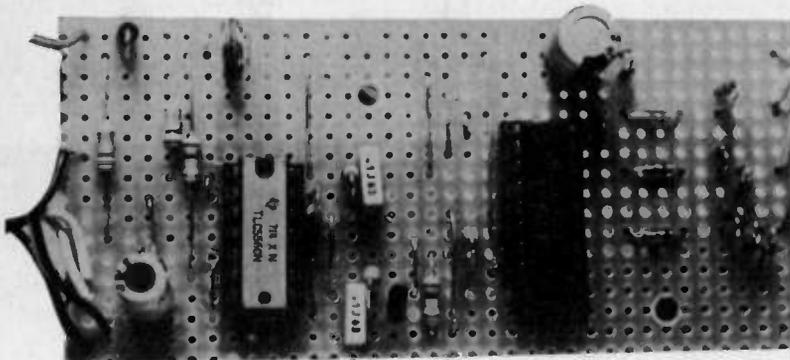

Completed mains version circuit board.

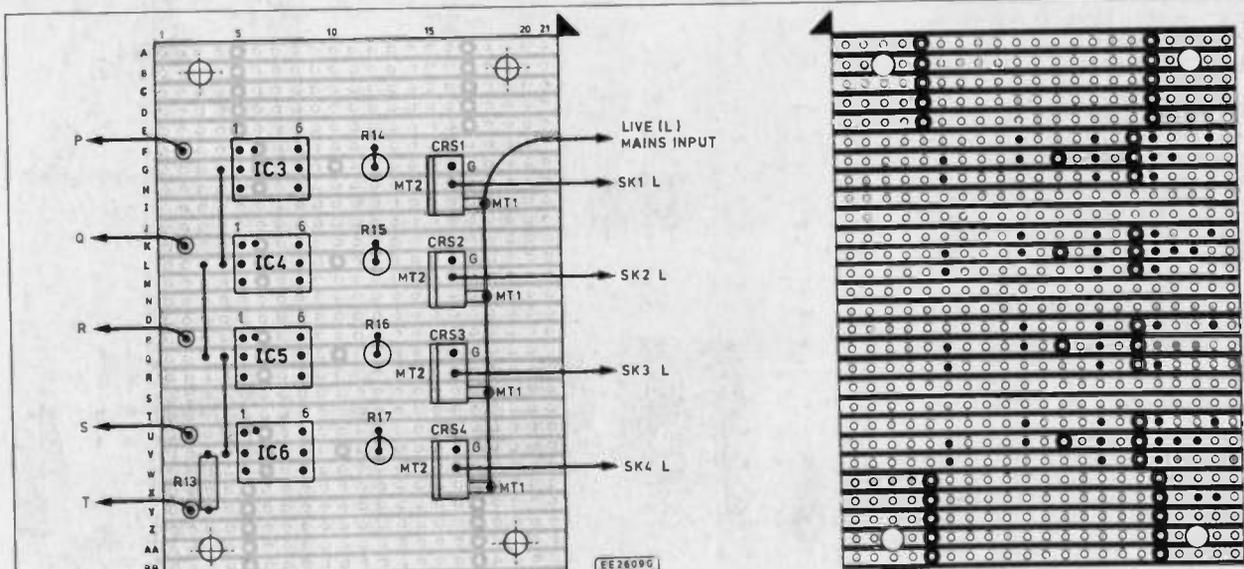


Fig. 6. Triac stripboard component layout and details of breaks in the underside copper tracks.

other panel, size 21 holes × 29 strips, is used for the optically-coupled triacs (IC3-IC6) and main triacs (CSR1-CSR4).

Cut the main circuit board to size and drill the two mounting holes. Follow with the track breaks and inter-strip links as indicated.

Mount and solder in position all on-board components as shown in Fig. 5. Pay particular attention to polarity sensitive components, such as the semiconductors and electrolytic capacitors.

Solder 10cm pieces of light-duty stranded connecting wire to strips A, G, M, N and P on the left-hand side. Solder 20cm pieces of similar wire to strips B, E, H and K on the right-hand side. Using different colours will help in avoiding errors.

Solder the negative battery connector wire to strip P on the left-hand side. Insert the i.c.'s without touching the pins and adjust VR1 sliding contact fully clockwise.

TRIAC PANEL

For safety reasons, great care must be taken when constructing the triac panel and all work must be carefully checked. In particular, all track breaks must be complete. Referring to Fig. 6, cut the strip-board to size, drill the four mounting holes, and make all inter-strip links and track breaks as indicated.

Solder the on-board components into position. The opto-triacs IC3 to IC6 are 6-pin devices and since matching sockets are not freely available, it may be necessary to cut/file 8-pin ones to size. Check the orientation of CSR1 to CSR4, noting that the left hand connection (MT1) on each is bent upwards away from the circuit panel and not soldered to copper strips as the other two triac connections (G and MT2) are.

Solder 10cm pieces of light-duty mains-type wire direct (that is, not through the copper strips) to the MT2 tags on the underside. Use similar wire to inter-connect the left-hand (MT1) triac connections.

Connect the wires from the right-hand side of the main circuit panel to strips F, K, P and U as indicated. Connect the wire from strip P on the main panel to strip Y on the triac panel. Finally, insert IC3 to IC6 into their respective sockets.

CASE

Note that everything is mounted in the lower section of the case with nothing on the lid. Prepare the box by making holes for S1 (THEY'RE OFF!), S2 (ON-OFF) also for the four mains output sockets (SK1-SK4). Mount these components (see photograph). Make holes for circuit panel mounting and drill one for the strain relief bush on the mains lead to be fitted later.

Refer to Fig. 6 and complete all interwiring. Note that all wiring shown in bold print must be made with mains-type wire of 3A rating minimum.

Make the mains input lead using 3-core mains wire - fit this with a mains plug carrying a 3A fuse. Secure it with the strain relief bush to prevent it from being pulled free in service and make the internal connections.

Note the solder tag at one of SK1 fixings which is used to EARTH the case. Secure the battery using an aluminium bracket to prevent it from moving in service.

Mount the circuit panels using short stand-off insulators and, as an additional precaution, a piece of thick cardboard



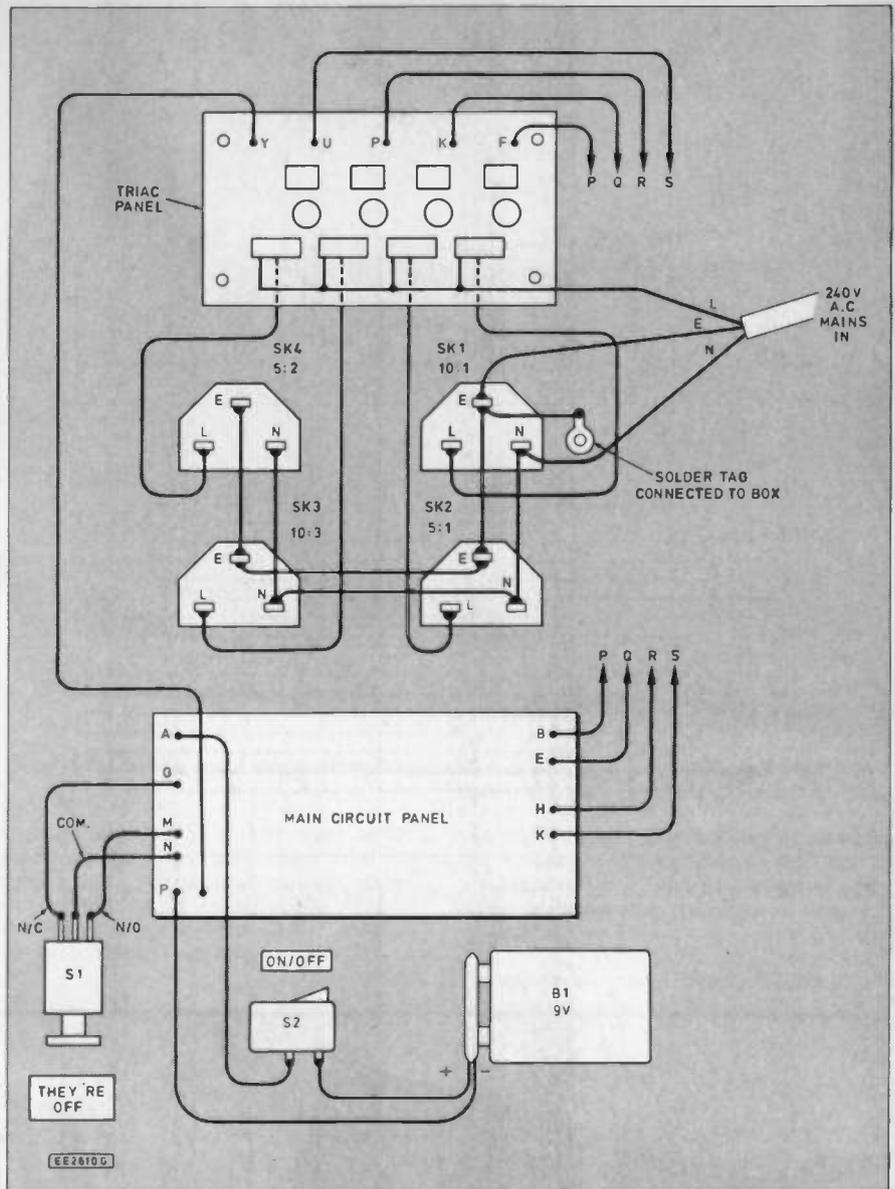


Fig. 7. Interwiring to the two mains version circuit boards. Use 3A wire for connecting up all mains sockets (SK1-SK4).

The completed opto/triac circuit board.

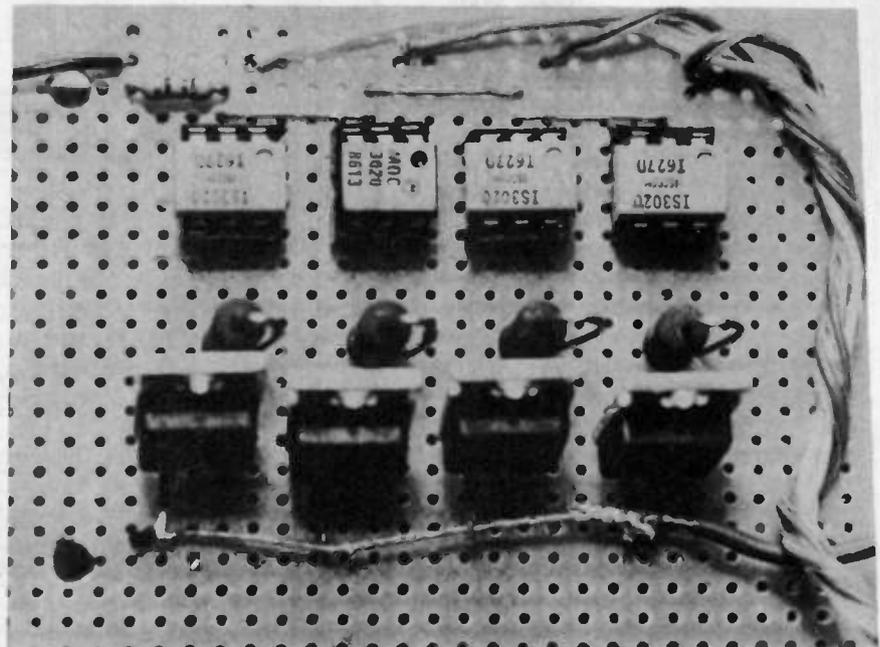

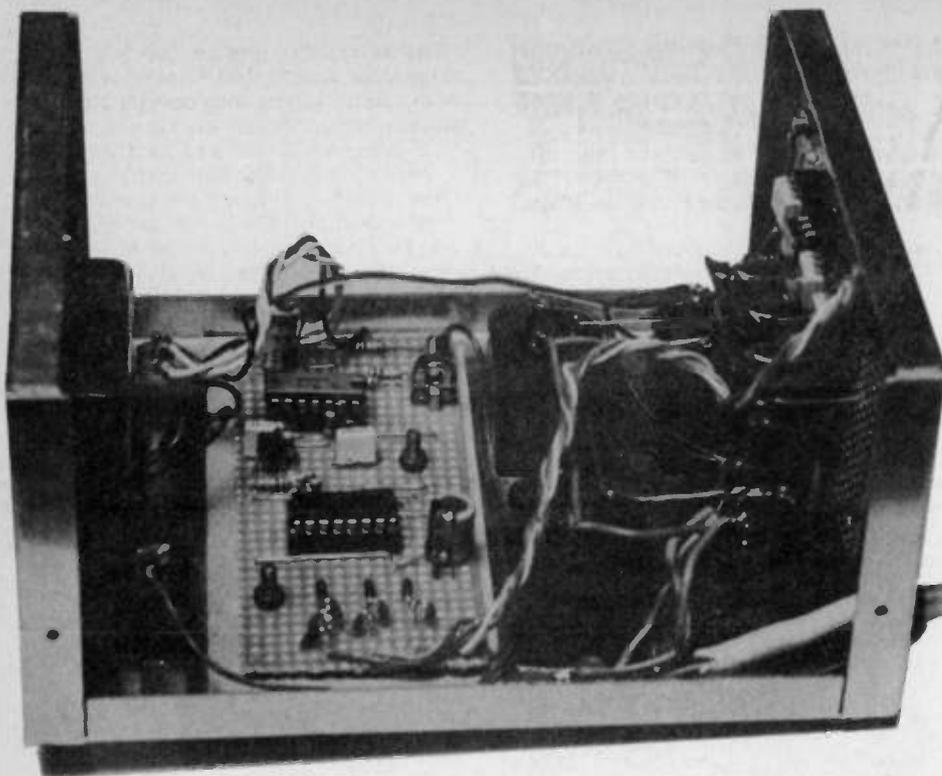

The completed mains version of the Grand National Game with the metal shroud removed to reveal positioning of components and wiring.

TESTING

Note that whenever the unit is plugged into the mains, the lid must remain on. This is because there are exposed live connections inside. Note also that although normal on-off switching is achieved using S2, the mains remains connected. At the end of a period of use, therefore, the unit MUST always be unplugged from the mains.

Insert the lamps. To prevent overheating of the triacs, these must NOT exceed 60W rating on 240V mains. Plug in the unit and switch on S2. Press S1 (THEY'RE OFF!). The lamps should flash rapidly and after a while only one should be left on.

To increase the operating time, adjust VR1 anticlockwise as required. Check the randomization part in the same way as with the battery circuit. Make up the horses and direct the spotlights on to them. Make signs to indicate the odds.

The mains circuit gives excellent service from an internal PP3 battery because the quiescent current requirement is only 10mA approximately compared with 60mA for the miniature version. For very long periods of use, a PP6 battery could be used since there is sufficient space inside the case of the mains version to accommodate this.

The miniature version gives reasonable service from a PP3 battery but this should be of the alkaline – or better still lithium – type. For long periods of use, an external battery should be used and here it is suggested that two type 126 4.5V batteries be connected in series.

It only remains to label the switches, place your bets and have fun at the Grand National! □

underneath each. Make certain that no connections on the copper strip side – or anywhere else – can touch the metalwork. Ensure a clearance of 3mm minimum here. Make a special check on the wires leading from the MT2 tag of each triac.

Connect the lampholders to pieces of

mains wire and fit Euro-style plugs to the other ends. Plug them into SK1-SK4. Secure the lid, checking for trapped wires and short-circuits as it is brought into position. Fit four self-adhesive plastic feet to the case to prevent scratching of the table top.



The New Circuit Summer Catalogue

- 100s new products
- £10 worth discount vouchers
- Latest books
- Low cost multimeters
- 184 pages
- Only £1.60 available from larger newsagents or directly from Circuit



Circuit Distribution Ltd.

Park Lane, Broxbourne, Herts EN10 7NQ
Telephone (0992) 444111

OUT NOW! OUT NOW! OUT NOW!

FOR YOUR ENTERTAINMENT

BY BARRY FOX

Not British

Earlier this year I heard, purely by chance, that the British Museum was demonstrating high definition television (HDTV). There was advance publicity for the "extraordinarily clear fine grained pictures" and "a wholly new experience" with an explanation that although the system was "originally developed with general broadcasting in mind, it is now clear that it has great potential in many fields such as industry and public exhibition".

The European electronics industry is currently spending literally hundreds of millions of pounds on developing the Eureka HD-MAC system to rival Japan's Hi Vision (the British Government has chipped in £5 million) so I initially assumed that the British Museum would be demonstrating the Eureka system. But no. The BM has wandered innocently into the minefield of HDTV politics by signing a deal with Japanese broadcasting station NHK on Japanese Hi Vision.

At a demonstration in the British Museum, NHK engineers proudly showed Hi Vision HDTV pictures on a 32 in. Sony monitor and 50 in. Panasonic rear projector. Why is the BM endorsing the very technology which European researchers are trying so hard to rival?

The answer is simple. When the BM last appealed for money, it was NHK which made an offer they could not possibly refuse. NHK is giving the British Museum £200,000 in return for the rights to make six programmes and publish a series of books about the museum's historic treasures.

Needless to say NHK and the consortium of ten Japanese manufacturers making Hi Vision equipment are making the most of the liaison and demonstrating the system to as many pillars of the British establishment as the BM can muster.

When push comes to shove, Europe only has Eureka's prototypes and promises to offer; Japan has a working system ready to use. The BBC has already adopted a similar pragmatic approach by using Hi Vision for the *Ginger Tree* series.

Drawing the Line

In the face of such enterprise, it seems churlish to say it, but NHK's demonstration of Hi Vision at the BM was one of the worst I have ever seen. Whereas pictures live from an HDTV camera were superb, the pictures off tape were blighted by nasty coarse horizontal lines.

Like everyone who sees HDTV for the first time, the historians watching the demonstration were bowled over. But once the picture defects were pointed out to them they saw them only too clearly. Faced with this unpalatable truth, the NHK engineers owned up and explained.

The pictures were being sourced from a half inch professional broadcast cassette recorder, modified to record 1125 line Hi Vision signals. Whereas the luminance bandwidth of an HDTV camera spreads over 30MHz, the tape VCR can only cope

with 22MHz. And the two colour difference signals only have half bandwidth (11MHz).

What's more these colour signals are interlaced, like a conventional TV picture. This is what causes the relatively coarse horizontal lines across the picture which NHK seemed to expect no-one would notice.

All That Jazz

Britain is now getting its first "incremental" local radio stations, the new local radio stations licensed by the IBA. The IBA's "flag ship" incremental is *Jazz F.M.* in London. What makes these stations special is the extraordinarily high level of technical automation. Being "green field" sites they equip them with all the latest high tech.

Jazz F.M. wants to be the first "paper free" radio station; the enabling technology is called Media Touch. Virtually everything in the studio can be controlled by touch sensitive screens, even from outside the studio.

A presenter miles away on an outside broadcast with a portable screen can use it to control CD players and DAT recorders in the studio by digital signals sent down a telephone line by modem. It isn't necessary even to have record sleeves and notes in the studio; these are electronically scanned and displayed on the touch sensitive screen. Computer software, called *Selector*, juggles the running order of records to suit the music mix which market research has shown listeners to prefer.

These stations, (along with other independent radio stations) are now distributing news programmes and commercials by satellite link, in one case piggy-back on top of consumer programmes on the *Astra* satellite, in other cases in digital code for unattended recording by DAT decks.

Crystal Gazing

No-one talks about crystal sets these days*.

In the twenties, many families used crystal sets, because they were cheap to make and cost nothing to run. With no active circuitry, they needed no power supply other than the aerial signal.

The idea dates back to 1906. A crystal of quartz (silicon dioxide), carborundum (silicon carbide) or galena (lead sulphide) works just like a modern transistor. It carries current in one direction only. When put into a circuit carrying radio signals down from an aerial to earth, the crystal rectifies or "detects" the sound which has modulated the radio signal.

The rectifying junction is between two crystals or, more often, between one crystal and a thin copper wire, known as a *cat's whisker*. A tuning circuit selects one radio frequency and rejects others. The detected signal is fed direct to a pair of earphones, without amplification. It's a *passive* system.

The snag of course is that the volume level is limited. Early loudspeaker radios

The technology used by *Jazz F.M.* and other new incrementals, was developed in the US to let one man operate a radio station. So far there are no plans to use it that way in the UK. And so far *Jazz F.M.* looks like being a runaway success.

So far the human touch will remain. But if other stations round the country run into financial problems, it doesn't take a genius to predict where the first cuts will be made - the people will go and one man, a guard dog and the technology will run the show.

The use of a computer to map out a running order of music tracks, timed to fit the programme length, is seen by some disc jockeys as a bogey.

But, as one ex-BBC man put it to me, "There is not really much difference between using a computer music scheduling system, to display a list of what tracks to play, than using a play list written by the producer. In one case you do what the computer says, in the other case you do what the producer says or get fired".

Moody Blues

"Off the record" DJ's talk frankly of their distrust of touch screen systems. They like the hard hands-on feel of the faders on their control desk; they don't like soft-touching a cursor on a TV screen, and then hoping that the electronics does what it should.

What DJ's worry about most, is the problem of how to "recover" if something goes wrong. In a traditional studio they can juggle jingle cartridges and flick faders, while apologising for having spilled the coffee on a record. But as anyone who has faced an LCD screen that blinks an error message well knows, there is a feeling of hopelessness when a digital system throws a moody.

Significantly, Martin Charman, Chief Engineer at *Jazz F.M.* tells of his conversation with the firm which had been contracted to fit an automated system before he was hired. "What happens if the computer crashes?" he asked. "It won't" he was told. "Yes, I know it won't" he countered "but what if it does?"

At his insistence the automation at *Jazz F.M.* can all be over-ridden by hand if "the impossible" happens, and the electronics go wrong.

relied on batteries and rechargeable lead-acid cells to deliver the D.C. voltages needed for the amplifier valves. Mains power came later, but many homes still did not have electricity. Cable radio stations pushed enough power down the line to drive a loudspeaker. Later these stations converted to TV distribution.

Today, passive systems are forgotten. But headphone listening is back in favour. Perhaps the time is right for the modern equivalent of a crystal set, with passive transistor detection and personal stereo headphones.

Radio stations put out plenty of power. The receiver would be cheap and cost nothing to operate, so it could be ideal for third world education. Batteries are like gold dust in some countries; the locals collect dead cells discarded by tourists. Of course a passive radio of this kind only works with A.M. transmissions but in practice most wide area coverage is on the A.M. band anyway.

* Barry, did you not read the Amateur Radio Supplement (*May '90*)? - Ed.

VIDEO CHECK



T. R. de VAUX-BALBIRNIE

A go/no-go light-level indicator for camcorder users

THE author recently bought a video camcorder and very satisfactory it is too. Later, it became clear that certain accessories were needed. This is probably the manufacturer's way of getting more money out of an unsuspecting public! Advertisements indicate that the equipment will work in amazingly low light levels – perhaps down to seven lux. It will – but what the blurb fails to say is that it does not work particularly well under these conditions. In low light, colour degradation and “noise” spoil the picture. Using extra light improves the results dramatically.

A video light could be the answer but these are expensive. Simply moving the subject or shifting the angle of view can greatly improve matters. Switching on some ordinary lights can also help – although a mixture of daylight and artificial light brings its own problems.

Note that the small black-and-white viewfinder picture gives no serious indication of picture quality. Also, any “low

light” warning tends to be optimistic showing an adequate rather than a reasonable working level.

THE PROJECT

This device, uses three l.e.d.s – arranged traffic light fashion – to indicate whether the light is “poor”, “adequate” or “good”. The small constructional cost makes it a worthwhile project to build and one which, as far as the author knows, is not available commercially.

The battery should last for a long time since power is used only when a push-button switch is operated. The current requirement is only 20mA approximately. Readers wishing to use the circuit for other purposes should note that it is not calibrated in terms of light intensity. It would, therefore, make only a very rough and ready photographic exposure meter.

The Video Check is designed as an “incident light” indicator. This means that it is pointed towards the camera position from

the subject. The button is pressed and the result noted. If the flashing red l.e.d. comes on, the light is inadequate. The yellow one shows that the light, although satisfactory, will lead to some loss of picture quality. The green l.e.d. shows that the light is sufficient for good quality recording.

CIRCUIT DESCRIPTION

The complete circuit of the *Video Check* is shown in Fig. 1 and centres around dual operation amplifier, IC1. This integrated circuit package contains two identical CMOS input operational amplifiers, IC1a and IC1b. These are used as voltage comparators. Thus, when the non-inverting (+) input voltage exceeds the inverting (–) one, the corresponding output will be high (supply positive voltage). In other cases it will be low.

Light is detected by light dependent resistor, LDR1, which has a response similar to that of the human eye or video camera. The resistance of this component rises as the light level falls. LDR1 forms the lower arm of a potential divider with fixed resistor R1 and preset VR3 forming the upper one. Thus, as the light intensity falls, an increased voltage is developed across LDR1 and this is applied to both IC1a non-inverting input (pin 3) and IC1b inverting input (pin 6).


IC1a inverting input (pin 2) receives a fixed voltage dependent on the adjustment of preset VR1 connected as a potentiometer across the supply. Similarly, IC1b non-inverting input (pin 5) receives a voltage dependent on the adjustment of preset VR2. VR2 is arranged in a slightly different way to VR1 and the reason for this will be explained later.

VOLTAGE LEVELS

To state typical values, suppose 3V is developed across LDR1 in dim light and 1V in adequate light. A voltage of less than 1V will then be produced in good light. VR1 will be adjusted at the end of construction to provide marginally more than 3V and VR2 marginally less than 1V at IC1a inverting input and IC1b non-inverting input respectively.

Under light which is too dim for video purposes and with S1 (TEST) pressed, IC1a will be on (pin 1 high) since the non-inverting input voltage exceeds the inverting one. The red (POOR) l.e.d. D2,

Fig. 1. Complete circuit diagram for the Video Alert.

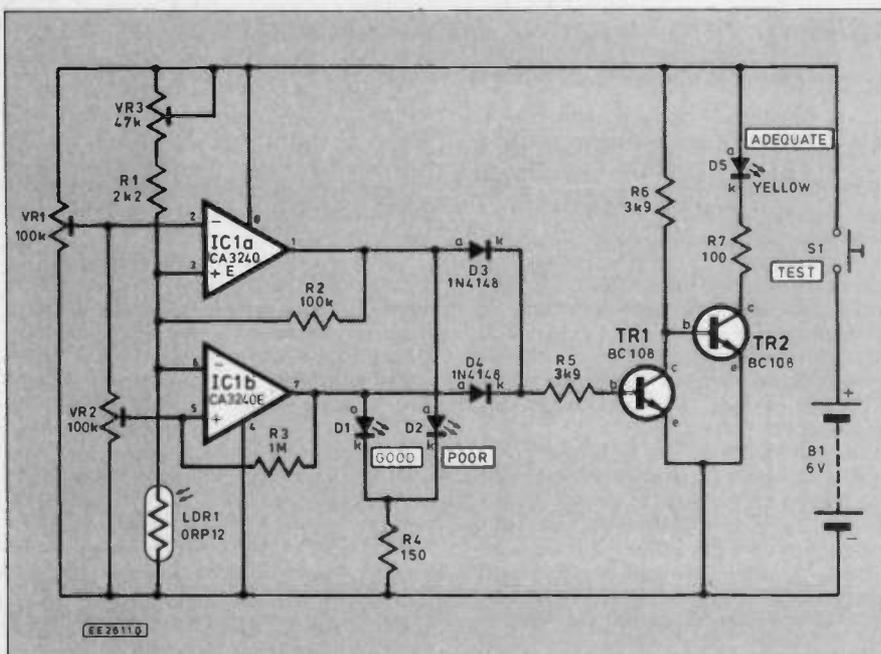

will then operate with current flowing from pin 1 through limiting resistor, R4.

Under light which is adequate, IC1a will be off since now the non-inverting voltage falls below the inverting one. IC1b will also be off because its inverting input exceeds the non-inverting one. The yellow (ADEQUATE) i.e.d., D5, will now operate in the manner to be described later.

Under good lighting conditions, IC1b will switch on with pin 7 high because the inverting input voltage now falls below the non-inverting one. The green (GOOD) i.e.d., D1, will operate through current limiting resistor, R4. It is acceptable for i.e.d.s D1 and D2 to share R4 as a common current limiting resistor since both are never on at the same time.

ADEQUATE LIGHT

The yellow (ADEQUATE) i.e.d., D5, operates in the following way. With both IC1a and IC1b off (that is, in conditions of adequate light) no base current flows into transistor TR1 which therefore remains off, with its collector high. Transistor TR2 is thus turned on with base current flowing through R6. This, in turn, lights D5 in the collector circuit with R7 limiting the operating current to the correct working value.

In conditions of either poor or bright light, current will flow through diode D3 or D4, as appropriate. Base current will then flow into transistor TR1 via resistor R5 so

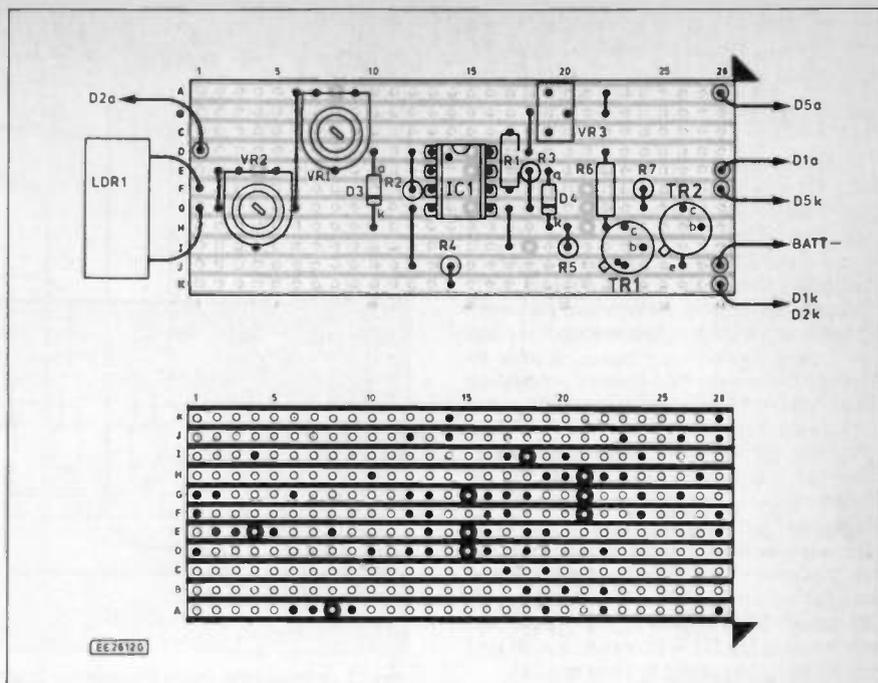


Fig. 2. Circuit board component layout and details for breaks required in the underside copper tracks.

turning it on. The collector then goes low turning off TR2 and hence D5.

Resistors R2 and R3 provide a small amount of positive feedback to IC1a and IC1b non-inverting inputs respectively. This provides for sharp switching of the op-amp in conditions of gradual changes in light level.

Note that VR2 upper track connection is connected to VR1 sliding contact. This is because the voltage at IC1b non-inverting input will always need to be less than that at IC1a inverting one and this arrangement ensures that this is so.

CONSTRUCTION

Construction of the *Video Check* is based on a circuit panel made from a piece of 0.1 inch matrix stripboard size 11 strips by 28 holes. Fig. 2 shows top and underside

details. Begin by making all track breaks and inter-strip links as indicated. Note that the track interconnecting IC1 pins 3 and 6 must be left intact. Follow with the soldered on-board components noting that diodes D3 and D4 must be connected the correct way round as shown.

Do not insert IC1 into its socket until the end of construction as it requires special handling precautions. Note the manner in which LDR1 is mounted. Sleeve its connections to within 2mm of their ends. Solder into position then bend the leads carefully so that the device takes up the position shown in the photograph. Take care to avoid bending the wires too near to the LDR body since they are easily broken off.

Solder 8cm pieces of light-duty stranded connecting wire to strip D on the left-hand side and to strips A, E, F, J and K on the right-hand side of the circuit panel. Make a

COMPONENTS

See
**SHOP
TALK**
Page 468

Resistors

R1	2k2
R2	100k
R3	1M
R4	150 (220 if 9V battery is used)
R5, R6	3k9 (2 off)
R7	100 (180 if 9V battery is used)
All 0.25W 5% carbon.	

Potentiometers

VR1, VR2	100k horizontal presets (2 off)
VR3	47k vertical preset

Semiconductors

IC1	CA3240E f.e.t. input bipolar output dual op.amp
TR1, TR2	BC108 npn silicon (2 off)
D1	5mm green i.e.d.
D2	5mm red i.e.d. (standard or flashing type)
D3, D4	1N4148 (2 off)
D5	5mm yellow i.e.d.
LDR1	ORP12 light-dependent resistor


Miscellaneous

S1	sub-miniature push-to-make switch
B1	4SR441 6V silver oxide battery 12.6mm diameter 25.2mm high or PP3 battery and connector (see text).

Stripboard; 0.1 inch matrix, size 11 strips by 28 holes; plastic case size 94 x 61 x 27mm overall (Verobox type 401); 8-pin i.c. socket; i.e.d. clips (3 off); stranded wire; solder; adhesive fixing pads etc.

Approx cost
guidance only

£9

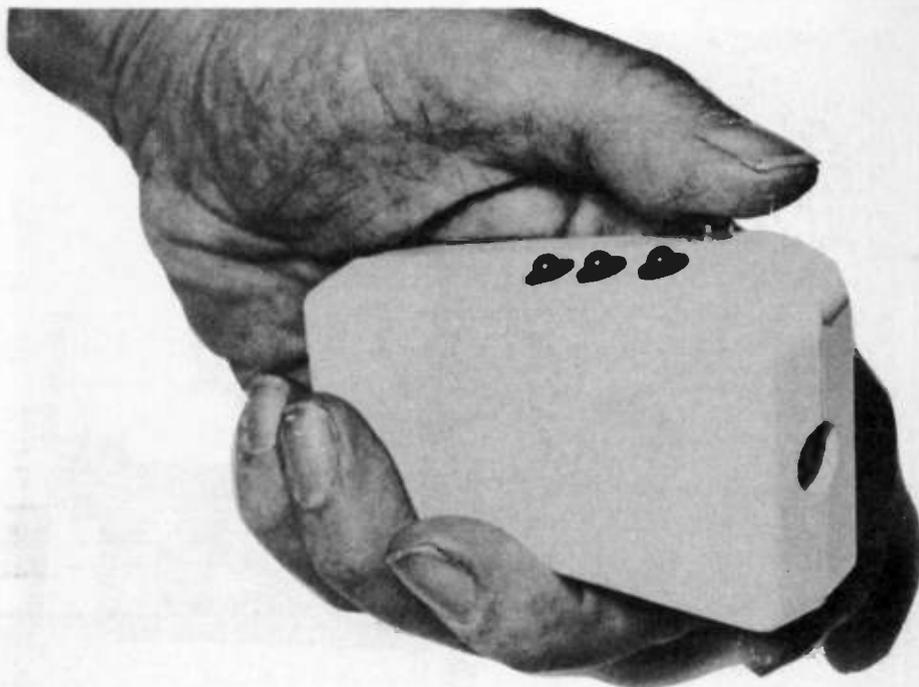

careful check of the completed panel then adjust VR1, VR2 and VR3 to approximately mid-track position.

CASE

The smart hand-held box specified in the parts list was used to house the prototype unit. This device is going to be used with expensive video equipment and should have a good appearance. However, to save money any small plastic box could be used.

Because space is at a premium, the small 6V silver oxide battery specified in the parts list is used. With larger boxes, it may be possible to house a PP3 battery – resistors R4 and R7 will then need to have the alternative values specified.

Prepare the case by marking out carefully and drilling holes for S1 and for the three l.e.d.s (see photograph). The best appearance is obtained by using proper l.e.d. clips but a reasonable job can be made by making holes which are a tight push fit and securing the l.e.d.s with a little adhesive on the inside. Note that a flashing red l.e.d. may be used for D2 – however, a standard non-flashing one could be used instead.

Hold the circuit panel temporarily in position (see photograph) and check the position of the LDR. Drill a hole 10mm in diameter in the side of the case corresponding to this position. This is best done by clamping the two halves of the case together using the plastic jaws of a small vice. A small pilot hole should then be drilled and the diameter increased progressively to the full size. It should then be smoothed carefully.

INTERWIRING

Secure the circuit panel using two or three adhesive fixing pads. This method is quite satisfactory and avoids ugly bolt heads on the outside of the case. Refer to Fig. 3 and complete all wiring observing the polarity of the l.e.d.s. Solder the connecting wires leading from the circuit panel direct to the l.e.d.s using minimum heat from the soldering iron. Bend the soldered connections apart to prevent short circuits. Adjust the LDR position if necessary so that it lies directly behind the hole in the case.

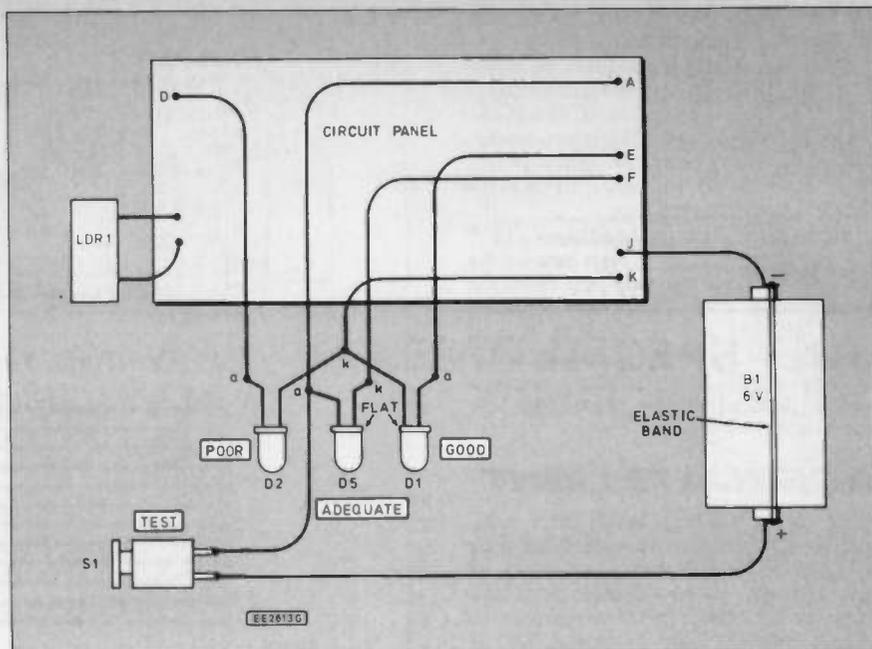


Fig. 3. Interwiring from the circuit board to off-board components.

FINAL CONSTRUCTION

Remove IC1 from its special packing and, without touching the pins, insert it into its socket with the correct orientation. It is necessary to take this precaution since IC1 is a CMOS device which could be damaged by any static charge existing on the body.

The silver oxide battery may be connected by removing the end 3mm of insulation from the wires, bending them double and tinning them with solder. A small elastic band may then be used to hold them in position. Do not attempt to solder the wires direct to the battery and do not allow the wires to touch the metal case of the battery or a short-circuit could be caused.

If a PP3 battery is being used then a standard PP3 battery clip will make the connections. Secure the battery to the base of the case using an adhesive fixing pad. Leave the lid off since access is required to adjust the presets.

SETTING-UP

Using normal room lighting, perform a basic check by shading the LDR with the hand and pressing S1. The display should go from yellow or green to red. If it remains yellow or green, rotate VR1 sliding contact clockwise and re-check. If it is red all the time, adjust VR1 anti-clockwise a little.


Now allow bright light to shine on the LDR and adjust VR2 so that the display is green – clockwise rotation increases the light level at which it comes on. With intermediate levels of light, the yellow l.e.d. should be on. If adjustment to VR1 or VR2 cannot achieve the desired effect, adjust VR3 a little – clockwise rotation (as viewed from VR1) will raise the light level at which all l.e.d.s operate.

Accurate adjustment of the presets is now required so that the *Video Check* operates at the correct light levels. This can only be done with the camcorder set up and the results viewed critically.

Attach a detailed object such as an Ordnance Survey map on the wall and set up the camcorder on a tripod at least 2m away to view it. Arrange a bright light source to shine evenly on the map. By moving the light back and forth and carefully viewing the recordings made on a colour T.V., find the least light which will provide a satisfactory picture, reasonably free from noise (a grainy appearance).

Point the *Video Check* towards the camera from the map position making sure that you do not shade any light which would otherwise reach it. Press S1 and adjust VR1 until the red l.e.d. is just off. Now re-adjust the lamp so that the best quality picture is just obtained. Adjust VR2 until the green l.e.d. is just on. At intermediate light levels, the yellow l.e.d. should be on. Secure the two halves of the case together taking care to avoid trapped wires and short circuits. The l.e.d.s and switch could be labelled but in the interest of giving a clean appearance, this was not considered necessary in the prototype unit.

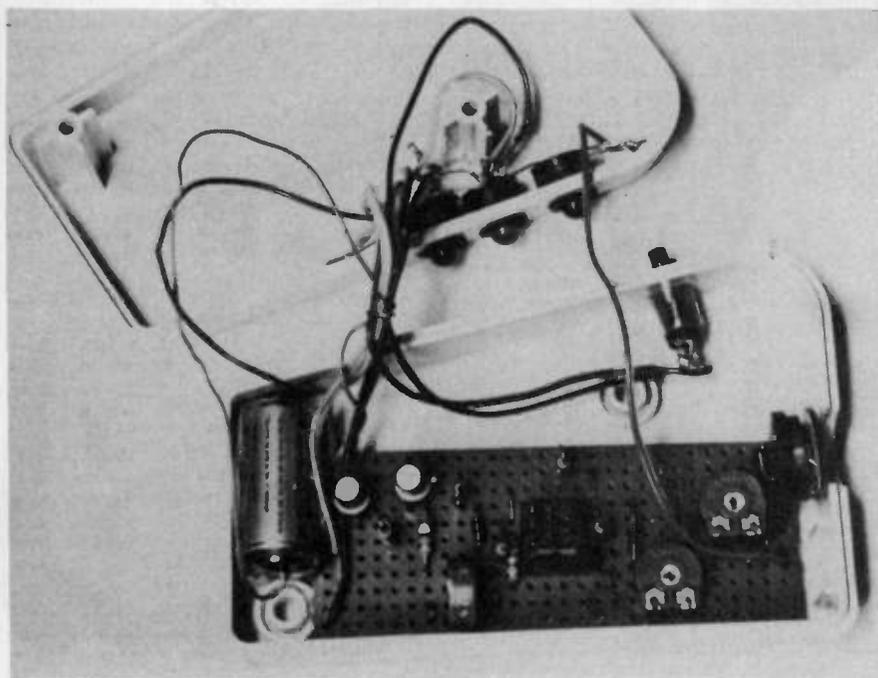In theory, the type of light used affects the results. The *Video Check* was tested in daylight, artificial (tungsten) and fluorescent light. Good indications were obtained in all cases. □



MARCO Trading

ELECTRONIC COMPONENTS & EQUIPMENT

24HR
ANSAPHONE



SEND ORDERS TO -
MARCO TRADING
THE MALTINGS, HIGH STREET, WEM
SHROPSHIRE SY4 5EN DEPT 7
Tel: (0939) 32763 Telex: 35565
Fax: (0939) 33800
ELECTRICAL & ELECTRONIC
COMPONENT SUPPLIERS


NEW CATALOGUE
200+ PAGE ELECTRONIC
COMPONENT CATALOGUE
(INCLUDING DISCOUNT
TICKETS) SEND **£1.00**

VISIT OUR SHOPS AT
SUPERTRONICS, 65 HURST STREET, BIRMINGHAM. 021 6666504
WALTONS, 55A WORCESTER STREET, WOLVERHAMPTON. 0902 22039

ALL
PRICES
INCL. VAT

Please add £1.50 P&P unless stated

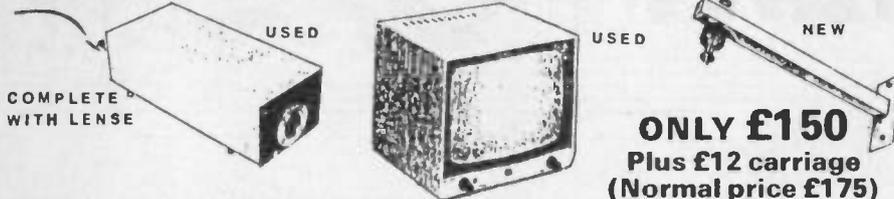JULY SPECIAL OFFER (ONLY VALID FROM 1st TO 31st JULY) "CLOSED-CIRCUIT" TELEVISION SYSTEM



A small range of "used" closed-circuit television equipment, offering exceptional value-for-money with a real saving over new, often unaffordable, equipment prices. Illustrations not to scale and for guidance only - items supplied may vary.

☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆

OSCILLOSCOPES

TEKTRONIX 2215. Dual Trace 16MHz, Delay Sweep with manual. New Probes. Limited quantity
£500
Inc. VAT (Carriage £12)

TELEQUIPMENT D755 OSCILLOSCOPE
Dual Trace, 50MHz Delay Sweep, Secondhand - Excellent Value - Solid State Full Manuals
£300
Inc. VAT (Carriage £12)

Supplied. ALSO OTHER SCOPES IN STOCK. PLEASE RING


HOME ALARM PACKAGE

- Includes:
- ★ Optima Alarm Control Panel
 - ★ External Red Bell Box
 - ★ 2 x 1 Internal Passive I.R.
 - ★ 2 x Door Contacts
 - ★ Siren for bell box
 - ★ 100 mtrs. cable and clips
 - ★ Full fitting instructions
- ONLY £115 + £2.50 CARRIAGE**
(Phone for further details)

FULL RANGE
LEAD ACID
BATTERIES IN
STOCK ONE TO
SUIT ALARMS
12V 1.9Ah
£14.99

12V TWIN FLUORESCENT LAMP 12" DOUBLE TUBES

ONLY £5.99

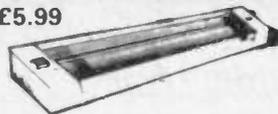

ATTRACTIVE WHITE FITTING, RIBBED PERSPEX DIFFUSER, ON/OFF SWITCH, 3FT CABLE, TRANSISTORISED CIRCUITRY, KEYHOLE FIXING 12V DC 8W TUBES, DIMENSIONS: 368 x 67 x 43MM

IDEAL FOR BOATS, CARAVANS, VANS, ETC

TEST PROBES-XI.XIO ONLY £14.99

FM TRANSMITTER

Very High Quality "MINI-BUG" - Ideal for baby alarms etc!! A very good range is obtainable - we have obtained over 1/2 mile, but it does depend on conditions. Simply remove cover - insert battery - and you're ready to go. Reception can be obtained on any FM radio. Frequency 105-109MHz FM. Power: PP3 9V battery (not included). Dimensions: 4.25" x 2.25" x 0.75". Order Code - 50.004. Price **£9.99**



BRAND NEW FANS

LIMITED STOCK

80mm - 240V Torin-TA300 **£3.50**
80mm - 12V 0-13A Panaflo **£4.50**

22SWG RESIN SOLDER

500gm. REEL. 1+ 10+ 100+
£4.99 £4.75 £3.99

ALSO 18SWG at £4.95 500gm

Orders of 5 or more reels please add a further 75p P&P

DESOLDERING PUMP

£2.99

ORDER CODE
TOOL/OESOL



RED LED'S 5MM

100 PACK **£4.00**
1,000 PACK **£15.00**

SPECIAL PRICE
ON 100'S
AND 1,000 OFF
LIMITED OFFER
WHILE STOCK SLAST

IEC MAINS LEADS

BLACK - 6A 250V
1 + 85P 100 + 65P
(2 metres)

ANTEX IRONS

C-15W IRON	£7.65
CS-17W IRON	£7.75
XS-25W IRON	£7.85
XS-KIT 25W	£10.85
CS-KIT 17W	£10.75
C-KIT 15W	£10.75

ALL BITS FOR IRONS - £1.60
ELEMENTS £3.95 STANDS £2.99

ORYX PORTASOL GAS
SOLDERING IRON
£18.75 TIPS £5.50

MARCO KITS

Ceramic 50V (125)	£3.99
Electronics Red (100)	£8.50
Fuse 20mm Q.B. (80)	£4.75
Fuse 20mm A.S. (80)	£8.50
Pre-set Pots Horiz. (120)	£7.75
Pre-set Pots Vert. (120)	£7.75

RESISTORS

0.25W Popular (1000)	£6.99
0.25W 5 off (305)	£3.75
0.25W 10 off (610)	£5.10
0.5W Popular (1000)	£10.75
0.5W 5 off (365)	£8.40
0.5W 10 off (730)	£8.75
1W 5 off (365)	£15.25
2W 5 off (365)	£25.00
Zener Diodes 5 off (55)	£3.99


EIGHTWAY SPLITTER

8-way splitter amplifier to supply 8 TVs from one antenna. White plastic box with aluminium panel. On/off switch with neon.
Band width.....40MHz-860MH
Gain.....3dB per channel. Total 21dB
Impedance.....75Ω
Max. output.....80mV (38dBmV)
signal/cross modulation = 6dB
Noise.....6dB
Isolation between outputs 40dB min
Power.....240Vac 50Hz
Dims.....250 x 100 x 60mm

£29.99



£19.99

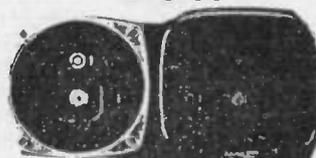

CAR EQUALIZER BOOSTER-120w

High power stereo equalizer/booster. twin 5-band graphic equalizer, fader control for front/rear speakers and twin 10-LED power indicators. inputs for high or low level from car stereo.
Mounting hardware included.

SPECIFICATION

Output power 120W per channel
Frequency response 30-20000Hz
Input level 300mV (low) 2.5V (high)
Input impedance 50ohm
Output impedance 4-Bohm
Power 12-14V d.c.
Dimensions 150 x 45 x 135mm

ORDER CODE
CAR/EB2
PRICE
£33.50



BT APPROVED

Master Socket (Flush)	£3.30
Master Socket (Surface)	£3.25
Secondary Socket (Flush)	£2.05
Secondary Socket (Surface)	£2.50
B.T. Cable (per metre)	15p
100M	£12.00
Line Jack Cord with Plug	£2.20
Extn. Lead 5 metres	£4.30

SERVICE MANUALS

SONY SL-C5/6/7/9
FERGUSON VHS1J1/3V00/MR33301K
FERGUSON VHS1J1/3V22/MR33201K
ALL **£8.00 EACH**

85W DOOR/SHELF SPEAKERS B009G RTS430

Hi-fi quality 3-way co-axial flush mounting speaker system. Unique design, gunmetal and black grill. 80W max. power handling per speaker
Maximum power.....85W
Frequency response.....80-22000Hz
Speaker size.....4" woofer, 1 1/2" mid, 1" tweeter
Impedance.....4Ω
Mounting depth.....43mm

NI-CAD CHARGER

Charges AAA, AA, C, D & PP3 Ni-Cads.
240V AC

£4.99




NI-CAD RECHARGEABLE BATTERIES

	PRICE	EACH
1+		10+
AAA	£1.50	£1.30
AA	95p	85p
C	£1.95	£1.80
O	£2.00	£1.85
PP3	£3.90	£3.75

ABS BOXES BLACK PLASTIC


INTERNAL DIMENSIONS mm	ORDER CODE	PRICE 1+
A B C		
76 58 35	BOX/MB1	£1.24
95 71 35	BOX/MB2	£1.32
115 95 37	BOX/MB3	£1.58
145 95 55	BOX/MB5	£2.20
165 119 75	BOX/MB7	£3.20
207 122 77	BOX/MB4	£4.96
213 142 57	BOX/MB6	£3.78

BOXES P.V.C. COVERED STEEL

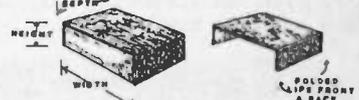

WD INCHES	DEP HT INCHES	WD MILLIMETRES	DEP HT MILLIMETRES	ORDER CODE	PRICE
4.5	2.25	2.0	114	57 51	BOX/J2 £1.70
6.0	4.0	2.0	153	102 51	BOX/J6 £2.30
8.0	5.5	2.0	204	140 51	BOX/J9 £3.10
11.0	11.0	2.0	280	280 51	BOX/J26 £5.40
4.0	3.0	2.6	102	76 64	BOX/J3 £2.00
6.0	3.0	2.5	153	76 64	BOX/J5 £2.40
8.0	4.0	2.5	204	102 64	BOX/J8 £3.00
9.0	5.25	2.5	230	134 64	BOX/J12 £3.40
5.0	6.0	3.0	127	153 76	BOX/J11 £3.10
8.0	6.0	3.0	204	153 76	BOX/J14 £3.70
8.0	8.0	3.0	204	204 76	BOX/J19 £4.40
11.0	6.0	3.0	280	153 76	BOX/J20 £4.80
11.0	7.5	3.5	280	190 90	BOX/J29 £5.80
17.0	7.5	3.5	433	190 90	BOX/J46 £8.20
6.0	4.0	4.0	153	102 102	BOX/J10 £3.10
6.0	6.0	4.0	153	153 102	BOX/J15 £3.70
6.0	9.0	4.0	153	230 102	BOX/J22 £4.80
8.0	7.0	4.0	204	178 102	BOX/J23 £4.80
8.0	6.0	5.0	204	153 127	BOX/J24 £4.90
11.0	6.0	5.0	280	153 127	BOX/J33 £5.90
15.0	6.0	5.0	380	153 127	BOX/J45 £7.10
8.0	11.0	5.0	204	280 127	BOX/J44 £6.80
11.0	11.0	5.0	280	280 127	BOX/J60 £8.70
15.0	11.0	5.0	380	280 127	BOX/J83 £10.80
7.0	10.0	7.0	178	254 178	BOX/J49 £7.80
10.0	10.0	7.0	254	254 178	BOX/J70 £9.60
17.0	10.0	7.0	433	254 178	BOX/J119 £13.80

CHOOSING AND USING TEST EQUIPMENT

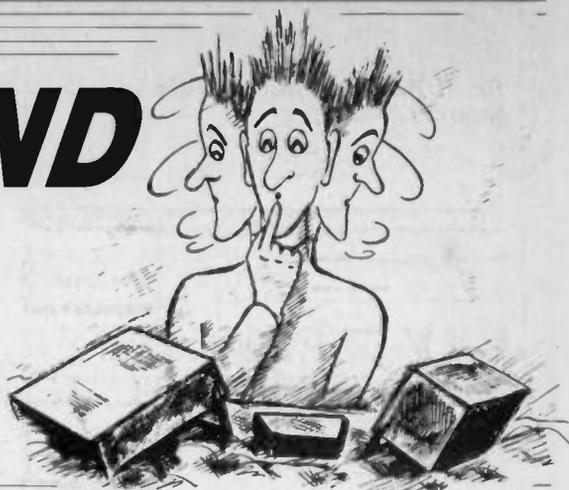

Robert Penfold

THE OSCILLOSCOPE

A short series of self-contained articles looking at the various items of test gear available.

How useful are they? How to use them! What to look for.

FOR sheer versatility the oscilloscope has no real competition. It can be used to undertake most of the testing that can be done using a multimeter, plus a great deal besides. It's not that an oscilloscope can reach the parts of circuits that other equipment cannot reach, but having reached it an oscilloscope will almost invariably be able to tell you exactly what is happening. More simple test equipment such as a multimeter will often give ambiguous results.

If a test point measures up at half the supply voltage, it is actually static at this

level, or is there a squarewave signal which is giving an average voltage equal to half the supply potential? A multimeter cannot distinguish between static levels and fast pulse signals, but an oscilloscope is unlikely to let you mistake one for the other.

Although an oscilloscope tends to be regarded as a device for viewing waveforms, it is actually a true measuring instrument. It can tell you the maximum and minimum voltages in a waveform, the duration of one cycle, or with a simple calculation, the frequency of the signal.

The accuracy of readings will not equal

that of sophisticated digital instruments, since you are having to take the readings from what is basically just a simple analogue scale, but the degree of precision is adequate for most purposes.


SCOPE BASICS

The basis of an oscilloscope is the cathode ray tube. This has a heated cathode at the rear which generates an electron beam, and in this respect it is similar to a conventional valve. The electrons are focused into a very narrow beam by sets of electrodes carrying suitable charges, and then travel on until they reach the phosphor screen at the front of the device. Where the electrons strike the screen light is produced, and the narrowly focused electron beam results in a small spot of light being generated (usually no more than about 1 millimetre in diameter).


In order for the c.r.t. to function in an oscilloscope it is essential to have some means of directing the beam to any desired part of the screen. This can be achieved by electro-magnets or by electro-static forces. It is this second method that seems to be preferred for oscilloscope c.r.t.s.

Two plates on either side of the beam and just ahead of the screen enable the spot to be moved from side to side, while plates above and below the beam provide vertical control. These are the "X" and "Y" plates respectively.

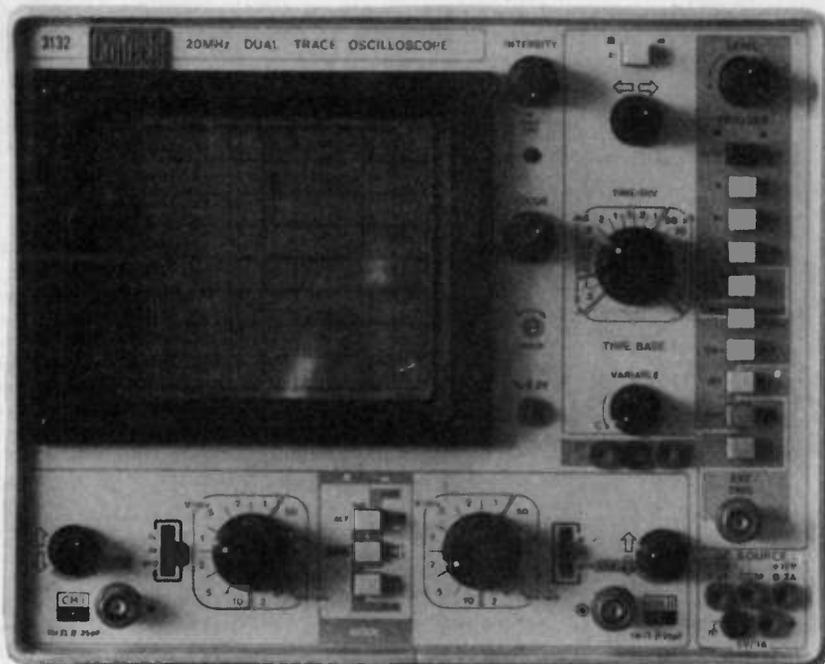A voltage difference across a pair of plates causes a shift in the spot, and the amount of shift is proportional to the voltage difference. The direction of the shift can be changed by changing the polarity of the voltage.




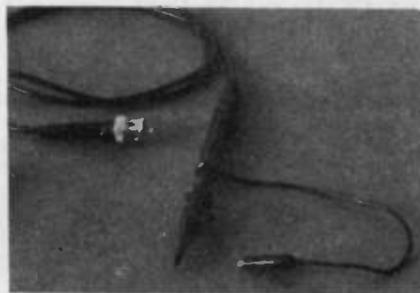A typical 20MHz dual trace oscilloscope. The Crotech 3132.



A $\times 10$ scope probe, this reduces the sensitivity by a factor of ten but boosts the input impedance from 1M to 10M. Input capacitance is reduced, aiding good results at high frequencies.

Fig. 1. The stages required for a basic oscilloscope.

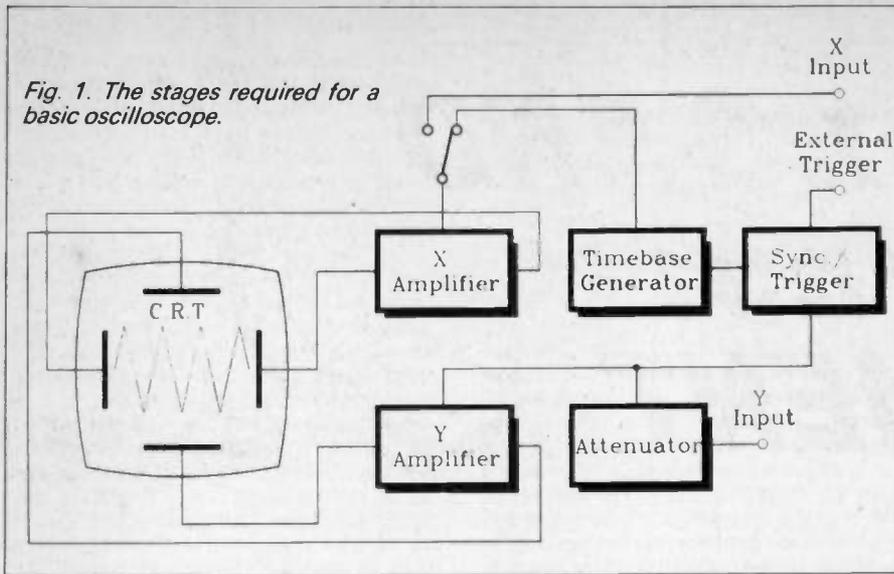

X AND Y AMPLIFIERS

In its most basic form an oscilloscope consists of the stages shown in Fig. 1. An obvious first requirement is for separate amplifiers to drive the X and Y plates. There is little difficulty in producing amplifiers having the required differential outputs, but there is a complication in that quite high voltages are needed.

At least a few hundred volts peak to peak is needed to drive the plates properly, and until relatively recently many oscilloscopes still used valves or a mixture of valves and semiconductors. Probably all new oscilloscopes now have semiconductor circuits. The amplifiers which drive the plates are, appropriately, called the X and Y amplifiers.

An oscilloscope is sometimes used with two external signals – one coupled to each amplifier. This produces shapes on the screen known as “lissajous figures”. However, this is not the normal way of using an oscilloscope, and usually the X signal is provided by an internal circuit.

This is called the “timebase generator” or “sweep generator”. It generates a sawtooth waveform that sweeps the spot across the screen from one side to the other (left to right) at a steady rate, and then rapidly moves it back to the left hand side of the screen again. The electron beam is blanked during the “flyback” period so that it does not leave a slight trace on the screen as it is moved back to the starting point.

INPUT

The input signal is applied to the Y amplifier, and it has the effect of moving the spot up and down as the timebase sweeps the spot across the screen. The spot therefore traces out the waveform of the input signal, with X axis representing time and the Y axis representing amplitude. At low sweep rates the spot will be clearly visible as such, and the waveform may not be clearly displayed.

Some oscilloscopes have a long persistence phosphor or a special form of c.r.t., so that the phosphor glows for some time after the spot has moved on. This elongates the spot into a line which clearly shows the input waveform.

Much testing is at sweep rates of more than about 25 hertz, and even with a short or medium persistence c.r.t. the spot will

appear to be a line. This is due to the inability of the human eye to perceive very fast movement properly.

FREE-RUNNING SINGLE SWEEP

The timebase can operate in the free-running or triggered modes. In the free-running mode the operator sets the sweep frequency, and the timebase runs continuously at this frequency. This is perhaps not strictly accurate, since this mode normally operates in conjunction with a synchronisation circuit. This synchronises the timebase with the input signal so that a stable display is obtained.

Without this synchronisation successive sweeps will start at a different point on the waveform (Fig. 2). This gives a waveform that appears to move across the screen, or if the timebase is well out of synchronisation the screen will probably just be a complete blur of lines.

This form of timebase is perfectly all right for repetitive waveforms, but it has a weakness in that the X axis cannot be accurately calibrated. In order to give a stable display, the synchronisation circuit will probably pull the sweep frequency well away from the one you have set. The exact sweep frequency will probably be unknown.

Another problem is that the synchronisation circuit is unlikely to have a very wide pull-in range. Quite small changes in the input frequency can result in the controls

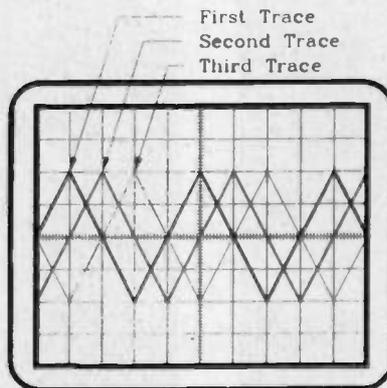


Fig. 2. With a lack of synchronisation each new sweep produces a trace that is offset from its predecessor. This gives a scrambled display.

having to be adjusted in order to give a stable trace again. Where accurate X scaling is not needed, and the input signal is a repetitive waveform of reasonably constant frequency, this form of timebase is perfectly satisfactory.

The more popular form of sweep these days is the “triggered”, or “single sweep” type as it is also known. The single sweep name is not necessarily a particularly apt one, since this type of timebase will be continuously triggered by a repetitive waveform. However, it is different to a true free-running type in one important respect.

A free-running timebase synchronises with the input signal at some multiple of the timebase frequency. A certain number of half cycles are therefore displayed on the screen, and changing the input frequency will leave the same number of half cycles displayed.

With the triggered timebase the sweep commences at the same point in the waveform each time a sweep occurs. The sweep rate controls the number of half cycles that are displayed, and the number displayed may not be an integer. If the set sweep duration happens to equal (say) 5.386 half cycles, then that is the number that will be displayed.

If the input frequency should change, then so will the number of half cycles displayed. The X (time) scaling is unaffected by the input frequency, and this type of timebase enables accurate time measurements to be made.

NON-REPETITIVE WAVEFORMS

Apart from being what is often a better form of free-running timebase, a triggered sweep facility is useful for monitoring intermittent or non-repetitive waveforms. Highly irregular or totally random waveforms are difficult to display with most oscilloscopes.

In order to obtain a stable and continuous trace the electron beam must be moved over exactly the same path time and time again. With irregular waveforms this is not possible, since they will not provide the same input signal over and over again.

The triggered sweep offers a means around this by permitting “single shot” operation. Usually the sweep can be triggered by the input signal, or by a signal connected to the trigger input.

Using the internal triggering, setting the trigger sensitivity quite low will give intermittent triggering, so that you get a series of separate glimpses of the signal, rather than a continuous jumble of lines. There is not usually any provision for manual triggering, but this is not too difficult to rig up via the external trigger socket.

You need to be aware that the single shot sweep mode has its limitations on an ordinary workshop oscilloscope. At low sweep speeds the spot is visible as such, with a relatively faint line trailing a short distance behind it. At higher sweep speeds you see a proper line trace, but only momentarily.

At very short sweep speeds the trace can be quite dim, even with the brightness at maximum. As mentioned previously, there are long persistence c.r.t.s that provide a storage effect so that fast traces can be maintained for some length of time.

These days there are also digital storage oscilloscopes which can store a waveform and output it repeatedly at a high rate. In practice you are unlikely to use an oscilloscope offering any of these facilities, as

they are simply not offered on the cheaper instruments. You therefore have to do the best you can with the available view.

DOUBLE VISION

It can often be useful to display two waveforms simultaneously so that their relative timing can be assessed. Ideally this is done using a dual beam oscilloscope. This is one which has a special c.r.t. with two electron beams. These are both controlled by the same X signal, but the vertical deflection of the beam is controlled via separate Y plates and amplifiers. This gives two separate waveform displays on the screen which can be set one above the other, or superimposed one upon the other.

Double beam oscilloscopes now seem to be something of a rarity, and as far as I can gather, there are no new low cost instruments of this type available. There are plenty of low cost dual trace instruments available though. These have an ordinary single beam c.r.t., but have a so-called "beam splitter" ahead of the Y amplifier. This can operate in either the "alternate" or the "chopped" mode.

In the alternate mode the two traces are produced on alternate sweeps, which gives a good quality display, but leaves the possibility of the relative timing of the two traces not being shown with absolute integrity. The chopped mode is better in this respect, and it operates by rapidly switching the beam from one trace to the other. This leaves little chance of the two waveforms being displayed with any relative X offset, but the display quality is often noticeably inferior to the alternate mode.

The traces are effectively formed by a series of dots, although this is not usually apparent. At certain input frequencies the display can become rather rough though, with bits of the traces missing. Ideally both alternate and chopped modes should be available so that you can choose the most appropriate one for each application.

SPECIFICATIONS

The main specification of an oscilloscope is its bandwidth. This tends to confuse beginners, as it tends to be assumed that the bandwidth figure is the highest input frequency that can be displayed properly. Actually, in order to be sure of obtaining an accurate waveform display the bandwidth must be several times higher than the input frequency. The reason for this is that a complex repetitive waveform consists of the fundamental frequency, plus harmonics (multiples) of that frequency. A squarewave for example, contains odd order harmonics (i.e. three times, five times, seven times the fundamental frequency, etc.).

If the bandwidth of the oscilloscope is only just adequate to accommodate the fundamental frequency, any harmonics will be greatly attenuated. A waveform containing just one frequency is a sinewave, and sinewave-like waveform is what will be displayed if the instrument's bandwidth is inadequate, regardless of the actual input waveform. Most current low cost instruments offer a bandwidth of about 10MHz to 20MHz, and this is adequate for most purposes.

SENSITIVITY

The other main figure in the specification is the sensitivity, which is normally given as so many millivolts per division. The screen of an oscilloscope has a graticule, which is a piece of transparent plastic marked with (usually) 10 millimetre squares, plus marks at 1 or 2 millimetre intervals along the main X and Y axis.


The "division" quoted in many specification sheets is the main 10 millimetre divisions, not the smaller ones. The higher the sensitivity the better, but for most purposes 10 millivolts per division will suffice, and most of the current low cost instruments comfortably exceed this figure.

Another important figure is the size of the screen. A large screen is preferable, but likely to be expensive. One about 100 by 80 millimetres or more should be perfectly adequate. The sweep speed should be variable over wide limits from; about 0.25 seconds per division to around 0.5 microseconds per division.


CHOOSING

As funds will presumably be limited, the choice is likely to be governed more by price than by selecting an instrument which has the features you desire. Funds permitting, I would certainly recommend buying a dual trace instrument (or one of the triple trace types that are now available).

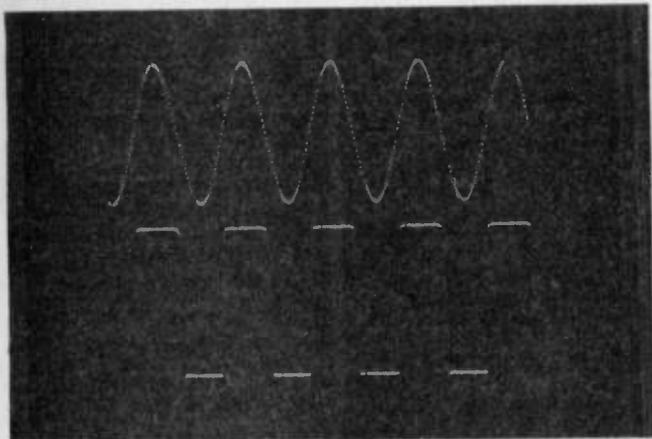
It is unlikely that any modern oscilloscope will provide anything other than good results. You can be reasonably sure that the instrument will live up to expecta-



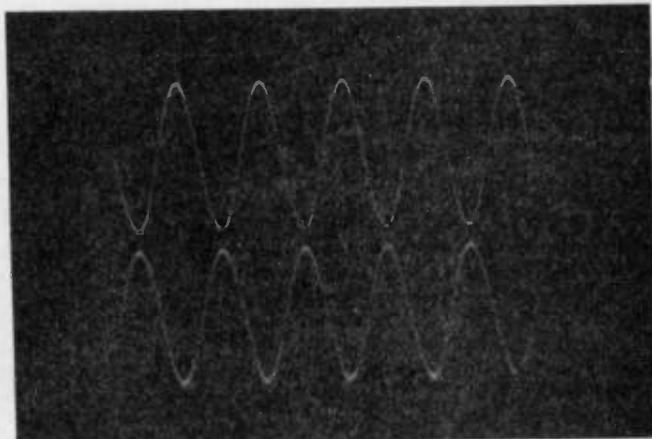
The "chopped" dual trace mode can give some undesirable effects as shown here.



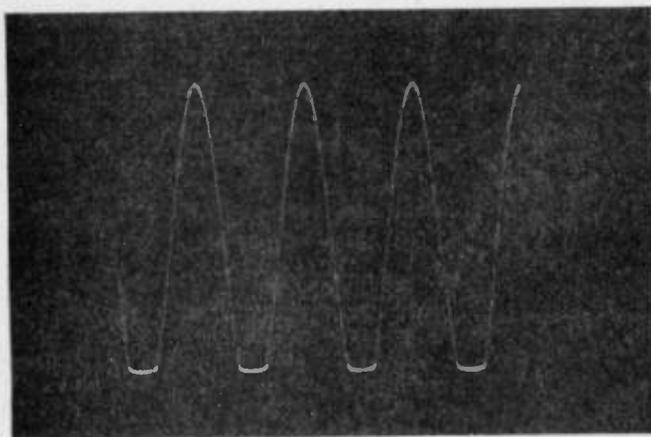Here the input (top) and output waveforms are in anti-phase. The blurring of the bottom trace is caused by noise.



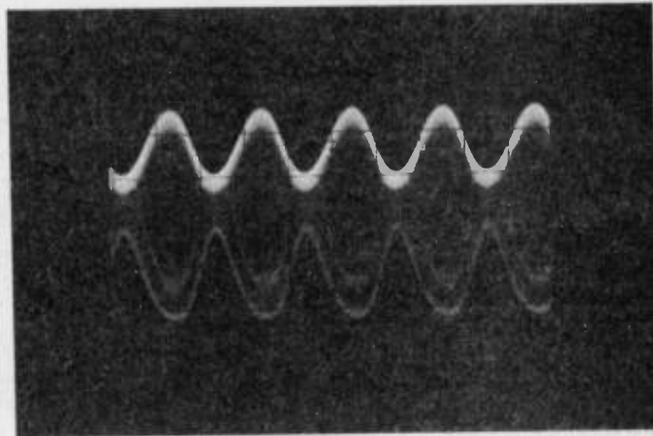Faulty biasing is causing negative half cycles to be clipped.



A high frequency signal modulated by an audio one. In audio equipment this indicates high frequency instability.

tions, and that it will provide many years of service.

The same is not true if you buy an old secondhand oscilloscope. Some quite cheap units with very high specifications can be obtained, but there are potential problems with these oscilloscopes. They are often extremely large and heavy, using valve rather than semiconductor circuits. They are designed to be used on special heavy duty trolleys or benches, and could well cause the collapse of the average kitchen table!

The main problem is that professional servicing might not be available, and would be prohibitively expensive anyway. It could be difficult (and potentially dangerous) to do any d.i.y. repairs. It is not difficult to find people who have experienced problems with old oscilloscopes, but satisfied users would seem to be a bit thin on the ground. A modern secondhand instrument might be a good buy, but an old unit is not something that could be recommended.

CONTROLS

Many of the controls on an oscilloscope are self explanatory. There is a brightness control, plus a focus control which is adjusted to give the sharpest possible trace. Multi-way switches provide a range of preset sensitivities and sweep speeds. There may also be continuously variable sensitivity and sweep rate controls. However, using these means that the graticule calibration is rendered invalid. X and Y position controls enable you to adjust the

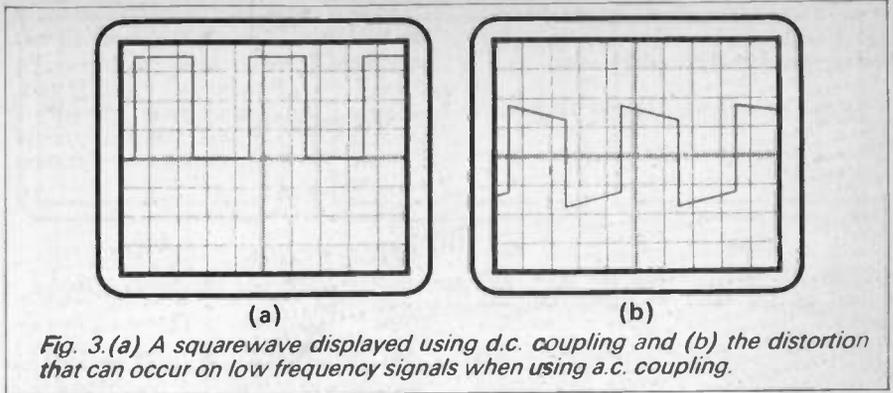


Fig. 3. (a) A squarewave displayed using d.c. coupling and (b) the distortion that can occur on low frequency signals when using a.c. coupling.

position of the trace, and with a dual trace instrument there will be separate Y position and sensitivity controls for each trace.

Virtually all oscilloscopes offer a choice of a.c. or d.c. coupling. D.C. coupling is better in that it enables you to measure the true voltages present in a varying d.c. signal. Most signals in a circuit are varying d.c. types and not true a.c. voltages (i.e. they are always positive and have no negative content). With a.c. coupling the peak to peak voltage can be measured, but no indication of the actual signal voltages will be provided.


D.C. coupling is also better in that it gives a more accurate representation of waveforms that have a significant low frequency content. A low frequency squarewave displayed using d.c. coupling will be shown properly, as in Fig. 3(a). Using the a.c. setting it would look more like Fig. 3(b). This waveform distortion is due to the inevitable low frequency roll-off

introduced by the d.c. blocking capacitor. The a.c. bandwidth of an oscilloscope is extended as far as reasonably possible, but this effect can never be eliminated.


A.C. coupling is best when you wish to view a low amplitude waveform that has a high d.c. content. Taking an extreme example, you might wish to measure the noise level on the output of a power supply. There could be a 30 volt d.c. level with a noise level of only a couple of millivolts peak to peak. Using d.c. coupling and high sensitivity there is little chance of the Y shift control being able to bring the trace onto the screen!

TRIGGER CONTROLS

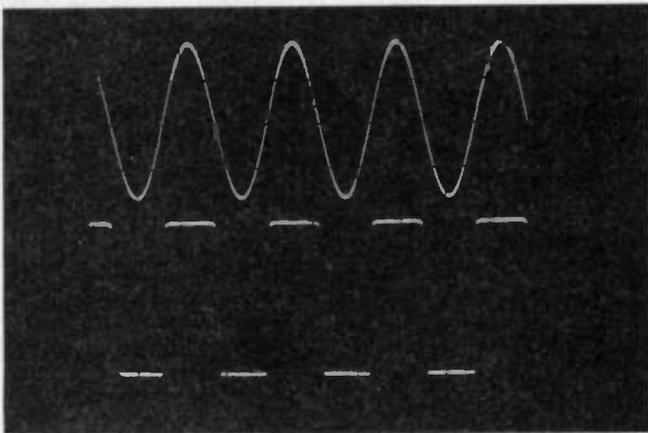
An important but sometimes rather confusing control is the trigger level one. This is occasionally in the form of a sensitivity



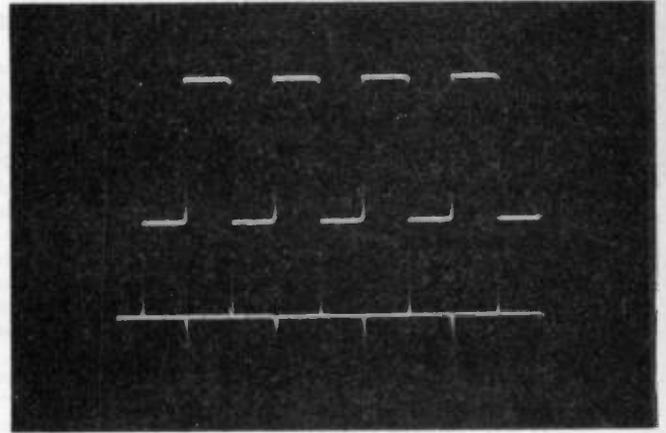
Getting the input level too high results in the sinewave signal (top) being clipped to produce a squarewave signal.



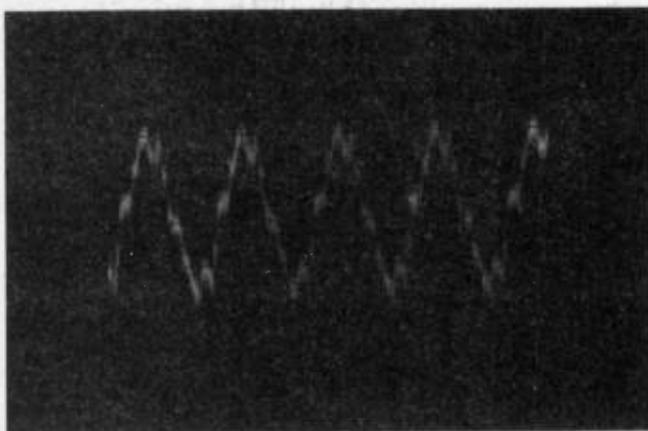Only very high frequencies in the squarewave (top) are being coupled to the test point giving the bottom waveform.



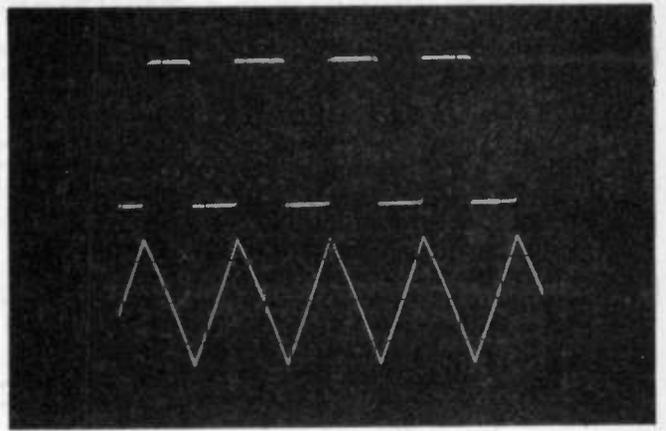Noise output from a power amplifier. This is predominantly 50Hz mains "hum".



The effect of inadequate bandwidth, low pass filtering has reduced the squarewave to a triangular signal.

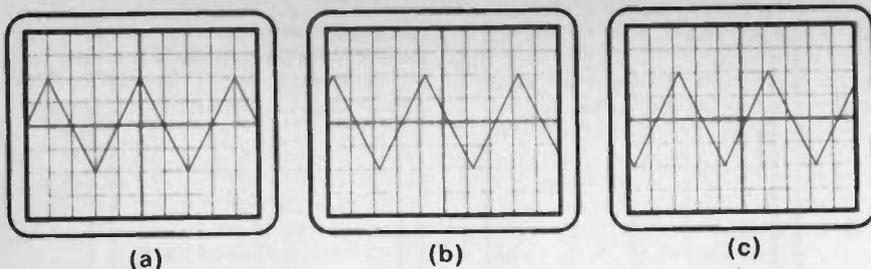


Fig. 4. Displays obtained with; (a) zero trigger level, (b) moderate positive trigger level, and (c) moderate negative trigger level.

control plus a positive/negative switch, but is more commonly a centre zero control which offers positive or negative triggering depending on which way it is adjusted. This controls the voltage at which triggering occurs and a new sweep commences.

In terms of the on-screen display, a setting near zero will give a display along the lines of Fig. 4(a). Setting quite high positive and negative settings gives a display of the types shown in Figs. 4(b) and 4(c). In other words, you are setting the point in the waveform at which the display commences.

Modern oscilloscopes seem to be equipped with large numbers of switches. If we consider some typical functions for these, a normal/auto triggering switch enables the sweep to be set so that in the event of an inadequate input level to the trigger circuit, the timebase triggers itself. In the normal mode with no triggering the result is a blank screen.

The trigger circuit often has highpass and lowpass filters that can be switched in if required. These are used where noise, or the nature of the waveform, results in an unstable trace. Switching in one or both of these will often effect a great improvement if trace instability is giving problems.

With a dual trace instrument there is usually a switch that enables you to select channel 1 or channel 2 as the source for the synchronisation signal. If an external synchronisation socket is fitted, there will be a switch to enable internal/external synchronisation to be selected.

Yet another trigger option is provided by the $+/-$ switch. Normally triggering occurs on the rising edge of the signal (Fig. 5(a)), but with the $-$ mode selected triggering occurs on the falling edge (Fig. 5(b)).

MAGNIFICATION

A sweep magnification switch is usually included, offering a magnification of typically about five times. This does not simply speed up the timebase by a factor of five so that the initial part of the waveform can be viewed in more detail. By using the X

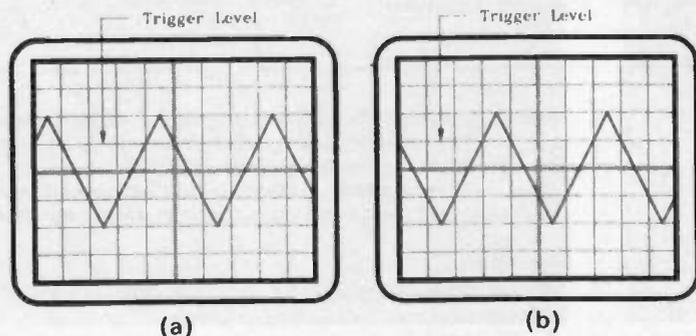


Fig. 5. (a) Type of display obtained using the normal positive edge triggering. (b) Shows the equivalent trace using negative edge triggering.

shift control it is possible to move along the waveform to examine any desired part of it in detail.

The effect is very much as if the trace is made five times wider than the screen width, with the screen providing a moveable window to permit the desired part of the waveform to be examined (as in Fig. 6).

A.C./D.C.

The a.c./d.c. switch will probably also include a "ground" setting. This disconnects the oscilloscope's Y input from the input signal and connects it to earth (ground) instead. This facility is used when the input has been fed with a strong d.c. signal that has effectively resulted in the trace being shifted a few metres off the screen.

If the signal is removed and you wait long enough, the trace will eventually come back onto the screen. Briefly switching to the "ground" setting provides a quicker means of restoring normality. Note that this feature is only needed when using a.c. coupling.

OTHER FEATURES

Other features that might be available include the ability to switch between single and double trace operation, with perhaps the option of selecting alternate or chopped mode in the dual trace mode. An interesting facility provided by some instruments is one which enables the voltage difference between two input signals to be displayed. This is useful for showing slight differences between signals that might be overlooked if the two waveforms are simply displayed one above the other, or with one superimposed on the other.

Some oscilloscopes have a switch that enables one channel to be inverted. This makes two signals easier to compare if they are in anti-phase, effectively making them in-phase.

TESTING

Much of the testing that can be undertaken using an oscilloscope is more

relevant to circuit design and development than to servicing. There are also some clever "tricks" that are quite interesting, but largely of academic importance. Here we will concentrate on using an oscilloscope for fault finding on projects.

For checking linear circuits an oscilloscope can be used as a sort of signal tracer. It is much better than a signal tracer in that it enables the signal levels to be accurately measured, and will clearly show the nature of any waveform distortion.

With an input signal applied to the unit under test, the oscilloscope can be used to measure the signal's amplitude at various points in the circuit. If you start at the input and work forwards, you will eventually find a test point where there is no signal, an inadequate signal level, or distortion of the waveform. The fault should be in the immediate vicinity of this test point.


If there is waveform distortion it may give a clue as to the fault. Normally a sine wave is used for this type of testing, but a square wave can sometimes give more informative results. If only brief spikes are obtained at the test point, this would suggest that only high frequency signals are being coupled through the unit, probably due to stray coupling. A faulty inter-stage coupling capacitor is then the likely culprit.

If the signal level is within the range that the stage should be able to handle, but one set of half cycles are being clipped (or removed altogether), this would seem to indicate a fault in the biasing circuit, or possibly in the amplifying device itself (transistor, op.amp., or whatever). Make sure that the amplitude of the input signal is appropriate. In particular, setting the input level too high will cause severe clipping at some points in the circuit, making some of the test results of relatively little value.

Remember that it can be worthwhile testing for signals where they should not be, rather than testing for a lack of activity in the signal path. This basically means testing to see if there is a significant signal level across the decoupling capacitors. If a significant signal level is found, then the decoupling capacitor in question is almost certainly faulty, or has one leadout not connected properly.

Many projects contain one or more oscillators, and an oscilloscope is ideal for checking that these are producing a

Without Magnification

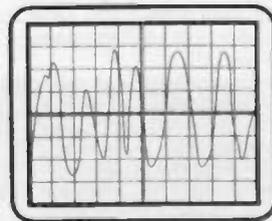

With Magnification

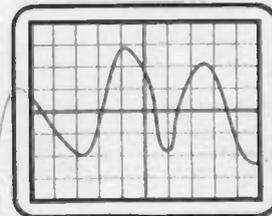


Fig. 6. The "multiply" facility effectively stretches the waveform.

suitable output frequency and waveform. In order to measure frequency it is necessary to use the X scale of the graticule to measure the duration of one cycle. Dividing one by the duration of one cycle gives the frequency of the signal. Measurements made in seconds, milliseconds, and microseconds respectively give answers in hertz, kilohertz, and megahertz.

DIGITAL TESTING

An oscilloscope is well suited to much digital testing. Many circuits have clock oscillators driving one or more frequency dividers, and there is obviously no difficulty in checking that the clock is producing an appropriate output, with suitably reduced frequencies from any divider stages.

With d.c. coupling selected it is quite straightforward to measure the maximum and minimum signal voltages to confirm that they are within the valid range for the logic family concerned. It is also possible to check static levels to see if they are at legal voltages.

Whereas a multimeter might indicate that a test point is at an invalid voltage when it is in fact pulsing and an average voltage reading is being produced, with an oscilloscope you can clearly distinguish between static and pulsing signals.

Some logic signals, particularly those in microprocessor circuits, are non-repetitive even over a fairly long time scale, there is then no chance of clearly viewing the waveform on a continuous basis. Single sweeps can give example glimpses of the waveform, but really you can do little more than check that a pulsing signal at suitable

levels is present. This is often all you will need to know.

While much linear testing only needs a single trace oscilloscope, a dual trace instrument is needed for a lot of digital testing. Often you need to know the state of one or more lines while a certain point in the circuit is pulsed to a certain state.

A typical example would be when testing a parallel printer port, where the strobe line goes low when a fresh byte of data is output. An obvious means of testing the port is to repeatedly output a certain byte, and to use the leading edge of the strobe pulse to trigger the sweep generator. With one channel used to monitor the strobe line, the other input can be connected in turn to each of the data and handshake lines. You can then check that these are set to the correct levels at the right time.

With a single trace scope you can do much the same sort of thing, but obviously the strobe pulse cannot be viewed on the screen at the same time as the other signal. It must be viewed first and its duration


noted, after which the other waveforms are viewed. With this method it is a little harder to interpret results, but with a little effort you should find out what you want to know.

For this system to work it is essential to have an oscilloscope with an external trigger input. Otherwise it is not possible to trigger the sweep from the strobe pulse while viewing a different signal.

VALUE

It is not possible to give a complete course on oscilloscopes in an article of this size, but this should at least give you a good idea of what an oscilloscope does, and how the electronics enthusiast can put one to good use.

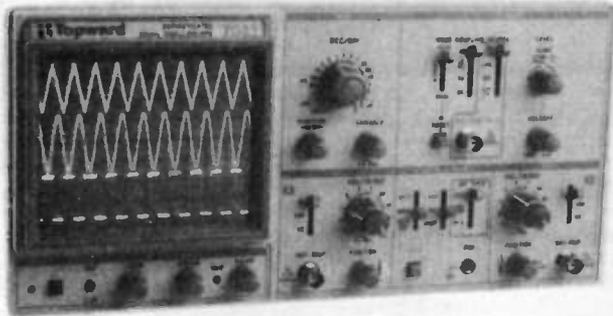An oscilloscope is an expensive piece of equipment, but if you undertake a lot of project building it is likely to be worth every penny. If you start designing your own circuits, an oscilloscope is virtually essential. □



The topward triple trace scope.

MARKET PLACE

WIFE forces clearout. Many ex-equip. odds and ends must go S.a.e. for details. Mr. M. Watte, 60 Greenford Close, Orrel, Wigan, Lancs WN5 8RH.

WANTED Sinclair +3 manual or any info about +3. Contact Adam on 061-766 8193, evenings.

AR LEGEND deck. SME 3009 series 2 arm, £150. Arm alone £70. SCM speakers £20. Jenkins, Southend (0702) 76019.

SCANNER Uniden Bearcat 50XL complete with ni-cads. Good condition. £50 plus £1.50 post insurance. Tel: (0481) 26168.

EIGHTY SWITCHES Maplin FP51F, with i.e.d., bezel, labelled knobs. Cost £2.00 new. Slightly used 50p each. O. L. Futter, 48 Calder Close, Tilehurst, Reading, Berks RG3 4XL.

LOGIDECK 5V power supply, pulse generator, buffered i.e.d.'s, inverters on one p.c.b. P.C.B. circuits, notes, £4.95. Mr A. Martin, 28 Neston Road, Leicester LE2 6RD.

WANTED Hobby Electronics article, April 1980 issue, R/C Speed Controller photocopy of mag. Costs paid. F. P. Jones, 170 Church Lane, Bedford MK41 0DJ. Tel: (0234) 43031.

TELE-PRINTER. Litton Westrex. Antique plus stand, punched tape. Fully working. Serial interface, £30 o.n.o. Buyer collects. N. Johnson, 2 Chapel Field, Dixter Road, Northiam, E. Sussex TN31 6PQ.

FOR SALE P.E. Oct. 81. Electronic ignition system working o.k. £5, p&p £1. L. T. Hill, 29 Stead Lane, Bedlington, Northumberland NE22 5LX.

FREE READERS ADS.

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Pen pals or items related to electronics only. No computer software. EE cannot accept responsibility for the accuracy of ads, or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a cut-out valid "date corner". Ads. will not appear (or be returned) if these rules are broken.

WANTED info circuit diagram service sheets for Akai open reel tape recorder Model X5000W. L. W. Guilford, 113 Vaisey Road, Stratton, Cirencester, Glos GL7 2JW.

FEMALE ELECTRONICS CLUB seeking fellow members of student age (16-25). Please write Jane Martyn (Workshop) Truro V1th Form Centre, Truro, Cornwall TR1 3AN.

WANTED diagram copy for Eddystone 830/8 as mine is rather poorly. Tony. Tel: (0203) 598587 after 6p.m.

Name & Address:			

BLOCK CAPITALS PLEASE

Please read the **RULES** then write your advertisement here— one word to each box. Add your name, address and/or phone no. Please publish the following small ad. **FREE** in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature Date

COUPON VALID FOR POSTING BEFORE 6 JULY '90

(One month later for overseas readers)

SEND TO: EE MARKET PLACE, EVERYDAY ELECTRONICS, 6 CHURCH STREET, WIMBORNE, DORSET BH21 1JH.

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid** "date corner"

EE MARKET PLACE
JULY

We deliver from stock - The fastest way to order is a fax !

ULTRASONIC CAR ALARM




Complete kit including case
44.367BKL £ 30.40

This system is specially designed to protect your car and its contents against potential thieves. Low current consumption and high noise immunity are just two of its distinguishing features.

In addition the system has a voltage sensing device i.e. the alarm is also triggered if appliances are switched on by an unauthorised person (e.g. the interior lighting when the door is opened).

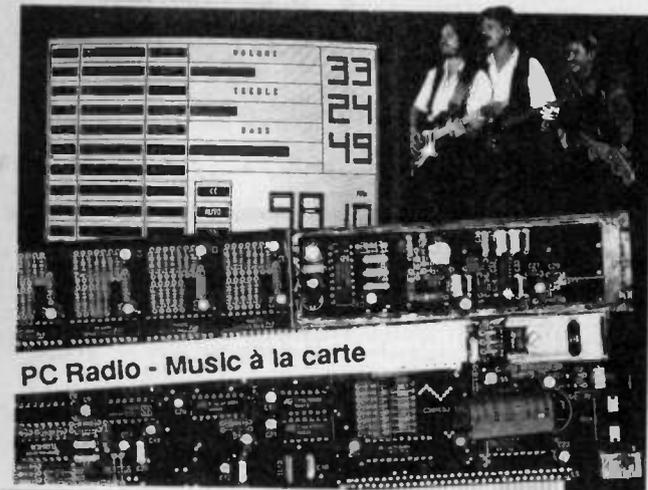PC Radio (Elektor Electronics February 1990)



PC Radio - Music à la carte

DIGITAL PROFESSIONAL ECHO 1000


(Elektor Electronics June 89)

This low cost echo unit is certain to impress music lovers - amateur and professional - everywhere. Excellent specification and top performance make the EU 1000 a winner and despite meeting professional requirements the unit will not make too big a hole in your pocket. Working on the delta modulation prin-

ciple on a digital base, delay times up to one second are possible at full bandwidth and large signal to noise ratio.

Complete kit
44.255BKL £ 99.50

Ready assembled module
44.255F £ 134.50

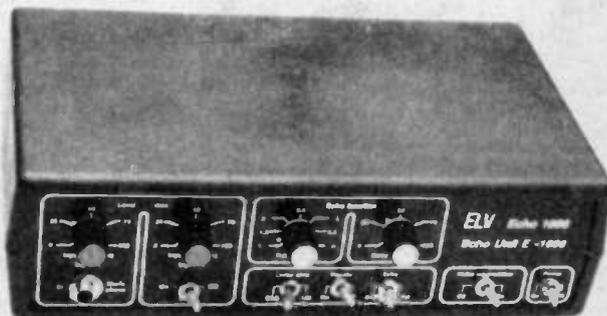

Specification

Input sensitivity:
Input 1 : 2 mV
Input 2 : 200 mV

Delay Time:
variable from 60 ms to 1 s

Bandwidth :
100 Hz to 12 kHz

Additional features:

- inputs mixable
- single and multiple echo
- adjustable delay level
- switchable vibrator
- switch-controlled noise suppression

This FM radio consists of an insertion card for IBM PC-XTs, ATs and compatibles and is available as a kit or a ready-built and aligned unit. The radio has an on-board AF power amplifier for driving a loudspeaker or a headphone set, and is powered by the computer. A menu-driven program is supplied to control the radio settings.

Complete kit
44.544BKL £ 82.75

Ready assembled module
44.544F £ 137.30

VM 1000 Video-Modulator (Elektor Electronics March 90)



Many inexpensive or older TV sets lack a SCART or other composite video input, and can only be connected to a video recorder or other equipment via an RF modulator. The modulator operates at a UHF TV channel between 30 and 40. Use is made of a single-chip RF modulator that couples low cost to excellent sound and picture quality.

Complete kit
44.546BKL £ 36.90

Ordering and payment:

- all prices excluding V.A.T. (french customers add 18.6%T.V.A.)
- send Euro-cheque, Bank Draft or Visa card number with order. Please add £ 3.00 for p & p (up to 2 kg total weight)
- postage charged at cost at higher weight Air/Surface -
- we deliver worldwide except USA and Canada
- dealer inquiries welcome

RFK 700 RGB-CVBS Converter

(Elektor Electronics October 89)

Nearly all computers supply as an output signal for colour monitors RGB signals. With the help of the RFK 7000 it is possible to record this signals with a videorecorder or to give them onto a colour TV (This is only possible, if the

computer delivers a vertical sync. of 50 Hz and a horizontal sync. of 15.625 Hz).

The voltage supply is gained from a 12V/300mA-DC voltage mains adaptor.

Complete kit
44.525BKL £ 66.50

Ready assembled module
44.525F £ 119.50

FRK 7000 CVBS-RGB Converter

With the help of the FRK 7000 e.g. it is possible to use a cheap colour monitor with RGB input on a video recorder. The voltage supply is gained from a 12V/300mA-DC voltage mains adaptor.

Complete kit
44.509BKL £ 66.50


Ready assembled module
44.509F £ 119.50



We deliver from stock - The fastest way to order is a fax !

LPS 8000 / LC 7000 Low Cost Show Laser

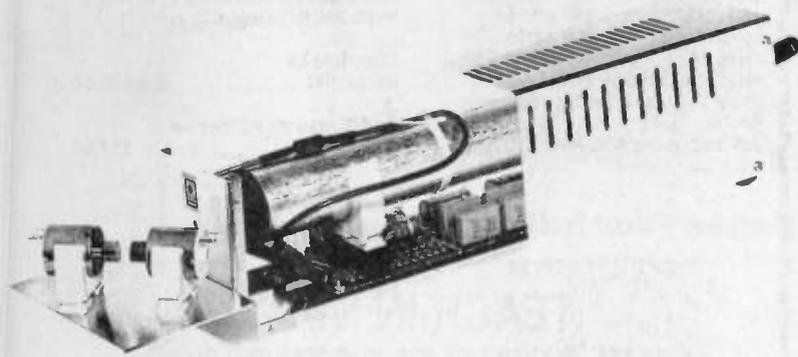(Electronics The Maplin Magazine Dec 88 + Feb-Mar 90)



An almost infinite number of circular patterns can be projected onto a wall or ceiling with this super laser show equipment.

The complete project includes a laser tube and accompanying power supply, housed in a metal case, and a laser controller, LC 7000. The laser controller drives the accompanying deflection unit, fixed onto the laser power supply case, which produces the numerous configurations.

Naturally the laser tube, together with the power supply, can produce beams without the laser controller and the controller can be used with other, similar lasers.

LPS 8000 Laser Power Supply, complete kit		
Version 240 Volts AC		
44.4288KL220	£	86.90
Version 220 Volts AC		
44.4288KL240	£	86.90
LC 7000 Laser Controller, complete kit		
Version 12 Volts DC		
44.427BKL	£	60.80
H-N Laser Tube 2 mW		
44.428LR	£	60.80


LPS 8000 Laser Power Supply, ready assembled module		
Version 240 Volts AC		
44.428F240	£	156.50
Version 220 Volts AC		
44.428F220	£	156.50
LC 7000 Laser Controller, ready assembled module		
Version 12 Volts DC		
44.427F	£	104.30
Laser Motor-Mirror Set, complete kit		
44.506M	£	22.95

VIDEO RECORDING AMPLIFIER

(Elektor Electronics April 89)

Losses can easily occur when copying video tapes resulting in a distinct reduction in quality. By using this video recording amplifier, with no less than four (!) outputs, the modulation range is enlarged and the contrast range of the copy increases.

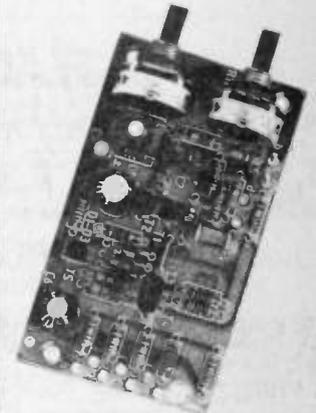Two level controllers for edge definition (contour) and amplification (contrast range) allow individual and precise adaptation.




Complete Kit
(including Box, PCB and all parts)
44.3248KL

£ 14.75

IBM PC Service Card

(Elektor Electronics May 1990)

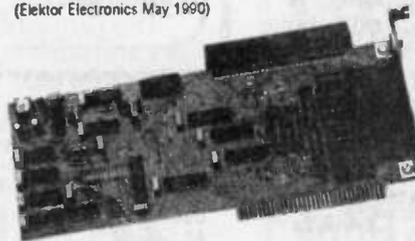This card was developed for assistance in the field of service, development and test. The card is used as a bus-extension to reach the measurement points very easy. It is also possible to change cards without having a "hanging computer".




Complete kit	
44.517BKL	£ 77.95
Ready assembled module	
44.517F	£ 137.95

TA 1000 Telephone Answering Unit

(Elektor Electronics January 1990)

This automatical telephone answering unit uses a 256-kbit voice recording circuit to store and replay your spoken message of up to 15 seconds. Noteworthy features are that it is available as a complete kit, provided a battery back-up facility and does not require alignment. No provision is made, however, to record incoming calls.


Complete kit	
44.433BKL	£ 45.65
Ready assembled module	
44.433F	£ 87.25

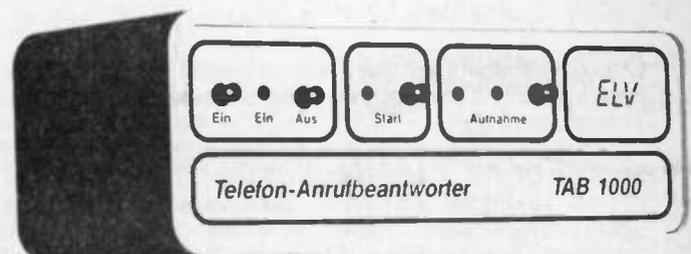

IC TESTER for IBM-PC-XT/AT

(Electronics The Maplin Magazine Jun-Jul 89 +
Elektor Electronics December 89)

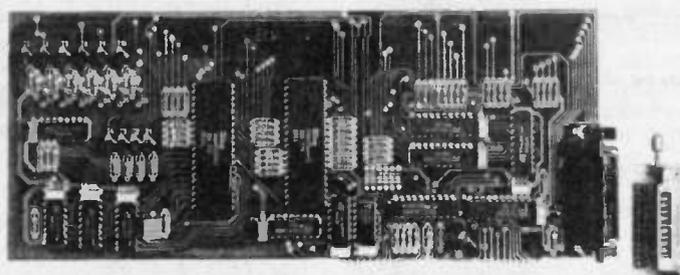With the ELV IC tester logic function tests can be carried out on nearly all CMOS and TTL standard components, accommodated in DIL packages up to 20 pin. The tester is designed as an insertion card for IBM-PC-XT/AT and compatibles. A small ZIF test socket PCB is connected via a flat band cable. Over 500 standard components can be tested using the accompanying comprehensive test software.



Complete Kit including Textool socket, connectors, sockets, Flat band cable, PCB, Software	
44.474BKL	£ 60.85
Ready Assembled Module	
4.474F	£ 113.00
Software, single	
44.474SW	£ 17.85

TEACH-IN, DATA & PROJECTS

FOUR SPECIAL PUBLICATIONS

FROM EVERYDAY ELECTRONICS



SEE DIRECT BOOK SERVICE pages—for full ordering details

TEACH-IN 88/89

INTRODUCING MICROPROCESSORS

£2.45 plus P & P

A complete City and Guilds Certificate Course for 726/303 Introductory Microprocessors

Written by Mike Tooley BA this course can lead successful readers to a City and Guilds Certificate. Everything you need to know is included—even pre-test papers, etc.

From Terminology, Integrated Circuits and Logic Families in Part One, the course progresses in easy stages up to High- and Low-level Languages, Flow Charts and Assembly Language. Also featured is a range of eight Data Pages giving information on popular microprocessor chips. A comprehensive index is included, making this a valuable reference manual.

ORDER CODE: TI 88/89

TEACH-IN No. 3

EXPLORING ELECTRONICS

£2.45 plus P & P

By Owen Bishop

Designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. The book does not contain masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

The text is split into 28 easily digestible sections, each with a separate project. The breadboard experiments assume no previous knowledge, start at semiconductor diodes and progress through bistables, timers, amplifiers, binary etc up to f.e.t.s and shift registers.

The projects include radio receivers, various timers and alarms, plus temperature sensors and water detectors etc.

An excellent source book for GCSE courses.

ORDER CODE TI3

ELECTRONIC PROJECTS Book 1

£2.45 plus P & P

Contains twenty of our best projects from previous issues of EE, each backed with a kit of components. The projects are:

Seashell Sea Synthesiser, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16K Sideways Ram, Simple Short Wave Radio, Insulation Tester, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser Ioniser, Bat Detector, Acoustic Probe, Mains Tester and Fuse Finder, Light Rider – (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.

ORDER CODE EP1

EVERYDAY ELECTRONICS DATA BOOK

£8.95 plus P&P

By Mike Tooley BA

Published by EE in association with PC Publishing, this book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but it also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous worked examples showing how theory can be put into practice using a range of commonly available components and devices.

A must for everyone involved in electronics!

Available from your local component supplier or direct from us.

ORDER CODE DATA

SEE DIRECT BOOK SERVICE pages—for full ordering details

MARC

MAINS APPLIANCE REMOTE CONTROL SYSTEM

CHRIS WALKER



Part Two: Mains Encoder

*Allows up to 15 different household mains appliances, placed anywhere in the house, to be controlled from the safety of your armchair.
Can be linked to the home computer.*

LAST MONTH we dealt with the handheld Infra-Red Transmitter for the MARC mains appliance remote control system. This month we move on to the Encoder circuit and construction.

The Encoder Unit is the most complicated part of the MARC system. Its job is to receive instructions from the IR Remote Controller or optional external microcomputer and encode these onto the 240 volt mains so that they can be picked up by the various decoder units placed through the house. The block diagram illustrated in Fig. 1.5, last month, outlined the operation of the Encoder Unit.

ENCODER CIRCUIT

The MARC Encoder was designed in a systems-based manner, making extensive use of integrated circuit technology.

Therefore, its circuit diagram bears some resemblance to the systematic (block) diagram of Fig. 1.5 (last month) but some points require extra clarification.

The complete Encoder circuit is built on two printed boards, the circuit diagram for Board A is shown in Fig. 2.1 and that for Board B in Fig. 2.2. Refer to Fig. 2.1 first.

The infra-red receiving diode D1 is reverse biased by resistor R1. Signals from the junction of these two components are coupled to the two-stage high gain amplifier containing transistors TR1 and TR2. Capacitors C1 and C2 also provide simple high-pass filtering to block 50Hz received signals.

Transistor TR3 is wired in the "switch" configuration and low-going signals from the collector of TR2 will produce positive 15V pulses at the collector of TR3 which are coupled, via capacitor C4, to the PPM input (pin 3) of the two demodulators IC1 and IC2.

Capacitor C5 together with resistor R8 and variable preset potentiometer VR1 set the frequency of the oscillator within IC1. C6, R9 and VR2 behave similarly for IC2. In order to receive the PPM code correctly from the SL490 transmitter i.e. this oscillator frequency should be adjusted to be forty times the transmitter clock frequency.

The four least significant bits of the received binary code are outputted on pins 5 to 8 of IC1 if the code is between 00000 and 01111 or pins 5 to 8 of IC2 if between 10000 and 11111. Each decoder i.e. waits to receive two consecutive and identical codes before responding. By using this method, receiving errors are greatly reduced. R10 to R17 act as pull-down resistors for the open drain outputs, in the absence of transmitted data these outputs will, therefore, remain low.

The two multiplex chips IC3 and IC4 will take data from the "A" inputs (pins 2, 5, 11 and 14) if the select control (pin 1) is low or from the "B" inputs (pins 3, 6, 10 and 13) when a high logic level is present on pin 1. Data for the "B" inputs and the select pin comes from the computer port on Board B. The multiplexer output is available on pins 4, 7, 9 and 12 of IC3 and IC4.

LATCH

When "receiver number" data appears on the output pins of IC3, the output of OR-gate IC8a goes high and triggers monostable IC7b which produces a negative-going 10ms pulse at pin 9. The rising edge at the end of this pulse is used to load the received data into latch IC5. A similar arrangement is provided for the "function code" data bits from multiplexer IC4.


The latch loading pulses, "X" and "Y", are also used to reset a ten second timer formed by IC9a. The output of this timer, "Z", will go high ten seconds after the last pulse is received at its input and this causes both latches IC5 and IC6 to reset.

The latches will hold data for a maximum of ten seconds or until new data is loaded by the OR-gate/monostable arrangement. Connections J to Q are decoded on Board B to provide the front panel display explained earlier.

The M145026 serial encoder, IC10 belongs to a group of three i.c.'s which form a very powerful remote control/data transfer facility. The M145027 receiver is utilised in the decoder units.

A low level on the "Transmit Enable" input (pin 14, IC10) initiates a sequence whereby the nine input data bits (pins 1 to

The complete MARC control system showing, from left to right, temperature mains interface, decoder, encoder, infra-red transmitter and temperature display.

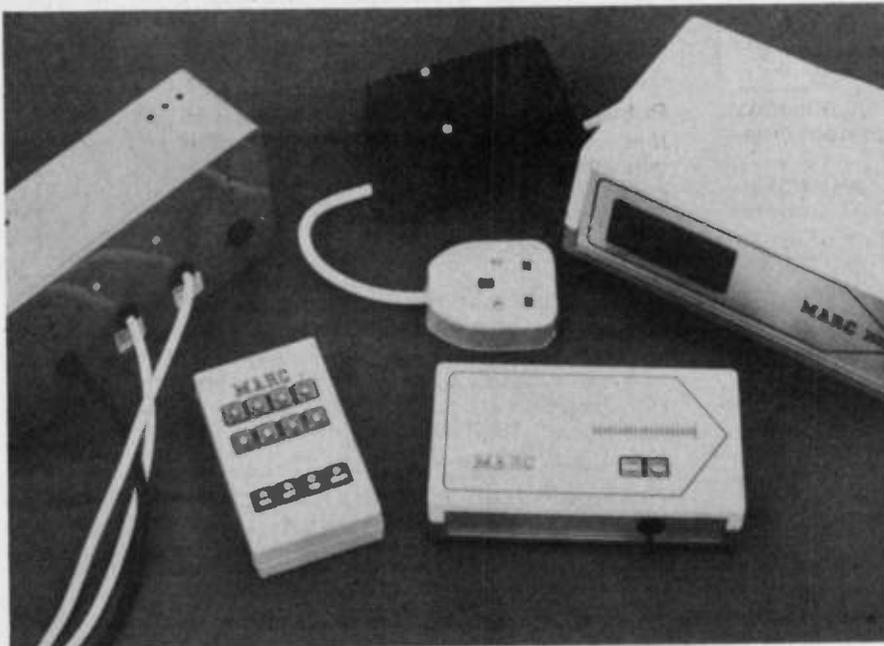

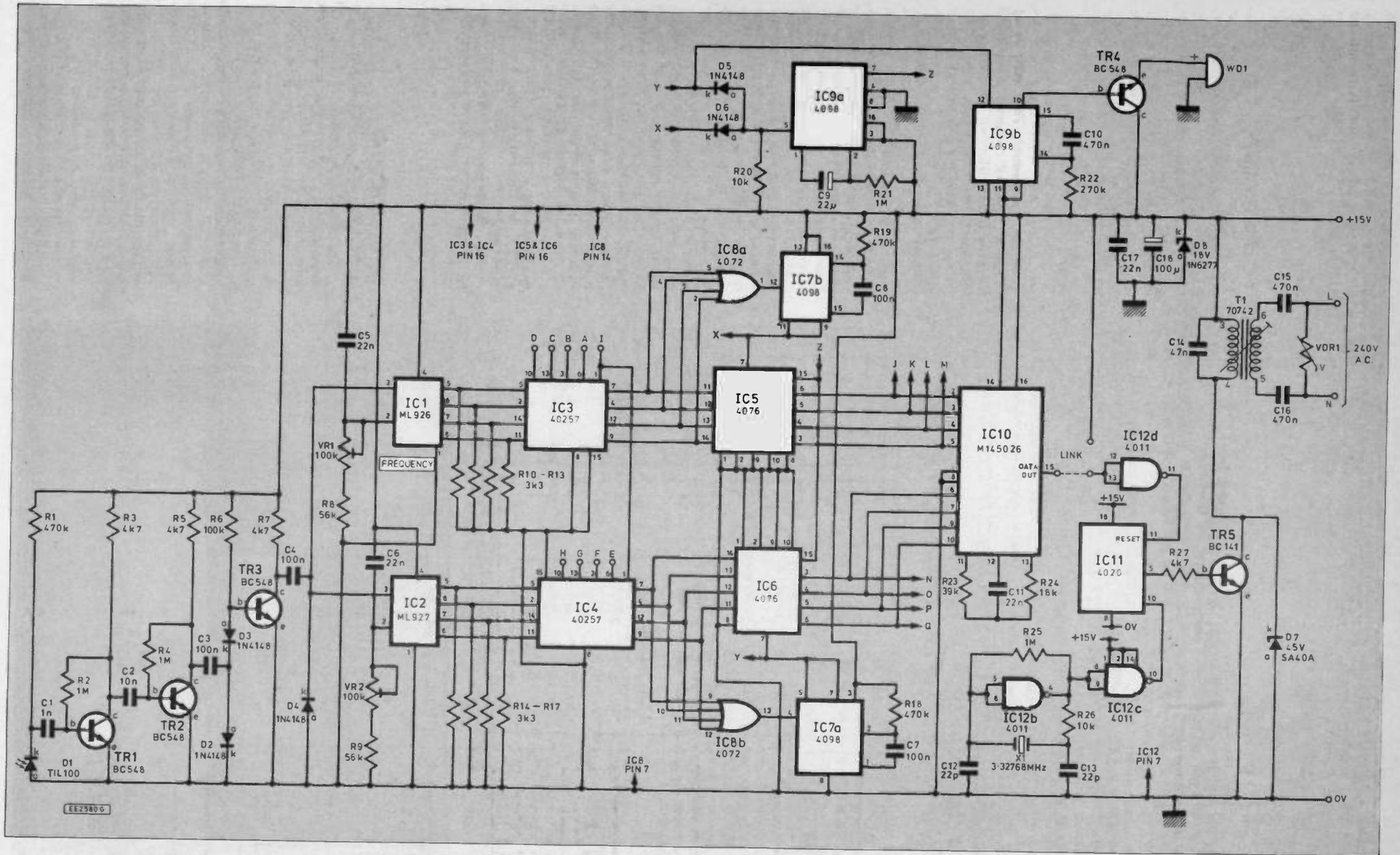


Fig. 2.1. Circuit diagram for the MARC Encoder Board A. Letters A to Q label connections to Board B.

7, 9 and 10) are transmitted from pin 15 by pulse width modulation (PWM); two short pulses for a "0" and two long ones for a "1". Two complete words are sent for the purposes of error reduction and the Decoder Modules i.c.'s will only respond when two consecutive and identical words are received.

Notice that pin 1 of IC10 is tied to 0V because nine data bits are not required in this application. Ambitious constructors wishing to utilise this pin can increase the number of addressable receiver units from 15 to 31.

Resistors R23 and R24 and capacitor C11 set the transmitter clock frequency. The manufacturers of these encoder/decoder chips state that no provision for clock frequency adjustment is necessary so long as 5 per cent tolerance timing components are used.

The 100ms long "Transmit Enable" pulse is generated by monostable IC9b

which, in turn, is triggered by the "Y" function code present pulse from IC7a. Therefore, it should be apparent that, in order to send a complete appliance command, one should first press a "receiver number" button on the handheld IR Transmitter Controller.

This causes data to be loaded into IC5. Then, within ten seconds, a function command is selected which loads data into IC6 and also initiates the encoded transmit sequence

The pin 10 output from monostable IC9b drives buzzer WDI via emitter-follower TR4. The short audible tone produced confirms transmission.

The NAND gate IC12b is wired as an inverter and together with quartz crystal X1 and its associated components forms a stable oscillator running at 3.32768MHz. This frequency is divided by 32 and reduced to 104kHz by ripple counter IC11.

The output from IC11 is available at pin

5 and a crude (but effective) form of keyed carrier modulation is achieved by feeding the inverted serial data from IC10 into the RESET pin of divider IC11. A temporary link between +15V and IC12d is used to generate a permanent carrier for setting-up purposes.

TUNED CIRCUIT

Transistor TR5 drives current into the tuned circuit formed by capacitor C14 and one half of matching transformer T1. This tuned circuit resonates at the carrier frequency and couples energy into the secondary winding of T1 and through capacitors C15 and C16 onto the mains wiring. These two capacitors all but block the low frequency 50Hz current from flowing through T1 secondary whilst presenting a low impedance to the 100kHz carrier.

Do not use any old capacitor for this job since they are connected directly between live and neutral. They must be of "Class X" standard, cheaper ones could fail disastrously. Transformer T1 acts as an impedance matching device between the driver transistor and the low impedance mains line.

Unfortunately, as well as transferring data onto the mains, these interface components will also allow spikes, glitches and other high-voltage "nasties", frequently present on the house wiring, to pass into the electronics of the Encoder Unit. Such spikes could easily damage the delicate electronic components if they are not removed.

Varactor VDR1 normally presents a high impedance to the 240V r.m.s. mains but should a spike appear which has an amplitude significantly greater than the peak value of the mains voltage its impedance drops and the spike energy is dissipated as heat. Should really vicious spikes break through this first line of defence they are (hopefully) removed by the transient suppressors D7 and D8.

These devices act in a similar manner to a Zener diode although with a much faster switching time (within one picosecond, 10⁻¹²s). D8 clamps the positive supply and prevents it rising above about 18V, D7 works in a similar manner for the collector of TR5, the clamping voltage here being about 45V.

Don't be tempted to omit these protection components or you will have had your "chips"!

ENCODER CIRCUIT-BOARD B

The circuit diagram of Fig. 2.2 should present no problems to most readers. The voltage regulator (IC13) and its associated smoothing and stabilising capacitors C19 to C21 produce the +15V rail from mains transformer T2. Notice that the 0V rail is connected to mains Earth.

The b.c.d. to 7-segment display decoder chip IC14 displays the current "receiver number" present on lines J to M from Board A on a common cathode seven-segment display X2. Resistors R28 to R34 are current limiters. The four front panel l.e.d.'s D11 to D14 indicate the selected function code ON, OFF, UP or DOWN and they are driven by transistors TR6 to TR9 wired as emitter followers.

Two quad opto-isolators IC16 and IC17 provide complete electrical isolation from the computer input connections DO to D7.

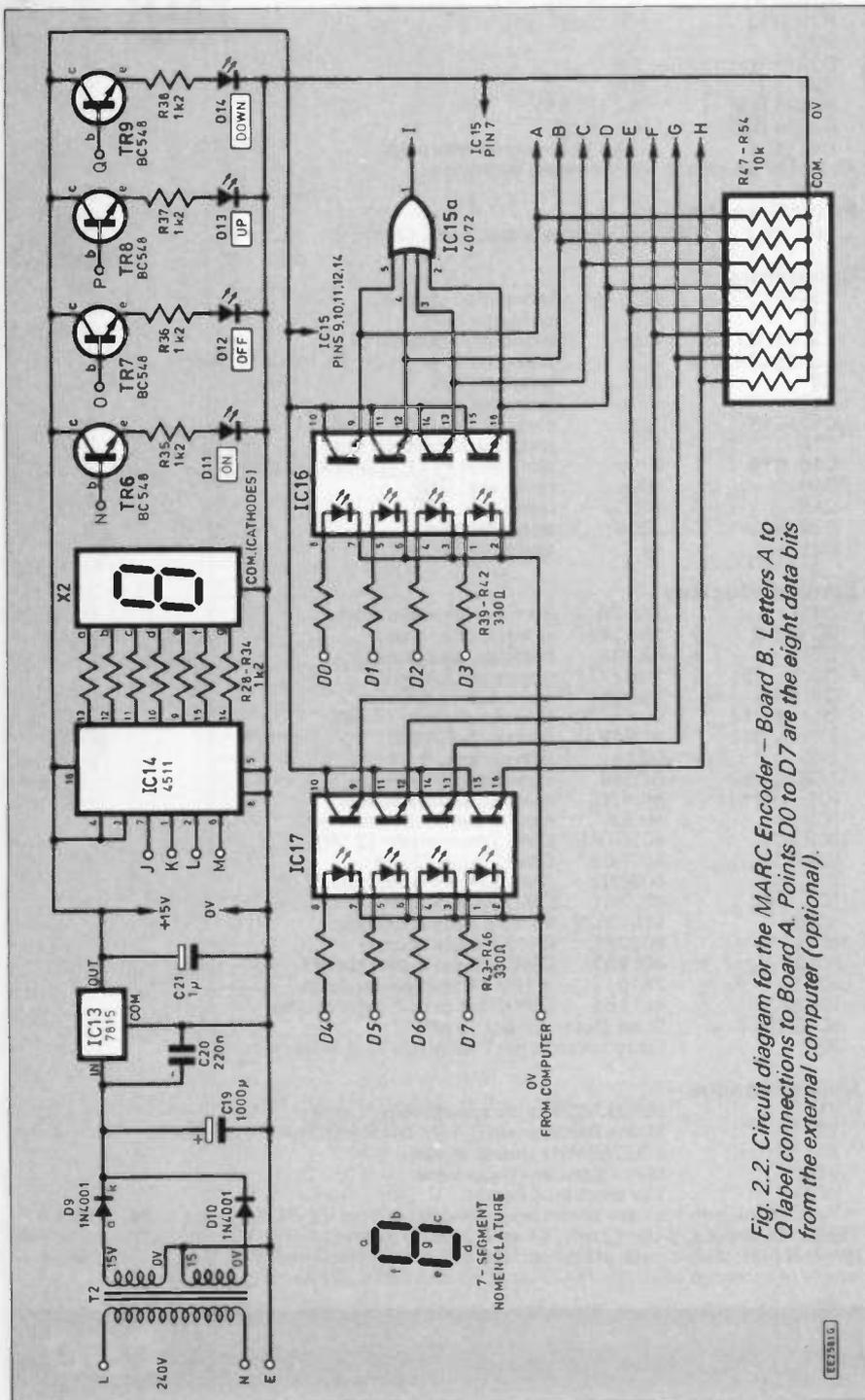


Fig. 2.2. Circuit diagram for the MARC Encoder - Board B. Letters A to Q label connections to Board A. Points D0 to D7 are the eight data bits from the external computer (optional).

The eight bits A to H go to the multiplexer i.c.'s on Board A, the s.i.l. resistor pack (R47-R54) provides the eight pull-down resistors. OR-gate IC15a detects the presence of data on the four least significant computer bits and a high level from the output of this gate causes the multiplexer to switch its source from the IR receiver to the computer port.

CONSTRUCTION - ENCODER

This project is not intended for the absolute beginner, so any constructor attempting to build the MARC system should not encounter any particular problems when assembling the encoder boards.

It is probably best to fully assemble both boards but do not make any interconnections between them at this stage. Figs. 2.3 and 2.4 detail the component layout and copper foil patterns for printed circuit boards A and B. These are available through the *EE PCB Service*, codes EE694 and EE695.

The use of i.c. sockets is strongly recommended. Do not insert the i.c.'s themselves until ready to test the boards, all the devices are CMOS and should be handled accordingly.

Board A requires some discussion. There are 19 wire links to insert, do these first before you forget. The use of terminal pins for all flying lead connections will eliminate the need to access the underside of the board later on. Transistor TR5 should be fitted with a clip-on heatsink (TO5 can); under normal conditions it won't need it but when generating the permanent carrier for alignment it tends to get a bit warm.

It is vital that the matching transformer T1 is orientated properly. Use a multimeter to check for continuity according to the pinout sketch in Fig. 2.3.

When soldered in place there should be **NO** continuity between the pins connected to capacitor C14 and those connected to capacitors C15 and C16. On all these transformers that I have purchased the identification number has been printed on the side shown, but I would still check to be sure.

At this stage you can decide whether you wish to include both the IR Receiver and the Computer Port as a data source. If only one is built then the components relating to the other can be omitted. Also, the multiplex chips can be left out but you will need to insert permanent wire links in their place to carry data between the appropriate pins.

Board B should present no problems either. Resistors R47 to R54 are contained in a 9-pin s.i.l. package consisting of eight "commoned" 10k resistors, the common end should be marked with a dot or something similar; again, the use of a multimeter will dispel any doubts.

The voltage regulator IC13 gets warm in use and should be fitted with a small heatsink, a scrap of aluminium will suffice. The use of terminal pins is recommended on this p.c.b. too.

SAFETY FIRST

The unit is connected to the mains via a thin 3-core cable. If the conductors in this cable are soldered to terminal pins in the printed circuit board it is very important to insulate these with sleeving to prevent accidental contact. Don't forget the Earth connection to the 0V rail.

Two wires from the printed circuit board

supply 240V to transformer T2 primary and the solder tags on this component must also be insulated. Stick some insulating tape over the live part of the board's copper tracks around the vicinity of the transient suppressor VDR1 and transformer T1.

This project involves direct connection to the mains and, in spite of the blocking capacitors, the area around transformer T1 must be considered LIVE when the unit is

connected to the mains. Also, although it provides impedance matching, T1 is NOT intended to provide guaranteed electrical isolation in the event of a failure. Therefore, take great care on the whole encoder circuit boards when carrying out live tests.

The mains transformer T2 has two secondary windings, 0-15V and 0-15V. These are wired in series to give a single 15V-0-15V winding with 0V at the centre join.

COMPONENTS

Encoder Unit

Resistors

R1, R18, R19	470k (3 off)
R2, R4, R21, R25	1M (4 off)
R3, R5, R7, R27	4k7 (4 off)
R6	100k
R8, R9	56k (2 off)
R10 to R17	3k3 (8 off)
R20, R26	10k (2 off)
R22	270k
R23	39k
R24	18k
R28 to R38	1k2 (11 off)
R39 to R46	330 (8 off)
R47-R54	10k s.i.l. 8-way resistor pack.

All 0.25W 5% carbon, unless stated otherwise.

Potentiometer

VR1, VR2	100k min. skelton preset, horiz. (2 off)
----------	--

Capacitors

C1	1n	monolithic ceramic
C2	10n	polyester layer
C3, C4, C7, C8	100n	monolithic ceramic (4 off)
C5, C6, C11, C17	22n	polyester layer (+/- 5% for C11) (4 off)
C9	22µ	tantalum 25V
C10	470n	polyester layer
C12, C13	22p	ceramic (2 off)
C14	47n	metallised polyester film
C15, C16	470n	metallised PETP (Class X) (2 off)
C18	100µ	radial elec. 25V
C19	1000µ	radial elec. 35V
C20	220n	polyester layer
C21	1µ	tantalum 35V

Semiconductors

D1	TIL100	infra-red sensitive diode
D2 to D6	1N4148	signal diode (5 off)
D7	SA40A	transient suppressor
D8	1N6277	transient suppressor
D9, D10	1N4001	rec. diode (2 off)
D11 to D14	l.e.d's	(various shapes) (4 off)
TR1 to TR4	BC548	npn silicon (4 off)
TR5	BC141	npn silicon
TR6 to TR9	BC548	npn silicon (4 off)
IC1	ML926	remote control decoder
IC2	ML927	remote control decoder
IC3, IC4	40257BE	CMOS multiplexer (2 off)
IC5, IC6	4076BE	CMOS latch (2 off)
IC7, IC9	4098BE	CMOS dual monostable (2 off)
IC8, IC15	4072BE	CMOS dual 4-input OR (2 off)
IC10	M145026	Remote control encoder
IC11	4020BE	CMOS ripple counter
IC12	4011BE	CMOS Quad 2-input NAND
IC13	7815	+15V 1A voltage regulator
IC14	4511BE	CMOS b.c.d. to 7-seg decoder
IC16, IC17	Quad Opto-isolator (2 off)	
X2	Common cathode 7-segment l.e.d. display	

Miscellaneous

T1	707VXA0242YUK transformer (Cirkit)
T2	Mains Transformer, 0-15V 0-15V 330mA secondaries
X1	3.32768MHz Quartz crystal
VDR1	Mains transient suppressor
WD1	12V electronic buzzer

Two single-sided printed circuit boards available from *EE PCB Service*, codes EE694, EE695; dil sockets, 8-pin (2 off), 14-pin (3 off), 16-pin (11 off); TO5 clip-on heatsink; terminal pins; plastic case; plain matrix board; display bezel; red filter; 3-core cable; short length of screened cable; multi-coloured ribbon cable; connecting wire; solder etc.

Approx cost.
Guidance only

£50

See
SHOP
TALK
Page 468

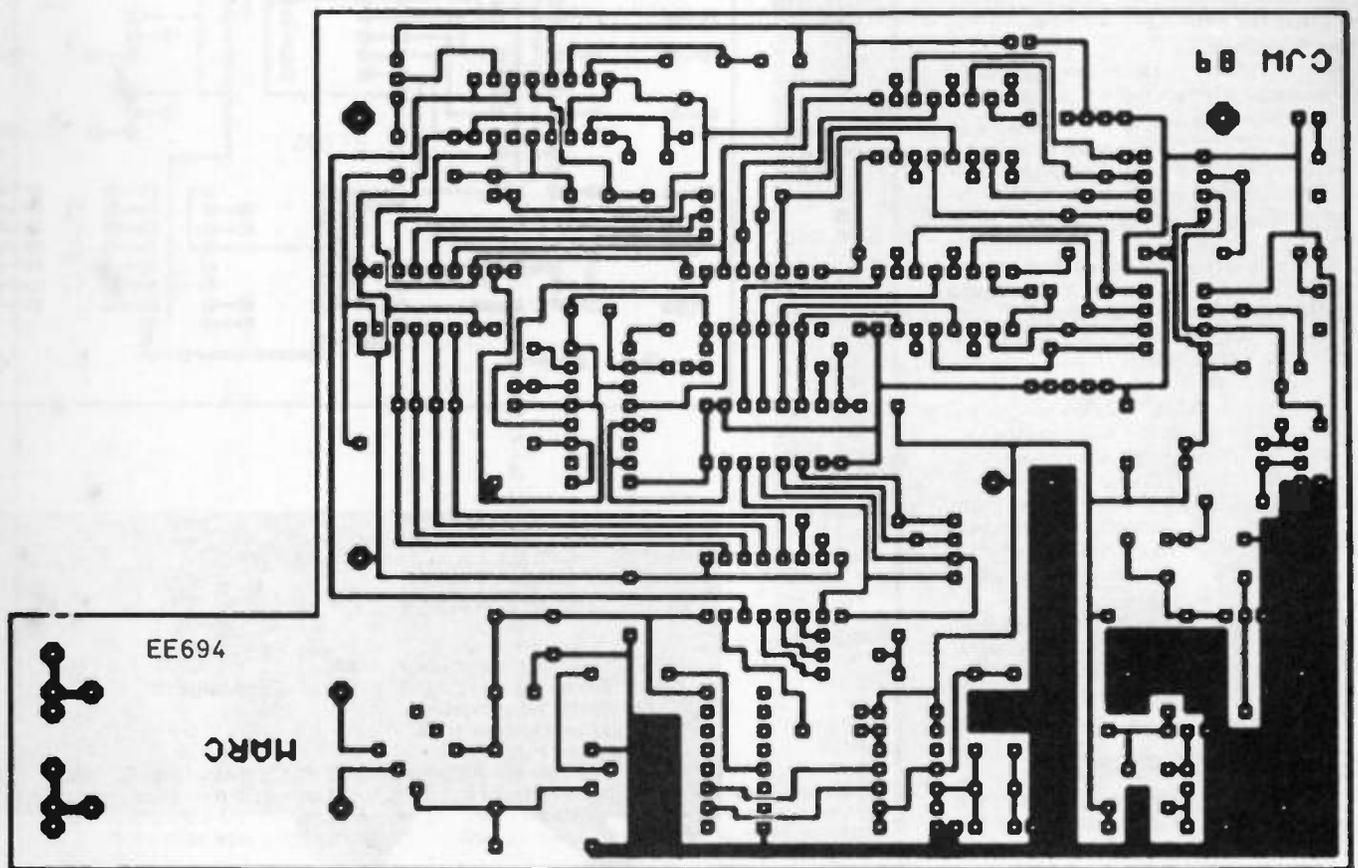
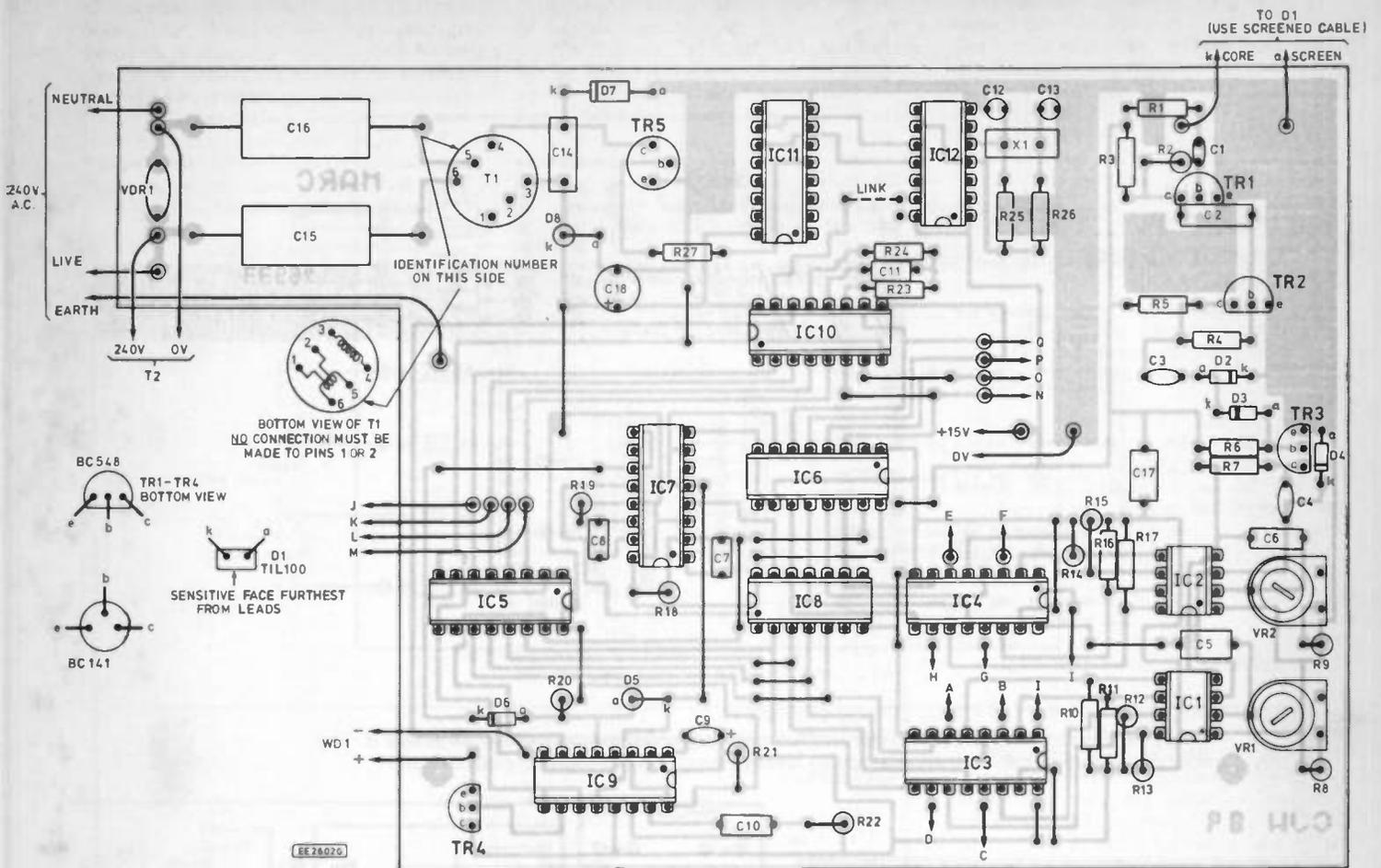


Fig. 2.3 Component layout and full size printed circuit board copper foil master pattern for Board A. The four inset diagrams to the left of the component layout give the connection details for the impedance matching transformer T1, the transistors and the infra-red sensitive diode D1. Diode D1 should be connected to the board using a screened lead.



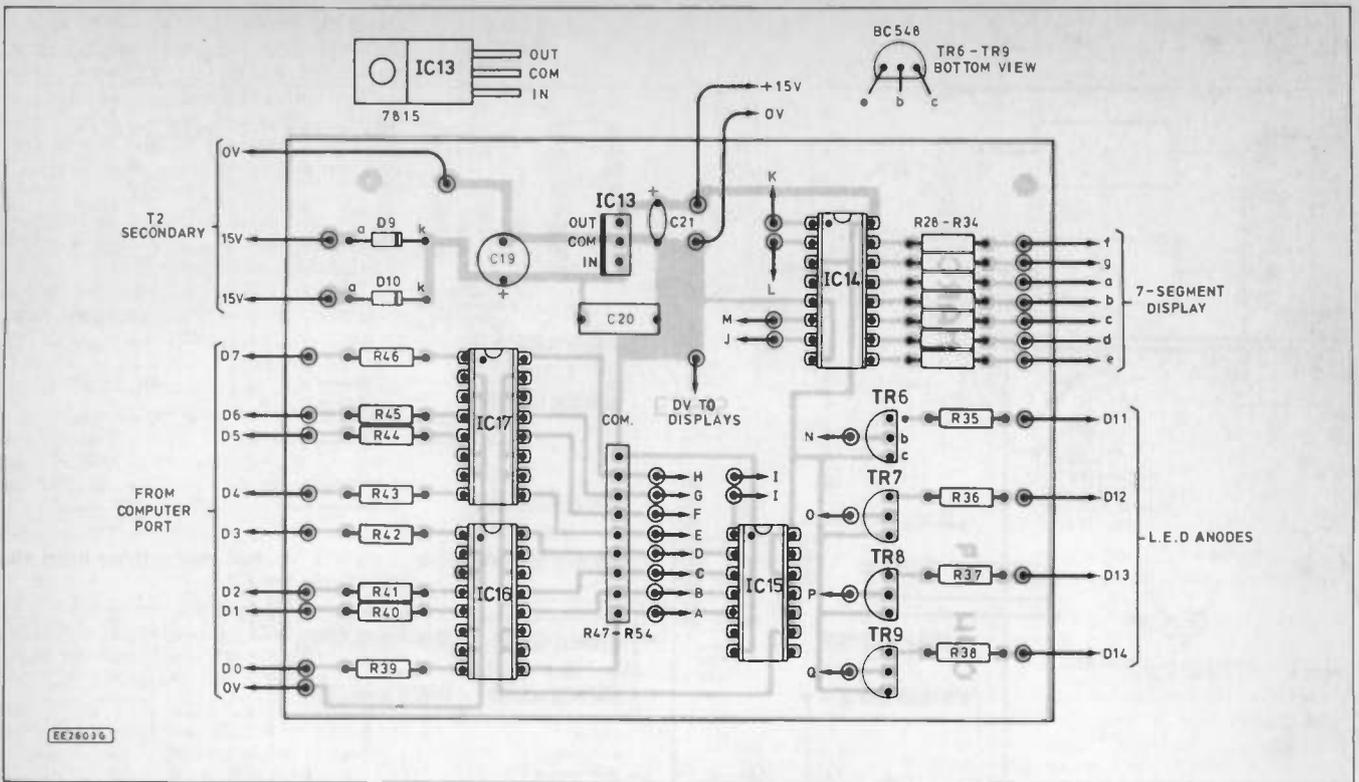
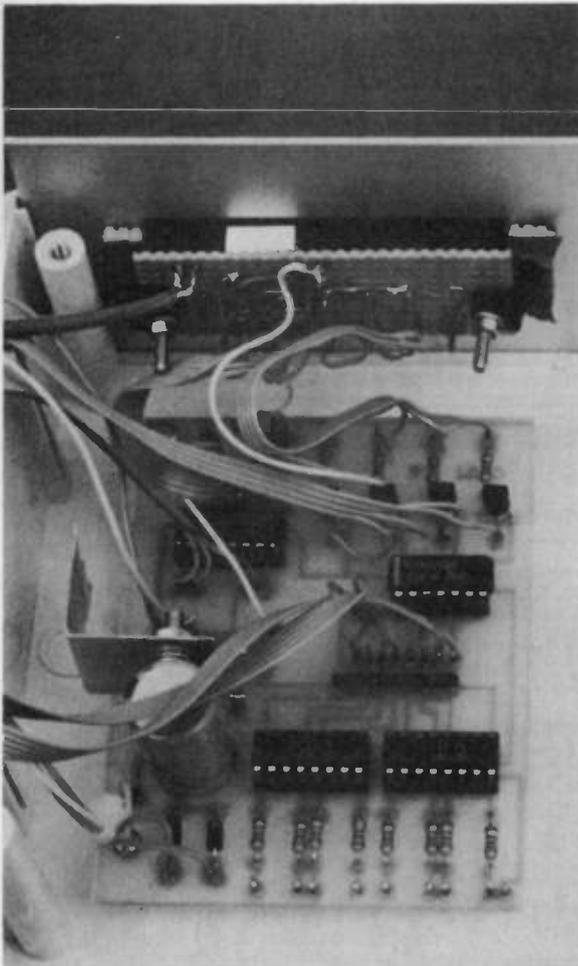



Fig. 2.4. Printed circuit board component layout and full size copper foil master pattern for Board B. The display components are mounted on a separate plain matrix board, see photograph bottom right.

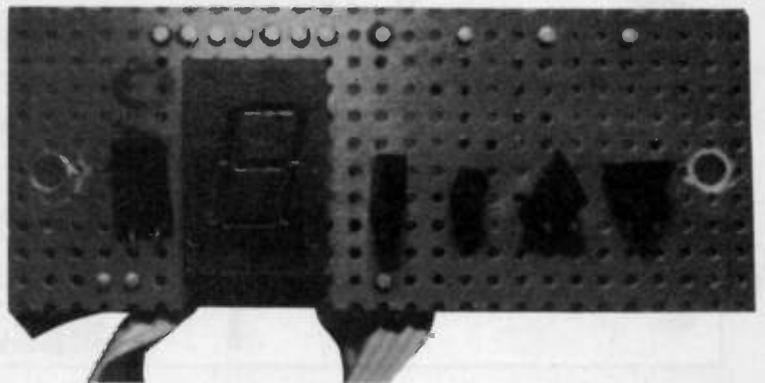

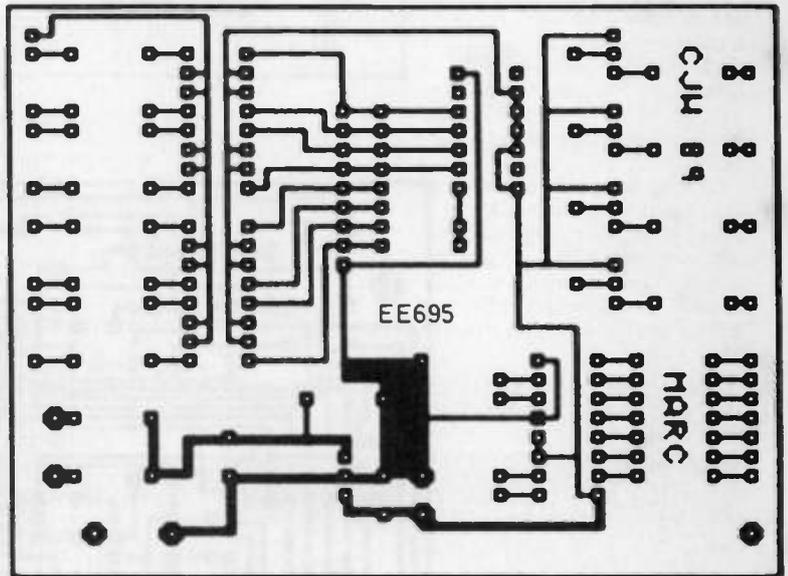Completed Board B wired to the rear of the display board. A small aluminium heatsink is bolted to the voltage regulator IC13.



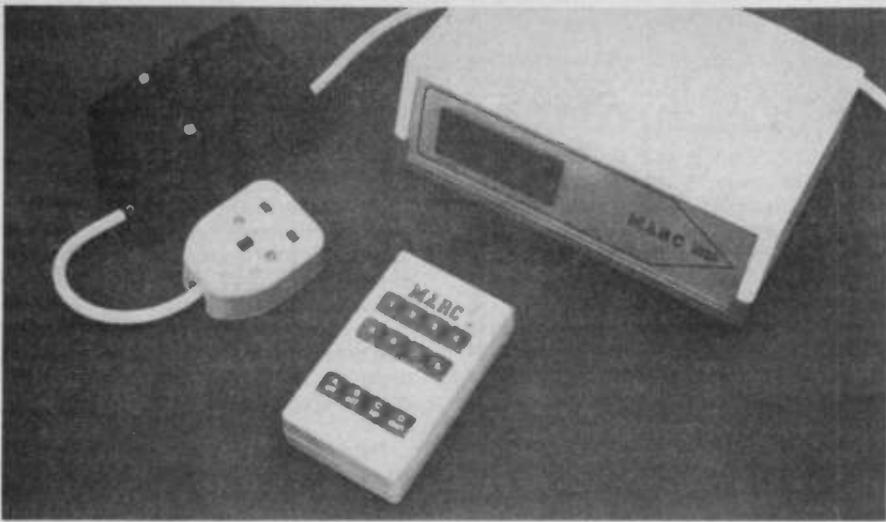Front view of the function display board showing the infra-red receiver diode, seven-segment display and the different shaped l.e.d.s.



The completed Decoder unit (next month), Encoder and the handheld Infra-red Transmitter (last month).


Link these terminals to Board B, apply a.c. power (CARE) and check for 15V between the power supply pins near IC13. If all is OK, switch off and complete all flying lead connections between the two boards then insert all integrated circuits (*be careful, not all devices face in the same direction*).

DISPLAY

In the prototype unit the display l.e.d.'s are mounted on a small piece of plain 0.1in matrix board and flying leads link this to the terminals on Board B. The cathodes (k) of all l.e.d.'s including the common connection of the 7-segment display can be brought back to the 0V terminal pin on this board.

During design it was not thought practical to make another p.c.b. for the display board since the pinouts of different makes of 7-segment displays vary greatly. The infra-red receiver diode D1 is also placed on this matrix board and a screened lead links it to Board A. The screen connects to 0V.

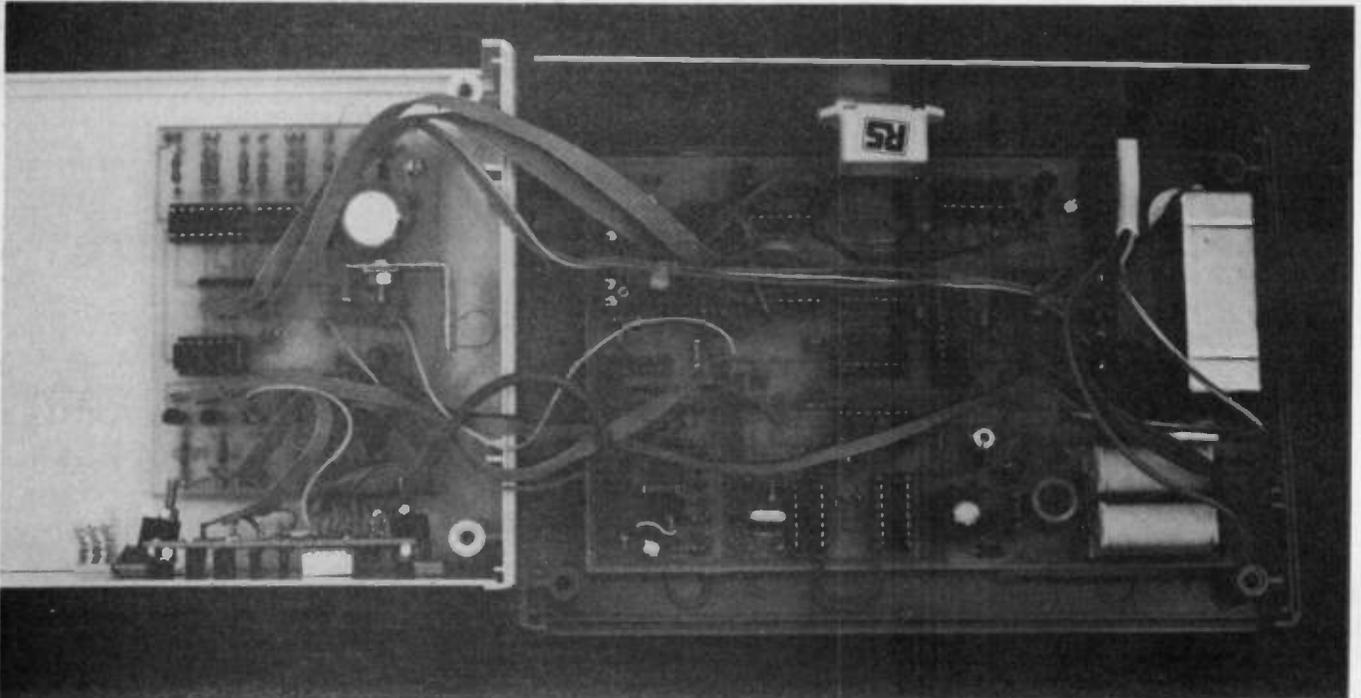The completed Encoder unit opened up to show board A mounted in the bottom of the case and board B positioned in the lid. The display board is mounted on one of the aluminium panels. A cutout must be made in this panel to take a display bezel and a strip of red filter.



CASE

Encasing the whole circuit is a simple task. The prototype is housed in a Verobox type 202-21035 with Board A and transformer T2 fastened in the bottom half and Board B in the lid.

To present a professional finish the display board is mounted behind a display bezel which includes a red filter for improved viewing contrast. Because of this it is not possible to use different coloured l.e.d.'s for the different function codes. Instead, I made use of the various l.e.d. shapes available as can be seen in the photographs.

ALIGNMENT

Commence the alignment procedure by making sure that the temporary link on Board A is connected between IC10 and IC12 pin 13. Connect an ammeter in series with the positive power supply lead from Board B to Board A and apply mains power.

The displayed current drain should be about 20mA, switch off if significantly

above this before the blue smoke starts to curl up! The 7-segment display should show a zero and no l.e.d.'s lit.

Now comes the time to test your infra-red transmitter and receiver circuits. Press a "receiver number" button on the transmitter (have you remembered to connect the battery and insert the i.c.? I forgot the latter, I must admit!). Adjust preset VR1 until the 7-segment display follows the selection on the transmitter.

Similarly, adjust VR2 until the function code buttons cause the appropriate l.e.d.'s to light and buzzer WD1 to sound (note that the ON l.e.d. always lights when UP and DOWN are selected). The display should clear after a ten second wait.

Disconnect power and move the temporary link between IC12 pin 13 and +15V. *Do not try to solder this link with power applied to the board* because an earthed soldering iron bit will cause short circuits if touched on anything other than the 0V line.

Re-apply power via the ammeter and bring the tuned circuit into resonance by adjusting the tuning slug in transformer T1 for *minimum* current drain (about 100mA when the carrier is running). Use a plastic trim-tool for this adjustment. A better method is to look at the carrier signal at TR5 collector using an oscilloscope and tune for maximum amplitude (somewhere in the region of 30V peak-to-peak). Replace the link between IC10 and IC12.

This completes assembly and testing of the MARC Encoder. Situate the unit away from TV's and other "electrically noisy" appliances as the front-end of the IR receiver is very sensitive and easily swamped. Alternatively you could screen TR1 and associated components using thin aluminium sheet connected to 0V.

COMPUTER INTERFACING

Many users may be quite happy to do away with computer control of the MARC system and only make use of the infra-red remote control link. Indeed, as was

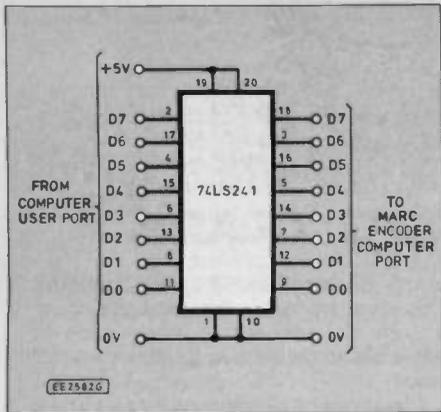


Fig. 2.5. Circuit diagram for buffering the computer user port to increase its current sourcing capacity.

mentioned earlier, the SL490 transmitter i.c. has the ability to send all the necessary codes to the encoder if extra switches are used on the handheld transmitter unit. Some constructors may like to take the trouble to purchase a data sheet for this i.c. and experiment along these lines.

Microcomputers are so commonly owned these days that it seemed an obvious addition to include a computer data input port during the design stage of this project. Also, since many micros have a "user-port" already fitted (or have provision for adding one) the MARC systems offers an ideal way to increase the power of "real-world interfacing" without the birds-nest of wires spewing from the computer and running around the house to all the appliances.

Resistors R39 to R46 are chosen to give

an opto-isolator diode current of about 10mA for a 5V high logic level. Your computer user-port must be capable of supplying 10mA per line, some output chips are not, e.g. the 6522 VIA on the BBC user-port or the Z80 PIO.

In these cases it will be necessary to buffer each line to increase the current sourcing capability and the use of an octal buffer/driver chip such as the 74LS241 will reduce the need for extra circuit building to a minimum. Fig. 2.5 shows how this i.c. can be used in such an application. It is important to note that the 5V power supply *MUST* come from the micro, any attempt to derive it from the MARC encoder supply defeats the aim of using an opto-isolator.

You should remember, from the preceding technical description, that the lower order four bits (D0-D3) of the data byte contain the binary code of the receiver to be accessed. Bits D4-D7 hold the "function code" for this receiver. All that is required to send this data byte along the mains is to place it on the MARC computer input lines for a time period *exceeding 10ms* (this is the length of the pulse which loads data into the encoder latches).


For example, say you wish to send "function code" 1 (ON) to receiver number three. The hexadecimal form of the data byte would thus be 13, which corresponds to binary 00010011. Send-

ing function 9 (DOWN) to receiver 12 (C, in hex) would mean outputting a byte of value 9C from the user port, 10011100.

Although function codes 1, 2, 5 and 9 are used by the MARC decoders to be described in future articles, there is nothing to stop designers using all 15 possible codes for their own purposes if desired.

The requirement for a 10ms "data-present" time will require some thought when writing software. It may be necessary to introduce a short delay loop to achieve this. Do not forget to clear the user-port lines to zero after sending the code, otherwise the continuous presence of data on the computer port will cause the multiplexer chips to ignore signals from the IR receiver circuit.

Next Month: Decoder ON/OFF Switch.

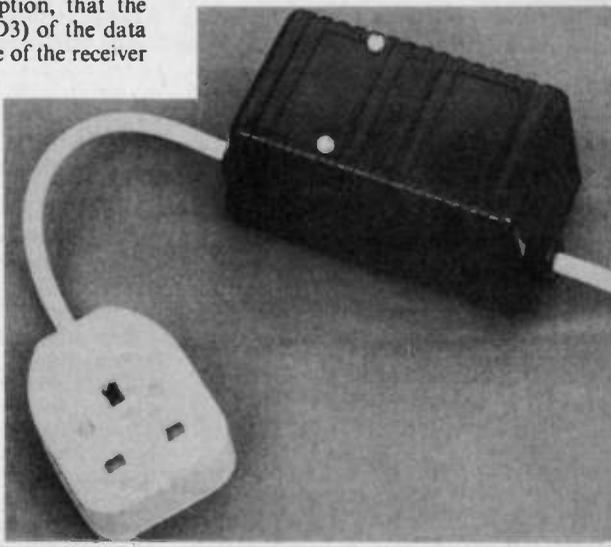

HART AUDIO KITS — YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard inducances and mountings make fitting easy on nearly all machines and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users.

HS16 Sendust Alloy Stereo Head. High quality head with excellent frequency response and hyperbolic face for good tape contact. £17.86
 HC40 NEW RANGE High Beta Permalloy Stereo head. Modem space saver design gives excellent high-frequency response with easy fitting and lower cost. Suitable for chrome, metal and ferric tapes, try a universal replacement head, with ample quality for Hi Fi decks and cheap enough for car players! £6.65
 HX100 Special Offer Stereo Permalloy Head £2.86
 HRP373 Downstream Monitor Stereo Combination Head £44.39
 HQ551 4-Track Record & Play Permalloy Head for auto-reverse car players or quadraphonic recording £16.79
 HS24 Standard Erase Head £2.59
 SM166 2/2 AC Erase Head, Standard Mount £12.60
 HS9510 2/4 Stereo DC Erase Head £8.70
 HQ751E 4/4 AC Erase Head, tracks compatible with HQ551 £57.06
 We can supply card reader heads for OEMs at very keen prices.

REEL TO REEL HEADS

999R 2/4 Record/Play 110mH. Suits Stuart tape Circuits £13.34
 998E 2/4 Erase Head 1mH. Universal Mount. Suits Stuart £11.96

TAPE RECORDER CARE PRODUCTS

HART TC1 TEST CASSETTE Our famous triple purpose test cassette. Sets tape azimuth, VU level and tape speed £5.36
 DEM1 Mains Powered Tape Head Demagnetizer, prevents noise on playback due to residual head magnetisation £4.08
 DEM115 Electronic, Cassette Type, demagnetizer £8.61

Our new Winter '89 price list is FREE. Send for your copy now. Overseas customers welcome, please send 2 IRCs to cover surface post, or 5 for Airmail.

We now accept inland and overseas orders by post or telephone on all Access, Master and Visa Credit Cards.

Please add part cost of carriage and insurance as follows:

INLAND: Orders up to £20 — £1; Orders over £20 —

£2.50; Next day — £9. OVERSEAS: Please see the ordering information with our lists.

Our latest lists also give details of our ranges of specialist high quality AUDIO CONNECTORS and LEADS, cassette decks and seasonal special offers. Write or telephone for your FREE copy. (Overseas 2 IRCs Please, or 5 for Airmail).



HART AUDIO KITS —

YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

LINSLEY-HOOD 400 SERIES SUPER HIGH QUALITY AM/FM TUNER SYSTEM

This is the ideal companion tuner to the 80W Audio Design Amplifier in any ultimate hi fi system with case size, front plate layout and even control pitches unified for stacking. Like the 80W Audio Design Amplifier this is your route to EX+ performance for a few tenths of the cost! Two designs by John Linsley Hood make up this combination of his ultra high quality FM tuner and stereo decoder described in "Electronics Today International" and the Synchronyne AM receiver described in "Wireless World". Novel circuit features in the FM section include ready built pre-aligned front end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together making a tuner which sounds better than the best of the high priced exotics but, thanks to HART engineering, remains very easy to build and set up. The Synchronyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HI-FI listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of its sheer sound quality, it is incredible value for money. To cater for all needs AM only and FM only versions are available as well as the full AM/FM model, with any unit being upgradable at any time. For further details see our fully illustrated lists.

K400 FM Only version, total cost of all parts is £211.90.
 Our special discount price for complete kit only £169.52
 K400 AM/FM version, Discount Price for complete kit £248.08

STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias circuit system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitting. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life. Suitable stereo heads are available at very reasonable prices.

K300W Stereo Kit with Wound Coils and Twin Meter Drive £90.68
 RJS1 Reprints of Original Descriptive Articles £2.00

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are suitable for use with any high quality cassette deck. Switched bias and equalisation to cater for chrome and ferric tapes. Very versatile and easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit £57.50
 VU Meters to suit £3.99 each.
 RLH1 & 2 Reprints of Original Articles £2.70

Our latest lists also give details of our ranges of specialist high quality AUDIO CONNECTORS and LEADS, cassette decks and seasonal special offers. Write or telephone for your FREE copy. (Overseas 2 IRCs Please, or 5 for Airmail).

HART KITS give you the opportunity to build the very best engineered hi fi equipment there is, designed by the leaders in their field, using the best components that are available.

With a HART KIT you have direct access to the friendly HART service, you are not dealing through, or paying for, any middlemen. Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

Telephone or write for our FREE LISTS giving full details of all our Kits, components and special offers. Here are a few selected items.

AUDIO DESIGN 80 WATT POWER AMPLIFIER

This fantastic amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi fi system. Featured on the front cover of the May issue of "Electronics Today International" this complete stereo power amplifier offers World Class performance with the option of a stereo LED power meter and a versatile passive front end giving switched inputs, volume and balance controls. Taps, CD players, or indeed any flat input may therefore be directly connected to bypass tone controls or give a 'stand-alone' facility. The amplifier can also be supplied in 'slave' and 'monobloc' versions without the passive input stage and power meter.

All versions fit within the standard 420x260x75mm case to match our 400 Series Tuner range. ALL power supplies are stabilised, the heavy current supplies using the same MOSFET devices as the amplifier. The power supply, using a toroidal transformer, is in fact a complete module contained within a heavy gauge aluminium chassis/heat-sink and fitted with IEC mains input and output sockets. All the circuitry is on a proper printed circuit with low-resistance blade connectors for the six stabilised DC outputs. HART KITS don't leave you to fasten a few capacitors to the floor of the main chassis and wire the power supply the hard way! Remember with a HART KIT you get the performance you want at the price quoted through proper engineering design and the right components. We do not insult your intelligence by offering a kit at what seems a fair price and then tell you that you have to spend three times as much to get an upgraded model!

K1100 Complete Stereo Amplifier Kit with LED Power Meter and 3-input Passive Stage. Total cost of all parts is £418.88

Our Discount Price for the Complete Kit £385.98

K1100S Stereo Slave Version, with plain Front Plate £309.43

K1100M 'Monobloc' mono version, with plain Front Plate £224.15

RLH10 Reprints of latest 'Audio Design Amplifier' articles £2.70

K1100CM HART Construction Manual with full parts lists £4.50

Reprints and construction manual can be purchased separately and their cost credited against subsequent kit purchase.


All versions are supplied with dual primary mains transformers for use on 220/240V or 110/115V mains. Monobloc price does not include the construction manual.

SPECIAL OFFER until the end of February the K1100 kit will be supplied with the new ALPS low noise precision pots at NO EXTRA CHARGE.


QUALITY AUDIO KITS

24hr SALES LINE
(0691) 652894

ALL PRICES INCLUDE VAT

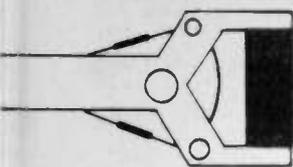

Robot Roundup

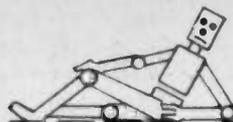

NIGEL CLARK

ROBOT WAYS

For anyone who has ever wondered what top and middle managers get up to when they go away on management training courses Stevenage Adventure Workpacks may have the answer. The company has been asked to look at the possibility of creating a robot game which can be used on such get-away-from-it-all jaunts.

The thought of high technology entering the world of management assessment appealed to George Walker and his colleagues at Adventure Workpacks and they have come up with an idea which he thinks many people may find interesting.

"I was approached by a large company which was looking for something different but interesting to do on its courses in the evenings," said Walker. "It was such a delightful suggestion and the thought of managing directors chattering around playing with robots made me chuckle so I set to and came up with this."

GREAT EGG RACE

What Walker came up with was a sort of Great Egg Race combined with model car racing.

Two teams begin with a set of components and the instructions telling how they should be put together to create a pick and place robot on wheels (see photo). When they have completed the construction of the robot, members of each team split into pairs and race each other to pick up an object, carry it through a course and place it in a container.

Possible adaptations on this basic theme include making the mobile robot negotiate an obstacle course and replacing the control board, which is basically a set of switches wired to the robot and set on a lump of wood which can be hung around the driver's neck, with a remote control system.

This brief explanation makes it appear quite simple but as Walker pointed out there are plenty of opportunities for getting things wrong in the construction and even if that is successfully achieved directing the robot needs a special skill of its own.

STEERING COMMITTEE

The steering is based on the tank principle with the movement of the wheels on one side relative to the movement on the other side governing the direction in which the robot travels.

One concession to the environment in which the game is likely to take place has been the rear wheels which are 10 inch diameter to allow the robot to travel across the deep pile carpets that are expected to be found in the premises in which the courses are likely to be held.

For companies wishing to know about the abilities of its management, accessors could be on hand to judge how the staff work together in teams, who has leadership potential and in the event of everything not running smoothly see who is best able to overcome the difficulties.

Walker said that the cost would be about £1,500 and expected the main market to be companies who were looking for something different in their training systems. As well as selling the game he is also considering hiring it out as part of a promotional or conference package.

REASSESSMENT

He has also been reassessing his kit range again. Under the banner of Starting Points he has introduced a series of packs intended to act as introductions to a range of electronic and mechanical concepts.

The results of completing one of the packs is that it looks similar to his original

Heath Robinson-like Robotech models. This time however, the intention is to provide an inexpensive introduction to the subjects rather than build a beautiful model.

The robotics kit contains motors, gears and switches for a pick and place robot as well as comprehensive building plans, instructions and ideas on how to work it. The structural components can be made from any junk material but there are plans for wooden components, some of the more complex of which are included in the kit.

To give the models computer control from a BBC B he has included a circuit diagram for an interface. There is also a circuit diagram for a switching board.

All this comes for £98 plus VAT. Anyone already having the necessary hardware can get the plans by themselves as well as the other documentation for £49.

NEW DRIVE

Hasfield Systems is continuing its moves to make the best use it can of the Armdroid, the manufacture of which it took up in 1988. Having brought out an improved version, named the Armdroid HS 1B, John Allright and his colleagues are now trying to increase its specification further by developing a new drive board.

The main basis of the improvement is coming from a decision to make the stepper motors bi-polar. This will have the advantage over the present machine of making the arm faster, up to three times faster has been claimed.


It is also claimed the lifting capacity is increased by up to four times. That would increase the capacity of the five-axis arm from 250gms to 1kg working at a maximum speed of three metres per second.

Another major change is that the standard gripper would be two-fingered instead of the present three finger standard. As before grip sensing is optional. Hardware development has been completed and the company is now working on the software which it expects to finish in the near future.

Their idea in upgrading the Armdroid is to give it a complementary role to the company's bigger Gamma arm, which is produced as part of a system for use in laboratories. While the full Gamma system can cost about £10,000, the improved Armdroid could be priced at about £1,500 which would allow laboratories to purchase one to give them an idea of how they could make use of a robot before perhaps investing in the full system.

Allright said that the company thought that the development work on the improvement had led to a useful by-product. It is a control board which can control up to eight bi-polar motors.

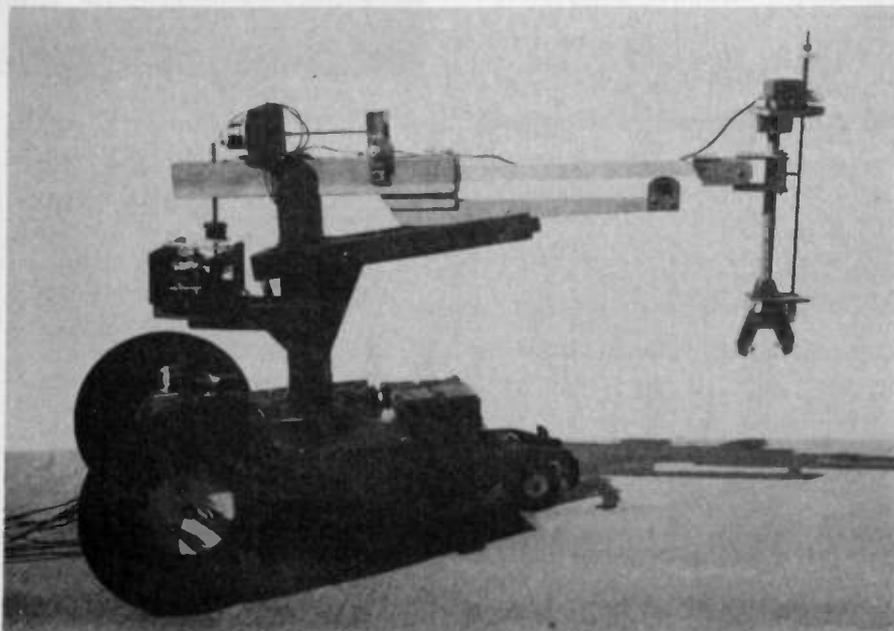The board would sell for about £300. Allright said it would allow people to power their machines cheaply.



TOW-TEST



PETER RAWNSLEY

Anyone can check out the tow socket wiring with this simple unit.

ANYONE who tows a caravan or trailer will come up against this problem sooner or later.

You're all hitched up and ready to roll when a voice from the back says, "Better check the lights are working." The owner of the voice is duly despatched to the rear of the outfit:

"SYSTEMS CHECK!"
 "RIGHT FLASHER?" - "O.K."
 "LEFT FLASHER?" - "O.K."
 "BRAKELIGHTS?" - "NO! TAILLIGHTS"
 "TAILLIGHTS?" - "NO! LEFT BRAKELIGHT"
 "OH! BO!!*RDS!"

Where do you start to locate such faults? In the above scenario, with the car probably loaded to the gunnels with the kids and luggage, all raring to go on that long awaited holiday, car ferry to meet at 6 p.m., the pressure is on. E.E. has the answer: -

SOCKET-TESTER

This device is basically a piece of test equipment used to test the correct function of the towing socket fitted to cars, vans etc,

and will be of use to all caravan/trailer owners. The sockets fitted to cars are prone to malfunction due to ingress of dirt and broken wires. But the main problem owners face when they find their lighting systems faulty is determining whether it is the car or caravan/trailer electrics at fault.

All cars equipped for towing are fitted with a black 7PIN(12N) socket wired to the European standard as shown in Fig. 1.

The *Tow-Test 12N Socket-Tester* is wired to this standard and is effectively a miniature trailer-board, consisting of six l.e.d.s mounted in a small handheld case, connected to a length of seven core trailer cable with a 7PIN(12N) trailer plug connected at the other end.

CIRCUIT

The circuit diagram for the tester is shown in Fig. 2. The six l.e.d.s D1 to D6 represent the lighting circuits, each has its own current limiting resistor R1 to R6 all are the same value which has been chosen to provide optimum brightness for the two l.e.d. colours used whilst easing construction.

Diode D7 provides reverse polarity protection for the l.e.d.s should this be caused by faulty wiring under test. The circuit is then connected via seven core trailer cable to the appropriate pin number of the 7PIN(12N) plug as shown in the diagram and Fig. 1.

COMPONENTS

Resistors

R1 to R6 470 0.6W (6 off)

Semiconductors

D1 5mm yellow l.e.d.
 D2 5mm red l.e.d.
 D3 5mm red l.e.d.
 D4 5mm red l.e.d.
 D5 5mm yellow l.e.d.
 D6 5mm yellow l.e.d.
 D7 1N4002 diode

See **SHOP TALK** Page 468

Miscellaneous

5mm l.e.d. panel mounting chrome bezel (6 off); 7-way tag strip (cut from 13-way); 3/16in grommet; 3/16in p-clip; type 401 handheld Verobox; 7PIN(12N) trailer plug; seven core trailer cable (see text); fascia panel (copied or cutout from page); 4BA x 1/2in csk screw (3 off); 4BA shakeproof washer (3 off); 4BA nut (3 off); 4in 22 s.w.g. tinned copper wire; solder.

Approx cost. Guidance only

£8

Fig. 1. Wiring of the 12N plug.


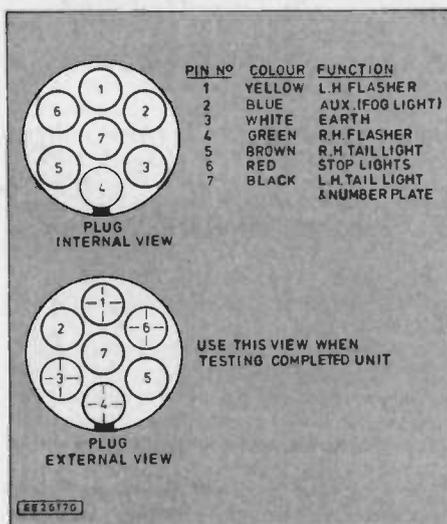


Fig. 2. Circuit diagram of the Tow Test.

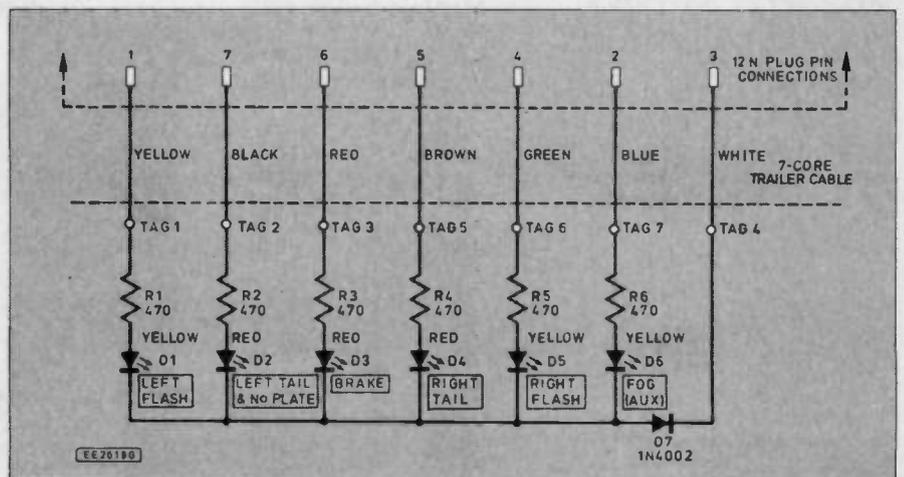

CONSTRUCTION

The case used for this project is a small handheld Verobox type 401. The l.e.d.s are panel mounted in chrome bezels with the rest of the components mounted via a seven-way tag strip.

Commence construction by marking out then drilling the case as shown in Figs. 3 and 4. The positioning of the l.e.d. bezels can be simplified by using the fascia panel Fig. 5. (use an actual size copy of Fig. 5) as a template, marking through to the plastic with the fascia in position on the case front.

With all holes drilled begin assembly, mounting the seven-way tag strip first using the 4BA countersunk screws. Position the fascia and stick in place. The l.e.d.

bezel mounting holes in the fascia will require enlarging to the size of those previously drilled in the plastic case beneath, before the bezels can be mounted.

The rest of the components are mounted and wired as shown in Fig. 6, observing that the correct polarity of the l.e.d.s and D7 is achieved. The 7PIN(12N) plug is wired via a length of seven-core cable long enough to reach from the socket on your car to the drivers seat and wired according to Fig. 1.

TESTING

Once completed the tester is nearly ready to use but resist the urge to plug it straight into your car. Faulty test equipment is of no


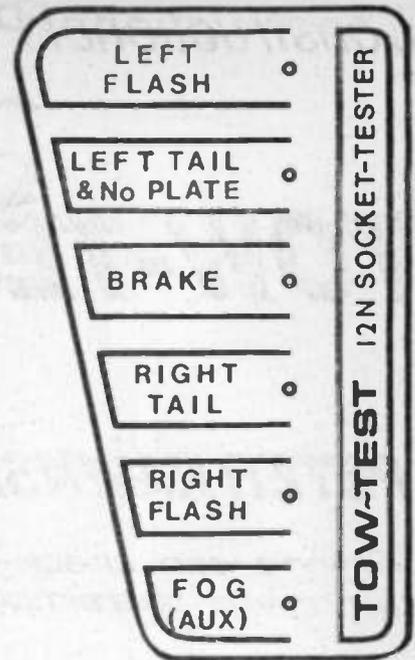
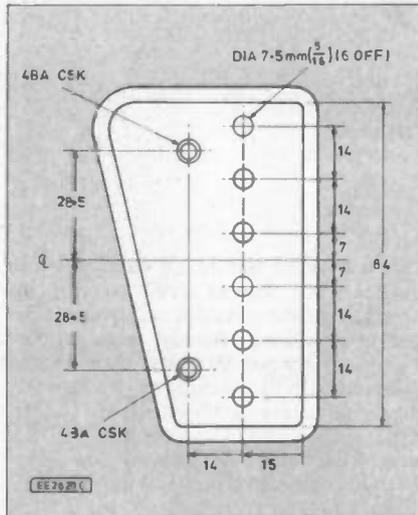
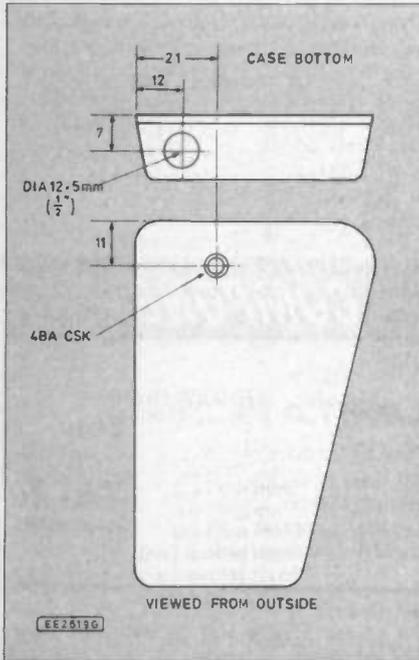


Fig. 5. Actual size facial panel.

Fig. 3. (far left) Case drilling details.

Fig. 4. (left) Drilling of the case top - outside view.

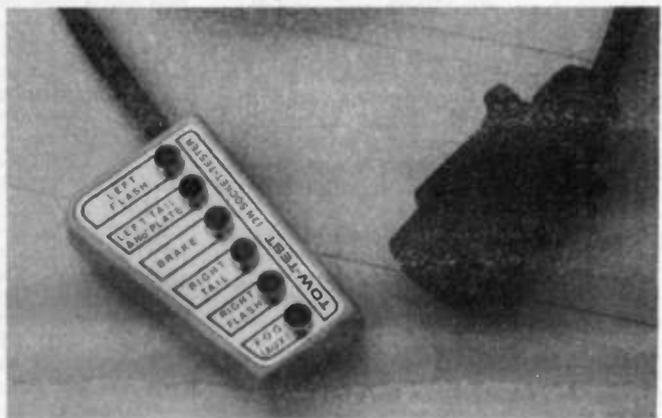

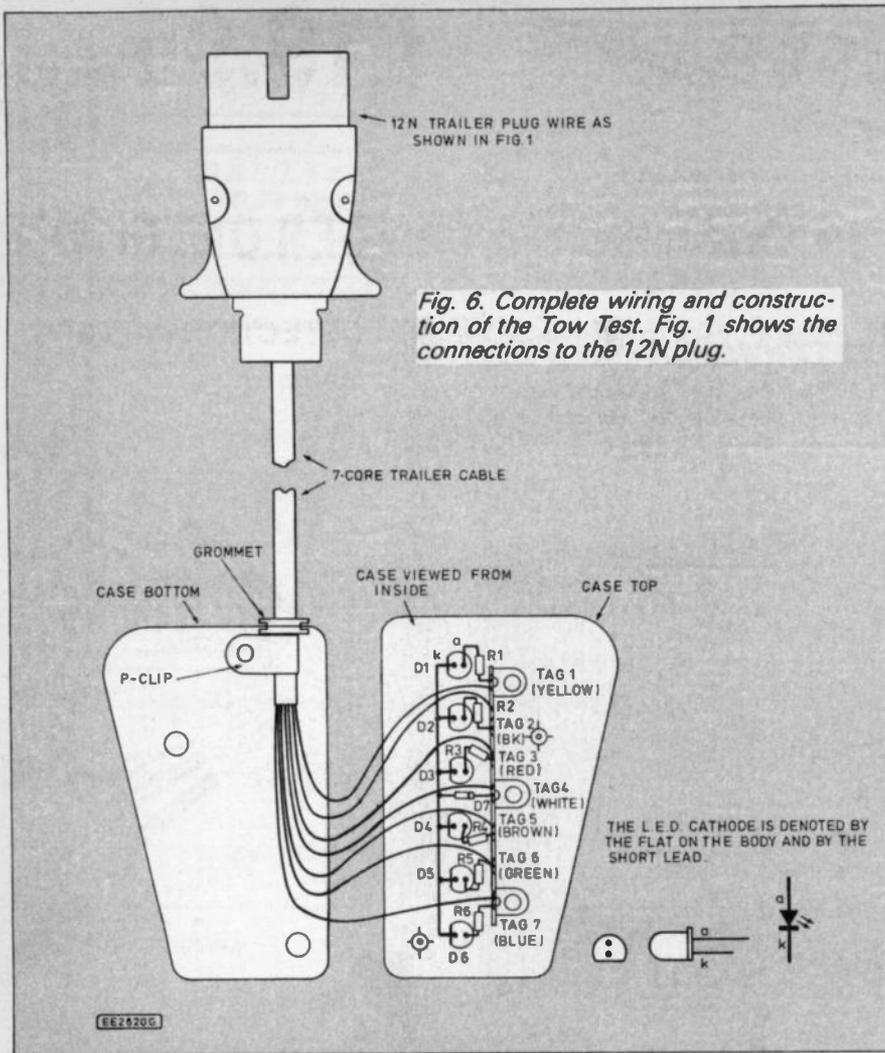


Fig. 6. Complete wiring and construction of the Tow Test. Fig. 1 shows the connections to the 12N plug.

use whatsoever! Carry out the following tests first using a 12V d.c. power supply or batteries. If a car battery is used include a 100mA fuse in the +ve supply lead to protect against accidental short circuits.

1. Connect -ve supply lead to pin 3 of the 7PIN(12N) plug.
2. Connect +ve supply lead in turn to the remaining six pins, observing the pin number and noting the resulting indication.

If all is well the pin numbers and resulting indications should correspond to each other as in Fig. 1. If not then recheck all the wiring and the polarities of the l.e.d.s and D7.

IN USE

Assuming all is well you can now proceed to single-handedly test the socket on your car/van. Plug the tester in and then, sitting in the drivers seat, operate the cars lighting system and observe the results on the tester.

If abnormal results are obtained then a fault exists on the car wiring and not the trailer/caravan. Check the socket wiring for loose or shorted connections or poor earthing and the pins for signs of corrosion and remedy any problems found.

It is unlikely that the socket will be wired incorrectly if it has functioned correctly up to this point. But it is a possibility on a new untried installation so check it is wired as in Fig. 1.

LIMITATIONS

The tester does not impose the same current loading on the connector as the actual lighting system would and therefore certain heavy current/bad earth related faults might not be detectable. Happy towing!

are obtainable through the *EE PCB Service*, codes EE694 and EE695 (see page 492 for details of prices).

Video Check

We do not expect any component buying problems to be encountered when building the *Video Check* project. Most component suppliers will be able to offer a suitable flashing l.e.d. at a reasonable price.

The light dependent resistor ORP12 or an equivalent should be stocked by most of our advertisers. It is not imperative that the specified handheld case be used, any small plastic case will do the job as long as there is sufficient room for the board, ORP12 and the push switch.

The Tester

The only component likely to cause concern when purchasing components for *The Tester* is the 2N4289 transistor. This a.f. low noise transistor (99p+VAT) appears to be only listed by Cricklewood Electronics (☎ 081 425 0161).

It is quite possible that the more common 2N3702 transistor may work in this circuit. This device has not been tried but select for high gain if it is used.

The small printed circuit board is available from the *EE PCB Service*, code EE969 (see page 492).

Tow-Test

The 7-pin 12N plug and 7-core trailer cable called for in the *Tow-Test* should be available from most large caravan accessories and motor spares shops. The handheld control case, type 401, used in the prototype was purchased from Maplin, code LL14Q (Verobox 401).

SHOP TALK

with David Barrington

Grand National Game

The components required for the miniature version of the *Grand National Game* are mostly standard "off the shelf" items and should not cause any purchasing problems. The rating of the m.e.s. lamps may vary very slightly from supplier to supplier, but should work quite happily in this circuit.

However, a couple of items called for in the Mains version may prove troublesome to locate locally. The optoisolators type MOC3020 are currently listed by Cricklewood, Omni and Greenweld.

The 3-pin Euro-style chassis sockets and plugs are sometimes listed in catalogues under the "Bulgin" name and are now fairly common. Although these are rather expensive items, because of the mains safety aspect we strongly recommend these types be used.

A complete kit of parts including lamps and case for the miniature version (£8.95) and a complete kit, including case, mains lamps and holders, for the mains version (£27.95) are available from Greenweld Electronic Components, Dept EE, 27D Park Road, Southampton, Hants SO1 3TB. Add £2 per order for post and packing.

Mains Appliance Remote Control

The *Encoder Unit*, this month's project in the *MARC* system, is the most complicated section and due to its connection to the mains supply only new first class components should be used.

The capacitors C15 and C16 are special types designed to withstand continuous mains voltage, other types must **NOT** be used as replacements. These capacitors were purchased from Maplin, code JR36P (IS Cap 0.47µ).

It is also important to use the specified mains transient suppressor. This was also obtained from Maplin, code HW13P (Mains Trans Supp). Both the transient suppressor and mains capacitors should be stocked by other advertisers.

The SA40A suppressor diode D7 (code QY71N), the ML926 and ML927 decoder i.c.s (codes QR57M, QR58N) and the M145026 encoder (code UJ49D) i.c. also came from Maplin. The other suppressor diode (D8) 1N6277 is an RS component and is available through Electromail (☎ 0536 204555), stock code 283-277.


The "impedance matching" transformer T1 was obtained from Cirkit and is listed under their "inductor" section. When ordering quote code 35-70742.

The two Encoder printed circuit boards


EE SPECIAL OFFER

£19.95 inc VAT & P&P

PASSIVE INFRA-RED INTRUDER DETECTOR

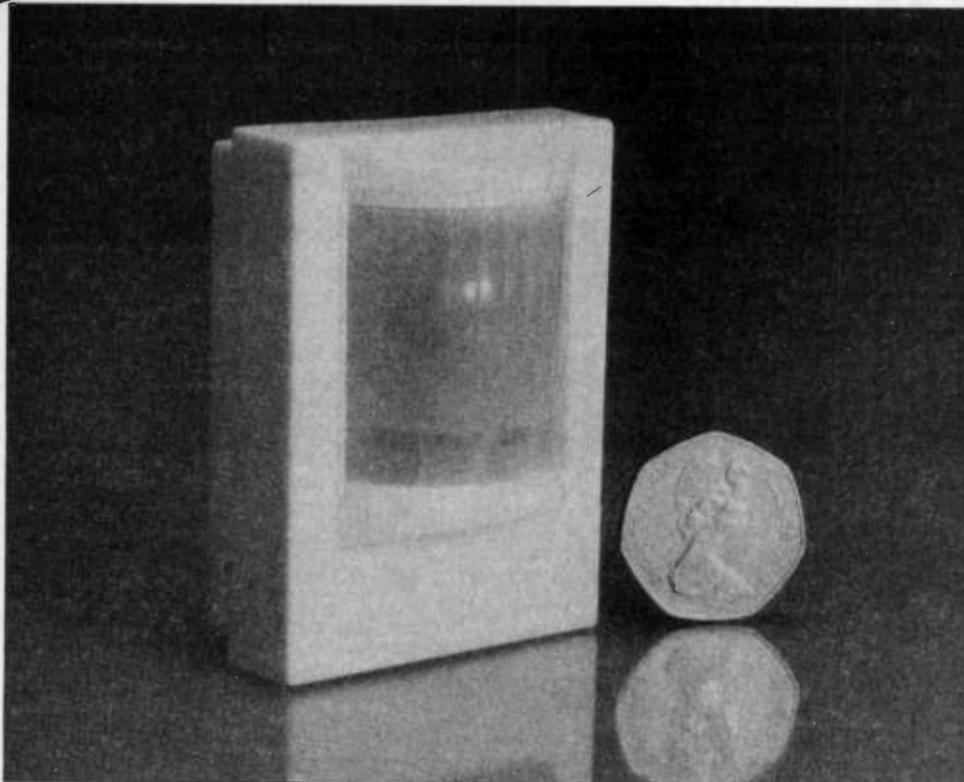

DETECTION PATTERN

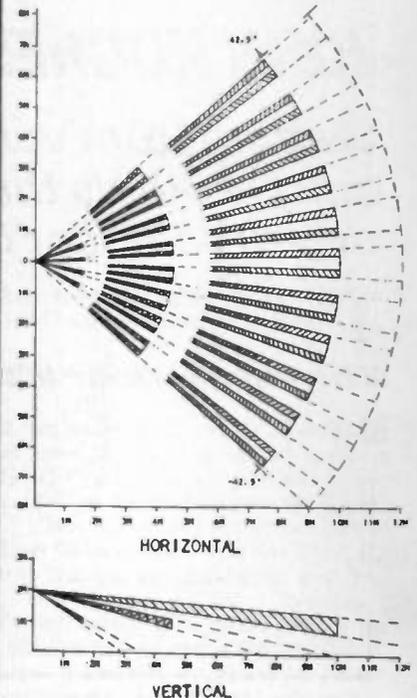

THE RP33 Riscomp passive infra-red intrusion detector is designed for use in both residential and commercial security systems. It operates by detecting the body heat of an intruder moving across the detection field. The detector employs a dual element pyroelectric sensor which is designed to overcome the effect of changes in ambient temperatures, thus ensuring a stable and reliable performance, while the considerable filtering employed in the advanced circuitry ensures that the sensor is unaffected by RF interference and electrical transients.

Installation is easily carried out on a flat surface or in a corner location without the need for additional brackets, whilst the angled rear of the case permits the unit to be mounted in an off-set position as may be required in some locations to achieve optimum coverage. Vertical adjustment of the detection pattern over a 10° range is provided, whilst the dual range facility allows the installer to optimise coverage for the intended location.

The RP33 is suitable for use with the Riscomp control units type CA 1382 and CA 1250, or any equivalent high quality control unit.

SPECIFICATION

Operating voltage:	9-15V d.c.
Current consumption:	14mA at 12V.
Relay output:	Normally closed contacts rated at 0.5A with 22 ohm resistor in series.
Anti-tamper switch:	Normally closed rated at 1A.
Detection range:	Switchable between 7 and 12 metres.
Detection zones:	24 in 3 planes.
Maximum operating angle:	85°
Mounting height:	2-3 metres.
Walk test:	Red l.e.d. (with disable switch)
Dimensions:	80mm x 60mm x 40mm.
Sensor type:	Dual element ambient cancelling.

POST TO: EE Intruder Detector offer, Riscomp Ltd., 51 Poppy Rd., Princes Risborough, Bucks HP17 9DB

INTRUDER DETECTOR OFFER

Please supply:

Quantity	Product	Price
	RP33 Intruder Detector	£

Prices include VAT and delivery Overseas Airmail Postage £ Total £

Please make cheques payable to Riscomp Ltd.

Access/Visa No.....

Card Ex. Date.....

Signature.....

I enclose cheque No.....

Name.....

Address.....

Normally sent within two days, but please allow up to 28 days for delivery

OFFER CLOSERS FRIDAY AUGUST 3, 1990

Readers outside of Europe please add £3 for airmail postage

MICRO IN CONTROL



JOHN HUGHES

Part Eight

Starting from very basic principles this series quickly builds through logic to simple microprocessor control.

THIS month we look at the three-floor lift logic and then meet the "Micro".

The three-floor lift:

T Now let's take a deep breath and start working out the logic for an extra floor. We've already got a plan (Fig. 8.1). How far can we adapt the circuit we've already worked out for the two-floor model?

S We'll still need a timer/and all the door and limit circuits/and the top and bottom floor logic?

T Seems reasonable, though our "bistable" approach may be less suitable for more than two floors. This time it might be a good idea to use a bistable (memory) for each floor. (Fig. 8.2). When does output A need to be 1?

S If P2 is called/or P1/only if the lift is below it/Oh, it CAN be above it, now/it's the same for B/only DOWN, A is for Up...

T Right, so we'll need extra TERMS in our Boolean equations, and they will OR with the others (remember the steps we discussed last time). A is 1 (for UP) if...?

S P2 is called (C2 is made 1) AND S2 is 1.

S (others) and T is 1, don't forget/and NOT B/let's leave out T, can we?

T So we can write as before, to start with:
 $A = (C2 + A).S2.B$
 T leaving out T for now:
 $A = (C2 + A).S2.B$

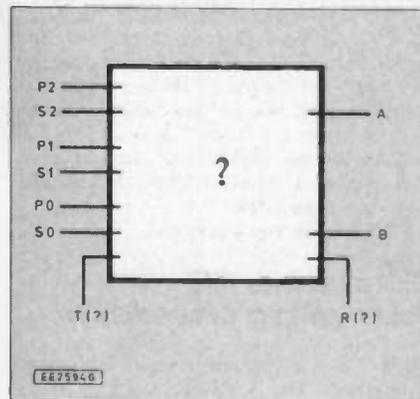


Fig. 8.1. Making a start on a three-floor version. T and R omitted initially. Note: Same outputs but, of course, more input signals.

S We don't need "OR A" with the bistable.

T Right, omit it. Also, A is 1 when P1 is called, if the lift is at floor 0.

S This gives $A = C1.S0$. with B, I suppose, again, so $A = C1.S0.B$

T If we combine the two alternatives (with OR), we have $A = C2.S2.B + C1.S0.B$

S And $B = C0.S0.A + C1.S2.A$ We'll need

a 7420 and more inverters (7404) and the 7432. Can we try it out?

T Certainly. The more snags you foresee, however, the less rebuilding needed. It'll test your dexterity.

S And my eyesight! But don't we need an "S1" somewhere to make the lift stop at floor 1?

T Good thinking. In the second term,

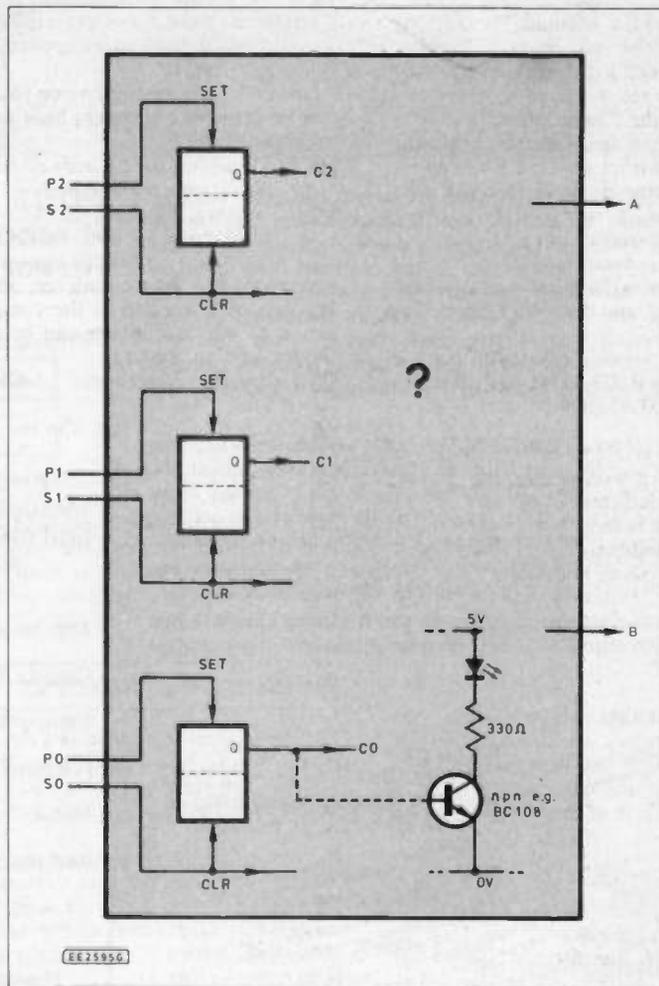


Fig. 8.2. Adding "memory" bistables (Set-Reset) for each call button. Indicator i.e.d.s could be driven from each bistable via a transistor, as suggested, but are not part of the control logic.

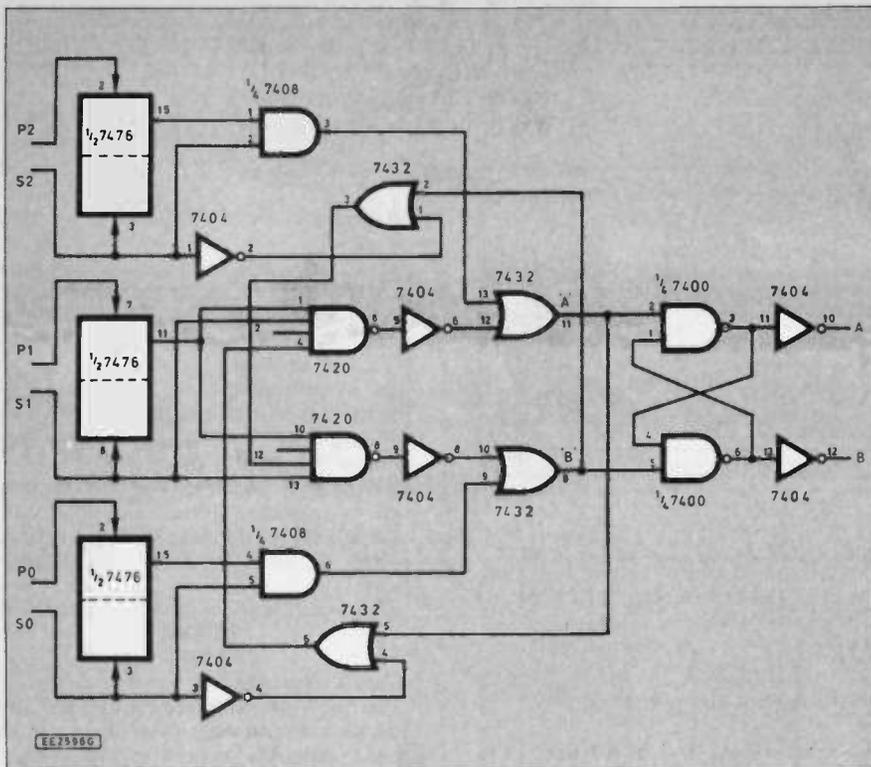


Fig. 8.3. "Three-floor" logic. Note unused (timer?) inputs of the 7420, left "floating" for now.

thus: $A = \bar{B}(C2.S2 + C1.S1.\bar{S0})$ Notice the slight rewriting, too. It may help.

S Won't the lift stop as soon as it leaves S0 or S2?

T Well done again. It could. We need the "OR" signals after all, in term 2. Let's think through the logic again. You may like, when you set it up, to meet a very useful device, the "logic probe". If you don't have one, a spare output indicator will help. Try to trace the logic levels either back from the output end or forward from the inputs, and see where there may be something we've overlooked.

S Or a wrong connection!

T We'd better write what we hope will cover everything, and draw a diagram (Fig. 8.3).

S I won't look till I've had a go myself! $A = B.(C2.S2 + C1.S1.(S0 + A))$
 $B = A.(C0.S0 + C1.S1.(S2 + B))$

T Remember, you can test the logic on your breadboard without the lift, if you have to, using indicators and switches or push-buttons as before. But be careful not to send signals indicating, for instance, that the lift is in two places at the same time!

S Short leads to dab on to the 0V line can simulate the sensors and call buttons. I had to do that, because I couldn't finish my model in time. The logic seems to work fine, though.

T Don't forget that there are alternative circuit arrangements which can work just as well. If some of you have finished testing, and want a new challenge, you could think about the sort of control system that might operate, say, a model railway.

S It would be best to start with a small loop or circle, I expect? Then add sidings and branch lines later. I might have a go at my lad's train set later on.

S (others) Ask him first! He means his own set.

T Anyway, you'd need sensors and motor drivers rather like the present ones. Perhaps more of them.

S And reversing circuits/and speed

controls/and signals/and a way of identifying them if you have more than one train. . . .

T So there's plenty to get your teeth into. It could become a major project. No doubt you'll think of many more applications for these logic systems.

However, we need to move on to see what can be done with a system built around a microprocessor.

S Presumably a model train could also be controlled by a microprocessor?

T Indeed, yes. We could equally well use a train to illustrate the two systems, direct logic control and control by a programmed (micro) system. As we shall see, one of the beauties of the micro is the comparative ease with which a change can be made in the action of the system

S Changing "software" instead of "hardware", I bet.

T That's it. That's why the micro is so flexible.

S Are there any advantages to straight logic circuits?

T The main ones are: Low cost for simple systems, and the fact that they can be much faster in their response than a programmed system, though some of these can be much faster than others, as we'll see.

Meet the Micro

T We've seen how logic circuits can be made to control a system such as a lift, and how, by means of gates and flip-flops anything seems possible, well, almost anything.

S But it can get complicated. I found the lift much more complex than I'd expected

S (another) Yes, but it IS complex. We assume that it just moves up (or down), but there's a lot more to it, and all sorts of conditions had to be met.

T Would you agree that one of the tiresome jobs is to alter a circuit so as to modify or improve its performance?

S Or to get it to work at all!

T Quite. Any change means rewiring, sometimes quite a lot of it.

Well, one of the beauties of using a micro is that much of this re-wiring can be done away with, as we shall see.

S How does a microprocessor work?

T Perhaps we can look briefly, then, at some of the basic units which form the microprocessor. We've already become familiar with most types of logic gates, and with bistables. I'd like to point out one or two important features, some of which will be apparent from what we've already been doing.

How many bits?

T You'll know that digital systems are nowadays sometimes called "information systems", and a thought about what we mean by "information" won't come amiss.

S Isn't it just messages, names and numbers?

T That's not a bad way to describe it. We know, too, that we'll be dealing with binary numbers, using 0 and 1 as our only digits.

S And using electrical on and off signals from them/the 0V and 5V levels/our "logic levels"/voltages.

T Good. Now just think of a single binary digit, a "bit". As you say, it can have either of just two elementary items of information, like "yes" or "no"?

S And the question must be decided beforehand. Like: "Can I come round tonight? Leave the bedroom light ON" for "Yes, the coast is clear" or OFF for "No, better keep away!"

S (others) he knows/the voice of experience/etc.

T A good example, anyway. How might a third message be conveyed?

S We'd need another light, downstairs, say. Then we could send three messages/four messages, in fact.

T Yes, Two "bits" can represent four different numbers, can't they. We've seen them written out:

0	0
0	1
1	0
1	1

representing 0, 1, 2, 3 respectively, in binary notation.

S We've counted up to fifteen (sixteen numbers, including zero) with FOUR BITS, in the binary counter chip.

S (another) and used gates to convert it to denary.

T Yes, so you can appreciate the need to use several bits (at least four) in, for example, a calculator unit.

S We've even written them in hex code!

T OK. So now, let's think of four bistables linked, not necessarily as a counter, but just as a "register" of four bits. The right-hand bit will be the "units" bit, the next on its left the "twos", next the "fours" and finally the "eights" bit, often referred to as the "most significant bit" (MSB). The right-hand one is the. . . ?

S LSB/"least significant bit"

Exercise 12 Handling the data

T We saw a four-bit counter in action, remember? The kind we used was an "asynchronous" counter, also called a "ripple-through" counter, because each stage triggers the next one in turn.

We should be aware that sometimes a "synchronous" counter is preferable.

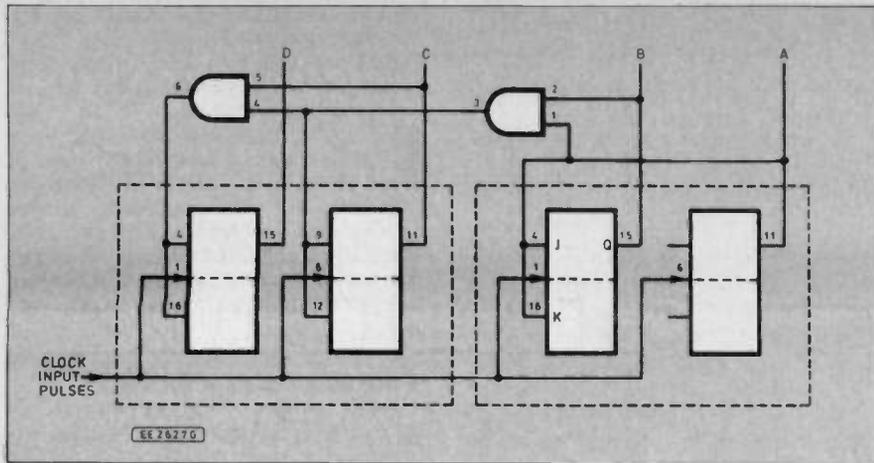


Fig. 8.4. Synchronous 4-bit counter using two 7476 and 1/2 7408. A, B, C and D linked to indicators.

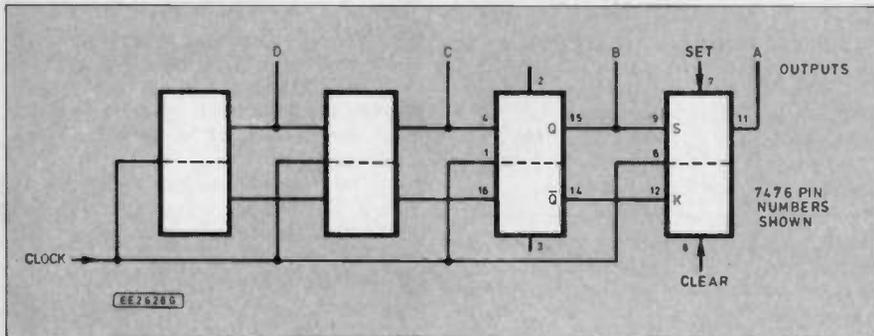


Fig. 8.5. Shift register. It could be reversed by crossing the links between Q, Q-bar and J, K. Note how a single SET signal can be shifted along on each clock pulse. It could be extended, or looped back into a "ring".

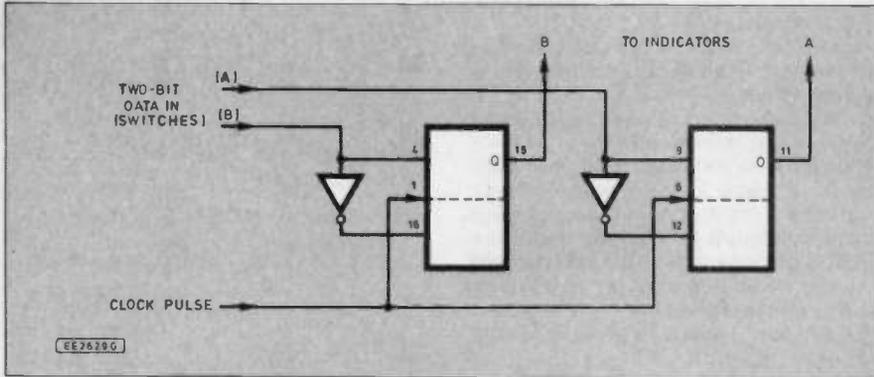


Fig. 8.6. Data latch using 7476. Note inverters (7404) linking J and K inputs. Clock pulse causes values on DATA lines to be stored on QA and QB. (The 7475 chip is a "ready made" 4-bit latch).

That's one in which each bistable is triggered by a common clock pulse, so they change (those whose turn it is) all at the same moment. For those of you who'd like to build a synchronous counter using 7476 chips, here's a circuit: (Fig. 8.4)

- S** It uses gates to do the dividing by two.
- T** Another useful circuit is a "shift register", in which a bit can be, as the name implies, "shifted" along the register from one end to the other (Fig. 8.5).
- S** What's the point?
- S** (others) it multiplies by two/or divides/or by four/or eight
- T** Exactly. And it has useful control applications, too.

Another register I'd like you to look at is called a "latch". It's important for its ability to catch and store binary numbers (data) (Fig. 8.6).

- S** As a memory store?
- T** Indeed. As you know, memory circuits abound in microprocessor applications. Let's now look at what sort of

circuits (we needn't draw them in detail) a microprocessor might contain. Some of them may be in adjacent chips, but a typical microprocessor will have:

- an ARITHMETIC and LOGIC unit (ALU), which can add or subtract binary numbers, and perform the AND, OR and NOT functions, with others, such as shifting up or down
- A number of storage REGISTERS, for temporary holding of working data, and COUNTERS, to keep track of events.
- Additional control GATES and BISTABLES, to direct incoming signals to the right areas, and to send out the appropriate data when needed.

We'll be more specific when we decide which type to use for our initial exercises.

- S** How can a micro add and subtract/multiply/divide?

T We'll spend a few minutes assuring ourselves that it can be done, if you like, by

building and testing a binary adder (let's have no cracks about snakes!)

Exercise 13 "one and one makes...?"

T This is really another exercise in logic design. First we must consider what inputs we have, and what outputs they must produce, so let's do some addition "sums". There are only a few possibilities, in binary, right?

- S** Four?/six?/eight?
- T** Any advance...
- S** We only need to add two numbers, then two more, and so on/but what if there's "one to carry"?

T Well done. It seems reasonable to consider two numbers, but also a "carry" from one column to the next (if it helps some of you, try some ordinary "denary" sums first)

Think of a couple of multi-digit numbers:

XXXXX
XXXXX

Any X can, of course, be a 0 or a 1.

As usual, we start adding at the right-hand column, so what possibilities will we need to deal with?

- S** Two noughts, two ones, or one of each/there are four cases, but two of them will give the same result.

T You've got it. Let's write them down:

Case 1	Case 2	Case 3 (and 4)
0	1	0 1
0	1	1 0
0	2	1 1

Hello, what have I done in Case 2?

- S** You can't write 2 in binary/you have to put down 0, with 1 to CARRY.

T There it is, we need TWO outputs, a SUM and a CARRY, so our "box" will look like this (Fig. 8.7). And we can write a Truth Table for it, and consider what gates we could use to build this "half adder" circuit. Try to work it out yourself before looking at my suggestion (Fig. 8.8).

- S** Why a "half adder"?
- T** Because we'll find we need an extra input to make a "Full Adder" when we deal with our second (and later) columns. Anyone explain why?

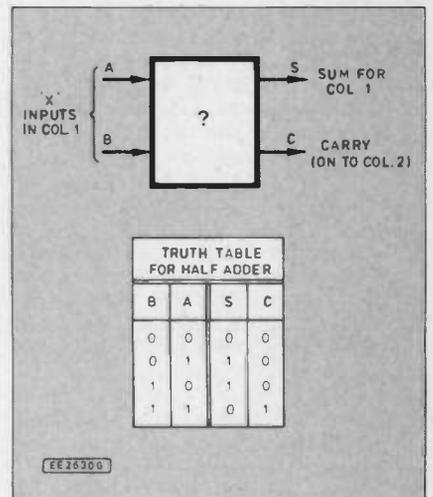


Fig. 8.7. Half-adder inputs and outputs. Note how C requires just an AND gate, S an "exclusive-OR" arrangement.

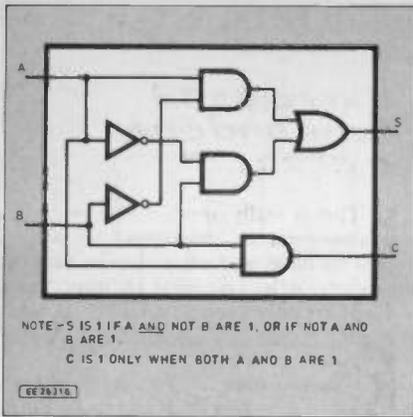


Fig. 8.8. Possible half-adder circuit.

S (after thought) To deal with the "carry" signal.

T Spot on. When we add the next two digits, we'll also have to add in the carry from the first (right hand) column, and this will happen for every column except the first.

S So we need one half adder and a number of full adders in an adding circuit.

T Yes. Can you design a full adder now? It'll have three inputs and two outputs (Fig. 8.9).

S (eventually) How about this (Fig. 8.10)? and its Truth Table, too.

T Good. I see some of you have used different gates to achieve the same result. Fine. Now we'd better move on.

S What about subtraction/multiplication, etc.?

T Well, they can all be built around adder circuits, with counters and some more logic thrown in. For example, the process of multiplication is really repeated addition, so a register could be used to hold one number, then the other number added to itself once, (and the register counts down ONE), then again, and again, until the register is zero, at which stage the addition will

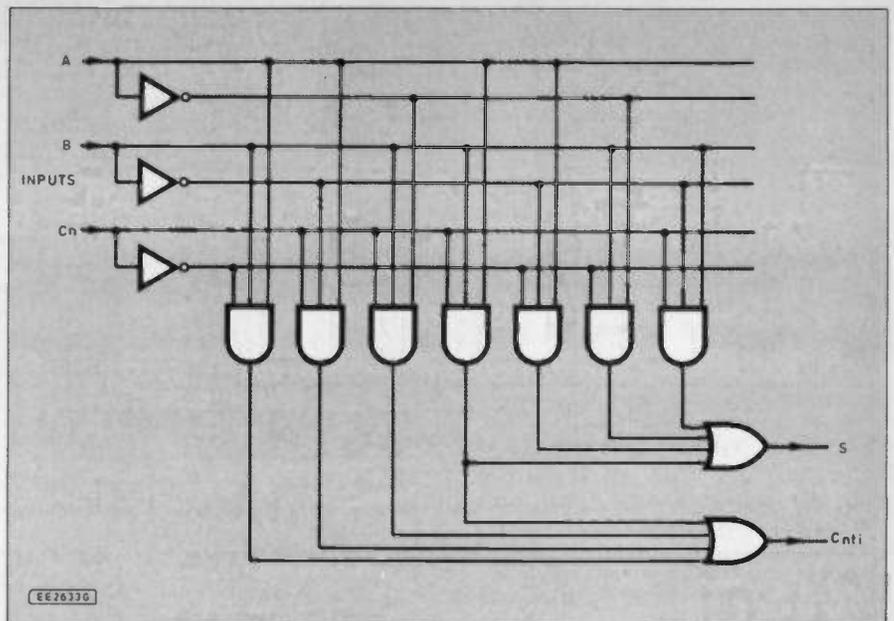


Fig. 8.10. Possible circuit for full adder (refer to Truth Table in Fig. 8.9) The $S=1$ rows give these AND terms (with OR relating each term): $C_n \cdot \bar{B} \cdot A + C_n \cdot B \cdot \bar{A} + C_n \cdot \bar{B} \cdot A + C_n \cdot B \cdot A$. The $C_{n+1}=1$ rows give: $C_n \cdot \bar{B} \cdot A + C_n \cdot \bar{B} \cdot A + C_n \cdot B \cdot A$.

have been done enough times to give the result of multiplying the two original numbers together. It sounds tedious, but the logic circuits can do it extremely quickly, as we've seen.

S We'd need comparator circuits, too, to check when the counter reaches zero.

T Quite, and they can also compare any two numbers. If you want to, you can (in your own time) build up comparators and other useful circuits using gates, but, of course...?

S (chorus) There are chips to do it for us.

T Indeed there are. Perhaps you'd be better occupied in getting to know some of them by testing them in your breadboard, and trying to assemble your own "computer" circuits.

We really must press on with a look at the micro, which is really an assembly of these fascinating circuits in itself. However, I shall just mention subtraction, which one of you wondered about.

S We could design a "subtractor" like we did for the adder circuits.

T You could, but it may be possible to use the adders themselves, by making use of a mathematical "trick."

The trick is, firstly, to "complement" (invert) each digit in the number to be SUBTRACTED, then ADD it to the original number. Add an extra 1 (in the "units" column), and ignore any final carry which may "spill over" from the left-hand column.

An example will help. Let's subtract five from eleven, say, in binary, of course:

11 becomes 1011

5 becomes 0101

S The 11 would be B in hex, wouldn't it?

T It would, as a matter of fact, but we'll stick to our binary for now. Now to do our sum. The 11 stays as it is, and we invert each digit of the 5:

1011

1010

10101

Adding, we get
Now, we add another 1, to get 10110, and knock out the initial 1, giving 0110, which is denary 6. OK?

So, by using some extra inverters, our ADDER circuit can also be made to SUBTRACT. In fact, you could build a com-

plete computer now from the various gates and flip-flop circuits you've already tried out. But a microprocessor does it all, anyway.

S It's good to understand a little of what's inside it, however. There must be many gates etc.

T Tens, even hundreds, of thousands. The story goes that it came about as a result of a request from a Japanese manufacturer to an American i.c. supplier for a series of chips for a range of calculators.

It was realised that a single chip might be possible which could fulfil all the required functions if it were designed to respond to extra control signals. Hence the microprocessor, at first with a four-bit capacity, later with eight. This was over twenty years ago, so the micro is about as old as some of you.

S Can we plug a micro into our breadboard?

T You could, and there are specially wide-gapped boards just for such very large scale integrated circuits (VLSI).

However, you would need many other chips to enable you to do anything useful with most micros, but it's just what a circuit designer has to do, as you may imagine. In the early days, firms who advertised micros in journals like this one soon found that they had to print a sort of "health warning" advising customers not to purchase a micro unless they knew how to drive it!

Fortunately there are available a number of "development systems" which can be used to investigate the behaviour of a microprocessor together with a suitable family of "support" chips (some of which, as we shall see, are almost as complex as the micro itself).

S Can we build such a system?

T The answer, again, is that you COULD, but it would be tedious, and might only appeal to a very dedicated enthusiast. Some are made by the chip makers themselves, others by specialist suppliers for education and training. We shall look at some typical systems.

S Is a home computer such a system?

T In some ways, yes, but it may not have adequate means of linking it to our sen-

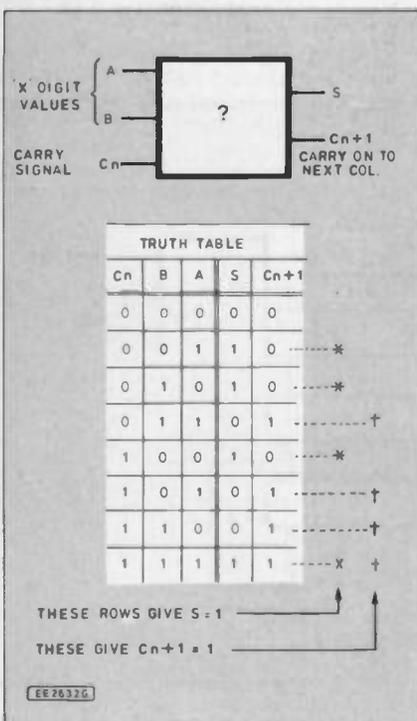


Fig. 8.9. Extra (carry) inputs included, from previous column.

sors and drivers, but we'll include some exercises using such a computer later on. Now we should consider briefly some typical microprocessors we might meet.

For our control purposes, we don't need a very large number of bits, and the popular and inexpensive eight-bit micros are fine. In fact, there are, in industrial use, specialised four-bit and even "one-bit" chips available. Designing a new microprocessor is, as you may imagine, a major and expensive development. Nevertheless, several have been launched, and a number have survived for many years.

Probably the most familiar and widely-used eight-bit chip is the Z80, derived from an earlier winner, the 8080. Another well-tried design is the 6800 micro, followed by the popular 6500 series, which we shall study more closely, because it had many features which make it particularly suitable for our purposes.

Some of you may have met, too, a few other types such as the 1802, or SC/MP (called "scamp" by some!). Each has its own attraction, but, unfortunately, the details of the individual designs make it impossible to do more than mention general similarities, and we must settle on one unit for a detailed understanding, if we are to make reasonably quick progress.

S I've heard of all those! I have a Z80 in my home computer! I have a 6502, I think.

T Good. Both these chips are extremely and deservedly popular, and hence are available at very reasonable cost.

S Will we have to programme them?

T Yes. Every microprocessor has to be programmed. It is designed to carry out small, simple instructions very quickly and in strict sequence, as you probably know. That's why we need memory circuits to store the necessary data and instructions.

S We'll still need our sensors and output circuits, won't we, to connect to the "real" world.

T Sure we will, so keep the motor and light cell units handy, and the "de-bounced" pulse and clock generators.

S Will our five-volt signals be OK?

T Yes, the micro circuits are all designed to accept these "TTL-compatible" signal levels. We need to take extra care, however, not to allow excessive voltages to reach our microprocessor system simply because the chips, though very good value indeed, are somewhat more costly than the small i.c.s we've used up to now!

S Can we make the micro control our model lift?

T I hope so, for that's the idea. It will enable us to make a convenient comparison between direct logic control and microprocessor control, since the same sensors ought to be suitable in both cases.

Let's now prepare the ground for looking in detail at our microprocessor system. We've talked a great deal about the need for memory storage circuits, so a practical exercise in the behaviour of a memory store may be welcome.

S Isn't it just the latch we looked at earlier?

T On the whole, yes, but we can go on to consider how to identify a particular part of a memory store, among other things. We'll start with a suitable chip, the 7475 4-bit latch which, as you say, we looked at earlier. Remember, it will only change state to correspond to an input signal if the ENABLE input is at logic 0. Note too that there are two separate enable lines, one for each pair of bistables.

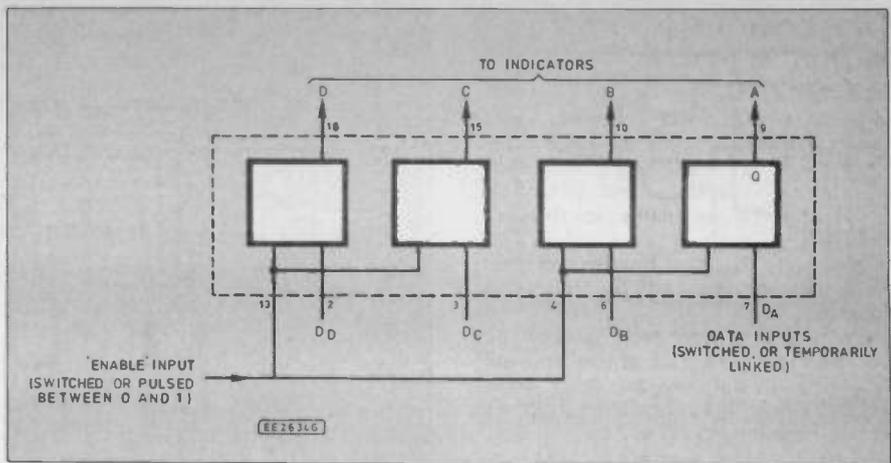


Fig. 8.11 Testing a data latch (7475). Set inputs D_A , D_B etc., to any 4-bit pattern, then note how a pulse to logic 0 on "enable" line will "store" the pattern on the bistable outputs.

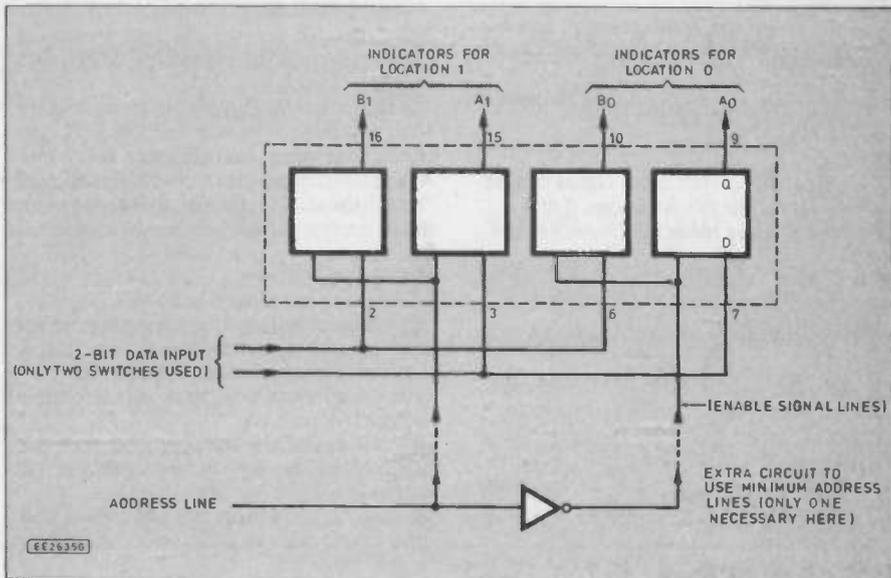


Fig. 8.12. Selecting a particular location using address signal (only two locations here!)

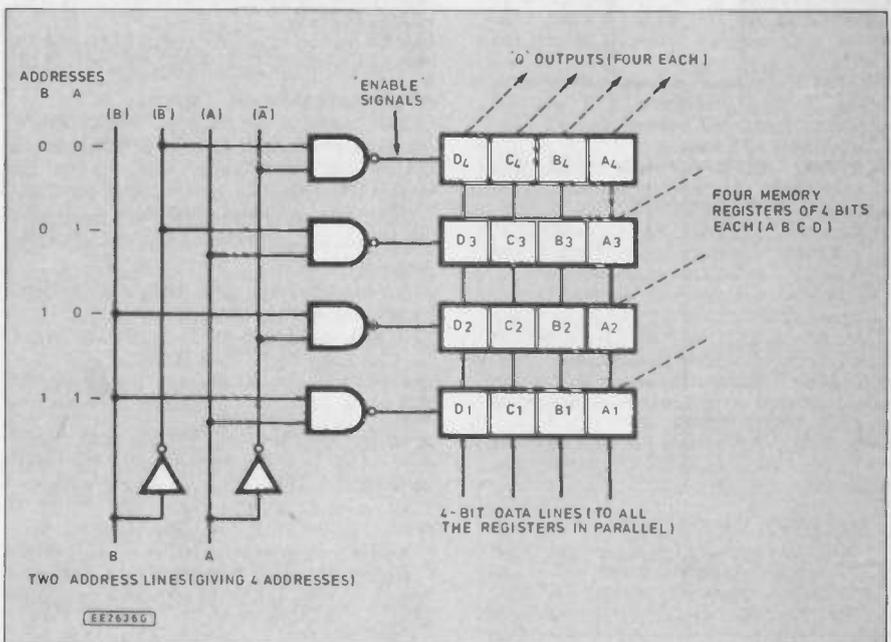


Fig. 8.13. Selecting any one of four addresses (locations).

Exercise 14 What's your address.

Set up the 7475 in your breadboard with an output indicator linked to each Q output (Fig. 8.11) and a switched input to each D (data) pin. You'll also need to be able to switch or plug the enable pins to either logic 0 or logic 1.

Check again that each bistable will store (on Q) the value on its data pin ONLY if it is enabled.

Now we'll re-arrange the "memory" to give just TWO units, each of two bits, and allow ourselves only two data lines (up to now we've used four). This means that we use two-bit numbers only as data.

S Sounds like something in a Western film!

T You know what I mean. The point is that we must now "tell" the chip whether we wish to store a particular data value in the left or right half location. We can choose.

S We need a gate or two (and an extra signal).

T Just so. Let's see if we can draw a possible circuit (Fig. 8.12). You'd better try it to confirm that we can now store our two bits of DATA in either of two LOCATIONS. Right?

S Or left!

T Clever. ... Now the extra signal can be used to "label" the two locations, 0 or 1.

S Is this what we mean by a memory "Address"?

T It is. Our "addresses" here are 0 or 1. That's all. So, make sure. The ADDRESS is a number which identifies a particular LOCATION in the memory store. This location can hold DATA, which is also a number. OK

S So every location in a memory address will have two numbers associated with it/its ADDRESS, and the DATA it may hold?

T Couldn't have put it better. Some of you may wish to go through this exercise

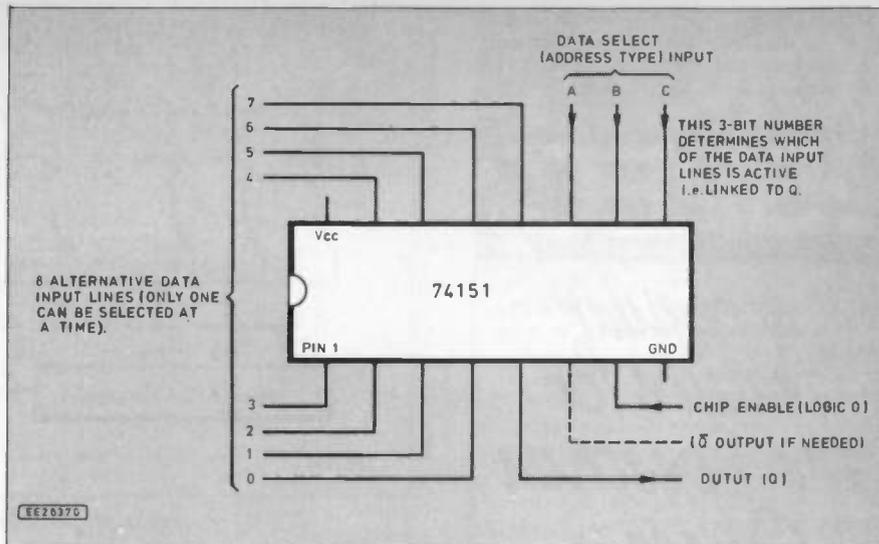


Fig. 8.14. A useful chip for sensing any one of eight inputs e.g. if A and C are at logic 0 and B at logic 1, then Q will follow input (010) i.e. line 2.

again and see how to change the data in either or both of the addresses. Make sure before you leave it.

Notice that the SAME data is sent to both locations, but the "address" signal selects which (if either) accepts it into store. A similar arrangement could be used to "read" the data value from one only of a number of locations.

S A real computer memory store would be much bigger and have more addresses?

T Sure. In the system we shall use, each location will be eight bits wide (to match the micro), and there will be many thousands of them available. But each will have its own address, and will of course contain its own data.

S How could we distinguish several addresses. Wouldn't we need more address signal lines

T Indeed we would, as we'll see. You

could use gates to select the various addresses. If you wish, you could experiment with selector circuits such as these (Fig. 8.13). Of course, yet again there are selector chips available, and they can have uses in control systems, too (Fig. 8.14). Try to find time to familiarise yourselves with some of them on the breadboard, using either indicators or even motors and sensors.

There are so many TTL and other logic chips that we can't possibly mention them all! But they can be fun as well as useful. For example, a long shift register driven by a medium-speed clock, can, with suitable drivers, produce flashing or moving light displays, and musicians could use binary dividers to lower the pitch of a note by one or more octaves.

Our next task, though, will be to study the 6502 microprocessor in action.

MARKET PLACE

FOR SALE ex. equip. toroidal transformer 12-0-12V. 120VA. 5A bridge and 22,000µF electrolytic all for £20 p&p inclusive. Paul Brown, 48 Lanndale Lawns, Springfield, Dublin 24, Eire.

FOR SALE Spectrum service manual Issue 2-Issue 6. New condition £14 includes postage. R. Garas, 147 Seaforth Avenue, New Malden, Surrey KT3 6JW.

EVERYDAY ELECTRONICS 1982-1988. Sell yearly lots only £15 each lot, includes postage. Derbyshire (0332) 862378.

STEREO CASSETTE Ferguson 3280K. Dolby system VU meters. Good cond. low sound hence £10. Tel: 081-647 2633.

FOR SALE Cinerex 8mm dual sound projectors. New boxed £65 or exchange for Commodore 64 Vic-20. David Wood, 17 Boydon Close, Ettingshall, Wolverhampton WV2 2NE.

WANTED old broken computers for college student. Will pay up to £20 including postage. Tel Shaun (0525) 319571.

OSCILLOSCOPE for sale. Lerkakit type with all manuals etc. would suit beginner. Any reasonable offer. Tel: (0373) 826454 evenings.

HANDHELD 22Mc/s AM BC RX. Will accept mini 160 mtrs. receiver of Vibroplex automatic keyer or similar. No callers please. Gebbs, 10 Woodcote Place, Norwood, London DE27.

HAS ANYONE managed to get a Greenwald Aderhoff Dictaphone to work? If so please contact me. Keith Twamley, 25 Davena Drive, Weoley Castle, Birmingham B29 5UL. Tel: 021-426 4471.

WANTED for Spectrum S1A-1 interface adaptor board, TIF1 transceiver interface CB converters. Tel Richard (Abingdon) (0235) 529005.

CAN ANYONE SUPPLY tie-clip mic's 1.5 metre cable. Will buy several if right price. Tel: (0884) 257040.

FLUKE digital meter £50. Avo 8 £110. Clamp meter £16. HV probe £16. Tel: 081-554 2913 6-8 p.m.

COMMUNICATIONS RECEIVER B40D 0.64-30MHz. AM/CW/SSB 240V. £60. 70cms beams 21 ELE £20. 12 ELE X Crossed £16. Tel: (0562) 743253.

BARGAIN TRS 80 Level II comp. monitor, interface, manuals also Dragon 32 with I/O interface with manuals £80 o.n.o. W. Daley, 071-582 7839.

CROTECH 3132 dual trace 20MHz 'scope with X10 probe and leads. Hardly used £220 o.n.o. Tel: (040377) 545.

SOLDER 2½kg reel 18 s.w.g. 60/40 Ersin Multicore £25. Tel: (0908) 502425.

WANTED solar panels, any condition, for my garden light project. Please ring Bob on Woking (0483) 755463 evenings.

WANTED Power supply (2 pin variety) and cassette recorder for VIC20. Must be fairly cheap! Matthew Aldridge, 2A West End Road, Silsoe, Beds. MK45 4DU. Tel: (0525) 60743.

WANTED BM81LS95N, DM81LS96N, two F2102LIPC RAM chips, 4116 DRAM chip. P. A. Murphy, 72 Southview Road, Carlton, Notts NG4 3QL. Tel: (0602) 873793.

BBC MODEL B with or without extras wanted by student. Will pay £130 max. No rubbish please. Colin O'Regan, 66 Meadow Grove, Black Rock, Ireland.

BEGINNER to electronics requires com-

ponents for nothing or a small price. Will pay for p&p. 109 Shenley Road, Bletchley, Milton Keynes MK3 7AS.

SWAP YAESU FDRX400 SW RX or Advance OS1000A DB scope, or Yamaha DSR100 for Amstrad 8512. Lancs (0744) 27067.

PENFRIEND University student looking for penfriends in the field of electronics, computer and communication. Reza Haseli, P.O. Box 336/71645, Shiraz 71645, I.R. Iran.

ADVANCE OS1000 twin trace Oscilloscope complete with probes, manual, very good condition. Bargain at £175.00. A. S. Davy, Springclove, Crestlands Corner, Alresford, Essex CO7 8AF.

SUMA VOX75 voice activated transmitter - advertised in EE has been assembled and is working well £15. John Gold, 35 Cavendish Place, Jesmond, Newcastle-upon-Tyne NE2 2NE.

WANTED, Leak valve preamp, power amp and pick-up. Garrard 301. Wharfedale corner speaker and cabinet (0745) 825036.

CIRCUIT please for 2nd parallel hand held r/control computer keyboard hard wired (have neck disability) DDS 081-550 7708

WANTED i.c. TDA1050 to complete a project. Price to L. Myers, 70A Lawford Road, London N1 5BL.

FOR SALE. EE Nov. 71 to Dec. 82. PW May 66 to Dec. 84. HE Nov. 78 to Dec. 82. Haywards Heath 416603.

WANTED Bearcat 220 switch pad for freq. control. Tel: (0642) 678869.

WANTED information on Mazda valves: EGC83/12AX7, ECL86/6GW8 and EM87/6HU6. Please write: N. A. Barnes, 30 Water Royd Crescent, Mirfield, West Yorkshire WF14 9SY.

ON SPEC

a regular feature for the Spectrum Owner...

by Mike Tooley BA

IN LAST month's instalment of "On Spec" we introduced the Spectrum Music Group and took a first look at MGT's SAM Coupé "Communications Interface". This month (in an effort to tempt readers to return to their soldering irons!) we present the first in a series of interface projects for the SAM Coupé. This project takes the form of an 8-Channel Analogue to Digital Converter (ADC).

SAM ADC

Regular readers may recall that I described the construction of an eight channel ADC for the Spectrum in *Everyday Electronics* for December 1986. This interface was based on a 7581 ADC chip and used just three other devices to provide a total of eight analogue input channels.

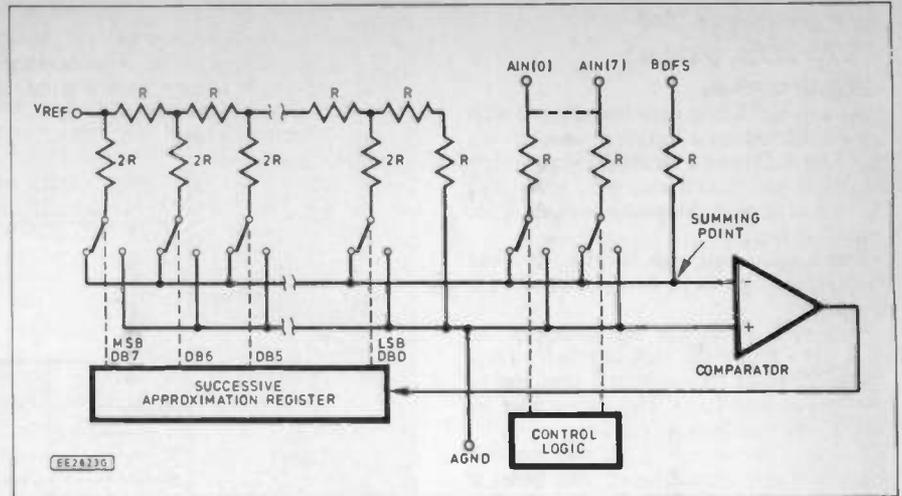


Fig. 3. Simplified internal circuit for the DAC.

Judging from the correspondence received, this simple interface attracted a good deal of interest from readers, many of whom reported excellent results when using it. With this in mind, I recently set about re-designing the unit for use with the SAM Coupé.

THE 7581

The 7581 (employed in our original 8-Channel Analogue interface) provides a simple solution to the need for a multi-channel analogue input capability. The chip is microprocessor compatible and incorporates its own internal 8x8 dual port memory buffers which are used to store the results of conversions on each channel until they are ready to be read by the microprocessor.

The simplified internal arrangement of the 7581 is shown in Fig. 1. The device contains a single 8-bit DAC and the eight analogue inputs are multiplexed before application to the internal ADC arrangement which employs successive approximation techniques. The 7581 is housed in a

28-pin DIL package, the pin connections for which are shown in Fig. 2.

The 7581 DAC is based on a conventional R-2R ladder network, as shown in Fig. 3. In sophisticated circuits, comparator offset may be trimmed out by means of the bipolar offset input (BDFS).



Conversion of a single channel takes 80 clock periods with a complete scan through all eight channels taking 640 clock cycles. With the 1MHz clock used in this latest interface circuit, conversion time for one channel amounts to 8µs whilst a complete scan of all eight channels requires 0.64ms.

When channel conversion is complete, the successive approximation register's contents are transferred into the appropriate internal dual port RAM location. The contents of this RAM can later be examined by placing the appropriate binary address pattern on the address latch select lines (A0, A1, and A2) whilst, at the same time, taking the CS line low.

To ensure that memory updates only occur when the host microcomputer is not addressing the converter's memory, automatic interleaved direct memory access (DMA) is provided by on-chip logic.

Fig. 1. Internal arrangement for the 7581.

Fig. 2. Pin connections for the 7581.

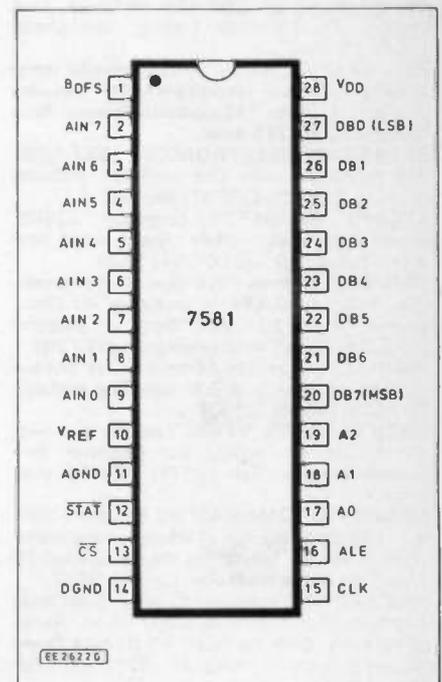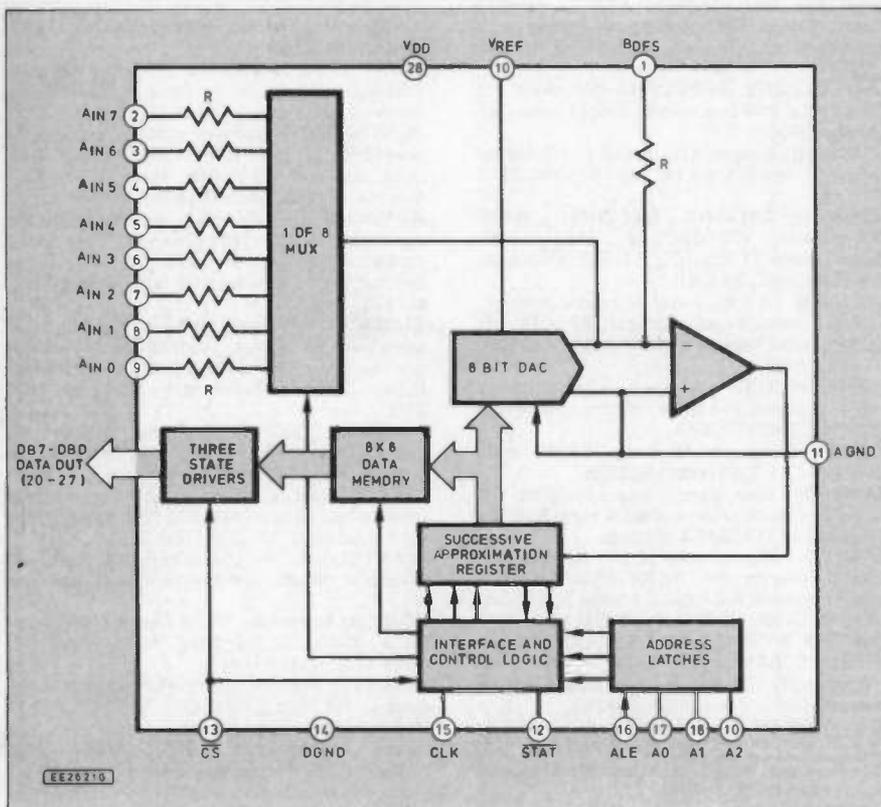

8-CHANNEL ANALOGUE-TO-DIGITAL CONVERTER

The complete circuit of a 7581-based SAM Coupé 8-Channel ADC is shown in Fig. 4. Address decoding for the CS line is provided by IC2 and IC3. This arrangement ensures that the output of the 7581 is only placed on the data bus when address lines A3 to A6 are all high with A7 and both RD and IORQ simultaneously low.

The remaining three address lines (A0 to A2) are taken to the 7581's address latch select inputs (where they are used to select individual analogue channels). This address assignment of the ADC is shown in Table 1.

A simple Schmitt oscillator, with buffered output, is formed by IC2f and IC2e. This configuration provides a square wave clock input to the 7581 at a frequency of approximately 1MHz (the precise frequency of this signal is unimportant).

The negative reference voltage required by the 7581 is provided by IC4 (a 555

timer) and associated components which form an astable oscillator. This arrangement produces a square wave output at approximately 7.25kHz which is fed to a voltage doubler arrangement provided by diodes D2 and D3.

The negative rectified output is filtered and then applied to a potential divider arrangement in order to produce a clean voltage reference of 2.55V at pin-10 of IC1. Note that 2.55V is chosen as the reference voltage (rather than the more usual 10V which was employed within our earlier Spectrum interface) in order to make the circuit operate in discrete steps of 10mV. This helps keep the software straightforward!

CONSTRUCTION

The eight channel ADC is assembled on a piece of stripboard measuring approximately 90mm x 90mm. The precise dimensions of the board are unimportant provided that it has a minimum of 32 copper tracks.

The DIN 41612 indirect edge connector (a plug type with rows *a* and *c*) should be

Table 1: Address assignment for the SAM Coupé 8-Channel ADC

Channel No.	(binary)	Address (decimal)	(hex.)
1	01111000	120	78
2	01111001	121	79
3	01111010	122	7A
4	01111011	123	7B
5	01111100	124	7C
6	01111101	125	7D
7	01111110	126	7E
8	01111111	127	7F

Fig. 4. Complete circuit of the SAM Coupé 8-channel ADC.

COMPONENTS

Resistors

R1	220
R2, R12	470 (2 off)
R3-R10, R13	1k (9 off)
R11, R14	10k (2 off)

All 0.25W 5% carbon

See
**SHOP
TALK**
Page 468

Capacitors

C1, C8	47µ p.c.b. elec. 16V (2 off)
C2	100n polyester
C3	1n5 polystyrene
C4 to C6	10µ p.c.b. elec 16V (3 off)
C7	10n polyester

Semiconductors

D1	red l.e.d.
D2, D3	OA91 germanium signal diode (2 off)
IC1	7581 8-bit 8-channel ADC
IC2	74LS14 Schmitt Hex inverter
IC3	74LS30 8-input NAND gate
IC4	555 timer

Miscellaneous

Low-profile d.i.l. sockets, 8-pin, 14-pin, 28-pin; 10-way 0.1in pitch p.c.b. mounting input socket; stripboard, 0.1in matrix (with 32-tracks) measuring approx. 90mm x 90mm; 64-way indirect edge plug DIN 41612 (with rows *a* and *c* (e.g. RS stock code 468-119)

Approx cost guidance only

£20

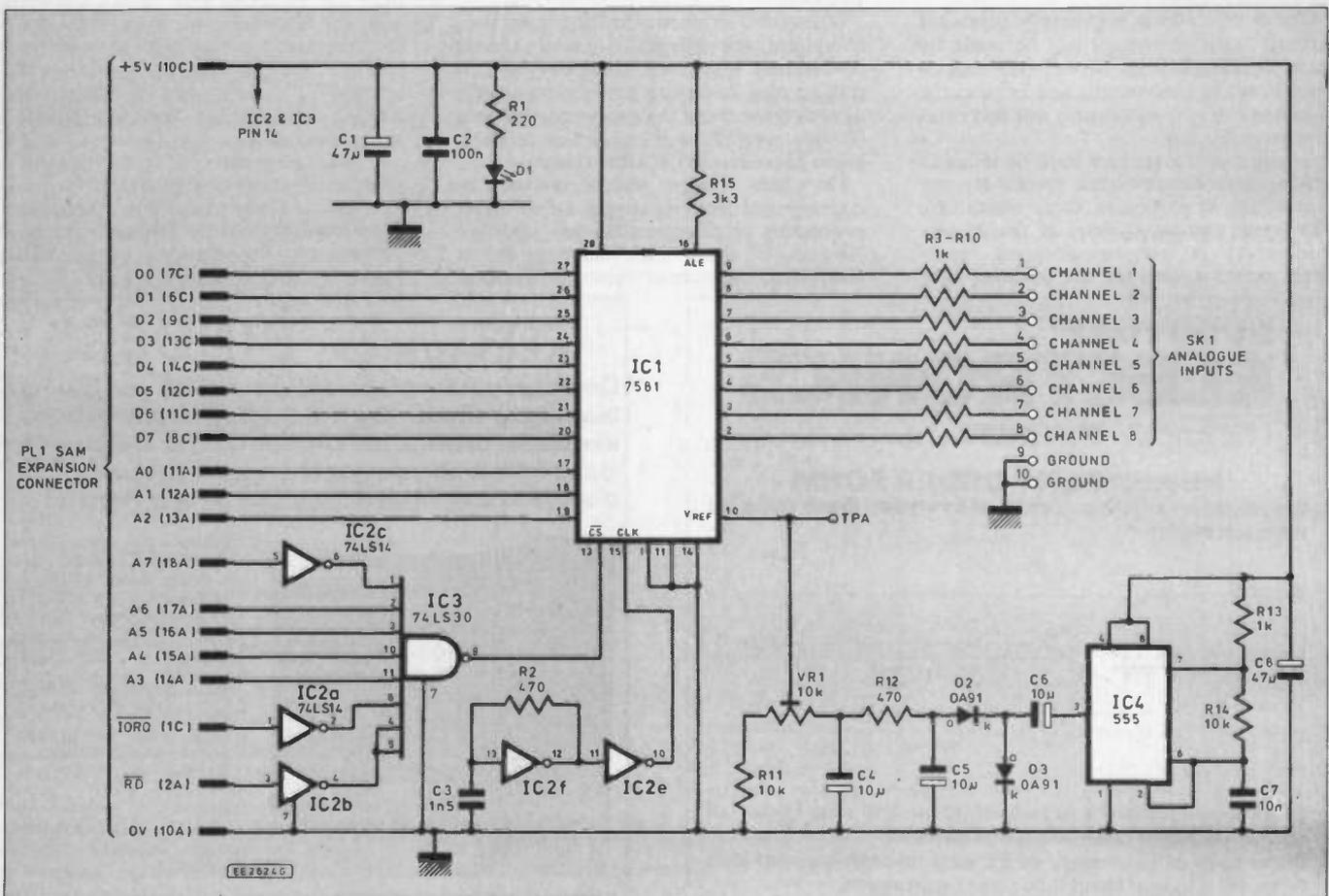


Table 2: Individual pin assignments for the SAM Coupé expansion connector

Pin	Signal	Pin	Signal	Pin	Signal	Pin	Signal
1A	DBDIR	1C	IORQ	17A	A6	17C	A14
2A	RD	2C	MREQ	18A	A7	18C	A13
3A	WR	3C	HALT	19A	A8	19C	A12
4A	BUSAK	4C	NM1	20A	A9	20C	A11
5A	WAIT	5C	INT	21A	A10	21C	DISC 2
6A	BUSREQ	6C	D1	22A	MSEINT	22C	ROMCS
7A	RESET	7C	D0	23A	XMEM	23C	EARMIC
8A	CM1	8C	D7	24A	8MHz	24C	DISC 1
9A	REFRESH	9C	D2	25A	RED 1	25C	PRINT
10A	0V	10C	+5V	26A	GREEN 1	26C	BLUE 1
11A	A0	11C	D6	27A	CSYNC	27C	ROMCSR
12A	A1	12C	D5	28A	SPEN	28C	AUDIO RIGHT O/P
13A	A2	13C	D3	29A	BLUE 0	29C	AUDIO LEFT O/P
14A	A3	14C	D4	30A	RED 0	30C	COMP. VIDEO
15A	A4	15C	CPU CLK	31A	BRIGHT	31C	GREEN 0
16A	A5	16C	A15	32A	+5V	32C	0V

Note that Row A is at the bottom and Row C is at the top. Pin 1 is at the left and pin 32 is at the right (see Fig. 6).

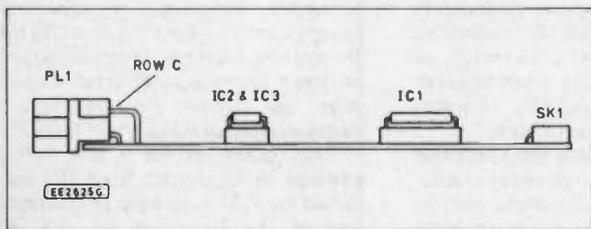


Fig. 5. Mounting the 64-way indirect edge plug.

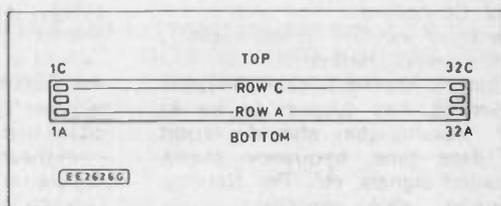


Fig. 6. Pin numbering for the SAM Coupé expansion connector.

fitted to the extreme edge of the board. The board will fit flush to the base of the connector as shown in Fig. 5. The pin numbering for the Coupé's expansion bus is shown in Fig. 6 whilst the individual pin assignments are given in Table 2.

Component layout is generally uncritical though some economies can be made by carefully planning the layout in advance of mounting the components and i.c. sockets. Readers are advised to carry out this exercise on paper first!

In any event, great care must be taken to ensure that all unwanted tracks are cut (including, in particular, those which link the upper and lower sides of the 28-way connector). A purpose designed "spot-face" cutter is ideal for this purpose, or if

such a tool is not obtainable, a small sharp drill bit may be used. Links on the underside of the board should make use of appropriate lengths of miniature insulated wire (of the type normally used for wire wrapping).

When the stripboard wiring has been completed, the integrated circuits should be inserted into their respective sockets (taking care to ensure correct orientation of each device) and the entire board should be very carefully checked before attempting to connect it to the SAM Coupé.

The Sam Coupé should *always* be disconnected from its supply *before* either connecting or disconnecting *any* interface module. If all is well, when power is re-applied, the normal copyright message

should appear. If not, disconnect the power, remove the interface and check again!

Next Month: We shall describe the procedure for adjusting and testing the ADC and will describe some basic applications for the interface (together with software routines). For good measure, we shall also attempt to dispell some of the mystery which surrounds the Spectrum BASIC's logical operators.

In the meantime, if you have any problems, queries or suggestions for inclusion in *On Spec*, please don't hesitate to drop me a line: Mike Tooley, Faculty of Technology, Brooklands College, Heath Road, Weybridge, Surrey, KT13 8TT.

EVERYDAY
ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

NEWSAGENT ORDER FORM

Please reserve/deliver a copy of *Everyday Electronics* for me each month.

Signed

Name and Address
(BLOCK CAPITALS PLEASE)

.....

.....

Everyday Electronics is published on the first Friday of each month and distributed by Seymour.
Make sure of your copy of EE each month—cut out this form, fill it in and hand it to your newsagent.

EVERYDAY
ELECTRONICS BINDERS

Don't let your valuable issues of *EE* get binned, burned or bitten (by the dog!). Get one of our exquisite orange hard-back binders, slip each issue into it as you get them and you will always know where they are — we hope!



Binders to hold one volume (12 issues) are available from Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH for £4.95 (£6.95 to European countries and £9.00 to other countries, surface mail) inclusive of postage and packing. Payment in £ sterling only please.

Binders are normally sent within seven days of receipt of your order but please allow up to 28 days for UK delivery — more overseas.

...REPORTING AMATEUR RADIO...

TONY SMITH G4FAI

INTRUDER WATCH

While various frequency bands are designated for amateur use on an "exclusive" basis they often suffer from interference caused by transmissions from non-amateurs. Some of these illegal transmissions are deliberate, some are unintentional.

The International Amateur Radio Union Monitoring System, formerly known as "Intruder Watch". Deals with this problem under the leadership of an International IARUMS co-ordinator who has access to the International Frequency Registration Board (IFRB) through the IARU Council. Each IARU Region has a Regional Co-ordinator and within the Regions most national radio societies have a National Co-ordinator.

The idea is that individual amateurs hearing what they suspect to be an intruder transmission should report details, date, time, frequency, mode, identification signals, etc. The National Co-ordinator, after assessing these reports, passes on details to his national licensing authority with a request for action. At the same time he reports to his Regional Co-ordinator who passes on appropriate details to the Co-ordinators of the other two Regions enabling the situation to be acted on world-wide if necessary.

DIVERSE REPORTS

In the UK the RSGB Monitoring System receives little publicity but in other countries individual amateurs are constantly urged to send in reports. In *Amateur Radio*, journal of the Wireless Institute of Australia, for instance, details are published monthly of intruders as diverse as taxi cab radio systems in Hong Kong, CBers from Asia and Indonesia, the Voice of America, the Chinese Diplomatic Service, Thai fishing boats, Russian broadcasts and Vietnamese News Agency bulletins from around the world.

On one occasion it was reported with some glee that a Russian intruder in the 40m band had been compelled to move frequency because of interference from another Russian station which was jamming an illegal station from another country! It was a limited celebration however as the frequency moved to was also within the amateur band!

Even when identified it is not an easy task to stop the offending transmissions. Some stations operate with official blessing and complaints or pressure via official channels have no effect.

Nevertheless, the Australians reported some notable successes when they celebrated the 20th anniversary of their Intruder Watch two years ago. These included the removal of Australian Defence Forces stations using obsolete transmitters causing harmonic radiation; the removal of French Polynesian R/T services in the 40m band; the removal of Chinese RTTY stations; and the removal

of licensed amateurs working maritime mobile and passing traffic on behalf of commercial interests.

Every victory is hard won, requiring hours, weeks or months of persistent monitoring and reporting, with the solution often plagued by diplomatic and political considerations. It is hard to realise sometimes that amateur radio is "just a hobby"!

ESPERANTO AND THE AMATEUR

At the first Congress of the International Amateur Radio Union, in 1925, Esperanto was recommended as a standard auxiliary language for radio telephony, for translations from periodicals and for use at Congresses. According to "World at their Fingertips" (the History of the RSGB), however, the Scandinavian representatives "held out for English claiming it to be the easiest to learn."

In theory an international language like Esperanto is ideal for amateur radio. Despite what the Scandinavians said in 1925, it is claimed to be easier to learn than any other language, having straightforward grammar and construction with no irregular features. Today, English is the assumed common language of amateur radio, but contacts with foreign stations demonstrate that in many cases what knowledge of the language they have does little to advance the claim that amateur radio breaks down barriers and generates international friendship.

I am involved in publishing a small international magazine concerned with Morse telegraphy. I receive many letters and articles from foreign subscribers who have what would normally be termed a "good command" of English but I often have to put a lot of work into "Anglicising" their contributions to make for good reading and comprehension. To my mind, despite the ever-increasing amount of English being taught worldwide, the need to use someone else's language is the greatest barrier to clear understanding between individuals.

With this background I was interested to learn recently about the activities of the Internacia Ligo de Esperantistaj Radio Amatoroj, the International League of Esperantist Radio Amateurs, or ILERA.

NO INTERPRETERS!

Last year the International Esperanto Congress was held in the UK, at Brighton. 2,400 delegates attended from 54 countries - without the need for a single interpreter!

ILERA set up a special event station, GBOUKE, operated by one French, one American, and three British Esperantists. The station had 183 contacts during which the operators took the opportunity to explain to non-Esperantists the value of their international language, and had 35 contacts overseas in Esperanto, including one with the President of ILERA, in Central Siberia, and one with ILERA's Secretary, in Hungary.

The objectives of ILERA are to encourage the use of amateur radio by existing Esperantists; to encourage radio amateurs to learn and use Esperanto; to organise nets and contests to keep members in touch with each other. Also, to establish a special event station at each Esperanto congress; to standardise Esperanto vocabulary of amateur radio matters; and to publish a quarterly news bulletin.

Esperanto was established in 1887 to make it easier for people of different countries to communicate with each other. It is not intended to replace any national language but to provide a simple secondary language to overcome language barriers. It seems an ideal medium for an international fraternal activity like amateur radio and a great opportunity was lost when the fledgling IARU decided against adopting it in 1925.

The following are a few "standard" phrases in Esperanto from the list published by ILERA to help encourage more use of the language on the amateur bands. In pronunciation there is only one sound to each letter, and emphasis is always given to the next-to-last syllable of a word.

CQ CQ CQ. Anyone in the Esperanto net? *Iu ajn, iu ajn, iu ajn. Generala alvoko en la esperanta reto?*

My shack is a small room at the top of the house. *Mia kabano estas malgranda cambro en la supro de la domo.*

Thanks for the contact. *Dankon pro la kontakto.*

I will QSL via the bureau. *Mi sendos konfirmkarton per la buro.*

If you want to hear Esperanto being spoken, listen to the French ILERA net on 7.066MHz at 0830 GMT, weekdays, or the international net on 14.266MHz around 1230 GMT on Sundays and Mondays. For more information about ILERA, contact *Barry Foreman GOEXS, 10 Wilmington Close, Brighton BN1 8JE.*

For those interested in learning Esperanto there is a free introductory postal course available from *The Esperanto Centre, 140 Holland Park Avenue, London W11 4UF. Tel: 071-727 7821.*


NOVICE LICENCE IN 1991

The DTI published a final draft of the proposed novice licence on 19th April. Work is in hand to set up arrangements for the training and examination of potential licensees and it is hoped the first licence will be issued in early 1991.

Applicants will be required to complete a practical training course run by the RSGB. There will be no minimum age for licensees and it is envisaged that the licence fee will be waived for those under 21.

Fees will be reviewed annually but it is intended to keep them as low as possible. I will provide more information on this important new entry route into amateur radio as soon as it becomes available.

THE TESTER

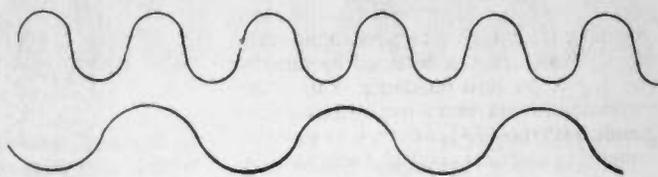

GEORGE HYLTON

*A handy bench aid with many uses
Connect it to a circuit and it makes
the circuit oscillate.*

THE TESTER performs only one trick, but it does it well. Connect it to a circuit and it makes that circuit oscillate. Simple, but very useful. It can help you to measure inductance, capacitance and Q . It can provide r.f. or a.f. test signals. It can act as a selective amplifier. After many years I still find new uses for it.

Reduce to essentials The Tester is a box containing a variable resistance R_v (Fig. 1) and equipped with input (X) terminals and output terminals. In use, the component or network under test is connected to X and R_v adjusted until the circuit just oscillates. The effective resistance of the circuit can then be read off the scale of R_v .

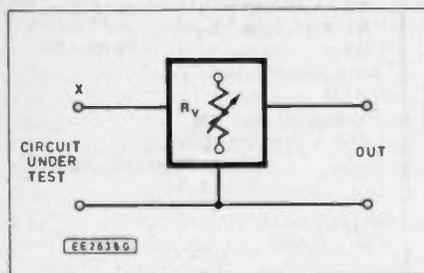


Fig. 1. Basic arrangement.

If, for example, you connect an unmarked resistor to X and adjust for the threshold of oscillation (indicated by listening with an earphone, for example), the scale tells you what its resistance is. Not very impressive? An ohmmeter does the job more easily? True, but if instead of a resistor a parallel-tuned LC circuit is connected to X the same adjustment of R_v tells you its effective resistance at its resonant frequency. You can't find that out with an ohmmeter.

CALIBRATION

Even uncalibrated The Tester can do some useful work, but it becomes more versatile if R_v is given a scale marked with resistance values. These are the resistances which when connected to X just allow the circuit to oscillate at that setting of R_v .

Calibration is child's play. After an initial "set infinity" adjustment (described later) you connect an ordinary 10k resistor to X (Fig. 2), set for the threshold of oscillation (with resistors this is at audio frequency and can be detected with a high impedance earphone at the output) and mark the scale of R_v "10k". Now repeat with 1k and 100k and you have the three major calibration points. You can get some intermediate points by using other resistor values.

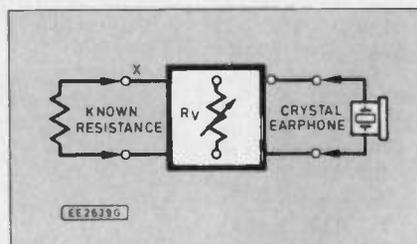


Fig. 2. Calibration method.

Since R_v is a log. law potentiometer its scale is nonlinear and may be quite cramped in places, so there's not much point in aiming at fine graduations. The minimal useful calibration is 300, 1k, 3k, 10k, 30k, 100k, 300k. If you have only E12 values you can use 330, 3k3, etc. This gives a scale which is unconventional but quite usable. (If you like, you can make 300 ohms by connecting 330 and 3k3 in parallel, and 3k by paralleling 3k3 and 33k, and so on.)

The lower limit of measurable resistance depends on the gains of the transistors used and on the supply voltage. With a voltage at the low end of the usable range (6V to 20V) some units go down to 100 ohms, some only to 150 ohms or 200 ohms. The upper end goes to infinity, but as with ohmmeters is very cramped and not very readable above about 300k.

Ordinary five percent tolerance carbon film resistors are quite accurate enough for the calibration. If you ever want to make precise measurements, use the resistance-box substitution method described later.

INPUT ARRANGEMENTS

The handiness of the circuit is enhanced by providing some extra facilities at the input (Fig. 3). Two pairs of input terminals are connected to a changeover switch ($S1$) which selects the operative pair. This enables one circuit or component to be compared with another and is useful for matching and calibration work.

In its essential form The Tester works properly only with circuits at X which are resistances or which behave like resistances at some frequency. If a purely reactive element such as a capacitance or inductance is connected to X , oscillation is still obtainable, but the significance of the critical R_v is no longer clear. It usually helps, in such cases, to turn the reactance into a tuned circuit by connecting a coil or capacitor across it. This is done by $S2$.

A capacitance at X can now be resonated with internal inductance standard L_s , or an inductance at X with internal capacitance C_s . Only one C_s and L_s are shown in Fig. 3, but of course you can usefully provide a selection. At least one position of $S2$ must be left free so that tests which do not require an internal shunt can still be made.

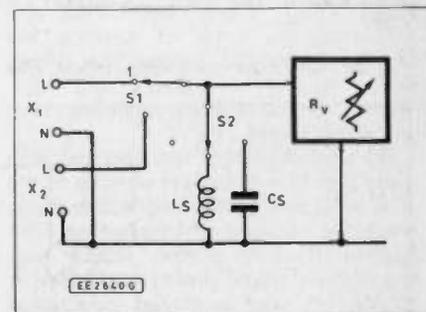


Fig. 3. Input arrangements. $S1$ enables one unknown (X) to be compared with another. $S2$ places inductances or capacitances across the input to assist measurement.

HIGH FREQUENCIES

As noted earlier, the oscillation is at a.f. when X is a resistor. An earphone can then be used to detect the onset of oscillation. But when X is an LC circuit with a resonant frequency above audio an ear-piece is not usable. You need a high-

frequency voltmeter, a good oscilloscope or, failing these, a radio receiver.

When searching for an r.f. output with a receiver an insulated wire from the live output terminal, wrapped a few turns round the whip aerial will inject plenty of signal. A direct connection may deliver too much and damage the receivers input transistor. Searching can be eased by initially turning R_v to zero resistance. This is the condition for maximum oscillation and the result, with most LC circuits, is to provoke squegging (oscillation which turns itself on and off at an audio frequency).


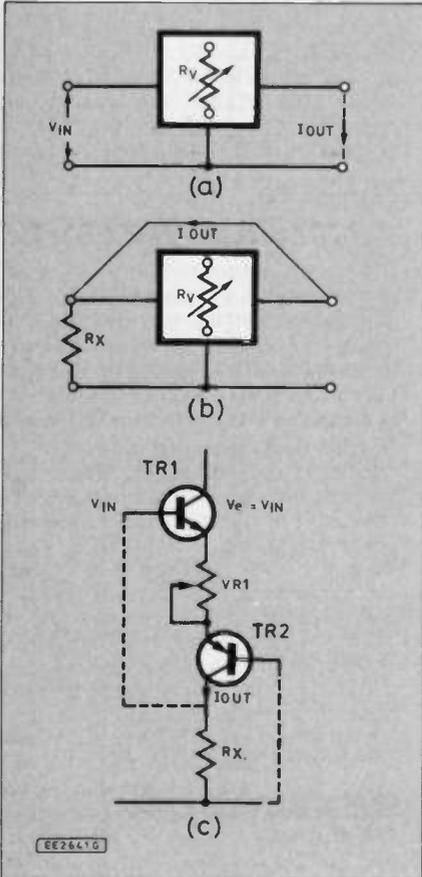
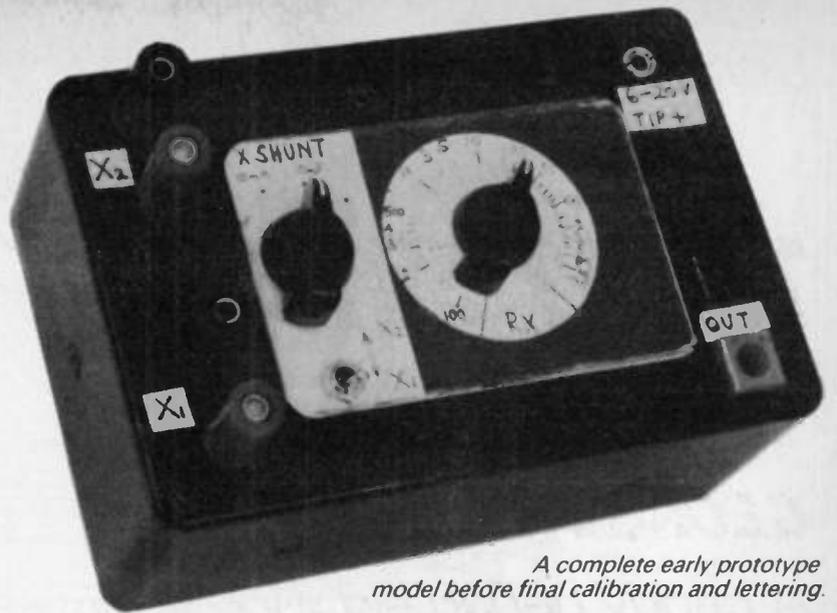


Fig. 4(a) Essential scheme, (b) feedback added, (c) basic oscillation circuit.

Fig. 5. The Tester complete circuit. The last three transistors form a buffer amplifier.

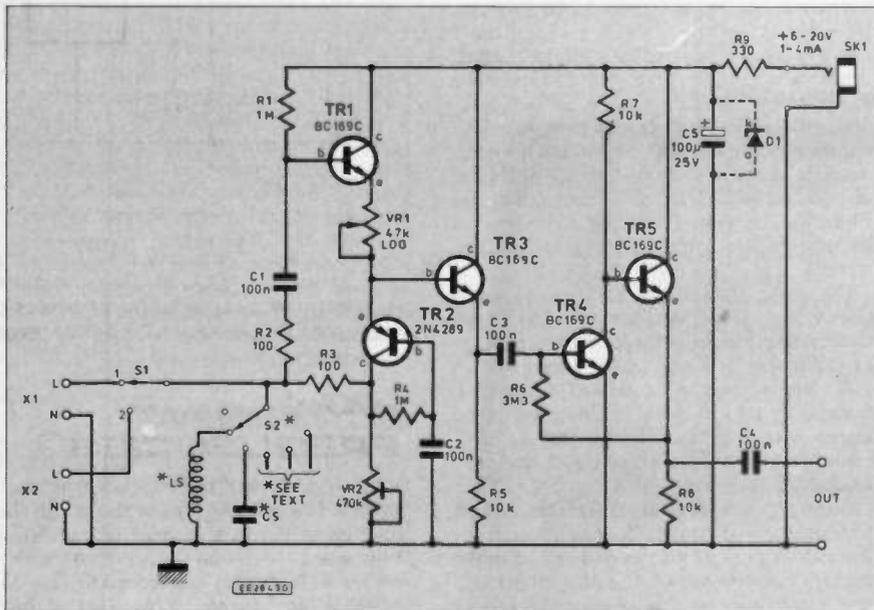

A complete early prototype model before final calibration and lettering.

The resulting deeply-modulated signal, rich in sidebands, is easy to find. Once found you reset R_v to give a pure signal, detectable by the "mush" it produces in the receiver. Whistles are also produced as The Tester interacts with other signals.

HOW IT WORKS

In Fig. 4a, an input voltage is applied to a "black box" which contains (among other things) a variable resistance R_v . The effect of the other things is to make the black box give out a current. The size of this current is V_{in}/R_v .

In Fig. 4(b), an unknown resistance R_x is connected to the input. To create an input voltage (V_m), the output current (I_{out}) is fed back through R_x . For V_m and I_{out} to exist the circuit must oscillate. Calculation shows that oscillation just starts when R_v is marginally less than R_x .

The essentials of the circuit in the black box are shown at Fig. 4(c), with bias and d.c. blocking components omitted for clarity. Here TR1 is an emitter follower with a voltage gain of 1. Thus the signal voltage at the emitter (V_e) is the same as V_m . This drives a current I_e through R_v . (Thus $I_e = V_m/R_v$).

This current is the input current to TR2, a common-base amplifier with a current gain of 1. Thus $I_{out} = I_e$, and $I_{out} \cdot R_x = V_m$. The condition for oscillation is $R_v = R_x$, or rather this is the borderline beyond which any reduction in R_v , however small, gives oscillation.

In practice, the gains for TR1 and TR2 are slightly less than 1, but this is allowed for in the calibration.

In the complete circuit (Fig. 5) the oscillator part is followed by a buffer amplifier which delivers an output signal at low impedance. The Tester will oscillate at frequencies up to about 30MHz, but its accuracy falls off with rising frequency.

COMPONENTS

Resistors

- R1 1M
- R2, R3 100 (2 off)
- R4 1M
- R5 10k
- R6 3M3
- R7, R8 10k (2 off)
- R9 330

All 0.25W 5% carbon

Potentiometers

- VR1 47k or 50k log.
- VR2 470k or 500k min. skeleton preset, lin.

Capacitors

- C1 to C4 100n polyester (C280) (4 off)
- C5 100µ elect. 25V

Semiconductors

- TR1, TR3, TR4, TR5 BC169C npn (4 off)
- TR2 2N4289 pnp
- D1 Zener diode, see text

Switches

- S1 s.p. changeover
- S2 s.p. wafer switch with three or more ways (see text)

Miscellaneous

Metal case (see text); printed circuit board available from *EE PCB Service*, code EE696; six terminals for input and output connections; jack socket for power input; knobs for S2, VR1; solder tags, solder etc.

Approx cost guidance only

£14

CONSTRUCTION

A printed circuit helps to ensure repeatable results and one has been designed. The component layout and full size copper foil master pattern is shown in Fig. 6. This board is available from the *EE PCB Service*, code EE 696.

Two points should be noted. First, the layout is for transistors with a "central collector" leadout arrangement. While in principle any small high-gain general purpose silicon transistors may be used the leads of some types will have to be bent to suit the layout. It helps if TR1 and TR2 have roughly the same current gain (H_{FE}) but close matching is not necessary.

Secondly, the layout envisages that the log. law pot VR1 is mounted on the "wrong" side of the p.c.b.; i.e. on the copper side. The clamping nut then presses the metal case to the copper to earth it. Another unconventional but useful arrangement (Fig. 7) is to solder the pot's case to the copper and run leads to the pads as shown. The potentiometer then carries the p.c.b. on its back and no other mounting arrangements are needed.

If you don't like this (or you must use a p.c.b. mounting pot with no bush), the pot can be placed on the component side of the board in the conventional way. However, the copper pattern then selects the wrong pair of tags (B and C instead of A and B) and this gives a "fierce" change of resistance as the spindle is rotated.

To avoid this you can either bend the tags clear of the copper and run leads from A and B to the p.c.b., or solder the tags to the board and make a minor change (Fig. 8) to the layout. You could also avoid the problem by using a reverse log. pot, if you can find one.

There are some spare pads to allow the use of different styles of miniature preset (VR2) and for the addition of a Zener diode across the smoothing capacitor C5.

SETTING UP

After assembly, connect a d.c. supply in the range 6V to 20V (the current drain is modest and a battery may be used) and monitor the output with a crystal (or high impedance magnetic) earphone. With no shunt across the input and VR2 max, a ticking, buzz or whistle will be heard at most positions of VR1.

Set VR1 fully clockwise (maximum resistance). Mark its scale with this end point of travel. Adjust preset VR2 until the oscillation just stops. Mark the point on the scale of VR1 where it restarts as "infinity". You can now calibrate VR1 as described earlier, using five percent (or better) resistors, or a resistance box if you have access to one. (The wirewound resistors in some old boxes are significantly inductive, especially the lower values. To prevent this from upsetting accuracy, put a capacitance of about 10n across the box, but remove it when using more than 1k.) Note that VR1 works "backwards"; clockwise rotation eventually prevents oscillation.

SCREENING

It is advisable to use a metal cabinet to minimise hand effects and hum pickup. If this is not possible and a plastic cabinet has to be used, line it with metal foil or sheet, connected to battery negative. A suggested method can be seen in the photograph on the next page.

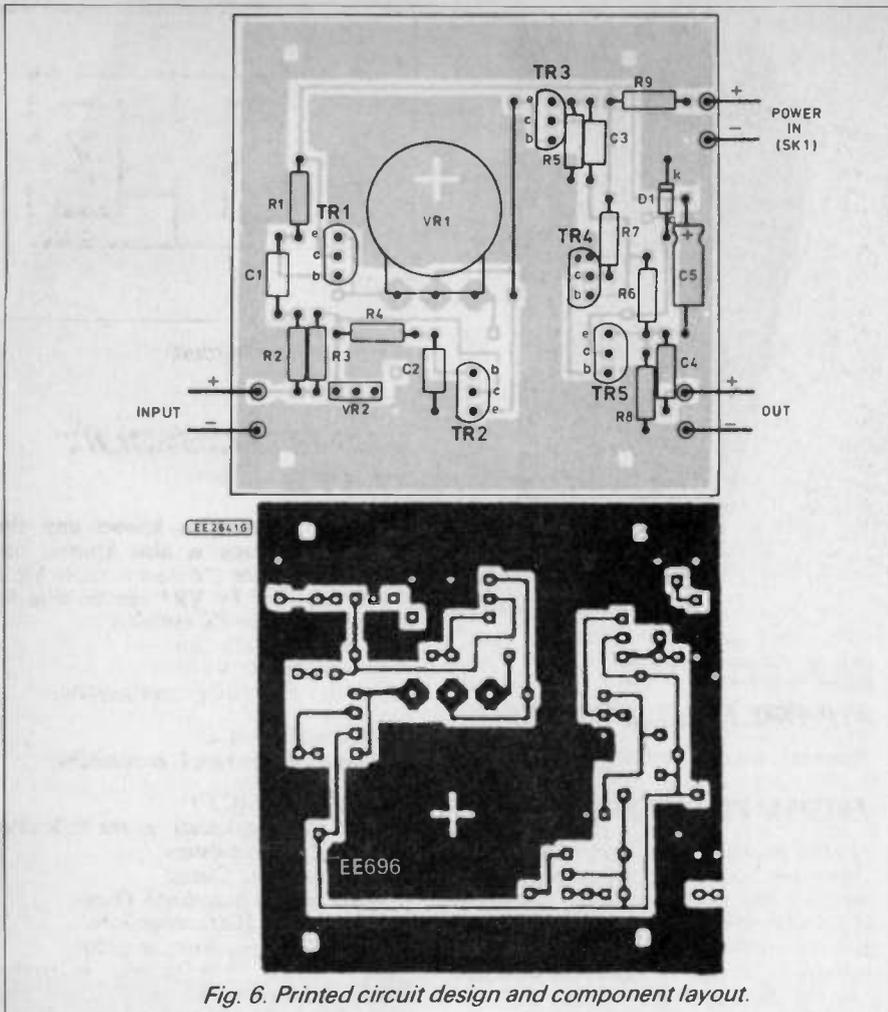


Fig. 6. Printed circuit design and component layout.

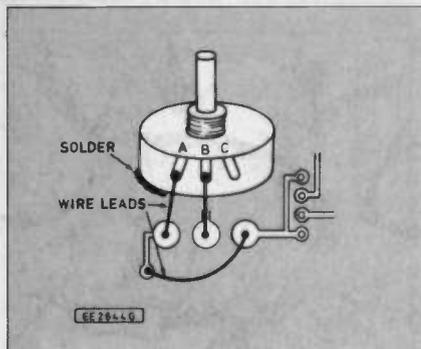


Fig. 7. Mounting the potentiometer so as to carry the p.c.b.



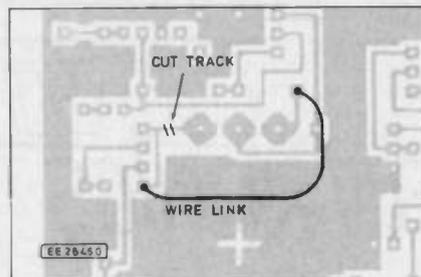


Fig. 8. Track modifications for conventional potentiometer mounting (viewed from track-side).

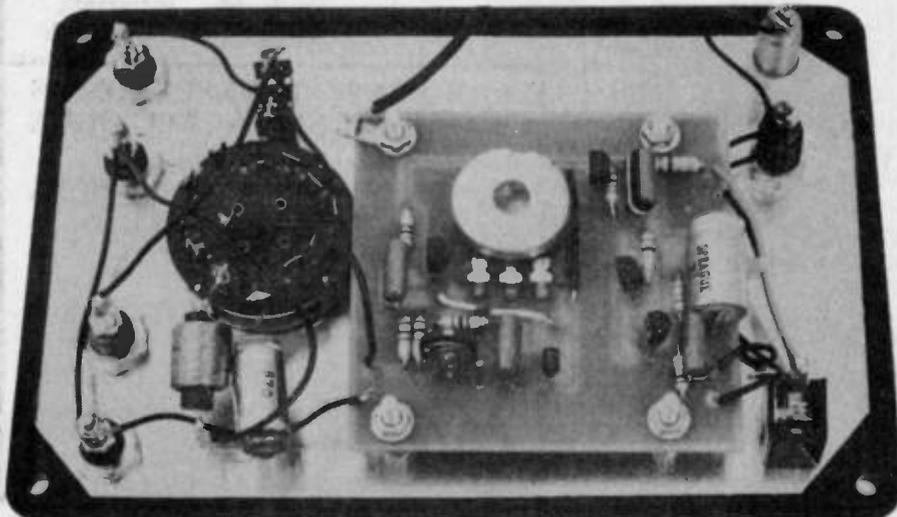All the components, including the p.c.b. are mounted on the lid of the case. The lead from the solder tag goes to the "screening" connection lead.



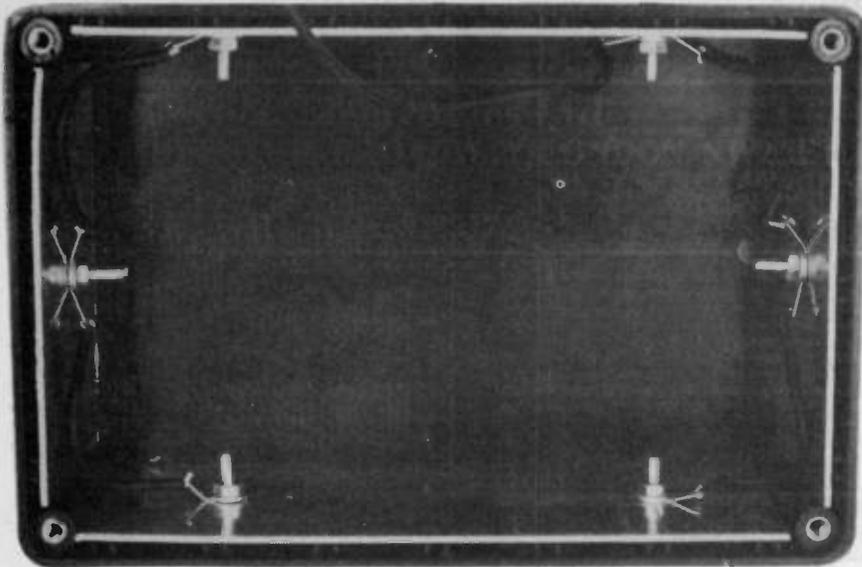

Screening panels mounted inside the plastic case and solder tags used to interlink them together and form the "Earth" connection.

PRECISION MEASUREMENTS

If a precise reading of the critical resistance is needed, connect the circuit under test to one pair of *X* terminals and an accurate resistance box to the other. Set VR1 critical with the "unknown" circuit selected by S1. Leave VR1 at this setting and use S1 to substitute the resistance box. Find a resistance which just gives oscillation. This is now the resistance (or effective resistance) of the "unknown".

SELECTIVE AMPLIFICATION

Connect an LC circuit tuned to the wanted frequency (Fig. 9) across the input (*X*). Feed a signal to it via a high resistance or small capacitance. Bringing VR1 near the critical setting provides selectivity.

Note that the LC circuit can in principle be sited inside an existent piece of equipment. With LC circuits of low *C* this may be impracticable because the input capacitance of The Tester (about 40p) can cause serious detuning.

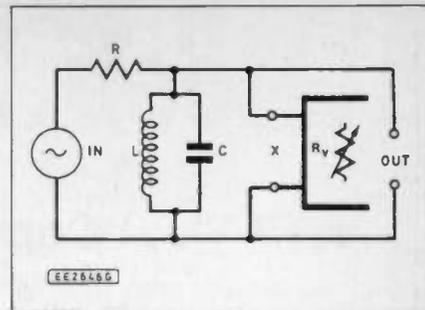


Fig. 9. Selective circuit.

TUNED CIRCUIT DATA

If either *L* or *C* is known and the resonant frequency is also known, the effective resistance ("dynamic resistance", *rd*) as measured by VR1 can be used to obtain the *Q* of the LC circuit.

$$Q = R_v / (6.28 \cdot f \cdot L)$$

$$\text{or } Q = R_v \cdot f / (6.28 \cdot C)$$

If *L* and *f* are known, *C* is calculable:

$$C = 25287 / (L \cdot f^2)$$

If *C* and *f* are known, *L* is calculable:

$$L = 25287 / (C \cdot f^2)$$

In the above calculations the following sets of units are consistent:

- Henries, Hertz, Ohms;
- microhenries, megahertz, Ohms;
- microfarads, Hertz, megohms;
- picofarads, megahertz, megohms.

Once tried The Tester becomes an invaluable workshop aid.

Remember
The Cricklewood
Service is Fast
and Efficient

CRICKLEWOOD ELECTRONICS

BIGGER
AND BETTER

1990 COMPONENTS CATALOGUE



- ONE OF THE LARGEST RANGES OF COMPONENTS IN THE UK
- FAST AND EFFICIENT SAME DAY PERSONAL SERVICE
- VERY COMPETITIVE PRICES; QUANTITY DISCOUNTS AVAILABLE
- DISCOUNT VOUCHERS INCLUDED
- NO MINIMUM ORDER

JUST LIKE A NEW CAR! YOU CAN ONLY JUDGE THE 1990 CATALOGUE BY LOOKING UNDER THE COVER. WITH OVER 13,000 STOCK LINES, CRICKLEWOOD ARE ABLE TO SUPPLY MOST OF THE COMPONENTS NEEDED FOR E.E. PROJECTS. PHONE US FOR YOUR SPECIAL NEEDS.

FILL IN THE COUPON AND POST IT WITH YOUR CHEQUE, PO ETC FOR £1.50 TO RECEIVE YOUR 1990 CRICKLEWOOD ELECTRONICS CATALOGUE AND VOUCHERS WHICH YOU CAN USE AGAINST YOUR NEXT PURCHASE

Cricklewood Electronics Ltd
40 CRICKLEWOOD BROADWAY, LONDON, NW2 3ET
Tel: 081-450 0995/452 0161
Fax: 081-208 1441 Telex: 914977



TELEPHONE ORDERS OUR SPECIALITY

CRICKLEWOOD ELECTRONICS 1990 COMPONENTS CATALOGUE

PLEASE SEND COPIES OF THE 1990 CRICKLEWOOD ELECTRONICS CATALOGUE AT £1.50 TO:

NAME

ADDRESS

.....

.....

.....

Remittance enclosed £..... **E**

Beeb...Beeb...Beeb...Beeb...Beeb

... RTTY ... Computer Communications ... RTTY ...

IN THE two previous "BEEB Micro" articles we have considered the subjects of Morse and RTTY tone decoding. This month we will conclude our look at this subject with some software to complete the RTTY decoding set up.

The story so far has a filter type tone decoder to decode the f.s.k. (frequency shift keying) signal into conventional serial types, an opto-isolator and level shifter circuit to couple this to a UART, with the latter then decoding the received five bit serial codes into corresponding five bit bytes of parallel data. I suspect that the term byte, which is generally taken to mean 8 bits of data, is incorrect when we are dealing with 5-bit chunks of data. A "nibble", which is four bits of data, would seem more appropriate in a way, but in the absence of a really concise term for these five bit codes I will continue to refer to them as bytes.

Clocking In

The basic way in which the UART is used was described in the previous BEEB Micro article. As UARTs have been covered in some detail in two or three BEEB Micro articles over the past few years I will not elaborate on their method of working on this occasion.

The suggested method of interfacing has the clock signal generated by the computer's timer/counters and output on line PB7 of the user port. This has the advantage of giving accurate and repeatable results without the need for any extra hardware, or any test equipment to aid accurate clock frequency adjustment.

If you wish to use this equipment with a computer other than the BBC micro, and no similar facility is available, then a simple R-C oscillator based on the indispensable 555 timer device will do the job quite well. However, you will need to have access to a frequency counter in order to permit the output frequency to be set with good accuracy, or a lot of trial and error will be called for.

The clock frequency must be at sixteen times the required baud rate, which gives the following frequencies for the popular baud rates:

BAUD RATE	UART CLOCK FREQ.
45.45	727.2Hz
50	800Hz
75	1200Hz
150	2500Hz
300	4800Hz

As these frequencies are all reasonably low, they can be obtained with quite good accuracy from the timer/counters. With just five bits per byte an error of even a few percent in the clock frequency would probably not produce malfunctions, and the timer/counters can certainly produce much better accuracy than this.

It is actually only timer 1 that is utilized in this case, and the length of one output

cycle is equal to $2 \times (N + 2)$ microseconds, where "N" is the value in timer 1. In the current context, what we need to know is that the timer value required for a given output frequency. This can be calculated by first dividing 1000000 by the required output frequency (in hertz), then halving this figure and deducting two.

This leaves a slight complication in that the timer/counter is a sixteen bit type, but it must be loaded using two 8-bit bytes. These are the high byte (the eight most significant bits) and the low byte (the eight least significant bits). The total counter value is equal to 256 times the number loaded into the high byte, plus the number loaded into the low byte.

It is not too difficult to calculate the two numbers required for a given total value, especially if you make use of the MOD and DIV functions of BBC BASIC. However, everything has already been worked out for you, and is summarised in the table below.

BAUD RATE	TIMER VALUE	HIGH BYTE	LOW BYTE
45.45	687	2	175
50	623	2	111
75	415	1	159
150	206	0	206
300	1665	0	102

The counter/timers are part of a 6522 VIA, and they are at addresses &FE65 (high byte) and &FE64 (low byte). At least, this is where the latch registers for this timer/counter are situated, and it is these that are used when setting the frequency of a squarewave output on PB7.

The operating mode of timer 2 is controlled by bits six and seven of the Auxiliary control register which is at address &FE6B. In order to set the mode where a squarewave output is produced on PB7 these bits must both be set high, which is achieved by writing a value of 192 (decimal) to address &FE6B.

Handshake Monitoring

Monitoring the handshake output of the UART is achieved using PB5, and this line going high indicates that a fresh byte of data is ready and waiting to be processed. This bit is easily masked using the logic AND function, giving a reading of 0 when it is low, or 32 when it is high.

Alternatively, line CB1 can be used as a high-to-low handshake input. However, using PB6 is probably a more simple and direct method.

The handshake output used to clear the data received flag of the UART can be either PB6 or CB2. CB2 cannot be used to automatically provide a negative output pulse each time the user port is read, as its automatic mode only works on write operations.

However, using a dummy write operation to the user port represents an easy way of producing the reset pulse, and is the one I recommend. CB2's mode is controlled by

bits five to seven of the peripheral control register at address &FE6C. To set the automatic output mode a value of 160 (decimal) must be written to this register.

Finally, the data direction register for port B must be set up for the right combination of input and output lines. With the suggested method of interfacing, PB0 to PB5 are all inputs, PB6 is unused and should therefore be left as an input, and PB7 is used as an output to provide the clock signal. This gives a value of 128 to be written to the data direction register at address &FE62.

However, setting timer 1 to the mode where it provides a squarewave output on PB7 also seems to set PB7 as an output line. Consequently it is not essential to set up the data direction register in this case.

Software

The accompanying program, Listing 1, enables the BBC micro plus the circuits featured in the past two BEEB Micro articles to function as a simple RTTY receiving terminal. This program is written on the assumption that the data will be read from the UART on PB0 to PB4.

The handshake output will be monitored by PB5, the clock signal is provided by PB7, and CB2 is used to reset the UART's handshake output. A different method of interfacing would almost certainly require minor modifications to the program.

Lines 30 to 70 set up the 6522 VIA correctly, and the values written to the timers at lines 60 to 70 are for a baud rate of 45.45. You can substitute values from the table provided previously if operation at a different baud rate is required.

The rest of the program is largely concerned with reading in bytes of data, and converting them from Baudot codes into corresponding ASCII characters which are then printed on the screen. I have not tried it in practice, but presumably using the standard Control-B method or the appropriate operating system command would result in everything being echoed to the printer as well if desired.

The program has to deal with the slight complication of the shift characters, and moving between the two Baudot character sets. You may sometimes find that the wrong character set is being produced.

This can easily occur if you tune in to a station in the middle of a message, or if interference causes corruption of the received data. You can shift manually between character sets simply by pressing the "S" key. If you wish to clear the screen and start afresh, press the "C" key.

In Use

The program and the hardware lack any "frills", but when used with a Yaesu FRG-8800 receiver I obtained quite good results. The main problem when using a computer with a communications receiver is usually one of electrical noise produced by the computer and monitor being picked up by the receiver. This can provide very

DOWN TO EARTH

BY GEORGE HYLTON

INTERFERENCE FILTERS

WHEN is a capacitor more than a capacitor? When it has four leadouts instead of two!

An interference filter is intended to prevent electrical noise energy from reaching circuits where it isn't wanted. A common case is found in a motor vehicle, where noise from the ignition system must be prevented from reaching a radio receiver in the car.

The first step is to place the aerial outside the car body where interference is low, and connect it via a screened cable to the screened receiver. This by itself is not enough. Interference can still get into the receiver via the battery connection.

CAPACITORS

The conventional solution is to suppress the interference where it arises. This is done partly by placing resistance in the high-tension circuit so that noise from the spark plugs is attenuated, and partly by connecting capacitors at strategic points to short the high-frequency interference currents to "earth" (i.e. the metal chassis or body).

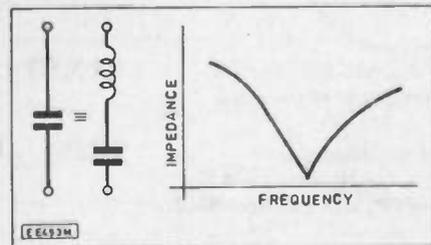


Fig. 1. At high frequencies a capacitor is an LC circuit.

In this case simple two-terminal capacitors may be enough. However, a practical capacitor of this kind always has inductance, if only in the connection leads.

The capacitor is in effect a capacitance in series with an inductance (Fig. 1). Its impedance varies with frequency as shown. There is a minimum when the inductive and capacitive reactances are equal and cancel one another out. The effectiveness of the capacitor at short-circuiting interference current is greater at this frequency and deteriorates at lower or higher frequencies.

TRANSMISSION-LINE FILTERS

Fortunately, for some applications, such as suppressing mains-borne interference, the materials used to make a capacitor can be arranged in a different way to form a more effective filter.

If a capacitor of the sandwich type (metal foil-dielectric-metal foil) is unrolled (Fig. 2a) and connections made at each end of the foil the capacitor becomes a transmission line. This is electrically equivalent to (Fig. 2b), which is a low-pass LC filter.

Interference entering at *a*, *b* is attenuated by the line on its way to *c*, *d*. The attenuation increases with frequency. In practice, of course, the filter capacitor is rolled up again for convenience.

Sometimes one foil is connected internally to a metal case. The filter is then a three-terminal one, with input *a* output *c* and common (the case *b*, *d*) connections.

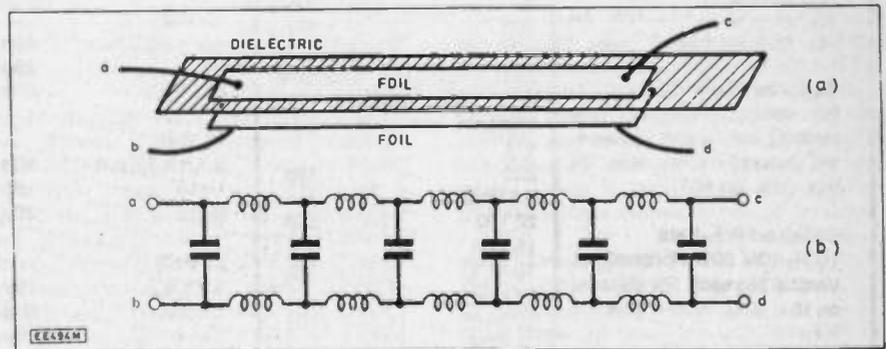


Fig. 2. A four-terminal capacitor acts as a low-pass filter. (a) Unrolled capacitor. (b) Equivalent circuit.

TRIPLE FILTER

The domestic mains (in Britain and many other countries) is carried round the house by a three-wire system: live (*L*), neutral (*N*) and earth (*E*). Interference filters often embody three capacitances (Fig. 3).

Here C1 comes across the mains (live, *L* and neutral, *N*), while C2 and C3 shunt the *L* and *N* wires to earth, *E*. The *N* lead is remotely earthed at the power station or some nearer point, but can still carry interference locally.

It would seem logical to make C1, C2 and C3 equal. However, there is a snag, if the earth connection of a piece of equipment becomes accidentally disconnected, then nominally earthed exposed metal parts are in fact connected to *L* and *N* by C2 and C3, and **LETHAL** shocks might be given to anyone touching the metal.

In theory, the risk could be reduced by making C3 much greater than C2. These two capacitors form a voltage divider in which the *E*-*N* section (C3) receives only part of the mains voltage. The greater C3 is with respect to C2 the less voltage appears at *E* if the earth connection is missing.

However, anybody who is careless

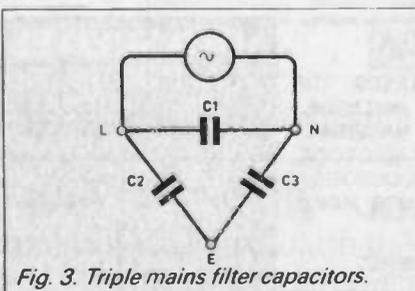


Fig. 3. Triple mains filter capacitors.

enough to leave off the earth at the mains plug may well also reverse *L* and *N*. C3 would then deliver a lethal current.

To be on the safe side, C2 and C3 are in practice made equal, so that whatever way *L* and *N* are connected only half the voltage can appear at *E*. They are also made small, to limit current.

Typical values are 100nF (0.1μF) for C1 and 2700pF (2.7n, 0.0027μF) for C2 and C3. All these capacitors **MUST** be rated to carry at least the full a.c. mains voltage (240V in Britain) continuously.

LC FILTERS

Where very large amounts of attenuation are required inductances may be incorporated in filters (Fig. 4). The inductors L1, L2 may be wound on the same iron or ferrite core. This reduces the risk of core saturation (which would lower the effective inductance).

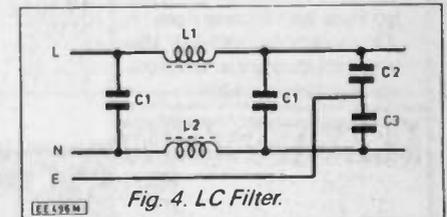


Fig. 4. LC Filter.

The use of inductance increases the size and cost of the filter but can produce high attenuation at the lower radio frequencies where capacitance-only filters may not be good enough.

FEED-THROUGH FILTERS

Conventional filters tend to be rather bulky. Where space is limited it is sometimes possible to utilise a type of filter capacitor which doubles as a connecting link between the inside of a metal cabinet and the outside world. (See Fig. 5).

When the interference is all at high frequencies a relatively small amount of capacitance may be enough. The resulting feed-through filter can then be very compact. Indeed, nowadays these filters are often built into the sockets used for conveying power or low frequency signals into or out of a cabinet or module.

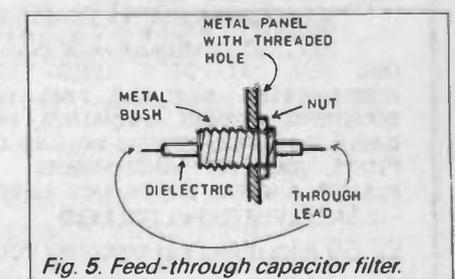


Fig. 5. Feed-through capacitor filter.

RESISTORS

Carbon Film 0.25W E12 or E24 series 1p each (min quantity 10 per value), 80p per 100, £6.00 per 1000.

** Special Offer **

Mixed Pack, of 1000 Carbon Film resistors, 1R to 10M, 100 different values all separately packed and labeled only £5.90

Metal Film 0.25/0.5 W E96 series 10R to 1M0 4p each (min quantity 10 per value), £3.00 per 100.

Ceramic/wirewound
4W 0R1-10K 35p each
7W 0R33-12K 37p each
11W 0R68-10K 40p each
17W 1R-10K 44p each
5% discount on 10+, 10% on 25+, 20% on 100+

Skeleton Pre-Sets
E3 series 100R-1M 20% Horizontal or vertical 18p each. 5% discount on 10+, 10% on 25+, 20% on 100+

Enclosed Pre-Sets
100R-10M 20% Horizontal or Vertical 24p each. 5% discount on 10+, 10% on 25+, 20% on 100+

20 Tum 3/4" Cermet Pots
10% tolerance 10R-2M 90p each, 5% discount on 10+, 10% on 25+, 20% on 100+

CAPACITORS

Radial Aluminium Electrolytic 20% tolerance

10/16/25/35 Volt
4.7, 10, 22, 33, 47, 100 12p
220, 330, 470 20p

1000 30p
2200 48p
3300 65p
4700 85p

50/63/ Volt
0.47, 1, 2, 2.2, 3.3, 4.7, 10 12p
22, 33, 47 20p
100, 220 30p
470 50p
1000 90p

100 Volt
0.47, 1, 2, 2.2, 4.7 12p
10, 22 20p
47 30p
100 50p

Ultra miniature Aluminium electrolytic radial 20% tolerance

4 V
220 18p

6.3 Volt
22, 100 18p

16 Volt
10, 22, 47 18p

25 Volt
10, 22, 33 18p

35 Volt
4.7, 10, 22 18p

50 Volt
0.1, 0.22, 0.33, 0.47, 1, 2, 2.2, 3.3, 4.7, 10 18p

CAPACITORS

Disc Ceramic 5%
tolerance 150Volt values in pF
15, 22, 33, 47, 68, 4p
100, 150, 6p
220, 330, 470 6p

10% tolerance value in pF
220, 330, 470, 680, 6p
1000, 1500, 2200
3300, 4700, 6800 8p

+80%-20% tol. value pF
4700, 10000 6p
22000, 47000 9p

Tant. Bead resin dipped 20% tolerance value in uF
6.3 Volt
10, 22 15p
47 25p

10 Volt
3.3, 4.7, 6.8 15p
10, 15 25p
22, 33, 47 35p

16 Volt
2.2, 3.3, 4.7, 6.8 15p
10, 15 25p
22, 33 35p

25 Volt
1, 2, 2.2, 3.3 15p
4.7, 6.8 25p
10, 15 35p

35 Volt
0.1, 0.22, 0.33, 0.47 15p
0.68, 1, 2, 2.3, 3 20p
4.7, 6.8, 10 30p

CMOS

4000	17p	4106	34p
4001	17p	4160	40p
4002	17p	4161	40p
4006	37p	4162	40p
4007	17p	4163	40p
4008	37p	4174	37p
4011	17p	4175	40p
4012	17p	4194	42p
4013	25p	4501	27p
4014	37p	4502	40p
4015	37p	4503	37p
4016	28p	4504	120p
4017	37p	4506	76p
4018	37p	4508	99p
4020	37p	4510	37p
4021	37p	4511	37p
4022	37p	4512	37p
4023	17p	4513	99p
4024	35p	4514	85p
4025	17p	4515	80p
4027	34p	4516	37p
4028	37p	4517	99p
4029	37p	4518	37p
4032	56p	4519	26p
4034	95p	4520	37p
4035	44p	4521	85p
4038	65p	4522	44p
4040	37p	4526	44p
4042	37p	4527	44p
4043	37p	4528	44p
4044	37p	4529	50p
4046	47p	4530	99p
4049	27p	4531	44p
4050	27p	4532	60p
4051	37p	4534	240p
4052	37p	4536	120p
4053	37p	4538	54p
4060	37p	4539	45p
4066	29p	4541	50p
4067	99p	4543	54p
4068	17p	4544	130p
4069	17p	4547	130p
4070	17p	4549	400p
4071	17p	4551	85p
4072	17p	4553	120p
4073	17p	4554	320p
4075	17p	4555	50p
4076	37p	4556	50p
4077	17p	4557	120p
4078	17p	4558	120p
4081	17p	4559	440p
4082	17p	4560	110p
4093	27p	call sales for	
4094	48p	4500 series	
4097	99p	above 4560	
4099	46p		

DIODES

1N914 5p
1N4148 4p
1N4001 3p
1N4002/3/4/5/6 4p
1N5401 7p
1N5402/4/6/8 11p

Zener Diodes 500 mW

24, 27, 33, 33.9, 47.5, 15.6, 62.6, 2
6.8, 8.2, 10, 11, 12, 13, 15, 16, 18
20, 22, 24, 27, 30, 33, 39, 43, 62, 68
75, 82, 91
All above voltages at 5p each

1.3 W

3.3, 3.9, 4.3, 4.7, 5.1, 5.6, 6.2, 6.8
7.5, 8.2, 9.1, 10, 11, 12, 13, 15, 16
18, 20, 22, 24, 27, 30, 33, 36, 39, 43
47, 51, 56, 62, 68, 75, 82, 91
All above voltages at 16p each

2.5W, 20W & 75W versions available

Bridges

W005 23p
W02 25p
W04 30p
W06/08 35p
2A 200V 65p
2A 400V 72p
2A 600V 90p
6A 200V 78p
6A 400V 84p
6A 600V 99p

Linear I.C.s
call for price

TRANSISTORS

BC107B	20p
BC108B	20p
BC109C	22p
BC184C	6p
BC212B	6p
BC239C	4p
BC307C	4p
BC548C	4p
BC558C	4p
ZTX300	17p

The above are a few examples from the 1000's of transistor types we have. We cover all ranges and types including JFET, SIPMOS, TMOS, TIP plastic & metal, FET & Darlington.

REGULATORS

7805	5V @ 1.5A	30p
7812	12V @ 1.5A	30p
7815	15V @ 1.5A	30p
7905	-5V @ 1.5A	30p
7912	-12V @ 1.5A	30p
7915	-15V @ 1.5A	30p

★ KITS ★ KITS ★ KITS ★

ALL KITS ARE SUPPLIED WITH MAINS TRANSFORMER, HIGH QUALITY GLASS FIBRE SILK SCREENED PCB, FULL INSTRUCTIONS, HEATSINK, SOLDER ETC. CASE NOT SUPPLIED BUT AVAILABLE

CONSTANT CURRENT NI-CAD CHARGER Charge your Ni-Cads safely, can be left on indefinitely without damage, batteries fully charged from flat in approx. 18 hours. Charge up to 12 batteries in series (except PP3). **£7.50**

FAST NI-CAD CHARGER Rapidly charge your Ni-Cad racing pack from mains or 12Volts. Charger guarantees a full charge every time, making maximum use of your pack. **£10.50**

BENCH POWER SUPPLY 2.5 - 35 Volt @ 2 Amps The following spec ensures excellent value for money for this most essential of workshop equipment. Line Reg. 0.03%, Load Reg. 0.1% Ripple Rejection 70 dB, Output Res. 1.5 milliOhm, Output Noise 80uV. **£8.00**

10 Amp BENCH POWER SUPPLY 5 - 33 Volt Use for powering C.B./ Ham Radios, or a very high powered bench power supply. Spec as 2A version above. **£32.00**

HUNDREDS OF KITS AVAILABLE - SEND FOR LIST

1990 CATALOGUE

OUR NEW CATALOGUE LISTS THOUSANDS OF COMPONENTS, SWITCHES, RELAYS, BUZZERS, SOUNDERS, FIXINGS, CHEMICALS, PCB MATERIAL, CABLE, MODULES, METERS, SOLDER, CONNECTORS, PLUGS, SOCKETS, TRANSFORMERS, INDUCTORS, PLASTIC & METAL BOXES, AND LOTS, LOTS MORE - **IN FACT EVERYTHING YOU NEED**

£2.50 (INCLUDING 5 £1 DISCOUNT VOUCHERS)

ADVANCED ELECTRONIC PRODUCTS LTD

P.O. BOX 10, Newton Abbot, Devon TQ12 1JP
Tel: (0626) 332091. Fax: (0626) 332381

MAIL ORDER TERMS: POSTAL ORDER OR CHEQUE WITH ORDER. PLEASE ADD 75p P&P TO COMPONENT ORDERS. £2.75 TO KIT ORDERS AND THEN 15% VAT. ACCESS & VISA HOLDERS PLEASE PHONE ORDER BEFORE 4.45PM FOR SAME DAY DESPATCH. ALL ORDERS UNDER 750 Grms SENT BY FIRST CLASS POST. OVERNIGHT CARRIER £9.

DIRECT BOOK SERVICE

The books listed have been selected as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

MORE BOOKS NEXT MONTH—MORE BOOKS NEXT MONTH

AUDIO & MUSIC

SYNTHESIZERS FOR MUSICIANS

R. A. Penfold
Modern synthesizers are extremely complex, but they mostly work on principles that are not too difficult to understand. If you want to go beyond using the factory presets or the random poking of buttons, this is the book for you.

It covers the principles of modern synthesis—linear arithmetic as used by Roland, phase distortion (Casio), Yamaha's frequency modulation, and sampling—and then describes how the instruments are adjusted to produce various types of sound—strings, brass, percussion, etc. The theoretical side of synthesis is treated in an easy to understand way—the technical information being restricted to what you need to know to use your instrument effectively.

168 pages Order code PC105 £6.95

AUDIO

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Analysis of the sound wave and an explanation of acoustical quantities prepare the way. These are followed by a study of the mechanism of hearing and examination of the various sounds we hear. A look at room acoustics with a subsequent chapter on microphones and loudspeakers then sets the scene for the main chapter on audio systems—amplifiers, oscillators, disc and magnetic recording and electronic music.

320 pages Temporarily out of print

INTRODUCTION TO DIGITAL AUDIO

Ian Sinclair

Digital recording methods have existed for many years and have become familiar to the professional recording engineer, but the compact disc (CD) was the first device to bring digital audio methods into the home. The next step is the appearance of digital audio tape (DAT) equipment.

All this development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages Order code PC102 £5.95

MAKE MONEY FROM HOME RECORDING

Clive Brooks

Now that you've spent a fortune on all that recording gear, MIDI and all, wouldn't it be nice to get some of it back? Well here's the book to show you how.

It's packed with money making ideas, any one of which will recoup the price of the book many times over. Whether you have a fully fledged recording studio at home, or just a couple of stereo cassette recorders and a microphone, you'll be able to put the ideas in this book into practice and make money.

105 pages Order code PC104 £5.95

TESTING & TEST GEAR

HOW TO TEST ALMOST EVERYTHING ELECTRONIC—2nd EDITION

Jack Darr and Delton T. Horn

Describes electronic tests and measurements—how to make them with all kinds of test equipment, and how to interpret the results. New sections in this edition include logic probes, frequency counters, capacitance meters, and more. (An American book.)

190 pages Order code T2925 £9.95

GETTING THE MOST FROM YOUR MULTIMETER

R.A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic products.

96 pages Order code BP239 £2.95

MORE ADVANCED USES OF THE MULTIMETER

R. A. Penfold

This book is primarily intended as a follow-up to BP239, (see above), and should also be of value to anyone who already understands the basics of voltage testing and simple component testing. By using the techniques described in chapter 1 you can test and analyse the performance of a range of components with just a multimeter (plus a very few inexpensive components in some cases). Some useful quick check methods are also covered.

While a multimeter is supremely versatile, it does have its limitations. The simple add-ons described in chapter 2 extend the capabilities of a multimeter to make it even more useful. The add-ons described include an active r.f. probe, a high resistance probe, an a.c. sensitivity booster, and a current tracer unit.

84 pages Order code BP265 £2.95

TEACH-IN THEORY & REFERENCE



EVERYDAY ELECTRONICS DATA BOOK

Mike Tooley BA

(published by EE in association with PC Publishing)
This book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but it also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous examples showing how theory can be put into practice using a range of commonly available "industry standard" components and devices.

A must for everyone involved in electronics!
256 pages Order code DATA £8.95

ELECTRONICS TEACH-IN 88/89—INTRODUCING MICROPROCESSORS

Mike Tooley BA (published by *Everyday Electronics*)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

Sections cover Microcomputer Systems, Microprocessors, Memories, Input/Output, Interfacing and Programming. There are various practical assignments and eight Data Pages covering the most popular microprocessor chips.

An excellent introduction to the subject even for those who do not wish to take the City and Guilds assessment.

80 pages (A4 size) Order code TI-88/89 £2.45

THE ILLUSTRATED DICTIONARY OF ELECTRONICS—4th EDITION

Rufus P. Turner and Stan Gibilisco

With more than 27,000 terms used in electronics today, this collection is THE most comprehensive dictionary available. Including all practical electronics and computer terms, it is as up-to-date as the latest advances in the field itself. Tables and data on subjects most often consulted for projects and experiments are included. Other conversion tables include English/metric and metric/English conversions for units of measurement of energy, power and volume, and Fahrenheit/Celsius temperature conversion charts.

Setting this edition apart from other electronic dictionaries is its emphasis on illustration. Featuring more than complete definitions, this fourth edition includes over 450 detailed drawings and diagrams.

All entries are listed in alphabetical order. Abbreviations and initials are listed in sequence with whole words. All terms of more than one word are treated as one word. (An American book.)

648 pages Order code T2900 £23.65

MICROPROCESSING SYSTEMS AND CIRCUITS

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

A truly comprehensive guide to the elements of micro-processing systems which really starts at the beginning. Teaches the reader the essential fundamentals that are so important for a sound understanding of the subject.

256 pages Temporarily out of print

ELECTRONICS TEACH-IN No. 3 — EXPLORING ELECTRONICS (published by *Everyday Electronics*)

Owen Bishop

Another EE value for money publication aimed at students of electronics. The course is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. The book does not contain masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

Exploring Electronics contains more than 25 useful projects, assumes no previous knowledge of electronics and is split into 28 easily digestible sections.

88 pages (A4 size) Order code T13 £2.45

ELECTRONICS—A "MADE SIMPLE" BOOK

G. H. Olsen

This book provides excellent background reading for our *Introducing Digital Electronics* series and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity.

330 pages Order code NE10 £4.95

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias—tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-current Circuits, Passive Components, Alternating-current Circuits, Networks and Theorems, Measurements.

256 pages Order code BP53 £3.95

MICROELECTRONIC SYSTEMS N2 CHECKBOOK

R. Vears

The aim of this book is to provide a foundation in microcomputer hardware, software and interfacing techniques. Each topic is presented in a way that assumes only an elementary knowledge of microelectronic systems and logic functions. The book concentrates on 6502, Z80 and 6800 microprocessors and contains 60 tested programs, 160 worked problems and 250 further problems.

Order code NE04N £6.95

ELECTRONICS-BUILD AND LEARN

R. A. Penfold
The first chapter gives full constructional details of a circuit demonstrator unit that is used in subsequent chapters to introduce common electronic components—resistors, capacitors, transformers, diodes, transistors, thyristors, relays and op amps. Later chapters go on to describe how these components are built up into useful circuits, oscillators, multivibrators, bistables and logic circuits.

At every stage in the book there are practical tests and experiments that you can carry out on the demonstrator unit to investigate the points described and to help you understand the principles involved. You will soon be able to go on to more complex circuits and tackle fault finding logically in other circuits you build.

120 pages Order Code PC103 £5.95

PRACTICAL ELECTRONICS HANDBOOK

Ian Sinclair
Ian Sinclair has now revised this useful and carefully selected collection of standard circuits, rules-of-thumb, and design data for professional engineers, students and enthusiasts involved in radio and electronics. Covering passive and active components, discrete component circuits (such as amplifiers, filters and oscillators) and linear and digital i.c.s, the book includes many items which are not elsewhere available in a single handy volume. The operation and functions of typical circuits are described, while mathematics is limited to that necessary for deciding component values for any application.

This revised edition contains more details on computers and microprocessors and has been brought up to date throughout. 199 pages Order Code NE06 £7.95

TRANSISTOR SELECTOR GUIDE

This unique guide offers a range of selection tables compiled so as to be of maximum use to all electronics engineers, designers and hobbyists.

Section 1: Covers component markings, endings and standards, as well as explaining the symbols used.
Section 2: Tabulates in alpha-numeric sequence the comprehensive specifications of over 1400 devices.
Section 3: Tabulates the devices by case type.
Section 4: Considers particular limits to the electrical parameters when compiling the tables.
Section 5: Illustrates package outlines and leadouts.
Section 6: Consists of a surface mounting device markings conversion list.
192 pages Temporarily out of print

CIRCUITS & DESIGN

ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF MODEL RAILWAYS

R. A. Penfold
Home computers may easily be applied to the control of model railways and really quite sophisticated control, which needs only simple programming, is not too difficult to achieve. The main problem lies in interfacing the computer to the layout, but fortunately it is not too difficult or expensive to build suitable interfaces, and this book shows you how.

The projects consist of various types of controller, including a high quality pulse type, as well as circuits for train position sensing, signal and electric points control etc. The use of computers does not have to be restricted to massive layouts. Something as simple as an oval of track with a single siding can be given a new dimension by adding computer control and much fun can be had from these relatively simple set-ups.

88 pages Order code BP180 £2.95

ELECTRONIC CIRCUITS HANDBOOK

Michael Tooley BA
This book aims to explode two popular misconceptions concerning the design of electronic circuits: that only those with many years of experience should undertake circuit design and that the process relies on an understanding of advanced mathematics. Provided one is not too ambitious, neither of these popularly held beliefs is true.

Specifically, this book aims to provide the reader with a unique collection of practical working circuits together with supporting information so that circuits can be produced in the shortest possible time and without recourse to theoretical texts.

Furthermore, information has been included so that the circuits can readily be modified and extended by readers to meet their own individual needs. Related circuits have been grouped together and cross-referenced within the text (and also in the index) so that readers are aware of which circuits can be readily connected together to form more complex systems. As far as possible, a common range of supply voltages, signal levels and impedances has been adopted.

As a bonus, ten test gear projects have been included. These not only serve to illustrate the techniques described but also provide a range of test equipment which is useful in its own right.
277 pages Order code NE05 £14.95

DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS


A. Michaels
Shows equivalents and pin connections of a popular selection of European, American and Japanese digital i.c.s. Also includes details of packaging, families, functions, manufacturer and country of origin.
256 pages Temporarily out of print

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

A. Michaels
Helps the reader to find possible substitutes for a popular selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.
320 pages Order code BP85 £3.50

CHART OF RADIO, ELECTRONIC, SEMICONDUCTOR AND LOGIC SYMBOLS

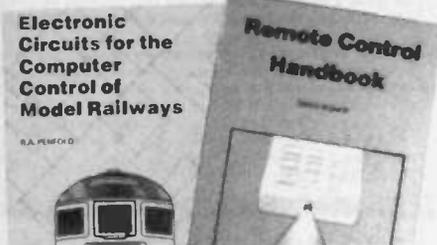M. H. Banani, B.Sc.(Eng.)
Illustrates the common, and many of the not-so-common, radio, electronic, semiconductor and logic symbols that are used in books, magazines and instruction manuals, etc., in most countries throughout the world.
Chart Order Code BP27 £0.95



REMOTE CONTROL HANDBOOK

Owen Bishop
Remote control systems lend themselves to a modular approach. This makes it possible for a wide range of systems, from the simplest to the most complex, to be built up from a number of relatively simple modules. The author has tried to ensure that, as far as possible, the circuit modules in this book are compatible with one another. They can be linked together in many different configurations to produce remote control systems tailored to individual requirements. Whether you wish simply to switch a table lamp on and off, or to operate an industrial robot, this book should provide the circuit you require.

226 pages Order code BP240 £3.95

AUDIO IC CIRCUITS MANUAL

R. M. Marston
A vast range of audio and audio-associated i.c.s are readily available for use by amateur and professional design engineers and technicians. This manual is a guide to the most popular and useful of these devices, with over 240 diagrams. It deals with i.c.s such as low frequency linear amplifiers, dual pre-amplifiers, audio power amplifiers, charge coupled device delay lines, bar-graph display drivers, and power supply regulators, and shows how to use these devices in circuits ranging from simple signal conditioners and filters to complex graphic equalizers, stereo amplifier systems, and echo/reverb delay line systems etc.

168 pages Order code NE13 £11.95

HOW TO DESIGN ELECTRONIC PROJECTS

R. A. Penfold
The aim of this book is to help the reader to put together projects from standard circuit blocks with a minimum of trial and error, but without resorting to any advanced mathematics. Hints on designing circuit blocks to meet your special requirements are also provided.
128 pages Order code BP127 £2.25

50 CIRCUITS USING GERMANIUM SILICON AND ZENER DIODES

R. N. Soar
Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most simple and inexpensive of components—the diode. Includes the use of germanium and silicon signal diodes, silicon rectifier diodes and Zener diodes, etc.
64 pages Order Code BP36 £1.50

KEY TECHNIQUES FOR CIRCUIT DESIGN

C. G. Loveday C.Eng MIERE
Deals with designing electronic circuits from scratch covering concepts such as target specifications, component selection (passive, discrete and i.c.s), the design cycle, derating and so on. Numerous design examples are given and several reader exercises all with fully worked solutions. The approach is essentially non-mathematical.
128 pages Order code BM1 £6.95

DESIGNING WITH LINEAR ICs

G.C. Loveday
A book that deals with the design of the vital area of analog circuitry covering design with modern linear integrated circuit devices. The first chapter introduces the reader to important design techniques, test strategies, layout, and protection and also includes a section on the use of a typical CAD tool. There are separate chapters that cover in depth the use of op-amps, comparators and timers each with detailed design examples and reader exercises. A final chapter brings all the previous work together in a number of complete design problems with fully worked solutions. The text is essentially non-mathematical and is supported by many diagrams.
180 pages Order code BM3 £8.75

OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston
A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the i.c.s and other devices used are inexpensive and readily available types, with universally recognised type numbers.
182 pages Order code NE14 £12.95



A MICROPROCESSOR PRIMER

E. A. Parr, B.Sc., C.Eng., M.I.E.E.
Starts by designing a small computer which, because of its simplicity and logical structure, enables the language to be easily learnt and understood. The shortcomings are then discussed and the reader is shown how these can be overcome by changes and additions to the instruction set. In this way, such ideas as relative addressing, index registers, etc., are developed.
96 pages Order code BP72 £1.75

POPULAR ELECTRONIC CIRCUITS - BOOK 1

POPULAR ELECTRONIC CIRCUITS - BOOK 2
R. A. Penfold
Each book provides a wide range of designs for electronic enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed construction information. Any special setting-up procedures are described.
BOOK 1 160 pages Order code BP80 £2.95
BOOK 2 160 pages Order code BP98 £2.95

CMOS CIRCUITS MANUAL

R. M. Marston
Written for the professional engineer, student or enthusiast. It describes the basic principles and characteristics of these devices and includes over 200 circuits. All the circuits have been designed, built and fully evaluated by the author; all use inexpensive and internationally available devices.
pages Order code NE12 £9.95



30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1

R. A. Penfold
Each project, which is designed to be built on a "Verobloc" breadboard, is presented in a similar fashion with a brief circuit description, circuit diagram, component layout diagram, components list and notes on construction and use where necessary. Wherever possible, the components used are common to several projects, hence with only a modest number of reasonably inexpensive components, it is possible to build in turn, every project shown. Recommended by BICC-Verobloc.
160 pages Order Code BP107 £2.95

BOOK 2 - All projects use CMOS i.c.s but the items on component identification etc., are not repeated from Book 1
160 pages Order code BP113 £2.25

PROJECT CONSTRUCTION

ELECTRONIC PROJECTS — BOOK 1

Published by *Everyday Electronics* in association with *Magenta Electronics*.

Contains twenty of the best projects from previous issues of *EE* each backed with a kit of components. The projects are: Seashell Sea Synthesiser, *EE* Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16k Sideways Ram, Simple Short Wave Radio, Insulation Tester, Visual Guitar/Instrument Tuner, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, *EE* Equaliser Ioniser, Bat Detector, Acoustic Probe, Mainstester and Fuse Finder, Light Rider — (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, *EE* Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.
128 pages (A4 size) Order Code EP1 £2.45

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold
Deals with the simple methods of copying printed circuit

board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.
80 pages Order code BP121 £2.50

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold
We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.
96 pages Order code BP110 £2.50

ELECTRONIC SCIENCE PROJECTS

O. Bishop
These projects range in complexity from a simple colour temperature meter to an infra-red laser. There are novelties such as an electronic clock regulated by a resonating spring, and an oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. The way they work, and how to build and use them are fully explained.
144 pages Order code BP104 £2.95

BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold
Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also includes examples in the form of simple projects.
112 pages Order code No. 227 £1.95

TEST EQUIPMENT CONSTRUCTION

R. A. Penfold
This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.
The following designs are included: AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Millivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe. The designs are suitable for both newcomers and more experienced hobbyists.
104 pages Order code BP248 £2.95

RADIO, TV, SATELLITE

BEGINNER'S GUIDE TO RADIO—9th EDITION

Gordon J. King
Radio signals, transmitters, receivers, antennas, components, valves and semiconductors, CB and amateur radio.
266 pages Order code NE08 £6.95

AN INTRODUCTION TO RADIO OXING

R. A. Penfold
Anyone can switch on a short wave receiver and play with the controls until they pick up something, but to find a particular station, country or type of broadcast and to receive it as clearly as possible requires a little more skill and knowledge. The object of this book is to help the reader to do just that, which in essence is the fascinating hobby of radio DXing.
112 pages Order code BP91 £1.95

A TV-DXERS HANDBOOK

R. Bunney
Roger Bunney is probably one of the leading authorities in this country on the subject. Includes many units and devices which have been designed and used by active enthusiasts, and often, considerable ingenuity and thought have gone into the development of such units to overcome individual problems. A practical and authoritative reference to this unusual aspect of electronics.
128 pages Order code BP176 £5.95

SATELLITE TELEVISION INSTALLATION GUIDE—2nd EDITION

John Breeds
This book is now firmly established as a leading study manual for satellite TV installers, technical colleges who run City & Guilds courses, and training schools in major companies. It will be invaluable to anyone who wants to set up a dish receiver.

It covers all aspects of satellite dish installation: Installation of indoor unit, Geostationary satellites, Site survey, Dish assembly, Signal polarisation, Setting up the dish, Polar mount dish, TV download and relay cable and F-connectors, EIRP footprint contours, Trouble-shooting guide, Glossary of terms and Useful addresses.
56 pages (large format) Order code JB1 £11.95

NEWNES SHORTWAVE LISTENING HANDBOOK

Joe Pritchard G1UQW
Part One covers the "science" side of the subject, going from a few simple electrical "first principles", through a brief treatment of radio transmission methods to simple receivers. The emphasis is on practical receiver designs and how to build and modify them, with several circuits in the book.
Part Two covers the use of sets, what can be heard, the various bands, propagation, identification of stations, sources of information, QSLing of stations and listening to amateurs. Some computer techniques, such as computer Morse decoding and radio teletype decoding are also covered.
224 pages Order code NE16 £12.95

DIRECT BOOK SERVICE

(A Division of Wimborne Publishing Ltd.)

TO ORDER

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add 75p to your total order for postage and packing (overseas readers add £1.50 for countries in Europe, or add £2.00 for all countries outside Europe, surface mail postage) and send a PO, cheque or international money order (£ sterling only) made payable to **Direct Book Service** quoting your name and address, the order code and quantities required to **DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET, BH21 1RW** (mail order only).

See next month's issue for another three page selection of books.

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of *Everyday Electronics*) before ordering from old lists.

Note—our postage charge is the same for one book or one hundred books!



COMPUTING

SERVICING PERSONAL COMPUTERS—2nd EDITION

Mike Tooley BA
The revised and enlarged second edition contains a new chapter on the IBM PC, AT, TX and compatibles. It is essential for anyone concerned with the maintenance of personal computer equipment or peripherals, whether professional service technician, student or enthusiast.
240 pages (hard cover) Order code NE15 £25

AN INTRODUCTION TO PROGRAMMING THE BBC MODEL B MICRO

R. A. & J. W. Penfold
Written for readers wanting to learn more about programming and how to make best use of the incredibly powerful model B's versatile features. Most aspects of the BBC micro are covered, the omissions being where little could usefully be added to the information provided by the manufacturer's own manual.
144 pages Order code BP139 £1.95

AN INTRODUCTION TO COMPUTER COMMUNICATIONS

R. A. Penfold
Provides details of the various types of modem and their suitability for specific applications, plus details of connecting various computers to modems, and modems to the telephone system. Also information on common networking systems and RTTY.
96 pages Order code BP177 £2.95

AN INTRODUCTION TO COMPUTER PERIPHERALS

J. W. Penfold
Covers such items as monitors, printers, disc drives, cassette recorders, modems, etc., explaining what they are, how to use them and the various types and standards. Helps you to make sure that the peripherals you buy will work with your computer.
80 pages Order code BP170 £2.50

HOW TO GET YOUR COMPUTER PROGRAMS RUNNING

J. W. Penfold
Have you ever written your own programs only to find that they did not work? Help is now at hand with this book which shows you how to go about looking for your errors, and helps you to avoid the common bugs and pitfalls of program writing. Applicable to all dialects of the BASIC language.
144 pages Order code BP169 £2.50

AN INTRODUCTION TO 6502 MACHINE CODE

R. A. & J. W. Penfold
No previous knowledge of microprocessors or machine code is assumed. Topics covered are: assembly language and assemblers, the register set and memory, binary and hexadecimal numbering systems, addressing modes and the instruction set, and also mixing machine code with BASIC. Some simple programming examples are given for 6502-based home computers like the VIC-20, ORIC-1/Atmos, Electron, BBC and also the Commodore 64.
112 pages Order code BP147 £2.95

THE PRE-BASIC BOOK

F. A. Wilson, C.G.I.A., C.ENG., F.I.E.E., F.I.E.R.E., F.B.I.M.
Another book on BASIC but with a difference. This one does not skip through the whole of the subject and thereby leave many would-be programmers floundering but instead concentrates on introducing the technique by looking in depth at the most frequently used and more easily understood computer instructions. For all new and potential micro users.
192 pages Order code BP146 £2.95

THE GOOD KIT GUIDE 2


For immediate attention to your Credit Card order, please phone 0600 3715 any time.

BRAINWAVE MONITOR ▷

The tiny electric currents generated by your brain have different rhythms according to your moods. The Alpha rhythm indicates a calm, relaxed, positive state of mind. Cool, calm and collected, you might say. When presented with a problem your brain enters Beta mode for concentrated attention to the matter in hand. Daydreamers, artists and creative types may find themselves drifting into the Theta mode, a kind of freewheeling reverie where ideas and images flow forth.

The Brainwave Monitor picks up these rhythms and allows you to measure or even listen to them. But that's only the start. By using the techniques of biofeedback you can strengthen the rhythms and switch between them as easily as you'd change channels on the TV. In other words it helps you to bring out the hidden, but perfectly natural, powers of your mind.

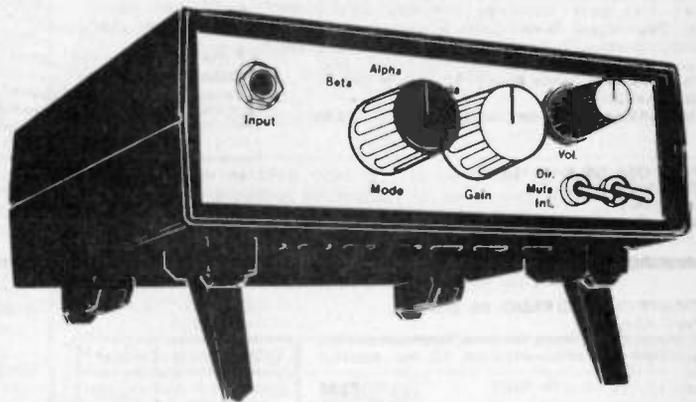The parts set includes everything you'll need to build and use the monitor. Perfectionists may like to silver plate and chloride the electrodes, so we have the compounds for doing this too. The information supplied with the set covers the basic biofeedback techniques, and for anyone who wants to push it to the limits there's a separate book available which covers the subject in depth.



- BRAINWAVE MONITOR £52.67 SILVER COMPOUND £4.37
 BIOFEEDBACK BOOK £4.50 CHLORIDE CONCENTRATE £2.53



◁ BIOFEEDBACK MONITOR


For anyone who wants to experiment with biofeedback without the expense of a sophisticated brainwave monitor, our GSR meter is just the thing. It records the stronger galvanic skin response, which also mirrors quite accurately the changes in your state of mind. So accurately, in fact, that a GRS is an essential part of the Polygraph lie detector commonly used in criminal investigations in the USA.

Our monitor is a highly sensitive self-balancing type which needs no setting up at all. Instructions include stress reduction techniques, experiments in lie detection, and even tell you how to beat the lie detector!

- BIOFEEDBACK MONITOR £19.32

SOUND EFFECTS COMPUTER ▽

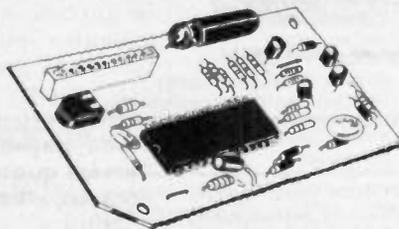Take a powerful PIC655A single chip computer, mask program it to produce the most outrageously realistic sound effects, add an audio amplifier to bring them up to loudspeaker level, and you have the SS42 Sound Effects Computer. How about a motor rally, complete with gear changes?



Or a ship hooting its mournful way through the fog? Or a fly so realistic it'll have you running for the swat? Sirens, helicopters, steam trains — you name it, it's all in there. The computer is easily programmed with the thirteen switches provided — in one mode you can even play it like a synthesizer!

With your computer we also give you a battery connector, loudspeaker, thirteen switches and a wiring diagram and programming instructions. You add a PP3 battery, a length of connecting wire, and ten minutes of your time to connect it all together. The ideal project for anyone taking their first steps in electronics, or anyone who just wants a fun project!

- SOUND EFFECTS COMPUTER SET £14.72

SURVEILLANCE PROJECTS

Do they work? You bet they do! 'Have you got it in writing?' sneered a salesman who'd been telling us some very expensive porkies. 'Well, you're going to have a hard time proving it, aren't you?' Not so very hard, since a little FM bug was transmitting every word of the conversation to a radio-cassette recorder elsewhere in the building. A useful thing to have in your pocket, the TX1. Less than a fiver to buy, and it saved us £5,000. Pretty good value, I reckon.

A single PCB is all you need to build every project, and a single set of instructions covers the lot too. Once you've got the PCB and instructions, just select the component sets for the projects you want to build. The TX1 is a voice bug, the TB1 will transmit telephone conversations, the BL1 is a bug locator to stop people bugging you, and the CG1 is a general purpose transmitter for whatever you care to use it for.

Please note that none of these transmitters are licensable for use in the UK, and you may not connect them to public telephone lines. In short, they're illegal, so be careful what you do with them.

- PCB FOR ALL PROJECTS £1.84
 CONSTRUCTION DETAILS AND CIRCUITS FOR ALL PROJECTS
 £2.30
 TX1 VOICE BUG COMPONENTS SET £4.49
 TB1 PHONE BUG COMPONENTS SET £3.87
 CG1 TRANSMITTER COMPONENTS SET £3.66
 BL1 BUG LOCATOR PARTS SET £4.66

Send to Specialist Semiconductors Ltd.,
 Room 111, Founders House, Redbrook,
 Monmouth, Gwent, NP5 4LU.

Please supply the items ticked above.

I enclose Cheque or Postal Order No..... value £.....
 or please debit my credit card no

Expiry date.....

Signed.....

Name.....

Address.....

UK orders: prices include VAT. Just add £1.15 postage and packing. Overseas orders: divide total by 1.15 to get VAT exclusive price. Add £5 carriage for Europe and Eire, elsewhere add £6 for surface mail or £18 for airmail.

Please order on a letter if you'd prefer not to cut the magazine.

PCB SERVICE

Printed circuit boards for certain constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to The PCB Service *Everyday Electronics*, 6 Church Street, Wimborne, Dorset BH21 1JH. Cheques should be crossed and made payable to *Everyday Electronics* (Payment in £ sterling only).

Boards for some older projects - not listed here - can often be obtained from *Magenta Electronics*, 135 Hunter St., Burton-on-Trent, Staffs DE14 2ST. Tel: 0283 65435 or *Lake Electronics*, 7 Middleton Close, Nuthall, Nottingham NG16 1BX. Tel: 0602 382509.

NOTE: While 90% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail. Please check price and availability in the latest issue before ordering. We can only supply boards listed in the latest issue. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Spectrum I/O FEB '87	557	£5.35
EE Buccaneer Metal Detector JULY '87	570	£4.10
Monomix	571	£4.75
Noise Gate SEPT '87	577	£4.41
Electronic Analogue/Digital Multimeter	579	£6.40
Transtest OCT '87	580	£3.32
BBC Sideways RAM/ROM NOV '87	585	£4.10
Twinkling Star DEC '87	588	£3.00
Capacitance Meter JAN '88	590	£4.10
Transistor Curve Tracer	592	£3.00
Game Timer FEB '88	583	£3.55
Semiconductor Tester MAR '88	594	£3.19
SOS Alert	595	£3.00
Stereo Noise Gate APR '88	597	£6.65
Pipe & Cable Locator	598	£3.00
Inductive Proximity Detector	574	£3.00
Multi-Chan Remote Light Dim MAY '88		
Transmitter	599	£3.00
Receiver	600	£3.07
Door Sentinel	605	£3.00
Function Generator - Main Board	606	£5.91
Function Generator - Power Supply	607	£4.19
Multi-Chan Remote Light Dim JUNE '88		
Relay/Decoder	601	£4.86
Dimmer Board	602	£3.07
Power Supply	603	£3.00
Mother Board	604	£7.76
Headlight Reminder	611	£3.00
Video Wiper JULY '88	61	£6.75
Isolink	613	£4.21
Tea Tune AUG '88	60	£3.00
Time Switch	614	£4.84
Suntan Timer	610	£3.07
Car Alarm	615	£3.12
Breaking Glass Alarm SEPT '88	61	£4.27
Amstrad PIO	618	£6.77
Eprom Eraser OCT '88	620	£4.07
Doorbell Delay NOV '88	616	£3.56
Micro Alarm	621	£3.12
Infra-Red Object Counter Trans Receiver } £9.28 as a set	622	£4.61
Display	623	£3.23
	624	£3.05
Seashell Sea Synthesiser	625	£4.84
Reaction Timer Main Board DEC '88	626	£3.46
Display Board	627	£3.00
Downbeat Metronome	629	£4.84
EPROM Programmer (On Spec) DEC '88	630	£8.29
Phasor	631	£5.64
Monkey/Hunter Game JAN '89	634	£3.36
Continuity Tester FEB '89	619	£2.67
4-Channel Light Dimmer	635	£7.67
Mini PSU	636	£3.23

Sound-to-Light Interface MAR '89	637	£6.24
Midi Pedal	639	£7.00
Midi Merge	640	£3.00
Audio Lead Tester	641	£5.77
Light Sentinel APR '89		
Main Control Board	632	£9.20
Remote Interface (4 boards)	633	£4.59
Electron User Port	638	£6.64
4-Channel Auto-Fader Interface	642	£6.00
Pet Scarer MAY '89	644	£3.00
Electron A/D Interface	645	£4.84
Spectrum EPROM Programmer JUNE '89	628	£7.87
Bat Detector	647	£4.95
Programmable Pocket Timer JULY '89	648	£3.82
Electronic Spirit Level AUG '89	649	£3.85
Distance Recorder	651	£5.23
Treasure Hunter	652	£3.73
Xenon Beacon SEPT '89	650	£4.13
Probe Pocket Treasure Finder	653	£4.12
Power Supplies { - Fixed Voltage	654	£4.08
{ - Variable Voltage	655	£4.48
Music on Hold OCT '89	646	£3.85
Power Supplies - 25V 700mA	656	£4.35
- 30V 1A	657	£4.55
EE Seismograph - Control	658	£4.08
- Detector	659	£4.22
Lego/Lego & Spectrum	660	£6.49
Wash Pro NOV '89	643	£3.83
Biofeedback Monitor - Front End	661	£4.52
- Processor	662	£4.56
Power Supplies - 1.5V-25V 2A	663	£4.78
Lego/Lego & Spectrum Interface	664	£5.60
EEG Electrode Impedance Meter DEC '89	665	£3.98
Biofeedback Signal Generator JAN '90	666	£4.08
Four-Channel Light Chaser	667	£6.70
Quick Cap Tester FEB '90	668	£3.92
Weather Station		
Anemometer - Freq/Volt Board	670	£3.94
- Optional Display	669	£3.73
Wind Direction	673/674	£4.22
System Power Supply	675	£3.59
Prophet In-Car Ioniser	676	£3.18
EE Weather Station MAR '90		
Display Driver	671	£4.47
Display & Sensor Boards	672 & 678	£4.22
Fermostat Mk2	677	£4.28
Superhet Broadcast Receiver-Tuner/Amp	679/680	£4.22
Stereo Noise Generator APR '90	681	£4.24
Digital Experimenter's Unit		
Pulse Generator	682	£4.46
Power Supply	683	£3.66
Enlarger Timer	684	£4.28
EE Weather Station		
Rainfall/Sunlight Display	685	£4.27
Rainfall Sen(687)/Sunlight Sen(686)	686/687	£4.16
Amstrad Speech Synthesiser MAY '90	689	£4.68
Quizmaster	690	£4.74
80 Metre Direct Conversion Radio JUNE '90	691	£4.95
Mains Appliance Remote Control		
Infra-Red Transmitter	692/693	£4.75
Mains Appliance Remote Control JULY '90		
Encoder Board A	694	£6.61
Encoder board B	695	£4.78
The Tester	696	£4.15

Please note it is important to give project title as well as order code.

EE PRINTED CIRCUIT BOARD SERVICE

Please send me the following p.c.b.s.

Order Code	Project	Quantity	Price
.....
.....

I enclose cheque/PO for £.....

Name.....

Address.....

Please allow 28 days for delivery (see note above)

BLOCK CAPITALS PLEASE

SURVEILLANCE PROFESSIONAL QUALITY KITS

A range of high quality kits as supplied to leading UK security companies, all in-house designed and produced, not to be confused with cheap imports. All kits come fully documented with concise assembly and setting-up details, fibreglass PCB and all components. All transmitters are fully tuneable and can be monitored on a normal VHF radio or tuned higher for greater security. Build up service available if required.

MTX. Micro-miniature audio transmitter. 17mm x 17mm. 9V operation. 1000m range	£12.95
VT500. Hi-power audio transmitter. 250mW output. 20mm x 40mm 9-12V operation. 2-3000m range	£15.95
VOX75. Voice activated transmitter. Variable sensitivity. 30mm x 40mm. 9V operation. 1000m range	£18.95
CTX900. Sub-carrier scrambled audio transmitter. Cannot be monitored without decoder fitted to radio. 30mm x 40mm. 9V operation. 1000m range	£21.95
DSX900. Sub-carrier decoder unit for monitoring CTX900. Connects to radio earphone socket. Provides output for headphones. 35mm x 50mm. 9-12V operation	£21.95
HVX400. Mains powered audio transmitter. Connects directly to 240V AC supply. 30mm x 35mm. 500m range	£18.95
XT89. Crystal controlled audio transmitter. High performance. 100mW output. Supplied with xtal for 108MHz. Others available to 116MHz. 85mm x 28mm. 9V operation. 2-3000m range	£36.95
TKX900. Tracker Bleeper transmitter. Transmits continuous stream of audio pulses. Variable tone and rate. Powerful 200mW output. 63mm x 25mm. 9V operation. 2-3000m range	£21.95
ATR2. Micro size telephone recording interface. Connects between telephone line (anywhere) and cassette recorder. Tape switches automatically with use of phone. All conversations recorded. Powered from line 10mm x 35mm	£12.95
TLX700. Micro miniature telephone transmitter. Connects to line (anywhere) switches on and off with phone use. All conversations transmitted. 20mm x 20mm. Powered from line 1000m range	£12.95
XML900. RF bug detector. Variable sensitivity. Triggers LED and bleeper when in presence of RF field. Detects MTX 15-20 feet. 55mm x 55mm. 9V operation	£26.95
XL7000. Professional bug detector locator. Variable sensitivity. Twin mode ten segment LED readout of signal strength with variable rate bleeper. Second mode AUDIO CONFIRM distinguishes between localised bug transmission and normal legitimate signal such as pagers, cellular etc. 70mm x 100mm. 9V operation	£54.95

UK customers please send cheques, PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft or Eurocheque and add £5.00 per order for shipment. Credit card orders accepted on 0827 714476. Trade enquiries welcome.

Send 28p stamp for New 1990 Full Catalogue



The Workshops, 95 Main Rd
Baxterley, Nr. Atherstone
Warks CV9 2LE



OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX · 031 667 2611

A COMPREHENSIVE RANGE WITH SERVICE SECOND TO NONE



OUR MUCH EXPANDED, BETTER ILLUSTRATED CATALOGUE WILL COST £1.50 - TO INCLUDE VOUCHERS TO USE AGAINST FUTURE PURCHASES. TO RECEIVE A COPY AS SOON AS THEY ARE READY, PLEASE SEND YOUR REMITTANCE WITH THE VOUCHER BELOW.

Please send me a copy of the 1990/91 OMNI catalogue as soon as it is ready. Payment of £1.50 enclosed.

NAME:

ADDRESS:

TELEPHONE:



Open: Monday-Friday 9.00-6.00
Saturday 9.00-5.00



electronize Car Electronics

MICRO-PRESSURE CAR ALARM

This new type of alarm is triggered by a unique pressure sensing system. As any vehicle door is opened, air is drawn out, causing a minute drop in air pressure. A sensor detects this sudden pressure change and sets off the alarm.

A sophisticated arrangement of electronic filters and timers provide features to match ultra-sonic systems but at a fraction of the cost.

- ▲ 1 Micro-Pressure Intruder detection.
- ▲ 2 Operates on all doors and tailgate.
- ▲ 3 No door switches needed.
- ▲ 4 Automatically armed 1 minute after leaving vehicle.
- ▲ 5 10 second entry delay with audible warning.
- ▲ 6 Sounds horn intermittently for 1 minute.
- ▲ 7 Easy fitting - only 3 wires to connect - no holes to drill.
- ▲ 8 Compact design can be hidden below dashboard.
- ▲ 9 All solid state Power MOSFET output - no relays.

MICRO-PRESSURE ALARM KIT	£12.95
ASSEMBLED READY TO FIT	£18.95

VOLT DROP CAR ALARM

Our latest alarm using the popular voltage drop method of triggering. Based on the timers of the micro-pressure alarm it offers features 4 to 9 above but relies on the existing door switch operation for triggering.

VOLT DROP ALARM KIT	£11.75
ASSEMBLED READY TO FIT	£17.75

TOTAL ENERGY DISCHARGE IGNITION

Our long established Extended CDI system retains the contacts to allow easy fitting whilst the electronics removes the adverse effects. The unique spark generating system still out performs the latest all electronic systems.

TOTAL ENERGY DISCHARGE IGNITION	£18.95
ASSEMBLED READY TO FIT	£24.90

All Electronize kits include clear, easy to follow Instructions, quality components and everything needed, right down to solder and heatsink compound.

Order direct (Please quote Ref. C08 and add or send for more details from:- £1 post and packing per item.)

ELECTRONIZE DESIGN tel. 021 308 5877
2 Hillside Road, Four Oaks, Sutton Coldfield, B74 4DQ

AGE

A & G ELECTRONICS LTD.

ELECTRONIC COMPONENTS MAIL ORDER COMPANY.

1990 COMPONENTS

Lowest prices for quality components.

CATALOGUE IS


AVAILABLE NOW.



This offer is for a limited period.



Dont miss out !!!

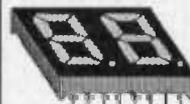

Order a catalogue now and we send you a
0.5" ORANGE DUAL LED DISPLAY
Value £ 2.00 absolutely free !!!

Simply complete and return the order form below and we will send your free gift.

PLEASE SEND COPIE(S) OF THE A & G ELECTRONICS CATALOGUE AT £1.00 (REFUNDABLE WITH MY FIRST ORDER) AND MY FREE GIFT(S) TO:

NAME

ADDRESS

I HAVE ENCLOSED £

A & G ELECTRONICS LTD.
Free Post, 100 Park Avenue
London E 6 2BR. (No Stamp Required)
TEL : 081-552 2386 Fax : 081 - 519 3419.

EVERYDAY ELECTRONICS

CLASSIFIED

Reach effectively and economically today's enthusiasts anxious to know of your products and services through our semi-display and classified pages. The prepaid rate for semi-display spaces is £8.00 (plus VAT) per single column centimetre (minimum 2.5 cm). The prepaid rate for classified advertisements is 30 pence (plus VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Electronics. VAT must be added. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 881749.

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY
 1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps A.C. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection.
 Fully variable. Operates from 240V AC. Compact Unit. size 9 x 5 1/2 x 3 in.



£42 inc. VAT + Post £2

RADIO COMPONENT SPECIALISTS
 337 WHITEHORSE ROAD, CROYDON SURREY, U.K. Tel: 081-684 1665
 Visa, Access, Barclaycard

List, Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

SERVICE MANUALS
 Available for most Video Recorders, Colour & Mono Televisions, Cameras, Test Equipment, Amateur Radio, Vintage Valve Wireless, Any Audio, Music Systems, Computers, Kitchen Appliances, etc.
 Equipment from the 1930's to the present and beyond.
 Over 100,000 models stocked, originals & photostats.
 FREE Catalogue Repair & Data Guides with all orders.

MAURITRON TECHNICAL SERVICES (EE)
 8 Cherry Tree Road, Chinnor, Oxfordshire OX9 4QY.
 Tel: (0844) 51694. Fax: (0844) 52554

N. R. BARDWELL LTD

200 - Signal diodes 1N4148.....	£1.00
100 - Rectifier diodes 1N4001.....	£1.00
100 - Zener diodes 6V8 400mW.....	£1.00
30 - Assorted DIL sockets up to 40 pin.....	£1.00
30 - Assorted Sockets/Cons. DIL, Edge, I.D.C., Header etc.....	£1.00
30 - Transistors BC478.....	£1.00
20 - Miniature SP/CO Slide switches.....	£1.00
20 - Magnetic ear pips + lead and Plug.....	£1.00
75 - Electrolytics 4 7uF 63V.....	£1.00
1 - 10watt stereo amplifier-4 controls + data.....	£2.95

Prices include VAT, postage 50p. All items new. Many other lines in stock. Shop open Mon/Sat 9.30-5.30. Lists S.A.E.
 288 ABBEYDALE ROAD, SHEFFIELD S7 1FL
 Tel: (0742) 552886. Fax: (0742) 500689

IF AN ADVERT IS IN PRINT, IS IT PROPER?

Most advertisements are perfectly proper. A few are not.

The Advertising Standards Authority not only monitors over 850 advertisements every month, it ensures compliance with the rules in the strict Code of Advertising Practice.

So when you question an advertiser, they have to answer to us.

To find out more about the role of the ASA, please write to the address below.

Advertising Standards Authority, Department X, Brook House, Torrington Place, London WC1E 7HN.



This space is donated in the interests of high standards in advertising.

M and ELECTRONIC SERVICES

H52-2961	Alt Flashing Signal.....	£2.99
H52-2963	Electrifying Apparatus.....	£8.45
H52-2967	IC Radio.....	£9.45
H52-2968	Fog Horn.....	£5.95
H52-2971	Moving Light Tube.....	£28.95
H52-2976	Apple Radio.....	£8.45
H52-2982	Metal Detector.....	£5.95
H52-2988	Antenna Amp.....	£4.95
H52-2989	Speed Control.....	£18.95
H52-2994	Diode Receiver.....	£10.99
H52-2998	Lie Detector.....	£5.95
H52-3002	Electronic Dice.....	£10.95
H52-3005	Antenna Amp 30-850MHz.....	£9.45
H52-3006	VHF Receiver.....	£19.95
H52-3021	MW Testing Transmitter.....	£4.99
H52-3022	Electronic Barking Dog.....	£19.45
H52-3033	Microwave Leak Detector.....	£6.95
H52-3112	Traffic Lights.....	£5.75
H52-3214	Test Oscillator.....	£6.75
H52-3236	Robot Voice.....	£9.49

SEND S.A.E. 9x6(24p) for catalogue. P&P per kit 60p
12B HIGH ST. MILDENHALL, SUFFOLK IP28 7EQ
 Tel: 0638 713329

ELECTRONIC COMPONENTS
 EVERYTHING FOR YOUR NEXT PROJECT

THE BIGGEST DISPLAY IN THE SOUTH IS AT

FRASER ELECTRONICS
 42 ELM GROVE ★ SOUTHSEA ★ HANTS
 Telephone 0705-815584

TECHNICAL INFO SERVICES (EE)
 76 Church St., Larkhall, Lanarkshire ML9 1HE
 Phone 0636 884545 Mon-Fri, 9-5
 any other time 0636 883334. FOR FAST QUOTES

WORLD'S LARGEST COLLECTION SERVICE MANUALS - Most unobtainable elsewhere. Prices range from only £4.50 - large size a any quotation, no obligation to buy.

WORLD'S SOLE Suppliers of TV & Video Repair manuals, etc from TV TECHNICAL, also such publishers as Henemann, Newras, TV Technic, Thom etc. Every published service sheet in stock, supplied full size, not bits & pieces. CIV's or any combination £3.50 plus Lsae, any other single item £2.50 plus Lsae. Complete Circuit Sets for most Videoorders only £7.95 (no serv shs made)

LSAE for QUOTATIONS plus GIANT CATALOGUE NEWSLETTERS BARGAINS - FREE S'sht as available.

Comprehensive TV Repair Manual £9.50. Complete Radio Service and Repair Course £9.50. Complete Repair & Service Manuals - Mono TV £12.50. CIV £17.00. Video £19.50. Complete Repair Data with circuit - Mono TV £9.50. CIV £12.50. Video £10.50

£2.00 plus LSAE BRINGS THE ONLY COMPREHENSIVE SERVICE SHEETS & MANUALS, CATALOGUES plus FREE CHASSIS GUIDE and £4.00 OF VOUCHERS

LOW COST COMPUTERS

12MHz AT 40meg HDD mono.....	£900 #
12MHz AT 20meg HDD mono.....	£825 #
6MHz AT 20meg HDD mono old style.....	£650 #
MONO MONITORS (bought with above).....	£45 #
XT MOTHERBOARD inc 640K RAM.....	£55 #
MONO CARD.....	£30 #
EGA CARD.....	£75 #
MODEM WS4000.....	£65 #

(All stock ex-demo (#) or new (#)). Private sale hence no VAT applicable
 BCS c/o 49 Kings Road, Brentwood, Essex
 Tel: 0277 230664 (days)

B.C.E. ELECTRONICS

Unit 3, Chasewood Park Business Centre, Hednesford Road, Heath Hayes, Cannock, Staffs WS12 5HL

Electronic Components, Service aids, Test gear and much more for the electronics enthusiast.
 Send 20p stamp for lists.
 Mon, Tues, Wed, Fri, Sat
 10.00-6.00
 Closed Thursday
 (0543) 77572

Kits

LOW COST kits for beginners. Ten different. £10.50 (+70p. p&p) or SAE for details. SIR-KIT ELECTRONICS, 70 Oxford Road, Clacton CO15 3TE.

Miscellaneous

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B.M.A. Circuits, 38 Poyning Drive, Sussex BN3 8GR, or phone Brighton 720203.
 FREE 4-U 50 new astd components! plus RC Wallchart. Return add plus £1 coin p&p to KIA 8 Cunliff Road, Ilkley LS29. 80W Mosfet poweramps £8.99 inc.

Manufacturers Original Spares

Available for many makes of TV, VIDEO & AUDIO EQUIPMENT. Also SINCLAIR, COMMODORE & AMSTRAD Computers. So whether it's a Custom Chip, a Remote Control Handset or maybe just a Manual you require... GIVE US A TRY!!!

We also stock a range of Electrical/Telephone Accessories, Aerials, Tools, Batteries, Soldering Equipment and MUCH MORE WHY NOT SEND FOR OUR CATALOGUE!!! Including our list of S. Offers and Components. Clearance Bargains. Simply send 2x20p stamps (UK) for your copy NOW. MAIL ORDER ONLY
 Tel: 0452 26883 MARAPET (EEH)
 1 Hornbeam Mews, Gloucester GL2 0UE

JUST RELEASED
THE IDEAL TEST OSCILLATOR!

Compact audio oscillator tunes right across audio band from 5Hz to 20kHz in a single range, making response tests quick and direct. Can also be voltage controlled.

Powerful 50-ohm drive with 0 to 2 volts output, sine or triangle wave, 40dB attenuator for low level setting.

Second 50 ohm BNC output produces 5 volt square wave or pulse for scope triggering or logic driving.

PP9 battery (not supplied) gives complete freedom from mains, earthing and hum problems, and total safety.

Robustly built. Ideal for test departments, experimenters, and education. Case size 60 x 90 x 150mm.

9 x 4 SAE brings details, or send just £64.95 + £3 p&p and 15% VAT = £78.14 total, quoting model P38.

Output cable: add £3.50. PP9 battery add £2.95 inc VAT.

COLEBOURNE ELECTRONICS,
 Dept EE, 20 Folley Lane, St Albans, Herts AL3 5JT.
 Tel: 0727 44785

CUSTOM ENGRAVING
 NAMEPLATES, CONTROL PANELS AND BADGES IN METAL OR PLASTIC SPECIALISTS IN TEXT AND GRAPHIC ENGRAVING

The Sign Studio
 182 FREISTON ROAD, BOSTON, Lincs PE21 0JR
 TEL: 0205 368276 FAX: 0205 358030

NEW VHF MICROTRANSMITTER KIT
 Tuneable 80-115 MHz, 500 metre range, sensitive electret microphone, high quality PCB, SPECIAL OFFER complete kit ONLY £5, assembled and ready to use £8.95 post free. Access/Visa orders telephone 021 411 1821 (24hrs)

Cheques/P.O.s payable to:
QUANTEK ELECTRONICS LTD
 (Dept. EE), 45a Station Road Northfield, Birmingham B31 3TE

PLEASE MENTION
EVERYDAY ELECTRONICS
 WHEN REPLYING TO
 ADVERTISEMENTS

SHERWOOD ELECTRONIC COMPONENTS 45 Rutland Street, Mansfield, Notts NG18 4AP

SPECIAL PACKS — All at £1.00 each

SP1 12x5mm Red LEDs	SP32 4xCmos 4077
SP2 12x5mm Green LEDs	SP33 4xCmos 4081
SP3 12x5mm Yellow LEDs	SP34 2xCmos 4510
SP4 10x5mm Amber LEDs	SP35 2xCmos 4511
SP5 36x5mm 1 part LED clips	SP36 20x10µF/25V Rad.Elect.Caps.
SP6 12x3mm Red LEDs	SP37 15x100µF/35V Rad.Elect.Caps.
SP7 12x3mm Green LEDs	SP38 20x47µF/25V Rad.Elect.Caps.
SP8 10x3mm Yellow LEDs	SP39 12x470µF/16V Rad.Elect.Caps.
SP9 40x3mm 1 part LED clips	SP40 15xBC237 Transistors
SP10 50x1N4148 signal diodes	SP41 25xmixed Transistors
SP11 25x1N4001 rectifier diodes	SP43 2xLM1458
SP12 25x1N4002 rectifier diodes	SP44 12x5mm Leds-4 each, Red, Green Yellow
SP13 25xRad.Elec. Caps. (1-1000µF)	SP45 25x1N4000 series rect. diodes
SP18 15xBC182 Transistors	SP46 15x400mW zeners — assorted/values
SP19 15xBC183 Transistors	SP47 5xminiature push button switches
SP20 15xBC184 Transistors	SP101 15 metres of 22SWG 60-40 solder
SP21 15xBC212 Transistors	SP102 15x8 pin DIL sockets
SP22 15xBC214 Transistors	SP103 12x14 pin DIL sockets
SP23 15xBC549 Transistors	SP104 12x16 pin DIL sockets
SP24 5xCmos 4001	SP105 5x74LS00 I.C.s
SP25 5x555 Timer	SP106 5x74LS02 I.C.s
SP26 5x741 Op-Amp	SP107 20xmixed presets — Hor. + Vertical
SP27 5xCmos 4002	SP108 15xBC382 Transistors
SP28 5xCmos 4011	SP109 15xBC557 Transistors
SP29 3xCmos 4013	SP110 4x74LS13 I.C.s
SP30 5xCmos 4025	
SP31 4xCmos 4071	

1 pack of your choice FREE when you buy any 10 of the above £1.00 packs.

ADDITIONAL PACKS

SP50 25x5mm Red LEDs	£2.00
SP51 25x5mm Green LEDs	£2.00
SP52 50xRad. Elec. Caps.	£1.95
SP53 30xDIL sockets 8, 14, 16	£2.00
SP54 1xTIL38+1xTIL100	£1.80
SP57 100x1N4148 diodes	£1.75
SP65 60x3mm+5mm Leds	£4.80

RESISTOR PACKS

0.25W Carbon Film resistors 10R-10M	
5 each value — total 365	£2.75
10 each value — total 730	£4.50
1000 popular values	£6.00
Individual resistors	2p ea.
10+ one value	1p ea.
100 one value	75p

CMOS

4000	25p	4070	27p
4001	25p	4071	27p
4002	25p	4072	27p
4011	25p	4073	27p
4012	27p	4075	27p
4013	38p	4077	32p
4017	55p	4081	27p
4023	30p	4093	27p
4025	25p	4510	65p
4027	50p	4511	65p
4040	70p	4514	£1.25
4047	65p	4515	£1.30
4049	40p	4516	65p
4066	40p	4528	70p

I.C.s

555	22p	78L05	25p
556	75p	78L12	25p
741	22p	78L15	26p
747	70p	79L05	30p
CA3140E	45p	79L12	30p
CA3240E	£1.25	79L15	30p
LM339	55p	1A	
LM380-14	£1.25	7805	35p
LM723	60p	7812	35p
LM1458	55p	7815	36p
TL071	60p	7905	36p
TL072	80p	7912	38p
TL081	40p	7912	38p
TL082	55p	7915	38p

V. REGS.

100mA	
78L05	25p
78L12	25p
78L15	26p
79L05	30p
79L12	30p
79L15	30p
1A	
7805	35p
7812	35p
7815	36p
7905	36p
7912	38p
7915	38p

Cheques or P.O. to:

SHERWOOD ELECTRONIC COMPONENTS
Please add £1 P&P to orders under £20.00

This only a small sample of components stocked, send 75p for new 1990 catalogue, contains vouchers redeemable against orders over £5.00. NO VAT

MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 9 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	TV, Video & Hi-Fi Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Refrigeration & Air Conditioning	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
CCSE / CCE / SCE over 40 examination subjects to choose from			

Name

Address

ICS

International Correspondence Schools Dept. ECS 70
Telephone 081-843 9568 or 041-221 2926 (24 hours) 312/314 High Street, Sutton, Surrey SM1 1PR

CAMBRIDGE COMPUTER SCIENCE LIMITED

★10MByte Winchester, used, 3 months Wty	£42.00 each
★5.25" Disk Drives, 80 TL, DSDD	£34.00 each
★5.25" drive cases, room for drive, PSU & fan	£10.00 each
★5.25" Disk Drives, 80 TL, DSDD Used, No Wty	£15.00 each
(The £15.00 drives are sold on a strictly "as is" basis)	
★25" Disks, DSDD, 48tpi boxes of 10	£3.00 box
★50W PSU 5V 6A, 12V 2.5A, -5V 0.5A, -12V 0.5A	£16.00 each
★40W PSU 5V 3.75A, 12V 1.5A, -12V 0.4A, cased with on/off switch	£10.00 each
★Dual Data lead (BBC Micro to 2 Disk Drives)	£4.00 each
★Power lead (BBC Micro to Disk Drive)	£2.00 each
★Dual power lead (BBC Micro to 2 Disk Drives)	£4.00 each
★68000 CPUs (The first orders get 10MHz chips)	£3.50 each
★Z80A CPU, CTC, PIO £1.20 each; DMA £2.00	£4.50 all 4
★74LS TTL, pick and mix, buy 10 or more for	£0.12 each
Types available: '00' '02' '04' '08' '11' '12' '13' '15' '20' '21' '26' '27' '30' '32' '33' '38' '42' '74' '83' '96' '107' '109' '122' '132' '136' '139' '145' '151' '153' '157' '158' '163' '164' '165' '191' '193' '298' '353' '365' '670	
★Z80 EPROMS (Ex-equipment)	£1.00 each
★27128 EPROMS	£2.50 each
★EPROMS 27C256-25	£3.50 each
★256K Byte DRAM Modules, removed from equipment	£6.00 each
★6116 2K Byte SRAM	£1.10 each
★6264 8K Byte SRAM	£1.80 each
★65256 32K Byte rams	£7.00 each
★8K Byte NV ram chips	£3.00 each
★Keyboard, 100 keys on board LCD & micro if	£8.00 each
★Toroidal mains transformer, 12V 4A & 0.4A, 12-0-12 1A & 2A, 9-0-9 2A	£4.00/1, £6.00/2, £8.00/3

Prices include postage. Add 50p (plus VAT) to orders below £5.00.
All items new unless stated. Add 15% VAT to all prices. (Please note mail order only)
Send an SAE for our latest list or for more info.
Dept EE, 374 Milton Road, Cambridge CB4 1SU
Tel: 0223 424602 or 0831 430496

Page Make-up for £185 plus VAT

IF YOU are looking for a superb, page make-up system complete with over 200 typefaces, that really works and won't cost you an arm and a leg, Typefit is the system for you. Why? Because for only £185 you get:

- Access to over £60k hard/software, and over 200 genuine Monotype and ITC fonts from 1 - 1000 pt.
- Disc processing through our typesetting bureau from £2.50 for an A4 page.
- Page make-up, on screen.
- Clear, accurate WYSIWYG.
- A system that's easy to learn and simple to use.
- Full on-screen help, and telephone back-up.
- Software that runs on IBM PCs and compatibles.

Send us your discs or modem your files and your typesetting will be returned the same day.

DON'T BELIEVE IT'S THAT GOOD? THERE'S A FULL MONEY BACK GUARANTEE IF NOT SATISFIED

Interested? Please 'phone Terry or Paul for further information or a demonstration disc. Please state disc size and density.

Typefit

THE TYPESETTING BUREAU LTD

6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 882299.
Fax: 841692. Modem: 882270. DX: 45314 Wimborne. Datalink: TYPBUR

EVERYDAY ELECTRONICS SUBSCRIPTION ORDER FORM

Annual subscription rates (1990): UK £16. Overseas £19.50 (surface mail) £37 (air mail)
To: Everyday Electronics, Subs. Dept., 6 Church Street, Wimborne, Dorset BH21 1JH.

Name

Address

I enclose payment of £..... (cheque/PO in £ sterling only payable to Everyday Electronics) Access or Barclaycard/Visa No.  

Signature..... Card Ex. Date.....

Please supply name and address of card-holder if different from the subscription address shown above.

Subscriptions can only start with the next available issue. For back numbers see the Editorial page.

TRANSFORMERS EX STOCK

MAINS ISOLATORS

Pri 120V x 2 or 220/240V or 415/440V. Sec 440 or 240V or 110V Centre Tapped

20 VA	£8.33	2.51
60	13.60	2.70
100	15.87	P 2.92
200	22.49	& 3.52
250	29.20	P 3.62
500	41.91	4.24
1000	76.01	5.33
1500	98.04	6.54
2000	117.96	7.64
3000	165.41	O/A
6000 VA	353.43	O/A

24/12V or 12-0-12V

2x12V Secs

24V	12V	£	P&P
0.15	0.3	3.44	1.87
0.25	0.5	3.64	1.90
0.5	1	4.36	1.98
1	2	6.08	2.09
2	A 4	7.01	2.20
3	M 6	12.08	2.36
4	P 8	12.87	2.42
6	S 12	15.62	2.64
8	16	18.59	3.08
10	20	25.02	3.52
15	30	31.10	3.63
20	40	44.40	4.12
30	60	63.75	4.89
41	83	73.41	6.32

AUTOS

105, 115, 200, 220, 230, 240V for step-up or down

80 VA	£	P&P
150	10.03	2.09
250	12.25	2.31
500	19.05	P 3.08
1000	34.93	& 3.68
1500	40.40	P 4.18
2000	60.41	5.11
3000	102.72	6.32
4000	133.35	O/A
5000	155.28	O/A
7500	239.70	O/A
10KVA	283.23	O/A

30/15V or 15-0-15V

2x15V Tapped Secs. Volts available: 3, 4, 5, 6, 8, 9, 10, 15, 18, 20, 27, 30V or 15-0-15V

30V	15V	£	P&P
0.5	1	4.55	1.81
1	2	6.19	1.98
2	A 4	10.01	2.20
3	M 6	11.60	2.42
4	P 8	13.84	2.53
5	S 10	17.72	2.74
6	12	19.41	2.92
8	16	25.94	3.02
10	20	29.94	3.24
12	24	33.42	3.35
15	30	37.43	4.01
20	40	51.10	6.54

50/25V or 25-0-25V

2x25V Tapped Secs to give 7, 8, 10, 13, 17, 20, 25, 33, 40, 50V or 20-0-20V or 25-0-25V

50V	25V	£	P&P
0.5	1	5.91	2.09
1	2	7.19	2.21
2	A 4	12.81	2.75
3	M 6	14.82	2.92
4	P 8	20.30	3.24
6	S 12	25.81	3.41
8	16	36.52	4.12
10	20	43.34	4.41
12	24	51.87	5.22

CASED AUTOS

240V Cable Input 3-pin 115V USA Socket Outlet

20 VA	£	P&P
80	9.85	2.03
150	13.39	2.14
250	17.34	2.53
500	21.13	P 3.57
1000	34.66	& 3.90
2000	48.65	P 4.90
3000VA	86.70	6.16
	124.46	O/A

AVO's & MEGGERS

Full range available

60/30V or 30-0-30V

2x30V Tapped Secs Volts available: 16, 18, 36, 40, 60V or 24-0-24 or 30-0-30V

60V	30V	£	P&P
0.5	1	6.72	2.09
1	2	10.25	2.21
2	A 4	13.17	2.53
3	M 6	19.05	2.64
4	P 8	21.72	2.75
5	S 10	27.46	3.19
6	12	31.32	3.41
8	16	44.04	3.93
10	20	51.28	4.40
12	24	59.09	5.22

96/48V or 48-0-48V

2x0.36-48V Secs to give 60, 72, 84, 96V, or 36-0-36V or 48-0-48V.

96V	48/36V	£	P&P
0.5	1	£7.16	1.76
1	2	12.80	2.31
2	A 4	21.05	2.91
3	M 6	25.49	3.02
4	P 8	32.54	3.32
5	S 10	46.21	4.18
6	12	57.87	4.40
8	16	63.12	5.28

TOOL TRANSFORMERS

240V to 110Vct O/P 2KVA £71 + £5.33 P&P

CONSTANT VOLTAGE

TRANSFORMERS For Spike-free Stable Mains

INVERTERS

12/24V DC to 240V AC Square or Sine Wave

TRANSFORMERS WOUND TO SPEC

Batch Winding 3VA to 15KVA TOROIDALS 30VA to 4KVA

Also Valve Mains & Output Transformers

Please add 15% V.A.T. to all items after P&P Send SAE for Lists

BARRIE ELECTRONICS LTD

TELEPHONE: 081-551 8454

PO BOX 70, ILFORD ESSEX, IG5 0AP

ADVERTISERS INDEX

ADVANCED ELEC. PRODUCTS...	487
A&G ELECTRONICS.....	493
BARRIE ELECTRONICS.....	496
BK ELECTRONICS.....	Cover (iii)
BULL ELECTRICAL.....	Cover (ii)
CAMBRIDGE COMP.SCIENCE.....	495
CIRKIT DISTRIBUTION.....	442
CRICKLEWOOD ELECTRONICS.....	483
CR SUPPLY COMPANY.....	496
ELECTRONIZE DESIGN.....	493
ELV FRANCE.....	454/455
GRANDATA.....	428
GREENWELD ELECTRONICS.....	429
HART ELECTRONIC KITS.....	464
HENRY'S AUDIO ELECTRONICS.....	430
HIGHGRADE COMPONENTS.....	431
ICS.....	495
JAYTEE ELECTRONIC SERVICES.....	430
KB COMPONENTS.....	496
LONDON ELECTRONICS COLLEGE.....	496
MAGENTA ELECTRONICS.....	432/433
MAPLIN ELECTRONICS.....	Cover (iv)
MARCO TRADING.....	447
NUMBER ONE SYSTEMS.....	485
OMNI ELECTRONICS.....	493
RADIO & TV COMPONENTS.....	426
SHERWOOD ELEC. COMP.....	495
SPECIALIST SEMICONDUCTORS.....	491
SUMA DESIGNS.....	493
TK ELECTRONICS.....	434
THE TYPESETTING BUREAU.....	495

BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

2 YEAR
BTEC National Diploma (OND)
ELECTRONIC & COMMUNICATIONS ENGINEERING
(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

1 YEAR
BTEC National Certificate (ONC)
ELECTRONIC ENGINEERING
1—INFORMATION TECHNOLOGY
(Electronics, Satellite TV, Networks, Telecomms)

2—ELECTRONIC EQUIPMENT SERVICING
(Electronics, Television, Video Cassette Recorders, CCTV, Testing and Fault Diagnosis)

3—SOFTWARE ENGINEERING
(Electronics, Assembler, BASIC, Pascal, CAD/CAM)

4—COMPUTING TECHNOLOGY
(Electronics, Computing Software/Hardware, Microelectronics)

10 MONTHS
BTEC Higher National Certificate (HNC)
COMPUTING TECHNOLOGY & ROBOTICS
(Microprocessor Based Systems, Control, Robotics)

These courses include a high percentage of college based practical work to enhance future employment prospects
No additional fees for overseas students
Shortened courses of from 3 to 6 months can be arranged for applicants with previous electronics knowledge
THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT AN EQUAL OPPORTUNITIES PROGRAMME

O.N.C. and O.N.D.
Next Course Commences
Monday 17th September 1990
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept. EE), 20 PENYVERN ROAD
EARLS COURT, LONDON SW5 9SU
Tel: 071-373 8721

Carbon Film resistors 1/4W 5% E24 series 0.51R to 10MΩ	1p
100 off per value—75p, even hundreds per value totalling 1000	£6.00p
Metal Film resistors 1/4W 10R to 1MΩ 5% E12 series—2p, 1% E24 series	3p
Mixed metal/carbon film resistors 1/2W E24 series 1R0 to 10MΩ	1 1/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms	5p
Linear Carbon pre-sets 100mW and 1/4W 100R to 4M7 E6 series	7p
Miniature polyester capacitors 250V working for vertical mounting	
.015, .022, .033, .047, .068-4p, 0.1-5p, 0.12, 0.15, 0.22-6p, 0.47-8p, 0.68-8p, 1.0-12p	
Mylar (polyester) capacitors 100V working E12 series vertical mounting	
1000p to 8200p - 3p, .01 to .068 - 4p, 0.1 - 5p, 0.12, 0.15, 0.22-6p, 0.47/50V-8p	
Submin ceramic plate capacitors 100V wkg vertical mountings E12 series	
2% 1.8pf to 47pf - 3p, 2% 56 pf to 330pf - 4p, 10% 390p - 4700p	4p
Disc/plate ceramics 50V E12 series 1P0 to 1000P, E6 Series 1500P to 47000P	2p
Polystyrene capacitors 63V working E12 series long axial wires	
10pf to 820pf - 3p, 1000 pf to 10,000pf - 4p, 12,000 pf	5p
741 Op Amp - 20p, 555 Timer	22p
cmos 4001 - 20p, 4011 - 22p, 4017	40p
ALUMINIUM ELECTROLYTICS (Mfds/Volts)	
1/50, 2.2/50, 4.7/50, 10/25, 10/50	5p
22/16, 22/25, 22/50, 47/16, 47/25, 47/50	6p
100/16, 100/25 7p; 100/50 12p; 100/100	14p
220/16 8p; 220/25, 220/50 10p; 470/16, 470/25	11p
1000/25 25p; 1000/35, 2200/25 35p; 4700/25	70p
Submin. tantalum bead electrolytics (Mfds/Volts)	
0.1/35, 0.22/35, 0.47/35, 1.0/35, 3.3/16, 4.7/16	14p
2.2/35, 4.7/25, 4.7/35, 6.8/16 15p; 10/16, 22/6	20p
33/10, 47/6, 22/16 30p; 47/10 35p; 47/16 60p; 47/35	80p
VOLTAGE REGULATORS	
1A + or - 5V, 8V, 12V, 15V, 18V & 24V	55p
DIODES (piv/amps)	
75/25mA 1N4148 2p, 800/1A 1N4006 6p, 400/3A 1N5404 14p, 115/15mA OA91	6p
100/1A 1N4002 4p, 1000/1A 1N4007 7p, 60/1.5A S1M1 5p, 100/1A bridge	25p
400/1A 1N 4004 5p, 1250/1A BY127 10p, 30/1.5A OA47	8p
Zener diodes E24 series 3V3 to 33V 400 mW - 8p, 1 watt	12p
Battery snaps for PPS - 6p for PPS	12p
L.E.D.'s 3mm, & 5mm, Red, Green, Yellow - 10p, Grommets 3mm - 2p, 5mm	2p
Red flashing L.E.D.'s require 5V supply only	50p
Mains indicator neons with 220k resistor	10p
20mm fuses 100mA to 5A Q/blow 5p, A/surge 8p, Holders pc or chassis	5p
High speed pc drill 0.8, 1.0, 1.3, 1.5, 2.0m - 30p, Machines 12V dc	£7.00
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£3.50p
AA/HP7 Nicad rechargeable cells 80p each, Universal charger unit	£6.50
Glass reed switches with single pole make contacts - 8p, Magnets	12p
0.1" Stripboard 2 1/2" x 1" 9 rows 25 holes - 20p, 3 1/2" x 2 1/2" 24 rows 37 holes	60p
TRANSISTORS	
BC107/8/9-12p, BC547/8/9-8p, BC557/8/9-8p, BC182, 182L, BC183, 183L, BC184, 184L, BC212, 212L-10p, BC327, 337, 337L-12p, BC727, 737-12p, BD135/67/8/9-25p, BCY70-15p, BFY50/51/52-20p, BFY88-15p, 2N3055-50p, TIP31, 32-30p, TIP41, 42-40p, BU208A-E1.20, BF195, 197-12p	
All prices are inclusive of VAT. Postage 25p (free over £5). Lists Free.	

THE CR SUPPLY CO

127 Chesterfield Rd., Sheffield S8 0RN
Tel: 0742 557771 Return posting

WATCH THIS SPACE MONTHLY...

for just a few examples from our extensive and changing stocks of
COMPONENTS, CAPACITORS, CONNECTORS, FUSES, HARDWARE, TEST EQUIPMENT, RELAYS, SWITCHES, SEMICONDUCTORS, MINI CIRCUITS, BAND FILTERS, etc. etc. etc.

CML FX 4070 module. Industry standard	£25.00 each
Mitsubishi power module amplifier IC 25W 12V 145-170MHz M57710	£22.50 each
Crystal Filters 21.4 megohm 15KT band width	£12.00 each
3 Pole Helical Filters 405 meg	£3.50 each
Siemens Intelligent displays DL 3416 & DL 2416T	£3.00 each
Siemens Intelligent displays DL 461T	£2.00 each
Power supply by Power Products PM 5932 115V-240mA In 15V-150mA out	£8.00 each
Speakers 8" diameter 8 ohm	£2.00 each
Speakers 57mm diameter Toptone Mylar	£3.00 each
Transceiver F1st microphone fitted flexilead and 12 pin din	£2.95 each
Cooling fans 12/24V d.c. 60mm sq x 20mm deep	£6.00 each
115/240V a.c. 80mm sq x 20mm deep	£6.00 each
119mm sq x 38mm deep	£6.00 each
92mm sq x 15mm deep	£6.00 each
92mm sq x 25.4mm deep	£6.00 each
Davall relays 25/2MS/185 ohm PCB mount	50p each
Gen. instruments 1 1/2 digit display ref. MAN 6730	50p each
Murata Piezo transmit PKD 33EQ	30p each

ALL PRICES INCLUDE VAT

Add £2 postage/packing

Allow 14 days for delivery

Payment. Cash/cheque/P.O. with order

A MONTHLY comprehensive list is available showing varying and changing stocks. Send £1 and SAE for listings as required

K.B. COMPONENTS

21 Playle Chase, Gt. Totham, Maldon, Essex CM9 8UT

Tel: 0621 893204

OMP POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

OMP POWER AMPLIFIER MODULES

Supplied ready built and tested.

OMP POWER AMPLIFIER MODULES Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, integral heat sink, Glass fibre P.C.B. and Drive circuits to power compatible Vu meter. Open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. PRICE £33.99 + £3.00 P&P.

NEW SERIES II MOS-FET MODULES



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor, >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 155 x 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 175 x 100mm. PRICE £79.99 + £4.50 P&P.

NOTE:— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS. STANDARD — INPUT SENS. 500mV BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) — INPUT SENS. 775mV BAND WIDTH 50KHz. ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 LED diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE:— INSTRUMENTS, P.A., DISCO, ETC.

- ALL MCKENZIE UNITS 8 OHMS IMPEDENCE**
- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £29.30 + £2.00 P&P
 - RES. FREQ. 80Hz FREQ. RESP. TO 14KHz SENS. 99dB
 - 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID. PRICE £35.58 + £2.50 P&P
 - RES. FREQ. 70Hz FREQ. RESP. TO 6KHz SENS. 100dB
 - 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID. PRICE £48.67 + £2.50 P&P
 - RES. FREQ. 45Hz FREQ. RESP. TO 7KHz SENS. 103dB
 - 12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. PRICE £37.59 + £3.50 P&P
 - RES. FREQ. 45Hz FREQ. RESP. TO 7KHz SENS. 98dB
 - 12" 100 WATT C12100TC TWIN CONE) HIGH POWER WIDE RESPONSE, P.A., VOICE, DISCO. PRICE £38.58 + £3.50 P&P
 - RES. FREQ. 45Hz FREQ. RESP. TO 14KHz SENS. 100dB
 - 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. PRICE £65.79 + £3.50 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 7KHz SENS. 100dB
 - 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. PRICE £87.51 + £3.50 P&P
 - RES. FREQ. 45Hz FREQ. RESP. TO 5KHz SENS. 100dB
 - 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. PRICE £55.05 + £4.00 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 5KHz SENS. 98dB
 - 15" 200 WATT C15200BS VERY HIGH POWER BASS. PRICE £75.10 + £4.00 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 4KHz SENS. 99dB
 - 15" 250 WATT C15250BS VERY HIGH POWER BASS. PRICE £82.54 + £4.50 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 4KHz SENS. 99dB
 - 15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS. PRICE £96.47 + £4.50 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 4KHz SENS. 102dB
 - 18" 400 WATT C18404BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. PRICE £172.06 + £5.00 P&P
 - RES. FREQ. 27Hz FREQ. RESP. TO 3KHz SENS. 99dB

EARBENDERS:— HI-FI, STUDIO, IN-CAR, ETC.

- ALL EARBENDER UNITS 8 OHMS**
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND**
 - 8" 50 WATT EB8-50 DUAL IMPEDENCE, TAPPED 4 8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 7KHz SENS. 97dB
 - 10" 50 WATT EB10-50 DUAL IMPEDENCE, TAPPED 4 8 OHM BASS, HI-FI, IN-CAR. PRICE £12.00 + £2.50 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 5KHz SENS. 99dB
 - 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £27.76 + £3.50 P&P
 - RES. FREQ. 35Hz FREQ. RESP. TO 3KHz SENS. 96dB
 - 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO. PRICE £21.00 + £3.00 P&P
 - RES. FREQ. 28Hz FREQ. RESP. TO 3KHz SENS. 92dB
 - 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £38.75 + £3.50 P&P
 - RES. FREQ. 26Hz FREQ. RESP. TO 3KHz SENS. 93dB
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 5 1/2" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
 - RES. FREQ. 63Hz FREQ. RESP. TO 20KHz SENS. 92dB
 - 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + £1.50 P&P
 - RES. FREQ. 38Hz FREQ. RESP. TO 20KHz SENS. 94dB
 - 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
 - RES. FREQ. 40Hz FREQ. RESP. TO 18KHz SENS. 89dB
 - 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
 - RES. FREQ. 35Hz FREQ. RESP. TO 12KHz SENS. 86dB

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W FM TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.49 + £1.00 P&P


FM MICRO TRANSMITTER (BUG) 100-108MHz VARICAP TUNED COMPLETE WITH VERY SENS FET MIC. RANGE 100-300m. SIZE 56 x 46mm, SUPPLY 9V BATT. PRICE £8.82 + £1.00 P&P



3 watt FM Transmitter

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

OMP VARISPEED TURNABLE CHASSIS

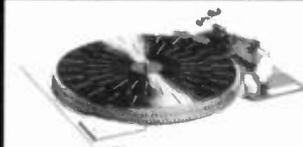

- ★ MANUAL ARM
- ★ STEEL CHASSIS
- ★ ELECTRONIC SPEED CONTROL 33 & 45
- ★ VARI PITCH CONTROL
- ★ HIGH TORQUE SERVO DRIVEN DC MOTOR
- ★ TRANSIT SCREWS
- ★ 12" DIE CAST PLATTER
- ★ NEON STROBE
- ★ CALIBRATED BAL WEIGHT
- ★ REMOVABLE HEAD SHELL
- ★ CARTRIDGE FIXINGS
- ★ CUE LEVER
- ★ POWER 220 240V 50 60Hz
- ★ 390 x 305mm
- ★ SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE

PRICE £59.99 + £3.50 P&P.

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500

PRICE £16.99 + 50p P&P

GOLDRING G850

PRICE £6.99 + 50p P&P

OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS:— MXF200 (100w + 100w)

MXF400 (200w + 200w) MXF600 (300w + 300w)

All power ratings R.M.S. into 4 ohms.

FEATURES: • Independent power supplies with two Toroidal Transformers • Twin L.E.D. Vu meters • Rotary indexed level controls • Illuminated on/off switch • XLR connectors • Standard 775mV inputs • Open and short circuit proof • Latest Mos-Fets for stress free power delivery into virtually any load • High slew rate • Very low distortion • Aluminium cases • MXF600 Fan Cooled with D.C. Loudspeaker and Thermal Protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.


- SIZES:— MXF 200 W19" x H3 1/2" (2U) x D11"
- MXF 400 W19" x H5 1/4" (3U) x D12"
- MXF 600 W19" x H5 1/4" (3U) x D13"

MXF200 £171.35

MXF400 £228.85

MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH

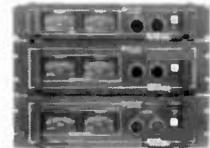

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS. FINISHED IN HARDWEARING BLACK VINYL WITH PROTECTIVE CORNERS, GRILLE AND CARRYING HANDLE. INCORPORATES 12" DRIVER PLUS HIGH FREQ HORN FOR FULL FREQ. RANGE 45Hz-20KHz BOTH MODELS 8 OHM. SIZE H18" x W15" x D12"

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.99 PER PAIR

OMP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL.— £12.00 PER PAIR

IN CAR STEREO BOOSTER AMPLIFIER




TWO SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS

- 150 WATTS (75+75) INTO 4 OHMS
- 300 WATTS (150+150) INTO 4 OHMS
- FEATURES:
- HIGH & LOW INPUT IMPEANCES
- HIGH & LOW INPUT SENSITIVITIES
- VARIABLE INPUT GAIN CONTROL
- SHORT CIRCUIT OUTPUT PROTECTION
- POWER REQUIREMENT 12V D.C.
- PRICES: 150 WATT £43.00
- 300 WATT £95.00 + £3.00 P&P EACH

PIEZO ELECTRIC TWEETERS—MOTOROLA

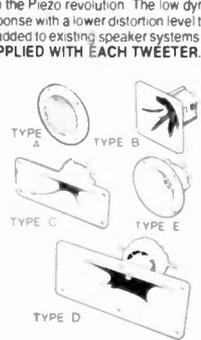Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.




- TYPE 'A' (KSN2036A)** 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-fi speakers. Price £4.90 each + 50p P&P
- TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 50p P&P
- TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £6.99 each + 50p P&P
- TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £9.99 each + 50p P&P
- TYPE 'E' (KSN1038A)** 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £5.99 each + 50p P&P
- LEVEL CONTROL** Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £3.99 + 50p P&P

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following — 3 Turntables (Mag), 3 Mics, 4 Line including CD plus Mic with talk over switch Headphone Monitor Pan Pot L & R. Master Output controls. Output 775mV Size 360x280x90mm Supply 220-240V.

Price £134.99 — £4.00 P&P

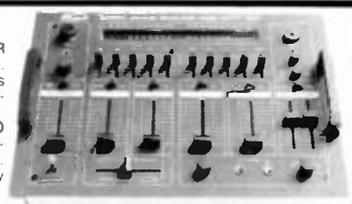

B. K. ELECTRONICS Dept EE
UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR
TEL: 0702-527572 FAX: 0702-420243



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. VISA ACCEPTED BY POST, PHONE OR FAX.





DIRECT CONVERSION SHORT WAVE RECEIVER

- ★ Receives speech (SSB, DSB, AM) and morse (CW)
- ★ Choice of amateur band, 160 – 10 metre
- ★ On-board voltage regulator and audio power amplifier

Sophisticated ready-made short wave receivers, often cost hundreds of pounds. Now, you can build a receiver of the direct conversion design that has the advantage of simplicity of construction and ease of alignment, with the minimum of test gear, for a fraction of the cost of a ready-made model. The amateur bands are: 160m, 80m, 40m, 20m, 15m & 10m. To include all these bands on one receiver would present switching & tracking difficulties, for this reason the receiver covers only one band (which needs to be decided upon before construction). The choice is up to you, but do not forget to order your tuning pack when ordering your receiver kit.


AMATEUR BAND	RECEIVER TUNING RANGE	TUNING PACK
160m		
1.810-2.000MHz	1.800-2.010MHz	1
80m		
3.500-3.800MHz	3.490-3.810MHz	1
40m		
7.000-7.100MHz	6.690-7.150MHz	2
20m		
10.100-10.150MHz	10.000-10.500MHz	2
14.000-14.350MHz	13.990-14.400MHz	3
18.068-18.168MHz	18.000-18.500MHz	3
15m		
21.000-21.450MHz	20.990-21.500MHz	3
24.890-24.990MHz	24.540-25.000MHz	4
10m		
28.000-29.700MHz	A. 27.975-28.525MHz	4
	B. 28.475-29.025MHz	4
	C. 28.975-29.525MHz	4
	D. 29.475-30.025MHz	4

A kit excluding the optional items, Box and Chassis, Pot Mounting Bracket, Front and Rear Panels and Tuning Kits is available. For full list of optional extras see Maplin Catalogue.

- LM60Q (Dir Conv Rx Kit) £64.95
- LM61R (Tuning kit 1) £3.45
- LM62S (Tuning kit 2) £3.45
- LM63T (Tuning kit 3) £3.45
- LM64U (Tuning kit 4) £3.45

ACTIVE AERIAL


An active aerial pre-amplifier having five selectable tuned RF ranges which cover a total frequency range of 150kHz to 30MHz. The unit includes a gain control operating on the MOSFET amplifier, and a low battery LED warning indicator. Connections to aerial and receiver are made using UHF series connectors, with a direct, straight through or 'by-pass' mode operative when the unit is switched off. A telescopic aerial is included for use where a proper outdoor aerial is not

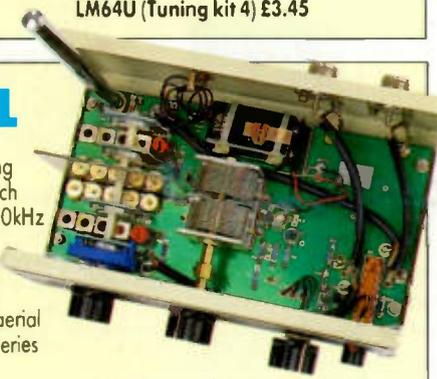

practical or possible. A printed stick-on front panel for the active aerial project is available as an optional extra.

- LM05F (Active Aerial Kit) £52.95
- Optional items:
- FA99H (Active Aerial f/panel) £3.95
- XY45Y (Case 222) £6.45

Photo shows Kit with some optional extras, see Maplin Catalogue for further details.

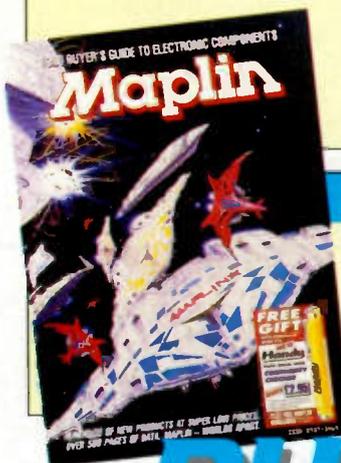


THE MAPLIN CATALOGUE

Further details and specifications on all the items shown on this page are to be found in the Maplin Catalogue. Over 580 pages of electronics ideas from Projects and Modules, Tools, Components, Books, Connectors, Batteries and Power Supplies to Test Gear, Audio, Video and Computers and much, much more. Available from branches of WHSMITH, Only £2.25, or by post £2.75 inc p&p (CA07H).

3 Royden

DXer's AUDIO PROCESSOR

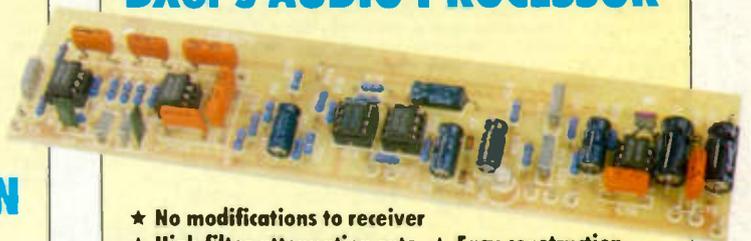

- ★ No modifications to receiver
 - ★ High filter attenuation rate
 - ★ Easy construction
- The processor features a low-pass filter giving a 36dB per octave attenuation under 150Hz and an expander which severely attenuates noise during pauses in the received speech. The unit is especially suited for SSB & FM CB reception and simply fits between the receiver's audio output and the headphones, thus no modification is necessary to the receiver. The single PCB makes construction very simple.

LM05F (DXer's Processor Kit) £11.95

Optional items: HB26D (Knob (3 off required)) 68p each
XY45Y (Case 222) £6.45 FM03D (9V PP6 Battery) £1.98

SW/MW AERIAL TUNING KIT



Given that the aerial impedance of most communications receivers is 50, unless the impedance of the aerial matches this exactly all of the RF energy will not be efficiently transferred from the aerial to the receiver. The greater the mismatch, then the weaker the signal will appear, and under adverse conditions it could vanish completely into background noise. This aerial tuning unit comprises two variable tuning capacitors and a tapped inductor in a passive 'T' configuration. This arrangement covers approximately 600kHz to 30MHz, and matches the aerial load impedance to the input impedance of the receiver. The ATU can also be used for transmitter aerial matching in the same frequency range, including the 27MHz citizen band, up to a power rating of 10Watts. A printed stick-on front panel is available as an optional extra for the aerial tuner unit.

LM06G (Aerial Tuner Kit) £36.95

Optional items: FD11M (Aerial Tuner f/panel) £3.95
XY45Y (Case 222) £6.45 FW38R (Pkt Stick-on Feet) 24p

Maplin ELECTRONICS

CREDIT CARD HOTLINE



PHONE BEFORE 5pm FOR SAME DAY DESPATCH

0702 554161

POP INTO A MAPLIN SHOP TODAY AND DISCOVER A UNIQUE NEW SHOPPING EXPERIENCE

All prices include VAT. Prices valid till 31st August 1990. All items subject to availability, all items will be on sale in our shops in Birmingham, Bristol, Leeds, Hammersmith, Edgware, Manchester, Nottingham, Newcastle-upon-Tyne, Reading, Southampton and Southend-on-Sea.

Orders by post to: P.O. Box 3, Rayleigh, Essex SS6 8LR.

AIR

75p carriage must be added to all orders (except if ordering catalogue only). In addition, if your order is below £9.25 add 75p, if between £9.25 and £10, make up to £10 (small order handling charge).

RULE THE WAVES

Maplin for the Art of Communication.